



ELECTRONICS
TODAY INTERNATIONAL

RS232 INTERFACE


**DIGITAL
CIRCUIT TESTER**

Out and About..?



THE 'GREEN' CAR
How environmentally friendly is your car?

Then build this 12→240V Mains Inverter

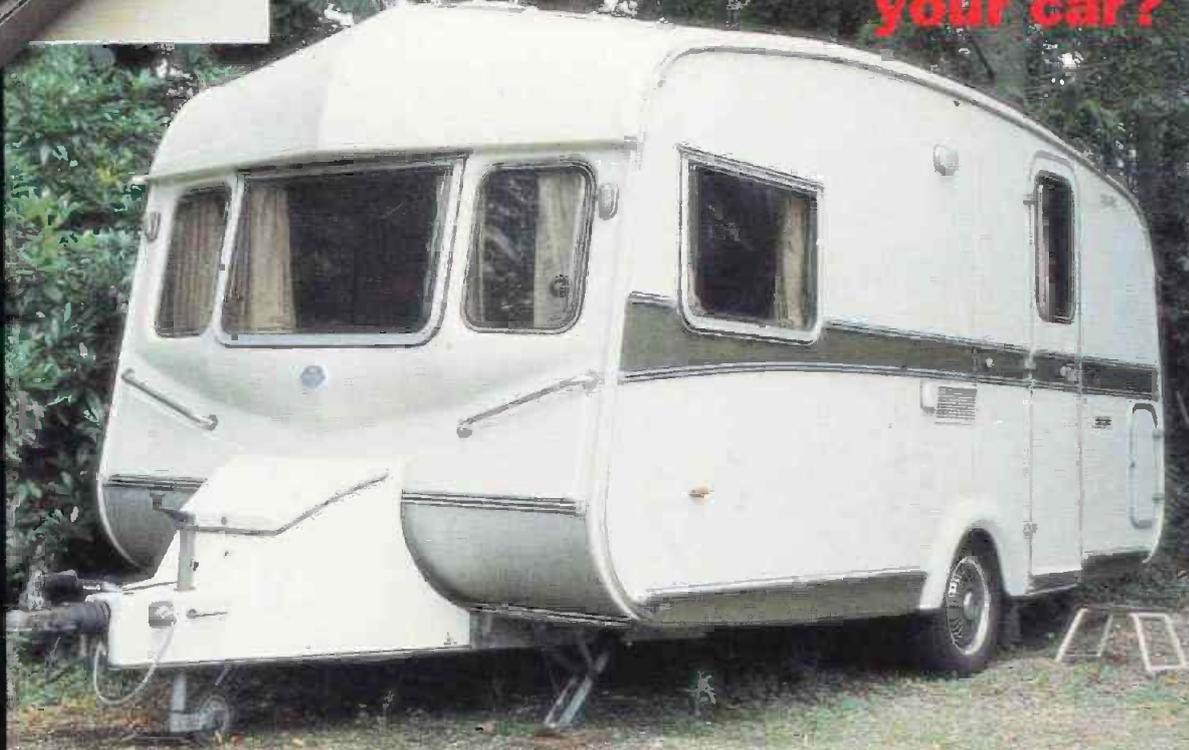

using our cover PCB

HYBRID LINE AMP

Please tell your retailer if the PCB is missing



12

9 770142 722023

Argus SPECIALIST PUBLICATION **BEST VALUE**

**OVP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK**

**THOUSANDS PURCHASED
BY PROFESSIONAL USERS**



**THE RENOWNED MXF SERIES OF POWER AMPLIFIERS
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)**

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin LED Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

- SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
- MXF400 W19" x H5 1/4" (3U) x D12"
- MXF600 W19" x H5 1/4" (3U) x D13"
- MXF900 W19" x H5 1/4" (3U) x D14 3/4"

**PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH**



OVP VARISPEED TURNTABLE CHASSIS



★ Manual arm ★ Steel chassis ★ Electronic speed control 33 & 45 R.P.M. ★ Vari pitch control ★ High torque servo driven DC motor ★ Transit screws ★ 12" die cast platter ★ Neon strobe ★ Calibrated balance weight ★ Removable head shell ★ 1/2" cartridge fixings ★ Cue lever ★ 220/240V 50/60Hz ★ 390x305mm ★ Supplied with mounting cut-out template.

PRICE £61.30 + £3.70 P&P

OPTIONAL MAGNETIC CARTRIDGES

**STANTON AL500mkII GOLDRING G950
PRICE £16.95 + 50p P&P STANTON £7.15 + 50p P&P**

STEREO DISCO MIXER DJ6500

★ WITH ECHO ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with tone control & talk-over switch, 7 Channels with individual faders plus cross fade, Cue Headphone Monitor. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.




Price £134.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

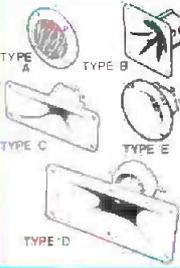Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series. **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/4" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 - 60p P&P.

OVP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE

Made especially to suit today's need for compactness with high output sound levels. Finished in hard wearing black vinyl with protective corners, grille and carrying handle. Each unit incorporates a 12" driver plus high frequency horn for a full frequency range of 45Hz-20KHz. Both models are 8 Ohm impedance. Size: H20" x W15" x D12".



CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

**OMP 12-100WATTS (100dB) PRICE £163.50 PER PAIR
OMP 12-200WATTS (200dB) PRICE £214.55 PER PAIR**

SPECIALIST CARRIER DEL. £12.50 PER PAIR

IN-CAR STEREO BOOSTER AMPS



**PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH**

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono


ALL POWERS INTO 4 OHMS
Features: ★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OVP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and H.F. etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

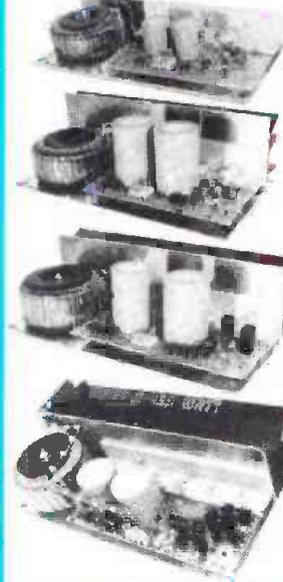THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P

OMP/MF 200 Mos-Fet Output power 200 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R -110 dB. Fan Cooled, D.C. Loudspeaker Protection. 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D.s (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control for very fast rise and decay times. Tough moulded plastic case, with acrylic tinted front. Size 84 x 27 x 45mm.
PRICE £8.70 + 50p P&P

LOUDSPEAKERS

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (50p STAMPED) FOR COMPLETE LIST.

P - From McKenzie Professional Series
S - From McKenzie Studio Series

MUSICAL INSTRUMENTS P.A. ETC

- ALL MCKENZIE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT P.C.8-100GP GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. RES. FREQ. 80Hz, FREQ. RESP. TO 7KHz, SENS 96dB. **PRICE £31.45 + £2.00 P&P**
- 10" 100WATT S.C10-100GP GUITAR, VOICE, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 72Hz, FREQ. RESP. TO 6KHz, SENS 97dB. **PRICE £38.89 + £2.50 P&P**
- 10" 200WATT S.C10-200GP GUITAR, KEYB D, DISCO, EXCELLENT HIGH POWER MID. RES. FREQ. 69Hz, FREQ. RESP. TO 5KHz, SENS 97dB. **PRICE £53.21 + £2.50 P&P**
- 12" 100WATT P.C12-100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 98dB. **PRICE £40.35 + £3.50 P&P**
- 12" 100WATT P.C12-100TC (TWIN CONE) HIGH POWER. WIDE RESPONSE. P.A., VOICE, DISCO. RES. FREQ. 45Hz, FREQ. RESP. TO 12KHz, SENS 97dB. **PRICE £41.39 + £3.50 P&P**
- 12" 200WATT S.C12-200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES. FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS 99dB. **PRICE £71.91 + £3.50 P&P**
- 12" 300WATT S.C12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARDS, DISCO ETC. RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 100dB. **PRICE £95.66 + £3.50 P&P**
- 15" 100WATT S.C15-100B BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 98dB. **PRICE £59.05 + £4.00 P&P**
- 15" 200WATT S.C15-200B VERY HIGH POWER BASS. RES. FREQ. 40Hz, FREQ. RESP. TO 3KHz, SENS 98dB. **PRICE £80.57 + £4.00 P&P**
- 15" 250WATT S.C15-250B VERY HIGH POWER BASS. RES. FREQ. 39Hz, FREQ. RESP. TO 4KHz, SENS 99dB. **PRICE £90.23 + £4.50 P&P**
- 15" 400WATT S.C15-400B VERY HIGH POWER, LOW FREQUENCY BASS. RES. FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS 100dB. **PRICE £105.46 + £4.50 P&P**
- 18" 500WATT S.C18-500B EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES. FREQ. 27Hz, FREQ. RESP. TO 2KHz, SENS. 98dB. **PRICE £174.97 - £5.00 P&P**

EARBENDERS' HI-FI STUDIO, IN-CAR ETC

- ALL EARBENDER UNITS 8 OHMS** (Except EB-50 & EB10-50 which are dual impedance lapped @ 4 & 8 ohm)
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND**
- 8" 50watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB. **PRICE £8.90 + £2.00 P&P**
- 10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB. **PRICE £13.65 + £2.50 P&P**
- 10" 100WATT EB10-100 BASS, HI-FI, STUDIO. RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB. **PRICE £30.39 + £3.50 P&P**
- 12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB. **PRICE £42.12 + £3.50 P&P**
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
- 5 1/4" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB. **PRICE £9.99 - £1.50 P&P**
- 6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB. **PRICE £10.99 - 1.50 P&P**
- 8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB. **PRICE £12.99 - £1.50 P&P**
- 10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB. **PRICE £16.49 - £2.00 P&P**

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE. RANGE UP TO 3 MILES. SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 - £1.00 P&P




PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS
UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA,
ESSEX, SS2 6TR,
Tel.: 0702-527572 Fax.: 0702-420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, P.L.C.s ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



**Volume 21 No.12
Dec 1992**

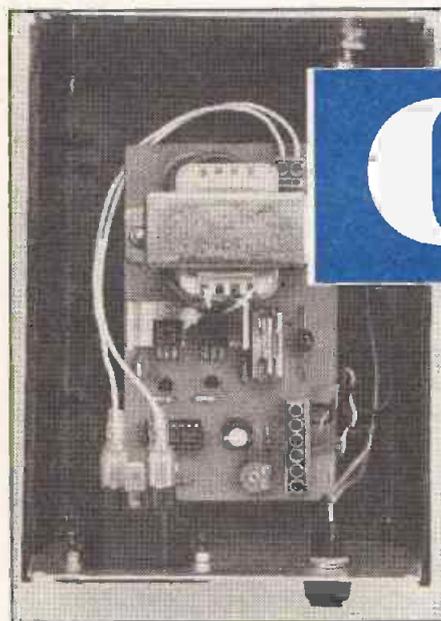

Page 32

Features & Projects

20/50/100watt Mains Inverter	16
Power up your mains equipment on the move from this 12 to 240V inverter. Mark Daniels reveals the details.	
The AutoMate Mixing Desk Part 8	23
Mike Meechan provides the EQ circuitry for the Automate Mixer	
Digital Circuit Tester	32
A project to test your logical digits. Daniel Brook explains.	
Hybrid Line Amp	36
Another in the valve/transistor catalogue of designs from Jeff Macaulay.	
Audio Response Measuring System Pt 2	42
Ralph Mantel now presents constructional and software details for a project to test the response of your loudspeakers.	
RS232 Interface	48
A serial communications interface for your computer. Construction by Keith Garwell.	
The Greening Of The Car	54
Douglas Clarkson reports on the way the car industry has made attempts to clean up its act.	

Contents

Regulars

Open Channel	4
News	5
News Stateside	9
Read/Write	10
PCB Foils	61
PCB Service	62

Editorial

by Paul Freeman

Firstly many thanks for the return of our reader survey. It certainly helps to know your views on the sort of material you require in ETI.

The convergence towards a certain computer format has emerged from your replies and that standardisation seems to be moving towards an IBM PC format. I think we would all agree that standardisation is essential if information is to flow freely and easily between computers and their operators. Japanese manufacture of PC clones must have played a significant role in this process bringing greater availability, portability and lower cost to the consumer.

Conflict of interests

I very often have a good laugh over how

media news journalists attempt to report on scientific concepts.

"The simplification process can end in further confusion for the viewer or reader. Their lack of comprehension illustrates the need for a very broad based education for journalists and many other individuals in society including government officials".

"The best people at present to simplify scientific jargon are scientists themselves when asked to do so. They have both the everyday language and specialist knowledge to do just that. The sooner the news media realises this the sooner we could start to address the terrible problem of the arts/science imbalance in education, governmental bias and a society fearful of technology".

OPEN CHANNEL



High definition television, in the guise of the HD-MAC derivative, long the spearhead of Europe's television manufacturers, looks as though it might finally bite the dust.

I've been predicting this for long enough, of course. My first qualms about the system have always been my main argument against it. It is not a digital system. MAC uses a quasi-digital principle - its very name (an acronym of multiplexed analogue component) tells you this - to transmit analogue signal elements of video and audio components, in a time-switched multiplexed manner. So, while Mac offers the benefits of higher picture and sound quality due to the separation and independent transmission of the signal parts, it still uses an analogue base.

This makes it little more than a temporary stepping stone to a more permanent digital transmission system.

Even more than this - the stepping stone which MAC affords us, as we cross the river from analogue to digital television technology, isn't even in the right direction. If we go the HD-MAC route, the stepping stone takes us out to the still waters of the river. And we know what still waters do...

The eventual aim of television broadcasting, is to transmit all signals totally digitally.

If we go the MAC route now, the stepping stone gives us a breather for a few years while we stand in the deep waters of the river, but then the jump to the riverbank on the digital side of the river is no shorter thanks to being there. We still need to jump, and being in the deep waters there may be a greater chance of drowning. To be honest, I see and understand what the European manufacturers are trying to do. By creating a new system they hope to create a new marketplace. Everyone in Europe will (they hope) buy a new MAC-based television, so everyone (especially the manufacturers) will be happy. But I believe now's not the time.

NICAM stereo and a change to a better PAL-based system (probably the format known as PALplus) can give excellent sound and pretty good pictures, too. True, technically not so good as HD-MAC, but cheaper, less confusing to Joe Public, and a stepping stone more in line with a cohesive transition from analogue to digital television.

Wait till a viable digital system has been developed. That's my advice.

What's On Radio?

Every now and again, the ether gets clogged up. Too many people broadcasting too many things, to too many receivers. You know the sort of thing; Radio 1 wants a new FM frequency but Radio 2 won't move. Well, yes. That's a simplification, but it illustrates the point.

Taken globally, what's good for one country may be an anathema to its neighbours. There is an established procedure setup to define what frequencies can be used by the various countries in the world, and for what specific purposes. The procedure is to hold a World Administrative Radio Conference (WARC), and to thrash out the requirements and frequency slots available to each member country,

and the purposes to which these frequencies can be put. Generally these WARCs, held every few years, plan for the foreseeable future with a pretty clear vision. There is therefore little argument over the conclusions, and they are binding as they are integrated into the Radiocommunications Regulation, which is an Internationally recognised treaty. Looking at the conclusions of one of these conferences, therefore, can give an idea of the way things are going to develop over the coming years. Developers request use of radio frequencies because they have a pretty good idea of what they want to do in the near future, so by looking at allocated frequencies it's possible to make some basic predictions about TV, radio, satellite and mobile comms.

The latest WARC was held earlier this year, albeit allocating frequencies mainly only available as from the year 2007. Nevertheless, its main conclusions are pretty interesting to us. First, high definition television allocations by satellite are allocated to the 21GHz waveband in Europe. The Americas' slot for the same will be the 17GHz band.

Second, digital sound radio services have been allocated two slots. Terrestrial services will be digitally broadcast in the VHF band, but satellite services will be in the 1450-1490MHz band.

Finally, and what personally is most interesting, low earth orbit (LEO) satellites have been allocated two bands. Radio location and data transmission satellites (called small LEOs) have frequencies below 1GHz. Large LEOs, on the other hand, are in the 1.6GHz band. These large LEOs will be used for voice telephony.

Low earth orbit satellites are those satellites which orbit quite closely to earth's surface. Because they orbit much closer to earth than geostationary satellites, their orbit time is much quicker, and several satellites need to be in operation to allow total global coverage. I mentioned Motorola's Iridium project a few months' ago in Open Channel and this is a classic example. Iridium is so named, because the system uses the same number of satellites in low earth orbit as the element iridium's atomic number, that is - 77. Such a system of LEO satellites will realise potential of a mobile communications network in which fairly simple hand-held (pocket-sized, wristwatch sized?) transmitter/receivers could be used anywhere around the world.

You're Calling It What?

Talking about low earth orbit satellites allots me to tell you something which you might find amusing. Motorola's Iridium project is being slightly redesigned. It's now planned to give each satellite greater transmission and reception capabilities by carrying 11 extra transponders. Because of this, fewer satellites will be needed to provide world coverage. Instead of 77 satellites, it's calculated that only 66 will be needed. This should greatly reduce costs, of course. But it does mean that the project name should be changed, doesn't it? Instead of Iridium, we'll have to start calling it by the name of the element with the atomic number of 66 - Dysprosium.

Keith Brindley

Face-to-face meetings between people at their desk-tops are now possible following BT Visual and Broadcast Services's launch of its VC7000 videoconferencing system.

Costing just £7,500, BT describes the VC7000 as the lowest

BT LAUNCHES LOWEST COST VIDEOCONFERENCING SYSTEM

cost videoconferencing unit in the world. It allows small groups of people to see each other and show documents and objects regardless of their location. It can also be used for giving presentations, showing product designs and holding training sessions.

BT believes that this low price will vastly increase the size of the visual services market. Steve Maine, BT's Director of Visual and Broadcast Services said: "Traditionally, users of videoconferencing have been large corporations, but the launch of this unit will enable smaller companies to reap the benefits of visual communication."

"The launch of the VC7000 is undoubtedly the first step towards the visual services mass market. It will radically alter the way peo-



ple do business by allowing them to have instant face-to-face meetings with colleagues, customers and suppliers regardless of location."

BT has already sold the first VC7000 units to National Power. Tony Stewart, National Power's Customer Services Manager, Telecommunications, said: "The VC7000 has completely changed the economics of videoconferencing and will play an important part in improving desk to desk communication between key people in National Power. I also see this as an enabler to a whole range of other business applications. For example, remote help desks could act

as a central core of expertise."

The unit is manufactured by the Norwegian company Tandberg and complies fully with the CCITT's H.320 series of international videoconferencing standards. It works over BT's dial up digital network ISDN, at 64 or 128kbits/sec.

"Because the unit conforms to international standards," continued Maine, "It will interwork with any currently existing standards-compatible product, including all the BT H.320 equipment that has been sold in the last three years."

"This is the first of many new products which will come onto the market in the next few years. Standards are vital because our

customers must be able to buy a kit which is compatible with equipment manufactured by other companies.

"In addition, the price of equipment will only drop if manufacturers can produce it in large quantities, and they will only do this if they are confident that the market will continue to grow."

BT also announced earlier this year that they will be launching a PC-based videophone, in collaboration with IBM, in the first quarter of 1993. Further launches of videophone products will take place later that year.

MINIDISCS IN EUROPEAN RECORD STORES BEFORE CHRISTMAS

The new portable audio system for digital recording and playback will be available in the shops for Christmas.

Focusing on portability, the first products on sale will be two types of Walkman, the playback/record and the playback only version, as well as a MiniDisc car stereo model.

An MD software catalogue will be available in time for product launch listing 300 titles, with 500 titles being available by the end of the year.

Many leading record compa-

nies have already confirmed that they will support the introduction of the new disc-based digital recording and playback system with a selection of albums from their top artists, resulting in an initial launch catalogue of around 300 titles, spanning the whole range of music repertoire, from classical to rock.

MD software will be available from: EMI Music (including labels such as EMI, Capitol, SBK, Chrysalis and Parlophone), Factory Records, Mute Records, ARS Records, Curb Records, Sony

Music (labels include Columbia, Epic, Def Jam and Sony Classical) Virgin Records (labels include Virgin, Circa and Ten) and most recently support from the Warner Music Group. Further backing from additional record companies is confidently expected. Many major artists are already scheduled for the launch catalogue, amongst them: Michael Bolton; Depeche Mode; Bob Dylan; Erasure; The Gipsy Kings; Michael Jackson; Lenny Kravitz; George Michael; Gary Moore; Robert Palmer; The Rolling

Stones; Roxette; Simple Minds; Soul II Soul; Bruce Springsteen; Talking Heads and Technotronic.

Not only has Sony confirmed its belief that Compact Disc should continue as the benchmark home audio format, but the company has enthused the record industry with its intention to prioritise portable - rather than home-based - music enthusiasts with an SCMS-equipped recording & playback MD Walkman, a playback-only MD Walkman and an MD in-car system.

Although within its protective

slim-line cartridge, an MD disc measures approximately 2.5" (6.4cm) in diameter, MD premastered software is based on the same optical disc recording principle as CD, with information recorded as pits on the disc's surface. Given that the shape and distribution of these pits are similar for both formats, MD software can be manufactured using existing CD production equipment with relatively minor modifications. Within the Sony group, three software production facilities in Europe (DADC Austria), Japan and the US are already custom pressing orders from record companies

and by the end of the year, monthly production from these plants will total 1.5 million discs worldwide.

Accolades for MiniDisc are coming in from throughout the music industry: "MD presents the consumer with the quality and convenience of CD, along with portability and recordability features," said Jim Fifield, President and CEO, EMI Music Worldwide. "The music fan will be very excited about this new optical carrier."

Bob Krasnow, Chairman, Elektra Entertainment, called MD the "best format since Thomas A. Edison."

Added George Michael, internationally renowned recording artist, writer and producer: "The sound is phenomenal....it's the future and I want the first one!"

Disc Media:

The Future of Audio


Ten years after the debut of Compact Disc, the introduction of MD brings a whole new dimension to the listener's enjoyment of music. The random access capability and ease of use offered by CD have always met with a very positive response from European consumers. Sony developed the high-tech MiniDisc because it is convinced that today's consumer

demands the features and benefits optical media can deliver - not only in the realm of home audio, but also in mobile, portable and personal listening applications where reliability and durability are critical. MiniDisc brings to Walkman, portable systems and in-car stereos the random access capability of a disc medium in a compact size. It also delivers a sound quality approaching that of CD, ease of handling and a simple, high quality recording capability vastly superior to that of the conventional compact cassette.

VOICE RECOGNITION FOR CONSUMER PRODUCTS

AT&T Microelectronics has produced a voice recogniser for speedier automatic dialling. Users can 'train' the hardware to act on up to 40 key words or phrases, which are recognised within 0.5sec, even under noisy conditions, such as those encountered on the move in a motor vehicle, or in an industrial environment. Sophisticated noise cancellation algorithms allow the voice recogniser to achieve 95% accuracy in such situations, a figure which exceeds 98% in environments with low background noise.

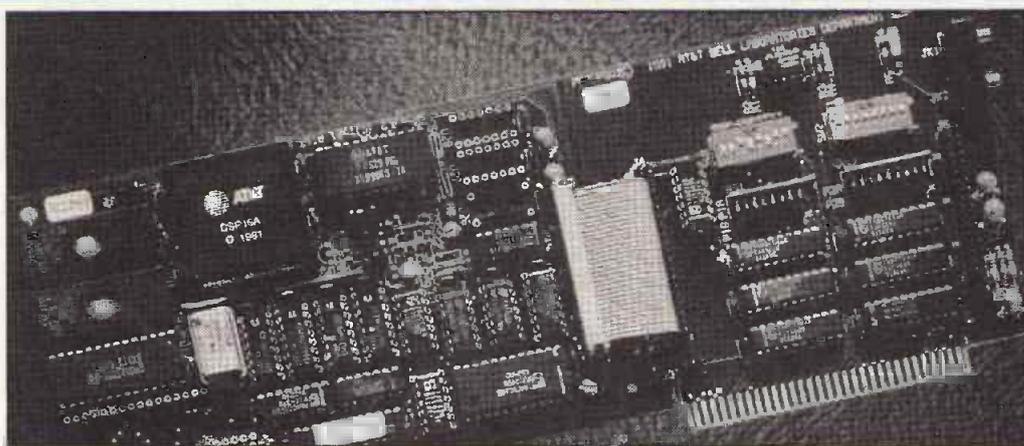Its principle application will be in automatic dialling where users can dial a number simply by speaking the name of the person to be called. The technology is also sufficiently flexible and low-cost to be used in products as



diverse as microwave ovens, industrial controls, and digital answering machines.

Based on AT&T's WE-DSP16A digital signal processor chip, the voice recogniser also includes a 32K x 8, 150nsec SRAM block, and the interface

logic required to marry host processor, DSP, and memory. The training algorithm is used to improve reliability of recognition. The target user says the key word or phrase, and the recogniser effectively stores this in memory. The hardware then asks the user

to repeat the key word, and combines the information obtained in the two passes, to improve recognition and reduce the possibility of false keyword detection.

Reader enquiries to Vic Drake, Admail 4 International Ltd, Tel: 0732 460424

ARTISTIC HARMONY BRIDGES THE EUROPEAN DIVIDE

In these uncertain economic and political times, Art is set to play an increasing role in developing a wider sense of communality between the diverse cultures of the new European Generation.

CEREC (Comite Europeen pour le rapprochement de l'economie et de la culture) and

Northern Telecom have launched the first ever pan-European Arts sponsorship programme.

Sponsored by global telecommunications company, Northern Telecom, Northern Telecom Arts Europe (NTAE) forms a unique funding programme designed to enable European Arts establish-

ments and artists to engage in collaboration and exchange.

Incorporating all Art forms, from the diverse fields of music and theatre to dance and photography, from classical to contemporary, this initiative aims to extend the boundaries of the familiar to stimulate new ideas.

NTAE is worth a minimum of £750,000 (sterling) to the Arts over a three-year period. In the first year, awards of £50,000 will be given to professional Arts organisations based in France, Germany and the UK., extending into at least three further European countries during 1994 and 1995.

FASTER FRACTAL COMPRESSION FOR WINDOWS

Iterated Systems Ltd has announced Images Incorporated version 2.0 for Windows, the next release of their Fractal Transform image compression and enhancement product for end users.

Version 2.0 offers faster fractal

compression in software alone, and now handles full screen Super VGA image files. It also supports batch processing, provides on-line help and has a simplified installation routine.

Alan McKeon, Managing Di-

rector of Iterated Systems Ltd, commented: "Responding to market demand, this new version overcomes the previous 640 x 400 pixel barrier, and compresses substantially faster." He added: "As part of our mass-market strategy,

we have reduced the price by one third to £299."

Images Incorporated v2.0 for Windows is designed for use in desktop publishing, desktop presentations and other image-handling situations. Users can build

up a library of photographic quality images conveniently compressed to very small file sizes using Fractal Transform image compression.

Compression ratios of 100 to 1 can be achieved, while retaining the image quality. Decompression is typically quicker than displaying the original image file. Further, fractal compressed im-

ages are resolution independent, meaning they can be decompressed and displayed at several scales.

Images Incorporated also features Fractal Transform resolution enhancement. This technique is applied to original, uncompressed image files, allowing a zoom in facility without pixelation. Additional detail is


fractally predicted and added virtually losslessly to the original image data, without compression. This is useful for resizing images, or for increasing the number of dots per inch to allow printing at a higher resolution than the image was scanned at. The technique is unique in that it predicts infinite detail, while other methods use pixel averaging which

causes smeariness.

Existing users can upgrade to version 2.0 for just £45 plus VAT.

Images Incorporated is available through selected dealers for £299 plus VAT. For nearest reseller, potential users should call Iterated Systems direct on 0734880261. Academic Discount is available to education establishments.

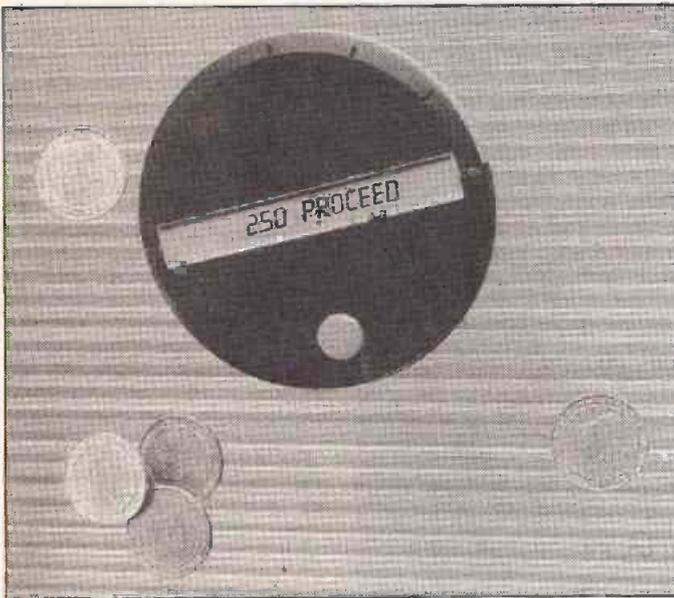ELECTRONIC TOLL & TRAFFIC MANAGEMENT SYSTEM



Dover Electronics, Binghamton, NY, and AT/Comm, Inc. of Marblehead, MA, have entered into an agreement that will allow them to exploit the burgeoning markets for radio frequency identification systems in the transportation industry. The first product is a system for non-stop electronic toll collection. This tested and patented technology allows motorists to travel non-stop through toll lanes, thereby reducing traffic congestion as well as fuel consumption and auto emissions. The

system was recently tested at speeds in excess of 90 mph. by New Hampshire State Police.

Designed and marketed by AT/Comm, this approach to toll collection is being heralded as the most advanced in the market based on its two-way radio communication techniques, known as 'read-write'. Europe, the Pacific Rim, and most recently the Illinois Tollway have specified microprocessor-based transponders with read-write capability for electronic toll collection. Most other com-

petitors for this multi-billion dollar market have only recently responded to AT/Comm's advancements, announcing plans to develop and test read-write systems of their own. AT/Comm owns broad patents on read-write technology.

In the electronic toll collection, read only refers to a non-stop toll collection process that uses either barcode tags or radio reflective tags to simply 'read' the ID of a passing vehicle. This process is very expensive and complex (and a worry to privacy advocates) because it requires toll agencies to centrally maintain toll accounts and travel records for all their once anonymous patrons. Moreover, read only systems require that all electronic toll lanes on a toll road be networked to validate possibly hundreds of thousands of motorists' account balances. If read only technology were applied on a regional basis, this would require a substantial new bureaucracy to manage possibly millions of toll accounts and to keep track of everyone's travel. For toll road agencies, which charge tolls based on entry and exit locations, read only is an impracticality.

Read-write refers to a non-stop toll collection process that provides intelligence in the trans-

ponder. Not only can this vehicle-borne device be 'read' as it passes through a toll lane, but information can also be 'written' onto the transponder. This could be the entry point of a turnpike so that the proper toll could be calculated upon exit.

The AT/Comm system is the most advanced form of read-write. It is known as microprocessor-based read-write, which allows the transponder to be 'read', be 'written' to, and also provides processing to manage the data internally. The smart, microprocessor-based transponder maintains prepaid toll accounts in the transponder, thus relieving the agency, and ultimately the motorist from the cost associated with centralized accounting. Like a postage meter, the transponder is electronically charged with a value, and that value is reduced each time the car passes through a toll lane. An LCD display and audio alarm on the device also gives the motorist real time information on his or her account.

The AT/Comm smart transponder is also a platform for other 'Intelligent Vehicle Highway Systems' (IVHS) applications such as incident warnings, automated parking, commercial vehicle access control at airports, and other traffic management uses.

TECHNOSHOP '92 - A PLAN TO HELP UK MANUFACTURERS BEAT THE RECESSION

Where manufacturing firms are trying to ride out the world recession by cutting back on R & D investment, they are naturally reluctant to spend money now on buying in new developments from outside.

But, many of the organisations around the world who have invested in R & D during this period are now having to prune their

operations even harder. Some research organisations, who normally market their top R & D output to major corporations, are keen to talk to any firms who are astute enough to be making their product plans ready for implementation when the end of the recession is in sight.

So there are some good 'buys' around in the technology market

and one UK organisation, a not-for-profit company called The Technology Exchange Ltd has published a two volume catalogue covering 5,000 currently available licence and joint venture offers following a search of over 3,000 organisations in 34 countries.

Organisations like Krupp and Aerospatiale, universities and in-

stitutes like MIT, UCLi and Cornell are amongst those whose offers have been selected for publication.

Firms buying the catalogues can choose the offers they require, get a confidential introduction by fax and post, then hold preliminary meetings at the annual Technoshop Fair.

Then negotiations, which gen-

erally proceed slowly, can be ready for implementation when the recession ends.

So manufacturers, can avoid making an investment until the last moment and be ready to launch

new technology products just when their competitors are reviving their old product lines which have been in cold storage for a couple of years at least.

In 1990, when the first two

volume catalogue set called "The Next 5,000 New Products" was published, over 800 firms in 51 countries used them and requested 3,000 introductions. Over 500 negotiations were underway

within six months after publication.


For further details fax: The Technology Exchange Ltd on 0525 860664 or write to them at Wrest Park, Silsoe, Beds MK45 4HS.

CHIPSET FOR TAPELESS ANSWERING MACHINE

A new telephone answering device (TAD) chipset, developed by AT&T Microelectronics, provides the core functions required to build a tapeless answering system, in either standalone or integrated products. By replacing the traditional mechanical tape recorder, the TAD chipset allows more reliable and low-cost answering machines to be designed.

The highly integrated DSP-based chipset enables a fully featured answering machine to be configured using just the chipset and a host microcontroller, memory and an analogue switch.

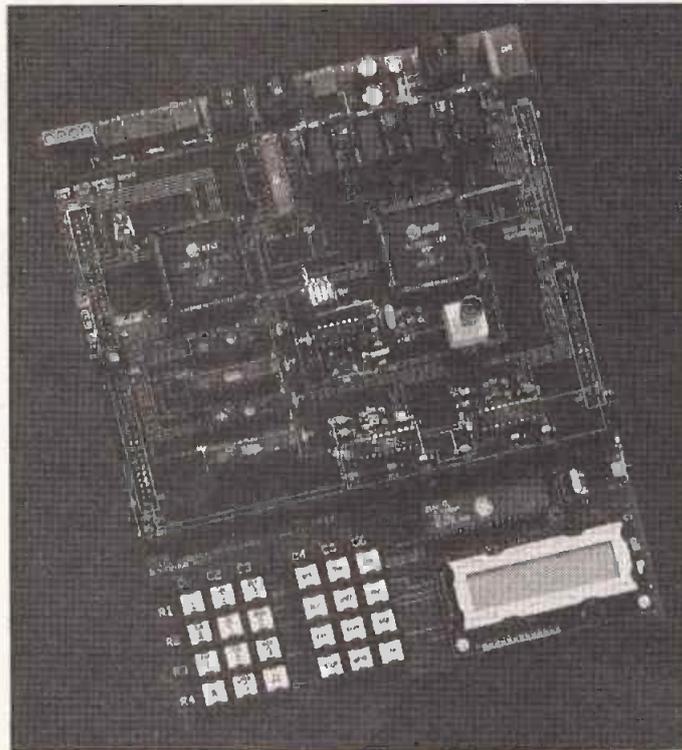The TAD chipset consists of a ROM coded DSP16A1, a T7513B 8-bit μ -law codec and an AT&T custom chip which provides the necessary clocks, control signals and power management. Incorporated in the chips are software algorithms to perform all the functions necessary for speech compression, telecommunications signalling, memory management and




remote operation via touch tone (DTMF) control.

A low bit rate, high quality, speech coding algorithm, developed by AT&T, enables approximately 2.5 minutes of message storage per Mbit of memory, allowing up to 76 minutes of recording in 32Mbit of memory. In addition, cost is reduced by a proprietary memory-management system, which allows the use of low-cost audio grade DRAM (ARAM) for incoming and outgoing message storage. The addition of a read-only memory enables the TAD to play synthesised voice and user prompts, instructions and deliver message time labelling.

The TAD chipset is controlled by a system microprocessor via a 4 or 8 bit interface using a command/response-based architecture. Reader enquiries to: Vic Drake, Admail 4 International Ltd, Tel 0732 460424

LOW COST FREQUENCY MEASUREMENT TO 1.3GHZ

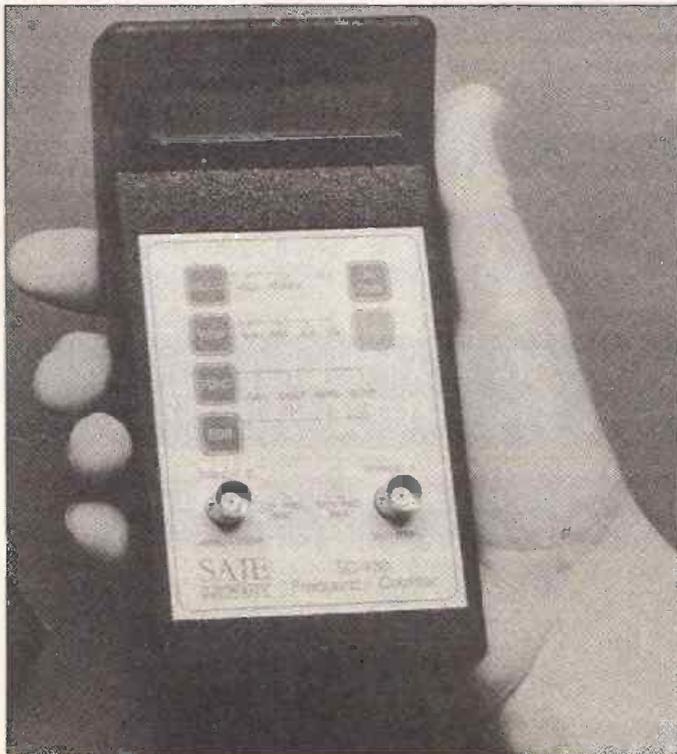

New from Saje Electronics are two microprocessor based hand-held frequency counters.

Their design incorporates an angle mounted 16 x 1 liquid crystal display giving excellent readability from a wide viewing area whether in hand held or bench applications.

Annunciators are displayed to assist in defining and editing set up and measurement criteria. A battery condition indicator gives readout of the battery condition.

Both instruments provide a full range of features including measurement of frequency, period, count and with a unique View facility enabling Min, Max, Average and Difference readings to be displayed. In Frequency mode a range of gating rates from 0.15 to 10 seconds is provided plus a switchable low pass filter. A display hold function is standard.

The SC-130 offers a frequency range of 5Hz to 1.3GHz and the SC-40 from 5Hz to 400MHz. Both

instruments provide good sensitivity and high accuracy.

The instruments are housed in rugged ABS cases with a separate battery compartment for a PP3 size battery.

The SC-130 is priced at £109.00 plus VAT and the SC-40 at £89.00 plus VAT. Both instruments are designed and manufactured in the UK by SAJE Electronics.

For further information please contact:-

SAJE Electronics, Tel: (0223) 425440 Fax: (0223) 424711

**More News
Next Month**




...Stateside...

Voice recognizer

A low-cost voice recognizer may pave the way for evolution of voice dialing as a ubiquitous feature of mobile cellular phones.

Up to 40 spoken key words can be stored in memory, enabling hands-free voice dialing in analogue or digital mobile cellular phones. AT&T claims the speech-recognition algorithm refinements embodied in the voice recognizer were 20 years in the making at AT&T Bell Labs.

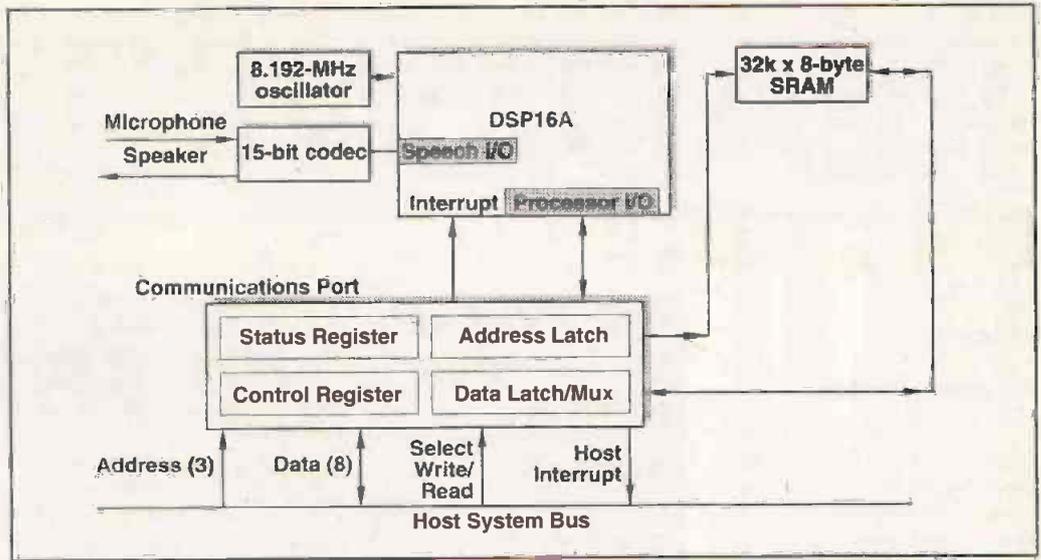Beyond cellular phones, AT&T see applications for the technology in digital answering machines, modems, industrial controls and consumer electronics.



According to market-research firm Herschel Shostek Associates the availability of low-cost voice recognizers will render cellular-phone voice dialing universal in a few years, though last year only 2-3% of cellular phones installed in the United States featured the capability.


The DSP16A with ROM-coded voice recognizer firmware on-chip will be available this autumn for \$20 apiece in quanti-

ties of 10,000.

In the training mode, the recognizer permits the user to store up to 40 spoken words, each of up to two seconds' duration. The recognition mode allows the user to control a process by speaking a phrase that has been encoded and stored in memory. For instance, in cellular-telephone applications, the user would dial a number by speaking a key word (person's name) that is associ-

ated with that telephone number. The voice recognizer's response time is said to be better than 0.5 seconds.

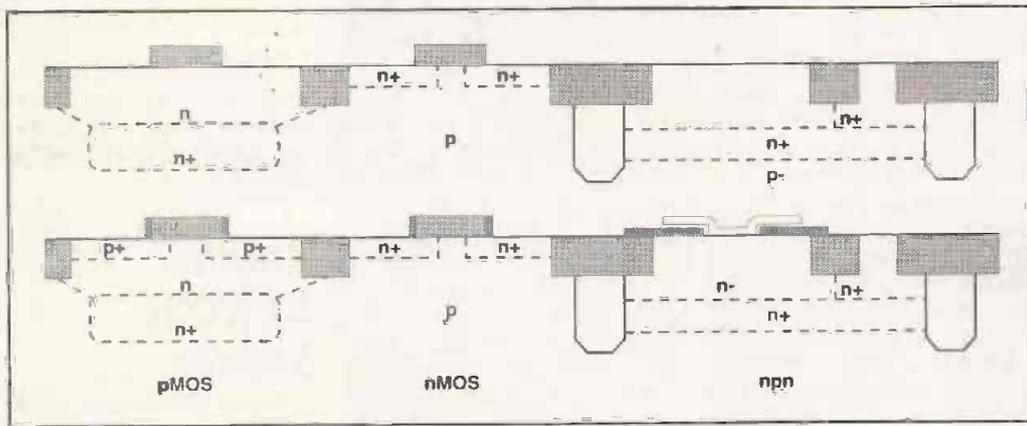AT&T Microelectronics has tested the recognizer in a car moving at 30 mph with the air conditioning on. In that situation, the recognizer "achieved 95% accuracy," meaning it could recognize a user command on the first try 19 out of every 20 times.



Manufacturing ferro-electric non destructive read-out memory

Sandia National Labs has agreed to help startup Radiant Technologies Inc. perfect the manufacturing of ferro-electric non-destructive read-out memory.

Radiant was formed by founders of Krysalis Semiconductor Corp. to focus on equipment for testing ferroelectric thin films. Radiant revealed it had won a patent on a special resistive element sandwiched in ferroelectric

and semiconducting layers of thin film.

The Sandia equipment will enable the team to take the first steps toward developing thin films based on plasma-enhanced metallo-organic vapour deposition.

Ferroelectric materials, a class of perovskite ceramics with the capacity to hold a polarization state, have been explored for sev-

eral decades as potential candidates for non-volatile memories. Recent work on ferroelectric thin films has linked the materials' future to improvements in thin-film deposition techniques, with many research teams exploring low-temperature deposition techniques to improve reliability.

Other materials research has sought to depart from the traditional, Lead zirconate-titanate (PZT) and Lead-Lanthanum Zirconate-titanate (PLZT) compounds used in ferroelectrics.

Since all memory reads in traditional ferroelectric devices require destructive readouts, which could be disrupted by single-event

upsets, a truly non-destructive readout memory device such as the one proposed by Radiant would move ferroelectric research a giant step forward.

Radiant's design calls for depositing a semiconducting thin film atop a PZT thin film. The conductivity of the top layer is modulated by the PZT layer's state of polarization. Reading the device merely involves monitoring the current.

Because it is configured similarly to a programmable resistor, the Radiant design could be used in programmable logic devices and, possibly, as a replacement for analogue elements in neural networks and AI computing.

The memory is expected to have 10¹² writes, unlimited reads and a minimum data retention of three years.

Radiant and Sandia will try to improve thin-film reliability along several axes, targeting the ability to process wafers at 400°C. The research team will look at biasing thermal substrate temperature and will also seek to adjust the chemistry of the processes by varying the metallo-organic precursors.

READ/WRITE **ETI** Letters

Window Opener Questioned

I refer to the article 'Window Opener' by Terry Pinnell. I imagine it would be a kind gesture if Terry was informed that it may be, cheaper, easier and not require keeping awake to operate a bedside control, if a simple fly screen was fitted to an open window in the first place before retiring with his book, when he could enjoy fresh air whilst reading.

Quite frankly, I cannot imagine a greater waste of effort on designing something for the sake of it.

J M Whiteley,
Ravenstone, Leics

Each to their own - Mr Whiteley. I agree in principle with what you say, but there could be occasions when the person in bed is not able to physically get out to open a window and it may be that a window is beyond normal reach say in tall buildings or industrial greenhouses. I think the idea is sound, but it is the application which must be questioned. - Ed.

Moving LED Display Requested

Having used circuits (or variations) from your magazine for many years, I am surprised that there is one item that I have not seen mentioned over the years. What I am trying to produce is an LED moving message display as seen in lots of shops and post offices. Although at first it seems quite simple, I soon discovered the whole problem can be quite complex. Can you or your readers give me any pointers towards any books/publications that can help me?

C N Eaton
Plympton, Devon

Yes, a good idea for a project and we will see what can be done - Ed.

DIY Warning for Electronics In Light Aircraft

Regarding the Light aircraft Intercom in the Sept '92 issue. As both a PPL and an electronics engineer, I feel I should warn readers that although the above project is an excellent design and certainly cheaper than any commercial unit, connection of this unit to the aircraft electrical/radio systems may invalidate the radio licence and could affect aircraft instruments, especially the magnetic compass. I'm afraid such systems must be certified by the CAA - Hence the high cost of such equipment. Many thanks for an excellent magazine.

Ed Dinning,
Newcastle

After a break of several years I recently purchased the September issue of ETI (I first started reading ETI in the seventies), and found it most interesting. However I must comment on the 'intercom for light aircraft' project. While this design is sound from the electronic view point, it has several drawbacks from the aviation side. While the author states that 'it is not wise to discard the previous microphone/phones etc immediately' in case of unit failure, this failure could happen at any time, and the headsets he describes are not compatible with

Loop Aerial System Requested

The Surround Sound Decoder in the July issue of ETI prompts me to write to you about a loop system for my own use at my home. I have great difficulty in listening to TV, or radio, because of a hearing problem, and the hearing aid develops condensation which makes matters worse.

standard aircraft radios. Commercial "carry on" units of this type normally use standard headsets with failsafe relay switching to by-pass the amplifier in case of failure or loss of supply. The legal situation also needs to be clarified. The Civil Aviation Authority regulates aviation in the UK, and any modification to an aircraft or its systems may only be carried out and certified by a licensed engineer or approved organisation. Any unapproved modification will render the aircraft's certificate of airworthiness invalid, and as a result the insurance also. This project could be considered a modification if it was directly wired to any of the aircraft systems, was physically attached, or derived its power from the aircraft supply. Velcro is not acceptable as a means of attaching equipment, the CAA recently issued a letter reminding approved organisation of the requirement to stress avionics installations so that equipment does not come loose in the event of an accident. For the record, I have been a CAA licensed engineer for ten years.

Robert Atkinson,
Christchurch, Dorset

Points noted, and in the interests of safety, I agree with you both entirely. Had the project originated from the UK, cautionary warnings may have appeared - who knows?. In retrospect, I'm sure the author would also agree that checking circuitry by other official sources is a must. - Ed.

I wonder if any of your technical contributors could furnish details of the loop system used in public buildings, or a similar circuit that I could assemble for my own use. I am not in the clear as to how that system works, so any instructions would be greatly appreciated. Also any hints on the use of lapel mic's used with these systems. If I could obtain a circuit of some rig-up for such a system it would be the answer to my terrible problem.

P Trayers
Wirral, Cheshire

Active speaker With A Difference

As a long time regular reader (and keeper of old issues) many thanks for a stimulating and educational magazine. Recently considering the purchase of a MIDI synthesiser addition to my piano set-up, I was introduced during the demo to an apparently active and effective amplifier/speaker arrangement. There was one bass unit, floor standing, and two high frequency units mounted about ear level. I feel this could be an interesting home build project, or for Blueprint, discussing the frequency ranges required, active filter characteristics, and power requirements. I do not recall any similar project to use as a basis - could it be a first for ETI?

Peter J Metcalf
Paisley, Scotland

We have published a few active speaker designs over the years which have been in one cabinet. This might be an interesting variation - Ed.

Another EPROM Service


Would you oblige if possible by publishing the following details of a service to ETI readers.

EPROM and CPU programming service to ETI readers, the following types at present programmed, 2708, 2716, 2732, 2764, 27128, 27256, 27512, 8048/49/50, 8748/8749/8750, data to be supplied on PC format disk 360k/720k 5" and Apple II 5" disk, £10 setting up charge, printed/typed lists also accepted, EPROMs supplied by customer or purchased from me, for further details contact:

Mr. D. J. Brown
2 Glentworth Avenue
Whitmore Park
Coventry
CV6 2HW

ETI

Christmas Special Offer

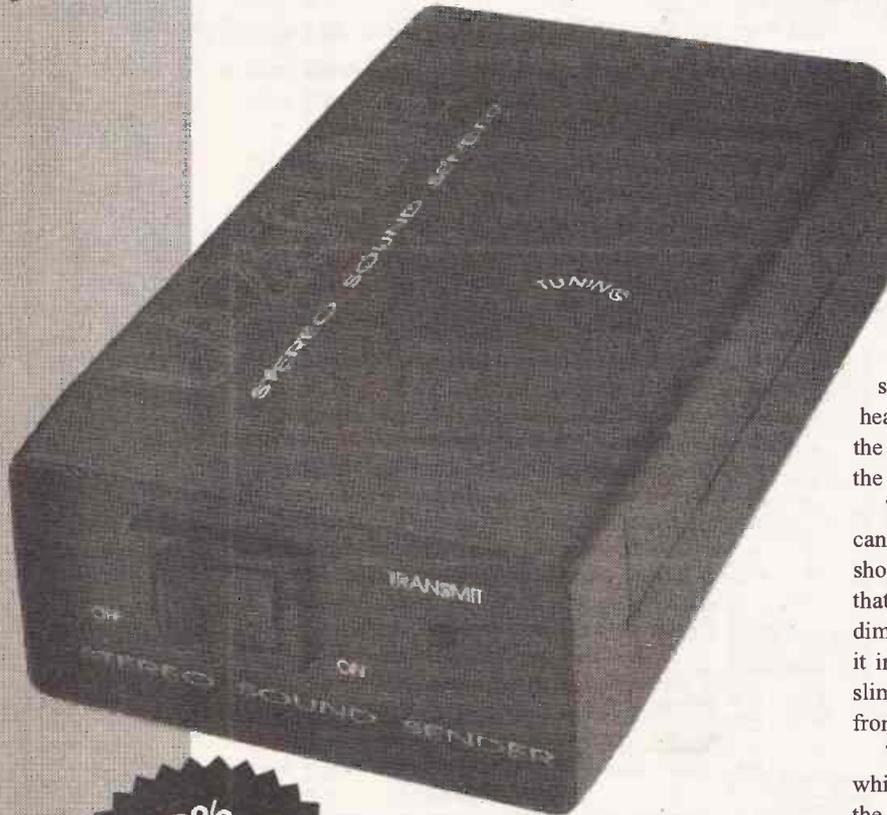

20% Discount to ETI Readers

receiver up to a 200-foot radius. All you have to do is tune your radio to the Sound Sender's frequency, and listen to your own music.

The Sound Sender can do other tricks, too. If you have a portable CD player, now you can listen to it in your car without disturbing the in-car wiring. Place it on a level surface, connect the Sound Sender - and tune in your car radio.

Used with a Walkman-style personal stereo radio and headphones, the Sound Sender acts as a cordless stereo headphone - useful if one of the family is hard of hearing. Connect the Sound Sender to the television, tune in the radio, and the listener can select a comfortable volume on the headphones, without disturbing other listeners.

The Sound Sender is battery powered (by one PP3) so you can use it anywhere. Using an alkaline battery, battery life should exceed 150 hours. Automatic gain control ensures that the modulation level is always correct, and compact dimensions - 2.5 x 1.5 x 4.75 inches - mean that you can slot it in alongside any audio kit from your television to your slimline CD player. Listening volume is fully controllable from the radio receiver you are using.

The Sound Sender can be connected to any sound source which has a stereo output - including technology not yet on the market. It works well with mono-only output, too, with a simple cable-adaptor.

You can re-tune the Sound Sender if the preset frequency is inconvenient for you - but this wouldn't normally be necessary, as the operating frequency is away from broadcast frequencies in most areas.


Have you ever relaxed in a hot bath, or shut yourself into your den for a peaceful hour or two - and wished you could take your CD/cassette/vinyl collection in there with you? Meanwhile, your hi-fi player is nestling snugly in its pride of place in the living room - and somebody else wants to watch the TV!

Dream no more. With the Lazerline Stereo Sound Sender, all you have to carry with you is a portable radio, and you can have the music of your choice anywhere in the house or garden.

The Lazerline Sound Sender is a powerful, full-stereo mini FM relay station. It can relay any audio signal (mono or stereo) from your CD player, hi-fi amplifier, television, VCR, etc., or any other audio signal source, to any FM

Specification

The unit draws 3.3mA typically from a 9V PP3 battery. The current drawn, and the range of transmission, decrease very slightly as the battery runs out. In practice this means that an alkaline manganese battery will normally run the Sound Sender for about 200 hours, but can be relied upon for at least 150 hours. The typical channel separation is 30dB, while the frequency response extends beyond 13kHz. The inputs cope with a signal range of approximately 150mV to 1V RMS. The practical result of all this is that on most program material the received signal from the Sound Sender

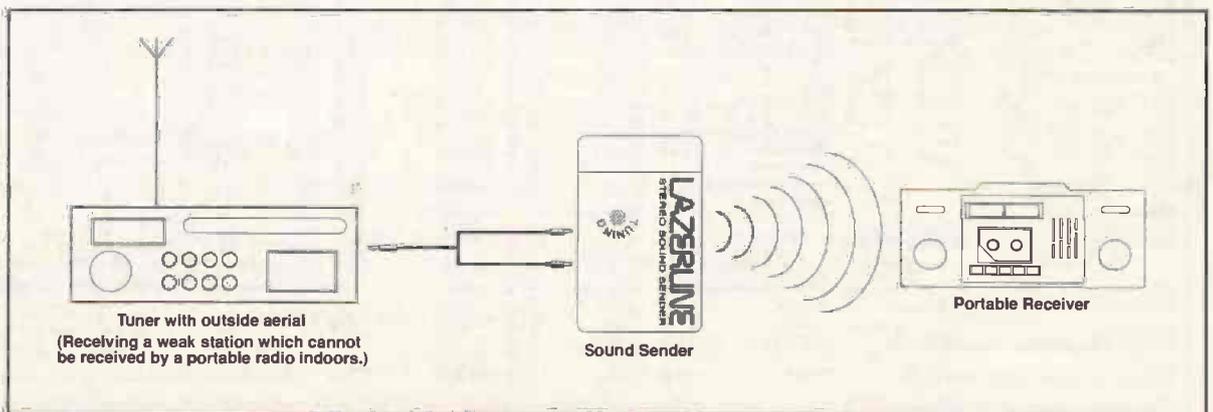

£30 off Europe's best selling oscilloscopes!

- Excellent quality, built to last a life time
- 2 year warranty
- Each 'scope supplied with 2 sets x10 probes, manual and mains lead.



Offer must end 31st Jan 93

PART NO.	DESCRIPTION	USUAL PRICE	OFFER PRICE
HM203-7	20MHz, dual channel	£397.15	£367.00
HM205-3	20MHz, storage 'scope	£716.75	£686.00
HM604	60MHz, dual channel	£716.75	£686.00
HM1005	100MHz, 3 channel	£930.60	£899.00



MULTIMETERS

The D-MM good value meters are now even D-MMer good value!!

The TM series of low cost meters, with 3 1/2 digit LCDs, full overload protection, strong ABS cases and packed with features. Supplied with test leads, battery and manual.

Offer must end 31st Jan 93

PART NO.	DESCRIPTION	USUAL PRICE	OFFER PRICE
TM 5315	DC current (10A) continuity and diode test	£19.99	£19.25
TM 5365	Capacitance and frequency (200kHz) ranges	£36.50	£29.99
TM 5375	Frequency range (20MHz) and HFE test	£36.95	£31.49
TM 115	AC & DC current (10A), HFE and continuity test	£32.50	£30.99
TM 175	Freq. (15MHz), capacitance ranges with HFE, diode, continuity & LED test	£53.60	£45.00
TM 8020	3 3/4 digit display, freq. (4MHz) capacitance (40uF), AC+DC current to 20A	£54.76	£49.95
TM 8030	3 3/4 digit display, freq (4MHz), temp. (inc probe), AC+DC to 20A	£59.96	£55.49
7705	Capacitance meter, 1pF to 20,000uF	£39.82	£35.90



SPECTRUM ANALYSER ADAPTOR

The new TSA250 will adapt any conventional 'scope into a highly cost effective spectrum analyser. With numerous applications in RF design and development work, EMC investigations, and education.

TSA250 **£399.00**


- 400kHz to 250MHz frequency range
- LC display of centre frequency
- Calibration marker



CIRKIT DISTRIBUTION LTD

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ Telephone (0992) 444111 · Fax (0992) 464457

OUT NOW!

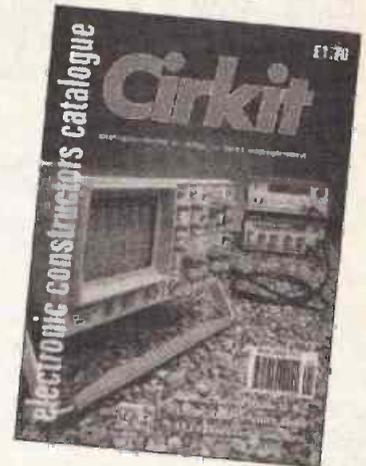

The Brand New Cirkit Electronic Constructors Catalogue Winter 92/93

- 192 pages
- £££'s worth discount vouchers
- 100s new products.....

Books - the latest titles.

Capacitors - new range ceramic discs, extended ranges electrolytic and polyester types.

Computers - new CAD PCB layout software.

Connectors - extended ranges of BNC, Jacks, XLR and PCB types.

Filters - new narrow band ceramic and low pass TV filters.

Hardware - additions include new range control knobs, cabinet hardware and heatsinks.

Inductors - more additions to our already extensive range.

Kits - new additions to the Velleman range.

Rigs - handheld 'CB' transceivers, wavemeters, scanning receiver accessories and aerials.

Semis - new linear ICs, transistors and a complete new range of LEDs including blue types.

Speakers - new radio mic systems.

Test Equipment - new hand-held frequency meter and satellite TV dish alignment system.

And much more besides.....

- Available at larger newsagents, from 12th November, or directly from Cirkit.



All prices include VAT at 17.5%.

Postage and packing; standard £1.40, next day delivery £4.60.


Prices correct at time of going to press, but may change in line with exchange rate fluctuations.



Low cost data acquisition for IBM PCs & compatibles...

All our products are easy to install - they connect directly to either the printer or serial port and require no power supply. They are supplied with easy to use software which collects data for either display or print-out.


ADC-10

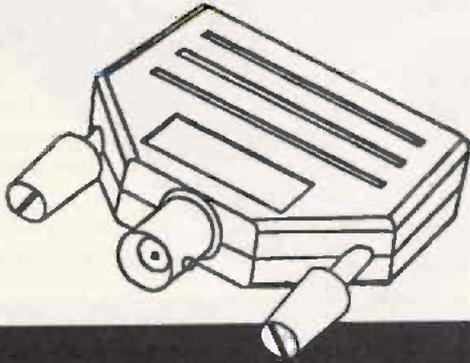

- 8-bit resolution
- one channel
- 10-25k samples per second
- Oscilloscope/Voltmeter software
- 0-5 V input range
- Connects to printer port

£49


ADC-11

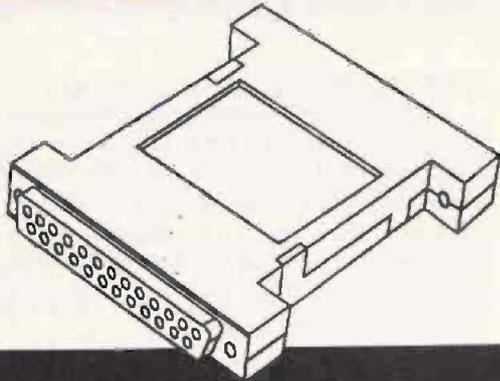

- 10-bit resolution
- 11 channel
- 5-10k samples per second
- Data logger software
- 0-2.5 V input range
- Connects to printer port

£75

ADC-16

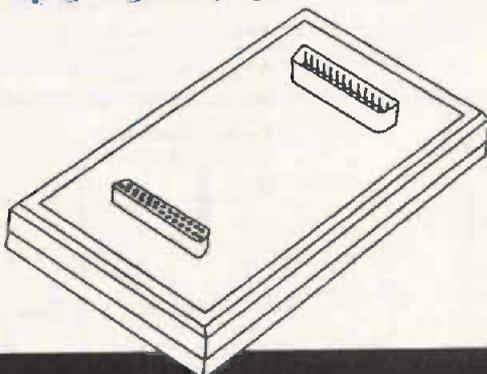

- 8, 12, 16-bit resolution + sign
- 8 s/e or 4 differential inputs
- 2 16 or 300 8-bit samples per second
- ± 2.5 V input range
- Data logger software
- Connects to serial port

£99

All prices exclusive of V.A.T.

PICO TECHNOLOGY LTD

Broadway House, 149 - 151 St Neots Road, Hardwick, Cambridge, CB3 7QJ



Tel: 0954 - 211716


Fax: 0954 - 211880

PICO TECHNOLOGY

Build a 20, 50 or 120Watt inverter for a portable mains power source using our cover PCB. Mark Daniels provides the details

A simple battery to mains inverter can be extremely useful for providing electrical power to small mains appliances in the event of a power failure, or for powering similar appliances in situations where no suitable mains supply is available.

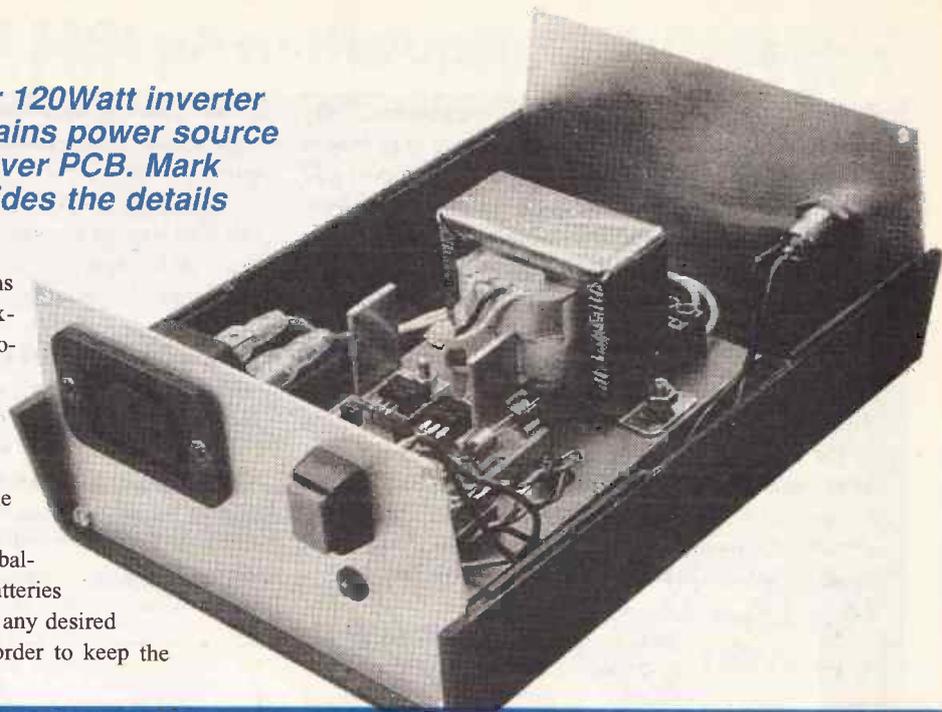Given a suitably large bank balance and an adequate stock of batteries it is possible to power virtually any desired load from an inverter, but in order to keep the



20/50/100Watt Mains

proportions within reason the load should be limited. As an example a 3kW load (about the maximum which can be safely run from a 13 amp socket outlet) would require an input current to the inverter of around 300 amps from a 12 volt battery, discharging a typical 60 ampere-hour car battery in about five minutes.

A more acceptable load limit for our typical car battery would be around 500 Watts, but this would still drain it in under one hour, which may be quite acceptable if the load is an intermittent one such as an electric drill or similar small power tool. Finding a suitable transformer ex-stock generally poses a problem with such a large inverter and added to that is the cost of suitable power transistors.

The smaller inverters, having an output of 100 Watts or less, are a much better proposition for the home constructor;

all the components being readily available at very low cost.

The circuit described in this article is designed to be used with equipment having a power requirement of less than 20 Watts in the first place. By simple substitution of heavier power components the output of this design may easily be increased to 50 Watts, this is described in detail later. If a little more work and expense can be tolerated a load capability exceeding 100 Watts may be achieved, as will be explained at the end of this article!

Generating AC

There are many ways of generating the AC required for an inverter, some of which are usable only in very small applications, others require expensive or difficult to obtain parts.

One obvious choice for generating the required timing

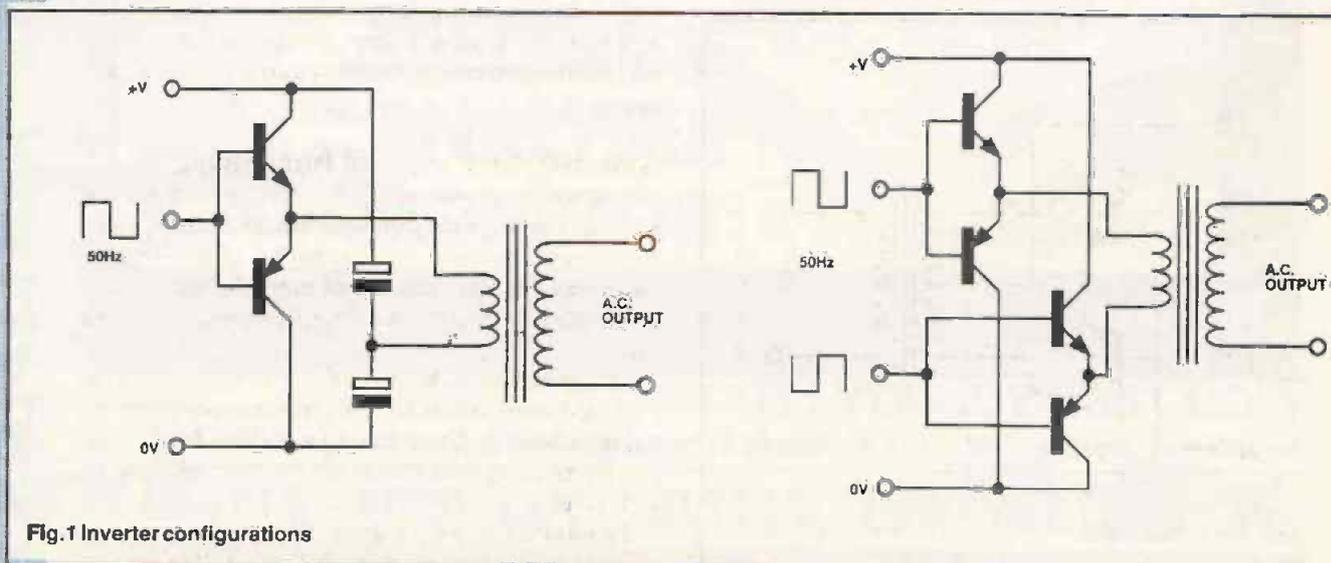


Fig.1 Inverter configurations

signals for the switching transistors is the ubiquitous 555 timer IC in its astable mode, which would have to be used in a single-ended or half-bridge configuration. This would result in quite a simple circuit, but it does pose two major problems; the worst of which is the low RMS output that is never able to exceed half the DC supply voltage. With a 12 volt supply the output is unlikely to be much better than about 4.5 Volts after transistor losses, etc. Also, the mark-space ratio of the signal from an unmodified 555 circuit will always be greater than the ideal 1:1 and consequently will not provide the best waveform for an inverter.

The two electrolytic capacitors in the half-bridge configuration of Figure 1a would need to have very large values for operation at a frequency as low as 50Hz if a practical amount of power is to be delivered to the load. The resulting design would work out much more expensive than is necessary.

A full bridge configuration, as in Figure 1b has a greatly improved output and does not require expensive electrolytic

Inverter

capacitors and could be used to good effect with a 12 Volt supply. It does, however, require twice as many power transistors as the half-bridge and a more complex timebase circuit, which is little advantage in this particular application.

There is a third configuration shown in Figure 1c, which at first glance appears to overcome all of the problems associated with the first two circuits, but not without introducing a couple of minor ones of its own.

The power transistors used in the bi-phase, or push-pull circuit, of Figure 1c require a V_{ce} rating in excess of twice the peak supply voltage which, with a high DC input voltage, can mean costly or difficult to obtain components. The inverter described in this article runs from a nominal 12 Volt supply and can use ordinary low voltage power transistors which are readily available and inexpensive. This configuration re-

quires complementary timing signals of equal mark-space ratio and obviously cannot be used with a standard 555 timebase.

Fortunately, most CMOS and TTL oscillators have complementary outputs and are ideal for this type of application. The CMOS option is chosen here for its additional advantage of wide supply voltage tolerance.

Printed Circuit Board Assembly

The majority of the components are assembled onto the single-sided glass-fibre printed circuit board, the component overlay for which is provided in Figure 4.

The easiest and safest method of assembly is to fit the small passive components and the socket for IC1 first, checking positioning and orientation before soldering. The three rectifiers, D1, D3 and D4 should be fitted next followed by transistors Q1 and Q2.

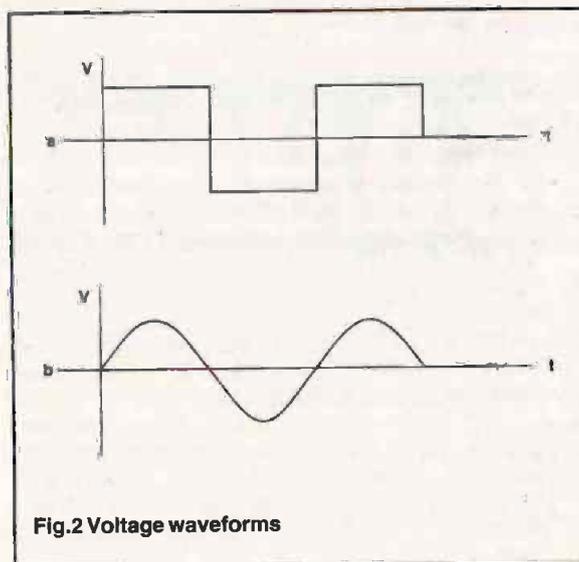


Fig.2 Voltage waveforms

The power transistors, Q3 and Q4 need fitting with small heatsinks which may conveniently be made from small pieces of 16swg (1.6mm) aluminium. If separate heatsinks are used then no isolating kits are needed, simply apply a small quantity of heatsink compound to the metal mounting tab of each transistor and bolt it to its respective heatsink, ensuring that the two cannot touch.


The fuseholder and preset, RV1 may be fitted next. If user adjustment of the output frequency is desired then an external potentiometer may be fitted as described under Modifications.

Assembly To Case And Interwiring

If a two part plastic case with aluminium front and rear panels is used as in the prototype then the PCB and transformer may be mounted in the bottom half of the case using countersunk machine screws and nuts. Use spacers or a couple of nuts to stand the PCB clear of the lower panel of the case.

Drill the mounting hole for SK1 in the rear panel of the case and de-burr it before fitting the miniature power connector. If the panel mounting option for RV1 has been chosen then the mounting holes for this will also need drilling in the back panel.

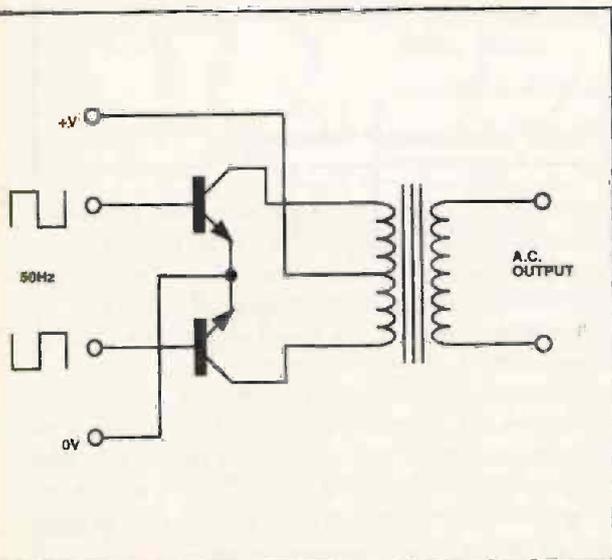Prepare the front panel to accept the IEC 6 Amp socket (if used), S1 and D1 in accordance with Figure 5. The cutout for



Setting Up and Testing

A 12 volt DC source capable of providing at least 2 amps (e.g. car battery) and a 4R7 2.5W wirewound resistor are the only items essential for testing the inverter. An analogue multimeter, although not essential, would be helpful particularly if fault finding becomes necessary.

Connect the 4R7 resistor in series with the inverter and battery and measure the output voltage of the inverter, which should be in excess of 200 volts. Allow it to run for a while and check that the power transistors do not get warm, switching it off immediately at any sign of a problem.

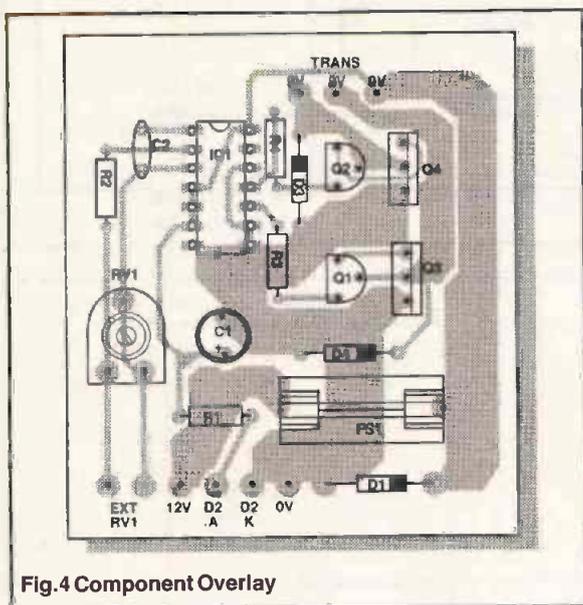


Fig. 4 Component Overlay

If all is well at this stage disconnect the 4R7 resistor, reconnect the unit to the power source and measure the open circuit output voltage, which should be around 300 to 340 volts. Apply a small load, such as a 15 Watt soldering iron and check that the output voltage does not fall below 240 volts.

To set the output frequency connect a digital frequency meter between pin 10 of IC1 and 0 volts and adjust RV1 until the desired frequency is obtained, normally 50Hz or 60Hz.

If no frequency meter is available an oscilloscope may alternatively be used to set the period of the waveform to

20ms for 50Hz or approximately 17ms for 60Hz.

The above two methods of setting the frequency require access to some fairly expensive test equipment, but with a little ingenuity this may be avoided. A high impedance loudspeaker connected between Q1 collector and the positive supply rail will produce an audible note which may be compared with any accurately known 50Hz or 60Hz tone (e.g. a speaker connected across the output of a low voltage transformer plugged into the normal household mains).

If the frequency is unimportant set RV1 to give the highest output frequency as this will also produce the greatest efficiency and output voltage. The two higher power versions of this inverter are tested in a manner similar to that outlined above, with the following differences; a higher current supply and suitably larger loads are required.

Fault Finding

This circuit should prevent no serious problems if assembled on the cover PCB as shown. Solder bridges across adjacent tracks on the board are the most likely problem.

Check the fuse first as this may have failed if the unit was incorrectly connected to the battery. If this is the case the reverse polarity protection diode may have failed to a short circuit and will also need replacing.

If the fuse fails a second time with the battery correctly connected check the orientation of all the diodes and replace any incorrectly fitted ones with new ones.

It is possible that the secondaries (used here as primaries) of the transformer have been connected in opposition, thus presenting a low impedance to the driver transistors. Check for this by removing the transformer from the circuit and connecting it to the mains in the normal manner. Measure its output across the ends of the centre tapped winding, which should produce around 18 to 20 volts AC. A reading of zero indicates that the connections to one of the windings have been reversed and will need swapping around.

Modifications

An external potentiometer may be fitted to the inverter to allow user adjustment of the output frequency and is connected as shown in Figure 7. The on-board preset shown in Figure 2 is then not needed and should be omitted if this modification is carried out.

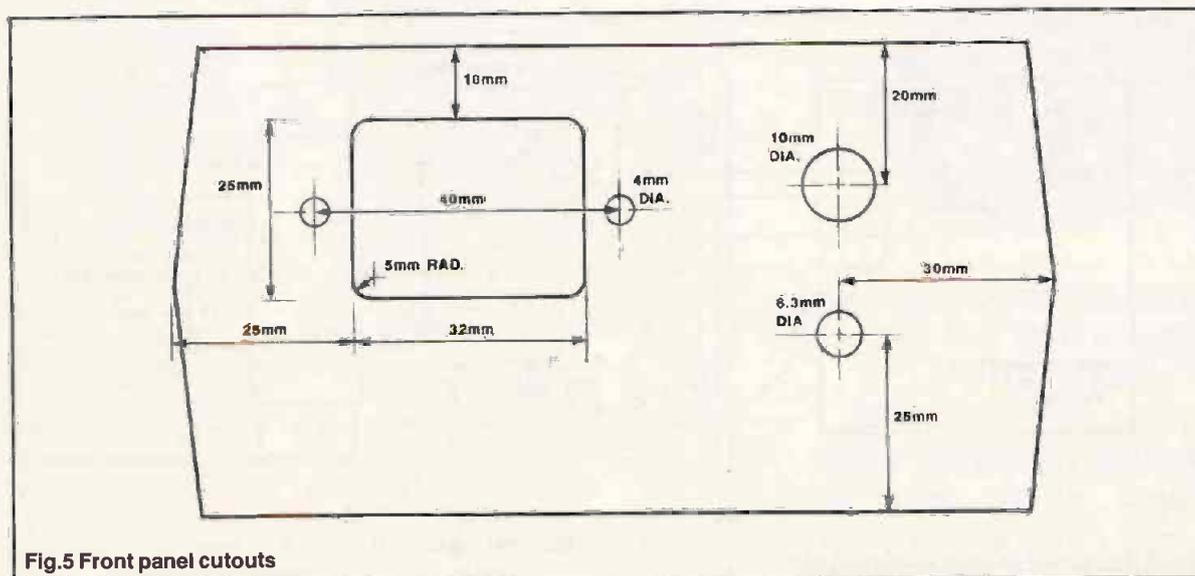


Fig. 5 Front panel cutouts

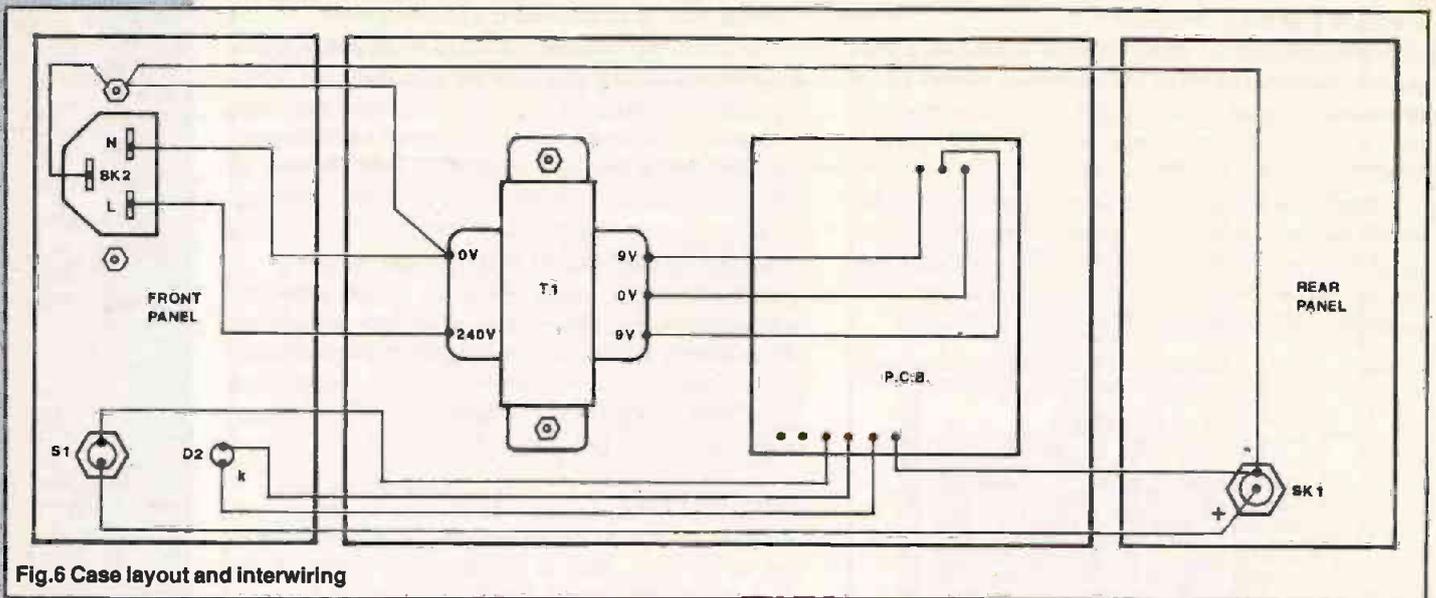


Fig. 6 Case layout and interwiring

For an increased output power of up to 50 Watts replace Q3 and Q4 with TIP41 devices, uprate T1 to 50VA and FS1 to 3 or 4 amps. Fit a larger heatsink to the power transistors, using isolating kits and heatsink compound.

For adequate reverse polarity protection D1 will need uprating to at least 6 Amps, otherwise it will have to be replaced each time incorrect battery connections are made and it will fail to a short circuit. The large areas of copper on the PCB which carry the full input current to the inverter, would benefit from heavy tinning if continuous use at high powers is expected. All interwiring on the low voltage side should also be suitably uprated to cope with higher input currents of upto 5 Amps at full load.

For maximum output power the TIP power transistors may be replaced with TO3 packaged power darlingtonts mounted off-board on a large heatsink, having a thermal resistance of less than 2°C/W. MJ4033 devices, having a current rating of 16 amps, may be used for Q3 and Q4 and should be fitted to the heatsink using isolating kits and heatsink compound. Connection to the PCB and transformer should be in accordance with Figure 8, using heavy connecting wire for all high current paths, indicated by the thicker lines in the drawing.

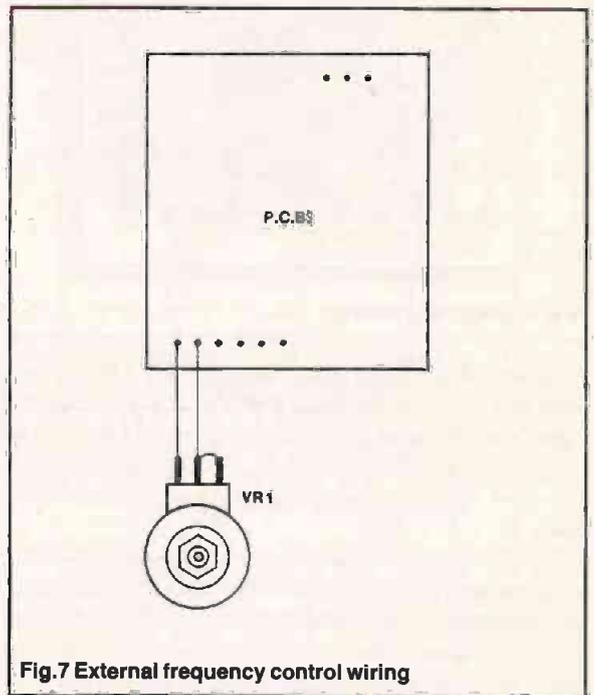


Fig. 7 External frequency control wiring

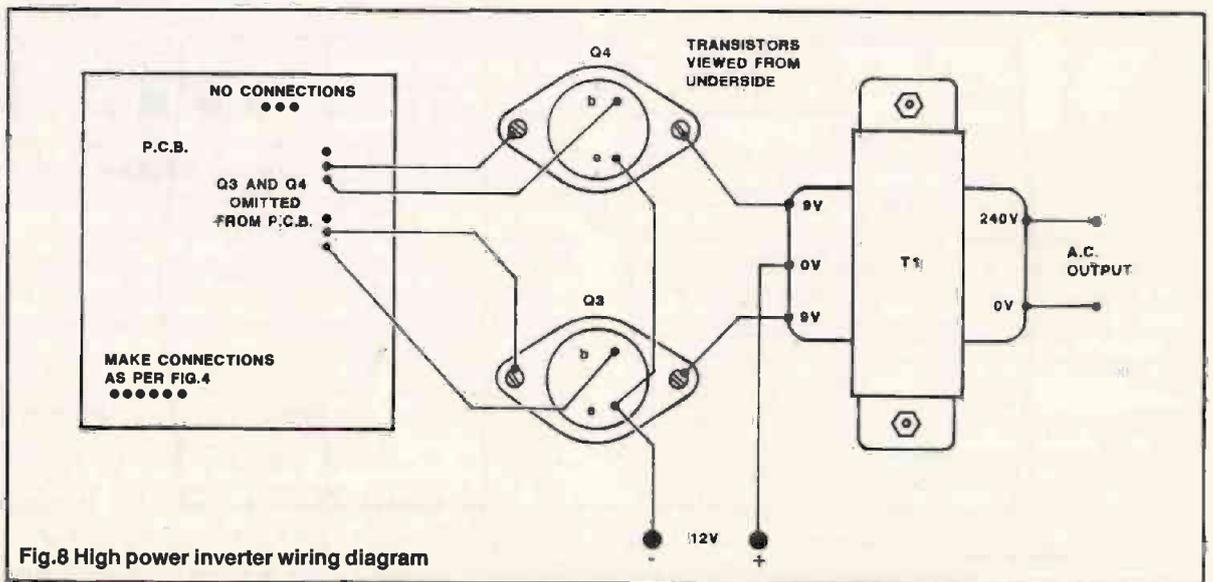


Fig. 8 High power inverter wiring diagram

For a full 120 Watts rating a toroidal type transformer is to be recommended for its lower magnetizing current requirement, which is reflected in the inverter's lower no-load current and considerably greater part load efficiency. As an

added bonus a toroidal device of this rating is very much cheaper than a conventional laminated transformer! A full load efficiency of around 80% can be expected.

PARTS LIST

RESISTORS (All 0.25W 5% Carbon Film)

R1	680
R2	330k
R3	2k2
R4	2k2
RV1	220k Sub-min Horiz Preset

CAPACITORS

C1	100µ 25V Radial Elec
C2	4n7 Polyester, 5mm Pitch

SEMICONDUCTORS

D1	1N4001 (uprate accordingly for 50/120W versions)
D2	5mm Green LED
D3,D4	1N4002 (2 off)
Q1,Q2	BC184L (2 off)
Q3,Q4	TIP31 (2 off for 20W)
	TIP41 (2 off for 50W)
	MJ4033 (2 off for 120W)
IC1	4047B

MISCELLANEOUS

T1	Mains Transformer	
	9-0-9V 20VA Rating	(20W)
	50VA Rating	(50W)
	120VA Toroidal	(120W)

S1	Push to Make Switch	(20W)
	5A Toggle Switch	(50W)
	16A Rocker Switch	(120W)
FS1	1.5A 20mm Quick Blow	(20W)
	3.15A 20mm Quick Blow	(50W)
	10A 1.25"	(120W)

PCB Mounting Fuseholder for FS1
(Panel Mounting Type for 120VA Version)
Large Crocodile Clips or Cigar Lighter Plug
Panel Mounting 6A IEC Socket Outlet and Plug to Suit
Panel Mounting DC Power Connector and Cable Mounting Plug
Ventilated Enclosure to Suit
Wire, Solder Tags, Crimp Terminals, Screws, etc.

BUYLINES

Ventilated enclosure is TEK K22 from West Hyde (Tel: 0453 731831) All other components are standard parts and were supplied by J.P.G. Electronics (Tel: 0246 211202), who can also supply a case if required.

HALCYON ELECTRONICS

Test equipment, video monitors, amateur radio gear, printers, power supplies, communications, disk drives, multimeters, oscilloscopes, scientific instruments, connectors, component bridges, frequency counters, signal generators, computers.

WANDEL/GOLTERMANN SPM-2 LEVEL METER	£169	'ANTIQUE' TEST EQUIPT, VARIOUS	POA
WANDEL/GOLTERMANN SPM-3 LEVEL METER	£189	COMMUNICATIONS RECEIVERS, VARIOUS	POA
WANDEL/GOLTERMANN PS-3 SIGNAL GEN	£169	200W U.V. SOURCE WITH TIMER	£85
ADRET 470A AM/FM SIG GEN 1-1120MHZ	£1995	1920's WIRELESS, REED & HORN SPKRS	POA
FARNELL FG1 FUNC GEN 2-2.2MHZ	£129	McMURDO SILVER CORD, 1 ONLY	£49
MARCONI TF2304 AM/FM MOD METER PRTBLE	£195	PERISCOPES MILITARY No 43 Mk. 3	£19
RACAL 9059 F/CTR 560MHZ MAINS/BATT	£145	LCR MARCONI TF1313A 0 1%	£95
19" RACK, 20U, 31" DEEP	£125	LCR MARCONI TF2701 IN SITU	£125
GOULD OS3300B 50MHz 2 TRACE DEL T/B	£269	LCR MARCONI TF868B	£69
TEK 453 50MHZ DUAL TRACE DEL T/B	£249	LCR COMPONENT COMPARATOR AVO CZ457/S	£75
TEK 465 100MHZ DUAL TRACE DEL T/B	£450	WAYNE KERR B221 B321 BRIDGES	EA539
SCOPEX 4D25 25MHZ DUAL TRACE	£169	HP1901A -05A -08A -17A 25MHz PULSE GEN	£125
BECKMAN 9020 20MHZ DUAL TRACE	£249	EKCO MARINER U834 L.M & 7S B'CAST RECR	£75
DATA PRECISION 6000 WITH 611 PLUG-IN AND 681 DISK DRIVE UNIT.		SCR 578B GIBSON GIRL EMERGENCY XMITTER	£75
GOULD OS3000A 40MHZ 2 TRACE, DEL T/B	£3995	AMF/VENNER 625/2 SIG GEN 1Hz-1MHz SIN/SQ	£89
HAMEG 203-S 20MHZ, 2 TRACE, COMP TESTER	£249	LEVELL TG152 3Hz-300KHz OSC SIN/SQ	£85
HITACHI VC 6015 10MHz DIGITAL STORAGE H.P. 1340A X-Y DISPLAYS.	£395	LEVELL TM88 MICRO V-METER 450MHZ	£95
LEADER LBO-9C ALIGNMENT SCOPE	£39	LEVELL TM88 MICRO V-METER 3MHZ	£85
TEK 514N 100KHz SPECT ANAL WITH 5110 M/F, 2x 5A18N, 5B10N TIME BASE	£195	TU8B/TU8B TUNER UNITS BRAND NEW	£29/£39
TELEQUIPMENT D75, 50MHz 2 TRACE DEL T/B	£750	OERTLING V20 SINGLE PAN BALANCES 200GM	£95
TEKTRONIX 7403N, DF1, 7D01 LOGIC ANAL	£225	SAGE 2-WAY CO-AX SWITCH SAN 2120 N CONNS	£95
TEK 545B, 585, 535A, 541A etc	£495	UDI 2026 SONAR SCANNER, SURFACE UNIT	£895
TEK 545/585 SERIES PLUG-INS	From £49	B&K 1013 BFO & 2305 LEVEL RECORDER	£195
HP 3490A DMM AC/DC/V OHMS 6 DIGIT	£125	UPA CAVI DERM CD8 P.T.H. TESTER	£750
XFORMERS SEC 30-0-30V 20A, UNIV PRIS, C-CORE	£20	MARCONI MARINE KESTREL 3	POA
WHOUSE 1/4HP REVBLE MOTORS 220V 1KRPM	£25	ANALYTICAL BALANCES WITH WEIGHTS	£69
CONSTANT VOLTAGE TRANSFS 150VA-2KV	POA	DECADE R/C/V/ BOXES	From £15
MARCONI TF2331 DISTN FACTOR METER	£175	KAYE DEE PNEUMO UV EXP UNIT 390x260mm	£175
BBC-B & MASTER COMPUTERS	From £99	VACUUM PUMPS TYP 100MBAR (28L/MIN)	£95
MARCONI TF2300 FM/AM MODULATION METER	£195	CALIBRATION STANDARDS C/V/L/R	POA
TEKTRONIX 834 PROG DATA COMMS TESTER	£395	COSSOR CRM533A VHF NAV/COM RF SIG GEN }	£750
VARIABLE OUTPUT PSUs HV & LV	From £29	COSSOR CRM511 ILS/VOR AUDIO SIG GEN }	£750
TEKTRONIX 520 521A PAL V/SCOPE	From £475	TOPAZ 91007-11 7.5KVA 120/240-120/240 ISOL	£249
		KINGSHILL NS1540 15V 40A PSU CASED	£295
		HP 626A, 628A, SIG GENs LAST FEW	£35 ea
		SIGNAL GENERATORS AF TO 21GHz	From £15

LIST AVAILABLE, BUT 1000's OF UNLISTED BARGAINS FOR CALLERS ALL PRICES EXC. OF P&P AND VAT
QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED.

423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383

PLASTIC BOXES



A RANGE OF SMALL PLASTIC BOXES,
CASES AND POTTING BOXES AVAILABLE
IN ANY QUANTITY.


SEND FOR FREE CATALOGUE

SLM (MODEL) ENGINEERS
CHILTERN ROAD, PRESTBURY,
CHELTENHAM, GLOS GL52 5JQ
FAX: 0242 226288




AMAZING ADAPTER BUG

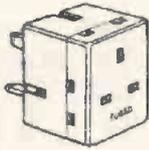Built into a standard 13A adapter, plugs into any 13A socket and transmits to a normal FM radio. Directly powered from the mains the unit will transmit conversations etc indefinitely! Price is £26.00 ref M26P1



WALKIE TALKIES 1 MILE RANGE

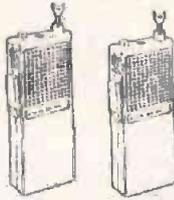Pair of small pocket sized walkie talkies complete with cases etc. They will operate (subject to buildings etc) up to 1 mile apart. 2 PP3 9v batteries required. £30.00 ref M30P1




CAR STEREO AND SPEAKERS

Complete system comprising of stereo cassette player, stereo FM radio plus AM band, Pair of good quality speakers all for just £19.00 ref M19P1



AMBER MONITORS

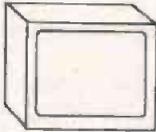12" high res screen 12v 1A supply needed. Hercules/TTL input ie sep HOR and VER sync plus video required. Brand new and housed in an off white plastic case. £22.00 ref M22P1.



12V SOLAR PANEL

Ideal for trickle charging car batteries etc. Panel is made from amorphous silicon, is waterproof and comes with fly leads. Size is 30cm x 30cm x 4mm. £15.00 ref M15P1. Other sizes stocked



C64 TAPE STREAMER


Originally made for the Commodore 64 Computer but may be adaptable for other machines. Unit is supplied with its own operating system, and two tapes. Approx 20 times faster than normal tape systems! £25.00 ref M25P1.



Extra tapes are available at £4.00 each ref M4P1 or 10 for £25.00 ref M25P2.

PC POWER SUPPLIES

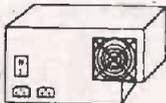
Brand new units made by Aztec either 110v or 240v input giving 5v at 15A, 12v at 5A, -5v at .3A and -12 at .5A. Fully cased with on/off switch and built in fan. £15.00 ref M15P2 Also available is a 200 watt version at £22.00 ref M22P2. Both types have standard PC fly leads.



40 PAGE CATALOGUE AVAILABLE CONTAINING OVER 1,500 SIMILAR PRODUCTS FREE ON REQUEST!

EMERGENCY LIGHTING SYSTEM

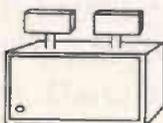Complete system give sup to 3 hours light from an integral 10AH sealed lead acid battery. The battery is kept fully charged by the mains, as soon as the mains fails the two powerful lamps are switched on and remain on until power is restored. Maintenance free. £19.00 complete with battery. ref M19P2



AMSTRAD 464 COMPUTERS

Customer returned units complete with a monitor and circuit diagrams. These units are generally not working and are not returnable. Price is £35.00 ref M35P1.



AMSTRAD 6128 COMPUTERS

Customer returned units complete with a circuit diagram and built in 3" disc drive. These units are generally not working and are not returnable. Price is £29.00 ref M29P1.




CORDLESS MICROPHONE

Small hand held battery operated microphone that transmits to a standard FM radio, good range. Our price £15.00 ref M15P3.



VIDEO SENDER

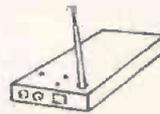Transmits video pictures from a video recorder or cam corder to any television in the house. Can also be used to transmit from cam corder to video recorder, no more trailing wires! £15.00 (ex psu) ref M15P4 £20.00 (inc psu) ref M20P1.



BUILT BUG

Built and tested superior FM bug 100m range, fits in match box all you need is a 9v battery and an ordinary FM radio! £14.00 ref M14P1.




ULTRASONIC ALARM SYSTEM

Complete alarm system that comprises a detector that simply plugs into a 13A socket in the area you wish to protect and a receiver which plugs into a 13A socket where you wish the alarm to sound. You could put one in the garage and one indoors or perhaps protect your neighbours house etc. Fully adjustable sensitivity. £25.00 for complete system ref M25P3.




TALKING TELEPHONE COIN BOXES

Phone bill too high? fit one of these and save. Fully programmable for different call rates, chargebands, time of day etc. accepts 10p, 50p and £1.00 coins. Phone box actually speaks to you with built in voice synthesiser. Wall or desk mounting. Two types available 1 with built in lock at £29.00 ref M29P2 the other with no lock but easily adaptable is just £23.00 ref M23P1. Unit takes 4 C cells and is used in conjunction with an ordinary phone. Supplied with full instructions, BT approved.

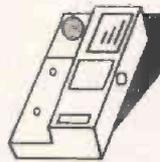


STEAM ENGINES

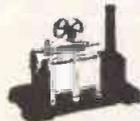Ever wanted one? brand new units made by the famous Mamod company complete with fuel, burner etc £30.00 ref M30P1. Other models stocked, including traction engine at £59.



PC CASES

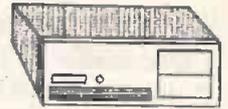Full size off white metal cases ideal for building your own PC four drive bays, attractive plastic front panel. £24.00 ref M24P1.



VIEWDATA SYSTEMS

Made by Tandata these contain every thing you need to start dialling into databases and bulletin boards such as Prestel etc just plugs into a standard tv or monitor. Complete with modem, infrared remote controlled keyboard and console. £20.00 ref M20P2

SPECTRUM +2 COMPUTERS

Refurbished popular computer with built in cassette deck and 128K of memory £32.00 each ref M32P1 PSU £15.00 ref M15P4



We also have some requiring attention at £19.00 (non returnable) ref M19P3


SPECTRUM +3 COMPUTERS

Refurbished popular computer with built in disc drive and 128k of memory £45.00 each ref M45P1 PSU £15.00 ref M15P5. We also have some requiring attention at £25.00 (non returnable) ref M25P4.



EPROMS

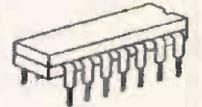Clean erased eeproms at bargain prices! 27C64 pack of 10 for £7 ref M7P1, 27C256 pack of 10 for £9 ref M9P1, 27C512 pack of 10 for £10 ref M10P1.



WINDUP SOLAR POWERED RADIO

Compact unit with built in hand charger and solar panel just a few turns of the handle powers the radio for some time! Our price is just £14.00 ref M14P2



BUGGING TAPE RECORDER

Contains voice activated switch so only actual conversations are recorded! takes a standard audio cassette and uses AA batteries. £20.00 ref M20P3



TALKING ALARM CLOCK

Wakes you up by telling you the time also speaks the time at the push of a button! Battery operated £14.00 ref M14P3.



BROADBAND RADIO RECEIVER

Covers VHF 54-176 mhz (CB, air FM, TV, PB, WB etc etc) hand held unit with squelch control and carrying strap £15.00 ref M15P6 Superb value.



12 BAND WORLD COMMUNICATIONS RECEIVER

Mains or battery operated covers 9 short wave bands plus FM, LW and AM bands. Exceptional value at £19. ref M19P4



SINCLAIR C5 MOTORS

12v 29A (full load) complete with 4 to 1 reduction gearbox giving 800 rpm output. Motor measures 8" x 4" with toothed pulley output. £40 ref M40P1. We also stock 13" wheels with tyres at £6 each ref M6P1, 16" at £6.00 ref M6P2 and an electronic speed controller kit at £17 ref M17P1.

BULL ELECTRICAL
250 PORTLAND ROAD HOVE SUSSEX
BN3 5QT TELEPHONE 0273 203500
MAIL ORDER TERMS: CASH PO OR CHEQUE
WITH ORDER PLUS £3.00 POST PLUS VAT.
PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY



NEXT DAY DELIVERY £8.00
SHOP OPEN MON-SAT
FAX 0273 23077



NOTE: SOME OF OUR PRODUCTS MAY NOT BE LICENSABLE FOR UK

This month, Mike Meechan presents some circuits which are guaranteed to raise the hackles and boil the blood of the anti-tone control brigade.

AutoMate Anniversary Mixer

Although some of our readership has intimated as much, and despite some scurrilous rumours to the contrary, I have yet to secure a deal with Steven Spielberg as regards a blockbuster movie of the Anniversary AutoMate - with screenplay by Stephen King and a musical score by Andrew Lloyd Webber - but T-shirt sales are doing well, book rights have been agreed upon and the album will soon be released! Anyway, enough of the frivolity and wishful thinking and down to business.

The Equalizer

No, not a guest appearance in this column by Edward Woodward, scourge of wrong-doers. At long last, we can now present the equalization circuitry of the AutoMate and I hope that all will agree that it's been worth the wait. At this late (EQ) stage in the game, it might be worthwhile pointing out that the AutoMate EQ is a true parametric equalizer. The name parametric and sweep equalizer have, in many ways, become synonymous. This is a quite false axiom since a sweep equalizer offers control only of centre frequency and boost/cut, not the other parameter necessary - that of Q control - which yields the TRUE parametric equalizer. It is as well to point this out here and now - like can therefore be compared with like in the case of the AutoMate and any potential commercial competitors.

Future topics for exploration and vivisection - in the style of previous sections - will include dynamics and switching (in next month's issue), monitoring, panning, mixing and finally AutoMation. We shall then start to publish some overlays for the mono mic/line channel strip before briskly moving on to other modules in the series including the stereo line/RIAA channel strip, group module, master module etc.

For the present, we'll content ourselves with looking at the comprehensive equalization circuitry of the AutoMate. Referring to the circuit diagrams of Figures 1 and 2, we should be able to see - after three months of intensive study of EQ and filter networks - that the featured circuits are a veritable smorgasbord of different types. This was flying somewhat in the face of popular fashion where conventional designs - for the parametric EQ at any rate - follow either one school of thought, the constant all-pass phase-shifting types (CAPS) invoked as variable and tunable admittances to ground or the other, state-variable method of implementation. I have used both types where I thought that the performance of one type in a particular aspect was superior to the performance of the other type in that same aspect. Sometimes, a slightly maverick approach to design is to be commended....


Figure 1 shows the High Pass Filter section. This is an outwardly conventional equal-component-type Sallen and Key HPF. Tacked onto the end of it is a reasonably meaty push-pull transistor stage which boosts current-sourcing capability by a good factor and means that long lines or jackfields can be driven with considerable ease. Feedback is therefore derived from the output of the two transistors and not from the op-amp. Referring to the discussion of some

months previous, we now know that the Sallen and Key type of filter has reasonable responses in all of the important areas. Also, with the equal component type, the methods used to produce better out-of-band roll-off ie a Butterworth response means that 4dB of gain is introduced. This was why the previous Line Trim stage was made to sustain an overall 4dB loss in the 0dB setting. There is thus no overall gain (or loss) through the system with all level controls set for 0dB.

Fazed by Phase

In the second stage of the EQ, each of the true parametric sections is able to be tuned over a 20:1 frequency range, from 50Hz to 1kHz at the lower end - I've called this section, somewhat misleadingly, low -mid - and from 1kHz to 20kHz at the upper end. On the face of it, there is no direct overlap of frequencies. This is important since both of the state-variable sections share a common Baxandall-style summing stage. The one caveat, however, (with both filters able to be tuned to the same frequency) is that if both sections *are* tuned to a particular crossover frequency, or a very similar one for that matter, the available cut or boost ratio is altered - you can't simply just add 15dB of boost at 1kHz in one section and also boost it by the same amount in the other! This is because the two stages are summed, not multiplied so the maximum possible (if the op-amp can do so without clipping) is 21dB. The use of both the gyrated admittances and state variable in the same package meant that the EQ stage had an unattractive overall phase inversion. Again, there has been much subjective argument about the need to maintain faithfully the integrity of the audio phase, with an overall in-phase response from input to output - sounds better, old boy. I can't comment authoritatively one way or the other but it is interesting to note that many of the most widely-used Japanese professional digital audio processors did, in fact, invert the signal phase of the signal. It is claimed that incorrect phase results in imaging that is perceived psychoacoustically as 'flat' and which sounds as if it emanates from a point near or behind the loudspeaker. Absolute phase, on the other hand, cause the image to tend to surround the listener and the depth and dimensional character of the mix are enhanced greatly. It makes one wonder just what absolute phase reference there is to believe in in many recordings. Phase is of particular importance with microphones, especially those arranged to capture a stereo source (where phase-reversed mics will cause images to wander) or where ambient as well as close-miking of the source is being done since mono will be affected, too, in this instance. Phase inversion can be used

8a

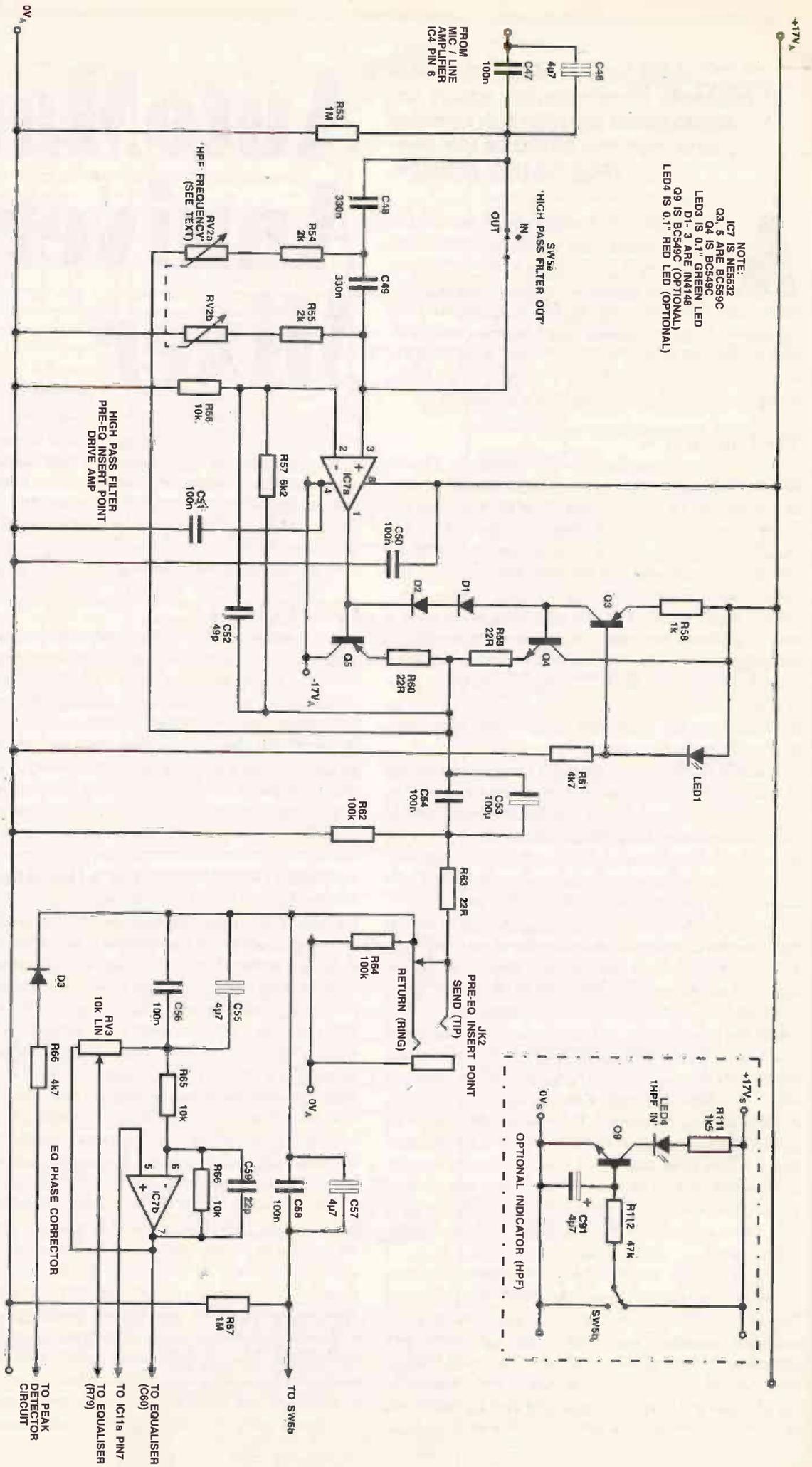

NOTE:
 IC7 IS NE5532
 Q3, 5 ARE BC559C
 Q4 IS BC549C
 LED3 IS 0.1" GREEN LED
 D1-3 ARE 1N4148
 Q9 IS BC549C (OPTIONAL)
 LED4 IS 0.1" RED LED (OPTIONAL)

Fig.1 AutoMate switchable high-pass filter

HOW IT WORKS

HIGH PASS FILTER AND EQ PHASE CORRECTION

The High Pass Filter utilizes an equal component second-order Sallen and Key type filter. This gives a 12dB/octave roll-off and a flattest amplitude response while the feedback necessary to create this response gives 4dB of gain. Faster roll-off for out-of-band signals has been compromised for a better in-band response.

The unity gain type, would, in any case, be difficult to tune, because of the non-similar values of R's and C's.

R54 and R55 and the associated part of RV2 set the turnover frequency of the filter. The pot may be omitted and replaced by two discrete resistors chosen from the values given in the attached table (Figure 7). Whatever the case, the filter turnover frequency can be varied from about 20 to 300 Hz. As already mentioned, the resistors may be supplemented with a dual gang 20k linear pot, thus allowing operator fully variable control of the turnover frequency. As mentioned in the general text, the control law, ideally, should be anti-log in nature so in practise, the linear pot gives a slightly cramped, though useable law.

SW5 switches the filter in and out of circuit. Conventionally, and if the filter caused the signal to sustain no overall loss or gain, ie a unity gain as opposed to equal-component value Sallen-Key, the switch would simply and wholly bypass all of the filter circuitry. This is advantageous in that the signal is passing through one less stage of amplification, which can only be good from a sonic point of view.

However, because the filter is a flattest amplitude type, and so gives 4dB of gain which has had to be assimilated into the overall level architecture, simple bypassing won't do and with the filter out of circuit, there must still be 4dB of frequency-insensitive -flat - gain. This is achieved by shunting out C48 and C49. DC paths around the switch are maintained during the switching operation and no clicks are evident on the output. The output of IC7a drives a reasonably hefty pair of line-driving transistors - Q4 and Q5 - in push-pull

configuration with Q3 behaving as a constant current source for these two. LED1 biases this transistor while overall feedback is provided from the node of R59 and R60 via R57. The C54/R62 combination AC couple and ground reference the output whilst R63 provides some protection against short-circuit or highly capacitive loads. C53 value was chosen so that there is no LF roll-off with the envisaged lowest load impedance of the FX unit - 600R - and the electrolytic is bypassed with non-polarized C54 to improve in-band response.

JK2 is the Channel Pre-EQ Insert point and comprises a 1/4" stereo jack socket with switched contacts. These are 'normalled' in the traditional way, providing an unbroken path for the signal unless a jackplug is inserted whereupon the signal travels out of the mixer through the 'tip' contacts. It then returns in processed form through the 'ring' contacts, with R64 providing a source impedance for any FX and ground-referencing the return path.

IC7b is the Insert Buffer/EQ Phase Corrector. Refer to Figure 4. With EQ inserted via SW6b, overall phase between the input of IC7b and the output of IC13b is unchanged. De-selecting the EQ takes the signal directly from the 'return' contacts of the jack to IC13.

One snag with the arrangement is the absence of the buffer when EQ is OUT but in practise this has proven not to be a problem with any FX units connected to the insert point. Again, each of the high-value polarized coupling capacitors have been bypassed.

LED 4 and associated components constitute an optional indicator operated by the second half of SW5's contacts and shows when the HPF is selected IN circuit. This is an important feature should the switch be part of RV2 since the pull on/pull-off operation needed to place the filter in circuit can be difficult to see at a glance when the control is buried amidst countless others. It can be omitted if so desired

creatively, too, to bring a vocalist to the front of the mix, for example, so that the listener is surrounded by vocals while the orchestra or backing instruments reside in the background. See Figure 3. We'll be looking more carefully at spatial positioning at a later stage.

From a purely practical point of view, absolute phase makes life easier for the designer if he knows that the output from each discrete stage should be in-phase with the input. This approach eradicates the need for individualism on particular cards or parts of the mixer - a killer in any modular system since they can then only be replaced by exactly the same type at a particular point. But this is to miss the main point. The problem of most concern here was that the signal was in-phase with the EQ bypassed and out-of-phase with the EQ in - a very unhappy state of affairs.

Consequently, I arranged for a compensatory phase reversal (transparent to the operator) to be introduced into the signal path whenever the EQ was placed in-circuit. The phase reverse amplifier (EQ absolute phase restorer) also serves as a Post-Insert Buffer Amplifier, although it can only be implemented as such when the EQ is in circuit. This is a slightly unorthodox arrangement and ideally, the buffer should have been present whether the EQ was in circuit or out. The original design configured this amplifier in an identical way to the one used in the phase switching arrangement of IC13a and associated components.

The amplifier became an inverter when EQ was IN and a follower when EQ was OUT. All was hunky-dory but for the clicks sometimes caused when switching EQ in and out of circuit (for purposes of comparison etc) with the fader open. It was thus abandoned. In any case, it makes for one less

detrimental amplification stage when EQ is switched out. Further details on this are given in the How It Works section. The signal path in each of the two conditions will be shown next month.

Taking the Law into One's Own Hands


There are some other rather quirky-but-nice design features. Again, I was completely stymied in my efforts to locate suppliers of anti-log pots so some cunning was required to bend the law of the frequency-setting pots from easily-available linear or log to the ideal anti-log law required.

It is important in any variable control - pot - that the available control is not cramped at the extremes of rotation. Figure 4 shows rotation laws for various pots when used, as is a common requirement, as frequency-determining controls. The use of star-delta transforms - as covered by A P Stevenson in an article in the January 1992 issue of ETI - facilitates powerful manipulation wherein networks of one type can be converted into the corresponding equivalents of the other type ie from star to delta or vice versa. We can thus approximate various different laws using standard pots and pull-up or pull-down resistors from the wiper to another terminal. See Figure 5. Just such an approach is used commercially in the quest for an financially-viable but also, from the oft-despised subjective point of view, aurally accurate, panpot control law. (We'll cover the pan-pot debate at a later point in the series). This 'law-faking' approach was used at four different points in the EQ - in each of the frequency determining controls for the four different sections.

I suppose that, as in the case of the Mic Gain-setting


FROM C58

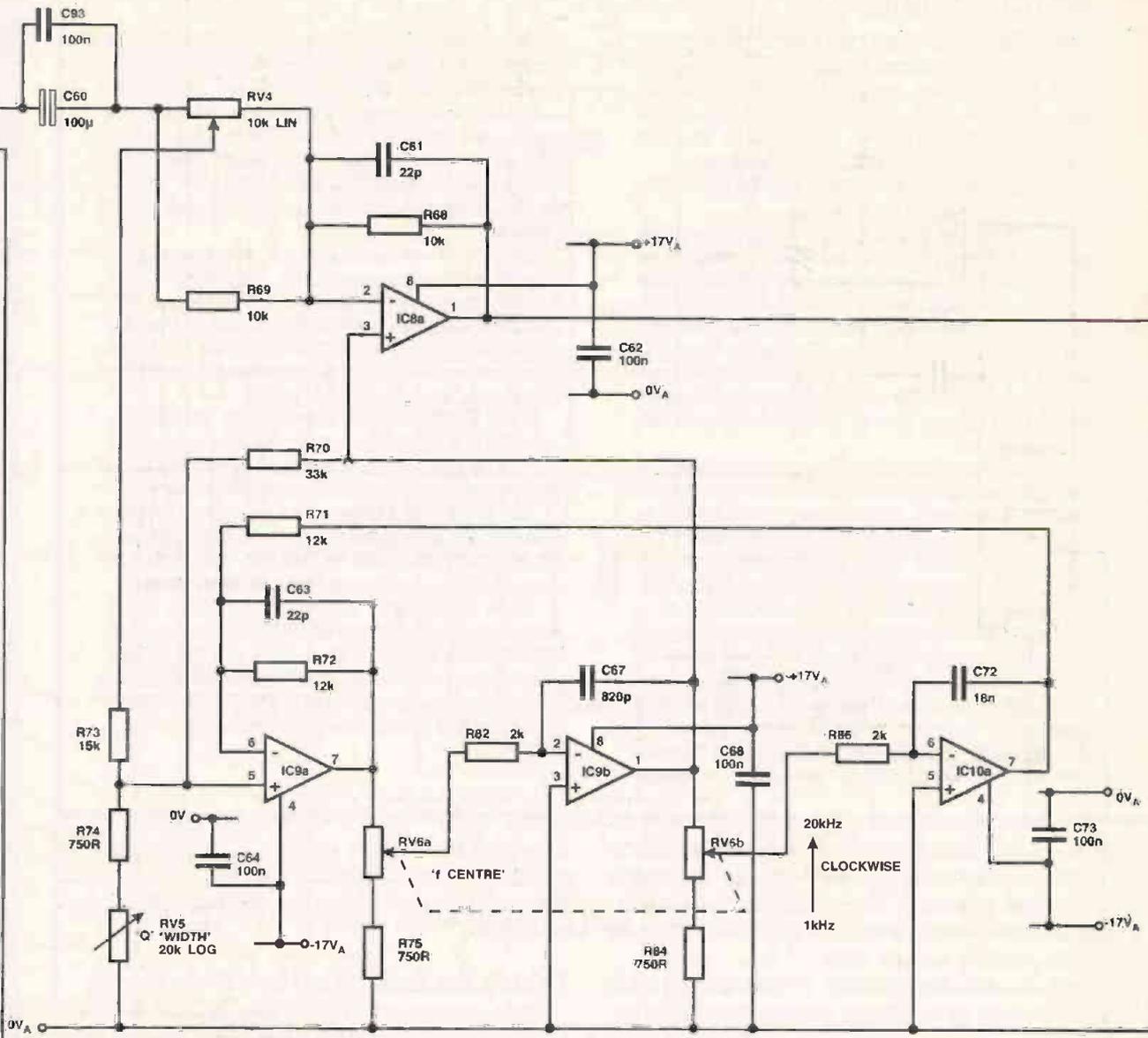FROM POST INSERT BUFFER AMP (IC7 PIN 7)
TO RV3 WIPER (FIGURE 1)






HI- MID EQUALISER

TO IC7b PIN 5


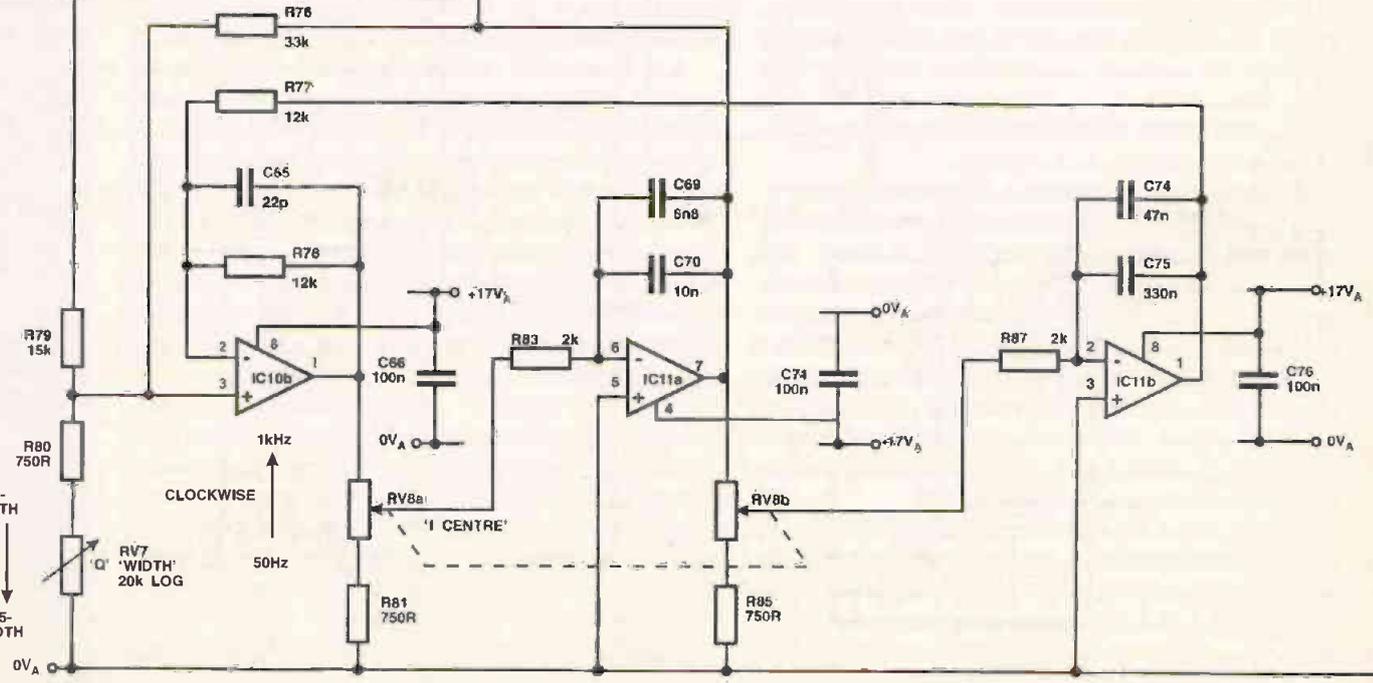


LO- MID EQUALISER

Fig.2 AutoMate 4-band equaliser

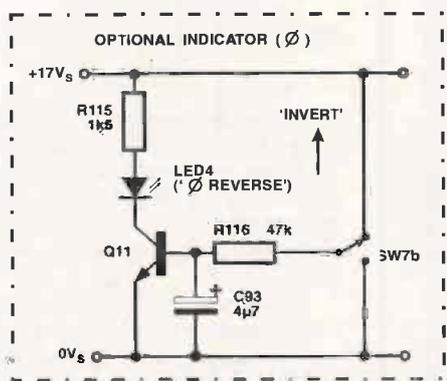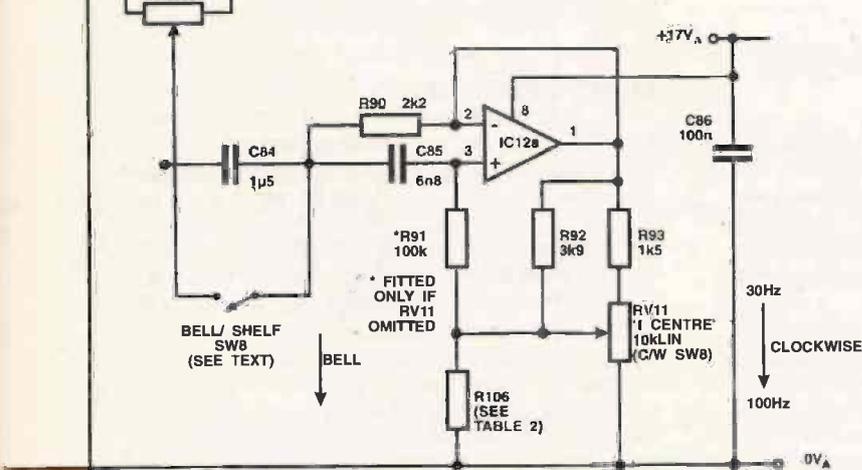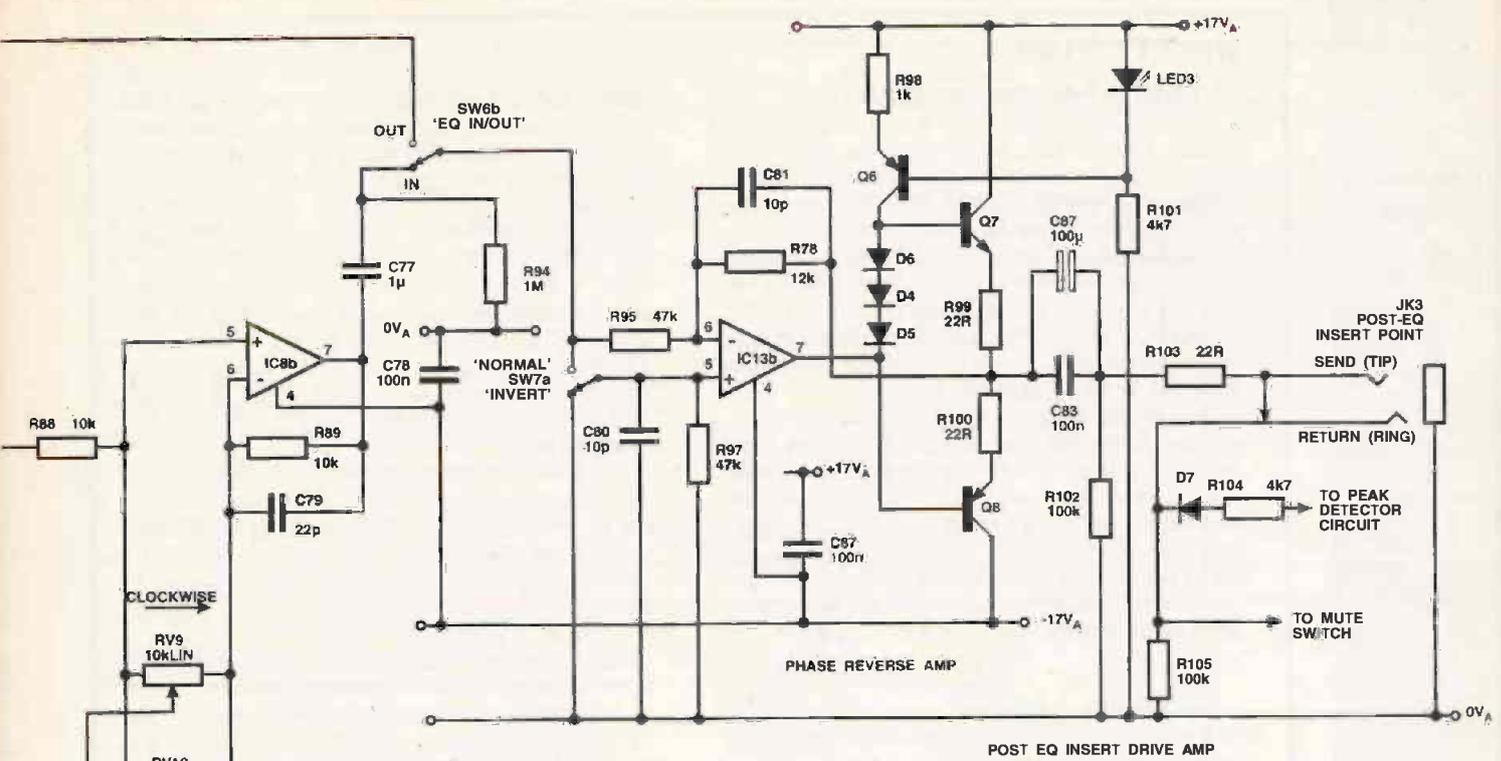

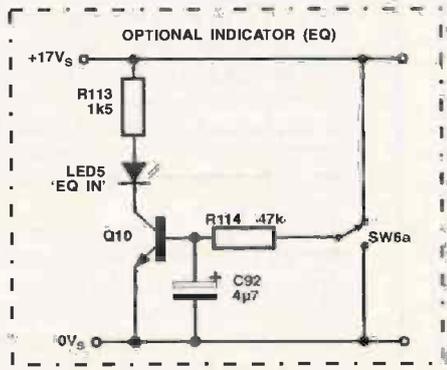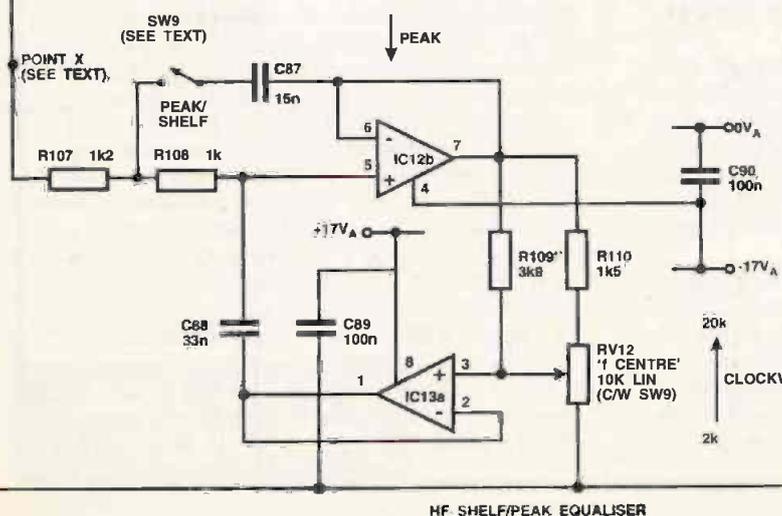NOTE: RV11 MAY BE OMITTED IN SOME VERSIONS. IN THESE CASES R92, 93 ARE ALSO OMITTED AND FILTER CENTRE FREQUENCY IS DETERMINED SOLELY BY R91 (VALUE CHOSEN FROM TABLE 2) AND R106.



NOTE:
 IC8 IS TL072
 IC9- 13 ARE NE5532
 Q6, 8 ARE BC559C
 Q7 IS BD549C
 D4- 6 ARE IN4148
 LED3 IS 0.1" GREEN LED
 Q10, 11 ARE BC549C (OPTIONAL)
 LED5, 6 ARE 0.1" RED LED (OPTIONAL)

HOW IT WORKS

AUTOMATE PARAMETRIC EQUALISER

The parametric section consists of two state-variable sections, identical in all respects but for the size of the frequency-determining capacitors. The state-variable has been discussed at length in previous parts of the article so we'll look only at those aspects of the design which set it apart from the bog-standard form. Only the high-mid equalizer as regards component numbering - will be investigated but as we've said, it is identical in electrical operation to the low-mid. Input signals are derived from the wiper of RV4 which is part of a conventional Baxandall-style ratiometric feedback/attenuation network. Resistor values are lower than is customary in this type of configuration to optimise noise performance.

From the wiper, the signal is injected into a reasonably conventional two-integrator loop state variable. The only quirks in the design which set it apart from other, more conventional types are all centred around the major frequency-determining components, RV6a and RV6b, R75, R82, R83 and R86, and C67 and C72. In straightforward textbook designs, both of the frequency-determining capacitors are kept identical in value. (It simplifies the calculations). Figure 9 will show a schematic diagram next month. Break frequency of the section can be determined quite simply from the equation:

$$f_{\text{centre}} = 1/2\pi C1R4$$

This is the simple expression and supposes that both C's are the same in value and that there is a single frequency-determining resistor per section. The full expression is as follows:

$$f_{\text{centre}} = 1/2\pi\sqrt{R6/R3C1R4C2R7}$$

With R3 equal to R6, the transfer function simplifies further to:

$$f_{\text{centre}} = 1/2\sqrt{1/R4C1R7C2}$$

In the AutoMate example, one of the capacitors is $\sqrt{22}$ times the value of the other ie scaled about the geometric mean value. From the equation, as in the simpler Sallen and Key types discussed some months ago, we can see the PRODUCT is important. So long as the product of the two calculates to be the same as the originally-needed pair of identical values of single capacitors, the break frequency remains the same.

In past issues, we have said circuits can be modified to realize LARGE Q values. Although it might seem strange now, it can be just as difficult realizing SMALL values with this manifestation of the state variable. This conventional state-variable with its single pot Q-adjust can't realize Q values much below 1. The devious business with the non-equal capacitors which was briefly outlined above becomes necessary. In fact, each capacitor has been removed from a middle value by a factor of $\sqrt{22}$, one being scaled up by a factor of $\sqrt{22}$ and the other scaled down although the product of the two remains constant. It is this product which determines the break frequency. Equal value capacitors mean that the lowest value of Q achievable is unity. We really want Q's down to values of 0.5 to 0.2 and these measures provide this range for us. Current through each of the integrating capacitors, C67 and C71, is shared non-equally. Around the integrator loop, R70 can be assumed to be the Q-determining component. Changing the current through this alters the Q value to around the required value of 0.5.

Values for the $f_{\text{resistor}}/f_{\text{capacitor}}$ have been chosen to give a 20:1 range, from 50Hz to 1kHz in one of the sections and from 1kHz to 20kHz in the other. As stated, the complete inavailability of anti-log pots to the hobbyist constructor prompted the use of a three resistor network to fake the anti-log law required. An anti-log control law yields the correct characteristic which should be one of resistance value being inversely proportional to frequency ie as resistance drops, filter break frequency increases.

So the frequency determining pot has an almost linear frequency change:percentage rotation characteristic which is good from an operational viewpoint. Figure 4 shows the effects of using three pots - linear, log and anti-log - for the control of frequency. Figure 5 shows the transmutation between star and delta networks, how the value of resistors in each network relate to one another and specifically how these values relate to our required law-bending exercise. These

resistor values have been chosen to compromise both good noise performance - values as low as possible but within the driving stage capability of the op-amp - whilst allowing the frequency determining capacitors to be of the polyester type rather than electrolytics etc. 10 μ caps become horribly expensive and bulky. RV5 is the Q-determining pot, with maximum Q - corresponding to 5 - when the pot is at its minimum value. Again, this control should have had an anti-log law so that as the control is turned clockwise, the Q value changes progressively and smoothly from a low to high value. Wiring a log pot the wrong way round yields a control where WIDTH is smoothly increased as the control is turned clockwise. SSL use this approach on their desks, so we are in good company! Its electrical effect upon the circuit is to attenuate the signal returned via R70 and so alter the Q.

The phase switcher is straightforward. In the inverting state, SW7 grounds the non-inverting input of IC13b and it behaves as an inverting amplifier of gain -1. Switching SW7 to the NORMAL position connects the signal input to the inverting and non-inverting input. Amplification through the IC is now 2 (non-inverting) plus -1 (inverting) so the overall gain is non-inverting. R97 and C80 prevent any oscillation or bursts of noise from the output as the switch contacts change over while each side of the switch has a DC path to earth to avoid clicks when EQ is switched in and out of circuit.

In addition, there is an insert point drive amp, comprised of Q6 - the constant current source - and Q7/Q8, the push-pull output stage. This is identical in operation to the line driving stage attached to the HPF op-amp output and reference is made to this.

LF AND HF EQUALISER

Both of these circuits could be termed 'unusual'. A gyrator - IC12a is used to synthesize an inductor to create a conventional shelving bass control. R90,91,92, and 93 with C85 (and C84 when in-circuit) set the turnover frequency with the network able to be supplemented by a 10k linear pot (RV11) so the operator can have fully variable control of this frequency. The table shown in Figure 7 gives component values for the range of turnover frequencies between 30Hz and 100Hz. Switching capacitor C84 In or Out of circuit using SW8 achieves a bell or resonant type of response rather than the shelving response yielded when the capacitor is shorted out. Again, the switching operation can be combined as a pull on/push off switch integral to RV11 if this is fitted or from a separate switch. Refer to the schematic shown in Figure 10 next month. The network transfer function is as follows:

$$f_{\text{centre}} = 1/2\pi\sqrt{1/C84C85R90R91}$$

A variable bootstrapping arrangement appears on the output of the op-amp. A linear pot is used which, with the law-faking resistors R91,92 and 93 and the bootstrapping technique, yields a very usable law with frequency rising logarithmically with pot rotation. In this way, Q varies as frequency is increased, with larger Q's - smaller bandwidths - at the lower end of the frequency range and the opposite as frequency is increased. This yields an audio characteristic which is subjectively very powerful and useful. Q is around the 1.5 mark at 30Hz and about 0.47 at 100Hz. It alters because the ratio of resistance:reactance changes with frequency, in effect making the network more 'lossy' at higher frequencies. C84 value has been chosen so that it swamps C85 and, also, the desired frequency is affected with the in-circuit resistor values. All of the impedances are quite critical, compromised in such a way that there is a reasonable cut and boost ratio to the required frequencies and little effect on the others ie those in the upper-mid and HF parts of the spectrum. The responses in Figure 11 next month, show the lazy Q value at the 100Hz control setting (with maximum boost) and means the stage has a lot of effect on frequencies extending into the lower mid region. Circuit impedances mean that even at HF, the response does not fall to unity. The worst case deviation in this design is in the order of plus or minus 1dB. When we consider there is a 15dB change to the frequencies at the lower end of the spectrum, the subjective effect upon HF is minimal.

control on the input amplifier, I could have used a multi-way switch coupled to a precision resistor string. This would have restricted flexibility (only discrete values of break frequency would then have been available) and added cost so I thought it better to stick with the preferred arrangement wherein some operational ease is sacrificed - the control law is very slightly cramped at one end of its rotation - but fully variable control is realized.

Admittedly, the star-delta arithmetic does become a little tedious but at the risk of sounding sanctimonious or just plain patronizing, to those 'in the know' or with very smart friends (most definitely the author's case), there do exist certain key values which can be used to yield the important law-faking curves. This alleviates calculator-induced insomnia!

Unfortunately, this law-fiddling approach can only work where the network is a three terminal type - this technique could not therefore be used in the Q-determining pots in the parametric sections. A reverse-connected log pot was therefore used and yields a workable compromise although WIDTH is increased as the pot is rotated clockwise compared to Q in conventional, commercial designs using anti-log types - one example of the maverick approach - but in operational use, no problems have been forthcoming. There is nothing to stop enterprising individuals who *do* manage to track down dual-gang anti-log pots at reasonable prices fitting them to this stage.

Where fully-variable operator control of the optional parts of the equalizer - High pass Filter and LF and HF Equalisers break frequencies - is NOT required, the respective pots can be replaced by resistor or resistors in the cases of the dual-gang types.

References

Sound Recording Practise (edited by John Borwick), Microphones John Borwick, Mixing Consoles, Analogue (Richard Sweetenham).

Sound Processing (Richard Elen) - Digital Recorders (Tony Faulkner) - Classical Music (Adrian Revill) - Popular Music (Mike Ross) - Radio Broadcasting (Dave Fisher) Oxford University Press.

Audio Electronics Handbook (edited by Ian R Sinclair) - Sound Recording Techniques (Don Aldous), Sound Waves (Dr W Tempest) -BSP Professional Books.

The New Audio Cyclopedia (edited by Glen M. Ballou) - Consoles and Systems (Steve Dove), Details of the Session (Chips Davies with Linda Jacobson) - Howard W Sams.

Active Filter Cookbook - First and Second Order Networks, Bandpass Filter Design, Bandpass Filter Circuits (Don Lancaster) - Howard W Sams.


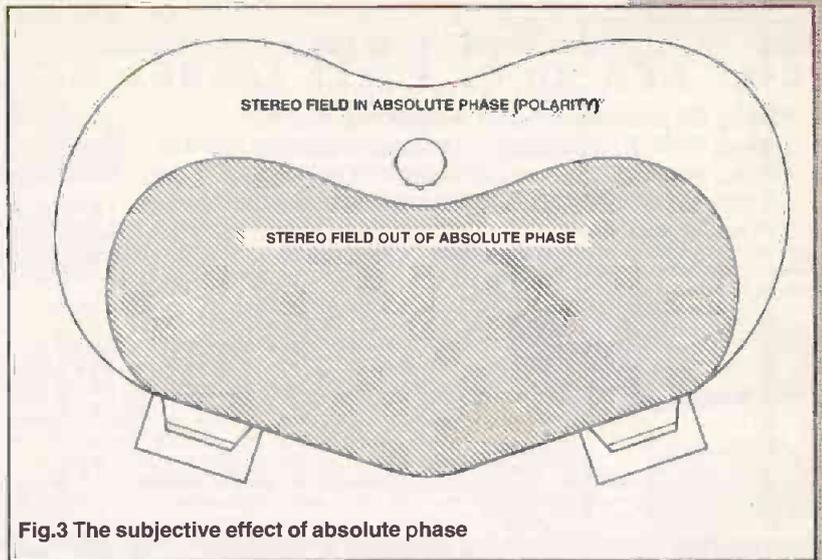
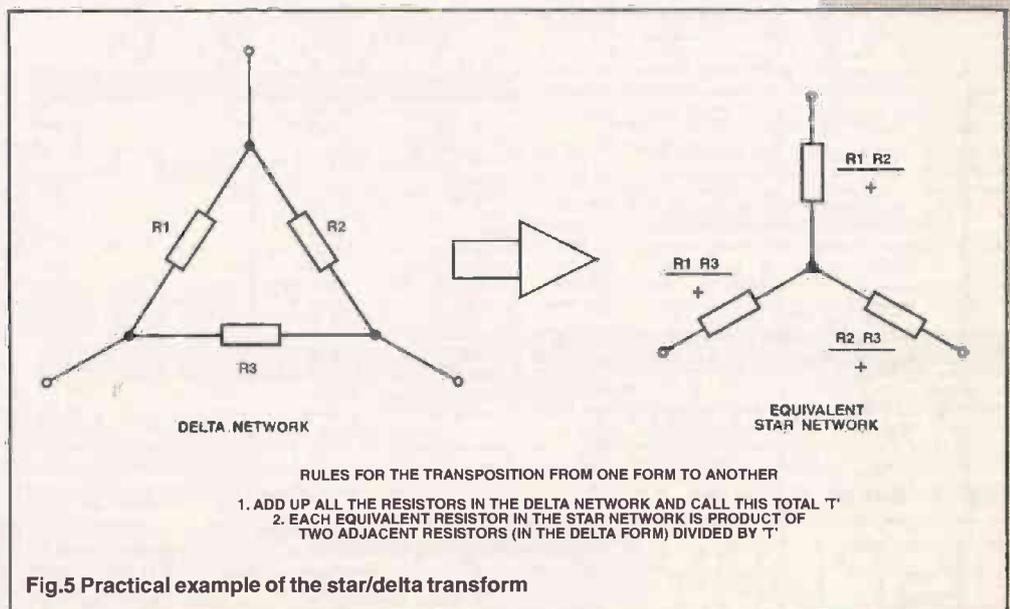


Fig.3 The subjective effect of absolute phase

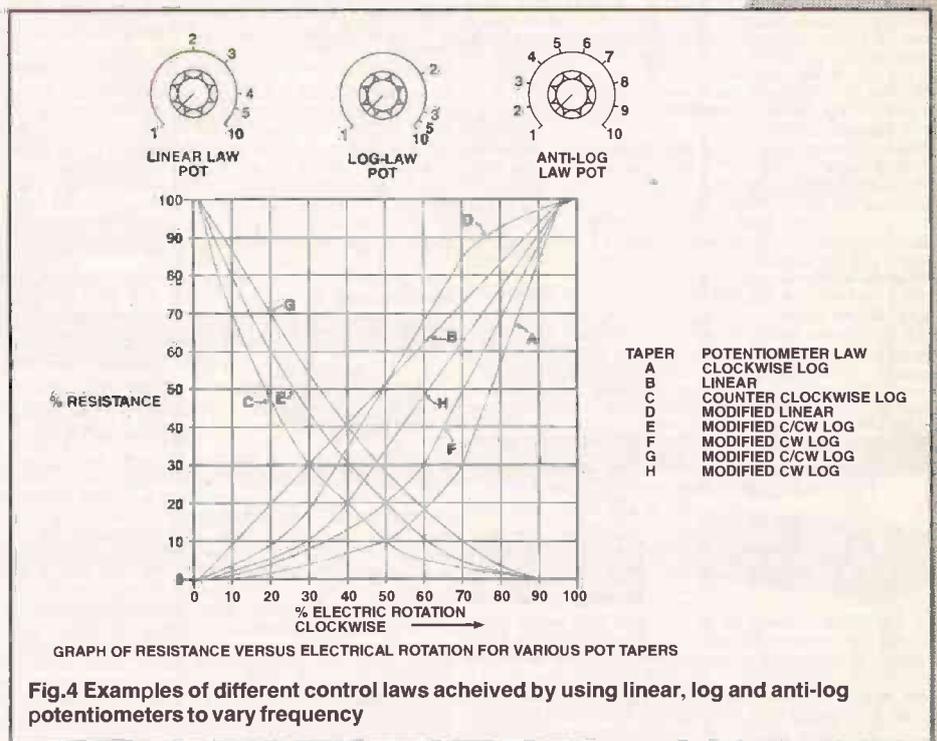

**MORE ON EQ
NEXT MONTH**

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

Surplus always wanted for cash!

COMPUTER SCOOPS


PC-AT 386 20-DX FULLY LOADED FOR £499!

- 20 Mhz DX processor
- 2 megs RAM. Exp 10 meg
- 40 meg hard drive
- 1.2 meg 5-1/4" floppy
- 32K cache exp. 64K
- installed VGA card
- Enhanced 102 key k/board
- Complete with MS-DOS 4.01
- 2 serial 1 parallel ports
- 8 free slots- 6 off 16 bit!



The MP386 quality made by Mitsubishi to last a lifetime! Brand new with all manuals and software plus Super PC-Quick Disk Accelerator for lightning disk access.

£499 (F)

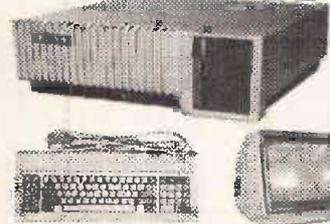

A COMPLETE IBM PC COMPAT SYSTEM FOR ONLY £99!!

Just plug in and go - fully expandable - the Display PC-99! System supplied complete with 12" mono monitor, 84 key keyboard, 360K 5-1/4" floppy disk drive, 128K RAM, 2 serial and 1 parallel port plus DOS with manual. Many other features include 7 slot backplane, all metal case, 150 watt PSU and US made motherboard. In very good used condition with 90 day guarantee. At the unique price of:

Optional FITTED extras: 256K RAM £15; 640K RAM £39. 12" CGA colour monitor with card £89. 2nd 5-1/4" 720K floppy (or 360K if preferred) £29.95. 2x power hard drive £99.

£99 (E)

FLOPPY DISK DRIVES

5 1/4" from £22.95 - 3 1/2" from £21.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported).

- 3.5" Panasonic JU364 720K* £21.95(B)
- 3.5" Mitsubishi MF353C-L 1.4 Meg. Laptops only* £29.95(B)
- 3.5" Mitsubishi MF353C-D 1.4 Meg. Non laptop* £29.95(B)
- 5.25" Teac FD-55(36) 360K half height £22.95(B)
- 5.25" Teac FD-55(72) 720K half height £24.95(B)

* Data cable included in price.
Shugart 800/801 SS refurbished & tested £175.00(E)
Shugart 851 double sided refurbished & tested £275.00(E)
Mitsubishi M2894-83 double sided switchable hard or soft sectors- BRAND NEW £250.00(E)

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply! Ideal as exterior drives! £499.00(F)
End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only.....£299(E)

THE AMAZING TELEBOX!

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television or video channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Composite and RGB video outputs are located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

- Telexbox ST for composite video input monitors £32.95
- Telexbox STL as ST but with integral speaker £36.50
- Telexbox MB as ST with Multiband tuner VHF-UHF-Cable. & hyperband For overseas PAL versions state 5.5 or 6mhz sound specification. £69.95
- Telexbox RGB for analogue RGB monitors (15khz) £69.95

Shipping code on all Telexboxes is (B)
RGB Telexbox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM / NTSC not available.

No Break Uninterruptable PSU's

Brand new and boxed 230 volts uninterruptable power supplies from: Densel. Model MUK 0565-AUAF is 0.5 kva and MUD 1085-AHBH is 1 kva. Both have sealed lead acid batteries. MUK are internal, MUD has them in a matching case. Times from interrupt are 5 and 15 minutes respectively. Complete with full operation manuals.....MUK.....£249 (F) MUD.....£525 (G)

POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims: 13" x 5" x 2.5". Fully guaranteed RFE. £85.00 (B)

- Power One SPL130. 130 watts. Selectable for 12v (4A) or 24v (2A). 5v @ 20A. ± 12v @ 1.5A. Switch mode. New. £59.95(B)
- Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a. +12v @ 2a. -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". New £22.95(B)
- Greendale 19ABOE 60 watts switch mode. +5v @ 6a. ± 12v @ 1a. +15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cms. £24.95(C)
- Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a. -5v @ 1a. ± 12v @ 6a. 27 x 12.5 x 6.5cms. New. £49.95(C)
- Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a. +12v @ 2.5a. -12v @ 0.5a. -5v @ 0.5a. £29.95(B)
- Farnell G6/40A. Switch mode. 5v @ 40a. Encased £95.00(C)
- Farnell G24/5S. As above but 24v @ 5a. £65.00(C)

BBC Model B APM Board



£100 CASH FOR THE MOST NOVEL DEMONSTRATABLE APPLICATION!

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board!! It is supplied complete with a connector panel which brings all the I/O to 'D' and BNC type connectors - all you have to do is provide +5 and ± 12v DC. The APM consists of a single PCB with most major ic's socketed. The ic's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dims: main board 13" x 10". I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only £29.95 or 2 for £53 (B)

SPECIAL INTEREST

- Trio 0-18 vdc bench PSU. 30 amps. New £ 470
- Fujitsu M3041 600 LPM band printer £2950
- DEC LS/02 CPU board £ 150
- Rhode & Schwarz SBUF TV test transmitter £6500
- 25-1000mhz. Complete with SBTf2 Modulator
- Calcomp 1036 large drum 3 pen plotter £ 650
- Thurby LA 160B logic analyser £ 375
- 1.5kw 115v 60hz power source £ 950
- Anton Pillar 400 Hz 3 phase frequency converter 75Kw POA
- Newton Derby 400 Hz 70 Kw converter POA
- ADDS 2020 VDU terminals - brand new £ 225
- Sekonic SD 150H 18 channel Hybrid recorder £2000
- HP 7580A A1 8 pen high speed drum plotter £1850
- Kenwood DA-3501 CD tester, laser pickup simulator £ 350

BRAND NEW PRINTERS


- Microline 183; NLQ 17x17 dot matrix. Full width. £139 (D)
- Hyundai HDP-920. NLQ 24x18 dot matrix full width. £149 (D)
- Qume LetterPro 20 daisy. Qume QS-3 interface. £39.95 (D)
- Centronics 152-2 9 x 7 dot matrix. Full width. £149 (D)
- Centronics 159-4 9 x 7 dot matrix. Serial. 9-1/2" width £ 99 (D)

MONITORS

MONOCHROME MONITORS

THIS MONTH'S SPECIAL!

There has never been a deal like this one! Brand spanking new & boxed monitors from NEC, normally selling at about £140! These are over-engineered for ultra reliability. 9" green screen composite input with etched non-glare screen plus switchable high/low impedance input and output for daisy chaining. 3 front controls and 6 at rear. Standard BNC sockets. Beautiful high contrast screen and attractive case with carrying ledge. Perfect as a main or backup monitor and for quantity users! £39.95 each (D) or 5 for £185 (G)

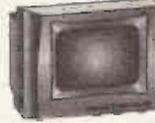

COLOUR MONITORS HI-DEFINITION COLOUR MONITORS

SAVE £59 - ONLY £100 WHEN BOUGHT WITH THE 386 ABOVE!



14" Philips Model CM8873 VGA multi-sync all the way up to 34Khz with 640 x 480 resolution. This one has everything! Two switches enable you to select CGA, EGA or VGA and digital/analog. Unusual for a professional monitor, sound is also provided, with a volume control. There is also a special "Text" switch for word processing, spreadsheets and the like. Compatible with virtually all computers including IBM PC's, Amiga, Atari, BBC, Archimedes etc. Good used condition (possible minor screen burns) 90 day guarantee. 15" x 14" x 12". Only.....£159 (E)

KME 12" high definition colour monitors. Nice tight 0.28" dot pitch for superb clarity and modern two tone plastic styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13.5" x 12" x 11". Also functions as quality TV with our RGB Telebox. Excellent used condition with 90 day guarantee. In nice two tone beige and brown case. Only.....£149 (E)

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. Only.....£129 (E)

NEC CGA 12" IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" L x 13" W x 12" H. The front cosmetic bezel has been removed for contractual reasons. Only.....£79 (E)

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

CALL FOR PRICING ON NTSC VERSIONS!

Superb Quality 6 foot 40u

19" Rack Cabinets

Massive Reductions

Virtually New, Ultra Smart! Less Than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2" H x 32-1/2" D x 22" W. Order as:
Rack 1 Complete with removable side panels.....£275.00 (G)
Rack 2 Less side panels.....£145.00 (G)

COOLING FANS

- 3 inch AC. 1 1/2" thick £ 8.50 (B)
- 92 mm AC 230 v. 18mm thick £12.95 (B)
- 3 1/2 inch AC ETRI slimline. Only 1" thick. £ 9.95 (B)
- 3 1/2 inch AC 230 v 8 watts. Only 3/4" thick £12.95 (A)
- 4 inch AC 110/240v 1 1/2" thick. £10.95 (B)
- 10 inch AC round, 3 1/2" thick. Rotron 110v As above but 230 volts £10.95 (B)
- 10 inch DC 1" thick. No 812 for 6/12v. 814 24v. £15.95 (A)
- 80 mm DC 5 v. Papst 8105G 4w. 38mm. RFE. £19.95 (A)
- 92 mm DC 12v. 18 mm thick. £14.95 (A)
- 4 inch DC 12v. 12w 1 1/2" thick £12.50 (B)
- 4 inch DC 24v 8w. 1" thick. £14.50 (B)

1992 Summer Issue of Display News now available - send large SAE - PACKED with bargains!

DISPLAY

MAIL ORDER & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET 32 Biggin Way,
Upper Norwood,
London SE19 3XF

LONDON SHOP
Open Mon-Sat 9-5.30
215 Whitehorse Lane,
South Norwood,
London, SE25

DISTEL The Original
Free dial-up database!
1000's of items On Line
V21, V22 & V22 bis
081-679-1888

ALL ENQUIRIES
081-679-4414
Fax-081-679-1927



-ELECTRONICS-

All prices for UK Mainland UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome-minimum account order £30. Carriage charges (A)=£2.00. (B)=£3.75. (C)=£5.50. (D)=£8.50. (E)=£11.50. (F)=£18.00 (G)=Call. Scotland surcharge: call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. Rights reserved to change prices & specifications without prior notice. Orders subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always wanted for cash.



AUTONA LTD
UK's leading module manufacturer since 1972

★ **AUDIO MODULES** ★

AL 12580-125W AMPLIFIER

A rugged high powered module that is ideal for use in discos & P.A. Systems where powers of up to 125W, 4 ohms are required. The heavy duty output transistors ensure stable and reliable performance. It is currently supplied to a large number of manufacturers where reliability and performance are the main considerations, whilst for others its low price is the major factor. Operating from a supply voltage of 40-80V into loads from 4-16 ohms.



£18.95
+ VAT

AL 2550-COMPACT LOW-COST 25W AMPLIFIER

One of our most popular audio modules with tens of thousands installed. Ideal for domestic applications where low distortion and compact size are the prime requirements. Used with supply raids of 20V-50V into loads of 8-16 ohms.

£6.55
+ VAT



MM 100-BUDGET 3-INPUT MIXER

With a host of features including 3 individual level controls, a master volume and separate bass and treble control, it provides for inputs for microphone, magnetic pick-up and tape, or second pick-up (selectable), and yet costs considerably less than competitive units. This module is ideal for discos and public address units and operates from 45V-70V.

£17.49
+ VAT



MM 100G GUITAR MIXER

As MM100 with two guitar + 1 microphone input intended for guitar amplifier applications.

£17.49
+ VAT

COMPLETE AUDIO RANGE FROM 10W-125W
SEND FOR DETAILS TODAY

SECURITY EQUIPMENT

MINIATURE PASSIVE INFRA-RED SENSOR-RP33

Switchable Dual range, detects intruders up to 6 or 12 metres
Quantity discounts start at 3 units.
This advanced sensor operates by detecting the body heat of an intruder moving within the detection field. Slow ambient changes such as radiators, etc. are ignored. Easily installed in a room or hallway. Providing reliable operation from a 12V supply, it is ideal for use with the CA 1382 or equivalent high quality control unit. Supplied with full instructions.
Size 80x60x40mm



£17.95
+ VAT

DIGITAL ULTRASONIC DETECTOR-US 5063

Crystal controlled movement detection module operating at 50KHz with an effective range up to 20ft. Suitable for operation in a household or vehicle security systems. 12V operation and built-in timing makes it suitable for a wide range of applications.



£14.93
+ VAT

Easily Installed

ADVANCED CONTROL UNIT-CA 1382

Automatic Loop Test on Switch On ★ Automatic Siren Re-Set ★ Audible Entry/Exit Warning Buzzer ★ Two Separate Loop Inputs ★ 24-hr Circuits ★ Easily Installed. Full Instructions Supplied.

This advanced control panel provides effective and reliable control for all security installations, yet its operation is sheer simplicity for all members of the family, and is supplied with two keys Housed in a steel case with an attractive moulded front panel, it compares with units costing twice the price.



£44.95
+ VAT

LOW-COST CONTROL UNIT-CA 1250

This tried and tested control unit provides the finest value for money in control systems, with many thousands protecting houses all over the country. A suitable steel enclosure is available separately.



Only £21.35
+ VAT

50FT INFRA-RED BEAM-IR 1470

The IR1470 consists of a separate transmitter and receiver providing a beam of up to 50ft which, when interrupted, operates a relay in the receiver which in turn may be used to control external equipment. The system requires only 65mA from a 12V supply. Size: (each unit) 82 x 52 x 57mm

£25.61
+ VAT

PLUS FULL RANGE OF SECURITY ACCESSORIES FOR COMPLETE HOME PROTECTION
TELEPHONE FOR FREE LITERATURE TODAY

DEPT ETI-11
51 POPPY ROAD
PRINCES RISBOROUGH
BUCKS HP17 9DB
TEL: (084 44) 6326
FAX: (084 44) 7102

Order by Credit Card for immediate despatch



Add VAT Carriage only £1.50
Export 10% minimum £1.50

RALFE ELECTRONICS

36 EASTCOTE LANE,
SOUTH HARROW
Middlesex HA2 8DB
Tel: 081 422 3593
Fax: 081 423 4009

"WANTED"

We are continually on the lookout to buy for stock 'High-end' equipment by brand names such as Hewlett-Packard, Tektronix, Marconi etc. and we would be grateful for the opportunity to offer for any items you may have available now or in the future.

MILLIONS OF QUALITY COMPONENTS AT LOWEST EVER PRICES

Plus Tools, Watches, Fancy Goods, Toys.
Mail order only. UK only.

All inclusive prices
NO post, or VAT etc to add on.

Send 34p stamped self-addressed label or envelope for catalogue/clearance list.
At least 2,100 offers to amaze you.

Brian J Reed Electronics
6 Queensmead Avenue, East Ewell
Epsom, Surrey KT17 3EQ
Tel: 081-393 9055

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 range Plug-in Oscilloscopes	
7603 with 7A26 & 7B53A Dual Trace 100MHz Delay Sweep with Cursors	£450
7403N with 7A18 & 7B50 Dual Trace 60MHz	£300
7504 with 7A12 & 7B52 Dual Trace 80MHz Delay Sweep	£250
7503 with 7A12 & 7B50 Dual Trace 90MHz	£200
7633 with 7A26 & 7B53A Dual Trace 100MHz Delay Sweep Storage	£300
7313 with 7A18 & 7B53 Dual Trace 125MHz Delay Sweep Storage	£300
7A13 Differential Comparator Amplifier DC-105MHz	£125
Other plug-in options are available in 4 Trace etc.	
TEKTRONIX 2445B Four Channel 150MHz Delay Sweep with Cursors	
TEKTRONIX 2445A Four Channel 150MHz Delay Sweep	£1750
with Cursors	£1300
WAITSU 855711 Four Channel 100MHz Delay Sweep	£700
TRIO CS2100 Four Channel 100MHz Delay Sweep	£500
TEKTRONIX 2306 Dual Trace 100MHz Delay Sweep Pluggerised	£1000
HITACHI V1050F Dual Trace 100MHz Dual TB with 4 Channel Mode	£550
SEPLUMBERGER 5219 Dual Trace 200MHz Delay Sweep Trig View	
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£350
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£450
TRIMLIPS 3267 Dual Trace 100MHz Delay Sweep	£500
TEKTRONIX 2215A Dual Trace 50MHz Delay Sweep	£450
TEKTRONIX 2225 Dual Trace 50MHz Alternate PE Magnification	£500
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£400
GOULD OS3000A Dual Trace 30MHz Delay Sweep	£250
GOULD OS1100 Dual Trace 30MHz	£180
GOULD OS300 Dual Trace 20MHz	£200
WAITSU CS5702 Dual Trace 20MHz	£225
EQUIPMENT 066 Dual Trace 25MHz	£150
TRIO CS1720 Programmable 20MHz Dual Trace	£300
HITACHI V429 Dual Trace 20MHz Portable (AC-DC Operation)	£400
THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE	
JUST IN	
HAMEG 205 3 Dual Trace 20MHz Digital Storage with 2 Probes & Copy of Manual	only £450
RACAL Instrumentation Recorders Store 4D and Store 7D	from £500
KEITHLEY 224 Programmable Current Source	£1000
FERRUGRARI RT52 Recorder Test Set	from £150
FARNELL SS5230 Synthesised Sp Gen 10-520MHz	£500
FARNELL TTS220 Transmitter Test Set consisting of RF/AF Counter, RF Mod meter, RF Power Meter, AF Voltmeter, AF Distortion meter, AF Synthesizer	£500
SOLD as a pair for ONLY	£1000
SPEC TRIM ANALYSERS	
TEKTRONIX 494AP 10KHz-325GHz	POA
ANRITSU MS88B 10KHz - 4.4GHz	£4000
ANRITSU MS82B 10KHz - 170MHz	£2000
HP 1411 with 8555A & IF Plug-in 10MHz-18GHz	£2500
HP 1411 with 8554B & 8552B 50MHz-1250MHz	£1500
HP 1401 with 8554A & 8552A 500KHz-1250MHz	£1200
HP 1411 with 8556A & 8552B 20Hz-300KHz	£1250
TEKTRONIX 491 Option 01 1MHz to 2GHz	£1000

Used equipment - with 30 days guarantee. Manuals supplied if possible
This is a VERY SMALL SAMPLE OF STOCK. See Telephone for lists. Please check availability before ordering
CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 0734 268041 Fax: 0734 351696 Callers welcome 9am-5.30pm Mon-Fri (until 8pm Thurs)

PHILIPS PM3205 Multi Function DMM 4.5-5.5 digit with GHI/IEEE 488	only £300
THURLEY PL300T GP Bench PSU 0-30V 2 Amp	
Twice with GPIB	only £350
HAND HELD MULTIMETERS - 3.5 digit DM105-14 Ranges DC 2 Amp	only £18
M235-32 ranges AC/DC 10 Amps Diode/Transistor Tester; Freq Counter etc	£32.50
RACAL/DANA Syn Sig Gen 9084 0.01-104MHz	£500
RACAL/DANA RF Power Meter 9104	£900
RACAL/DANA 9341 Databridge Automatic measurements of L, C, R & Q	£350
WAYNE KERR B424 RCL Meter LCD Display	£165
WAYNE KERR 4210 LCR Meter Accuracy 0.1%	£500
AVO AC/DC Breakdown Leakage & Ionisation Tester RM215/2	£600
MARCONI DIGITAL FREQUENCY METERS	
Type 2434 10MHz-40MHz	£125
Type 2431A 10MHz-200MHz	£130
MARCONI UNIVERSAL COUNTER TIMERS	
Type 2437 DC-100MHz	£175
Type 2438 DC-500MHz	£225
THORN PSU 0-40V-0.50 Aamps Metered	£300
FARNELL PSU 80X25 0-40V 0.25 Aamps Metered	£400
FARNELL PSU 130X 0.30V 0.5 Aamps Metered	£80
TELEQUIPMENT CT71 Curve Tracer	£250
MARCONI TF2700 Universal LCR bridge, battery	from £125
MARCONI TF2337A Auto Distort Meter 400Hz-1KHz 0.01%	£175
RACAL 9915 Freq Counter 10Hz-520MHz (Crystal Over)	£150
MANESMAN TALLY Poly 3XV plotter RS22	£100
AVO MULTIMETERS	
Model: 6 or 9 (what's available)	£40 each
Test Set No.1: BK, BSX	from £45
8 Mks 5 with Carrying Case	£50
8 Mks 6 with Carrying Case	£120
All Meters Supplied with Batteries & Leads	
NEW EQUIPMENT	
HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay	£790
Farnelco	
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Sweep	£510
FHAMEG OSCILLOSCOPE HM203 Dual Trace 20MHz Component	£330
Testa	
FHAMEG OSCILLOSCOPE HM205.3 Dual Trace 20MHz Digital Storage	£510
All other models available - all oscilloscopes supplied with 2 probes	
BLACK STAR EQUIPMENT (p&p all units £5)	
APOLLO 10 - 100MHz Counter Times Ratio/Period/Time Interval etc	£222
APOLLO 100 - 100MHz (as above with more functions)	£325
METEOR 100 FREQUENCY COUNTER 100MHz	£109
METEOR 600 FREQUENCY COUNTER 600MHz	£135
METEOR 1000 FREQUENCY COUNTER 1000Hz	£178
JUPITOR 500 FUNCTION GENERATOR 0.1Hz-500KHz Sine/Sq/Tri	£110
ORION COLOUR BAR GENERATOR Pal/TV/Video	£229
All other Black Star Equipment available	
OSCILLOSCOPE PROBES Switchable x1 x10 (p&p £3)	£11

Digital Circuit Tester


Daniel Brook constructs an invaluable piece of test equipment

In theory it should be easy to test digital circuits as any point can only be at one of two voltage levels, and for simple circuits the theory holds true. All that is required is a logic probe to display the high/low status of the point being tested.

However, simple gates rapidly get built up into counters, microprocessors etc. with buses of logic signals, and in these situations it can be difficult and/or impractical to test the system using only a single logic probe to find the value of a word on a typical 8-bit bus would require eight tests and a calculator (or a good memory and head for figures!)

Even using eight logic probes together, you would still have to convert the binary word to a base more manageable by the human brain.

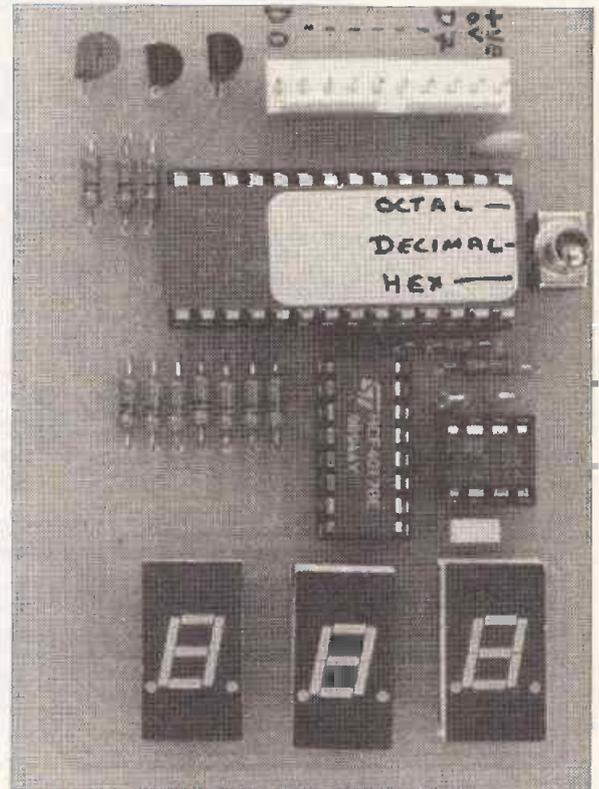The solution to this problem is BUSTEST. This project has eight TTL logic inputs, and will display the value at the inputs on three 7 segment displays. The display is switchable between octal, decimal and hexadecimal number bases, each of which can be useful, depending on the situation.



a number of digits, but these are designed to be used with microprocessors, and most will only produce output in one number base (usually hex or decimal).

Solution

The solution presented here uses an EPROM and a simple multiplexer circuit to directly drive each of the three digits that make up the display (see Figure 1). The EPROM acts like a look-up table to display the correct number in each display, according to the word on the input pins. By choosing a large enough EPROM, there is provision for switching between octal, decimal and hex number bases.

EPROM

The EPROM required is a 2764 device which needs to be programmed. Rather than present a lengthy hex dump of the EPROM contents, which would require a tedious amount of (error prone) typing in, I present a BASIC program. The program (Figure 4) was written in GW BASIC on a PC clone, and generates a binary file called 'BUSTEST.BIN'. This file contains the required EPROM contents, which can be loaded into a programmer and then used to blow the EPROM.

Alternatively, I can supply pre-programmed EPROMS (See Buylines).

Construction

Construction is fairly simple. Start first with the resistors (note that R6 and R7 are mounted vertically), then the IC sockets, capacitors, the connector (if required) and the

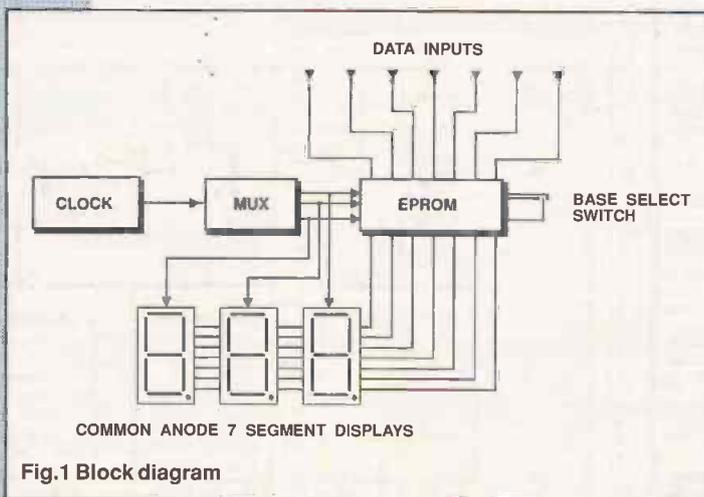


Fig.1 Block diagram

Design Considerations

The unit must be fairly compact as it is a piece of test gear, simple to use (but still useful), and reasonably cheap. Also it must be 5V TTL compatible as most complex digital systems fall into this category.

The obvious solution to the problem would seem to be to use a 7-segment display driver IC such as the 4511, but closer investigation shows that this approach won't solve the problem. This is because the 4511 and similar drivers only convert the 4 binary inputs to a single decimal digit, according to the BCD (Binary Coded Decimal) system, which isn't acceptable for this application.

More expensive driver ICs are available that will control

HOW IT WORKS

IC1, R1, R2 and C1 form an astable oscillator, running at approximately 42kHz. This clock output is fed into IC2, a decoded decade counter. Three outputs from the decade counter switch on the displays via resistors R3-5 and transistors Q1-3 (see circuit diagram, Figure 2). To turn on a segment or segments in any particular display, the EPROM must sink current through the required segment and resistor. R8-14 limit the current through the LED segments and EPROM pins to about 5mA, but TTL can sink 16mA max, so this is within limits.

The EPROM can only light segments in one display at any one time, but cycles through all the digits so quickly (as determined by the clock) that persistence of vision makes us believe that all the digits are on together.

The segments the EPROM turns on are determined by the 'look-up tables' programmed into the EPROM. The part of the table that is 'looked at' is, in turn, determined by the EPROM address. The address is partly made up from the input signals (D0-D7) which connect to A0-A7. The next two address bits, A8 and A9, select the table for the desired number base. Both lines are normally pulled high by R6 and R7, but one or other or none of the two can be set low by switch SW1. When they are both high, decimal is selected. When A8 is low, octal is selected, and when A9 is low, hex is selected. The final three bits of the address come from the counter, IC2. When A11 is high, the EPROM outputs the code for DISP3. When A10 is high, the code for DISP2 is output, and when A12 is high the code for DISP1 is output.

IC2 outputs Q1, Q3 and Q5 control address lines A11, A10 and A12 respectively. IC2 outputs Q0, Q2 and Q4 are not used so that there is a gap between one display turning off and the next turning on.

Output Q6 resets the counter to begin the cycle again.

switch. The switch used is a small PCB mounting SPDT device with on-off-on action. i.e. the moving pole can touch either, or neither, of the two throws. This provides the switching between the three number bases.

Next fit the displays, which may be socketed if desired (remove pins 4,5 and 12 from a 14 pin DIL socket), and then the ICs. Note that IC2 is a CMOS device so take anti-static precautions when handling it.

Finally, you will need to connect some test leads (see Figure 3). Mini probe clips on short lengths of wire are ideal for general purpose use, or you can make up custom leads to suit your requirements. It is advisable to at least colour code the power leads, if not the test inputs as well. If you have fitted a connector to the PCB the leads will have to connect to the other half of the connector (the socket). Alternatively, solder the leads to PCB pins, or directly to the pads. The unit wasn't designed to be cased, although small boxes are available should you wish to enclose the unit. One final touch, whether you decide to case the unit or not, is to put a piece of red filter in front of the displays to improve their readability.

Testing

Before connecting up the circuit, check the board for solder shorts, make sure the components are in the correct

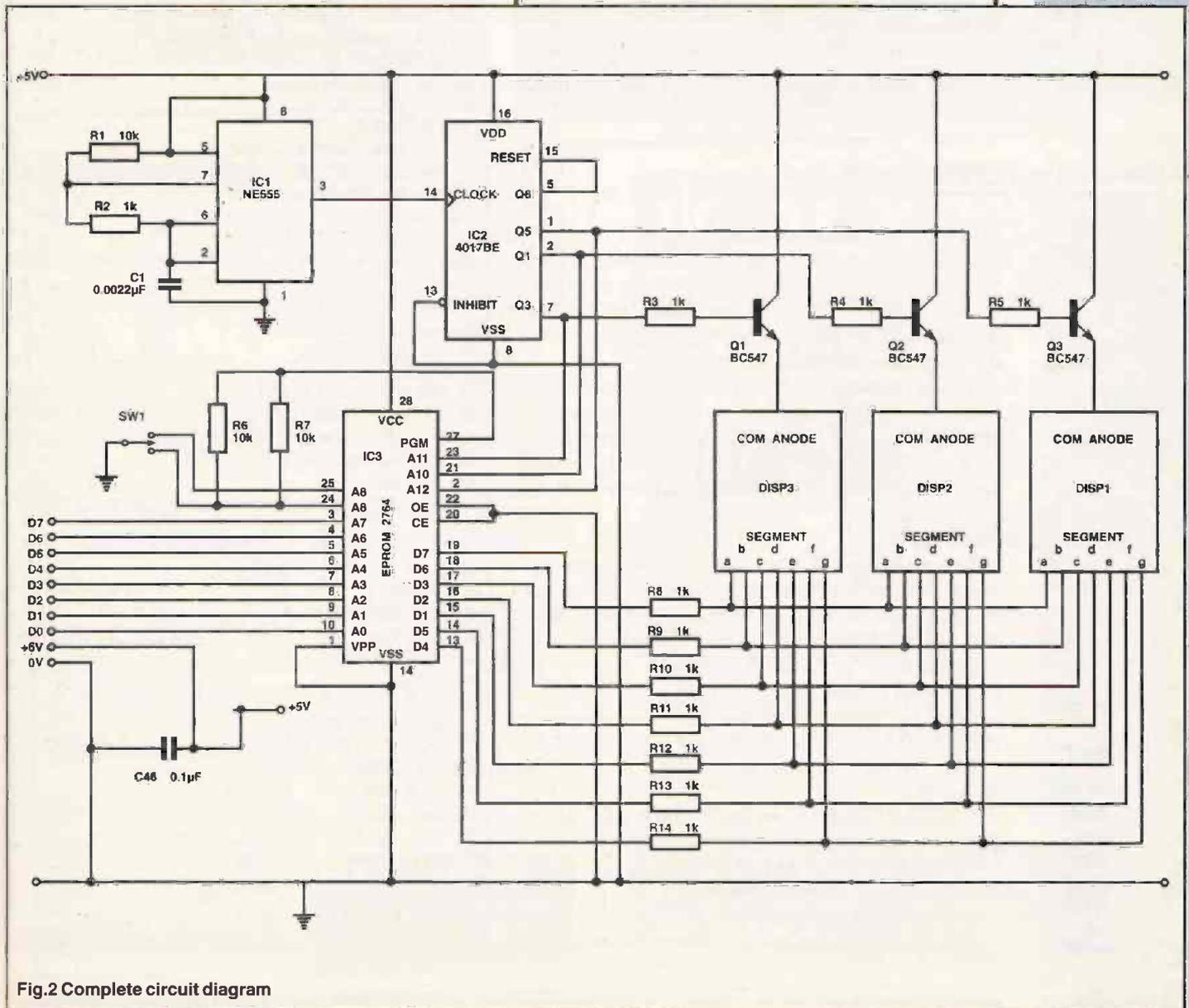


Fig.2 Complete circuit diagram

places and that IC's are the right way round in their sockets.

Assuming that all is okay so far, connect the power leads to a 5V DC supply, and ground all of the inputs. Flicking the switch between octal and decimal should produce three zeros, whilst in hex only two zeros should be displayed.

Now connect the inputs to +5V. The display should show 377 for octal, 255 for decimal and FF for hex.

If the unit has worked so far, it is unlikely that anything is wrong, but to satisfy yourself you may wish to apply various

a separate digit displaying the value of each word. When used in this way, the left-hand digit shows the value on D4-D7 (D4 is LSB, D7 is MSB), and the right-hand digit shows the value on D0-D3 (D0 is LSB, D3 is MSB).

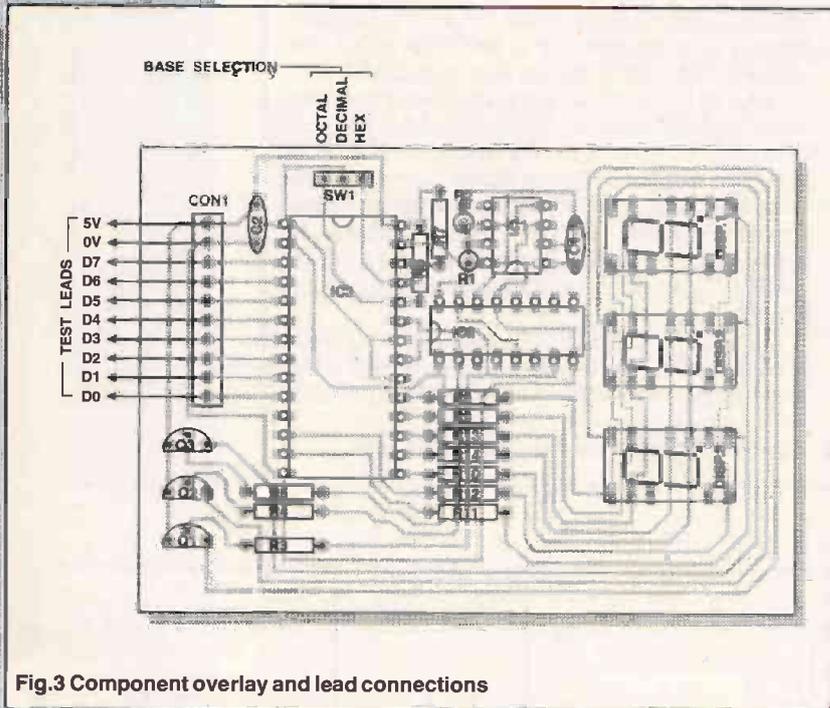


Fig. 3 Component overlay and lead connections

words to the unit and check the output.

If the unit has not yet shown signs of life, switch off and recheck the component positions and solder joins. If you have a 'scope, check there is a clock output from IC1 pin 3 and that this reaches IC2 pin 14. Also check that pins 1, 2 and 7 of IC2 are being pulsed regularly.

If the unit still doesn't work, it is likely that the EPROM has not been programmed correctly or is of the wrong type - it must be a standard TTL 2764, NOT a CMOS version. If you programmed your own EPROM, check that you have entered the program correctly, then erase and reprogram the EPROM.

In Use

Operation of the unit is very straight-forward. Remember to always connect the power supply lines before connecting any of the inputs D0-D7. D0 is the least significant bit (LSB) and D7 the most significant bit (MSB). The inputs should be connected to the circuit under test bearing this in mind, otherwise the output will make no sense.

If less than 6 bits are being tested, unused lines should be grounded (these will be at the MSB end of the inputs).

I will now briefly mention the merits of each of the three number bases:

Octal digits map to 3 binary digits, enabling easy conversion back to binary if required.

Decimal is the easiest base for us humans to manipulate, as it is the one we are most used to.

Hexadecimal digits map to 4 binary digits. With this in mind, it is possible to monitor two words of up to 4 bits, with

Program for Digital Circuit Tester

```

10 CLS
20 REM Program to build EPROM file for use with BUSTEST project.
30 REM Written in GW BASIC by D. BROOK 21/5/92.
40 OPEN "BUSTEST.BIN" AS #1 LEN=1
50 FIELD #1,1 AS DGC$
60 FOR LOOP=1 TO 8192
70 LSET DGC$=CHR$(255)
80 PUT#1,LOOP
90 NEXT
100 PRINT "CREATED EMPTY FILE"
110 REM Read "character codes" for 7 segment displays into array DG(n)
120 REM where n is the value (0-15) of the corresponding character.
130 DIM DG(15)
140 FOR LOOP=0 TO 15
150 READ DG(LOOP)
160 NEXT LOOP
170 REM Do the MAJOR loop 3 times (for octal, decimal, then hex data).
180 FOR MAJOR=1 TO 3
190 IF MAJOR=1 THEN PRINT "FILLING IN OCTAL DATA"
200 IF MAJOR=2 THEN PRINT "FILLING IN DECIMAL DATA"
210 IF MAJOR=3 THEN PRINT "FILLING IN HEX DATA"
220 READ NUMBASE,LPA,LPB,LPC,MULB,MULC
230 REM Constants for loop set up.
240 REM Begin the MAJOR loop:
250 FOR DGTC=0 TO LPC
260 FOR DGTB=0 TO LPB
270 FOR DGTA=0 TO LPA
280 BASEREC=((DGTC*MULC)+(DGTB*MULB)+DGTA+NUMBASE)+1
290 REM Base record number set up.
300 REM Output code for digit A to the file.
310 LSET DGC$=CHR$(DG(DGTA))
320 REC=BASEREC+4096
330 PUT#1,REC
340 REM Now output for digit B.
350 LSET DGC$=CHR$(DG(DGTB))
360 REC=BASEREC+1024
370 PUT#1,REC
380 REM Now output for digit C.
390 LSET DGC$=CHR$(DG(DGTC))
400 IF MAJOR=3 THEN LSET DGC$=CHR$(255)
410 REC=BASEREC+2048
420 PUT#1,REC
430 REM Check if loop should end (i.e. all 256 (including 0) records
output).
440 IF ((DGTC*MULC)+(DGTB*MULB)+DGTA)=255 THEN
DGTC=LPC:DGTB=LPB:DGTA=LPA
450 NEXT DGTA
460 NEXT DGTB
470 NEXT DGTC
480 NEXT MAJOR
490 CLOSE
500 PRINT "***** FINISHED FILE CREATION *****"
510 REM Character data (0-15):-
520 DATA 16,182,40,34,134,66,64,54,0,2,4,192,88,160,72,76
530 REM Constants for OCTAL:-
540 DATA 512,7,7,3,8,64
550 REM Constants for DECIMAL:-
560 DATA 768,9,9,2,10,100
570 REM Constants for HEXADECIMAL:-
580 DATA 256,15,15,1,16,256

```

Fig. 4 Basic Program

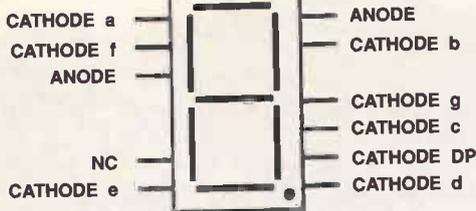


Fig.5 Display Pinouts

BUYLINES

The 7-segment display is available from MAPLIN (Telephone 0702 554161), order code FR36P. Other types may be suitable - check the pin connections with Figure 5.

The switch used in the prototype is marked RS, but may be available from other suppliers. MAPLIN can supply a switch with suitable action, but it will not fit on the PCB.

For a pre-programmed EPROM, send a cheque for £6 to: Daniel Brook, 119 Hale Drive, Mill Hill, London NW7 3EJ.

PARTS LIST

RESISTORS (All 1/4 Watt, 5% or better)

- R1,6,7 10k (3 OFF)
- R2-5,8-14 1k (11 OFF)

CAPACITORS


- C1 2n2
- C2 100n

SEMICONDUCTORS

- IC1 NE555
- IC2 4017BE
- IC3 Programmed EPROM 2764 (not CMOS)
- Q1-3 BC547 (3 OFF)
- DISP1-3 common anode 7seg display (3 OFF)

MISCELLANEOUS

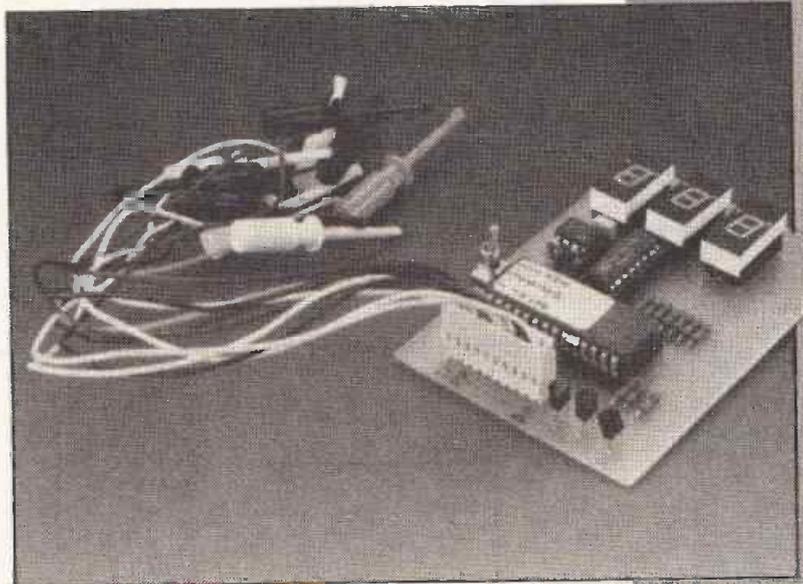- SW1 SPDT Toggle switch ON-OFF-ON (See text)
- CON1 10 WAY PCB mount plug (If required)
- PCB, IC sockets, probe clips, wire, plug to suit CON1, display filter, case



- LEDs 3mm or 5mm red or green 6p each, yellow 11p each, High intensity red, green or yellow, 5mm 30p each
- Cable ties 1p each, £5.95 per 1000, £49.50 per 10,000
- Stepping motor 4 phase 12V 7.5 step - 50 ohms £8.95
- SAA1087 stepping motor driver chip £3.85
- FM Transmitter kit, good quality sound, £8.80
- High quality photo resist copper clad epoxy glass boards
- single sided double sided
- 3/4 inches £0.95 £1.07
- 4/8 inches £2.40 £2.68
- 6x12 inches £5.37
- 12x12 inches £10.85

- Resistor jumbo pack 25000, 1/4 and 1/2W resistors our choice of values and size, will be mainly in boxes or rolls of 1000, 2000 and 5000 of one type £25.00
- Qwerty keyboard, 58 key good quality switches, new £5.00
- Qwerty keyboard with serial output, no data (used) £6.00
- Polyester capacitors, box type, 22.5mm lead pitch
- 1µf 250V dc 20p each, 15p 100+ , 10p 1000+ , 2.2µf 250V dc 30p each, 20p 100+ , 15p 1000+ , 3.3µf 100V dc 30p each, 20p 100+ , 15p 1000+ , 1µf 50V bipolar electrolytic axial leads, 15p each, 7.5p 1000+ , 0.22µf 250v polyester axial leads, 15p each, 100+ 7.5p each
- Philips 123 series solid aluminum axial leads, 33µf 10V & 2.2µf 40V 40p each, 25p 100+
- Multilayer AVX ceramic capacitors, all 5mm pitch, 100V 100p, 150p, 220p, 10 000p (10n)
- 10p each, 5p 100+ , 3.5p 1000+
- Wetwyn W23 9W 120 ohm 35p each, 20p 100+ 680 ohm 2W metal film resistor, 4p 100+ , 2p 1000+ , 10p 1000+
- Solid carbon resistors, very low inductance, ideal for RF circuits, 370mm 2W, 68ohm 2W 25p each, 15p each 100+ , we have a range of 0.25W, 0.5W, 1W and 2W solid carbon resistors - please send SAE for list
- Intelligent 4 digit alphanumeric (5x7 dot 0.145") red LED display, 12 pin 0.6 inch wide package, Siemens type DLR1414 £2.50 each, £2.00 30+ , data sheets £1.00
- AMD 27256-3 Eproms £2.00 each, £1.25 100+
- DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each, 40p 100+

- #### Rechargeable Batteries
- AA (HP7) 500MAH £0.99
 - AA 700MAH £1.95
 - C 2AH with solder tags £3.80
 - D 4AH with solder tags £4.86
 - 1/2AA with solder tags £1.55
 - AAA (HP16) 180MAH £1.75
 - AA 800MAH with solder tags £1.55
 - C (HP11) 1.8AH £2.20
 - D (HP2) 1.2AH £2.60
 - PP3 3V 110MAH £4.95
 - Sub C with solder tags £2.50
 - 1/3AA with tags (Philips CTV) £1.95
 - Standard charger, charges 4 AA cells in 5 hours or 4Cs or 4Ds in 14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time) £5.95
 - High power charger, as above but charges the Cs and Ds in 5 hours, AA, Cs and Ds must be charged in 2s or 4s £10.95

- #### MODEMS
- V22/V22bis IBM PC internal full length card modem, BT approved, can be set to com 1 or 2, 1200/2400 baud with software and manual, not Hayes compatible, made by Plessey £55.00
 - V32 9600 baud and 4800 baud GEC Plessey telecom external modem, model 9832, Hayes compatible and BT approved, with auto call, protocols and V34 remote + local diagnostics. It does not work on slower speed, V22/1200 baud etc and needs 1 internal dip switch to be switched on to select Hayes commands. It comes with a 100+ page comprehensive AA size manual. An all together brilliant machine for only £239+ VAT = £233.83

- #### Special offers - please check for availability
- F cells 32dia x 87mm £3.85
 - F cell with solder tags 1.2V £4.30
 - 42mm x 16mm dia, 1.2V £1.45
 - Stick of 4 171mm x 18mm dia, with red & black leads 4V £5.95
 - 4 cell battery 94mm x 25mm dia, (1/2C cells) £3.50
 - Computer grade capacitors with screw terminals, 38000µf 20V £2.50, 87000µf 10V £1.95, 68000µf 15V £2.95, 10000µf 18V £1.50
 - 7 segment common anode led display, 12mm £0.45
 - LM2931AT 5.0 low drop out 5V regulator TO220 package £0.85
 - 7812 and 7812 12V 1A regulators £20.00 per 100
 - LM337N TO3 case variable regulators £1.80
 - 100+ £1.10
 - BE250 P channel mosfet 45p, 8C559 transistor per 100 £3.95
 - £10.00 per 100
 - Used 8748 Microcontroller £3.50
 - SL952 UHF Limiting amplifier LC 15 surface mounting package with data sheet £1.95
 - AM27502 £1.25 each; 80p 100+ , CD4007UB £1.00 10p 100+ , 5p 1000+
 - TV Mains switch, 4A double pole with momentary contacts for remote control, pack of 10 £3.95
 - box of 60 £18.95
 - DC-DC converter, Reliability model, V12P5, 12V in 5V 200mA out, 300V input to output, isolation with data, £4.95 each or pack of 10 = £39.50
 - Hour counter used 7 digit 240V ac 50Hz £1.45
 - Resistor pack 2500 resistors 1/8-2W 50 different values £8.95

- All products advertised are new and unused unless otherwise stated.
- Wide range of CMOS TTL 74HC 74F Linear Transistor kits, rechargeable batteries, capacitors, tools etc. always in stock
- Please add 95p towards P&P VAT included in all prices

IPG ELECTRONICS
276-278 Chatsworth Road
Chesterfield S40 2BH
Access Visa Orders
(0246) 211202
Callers welcome

HENRY'S

NEW STOCKS AND SPECIAL OFFERS

- #### ASTEC SW mode power supply
- Three pin mains socket input, on/off switch, Output +5 volt 3.75 amp, +12 volt 1.5 amp, -12 volt 0.4 amp, 115-230 V AC input, Size 7.0 x 5.3 x 2.5 ins with circuit. **£12.95** incl VAT

- #### 'POCKET TEST INSTRUMENTS' (with case) Prices incl VAT
- 135 Satellite Signal Finder, FS + Compass £29.95
 - 1085 Digital Lux Meter - 3 Ranges £61.00
 - 120N Sound Level Meter - 2 Ranges £45.00
 - 200A 20MHz to 200 MHz, 2 Range Free Counter £104.50
 - 555 Sine/Sq, 20 Hz to 150 KHz, Audio Gen, Switch Freq £47.95
 - 50 Digital Capacitance Meter upto 2000 mid £51.00
 - KDMM, IR and Dip, 6 Ranges 1.5 to 250 MHz £82.00
 - V225V, VHS Video Head Tester £38.95
 - M205, Component Tester - Add to any Scope £41.00
 - 1000µf 50V Electrolytic Capacitor, 0/300A, 0/600V, 0/1Kohm SPECIAL PURCHASE £25.95
 - 285, 0/2000 amp AC Clamp - Add to Dmm £15.95
 - 202, 0/200/2000 Amp AC/DC Version £33.95
 - 320P, Waller Type Digital Multimeter SPECIAL PURCHASE £21.95

- #### LCR DIGITAL METER Pocket size Instrument
- 3 1/2 digit LCD, 20 ranges.
 - 7 Capacitance, 0/200 mid
 - 6 Inductance, 0/200H
 - 7 Resistance 0/200 M ohm
 - £69.95** incl VAT
 - with leads and battery

- #### TL34
- 33 Range 3 1/2 digit mm 24mm Large Display
FEATURES: 5 Capacitance ranges, 6 resistance ranges to 20M ohm Diode and transistor test, AC/DC volts ranges, 5 ranges AC/DC current to 20 amps. With leads, battery and instructions **£25.95** incl VAT
- #### TL3400
- 31 range 3 1/2 digit mm with 25mm Large Display
FEATURES: 4 Capacitance ranges, AC/DC volts, AC/DC current to 20 amps, 6 resistance ranges to 40M ohm Diode test, Continuity test, Logic checker with buzzer, Auto range frequency counter, Peak hold button, Temperature test. **£39.95** incl VAT

- #### IN STOCK AUDIO-ELECTRONICS
- (Details in colour catalogue and supplements)
- #### FULL RANGE OF TEST INSTRUMENTS -
- Scopes
 - Counters
 - Power Supplies
 - Generators
 - Meters
 - Homeg
 - Metax
 - Blackstar
 - Testlab
 - Thurley
 - Thandar
- #### SECURITY AND COMMUNICATIONS -
- Alarms
 - Lighting
 - Detectors
 - Intercomms
 - Doorphones
 - CCTV and CB Radio
- #### AUDIO EQUIPMENT -
- For Public Address
 - Hi-Power Car Systems
 - Disc and Hi-Fi
 - Speakers
 - Amplifiers
 - Mics
 - Effects etc
- #### COMPONENTS AND TOOLS - Large Range inc.
- Fans
 - Large Value Caps
 - Relays
 - Transistors
- #### ACCESSORIES -
- For TV
 - Video
 - Hi-Fi
 - Telephones
 - CB etc etc.


Open 8 days a week for callers and telephone orders
UK Cont/Post/Ins £2.05
Post Free any two items

COLOUR CATALOGUE with supplements
Send £4 (UK) £5 (overseas)
£2 for callers
FREE updates for your 91/92 catalogue send large SAE (34p stamp)
FREE catalogues with trade prices for trade and education - write or fax.

HENRY'S 404 Edgware Rd, London W2 1ED
Instruments, Audio, Equipment 071-724 3564
Security, CCTV, Communications 071-724 0323
Components, Service Aids 071-723 1008
QUANTITY, EXPORT AND EDUCATION DISCOUNTS,
OFFICIAL ORDER SALES Tel: 071-258 1831 Fax: 071-724 0322

The ETI Line

A hybrid line amplifier by Jeff Macaulay

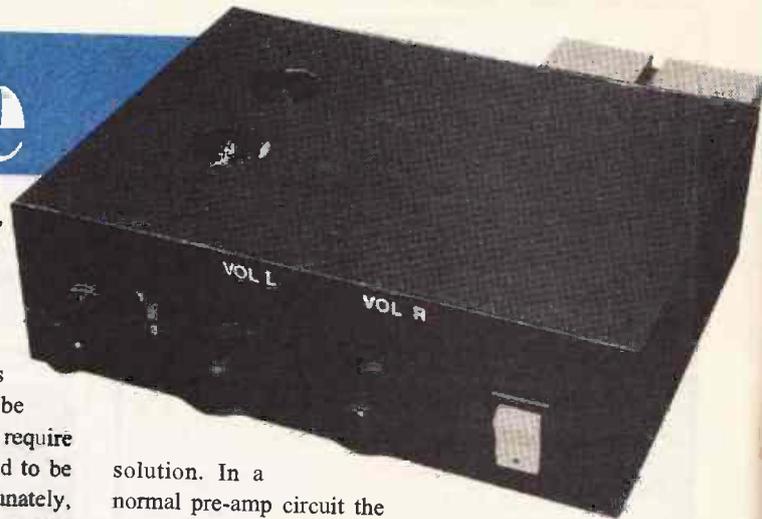

With the rapid demise of vinyl records the role of the preamplifier in an audio system is being re-evaluated. Most sources currently available and those likely to be encountered in the future are 'flat'. That is to say they require no frequency response equalisation but merely need to be matched to the power amplifier's input. Unfortunately, speaking from experience, I have yet to find two sources with the same output level or impedance characteristics.

Output levels can vary from 50mV or so to 1V, a twenty to one range. Moreover the electronics providing the signal most definitely work better when fed into a high impedance. Even CD players operate better into such a load since the now

solution. In a normal pre-amp circuit the line level amp is already in evidence. However most of these are not 'state of the art' and this fact prompted the design described here.

Before I delve too deeply into the actual mechanics of the circuit it is useful to look at the problem in more detail and the solutions used. First let's really get down to basics. I have

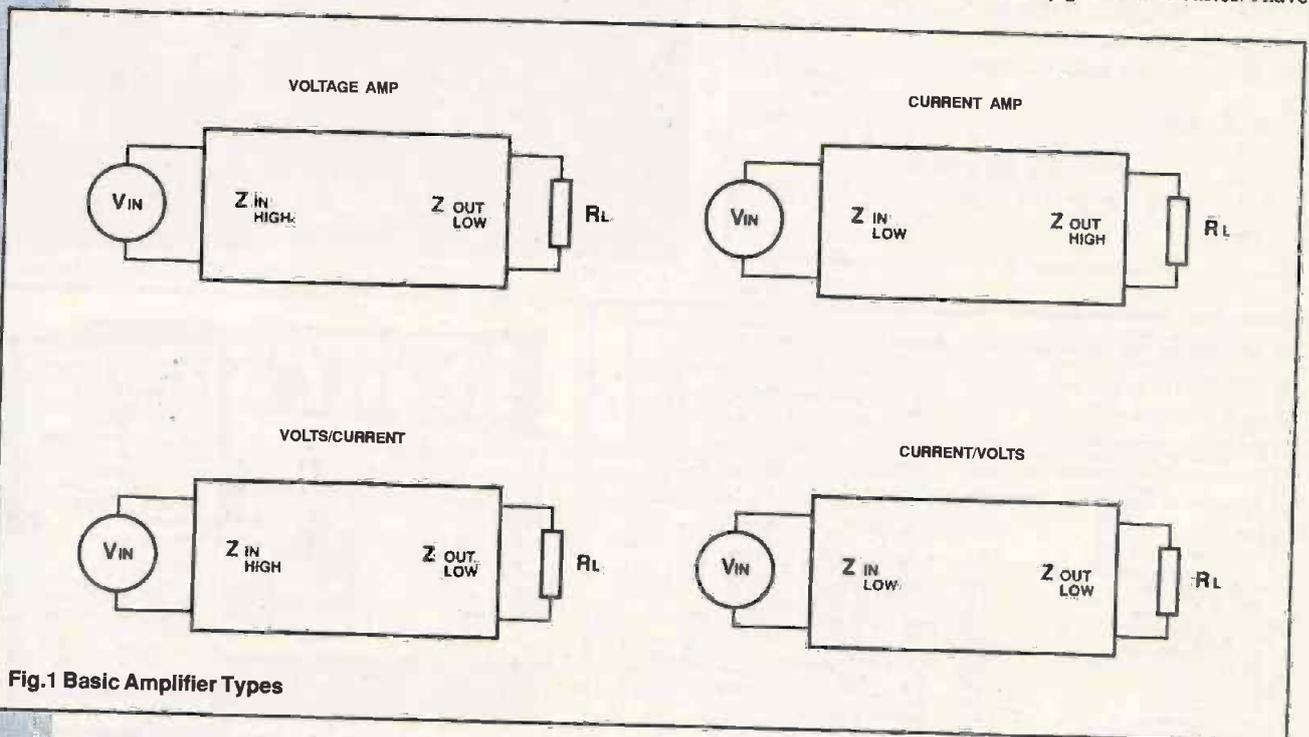


Fig.1 Basic Amplifier Types

traditional 10k passive pot can upset the operating mode of the final op-amp in the player. Shifting the output into class B with it's associated distortion.

With this in mind the question arises, how can one mix and match these sources with the existing power amps without compromising the input signal? The simplest solution is to produce a really high quality line level stage with switched gain and a high input impedance. At the output end of the circuit we require both a low impedance drive and a high overload level for driving the amp.

Placing a high impedance pot between the source and amp can provide an increase in performance but only when the signal level is already adequate.

Furthermore a pot in this position will mean that the signal to noise ratio of the output will depend on the slider position. The separate line amp is an altogether better

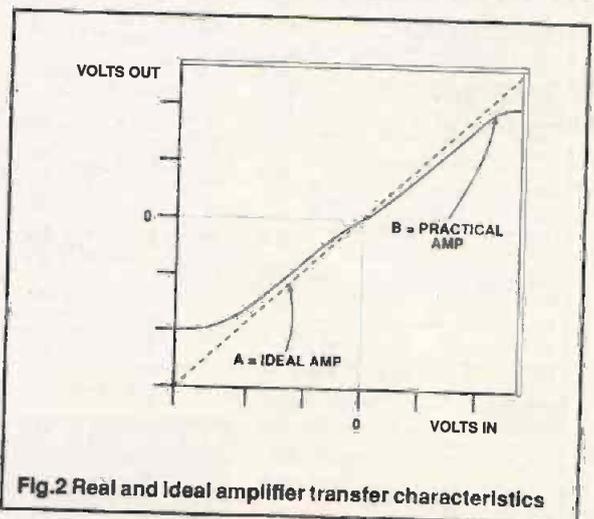


Fig.2 Real and Ideal amplifier transfer characteristics

PROJECT

written on this topic before but it bears repeating. An amplifier, regardless of the technology employed produces an enlarged copy of the electrical signal presented to it's input. To do this it modulates an external power supply and thus doesn't contravene the laws of physics.

In actual fact there are only four basic types of amplifier and these are shown in Figure 1. The difference between them is defined by their input and output impedances. Figure 1 shows the possibilities as black boxes. Figure 1a shows the voltage amplifier. In order not to load the input voltage provided by the source the input impedance must be as high as possible, preferably infinite. On the output end we want a voltage output which is independent of the load impedance. This requires zero output impedance.

Figure 1b shows a current amplifier. Here we are unconcerned with the voltage provided by the source but we need to take maximum current from it. In consequence the input impedance must be very low, preferably zero.

Turning to the output we need here to provide a current output independent of the load impedance. For this reason the output impedance must be high, preferably infinitely so.

The other two amp types shown are rather oddities but very useful nonetheless. Figure 1c shows a voltage to current converter, high input and output impedances whilst Figure 1d shows the opposite. A current to voltage converter. Here the input impedance is low as well as the output impedance.

For our application we need Figure 1a. A voltage amplifier. Figure 2 shows the ideal input output characteristics of such an amp. As you might expect this is a straight line whose slope is proportional to the voltage gain. Curve b gives a more realistic transfer characteristic which gently curves. What can be done to minimise the non linearity? First we can restrict the output voltage to small level. As John Linsley-Hood once remarked in these pages a small enough section of any curve approaches a straight line. The curve assumes a class A output stage. If we were to operate in class B the non linearity would increase with decreasing signal level.

Curve B also illustrates the linearity conundrum faced by designers. If we restrict the output level sufficiently distortion reduces approximately in proportion. Theoretically with zero out we have zero distortion. However although this is a sure fire way of reducing non linearity of all kinds it leads us into unacceptable noise

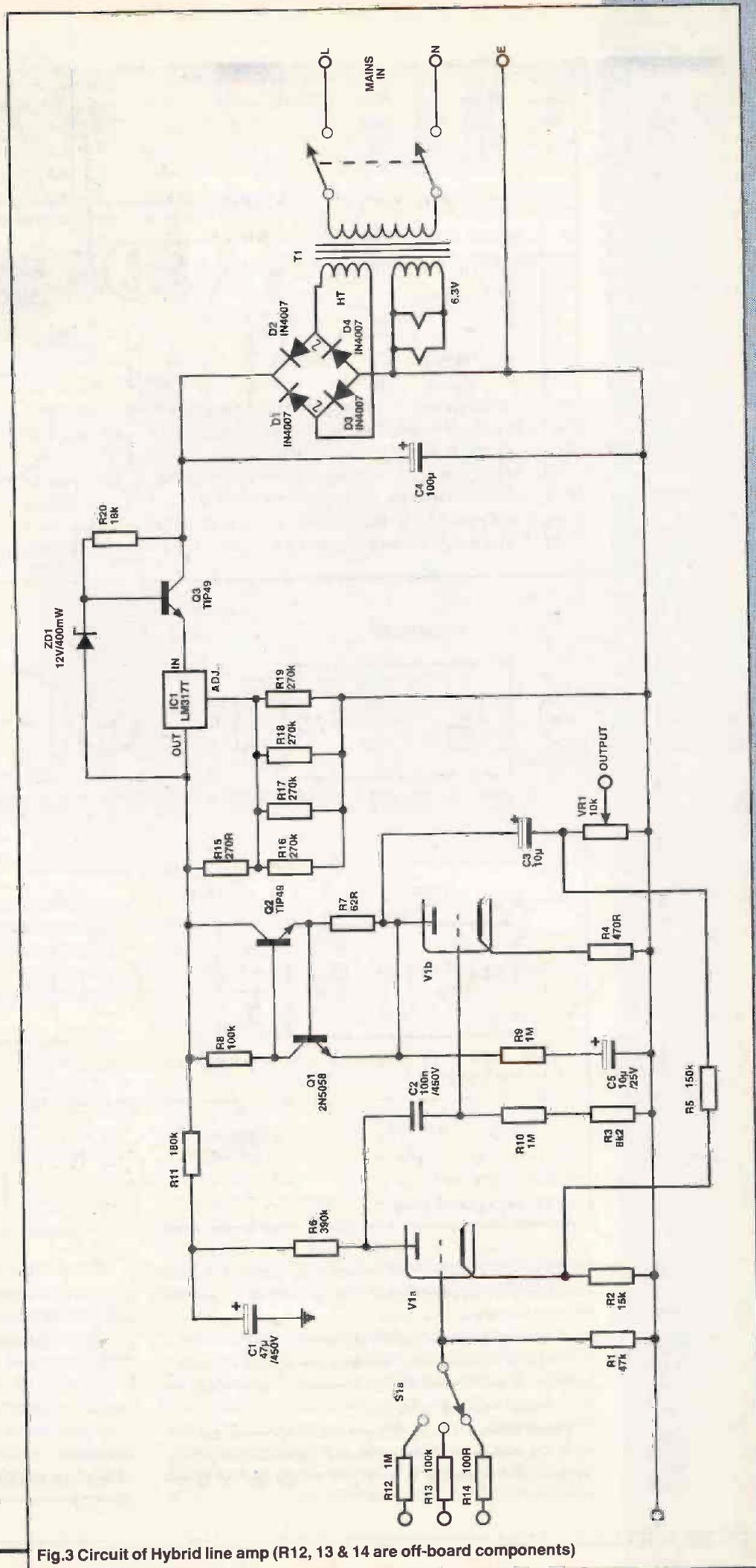


Fig.3 Circuit of Hybrid line amp (R12, 13 & 14 are off-board components)

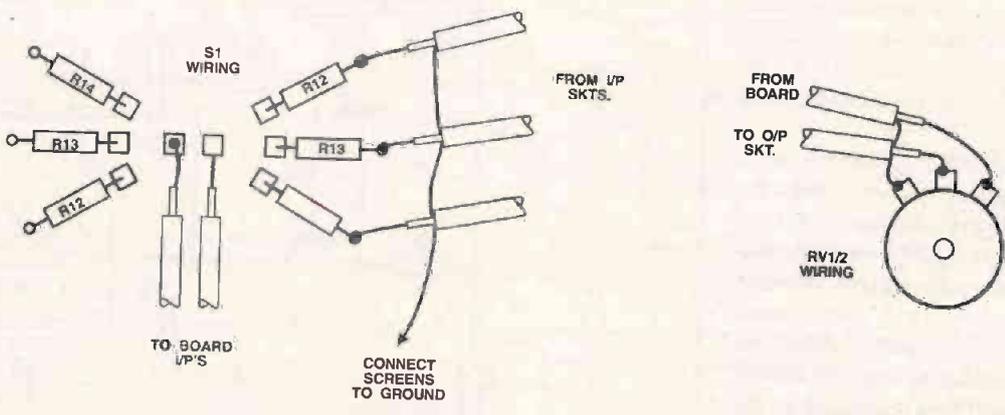
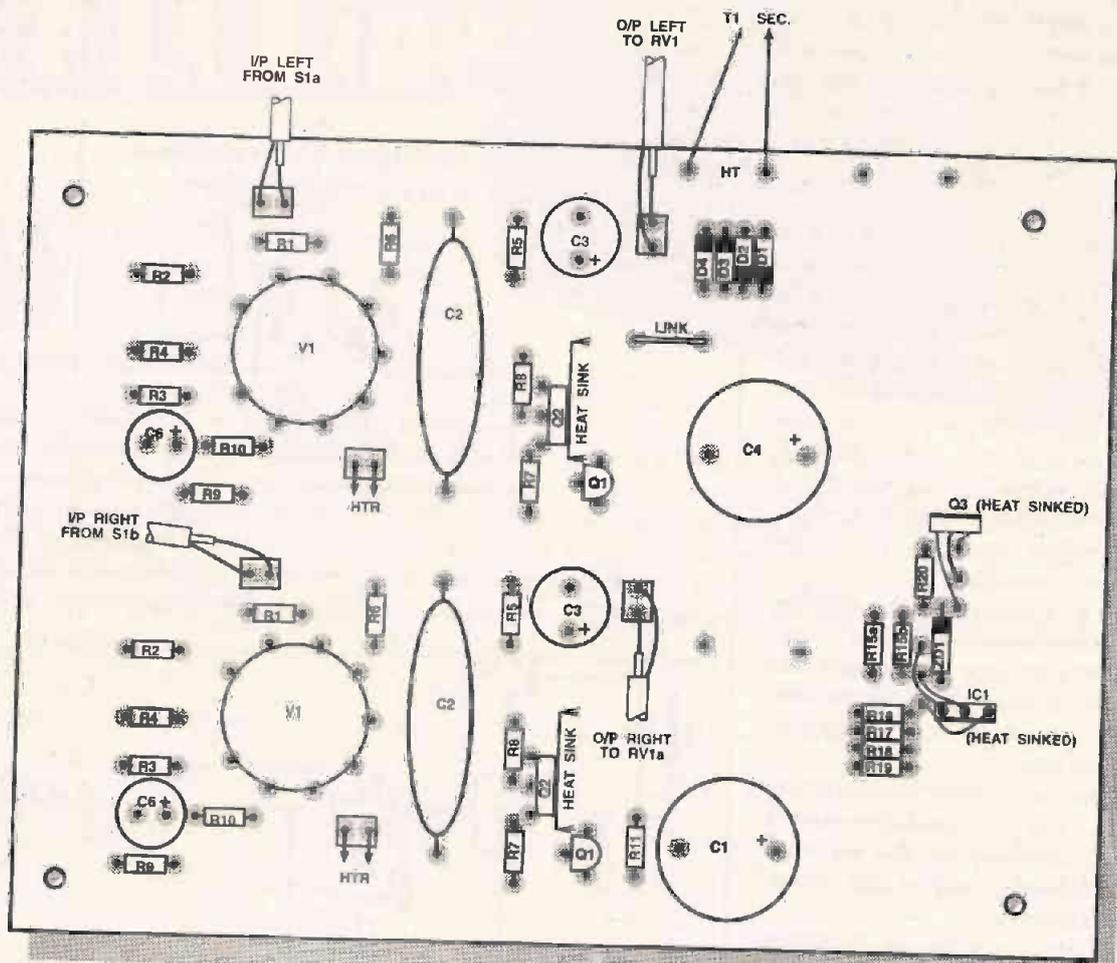


Fig.4 Component Overlay

levels. An alternative is to build an amplifier capable of huge signal excursions. This achieves the same results by the back door, so to speak.

This is essentially the reason that a high overload ratio is of vital importance when seeking to design for maximum linearity. Too often this aspect of design is relegated to the back burner and high overall linearity is sought by other means. In particular the overuse of negative feedback. Feedback has been given a bad name in some quarters recently. Certainly if an attempt is made to rescue a poor design by this means it is possible to run into difficulties.

If on the other hand the design is made linear to start with and has an adequate bandwidth negative feedback will improve matters both objectively and subjectively.

Another factor which has an important bearing on the final performance of any amp is the power supply to which it is attached. If the voltage level varies with the drive level, sadly a common occurrence, the transfer characteristic can look more like an ellipse than a straight line with attendant dire sound. Again, if ripple, RF noise on the supply line are allowed to reach the output the sonic consequences are disastrous.

Please note nothing which I have described involves any form of metaphysics, super components, grain orientated wire, just simple physics! Having described the problem I will now present my solution. I don't believe that it's the ultimate circuit, there's simply no such thing but it's the best sounding line amp that I've ever designed or used. The basis for the circuit is a single dual triode valve. I've used one per channel.

The particular valve features a low anode impedance, wide frequency response and large signal swings at adequate current for the application in mind.

The circuit is shown in Figure 3 of one channel, the other being identical. Being a valve circuit it uses a high operating voltage. This need not be dangerous providing that simple safety rules are applied. I'll come back to this aspect of things later in the article. The circuit acts as a super buffer with high input impedance and programmable gain via SW1. Output impedance is less than 100R so that long cables can be driven with ease.

The circuit configuration employed uses a series feedback connected pair of triodes. In many ways this is a classic valve circuit dating back to the 1940's. It's virtues are many with very few vices. Implemented with high performance RF triodes it has a bandwidth that extends well above 20kHz before the application of feedback. Distortion levels, with a standard line level output, 775mV, are well below 0.1%, again before the application of negative feedback.

One of these days the semiconductor industry will provide a device with the virtues of a valve. The average valve is ten times more linear than an equivalent transistor stage and has an input impedance of approximately 100 Megohms. Although VFET characteristics come closest they haven't yet cracked the problem of large input capacitances which tends to negate the advantages of the high DC input impedances of these devices. All this leaves the valve as the premier device for this particular application and this is why they are being used.


Astute readers will however notice the presence of semiconductor devices in this circuit. These are not however used directly in the signal path but are rather employed in a supporting role. To provide the output stage with a constant current source. This enables the amplifier to provide far larger symmetrical signal swings than would be available with a simple resistor anode load. If a resistor were to be used it would appear to be in parallel with the load reducing the signal swing.

The Circuit

Turning to Figure 3 the signals are applied to the voltage divider resistors selected by SW1. The reasoning behind this is to provide the amp with a uniform input voltage of about 70mV. Regardless of the actual input level. R1 maintains the input impedance constant at 100k. Signals from the input attenuator are directly applied to the grid of V1a. One half of the dual triode. This is operated with a low level of anode current to ensure that the overall feedback loop connected from the output to the cathode resistor R2 won't load the output stage unduly.

The valve is used in the common cathode mode, analogous to the common emitter mode in a transistor amplifier and thus gives a fair measure of voltage gain. The valve operates very much like a J-FET. To provide correct bias the grid voltage need to be negative with respect to the cathode. In fact the stage will only work correctly when the grid is negative, distortion levels increase dramatically if the grid is taken positive. Luckily setting the correct anode current can be achieved by selecting an appropriate sized resistor for the cathode circuit, R2.

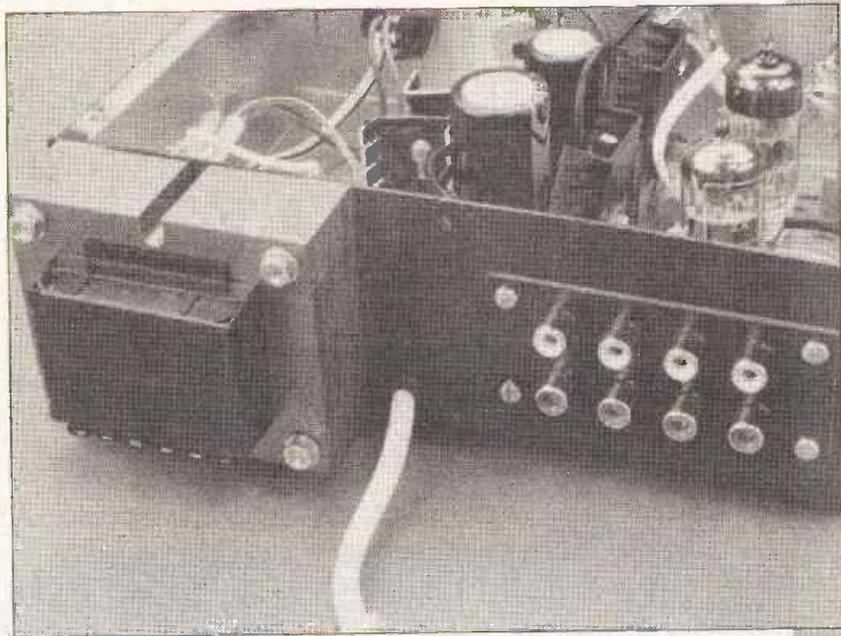The output signal from the valve is generated across R6. R11 and C1 form a very effective decoupling filter which removes any noise and ripple from the supply voltage. The signal is coupled to the other stage, built around V1b, via the



DC blocking capacitor C2. A good quality polypropylene type is used here for its wide frequency response.

The output stage itself requires some explaining. As I mentioned earlier I decided to use a constant current source for the anode load of this stage. This prevents loading but it also defines the anode current. Because of device to device variation it is necessary to provide a DC feedback loop around the stage. This is the function of R10, R3 and R9. R10 and R11 provide shunt feedback to stabilise the operating point. C5 completely removes any AC signals fed back by R9 by decoupling the junction of R10 and R3 to ground.

The anode current of V1b is set by the resistor R7 which is in the constant current source formed by Q1, Q2, R7 and R8. The operation of this is quite conventional. On switch on, R8 biases Q2 hard on. Its collector current increases until approximately 0.6V is generated across R7. This then turns on Q1 which stabilises the current to a level defined by $0.6/R7$ amps. With the component values used this is 12mA/channel.

Lastly the amp's output voltage is supplied to the outside world via the DC blocking capacitor C3 to RV1. Overall negative feedback is applied to the cathode of V1a via R5. The voltage gain being set by the ratio of R5 to R2.

Power Supply

The most difficult area of valve design is the power supply. Apart from the fact that some of the electrolytics are

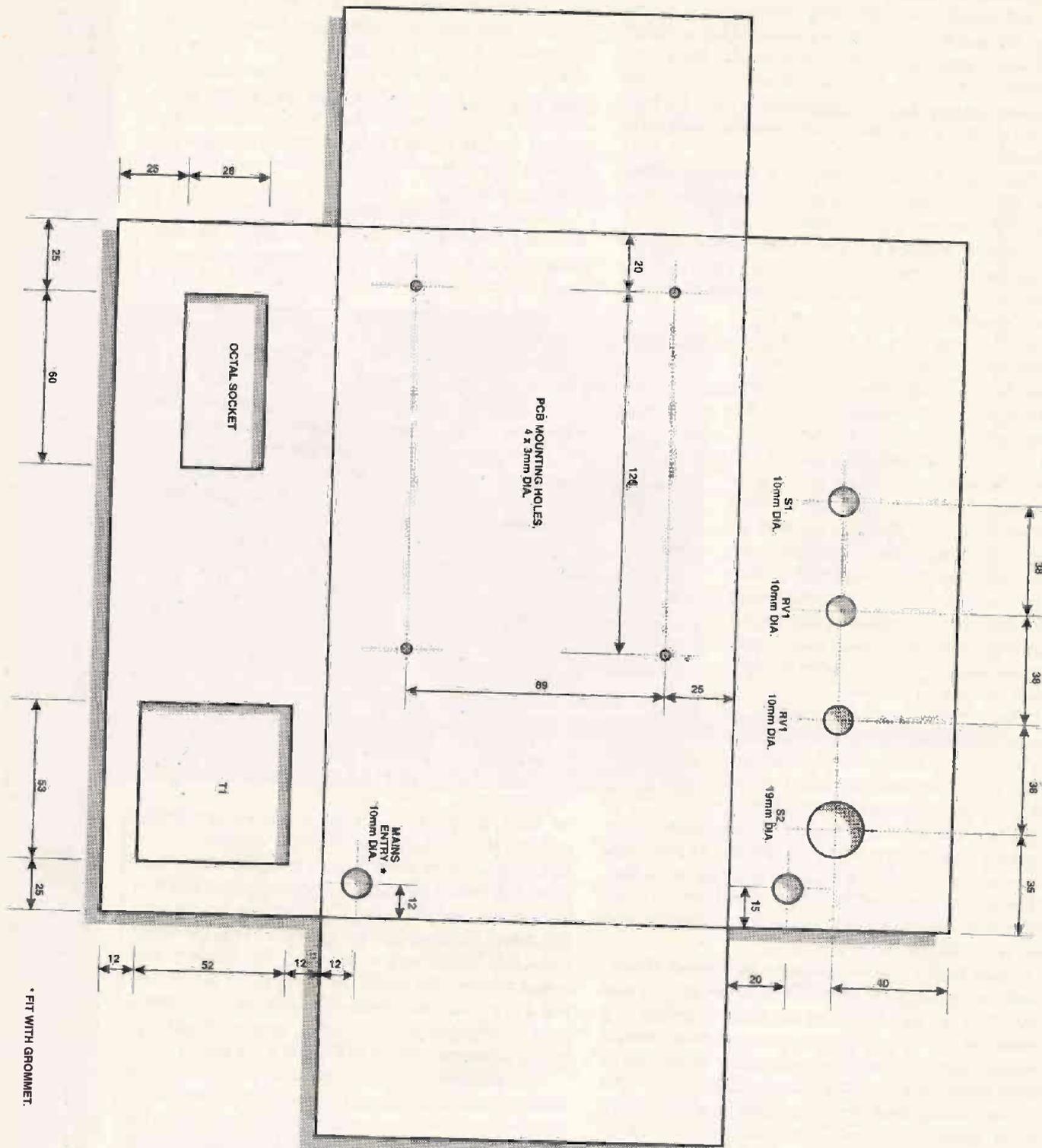


Fig.5 Case drilling detail

hard to find resistors tend to pose a problem as well. At high voltages surprisingly large levels of power dissipation occur. Put into simple language things can tend to get hot!

Large electrolytics of adequate voltage rating are thin on the ground and so other methods of smoothing the power supply must be sought. The most obvious answer is to use a floating voltage regulator of the LM317 type. These work well but have a low output impedance which requires care while commissioning. Furthermore they cannot stand more than 40V between the input and output terminals and will

turn themselves off if adequate heatsinking is not provided.

The circuit diagram of the power supply is also shown in Figure 3. Here the HT voltage is full wave rectified by D1-4 and the resulting raw DC is smoothed by C4. To avoid overdissipation of IC1, the 317T regulator, Q3 is used as a 'power dump'. This component is biased from ZD1 and R21 and prevents high voltages being applied across the chip. Advantage is taken of the current flow through R14 to provide on indication via LED D9. IC1 needs to float and this is achieved by utilising the fact that the adjust pin must be

1.25V below the output for proper operation.

R15 sets the quiescent current of IC1 at approximately 4mA and the adjust pin is lifted of ground by this current flowing through the parallel resistors R16 to R19.

Construction And Testing

Most of the components are mounted on the PCB panel, see overlay. The most important thing to watch is that you have inserted the electrolytics the correct way round. If anything is liable to produce problems a reversed electrolytic will. None of the other components require comment. Just follow the overlay. The two Q1's and IC1 require mounting on a heatsink. Small finned types are used for these devices. Note the two way PCB mounting plugs. Use Veropins for the HT input as these are added to the circuit last

Having completed the board attention can be turned to the mechanical aspects of the design. Figure 5 shows the mechanical drilling detail of the unit. Once the holes have been drilled the case can be finished to taste. I chose to spray mine matt black. Legends were then applied with white rub down lettering and fixed with clear spray varnish. Both the latter items were obtained from my local art shop.

Having finished the case the inevitable self adhesive rubber feet were applied to the bottom of the case. Now the real work can commence! Fit the transformer and PCB into the case and also the pots and sockets.

Note that the heater and input wiring, shown in Figure 6 terminate in 2 way PCB plugs that mate with the sockets on the board. In the first instance don't wire the HT leads in.

The reason is that to ensure safety it is important that the

valve heaters light up. With the valves on the HT supply is rapidly discharged by the circuit's current when the power is removed. Otherwise a potentially dangerous HT voltage will linger across C4.

Testing the unit consists of two stages. First with the HT supply from T1 and the mains earth lead unconnected switch on the unit. After a few seconds the valve heaters should start to glow. If not switch off and find your wiring error. Assuming all is well here the second stage of the testing can commence. First a number precautions. When testing the HT rail switch your testmeter to a range which will clearly show 300V DC. Ensure that you have made the connection between system earth and the case. Lodge the negative testmeter probe securely in the case so that it makes a connection with the metal work. Second always keep one arm behind your back when testing.

Attach the HT leads to the Veropins on the board. Take a deep breath and switch on. Take the positive test lead and hold it against the metal tab of IC1. Keep the other hand behind your back! You should read 300V, a few volts either way is inconsequential. remove your test lead and switch off. Reapplying it to IC1 tab should show the voltage decaying rapidly. In any event don't touch the circuit until this voltage has decayed below 100V.

Having got this far the next stage is to actually try the unit out. First connect the mains earth, your inputs and outputs.

Power up again. After a few seconds warm up sweet music should emanate from your system! If you have wired the circuit up as described no further problems should be encountered and all that remains is to enjoy!

PARTS LIST

RESISTORS


R1	47k
R2	15k
R3	8k2
R4	470R
R5	150k
R6	390k
R7	62R
R8	100k
R9,10	1M
R11	180k
R12	1M
R13	100k
R14	100R
R15	270R
R16,17,18,19	270k
R20	18k
RV1,2	10k log pots

CAPACITORS

C1	47 μ 450V
C2	100 μ 1000V
C3	10 μ 450V
C4	100 μ 450V
C5	10 μ 25V

SEMICONDUCTORS

V1	CV2493
Q1	2N5058
Q2,3	TIP49
D1-4	1N4007
IC1	LM317T
ZD1	12V/400mW
D5	Panel LED

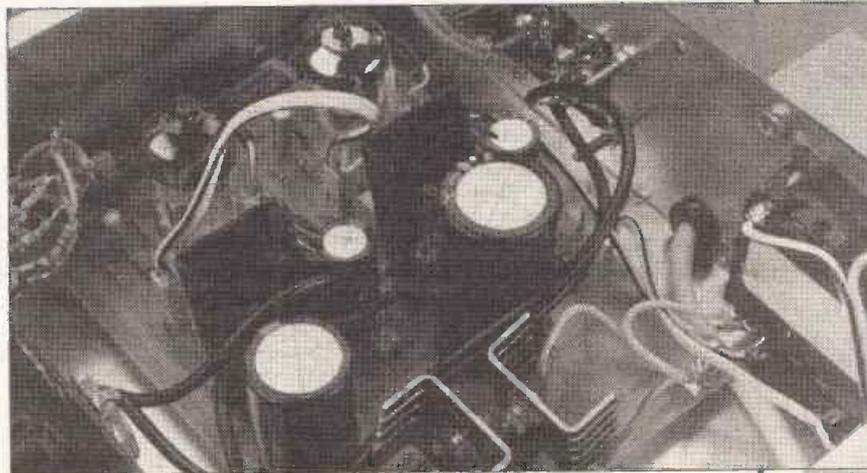

MISCELLANEOUS

B9A PCB valve base
4 small heatsinks
T1 220V 150mA 6V 1A secondary transformer
PCB
Case
4P 3W rotary switch
Knobs
Octal phono socket

Specifications

The following measurements were made on the prototype unit, loaded with a 10k pot.
S/N ratio -101dB unweighted below 775mV (input shorted)
THD <0.005% at 1kHz, 775mV out
Frequency response -3dB at 0.8Hz and 150kHz
Clipping level +39.5dB above 775mV (74V RMS)

Automatic Audio Response Measuring System

2

PROJECT

Ralph Mantel continues his report from Germany on a convenient way to check the response from a loudspeaker.

The complete circuit diagram from MEPEG is shown in Fig.8a and b. The complete system, with the exception of the mains transformer, is constructed on a single eurocard.

As stated MEPEG uses a parallel (centronics) port and the loudspeaker output of the PC. The loudspeaker output is used solely for generating the measuring signal. All control functions are achieved solely through the parallel port.

Construction

The construction of the boards should not cause any problems, only the connections to the PC tone generator should perhaps be described in some detail.

The loudspeaker output from the PC tone generator should be connected to the 9 pin Sub D socket on the rear of

HOW IT WORKS

IC1 is a low noise input amplifier with an amplification of 1 for normal use and 30 for microphone use. The amplification is automatically controlled by the computer via relay RLY2. R5, ZD1 and ZD2 provide over voltage protection up to 70V. Direct connection of the microphone is via a XLR socket. The microphone used is an asymmetrical electret condenser microphone which requires a DC voltage to function correctly. This voltage is fed to the microphone via R1/R2. Inserting the microphone plug in the XLR socket on input 2 shorts pin 1 with pin 2 via a bridge in the socket. The signal therefore is imposed on the DC supply line and fed to the input amplifier. If required, input one can be used to observe the microphone input signal using an oscilloscope. Resistor RCal is used as a calibration resistor during impedance measurements (e.g. TH/SM parameters) and is connected using RLY1 automatically by the computer when required.

IC2/IC3 form a zero loss full way rectifier which rectifies the AC input voltage to a DC voltage. IC2 works as an inverting one way rectifier, the negative half waves of the input signal being short circuited by D4. The circuit is then extended using IC3 as a sumator. Here, the negative half wave and the 'complete' signal voltage via R13 are added together to form our full way rectifier. The resulting DC voltage is integrated by C10 and using P2 this DC voltage is set to the same level as the effective input signal level. The selection of the OPs is very critical as the circuit must work over a large voltage range linearly and without loss. The accuracy of this circuit is dependent primarily on the diodes used and the slew rate of the OPs. IC4 works as a normal inverter. IC5 and IC6 work as an V/F converter (Voltage/frequency-converter)[6]. The voltage on the inverting input of IC5 is converted into a proportional frequency in the ratio of 1 to 2; i.e. an input of 1000mV would result in a frequency of 2000Hz on pin 3 (output) of IC6. The resolution would be 0.5mV. Pin 3 of IC6 is an 'open collector' and is connected directly to pin 10 on the parallel port. This pin carries 5V under 'no signal' conditions. Every negative pulse (change from +5 to 0) on this pin starts a system interrupt in the computer. The time between two interrupts is exactly the period of the input frequency. The time is measured by the computer using an assembler routine. The computer therefore has the value of the input signal as a proportional frequency (Fig. 9). The advantages of this so called serial A/D conversion are a) the accuracy over a wide range and b) the high resolution (see Table 1) for a relatively low cost.

Measuring signal generation is achieved using the computers internal sound generator. For our circuit the signal to the normal internal loudspeaker is diverted to IC7. The connection is, however, made by RLY5 and only after the system has been switched on. When the measuring system is switched off the loudspeaker is available for normal use by the computer. Both generator outputs carry a DC voltage. The plus pole also carries the generator

square wave signal on top. This square wave is directed through IC7 to IC8. This IC works as a frequency divider and reduces the generator frequency by a factor of 10. This frequency is fed to pin 1 and 13 of IC8 and is used in the frequency range <150Hz. for controlling the Phase Locked Loop (IC9, IC10) i.e. for signal generation. From 150Hz relay RLY3 switches the original frequency back in to pin 14 on IC9. This process is necessary in the lower frequencies in order to obtain a sufficiently high resolution. For example a computer is not able to generate a frequency of say 20.47Hz so this frequency is generated from 204.7Hz divided by 10. IC9 and IC10 work as a Phase Locked Loop (PLL) and form the actual sine wave generation part of the circuit. The detailed function of a PLL cannot be described here. However sufficient to say that IC9 compares the signal from the PC on pin 14 with the signal from IC10 (VCO) on pin 3. According to the frequency difference (phase difference) between these two signals there appears on pin 13 an 'error signal' which is then integrated via a low pass filter (R32, C22, R33) and is used as a control signal for IC10. In other words the square wave signal from the PC fed to pin 14 of IC9 is used to generate a sine wave of the same frequency at pin 2 of IC10. Every frequency change at pin 14 IC9 has an equivalent frequency change at the output of IC10 (pin 2). Further, pin 1 of IC9 contains a 'lock' signal which is used via pin 12 of the parallel port to signal that the PLL is locked on. i.e. a check is made to ensure that the output of IC10 is similar to the input of IC9 (pin 14); if this is not the case, the program gives an error message.

The capacitors on IC10 pins 5 and 6 control the frequency range of the VCO. In the range 20-150Hz both relays are de-energised i.e. C26 is in circuit. In the range 150-1500Hz RLY3 is switched by the PC and C25 is then in use. The other contacts on RLY3 switch the input frequency on pin 14, IC9 as already described. From 1500Hz RLY4 is activated and connects C24 in series with C25 resulting in a drop in the total capacity. By this method the VCO is kept in its optimal voltage range. Trimmers P6 and P7 are used to fine tune the form and symmetry of the sine wave output signal. By careful adjustments it is possible to obtain a distortion figure of <1%. A description of remaining components around IC9 and 10 is not necessary for an understanding of the overall circuit.

The output frequency on pin 2 of IC10 is connected via IC11a to the various outputs. P8 sets the signal amplitude. IC11b via R106 provides a constant current output which is essential for all impedance measurements e.g. Thiele/Small. The output via R106 will generally be used for all other measurements that do not require a powerful output. The power output is achieved using IC12 and can be used for example to directly drive a loudspeaker. Specifications can be seen in Table 1.

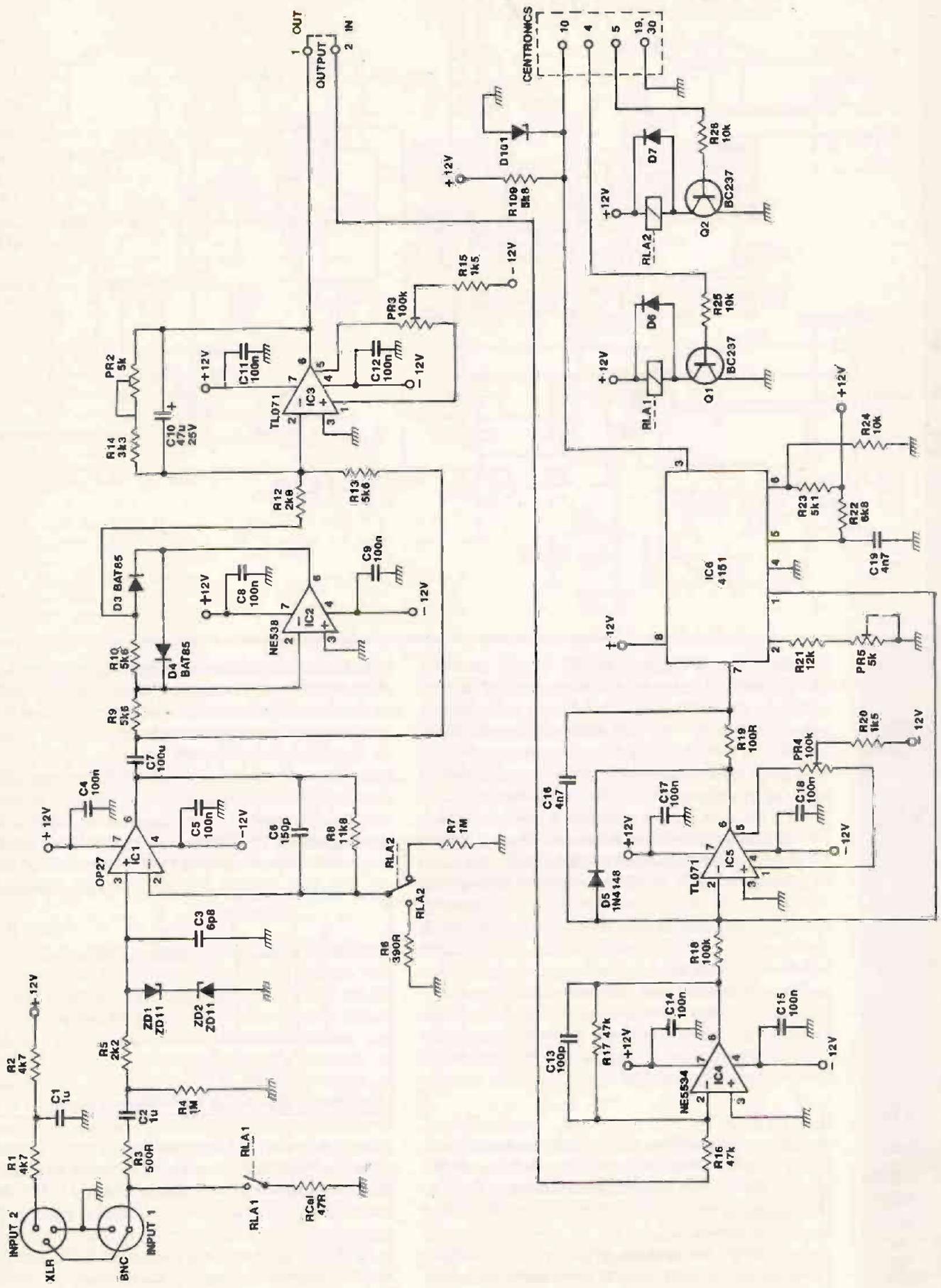


Fig. 8a & b Complete circuit diagram of system

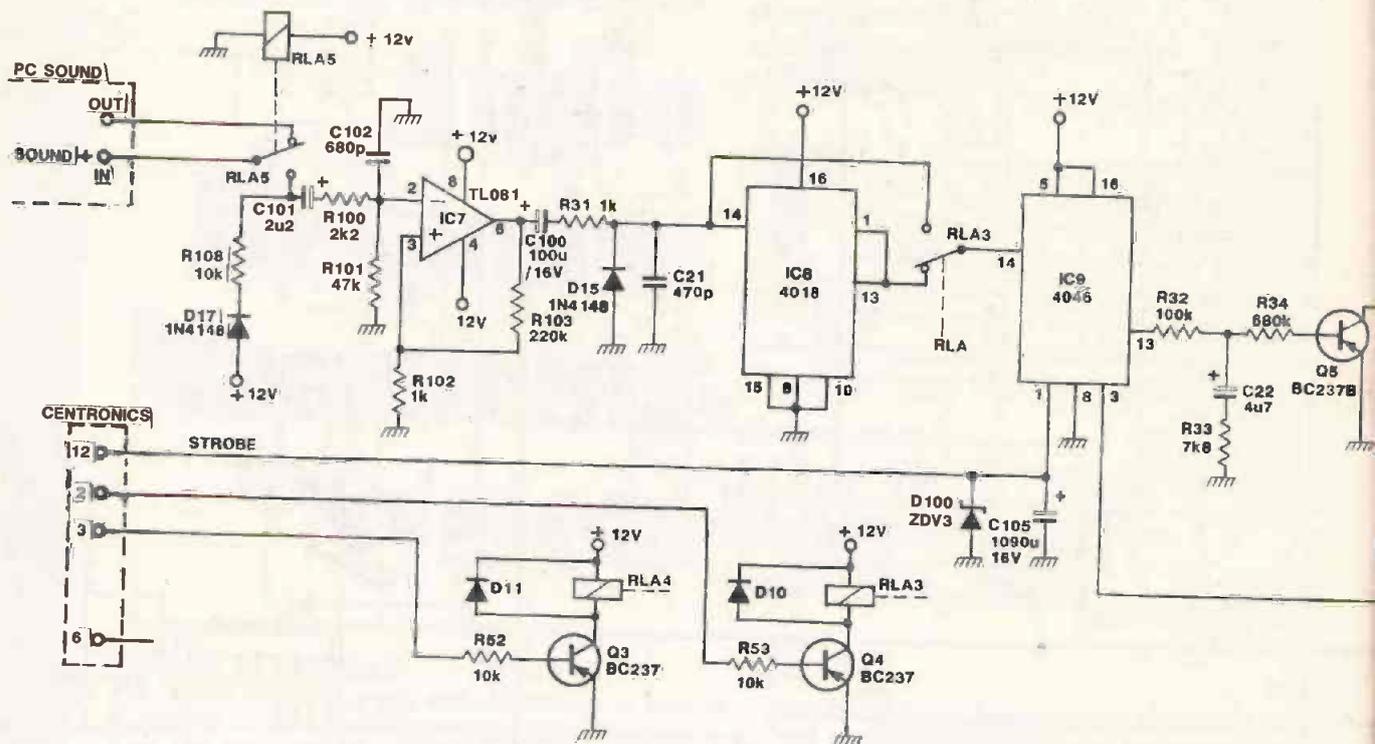


Fig. 8b

the computer as shown in Figure 10. The PC speaker is usually connected to the motherboard via a 4 pin plug. Pin 1 carries the signal (positive pole) and pin 4 is the negative pole. Normally it is a simple matter of de-soldering the positive wire from the loudspeaker and connecting this wire to the Sub D socket. The return connection from the generator card (+out) is only needed when the loudspeaker is to remain in use. If this is the case the connection is then to be made to the de-soldered connection on the speaker as shown in Figure 10. If the speaker plug is not marked + and - the signal carrying pin can easily be determined by connecting one of the wires up and testing to see if the signal generator card functions. If this is not the case simply swap the wires on the speaker connection over and retry. This trial and error method will not damage the circuit.

The connection between MEPEG and the PC is via a 25 pin Sub D plug, i.e. a normal parallel interface configuration. The individual pin connections are shown in Figure 8a/8b.

The connecting cables from the two interfaces should have a maximum length of 2m.

Adjustment

Before any adjustments can be made the circuit board, must be working satisfactorily and be connected to the PC. Also the software must be installed and running on the PC as the program is used in the adjustment process. (See section on software installation).

A voltmeter, oscilloscope and if available distortion measuring equipment are necessary for adjusting the system.

With output 2 connected to input 1 adjustment of PR6 and PR7 can be made. The program must firstly be started with

<MEPEG> and from the main menu <begin> selected. We then arrive in the measuring menu and should then select No. <6 -Voltmeter>. The program then asks :

Do you use measuring microphone(y/n)?

To which you should answer <n>.

If the circuitry is functioning, MEPEG generates a 1kHz signal and the program is in voltmeter mode. If the card is not correctly connected to the PC an error message will most probably appear. The amplitude of the sound wave signal at output 2 is set to 5Vpp using PR8. Trimmer PR7 is set to


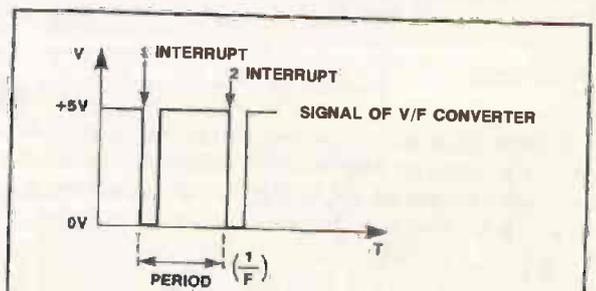


Fig. 9 Input signal as a proportional frequency

midway and using PR6 the signal is adjusted to minimum distortion. If distortion measuring equipment is not available the adjustment must be made 'by eye'. Set PR6 to 200 ohms and using PR7 adjust the wave for optimal symmetry using an oscilloscope.

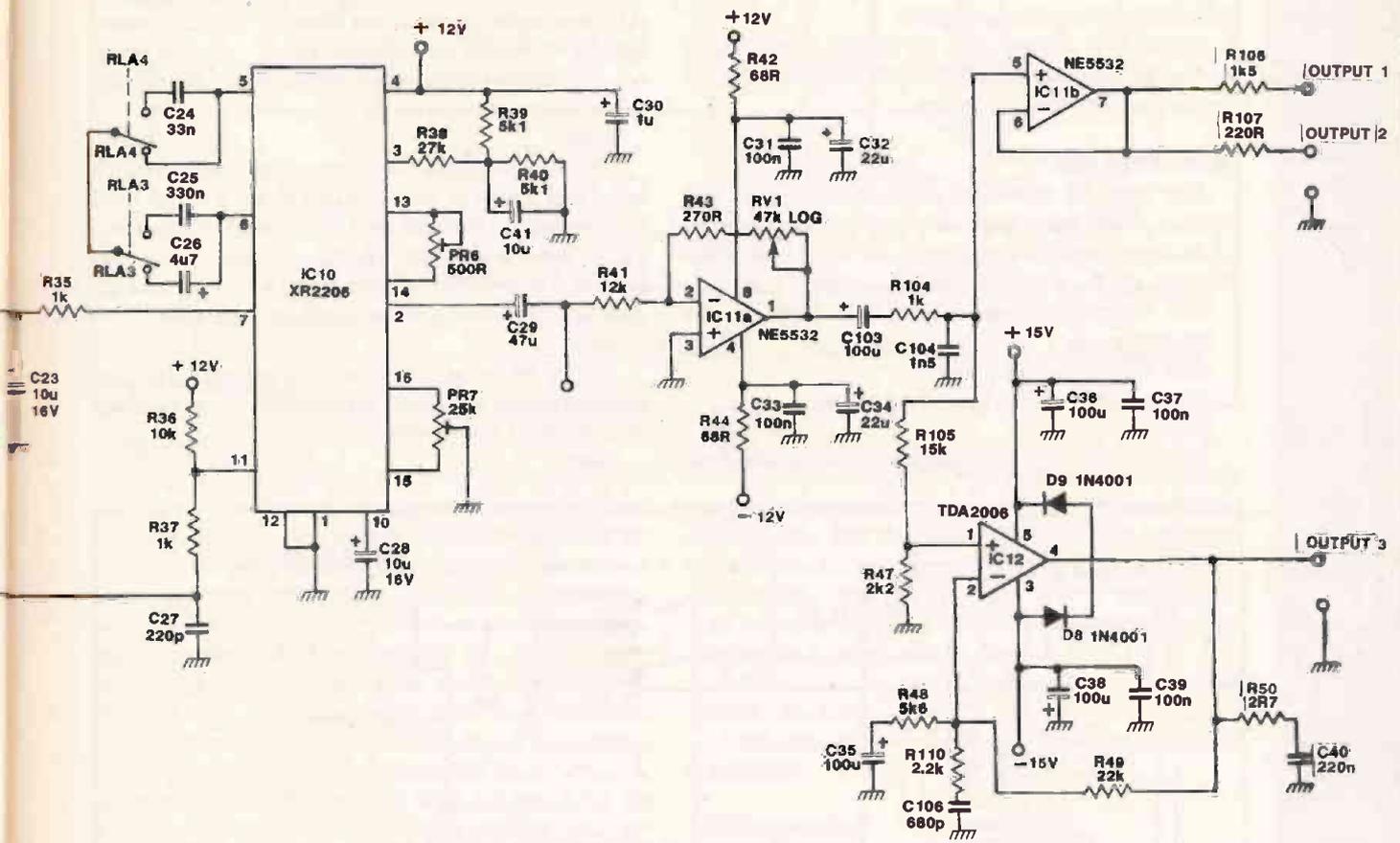With the help of a voltmeter adjust the 1kHz signal on output 2 to 1000mV (output 2 still connected to input 1). Then adjust the output of IC3 to 1000mV DC using PR2. (Remember to change the voltmeter range from AC to DC!).



Now disconnect the generator signal from input 1 and short circuit it to earth. Using PR3 adjust the output of IC3 to 0mV (Offset). The generator output 2 is then again connected to input 1. The generator signal should now be adjusted to 10mV. Now adjust trimmer PR4 until the measuring bar on the screen <Vmess> also shows 10mV. Then using the voltmeter set the generator signal to 4000mV. Then adjust PR5 until the screen measuring bar shows 4000mV. On completion of these adjustments MEPEG is calibrated and ready for use. Now press <Esc> to leave the voltmeter mode and return to the main menu.

Software

No great computer expertise is required to use MEPEG. As mentioned in the introduction the majority of functions are fully automatic, only measuring functions and parameters need be entered by the user. The program catches most errors which occur due to incorrect use or incorrect entries. Problems with the hardware are also detected e.g. measuring beyond the allowed range or PLL not locked on, all of which could lead to inaccurate results. The program works with a temporary store which is able to store up to 30 measured curves and associated data. This temporary store, unlike many other programmes, is held on the Hard/Floppy drive. This has the advantage of not occupying valuable memory and also should the system crash the data is not lost. The temporary store is cleared before and after each session.

The minimum configuration for the use of MEPEG is an IBM* or 100% compatible AT computer running DOS 2.0* or higher with an EGA or VGA graphic card. Colour or monochrome monitors may be used although by colour the

associated graphic card should have at least 128Kb of memory. A parallel interface, LPT1, on port &H378 is also required. If a second interface is available it is possible to measure on LPT1 and print on LPT2. If this is not the case measurement and printing are both via LPT1. The software has been tested on several different IBM compatible computers with the above configuration and should therefore run on most PCs without problem.

- The following files are contained on the original disk;
- Setup.exe** Program to set the hardware configuration
 - Compens.dat** Compensation file for the microphone
 - Ralf.exe** File for main Program
 - Runmepeg.bat** Batch file for system startup
 - Mepeg.exe** Main program

Several demonstrations are also available.

The DOS routine 'Graphics' is used to enable screen hard copies to be printed. Runmepeg.BAT loads 'Graphics' before starting the main program. Hardcopies are therefore available on all printers this routine supports; typically Epson or IBM compatible 9 or 24 pin dot matrix.

Installation

All important settings with regard to hardware and the installation of the software are carried out by the program <SETUP.EXE>. Insert the disk in drive <A> or and start the installation by typing SETUP and pressing 'return'. (For safety reasons only use the original disk for installation purposes !!). The setup program is self explanatory and requires no further explanation. When all the necessary parameters have been entered the system software is automatically installed. 'Setup' suggests <C:\MEPEG> as target

directory, but this can of course be changed by the user. Finally 'setup' writes a further file 'setup.dat' in which all the necessary parameters are stored.

NOTE: it is essential that the SETUP is run before starting the main program. The main program will not function correctly if this is not done.

Main Program

After successful completion of the installation we find ourselves in the chosen target directory. All data operations i.e. the storing and loading of curves are carried out in this directory. The temporary store is also contained in here.

With <Mepeg> we start the main program and come to the main menu.

Main menu Functions

The menu contains the following functions:

Begin

With for Begin a measuring session is started and the

parameters. The requests are clear and require no further explanation. (Function 1-3 ask for a 'reference frequency'. As already explained, using this frequency the system calculates the '0 Decibel line reference value'). After all entries are complete the measurement procedure starts. The user can follow the measurement on the screen.

Load

<L> for load, shows the contents of the current directory and allows files to be loaded into the temporary store. Only MEPEG files i.e. files with the *.MPG extension are shown. The last curve to be loaded using this command is the 'actual' curve and is immediately available for use. i.e. it does not have to be recovered from the temporary store again.

Save

<S> for Save, saves curves and their associated data to the current directory. File names can be specified by the user and are given the *.MPG extension.

Quit

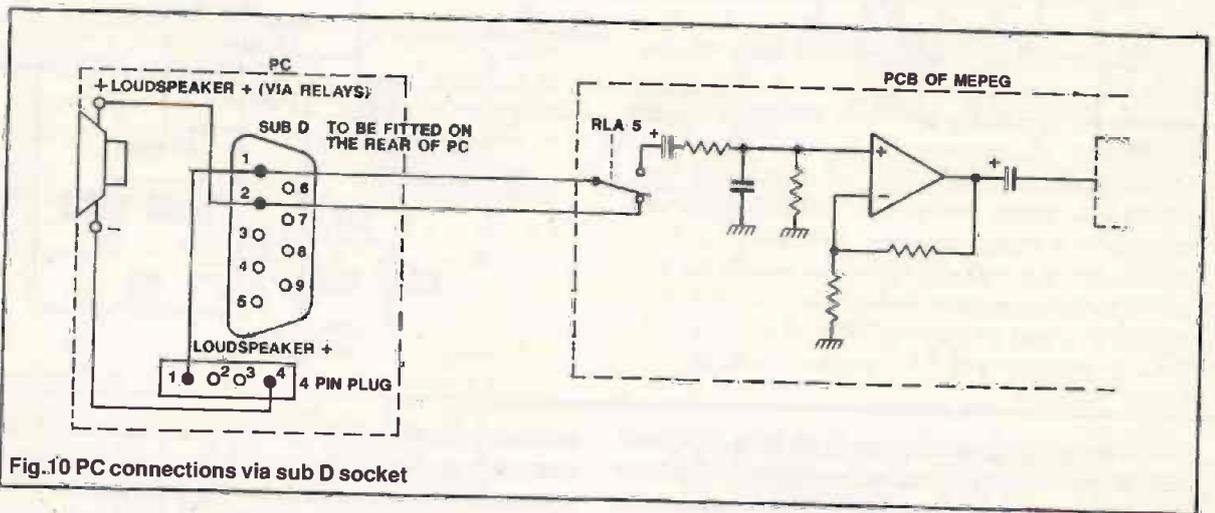


Fig.10 PC connections via sub D socket

measuring menu appears in which measuring functions can be selected and parameters entered. If the temporary store contains a curve the following message is given:

Do you want to enter new Parameters (y/n)

If this is answered with <N> then the existing functions, parameters and reference values are kept and used in the new session. By a series of measurements (e.g. sound level measurement) this elevates the need to enter the values every time.

Then the measuring procedure is immediately started.

If the question is answered with <Y> then the user can enter new parameters etc.

The measuring menu then appears offering the following functions:

1-Level measurement	
2-Spl measurement	Sound level measurement
3-Nearfield measurement	Near field measurement
4-Impedance measurement	Impedance measurement
5-Th/Sm measurement	Thiele/Small Parameter measurement
6-Voltmeter	Voltmeter mode
7-Generator	Computer controlled sine wave generator

The individual measurement functions and their properties have already been described in part 1. Depending on which function is chosen the user is asked for certain

<Q> for Quit to exit MEPEG. The contents of the temporary store are deleted and all unsaved curves are lost. MEPEG does however check if the user wants to save any data before leaving the program!!

Plot diagram

<P> for Plot diagram plots a curve on the screen. The curve can be either from the last measurement or from disk. On the lower right of the screen is a small menu with the following options:

Copy

<C> for Copy sends a hard copy of the current screen to the printer

Text

<T> for Text enables the user to add a comment to the diagram (up to 28 characters).

Res

<R> for Resolution enables the scale of the Y axis to be changed. See Table 1 for the various possibilities

Gerv

<G> for Get curve allows different curves to be loaded from the temporary store either into the current diagram, for comparison purposes. If several curves are shown in the same diagram the parameters shown apply the last curve to be loaded.

Esc

With Esc the current measurement functions can be interrupted i.e. to leave the graphic mode.

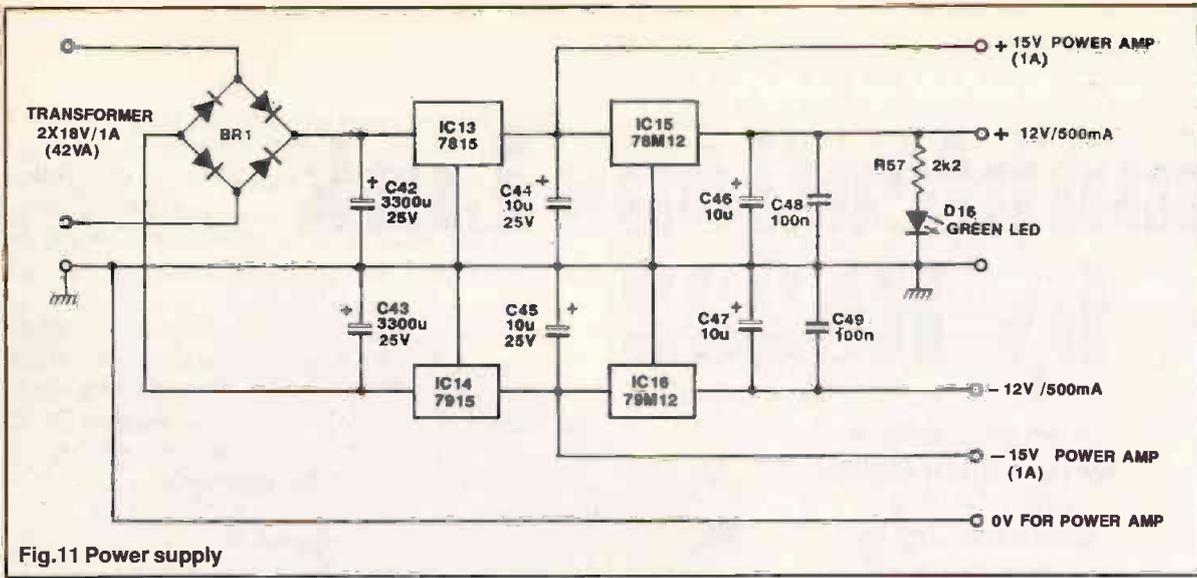


Fig.11 Power supply

Difference

Using <D> for Difference it is possible to calculate the difference between curves currently in the temporary store. The available curves are shown in a window on the left of the screen and can be selected using the cursor keys. The selected curves are shown in the window on the right. The difference calculation is only possible with curves which have been measured under the same conditions i.e. with the same measuring functions and parameters. During this process the original cuves remain unchanged. After every difference calculation the user is asked if he wishes to save the resulting curve in the temporary store. If the answer is yes the user is prompted for a name for the curve. If the user answers no, the cuve is nevertheless saved in the temporary store under the filename "Nname".

Average

<A> for Average calculates the average of the curves currently in the temporary store. The usage is the same as for 'Difference'.

Octave

<O> for 1/3 octave calculates the 1/3 octave response curve from a sound level or level curve measured in High resolution mode. During this process the original curve remains unchanged. Again, see 'difference' for use of this function.

Get curve

<G> for Get curve loads a chosen curve from the Temporary Store. This replaces the curve currently in use. (NB. the curves in the temporary store are saved in the current directory with the file extension *.STR. In the event of a possible system crash the files can be found here !!).

New

<N> for New deletes all the curves currently in memory and the temporary store and re-reads the compen.dat and setup.dat files. This function is used primarily by a "Renew" of the temporary store. A renew is automatically requested by the programm when there are more than 30 curves in the store. Before this is carried out there is of course the possiility of saving one or more curves.

* IBM is the recognised Trademark of International Business Machines

* MS-DOS is the recognised trademark of Microsoft Corporation

Bibliography:

Low-Frequency Loudspeaker Assesment by Nearfield Sound-Pressure Measurement: D.B.Keele jr. in: Journal of the Audio Engineering Society (JAES), Vol.22, No.3/1974.

Loudspeaker Measurements and Their Relationship to Listeners Preferences: F.E.Toole Part1, in JAES, Vol.34, Nr.4/1986; Part2, in JAES, Vol.34, No.5/1986.

Direct-Radiator Loudspeaker System Analysis: R.H.Small in: JAES, No.6/1972.

Hifi-Lautsprecher: H.Sahm, Franzis Verlag.

Frequenzweichen fnr Hifi-Lautsprecher: J.Panzer Franzis Verlag.

Applicationsschrift zum U/F-Umsetzer 4151: Raytheon Company, USA.

Halbleiter-Schaltungstechnik: U.Tietze/Ch.Schenk, 9 Auflage, S.954 ff, Springer Verlag.

Acknowledgement: Thank you to C.A Taylor for his support through this whole project.



CRICKLEWOOD ELECTRONICS

CRICKLEWOOD ELECTRONICS LTD, 40 CRICKLEWOOD BROADWAY, LONDON NW 2 3ET
Tel: 081 452 0161 Fax: 081 208 1441


SEND NOW FOR THE **CRICKLEWOOD ELECTRONICS** COMPONENT CATALOGUE
 ONE OF THE BEST RANGES AVAILABLE

Name.....
 Address.....

Please send me my free copies of Cricklewood Electronics Catalogue

Communications Link by RS232

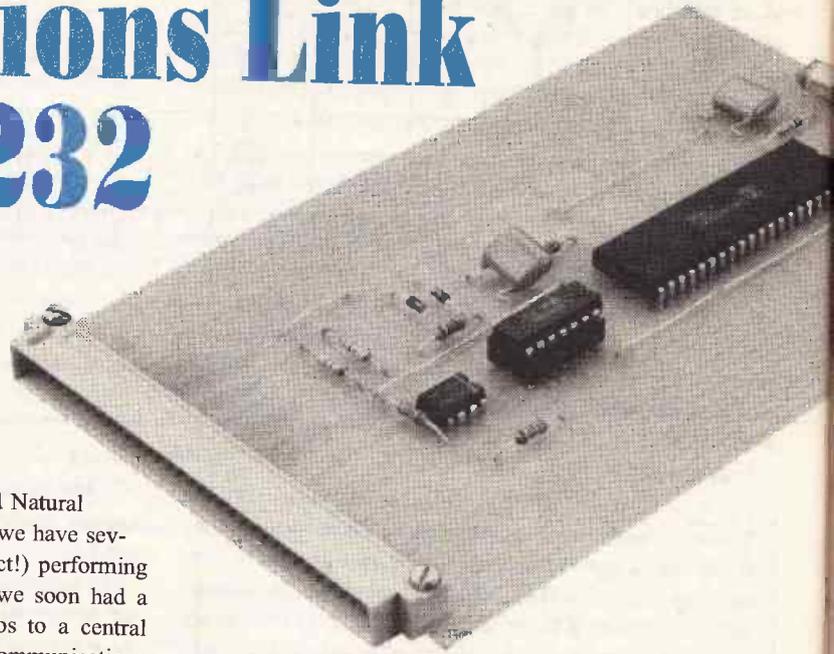*A project where
'Device Shall Speak
Unto Device'.
Commentary by
Keith Garwell*



At the Newchapel Observatory and Natural Sciences Centre, Stoke on Trent, we have several small micros (Dragons in fact!) performing various jobs round the site and we soon had a requirement to pass data from these micros to a central machine. Unfortunately the micros had no communications interface.

Due to my general interest in electronics I often thought it would be useful if I could couple my own IBM PC look-alike to other equipment. To digitisers, controllers, and because of an interest in amateur theatre even to a theatre

not too large. There was then no need to modify anything and the serial interface is well protected, electrically, from accidents. It also has the advantage that only three wires are needed between the PC and the device in question. From this came the idea of adopting a standard for myself and the Centre and producing a 'standard' interface board. The end product enables 240 bytes of data per second to be sent in either direction.

The serial interface is known as RS232 and there is a complete official specification for it. Which is perhaps a roundabout way of saying it's quite popular and there are many instances of it. It also means that, in this case, whatever applies to an IBM PC or look-alike will also apply to any other computer fitted with this interface.

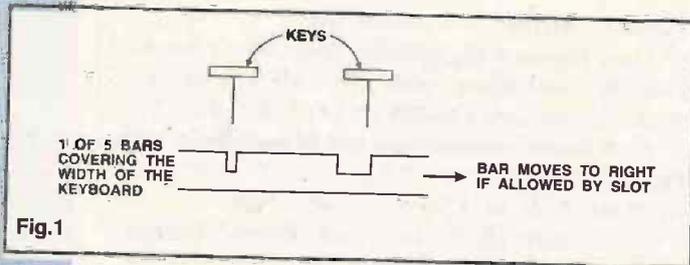


Fig.1

lighting system.

However to me the PC is an expensive device and I am rather loath (though a competent computer engineer) to meddle with or modify its innards.

A certain amount of cogitation later I concluded that the serial interface on the PC was the best means of connection provided that the speed at which data had to be passed was

The Early Years

The origin of RS232 is ancient and goes back to the days when the only means of communication was by way of a morse key, sounder, battery, and a single wire with earth return. For further information see any wild west film!

With the diversification of business the morse key became too slow and so ways of speeding up communication

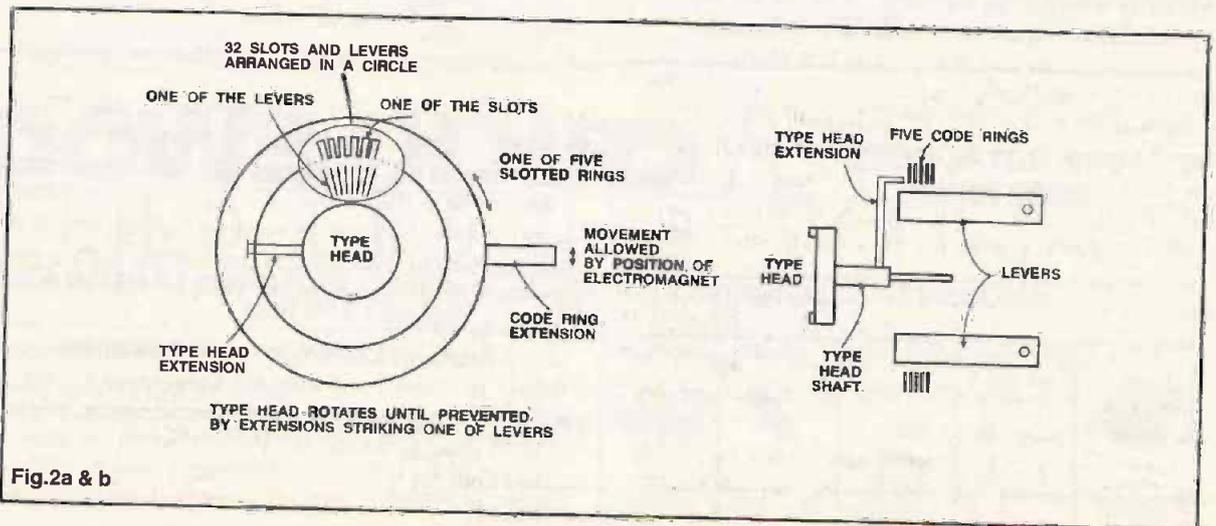


Fig.2a & b

developed. In the first instance the morse dots and dashes were punched onto paper tape by operators working together. The paper tape was then used by mechanical senders to transmit the information at a much higher speed, still via a single wire and earth return. At the far end the sounder was replaced by a mechanical device which wrote or punched the data onto paper tape again.

Meanwhile back at the ranch the typewriter had appeared. So why couldn't the pressing of keys at one end of a line be made to operate the type at the far end. Eventually it could and became the world famous Creed teleprinter.

Apart from a pair of contacts at the sending end and an electromagnet at the receiving end the device was entirely mechanical. The mechanics in principle were relatively simple but in practice exceedingly intricate. Very briefly, at the sending end pressing a key released five bars running the

punctuation two special shift characters were used. After sending one of these characters all the printed characters changed until the second character was sent.

Later to increase the distance over which messages could be sent the single battery system was replaced by a dual positive and negative supply with change over contacts at the transmitter and a polarized electromagnet at the receiver. Other enhancements included electromagnetic repeaters and with the advent of amplifiers, voice frequency keying.

The teleprinter was the mainstay of the telegram service in the 40s printing onto a sticky paper tape which could be stuck onto a telegram form.

During WW2 a page printing version was very popular with the meteorological service as used by the forces. An American version was produced known as a Teletype which employed a different mechanical system (presumably to avoid infringement of Creed patents). It took up less table space than the Creed machine and became popular with early computer systems particularly as the computer operators machine.

The start bit, 5 data bits, and stop bit system of serial data transmission was soon adopted as a standard. To extend the print repertoire the number of data bits was extended, and error detection added. Thus was borne today's RS232.

Today's RS232

This is a more sophisticated system having more data bits to extend the available codes plus if required a bit intended to enable errors in transmission and reception to be detected.

As before the start bit is just that, it indicates the start of the character and can be followed by either 5, 6, 7 or 8 data bits. These in turn can optionally be followed by the error detection bit, known as the parity bit. Finally either 1, 1.5 or 2 stop bits. One and a half bits sounds odd but in fact means a duration of 1.5 bits.

Now let's look at an example in further detail. The letter C can be represented by the binary code 0100011. The data is sent in reverse order to how it would normally be written ie with the least significant bit first. A dual voltage supply is used and the quiescent condition is negative. Figure 3 shows

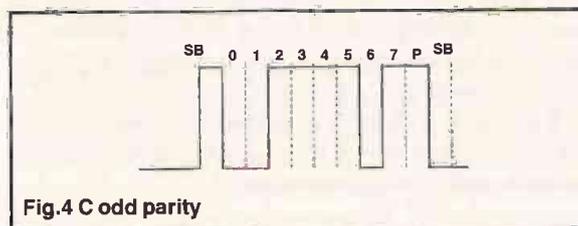


Fig.4 C odd parity

how the C would appear on an oscilloscope in the normal sense with positive at the top using eight bits, one stop bit and without parity. (Let's not complicate the issue too soon).

The start bit is thus positive going followed by the first data bit which is a 1 and is thus negative. Then the next data bit a 1 also. Next the four zeroes as positive then bit 7 a 0 and finally the stop bit which returns the line to its original condition as negative.

Just to sidetrack the issue for a moment. Why did I choose 0100011 to represent the letter C? Answer. For the very good reason that the most commonly used character code is the ASCII code. In which the initials stand for American Standard Code for Information Interchange. Strictly speaking this code is a seven bit code but is frequently used as an

Fig.3 C no parity

length of the keyboard and which carried a code for each key one of which is shown in Figure 1. The final position of the ends of the bars corresponded to the key code. Following this action a set of cams rotated once causing the code at the bar ends to be applied to a pair of contacts in sequence. Thus five consecutive makes/breaks identified the character. The completed rotation of the camshaft restored the bars to their original position ready for the next key to be pressed.

To complete the sequence and to start the mechanism at the far end, before the five codes were sent, a start break was performed. (The contacts at the transmitter were normally closed so that at rest current flowed through the line. This enabled the operators to check that the wire was still intact before sending the message). To ensure the receiver mechanism was always given time to complete its task a delay was inserted between each character by the transmitter equal in duration to at least the length of a data bit. Nowadays known as the stop bits.

At the receiving end an electromagnet responded to the interruptions in the line current. The first break started a camshaft rotating. During this rotation the following five bits of the code either allowed or inhibited a small rotation of five rings. See Figure 2a for the face view and Figure 2b for the side view. The rings had slots on their inner edge which corresponded to the key codes. Because of the rotary movement, at one particular point in the circle the slots all lined up allowing a lever to move outward into the slots. Figure 2b. The lever stopped the type head rotating so that the correct character was aligned with the paper and on the next rotation of the mechanism the character was pressed against the paper. The characters received were thus printed one step behind the characters being sent.

Each character was therefore represented by a code consisting of start bit, five data bits and two stop bits. To allow for all letters of the alphabet plus numbers and

eight bit. The eighth bit being used for special purposes. For instance in the IBM PC and all its look-alikes the eighth bit is used for special characters such as foreign language characters and graphics characters ie. characters used for drawing.

Error detection and parity

With RS232 a parity bit is available and follows the most significant bit of the data. Parity can be either odd or even and it works like this.

The parity bit is generated by the electronics in such a way that the number of ones in the combined data plus parity is either odd or even.

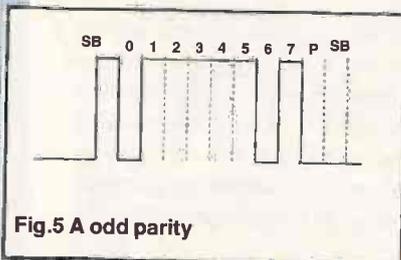


Fig.5 A odd parity

As an example again suppose the letter C is being sent represented by eight bits.

If parity is declared as odd then in the case chosen the ninth bit, the parity bit, would be a 0 ie. in the nine

bits there are 3 ones and the remainder are zeros. See Figure 4.

If the letter A was being sent the parity bit would be a 1 because the eight bit code for A is 01010001 which only has two ones. See Figure 5.

At the receiving end the electronics will count the number of ones in each character as they are received. If parity is odd then the ones count for each complete character received must be odd also. If this is not so then an error signal is given.

Reception And Stop Bits

At the receiver, the electronics will detect the leading edge of the start bit. It then waits for one and a half bit times before strobing the input. The strobe should therefore come exactly in the middle of the first data bit. It then waits for one bit time and strobcs again putting the second strobe in the middle of the second bit and so on as shown in Figure 6. After the 8th strobe the electronics is reset during the stop bit to wait for the next start bit.

It is important to appreciate that although the start bit must not occur before the expiration of the stop bit time ie. there is a minimum delay before the next character - there is no maximum delay.

The stop bit is intended to prevent characters running in to each other and to allow time for the electronics and the line to recover before the next character.

Baud Rates

Although we have just been discussing duration of the pulses or bits the more usual consideration is frequency. RS232 allows for a wide variety, from 100 bits per second to 9600 and the bit rate is termed as so many Baud. After a well known character who was big in data transmission!

The standard Baud rates for RS232 are 110, 150, 300, 600, 1200, 2400, 4800, and 9600. The actual rate at which characters are sent will depend on the Baud rate and the number of bits per character. For instance 1200 Baud, 7 data bits, no parity, and one stop bit will give $1200/9$ or 133 characters per second. 1200 Baud, 8 data bits, parity and 2 stop bits would be $1200/12$ or 100 characters per second.

The shape of the pulses will be distorted by the electrical properties of the connecting line and these in turn will

depend upon the length and type of line. The Baud rate chosen is therefore a trade-off between freedom from errors and the time available for transmission.

There is also a further point of significance, namely the accuracy of timing of the electronics. Consequently RS232 links are usually crystal controlled. From Figure 6 it can be seen that for 8 bits no parity the permissible error before the 8th bit is misread is plus/minus 0.5 after an interval of 8.5 which is 1 in 17 or just under 6%.

Plugs and Sockets

As well as standardising the methods of transmission the plug and socketry is also included in the specification. The standard is a 25 pin D type connector which at the processor is male ie. its a plug. The pin out of which is as follows. (The pins not mentioned are not used).

1. Frame or screen.
2. Tx Transmit, the serial output.
3. Rx Receive, the serial input.
4. RTS Request to send.
5. CTS Clear to send.
6. DSR Data set ready.
7. Signal ground The common line.
8. DCD Data carrier detected.
20. DTR Data terminal ready.
22. RI Ring indicator.

It will be seen from the above that only three connections are actually needed for the data exchange. Pins 2 and 3 data transmit and receive, and pin 7 the common line which is ground, 0 volts, or earth, call it what you will.

The remainder are handshaking signals intended for use principally between a computer and a modem. Modem stands for modulator/demodulator and is a device which at the

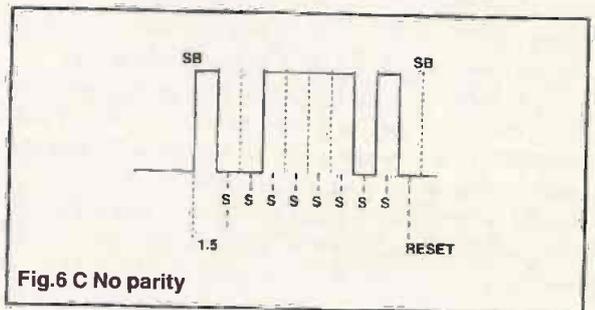


Fig.6 C No parity

sending end converts the DC signals to voice frequencies suitable for sending over a telephone line, radio link etc. That's the modulator. At the receiving end the voice frequencies are converted back to the DC signals. That's the demodulator.

An alternative connector frequently used these days particularly on physically small machines eg. portables, is a 9 pin D type connector. The pin-out is usually as follows.

1. DCD
2. Rx
3. Tx
4. DTR
5. Signal ground
6. DSR
7. RTS
8. CTS
9. RI

The Chips

The chip chosen to convert the parallel to serial data and vice versa is the IM6402, readily available and compatible with industry standards. These devices are known as UARTs ie. Universal Asynchronous Receiver Transmitters. The data bits, commonly known as the word length can be 5, 6, 7 or 8 bits. Parity can be odd, even or none, and there can be one, one and a half or two stop bits. The chip is a 40 pin DIL. As well as its use as a terminal unit for equipment of all sorts it can also be used in conjunction with a microprocessor for which reason it is possible to switch all its output signals to a high impedance state.

Figure 7 shows the pin layout with names and I am sure a quick run through their purpose will do no harm. Starting at pin 1. High level is +5 volts, low level is 0v.

- | | |
|-------|--------------------------------------------------------------------------------------------------------------------------------------|
| 1 | VDD the positive supply 5 volts. |
| 2 | NC not connected. |
| 3 | VSS the negative supply, ground or 0 volts. |
| 4 | RRD Read Register Disable. A high level on this line forces the receiver outputs to a high impedance state. |
| 5-12 | RBR8 to RBR1 the Receive Buffer Register ie. the receiver output. The least significant bit is RBR1. |
| 13 | PE Parity Error a high level on this pin indicates a parity error has been detected. |
| 14 | FE Framing Error a high level indicates an invalid stop bit. |
| 15 | OE Overrun Error a high level indicates receive data not read soon enough. |
| 16 | SFD Status Flags Disable a high level applied to this pin forces the status lines PE, FE, OE, DR and TBRE to a high impedance state. |
| 17 | RRC the Receive Register Clock, this input should be driven at 16 times the Baud rate. |
| 18 | DRR (N) Data Received Reset a low level here clears the receiver output. |
| 19 | DR Data Received a high level indicates a character has been received. |
| 20 | RRI Receive Register Input ie the incoming serial data.
<i>And going back up the other side -</i> |
| 21 | MR Master Reset a high on here resets everything except the receive buffer register. |
| 22 | TBRE Transmit Buffer Register Empty ie ready for the next character. |
| 23 | TBRL (N) Transmit Buffer Register Load a low here transfers data from the input terminals to the buffer register. |
| 24 | TRE Transmitter Register Empty a high indicates data has been sent. |
| 25 | TRO Transmitter Register Output ie. the serial data. |
| 26-33 | TBR1 to TBR8 Transmit buffer register ie. input to transmitter. |
| 34 | CRL Control Register Load a high level here loads the control register. |
| 35 | PI Parity Inhibit a high level selects no parity. |
| 36 | SBS Stop Bit Select a high selects 1.5 stop bits for 5 bit data and 2 stop bits for all others. A low selects 1 stop bit. |
| 37&38 | CLS2 and CLS1 Character Length Select. The appropriate combination of levels on these pins select 5, 6, 7 or 8 data bits. |
| 39 | EPE Even Parity Enable a high level selects even parity providing pin 35 is low. Low selects odd parity. |
| 40 | TRC Transmitter Register Clock this should be 16 times the transmitter Baud rate. |

The remaining 3 chips used are quite common and familiar to most I would imagine.

The clock oscillator is a TLC555 the CMOS version of the 555 and is used to generate both transmitter and receiver clocks.

A 4011 CMOS quad NAND gate is used for generating some of the control signals, see 'How it works'.

A CA3401 op-amp is used for converting the 0v and +5v signals to -12v and +12V.

The Power Supply

The power requirements are quite small. About 10mA at 5V for the chips and the same for the ± 12 volt supplies for the line driver. The smallest commonly available mains transformer is usually 100mA which is rather more than enough! In fact remarks about sledge-hammers and nuts would be justified. So before embarking on a power supply for the conversion board (just CB in future) consider any options such as sharing a supply. Another option is to run from a single 12V supply. See below.

Conventional power

If a mains supply is going to be used to drive the RS232 board only, then the simplest arrangement is shown in Figure 9. Using a 12-0-12 transformer with half wave rectification to produce a peak output of 12×1.4 ie. approx 17 volts. This leaves plenty of headroom to drive two 100mA 12V regulators eg. $\mu A78L12$ and $\mu A79L12$. In addition the +5V ($\mu A78L05$) comes off the +12V. Don't forget the capacitor on the negative rail is upside down ie. its positive leg is connected to 0V.

The current output of such a simple arrangement can be full wave rectification and using larger capacitors. The new configuration of transformer secondary, diodes and capacitors is shown in Figure 10 otherwise its the same as Figure 9.

DC to DC convertors

Because the current consumption of the board is so small there are alternatives to conventional power supplies. Indeed in my case the boards are all run from a +12 volt battery supply. This involves DC to DC conversion.

Various DC to DC voltage convertors are available. The RC4190 micropower switching regulator will convert almost anything to anything! (Maplin UR15R). The TBA820 (Maplin WQ63T) which we all know is a small audio power amplifier can also be configured as a voltage convertor. Figure 11 shows how to use it to generate ≈ 12 from +12. This is how we use the device. The 5V comes off the +12 via a 100mA regulator as before. In Figure 11 the TBA820 operates as a high frequency (40kHz) square wave power oscillator. At pin 5 a peak to peak voltage of 12V is available which is inverted by the the two diodes and capacitor following. The diodes in these circuits are all 1N4148.

Building the Conversion Board

Assembly (Refer also to the copper design and component placement)

Immediately it's decision time. How is the board to be fitted with plugs and sockets? It's easy for plug and socketry to cost as much as all the electronics put together so it's as well to give some consideration to the problem.

As we made several of these boards for various purposes we decided on a 'standard' board which would be fitted with

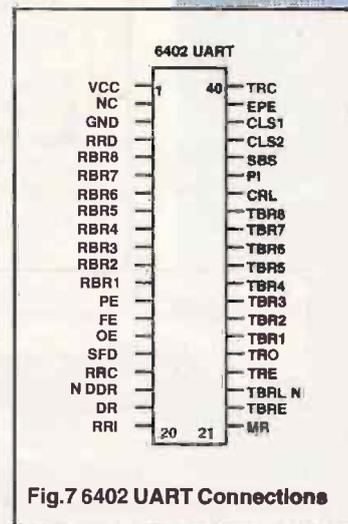


Fig.7 6402 UART Connections

HOW IT WORKS

The Conversion Board

Our general requirement for RS232 links was fairly specific. It had to be as simple as possible and of course reliable. No great distances are involved, 100 metres being the absolute maximum. The final choice was 2400 Bd, no parity, 8 data bits and 1 stop bit. At 2400 Bd this allows a character rate of 240cps. As there is no allowance for any sort of retransmission or handshaking parity would be pointless as nothing could be done if a parity error did occur. 8 data bits was the maximum possible and allowed for the transmission of standard 8 bit bytes. This format has proved very reliable in practice. Its not at all uncommon to transfer 20 to 30Kbyte chunks of data, and touch wood so far without error.

Sending

Figure 8 shows the schematic with data flow as far as possible from left to right. The P numbers on the lines are the pin numbers on the board connector. First the transmit side, 8 bit data input to serial output which is suitable for converting standard Centronics printer data to serial data. At the top left the 8 data lines T1 to 8 go to pins 26 to 33 on the 6402 IC. TXS is the line which strobes the data in, and would be connected to the Centronics strobe line. Busy is returned by inverting, via IC4, the signal on pin 22 of the 6402 which is transmit buffer empty, the inverse condition will be transmit buffer full which gives busy.

On the output side the serial data is on pin 25 of IC1. This is inverted by connection to the inverting input of the op-amp IC3. The non-inverting input of which is reference to the mid point of the 5 volt supply by the two 470R resistors. The supplies to IC3 are +12 volts on pin 7 and -12 volts on pin 4. Pin 6 therefore gives an inverted version of the serial output at ± 12 volts. The 3k3 resistor just acts as a current limiting resistor to the serial output TX OUT.

Receiving

In the case of the receiver serial data appears on the left at RX IN. By means of the 10k resistor and the two clamping diodes the input is restricted to 0 volts and +5 volts. This is inverted by another section of IC4 to feed the serial input of the 6402 at pin 20.

The 8 bits of serial data will appear in parallel on pins 5 to 12 of IC1 thence to R1 to R8 of the output highway. The data ready signal appearing at pin 19 is delayed by the resistor capacitor combination R6 and C1 and inverted by another section of IC4 to generate the data received reset signal at pin 18. This signal is also provided at the output as RXDR receiver data received. Working in this way data received at the serial input appears on the parallel highway and remains there until the next character is received.

Clock generation

At the bottom of Figure 8 and to the left is the clock generator. This is a CMOS 555 IC in a standard arrangement generating a nearly symmetrical square wave. The 10k preset potentiometer allows for setting the frequency (see setting up and testing). The clock generator runs at 38.5kHz which is 16 times the Baud rate.

Miscellaneous

At the bottom and to the right. A 100nF capacitor is connected across the 5 volt power supply rails. The fourth section of IC4 is spare its inputs connected to 5 volts to hold the output down to 0v. These connections can be cut if the NAND gate is required for any purpose.

Finally the following pins set the operational parameters for the 6402. Pin 35 to 5V to give no parity. Pins 37 and 38 to 5V to give 8 bits. Parity is not being used but pin 39 must be connected somewhere and its convenient to connect it to +5V. Pin 36 is connected to 0v to give 1 stop bit.

Pins 13, 14 and 15 are not used and not connected.

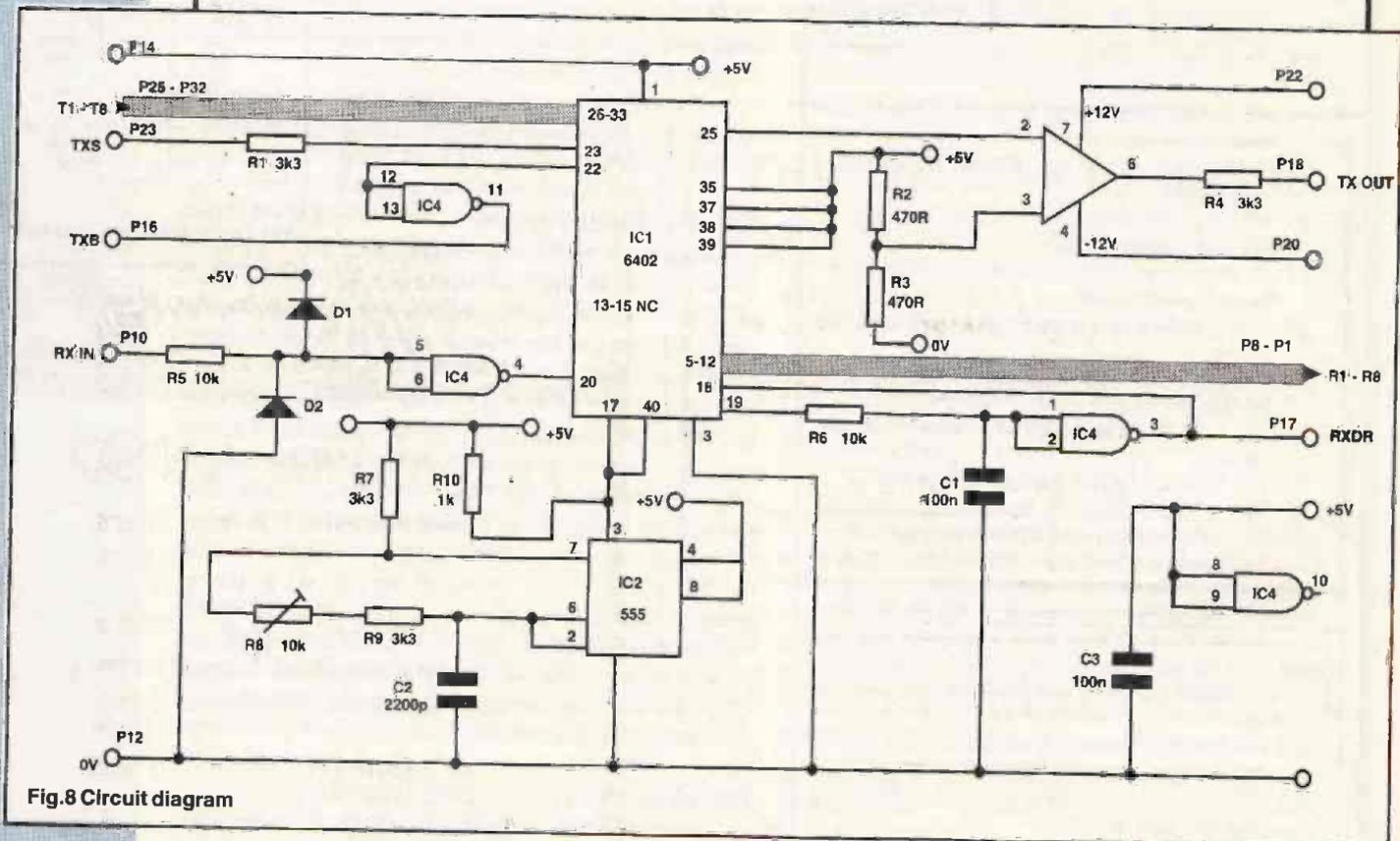


Fig.8 Circuit diagram

a multi-pin plug. The components list identifies this item and the pin numbers are shown on the board schematic drawing. (Numbered P1 to P32). A corresponding mother board is fitted with the mating 32 way socket at one end and a convenient board for the purpose is a 39 way by 39 holes, 4 x 4 inches. Maplin JP49D. We also run ours from a single

12V supply, so additionally we build a small power supply board which connects with the 12V and 0V and carries a 5V regulator and an inverter for the -12V based on the TBA820 mentioned earlier. This power supply board is built on a small piece of strip-board and connected to the mother board via gold-plated PCB connectors. Maplin WQ15R and WQ16S.

This arrangement is very convenient and flexible. Additional boards for other circuitry can be made and fitted via the same style of 32 way plugs and sockets or such other sockets as necessary wired from the mother board. However this is a bit over the top if the board is dedicated to converting a Centronics printer output to RS2322 with its own power supply. In which case it would be easier and cheaper to mount the conversion board along with its power supply and wire it directly to the board along with a Centronics socket and RS232 socket. (See later under usage for pin connections).

So, if you are going to fit the 32 way plug, do it first. The end of the PCB will need trimming to make a good fit. To do this temporarily insert the pins in the board. The plug should be on the same side as the other components. Mark the piece to be trimmed with pencil and mark the fixing holes. Then remove the plug and saw off the unwanted portion of the PCB with a fine hacksaw. A Junior is the easiest.

Fit and solder the remainder of the components with the exception of the 10k preset. The 4 links can be bare or covered wire. Bare is obviously cheaper unless you would have to buy some specially in which case use covered! The diodes must be the right way up. Facing the component side of the board with the plug on the

right, then the left hand diode should have its band at the top and the right hand diode its band at the bottom.

The 10k square 22 turn Cermet preset is actually intended for vertical mounting but is best fitted on its back with the adjusting screw at the outside edge of the board. Only two connections need be made using the centre lead and one of the others. Bend them to fit the holes marked 1 and 2 on the placement drawing and leave the other lead alone. Glue the preset to the board using 'UHU', 'Clear Bostic' or similar adhesive. Hold it in place until the glue sets with a paper clip, clothes peg, or whatever is handy. This done, the board is ready for testing.

**Part 2
Next
Month**

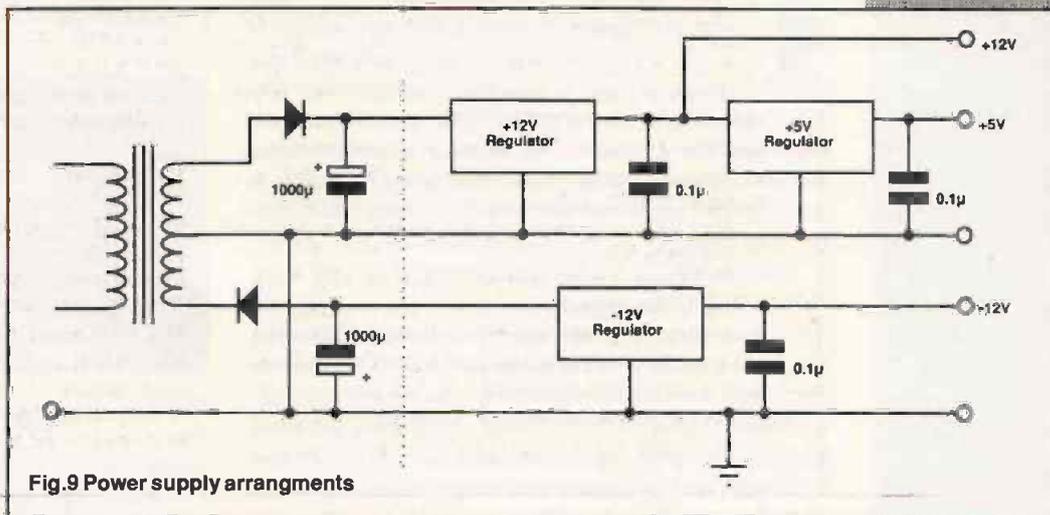


Fig.9 Power supply arrangements

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX · 031 667 2611

- ★ The supplier to use if you're looking for
- ★ A WIDE RANGE OF COMPONENTS AIMED AT THE HOBBYIST ★
- ★ COMPETITIVE VAT INCLUSIVE PRICES ★
- ★ MAIL ORDER - generally by RETURN OF POST ★
- ★ FRIENDLY SERVICE ★

Open: Monday-Thursday 9.15-6.00
Friday 9.15-5.00 Saturday 9.30-5.00



Hesing Technology

Cromwell Chambers, 8 St. Johns Street,
Huntingdon, Cambs. PE18 6DD

Tel: (0480) 433156
Fax: (0480) 214488

- | | |
|-----------------------|---------------------------|
| TEST EQUIPMENT | SYSTEM CONSULTANCY |
| Supply | Replacement Parts |
| Maintenance | Supply of Service & |
| Commissioning | Operators Manuals |
| | Components |

Distributors for:
WAUGH INSTRUMENTS, RAMTEST LTD, KRENZ ELECTRONICS, PANTHER



New for 1992

- ★ **New MOSFET Amplifiers**
improved range of SMOS modules
30W, 30+30W, 60W, 120W
- ★ **20 watt Class A Amplifier**
- ★ **Low profile PCB Transformers**
a range of encapsulated transformers
4VA, 6VA, 10VA, 18VA, 24VA, 30VA

Write or phone for data and prices...
which include details of standard range of toroidal transformers and audio modules.

No price increase for 1992

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254. Fax: (0227) 365104

The Greening of the Car

by Douglas Clarkson

The car is probably a superb example of something that 'just happened' - meaning it was a process of social and economic change which from very humble beginnings developed in an unpredictable way to become a very major element in the economies of the developed world. The car has become an indispensable element of modern life but in seeking to provide freedom to the individual, it is becoming a collective problem in relation to use of resources and pollution of various types.

Car manufacture has been an industry sector which has received a lot of encouragement over the years from governments. They have been encouraged to set up new production facilities - manufacturers have been quick to do so. Governments have been unenthusiastic to restrict the role of the car in respect of environmental factors - they sense this as an adoption of principles of economic downturn. Manufacturers like to consider that they adopt an 'everything we do is driven by you' attitude towards car development. The customer gets precisely what they want - nice wheel trim - reclining seats - electric power windows - nippy acceleration and a top speed of 120 mph.

The private individual and environmental pressure groups may identify features that they wish to be included in car design -but have little in the way of collective 'clout'. Environmental groups have a role in influencing public opinion and to focus on the 'green' car lobby.

Since the energy crisis of the early 1970's, pressure groups have been steadily growing. Although the USA took little part in the early technology of the car, it has in fact forced the pace of key elements of 'green' car policy which relate to emission levels as outlined in Figure 1. This is because the USA was the first to witness high levels of car exhaust pollution.

Aspects of Emission Control

The topic of emission control deals with one specific undesirable feature of the car. While it is a useful and necessary step forward, it is not the end point of the process of a 'green' car policy. It is appropriate, however, to examine the various types of offending emissions from cars and see how they can be minimised.

Lead in Petrol

Petrol is normally produced by refining crude oil. In the internal combustion engine, fuel tends to ignite before the gas mixture is fully compressed. This is because the work done in compressing the gas is transferred as thermal energy to the gas molecules themselves (adiabatic compression). The use of Lead Tetra Ethyl prevents this pre-combustion and provides a more efficient combustion of the petrol/air mixture.

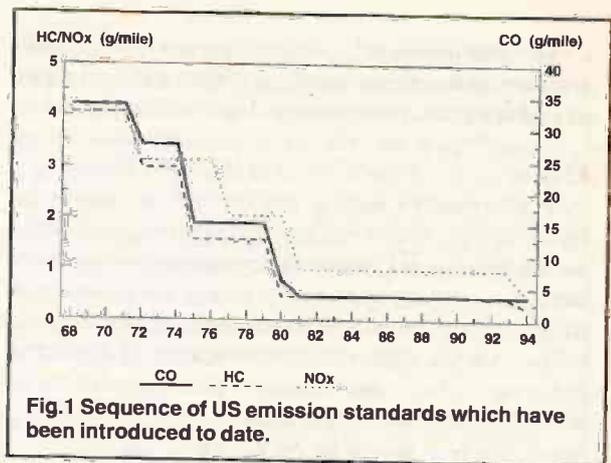


Fig.1 Sequence of US emission standards which have been introduced to date.

Year	Amount of lead (thousands of tons)
1982	6.8
1983	6.9
1984	7.2
1985	6.5
1986	2.9 (unleaded available)
1987	3.0
1988	3.1
1989	2.6

Table 1: Variation of lead released in UK on yearly basis

The total amount of lead released is probably still moving downwards. While this is the overall picture, it does not take into account instances of high deposition in inner city areas where

traffic densities are alarmingly high. If the UK was divided into a 100 by 100 grid, there would be some squares with alarmingly high lead concentrations.

There is regional variation within the EEC however, on the level of uptake of unleaded petrol. Within (West) Germany the level is approaching 80%, within France around 25% and within the UK around 40%. Interestingly, the significant early days of the car unfolded in Germany.

The bulk of the research into lead uptake in the population has been undertaken by the academic community and not by government agencies. Lead and its effect on individuals is a very complex field. Lead compounds were removed from petrol in the USA during the 1970's. The levels of lead in the general USA population was observed to fall. At the same time, the level of 30 micrograms per decilitre which was once considered 'safe' has been identified with neurobehavioral defects in children and increased blood pressure levels in adults.

There is also evidence that lead which has accumulated in the bones can be 'leached' out as a result of changed metabolic conditions. Thus it may be the case that lead accumulated in the bones of a pregnant mother can be released with potential toxic effects on both the fetus and the mother. There is also indication that increased levels of lead is associated with cardiovascular diseases.

All in all, and perhaps later rather than sooner, lead from petrol is a diminishing but still relevant concern.

Carbon Monoxide

Carbon monoxide is a product of incomplete combustion which reduces the ability of the bloodstream to carry oxygen. If sufficiently high levels are breathed in, the consequences can be fatal. The invisible gas is heavier than air and it can accumulate when stagnant air masses are in contact with cold ground surfaces. The pollutant is a greater risk to individuals who already have an impairment of their heart/lung system - eg angina sufferers or chronic bronchitis. The level of 9.5 parts per million over an 8 hour period is generally taken as

a level which if exceeded can result in adverse effects for high risk individuals and also impair the performance of 'normal' individuals - cause drowsiness or loss of concentration.

Ozone

While there are worries about ozone depletion in the upper atmosphere there are also worries about environmental pollution caused by ozone. Ozone is considered to inflame and scar the airways of the lung - bringing about a reduction of lung capacity which is both short term and long term in its effect. Indeed, in the worst affected areas of California, reductions in lung capacity of some 50 to 75% have been observed in some individuals. During most normal activities, such a loss of capacity may not be noticed though this will significantly reduce the level of exercise that the individual could sustain.

In the USA the 'threshold' level is considered to be 0.12 parts per million.

Children would appear to be more vulnerable to air pollution in general, because they tend to breathe more through their mouths. The human nose, it appears, is able to remove up to 90% of pollutants from inhaled air. Confirmation of the reduced lung capacity of children due to Ozone pollution was obtained when a study of children who grew up in the Los Angeles basin revealed that they had a reduced capacity of between 10 and 15% when compared with equivalent children in a 'clean' environment.

Paradoxically, athletes who on average breathe more than the average individual can damage their lungs when they exercise in an ozone rich environment. There is also some evidence from animal experiments that ozone can impair the immune system.

In the USA the top of the poll of worst offenders in 1989 was, not surprisingly, Los Angeles with a tally of 137.5 days in which the level was above the 0.12 ppm standard.

If in the UK, freedom of information is not a problem, where are the comparable statistics for UK ozone level pollution?

Oxides of Nitrogen

Nitric oxide and nitrous oxide are formed during the combustion process. Where they are present in high concentrations they can appear as a yellow-brown hue in the sky. They are considered to be respiratory irritants and cause lower resistance to infection.

Fine Particulates

Everyone will be aware that exhausts from vehicles discharge smoke particles into the atmosphere. In relation to air pollution this aspect is termed - 'fine particulates'. It has been shown that such particles can lead to lung cancer and contribute to respiratory illness. Medical researchers consider that this form of pollution in association with other agents may be responsible for the rise in incidence of asthma within the population in the UK.

Carbon Dioxide

The role of carbon dioxide as a polluter is constantly under review in an assessment of how it will influence global warming. This 'pollutant' is very much for the collective health of the planet and not the immediate health of a cyclist pedalling through rush hour traffic in London. In various ways, government in the developed world have pledged to

establish emission by the year 2000 at 1990 levels.

This policy pledge will certainly be the final hurdle to cross to perfect the ultimate non-polluting mode of transport. In the short term it relates to making vehicles more fuel efficient and in the longer term finding alternate fuels and developing radical new technologies to source energy.

Hydrocarbons

Fuel for the internal combustion engine does not completely burn. Unburnt hydrocarbons are released into the environment and react with other pollutants and sunlight. Surprisingly large volumes of hydrocarbons are also released into the atmosphere by spillages at petrol stations. There should perhaps be notices of petrol pumps warning customers to minimise any spillages.

Table 2 shows the relative contributions of road transport in the UK to various emissions. Power stations produce an equal amount of nitrogen oxide emissions and industry is responsible for around 52% of hydrocarbon emissions. Thus road transport is not wholly to blame for poor air quality in the UK.

Emission	% Emission by road transport (UK)
Carbon monoxide	85
Nitrogen oxide	40
Hydrocarbons	28

Catalytic Clean Up

Assuming that the legacy of lead pollution is if not al-

together vanquished then on the wane, attention is focusing on the key pollutants of carbon monoxide, ozone and oxides of nitrogen. One solution has been to try and develop 'lean burn engines' where the pollution problem would be treated at source - within the engine itself. While progress has been made in this regard - most manufacturers have opted for a 'bolt on' catalytic converter 'cure'.

Various catalytic converters have been developed. The two way (oxidation) catalyst of Palladium and Platinum treats only the two pollutants carbon monoxide and hydrocarbons. The unit requires to be heated initially to over 300°C - necessitating location of the unit close to the engine.

The open-loop (unregulated) three-way catalyst is primarily intended as an 'aftermarket' device which does not integrate with the engine or the fuel system of the car. A platinum catalyst oxidises hydrocarbons and carbon monoxide while a Rhodium catalyst reduces oxides of Nitrogen to simple atomic nitrogen.

The closed-loop (regulated) three way catalyst functions in a more complex way. In this system the air fuel ratio is maintained at a value of 14.7 to 1. This allows for optimum oxidation of hydrocarbons and carbon monoxide and in addition ensures optimum removal of nitrogen oxides. This control system is usually only available on more expensive cars with complex engine management systems.

Cars equipped with catalytic converters run the risk of 'poisoning' them with leaded fuel which acts to block the pores of the active surfaces. Consequently, the fuel inlet ports of such cars are restricted to accommodate only the slimmer nozzle of unleaded petrol pumps. There is also typically a small loss of engine performance associated with a catalytic converter - typically around 3%.

Action on Emissions

The initiative for cleaning up the car has mainly stemmed from directives in the USA where pollution in Southern

Table 2: Relative contribution of road transport to major emissions.

California has been an acute problem for over 30 years. Figure 1 shows the sequence of US emission standards which have been introduced to date. The reduction in emission levels is largely achieved through the use of more efficient engines and catalytic converters.

More recent legislation in the USA will further reduce nitrous oxide emissions by 60% (to 0.4 g/mile) and hydrocarbons by 40% (to 0.25 g/mile). These changes were initially scheduled between 1994 and 1996, though California and various other states will implement them from 1993.

The anticipated expansion of cars in the Los Angeles area would, around the turn of the century, continue to cause pollution problems even with the more stringent emission levels. Rather than lower emission levels still further based on conventional car technology, future plans relate to the phasing out of all polluting vehicles. In this process the following categories of vehicle are specified:-

- TLEV - transitional low emission vehicle
- LEV - low emission vehicle
- ULEV - ultra low emission vehicle
- ZEV - zero emission vehicle

Between 1994 and 2010 it is proposed to change the mix of these vehicles so that there is a steady progression towards ZEV types of transportation. This focuses attention on what will be on the streets of Los Angeles in 2010. The question also arises - what will be on the streets of Europe at this time? There is no comparable plan such as the TLEV to ZEV transition which is scheduled for California. Based on the

low of precedence, the standards about to be introduced in the EEC in 1993 are almost identical to those introduced in the USA in 1983 - a response time of some 10 years. Various member countries, such as Denmark and West Germany, however, accepted this deadline 'ahead of time'.

People, however, are only beginning to look at the environmental impact of the car. Progress is being made. The phasing out of lead in petrol is a blessing - but one which should have come sooner. The reduction of emissions from car exhausts is also good - although it will be some time before the benefits of this filter through to the general public as the 'fleet average' levels diminish to safer levels. It is particularly surprising, that the effect of such emissions on the health of the population seems to have been researched at a level out of all proportion to its importance. Why is this?

People, however, are only beginning to look at the environmental impact of the car. Progress is being made. The phasing out of lead in petrol is a blessing - but one which should have come sooner. The reduction of emissions from car exhausts is also good - although it will be some time before the benefits of this filter through to the general public as the 'fleet average' levels diminish to safer levels. It is particularly surprising, that the effect of such emissions on the health of the population seems to have been researched at a level out of all proportion to its importance. Why is this?

Reducing CO₂ Emissions

General Aspects

Attention is now being directed towards the ultimate greening of the car - the reduction or the elimination of Carbon Dioxide emissions in order to slow the effect of global warming.

There has been a significant switch in emphasis recently to view the carbon dioxide emissions as the most sinister in the long term. While some governments remain on the sidelines to wait and see how new technologies emerge, others are taking an active part in developing solutions which

could in the not too distant future reap immense commercial rewards.

In this initiative, there are a range of options ranging from stabilising or reducing emissions to establishing zero net emissions. Within Europe, Germany has adopted the more ambitious plan than the UK of reducing CO₂ emission by 25% between 1990 and 2000. By comparison, the UK has plans only to stabilise emission between 1990 and 2005.

The drive towards more fuel efficient cars is certainly a step in the right direction - and fuel economies of cars are generally rising. In the USA the so called CAFE scheme (Corporate Average Fuel Economy) has raised its standards averaged over groups of manufactured cars from 18.0 US mpg in 1978 to 27.5 USmpg in 1990. Various Bills in the US, however, to improve on this rating have been defeated.

Diesel engines offer the best fuel efficiency. Urban cycle efficiencies of 48.6 mpg can be achieved for cars such as the Rover Montego 2.0 DSLX Turbo. Public worries about pollution, however, still limit their widespread uptake by the public. It is likely, however, that fuel efficiency figures will continue to rise based on 'incremental' development. More fundamental advances may also help achieve improved performances. It seems unlikely, however, that even significant rises in fuel efficiency will diminish total levels of CO₂ emissions since road traffic is itself rising rapidly - both in the developed world and also in the developing world.

There is no doubt that the real underlying need for fuel efficiency is the need to reduce CO₂ emissions. The countries in the world such as Germany who have taken a more progressive line on meeting targets for reducing such emissions have at the same time provided a real market stimulus for developing the technologies to meet the perceived challenges.

Vehicle Design

Table 3 shows typical way in which energy is consumed in petrol driven vehicles. Usually only some 28% of energy in the petrol is converted to power at the crankshaft.

This indicates that some 42% of the energy available for mechanical motion is dissipated in losses within the vehicle (gearbox, drivetrain etc). There would seem ample opportunity to reduce this figure using technology of new materials and engineering.

For many years engineers have been trying to develop continuously variable transmissions which would provide improved fuel efficiency. Recently a device described as an infinitely variable transmission (IVT) has been developed by Epilogics Inc. in Los Gatos, California. Rotary motion on one side is converted to oscillatory motion and back to rotary motion at the output shaft. Such a system of continuous gearing is being investigated by various companies in the USA. It is known, that the motor racing industry is keenly aware of the potential benefits of such technology. It is possible, this technology will first be proved on the Grand Prix race tracks of the world before it is available for the family car.

The coefficient of aerodynamic drag (Cd) is an indication of the level of air resistance of a specific design. Citroen cars have a history of low Cd values. The Citroen Activa prototype has a Cd value of 0.25 while most modern cars have values of around 0.32.

Vehicles of smaller mass will accelerate more rapidly (acceleration is force divided by mass). Thus a vehicle with a

Table 3: Typical use of energy within an internal combustion vehicle. Only a relatively small part goes to propel the vehicle.

Function	Percentage Loss
Alternator/cooling fan	9%
gearbox	6%
differential	4%
drivetrain	5%
rolling resistance	18%
air resistance	40%
direct drive	18%


5% reduction in mass will have a similar improvement in acceleration performance and contribute to improvement in fuel economy. There has been a tendency, however, to increase the weight of modern cars with the array of refinements and adornments which now accompany most cars.

Alternative Fuels

The use of fuels produced from crops such as sugar cane and sunflower seeds has been undertaken in countries such as Brazil and South Africa for reasons of economic necessity. It is unlikely, that such methods of production would contribute any useful amount of fuel to the world economy.

The use of Hydrogen has long been considered as an alternative fuel. The only product of its combustion in air is water. The hydrogen can either be provided in liquid form or stored in a metal hydride cartridge which releases the gas when it is heated. A development car produced by the Sanyo Electric Company in Japan has created a car which uses a phosphoric acid fuel cell which runs off hydrogen and air. Solar radiation or the output from the fuel cell can directly charge the nickel cadmium batteries which in turn drive a brushless DC motor. The energy density, of such a hydrogen fuel cell is about 3.6 watts per pound which is less than one third than that of current lead acid battery technology.

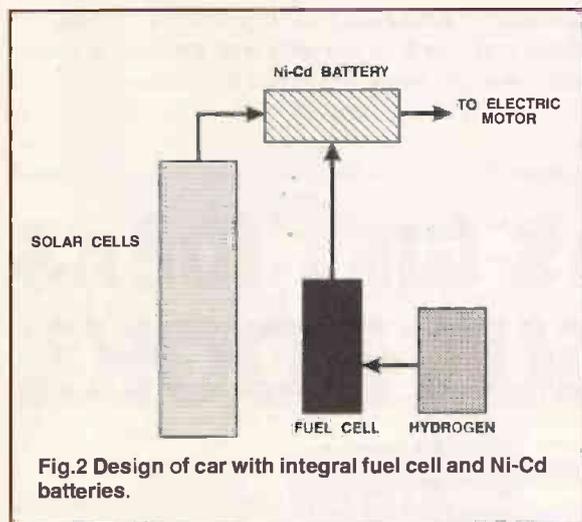In the USA, the American Hydrogen Association lobbies for the increased use of hydrogen in the energy infrastructure



of the world. The president of this group, Roy McAlister, Professor of Thermodynamics at Arizona State University anticipates that in the future solar power will be used to produce Hydrogen from sea water - apparently the Saudi Arabia plan to produce 25% of the world's energy requirements from Hydrogen.

One of the schemes which is being evaluated in the USA is one which involves the use of Methanol in a mixture 85% methanol and 15% petrol (M85). The value of methanol as a 'greenhouse friendly' gas, depends very much on its origin. Methanol can in fact be synthesised from a range of feedstocks such as natural gas, coal, sugar cane or even wood. Natural gas is in many respects a waste product of oil extraction when it is flared off at sites too remote for pipeline collection.

The use of methanol, would require some changes to both systems of distribution and use within vehicles. M85 has less calorific value than petrol. About one gallon of petrol is equivalent to 1.6 gallons of M85. This will require that fuel

tanks in vehicles should be larger and also the distribution system for the fuel will need additional capacity compared with petrol. The M85 mixture, however, has a tendency to corrode present fuel system components.

Battery Technology

There is no doubt that technology is inching towards battery vehicles which can draw on non polluting sources of power. The fundamental breakthrough in battery storage technology, has yet to be announced. It may be, that such a breakthrough has already taken place and that the ink is nearly dry on the patent applications.

There is no doubt, that relatively large sums are being spent on developing battery technology. In the USA the major motor manufacturers General Motors, Ford and Chrysler have formed a co-operative group to develop battery technology. There is also intense activity in Japan and Europe.

The types of battery currently being developed include Nickel-Cadmium, Zinc-Bromine and Sodium-Sulphur. The Sodium-Sulphur battery which is being developed by ASEA-Brown Boveri (ABB) of Switzerland and Chloride in the UK has the advantage of four times the energy density of lead acid batteries. One drawback, however, is that the chemicals require to be at temperatures between 299°C and 329°C. This requires that some of the energy stored in the battery is required to bring the battery to its optimum operating temperature.

One major development in electric vehicles was that of the 'Impact' sports car developed by General Motors. While using conventional lead acid batteries, the car used a compact and efficient DC to AC voltage converter which allowed use of more efficient AC motors. The 'Impact', is still created in the traditional image of the car - stylish, assertive and trendy. Table 4 indicates the performance of a range of electric cars. The 1990's will no doubt see increasing numbers of electric vehicles on the road.

There is increasing interest in utilising solar energy as the energy source for powered vehicles. The World Solar Challenge which was first run in Australia in 1987 between Darwin and Adelaide proved that solar powered vehicles need to be taken seriously. The winner of the race was the General Motors SunRacer which completed the distance at an average speed of 66 kmh and which achieved a top speed of 113 kmh. This success was due in part to the use of a high

Make	Range	Top Speed	Acceleration
GM Impact	192 km	160 km/h	0-50 km/h in 4.2 secs
Volkswagen Jetta CitySTROMer	120 km	105 km/h	0-50 km/h in 12 secs
BMW 3-series	115 km	100 km/h	0-50 km/h in 12 secs

Table 4:
Performance of various electric cars

efficiency 'Magnequench' electric motor manufactured by GM Delco Remy division.

The race was subsequently held again in 1990. The winner this time was an entry from the Biel School of Engineering in Switzerland. Their vehicle used high efficiency solar cells and were developed at the University of New South Wales using a laser technique to etch the cell surface and so increase its active area.

By the late 1980's, efficiencies for Silicon cells and those made using Gallium Arsenide were in excess of 20%. Subsequently a Gallium Arsenide device which operates in conjunction with a focusing element has achieved an efficiency of 37%. To provide an element of historical perspec-

tive, efficiency values were around 1% in the 1930's and 6% in the mid 1950's.

Assuming a vehicle surface area of 5 square metres on a partially sunny day with a solar radiation of 0.5kw/m² and with cells with 30% efficiency, there would be approximately 0.75kW of power available. For a vehicle of 1000kg and assuming 75% efficiency in the electric motors, this will produce speed of about 35kmh in 10 seconds. Such vehicles, must surely operate with significant battery reserves within the vehicle to augment conditions of poor solar radiation.

In fact it makes more sense to use the larger surface areas of the roofs of domestic houses to capture solar energy than the relatively small area of a motor vehicle. Where such areas can be utilised for solar power collection values of areas can be quite significant eg around 20 square metres. Assuming 6 hours of sun on average at 0.5kw/m² and at 30% collection efficiency, this equates to 65MJ of energy or 18kWh (kilo watt hours). The cost of this amount of energy through the National Grid is £1.33 at a cost of 7.37p/kwh. Already in Switzerland, this process of charging vehicles from solar panels on buildings is becoming common.

Reference should also be made to 'flywheel technology' where the energy of a spinning disk is used to propel a vehicle. Such devices usually operate within a vacuum environment and utilise ultra low resistance bearings. The materials used require to be ultra strong to prevent fracturing due to the large centripetal forces. While such vehicles have been demonstrated, no major car manufacturer has so far adopted this method of energy storage.

Summary: Due to a combination of technological advance

and the need to reduce car emissions still further (particularly CO₂), the 1990's will no doubt see the beginning of the end of polluting vehicles. The whole process, however, will need a switch in investment on a colossal scale if this is to come about. With the public increasingly willing to be responsible in their use of the resources of Planet Earth it should be increasingly easy to convince the industrialists that the models in their showrooms are going to experience major changes in design and function. Why not write to them and communicate your views to them?

Further Reading:

The Green Car Guide, Paul Nieuwenhuis, Peter Cope and Janet Armstrong, Green Print, 1992.

Useful addresses:

Air Resources Board, PO Box 2815, 1102 Q Street, Sacramento, CA 95814, USA.

Electric Vehicle Association of Great Britain Ltd., 13 Golden Square, Piccadilly, London, W1R 3AG.

Electric Vehicle Council, 1111 19th Street NW, Washington DC 20036, USA.

Energy and Environment Research Unit, Faculty of Technology, The Open University, Milton Keynes, MK7 6AA.


General Motors Environmental Activities, 30400 Mound Road, Warren, Michigan, 48090-9015, USA.

Greenpeace, 30-31 Islington Green, London, N1 8XE.

National Society for Clean Air and Environmental Protection, 136 North Street, Brighton, BN1 1RG.



CHRISTMAS GIFT IDEAS FROM ARGUS BOOKS

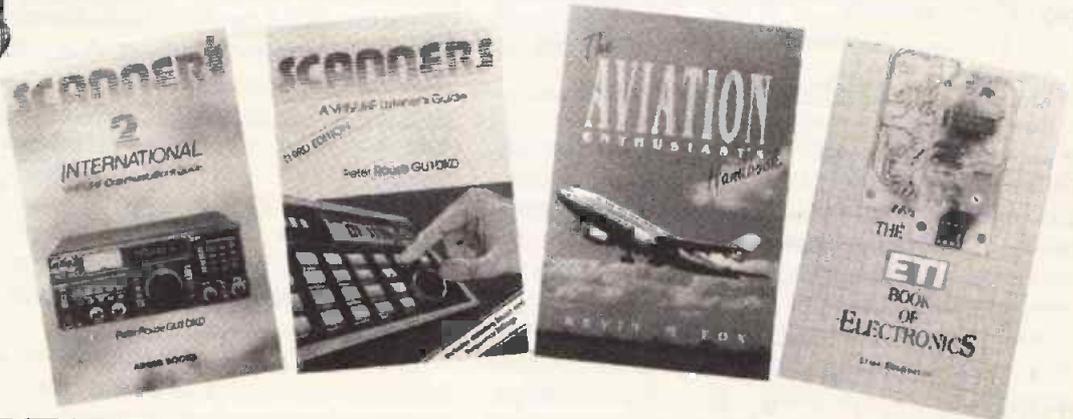

ORDERS RECEIVED AFTER 14/12/92 CANNOT BE GUARANTEED FOR XMAS DELIVERY

HOW TO ORDER BY POST

- | | |
|--------------------------------------------------------------------|--------|
| <input type="checkbox"/> 085242924X SCANNERS 2 INTERNATIONAL | £10.95 |
| <input type="checkbox"/> 1854860062 SCANNERS 3rd EDITION | £8.95 |
| <input type="checkbox"/> 1854860542 AVIATION ENTHUSIAST'S HANDBOOK | £9.95 |
| <input type="checkbox"/> 1854869282 ETI BOOK OF ELECTRONICS | £10.95 |

Signature

Name

Address

Please ensure that all cheques are made payable to

Bailey Distribution and, together with the completed form send to:

Bailey Distribution Ltd, Units 1a/1b Learoyd Road, Mountfield Road Industrial Estate, New Romney, Kent TN28 8XU.

I enclose my remittance of £ Postage & Packing FREE

Please charge my access/mastercard/barclaycard/visa No Expiry date

TO ORDER BY PHONE

Tel: (0679) 66905

and quote

Mastercard/

Visa.

Allow up to 28 days for delivery.




INTRODUCTORY
PRICE JUST £179

SCHEMATIC DRAWING FOR WINDOWS

NEW

ISIS ILLUSTRATOR combines the high functionality of our DOS based ISIS products with the graphics capabilities of Windows 3. The result is the ability to create presentation quality schematics like you see in the magazines. **ILLUSTRATOR** gives you full control of line widths, fill styles, fonts, colours and much more. When the drawing is complete, transferring it your WP or DTP program is simply a matter of cutting and pasting through the Windows Clipboard.

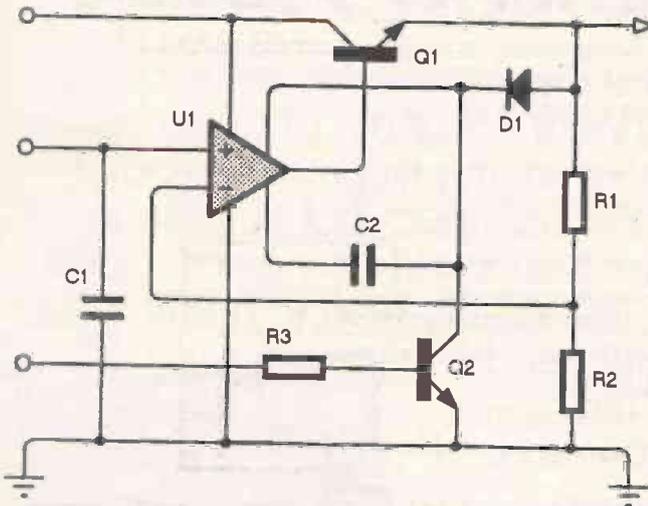

Features

- Runs under Windows 3.0 or 3.1.
- Full control of drawing appearance including line widths, fill styles, fonts, colours and more.
- Curved or angular wire corners.
- Automatic wire routing and dot placement.
- Fully automatic annotator
- Comes complete with component libraries; edit your own parts directly on the drawing.
- Full set of 2D drawing primitives + symbol library for logos etc.
- Output to Windows printer devices including POSTSCRIPT and colour printers.
- Loads ISIS SUPERSKETCH and DESIGNER files directly.

CADPAK - Two Programs for the Price of One.

ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

Only
£79

Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.

PCB II

High performance manual PCB layout package for DOS. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

Graphical User Interface with intuitive "point and do" operation gives unparalleled ease of use.

ISIS and ARES - The Professional's Choice

ISIS DESIGNER

from £275

ISIS DESIGNER forms the ideal front end of your CAD system, providing schematic capture, netlisting, bill of materials and electrical rules checks.

DESIGNER+ adds advanced design management features and is one of the most advanced DOS based schematics programs on the market.

ARES

from £275

The ARES range of advanced PCB design products links with ISIS DESIGNER and other schematics programs. Working from a netlist, ARES helps you get it right first time with each connection automatically verified against the schematic.

ARES AUTOROUTE adds multi-strategy autorouting, whilst for the ultimate in performance, ARES 386 goes up to 400% faster with unlimited design capacity.

labcenter
Electronics




Call us today on 0274 542868 or
fax 0274 481078 for a demo pack.
Combination, multi-copy and educational
discounts available. Prices exc P&P and VAT.

14 Murriner's Drive, Bradford, BD9 4JT.

PCB Foils

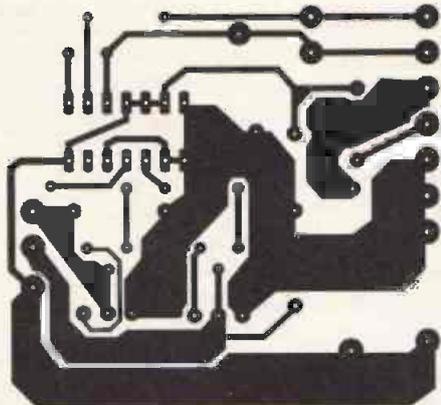The PCB foil patterns presented here are intended as a guide only. They can be used as a template when using tape and transfer for the creation of a foil.



Mains Inverter



MIDI Keyboard August '92


The PCB overlay is correct but in Figures 1a, 1c 3 and 4 all references to NC (normally closed) should read as referring to NO (normally open), and vice versa. On circuit diagram, R3 should go to +5V, and R4 to 0V.

Pin	PL2 Connection	PL3 Connection
10	Highest NO busbar	Highest NC busbar
9	Next NO busbar	Next NC busbar
8	"	"
7	"	"
6	"	"
5	"	"
4	"	"
3	"	"
2	Lowest NO busbar	Lowest NC busbar
1	+5V to pull ups	+5V to pull ups


It is necessary to connect each common key contact to the common line through diode (1N4148), anode to the key contact, cathode to the common line to provide extra isolation.

Aerial Tuner Unit Oct '90

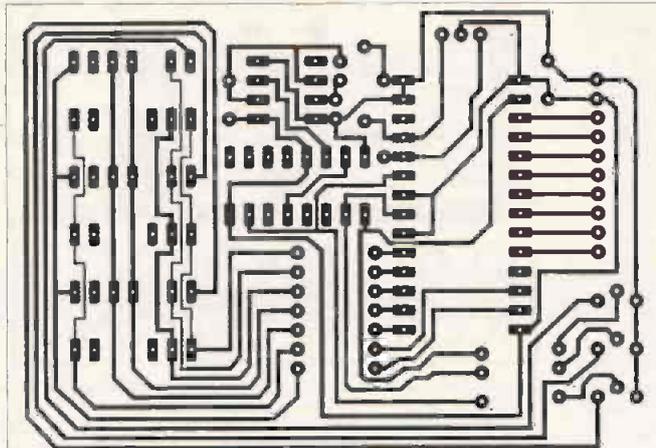The circuit diagram in figure 1 should not show a connection between inductor L1 and the screened case. Follow the wiring diagram in Figure 3 as this is correct.



Digital Circuit Tester

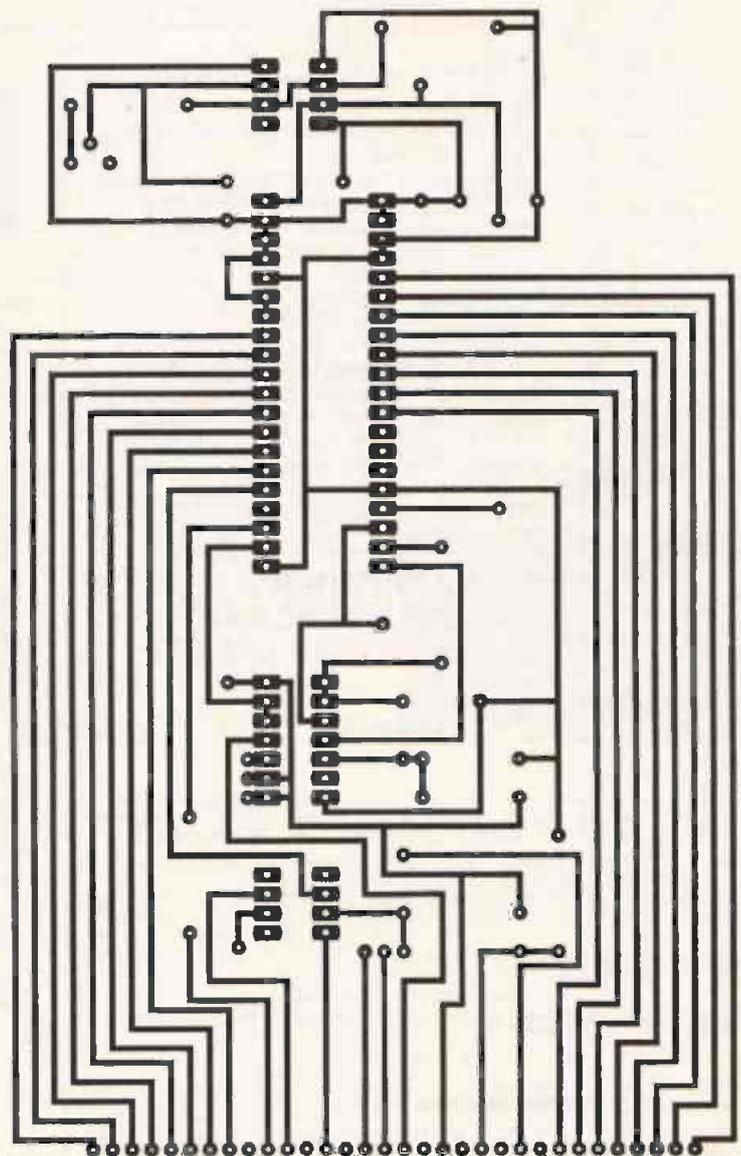

RS232 Interface

TELEPHONE
ORDERS
may be made on
(0442)
66551
ACCESS or VISA



PCB Service December

Price code	Price (inc. VAT)
C	£1.80
D	£2.50
E	£3.25
F	£4.00
G	£4.75
H	£5.50
J	£6.62
K	£7.20
L	£8.80
M	£10.60
N	£13.10
O	£15.80
P	£17.90
Q	£21.80
R	£23.90
S	£25.90
T	£29.00
U	£32.20
V	£35.80
W	£37.90
X	£40.70

- E9212-1 Digital Circuit Tester F**
- E9212-2 Communications Link by RS232 L**
- E9212-FC Mains Inverter E**

PCBs for the remaining projects are available from the companies lists in Buylines.
Use the form or a photocopy for your order. Please fill out all parts of the form. Make sure you use the board reference numbers. This not only identifies the board but also tells you when the project was published. The first two numbers are the year, the next two are the month.
Terms are strictly payment with order. We cannot accept official orders but we can supply a proforma invoice if required.
Such orders will not be processed until payment is received

E9107-4	The Consort Loudspeaker	H
E9108-1	Pulsed Width Train Controller	E
E9108-2	Model Speed Controller-Main Board	F
E9108-3	Model Speed Controller-Power Supply	F
E9109-1	Geiger Counter	E
E9109-2	Hemisync Waveform Generator Board	G
E9109-3	Hemisync Pulse Generator Board	F
E9109-4	Hemisync Power Supply Board	C
E9109-5	Nightfighter Main Processor Board	O
E9110-1	Freeze Alarm	E
E9110-2	Document Saver	E
E9110-3	Prototype Designer	J
E9110-4	Nightfighter - Sound to Light (2 sided)	L
E9110-5	Nightfighter - Ramp Generator Board	F
E9110-6	Nightfighter - Cyclic Crossfade (2 sided)	M
E9110-7	Nightfighter - Strobe Board (2 sided)	J
E9110-8	Nightfighter - 8 Channel Triac Board	N
E9111-1	Digital Code Lock	L
E9111-2	Switched Mode Power Supply	E
E9111-3	Nightfighter Mode Selection (2 sided)	J
E9111-4	Nightfighter - Display Board (2 sided)	M
E9111-5	Nightfighter - Bass Beat Trigger (2 sided)	L
E9111-6	Nightfighter - Sequence Select (2 sided)	H
E9111-7	Nightfighter - Master Controller PSU	K
E9111-8	Nightfighter - Output Switch (2 sided)	M
E9112-1	Nightfighter Sensor Switch Master Control (2 sided)	L
E9112-2	Nightfighter Sensor Switch Channel Control (2 sided)	L
E9112-3	Nightfighter Sensor Switch Sound Trigger	H
E9112-4	Nightfighter Connector Board	F
E9112-5	Nightfighter Sensor Switch PSU	K
E9112-6	Nightfighter 8-Channel Input Interface (2 sided)	P
E9112-7	Power On and Overload Regulator	P
E9201-1	Laboratory Power Supply	F
E9201-2	Test Card Generator Board	M
E9201-3	LED Star (2 sided)	L
E9201-4	Enlarger Timer Main PCB (2 sided)	N
E9201-5	Enlarger Timer Selector Board (2 sided)	K
E9201-6	Enlarger Timer Switch PCB	E
E9203-1	MIDI Switcher- Main Board	L
E9203-2	MIDI Switcher- Power Supply	E
E9203-3	Sine Wave Generator (surface mount)	F
E9204-1	Auto Car Lights	F
E9205-1	Bat Detector	E
E9205-2	Pond Controller	F
E9206-FC	Stereo amplifier	J
E9206-2	Xenon flash trigger Main Board	J
E9206-3	Xenon flash trigger Flash Board	F
E9206-4	Scanner for audio generator	D
E9207-1	Improved Rear Bike Lamp	D
E9207-2	Mini Baby Bug Monitor	C
E9207-3	Ultrasonic Audio Sender (2 boards)	H
E9207-4	Camera Add-on unit (4 boards)	O
E9207-5	AutoMate 5V/48V Mixer power supply	J
E9207-6	AutoMate Precision 17V power supply	J
E9207-FC	Surround Sound Decoder	F
E9208-1	Dynamic Noise Limiter	F
E9208-2	Touch Controlled Intercom (2 boards)	H
E9208-3	MIDI Keyboard	K
E9208-FC	Battery charger	F
E9209-1	Intercom for light aircraft	H
E9209-2	Alarm protector	C
E9209-3	Temperature controller	M
E9209-FC	45W Hybrid power amp	F
E9210-1	Universal I/O Interface for PC (2 Sided)	N
E9210-2	Rapid Fuse Checker	E
E9210-3	Heartbeat/Audio Listener	E
E9210-FC	Wizards Hat	E
E9211-1	Electronic Die	E
E9211-FC	Car Alarm	F

**ETI PCB SERVICE, READER'S SERVICES,
ARGUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD HP2 7ST**

Please supply:

Quantity	Ref. No.	Price Code	Price	Total Price
----------	----------	------------	-------	-------------

Post & Packing £0.75

Total Enclosed £

Please send my PCBs to:

Name

Address

.....Postcode

CHEQUES SHOULD BE MADE PAYABLE TO ASP Ltd.

ETI DECEMBER 1992

ETI Classified



Lucy Hughes
0442 66551

Send your requirements to:
ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 60p per word (+VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£15.00 per single column centimetre (+VAT) } Per
Electromart £24.00 (+VAT) } Insertion



Ring for information on series bookings/discounts.
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

Special offers - please check for availability

F cells 32dia x 87mm	£3.95
F cells with solder top, 1.2V	£4.30
42mm x 16mm dia 1.2V	£1.48
Stick of 4 171mm x 15mm dia., with red & black leads 4.8V	£5.95
4 cell battery 34mm x 25mm dia (172C cells)	£3.50
Computer grade capacitors with active terminals	
35000µf 20V £2.80; 87000µf 10V £1.95;	
68000µf 15V £2.95; 100000µf 16V £1.80	
7 segment common anode led display, 12mm	£0.45
LM2831 AT 5.0V low drop out 5V regulator TO220 package	£0.85
7812 and 7812 12V 1A regulators	£20.00 per 100
LM337V TO3 case variable regulator	£1.80
100 + £1.10	
BS260 P channel mosfet 45p, BC559 transistor	per 100 £3.95
74LS06 hex inverter	£10.00 per 100
Used 8748 Microcontroller	£3.50
SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet	£1.95
AM27502	£1.25 each; 90p 100 + CD4007UB 10p 100 + 6p 1000 + TV Mains switch, 4A double pole with momentary contacts for remote control, pack of 10 £3.95
box of 50 £19.95	
DC-DC converter, Reliability model, V12P5, 12V in 5V 200mA out, 300V input to output, isolation with data, £4.95 each or pack of 10 - £39.50	
Hour counter used 7 digit 240V ac 50Hz	£1.45
Resistor pack 2500 resistors 1/8-2W 50 different values	£8.95

MODEMS

V22/V22bis IBM PC internal full length card modem, BT approved, can be set to com 1 or 2, 1200/2400 baud with software and manual, not Hayes compatible, made by Plessey, £55.00

V32 9600 baud and 4800 baud GEC Plessey telecom external modem, model 9532, Hayes compatible and BT approved, with auto call, auto answer, using V25, V25bis and Hayes AT protocols and V54 remote + local diagnostics. It does not work on slower speeds, V22/1200 baud etc and needs 1 internal dip switch to be switched on to select Hayes commands. It comes with a 100 + page comprehensive A4 size manual. An all together brilliant machine for only £199 + VAT = £233.83

All products advertised are new and unused unless otherwise stated.

Wide range of CMOS TTL 74HC 74F Linear Transistors kits, rechargeable batteries, capacitors, tools etc. always in stock

Please add 95p towards P&P
VAT included in all prices

IPG ELECTRONICS
276-278 Chatsworth Road
Chesterfield S40 2BH
Access Visa Orders
(0246) 211202
Callers welcome

Metal detector boards with data, has tuner, mode, discriminata, headphone jack, on/off/volume and push button facilities £7.95 ea

Dictaphone cassette, mech/record erase playback heads, 6V solenoid, motor, hall effect switch £2.00 ea

35mm Camera returns with Auto Flash/Wind on etc £5 ea or 2 for £10

TV/Printer stands £2.95 ea

Bicc-Voro Easiwire construction kit £4.95 ea

Cabinet Speakers fro NI-cam TV-Video use £14.95 pair

PCB with Lithium Battery, 2732, 34 IC's + Transisto Fuse, Crystal, R's + C's £4.95 ea

TTL/CMOS short circuit snooper £4.95

Dot matrix LCD 10x2 lines £3.75 ea

with Data £4.95

40 character + 1 line dot matrix display with data £14.95 ea

2 digit 16 segment VF display with data £2.95 ea

4 digit Intelligent dot matrix display £8.00

17 segment VF display with driver board and data £2.99 ea

8 digit liquid crystal display £1.75 ea

4 digit LCD with 7211 driver chip £3.50 ea

Digital clock display £2.50

11 key membrane keypad £1.50 ea

Keyboard 392mmx180mm/100 keys on board + LCD + 74HC05/80C49 easily removable £4.95

18" 3U sub rack enclosures £8.95

12V stepped motor board with slotted opto-2 mercury tilt switches £3.95 ea

1000 mixed 1/4 watt 1% resistors £4.95 ea

250 electrolytic axial/radial caps £4.95 ea

200 off mixed polyester caps £7.95

100 Mixed trimmer caps popular values £4.95

Cable box UHF modulator/video preamp/transformers/R's + C's/leads £6.95

1000 off mixed Multilayer Ceramic Caps £7.95

25 off Mixed crystal oscillators £9.95

Audio Cassette Cleaning + De-magnetizing Kit £1.50

Car Burglar alarm vibration auto entry/exit delay £5.95 ea

Single zone alarm panel auto entry/exit delay housed in domestic light socket £9.95 ea

P.C. P.S.U. 50 watt 115-230V input+5V 4A-12V 2.5A output with built-in fan, IEC inlet-on off £9.95 ea

STC P.S.U. 240V input 5V 6A output (converts to 12V 3A details available) £5.95 ea

240V input 5V 10A output (converts to 12V 5A no details) £5.95 ea

600 line output transformers £1.25 ea

240V in 0-28V 62VA out transformer £2.75

Transformer+PCB gives 2+7.5V 32VA with skt for 5 or 12V regulator, will power floppy drive £3.75 ea

Ultrasonic transducer (transmit+receive) £1.50 pair

3 to 16V Piezoelectric sounders 50p

9V DC electromechanical sounder 50p

24V DC electromechanical sounder 50p

removable in two positions £1.50

DIL switches PCB MT 3/4/6 way 35p

5V SPCO SIL reed relay 40p

5V 2PCO DIL miniature relay 60p

12V 2PCO or 4PCO continental relay 60p

12V 10A PCB MT (to make contact) relay 95p

3 to 12V electro magnetic acoustic transducer with data 75p

2.45/6/8.832/21.10 MHz crystals 50p ea

Bridges 25A 200V £1.00

2A 100V 50p

31b Mixed components pack £4.95

25 off mixed relays £5.95

40 off mixed toggle switches £9.95

50 off mixed switches, toggle, rocker, micro, slide £9.95

miniature axial chokes, 0.1, 0.18, 0.12, 0.33, 0.39, 0.15, 1, 3.30H 10p ea 100 for £7.50

50 Mixed terminal blocks £2.95

250 off 16/22/24/40 way IC Skts £4.95

Crystal Oscillators 10/24/48 MHz £1.00 ea

Spider Plug Leads 75p

100 off Phono plugs (red/blk/grey) £3.50

QUANTITY DISCOUNTS AVAILABLE - PLEASE RING

WE ALSO BUY ALL FORMS OF ELECTRONIC COMPONENTS, P.B.U.S., DISK DRIVERS ETC, LISTS TO BELOW ADDRESS

ALL PRICES INCLUDE V.A.T.
PLEASE ADD £2.00 P&P EXCEPT ITEMS MARKED WHICH ARE 50p S&E FOR BULK BUYING LIST PAYMENT WITH ORDER TO

Dept ETI, COMPELEC,
14 Constable Road, St Ives,
Huntingdon, Cambs PE17 6EQ
Tel/Fax: 0480 300819

Motherboards

286 16 MHz motherboard	£57.00
386SX 25 MHz motherboard	£108.00
386SX 33 MHz motherboard	£118.00
386DX 40 MHz motherboard 64K cache	£195.00
486DX 33 MHz motherboard 256K cache	£395.00
RAM 1 MB SIM module 70ns	£22.50

Interface Cards

IDE Controller, 2 HD, 2FD, 2 Serial, 1 Parallel, 1 Games	£15.95
I/O, 2 Serial, 1 Parallel, 1 Games	£9.95
Mono (Hercules) Interface Board	£12.95
VGA 256K Colour Graphics Board	£29.50
VGA 612K Colour Graphics Board	£35.00
VGA 1M Colour Graphics Board	£49.00
VGA 1M Colour Graphics Board TSENG	£75.00

Cases

features:
★ 200 Watt PSU with Fan and Auxillary Power Socket
★ 7 Segment LED Speed Display
★ LED Indicators for Power, Turbo and HDD
★ Keyboard lock

Desktop Case	£55.00
Mini Tower Case	£54.00
Slim Line Desktop Case	£64.00
Medium Tower Case	£65.00
Full Tower Case	£89.50

Drives

5.25" 1.2 MB Floppy Disk Drive	£37.00
3.5" 1.44 MB Floppy Disk Drive	£30.00
3.5" 40 MB IDE Hard Disk Drive 21ms	£120.00
3.5" 80 MB IDE Hard Disk Drive 17ms	£195.00
3.5" 120 MB IDE Hard Disk Drive 15ms	£235.00
3.5" 210 MB IDE Hard Disk Drive 15ms	£375.00

Monitors

Hercules Mono/TTL monitor	£79.50
VGA 14" Mono Monitor Paper White	£75.00
SVGA 14" Colour Monitor 0.28mm dot	£175.00

Sundry

102 key keyboard (tactile) UK Layout	£22.00
102 key keyboard (alternative) UK layout	£29.50
Mouse + Driver Software	£11.95
Microsoft MSDOS 5.0	£35.00
Microsoft Windows 3.0	£25.00
Microsoft Windows 3.1	£44.00
Printer Cable 25D to 38C	£2.90
3.5" Drive Mounting Kit	£3.75
3.5" Floppy Diskette (inc labels)	£0.49
3.5" 720K Floppy Diskette (pk of 50)	£18.00
3.5" 1.44M Floppy Diskette (inc labels)	£0.87
3.5" 1.44M Floppy Diskette (pk of 50)	£24.50
3.5" Plastic Library Case 10 capacity	£3.95
3.5" Plastic Library Case 40 capacity	£4.45
3.5" Plastic Library Case 80 capacity	£5.45

Base System

All systems include:
★ Mother Board. Now all with 4 MB RAM as standard!
★ Mini Tower or Desk Top Case
★ Interface Controller Card 2xIDE, 2xFloppy, 2 Serial, 1 Parallel, 1 Games Port
★ 3.5" 1.44MB Floppy Drive
★ 102 Key UK Keyboard
★ Includes Cables, Mains Plug

All that is required to make a full system is choose hard disk drive (if required), VDU interface and monitor.

Base System Prices

Grel. 386sx 33MHz	£329.95
Grel. 386dx 40MHz 64K cache	£395.95
Grel. 486dx 33MHz 256K cache	£595.95

All items available separately, please send see for full list.

Terms

Carriage, terms (ADD VAT TO ALL PRICES inc carriage)
carriage on Grel. Systems Components; small items £2.00, maximum £7.95 plus £3.00 insurance if required. Overseas customers No VAT, please ask for quote for carriage.

Payment with order
Credit Cards (Access, Visa) accepted, no surcharge

Interak 1
Z80 Modular Computer System.
Also SBC-1 Z80 Controller (48 i/o lines)
Please send for free leaflet.

Greenbank Electronics Dept ETI12, 460 New Chester Road,
Rock Ferry, Birkenhead, Merseyside L42 2AE. Tel: 051-645 3391.

GREL SYSTEMS

TRADE DISPOSAL SALE

Due to emigration/retirement a dealer in components & equipment has entire stock for disposal. Mostly new components (every type) and various s/h equipment. Available in job lots of our selection. Ideal for radio rallies, shops, mail order, etc. Various size lots from £80 (fill a car), £200 (Transit van), £450 (Luton van), Cash & Carry only. Rock bottom price with excellent profit margin (300%, 400%, Plus) for quick clearance. Bring your vehicle & cash - you won't be disappointed!

Tel: 021 446 4346

Semiconductor Clearance!!

Z80-CPU ED 591! 27C256 £1.37!!! LM334Z ED 491 8085AHC £1.33 6522 £1.43, NE531 ED 79, etc., etc., etc.!!!!

Workshop reorganization enables us to offer a limited quantity of unused stock at an appreciable fraction of the normal price. All components are 100% non-obsolete guaranteed (1000's of items). Microprocessor, logic, linear, discrete, hardware etc., etc. S.A.L.E. for free extensive list.

Profile Electronics (ETI), 100-102 Woodhouse Rd., Leytonstone, London E11 3NA. Minimum order £10.00 please add £2.50 P&P plus VAT at the current rate.
+ 10% Educational Discount on all official orders +

AT LAST HERE IT IS "The World of Bug & Mini Transmitters"

Dozens of circuits in one book. Limited edition only 1,000 copies available. Special Offer only £7.95 inc P&P Cheques, Postal orders to: Gainsford Electronics, 71, Gainsford Road, Southampton, SO2 1AW

FOR SALE

WANTED

TOP QUALITY ★ NEW ★ EX-SOCKET ★ D/SOLD ★ COMPONENTS

DRAM'S		DRAM'S	
8118	ex sock 0.47	4164	NEW 0.71
4164	ex sock 0.47	41256	NEW 1.77
41256	ex sock 0.71	41C1000	de/sol 1.18
41464	de/sol 1.18		
STATIC'S		STATIC'S	
6167LP-8	ex sock 0.71	6116	0.59
6264LP	ex sock 1.18	62256LP	ex sock 2.35
MISC		MISC	
AM7910DC	ex sock 3.53	D765AC	ex sock 0.58
8031AH	ex sock 0.71	80C85A	ex sock 1.18
81C55	ex sock 0.71	AY-3-8910	ex sock 1.18
8237A	NEW 1.18	8250N	ex sock 1.41
8255A	ex sock 1.18	8753H	ex sock 2.35
Z80ACPU	ex sock 1.18	8755A	NEW 3.53
8748H	ex sock 2.94	8749H	ex sock 2.94
Z80BCPU	NEW 1.41	V20-8	NEW 3.53

UK Customers only. Please send cheques PO's or reg' cash. Please add 1.20 for P&P. Goods despatched ASAP allowing for cheque clearance. ALL above components are including VAT. Please make cheques PAYABLE TO: "MAIL ELECTRONICS".

UNIT 6 FORBES COURT, BILLINGTON ROAD, BURNLEY, LANCAS, BB1 5UB TEL/FAX 0282 26670

WE ALSO STOCK NEW: CAPS, DIODES, REGULATORS, IC SOCKETS EPROMS, XTALS, OSC, CMOS, 74, LS, HC, HCT, ALS, TRANSISTORS, LINEARS, ALL AT LOW LOW PRICES. RING TODAY 0282 26670 Note - ALL PRICES ARE SUBJECT TO AVAILABILITY AND CHANGE WITHOUT NOTICE.

CATALOGUE £1.00 + 25p P&P

LED's 3mm or 5mm red or green 10p each yellow 11p each
High intensity red green or yellow 30p each
Cable ties 1p each ES 95 per 1000 £49.50 per 10,000
Sleeping motor 4 phase 12v 1/8 amp 50 £8.95
SAI1027 sleeping motor driver 800 27.95
FM Transmitter kit good quality based 18.00
High quality photo resist copper clad epoxy glass boards
Dimensions angle edged double sided
34 inches £3.95 £1.07
44 inches £2.40 £2.85
8x12 inches £5.27 £1.66
12x12 inches £10.66
Special Offers
20 regular grade capacitors with screw terminals 39000uf 20v £2.50
87000uf 10v £1.95, 66000uf 15v £2.95, 10000uf 15v £1.50
4 weight common anode led display 12mm 10.45
L42S31AT3 0 low drop out 5v regulator TO220 package 08.95
ES250 P channel mosfet £8.45, OC159 transistor £3.95 per 100
74LS50 hex inverter £10.00 per 100, used 8748 Microcontroller £3.50
TV Motor switch 44 double pole with momentary contacts for remote control pack of 10 £3.95 box of 60 £19.95
DC-DC converter Reliability model V12PS 12v in 5v 200ma cl. 300v input to output isolator with data £4.95 each or pack of 10 £30.50
Rear counter used 7 digit 240v ac 50Hz £1.45
White range of CMOS TTL R4NC 74F Linear Transistors kits
Resistor pack 2500 resistors 1/8 20 different values 10.00
CONVERTY keyboard 50 keyboard output no data (used) 25.00
Wide range of CMOS TTL R4NC 74F Linear Transistors kits
rechargeable batteries cassette tape etc always in stock. Please add 50p towards P&P per order

JPG ELECTRONICS
278-278 Chatsworth Road Chesterfield S40 2BH
Access/Via Orders (0246) 211202 callers welcome

TURN YOUR SURPLUS TRANSISTORS, IC'S ETC INTO CASH immediate settlement.

We also welcome the opportunity to quote for complete factory clearance.

Contact: **COLES-HARDING & CO.**
Sandall Road, Wisbech, Cambs PE13 2PS

BUYERS OF SURPLUS INVENTORY ESTABLISHED OVER 15 YEARS
Tel: 0945 584188
Fax: 0945 475216

EDUCATIONAL

STUDY ELECTRONICS ON A 'PC'. Over 80 fully interactive, menu driven, graphics screens, containing charts, graphs, circuit diagrams, formulae and theory. With user inputs and calculated outputs. Covers subject from electron flow, through analysis of AC and DC circuits, to semi-conductors. £39.95 + £2.00 p.p. Credit Card orders 0376-514008. SAE for details.
E.P.T. Educational Software, Pump House, Lockram Lane, Wiltham, Essex CM8 2BJ.

FREE I.C. AMPLIFIER module! Built & directions - return add + £1 p.p. K.I.A. 1 Regent Road, Ilkley. Stereoamps & controls, sockets - Reg/PSU - 60W/£10.

KITS

NEW VHF MICROTRANSMITTER KIT tuneable 80-135 MHz, 500 metre range, sensitive electret microphone, high quality PCB, SPECIAL OFFER complete kit ONLY £5.95, assembled and ready to use £9.95 inclusive P&P. Credit card orders telephone 021 411 1821, Fax: 021 411 2355. Cheques/PO's to: Quantek Electronics, (Dept ETI) 3 Houldry Rd, Birmingham, B31 3HL. Send S.A.E. for details of this and other kits. - Callers welcome.

Are you looking for true quality. Micro, FM, Transmitter Kit. The superb all new model Vancap tuned, a plifier stage, Omni Directional Mic, Roller Tined, Fibre Glass PCB, true 1 mile range 9V DC £5.95 inc pp. Mini Micro Kit. As above only 1/2 size 25x154/M. 1 1/2 VDC Watch battery, 1/2 mile range Roller Tined PCB £8.95 inc pp. Immediate next day despatch from stock.
PRECISION TIME, 65, Roseland Road, Wauverhydd, Swansea SA5 4ST.

HEATHKIT. U.K. spares and service centre/Educational Products Distributor. Cedar Electronics, 12, Isbourn Way, Winchcombe, Cheltenham GL54 5NS Tel. (0242) 602402.

TEST EQUIPMENT

LOGIC ANALYSER
Turn your PC Compatible into a powerful Logic Analyser. Full graphics display, Max 16 Channels, 4 combinational triggers, auto calibration. Excellent value. Includes 8 input lead probes. Send £29.99 or S.A.E. for details.
J.P. Shay (Dept ETI) 211 Ainsworth Road, Redcliffe, Manchester M26 0EE.

COOKE INTERNATIONAL TEST INSTRUMENTS

AUTUMN CLEARANCE BARGAINS

Scopex 456 Single Beam Scopes	£65.00
Tequipment D61 Portable Scopes DC-15MHz	£95.00
Fluke 8300A Digital Voltmeters	£125.00
Racal 835 Universal Timer/Counters DC-15MHz	£35.00
H.P. 612A UHF Signal Generators 450-230MHz	£90.00
Advance P.S.U. 0-60V 0-1A	£35.00
H.P. 1402A Dual Trace Amp DC-20 Mhz	£25.00
Marconi TF 1245 Magnification "Q" Meters	£155.00
Marconi TF 1246 Oscillators for above	£95.00

Many more items available. Send S.A.E. for lists. Original W/Shop manuals for sale send S.A.E. for lists. Computers, monitors etc. In stock. Phone for details.

All prices exclude VAT & Carriage. Open Mon-Fri 9am-5pm Saturday by arrangement. Cooke International, Units 4/5 Fordingbridge Site, Main Road, Barnham, Bognor Regis West Sussex PO22 0EB.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60 OUTPUT 0-280V

Output	Price	P&P
0.5KVA 2.5 amp max	£29.00	£4.65
	(£39.54 inc VAT)	
1KVA 5 amp max	£37.40	£6.25
	(£51.29 inc VAT)	
2KVA 10 amp max	£64.00	£7.80
	(£72.62 inc VAT)	
3KVA 15 amp max	£71.50	£7.80
	(£93.18 inc VAT)	
5KVA 25 amp max	£126.60	

(Plus Carriage)
Buy direct from the Importers. Keenest prices in the country

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO

(110-240V Auto transfer either called with American socket and mains lead or open frame type. Available for immediate delivery.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 4 watt £12.00 (callers only)	(£14.10 inc VAT)
2ft 20 watt £7.44 + £1.25 p&p	(£10.21 inc VAT)
13in 10 watt £6.80 + 75p p&p	(£7.70 inc VAT)
12in 8 watt £4.80 + 75p p&p	(£6.82 inc VAT)
9in 8 watt £3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt £3.96 + 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £6.50 + £1.15 p&p (£7.81 inc VAT)
For 13in tubes £6.00 + £1.35 p&p

400 WATT UV LAMP

Only £34.00 - £2.50 p&p (£42.89 inc VAT)
160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB

Available with BC or ES fitting, price inc VAT & p&p and VAT £25.55

SAVE POUNDS. Build your own forged bank note detector. Will detect counterfeit amongst quantity of notes. Complete kit & parts less case for 240 volt AC OP inc. 6" UV black light tube/ starter and holder. Pair Bi-pin leads circuit instruction.
Total price P&P VAT £13.06

SUPER HY-LIGHT STROBE KIT

Designed for Disco. Theoretical use etc. Approx 15 joules. Adjustable speed £60.00 + £3.00 p&p (£62.28 inc VAT)
Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT). SAE for further details including Hy-Light and industrial Strobe Kits.

"BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit, internally in excellent condition. Designed primarily to eject a precisely controllable amount of fluid from a medical syringe (filter not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS. Escap Precision 12V DC Motor with precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends. Audible warning.
These are sold for the dismantling of the exceptional quality components. Regret no Circuits available. Ridiculously low price £16.00 + £4.00 p&p (£23.50 inc VAT).

WIDE RANGE OF XENON FLASHTUBES

Write/Phone your enquiries

12V D.C. GEARED MOTOR

12V D.C. Reversible precision-built Motor. Output speeds no load approx. 12V-28 rpm; 9V-20 rpm; 6V-12 rpm. Will work at lower voltages and still retain a reasonable torque. Ideal for robotics etc. Size: L 40mm, W 29mm, H 39mm. Shaft: 3mm dia x 10mm long. Price: £8.00 + 50p p&p (£10.00 inc VAT)

TORIN CENTRIFUGAL BLOWER

230V AC, 2800 RPM, 0.9 amp, 130mm diameter, impeller outlet 63 x 37mm, overall size 165 x 150 x 150mm long. Price £17.50 + £2.50 p&p (£23.50 inc VAT)

SOLID STATE RELAY

7 amp in 240V, A.C. when mounted on suitable Heat-sink. Can be driven from T.T.L. or Computer output between 3-10V D.C. Size 24mm x 17mm x 15mm high. Firing centres 30mm (TO-3). Price: £3.00 + 40p p&p (£4.00 inc VAT)

GEARED MOTORS

71 RPM 20th inch torque motors 115V AC in. put including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £23.50.

SOLID STATE EHT UNIT

Input 230/240V AC. Output approx 15kV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec. 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

12V D.C. BILGE PUMPS

Buy direct from the importers.
500 GPH 15ft head 3 amp £18.21
1750 GPH 18ft head 9 amp £31.72
PRICE INCLUDE P&P & VAT

EPROM ERASURE KIT

Build your own EPROM ERASURE kit for a fraction of the price of a made-up unit. Kit of parts less case includes 12in 8 watt 2637 Argon Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £14.00 + £2.00 p&p (£18.80 inc VAT)



COMPONENTS

"ELECTRO COMP"

WE CLEAR

Electronic Components • Semiconductors
Computer Equipment • Electronic Test Equipment
Populated Boards

In fact anything with an electronic bias
JOB LOTS, FACTORY CLEARANCE A SPECIALITY
Decision normally within 24-36 hours

LOOKING FOR COMPONENTS!! As an ex Industrial buyer for 25 years I won't sell you reject or faulty product!! Only top quality components at the right price!! No Mail Order only production quantities!!

SNAGS only one. My terms are C.O.D. Deliveries normally made within 48 hours

Phone or Fax your list or enquiry to: 0635 46496
ELECTROCOMP 36 Talbot Close, Newbury, Berks RG13 1UA

SERVICE TRADING CO
57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
FAX 081 995 0549 081-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

Visa
Ample Parking Space



EDITORIAL

Editor *Paul Freeman*

CREATIVE

Art Editor *Peter Kirby*

Designer *Iain Houston*

Technical Illustration *Tony Burlinson*

Photography *Manny Cefai*

ADVERTISEMENT SALES

Advertisement Manager

Mark Linacre

Advertisement Sales

Michele Donovan

Advertisement Copy Control

Marie Quilter

Key Accounts Manager

Donna Wells

MANAGEMENT

Managing Director

Terry Pattison

Circulation & Promotions Manager

Debra Stupple

Production Manager

Tony Dowdeswell

Group Editor

Stuart Cooke

Group Advertisement Manager

Claire Jenkinson

ISSN
0142-7229



Member of the
Audit Bureau
of Circulation

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and reproduction requires the prior written consent of the company ©1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

● Subscription rates... UK £23.40 Europe £29.50 Sterling Overseas £31.00 US Dollars Overseas \$62.00

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST. Telephone (0442) 66551. UK newstrade distribution by SM Distribution Ltd, 6 Leigham Court Road, London SW18 2PG. Telephone 081 667 8111. Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST. Telephone (0442) 66551. Subscriptions by Argus Subscription Services, ETI Queensway House, 2 Queensway, Redhill, Surrey RH1 1QS. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. Telephone (310) 375 6258. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd, Bristol.



Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (0442) 66551 Fax (0442) 66998

Next Month

In our Christmas issue we have an interesting selection of projects for you. The next two cover PCBs will form the basis of a four channel infra-red remote controlled switching system. The receiver, presented next month is built to fit into a 'lightswitch-sized' box and is designed to work with commercially available touch dimmers. The transmitter will follow on in the February issue.

Something completely different on the project front for next month is a Macro-Heliograph receiver. A what? - you say! It's a device to detect very low frequency/very low power sound waves emanating from your garden using sunlight. There's nothing quite like it!

We also have an EPROM Programmer project for you to construct. Then there will be no fear of tackling projects containing EPROMs. Also as it is Christmas, the seasonal fading fairy lights could adorn your tree. See the January issue for details. **Out on Friday December 4th.**

The above articles are in preparation but circumstances may prevent publication

Last Month

Our November issue featured:

- Nanotechnology
- The Ten Year Capacitor
- Auto Protection
- AutoMate Pt7b
- Audio Response Measuring System
- Basic Multimeter Circuits
- Universal I/O Interface for the PC Pt2
- Electronic Die for Board Games
- Differential Calculus

Back issues can be obtained from Argus Subscription Services. Address in column to left.

ADVERTISERS' INDEX

AUTONA	31	JPG ELECTRONICS	35
BK ELECTRONICS	IFC	LABCENTRE	60
CIRKIT	14	M & B	IBC
CRICKLEWOOD ELECTRONICS ...	47	MAPLINE ELECTRONICS	OBC
DISPLAY ELECTRONICS	30	NUMBER ONE SYSTEMS	13
ESR ELECTRONICS	11	OMNI ELECTRONICS	53
HALCYON ELECTRONICS	21	PICO TECHNOLOGY	15
HENRY'S	35	RALFE ELECTRONICS	31
HENSING TECHNOLOGY	53	REED ELECTRONICS	31
J&N BULL	22	S.L.M. MODEL ENGINEERING	21
JAY TEE ELECTRONICS	53	STEWARTS OF READING	31

- £1 BARGAIN PACKS -

In fact, cheaper than £1 because if you buy 10 you can choose one other and receive it free!

- 2 x 25W CROSSOVERS for 4 ohm loudspeakers. Order Ref. 22
- 2 x NICAD CONSTANT CURRENT CHARGERS easily adaptable to charge almost any nicad battery. Order Ref. 30
- 10m TWIN SCREENED FLEX white pvc cover. Order Ref. 122
- 2 x WHITE PLASTIC BOXES with lids, approx. 3" cube. Lid has square hole through the centre so these are ideal for light operated switch. Order Ref. 132
- 2 x REED RELAY KITS you get 8 reed switches and 2 coils sets with notes on making relays and other gadgets. Order Ref. 148
- 1 x BIG PULL SOLENOID mains operated. Has 1/2" pull. Order Ref. 871
- 1 x BIG PUSH SOLENOID mains operated. Has 7/8" push. Order Ref. 872
- 1 x MINI MONO AMP 3W into 4 ohm speaker or 1W into 8ohm. Order Ref. 268
- 1 x MINI STEREO 1W AMP. Order ref. 870
- 1 x IN-FLIGHT STEREO UNIT is a stereo amp. Has two most useful mini moving coil speakers. Made for BOAC passengers. Order Ref. 29
- 1 x MAGNETIC SECRET SWITCH does not look like a switch and is supplied with a separate magnet to to operate it. Order Ref. 873
- 1 x 0-1mA PANEL METER full vision face 70mm square. Scaled 0-100. Order Ref. 756
- 2 x LITHIUM BATTERIES 2.5V penlight size. Order Ref. 874
- 2 x 3M TELEPHONE LEADS with BT flat plug. Ideal for phone extensions, fax, etc. Order Ref. 552
- 1 x 12V SOLENOID has good 1/2" pull or could push it modified. Order Ref. 232
- 4 x IN-FLEX SWITCHES with neon on/off lights saves leaving things switched on. Order Ref. 7
- 2 x 6 1A MAINS TRANSFORMERS upright mounting with fixing clamps. Order Ref. 9
- 12 x 30 WATT REED SWITCHES. It's surprising what you can make with these - burglar alarms, secret switches, relay, etc. Order Ref. 13
- 2 x HUMIDITY SWITCHES, as the air becomes damper the membrane stretches and operates a micro switches. Order Ref. 32
- 3 x 13A ROCKER SWITCH three tags so on/off, or changeover with centre off. Order Ref. 42
- 2 x FLAT SOLENOIDS you could make your multi tester read AC amps with this. Order Ref. 79
- 1 x SUCK OR BLOW OPERATED PRESSURE SWITCH or it can be operated by any low pressure variation such as water level in water tanks. Order Ref. 67
- 1 x 6V 750mA POWER SUPPLY, nicely cased with mains input and 6v output leads. Order Ref. 103A
- 2 x STRIPPER BOARDS, each contains a 400V 2A bridge rectifier as well as dozens of condensers, etc. Order Ref. 120
- 12 x VERY FINE DRILLS for pcb boards etc. Normal cost about 80p each. Order Ref. 128
- 5 x MOTORS FOR MODEL AEROPLANES, spin to start so needs no switch. Order Ref. 134
- 6 x MICROPHONES INSERTS magnetic 400 ohm also act as speakers. Order Ref. 139
- 6 x NEON INDICATORS in panel mounting holders with lens. Order Ref. 180
- 1 x MAINS SOLENOID very powerful as 1/2" pull or could push it modified. Order Ref. 199
- 1 x ELECTRIC CLOCK mains operated, put this in a box and you need never be late. Order Ref. 211
- 4 x 12V ALARMS makes a noise about as loud as a car horn. All brand new. Order Ref. 221
- 2 x (8" x 4") SPEAKERS 16 ohm 5 watts so can be joined in parallel to make a high wattage column. Order Ref. 243
- 1 x PANOTSAT controls output of boiling ring from simmer up to boil. Order Ref. 252
- 2 x OBLONG PUSH SWITCHES for bell or chimes, these can switch mains up to 5A so could be foot switch if fitted in pattern. Order Ref. 263
- 50 x MIXED SILICON DIODES. Order Ref. 293
- 1 x 6 DIGIT MAINS OPERATED COUNTER standard size but counts in even numbers. Order Ref. 28
- 2 x 6V OPERATED REED RELAYS one normally on, other normally closed. Order Ref. 48
- 1 x CABINET LOCK with 2 keys. Order Ref. 55
- 1 x MAGNETIC BRAKE for stopping motor or rotating tool. Order Ref. 65
- 1 x SHADED POLE MAINS MOTOR 1/2" stack so quite powerful. Order Ref. 85
- 2 x 5" ALUMINIUM FAN BLADES could be fitted to the above motor. Order Ref. 86
- 1 x CASE 3 1/2 x 2 1/2 x 1 1/2 with 13A socket pins. Order Ref. 845
- 2 x CASES 2 1/2 x 2 1/2 x 1 1/2 with 13A pins. Order Ref. 565
- 4 x LUMINOUS ROCKER SWITCHES 10A mains. Order Ref. 793
- 4 x DIFFERENT STANDARD V3 MICRO SWITCHES. Order Ref. 340
- 4 x DIFFERENT SUB MIN MICRO SWITCHES. Order Ref. 313
- LIGHTWEIGHT STEREO HEADPHONES moving coil so superior sound. Order Ref. 896
- LOUDSPEAKER 6 1/2" 4 OHM 12 Watt max. Order Ref: 900.

BARGAINS - GALORE

DRY BATTERIES CAN BE RECHARGED but not with a normal d.c. charger, it must be a periodic current reversal type. We can supply the kit, with data. £9. Order Ref. 9P10.

SOLAR ENERGY EDUCATIONAL KIT - an ideal present for electronics students, it shows how to make solar circuits and electrical circuits, how to increase the voltage or current, how to use solar power to work a radio, calculator, cassette player and to charge nicad batteries. The kit comprises 8 solar cells, one solar motor, fan blades to fit motor and metal frame to hold it to complete a free-standing electric fan. A really well written instruction manual makes this a lovely little present. Price £8.00. Order Ref. 8P42B

HEAVY DUTY FLEX 3 core 15A, grey outer, 10m for £2.50, Order Ref. 2 5P3 3 core 20A, white outer, 10m for £3, Order Ref. 3P109 2 core 20A, 15m for £3, Order Ref. 3P110

HIGH POWER SWITCH MODE PSU normal mains input. 3 outputs: -12V at 4A, +5V at 16A and -12V at 1/2A. Completely enclosed in plated steel case. Brand new. Our special offer price of £9.50 extended until 31st August. Order Ref. 9 5P1

MULTI-CORE CABLES all with 8A 230V cores so suitable for disco and other special lighting effects. With earthen cable woven screen and thick pvc outer. 3 core, 30p per metre, 16 core 50p per metre, 18 core, 80p per metre, 25 core, £1 per metre and 36 core, £1.50 per metre

ULTRA THIN DRILLS Actually 0.3mm. To buy these regular cost a fortune. However, these are packed in half dozens and the price to you is £1 per pack. Order Ref. 797B

YOU CAN STAND ON IT! Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools. Internal size approx. 10 1/2" x 4 1/2" x 6" high. These are complete with snap closure lip and shoulder-length carrying strap. Taken from used equipment but in good condition, price £2. Order Ref. 2P283B

POWER SUPPLY WITH EXTRAS mains input is fused and filtered and the 12V dc output is voltage regulated intended for high class equipment, this is mounted on a PCB and also mounted on the board but easily removed, are 2 12V relays and a Piezo sounder. £3. Order Ref. 3P80B

ULTRA SONIC TRANSDUCERS 2 metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref. 1 5P/4

100W MAINS TRANSFORMER normal primary 20-0-20 at 2.5A. £4. Order Ref. 4P24 40V at 2.5A, £4, Order Ref. 4P59 50V at 2A, £4, Order Ref. 4P60

PHILIPS 9" HIGH RESOLUTION MONITOR black & white in metal frame for easy mounting, brand new still in maker's packaging, offered at less than price of tube alone, only £15, Order Ref. 15P1

16 CHARACTER 2-LINE DISPLAY screen size 85mm x 36mm, Alphanumeric LCD dot matrix module with integral; micro processor made by Epson, their Ref. 16027Ar, £8, Order Ref. 8P48

INSULATION TESTER WITH MULTI METER internally generates voltages which enables you to read insulation directly on megohms. The multimeter has four ranges, AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each yours for only £7.50, with leads, carry case £2 extra, Order Ref. 7 5P/4

MAINS 230V FAN best make "PAPST" 4 1/2 square, metal blades, £8. Order Ref. 8P8

2MW LASER Helium neon by Phillips, full spec. £30, Order Ref. 30P1. Power supply for this kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well £18, Order Ref. 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £69, Order Ref. 69P1

1/3 HP 12V MOTOR - THE FAMOUS SINCLAIR C5 brand new. £15, Order Ref. 15P8

SOLAR CHARGER holds 4AA nicads and recharges these in 8 hours, in very neat plastic case, £6, Order Ref. 6P3

FERRITE AERIAL ROD 8" long x 3/8 diameter, made by Mullard. Complete with 2 coil forms. 2 for £1, order Ref. 832B

AIR SPACED TRIMMER CAPS 2-20 pF ideal for precision tuning UHF circuits, 4 for £1, Order Ref. 818B

MAINS ISOLATION TRANSFORMER stops you getting "to earth" shocks. 230V in and 230V out. 150 watt upright mounting, £7.50, Order Ref. 7 5P/5 and a 250W version is £10, Order Ref. 10P79

5RPM MAINS DRIVEN This is a shaded pole motor. £5, Order Ref. 5P54

POWER SUPPLY UNIT mains in, dc out, cased 4 5V 100mA £1, Order Ref. 104 6V 200mA £1, Order Ref. 103 6V 700mA £1, Order Ref. 103A 24V 200mA £2, Order Ref. 2P4 12V 2A £6, Order Ref. 6P23

AMSTRAD POWER UNIT 13 5V at 1.9A encased and with leads and output plug, normal mains input, £6, Order Ref. 6P23

ATARI 65XE at 65K this is quite powerful, so suitable for home or business, unused and in perfect order but less PSU, only £19.95, Order Ref. 19 5P/5B

80W MAINS TRANSFORMERS two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref. 3P106 the other 40V 2A, Order Ref. 3P107, only £3 each

PROJECT BOX is approx 8" x 4" x 4 1/2" metal sprayed grey, louvred ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref. 3P74

WATER VALVE 230V operated with hose connections, ideal for auto plant spray or would control air or gas into tanks etc. £1 each, Order Ref. 370

BT POWER SUPPLY UNIT output 9 5V AC at 600mA, in black plastic case with 13A plugs to go straight into socket and approximately 3 metres of twin output lead. Price £1.50, Order Ref. 1 5P7

BUILDING YOUR OWN PSU, battery charger, night light, or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket? We have two cases, one 3 1/2" x 2 1/2" x 1 1/2" deep, £1 each, Order Ref. 845. The other one is 2 1/2" x 2 1/2" x 1 1/2" deep, 2 for £1, Order Ref. 565.

500V BRIDGE MEGGER developed for GPO technicians the Ohmter 18B is the modern equivalent of the bridge megger. 9V battery operated, it incorporates a 500V generator for insulation testing and a null balance bridge for very accurate resistance measurement. Ex B.T. in quite good condition with data & tested. Yours for a fraction of the original cost, £45, Order Ref. 5P167

EXPERIMENTING WITH VALVES don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250V at 75mA and 6.3V at 3A. £5, Order Ref. 5P167

15W 8 OHM 8" SPEAKER & 3" TWEETER made for discontinued high quality music centre, gives real hi-fi, and only £4 per pair, Order Ref. 4P57

3V SOLAR PANEL price £3, Order Ref. 5P189

WATER PUMP very powerful with twin outlets, an ideal shower controller, mains operated, £10, Order Ref. 10P74. Ditto but with a single outlet, same price & order ref. Please specify which one you require

0-1MA FULL VISION PANEL METER 2 1/2" square, scales 0-100 but scale easily removed for re-writing. £1 each, Order Ref. 756

VU METER illuminate this from behind becomes on/off indicator as well, 1 1/2" square, 75p each, Order Ref. 366

EDGE-WISE PANEL METER ideal when short of panel space only 40 x 14mm, also have built-in led, 500µA f.s.d., scaled 0-5, £1 each, Order Ref. 131

THIS MONTH'S SNIP is a Japanese-made 12v DC or battery operated, brushless axial fan. 93mm square, its optimum is 12 bit it performs equally well at only 6v and its current then is only 100mA so it could be made into a hand-held dry battery-operated cooler. Or, on your desk operated by a p.s.u. or in the car using the lighter socket. Snip price only £4, Order Ref. 4P65. Mains power unit to operate this at variable speeds, £2, Order Ref. 2P3

MOVEMENT ALARM goes off, with the slightest touch. Ideal to protect car, cycle, doorway, window, stairway, etc. etc. Complete with Piezo shrieker, ready to use. Only £2 (PP3 battery not supplied). Order Ref. 2P282

PROJECT BOX a first-class, Japanese two-part moulding size 95 x 66 x 23mm held together by 2 screws, take a battery and a PCB and is ideal for many projects. To name just a few, the washer bottle monitor, the Quickestest and the model railway auto signal, described in September's issue of E.E. This is nicely finished and very substantial. You get 2 for £1, Order Ref. 876

HOLD IT MAGNETIC BASE embedded in a circular metal shallow disc, diameter approx. 65mm (2 1/2"), is the most powerful magnet. We have yet to find anyone who can remove this with his fingers. Ideal for adding extra shelves inside a metal case or to glass without drilling. Its uses, in fact, are innumerable. Price £2 each, Order Ref. 2P296

AM/FM MAINS RADIO CHASSIS with separate LCD module to display date and time. This is complete with loudspeakers and is main powered but it is not cased. Price £3.50, Order Ref. 3 5P5

2, 3 AND 4 WAY TERMINAL BLOCKS the usual grub screw types. Parcel containing a mixture of the 3 types, giving you 100 ways for £1, Order Ref. 875

12/24V DC SOLENOID constructed so that it will push or pull, plunger is a combined rod and piston. With 24v is terrifically powerful but is still very good at 12v and, of course, with any intermediate voltage with increasing or decreasing power. It has all the normal uses of a solenoid and an extra one, if wired in series with a make and break, this could be a scribing tool for marking plastics and soft metals. We welcome other ideas and will give a £25 credit voucher for any used. Price £1, Order ref. 877

2M 3-CORE LEAD terminating with flat pin instrument socket, £1, Order Ref. 879. Ditto but with plug on the other end so that you could use this to extend an instrument lead. £1.50, Order Ref. 1 5P10

20W 5" 4 OHM SPEAKER mounted on baffle with front grille, £3, Order Ref. 3P145. Matching 4 ohm 20W tweeter on separate baffle, £1.50, Order Ref. 1 5P9

LIMITED SUPPLY ITEMS

are only described in our newsletter. Over 50 appear in our current issue. If you order something this month you will receive this and the next three issues posted to you free of charge.

Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing. Order over £25 post free.

M & B ELECTRICAL SUPPLIES LTD

12 Boundary Road, Hove, Sussex BN3 4EH


Telephone (0273) 430380
Fax or phone (0273) 410142

BUYER'S GUIDE TO ELECTRONIC COMPONENTS 1993

Maplin



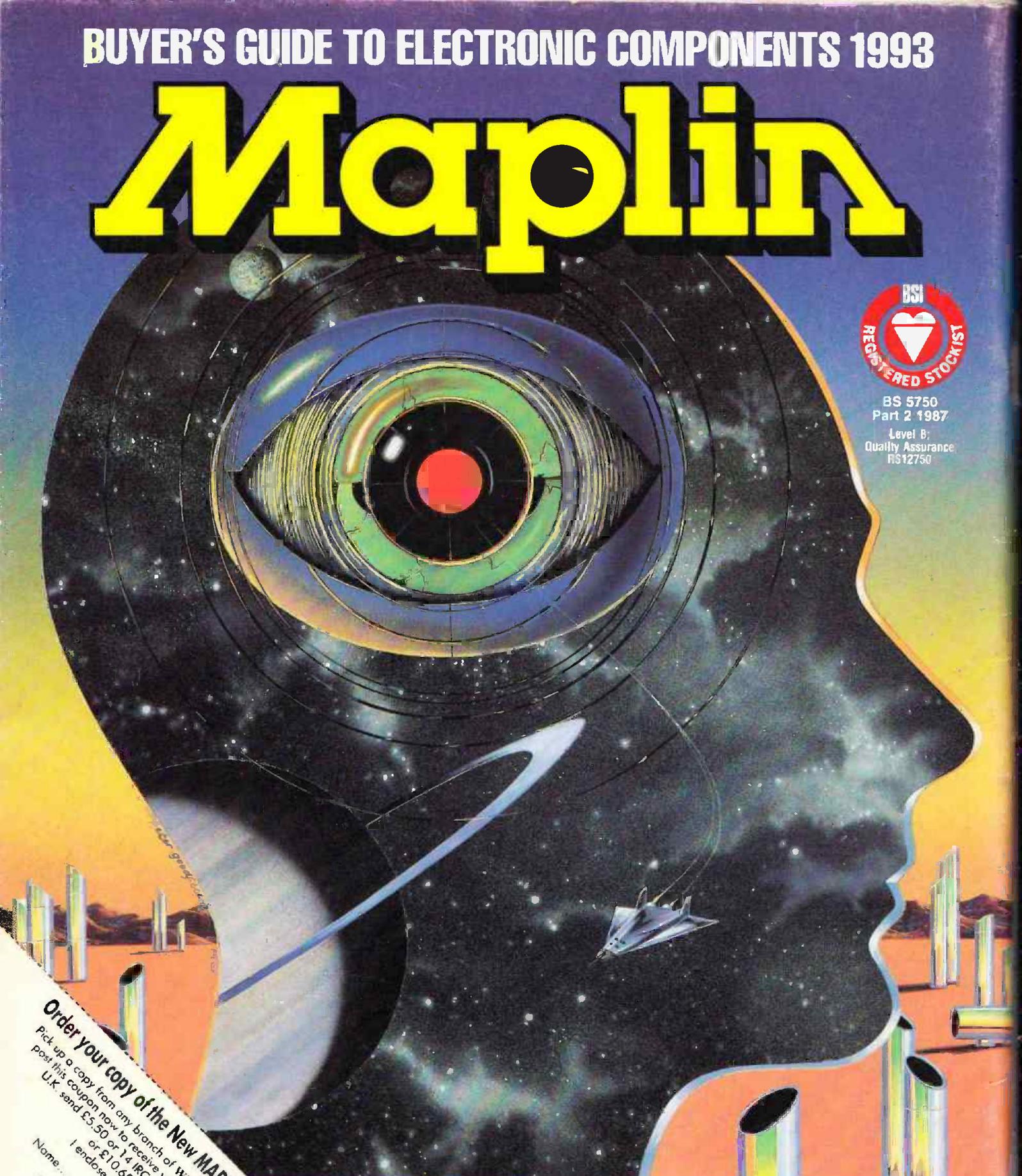BS 5750
Part 2 1987
Level B:
Quality Assurance
RS12750



Order your copy of the New MAPLIN Catalogue on sale NOW!
Pick up a copy from any branch of WHSMITH or from our chain of shops for just £2.95 or
post this coupon now to receive your copy for just £3.45 inc. p&p. If you live outside the
U.K. send £5.50 or 14 IRC's for Airmail in Europe/surface mail outside Europe.
I enclose £3.45/£5.50/£10.65 (delete as applicable).

Name.....
Address.....
Post Code.....
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England,
SS6 8LR,
E193

**Over 700 product packed pages with
hundreds of brand new products.
On sale now, only £2.95**

Available from all branches of WHSMITH and
Maplin shops nationwide. Hundreds of new
products at super low prices!