




ELECTRONICS
TODAY INTERNATIONAL

JANUARY 1993 £1.95

**REMOTE CONTROLLED
INFRA RED FOUR CHANNEL**

DIMMER
**Build this IR
receiver**

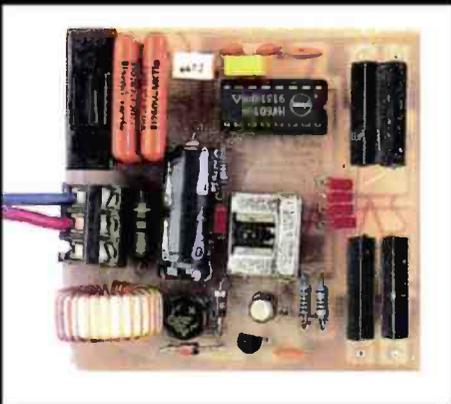

**using our
cover PCB**

Please tell
your retailer
if the PCB
is missing



FADING FESTOONERY

**Make your tree lights
twinkle**




**EPROM
PROGRAMMER**



**MACRO-
HELIOGRAPH
RECEIVER**

**Detect the
undetactable**

**BASIC
MULTIMETER
CIRCUITS**

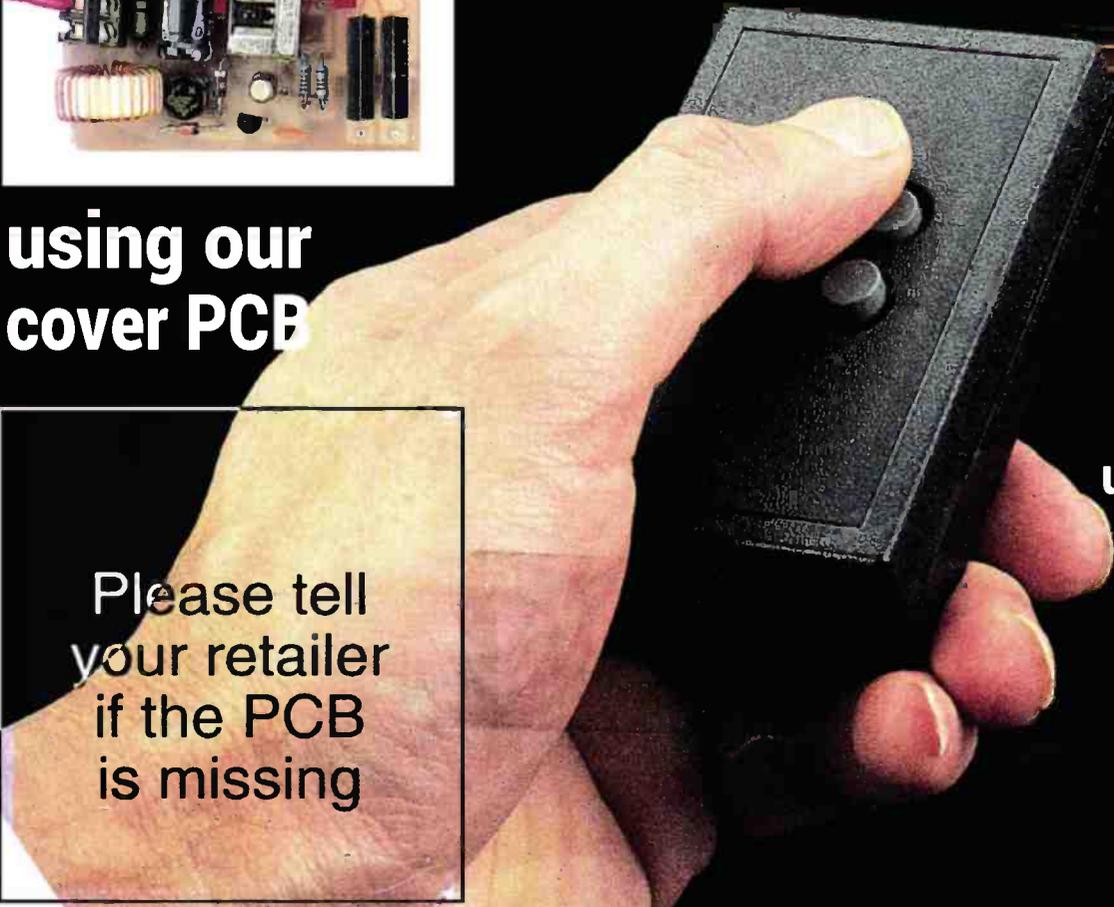

OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)
ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ KLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker end thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
MXF400 W19" x H5 1/4" (3U) x D12"
MXF600 W19" x H5 1/4" (3U) x D13"
MXF900 W19" x H5 1/4" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH



OMP VARISPEED TURNABLE CHASSIS



★ Manual arm ★ Steel chassis ★ Electronic speed control 33 & 45 R.P.M. ★ Vari pitch control ★ High torque servo driven DC motor ★ Transit screws ★ 12" die cast platter ★ Neon strobe ★ Calibrated balance weight ★ Removable head shell ★ 1/2" cartridge fixings ★ Cue lever ★ 220/240V 50/60Hz ★ 390x305mm ★ Supplied with mounting cut-out template.

PRICE £61.30 + £3.70 P&P

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500MKII GOLDRING G950
PRICE £16.95 + 50p P&P PRICE £7.15 + 50p P&P

STEREO DISCO MIXER DJ6500

★ WITH ECHO ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalizers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with tone control & talk-over switch, 7 Channels with individual faders plus cross fade, Cue Headphone Monitor. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.

Price £134.99 + £5.00 P&P



SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series. FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.

- TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
- TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
- TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
- TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
- TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
- LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE

Made especially to suit today's need for compactness with high output sound levels, finished in hard wearing black vinyl with protective corners, grille and carrying handle. Each unit incorporates a 12" driver plus high frequency horn for a full frequency range of 45Hz-20KHz. Both models are 8 Ohm impedance. Size: H20" x W15" x D12".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100WATTS (100dB) PRICE £163.50 PER PAIR
OMP 12-200WATTS (200dB) PRICE £214.55 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR



IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS

150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 - 125) Stereo, 250W Bridged Mono
400 WATTS (200 - 200) Stereo, 400W Bridged Mono

ALL POWERS INTO 4 OHMS
Features:
★ Stereo, bridgeable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection

OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



**OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P**



**OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P**



**OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P**



**OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P**

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D.s (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control for very fast rise and decay times. Tough moulded plastic case, with acrylic tinted front. Size 84 x 27 x 45mm.
PRICE £8.70 + 50p P&P

LOUDSPEAKERS

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (50p STAMPED) FOR COMPLETE LIST.

From McKenzie Professional Series
From McKenzie Studio Series

McKENZIE- INSTRUMENTS, P.A., DISCO, ETC

- ALL MCKENZIE UNITS 8 OHMS IMPEDANCE
- 8" 100 WATT CB-100GP GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £31.45 + £2.00 P&P
- RES. FREQ. 30Hz, FREQ. RESP. TO 7KHz, SENS 96dB.
- 12" 100 WATT C10-100GP GUITAR, VOICE, KEYBOARD, DISCO, EXCELLENT MID. PRICE £38.89 + £2.50 P&P
- RES. FREQ. 72Hz, FREQ. RESP. TO 6KHz, SENS 97dB.
- 10" 200 WATT C10-200GP GUITAR, KEYB'D, DISCO, EXCELLENT HIGH POWER MID. PRICE £53.21 + £2.50 P&P
- RES. FREQ. 69Hz, FREQ. RESP. TO 5KHz, SENS 97dB.
- 12" 100 WATT C12-100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. PRICE £40.35 + £3.50 P&P
- RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 98dB.
- 12" 100 WATT C12-100TC (TWIN CONE) HIGH POWER, WIDE RESPONSE, P.A., VOICE, DISCO. PRICE £41.39 + £3.80 P&P
- RES. FREQ. 45Hz, FREQ. RESP. TO 12KHz, SENS 97dB.
- 12" 200 WATT C12-200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. PRICE £71.91 + £3.50 P&P
- RES. FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
- 12" 300 WATT C12-300B HIGH POWER BASS, LEAD GUITAR, KEYBOARDS, DISCO ETC. PRICE £95.66 + £3.50 P&P
- RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 100dB.
- 15" 100 WATT C15-100B BASS GUITAR, LOW FREQUENCY, P.A., DISCO. PRICE £59.05 + £4.00 P&P
- RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 98dB.
- 15" 200 WATT C15-200B VERY HIGH POWER BASS. PRICE £80.57 + £4.00 P&P
- RES. FREQ. 40Hz, FREQ. RESP. TO 3KHz, SENS 98dB.
- 15" 260 WATT C15-260B VERY HIGH POWER BASS. PRICE £90.23 + £4.50 P&P
- RES. FREQ. 39Hz, FREQ. RESP. TO 4KHz, SENS 99dB.
- 15" 400 WATT C15-400B VERY HIGH POWER, LOW FREQUENCY BASS. PRICE £105.46 + £4.50 P&P
- RES. FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS 100dB.
- 18" 600 WATT C18-600B EXTREMELY HIGH POWER, LOW FREQUENCY BASS. PRICE £174.97 + £3.00 P&P
- RES. FREQ. 27Hz, FREQ. RESP. TO 2KHz, SENS 98dB.

EARBENDERS- HI-FI, STUDIO, IN-CAR, ETC

- ALL EARBENDER UNITS 8 OHMS (Except EB8-5B & EB10-5B which are dual impedance tapped c. 4 & 8 ohms)
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
- 8" 50 WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
- RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
- 10" 50 WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
- RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 96dB.
- 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
- RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
- 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
- RES. FREQ. 26Hz, FREQ. RESP. TO 3KHz, SENS 93dB.
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
- 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
- RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
- 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
- RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
- B" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
- RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB.
- 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
- RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz. VARCAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES. SIZE 36 x 123mm. SUPPLY 12V @ 0.5AMP
PRICE £14.95 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz. VARCAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 58 x 44mm, SUPPLY 9V BATTERY.
PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS


UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR.
Tel.: 0702 - 527572 Fax.: 0702 - 420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.

Features & Projects



Volume 22 No.1
Jan 1993

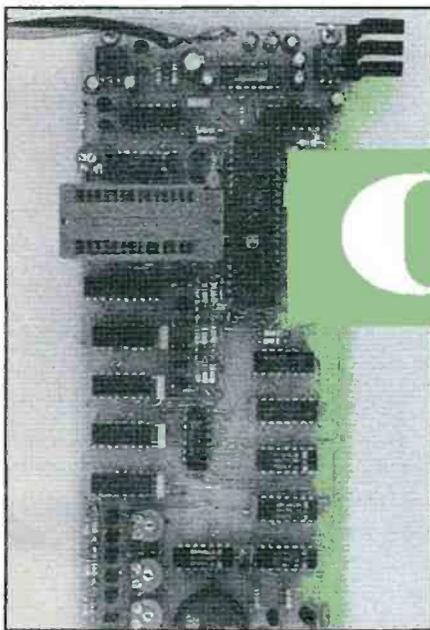

Macro-Heliograph Receiver	12
Ever wanted to hear what subsonic sounds a whole variety of insects make? This ingenious receiver devised by I.P. Wilkinson can open up a new series of investigations into low frequency low amplitude waves.	
EPROM Programmer Part 1.....	16
Paul Stenning is back with a very useful piece of equipment saving the constructor much in the way of hard cash. This EPROM programmer does not require a programmed EPROM to work but instead relies on your friendly computer.	
The AutoMate Mixing Desk Part 8b.....	24
Mike Mecchan continues with the EQ circuitry for the Automate Mixer	
IR Remote-Controlled Lighting System Part 1.....	32
Use our cover PCB to construct this four channel receiver board for controlling this application of light dimming. Ken Blackwell has the details.	
Fading Festoonery.....	37
As the Christmas season is upon us, why not try your hand at giving the tree lights an extra bit of sparkle. Richard Sagar provides the talking point at the party.	
Basic Multimeter Circuits	40
Ray Marston continues his Test-Gear series with a look at moving-coil meter circuits.	
RS232 Interface Part 2.....	48
A serial communications interface for your computer. Further details by Keith Garwell.	

Contents

Regulars

Open Channel	4
News.....	5
News Stateside	9
Read/Write.....	10
PCB Foils.....	54
PCB Service	56

Editorial

by Paul Freeman

The 'Smart age'

Just recently the term smart has taken on a whole new meaning. The term ascribed to the neat, well-dressed individual could fall into insignificance compared with the 'intelligent' use of the term. Soon, you will not be the 'smart Alec' for using the latest technology to be one step ahead, rather it's use will be required by you.

Although smart-cards have been in use in France mainly for bank transactions and cash flow, they are not in general use in the UK yet. Their ultimate introduction could be from a different angle your CV-ID card. Information stored on your plastic friend could be your medical, educational and criminal history, financial liability, insurance risk factor, to name but a few -

in fact your passport (or not) to the many activities in life.

Enter The Smart Book

About to appear is a single 3.5" disk called a SMART book. Most of us with computers know how much text can be crammed onto a disk, but the cramming, stacking or compression on these magnetic floppies has got the stage where 100 colour images accompanying 100 pages of text is possible.

The tools are now there for anyone in educational, medical and publishing environments to create your own books. One simple advantage to this electronic book as opposed to the CD-ROM is the simple application of updating, adding and correcting your latest publication. Here comes the revolution!

OPEN CHANNEL



Every once in a while on a consumer magazine the likes of ETI, something takes the fancy of readers. Indeed, something I wrote in this column a few months back has generated more mail than anything else I've ever written. My original comment was quite flippant (as many of my comments are!) and was regarding dogs, and an electronic dog collar which vets in the States are currently (pun intended) using to train noisy dogs to keep quiet. Every time the dog barks it gets an electric shock. Eventually the dog learns to keep its big mouth shut.

First letter I received was from a dog collared human who was fed up getting attacked and bitten, as he made his way around his parish visiting his security-dog-guarded flock. He was most interested in whether ETI could publish a design for a dog repellent. He'd built one which had been published earlier in a rival magazine. Apparently it did work, but parts had been difficult to come by, and he wanted a new version.

As part of what has turned out to be quite an on-running saga, I asked other readers if they knew of, or could design, a suitable dog repellent which could be presented in project form in ETI. Although no such dog repellent has yet come my way I've had a significant number of letters from readers to suggest that such a project would be extremely popular.

Indeed, I've even had a letter from a British Amateur Electronics Club member who even seems to deny the existence of the original dog repellent reported to me. Apparently, the BAEC has conducted a forum over the last two years or so regarding pet/pest repellents and none of the contributing members could suggest an electronic circuit. The member even went on to suggest it couldn't be done. Well I've news for the member - the Post Office issues electronic dog repellents to its postal delivery staff who feel threatened by dogs on their delivery rounds. So an electronic dog repellent is viable, and maybe a more positive attitude should be adopted by BAEC members.

What's needed, is a hobbyist's version. Unfortunately, I've filed the original letter in that great filing cabinet called our local tip, and can't reply directly to the author to ask him for more information about the dog repellent first published in an electronics magazine. So, if he's reading ETI this month, could I ask him to get back to me regarding the first dog repellent. I'd like to see the design myself. Meanwhile, perhaps other readers could put their designing hats on, and suggest a new circuit.

Balancing Act

Other mail arrived on my desk recently, regarding one of the terrestrial television broadcasters' last main arguments against satellite television - NICAM. Now, NICAM is a clever way of adapting the old PAL television format, to give high-quality digital audio alongside the vision signal. It's, in fact, an ingenious method of upgrading sound, and suitably equipped television receivers can be used to take the PAL signal received from terrestrial transmitters and give excellent stereo sound.

Satellite television channels all come with stereo sound, so terrestrial television channels has more-or-less had to upgrade simply to compete. In the past, another of terrestrial television's arguments

against the need for viewers to go to a satellite reception system was that the standard of program-ming on satellite channels was not as good as that from terrestrial channels. Well, some think that's changing now - there are currently thirteen English-speaking satellite channels from Astra, and while these channels tend to be quite specialised in what they transmit, they give a wide variety of quality programming (some of it indeed excellent). So, terrestrial television is about to be given a run for its money.

Considering this, it disappoints me to bear from unsatisfied viewers who want NICAM. stereo sound - and have gone out and bought a NICAM equipped television receiver - yet still have to wait for the terrestrial broadcasters to upgrade their transmitters to be NICAM-capable. Worse, some viewers have now been told no upgrade of their transmitter to NICAM is planned. I sympathise with ETI readers and others in this position because I suffered similarly myself until recently. Even now I can only receive the independent channels with NICAM. BBC channels aren't yet available.

The BBC proudly boasts - on its own teletext service - that it currently serves over 90% of the population with NICAM. I only have one thing to say - only 90%? Where does that leave the other poor 5.4 million suckers?

Frankly, it is an appalling situation. The broadcasters have us believe reasonable national NICAM coverage is available, yet the situation is far from this. Worse still, there appears to be little or no effort - particularly by the BBC - to expand towards a proper national coverage at a rate which could be even construed reasonable. The reader who wrote to me to express his disquiet against the situation lives in Hereford. I live in the East Midlands. We're not talking about being in the back of beyond here, although the BBC appears to think it.

NICAM is one of the terrestrial broadcasters' last arguments against satellite television. Are they going to waste it? Remember that satellite television has 100% coverage.

Ring the changes

Every now and again it becomes necessary to fine tune telephone numbers. Sometimes this is to incorporate changes in the telephone system brought about by combinations of small local exchanges, into a single and much larger district exchange. Typically, this entails only those users originally on the local exchanges having an extra digit applied to their user number. Sometimes, this is undertaken on a larger level where a single dialing code changes to incorporate expansion - consider the change a year or so ago when the London code of 01 was changed to either 071 or 081.

Rarely, is a change undertaken like the one which is planned for April 1995, in which all dial codes in the system will have an extra digit 1 after the initial 0. So, as examples, Birmingham will become 0121, London will be either 0171 or 0181 and Bristol becomes 01272. At the same time the international dialing code (currently 010) will change to 00.

Although still well over two years away, April 1995 is the chosen date to allow manufacturers and service providers in the telecommunications industry time to modify equipment.

Keith Brindley

THEY'VE GOT THE POWER

BK Electronics have doubled the power with the release of their new 1000 watt MOS-FET amplifier module. The OMP/ MF 1000 has taken over from the popular OMP450 as the flagship of the OMP module range.

Delivering 1000 watts RMS into a 2 Ohm load, the OMP/ MF 1000 provides a no compromise price/power/performance ratio and, as with all of the OMP range, its advanced MOSFET circuitry


achieves sonic clarity and reliability. The OMP/MF1000 is priced at

£259.00, including V.A.T., plus £12.50 delivery, and is available from BK Electronics, Units 1 & 5

Comet way, Southend-on-Sea, Essex. SS2 6TR Tel: 0702 527572



NEW PORTABLE TRAFFIC INFORMATION SERVICE

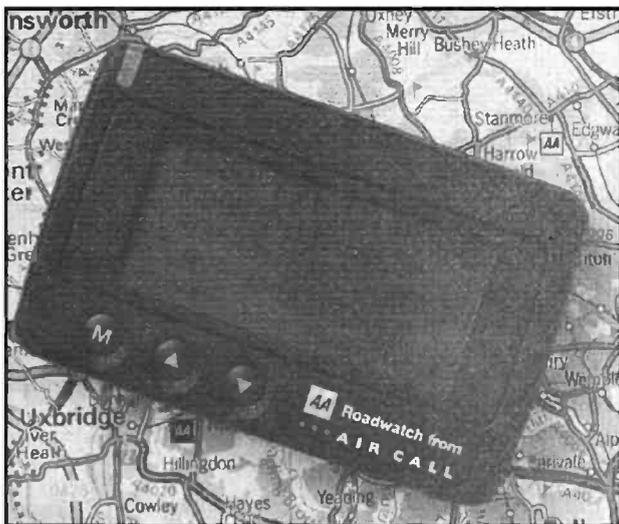

The UK's first portable traffic information service that delivers live national and regional traffic information has been launched by Air Call Communications. The service

will be of benefit to businesses and individuals who rely on the road system such as salesmen and distribution, fleet and retail companies.

Air Call's AA Road-watch service sends live traffic information direct from the Automobile Association (AA), via Air Call's national radio paging network, to be displayed on pocket-sized four line message pagers. The service operates day and night, 365 days a year. Subscribers receive traffic information relevant to the regional zone they are traveling in. As they travel through regions the traffic information received on Pagers will automatically change accordingly. There are a total of 10 regional zones. With access to live traffic information, drivers can plan routes in advance and avoid traffic congestion. To help with long distance journey planning, major national traffic incidents are sent to all subscribers.

Information is transmitted within 60 seconds of it being received by the AA and updates are sent until the congestion clears. Users are notified of incoming information by a flashing red light or by an audible tone.

The British Road Federation estimates the cost of idle vehicles to be £16 per hour including man hours. The CBI estimates that traffic congestion costs British business £15 billion per year in higher fuel and vehicle maintenance costs and in lost man hours. Air Call believes that these costs can be reduced by using its AA Road-watch service.

Subscribers can opt for either a fixed cost monthly rental package of £19.95 or they can purchase the AA Road-watch Pagers at £160 and pay a fixed monthly subscription of £7.50 for the information service.

Information received on AA Road-watch Pagers warns drivers of traffic congestion and details its cause such as burst water mains or traffic lights out of order. Where available, alternative routes are suggested.

SONY ANNOUNCE SMALLEST CAMCORDER YET

Sony has released details of the new CCD-TR8 camcorder. This is the smallest camcorder produced by the company to date and weighs 690grams.

Set to transform the camcorder market, Sony have developed a Lithium Ion battery for camcorder use.

The NP-500 powers the CCD-TR8 and becomes an integral part of the camcorder.

Lithium Ion batteries do not suffer from the 'memory effect' as do conventional camcorder batteries and do not therefore have to be fully discharged before recharging.

The battery can now be 'topped-up' at any time, without having to discharge it first.

The CCD-TR8 is a stereo Hi8 camcorder, which utilizes a high precision 1/3" CCD imager with 440,000 effective pixels, this provides the highest picture quality.

Full range auto focus is maintained by way of the Sony Inner Focus system, manual control is possible with a dial at the front of the camera. Manual control over exposure and gain is also provided in 24 steps, while program auto exposure features portrait,

sports and HSS modes.

The CCD-TR8 has an 8x power zoom with a variable speed of 1.5-16 seconds while the lens is protected with an automatic lens cover, controlled by the power

switch.

Supplied with the CCD-TR8 is a Sony camcorder station. The station can be left permanently connected to the television, while the CCD-TR8 is clipped and

unclipped from its base. Also, when connected to the camcorder station, automatic charging of the battery takes place. For longer periods away from home the AC adaptor unclips from the

camcorder station and can be used elsewhere.

The CCD-TR8 supplied with accessories, including remote control is available in the UK from December.

TV ON YOUR PC!

Imagine Graphics Ltd has launched a television and video adaptor for use with all VGA based PCs. Now one monitor can be used to display the two different sources of information.

The Videomate, model JV-819PT, is a real time video standards converter using the latest in microprocessor technology to change a low resolution, interlaced, composite PAL signal to a high quality, non-interlaced, VGA RGB signal.

The VIDEOMATE provides PC users with the ability to display TV and video signals on any standard VGA, SuperVGA or autosync colour monitor. Sound is also provided by an audio amplifier and built-in speaker. The user simply switches between TV/video and a standard VGA PC display allowing the PC to carry on processing data or compiling a

program while the user watches TV or video.

Application areas include: education, training, corporate presentations, security, financial dealing rooms, factory floor automation and leisure.

An infra-red remote control is provided allowing users to automatically or manually tune and store up to 41 UHF and VHF/cable TV channels, switch to a video source such as a VCR or camera, adjust colour, contrast, brightness and volume - just like a modern, sophisticated TV set. An on-screen display shows all these functions plus time of day and on-off timer.

The VIDEOMATE is priced at £269+VAT.

For further details contact:

Norman Garland - Imagine Graphics Ltd, Tel: 0727 830638



Autumn 1992 sees the launch of three models of Data Discman, the electronic book player, from Sony.

The first of these models, the DD-DR1 is an electronic book drive unit, without an LCD screen,

for use with a personal computer. An RS232C interface to link with an IBM PC (or IBM compatible) is included, with emulator software providing audio, text and graphics playback.

This unit, which will also play-

THREE NEW ELECTRONIC BOOK PLAYERS ON SALE FROM OCTOBER

back 8cm CD audio singles, may be powered by a dry cell battery, in-car, with a car adaptor, or from an AC power supply. Continuous playback of six hours is possible with six AA batteries.

Supplied with an AC power adaptor, EBIF lead and software for IBM and IBM compatible PC, the DD-DR 1 will retail for £299.99 and will be available from November.

The DD-8 is a portable electronic book player with a fixed 4" LCD screen display and a front-loading mechanism for electronic book insertion. The screen can display ten lines of 30 characters, and graphics with a resolution of 256(horizontal) x 200(vertical) pixels.

A truly portable machine weighing only 450g, the DD-8 will playback speech, music translations, or any other audio that is included in the text of the electronic books.

The DD-8 incorporates a book-

mark facility that will resume play where it left off. An auto scroll facility is also included, with variable speed control. The machine can be powered by dry cell AA batteries, in-car with a car adaptor, or from an AC power supply.

Supplied with headphones, a video lead for connection to a television, an AC power adaptor and carrying case, the DD-8 is priced at £279.99.

The DD-10EX, a portable machine which features all the facilities of the above model, also has a backlit 3.5" LCD screen which flips up and is adjustable for angle.

The DD-10EX also operates from a supplied rechargeable battery, or dry cell batteries, as well as from the supplied AC power adaptor. Complete with headphones and video connecting lead, the DD-10EX will retail for £379.99.

WORLD'S FIRST ROBOTIC EATING AND DRINKING MACHINE

The world's first robotic eating and drinking machine which will give a measure of independence to severely disabled people, was unveiled at Keele University in September.

A machine with a robotic facility to aid eating has already been commercially developed by Keele University's rehabilitation robotics department, and the drinking facility is another major breakthrough.

Now, with the help of a £5,000.00 Care Grant from United

Norwest Co-operatives, the inventor, Mike Topping, plans further development of the machine which has already astonished scientists and medical engineers.

"We believe that with a little further development the machine will clean teeth, shave, apply cosmetics and give a facial massage. The machine already has the capacity to add seven other functions" he said.

Mr Topping, who has a computer background, has had to pick up engineering skills as he

has progressed, and his department has had to rely heavily on public donations to develop his project. Mike got the idea for the machine after seeing how some children at a special school were so depend-ent on others to feed them.

Be developed the machine during a research period at Keele University following a spell of unemployment. His assistant on the project is a teenage electronics technician, Robert Finney.

Mr John Thomson, chief executive of United Norwest

co-operatives, said the £5,000 grant was one of the largest grants made nationally as part of the Coop's community care scheme, and the feeding and drinking machine was one of the most exciting and rewarding projects with which they had been involved.

"It will prove a boon to severely disabled people all over the world and will be of particular help to people with cerebral palsy" he said.

AT & T LAUNCHES HOBBIT MICROPROCESSOR

AT&T Microelectronics has launched the Hobbit microprocessor, a device which will form the basis for future generations of personal communicators.

AT&T estimates that, by the year 2000, there will be around 1 billion potential users of personal communicators, devices which will combine voice messaging, electronic mail and portable fax and modern functions, but which could eventually incorporate advanced features such as graphics and full-motion video communications.

"The technology to build superior mobile communications devices is here today," said William Warwick, AT&T Microelectronics president. "You'll see the first Hobbit-based personal communicators before the end of this year," he added.

The ATT92010 Hobbit processor, which was developed at AT & T Bell Laboratories, combines high performance, low power consumption, and a full range of communications facilities. To support the processor itself, AT & T Microelectronics has introduced four highly integrated peripheral support chips, which provide a complete solution for building a personal communicator. These include handling of external storage devices, power management, and display handling.

"Personal communicators represent the next step in giving



mobile users access to global communications services," said, Dan Lankford, head of AT&T ME's operations in Europe. "Europe has traditionally been at the forefront of communications technology, a lead which continues today. We see vast potential for these new devices, and we are proud to be the first to offer a complete silicon solution to personal communicator manufacturers."

The Hobbit microprocessor will be supported by Go's Pen Point operating system, which is tailored for the needs of both pen-based input, and communications devices in general. Pen Point provides task handling facilities, to guarantee that a personal communicator will simultaneously handle communications functions such as call exception, and user functions such as writing a memo

a memo. The software also provides a consistent user interface, which will make communicators as easy to use as a standard telephone.

The processor is optimise for communications and portable applications. The 20MHz, 32-bit Hobbit chip delivers 37 VAX MIPS per watt, nearly five times the figure for Intel's i486DX, and nearly 30 times that for Intel's 386SL. It is designed for fast context switching and interrupt response, so that the chip can quickly switch between various tasks, for instance editing a document, receiving incoming email, and sending a fax.

Because the ATT92000 Hobbit chip set has been designed with communications in mind, and without having to retain backward compatibility with existing devices, it represents a very efficient silicon implementation

of the required functions. The CPU, for instance, consists of just 400,000 transistors: processors with similar performance commonly exceed 1 million transistors.

To achieve the low power consumption necessary for battery powered mobile operation, the entire Hobbit chipset runs at 3.3V, rather than the older standard 5V. System software can stop the processor clock, putting the chip in a low-power standby mode which consumes just 50µW (50 millionths of a Watt) of power.

AT & T will supply a complete set of development tools for the Hobbit processor and its associated support chips, allowing designers to quickly realise real-world personal communicator solutions.

LOW COST DATALOGGER

Pico Technology Limited announce a new addition to their range of PC based data acquisition products. The ADC-16 is a high resolution data logger that plugs directly into the serial port, requiring no external power. It features 8 channels of analogue input at 16 bit resolution.

Unlike plug-in cards it uses no expansion slots making it easy to install and use with portable PC's. The use of a serial connection cable means the unit can be positioned near the experiment to minimise noise pick up.

It is supplied with PicoLog data logging software which al-

lows full use of the ADC-16's features: involving selection of resolution for each channel from 8 to 16 bits and either single ended or differential inputs. Each recorded sample can be the maximum, minimum or average of a number of readings, collected over a period of a few milliseconds to a day. The software also includes a comprehensive range of graphical and text reporting tools.

The ADC-16 costs £99 (plus VAT) which includes software drivers and a manual.

Further details contact Pico Technology Ltd, Telephone 0954 211716.



UK FAILING TO EXPLOIT ITS TECHNICAL 'KNOW-HOW' SAYS IEE PRESIDENT

Although it has long regarded itself as a nation of inventors, the UK is significantly failing to exploit its own technical 'know-how' and expertise. It is also failing to recognise the importance of buying in the best know-how technology from elsewhere, and as a result is lagging behind its overseas competitors.

This was the message given by Professor Peter Lawrenson in his Inaugural Address as President of the Institution of Electrical Engineers (IEE), Europe's largest professional engineering society.

World trade in technical 'know-how', or disembodied technology as it is sometimes called, now amounts to \$34 billion a year - more than the total of all international passenger fares - and is set to increase. However, Professor

Lawrenson warned, this trade is increasingly being exploited by the USA, Japan and Germany.

"Although the UK" he said "has always given rather 'mystical' prestige to inventions and patents, it has failed to award similar prestige to innovative success following from patents and the exploitation of knowledge through design rights, copyrights, trademarks and licensing".

"For too long we have suffered from a belief that cleverness in technology, and particularly science, is the key to success. Rather it is the exploitation of technical know-how and innovation that leads to the creation of benefit and wealth".

"The emphasis being placed internationally on knowledge and innovation, technology property and technology licensing has in-

creased significantly within the last decade. Furthermore there is a close correlation between those countries with high and increasing patent activity and those achieving industrial success. Against this background the performance of the UK is disappointing, at the very least".

+The percentage of patents granted in the USA to UK inventors shows a steady decline whereas those of our main competitors, Germany and Japan, show a significant increase, reflecting the importance being attached in those countries to new technical knowledge".

The new IEE President went on to comment on the current UK situation.

"Some companies" he said "do have a positive attitude to patenting and to know-how trans-

actions, including buying-in from outside, and are aware of the need to stay continuously abreast of worldwide best practice. Unfortunately, far too many companies seem to have no policy whatever in relation to patenting or licensing strategy".

Professor Lawrenson ended his Address with a call for a change in UK attitudes and for a new framework for positive action.

"There is a clear need for the implementation of vigorous policies to encourage the exploitation of know-how and technology, both by purchase and sale, to ensure that our manufactured products are truly of world class design and quality and that every possible compensation is made for high labour and production costs and for restricted R & D budgets".

ELECTRONIC CAR IMMOBILISER



UK Electronics have designed and manufactured a new car immobiliser in conjunction with Acorn Auto Electrical Specialists. Using the latest technology, the two Oldham based companies have produced and launched this new security product in response to repeated customer demand.

Designed to stop vehicles going missing, 'Active 8' is inexpensive and easy to fit. It works by cutting out two electrical circuits, normally starter motor and ignition, to make it doubly safe and secure. Another major benefit is that it is fully automatic: once the

ignition key is removed it is activated in 8 seconds, hence the name Active 8. Simple and convenient to use, with no remote controls to be carried, it works whenever the car is left - even when paying for petrol.

The system is de-activated by turning on the ignition and pressing a virtually invisible micro thin pad, positioned for the driver's convenience. A new company, Active 8 Ltd has been established to market and distribute the immobiliser via car security specialists and other automotive outlets.

...Stateside...

Advances in photo-detectors

The recent discovery that porous silicon emits light has been followed by a number of breakthroughs, including an all silicon light-emitting diode. Researchers are now discovering that porous-silicon layers make superior photo-detectors and high efficiency solar cells, and could turn out to be a superior optical recording medium. While the underlying physics that produces the unusual photonic effects is still a mystery, the new material is proving to be highly cooperative in application-oriented research. The ability of porous silicon to absorb photons surprised a


search group at the State University of New York at Buffalo, which has produced a metal/porous silicon/silicon photo detector. It was found that the MRS photo diode is comparable in performance to

captured in the silicon lattice. Experiments suggest that a porous-silicon layer is able to trap 100% of the photons striking it, eliminating the additional anti-reflection processing step.

for the detector, and a second electrode is formed by depositing aluminium on the backside of the wafer. Measurements of the detector response showed that it had a very high conversion efficiency - 97%. Since about 2% of the light falling on the 3mm-square area was reflected, it was concluded that the porous-silicon layer converts virtually all the light that is trapped. This would make porous silicon an ideal candidate for high-efficiency solar cells.

Since this is only the first pro-prototype, it is reasonable to expect better performance can be obtained by varying process parameters. The only caveat with this new process is the question of long-term stability.

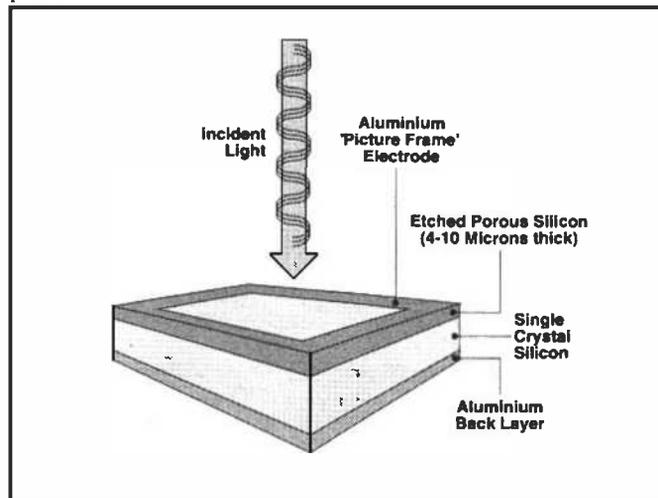Since research on porous silicon is moving so fast, there is no data on the long-term variation of parameters. If the material turns out to be as stable as normal silicon, porous-silicon devices could easily be incorporated into VLSI designs with only a few additional processing steps.



commercially available silicon photo diodes, but without needing an anti-reflection coating.

Standard silicon photo diodes need additional surface treatment to keep photons from bouncing off before they are

The MRS device is formed by depositing a square frame of aluminium over a porous-silicon layer etched into a standard single-crystal silicon substrate. The frame acts as one electrode

Reducing cost of fibre optics

What it calls a circular-grating surface-emitting laser, which emits a circular column of light from its surface has been produced by Bell-Northern Research. The company said this improves the efficiency of coupling laser light to optical fibres. In contrast, conventional lasers generate a divergent light beam that requires precise positioning of the fibre to capture light efficiently.

Packaging that will hold lasers and wires in precise alignment still makes up more than 70% of the final cost of fibre-optic wiring. The Bell-Northern development makes it possible to relax these tolerances, and to substantially cut costs.

Sub-micron contaminants research

A recent \$62 million Co-operative Research and Development Agreement announced by the US Department of Energy includes an initial \$6 million nine-month funding for a joint centre to be created by Sandia National Labs and Sematech.

The research centre will study

the feasibility of 0.1 micron manufacturing methods, by looking at new ways to remove clean-room contaminants as small as 0.01 micron. Also being explored are ways to isolate particulate sources.

Turning compost automatically

A US company has introduced a machine that turns compost automatically. Key to its operation is a solar panel that charges a 12V battery, which in turn powers a drive

mechanism. The heavy duty battery is sealed and will run up to 28 days without sunlight.

Called The Swisher Solar Composter, from Swisher Mower

and Machine Co, Inc., Warrensburgh, Missouri, it is made in various sizes, the largest of which is 184 gallons. A dual compartment model allows simultaneous composting

and storing the compost container is recycled galvanized steel and is square for mixing and folding. A patent is pending.

Wireless communicator

Service workers - including quality-control inspectors, warehouse clerks, nurses, couriers, and waiters - do not need a portable computer, but rather a simple and fast way to communicate information.

Granite Communications Inc., Amherst, New Hampshire, has recently introduced a hand-held,

wireless, data-communications tool. The Videopad contains a microprocessor with 1 M-byte memory and uses a menu-driven touch screen that displays alphanumeric, icons, and graphics. Videopad is custom designed for the application and can be easily re-programmed. Models are differentiated by their communications

interface, either spread-spectrum radio or modem. In operation, a user enters data on the touch screen, then sends data to a receiver, which is connected to a host computer or network. Up to 100 Videopads equipped with spread-spectrum radio can communicate simultaneously with the receiver at distances

of up to 1,000ft. The modem is particularly useful for store and forward applications, but can also operate in real time. Videopad is about one-third the price of notebook and pen computers and, at 18-oz, one-quarter the weight. The batteries that power the unit are rechargeable.

Throwing some light on the subject of LEDs

Having read the letter from I. Field in the September issue of ETI, I have researched the problem of comparing the light output of LEDs and lamps. The light output of lamps is usually stated in lumens, which is the luminous power or flux, while the

brightness of LEDs is stated in candela, the unit of luminous intensity.

It is possible to find the output of an LED in lumen's if the view angle is given. It must be assumed that the luminous intensity given is the average over this solid angle. Candela (cd) is another name for the units lumen's per steradian (lm/sr). The view angle must therefore be converted into a number of steradians. If 'v' is the view angle, then the number of steradians is:

$$2\pi[1-\cos(v/2)]$$

This number of steradians can now be multiplied by the number of candela to give the luminous power of the LED. This calculation can produce interesting results, for instance, it can show that an LED with a much greater brightness in candela than another LED, may actually have a lower luminous power.

All the units used so far have been photometric, that is they are adjusted to the response of the eye. The eye is at its most sensitive at 555nm and at that wavelength one watt of radiant energy

is equal to 680 lumen's. On either side of this wavelength the number of lumen's per watt reduces according to the sensitivity of the eye. It is interesting to work out the radiant power of LEDs (in watts) as their efficiency can then be found.

I think the readership of ETI would find this an interesting topic for an article. I'd like to take this opportunity to thank you for producing the best electronics magazine in this country.

Robert Johnstone.
Worcester Park, Surrey.

Induction Loop Systems

In response to Mr Trayers request for information regarding Induction Loop systems for the hard of hearing on the letters page of the December issue of ETI.

We have been manufacturing loop systems for the hard of hearing since 1989 and have many units installed at various sites including concert halls, Hospitals, Churches and Conference centres.

Mr Trayers might be interested in our equipment.. The PDA100 is designed specifically for applications such as his.

Grants are often available from the local authority to help with the purchase of loop products and VAT is not normally charged for personal purchases by disabled persons.

Steve Mehew, A VX Systems, Washington, Tyne & Wear.

Audio response measuring system - Buylines

Somehow the Buylines section on of our two part project Automatic audio response measuring system in the November/ December issues was missed out.

We produce it here.

Automate Requirements

Firstly I would like to congratulate you on the improvement of the magazine.

The main point of this letter is to deal with the Automate Mixer Project. I must say it is quite an impressive project - one that a few of us here are especially interested in. There is one thing that worries me about the project

Buylines

The address for all orders is:
Ralph Mantel,
Pipinstr.23
W-4790 Paderborn,
Germany.

The prices for the UK in pound sterling are:
Compensated measuring microphone with cable and plug £39
Software £29
PCB with printed overlay £19.
All three items together for the favorable price of £79 (saving £8)
Complete kit or ready built PCB please enquire.

and that is the number of magazines it is going to take to see it through to the end. At this rate I would suggest that by the time it is completed the technology will be out of date that one would be better off by buying one off the shelf

Why not give your readers the option of buying a manual containing the complete documentation for the project. I know that I would be willing to pay in the region £25 - £30 for

such a document. I myself are in need of a decent mixer for my MIDI based system, I know of a band here that is in need of a decent mixer for their events, and there was inter-est expressed by the campus radio station here who could use the mixer as part of an automatic music request system.

David Ingles
Lancaster University
Points noted Ed

SECURITY EQUIPMENT

INSTALL YOURSELF & SAVE! SAVE!

Complete range of security parts to protect your house and property. Passive infra-red sensors ultrasonic movement detectors, control panels, cable, etc etc supplied with instructions.

QUALITY AUDIO MODULES

Power amplifiers from 10-25W, mixer units, pre-amplifiers etc. Build your own disco units, guitar amps, public address systems etc, etc.

CALL FOR FREE LITERATURE TODAY

AUTONA LTD TEL 084 44 6326
51 POPPY ROAD, PRINCES RISBOROUGH, BUCKS HP17 9DB

Hesing Technology



Cromwell Chambers, 8 St. Johns Street,
Huntingdon, Cambs. PE18 600

Tel: (0480) 433156
Fax: (0480) 413357

TEST EQUIPMENT

Supply
Maintenance
Commissioning.

SYSTEM CONSULTANCY

Replacement Parts
Supply of Service &
Operators Manuals
Components

Distributors for:
WAUGH INSTRUMENTS, RAMTEST LTD, KRENZ ELECTRONICS, PANTHER

MICROWAVE CONTROL PANEL Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. Now only £4.00 ref 4P181. Good experimenter's board.

FIBRE OPTIC CABLE Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R or £2 a metre.

12V SOLAR CELL 200mA output ideal for trickle charging etc. 300mm square. Our price £15.00 ref 15P42R. Gives up to 15v.

PASSIVE INFRARED MOTION SENSOR. Complete with daylight sensor, adjustable lights on timer (8 secs - 15 mins), 50' range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. Now only £19.00 ref 19P29

Pack of two PAR35 bulbs for above unit £12.00 ref 12P43R

VIDEO SENDER UNIT Transmits both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range (tune TV to a spare channel). 12v DC op £15.00 ref 15P39R Suitable mains adaptor £3.00 ref 3P191R Turn your camcorder into a cordless camera!

FM TRANSMITTER housed in a standard working 13A adaptor (bug is mains driven). £26.00 ref 26P2R. Good range device.

MINIATURE RADIO TRANSCEIVERS A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x155mm. Complete with cases and earpieces. £30.00 ref 30P12R

FM CORDLESS MICROPHONE Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 battery. Tuneable to any FM receiver. Our price £15 ref 15P42AR

12 BAND COMMUNICATIONS RECEIVER. 9 short bands, FM, AM and LWDX/folder switch, tuning 'eye' mains or battery. Complete with shoulder strap and mains lead. £19 ref 19P14R Ideal for listening all over the world.

CAR STEREO AND FM RADIO Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than 45db. Now and flutter less than .35%. Neg earth. £19.00 ref 19P30

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Our price £8.00 a pair ref 8P50R Ideal for garden use or as an educational toy.

20-21KHZ GRAPHIC EQUALIZER plus a 60 watt power amp! 7x2CHXZ 4-8R 12-14v DC negative earth. Cased. £25 ref 25P14R.

NICAD BATTERIES. Brand new top quality. 4 x AA's £4.00 ref 4P44R 2 x C's £4.00 ref 4P73R, 4 x D's £9.00 ref 9P12R, 1 x PP3 £6.00 ref 6P35R Pack of 10 AAA's £4.00 ref 4P92R

TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE. The ultimate equivalent's book. New ed. £20.00 ref 20P32R.

GEIGER COUNTER KIT. Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R

FM BUG KIT. New design with PCB embedded coil. Transmits to any FM radio. 9v battery req'd. £5.00 ref 5P158R. 35mm square.

FM BUG Built and tested superior 9v operation. £14.00 ref 14P3R

COMPOSITE VIDEO KITS. These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R.

SINCLAIR C5 MOTORS 12v 29A (full load) 3300 rpm 6"x4" 1/4" O/P shaft. New. £20.00 ref 20P22R. Limited stocks.

As above but with fitted 4 to 1 inline reduction box (800rpm) and toothed nylon belt drive cog £40.00 ref 40P8R. 800 rpm.

ELECTRONIC SPEED CONTROL KIT for c5 motor. PCB and all components to build a speed controller (0-85% of speed). Uses pulse width modulation. £17.00 ref 17P3R. Potentiometer control.

SOLAR POWERED NICAD CHARGER. Charges 4 AA nicads in 8 hours. Brand new and cased. £6.00 ref 6P3R 2x C cell model £6.00.

ACORN DATA RECORDER ALF503 Made for BBC computer but suitable for others. Includes mains adapter, leads and book. £15.00 ref 15P43R

VIDEO TAPES. Three hour superior quality tapes made under licence from the famous JVC company. Pack of 10 tapes. New low price £15.00 ref J15P4

PHILIPS LASER 2MW HELIUM NEON LASER TUBE. BRAND NEW FULL SPEC £40.00 REF 40P10R. MAINS POWER SUPPLY KIT £20.00 REF 20P33R READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4R.

12 TO 220V INVERTER KIT as supplied it will handle up to about 15w at 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17R. Larger transformer £12.00 ref 12P41R.

VERO EASY WIRE PROTOTYPING SYSTEM Ideal for designing projects on etc. Complete with tools, wire and reusable board. New low bargain price only £2.00 ref 82P1

25 WATT STEREO AMPLIFIER STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P89R (Circuit dia included).

BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10 £4.00 REF 4P92R, PACK OF 100 £30.00 REF 30P16R

FRESNEL MAGNIFYING LENS 83 x 52mm £1.00 ref 8D627R

12V 19A TRANSFORMER Ex equipment £20 but OK.

ULTRASONIC ALARM SYSTEM. Once again in stock these units consist of a detector that plugs into a 13A socket in the area to protect. The receiver plugs into a 13A socket anywhere else on the same supply. Ideal for protecting garages, sheds etc. Complete system now only £19!!!

286 MOTHER BOARDS. Brand new and tested complete with technical manual. £34.00 ref 134P1

UNIVERSAL BATTERY CHARGER. Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £8.00 ref 8P36R

IN CAR POWER SUPPLY. Plugs into cigar socket and gives 3.4, 6.7, 9.9, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167R

RESISTOR PACK. 10 x 50 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170R

QUICK CUPPA? 12v immersion heater with lead and cigar lighter plug. £3.00 ref 3P92R. Ideal for tea on the move!

LED CABLE. 50 red, 50 green, 50 yellow all 5mm. £8.00 ref 8P52

IBM PRINTER LEAD. (D25 to centronics plug) 2 metre parallel. £5.00 ref 5P186R. 3 metre version £8.00 ref 6P50.

COPPERCLAD STRIP BOARD 17" x 4" of 1" pitch 'vero' board. £4.00 a sheet ref 4P62R or 2 sheets for £7.00 ref 7P22R.

STRIP BOARD CUTTING TOOL £2.00 ref 2P352R.

WINDUP SOLAR POWERED RADIO! FM/AM radio takes rechargeable batteries. Complete with hand charger & solar panel 14P200R. Set of 2 AA nicads £2 ref 12P9

PC STYLE POWER SUPPLY Made by AZTEC 110v to 240v input. +5 @ 15A, +12 @ 5A, -12 @ .5A, -5 @ .3A. Fully cased with fan, on/off switch, IEC inlet and standard PC fly-leads. £15.00 ref F15P4



AMSTRAD MP3

UHF/VHF TV RECEIVER/CONVERTER

CONVERTS COLOUR MONITOR INTO A TV!

£9.00

TELEPHONE HANDSETS

10 brand new handsets with mic and speaker only. £3.00 ref 3P146R

BENCHPOWER SUPPLIES

Superbly made fully cased (metal) giving 12v at 2A plus a 6V supply. Fused and short circuit protected. For sale at less than the cost of the case! Our price is £4.00 ref 4P103R

SPEAKER WIRE

Brand twin core insulated cable 100 feet for £2.00 REF 2P79R

DISC DRIVES

Customer returned units mixed capacities (up to 1.44M) We have not sorted these so you just get the next one on the shelf. Price is only £7.00 ref 7P1R (worth it even as a stripper)

MICROSCOPE 1200X MAGNIFICATION

Brand new complete with shrimp hatchery, shrimp, prepared slides, light etc. £29.00 ref J29P4.

LIGHT ALARM SYSTEM

Small cased alarm that monitor a narrow beam area for sudden changes in light level. Complete with siren that sounds for a preset time when unit is triggered. £7.00 ref J7P1

JOYBALLS

Back in stock popular Commodore/Atan equiv (replace standard joystick) £5.00 ref J5P8

AMSTRAD 16400D BASE UNITS

BRAND NEW AND CASSED

TWO BUILT IN 5 1/4" DRIVES

MOTHER BOARD WITH 640K MEMORY

KEYBOARD, MOUSE & MANUAL

OUR PRICE JUST

£79!!!!

CAR BATTERY CHARGER

Brand new units complete with panel meter and leads. 6 or 12v output £7.00 ref J7P2.

CUSTOMER RETURNED SPECTRUM +2

Complete but sold as seen so may need attention £25.00 ref J25P1 or 2 for £40.00 ref J40P4

CUSTOMER RETURNED SPECTRUM +3

Complete but sold as seen so may need attention £25.00 ref J25P2 or 2 for £40.00 ref J40P5

SCART TO D TYPE LEADS

Standard Scart on one end, Hi density D type (standard VGA connector) on the other. Pack of ten leads only £7.00 ref 7P2R

OZONE FRIENDLY LATEX

250ml bottle of liquid rubber sealer 2 hours. Ideal for mounting PCB's fixing wires etc. £2.00 each ref 2P379R

VIEWDATA SYSTEMS

Brand new units made by TANDATA complete with 1200/75 built in modem infra red remote controlled qwerty keyboard BT approved. Preset compatible, Centronics printer port RGB colour and composite output (works with ordinary television) complete with power supply and fully cased. Our price is only £20.00 ref 20P1R

AC STEPDOWN CONVERTER

Cased units that convert 240v to 110v 3" x 2" with mains input load and 2 pin American output socket (suitable for relative loads only) our price £2.00 ref 2P381R

CURLY CABLE

Extends from 8" to 8 feet! D connector on one end, spade connectors on the other ideal for joysticks etc (5 core) £1.00 each ref CD44R

COMPUTER JOYSTICK BARGAIN

Pack of 2 joysticks only £2.00 ref 2P382R

BUGGING TAPE RECORDER

Small hand held cassette recorders that only operate when there is sound then turn off 8 seconds after so you could leave it in a room all day and just record any thing that was said. Price is £20.00 ref 20P3R

NEW SOLAR ENERGY KIT

Contains 8 solar cells, motor, tools, fan etc plus educational booklet. Ideal for the budding enthusiast! Price is £12.00 ref 12P2R

286 AT PC

286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1 (no I/O cards or drives included) Some metal work req'd phone for details.

286 AT PC

286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1 (no I/O cards or drives included) Some metal work req'd phone for details.

286 AT PC

286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1 (no I/O cards or drives included) Some metal work req'd phone for details.

286 AT PC

286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1 (no I/O cards or drives included) Some metal work req'd phone for details.

286 AT PC

286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1 (no I/O cards or drives included) Some metal work req'd phone for details.

BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX

BN3 5QT TELEPHONE 0273 203500

MAIL ORDER TERMS: CASH PO OR CHEQUE

WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY

FAX 0273 323077

VISA

CAMERAS Customer returned units. 3 for £10 ref L10P2

STEAM ENGINE Standard Mamod 1 engine complete with boiler piston etc £30 ref 30P200

TALKING CLOCK

LCD display, alarm, battery operate. Clock will announce the time at the push of a button and when the alarm is due. The alarm is switchable from voice to a cock crowing! £14.00 ref 14P200 R

HANDHELD TONE DALLERS

Small units that are designed to hold over the mouth piece of a telephone to send MF dialling tones. Ideal for the remote control of answer machines. £5.00 ref 5P209R

AMAZING TALKING COINBOX!

Fully programmable talking, lockable coinbox BT approved, retail price £79 ours is just £29! ref J28P2.

ANSWER PHONES £15

Customer returned units with 2 faults one we tell you how to fix the other you do your self! £16 ref J18P2 or 4 for £60 ref J60P3 BT approved (retail price £79.95 each)

COMMODORE 84 MICRODRIVE SYSTEM

Complete cased brand new drives with cartridge and software 10 times faster than tape machines works with any Commodore 84 setup. The original price for these was £49.00 but we can offer them to you at only £25.00! REF 25P1R

90 WATT MAINS MOTORS Ex equipment but ok. Good general purpose unit £9.00 ref F9P1

HI FI SPEAKER BARGAIN Originally made for TV sets they consist of a 4" 10 watt 4R speaker and a 2" 140R tweeter. If you want two of each plus 2 of our crossover you can have the lot for £5.00 ref F5P2

EMERGENCY LIGHTING SYSTEM

Fully cased complete with 2 adjustable flood lights. All you need is a standard 6V lead acid battery. Our price is just £10 ref J10P29

AMSTRAD 484 COMPUTERS

Customer returned units complete with a monitor for just £35! These units are sold as faulty and are not returnable.

WOLSEY DMAC DECODERS

Made for installation in hotels etc as the main set receiver no data but fully cased quality unit. £20 ref K20P1. Suitable psu £8 ref K8P3.

SWITCHED MODE PSU

Fully cased unit 215mmx145mmx55mm giving +5, +12 and +20v well made case complete with mains lead. £8 for K8P3.

REMOTE CONTROLS

Brand new infra red CONTROLS originally made for controlling WOLSEY satellite receivers. £2 ea ref K2P1 or 20 for £19 ref K19P1.

TELEPHONES

Modem 1 piece phones BT approved. Last no retail. £8 ref K8P1.

386 TOWER SYSTEMS

Tower case 520mmx400mmx200mm. 2 fans, speaker, 275w psu, IEC I/O and O/L, 386 motherboard with onboard disc controller, ethernet, display driver, parallel and serial ports. There are several IC's missing from the motherboard plus no data! £79 ref K79P1.

DOS PACKS

Complete set of PC discs with MS DOS 3.2. Locomotive basic, gemdesktop and gemprint. No manuals. 5 1/4" discs. £10 ref K10P2

CORLESS TIE CLIP MICROPHONE

transmits between 88-108MHz FM. 5.2cm x 2cm. uses LR44 watch battery. Complete with wire aerial & battery. £16 ref K16P1.

CHASSIS MOUNT TRANSFORMERS

240v primary, 12v secondary 20VA £2 ref M2P2

240v primary, 16v secondary 10A (split winding). £10 ref L10P1

100 RED LED PACK (SMM) £5 REF K5P2

12v STEPPER MOTOR Ideal for models etc. 3" dia. £2 ref J2P14

INFRA RED BEAM SWITCH 24v DC 5m range source & sensor housed in plastic case. £12 ref J12P1

CAPACITOR BARGAIN PACK 100 CERAMICS £2 REF J2P2.

SPECTRUM JOYSTICKS TWO FOR £5 REF J5P2.

AMSTRAD PC CASE, POWER SUPPLY AND 1.44 FLOPPY DRIVE ALL THIS FOR £44 REF L44P1

BUMPER PACK NO 1 10 of our popular £1 packs for just £5 our choice of contents.

BUMPER PACK NO 225 of our popular £1 packs for just £12. Our choice of contents.

LCD 1 X 32 DISPLAY Bargain price of just £3 complete with loads of data for a similar display. £3 ref L3P1.

USEFUL POWER SUPPLIES. 18v 900mA dc output (regulated) fully cased with mains cable and DC out cable. £5 ref K6P1

UNCASSED PC POWER SUPPLIES. Standard PC psu without case, fan etc. Good for spare or low cost PC! £4 ref L4P8

RADAR DETECTORS. Detects X and K bands (the speed traps). Not legal in the UK so only available if you intend to export it. £59 ref J59P1.

100 WATT MOSFET PAIR. Same spec as 25k343 and 25J413 (8A, 140v, 100w) 1 N channel and 1 P channel. £3 a pair ref J3P9.

LOW COST CAPS. 1,000 capacitors £3 (33u/25v) ref J3P10.

VELCRO. 1 metre length 20mm wide, blue. £2 ref J2P16

JUG KETTLE ELEMENTS. Good general purpose heating element just £3 ea ref J3P8 or 5 for £10 ref J10P3

VERY BIG MOTOR. 200v induction 1 1/2" 1410 rpm 10x7" GEC 1" keyed shaft. Brand new. £95 ref J95P1

BIG MOTOR. 220-240v 1425rpm 2.8A 5/8" keyed shaft GEC 6 5" x 8" complete with mounting plate. £38 ref J38P1

SMALL MOTOR. Electrobox 160 watt 3,000 rpm, 220-240v 3/8" shaft precision built £18 ref J18P1.

EPROMS 27C84 PACK OF 10 £7 REF M7P1.

EPROMS 27C256 PACK OF 10 £9 REF M9P1.

EPROMS 27C512 PACK OF 10 £10 REF M10P1.

MODEMS FOR £1.25? These modems are available for stripping only hence they are only 4 for £5 ref J5P3.

SOLAR POWERED WOODEN MODELS. Complete with solar panel, motor and full instructions. £9 ref J9P2 3 diff £20 ref J20P3

TV SOUND RECEIVER Fully cased, mains powered, that need a speaker for stand alone use or could be wired into hi fi. £12 ref 12P22

SOUND OPERATED LIGHT. Clap your hands and light comes on. Turns after preset delay. (4 AA's req'd) £2 ref J2P3.

FERGUSON SRB1 REMOTE CONTROLS. Brand new units ideal for a spare or have two remote! £4 each.

AMSTRAD PC CASE, POWER SUPPLY AND 1.44 FLOPPY DRIVE ALL THIS FOR £44 REF L44P1

BUMPER PACK NO 1 10 of our popular £1 packs for just £5 our choice of contents.

BUMPER PACK NO 225 of our popular £1 packs for just £12. Our choice of contents.

LCD 1 X 32 DISPLAY Bargain price of just £3 complete with loads of data for a similar display. £3 ref L3P1.

USEFUL POWER SUPPLIES. 18v 900mA dc output (regulated) fully cased with mains cable and DC out cable. £5 ref K6P1

UNCASSED PC POWER SUPPLIES. Standard PC psu without case, fan etc. Good for spare or low cost PC! £4 ref L4P8

RADAR DETECTORS. Detects X and K bands (the speed traps). Not legal in the UK so only available if you intend to export it. £59 ref J59P1.

100 WATT MOSFET PAIR. Same spec as 25k343 and 25J413 (8A, 140v, 100w) 1 N channel and 1 P channel. £3 a pair ref J3P9.

LOW COST CAPS. 1,000 capacitors £3 (33u/25v) ref J3P10.

VELCRO. 1 metre length 20mm wide, blue. £2 ref J2P16

JUG KETTLE ELEMENTS. Good general purpose heating element just £3 ea ref J3P8 or 5 for £10 ref J10P3

VERY BIG MOTOR. 200v induction 1 1/2" 1410 rpm 10x7" GEC 1" keyed shaft. Brand new. £95 ref J95P1

BIG MOTOR. 220-240v 1425rpm 2.8A 5/8" keyed shaft GEC 6 5" x 8" complete with mounting plate. £38 ref J38P1

SMALL MOTOR. Electrobox 160 watt 3,000 rpm, 220-240v 3/8" shaft precision built £18 ref J18P1.

EPROMS 27C84 PACK OF 10 £7 REF M7P1.

EPROMS 27C256 PACK OF 10 £9 REF M9P1.

EPROMS 27C512 PACK OF 10 £10 REF M10P1.

MODEMS FOR £1.25? These modems are available for stripping only hence they are only 4 for £5 ref J5P3.

SOLAR POWERED WOODEN MODELS. Complete with solar panel, motor and full instructions. £9 ref J9P2 3 diff £20 ref J20P3

TV SOUND RECEIVER Fully cased, mains powered, that need a speaker for stand alone use or could be wired into hi fi. £12 ref 12P22

SOUND OPERATED LIGHT. Clap your hands and light comes on. Turns after preset delay. (4 AA's req'd) £2 ref J2P3.

FERGUSON SRB1 REMOTE CONTROLS. Brand new units ideal for a spare or have two remote! £4 each.

AMSTRAD PC CASE, POWER SUPPLY AND 1.44 FLOPPY DRIVE ALL THIS FOR £44 REF L44P1

BUMPER PACK NO 1 10 of our popular £1 packs for just £5 our choice of contents.

BUMPER PACK NO 225 of our popular £1 packs for just £12. Our choice of contents.

LCD 1 X 32 DISPLAY Bargain price of just £3 complete with loads of data for a similar display. £3 ref L3P1.

USEFUL POWER SUPPLIES. 18v 900mA dc output (regulated) fully cased with mains cable and DC out cable. £5 ref K6P1

UNCASSED PC POWER SUPPLIES. Standard PC psu without case, fan etc. Good for spare or low cost PC! £4 ref L4P8

RADAR DETECTORS. Detects X and K bands (the speed traps). Not legal in the UK so only available if you intend to export it. £59 ref J59P1.

100 WATT MOSFET PAIR. Same spec as 25k343 and 25J413 (8A, 140v, 100w) 1 N channel and 1 P channel. £3 a pair ref J3P9.

LOW COST CAPS. 1,000 capacitors £3 (33u/25v) ref J3P10.

VELCRO. 1 metre length 20mm wide, blue. £2 ref J2P16

JUG KETTLE ELEMENTS. Good general purpose heating element just £3 ea ref J3P8 or 5 for £10 ref J10P3

VERY BIG MOTOR. 200v induction 1 1/2" 1410 rpm 10x7" GEC 1" keyed shaft. Brand new. £95 ref J95P1

BIG MOTOR. 220-240v 1425rpm 2.8A 5/8" keyed shaft GEC 6 5" x 8" complete with mounting plate. £38 ref J38P1

SMALL MOTOR. Electrobox 160 watt 3,000 rpm, 220-240v 3/8" shaft precision built £18 ref J18P1.

EPROMS 27C84 PACK OF 10 £7 REF M7P1.

EPROMS 27C256 PACK OF 10 £9 REF M9P1.

EPROMS 27C512 PACK OF 10 £10 REF M10P1.

MODEMS FOR £1.25? These modems are available for stripping only hence they are only 4 for £5 ref J5P3.

SOLAR POWERED WOODEN MODELS. Complete with solar panel, motor and full instructions. £9 ref J9P2 3 diff £20 ref J20P3

TV SOUND RECEIVER Fully cased, mains powered, that need a speaker for stand alone use or could be wired into hi fi. £12 ref 12P22

SOUND OPERATED LIGHT. Clap your hands and light comes on. Turns after preset delay. (4 AA's req'd) £2 ref J2P3.


FERGUSON SRB1 REMOTE CONTROLS. Brand new units ideal for a spare or have two remote! £4 each.

IN SUSSEX? CALL IN AND SEE US!

Macro Heliograph Receiver

PROJECT

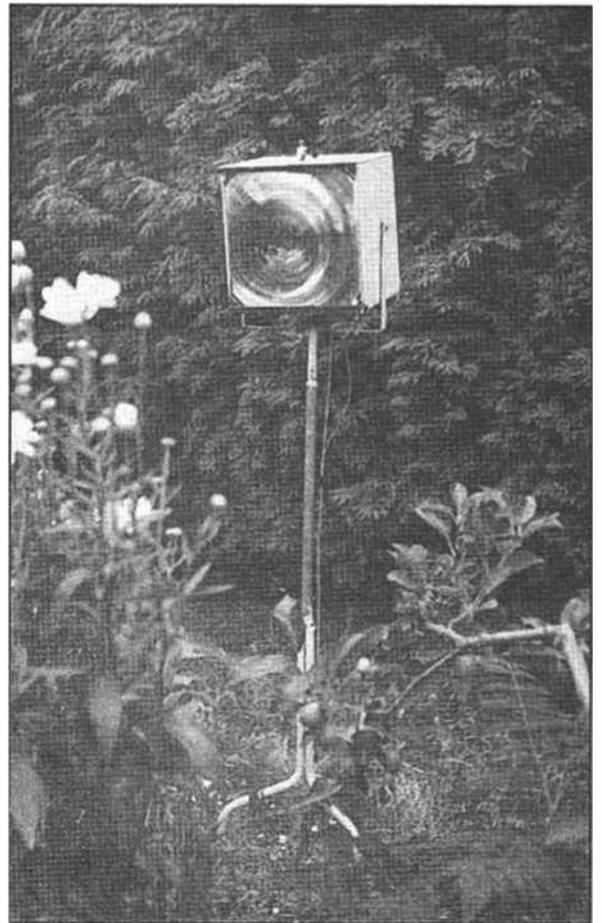Investigate sub-sonic low intensity frequencies with this receiver. I P Wilkinson provides the details.



Plop, whine, click, growl, buzz, (deep and high) and other such sounds are the sort of signals that can be heard on the headphones plugged into a Macro Heliography receiver. These signals are the result of sunlight being reflected from the shiny membrane, comprising the wing or wings, of a flying insect, much like the heliography used at sea.

This tiny amount of reflected sunlight is observable, after amplification, and can lead to many hours of fascinating study in wing beat frequencies, and thus the 'signature' of particular species of insect. Since there are more than 400

varieties in our countryside, this adds up to a lot of sound effects.

The essential ingredient required is of course sunlight. This has to be of sufficient strength to at least, cast a shadow. I have devised a simple table, for reference see Table 1.

Sun factor 1 is the PSD (Photo Synthetic Datum) defined as the, minimum light level required for photo synthesis

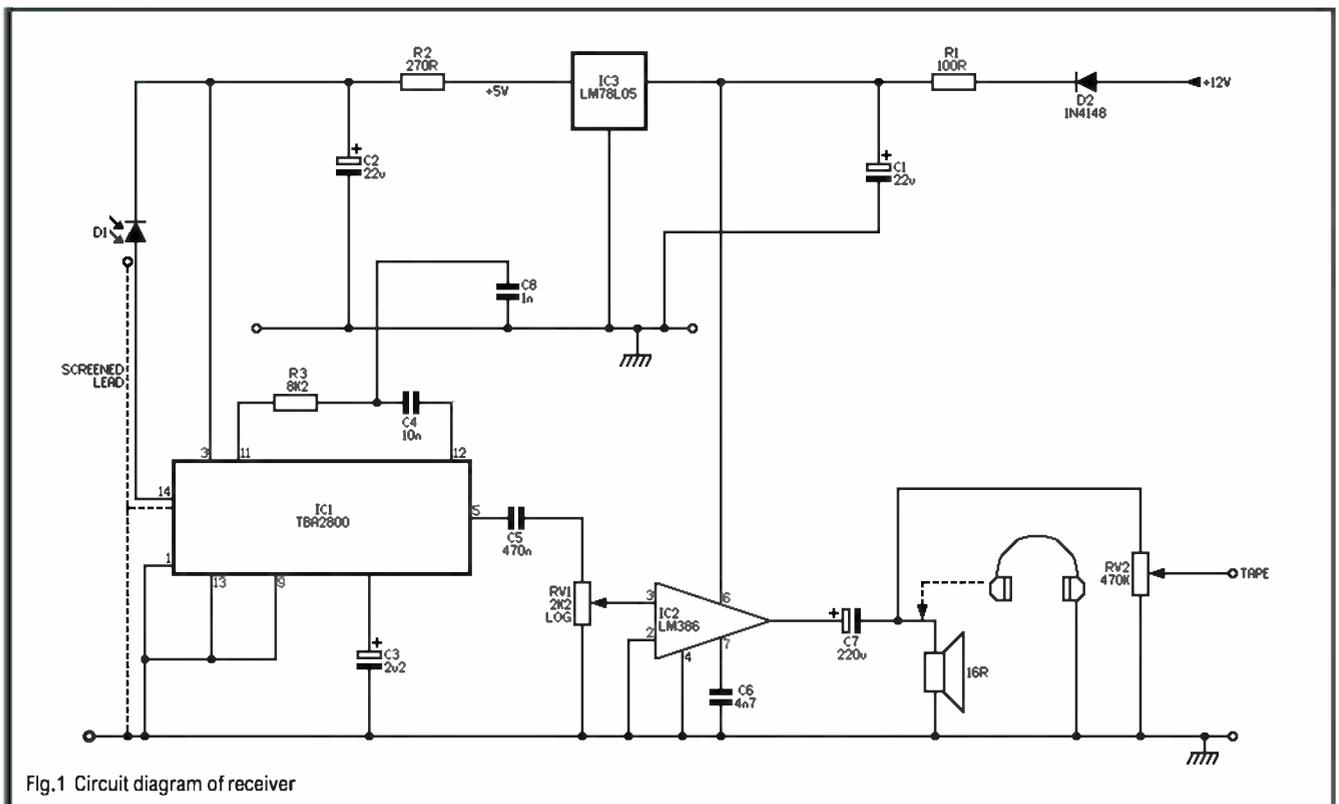


Fig.1 Circuit diagram of receiver

activity in plants. Safe sunbathing for sensitive skins of no more than 20 minutes a day, a SF of 2.5 is reasonable.

Looking at a shadow, estimation becomes quite easy with practice, and is born out by the signal results. For example at SF3 a hover fly, species *Episyrphus balteatus*, is detectable at a distance from the receiver of about 15 feet.

Butterflies are not easily detectable mainly because the wings are less reflective and show moving. At best at SF5 you might hear the odd Plop! sort of sound a small butterfly signature makes a few feet away.

Given the high resolution and sensitivity of the MH Rx other 'things' are detectable. A dew laden cobweb vibrating in the wind or under the movement of the spider or the spiders lunch can register. No doubt other things will come to mind, ripples on water etc.

Construction of the receiver is simplicity itself. Just two ICs and a few components mounted on strip board, a plastic lens a photo detector and a box to stick it all in. Mount the box a frame much like a camera on a tripod, connect phones and battery, 'aim' at the local flower patch or pond, sit back in the deck chair relax and listen to an aphid winging its way to wherever aphids wing their way to on a balmy sunny day.

Sun factor	Amount of Light	Signal strength.
0	No shadow	Nil
1	Very faint shadow	Poor
2	Shadow	Weak but usable
3	Good shadow	Fairly good
4	Strong shadow	Good
5	High contrast shadow	Very good

The detection corridor is determined by the cross-sectional area of the lens and the overall gain of the system. So the aphid winging its way at say, 10 mph, is not going to impress you for long. A hover fly is more entertaining as it generally stays in one place.

If you imagine you are looking down a tube 20 feet long and some few inches in diameter, and an insect can fly from from one side, and out of the other, you might get a better impression of what I mean. Aiming this invisible tube at say a cluster of flowers where the insects are flying in circles then signals are going to be better maintained.

So now we come to the lens, and bearing in mind the comments in the last paragraph, it needs to be a little larger in cross section than your average camera lens. It has also, in photographic optical parlance, got to be a 'fast' lens. Able in other words, to be usable at low light levels.

Now this might sound like a tall order in terms of expense, weight, etc. The lens happily for us, is a cheap plastic one, and low in the weight stakes, and 'fast'. A Fresnel lens, commonly used on overhead projection lamps, varying around 8 to 14 inches square, with a short focus satisfies all the criteria I have outlined. For those of you with a photographic bent, I am talking of an f stop faster than a 1.2 probably less than a ONE, with some of these types of lenses.

A perfect optical focus is not required, a pin photo diode not being so demanding as the human eyeball. Thus saving in cost compared with high resolution glass lenses is achieved.

Deciding on the cross-sectional area of the lens, will determine the size of the housing for it, and the overall bulk of the finished project. I started off with a 13" lens, which I still use, but one can get by quite well with a 5" lens, a considerable saving in the enclosure materials.

Reference to Figure 3 gives you some idea as to the general fabrication of the enclosure, using thin ply, dowel and glue. Build the unit around the lens, after determining the focal length. Focus the sun on a bit of card and measure the distance from the back of the lens to the card, and make a note. Adding roughly a quarter of an inch to this focal length, will give the position for the photo diode.

Fine focus for best results is achieved by adjusting the position of the Veroboard, when mounting inside the enclosure. A target comprising a model electric motor with a 1" tin plate propeller set some 15 feet away (in sunlight SF3 or greater) will provide an ideal focusing and test rig.

Some method of sighting is required, and reference to Figure 2 shows a crude but workable method using basic hardware. Adjust the rear sight using the motor simulator as the target. Once the focusing and sighting arrangements

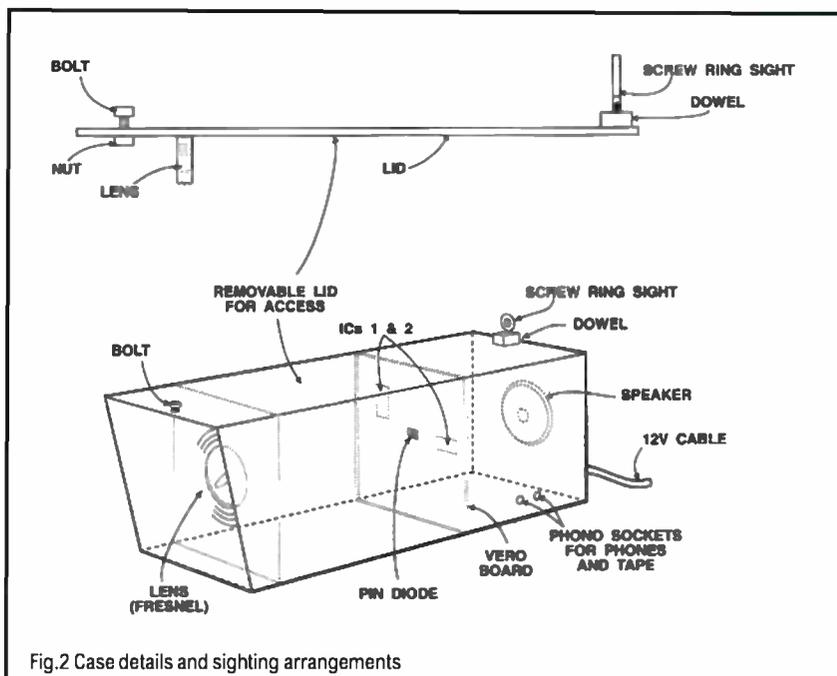


Fig.2 Case details and sighting arrangements


have been made secure with glue and pins to prevent disturbance to these settings.

Build the MH Receiver on an area of Veroboard to fit snugly inside the enclosure vertically as shown, with the photo diode centrally placed on the lens axis. (Figure 2). Recess the lens well back inside the enclosure approximately 2 inches on the base. It is wise to use the MH Receiver in a sheltered place, from inside an open window, under a tree to avoid accidental direct exposure to the sun.

Assembly of the electronics is simple enough, start off with the pin diode mounted in the centre of the strip board and check alignment in the enclosure with the lens axis, the actual mounting of the board on two blocks of dowel for support is the method I used. Commence with mounting the IC socket for IC1 orientated in such a way, that pin 14 is closest to the anode of the pin diode photo detector. Cut away any excess track to avoid stray pick up. If for some reason you want to mount the diode on a pillar, then ensure the lead from the anode is kept short and well screened.

IC2 you can solder straight in to the board, screening the lead if a long run, to pin 3. RV1 can be a preset mounted on the board, adjust for minimum volume consistent with a

PROJECT

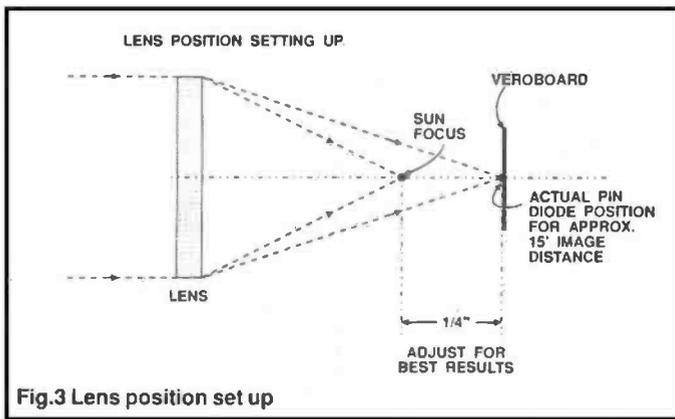

reasonable level of output.

D1 is for reverse polarity protection for when running this receiver from a battery out in the field or garden etc. The gain of the receiver is around 70db, and like most high gain systems, noise starts to rear its ugly head, especially when we are amplifying what after all is a change of leakage current in a reversed biased diode, a notorious source of noise, which in this application increases with the light level on the diode.

The RC network between pins 11 and 12 of ICI reduce this noise factor somewhat, at expense of bandwidth, C1 being the most critical value,

should you wish to experiment. C2 is a decoupling capacitor and is located as near to the IC pins as possible. All resistors are 1/4 watt, all capacitors polyester or min layer types. Headphones are better for this sort of activity, and can be directly connected across the loudspeaker of 16 ohms. RV2 is set to about 80k on the wiper. This provides about the right level for tape recording the various sounds detected. A supporting frame to allow hands free operation is recommended, much along the lines of a camera tripod. I utilised part of an old bar stool with an extended centre column, and mounted a bracket at the top of this to, give azimuth, and tilt capability.

This project would provide a challenge in building over the winter months ready for the forthcoming summer. Take care with cutting the lens down to size, especially if it is the two layer Fresnel type, to avoid getting chaff between the two slices. Clamp together when sawing, then glue round the edge.

Source for lenses: Anchor Supplies, Nottingham. Large (worn round the neck) plastic reading lenses, are an alternative.

Good luck and good hunting.

PARTS LIST

RESISTORS

R1	100R
R2	270R
R3	8k2
RV1	2k2 log
RV2	470k

CAPACITORS

C1,2	22u
C3	2u2
C4	10n
C5	470n
C6	4n7
C7	220u
C8	1n

SEMICONDUCTORS


IC1	TBA2800
IC2	LM386
IC3	LM78L05
D1	Photo Diode
D2	1N4148

MISCELLANEOUS


LS1 loudspeaker 16R or headphones

EASY-PC PCB and Circuit Diagram CAD

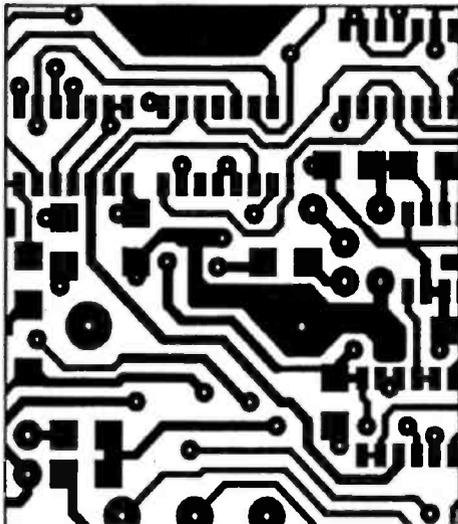Forget using tapes and light-box! Create your Circuit Boards using CAD - like the professionals.



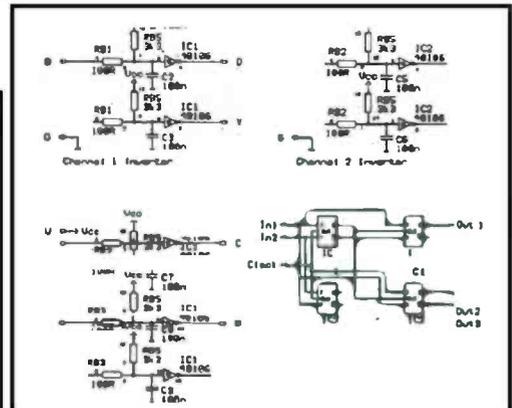- Runs on PC/XT/AT etc. with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design Schematics Single and Double sided and Multilayer boards including Surface Mount.
- Standard output includes Dot Matrix/ Laser/ Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill
- Extremely powerful.
- Very easy to use.
- Not copy protected.



EASY-PC

Technical support is free, for life!

Only £98.00!

Plus P&P+VAT

Over 13,000 Installations in 70 Countries Worldwide!

For full info' please write, phone or fax:


Number One Systems Ltd.

The Electronics CAD Specialists.

REF: ETI, HARDING WAY, ST. IVES, HUNTINGDON, CAMBS, PE17 4WR, ENGLAND.

Telephone: 0480 61778 (7lines) Fax: 0480 494042 ACCESS, AMEX, MASTERCARD and VISA Welcome.

PROJECT

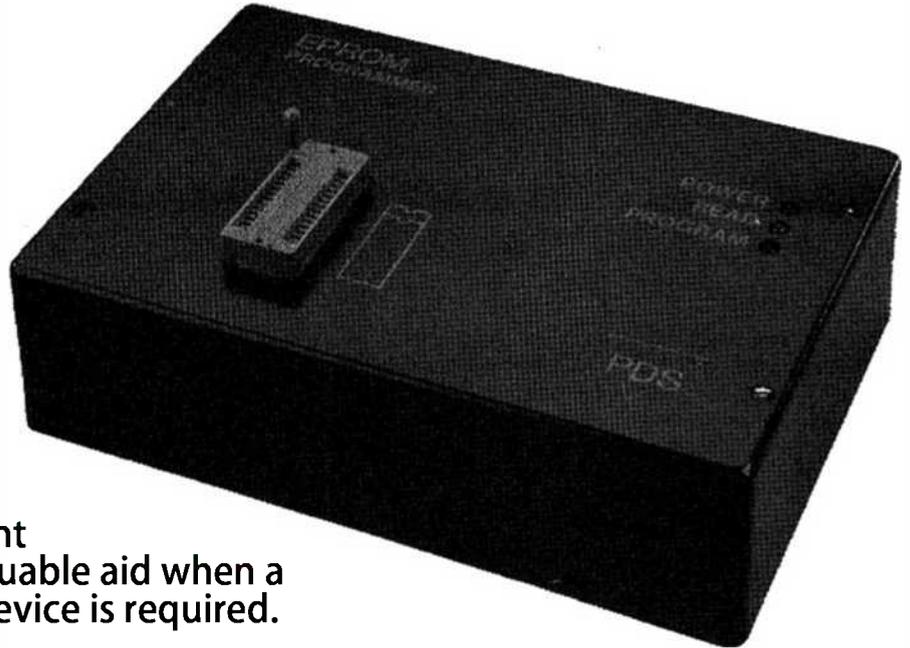

A project as an aid to other projects. Paul Stenning provides an excellent design and an invaluable aid when a pre-programmed device is required.

EPROM Programmer

There has long been a requirement for a cheap straight-forward EPROM Programmer, suitable for occasional home use, without the extra features found on many commercial units. The EPROM Programmer presented here will program the standard 27 family of devices, from 2716 to 27512, and can be used with any computer which has an RS232 serial port. I have avoided the usual "Catch 22" situation of requiring a programmed EPROM to make the EPROM programmer work! This design uses readily available components to reduce the likelihood of obsolescence.

The unit is powered from an external PSU, since this is cheaper than buying the individual parts! One of the low cost unregulated types with an integral mains plug is suitable, providing it is capable of supplying between 10 and 18 Volts. DC at 500mA without too much ripple, the voltage regulator IC21 will run cooler if the voltage is nearer the lower end of this range. The types sold for powering electronic keyboards appear to be the most suitable. The prototype is powered by an old Sinclair ZX81 PSU (type UK.1200).

The programmer itself is dumb and is fully controlled by the host computer via the serial port. Control software can be written in BASIC, and a suitable listing for IBM PC compatible computers is given later. Additional software listings are given for initial testing, and to convert to and from standard Intel-HEX files. A disk is available from the author, containing these programs, as well as comprehensive menu driven control software and a selection of useful utilities, see Buylines for details.

Please note that the programming algorithms used may not be exactly as specified in some EPROM manufacturer's data sheets. Because of this the unit cannot be guaranteed to program every device successfully, however no problems have been experienced to date.

HOW IT WORKS HARDWARE

The circuit may appear complicated initially, however a comprises of several relatively straight-forward sections. It is not necessary to understand the operation of the circuit to build and operate the unit with the software given, however a good understanding is most useful if you wish to write your own control software.

Note that when a number is followed by an 'h' in the following description, for example 27h, is a hexadecimal number, and when a number is followed by a 'b' it is binary, other numbers are decimal. Any signal name which is followed by a "-", for example STROBE-, is active low, on the circuit diagram this will be shown with a bar over the name.

Useful information on EPROM pin-outs and programming requirements can be found on pages 498-499 of the 1993 Maplin catalogue, the project was designed around this data (note that the Maplin programming information for the 2732 is incorrect).

IC2 and surrounding components generate the Baud Rate clock signal (CLOCK1) for IC3, with the rate selectable by LK1. The CLOCK2 signal is used to produce the programming timing pulses, see later. IC3 is a 6402 "Universal Asynchronous Receiver/Transmitter" (UART). In this application it is configured for 8 data bits, 1 stop bit, no parity checking. Note that unused pin 2 is taken low, this pin is used on the RCA CDP1854 to select standard operation mode, this device is otherwise pin compatible can therefore be used in place of the 6402. IC3 is reset by IC4:A and associated components.

When serial data is received on pin 20 of IC3, is converted to a parallel output on pins 5-12 (R0-R7), and pin 19 goes high. A short time later (set by R4 and C8) pin 18 is taken low, which clears the high on pin 19. The pulse so generated on pin 19 is referred to as the STROBE signal, and indicates to other parts of the circuit that data has been received and is valid.

If pin 23 of IC3 (SEND) is pulsed low, data on pins 26-33 (D0-D7) is transmitted in serial form on pin 25.

PROJECT

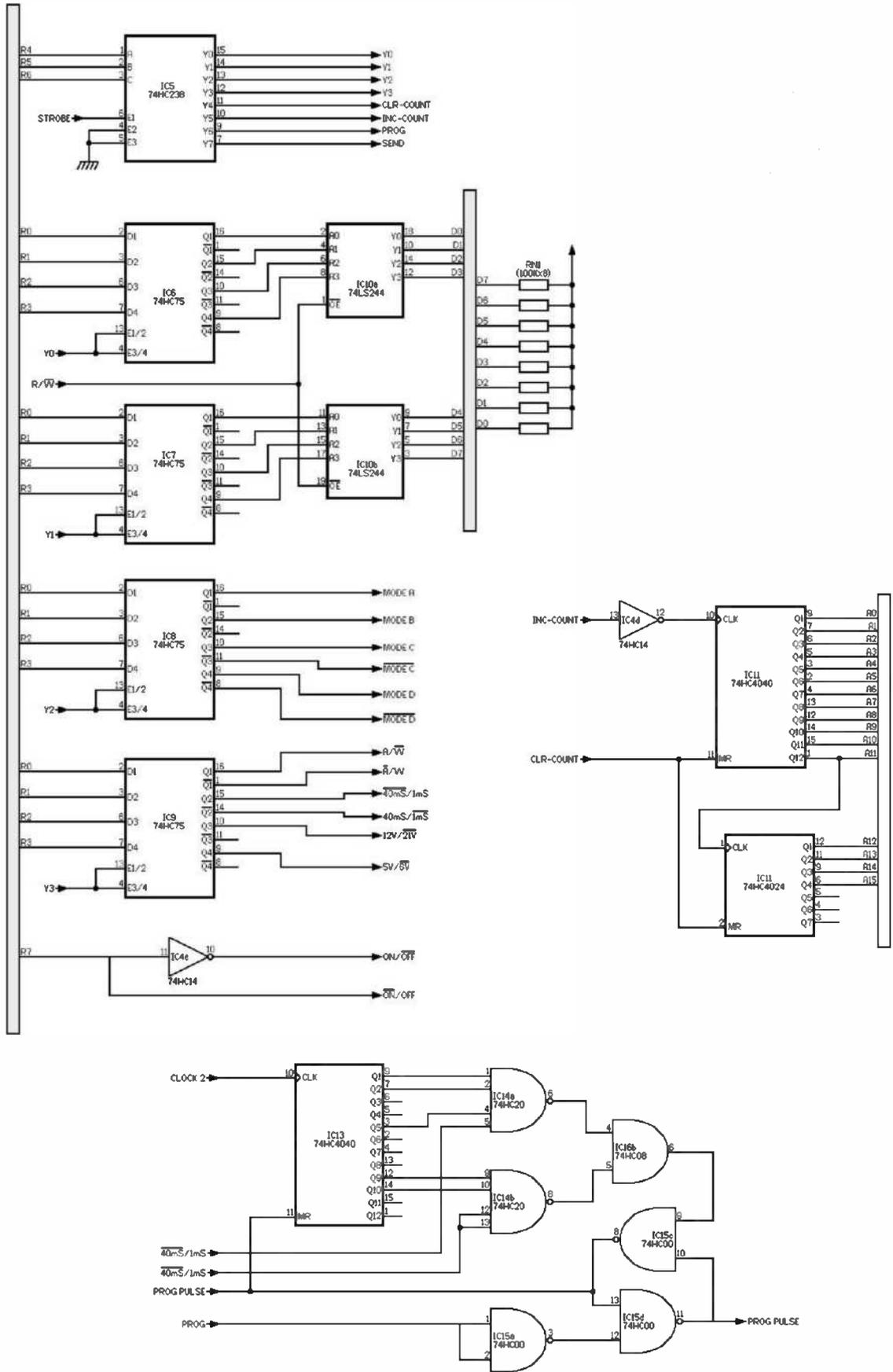


Fig. 2 EPROM Programmer Logic

IC1 is the serial line driver/receiver, which converts RS232 standard serial signals to from standard 5V TTL levels. This IC contains voltage converters to produce the required transmission voltages (9V) from a single +5V supply.

In this application the 8 bit received data is used as 4 data bits on R0-R3 and 4 control bits on R4-R7. 3 of these control lines (R4-R6) are taken to a 3 To 8 Line Decoder, IC5. The STROBE signal is taken to one of the Enable lines on IC5, thereby causing the outputs from this IC to be short pulses. For example, if 00h is received, lines R4-R6 will be low, STROBE will pulse high and consequently pin 15 of IC5 will pulse high and the remaining outputs will stay low.

The remaining control bit (R7) controls the power to the EPROM, when it is high all power is removed from the EPROM socket so the device can be inserted or removed. When the device is being read or programmed this line is taken low.

The 4 data lines are taken to the inputs of 4 Quad D-Type Latch, IC6-IC9. The Latch Enable lines on these ICs are connected to 4 of the outputs of IC5 (Y0-Y3). Data can therefore be stored in these latches by seeing the required data on lines R0-R3 and the latch number (0-3) on lines R4-R6. The data will be continuously available on the latch output lines. Referring back to the previous example, if 00h is received, lines R0-R3 will all be low, and line Y0 will pulse high, storing 0h (0000h) in IC6. Similarly seeing 35h will store 5h (0101h) in IC9.

Latch IC6 is used to hold the least significant nibble (4 bits half a byte) of the data which will ultimately be programmed into the EPROM, whilst IC7 holds the most significant nibble. IC5 holds the EPROM type information (see later), and IC9 holds 4 setup bits. Bit 1 of IC9 controls whether the unit is in Read or Write (Program) mode, bit 2 sets the programming pulse length to either 1 or 40 milliseconds, bit 3 sets the programming voltage to either 12 or 21 volts, and bit 4 sets the supply voltage whilst programming to either 5 or 6 volts. Note that the latches have active-high and active-low outputs, and one or both may be used.

The data outputs from IC6 and IC7 are taken to a tri-state buffer (IC10), which in turn drives the EPROM data lines. IC10 is controlled by the RN-line, such that its outputs are enabled in Program mode and tri-state in Read mode.

The EPROM data lines are also connected to the data input lines on the UART (IC3), and the Y7 output from IC5 is connected to pin 23 of IC3 (SEND). Therefore if 70h is received, the data currently on the EPROM Data Lines is transmitted back along the serial interface to the computer.

The EPROM Address lines are controlled by counters IC11 and IC12. These are connected to lines Y4 and Y5 from IC5, and are therefore cleared to 0000h by sending 40h and the count is incremented by sending 50h. This approach is quicker than having to set the actual address each time since it only requires one byte to be sent along the serial link.

Line Y6 from IC5 (PROG) is used to start a programming pulse. The programming pulse (either 1ms or 40ms) is produced by dividing down the CLOCK2 signal. This signal has a frequency of 19.2kHz (24576MHz divided by 128), which equates to a period of 52.1us. This is fed to counter IC13, which is normally held reset by the Set Reset flip-flop built from IC15c and IC15d. When the PROG line pulses high the flip-flop changes state and the counter starts counting the CLOCK 2 pulses. If a 1ms pulse is required, pin 5 of IC14 will be high and pins 12 and 13 of IC14 will be low. When the count reaches 19 (52.1us x 19 = 989.9us), all the inputs of IC14 will be high, its output will therefore go low, changing the state of the flip-flop again via IC16d, and resetting the counter. A 0.99ms pulse will therefore be present on the output of the flip-flop, 0.99ms being well within the 1ms +/-5% specification. If a 40ms pulse is required IC13 counts 768 CLOCK2 pulses (52.1us x 768 = 40.01ms).

The PROG PULSE and STROBE signals are coupled via IC18a and IC1 to the RS232 CTS (Clear To Send) line. This prevents the host computer from sending further data whilst a program pulse is programming while STROBE is still high. This means that data can be sent as fast as possible and no delays are needed in the software.

PROG PULSE is coupled with the SEND signal to IC3 by IC16a. This prevents the SEND signal getting through whilst PROG PULSE is low. This situation will never occur in normal use, however during initializations the software requests a 40ms program pulse immediately followed by a SEND. If the RS232 CTS line is present and working then data will be sent, since the CTS line will stop the computer sending the SEND request until after the program pulse has finished. If CTS is not working the SEND request will be sent immediately but no data will be returned due to IC16a stopping the SEND pulse reaching IC3. The software notes the lack of received data, prints a warning and then adds delays to allow for the program pulse. You should try to get CTS working properly as there will be a significant speed penalty otherwise.

We now come to the connection switching required for the different EPROM types. The table below shows the pin-outs for the 6 types of EPROM this unit will program. 2716 and 2732 are 24 pin devices and fit into pairs 3 to 26 of the EPROM socket, the pin-outs shown below relate to the socket not the device.

PIN	2716	2732	2764	27128	27256	27512
#1	**	**	VPP	VPP	VPP	A15
2	**	**	A12	A12	A12	A12
3	A7	A7	A7	A7	A7	A7
4	A6	A6	A6	A6	A6	A6
5	A5	A5	A5	A5	A5	A5
6	A4	A4	A4	A4	A4	A4
7	A3	A3	A3	A3	A3	A3
8	A2	A2	A2	A2	A2	A2
9	A1	A1	A1	A1	A1	A1
10	A0	A0	A0	A0	A0	A0
11	D0	D0	D0	D0	D0	D0
12	D1	D1	D1	D1	D1	D1
13	D2	D2	D2	D2	D2	D2
14	GND	GND	GND	GND	GND	GND
15	D3	D3	D3	D3	D3	D3
16	D4	D4	D4	D4	D4	D4
17	D5	D5	D5	D5	D5	D5
18	D6	D6	D6	D6	D6	D6
19	D7	D7	D7	D7	D7	D7
#20	CE/PP+	CE/PP-	CE	CE	CE/PP-	CE/PP+
21	A10	A10	A10	A10	A10	A10
#22	OE	OE/VPP	OE	OE	OE	OE/VPP
#23	VPP	A11	A11	A11	A11	A11
24	A9	A9	A9	A9	A9	A9
25	A8	A8	A8	A8	A8	A8
#26	VCC	VCC	NC	A13	A13	A13
#27	**	**	PP-	PP-	A14	A14
28	**	**	VCC	VCC	VCC	VCC

- ** = No Pin
- NC = No Connection
- PP+ = Program Pulse, Positive Going
- PP- = Program Pulse, Negative Going
- OE = Output Enable (Active Low)
- CE = Chip Enable (Active Low)
- VPP = Programming Voltage
- VCC = Supply Voltage
- GND = Ground (0V)

It can be seen from the above that most of the pins are the same for all devices. Only 6 pins require special attention, these are 1, 20, 22, 23, 26 and 27, and are marked with a '#' next to the pin number.

The four MODE lines from IC9 control the function of these six pins and are set up by the software to suit the EPROM type required. Note that two of the active-low levels are also used. The table below shows the logic levels on each of these lines, for each of the 6 types of EPROM, together with the code that needs to be sent to select that type.

PROJECT

EPROM TYPE	MODE LINE						SETUP CODE
	A	B	C	C-	D	D-	
2716	1	1	1	0	1	0	2Fh
2732	1	0	1	0	0	1	25h
2764	1	1	0	1	0	1	23h
27128	1	1	0	1	0	1	23h
27256	1	0	0	1	0	1	21h
27512	0	0	0	1	0	1	20h

I will now describe what this means for each type of EPROM

2716:

PIN 1: not used.

PIN 20: MODE B and MODE D are both high, so IC17b pin 6 remains high, IC16c pin 8 follows PROG PULSE, as does IC17c pin 8 which is coupled via O6 to PIN 20. PIN 20 is only pulled up in Program mode, so in Read mode it is permanently low.

PIN 22: MODE A and MODE D are both high, so IC15b pin 6 is low and O1 and O2 remain off. R-/W is coupled to the pin via O2.

PIN 23: MODE D is high, so Q5 and Q6 are on, coupling VPP to PIN 23.

PIN 26: MODE C is high, so Q7 and Q8 are on, coupling V+ to PIN 26.

PIN 27: not used.

2732:

PIN 1: not used.

PIN 20: MODE B and MODE D are both low. IC16c pin 8 will remain low and U17:B pin 6 will follow PROG PULS. IC17c pin 8 will therefore be PROG PULSE inverted, and is coupled via O6 to PIN 20. PIN 20 is only pulled up in Program mode, so in Read mode it is permanently low.

PIN 22: MODE D and MODE A is high, so IC15b pin 6 is high. This switches on O1 and O2, coupling VPP to PIN 22

PIN 23: MODE D is low, so Q5 and Q6 remain off. A 11 is coupled to PIN 23 via O4.

PIN 26: as 2716.

PIN 27: not used.

2764 and 27128:

PIN 1: MODE A is high. This switches on O3 and O4, coupling VPP to PIN 1.

PIN 20: MODE B is high and MODE C is low. IC16c pin 8 remains low and U17:B pin 6 remains high, therefore IC17c pin 8 remains low.

PIN 22: MODE A and MODE C are both high, so IC15b pin 6 is low and O1 and O2 remain off. R-/W is coupled to PIN 22 by O2.

PIN 23: as 2732.

PIN 26: MODE C is low so O7 and Q8 remain off. A13 is coupled

to PIN 26 by O5. Note that in a 2764 EPROM there is no connection to PIN 26.

PIN 27: MODE B is high and A14 will remain low since it is outside the addressing range. IC17d pin 11 will therefore follow PROG PULSE.

27256:

PIN 1: as 2764.

PIN 20: as 2732.

PIN 22: as 2764

PIN 23: as 2732

PIN 26: as 2764

PIN 27 - MODE B is low so IC16 pin 11 will remain low.

IC17d pin 11 will follow A14.

27512:

PIN 1: MODE A is low so Q3 and Q4 will remain off. A15 is coupled to PIN 1 by O3.

PIN 20: as 2732.

PIN 22: MODE A is low so IC15b pin 6 will be high, switching on Q1 and Q2, coupling VPP to PIN 22.

PIN 23: as 2732.

PIN 26: as 2764.

PIN 27: as 27256.

Note that D6 and D7 are germanium types, since silicon types would cause the logic 0 inputs to the EPROM to be at the limit of the specifications.

The two logic gates which would otherwise be unused, are used to control Read and Program LED's. IC18b pin 6 goes low when R-/W and ON-/OFF are both low, lighting O9 (Read) via O10, whilst IC18c pin 8 goes low when R/W and ON-/OFF are low, lighting O8 (Program) via O9. When both LED's are off it is safe to fit or remove the EPROM, the other lines would have been set low by the software before taking ON-/OFF high.

IC21 is the main 5 Volt regulator and powers all the logic IC's. D11 protects the whole circuit against reverse polarity, since it is easily possible to reverse the polarity on the sort of PSU used. LED D10 indicates that the unit is powered up.

IC20 supplies the power to the EPROM, and is enabled by the ON/OFF- line via Q17 and Q18. Q19 raises the GND pin of IC20 by 1 Volt, giving 6 Volts. When 5 Volts is required Q19 is shorted out by Q20 controlled by IC18d, this happens when 5V/6V or R/W- is low.

IC19 is a step-up switching regulator which produces the programming voltage required. The voltage is set by shorting out sections of the resistor chain with transistors. 2716 EPROMs require 25 Volts, not 21 Volts, so the MODE D- line is used to set this. The R-/W line controls Q15 and Q16 which connect the power to the EPROM when the unit is in Program mode.

PARTS LIST

RESISTORS (all 1/4W 5% or better)

R1,6-19,27-33,36-38,41,42 10k

R2 4M7

R3 2k2

R4 1k0

R5 47k

R20,21 22k

R22,23,40 330R

R24 0R47 (or 2 x 1R0 in parallel)

R25 1k2

R26 8k2

R34 5k6

R35 1k5

R39 470R

RN1 100k x 8 SIL resistor network

RV1 470R or 500R horizontal preset

RV2-4 4k7 or 5k0 horizontal preset

CAPACITORS

C1-5,9,15,16 10µ 16V radial

C6,7 22p 0.2" pitch ceramic

C8 2n2 0.2" pitch ceramic

C10 220p 0.2" pitch ceramic

C11 470n 0.2" pitch

C12 47µ 35V radial

C13 47µ 16V radial

C14,17 1µ0 16V radial

C18-20,22-27 100n 0.2" pitch

C21 220µ 25V radial

INDUCTORS

L1 470µH 2.3A bobbin type

SEMICONDUCTORS

IC1 MAX232

IC2 74HC4060

IC3 6402

IC4 74HC14

IC5 74HC238

IC6-9 74HC75

IC10 74LS244

IC11,13 74HC4040

IC12 74HC4024

IC14 74HC20

IC15 74HC00

IC16 74HC08

IC17,18 74HC32

IC19 TL497

IC20,21 7805

Q1,3,5,7,15,17 ZTX750/751/752

Q2,4,6,8,13,14,16,18-20 BC547/548/549

Q9-12 BC557/558/559

PROJECT

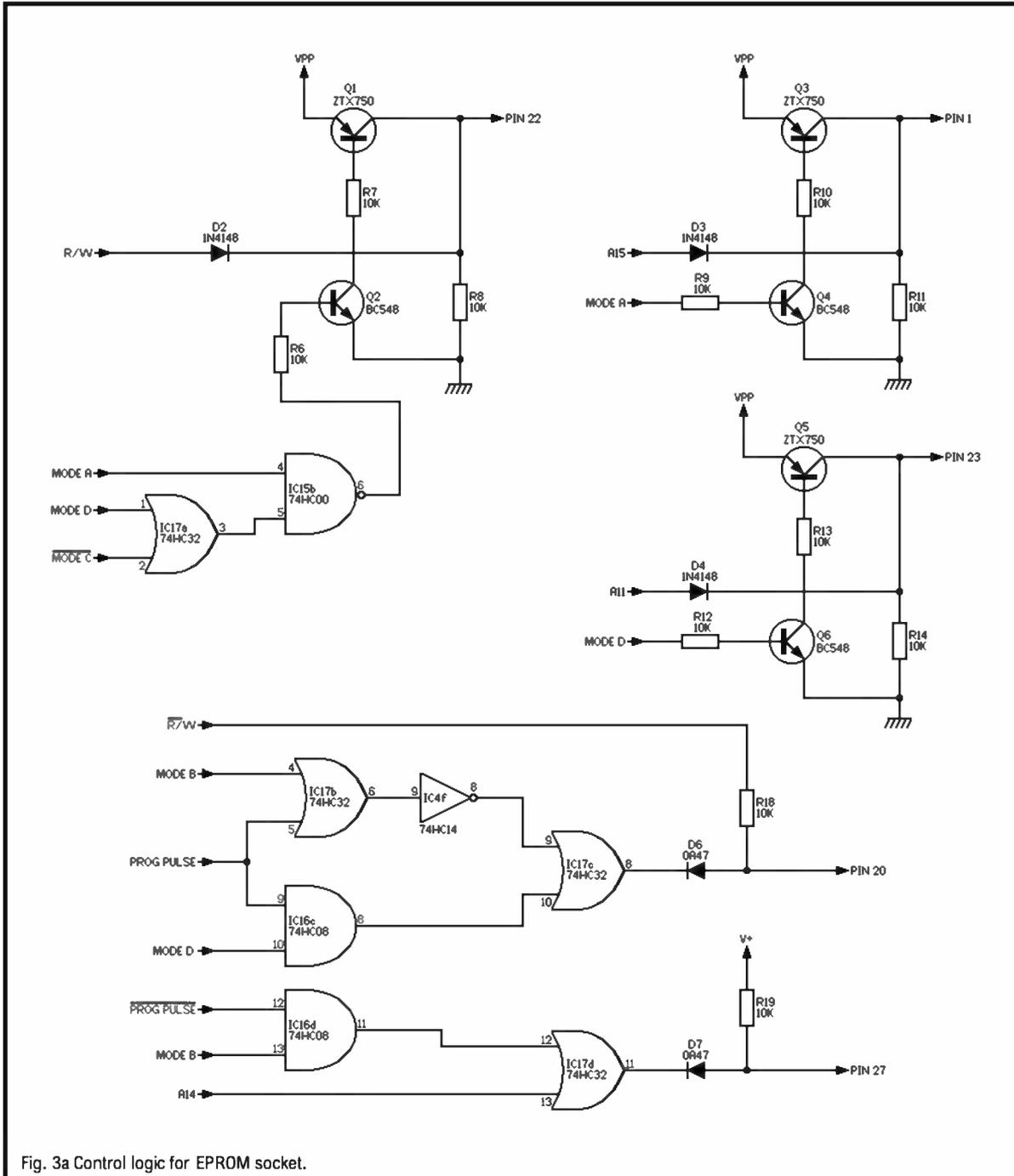


Fig. 3a Control logic for EPROM socket.

- D1-5 1N4148 silicon signal diode
- D6, 7 0A47 germanium signal diode
- D8 Red LED
- D9 Yellow LED
- D10 Green LED
- D11 1N4001

MISCELLANEOUS


- SK1 28-way ZIF Socket
- XT1 2.4576MHz crystal

Power Supply (10-18V DC@ 500mA), DIL IC sockets (1 x 40 way, 1 x 14 way and 3 x 28 way), Heat sink for IC21, PCB, Case type MB6, M3 hardware, Connectors for power and RS232, Veropins, Tinned copper wire (24SWG) or through-PCB pins.

BUYLINES

All components are available from Maplin, the majority can probably also from your usual supplier. Small 0.47R resistors do not appear to be readily available. use two 1R0 components in parallel. The PCB will be available from the ETI PCB service, next month. Before purchasing a power supply, check the latest bargain list from Greenweld (0703 236363), they often list suitable units for about £3. The software listed in this article, together with a comprehensive menu driven control program and some useful bits and pieces (IBM PC or compatible only) is available from the author at the following address: Paul Stenning, 1 Chisel Close, Hereford, HR4 9XF. Please send a blank PC formatted disk (3.5" or 5.25"), together with a cheque or postal order for £10, a return address label and adequate return postage (overseas 2 International Reply Coupons). If you do not have a disk send £12 and I will supply one (please specify size). BAE.C. members see newsletter for a special offer! The author would also be interested to hear from users of other computers who have either written suitable control software or who are looking for some - he will attempt to put one in touch with the other! Please write with an SAE.

PROJECT

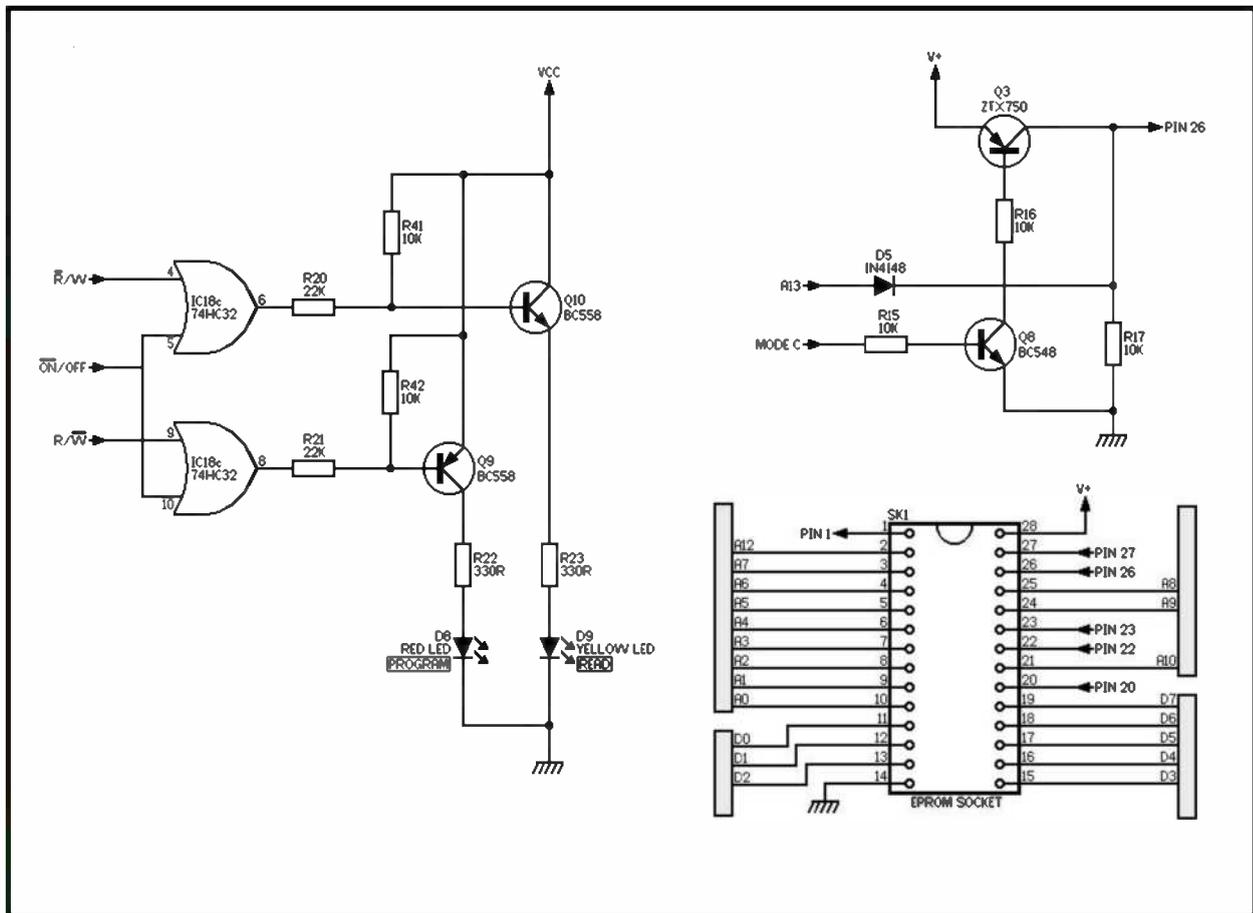

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

7403N with 7A18 & 7B50 Dual Trace 80MHz	£50
TEKTRONIX 2336 Dual Trace 100MHz Delay Sweep Ruggedised	£1000
NIATSU SS5711 Four channel 100 MHz Delay Sweep	£700
HITACHI V1050F Dual Trace 100 MHz Dual TB with 4 Channel Mode	£650
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£550
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£450
TEKTRONIX 2213 Dual Trace 60MHz	£350
TEKTRONIX 2225 Dual Trace 50MHz Alternate TB Magnification	£450
PHILIPS PM2211 Dual Trace 50MHz Delay Sweep	£400
GOLLO OS3500 Dual Trace 50MHz Delay Sweep	£325
GOLLO OS1100 Dual-Trace 30MHz	£180
GOLLO OS3000 Dual-Trace 20 MHz	£200
NIATSU CS5702 Dual-Trace 20 MHz	£825
HAMEG 205.3 Dual-Trace 20MHz Digital Storage	£450
GOLLO 1421 Dual Trace 20MHz Digital Storage	£350

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

PHILIPS PM5131 PROGRAMMABLE SYNTHESIZER/FUNCTION GENERATOR
0 to 10Hz IEEE-488 As new £1500

MARCONI 2440 20MHz Microwave Counter	£1500
MARCONI 2610 True RMS Voltmeter	£800
FARNELL SSC1000 Sig Gen 10MHz-1GHz Syn	£1180
FARNELL Syn Oscillator DSG1 - 0.0001Hz-99.99kHz	£150
MARCONI TF2015 AM/FM 10-520MHz Sig Gen	£380
MARCONI TF 2015 with Synchroniser TF2171	£300
MARCONI TF2016 AM/FM 10kHz-120MHz with TF2173	£300
MARCONI TF2016 without Synchroniser TF2173	£150
MARCONI BA400 8MHz Sig Source Various models Covering 400kHz-8.5GHz	from £260

RACAL Instrumentation Recorders
Store 4D and Store 7D from £500

KEITHLEY 224 Programmable Current Source £1800

PERKINELMER R15 Recorder Test Set from £280

GOLLO BROMATON K5000 Logic Analyser £750

HIP PULSE GENERATOR type 214B £750

RACAL/DANA 1991 Handcount Universal Counter £800

FARNELL SS3520 Synthesised Sig Gen 10-520MHz £400

FARNELL TY5320 Transmitter Test Set Consisting of RF AF Counter RF Mod Meter RF Power Meter AF Voltmeter AF Deflection Meter AF Synthesiser £400

SOLD as a pair for ONLY £750

SPECTRUM ANALYSERS

TEKTRONIX 4M4P 10kHz-210kHz (225 GHz with additional modules)	£15,000
HP 1411 with 8554A & 8552A 10MHz-18GHz	£2,800
HP 1411 with 8554B & 8552B 500kHz-1250MHz	£1,300
HP 1401 with 8554A & 8552A 500kHz-1250MHz	£1,800
HP 1411 with 8556A & 8552A 10kHz-110MHz	£1,800
HP 1401 with 8556L & 8552A 10kHz-110MHz	£800
MARCONI TF 2370 30kHz-110MHz	£1,580
HP 142c with 8556 100kHz-1500MHz	£1,580

Used Equipment - Guaranteed. Manuals supplied if possible.
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering.
CARRIAGE on all units £16. VAT to be added to total of Goods and Carriage.

STEWART OF READING
110 WYKHAM ROAD, READING, BERKS, RG6 1PL
Tel: (0734) 268041 Fax: (0734) 351696. Callers welcome 9am-5.30pm Mon-Fri (until 8pm Thurs)

P.S.

WHAT HAVE YOU MISSED IN 1992

THERE'S NO NEED TO WORRY ABOUT THE ISSUES OF ETI YOU'VE MISSED IN 1992

Make a New Year's resolution and phone the ETI Back Issues Service. The last 12 months issues are available only while stocks last so call: 0737 768611 today and check availability to avoid disappointment.

Back Issues of ETI cost the cover price plus 60p postage and packing. Order by phone or write to ETI Back Issues, ABP, Queensway House, 2 Queensway, Redhill, Surrey, RH11QS.

Cheques should be made payable to ASP.

1992

READER OFFER

MINI POWER TOOL ACCESSORY PACK

SAVE £15



**ONLY £13.99
R.R.P. £30.00**

Purchasers of this bargain pack will avail themselves of an instant selection of tooling ideally suited for use with any of the variety of Mini-Drills currently available.

Whilst the individual contents may vary from pack to pack, the kit supplied for review contained a very useful selection of small drills, burrs, rotary brushes, mounted abrasive points and a threaded mandrel together with a couple of rubber bonded abrasive points. Whatever the special interest, you are bound to find many applications for items in this bargain pack and when a favourite finally wears out it should be relatively easy to replace from your local stockist, but not at this price!

We have arranged a very special price saving you over 50%, so hurry, as we have only a limited quantity. Our price to you £13.99 (normally retails at £30.00) + £1.00 p&p.

Telephone Orders... 0442 66551 (24 HRS)

Please supply ROME6/68 @ £13.99 + £12.00 p&p.
I enclose my cheque/P.O. for £ made payable to ASP or please debit my Access/Visa Expiry

Signature

Name

Address

Post Code

Coupon to: ASP Reader Offers, Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST
Please allow 28 days for delivery U.K. only - Overseas upon request.
Please note that from time to time you may receive information about offers and services which may be of interest to you.



UK DISTRIBUTOR AND STOCKIST FOR THE COMPLETE ILP RANGE

- ★ AMPLIFIER MODULES
- ★ PRE-AMPLIFIERS
- ★ 100V LINE TRANSFORMERS
- ★ TOROIDAL TRANSFORMERS
- ★ LIGHTING TRANSFORMERS

Write, phone or fax for data and prices

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254. Fax: (0227) 365104

LEDs 3mm or 5mm red or green 6p each, yellow 11p each. High intensity red, green or yellow, 5mm 30p each	Resistor Jumbo pack 25000, 1/4 and 1/2W resistors our choice of values and size, will be mainly in boxes or rolls of 1000, 2000 and 5000 of one type. £25.00
Cable ties 1p each. £6.95 per 1000. £49.50 per 10,000.	Qwerty keyboard, 58 key good quality switches, new. £5.00
Stepping motor 4 phase 12V 7.5 step 50 ohms. £9.95	Qwerty keyboard with serial output, no data (used). £6.00
SAW1027 stepping motor driver chip. £3.95	Polyester capacitors, box type, 22 5mm lead pitch
FM Transmitter kit, good quality sound. £8.60	1uf 250V dc 20p each, 15p 100+ , 10p 1000+
High quality photo resist copper clad epoxy glass boards	2.2uf 250V dc 30p each, 20p 100+ , 15p 1000+
Dimensions single sided double sided	3.3uf 100V dc 30p each, 20p 100+ , 15p 1000+
3/4 inches £0.96 £1.07	1uf 50V bipolar electrolytic axial leads, 15p each, 7.5p 1000+
4/8 inches £2.40 £2.68	0.22uf 250V polyester axial leads, 15p each, 100+ 7.5p each
6x12 inches £5.37	Philips 123 series solid aluminum axial leads, 33uf 10V & 2.2uf 40V 40p each, 25p 100+
12x12 inches £10.66	Multilayer AVX ceramic capacitors, all 5mm pitch, 100V 100pf, 150pf, 220pf, 10,000pf (10n)
Rechargeable Batteries	10p each, 5p 100+ , 3.5p 1000+
AA (HP7) 500mAh. £0.99	Welwyn W23 9W 120 ohm 35p each, 20p 100+ 680 ohm 2W metal film resistor, 4p 100+ , 2p 1000+
AA 700mAh. £1.95	Solid carbon resistors, very low inductance, ideal for RF circuits, 27 ohm 2W 680hm 2W 25p each, 15p each 100+ , we have a range of 0.25W, 0.5w, 1w and 2w solid carbon resistors - please send SAE for list
C 2AH with solder tags. £3.60	Intelligent 4 digit alphanumeric (5x7 dot 0.145") red LED display, 12 pin 0.6 inch wide package
D 4AH with solder tags. £4.95	Siemens type DL1414 £2.50 each, £2.00 30+ data sheets £1.00
1/2AA with solder tags. £1.55	AMD 27256-3 Eproms £2.00 each, £1.25 100+ DIP switch 3PCD 12 pin (ERG SOC: 3-023) 60p each, 40p 100+
AAA (HP16) 180mAh. £1.75	Disk Drive Boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm £7.95 or £49.50 for 10
AA 500mAh with solder tags. £2.20	Hand Held Ultrasonic remote control £3.95
D (HP21) 1.2AH. £2.60	Computer grade 5800uf 60v capacitors with screw terminals £4.95
PP3 8.4V 110mAh. £4.95	CV 2486 gas relay 30mm x 10mm dia with 3 wire terminals will also work as a neon light 20p each, £7.50 per 100
Sub C with solder tags. £2.50	A23 12v car alarm remote control and lighter battery 75p each, £50.00 100+
1/3 AA with tags (Philips CTV). £1.95	4uf 370vac motor start capacitor (dielectric type containing no PCBs) £5.95 each £49.50 for 10.
Standard charger, charges 4 AA cells in 5 hours or 4Cs or Dsrn 12, 14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time). £6.95	
High power charger, as above but charges the Cs and Ds in 5 hours: AAA, Cs and Ds must be charged in 2s or 4s. £10.95	
Special offers - please check for availability	
F cells 32da x 87mm. £3.95	
F cell with solder tags, 1.2V. £4.30	
42mm x 16mm dia, 1.2V. £1.45	
Stick of 4 171mm x 16mm dia, with red & black leads 4.8V. £5.95	
4 cell battery 94mm x 25mm dia (1/2C cells). £3.50	
Computer grade capacitors with screw terminals, 3800uf 20V £2.50; 8700uf 10V £1.95; 68000uf 15V £2.95; 10000uf 16V £1.50	
7 segment common anode led display, 12mm. £0.45	
LM2931AT 5.0 low drop out 5V regulator 10220 package. £0.85	
7812 and 7912 12V 1A regulators £20.00 per 100	
LM337k 103 case variable regulator. £1.60	
100+ £1.10	
B6250 P channel mosfet 45p, BC559 transistor per 100 £3.96	
74LS05 hex inverter. £10.00 per 100	
Used 8748 Microcontroller. £3.60	
SL862 UHF limiting amplifier LC 16 surface mounting package with data sheet. £1.95	
AM27802. £1.25 each, 80p 100+	
CD4007UB. 10p 100+ , 6p 1000+	
TV Mains switch, 4A double pole with momentary contacts for remote control, pack of 10 £3.96	
box of 60 £19.95	
DC-DC converter, Reliability model, V12P5, 12V in 5V 200mA out, 300V input to output, isolation with data, £4.95 each or pack of 10 £39.50	
Hour counter, used 7 digit 240V ac 50Hz. £1.45	
Resistor pack 2500 resistors 1/8-2W 50 different values. £8.95	

All products advertised are new and unused unless otherwise stated.
Wide range of CMOS TTL 74HC 74F Linear Transistors, kits, rechargeable batteries, capacitors, tools etc. always in stock
Please add 95p towards P&P VAT included in all prices

JPG ELECTRONICS
276 278 Chatsworth Road
Chesterfield S40 2BH
Access Visa Orders
(0246) 211202
Callers welcome

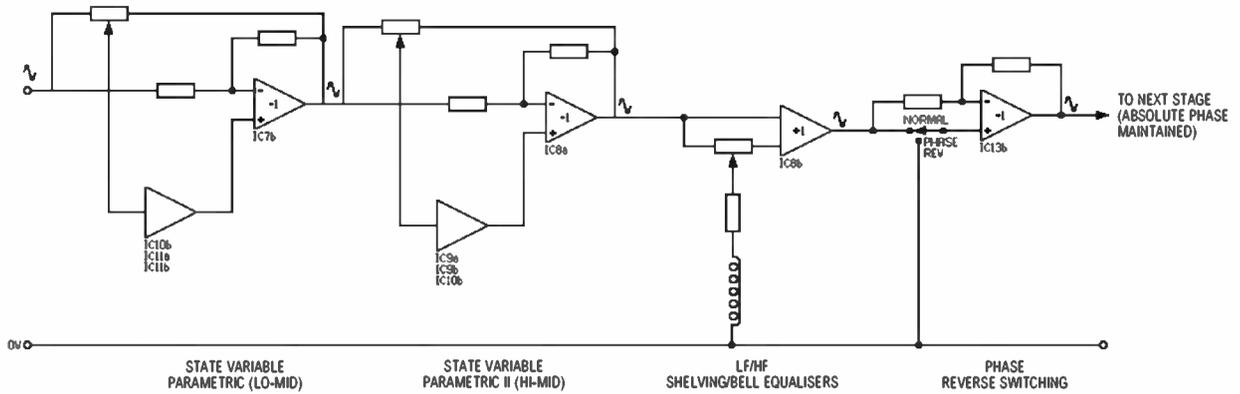


Fig.6 Block schematic of EQ phase manipulation through equalisation.

Automate Anniversary Mixer

PROJECT

This month, we weigh up the pros and cons of the different designs used in the Equaliser.

You've probably been wondering what happened to some of the diagrams mentioned in part 8. I think that the very mention in the opening paragraphs of Steven Spielberg brought every Gremlin in the vicinity out of the woodwork to bear upon last month's installment! Space restrictions meant that we had to undertake some open-heart surgery on that particular episode (so that it would fit into the magazine) and regrettably, the missing

diagrams were part of this surgery. The gremlins (aside from those already mentioned) seem to have been on piece rate because the How It Works of the HF equaliser section was omitted. Quell barbe! All of the aforementioned means that any interested parties - there are still some of you left out there, I hope will have to constantly refer to last month's issue. (You have still got last month's ET1 ...). I went on at some length in last month's issue about the importance of retaining absolute phase throughout the system and the text mentioned an absolute phase restorer pre-EQ. The original design was implemented as described but combining both

parametric sections in one Baxandall summing stage did give some headaches especially when both stages were set to similar frequencies.

With a bit of lateral thinking (and some nifty redesign work), the summing section for the low-mid parametric was transferred as per the circuit diagram to the op-amp IC9b previously-described as the 'absolute phase restorer'. In this way, the inverting action of this stage was used 'constructively' as it were to separate the two parametric sections and so prevent interaction (though the EQ overall still retained the necessary in-phase response).

HPF BREAK FREQ. (Hz)	R(freq.) (R56,R57)	Rpreferred	LF BREAK FREQ. (Hz)	R91 (calculated)	R91,R106 (preferred)
20	22.1k	22k,100R	30	780k	750k,30k
30	16.1k	16K,100R	35	670k	620k,50k
40	12.05k	12k,56R	40	585k	560k,24k
50	9.64k	9k1,560R	45	520k	510k,10k
60	8.0k	7k5,560R	50	470k	470k,11k
80	6.03k	6k,27R	55	425k	390k,33k
100	4.82k	4k7,120R	60	390k	390k,link
120	4.02k	3k,10R	65	360k	360k,link
140	3.44k	3k,430R	70	330k	330k,11k
160	3.01k	3k,10R	75	310k	300k,10k
180	2.68k	2k4,270R	80	290k	270k,22k
200	2.41k	2k4,10R	85	270k	270k,11k
220	2.19k	2k2	90	260k	240k,22k
240	2.1	2k0	95	245k	240k,5k1

Fig.7 (Table 2) Discrete resistor values for active filter sections (LF).

Volunteering an Op-Amp for the Job

Okay, so much for the error round-up. This month, we'll be looking at some of the problems which had to be surmounted during the design of the EQ.

The choice of op-amp was a difficult one. With so much written in previous issues about the subjects of both op-amps and equalization, all should have some idea of the attributes necessary of such a device in this application. Key requirements are, of course, high gain/bandwidth product, fast slew rate, low noise and a reasonable current sourcing output stage. Absolute noise internally generated by the semiconductor is a lesser consideration because the noise floor has been determined by the choice of circuitry in earlier stages, but the final choice of op-amp shouldn't worsen unduly the noise performance of the equalization stages.

At first, the TLO series of FET op-amps looked attractive in many ways. This would have seemed to have been particularly true of the TL074 type this four op-amps in a single package IC would have allowed one whole stage of EQ within a single IC. Noise performance is reasonable for such an application because, as previously shown, the noise floor has already been determined by the previous input stage. FET architecture means that bias currents are usually very low and so DC offsets are minimized.

This is important because an obvious requirement is for the EQ to be switched in or out of circuit for purposes of comparison etc and any DC present as we switch between the 'wet' and 'dry' signal paths will impinge itself upon the audio as a click. Output stage current sourcing capability - necessary for the integrators - is also reasonable with this family of chip.

The only down-point is that the device has a rather disappointing gain/bandwidth product - 3MHz - which is somewhat limiting to good high level, high frequency performance, a major pre-requisite for any high quality EQ. I have therefore used dual op-amp packages which make for a less tidy layout than the quad package but can yield better flexibility.

This is the case because the specification calls ostensibly for the fitting of the NE5532 dual bipolar op-amp in the key areas of the EQ. The TL072 is used as a summer where performance is less critical and DC offset reduction is of greater importance. Using dual package op-amps - as opposed to the quad type of the TL074 means that we can interchange between the two types, fitting all of one family - bipolar - or all of the other - FET - if so desired or the application demands greater performance in one aspect. To the best of the author's knowledge, there are as yet no good quality quad bi-polar op-amp packages available at reasonable cost although I stand to be corrected on that one.

In simple terms, this means the user fitting FET op-amps where click elimination is of paramount importance and fitting bipolar types where the requisite is for good performance

up to and beyond HF. Good performance is a relative term and it should not be thought that overall performance in any aspect is compromised by the fitting of a particular type - with both types, it is excellent in all aspects and the difference is basically a paper one- ie visible on a spec. sheet but not audible.

Options, Options, Options!

Various options have also been included for your delectation. Whether or not they are to be included on your version depends upon the importance-versus-cost-considerations that you place upon such items. Without wishing to sound like an out-of-work advertising copywriter or a frustrated estate agent, these include a switchable high pass filter with fixed or sweepable centre frequency, an LF equalizer with switchable bell or shelving characteristics and variable turn-over frequency and an HF equalizer also with variable turnover frequency and bell or shelving response, all available with

easy-payment plans! I saw no good reason for *not* including them and to configure them out of circuit, whether permanently or until such times as money permits their inclusion, is but a trivial operation with a soldering iron and a few wire links or resistors. Both of these sections (LF and HF) are extremely flexible and as such, extremely useful, too. They are both sufficiently innovative to be called 'original' which is no mean feat in an audio environment plagued by copies and modifications of existing, proven designs. This is not to say that I have not done the same thing myself but an 'own-design', especially in the world of mixing desks, helps to avoid any impending accusations of AUDIO piracy in the courts! As far as the question of whether any or all of the options should be fitted, cost is not the only consideration here. A basic


two band shelving and two band full parametric, able to be switched in and out as required, needs a minimum of eight knobs and one switch. Making the LF frequency variable, with switchable bell or shelving responses, and the HF control with variable slope adds another two rotary controls and a switch to our already-swollen ensemble of controls. (It would have been nice to have had the HPF In/Out switch back-stop operated as an integral part of the frequency pot but dual-gang pots with switches proved impossible to find).

Space - The Final Frontier?

Fitting all of the different controls physically onto the panel without ending up with a channel strip which requires the arms of a gorilla to operate the furthestmost control - is a conspicuously difficult task. Commercial designers can specify to the pot suppliers that they need x amount of dual concentric triple-gang 50k anti-log pots with integral push-on/push-off


FREQ.	CALCULATED C	PARALLEL C(preferred)
2k	36n	33n,3n3
2k5	29n	27n,2n2
3k	24n1	22n,2n2
3k5	20n67	18n,2n7
4k	18n1	18n,100p
4k5	16n1	15n,1n2
5k	14n5	12n,2n7
5k5	13n1	12n,1n2
6k	12n1	12n,100p
6k5	11n1	10n,1n2
7k	10n3	10n,330p
7k5	9n6	8n2,1n5
8k	9n0	8n2,820p
8k5	8n5	8n2,330p
9k	8n	6n8,1n2
9k5	7n6	7n5,100p
10k	7n2	6n8,390p
12k	6n0	5n6,390p
14k	5n2	4n7,470p
16k	4n5	3n9,560p
18k	4n0	3n9,100p
20k	3n6	3n6

Fig.8 Table of values for HF equaliser.

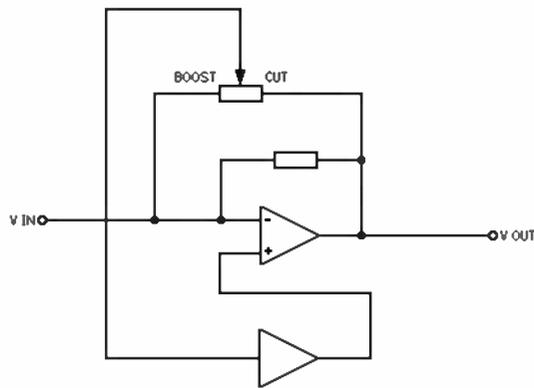

STATE - VARIABLE
BANDPASS FILTER
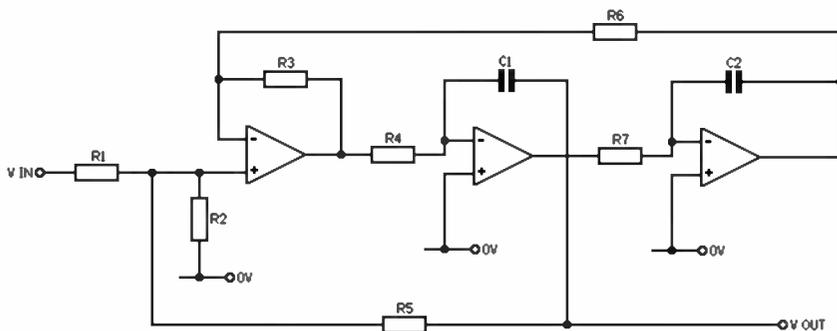
$$\frac{V_{OUT}}{V_{IN}} = \frac{-G}{2}$$



$$A \text{ VF CENTRE} = \frac{R5 (R1+R2)}{R1 (1+R2)}$$

$$\text{VF CENTRE} = \frac{1}{2\pi} \sqrt{\frac{1}{R4 C1 R7 C2}}$$

Fig.9 Parametric EQ sections on schematic form.

PROJECT

switch and an auxiliary switch - you know the type, they prevail on car radio cassette players. These are able to be moved simultaneously in about four different axes of movement, and can control volume, balance, fader, on/off and space and time functions all from one rotary shaft! In this way, two controls can be piggy-backed one on top of the other (normally Q and centre frequency in the case of equalisers), with a corresponding saving in valuable physical panel space. The plebeian DIY designer, on the other hand, doesn't, have this avenue of escape open to him/her and so must struggle with what he/she's got, fitting all separate pots and discrete switches in as tight a squeeze as possible. Anyway, that was MY problem!

The inclusion of TWO insert points (nothing to do with an acupuncturist's map) - both pre and post EQ - might be intriguing to some of our slightly more au-fait readers perhaps used to seeing just one insert point - the pre-EQ one in the channel strip.

The whole subject of dynamics will be covered at a later date. As far as we are presently concerned, however, it relates to the channel as a completely entity in that we have to

decide where in the audio pathway we may wish to externally process the signal. Again, from a commercial point of view, wishing and having are two completely viewpoints. Next month, we'll show diagrams of the points in the signal pathway where we may wish to access audio and conversely the points where normally we actually CAN in many commercial products. The money which was saved by not including any internal dynamics control has been put to good use - for a cost of about £0.80 per channel, it has been used to provide another insert point at a post EQ stage. This is a definite rarity but it is a most useful facility to have. For this to be so, we only have to cast our minds back a few months to what I said about over-zealous use of the EQ and the fact that this very quickly robs the whole channel of headroom. Being able to access the channel Post EQ means that equalization produced transients can be controlled with an external gain control of good pedigree. In this way, the gain of the whole channel can, in effect, be controlled. For the sake of a couple of drive amps - a luxury, really - and a jack socket, I cannot see why it is not included on more desks hovering around the mid price range. The pre-EQ insert point is the more usual one to have. To think of it more as a POST FRONT-END or POST INPUT STAGE gives a better clue to the kind of use to which it's normally put. A dynamics processor, for example, can be inserted here and used to control signals which are periodically unruly and may cause the channel to clip at a later stage - the channel gain control has been set for the average signal level (so that signal-to-noise ratio is good) but it can't cope with transient extremes. Any close mic'd drum kit or other percussive section is bound to output signals which are strongly transient in nature and a bass guitar, especially if it has been Direct Injected has a very wide dynamic range. Sibilance or

plosive from vocalists' microphones can also cause annoying momentary overloads and these, too, can be controlled.

Gain control can also be used for creative (rather than corrective) measures, enabling a voice which is perhaps lacking in certain registers to maintain a reasonably constant loudness level out of the recorder or it may be used to 'tighten up' up a bass guitar or bass drum. Bass guitar is a good example to quote, as it transpires. Although many (or most) bass guitarists will want their sound directly injected, some engineers prefer to mike the guitar, too. Direct injection bass will be clear and pure but will lack forcefulness (known in the trade, somewhat vulgarly, as 'balls') while miked bass is usually too boomy and lacks clarity. It is therefore necessary to input the dynamic range of the bass guitar on two channels.

Other FX processors such as noise gates or expanders may be used. As the insert point is almost invariably post High Pass Filter -as in the Automate - any high level LF such as rumble or air conditioning burble can be effectively removed before it can cause spurious triggering of the processor.

HOW IT WORKS LF AND HF EQUALISER


It is useful to have a bell type equaliser at the low end of the spectrum since it means that boost to bass frequencies, can be given without increasing lower frequency intrusions or disturbances such as air-conditioning burble, mic handling noise or platter rumble. I have included also graphs of the boost/cut responses with an ideal control law as well as those from the 10k pots used. (Figs. 11d,13b). It can be seen that the control has slightly more effect at the extremes of rotation. This is caused by the loading effect of the (relatively) low value pot -which has been used to minimise Johnson noise as much as possible but in practice, the effect is barely noticeable. Larger value pots -10ksay-would minimise this to a certain extent, at the expense of slightly worse noise performance. If the individual wishes to fit this larger value, it will mean wading through a horrendous amount of maths to re-jig identical responses. C'est la vie!

The HF equaliser is another unusual and rather unconventional type. It uses a circuit arrangement which in shelving mode, is, in essence, the reciprocal of the LF control although such a function cannot be yielded simply by transposing the positions of the resistors and capacitors. It incorporates an unusual modification to the shaping of the curve through the addition of the capacitor to the network which can be switched IN or Out as required using SW9 (which will normally be part of RV12 when this is fitted). The turnover frequency can be changed by varying the effective capacitance to ground using a variable bootstrapping technique centered around IC13a. This arrangement, by virtue of the way that current magnitudes are altered around the loop, changes the effective value of the capacitor from 3n3 at the most clockwise setting (max frequency) of RV12 to 33n at its minimum setting. The break frequencies can be determined as follows:

$$f_{\text{corner low}} = \frac{1}{2\pi(R107+R108)C88_{\text{effective}}}$$

$$f_{\text{corner high}} = \frac{1}{2\pi(RV9+RV107+R108)C88_{\text{effective}}}$$

The value of C88 has been chosen to give a noticeable change in subjective character of the sound without excessive colouration. It allows the generation of more steeply rising 'boost' curves than is usual with this type of control since it sharpens the corner of the curve. While it cannot be described as a true 'bell' type response, nonetheless, it has the potential to produce greater subjective brightness enhancement than a conventional shelving equaliser.

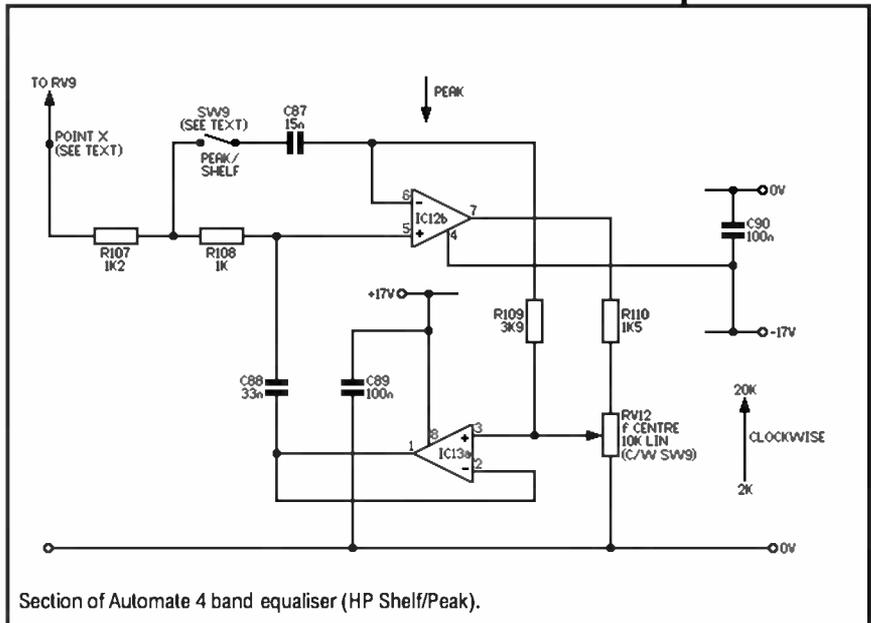

Section of Automate 4 band equaliser (HP Shelf/Peak).

Phew! The response curves shown in Figure 11 show far more elegantly what all of this means.

There is available the option to fit an inductor into the network in the arrangement shown in Figure 14a. This does achieve the desired bell response at the expense of using an inductor (with some of its associated problems). In some ways, this is a better arrangement than the previous switched capacitor type. Switching the capacitor into circuit achieves the bell resonant type response, again with C88 arranged effectively as a variable capacitance to ground. The diagram in Figure 14a shows just what all this means while Figure 11a gives the response curves. It is left to the individual's discretion as to which of the two is the more preferable as regards desired response. Should the frequency determining pot RV12, be omitted from the finished board, the break frequency is determined using C88 tied to ground directly (avoiding the use of IC13a), with a value chosen from the table in Figure 8. A typical arrangement is shown in Figure 14b. Each of these two equalisers are then arranged as variable admittances to ground in the so-called swinging input style cut and boost arrangement of IC8b. C77 and R94 minimise clicks on the output as SW6 is operated. Again LED 5, 6 and associated components provide an optional indication of EQ IN and PHASE REVERSE respectively.

PROJECT

PARTS LIST

HIGH PASS FILTER/PHASE REVERSING SWITCHING

Resistors (all 1/4W unless otherwise stated)


R53,67	1M
R54,55	2k (or see Table 1)
R56,65,66	10k
R57	6k2
R58	1k
R59,60,63	22R
R61,66	1k
R62,64	100k
R111	1k5 (optional - see text)
R112	47k (optional - see text)
RV2 (optional)	20k dual miniature PC mounting (with switch)

CAPACITORS

C46,55,57	4u7 non polarised
C47,54,56,58	100n polyester
C48,49	330n polyester
C50,51	100n disc ceramic
C52	47p polystyrene
C53	100u 40V miniature radial non polarised
C59	22p polystyrene
C91	4u7 25V radial electrolytic (optional)

SEMICONDUCTORS


IC7	NE5532
Q3,5	BC559C
Q5,9	BC549 (Q9 optional - see text)
D1,2,3,7	1N4148

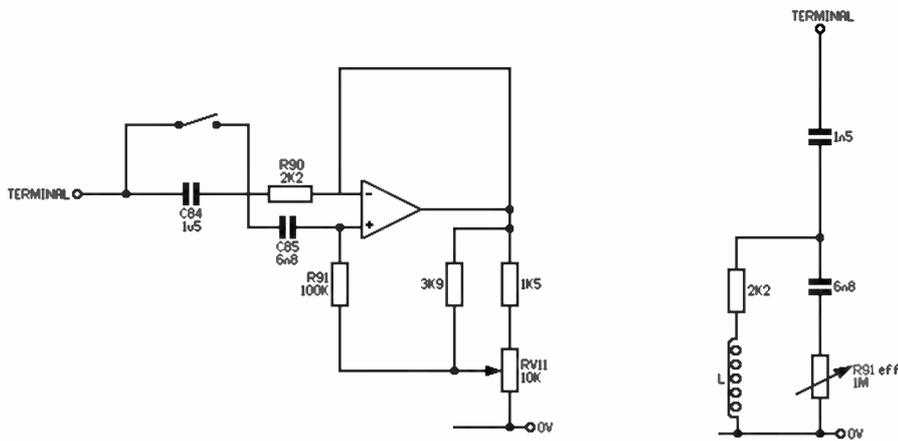

LF SHELF/BELL EQUALISER SHOWN WITH SHELF RESPONSE SELECTED, RV2 FREQUENCY CONTROL SET FOR MAX (30hz)

RESONANT
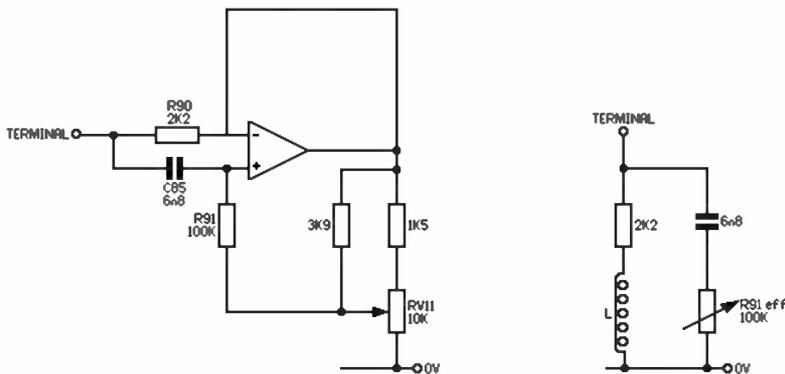
$$f \text{ CENTRE} = \frac{1}{2\pi} \sqrt{\frac{1}{C84 C85 R90 R91 \text{ eff}^2}}$$



LF SHELF/BELL EQUALISER SHOWN WITH SHELF RESPONSE SELECTED, RV2 FREQUENCY CONTROL SET FOR MAX (100hz)

SHELVING

$$f \text{ CENTRE} = \frac{1}{2\pi C85 R91 \text{ eff}}$$

OR

$$X_L = 2\pi fL \text{ WHERE } X_L = 2k2 \text{ AND } L = C85 R90 R91 \text{ eff}$$

$$f \text{ CENTRE} = \frac{X_L}{2\pi L}$$

Fig. 10 LF equaliser in schematic form.

R73,79	15k
R74,75,80,81	750R
R84,85	750R
R82,83,86,87	2k
R90	2k2
R91,102,105	100k
R92,109	3k9
R93,110,113,115	1k5 (R113,115 optional - see text)
R94	1M
R98,108	1k
R99,100,103	22R
R101,104	4k7
R106	(see Table 2)
R107	1k2 (see text)
R114,116	47k (optional - see text)
R117,118	(see Table 3)
RV3,4,9,10	PC mounting miniature 10k LIN
RV5,7	PC mounting miniature 20k LOG
RV6,8	PC mounting miniature 10k dual LIN
RV11 (optional)	PC mounting miniature 10k LIN c/w integral push DPDT switch
RV12 (optional)	PC mounting miniature 10k LIN c/w integral push switch

CAPACITORS

C60,83	100u 40V non polar radial electrolytic
C61,63,65,79,81	22p polystyrene
C62,64,66,68,71,73,76,78,82	100p disc ceramic
C67	820p polystyrene
C69	6n8 polystyrene
C70	10n polystyrene
C72	18n polystyrene
C74	47n polystyrene
C75	330n polyester
C77	1u polycarbonate
C80	10p polystyrene
C84	1u5 polycarbonate
C85	6n8 polystyrene
C87	15n polystyrene
C88	33n polystyrene
C92,93	4u7 (optional - see text)

SEMICONDUCTORS

IC8	TL072
IC9,13	NE5532
Q6,8	BC559C
Q7,10,11	BC549C (Q10,11 optional - see text)
LED2	0.1" green LED
LED5,6	0.1" red LED (both optional - see text)
D4,5,6	1N4148

PROJECT

LED1 0.1" Green LED
LED4 0.1" Red LED (optional - see text)

MISCELLANEOUS

SW5 PC mounting DPDT push switch (which may be combined with RV2)
JK2 PC mounting 1/4" stereo jack socket with switched contacts 8 pin DIL Sockets to suit, PCB, Veropins, M3 mounting hardware, knobs and buttons to suit

4 BAND EQUALISER

RESISTORS (all 1/4W 1% unless otherwise stated)

R68,69,88,89	10k
R95,96,97	47k
R70,76	33k
R71,72,77,78	12k

MISCELLANEOUS

L1 27mH inductor
SW6,7 PC mounting push on DPDT switch
SW8 PC mounting push on DPDT switch (or may be integral to RV11 if fitted)
SW9 PC mounting push on DPDT switch (or may be integral to RV12 if fitted)
JK2 PC mounting 1/4" stereo jack socket with switched contacts
8-pin IC sockets to suit, Veropins, PCB, Control knobs, switch caps to suit, M3 mounting hardware

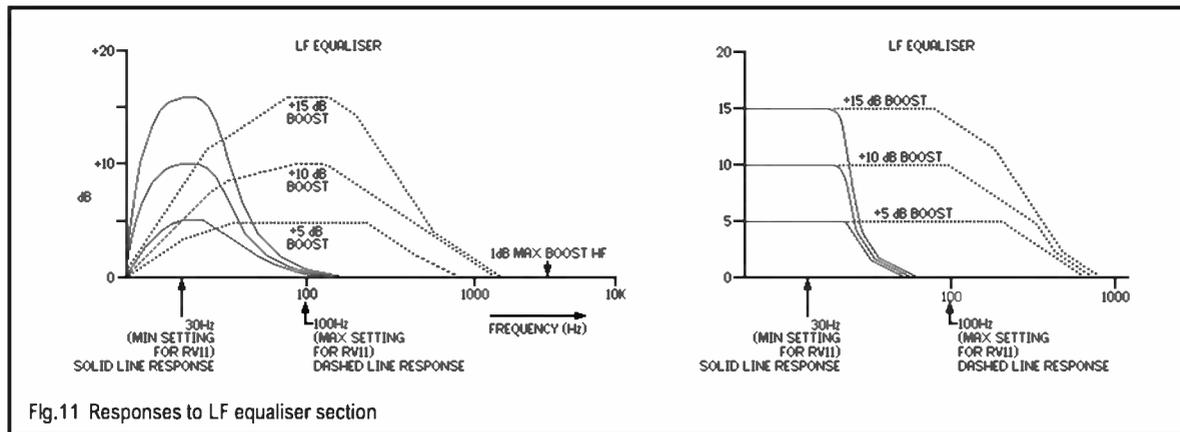


Fig.11 Responses to LF equaliser section

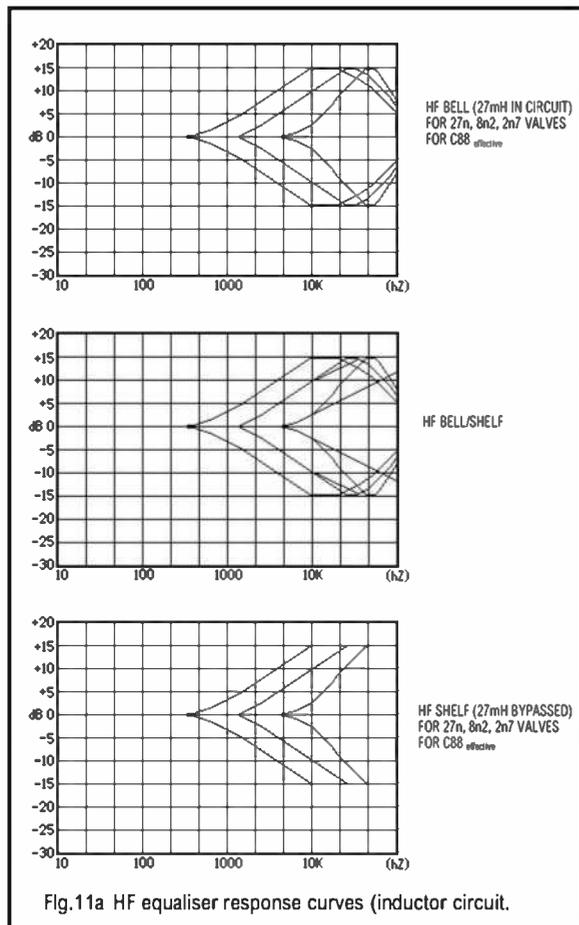


Fig.11a HF equaliser response curves (inductor circuit.)

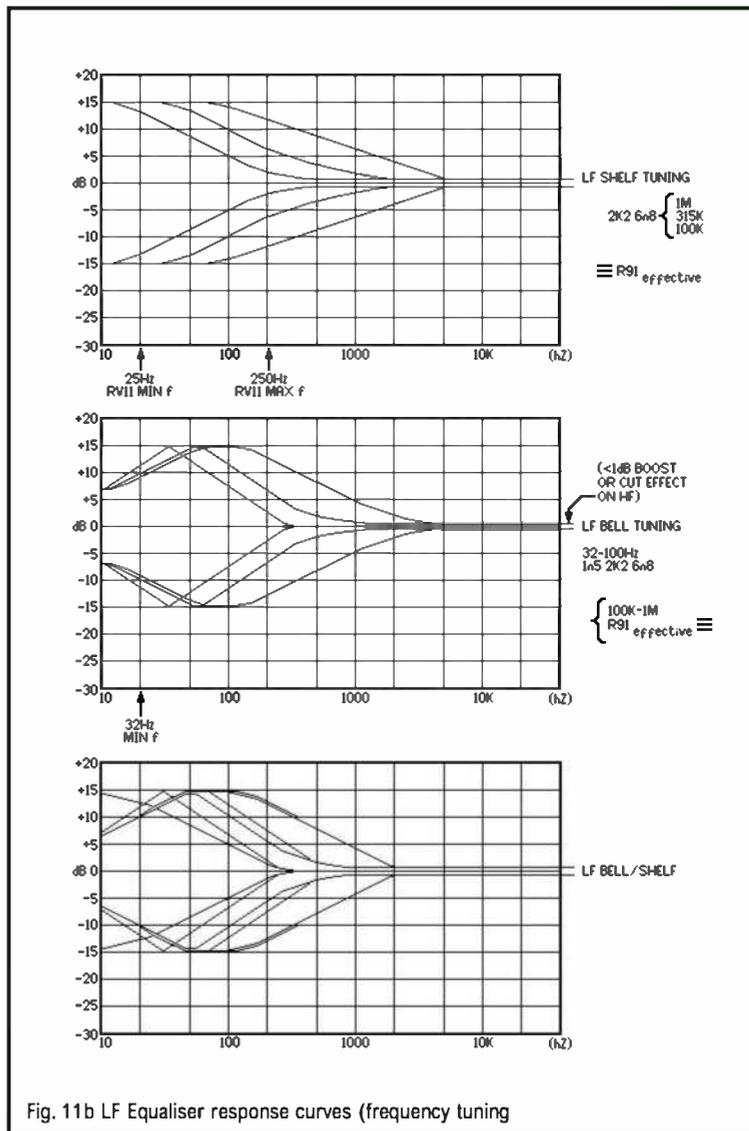


Fig. 11b LF Equaliser response curves (frequency tuning)

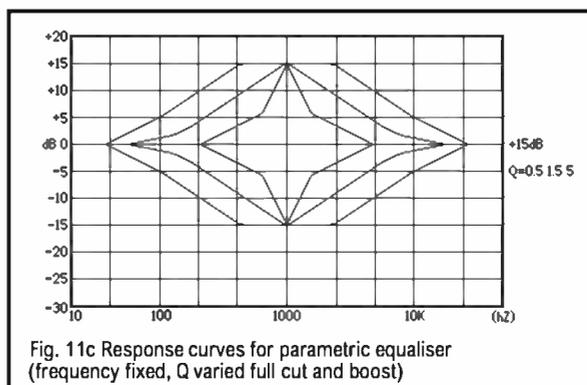


Fig. 11c Response curves for parametric equaliser (frequency fixed, Q varied full cut and boost)

References



Sound Recording Practice (edited by John Borwick), Microphones John Borwick. Mixing Consoles, Analogue (Richard Sweetenham)

Sound Processing (Richard Elen) - Digital Recorders (Tony Faulkner) - Classical Music (Adrian Revill) - Popular Music (Mike Ross) - Radio Broadcasting (Dave Fisher) Oxford University Press


Audio Electronics Handbook (edited by Ian R Sinclair) - Sound Recording Techniques (Don Aldous), Sound Waves (Dr W Tempest) -BSP Professional Books

The New Audio Cyclopedia (edited by Glen M. Ballou) - Consoles and Systems (Steve Dove), Details of the Session (Chips Davies with Linda Jacobson) - Howard W Sams

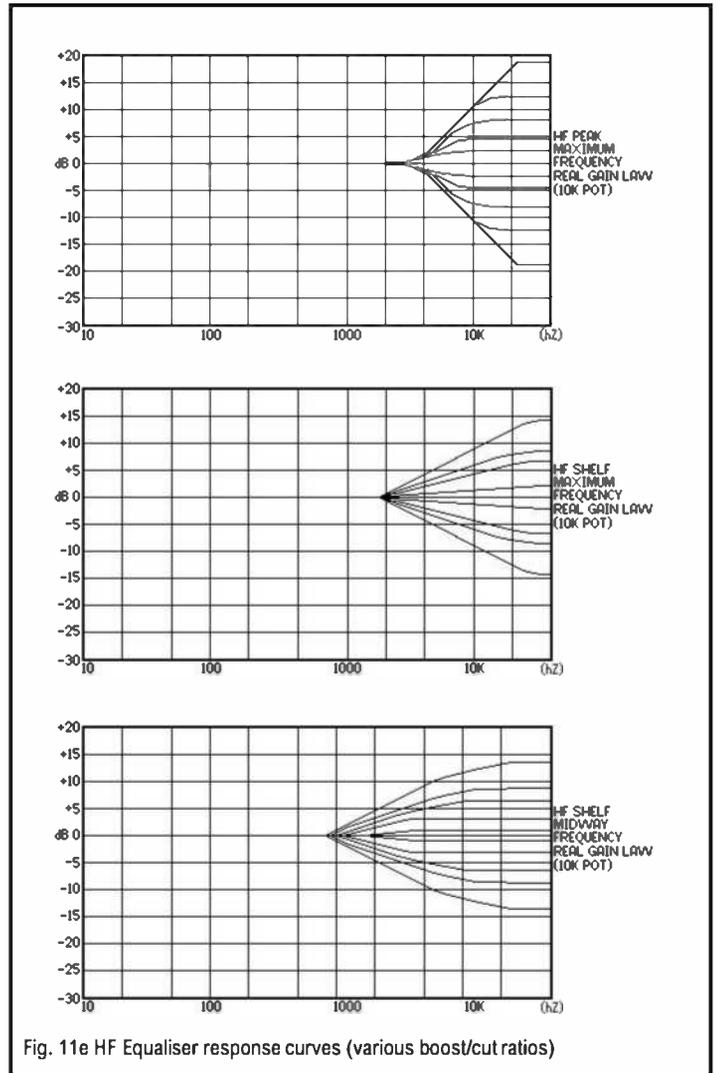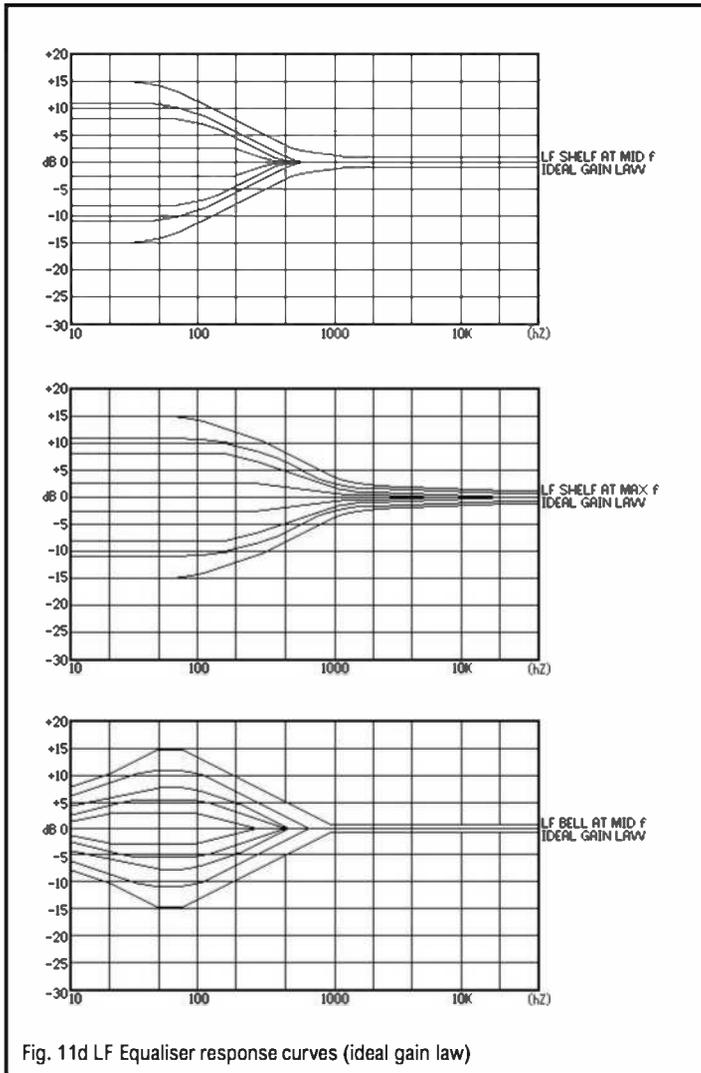Active Filter Cookbook - First and Second Order Net-works. Bandpass Filter Design, Bandpass Filter Circuits (Don Lancaster) - Howard W Sams.



PROJECT

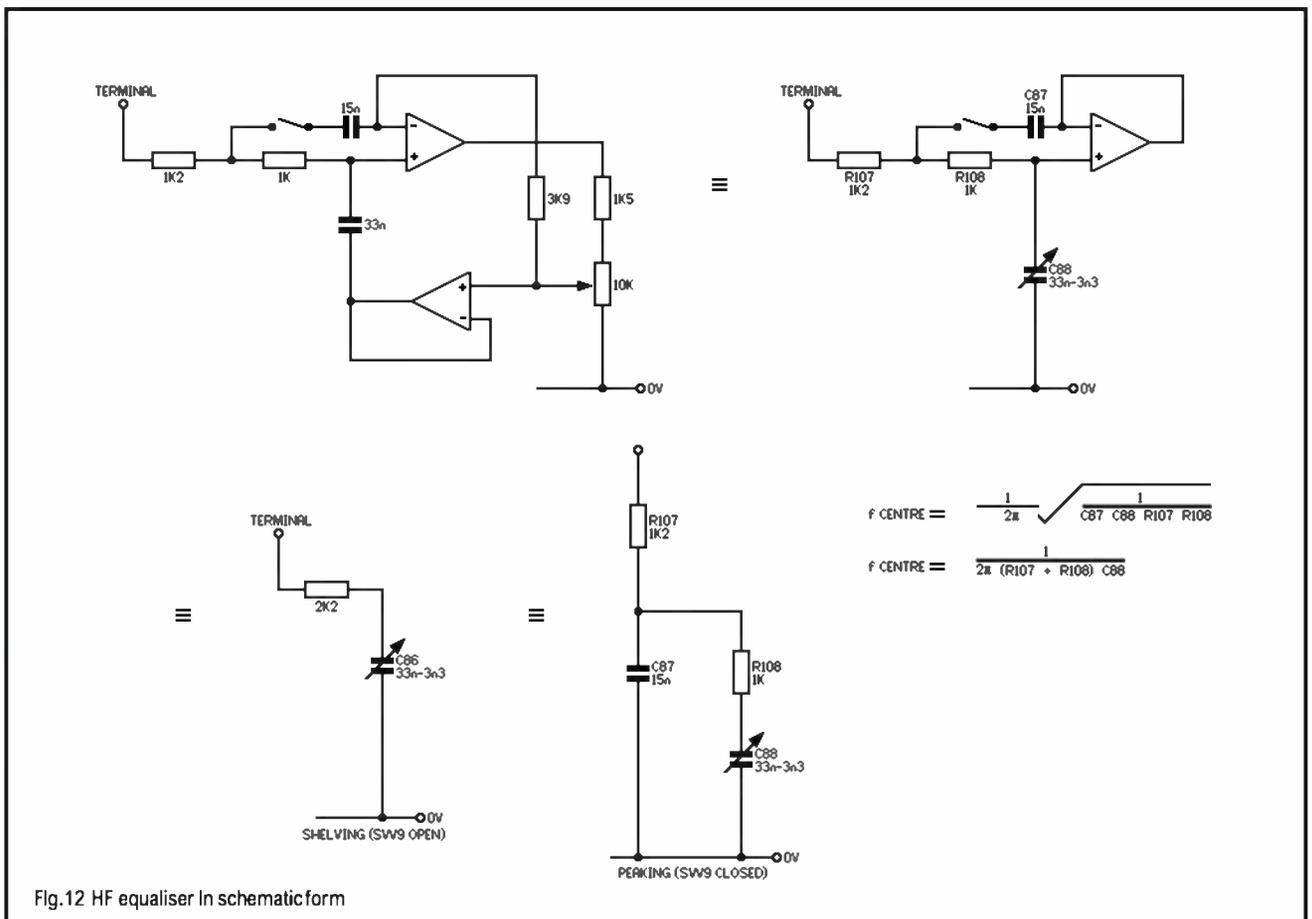

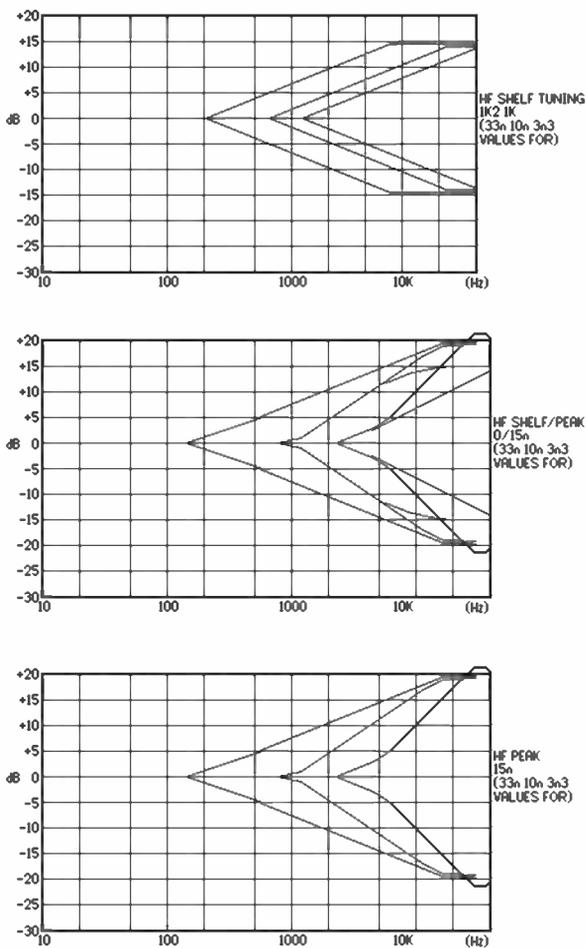


Fig 13a HF Equaliser response curves (Frequency tuning)

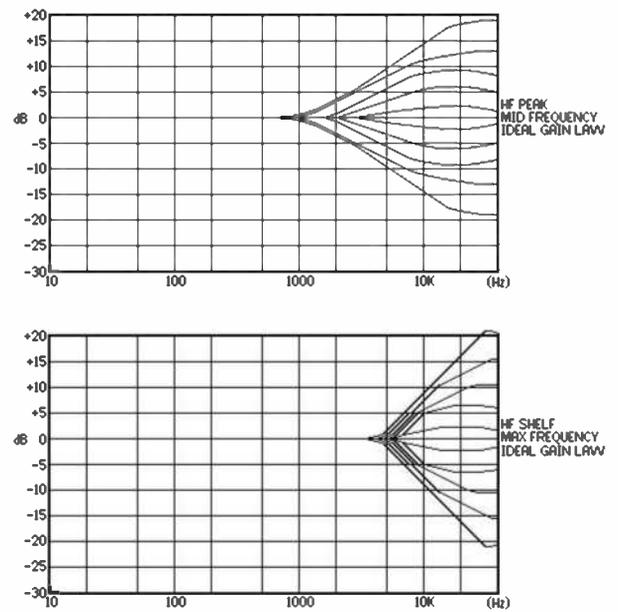



Fig. 13b HF Equaliser response curves (various cut and boost ratios)

Errata

Last month, figure 1 should have included diode D7 in series with D1, D2.

Figure 2 amendments include: replace R78 with R96-47k, C87-100n with C91-100n and C87-100µ with C82-100u. '*fitted only if RV11 omitted' refers to R106 not R91. HF SHELF/BELL EQUALISER should read LF SHELF/BELL EQUALISER.

PROJECT

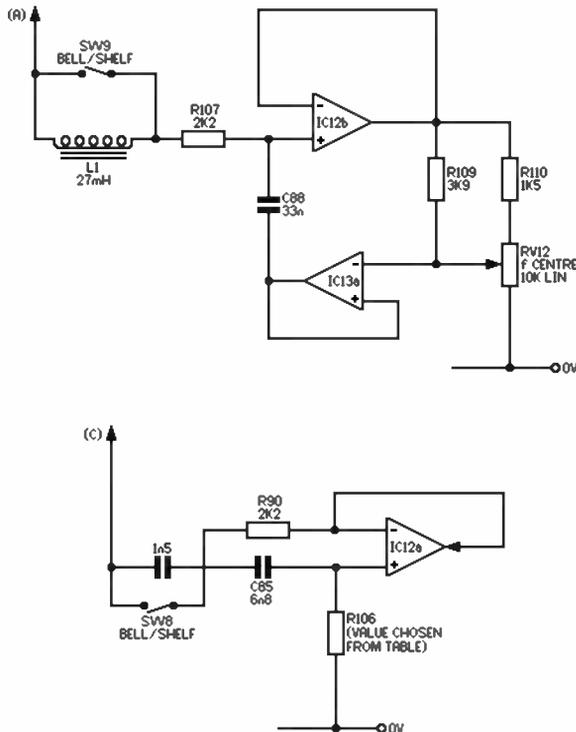


(a) HF EQUALISER WITH C87 OMITTED, R108 ALSO REPLACED BY SINGLE 2K2 RESISTOR AND 27MHZ INDUCTOR TO ACHIEVE TRUE BELL TYPE RESPONSE.

(b) HF EQUALISER WITH VARIABLE FREQUENCY CONTROL, RV12, (AND IC13a, R109, R110) OMITTED AND REPLACED BY 'FIXED' CAPACITOR TO GROUND JOIN AT POINT X.

(c) LF EQUALISER WITH VARIABLE FREQUENCY CONTROL, RV11 (AND R91 - R93) OMITTED AND REPLACED BY FIXED RESISTOR R106.

Fig. 14 Possible modifications to the standard equaliser

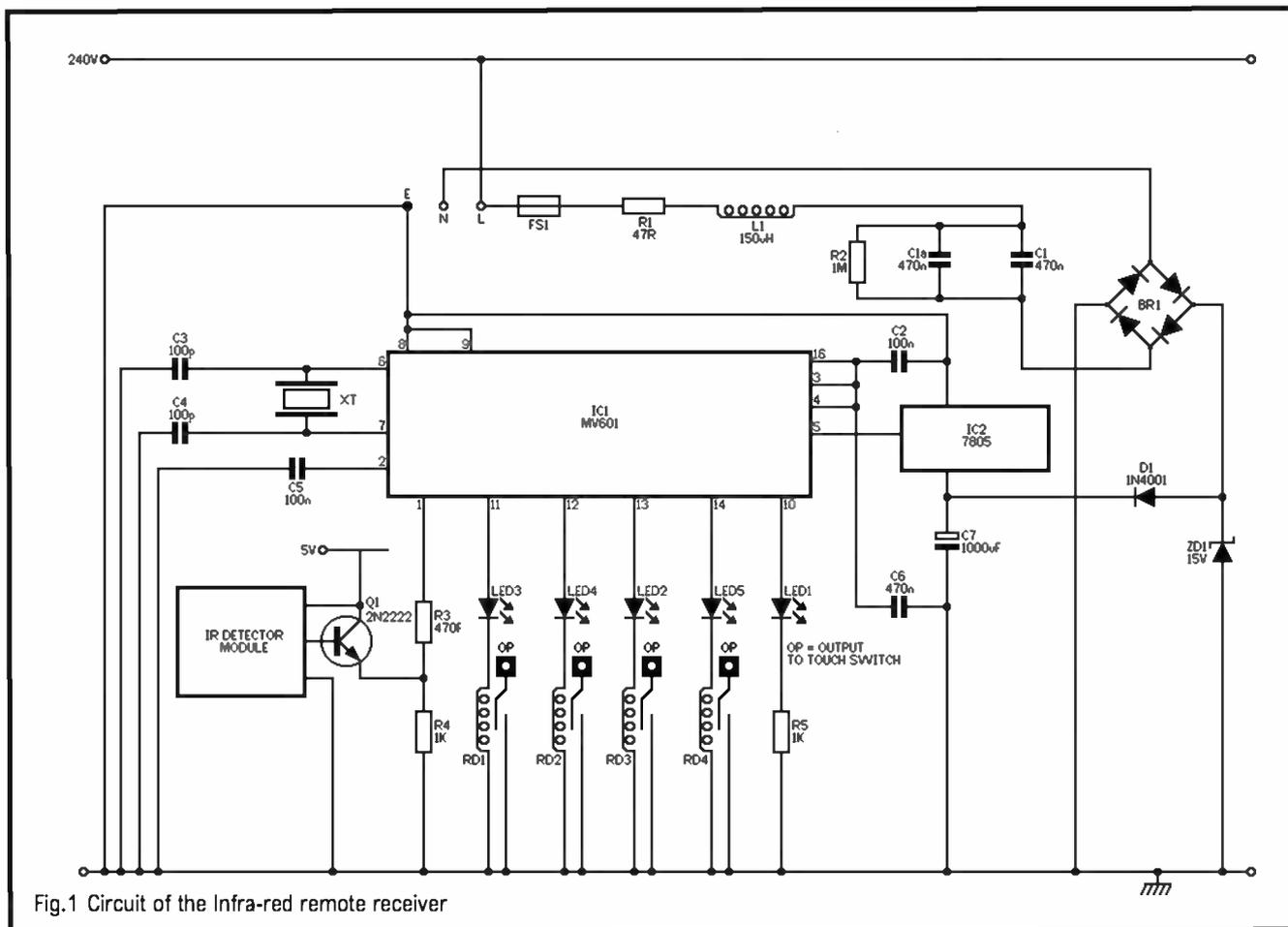

Predictably in the future, domestic remote controlled lighting and dimming will be as common as the television remote control and with the availability of multi programmable transmitters on the market, eventually all domestic systems will be programmed into one master transmitter.


With mains lighting, the design criterion requires that the lighting system must not depend entirely on remote control.

Manual switching is the most convenient simple method of switching, the remote operation is the added practical refinement of modern living, and probably only used during relaxation times or as an aid to the unfortunate handicapped or bed-ridden patients. The greatest advantage is the means of controlling the dimming level of lighting from a position of relaxation.


In the case of the following Infra-Red remote design any

Four Channel Remote

PROJECT

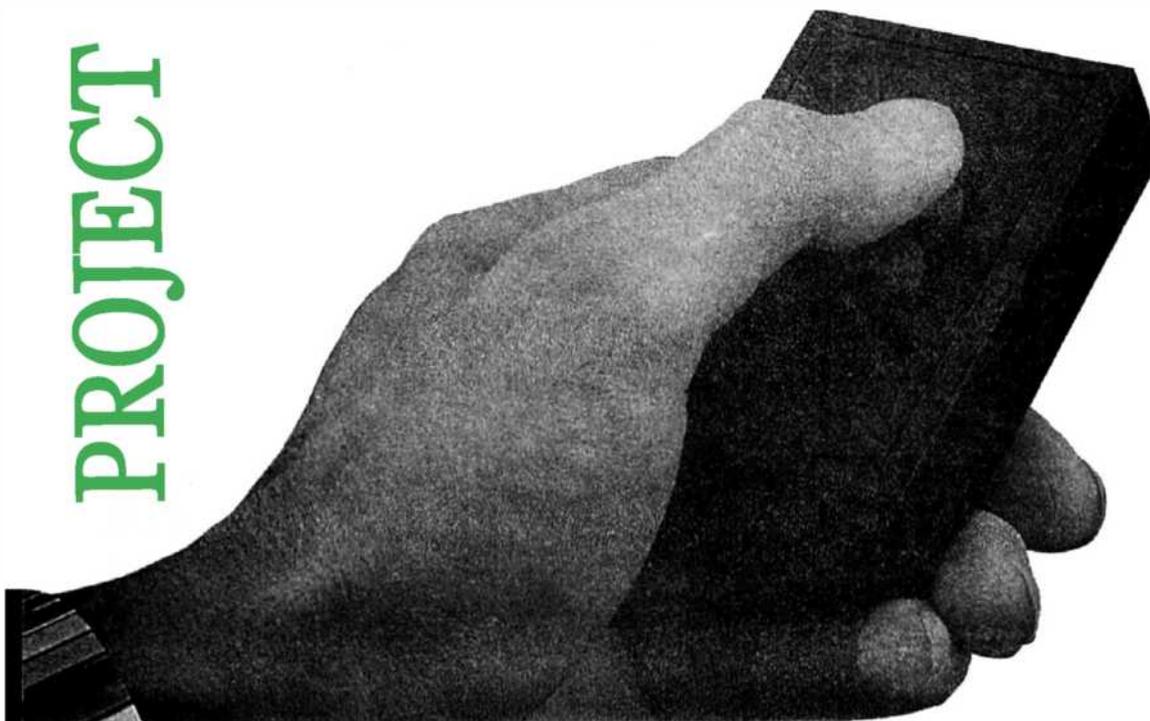

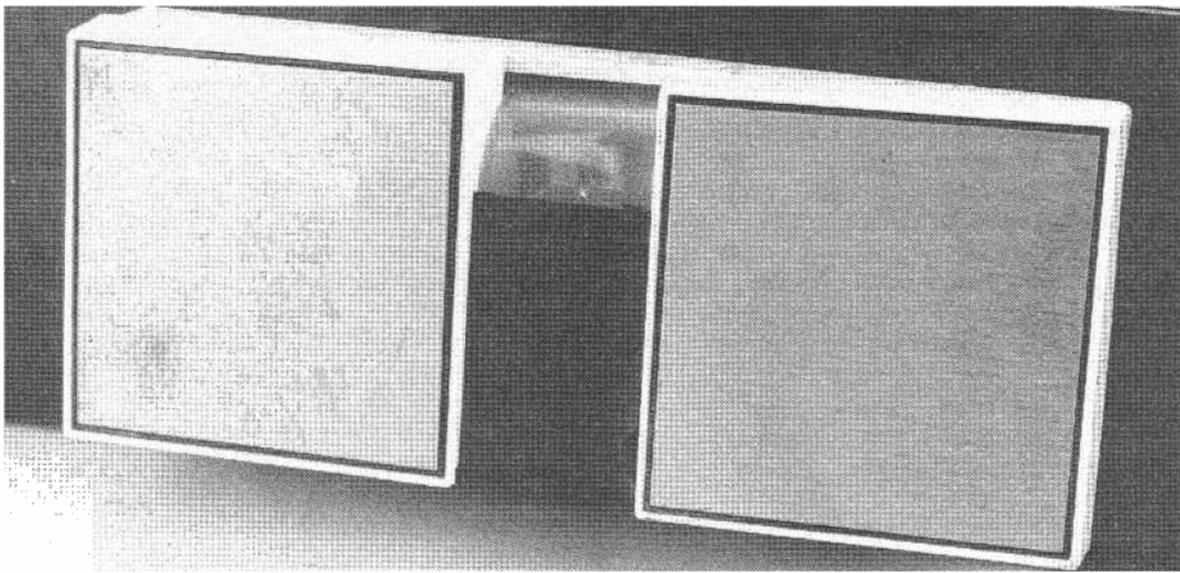An effective way to control and dim four sets of lights independently. A description by Ken Blackwell.



HOW IT WORKS IR RECEIVER

Mains power is connected to the terminal block 240V AC and is fed through to the bridge rectifier via a 47R wire-wound resistor and a choke. The choke removes most of the AC noise, then to the capacitors which charge and discharge a limited current. The bridge rectifier changes the AC sine wave to DC. The zener diode reduces the voltage to a manageable 15V. The current passes through the 1N4001 rectifier diode to continue to smooth and remove AC pulses. Finally, voltage is smoothed by the 1000u capacitor. As the components in this circuit are rated at 5 volts, a voltage regulator 78L05 feed is connected to the positive line at the 1000u capacitor junction.

The receiver is designed to match the PPM output signals generated from the IR transmitter by receiving the word notations on ABCD only. The Tandy receiver/demodulator unit receives the IR signals generated by the transmitter, any unwanted noise or signals are filtered leaving a clean square wave pulse. This pulse is amplified by Q1 to eventually pass a signal to IC1 pin 1.

The configuration of the MV601 chip is set to give stable momentary outputs to the four relay positions.

The stability is derived from the 500kh ceramic resonator.

Each LED will illuminate as a signal is received. As the reed relay operating resistance is very high, the outputs from IC1 will directly drive each relay without any current amplification. A protection diode is integrally built into the relays.

As each relay operates, earth potential is connected to the touch plate (being hard wired to the touch plate on a dimmer switch), giving the effect of manually touching the switch plate.

This receiver has been designed to minimise the passive components used by installing 'off-the-shelf' units such as the Tandy receiver/demodulator. This unit obtains the same results as a complex IR preamp integrated circuit with its array of passive components.

SIL connectors are used for the relays giving a plug in connection and allowing a combination of various positions in which to place up to four relays thus allowing more than one receiver circuit in any one room.

Control Dimmer

combination, MANUAL 'OR' REMOTE switching and dimming can be operated from each separate touch dimmer switch.

From customers various comments and the practical operation of remote lighting, I have used a guide line to bring to attention the main practical points desired by the customer, to form a suitable remote domestic lighting control, whilst not interfering with any manual switching. They are:

- a) Cost effectiveness
- b) Must be manual and remote. Not either one or the other.
- c) Easy to operate multi-coded transmitter.
- d) Dimming and switching function.
- e) Compact.

The remote system is coupled to control a suitable easily available touch dimmer switch, manufactured by Home Automation. These units are very attractive cost effective units, obtainable in either silver or gold coloured brushed anodized aluminium touch plates, rated at maximum 200 watts each unit.

You could also experiment with other makes as most of them work on the same principle.

Basic Operation.

By parallel earthing the dimmer switch touch plate via a normally open reed relay switch will exactly duplicate the touch switch operation, mechanically. From a relay pulse or tap, the lighting turns 'On'. A further pulse or tap switches 'Off'. Relay held in, or finger held on switch, controls the lighting level. Release at desired light level. It must be emphasized that by pulsing manually just one Infra Red transmitter button, (one channel) control over all these various dimmer switch functions via the receiver reed relay, a full control can be obtained. Further dimmer switch connections can be added to each decoded relay output, to make a total of four coded relay positions on each receiver, giving 800 watts of controlled lighting.

Operation

The transmitter, the construction of which appears next month, together with cover PCB, operates four channels and basically of standard construction, with a couple of selected components to give increased range. Push switch connections are made to operate only digital ABCD logic outputs, thus allowing only one of the four relays to operate at each desired selection.

The receiver is mains powered and converted to give a DC supply output via a zener voltage of 15 volts at 35mA, then again regulated to supply various components with a smooth 5 volt supply. Detection of infra red pulses are amplified and filtered by the Tandy IR Detector unit, a hybrid receiver/demodulator. These output signals are transistor amplified and passed to the remote control receiver IC pin 1. With matching pulse position modulation, the momentary switch selected ABCD logic couples directly to one of four

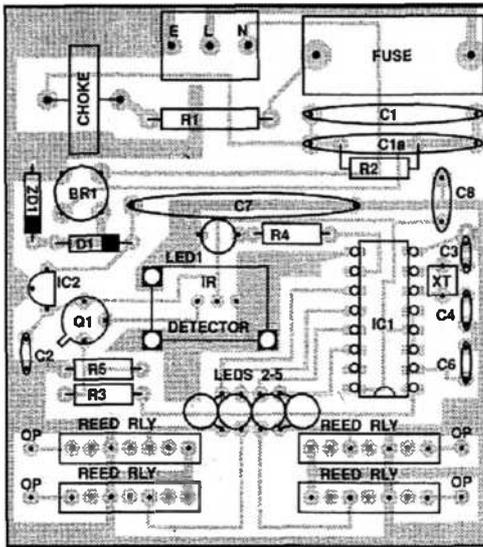


Fig.3 Component Overlay of receiver.

miniature 5V DC plugin reed relays. The normally open relay contacts, close, making an earth connection to the appropriate dimmer switch touch plate, completing the dimming/switching cycle.

Receiver Construction

NO SETTING UP REQUIRED

WARNING. MAINS POWER ON CIRCUIT USE CAUTION DURING OPERATION. Assembly is straight forward and if each component is double checked during assembly for correct polarity no problems will be encountered.

Start from initial mains 240 volt power input connector and solder the components in the operating sequence finally fitting the reed relays. Not only will these procedures safe-guard damaging components, but it will enable testing voltages from mains down to the final 5 volts DC before any semiconductors are fitted. Solder the components in order, working from the mains connector-fuse-47ohm resistor -choke -two 470n/250v capacitors -1M resistors -Bridge rectifier (imperative that must be positioned top right hand side). Zener diode -diode -finally 1000u electrolytic capacitor, observing polarity. This completes the high voltage conversion. Connect mains power to connecting block ensuring correct polarity.

Before proceeding ensure that the voltage across the electrolytic capacitor is no more than 15V DC. Solder in the 5 volt regulator. Before proceeding, check for the existence of 5 volts between earth and LH pin. Solder the remaining components into circuit board. Plug in IC1. Plug in Reed relays to desired SIL outputs. If correctly assembled LED 1 will illuminate. On a signal from the transmitter (to be featured next month with accompanying cover PCB) one of the four LEDs will illuminate via a relay, whilst LED 1 turns OFF. OP (Relay Outputs) via earth, are hard wired connections to the dimmer switch touch plates. Sub miniature single strand wire is suitable.

Worth-while Tips.

LEDs are normally supplied with the live side leg the longer of the two. The tag on the transistors is the emitter facing towards ground potential. Tantalum capacitor+ mark towards R6. IC1 pin 1 nearest XT. SIL Reed relay 5volts Live connection opposite "S" mark on side of relay. Increase range of receiver by installing a red plastic lens available from Maplin. Part number FA95D.

PARTS LIST RECEIVER

RESISTORS

R1	47R 2W
R2	1M
R3	470R
R4, 5	1K

CAPACITORS

C1, 1a	470n 250V AC
C2, 5	100n min disc ceramic
C3, 4	100p min disc ceramic
C6	470n min polyester
C7	1000u 16V electrolytic

SEMICONDUCTORS

IC1	MV601 Plessey IR receiver
IC2	78L05 5V regulator
Q1	2N2222
ZD1	15V zener 1.3W
BR1	W004
D1	1N4001
LED1-5	Red LED rectangular 5mmx2mm
IR1	Infra-red detector module Tandy GP1V52X

MISCELLANEOUS

FS1	1A fuse and holder
L1	Mains choke 150uH
XT1	500kHz ceramic resonator
RLA1-4	(4 pins used) SIL PCB miniature 5V SPNO relay
	3-pin mains connector block
	DIL socket 16-pin
	32 pin low profile socket

BUYLINES

Most of the parts are available from Rapid Electronics. The Infra-red receiver module is from Tandy Stores. The choke is from Maplin (JL72P). The MV601, resonator and MV500 are available from Electromail. A kit of parts (excluding box and battery) for £25 is available from ADVF Service, 131 Aldermans Drive, Peterborough, Cambs PE3 6BB



A seasonal project to provide some extra glitter on the Christmas tree by Richard Sagar.

Fading Festoonery

There are plenty of flashing LED circuits about that can be used for the star on the top of your Christmas tree. One problem with LED arrangements is that they can barely be seen during bright daylight hours, or when the tree is brightly illuminated by a nearby lamp. The circuit in Figure 1 is designed to give a pleasing flash, well more of a twinkle really, and can power mains lights and hence be bright enough for use at any time of the day.

Mains Control

To switch a high voltage (mains) bulb a Silicon Controlled Rectifier (SCR) is generally employed, here a triac, as these are capable of switching currents in amps or 10s of amps range and voltages of 100's or even 1000's of volts. Being silicon devices with no moving parts they are also faster to switch and more reliable than relay and other mechanical switches. The standard way of giving a dimmed effect using an SCR is to switch the bulb on and off at high speed, using the full supply voltage, and making the percentage of time spent on longer for a bright glow, or shorter for a dim glow. This technique is also used for speed control in motors as it gives better control at low speeds than would be

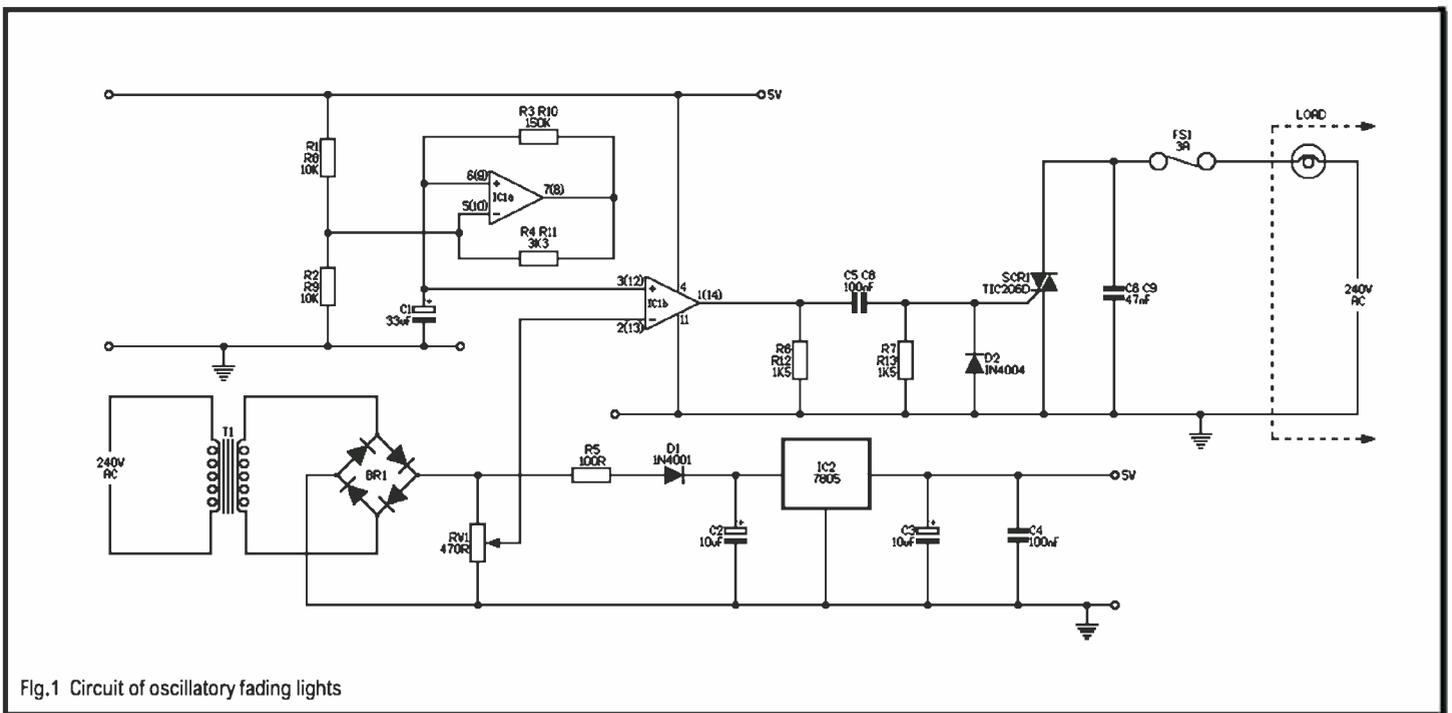
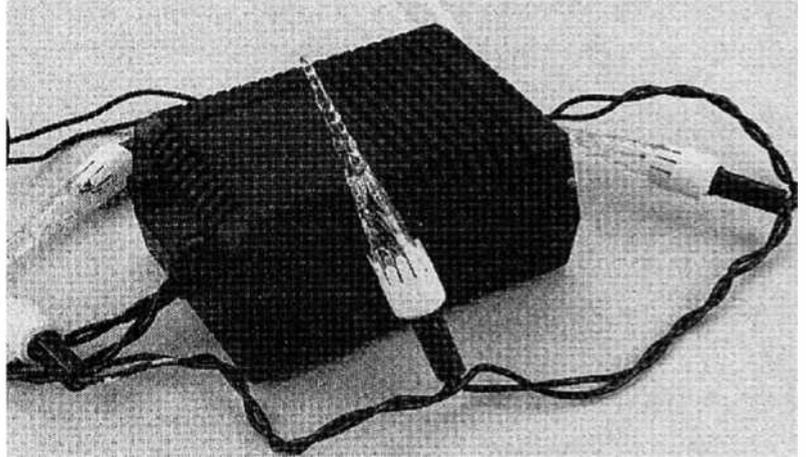


Fig.1 Circuit of oscillatory fading lights

How It Works

IC1b is used as an astable oscillator, the oscillations depend on the signal at pin 6 ramping up and down to cross the voltage at pin 5, causing the output to change state. This only works because R4 provides hysteresis to the circuit, giving the voltage on pin 5 a different value when the output (pin 7) is high, to its voltage when the output is low. Consider the case when the output is high; assuming the output is 5V (the positive supply), then R4 will effectively be in parallel with R1, making the voltage at pin 5 approximately 60% of the supply voltage.

When the output is low, R4 is in parallel with R2 and the voltage at pin 5 will now only be 20% of the supply voltage.

Figure 2 shows how the voltage on pin 6 changes in relation to the output voltage. Normally on flasher circuits it is the voltage at pin 7 that is used to flash the LED's, but in this case the voltage at pin 5 is used to give the aforementioned 'twinkle'. The sawtooth waveform cannot be used directly to drive the light bulb, as the current and voltage are far too low.

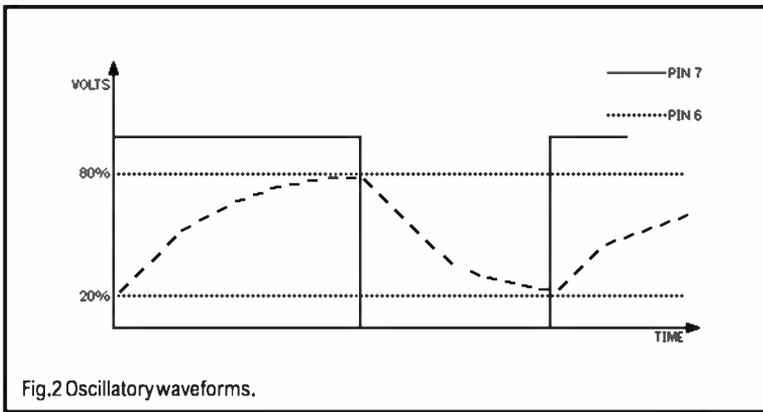


Fig.2 Oscillatory waveforms.

given by dropping voltage across a resistor, it is also more efficient as less energy is wasted through I^2R losses. One interesting point about the SCR is that once the device has been turned on (with a pulse on its GATE input of 1V-2V at 10mA) it will remain on when the gate input is disconnected, as long as the current through the main terminals continues to flow. In AC circuits such as this there is no real problem as the supply regularly turns itself off (100 times a second), however any circuit that used a DC supply would need some additional circuitry to switch off the load current and hence turn off the SCR. Figure 3 shows the voltages at the important points in the circuit. Figure 3a is the rectified output of the transformer, before smoothing. This signal is

it is known) which is exactly what we require to give the dimming effect. Note that the comparator output is fed through capacitor C5 before driving the GATE input of the triac. This is to allow the GATE current to fall quickly back to zero (Figure 3c) after the positive transition of the comparator, this prevents the triac being held on past the zero crossing of the load current, which would keep the triac switched-on continually again no good for a dimming circuit.

Power Supplies and Interference

The transformer should have an output of 9V to 12V. The bridge can either be a bridge rectifier in a pack or made-up of four diodes and need only be rated at 1 amp. Obviously care must be taken when connecting up the transformer primary and it may be advisable to find a sealed unit that provides the low voltage output and no access to the 240V primary. The 5V supply for the op-amp circuit needs to be stable, to generate a good sawtooth waveform, however the not smoothed transformer signal (Figure 3a) is required to generate the switching signal for the comparator (IC 1a). To allow both to be provided R5 and D1 are used to separate the bridge and the regulator portions of the supply circuit. It is worth noting that the voltage at the input to the regulator (IC2) needs to be 7V or over, so the current through R5 and hence the volts drop across it cannot be too high. Smoothing of the supplies is provided by both large electrolytic and

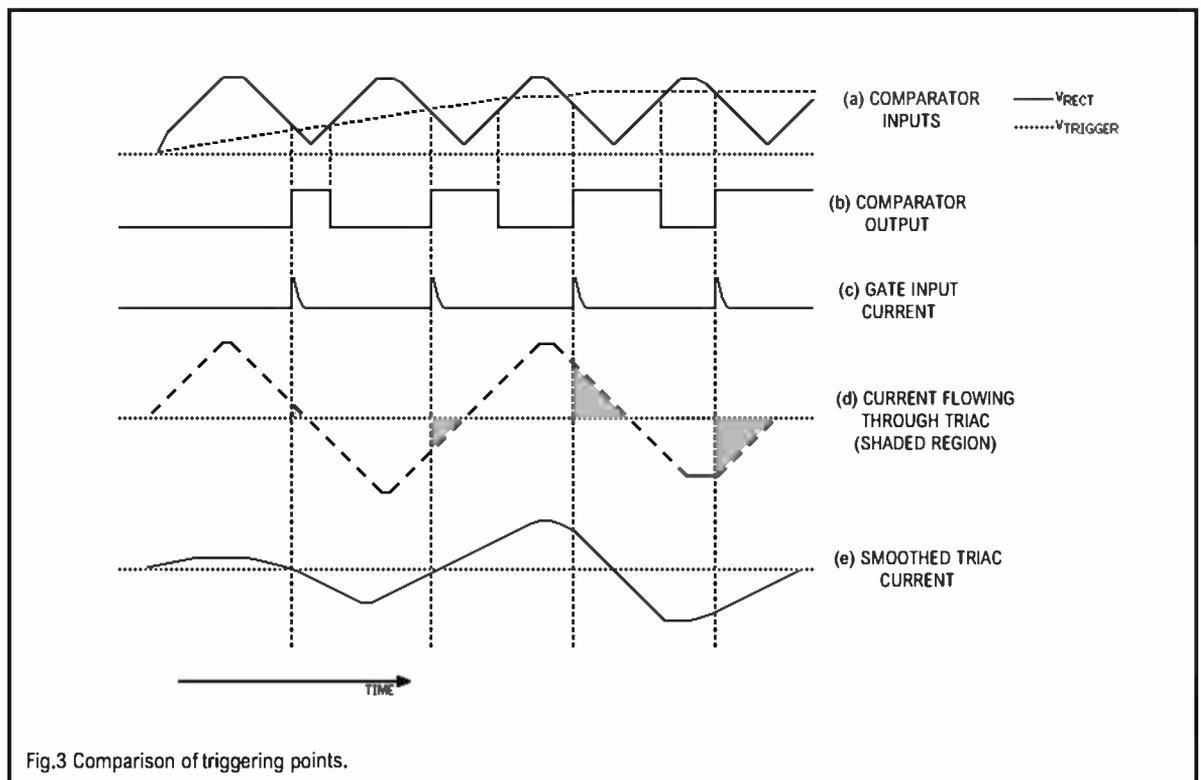


Fig.3 Comparison of triggering points.

used for determining when to apply pulses to the GATE input of the triac. A pulse needs to be provided at least once per mains cycle otherwise the triac will spend all its time switched off. By comparing the size of the voltage on pin 5 of IC1 ($V_{trigger}$) with the rectified transformer output (V_{rect}) the time at which the triac is switched on will change, earlier in the cycle for high values of $V_{trigger}$ and later for low values of $V_{trigger}$ (Figure 3b). This gives the effect of varying the ratio of the ON to OFF time of the triac (the MARK-SPACE ratio as

smaller value ceramic or polyester capacitors. The electrolytic capacitors provide smoothing of the mains ripple, whereas the smaller capacitors are used to remove high frequency noise that the fast switching of the triac can induce. The capacitors should be kept as close to the supply connections on IC1 as possible. In parallel with the triac is a further smoothing capacitor which smooths the current through the load (transforming Figure 3d into something more like Figure 3e, to reduce the sharp current spikes that cause radio frequency interference.

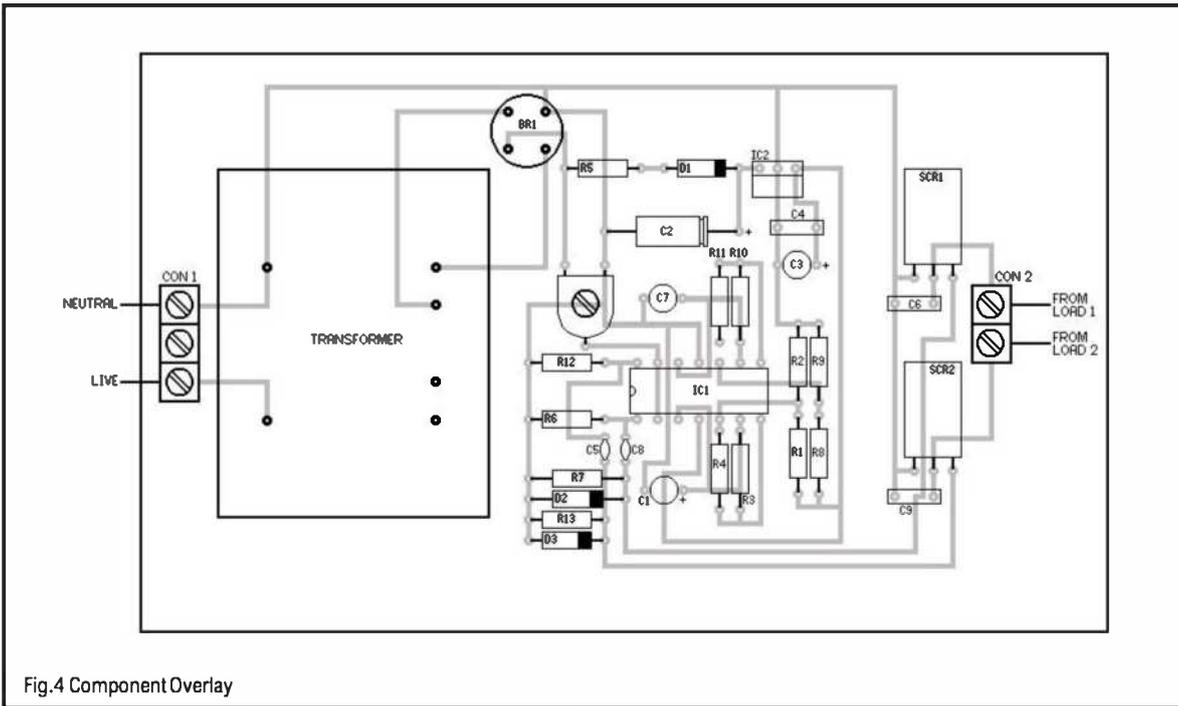


Fig.4 Component Overlay

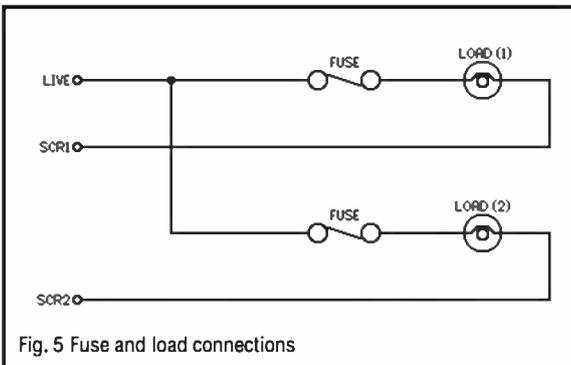


Fig. 5 Fuse and load connections

Practical Aspects

The best use for the circuit is in conjunction with a set of fairy lights, or to be more accurate two sets of fairy lights. The reason for specifying a quad op-amp was to allow two copies of the circuit in Figure 1 to be built up easily. Two slightly different values of the combination C1/R3 can be selected so the two 'twinkles' change at different speeds and give quite a soothing Christmas effect, even if I do say so myself.

Another important practical aspect of any mains control is to make sure the electronics is housed within a good insulating box or case. As this design is solely for Christmas lights, it would be wise to house power supply and control circuits in the one box, leaving just a 'mains in' lead and 'controlled mains' out lead.

The triacs used have a rating of five amps which is fine for Lighting circuits, however in the excitement of experimenting with the unit it is all too easy to run round the house connecting everything to it, and the simple mistake of connecting a hair drier to the unit could ruin your whole days work (or even your Christmas). It is therefore necessary to place a 3 Amp fuse in series with the triac, as shown in Figure 1, this will also protect the circuit from the usual mains faults.

Setting Of RV1

The variable resistor, RV1, controls the height of the signal (V_{rect}) feeding pin 2 of IC1a. Referring to Figure 3a $V_{trigger}$ should not be greater than the peak value of V_{rect} otherwise the comparator will not switch during that cycle, the triac will not be triggered and the lamp will remain off. Using an oscilloscope the two signals can easily be displayed one on top of the other and the pot adjusted to make V_{rect} big enough. If an oscilloscope is not available setting up is still possible using a voltmeter as follows: (1) measure the two voltage levels of pin 5 on IC 1, which should be approximately 20% and 80% of the supply voltage, as mentioned above; (2) Measure the voltage at pin 2 of IC1 (using the DC range of the voltmeter), this will be the average value of the waveform V_{rect} . For a rectified sinusoid the peak value is $(n/2)00V$ and hence the pot can be adjusted until the voltmeter reading is high enough to satisfy V_{rect} greater than $V_{trigger}$.

PARTS LIST

RESISTORS

R1,R2,R8,R9	10k
R3,R10	150k
R4,R11	3k3
R5	100R
R6,R7,R12,R13	1k5
RV1	470R

CAPACITORS

C1	33uF 16V
C2,C3	10uF 16V
C4,C5,C8	100nF
C6,C9	47nF 400V

SEMICONDUCTORS

IC1	LM324
IC2	7805
BR1	1A 50 PIV bridge
D1	1N4001
D2	1N4002
SCR1	TIC 206D

MISCELLANEOUS

T1	9-12V secondary, mains input transformer
FS1	Fuse 3A and fuse-holder

Basic Multimeter Circuits

Ray Marston takes a further look at analogue meter circuitry.

2

The last episode of this 'test gear' series outlined the main principles of the moving-coil meter and showed how it can be used to make AC and DC voltage and current measurements. This month's article continues the theme by showing how it can also be used in ohmmeter and multimeter applications, and concludes by introducing various other types of electro-mechanical 'moving-pointer' meter.

The Series-type Ohmmeter

There are several ways of using a moving-coil meter to read resistance values. The best known of these uses the basic 'series connected' ohmmeter circuit of Figure 18a, which is used in most commercial analogue multi-meters. This battery powered circuit has a variable shunt wired across the meter and has a range-setting resistor wired in series with the combination. In use, the X terminals are first shorted together, causing a current (I) of V/R_{range} to flow in the meter, and the variable shunt is then trimmed to bring the meter pointer to FSD; since zero ohms are connected across the X terminals under this condition, this is called the 'set zero' operation. The unknown resistor (Rx) is then connected in series with R1 by fitting it across the X terminals, and the new current reading (i) noted; the value of Rx can then be calculated from $R_x = R_{range} [(I/i) - 1]$

If Rx has the same value as R_{range} the "i" value will equal 1/2, and the meter will give a centre scale reading.

Circuits

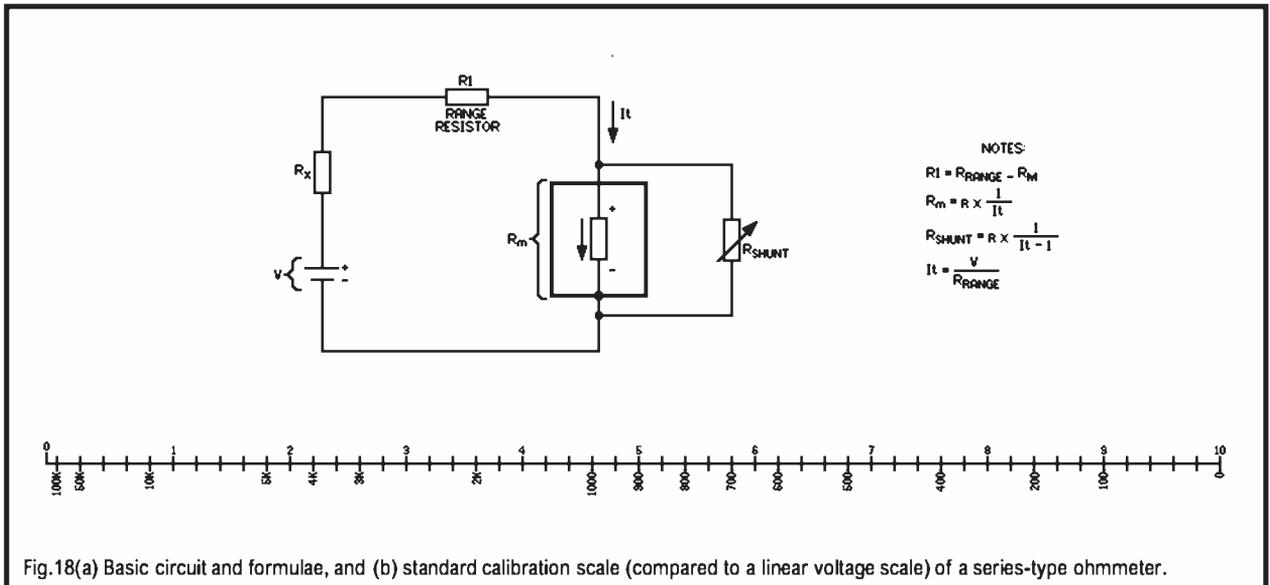


Fig.18(a) Basic circuit and formulae, and (b) standard calibration scale (compared to a linear voltage scale) of a series-type ohmmeter.

Consequently, when designing such meters, the R range value is used to set the instrument's center-scale value.

All meters of the Figure 18a type generate a scale shape of the exact form shown in Figure 18b, with a zero to the right with the 'range' value in the dead-center of the scale, and with X10 and X0.1 values at 9% and 91% of FSD respectively. Consequently, this scale can be applied to any series-type ohmmeter, provided that its values are all multiplied by an appropriate amount. For example, the old Avo-minor used a centre-scale value of 113 ohms, and the Avo 8 uses a centre-scale value of 2000 ohms, and many other meters use center-scale values of 285 ohms, but all use the precise scale shape shown in Figure 18b.

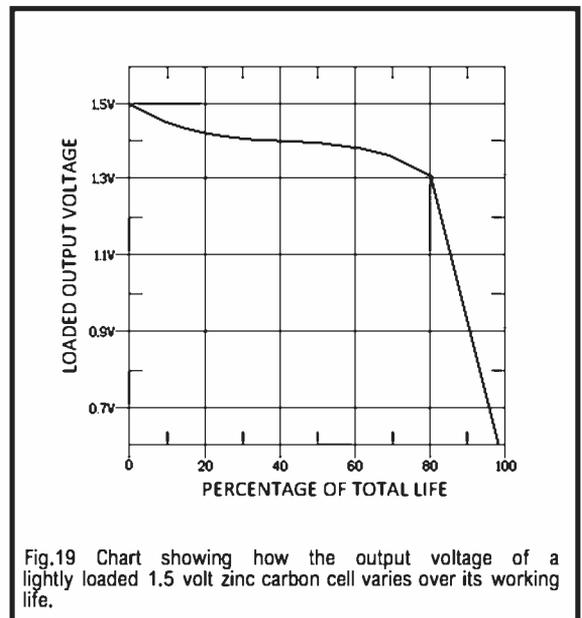


Fig.19 Chart showing how the output voltage of a lightly loaded 1.5 volt zinc carbon cell varies over its working life.

Superficially, the Figure 18a circuit looks easy to design, but in practice matters are complicated by the facts that the design must allow for large variations in battery voltage and R_{shunt} (and thus R_m) values, and by the fact that the circuit's mid-scale value is set by the combined values of the fixed R1 and the variable R_m. Figure 19 shows how the voltage of a 1.5V zinc carbon cell varies with usage; clearly, an ohmmeter designed for operation from such a cell should have its

component values optimized for operation at 1.4V, but should be capable of operating over the range 1.1V to 15V. To design a circuit of the Figure 18a type, the meter's basic sensitivity and 'r' value must first be known and the battery voltage and mid-scale 'range' resistance decided on; the circuit's component values can then be calculated. Figure 20 shows a practical 3-range series-type ohmmeter, designed around a 50µA, 3kΩ meter; on each range, SW1a selects the range resistor and battery, and SW1b selects the zero setting R_{shunt} resistors; note that the circuit uses a 10.5V supply on the 'x100' range, and that all shunts are wired in series across the meter. Figure 21 lists the full set of calculations made while

meter and reduces its current reading to 'i'. R_x can then be calculated from:

$$R_x = r \times (I/[I-i])$$

Thus, the meter reads half-scale when R_x = r. In practice, the effective r value can be varied by wiring a shunt across the meter, and the circuit can be used to measure very low values of resistance. Nowadays this circuit is obsolete, and it is presented here purely as a matter of technical interest.

Meter Overload Protection

Moving-coil meters are delicate instruments and can easily be damaged by large overload currents. If the meter is

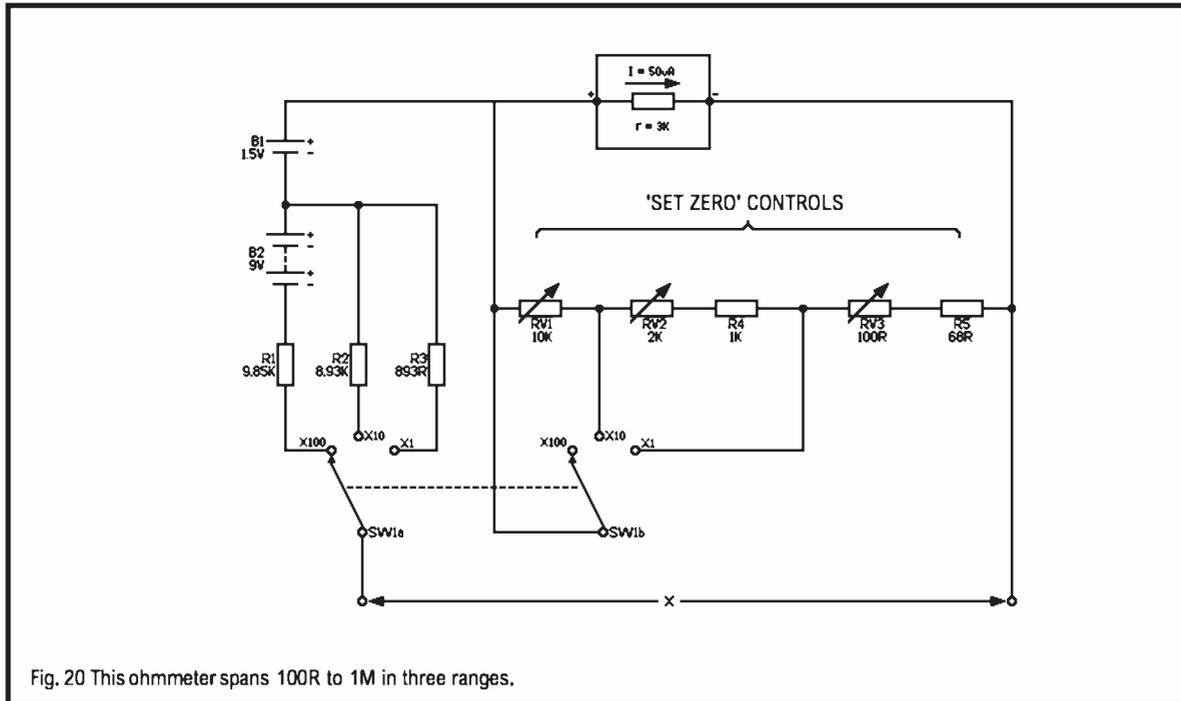


Fig. 20 This ohmmeter spans 100R to 1M in three ranges.

converting the basic circuit of Figure 18a into the practical design of Figure 20. Thus, on the 'x1' (1K) range, the design is first optimized for 1.4V operation (using the formula of Figure 18); at 1.4V the meter needs a FSD value of 1400µA, so R_{shunt} (= R5 + RV3) needs a value of 111.1 ohms, and R_m equals I 07.1 ohms: consequently, 'R1' (= R3 of Figure 20) needs a value 893 ohms. Once the R1 value has been settled, new sets of calculations must be made for 1.5V, 1.2V, and 1.1V operation. To enable the spread of R_{shunt} values and percentage mid-scale errors to be determined, as shown. Thus, R_{shunt} must be variable between at least 103 and 143 ohms. and the circuit's mid-scale reading is 0.7% low (at 993 ohms) at 1.5V and 2.9% high (at 1029 ohms) at 1.1V. Similar sets of calculations are made on the 'x10' and 'x100' ranges; the 'x100' range design is optimized for 10V operation.

The Parallel-type Ohmmeter

Another well-known ohmmeter is the parallel (shunt) type, which can be used to measure low values of resistance. Figure 22 shows the basic circuit; in use, SW1 is first closed and the meter calibrated by trimming RV1 to set the meter to read FSD with the X terminals open circuit; under this condition the meter current equals I, and the effective FSD 'resistance' value equals r. The unknown resistor (R_x) is then connected across the X terminals, so that it shunts the actual

used in conjunction with a swamp resistor, excellent overload protection can be gained by connecting a pair of silicon diodes as shown in Figure 23. Here, the swamp resistor is split into two parts (R1 and R2), with R2's value chosen so that 200mV is generated across the diodes at FSD; at overloads in excess of twice the FSD value the diodes start to conduct, and thus limit the meter's overload current; R1's value is chosen to limit the diode overload currents to no more than a few mA.

Multi-function Meters

A single moving-coil meter is often built into an item of test gear and used to act as a multi-function 'volts and current' meter. The designing of such meters is usually quite a simple matter, the basic principle being that all multiplier and shunt resistors are permanently wired into circuit, the meter simply being switched in series or parallel with the appropriate element. Thus, if a common measuring point can be found the switching can be made via a single-pole switch, as in the case of the Figure 24 circuit, which uses a single meter to monitor the output voltage and current of a regulated power supply unit. If a common measuring point can not be found, the switching must be done via a 2-pole multi-way switch, as in the case of the circuit of Figure 25, which can monitor several independent DC voltage and current values.

	BATTERY VOLTAGE	MID-SCALE RANGE VALUE	METER FSD CURRENT (uA)	Rshunt VALUE (Ohms)	Rm VALUE (Ohms)	NOMINAL R1 VALUE (Ohms)	MID SCALE ERROR
x1 (1K) RANGE	1.5V	1K	1500	103.5	100	900	-0.7%
	1.4V	1K	1400	111.1	107.1	893	0%
	1.2V	1K	1300	130.4	125	875	+1.8%
	1.1V	1K	1200	142.8	136.4	864	2.9%
x10 (10K) RANGE	1.5V	10K	150	1500	1000	9000	-0.7%
	1.4V	10K	140	1667	1071	8930	0%
	1.2V	10K	120	2143	1250	8750	+1.8%
	1.1V	10K	110	2500	1364	8636	2.9%
x100 (100K) RANGE	11V	100K	110	2500	1364	98.64K	-0.14%
	10V	100K	100	3000	1500	98.50K	0%
	9V	100K	90	3750	1667	98.33K	+0.17%
	8V	100K	80	500	1875	98.12K	+0.37%
	7V	100K	70	7500	2143	97.86K	+0.64%

Fig.21 Design-calculation chart for the 3 - range ohmmeter.

Analogue Multi-meters (VOMs).

Modern analogue multi-meters (called Volt-Ohm Meters, or VOMs, in the USA) are provided with a good selection of ohm and AC and DC volt and current ranges. Such meters are usually such excellent value-for-money that it is simply not cost-effective for the amateur to consider building, rather than buying, a multimeter, and this situation has pertained for at least twenty years. Figure 26, for example, shows the

awkward) meter with a similar specification. There are occasions, however, when it is worthwhile building a multimeter; these are usually when a meter with special ranges is required, or when a use is wanted for a spare meter. or when the need is felt for a challenging or educational construction project. In such cases the do-it-yourself 18 range meter of Figure 27 may be considered; it uses a readily available 50uA meter, which is protected by a couple of silicon diodes, and

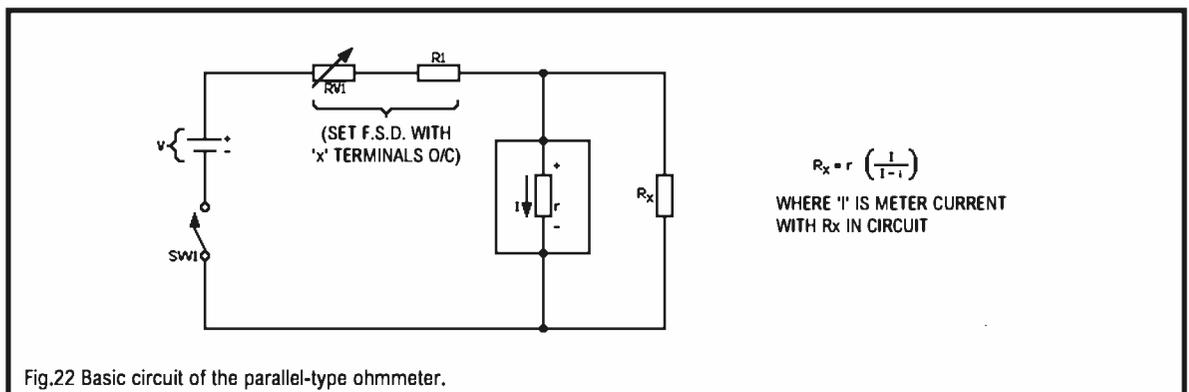


Fig.22 Basic circuit of the parallel-type ohmmeter.

circuit of a popular medium-priced British-built 18-range instrument of the 1970's, the Avo Multi-minor Mark 5. This ancient and obsolescent instrument uses half-wave rectification on its AC voltage ranges (as in Figure 15), and has a basic sensitivity of 1k/volt on the AC ranges and 10k/volt on its DC voltage ranges. Even so, note that it uses a special moving-coil meter which, with a swamp resistor fitted, has an FSD sensitivity of 100mV, and uses a purpose-built 2-pole 18-way range switch that can handle currents up to 1 Amp and has 1kV of insulation between switch contacts. Also note that it uses a variety of odd-valued precision resistors, and that the 7M5 resistor needs an insulation rating of at least 750 volts. The amateur has no chance of buying such components at an affordable price.

Modern multi-meters are an even greater challenge; they use the latest technology, usually have between 18 and 40 ranges, and typically cost less than half as much as it would cost the amateur to make a homebuilt (and usually ugly and

has a sensitivity of 10k/volt on its AC voltage ranges and 20k/volt on its DC voltage ranges.

The reader should have little difficulty in following the circuit of Figure 27. The multimeter's DC current circuitry is derived from Figure 10, its AC voltage section from Figure 13, and its ohms section from Figure 20. No attempt has been made to provide the reader with a rigid range-switching diagram, but switching problems have been eased by providing separate terminals for the 1 Amp and 1kv inputs. so range switches need maximum current ratings of only 100mA and contact insulation ratings of 250 volts.

Using A Multimeter

Analogue multi-meters are fragile and easily-damaged instruments: when using them, always remember the following basic rules.

(1). Most analogue multi-meters arc designed to operate with their faces in one specific physical orientation, usually

horizontal. If such meters are sloped at an angle or are placed vertically when in use, measurement accuracy may be impaired.

(2). When measuring an unknown voltage or current, always set the meter to its highest range and then work down the ranges until the right one is found.

(3). When measuring an in-circuit voltage, connect the meter across the voltage source, as shown in

Simple volt-current-ohm moving-coil meters are the most widely used types of electro-mechanical analogue meter used in electronics, but they are not the only ones. The following list gives brief details of a few other popular variations and types worthy of mention:

dB Meters. In AC signal-voltage measurement, the decibel or dB is used as a means of expressing the relative ratios of signal strengths, a value of 1 dB representing a ratio of 1.122. Thus, a signal that is 1 dB up on a 10V reference has a strength of $10 \times 1.122 = 11.22$ volts, and one that is 1 dB down on the same reference has a strength of $10/1.122 = 8.91$ volts. The scale of any linear AC voltmeter can be graduated in dB by selecting an arbitrary '0 dB' reference voltage and then calculating the appropriate positions for the dB graduation marks. Figure 29 shows an example of such a scale applied to the 10V range of a meter; in this case 7.94V has been selected as the '0 dB' reference value, because it is precisely 2 dB down in 10V

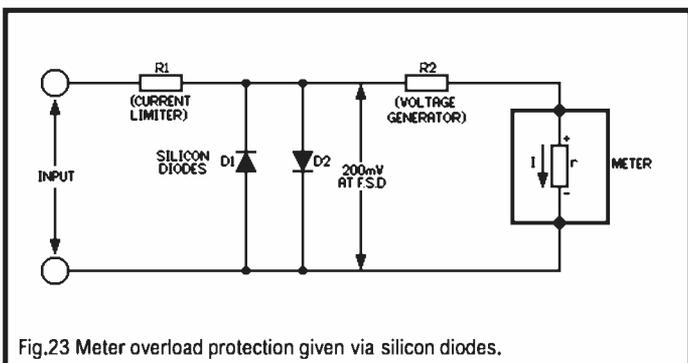


Fig.23 Meter overload protection given via silicon diodes.

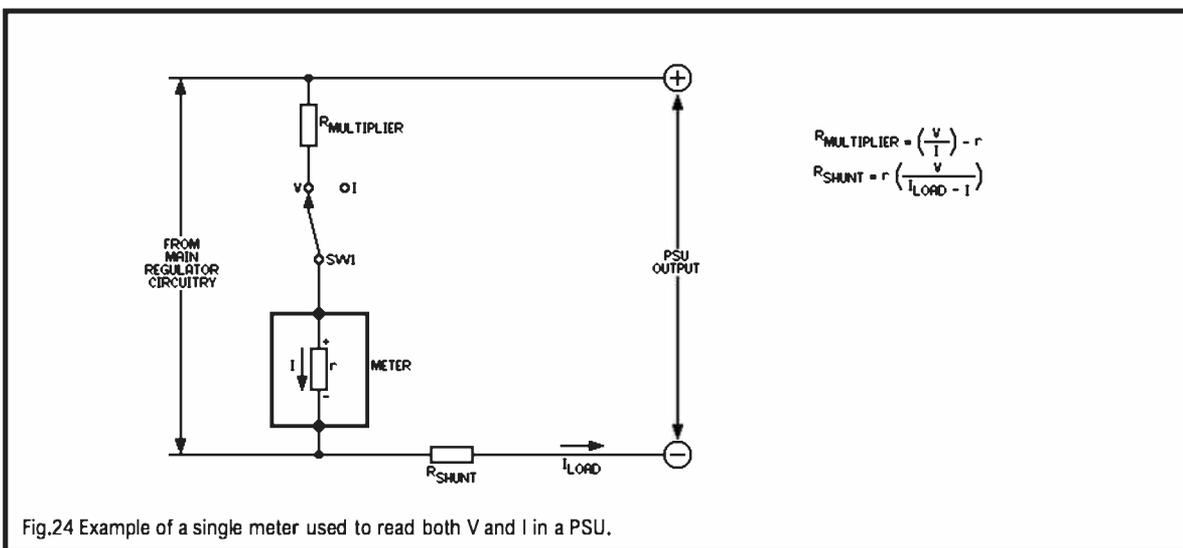


Fig.24 Example of a single meter used to read both V and I in a PSU.

Figure 28a. Always remember that the voltmeter's input impedance (the product of its 'V' range value and its ohms-per-volt sensitivity) will shunt any resistance that it is connected to and will thus reduce the apparent value of its generated voltage; allow for this 'disturbance' effect when taking measurements.

(4). When measuring an in-circuit current, connect the meter in series with the current source as shown in Figure 28b. Always remember that the current meter will generate a significant volt drop (usually between 100mV and 500mV at FSD), and that if it is used in low voltage circuits its presence may have a disturbing effect on the magnitude of the test currents.

(5). When measuring an in-circuit resistance always isolate the resistance from all other circuitry and then connect the meter across the resistor, as shown in Figure 28c. Never try to measure the value of a resistance that has a voltage source applied to it. Always remember that the ohmmeter is itself a voltage generator, and that when connected to a semiconductor junction its readings may depend on the polarity of connection: thus, a diode may give a low reading in one direction and a high reading in the other.

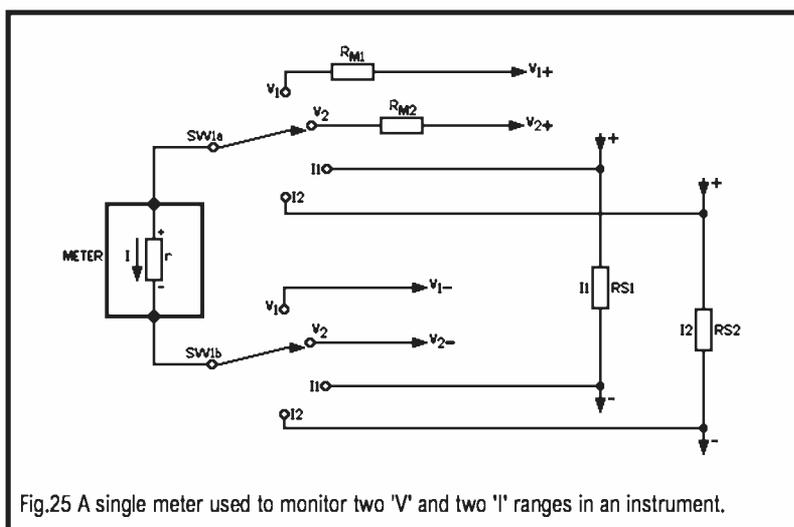


Fig.25 A single meter used to monitor two 'V' and two 'I' ranges in an instrument.

and thus enables the meter's FSD point to be used as the '+2dB' point. The table lists the positions for the dB graduation points in terms of percentage of FSD. **Watt-meters.** A true watt meter makes independent measurements of a load's voltage and current, and gives an output

Circuits


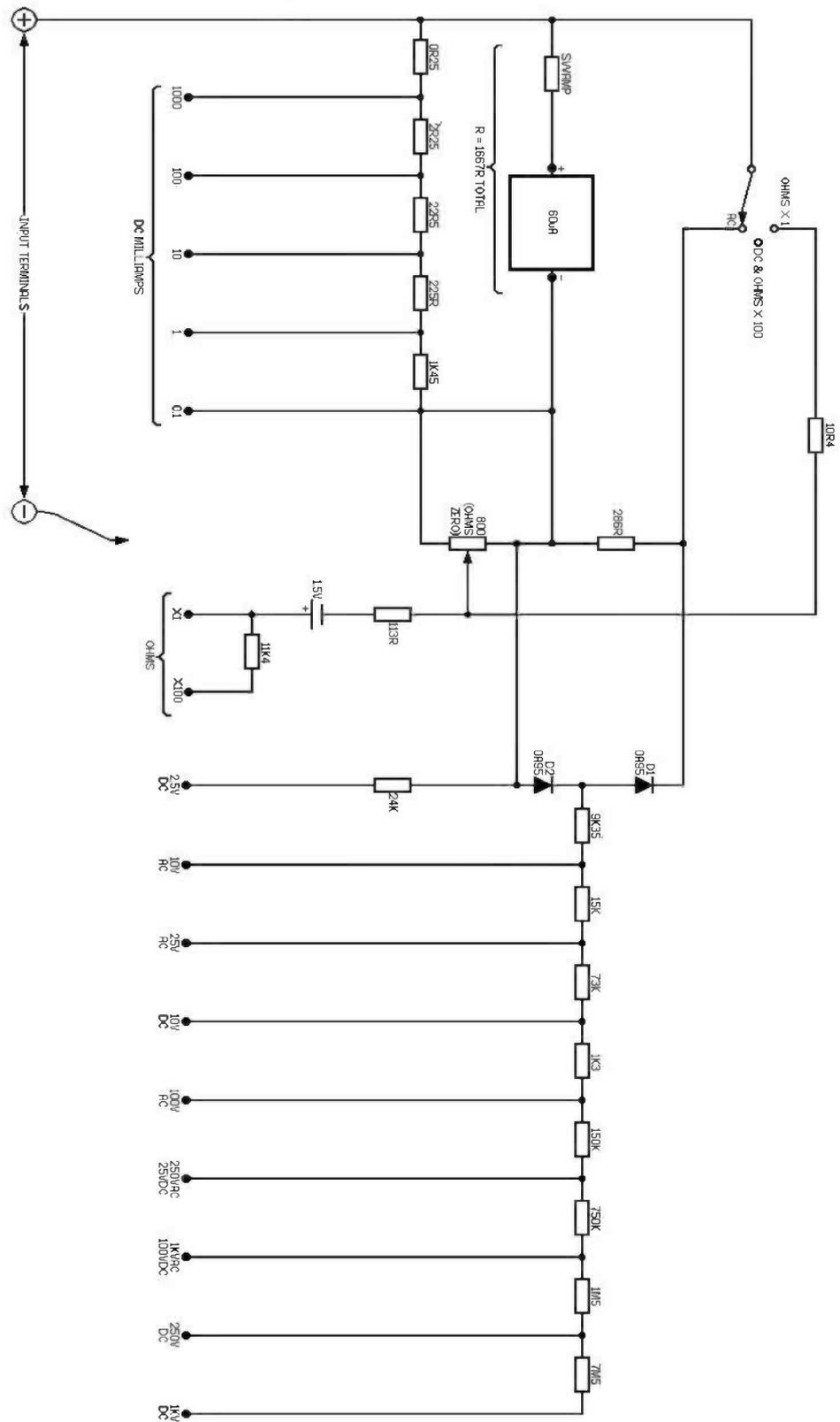
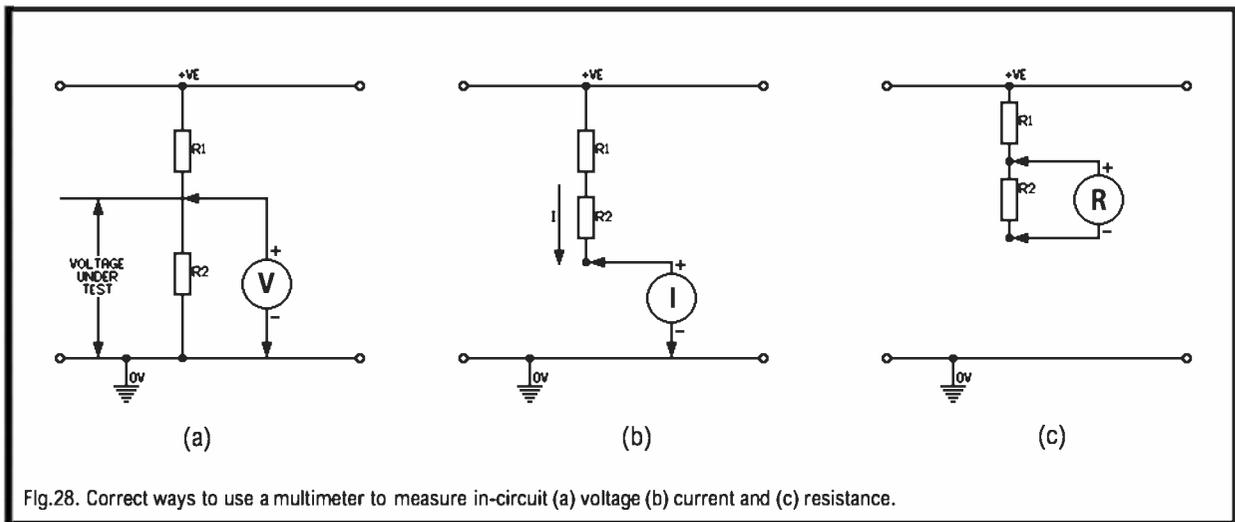


Fig. 26. Circuit of the 18-range Avo Multimeter Mark 5 of the 1970's era (reproduced by courtesy of Avo Limited, Dover, UK).

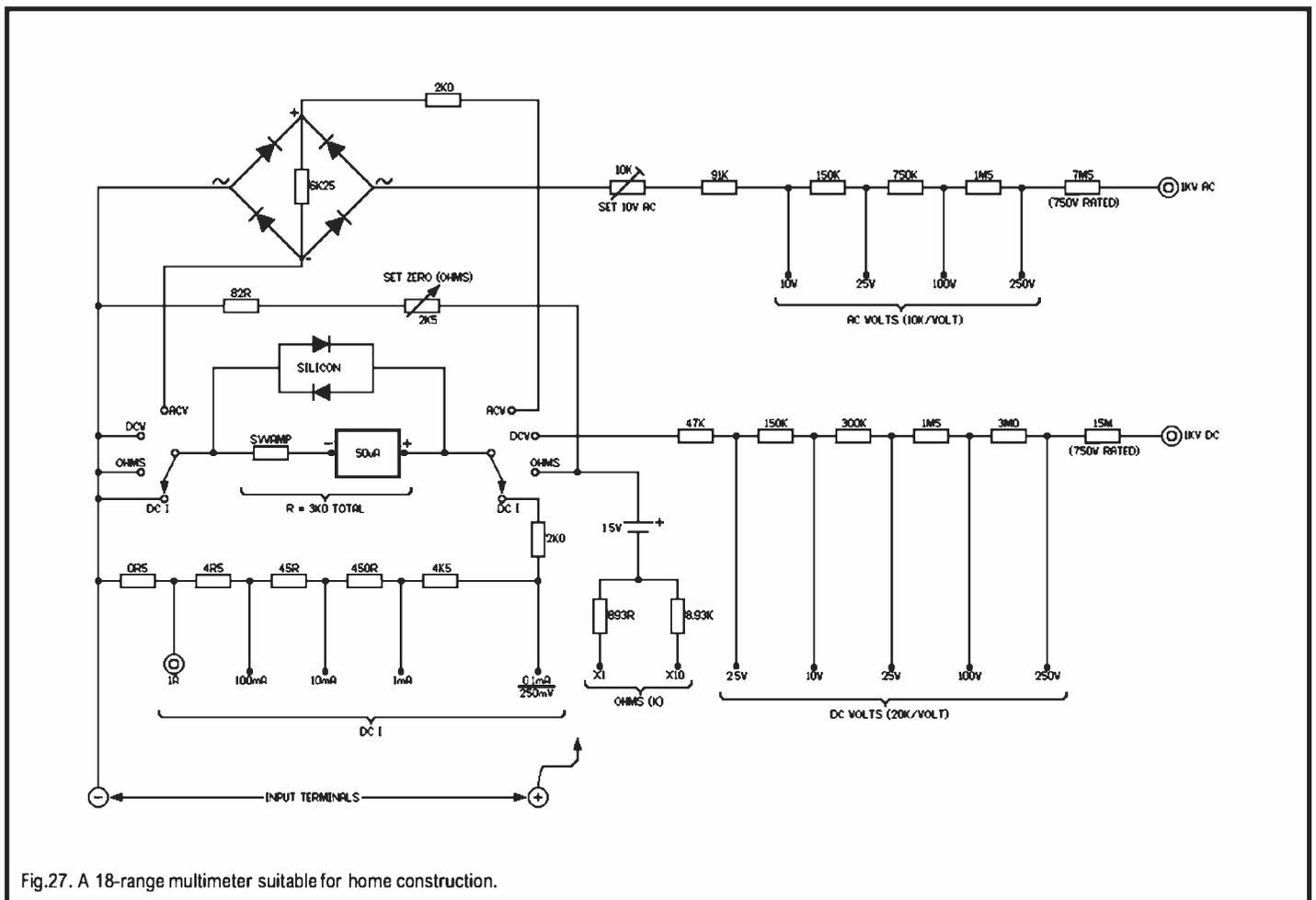


Circuits

reading that is equal to their product and is independent of variations in load resistance. Such meters are expensive. If power measurements are to be made into a fixed load resistance, however, an inexpensive pseudo-watt-meter can be made by simply using an AC voltmeter to monitor the resistor's output voltage, as shown in Figure 30, and calibrating the meter scale on a basis of $W=(V^2)/R$. Such a meter has a non-linear scale, as shown, since its voltage reading is proportional to the square root of power.

Thermocouple Meters. Thermocouple meters are often used as RF current or power indicators at frequencies up to hundreds of MHz, or as wide-band AC/DC transfer standards

in electrical calibration work. They consist of a thermocouple (a junction of two wires made from dissimilar metals, which generates a cross-junction voltage when heated) that is connected directly to a moving-coil meter, and an externally energised 'heater' that is in thermal contact with the thermocouple. When an external current is fed through this second pair of wires it causes the thermocouple to heat up and generate a proportionate current in the moving-coil meter. This current is proportional to the true RMS input current, and is not influenced by the shape or frequency of the waveform, and such meters can thus be used at frequencies from DC to hundreds of MHz. These meters have a square-

Circuits

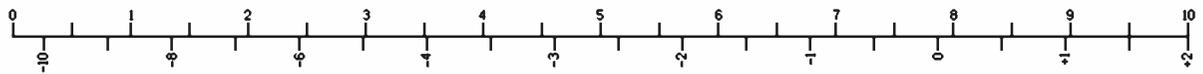

% FSD	dB	% FSD	dB	% FSD	dB
100	+2	50.1	-4	25.1	-10
89.1	+1	44.7	-5	20.1	-12
79.4	0	39.8	-6	15.9	-14
70.8	-1	35.5	-7	12.6	-16
63.1	-2	31.6	-8	10.0	-18
56.2	-3	28.2	-9	7.9	-20

Fig.29. A dB volts scale compared with a linear 10V scale, using 7.94V as a '0dB' reference, to give a value of +2dB at FSD.

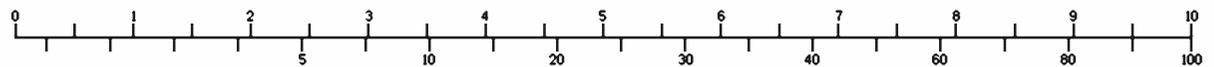
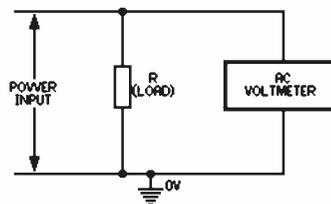


Fig.30. Basic circuit and typical non linear scale of a simple pseudo-watt-meter.

law scale. The thermocouples are very fragile and easily burnt out.

Moving Iron Meters. These meters are widely used as AC or DC volt or current meters in low-accuracy applications, etc. They have a fixed coil (through which the measured current flows) and a balanced iron vane that carries a pointer and deflects when the coil is externally energised. Such meters are cheap and robust but have a low sensitivity. They respond equally well to AC and DC; their scales are non-linear, and are cramped at the low end.

Electrostatic meters. These are usually built to read voltages in the 1kV to 30kV range. In essence, they act as one

fixed and one movable set of capacitive vanes; a pointer is fixed to the movable vane, which is deflected electrostatically when an external voltage is applied. Such meters respond to both DC and AC voltage (they draw zero current from DC sources and a frequency-dependent current from AC sources). Their meter scales are non-linear, and are cramped at the low end. Such meters were once widely used for high voltage measurement, but they are now rarely used.

The next episode of this series will look at electronic analogue meter circuitry.

HALCYON ELECTRONICS

Test equipment, video monitors, amateur radio gear, printers, power supplies, communications, disk drives, multimeters, oscilloscopes, scientific instruments, connectors, component bridges, frequency counters, signal generators, computers.

TELEQUIPMENT D57A 25MHz, 2T, DEL T/B	£215	DEBRILLATOR 50-400 JOULES BATT MAINS	£149
H P 1700A 35MHz DUAL TRACE	£249	FARNELL FGI FUNC GEN 2-2.2MHz	£129
GOULD 05300B 50MHz 2 TRACE DEL T/B	£269	'COLLECTORS' TEST EQUIPT, VARIOUS	POA
TEX 453 50MHz DUAL TRACE DEL T/B	£249	COMMUNICATIONS RECEIVERS, VARIOUS	POA
TEX 465 100MHz DUAL TRACE DEL T/B	£650	200W U.V. SOURCE WITH TIMER	£35
SCOPEX 4D25 25MHz DUAL TRACE	£189	1920s WIRELESS, REED & HORN SPKRS	POA
BECKMAN 9020 20MHz DUAL TRACE	£249	McMURDO SILVER CORD, 1 ONLY	£49
DATA PRECISION 6000 WITH 611 PLUG-IN AND 6B1 DISK DRIVE UNIT.		PERISCOPES MILITARY No. 43 Mk 3	£119
GOULD 05300A 40MHz 2 TRACE, DEL T/B	£395	LCR MARCONI TF1313A 0.1%	£36
HAMEG 202-6 20MHz, 2 TRACE, COMP TESTER	£249	LCR MARCONI TF2701IN SITU	£125
HITACHI VC 8015 10MHz DIGITAL STORAGE	£249	LCR MARCONI TF668B	£69
H.P. 1340A X-Y DISPLAYS	£345	LCR COMPONENT COMPARATOR OVAO C2457S	£75
LEADER LBO-9C ALIGNMENT SCOPE	£99	WAYNE KERR B321 LOW IND. BRIDGE	£39
TEX 5L4N 100KHZ SPECT ANAL WITH SI 10MF, 2x SA18N, 9810N TIME BASE	£195	HP1901A -05A -08A -17A 25MHz PULSE GEN	£125
TELEQUIPMENT D75, 50MHz 2 TRACE DEL T/B	£750	SCR 578N GIBSON GIRL EMERGENCY XMITTER	£75
TEKTRONIX 7400N DFI, 7D01 LOGIC ANAL	£225	AMFVENNER 625/2 SIG GEN 1Hz-1MHz SIN/SQ	£89
TEX 545B, 585, 585A, 526A, 541A, 515A	£495	LEVELL TG152 3KHz-300KHz OSCIN/SO	£85
TEX 545/585 SERIES PLUG-INS	From £49	LEVELL TMB3 MICRO V-METER 450MHz	£36
WANDERL/GOL TERMAANN SPM-2 LEVEL METER	From £10	LEVELL TMB3 MICRO V-METER 3MHz	£85
WANDERL/GOL TERMAANN SPM-3 LEVEL METER	£169	TU88/TU98 TUNER UNITS BRAND NEW	£29/39
WANDERL/GOL TERMAANN PS-3 SIGNAL GEN	£189	OERTLING V20 SINGLE PAN BALANCES 200GM	£35
MARCONI TF2301 AM/FM MOD METER PRTBLE	£169	SAGE 2-WAY CO-AX SWIT CH SAN 2120 NCONNS	£35
RACAL 9059 FCTR 560MHz MAINS/BATT	£195	UDI 2026 SONAR SCANNER SURFACE UNIT	£385
19' RACKS 20L, 31' DEEP	£145	UPA CAVIDERM CD6 P.T.H. TEST ER	£750
HP 3480A DMM AC/DC/V OHMS 6 DIGIT	£125	MARCONI MARINE KEST REL 3	£49
XFORMERS SEC 30-0-30V 20A, URIV PRVS, C-CORE	£20	ANALYTICAL BALANCES WITH WEIGHTS	From £15
WHOUSE 1/4HP REVIVE MOTORS 220V 1K RPM	£25	KAYE DEE PNEUMO U/V EXP UNIT 390x260mm	£175
CONSTANT VOLTAGE TRANSFS 150VA-2KV	POA	VACUUM PUMPS TYP-100MBAR (20L/MIN)	£35
MARCONI TF2301 DISTN FACTOR METER	£175	CALIBRATION STANDARDS CWA/LR	POA
BBC-B & MASTER COMPUTERS	From £99	COSSOR CRMS33A VHF NAV/COM FF SIG GEN	£750
MARCONI TF2300 FM/AM MODULATION METER	£249	COSSOR CRMS11 IL S/VOR AUDIO SIG GEN	£249
VARIABLE OUTPUT PSU's HV & LV	£395	TO PAZ 91009-117.5kVA 120/240-120/240 150L	£249
TEKTRONIX 980 52W PAL V/SCOPES	From £275	KINGSHILL NS1540 15V 40A PSU CASED	£296
	From £49	HP 626A, 628A, SIG GEN. LAST FEW	£35 ea
		SIGNAL GENERATORS AF TO 21 GHz	From £.15

LIST AVAILABLE, BUT 100% OF UNLISTED BARGAINS FOR CALLERS ALL PRICES EXC. OF P&P AND VAT
QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED.

423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383

PLASTIC BOXES



A RANGE OF SMALL PLASTIC BOXES, CASES AND POTTING BOXES AVAILABLE IN ANY QUANTITY.

SEND FOR FREE CATALOGUE

SLM (MODEL) ENGINEERS
CHILTERN ROAD, PRESTBURY,
CHELTENHAM, GLOS GL52 5JQ
FAX: 0242 226288

HENRY'S

NEW STOCKS
AND SPECIAL OFFERS

ASTEK SW mode power supply

Three pin mains socket input, on/off switch. Output +5 volt 3.75 amp, +12 volt 1.5 amp, -12 volt 0.4 amp. 115-230 V AC Input. Size 7.0 x 8.3 x 2.5 ins with circuit. **£12.95** incl VAT



'POCKET' TEST INSTRUMENTS (with case) Prices incl VAT

- 138 Satellite Signal Finder, FS + Compass **£29.95**
- 1048 Digital Lux Meter - 3 Ranges **£81.00**
- 1206 Sound Level Meter - 2 Ranges **£45.00**
- 206A 20KHz to 200 MHz **£104.58**
- 2 Range Freq. Counter **£47.98**
- 888 Sine/Sq. 20 Hz to 150 KHz. Audio Gen. Switch Freqs **£81.00**
- 80 Digital Capacitance Meter upto 2000 mfd **£82.00**
- NDA16. Tri Grid Dip. 6 Ranges 1.5 to 250 MHz **£38.05**
- *Y226V. VHS Video Head Tester **£41.00**
- H288. Component Tester - Add to any Scope **£25.95**
- *T3900. AC Clamp Meter. 0/300A. 0/600V. 0/1 Kohm **£15.95**
- SPECIAL PURCHASE **£53.95**
- 208. 0/2000 amp AC Clamp - Add to Dmm **£21.95**
- 292. 0/200/2000 Amp AC/DC Version **£21.95**
- *320P. Waiver Type Digital Multimeter. SPECIAL PURCHASE **£21.95**

LCR DIGITAL METER Pocket size instrument

- 3 1/2 digit LCD, 20 ranges.
 - 7 Capacitance, 0/200 mfd
 - 6 Inductance, 0/200H
 - 7 Resistance 0/200 M ohm
- £69.95** incl VAT with leads and battery



TL34

33 Range 3 1/2 digit mm

24mm Large Display

FEATURES: 5 Capacitance

ranges, 6 - resistance

ranges to 20M ohm Diode

and transistor test. AC/DC

volts ranges, 5 ranges

AC/DC current to 20 amps.

With leads, battery and

instructions. **£25.95** incl VAT

TL3400

31 range 3 1/2 digit mm

with 25mm Large Display

FEATURES: 4 Capacitance

ranges, AC/DC volts,

AC/DC current to 20 amps, 6 resistance

ranges to 40M ohm Diode test, Continuity test, Logic

checker with buzzer, Auto range frequency

counter, Peak hold button, Temperature test. **£39.95** incl VAT

IN STOCK AUDIO-ELECTRONICS

(Details in colour catalogue and supplements)

FULL RANGE OF TEST INSTRUMENTS -

Scopes ■ Counters ■ Power Supplies

Generators ■ Meters ■ Hameg ■ Metex

Blockstor ■ Testlab ■ Thurlby ■ Thandar

SECURITY AND COMMUNICATIONS -

Alarms ■ Lighting ■ Detectors ■ Intercomms

Doorphones ■ CCTV and CB Radio

AUDIO EQUIPMENT - ■ For Public Address

Hi-Power Car Systems ■ Disco and Hi-Fi

Speakers ■ Amplifiers ■ Mics ■ Effects etc

COMPONENTS AND TOOLS - Large Range Inc.


Fans ■ Large Value Caps ■ Relays

Transistors

ACCESSORIES - ■ For TV ■ Video ■ Hi-Fi

Telephones CB etc etc.

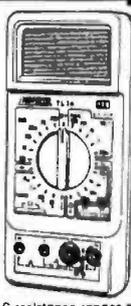Open 6 days a week for callers and telephone orders
UK Cont/Pack/Ins £2.05 - Post Free only two items




COLOUR CATALOGUE with supplements. Send S4 (UK), S8 (abroad) £2 for callers. FREE updates for your 01/82 catalogue send large SAE (34p stamp). FREE catalogues with trade prices for trade and education - write or fax.

Professional WEATHER MONITORING at low cost

FEATURES (depending on model)

- WIND DIRECTION
- WIND SPEED
- GUST ALARM
- GUST SPEED
- RAINFALL
- SUNSHINE
- OUTSIDE TEMPERATURE
- MIN-MAX TEMPERATURE
- RELATIVE HUMIDITY
- BAROMETRIC PRESSURE
- WOODEN CABINET
- MAINS & 12-24V DC

★★ All main readings at a glance ★★

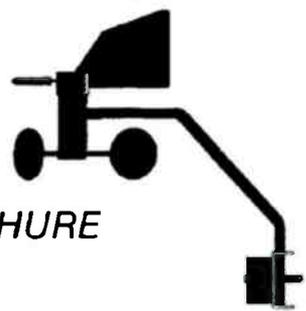

SEND FOR COLOUR BROCHURE

Prices from only **£189** inc. VAT

R&D ELECTRONICS, PERCY AVENUE,
KINGS GATE, BROADSTAIRS, KENT CT10
3LB. TEL: (0843) 866662 FAX (0843) 866663



HENRY'S 404 Edgware Rd, London W2 1ED

Instruments, Audio, Equipment 071-724 3564

Security, CCTV, Communications, 071-724 0323

Components, Service Aids, 071-723 1008

QUANTITY, EXPORT AND EDUCATION DISCOUNTS,
OFFICIAL ORDER SALES Tel. 071-258 1831, Fax: 071-724 0322

Communications Link by RS232

Testing

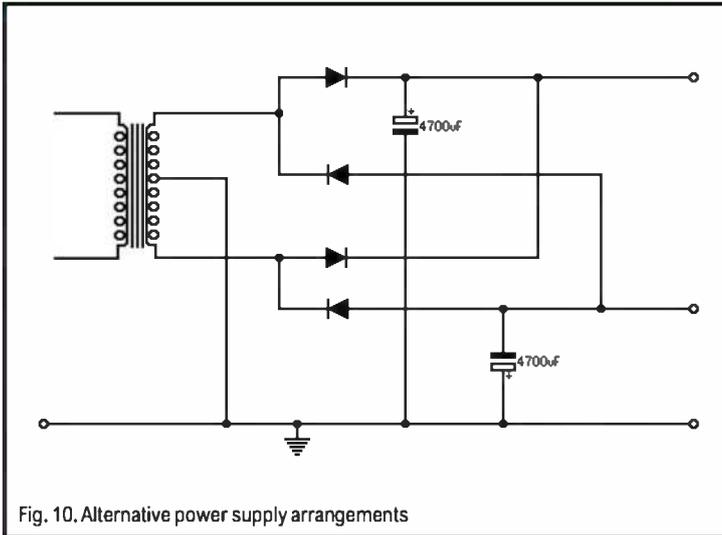


Fig. 10. Alternative power supply arrangements

a large capacitor across the DVM (a 1µF or thereabouts is OK) and a 470k approx in series with the OSC connection to filter out the oscillator frequency. If the oscillator isn't running check the component placements particularly for chips the wrong way round. Given the oscillator is running and no frequency meter is available the next job is to set its frequency as accurately as possible. The modus operandi is to connect a meter between bit 7 of the receiver and 0V then repeatedly send alternate bursts of @ signs ASCII 40H ie. 01000000 followed by a burst of SOHs ASCII 01H ie. 00000001, with a short break between. Do this continuously and adjust the preset until bit 7 changes between 0 and 1 as the burst of characters are received. Then determine the positions of the preset at which this fails and finally set the preset midway between these two extremes.

This done, check with the meter that bit 1 is also changing between 0 and 1.

This data sending is obviously most easily done using a computer! What is required is a burst of @ about 1 second long, a short pause of at least 2 characters duration followed by a burst of SOH followed by a pause. About 300 characters are a suitable burst length. As an illustration it can be done in the following way using an IBM PC or look-alike.

Connect the board to the PC (see 'In Use') for details and switch on the power to the board. Switch the PC on as well! Set up a file with about a250@ in it. If you want to use your favourite word processor by all means do so but be sure there are no embedded format characters, it should be a straight

2

**A project where
'Device Shall Speak
Unto Device'
Commentary by
Keith Garwell.**

We continue our RS232 link by looking at the testing procedure. Connect the power lines +12, -12, +5, and 0 volts either direct or via the mother board depending on the decisions arrived at earlier. If you have a frequency meter then the rest is easy. Connect it between the link marked OSC and the link marked 0V on the placement diagram (Figure 15). Adjust the 10k preset until the required frequency of 38.5kHz is obtained and that's all there is to setting up.

Failing a frequency meter then the first step is to check that the oscillator is running. A 'scope is handy at this point but if no 'scope is available use a conventional (moving coil is conventional to me - that dates me doesn't it!) meter between the OSC and 0V links. The voltage should be approximately half the working voltage ie. 2.5 volts as the oscillator has an even mark to space ratio. If you don't have a moving coil meter use a DVM but if it gives a silly answer it may be because of interaction between the oscillator and the sampling system in the DVM. If this is the case connect

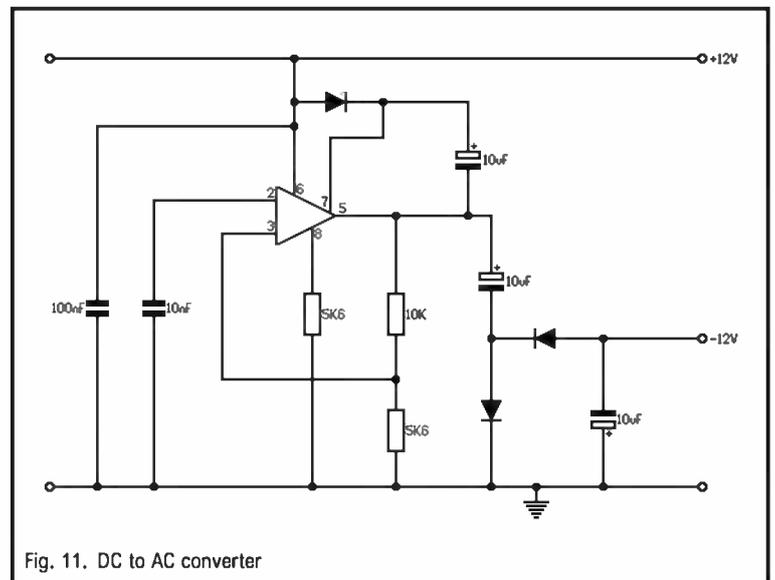


Fig. 11. DC to AC converter

PROJECT

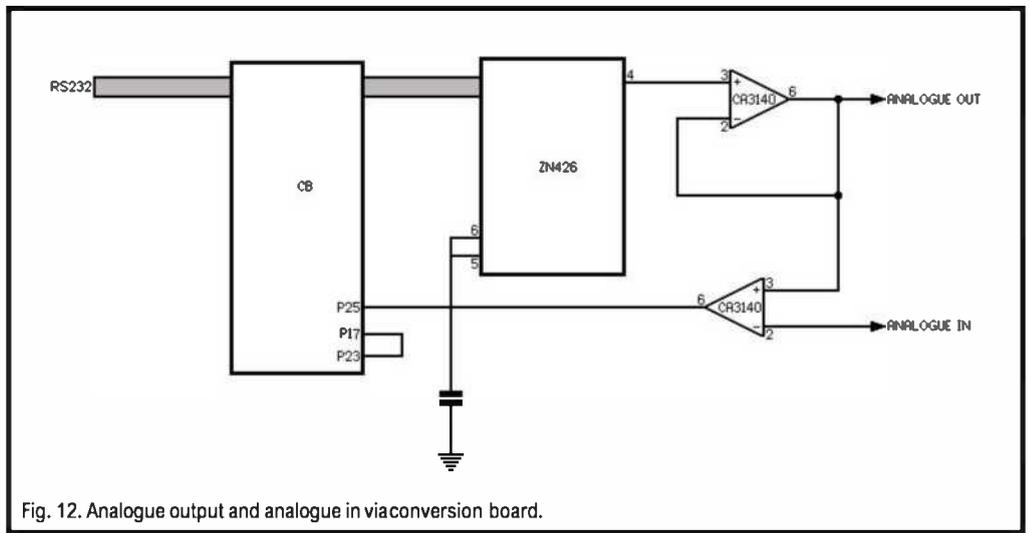


Fig. 12. Analogue output and analogue in via conversion board.

ASCII file without carriage returns or line feeds. Alternatively the built-in DOS commands will do it as follows - (depressing the Enter key after each command is implied).

COPY CON AT

Followed by typing two and a half lines of @ signs then control and Z then enter.

The file AT thus contains the @ signs. Now for the file containing the SOH or 0 1 characters. Your favourite word processor may not be able to do this! But the operation is similar to the previous one viz.

COPY CON SOH

Type 5 lines of control and A then control and Z then enter. Control and A is usually shown as "A so there are only 40 real characters per screen line hence 5 lines to make it the same length as the AT file. The number of characters doesn't matter within a few, just so long as it takes about a second to send. Excluding the time to get the file.

Now make a batch file the contents of which are as follows-

COPY CON SENDALTS.BAT

:AGAIN

COPY AT TO COM1:

COPY SOH TO COM1:

GOTO AGAIN

Now set the Baud rate word length etc with the

MODE command by typing -

MODE COM1 : 2400,N,8,1,P

Now set it all in motion by typing -

SENDALTS

The batch file will read the two files from disc and send them. The disc reads giving the required short pause between sending each block. This pause is important as it forces the conversion board to resynchronize. Without it the characters will just pour out continuously and twiddling the preset will cause synchronization to be lost.

When ready stop the batch file running by pressing CTRL and C.

In Use

The computer end - setting up. All the remaining explanations will be illustrated using an IBM PC or look-alike hereinafter referred to as the PC. Other machines will have similar commands although the command names may not be identical. Only the commands are given below, pressing Enter to activate the command is implied.

First the RS232 computer link must be set up to correspond to our board. (Not Baud! and surely not bored!). To set up the first channel on the PC the MODE command is used as follows -

MODE COM1:2400,N,8,1,P

If it were the second channel then COM2: would be used. In fact I use a batch file (a file containing system commands, often referred to as the System Control Language) called M2400.BAT containing -

ECHO OFF

MODE COM1:2400,N,8,1,P

Then all I have to do to set up the link is type M2400. Alternatively the Mode command can be inserted in the system start-up file AUTOEXEC.BAT so that the PC is automatically set correctly at switch-on.

Before I forget the P at the end of the MODE command causes the receiver to ignore time-outs. By way of explanation the program which drives the RS232 in the PC will only wait a limited amount of time for an incoming character before it gives up and returns a null (a character of zero). Without the P every null character would be inserted into the file (see below). The next job is to make up the connecting cable. The cheapest possible cable 'is ideal! Only 3 wires are used so a very thin mains cable would do if you have some and only a short length is required. However mains cable is not the cheapest solution if you have to go out and buy. In this case the four wire cable often referred to as signal cable or burglar alarm cable is the cheapest (Maplin). The connectors used for RS232 on a computer are D type plugs, the standard being a 25 pin. An alternative sometimes used, especially on physically small machines is a 9 pin D type.

As well as the two data lines and the common ground or 0V these plugs carry control signals intended to show the state of readiness (status) of the computer and attached modem. These control lines must be correctly driven otherwise the link will not run. In our case this is achieved by linking some of the lines together.

For a 25 pin socket the connections are:

Pin 2 is the transmit or output and is connected to P10 on the conversion board (CB).

Pin 3 is receive or input and goes to P18 on CB.

Pin 7 is the common and goes to 0V that is P12 on CB.

Pins 4 and 5 are Request To Send and Clear To Send, RQS and CTS and should be linked together.

Pins 6, 8 and 20 are respectively Data Set Ready, Data Carrier Detected and Data Terminal Ready, DSR, DCD and DTR and should be linked together.

For a 9 pin socket the connections are:

Pin 3 is transmit and goes to P10 on CB.

Pin 2 is receive and goes to P18 on CB.

Pin 5 is the common and goes to 0V that is P12 on CB.

PROJECT

PROJECT

Pins 7 and 8 (RQS CTS) should be linked together.
Pins 6, 1 and 4 (DSR DCD DTR) should be linked together.

The Computer End -Driving The Link

There are three approaches to the problem. Use the features built in to MSDOS to link communications with files. Design the handling into the program(s) which will use the Conversion Board using communications commands. Drive via the BIOS (Basic Input/Output System a part of MSDOS) interrupts from the program(s) using the board.

By sending or receiving a file via the communication link using MSDOS commands. Given that the name of the file to be sent is TX.DAT and that any data received is to be inserted into the file RX.DAT then the commands are:

```
COPY TX.DAT COM1:
or
COPY COM1: RX.DAT
```

In the first case the whole file contents will be sent as one block without pause. Whilst for the receiver command the PC will buffer up the data and only establish the file upon receipt of the normal PC file terminator ASCII 26 (generated by control and Z and represented on screen by Z. Note it is not necessary for the data to be a continuous block the receiver will sit for ever collecting characters until the terminator is received.

The second method is to use BASIC or any other language which will handle the communications port. GWBASIC which is often supplied with a PC is suitable. The file is opened with the statement:
OPEN 'COM1: J400,N,8,1' as file number, length
Then use statements to write/read to the specified file number as for any other file.

The third method is perhaps more appropriate to machine code but will usually be available in compiled languages. It consists of making calls to interrupt 14 in the BIOS with certain contents in the machine registers. For example

To initialize the communications to 2400B,NP,8 bits,!
SB call interrupt 14H with AH=0, bX=0, AL=101000! I (A3Hex). On return from the routine AX will contain status information.

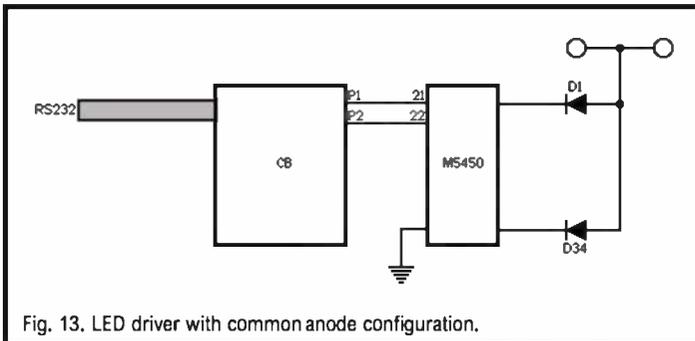


Fig. 13. LED driver with common anode configuration.

To send a char call interrupt 141-I with AX=01H, DX=0, AL= char to be sent. AH contains status on return.

To receive a char call interrupt 14H with AH=02H, DX=0. On return AL=char received, AH=status. Note that if a char is not received within the 'specified' time-out the routine will return with a null character. The 'specified' time is set as part of the initializing routines when setting up the PC in the first place and is usually stored in battery backed RAM.

As A Converter From Centronics To RS232

This was the original reason for the existence of the converter board. I use a Dragon micro for various jobs from time to time and often wanted to pass data to a PC for processing. However the Dragon only has a Centronics printer connection. Centronics implies a particular connector and style of data handling for 8 bit parallel data. I must be honest and admit that I don't know where the name came from. I suspect it was an original manufacturer. Anyway the interface has become a 'standard'

I'm sure it could be a good idea to go over the operation of the Centronics printer interface so that we can see how it applies to the conversion board. It is also typical of the way in which many parallel interfaces work.

There are 8 data lines along with their own returns to 0 volts, +5 on a data line indicates logical true or 1. Imagine the sequence. The processor puts the appropriate voltage levels on the 8 data lines for the first character. To ensure that the printer does not misread any of the data whilst it is in a state of change the processor applies a signal to a 'strobe' line to indicate that the data is no longer in a state of change and can be read by the printer. Before changing the data for the next character the OK signal is removed from the strobe line. The sequence is then repeated for each character.

This arrangement works admirably so long as the printer can handle the characters more quickly than the processor can send them otherwise data will be lost. As it happens this state of affairs is very unlikely. The printer is a mechanical device so will be much slower than the processor. Consequently there must be some means of slowing down the processor. On the Centronics interface this can be done in either of two ways. There are two other lines, one called BUSY, and one called ACKNOWLEDGE (usually abbreviated to ACK) both under the control of the printer. +5 on the busy line indicates to the processor that the printer is unable to accept further data while 0V on the acknowledge line indicates to the processor that the data has been received and the printer is ready to accept further data. Putting it round the other way, +5 on the acknowledge line indicates the printer is not ready. Whichever one is used the other must be set to the not true condition. If the busy line is to be used then ACK must be set to NOT ACK ie. to +0V. Conversely if ACK is 10 be used then BUSY must be set to NOT BUSY.

In our case we use the busy line. The connections between the Centronics socket and the conversion board are shown in the following table where CS indicates the pin number on the Centronics socket and CB indicates the connection number on the conversion board.

CS	Use	CB
1	Strobe (N)	23
2	Data 1	25
to		
9	Data 8	32
10	Ack (N)	not used
11	Busy	16
19	Gnd or 0V	12
20		
to Not used		
29		

In use set the PC to read data from the RS232 line for example with the command;

```
COPY COM 1: MICRO.DAT
```

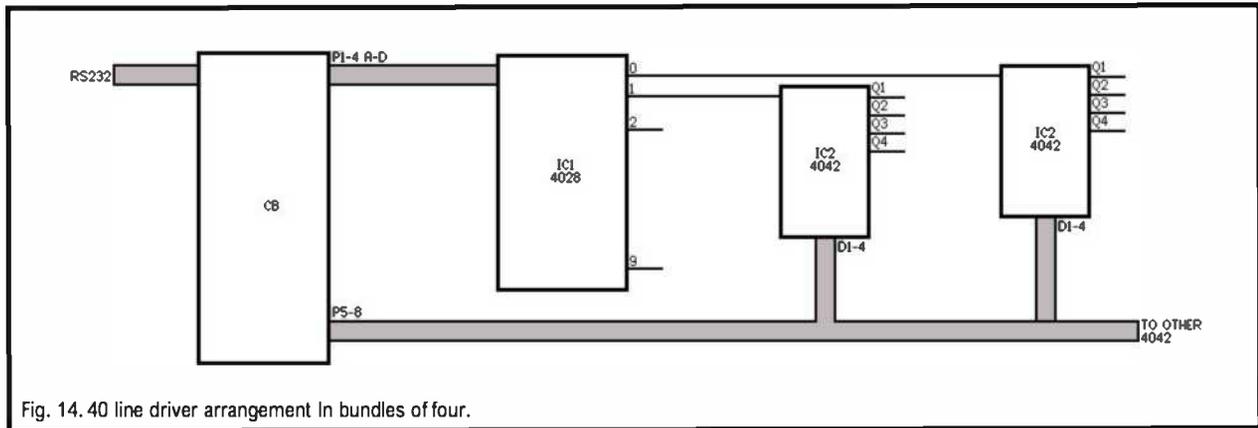


Fig. 14. 40 line driver arrangement in bundles of four.

PROJECT

The PC will sit patiently waiting for data. Now fire up the micro so that it behaves as though it were passing data to the printer. When it has finished the terminating character 26 must be sent. The PC will put the data away in the file MICRO.DAT.

As A Digitiser

Figure 12 shows the arrangement required to provide analogue output and analogue input via the conversion board and RS232 link. The shaded bars indicate connections of more than one line.

The analogue output is quite straightforward. A character sent to the conversion board via RS232 appears on pins P8 to P1 (LS pin first) this is coupled to the input pins of the ZN426 (Maplin) where it is converted to an equivalent analogue voltage at the output. NOTE. On DAC chips the MS. bit is often labeled 1 and the 1s bit 8. The conversion is in the range 0 to 2.55 which corresponds to the possible character values of 0 to 255.

The analogue output is buffered by the CA3140. This particular op-amp has the advantage that it includes 0V in its operating range. It isn't absolutely essential but the output impedance of the ZN426 is 10K and for accuracy the load resistance would need to be of the order of 220K at least. For the sake of the few coppers that a 3140 costs the 'old halfpence of tar' really applies. The 3140 also offers the facility for scale changing if required. It is as well to run the 3140 from more than 5 volts if possible because the output of this op-amp will not get closer to the positive rail than 2.25 volts which with a maximum output from the ZN426 of 2.55 gives 4.8 which at 5 volts only leaves 0.2 volts spare. That is sailing close to the wind!

The analogue value will appear immediately the character is sent from the PC (well nearly), so there's a simple waveform generator.

The analogue input is less straightforward, in fact its positively crooked! From Figure 12 it will be seen that the analogue input is compared with the analogue output by means of the second CA3140.

The result of comparison, the output of the 3140, is connected to one of the inputs to the conversion board. I have shown the connection as being to bit 1 and what follows assumes this to be the case. However it need not be, any bit will do, especially if it is more convenient because you are using the bit for something else.

Figure 12 also shows the signal RXDR Receiver Data Received tied to TXS the Transmit Strobe. Thus sending

a character to the DAC will result in RXDR going low and loading the comparator output into the transmit buffer. When RXDR goes high the character will be sent. Thus bit 1 of the character being returned to the PC will indicate whether the analogue input is less than or greater than the analogue output.

From this arrangement it is possible to determine the actual value at the analogue input by means of a little software routine. The demonstration code is written in BASIC. Note, my WP interprets the hash sign as a pound sign, it should be written hash 1 and input hash 1 in line 120.

```

10 DIM UD(9)
20 UD(1)=&H40 : UD(2)=&H20 : UD(3)=&H10 :
   UD(4)=&H8
30 UD(5)=&H4 : UD(6)=&H2 : UD(7)=&H1 :
   UD(8)=&H1
40 OPEN 'COM1 : 2400,N,8' AS #1
100 CV=&H80 : LC=0
110 FOR I = 1 TO 9
120 WRITE # 1,CHR$(CV) : INPUT #1,RX$
130 IF ASC(RX$) = 0 THEN CV = CV - UD(LC) ELSE
   CV = CV + UD (LC)
140 NEXT
150 RETURN "CV contains the current value"

```

It works by what is known as successive approximation. But before attempting to get it working check the code, particularly in lines 40, and 120 which is the input/output and a place where different dialects of Basic will probably differ. It can be called as a subroutine at line 100.

On entry CV is set to &H80 where the most significant bit is a one. This value is sent down the line and the returned value will indicate whether it is too large or too small in line 130 and the value is adjusted by adding or subtracting the next bit by adding or subtracting &H40. Then round the loop again until all 8 bits have been done. The answer given can be one bit too small, 0.01 volt too small. This is because the comparator only returns too large or too small there is no equal return.

Whilst on the subject of digitiser if you haven't experimented with them before you may wonder why it sometimes can't make up its mind and keeps returning two answers which differ by 1. This is because if the analogue voltage is just exactly equal to one of the possible answers circuit noise can make the answer swing either way. In other words if the analogue value is exactly 1.82 you may get answers of 1.81 or 1.82.

The output of the conversion board provides 8 lines, one of which must provide the common clock pulses. The remaining 7 are each able to supply data to an M5450. This will give the capability of driving 7 M5450s each in turn driving 34 LEDs or logic outputs. I make it 238 LEDs in total.

Since the clock input requires a level change for each data bit to enter the shift register in effect two characters have to be sent for every bit, a total of 38 characters plus the extra bits for gating the output buffer that's 72 altogether plus a final bit to restore the clock to its starting condition, 73 characters. As the system is running at 2400 Baud that's 240 characters per second so in fact it takes less than a third of a second to update 238 LEDs or logic outputs.

Referring to Figure 13 again where bit 0 is connected to the clock and bit 1 to the data. As an illustration suppose the first 4 bits to be entered into the M5450 are 0110 then the characters sent would be -

```

xxxxxx00
xxxxxx01
1st bit transferred
xxxxxx10
xxxxxx11 2nd bit
xxxxxx10
xxxxxx11 3rd bit
xxxxxx00
xxxxxx01 4th bit

```

Note two points.

First that since only the first two character bits are used to drive the M5450 it doesn't matter what the value of the others are, indicated by an x in the above. This means that the remaining 6 bits can be used for something else, for example to drive up to 6 other M5450s as suggested above. The clock can be common to all.

Second that the data shifted in is most significant bit first so the first data bit sent will appear on output 34.

Just to reiterate the actual pulses applied to pin 22. The first is a dummy, not used, the 2nd will appear as output 34. the 35th as output bit 1 and the 36th will gate the data onto the output lines.

As A Logic Driver

In the previous example (Figure 13) the data could only be changed to all the M5450 ie. all the lines. Certainly the same data could be rewritten so in effect only one output need change but they would all have to be written to. This example, Figure 14, can drive up to 40 lines in bundles of 4

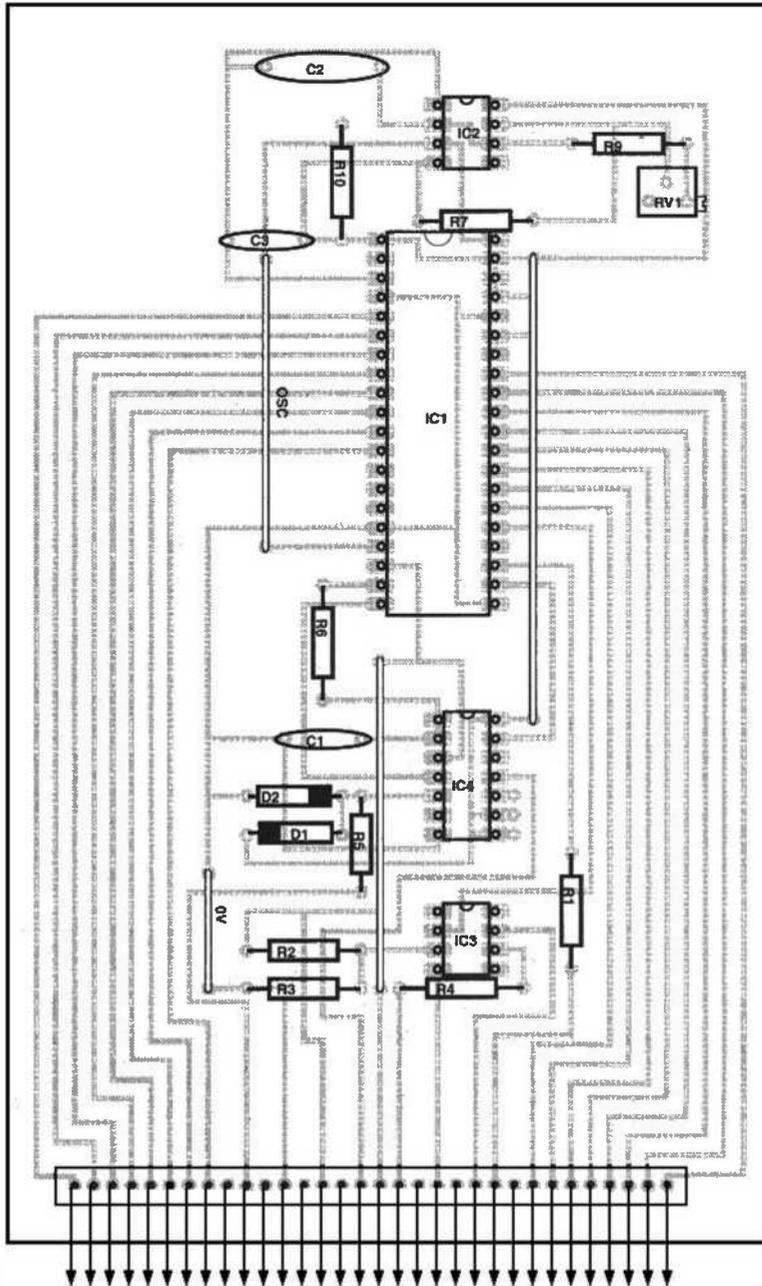


Fig. 15. Component overlay.

A Lots-of-LEDs driver

A very handy device is the M5450 (Maplin) which will drive 34 LEDs. Only one additional component is required to set the current through the LEDs. This is enough to drive four 7 segment displays with decimal point if required. If such displays are used they must be common anode. As an alternative to LEDs, resistors may be used in which case 34 logic outputs are available.

Figure 13 shows the outline detail of the arrangement. The M5450 is a serial device. It has one data input (pin 22) and a clock input (pin 21). A transition from low to high clocks in to a 34 bit shift register whatever level is on the data input. Thus 34 transitions shift in 34 data bits. Two additional bits are required, one before and one after the 34 data bits, both of which should be ones, making 36 bits in all. The 36th transition gates the shift register data into the output buffer to drive the LEDs. There is no intermediate condition at the output. The data changes only on the instant of the 36th clock pulse.

lines. The 4 line blocks are directly addressable and so can be written independently, It works like this.

The processor drives the Conversion Board CB as in all the other examples. The first four bits of the output from CB drives a 4028 which is a 4 line to 10 line multiplexer. In other words any number between 0 and 9 being applied to the inputs A to D will select the corresponding output line 0 to 9. Applying 15 to the input will leave all the output lines unselected (at 0V). Each of these ten lines can be connected to the enable input of a 4028 quad latch. So any one of ten latches can be addressed directly,

The remaining 4 output lines from CB are linked to the 4 inputs of the 4042 latches in parallel. These multi-line highways are indicated by the shaded bars in Figure 14.

The four outputs (Q1-4) plus the four inverted outputs from each 4042 are available four driving logic. For example the eight outputs from IC2 and 3 could drive a ZN426 digital to analogue converter. The outputs from other 4042 could drive analogue switches which could be used to switch the output of the DAC to up to 32 destinations.

An alternative technique is to use 4 quad latches, the first two driving a DAC as before. The second pair acting as the, address to drive multiplexing switches. This in fact is a technique proposed for remotely driving a theatre lighting system.

In action a similar driving technique can be used to that of the previous system, by sending pairs of characters. For example to set the output of IC2 to 0110 send the following characters:

01100010 1st character selects latch and applies data

01101111 2nd character deselected latch keeping data constant.

In action the MS four bits of the character act as the data and the Ls. four bits select the quad latch to which the data is directed. The second character carries the same data but the address bits contain 15 which deselected the quad latch. Thus any latch can be set up by means of only two characters allowing much faster operation. The DAC data should only be changed when its output is not directed to any destination otherwise the destination will receive the change noise.


References -1. Newchapel Observatory & Natural Sciences Centre. Newchapel, Stoke on Trent ST7 4PT.

PARTS LIST

IC1	UART IM6402 or AY 31015
IC2	CMOS Timer TLC555
IC3	FET OP-AMP CA3140
IC4	CMOS Quad NAND 4011
D1,D2	Diode 1N4148
R1,R4,R7,R9	3k3
R2,R3	470R
R5,R6	10k
RV1	10k Square 22 turn Cermet preset
C1,C3	100nF radial Metalized Polyester film
C2	2200pF Polystyrene

All resistors are Metal Film 0.6W.
PCB Connector is DIN 41612 Indirect Card-frame connector right-angled-plug 32way.

Photo-Copies

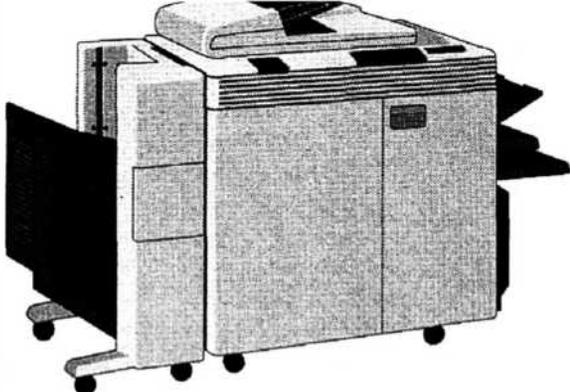

ETI has been published for over 20 years and in thistime a great many interesting features and valuable projects have graced it's pages. Although back numbers are available for only the past 12 month's issues we can supply photo copies of any individual article ever published in ETI.

Photocopies cost £ 2.00 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £ 2.00.

PCB foil patterns (where published) and any errata are included with all photocopies as applicable.

Please supply photocopies of the following articles from ETI (Complete in BLOCK CAPITALS):

MonthYearPage (if known)

Title.....

MonthYearPage (if known)

Title.....

MonthYearPage (if known)

Title.....

I enclose a cheque/postal order made out to ASP Ltd. to the value of £ 2.00 per photocopy ordered.

Total remittance £ Date

Name


Address

.....Postcode


Send the completed form and your remittance to:
ETI Photocopy Service, Argus House, Boundary Way, Hemel Hempstead, Hertfordshire, HP2 7ST

PCB Foils

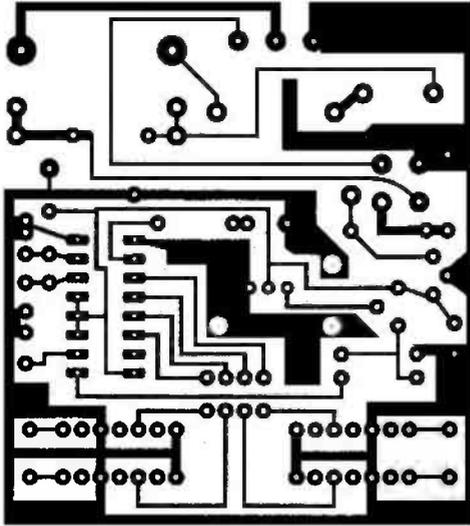
The PCB foil patterns presented here are intended as a guide only. They can be used as a template when using tape and transfer for the creation of a foil.




Infra-red receiver

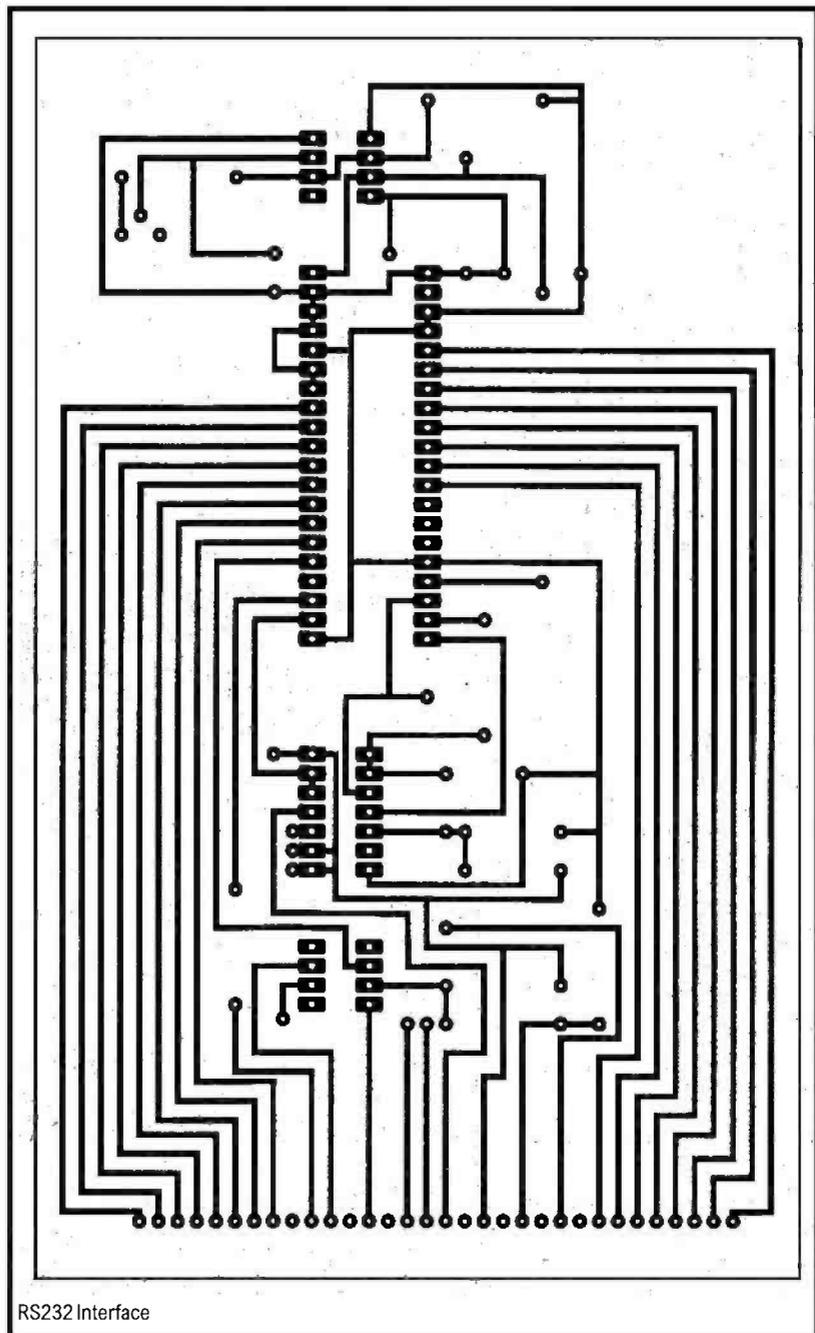

RS232 Interface

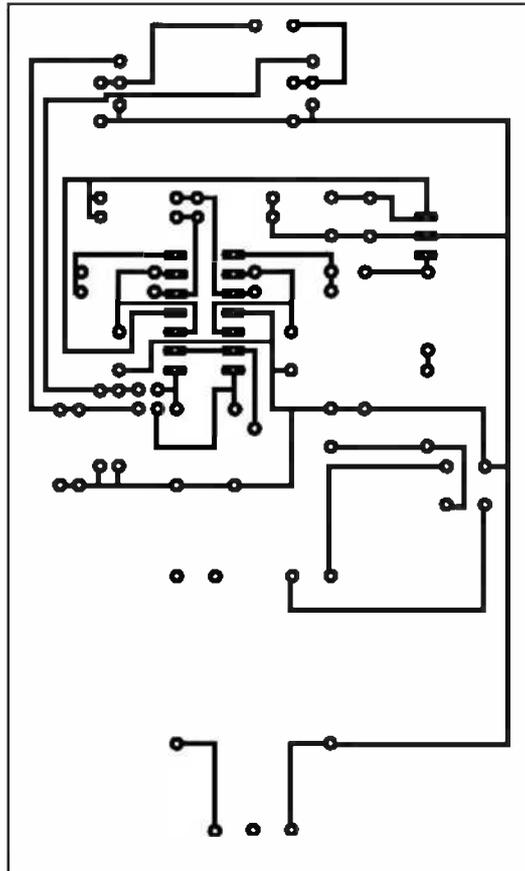

Fading Festoonery

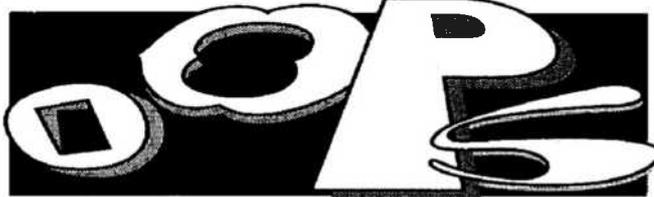

Automatic Audio Response Measuring System-Dec '92
The following section was missed from the article, we
reproduce it here:

Buylines

The address for all orders is:
Ralph Mantel,
Pipinstr.23
W-4790 Paderborn,
Germany.

The prices for the UK in pound sterling are:
Compensated measuring microphone with cable
and plug £ 39 Software £ 29
PCB with printed overlay £ 19
All three items together to the favorable price of
£ 79 (saving £ 8). Complete kit or ready build
PCB please enquire.

TELEPHONE
ORDERS
may be
made on
(0442) 66551



PCB Service January

Price
(inc.
VAT)
C £1.80
D £2.50
E £3.25
F £4.00
G £4.75
H £5.50
J £6.62
K £7.20
L £8.80
M £10.60
N £13.10
O £15.80
P £17.90
Q £21.80
R £23.90
S £25.90
T £29.00
U £32.20
V £35.80
W £37.90

- E9212-2 Communications Link by RS232 L**
E9301-2 Fading Festoonery G
E9301-FC Infra-Red Receiver F

PCBs for the remaining projects are available from the companies lists in Buylines.
 Use the form or a photocopy for your order. Please fill out all parts of the form. Make sure you use the board reference numbers. This not only identifies the board but also tells you when the project was published. The first two numbers are the year, the next two are the month.
 - Terms are strictly payment with order. We cannot accept official orders but we can supply a proforma invoice if required.
 Such orders will not be processed until payment is received.

- E9108-2 Model Speed Controller-Main Board F
 E9108-3 Model Speed Controller-Power Supply F
 E9109-1 Geiger Counter E
 E9109-2 Hemisync Waveform Generator Board G
 E9109-3 Hemisync Pulse Generator Board F
 E9109-4 Hemisync Power Supply Board C
 E9109-5 Nightfighter Main Processor Board O
 E9110-1 Freeze Alarm E
 E9110-2 Document Saver E
 E9110-3 Prototype Designer J
 E9110-4 Nightfighter - Sound to Light (2 sided) L
 E9110-5 Nightfighter - Ramp Generator Board F
 E9110-6 Nightfighter - Cyclic Crossfade (2 sided) M
 E9110-7 Nightfighter - Strobe Board (2 sided) J
 E9110-8 Nightfighter - 8 Channel Triac Board N
 E9111-1 Digital Code Lock L
 E9111-2 Switched Mode Power Supply E
 E9111-3 Nightfighter Mode Selection (2 sided) J
 E9111-4 Nightfighter - Display Board (2 sided) M
 E9111-5 Nightfighter - Bass Beat Trigger (2 sided) L
 E9111-6 Nightfighter - Sequence Select (2 sided) H
 E9111-7 Nightfighter - Master Controller PSU K
 E9111-8 Nightfighter - Output Switch (2 sided) M
 E9112-1 Nightfighter Sensor Switch Master Control (2 sided) L
 E9112-2 Nightfighter Sensor Switch Channel Control (2 sided) L
 E9112-3 Nightfighter Sensor Switch Sound Trigger H
 E9112-4 Nightfighter Connector Board F
 E9112-5 Nightfighter Sensor Switch PSU K
 E9112-6 Nightfighter 8-Channel Input Interface (2 sided) P
 E9112-7 Power On and Overload Regulator P
 E9201-1 Laboratory Power Supply F
 E9201-2 Test Card Generator Board M
 E9201-3 LED Star (2 sided) L
 E9201-4 Enlarger Timer Main PCB (2 sided) N
 E9201-5 Enlarger Timer Selector Board (2 sided) K
 E9201-6 Enlarger Timer Switch PCB E
 E9203-1 MIDI Switcher - Main Board L
 E9203-2 MIDI Switcher - Power Supply E
 E9203-3 Sine Wave Generator (surface mount) F
 E9204-1 Auto Car Lights F
 E9205-1 Bat Detector E
 E9205-2 Pond Controller F
 E9206-FC Stereo amplifier G
 E9206-2 Xenon flash trigger Main Board J
 E9206-3 Xenon flash trigger Flash Board F
 E9206-4 Scanner for audio generator D
 E9207-1 Improved Rear Bike Lamp D
 E9207-2 Mini Baby Bug Monitor C
 E9207-3 Ultrasonic Audio Sender (2 boards) H
 E9207-4 Camera Add-on unit (4 boards) O
 E9207-5 AutoMate 5V/48V Mixer power supply J
 E9207-6 AutoMate Precision 17V power supply J
 E9207-FC Surround Sound Decoder F
 E9208-1 Dynamic Noise Limiter F
 E9208-2 Touch Controlled Intercom (2 boards) H
 E9208-3 MIDI Keyboard K
 E9208-FC Battery charger F
 E9209-1 Intercom for light aircraft H
 E9209-2 Alarm protector C
 E9209-3 Temperature controller M
 E9209-FC 45W Hybrid power amp F
 E9210-1 Universal I/O Interface for PC (2 Sided) N
 E9210-2 Rapid Fuse Checker E
 E9210-3 Heartbeat/Audio Listener E
 E9210-FC Wizards Hat E
 E9211-1 Electronic Die E
 E9211-FC Car Alarm F
 E9212-1 Digital Circuit Tester F
 E9212-FC Mains Inverter E

ETI PCB SERVICE, READER'S SERVICES,
ARGUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD HP2 7ST

Please supply:
Quantity. Ref. No. Price Code Price Total Price

Post & Packing £ 0.75

Total Enclosed £

Please send my PCBs to:

Name

Address

.....Postcode

CHEQUES SHOULD BE MADE PAYABLE TO ASP Ltd.



ELECTRONICS
TODAY INTERNATIONAL

Project Index 1992

AUDIO	MONTH	PAGE		MONTH	PAGE
Acousdix 20W amplifier	February	51	Errata	November	59
Audio pre-amp, High quality	April	16	Intercom for light aircraft	September	13
Part 2	May	31	LED Rear bike light	June	20
AutoMate Audio			LED rear bike lamp - Improved	July	13
mixing desk Part 1	April	38	Mains Inverter 20/50/100W	December	16
Part 2	May	17	Mains switched timer	February	32
Part 3	June	46	Errata	June	72
Part 4	July	58	MIDI Keyboard	August	40
Part 5	August	52	Errata	December	61
Part 6	September	60	MIDI switch MIDIrouter/exchange	March	16
Part 7	October	38	Errata	June	72
Part 7b	November	74	Mini Baby bug monitor	July	47
Part 8	December	23	Photographic Enlarger timer	January	31
Hybrid Line Amp	December	36	Pond level controller	May	37
Hybrid Power Amp 45W	September	26	Errata	July	73
Intercom for light aircraft	September	13	Power supply Laboratory	January	16
Stereo IC Amplifier	June	26	RS232 Interface	December	48
Surround sound decoder	July	26	Rapid fuse checker	October	12
Aerial tuner unit	October	52	Star of the Month - LED Christmas		
Errata	December	61	decoration	January	44
Alarm protector unit	September	36	Sine wave generator	March	52
Audio Pre-amp,High quality	April	16	Scanner for sine wave generator	June	22
Part 2	May	31	Smart Battery charger	August	26
Auto Car light control	April	38	Errata	September	78
Auto protection	November	16	Stereo IC amplifier	June	26
AutoMate audio mixing desk Part 1	April	22	Errata	July	73
Part 2	May	17	Surround sound decoder	July	26
Part 3	June	46	Temperature controller	September	54
Part 4	July	58	Test-card and test pattern		
Part 5	August	52	generator Part 2	January	52
Part 6	September	60	Test-card update	May	29
Part 7	October	38	Errata	March	61
Part 7b	November	24	Touch Intercom	August	13
Part 8	December	23	Ultra-sonic audio sender	July	50
Automatic audio response			Universal Interface for PC Part 1	October	16
measuring system	November	32	Part 2	November	46
Part2	December	42	Window opener	September	49
Bat detector	May	42	Xenon flash trigger	June	38
Camera add-on unit	July	32	Errata	July	73
Digital circuit tester	December	32			
DIY Aerial system	August	48	Test gear		
Dynamic noise limiter	August	30	Automatic audio response		
Errata	October	62	measuring system	November	32
Earth charge recorder Part 1	March	42	Part 2	December	42
2	April	52	Digital circuit tester	December	32
Electronic die for board games	November	52	Frequency meter range extender	June	36
Flashy wizard's hat	October	48	Laboratory power supply	January	16
Frequency meter range extender	June	36	Rapid Fuse Checker	October	12
Errata	July	73	Sine-wave generator	March	52
Heartbeat monitor	October	30	Scanner for sine-wave generator	June	22
Hybrid line amplifier	December	36	Test-card and test pattern		
Hybrid Power amplifier 45W	September	26	generator Part 2	January	52

BARGAINS - Many New Ones This Month

THIS MONTH'S SNIP is a 250 Watt Toroidal Transformer which has tapped main input and 3 secondaries: 230v 1amp 20v and 6v but if these voltages are not quite what you want it is very easy to add an extra winding, 4 turns adds or subtracts 1 volt. You can also use this as a 250 watt isolation. Price only £10 but it's heavy so please add £2 carriage if not collecting. Order Ref. 10P97.

ANOTHER SNIP extra lightweight stereo headphones. Superior sound quality as these were made for a world famous airline. Adjustable headband makes these extra comfortable and they come complete with washable foam earpieces. Suitable for use with all types of cassette players and radios, good long lead terminating with 3.5mm jack plug. Yours for only £1 per pair, Order Ref. 878.

6-12V AXIAL FAN is a Japanese-made 12v DC or battery operated, brushless axial fan. 93mm square, its optimum is 12 bit it performs equally well at only 6v and its current then is only 100mA so it could be made into a hand-held dry battery-operated cooler. Or, on your desk operated by a p.s.u. or in the car using the lighter socket. Snip price only £4, Order Ref. 4P65. Mains power unit to operate this at variable speeds, £2, Order Ref. 2P3.

F.M. CORDLESS RADIO MIKE hand-held battery-operated professional model, has usual shaped body and head and is tuneable to transmit and be picked up on the F.M. band of any radio. Yours for only £8.50, Order Ref. 8.5P1

4 MORE SPEAKERS:

Order Ref. 1.5P11 is Japanese made 6", 8ohm, rated at 12W max. This is a very fine preproducer. The makers are SANYO. Yours for £1.50

Order Ref. 900 is another Far East made 6", 4ohm, 12W max. speaker. Very nicely made, using Japanese Hitachi tools and technique, only £1.

Order Ref. 896 is 6", 6ohm, 10W, exceptionally good sounder and yours for only £1.

Order Ref. 897 is another 8ohm speaker rated at 5W but its unusual feature is that it has a built-in tweeter. Still only £1.

MULTI-CORE CABLES all with 8A 230V cores so suitable for disco and other special lighting effects. With earth cable woven screen and thick pvc outer. 3 core, 30p per metre, 16 core 50p per metre, 18 core, 80p per metre, 25 core, £1 per metre and 36 core, £1.50 per metre.

ULTRA THIN DRILLS Actually 0.3mm. To buy these regular cost a fortune. However, these are packed in half dozens and the price to you is £1 per pack, Order Ref. 797B.

YOU CAN STAND ON IT! Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools. Internal size approx. 10 1/2" x 4 1/2" x 6" high. These are complete with snap closure lip and shoulder-length carrying strap. Taken from used equipment but in good condition, price £2. Order Ref. 2P283B.

BUILD YOUR OWN NIGHT LIGHT, battery charger or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket. We have two cases, one 3 1/2" x 2 1/2" x 1 1/2" deep, £1 each Order Ref. 845. The other one is 2 1/2" x 2 1/2" x 1 1/2" deep, 2 for £1, Order Ref. 565.

SAFETY LEADS curly coil so that they contract but don't hang down. Could easily save a child from being scalded. 2 core, 5A, extends to 3m, £1, Order Ref. 846, 3 core, 13A extends to 1m, £1 each, Order Ref. 847, 3 core, 13A, extends to 3m, £2 each, Order Ref. 2P290.

POWER SUPPLY WITH EXTRAS mains input is fused and filtered and the 12V dc output is voltage regulated intended for high class equipment, this is mounted on a PCB and also mounted on the board but easily removed, are 2 12V relays and a Piezo sounder. £3, Order Ref. 3P80B.

ULTRA SONIC TRANSDUCERS 2 metal cased units, one transmits, one receives. Built to operate around 40KHz. Price £1.50 the pair, Order Ref. 1.5P/4.

100W MAINS TRANSFORMER normal primary 20-0-20 at 2.5A, £4, Order Ref. 4P24. 40V at 2.5A, £4, Order Ref. 4P59. 50V ar 2A, £4, Order Ref. 4P60.

PHILIPS 9" HIGH RESOLUTION MONITOR black & white in metal frame for easy mounting, brand new still in maker's packaging, offered at less than price of tube alone, only £15, Order Ref. 15P1.

16 CHARACTER 2-LINE DISPLAY screen size 85mm x 36mm, Alphanumeric LCD dot matrix module with integral micro processor made by Epson, their Ref. 16027Ar, £8, Order Ref. 8P48.

INSULATION TESTER WITH MULTI METER internally generates voltages which enables you to read insulation directly on megohms. The multimeter has four ranges, AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each yours for only £7.50, with leads, carry case £2 extra, Order Ref. 7.5P/4.

MAINS 230V FAN best make "PAPST" 4 1/2 square, metal blades, £8, Order Ref. 8P8.

2MW LASER Helium neon by Philips, full spec. £30, Order Ref. 30P1. Power supply for this kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well £18, Order Ref. 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £69, Order Ref. 69P1.

1/3 HP 12V MOTOR — THE FAMOUS SINCLAIR C5 brand new, £15, Order Ref. 15P8.

SOLAR CHARGER holds 4AA nicads and recharges these in 8 hours, in very neat plastic case, £6, Order Ref. 6P3.

FERRITE AERIAL ROD 8" long x 3/8 diameter, made by Mullard. Complete with 2 coil formers. 2 for £1, order Ref. 832B.

AIR SPACED TRIMMER CAPS 2-20 pf ideal for precision tuning UHF circuits, 4 for £1, Order Ref. 818B.

FIELD TELEPHONES just right for building sites, rallies, horse shows, etc., just join two by twin wire and you have two way calling and talking and you can join into regular telephone lines if you want to. Ex British Telecom in very good condition, powered by batteries (not included) complete with shoulder slung carrying case, £9.50, Order Ref. 9.5P/2.

MAINS ISOLATION TRANSFORMER stops you getting "to earth" shocks. 230V in and 230V out. 150 watt upright mounting, £7.50, Order Ref. 7.5P/5 and a 250W version is £10, Order Ref. 10P79.

LIMITED SUPPLY ITEMS

are only described in our newsletter. Many appear in our current issue. If you order something this month you will receive this and the next three issues posted to you free of charge.

MINI MONO AMP on PCB. Size 4" x 2" with front panel, loading volume control and with spare hole for switch or tone control. Output is 4 watt into 4 ohm speaker using 12V or 1 Watt into 8 ohm using 9V. Brand new and perfect, only £1 each. Order Ref. 495.

AMSTRAD POWER UNIT 13.5V at 1.9A enclosed and with leads and output plug, normal mains input, £5, Order Ref. 6P23.

ATARI 65XE at 65K this is quite powerful, so suitable for home or business, unused and in perfect order but less PSU, only £19.95, Order Ref. 19.5P/5B.

80W MAINS TRANSFORMERS two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref. 3P106 the other 40V 2A, Order Ref. 3P107, only £3 each.

PROJECT BOX is approx 8" x 4" x 4 1/4" metal sprayed grey, louvered ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref. 3P74.

12V SOLENOID has good 1" pull or could push if modified, size approx 1 1/2" long x 1" square, £1, Order Ref. 232.

500V BRIDGE MEGGER developed for GPO technicians the Ohmeter 18B is the modern equivalent of the bridge megger. 9V battery operated, it incorporates a 500V generator for insulation testing and a null balance bridge for very accurate resistance measurement. Ex B.T. in quite good condition with data & tested. Yours for a fraction of the original cost, £45, Order Ref. 5P167.

15W 8 OHM 8" SPEAKER & 3" TWEETER made for discontinued high quality music centre, gives real hi-fi, and only £4 per pair, Order Ref. 4P57.

3V SOLAR PANEL price £3, Order Ref. 5P189.

SOLAR ENERGY EDUCATIONAL KIT an ideal present for electronics students. It shows how to make solar circuits and electrical circuits, how to increase the voltage current, how to use solar power to work a radio, calculator, cassette player and to charge nicad batteries. The kit comprises 8 solar cells, one solar motor, fan blades to fit motor and metal frame to hold it to complete a free-standing electric fan. A really well written instruction manual makes this a lovely little present. Price £8, Order Ref., 8P12B

BT TELEPHONE LEAD 3m long and with B.T. flat plug ideal to make extension for phone, fax, etc. 2 for £1, Order Ref. 552.

WATER PUMP very powerful with twin outlets, an ideal shower controller, mains operated, £10, Order Ref. 10P74. Ditto but with a single outlet, same price & order ref. Please specify which one you require.

0-1MA FULL VISION PANEL METER 2 1/2" square, scales 0-100 but scale easily removed for re-writing. £1 each, Order Ref. 756.

PROJECT BOX a first-class, Japanese two-part moulding size 95 x 66 x 23mm. held together by 2 screws, take a battery and a PCB and is ideal for many projects. To name just a few, the washer bottle monitor, the Quicktest and the model railway auto signal, described in September's issue of E. E. This is nicely finished and very substantial. You get 2 for £1, Order Ref. 876.

HOLD IT MAGNETIC BASE embedded is a circular metal shallow disc, diameter approx. 65mm (2 1/2"), is the most powerful magnet. We have yet to find anyone who can remove this with his fingers. Ideal for adding extra shelves inside a metal case or

to glass without drilling. Its uses, in fact, are innumerable. Price £2 each, Order Ref. 2P296.

ELECTRONIC BUMP & GO SPACESHIP sound and impact controlled responds to claps and shouts and reverses or diverts should it hit anything! Kit with really detailed instructions, will make ideal present for budding young electrician. Should be able to assemble but you may have to help with the soldering of the components on the PCB. Complete kit, £8.96, Order Ref. 9P9.

OPD DUAL MICRO DRIVE UNIT this is a twin unit, each unit having its own motor, record/playback head and PCB with all electronics. In addition to being a direct replacement in the OPD, this can also be used with the Spectrum or the QL. We have a copy of the procedure necessary and will gladly supply a photostat of this if you require it when you purchase the unit. The price is £5, Order Ref. 5P194.

12V 2A MAINS TRANSFORMER upright mounting with mounting clamp. Price £1.50, order Ref. 1.5P8.

AM/FM MAINS RADIO CHASSIS with separate LCD module to display time and set off alarm. This is complete with loudspeaker but it is not cased. Price £3.50. Order Ref. 3.5P5.

2, 3 AND 4 WAY TERMINAL BLOCKS the usual grub screw types. Parcel containing a mixture of the 3 types, giving you 100 ways for £1, Order Ref. 875.

12/24V DC SOLENOID constructed so that it will push or pull, plunger is a combined rod and piston. With 24v is terrifically powerful but is still very good at 12v and, of course, with any intermediate voltage with increasing or decreasing

power. It has all the normal uses of a solenoid and an extra one, if wired in series with a make and break, this could be a scribing tool for marking plastics and soft metals. We welcome other ideas and will give a £25 credit voucher for any used. Price £1, Order ref. 877.

2M 3-CORE LEAD terminating with flat pin instrument socket, £1, Order Ref. 879. Ditto but with plug on the other end so that you could use this to extend an instrument lead. £1.50, Order Ref. 1.5P10.

ASTEC 135 WATT P.S.U.

230v or 115v input with outputs of +12v at 4A — +5v at 16A and -12v at 1/2A completely enclosed in plated steel case.

Brand new and yours for £9.50

JUST ARRIVED


Infra Red Receiver Controller made by Thom to channel switch their T.V. receivers.

Mounted on panel with luminous channel indicator, mains on/off switch, leads and plugs all yours for £2, Order Ref. 2P304

Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3.00 post and packing. Order over £25.00 post free. You can order until 9pm Mon-Fri on 430380.

M & B ELECTRICAL SUPPLIES LTD
Boundary Road, Hove, Sussex BN3 4EH
Telephone (0273) 430380
Fax or phone (0273) 410142

OLYMPIA LONDON W14

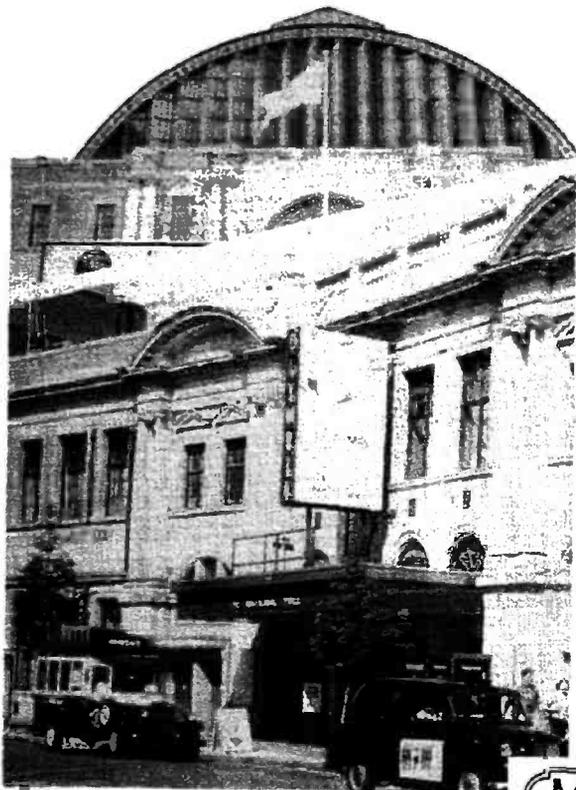

Easy to find

- and, the parking is half price!

How to get to Olympia - the new venue for the 1993

Model Engineer Exhibition

The Olympia Grand Hall is situated in Olympia Way off Hammersmith Road, Kensington W14.

It is very well served by all forms of public transport and easy to reach by road and rail as follows...


● **Buses:** Local LT bus routes numbers 9A, 10, 27, 28 stop outside Olympia in Hammersmith Road. Green Line routes also pass the door.

● **Underground:** District Lines tube trains run from Earls Court/High Street Kensington to Olympia's own station opposite the Grand Hall entrance. This is a 15 minute service.

● **Half Price Car Parking.** For the duration of the exhibition, rates for the Olympia multi-storey car park will be reduced to half price - £5 per day - and until the 6th of January the Earls Court, Seagrave Road car park will also be at half price - £5.

Olympia is one stop on the tube train from Earls Court. On the opposite side of the railway to Olympia, a proportion of Russell Road car park is available at £4 per day. There are, of course, numerous other car parks in the vicinity.

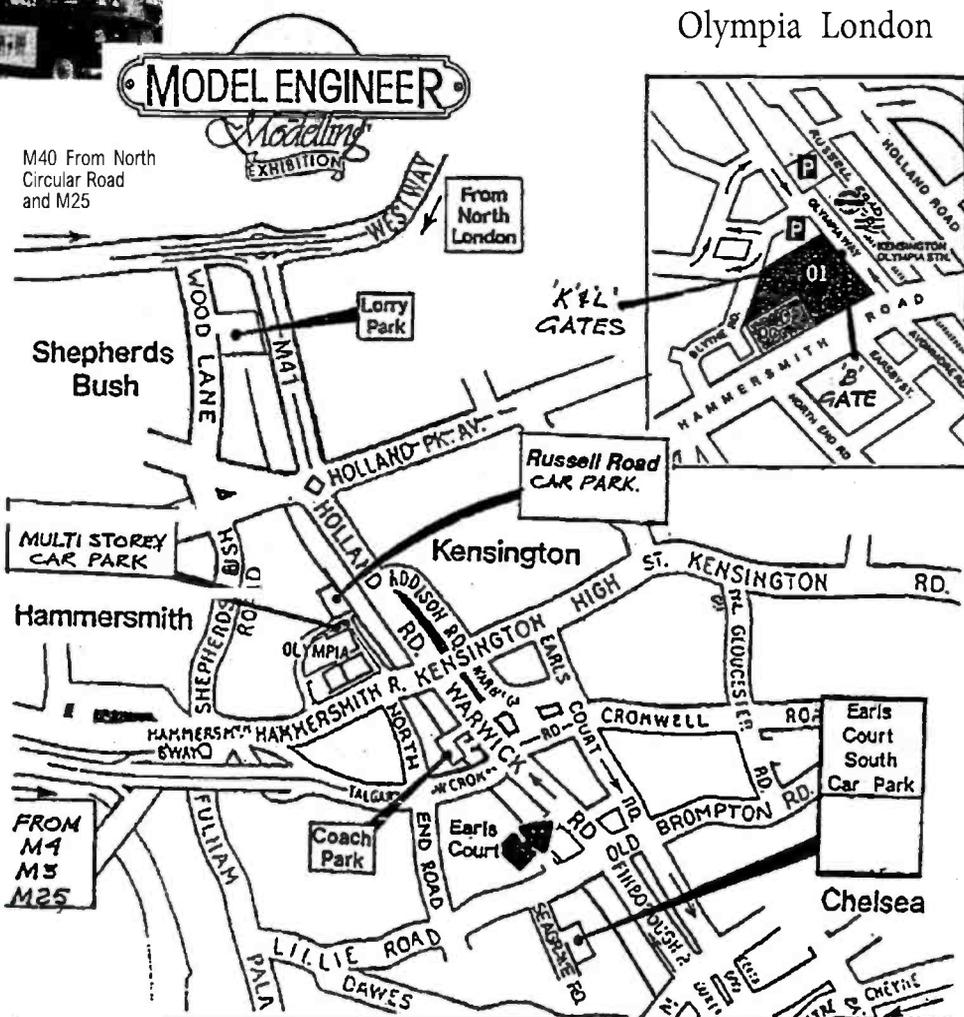● **Local facilities:**
 Nat West Bank: Hammersmith Road, opposite Olympia 2.
 Post Office: Blythe Road, Opposite K Gate.



M40 From North Circular Road and M25

From North London

Olympia London

MODEL ENGINEER

Modelling EXHIBITION

MODEL ENGINEER EXHIBITION AT OLYMPIA January 1st - 9th 1993

INTERNATIONAL
62nd

NOW AT OLYMPIA

MODEL ENGINEER

AND
Modelling
EXHIBITION

1st JAN - 9th JAN 1993
or let the *train* take the strain...

AMPLE CAR
PARKING AT
HALF PRICE

Mainline &
Underground
Stations
Adjacent

Don't miss the 62nd Model Engineer Exhibition

For the first time at Olympia come and see hundreds of competition entries on display as well as scale model boats, aircraft, cars, locomotives and over 100 trade exhibitors

Opening Times

10am-6pm every day except Thursday 7th January 10am-8pm

Catalogue available from 4th December **PRICE £1.60**

Competition Entry Forms now available - Loan Entry Exhibits welcome.

Admission Prices



Adults £5.00

Senior Citizens £4.00

Children £2.00

Ample Car Parking £5.00

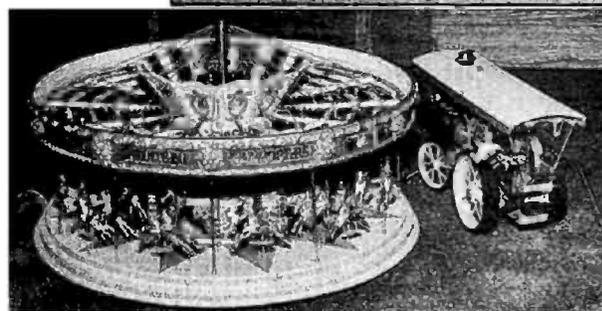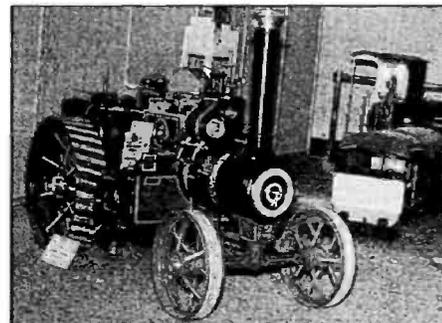Olympia, Grand Hall is easily accessible by Road, Rail, Underground and Bus.



ARGUS SPECIALIST EXHIBITIONS

Argus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST Tel: 0442 66551

Argus Specialist Publications and Hilton Hotels are offering special rates for the duration of the Exhibition.

The Clive Hotel	Small & welcoming close to Hampstead and it's Heath	£23.00
The Sherlock Holmes	Near Madame Tussauds & London Zoo	£29.75
The Regents Park Hilton	Near Regents Park and overlooking Lords Cricket ground	£28.75
Plaza on Hyde Park	Close to Victoria and Albert & Kensington Palace	£27.60
London Olympia Hilton	On Kensington High Street, ideal for shopping	£28.75
Kensington Hilton	Close to London's West End	£36.39
The Langham Hilton	Situated in London's West End and close to Oxford Street	£69.00
London Hilton on Park Lane	In the heart of Mayfair and its elegant shopping district	£69.00

Prices are for each guest each night for Twin/Double Room (£14 single supplement) and include Continental breakfast, (except The Langham Hilton and London Hilton on Park Lane which include English breakfast), private bath/shower, tea/coffee making facilities and VAT. There is a supplement of £5.50 for full English breakfast.

HILTON

Booking Form - International Model Engineer & Modelling Exhibition

Make it a Model Stay

Name Address

..... Postcode Tel No

Accommodation required: Double Twin Single No in party No of nights

Choice of hotel Dates required

Payment by: cheque Access Visa Diners AmEx My Credit Card No Expiry date

There will be a return coach service direct to the Exhibition at a cost of £6.00 per person on the dates shown. Please tick if required: January 2nd January 9th

Return booking form to: Heidi Ross, CRO, Hilton International, PO Box 137, Watford, Herts WD1 1DN. Tel: (0923) 238877.

Olympia, Hammersmith Road, Kensington W.



1st-9th January 1993

ADVANCE BOOKINGS

Adults at £ 4.50 No.....
 Senior Citizens at £ 3.50 No.....
 Children (5-16) at £ 2.00 No.....

PARTY BOOKINGS (for groups of 10 or more)

Adults at £ 4.25 No..... Amount £
 Senior Citizens at £ 3.25 No..... Amount £
 Children (5-16) at £ 2.00 No..... Amount £
 1 free ticket per 25 people

SCHOOL BOOKINGS (for groups of 10 or more, one teacher free per 10 pupils)

Teachers at £ 4.25 No..... Amount £
 Pupils at £ 2.00 No..... Amount £
 Teachers-free of charge No.....

Total enclosed £

ADVANCE BOOKING INFORMATION

I enclose cheque/P.O. for the total amount stated above, together with an S.A.E. for return of tickets.

Cheques made payable to Argus Specialist Exhibitions (AT) and sent to Argus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST. Tel: 0442 66551

Name

Address

.....


.....

Closing date - December 7th 1992

DYNAUDIO[®]

AUTHENTIC FIDELITY

Dynaudio is considered one of the most distinguished manufacturers in audio. By means of untiring and successful research and exceptional solutions to questions of concept, design and construction Dynaudio has acquired this excellent reputation, yet success has not altered their independence and single minded concentration on creating products of the highest quality. Dynaudio continues to search for solutions to the basic problems of loudspeaker engineering and then puts these solutions to the test in loudspeakers of their own design. This is especially true for chassis technology. They have

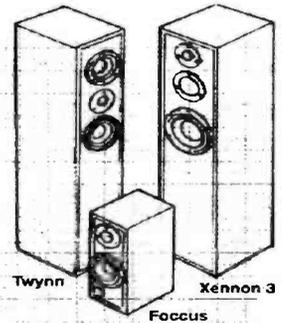

There are three new speaker kits available from Wilmslow Audio, each kit contains all necessary components to build a superb pair of speakers. 18mm M.D.F. flat pack cabinets are also available.

	Plus Kit	Carr/Ins	Total Kit	Carr/Ins
Gemini	£590.00	£10.00	£645.00	£15.00
Foccus	£360.00	£10.00	£395.00	£15.00
Twynn	£425.00	£10.00	£510.00	£18.00
Xennon 3	£675.00	£10.00	£750.00	£20.00
Finale	£1200.00	£15.00	£1600.00	£25.00

Wilmslow Audio

Dept. ET1
 Wellington Close,
 Parkgate Trading Estate
 Knutsford, Cheshire
 WA16 8DX
 Tel: (0565) 650605
 Fax: (0565) 650080
 Telephone credit card orders welcome

DIY Speaker catalogues £2.00 4 colour reproduction rooms available.
 post free (export £3.50)

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX • 031 667 2611

The supplier to use if you're looking for
 A WIDE RANGE OF COMPONENTS AIMED
 AT THE HOBBYIST
 COMPETITIVE VAT INCLUSIVE PRICES
 MAIL ORDER generally by
 RETURN OF POST
 FRIENDLY SERVICE

Open: Monday-Thursday 9.15-6.00 Friday
 9.15-5.00 Saturday 9.30-5.00

BADGER BOARDS

Printed Circuit Boards

Prototype-Singles-Multiple runs. Minimum charge £15.00. Artwork, Plotting from Schematic to final board layout. Send S.A.E. now for Catalogue of Kits-Boards-Projects available. Many magazine boards produced for individual customers.

Dept: HRT 87, Blackberry Lane, Four Oaks, Sutton Coldfield, B74 4JF • 021-353 9326

PROFESSIONAL SERVICES

We offer a full R.F. DESIGN SERVICE from design and development to prototype. Our extensively equipped laboratory with screened room is available for EMC PRE-TESTING to ensure products comply with the EC Directive on emissions and susceptibility.

R. N. Electronics EMC

1 ARNOLDS COURT, ARNOLDS FARM LANE, MOUNTNESSING
 ESSEX CM13 1UT. Tel: 0277 352219 Fax: 0277 352968

ETI Classified



Lucy Hughes
0442 66551

Send your requirements to:
ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 60p per word (+VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£15.00 per single column centimetre (+VAT) } Per
Electromart £24.00 (+VAT) } Insertion



Ring for information on series bookings/discounts.
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60	OUTPUT 0-280V	Price	P&P
0.5KVA 2.5 amp max		£29.00	£4.66
		(£39.54 inc VAT)	
1KVA 5 amp max		£37.40	£6.25
		(£51.29 inc VAT)	
2KVA 10 amp max		£54.00	£7.80
		(£72.62 inc VAT)	
3KVA 15 amp max		£71.50	£7.80
		(£93.18 inc VAT)	
5KVA 25 amp max		£128.60	

Buy direct from the Importers. **Kaestner Prices** in the country (Plus Carriage)

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-450LWAT & AUTO

110-240V Auto transfer either cased with American socket and main lead or open frame type. Available for immediate delivery.
ULTRA VIOLET BLACK LIGHT FLOURESCENT TUBES

4R 40 watt £12.00 (cables only)	(£14.10 inc VAT)
2R 20 watt £7.44 + £1.25 p&p	(£10.21 inc VAT)
13n 10 watt £5.80 + 75p p&p	(£7.70 inc VAT)
12n 8 watt £4.80 + 75p p&p	(£6.52 inc VAT)
8n 4 watt £3.95 + 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT
For either 6n, 8n or 12n tubes £5.50 + £1.15 p&p (£7.81 inc VAT)
For 13n tubes £6.00 + £1.35 p&p (£8.64 inc VAT)



400 WATT UV LAMP £42.89 inc VAT
160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB
Available with 8n or 8S fitting, price inc VAT 8 p&p and VAT £25.65

SAVE POUNDS. Build your own forged bank note detector. Will detect counterfeit amongst quantity of notes. Complete kit & parts less case for 240 volt AC OP inc. 6" UV black light tube/ starter and holder. Pair Bi-pin leads circuit instruction.
Total price P&P VAT £13.06

SUPER HV LIGHT STROBE KIT
Designed for Disco, Theatrical use etc.
Approx. 16 joules. Adjustable speed £50.00 + £3.00 p&p (£82.28 inc VAT)
Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT).
SAE for further details including Hy-Light and industrial Strobe Kits

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 6BB
FAX 081 995 0549 081-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

COOKE INTERNATIONAL TEST INSTRUMENTS

Marconi 6600A Microwave Sweep Oscillator with 6611 I.0 - 2.0 GHz Plug In and 6651 26.5 - 40.0 GHz Plug In £1500.00
H.P. 4204A Oscillator 10Hz - 1MHz £160.00
SOLARTRON 4601 Frequency Synthesizer SK Hz - 180 MHz AM/FM and Sweep £320.00
Marconi TF 1370A RC Oscillator 10Hz - 10MHz Sine, Square Wave £160.00
Tequipment D61 Dual Trace Portable Scope DC-15MHz £95.00
Marconi TF 1245 Magnification "Q" Meier £155.00
Marconi TF 1246 Oscillator For "Q" Meier £95.00

Many more items available. Original W/Shop manuals for sale send S.A.E. for lists. Computers, monitors etc. In stock. Phone for details.

All prices exclude VAT & Carriage. Open Mon-Fri 9am-5pm Saturday by arrangement.
Cooke International, Units 4/5 Fordingbridge Site, Main Road, Barnham, Tel: 0243 545111 Bognor Regis West Sussex PO22 0EB. Fax: 0243 542457

"BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit. Internally in excellent condition. Designed primarily to select a precise controllable amount of fluid from a medical syringe (letter not supplied). Contains the following removable components: Dual Micro Processor Boards and PROMS. Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends. Audible warning.

These are sold for the dismantling of the except one quality components. Request no Circuits available. Ridiculously low price: £18.00 + £4.00 postage. (£23.90 incl VAT)

WIDE RANGE OF XENON FLASH TUBES

12VD C. GEARED MOTO
2V D.C. Reversible precision-built Motor Output speeds no load approx. 12V 20 rpm, 9V 20 rpm, 6V 12 rpm. Will work at lower voltages and still retain a reasonable torque. Ideal for robotics etc. Size: L 10mm, W 29mm, H 39mm. Shell: 3mm dia x 10mm long. Price: £8.00 + 60p p&p (£10.00 inc VAT)

TORIN CENTRIFUGAL BLOWER
230V AC. 2.800 RPM. 0.9 amp. 130mm diameter impeller outlet 63 x 37mm. Overall size 195 x 160 x 100mm long. Price £17.50 + £2.50 p&p (£23.50 inc VAT)

SOUO STATE RELAY
1 amp in 240V AC. when mounted on suitable Heat-sink. Can be driven from TTL or Computer output between 3-10V D.C. Size: 24mm x 17mm x 16mm high. Using centres 30mm (T0-3). Price: £3.00 + 40p p&p (£4.00 inc VAT)

GEARED MOTORS
1 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT 8 p&p £23.50.

SOUO STATE UNIT
input 220/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec. 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

12V D.C. BILGEPUMPS
Buy direct from the Importers.
500 GPH 15ft head 3 amp £18.21
1750 GPH 16ft head 9 amp £31.72
PRICE INCLUDE P&P & VAT

EPROM ERASURE KIT
Would you own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes:
12n 8 watt 2537 Argon Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and secure £14.00 + £3.00 (18.00 inc VAT)

Metal detector boards with data, has tuner, mode, discriminate, headphone jack, on/off/volume and push button facilities £7.95 ea
Dictaphone cassette, mech/record erase playback heads, 6V solenoid, motor, hall-effect switch £2.00 ea
35mm Camera returns with Auto Flash/Wind on etc. £8 ea or 2 for £10
TV/Printer stands £2.95 ea
Bioc-Vero Easiwire construction kit £4.95 ea
Cabinet Speakers from Ni-cam TV-Video use £14.95 pair
PCB with Lithium Battery, 2732, 34 IC's + Transisto Fuse, Crystal, R's + C's £4.95 ea
TTL/CMOS short circuit snooper £4.95
Dot matrix LCD 10x2 lines £3.75 ea with Dots £4.95
40 character x 1 line dot matrix display with data £14.95 ea
2 digit 16 segment VF display with data £2.95 ea
4 digit intelligent dot matrix display £8.00
17 segment VF display with driver board and data £2.99 ea
8 digit liquid crystal display £1.75 ea
4 digit LCD with 7211 driver chip £3.50 ea
Digital clock display £2.50
11 key membrane keypad £1.50 ea
Keyboard 392mm x 180mm/100 keys on board + LCD + 74HC05/80C49 easily removable £4.95
19" 3U sub rack enclosures £6.95
12V stepped motor board with slotted opto-2 mercury tilt switches £3.95 ea
1000 mixed 1/4 watt 1% resistors £4.95 ea
250 electrolytic axial/radial caps £4.95 ea
200 off mixed polyester caps £7.95
100 Mixed trimmer caps popular values £4.95
Cable box UHF modulator/video preamp/transformers/R's + C's/leads £8.95
1000 off mixed Multilayer Ceramic Caps £7.95
25 off Mixed crystal oscillators £9.95
Audio Cassette Cleaning + De-magnetizing Kit £1.50
Car Burglar alarm vibration auto entry/exit delay £5.95 ea
Single zone alarm panel auto entry/exit delay housed in domestic light socket £9.95 ea

P.C. P.S.U. 50 watt 115-230V input+5V 4A+12V 2.5A output with built-in fan, IEC inlet+on off £9.95 ea
STC P.S.U. 240V Input 5V-8A output (converts to 12V 3A details available) £5.95 ea
240V input 5V 10A output (converts to 12V 5A no details) £5.95 ea
600 line output transformers £1.25 ea
240V In 0-28V 62VA out transformer £2.75
Transformer+PCB gives 2x7.5 32VA with skt for 5 or 12V regulator, will power floppy drive £3.75 ea
Ultrasonic transducer (transmit+receive) £1.50 pair
3 to 16V Piezoelectric sounders 50p
9V DC electromechanical sounder 50p
24V DC electromechanical sounder 50p
removable in two positions £1.50
DIL switches PCB MT 3/4/6 way 35p
5V SPCO SIL reed relay 40p
5V 2PCO DIL miniature relay 60p
12V 2PCO or 4PCO continental relay 60p
12V 10A PCB MT (to make contact) relay 95p
3 to 12V electro magnetic acoustic transducer with data 75p
2.4576/8.8329/21.10 MHz crystals 50p ea
Bridges 25A 200V £1.00
2A 100V 50p
31b Mixed components pack £4.95
25 off mixed relays £5.95
40 off mixed toggle switches £9.95
50 off mixed switches, toggle, rocker, micro, slide £9.95
miniature axial chokes, 0.1, 0.18, 0.12, 0.33, 0.39, 0.15, 1, 3.30H 10p ea 100 for £7.50
50 Mixed terminal blocks £2.95
250 off 16/22/40/40 way IC Sockets £4.95
Crystal Oscillators 10/24/48 MHz £1.00 ea
Spider Plug Leads 75p
100 off Phono plugs (red/black/grey) £3.50
QUANTITY DISCOUNTS AVAILABLE - PLEASE RING
WE ALSO BUY ALL FORMS OF ELECTRONIC

TO BELOW ADDRESSES
ALL PRICES INCLUDE V A T
PLEASE ADD £2.00 p&p EXCEPT ITEMS MARKED WHICH ARE 50p. SAE FOR BULK BUYING LIST PAYMENT WITH ORDER TO
Dept ETI, COMPELEC,
14 Constable Road, St Ives,
Huntingdon, Cambs PE17 6EQ
Tel/Fax: 0480 300819

CATALOGUE £1.00 + 25p P&P

LEDs 3mm or 5mm red or green 1p each yellow 11p each
High intensity red, green or yellow 5mm 30p each
Cable ties 1p each £3.95 per 1000 £4.95 per 10000
Stepping motor 4 phase 12v 7.5 step 50 ohms £8.95
SAA1027 stepping motor driver chip £3.95
FM Transmitter kit good quality sound £8.00
High quality photo resist copper clad epoxy glass boards
Dimensions single sided double sided
3x inches 10 95 11 07
4x inches 12 49 12 88
6x inches 15 37
12x12 inches 110 66
Special Offers
Computer grade capacitors with screw terminals 30000uf 20v £2.50
87000uf 10v £1.95, 80000uf 15v £2.95, 10000uf 16v £1.50
7 segment common anode led display 12mm 10 45
L4850 IAT80 low drop out 5v regulator TO220 package 10 85
6S250 P channel mosfet TO 45, 8C559 transistor £3.95 per 100
74LS05 hex inverter £10.00 per 100, used 8748 Microcontroller £3.50
TV Mains switch 6A double pole with memory contacts for remote control pack of 10 £3.95 box of 10 £18.95
DC DC converter (Heslably model V12PS) 12v in 5v 200ma out 300v input to output isolation with data £4.95 each or pack of 10 £39.50
Motor coupler uses 7 digit 240v ac 50Hz £1 45
Resistor pack 2500 resistors 1/8 2W 50 different values £8.95
OVERTY keyboard 58 keypad output switches new £5.00
OVERTY keyboard with serial output no data (used) £5.00
Wide range of CMOS TTL 74HC 74F Linear Transistors 1k5 rechargeable batteries capacitors 100s inc sleepers in stock. Please add 95p towards P&P vat included.

JPG ELECTRONICS
278-278 Chertworth Road Chertsey Rd B40 2BH
Ascot/Via Orders (0248) 211202 callers welcome

Semiconductor Clearance!!
Z80-CPU 60 59p! Z8C56 £1.33! I8143! M3342 £0.99! 8085A/C £1.33 6802 £1.43, NE511 £0.79, etc. etc., etc., etc.!!!!
Workshop reorganisation enables us to offer a limited quantity of surplus stock at an unrepeatable fraction of the normal price. All components are 100% untested, guaranteed 100% of them! Microprocessor, logic, linear, diodes, transistors etc. etc. Send £1.50 for lists.
Profile Electronics (ETI), 100-102 Woodhouse Rd., Luton, Bedfordshire LU1 3SA. Minimum order £10.00 plus add £2.50 P&P plus VAT at the current rate. 10% Educational Discount on all official orders.

3 WIRE INDUCTIVE proximity switches German manufacture 10-55v PNP 400mA 10mm sensing distance LED indicator mounting clamps new boxed unused only £5.00 each (0733) 322745.

FOR SALE

N. R. BARDWELL LTD (ETI)

200 Signal diodes 1N4148	£1.00	20 24-way turned pin I.C. sockets	£1.00
78 Rectifier Diodes 1N4001	£1.00	16 40 pin d.11. wire wrap I.C. sockets	£1.00
56 Rectifier Diodes 1N4007	£1.00	2 ORP12 light dependent resistors	£1.00
50 Rectifier Diodes 1N5401	£1.00	200 Printed circuit board 20mm fuse clips	£1.00
100 Assid Zeners	£1.00	200 Assid. disc ceramic capacitors	£1.00
10 NE555 Timer ICs	£1.00	80 Assid. capacitors 1nf to 1ul	£1.00
8 C106D 400V 8 amp thyristors	£1.00	80 Assid. electrolytic capacitors	£1.00
8 BF51 Transistors	£1.00	80 4.7UF 18V Radial electrolytics	£1.00
30 BC478 Transistors	£1.00	75 4.7UF 83V Radial electrolytics	£1.00
30 MPS42 Transistors	£1.00	80 10UF 18V Radial electrolytics	£1.00
50 Rectangular red l.a.d.s	£1.00	80 10UF 50V Radial electrolytics	£1.00
25 Assid. high brightness l.a.d.s	£1.00	80 22UF 25V Radial electrolytics	£1.00
24 Miniature red l.a.d.s 3mm dia	£1.00	80 33UF 18V Radial electrolytics	£1.00
50 Axial l.a.d.s (Diode package) wide angle	£1.00	50 47UF 50V Radial electrolytics	£1.00
l.a.d.s	£1.00	60 100UF 10V Radial electrolytics	£1.00
12 Assid. seven segment displays	£1.00	50 220UF 16V Radial electrolytics	£1.00
30 Assid. I.F. transformers	£1.00	60 470UF 10V Radial electrolytics	£1.00
48 Assid. coil formers	£1.00	40 1000UF 10V Radial electrolytics	£1.00
100 Assid. RF chokes (inductors)	£1.00	12 1000UF 25V axial electrolytics	£1.00
30 Assid. connectors edge-dil. etc	£1.00	1 1 Farad 5.5V memory back up	£1.00
10 4P 3W MBB min. rotary switches	£1.00	capacitor	£1.00
20 1 inch Glass reed switches	£1.00	Peltier effect heat pump	£1.00
20 Magnetic ear pipe plus lead & plug	£1.00	10 watt Stereo amplifier, 4 controls plus	£2.95
20 Mini SP/CO slide switches	£1.00	data	£2.95
30 Assid. diil sockets up to 40 pin	£1.00		

Prices include VAT, postage £1.25. Stamp for Lists

288 Abbeyle Road, Sheffield S7 1FL
Phone (0742) 552886. Fax (0742) 500689

HOME AUTOMATION

LAMP MODULE Plugs in to wall socket to control incandescent lamps up to 300W
Responds to ON/OFF/DIM/BRIGHT commands from controllers. LM585 £22.45

MINI TIMER Timed control of up to 4 modules twice a day. Also features direct ON/OFF/DIM/BRIGHT control plus clock functions. MT522 £29.95

ENERLOGIC 1400e Controller

The first intelligent home automation system. A remarkable hardware + software package that adds brains to the range of X-10 modules and controllers. £349.95

Part of a remarkable range of home automation components from
SMART HOUSE SYSTEMS LTD
3 Buchanan Street, Largs, Ayrshire KA30 8PP
Tel: 0475 672589

UNDERSTANDING & INSTALLING HOME SYSTEMS, How to Automate Your Home
The best practical guide to date for the home automation enthusiast. Packed full of advice and ideas on installing home systems and equipment. 140 pages and 120 illustrations of the most up to date data on home automation. £22.95

MENDASCOPE LTD

REPAIR & RECALIBRATE OSCILLOSCOPES ALL MAKES AND MODELS NATIONWIDE COLLECTION & DELIVERY

FREE ESTIMATES
Llangollen, Clywd, N. Wales LL20 7PB
PHONE: 069 172 597

ANY MODULE £5 Delete & return. Slider power supply 9-25V. Stereo preamplifier + controls. 30w power amp + heat-sink. K.I.A. 1 Regent Road, Ilkley + 100 ASTID Components.

FAX YOUR ADVERT 0442 66998

FOR ALL DETAILS OF ADVERTISING RATES TELEPHONE 0442 66551

Logic Analysis breaks the £1,000 barrier


The Thurlby LA3200 and LA4800 logic analysers set new performance standards for low-cost logic analysers.

- 32 or 48 channels
- Multi-level triggering
- 100MHz asynch. capture
- Non-volatile data storage
- 5ns glitch capture
- Disassemblers for popular μ Ps

The new LAs incorporate a vast array of features as standard and options are available to connect to a very wide range of target systems. Contact us now for full technical details:

THURLBY-THANDAR

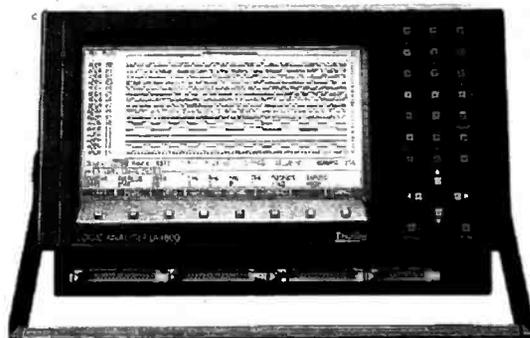Thurlby-Thandar Ltd., Glebe Road, Huntingdon, Cambs. Tel: (0480) 412451



High performance 2MHz function generators

The new TG200 series from Thurlby-Thandar represents the current state of the art in 2MHz function generators.


Waveform quality is exceptionally high at all frequencies and at all levels. Each range is sweepable by over 1000:1 and constant frequency variable symmetry is provided.

Other features of the series include full internal lin/log sweep, amplitude modulation, and digital readout of frequency, amplitude and dc offset.

The TG200 series is priced between £169 and £249 (+vat). Contact us now for technical details of all our function generators.

THURLBY-THANDAR

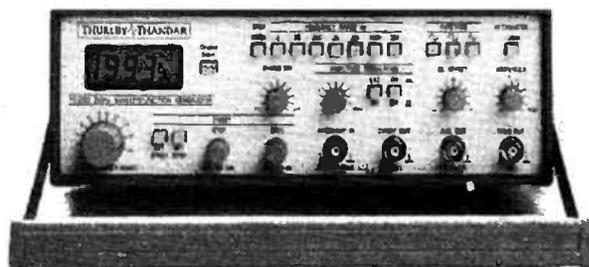Thurlby-Thandar Limited, Glebe Road, Huntingdon, Cambs. PE18 7DX Tel: (0480) 412451



WANTED

TURN YOUR SURPLUS TRANSISTORS, ICS ETC INTO CASH Immediate settlement. We also welcome the opportunity to quote for complete factory clearance.

Contact:
COLES-HARDING & CO.
Sandall Road, Wisbech,
Cambs PE13 2PS
BUYERS OF SURPLUS INVENTORY
ESTABLISHED OVER 15 YEARS
Tel: 0945 584188
Fax: 0945 475216

EDUCATIONAL

STUDY ELECTRONICS ON A 'PC'. Over 80 fully interactive, menu driven, graphics screens, containing charts, graphs, circuit diagrams, formula and theory. With user Inputs and calculated outputs. Covers subject from electron flow, through analysis of AC and DC circuits, to semi-conductors. £39.95 + £2.00 p&p. Credit Card orders 0371-514001, SAE for details. E.P.T. Educational Software, Pump Houaa, Lockrem Lane, Wilham, Essex CM8 2BJ.

COMPONENTS

"ELECTRO COMP"

WE CLEAR
Electronic Components • Semiconductors
Computer Equipment • Electronic Test Equipment
Populated Boards

In fact anything with an electronic bias
JOB LOTS, FACTORY CLEARANCE A SPECIALITY
Decision normally within 24-36 hours

LOOKING FOR COMPONENT As an ex Industrial buyer for 25 years I won't sell you reject or faulty product!! Only top quality components at the right price!! No Mail Order only production quantities!!

• **SNAGS:** only one. My terms are C.O.D. Deliveries normally made within 48 hours

Phone or Fax your list or enquiry to: 0635 46496
ELECTRO COMP 36 Talbot Close, Newbury, Berks RG131UA

TEST EQUIPMENT

LOGIC ANALYSER
Turn your PC Compatible into a powerful Logic Analyser. Full graphics display, Max 16 Channels, 4 combinational triggers, auto calibration. Excellent value. Includes 8 input lead probes. Send £29.99 or S.A.E. for details.
J.P. Shay (Dept ETI) 211 Ainsworth Road, Radcliffe, Manchester M26 0EE.

WANTED
RE-USABLE AND ALL TYPES OF ELECTRIC SCRAP
P.C.B's, PLUGS AND SOCKETS, EDGE CONNECTIONS, TEST EQUIPMENT, VALVES, ETC.
PAID ON CLEARANCE.

A.R.S.
2 NORMANS LANE, RASLEY
HEATH, WELWYN,
HERTS AL6 9TO
TEL: 0438 812193 FAX: 0438
812387 MOBILE: 0860 214302

ELECTROMART

KITS

HEATHKIT. U.K. spares and service centre/Educational products Distributor. Cedar Electronics, 12, Isbourn Way, Winchcombe, Cheltenham GL54 SNS Tel. (0242) 602402.

NEW VHF MICROTRANSMITTER KIT tunable 80-135 MHz, 500 metre range, sensitive electret microphone, high quality PCB, SPECIAL OFFER complete kit ONLY £5.95, assembled and ready to use £9.95 inclusive P&P. Credit card orders telephone 021 411 1821, Fax: 021 411 2355.

Cheques/PO's to: Quantek Electronics, (Dept ETI) 3 Houldey Rd, Birmingham, B31 3HL Send. S.A.E. for details of this and other kits. - Callers welcome.

TO
ADVERTISE
IN ETI
TELEPHONE
0442 66551
FOR ALL
DETAILS OF
RATES

AVON

L.F.HANNEY
Your Electric Component Specialist for Avon, Wilts & Somerset.
77 Lower Bristol Road, Bath, Avon.
Tel: 0225 424811

LIVERPOOL

PROGRESSIVE RADIO
87/93 Dale Street
Tel: 0512360982 051 236 0154
47 Whitechapel
Tel: 051 236 5489
Liverpool 2
'THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30

MANCHESTER


THE ELECTRONIC SHOP
Electronic components, test equipment, telephone accessories, computer accessories, microphones, disco lighting, speakers, turntables, mixers, meters, stylus.
29 Hanging Ditch,
Manchester M4 3ES
Telephone & Fax 061 834 1185

SERVICE MANUALS
Available for Most Equipment TV, Video, Audio, test etc. Any Age, Make or Model.
Write or phone for quotation.
MAURITRON (ETI)
8 Cherry Tree Road,
Chlnnor, Oxon, OX9 4QY.
Tel:- (0844) 351894.
Fax:- (0844) 352554

FOR SALE

THE AFFORDABLE COMMUNITY BROADCAST MIXING DESK ELEGANT IN STYLE SOUND AND QUALITY THE NO SQUARE BOX LOOK

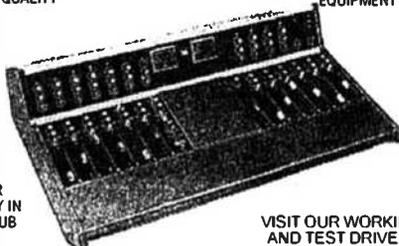MANUFACTURERS OF MIXERS AND AUDIO EQUIPMENT SINCE 1951



TRIED & PROVEN PRODUCTS

EVERY PART OF THIS FULLY MODULAR MIXER AVAILABLE SEPARATELY IN KIT FORM OR TESTED SUB UNITS FOR DESIGNER CONSTRUCTORS CLIENT DESKS

VISIT OUR WORKING STUDIO AND TEST DRIVE THIS DESK
PHONE 0268 793256

- ★ Uncluttered Operational Area
- ★ Presenter Designed Layout
- ★ Full Remote Control Facilities
- ★ The Low Profile User Friendly

PARTRIDGE ELECTRONICS

WORKS: UNIT 0,
318 HIGH ROAD,
BENFLEET, ESSEX, SS7 5HB

A.C. PARTRIDGE LTD.
PHONE: 0268 793381 FAX: 0268 565759

COURSES

Start training now for the following courses.
Send for our brochure -
without obligation or Telephone us on
0626 779398

Name..... Telecomms
..... Tech C&G 271
..... Radio Amateur
..... License C&G
..... Micro-processor
..... Introduction to
..... television

Radio & Telecommunications Correspondence School 12
Moor View Drive, Telgmouth, Devon TQ14 9UN

ETI

ELECTRONICS

TODAY INTERNATIONAL

EDITORIAL

Editor Paul Freeman
Art Editor Peter Kirby

CREATIVE

Designer Iain Houston
Technical Illustration Tony Burlinson
Photography Manny Cefal

ADVERTISEMENT SALES

Advertisement Manager
Mark Linacre
Advertisement Sales
Michele Donovan
Advertisement Copy Control
Marie Quilter
Key Accounts Manager
Donna Wells

MANAGEMENT

Managing Director
Terry Patisson
Circulation & Promotions Manager
Debra Stupple
Production Manager
Tony Dowdeswell
Group Editor
Stuart Cooke
Group Advertisement Manager
Claire Jenkinson



ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and reproduction requires the prior written consent of the company 1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription rates...UK£23.40 Europe £29.50 Sterling Overseas £31.00 US Dollars Overseas \$62.00

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST. Telephone (0442) 66551. UK newstrade distribution by SM Distribution Ltd, 6 Leigham Court Road, London SW16 2PG. Telephone 081-667 8111. Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST. Telephone (0442) 66551. Subscriptions by Argus Subscription Services, Ell. Queensway House, 2 Queensway, Redhill, Surrey RH1 10S. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. Telephone (310) 375 6258. Typesetting and origination by Ebony, Uskeard, Cornwall. Printed by Willshire Ltd, Bristol.

Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (0442) 66551 Fax (0442) 66998

Next Month

Just to make sure we give you a complete helping hand with our Infra-red remote control project, ETI next month will not only contain details of the transmitter but will also give you the PCB on the front cover.

If you have ever fancied being accompanied by other musical instruments with just a whistle for a tune or an acoustic guitar then maybe our Sound to MIDI project is for you. A one-man-band could take on a new meaning.

We continue with the EPROM programmer project providing software and constructional details, and we also have yet another computer controlled lightshow.

A project for beginners next month is an alarm for detecting pools of water in the kitchen. AU this together with more on multi-meter circuits in our February issue.

Out at your newsagents 011 January 1st.

The above articles are in preparation but circumstances may prevent publication

Last Month

Our December issue featured:

20/50/100 watt Mains Inverter
The Auto-Mate Mixing Desk Part 8
Digital Circuit Tester
Hybrid Line Amp
Audio Response Measuring System Part 2
RS232 Interface
The Greening of the Car


Back issues can be obtained from Argus Subscription Services. Address in column to left.

ADVERTISER'S INDEX

AUTONA	10	M & B ELECTRICAL	58
BKELECTRONICS	IFC	M&B RADIO	53
BADGER BOARDS	61	MAPLINELECTRONICS	OBC
CIRKIT	IBC	NUMBER ONE SYSTEMS	14
CRICKLEWOOD ELECTRONICS	46	OMNIELECTRONICS	61
HALCYONELECTRONICS	47	PICO TECHNOLOGY	15
HENRY'S	47	R&DELECTRONICS	47
HESINGTECHNOLOGY	10	RNELECTRONICS	61
J&NBULL	11	S.L.M. MODEL ENGINEERING	47
JAYTEE ELECTRONICS	23	STEWARTS OF READING	22
JPGELECTRONICS	23	WILMSLOWAUDIO	61

£30 off Europe's best selling oscilloscopes!

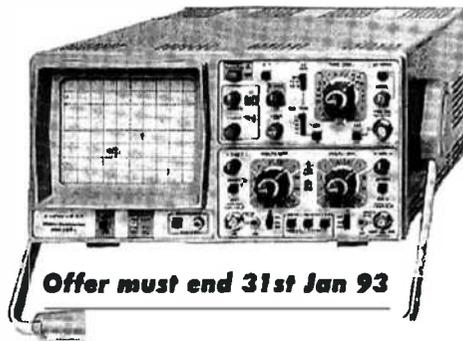- Excellent quality, built to last a life time
- 2 year warranty
- Each 'scope supplied with 2 sets x10 probes, manual and mains lead.



Offer must end 31st Jan 93

PART NO.	DESCRIPTION	USUAL PRICE	OFFER PRICE
HM203-7	20MHz, dual channel	£397.15	£367.00
HM205-3	20MHz, storage 'scope	£716.75	£686.00
HM604	60MHz, dual channel	£716.75	£686.00
HM1005	100MHz, 3 channel	£930.60	£899.00

OUT NOW!



The Brand New Circuit Electronic Constructors Catalogue Winter 92/93

- 192 pages
- £££'s worth discount vouchers
- 100s new products.....

Books - the latest titles.
Capacitors - new range ceramic discs, extended ranges electrolytic and polyester types.
Computers - new CAD PCB layout software.
Connectors - extended ranges of BNC, Jacks, XLR and PCB types.
Filters - new narrow band ceramic and low pass TV filters.
Hardware - additions include new range control knobs, cabinet hardware and heatsinks.
Inductors - more additions to our already extensive range.
Kits - new additions to the Velleman range.
Rigs - handheld 'CB' transceivers, wavemeters, scanning receiver accessories and aerials.
Semis - new linear ICs, transistors and a complete new range of LEDs including blue types.
Speakers - new radio mic systems.
Test Equipment - new hand-held frequency meter and satellite TV dish alignment system.
And much more besides.....

- Available at larger newsagents, from 12th November, or directly from Cirkuit.



All prices include VAT at 17.5%.

Postage and packing; standard £ 1.40, next day delivery £ 4.60.

Prices correct at time of going to press, but may change in line with exchange rate fluctuations.



MULTIMETERS

The D-MM good value meters are now even D-MMer good value!!



The TM series of low cost meters, with 3 1/2 digit LCDs, full overload protection, strong ABS cases and packed with features. Supplied with test leads, battery and manual.

Offer must end 31st Jan 93

PART NO.	DESCRIPTION	USUAL PRICE	OFFER PRICE
TM 5315	DC current (10A) continuity and diode test	£19.99	£19.25
TM 5365	Capacitance and frequency (200kHz) ranges	£36.50	£29.99
TM 5375	Frequency range (20MHz) and HFE test	£36.95	£31.49
TM 115	AC & DC current (10A), HFE and continuity test	£32.50	£30.99
TM 175	Freq. (15MHz), capacitance ranges with HFE, diode, continuity & LED test	£53.60	£45.00
TM 8020	3 1/2 digit display, freq. (4MHz) capacitance (40uF), AC+DC current to 20A	£54.76	£49.95
TM 8030	3 1/2 digit display, freq (4MHz), temp. (inc probe), AC+DC to 20A	£59.96	£55.49
~705	Capacitance meter, 1pF to 20,000uF	£39.82	£35.90



SPECTRUM ANALYSER ADAPTOR

- 400kHz to 250MHz frequency range
- LC display of centre frequency
- Calibration marker

The new TSA250 will adapt any conventional 'scope into a highly cost effective spectrum analyser. With numerous applications in RF design and development work, EMC investigations, and education.

Cirkuit

CIRKIT DISTRIBUTION LTD

Park Lane, Broxbourne, Hertfordshire, EN10 7NQ Telephone (0992) 444111, Fax (0992) 464457

BUYER'S GUIDE TO ELECTRONIC COMPONENTS 1993

Maplin



BS 5753
Part 2: 1987
Level B:
Quality Assurance
RS12750



Order your copy of the New MAPLIN Catalogue on sale NOW!
Pick up a copy from any branch of W.H. SMITH or from our chain of shops for just £2.95 or
post this coupon now to receive your copy for just £3.45 inc. p&p. If you live outside the
U.K. send £5.50 or 14 IRC's for Airmail in Europe/surface mail outside Europe.
or £1 0.65 or 27 IRC's for Airmail outside Europe.
I enclose £3.45/£5.50/£1 0.65 (delete as applicable).

Name.....
Address.....
Post Code.....
Send to Maplin Electronics,
P.O. Box 3, Royleigh,
Essex, England,
SS6 8LR.
EN93

Over 700 product packed pages
with hundreds of brand new
products. On sale now, only £2.95

Available from all branches of W.H. SMITH
and Maplin shops nationwide. Hundreds of
new products at super low prices!