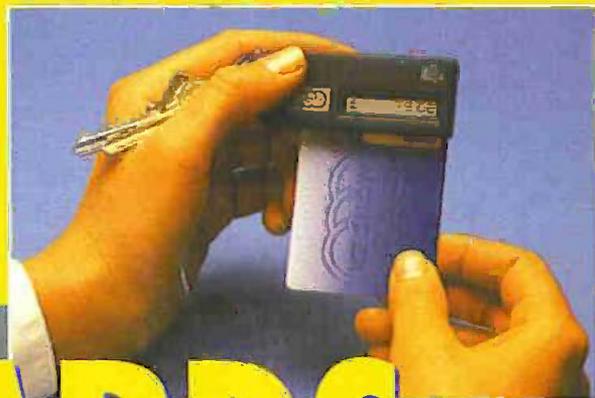


Peaceful Waves Biofeedback



SMART CARDS

BY THE MILLION



PLUS

PCB Shake'n'etch

- **New Series! Experimenting with Video**
- **ETI Remote Data Logger**
- **Cupid's Arrow!**

9 770142 722146


FOR ENTHUSIASTS BY ENTHUSIASTS
NEXUS

VOLUME 26 No. 1



"extremely good value for money for such a comprehensive package"

Practical Wireless July 98

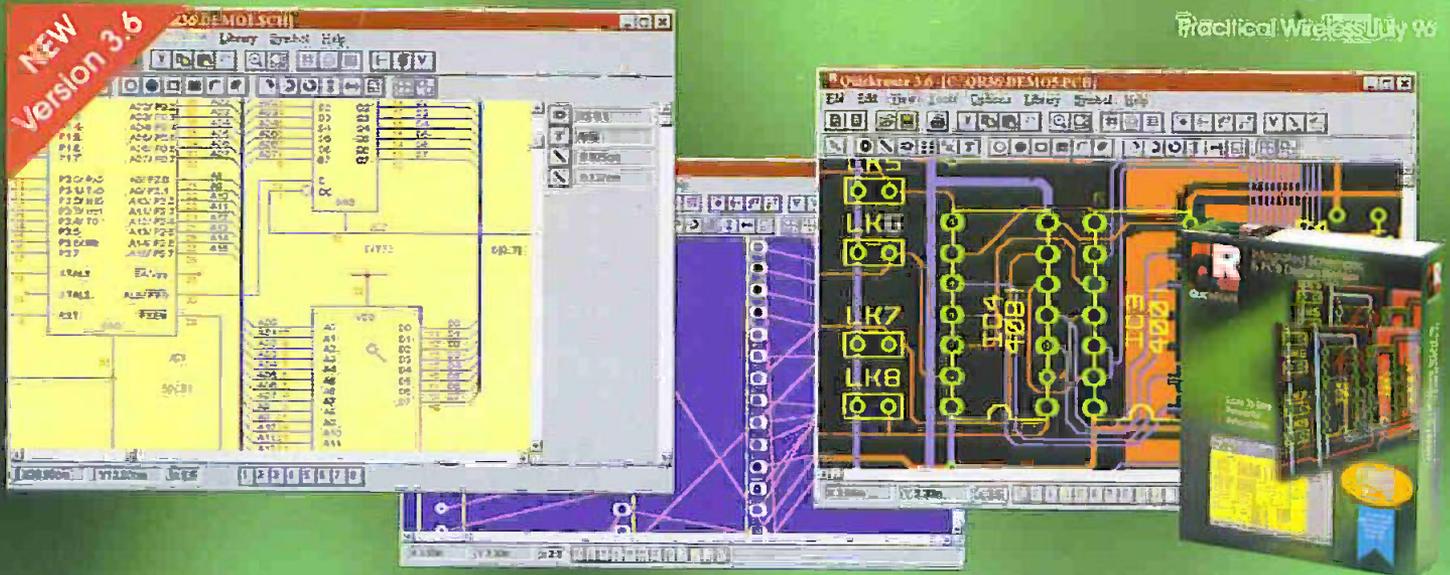

Schematic capture, Autorouting & Design Checking for just £149*

NEW
Quickroute 3.6 Designer £149*

Take a look at Quickroute 3.6 Designer and you might be surprised! For just £149* you get easy to use schematic design (automatic junction placement, parts-bin, etc), "one click" schematic capture, autorouting on 1 or 2 layers, design rule & connectivity checking and a starter pack of over 260 symbols.

NEW
Quickroute 3.6 PRO+ £399*

For those needing more power & more features there is Quickroute 3.6 PRO+. For just £399 you get multi-sheet schematic capture, 1 to 8 layer autorouting, net-list import/export, links to simulators, CAD/CAM file export, Gerber import/viewing, DXF WMF & SPICE file export, copper fill, advanced connectivity checking with automatic updating of a PCB from a schematic, the basic set of over 260 symbols and library pack which includes a further 184 symbols. More symbols are available in additional library packs available separately.

Prices are Quickroute 3.6 Designer-£149, Quickroute 3.6 PRO+ £399, SMARTRoute 1.0 £149.00, Library Packs £39 each. Post & Packing per item is £6 (UK), £8 (Europe) and £12 (World). V.A.T must be added to the total.

NEW PLUG IN AUTOROUTER



SMARTRoute is a new 32-bit autorouter from Quickroute Systems rated in 'category A' by Electronics World (Nov 96). SMARTRoute plugs straight into Quickroute 3.6, automatically updating Quickroute's menus with new features and tools.

SMARTRoute 1.0 uses an iterative goal seeking algorithm which works hard to find the best route even on single sided PCB's. SMARTRoute allows you to assign different algorithms, design rules, track & via sizes, layers used, etc to groups of nets for total flexibility. SMARTRoute 1.0 costs just £149*.



Tel 0161 476 0202 Fax 0161 476 0505

Quickroute Systems Ltd, Regent House, Heaton Lane, Stockport, SK4 1BS, U.K.

WWW: www.quickroute.co.uk EMail: info@quicksys.demon.co.uk



Prices and specifications subject to change without notice. All trade marks are acknowledged & respected. All products sold subject to our standard terms & conditions (available on request).

Contents

Volume 26 No.1

& Features & Projects



Smart Cards by the Million 11


Smart Cards are quietly becoming part of our everyday lives - they are even taking over the phone boxes. Nick Hampshire examines the development and problems facing this technology in the future.

Experimenting With Video (Part 1) 22

In the first part of this new series, Robin Abbott introduces video signals and shows how a sync separator module can be incorporated into other circuits.

Peaceful Waves Biofeedback 33

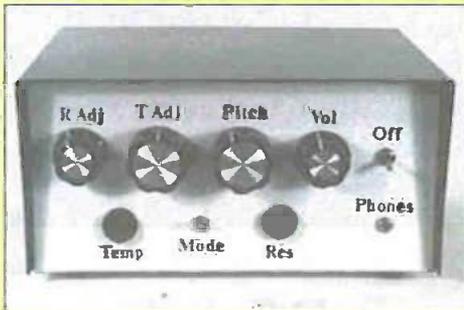The best way to use biofeedback to combat stress is to have a really soothing sound to respond to your moods. Robert Penfold's biofeedback monitor will take you "down to the sea again".



ETI Remote Data Logger 41

Not only portable for field and classroom experiments, Richard Grodzik's PIC-driven data logger uses the minimum components, runs on 3 volts, uploads to the home PC, and can import to Lotus and Excel spreadsheets.

Cupid's Arrow 51

A St. Valentine's special: the Blindfold Bowman will no doubt give up his darts and opt for this modern, user-friendly LED-fuelled heart-targeter devised by Terry Balbirnie -and it's nearly as capricious as Cupid himself!



PCB Shake'n'Etch 57

Making your own PCBs a highly desirable accomplishment, but involves handling of chemicals that can corrode and stain. Bob Noyes' self-rocking etching tray helps to get a better result more safely and with less risk of mess.

Virtual Stonehenge 65

We find a web site that looks into the high tech past.

Regulars

News	5,7,9
Subscriptions	27
PCB foils	68
Practically Speaking	70
Terry Balbirnie explains wire gauge standards, and how to measure it for yourself.	
Round the Corner	74



Subscribe & Save

Phone the hotline and take advantage of our special offer detailed on page 31

SUBSCRIPTIONS
& BACK ISSUES HOTLINES:
01858 435344

ORDERS
ENQUIRIES:
01858 435322

1 year, 6 issues - £10.00

New low-cost PIC training

Kanda Systems - who are also the sponsors of the Kanda/ETI Design Competition (see last month) - have added a new, low cost PIC training system to their catalogue, the Kanda PIC Explorer. "Imagine being able to lift the lid off the processor and see what happens inside as it responds to your code", is how they describe the new package. "The system contains everything you need to fully explore the workings of the chip, you just need to add a PC and a bit of grey matter."

The software includes a full-function editor, an assembler (which links to the editor to highlight errors) and the Explorer screen. The Explorer screen allows you to see exactly what is happening inside the processor as it shows all the register values and the code as it is being run.

The hardware features switches for setting input bits, plus a push button switch for creating interrupts (the unit

can also generate timer and "change on port B" interrupts). Changing the switch values will immediately change the port register values, and pressing interrupt will make the code jump to the interrupt vector address. The output is displayed on either LEDs (arranged in the familiar traffic light pattern) or on a seven-segment display. The reference manual explains the functions of the PIC family in plain English, and the training (based around the GNVQ Microelectronics syllabus) allows you to understand how to use the device, from binary numbering, through to complex interrupt functions.

Operation is either by single-step (where you see the effect of each line of code being reflected in both the hardware the on the Explorer screen) or run, which runs the code in real time (processor dependent) so that you can see exactly how your code runs at speed.

Designed as a dedicated introduction to the PIC processor family (and processors in general), the PIC Explorer costs £99 plus VAT and is available now.

Contact Kanda Systems Ltd. for more details. Tel 01974 282670 Fax 01974 282356 email Info@Kanda-Systems.com



Turn your PC into a digital oscilloscope

Pico Technology's new ADC 200 converter plugs into the parallel port of a PC laptop or desktop, to operate the computer as a 50 MSPS dual channel storage oscilloscope, a 25 MHz spectrum analyser or a multimeter for less than £500.

The PicoScope software has recently gone into a Windows version, with full on-line help, and offers advanced features such as the simultaneous display of multiple views of the same signal. Data such as the waveform itself, its frequency components, AC voltage and frequency can be displayed on-screen at the same time. As well as oscilloscope features, the ADC 200 provides FFT spectrum analysis, waveform storage and printing facilities normally found on Dual Storage Oscilloscopes costing well into four figures. There is also an advanced triggering mode that makes it possible to capture infrequent one-off events.

The 50 MSPS ADC 200 is priced at £459. There is a 20 MSPS unit available at £359.

For information and sales contact Pico Technology Ltd, Broadway House, 149-151 St Neots Road, Hardwick, Cambridge CB3 7QJ Tel 01954 211716 Fax 01954 211880 email post@picotech.co.uk

10 GHz amateur band to go in April '97

The Radiocommunications Agency has announced the date for the withdrawal of part of the represent 10GHz amateur band from amateur use. The frequency allocation 10.15 to 10.30 GHz will be withdrawn from the 1st April 1997.

The reason given for the withdrawal, which was announced some time ago, is the continuing demands on the radio spectrum for existing and new radio services. The allocation of new amateur bands in spectrum under less pressure of demand is being explored constantly, with the recent introduction of a new Low Frequency amateur band allocation as an example of this shift.

DIFFERENTIAL THERMOSTAT KIT Perfect for heat recovery, solar systems, boiler efficiency etc. Two sensors will operate a relay when a temp difference (adjustable) is detected. All components and pcb. £29 ref LOT83

MAGNETIC RUBBER TAPE Self-adhesive 10 metre reel, 6mm wide perfect for all sorts of applications! £15 ref LOT87

RADIO METERS - REMEMBER THESE? Glass bulb on a display stand that contains four vials that rotate when exposed to sunlight, scientific novelty for £8.99 ref SD120

MAINS POWER SAVER UK made plug in unit, fitted in seconds, can reduce your energy consumption by 15%. Works with fridges, soldering irons, conventional bulbs etc. Max 2A rating. £9 each ref LOT77, pack of 10 £59 ref LOT72

YUASHA SEALED LEAD ACID Batteries, ex-equipment but ok bargain price just £5.99 each ref YA1, 100 or more £3.50 each

DC TO DC CONVERTERS

DRM56 input 10-40vdc output 5v 6A E15 DRM126 input 17-40vdc output 12v 6A E16 DRM156 input 20-40vdc output 15v 6A E18 DRM245 input 29-40vdc output 24v 6A E12 DRS123 input 17-40vdc output 12v 3A E10 DRS153 input 20-40vdc output 15v 3A E20 DRS243 input 25-40vdc output 24v 3A E8

INSTALL A COINBOX FOR LESS THAN £20 Convert any standard phone into a coinbox with this kit, some models require plus hinges and a lock. £19 ref CB1

HITACHI LM225X LCD SCREENS 270x150mm, standard 12 way connector, 640x200 dots, tac spec sheet. £35 each ref LM2

VARIABLE CAPACITORS Dual gang, 50x23x45mm, reduction gearing, unknown capacity but probably good quality (military spec) general purpose radio tuner. £9 ref VC1

ELECTRONIC FLASH PCB Small pcb fitted with components including a flash tube. Just connect 12vdc and it flashes, variable speed potentiometer. £6 ref FL1

THIEF PROOF PEN! Amazing new ball point pen fitted with a combination lock on the end that only you know! £2.49 ref TP2

JUMBO BI COLOUR LEDS PCB with 19 fixed also 5 giant seven segment displays (50mm) £5 ref JUM1

HOME DECK CLEARANCE These units must be cleared! Leads a infra red remote control keyboard and receiver, a standard UHF modulator, a standard £200/75 BT approved modem and loads of chips, capacitors, diodes, resistors etc all for just £10 ref BAR33

6.8MW HELIUM NEON LASERS New units, £55 ref LOT33

COINSLOT TOKENS you may have a use for these? mixed bag of 100 tokens £5 ref LOT20

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minor! £65 ref FXP01

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks just produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £45 ref FTRK1

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put yourself under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment & parties etc only, by those experienced in its use. £15 ref FHR2

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small meca-space ship out of simple materials and without any visible means - cause it to levitate. £10 ref FAGRA1

WORLDS SMALLEST TESLA COIL/LIGHTNING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects. "Plasma in a jar". St. Elmo's fire, Corona, excellent science project or conversation piece. £5 ref FBT/CT/LS

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherence and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NCSG in Israel. £10 ref FFDV1

VOICE SCRAMBLER PLANS Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and eavesdropping. £8 ref FVSS

PULSED TV JOKER PLANS Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound! Works on FM too! DISCRETION ADVISED. £8 ref FITJ5

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £8 ref FGH11

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting plastics, textiles etc. £12 ref FAL2

MYSTERY ANTI GRAVITY DEVICE PLANS Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £6 ref FIANTRK

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PCB boards, jewelry, coins, small parts etc. £6 ref FAULB1

ULTRA HIGH GAIN AMP/STETHOSCOPIC MIKE/ SOUND

AND VIBRATION DETECTOR PLANS Ultra-sensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £8 ref FHHGA7

WOLVERHAMPTON ELECTRONICS
STORE NOW OPEN IN
WORCESTER ST TEL 01902 22039

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £8 ref FIDOG2

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £12 ref FFL1

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 ref FLLS1

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £6 ref FPPS4

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! Simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 ref FITELEGRAB

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £8 ref FIBD1

ELECTROMAGNETIC GUN PLANS Projects a metal object a considerable distance - requires adult supervision. £5 ref FEMAL2

ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £5 ref FEMAL1

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in hard to get or hostile premises. Uses satellite technology to gather distant sounds and focus them to your ultra sensitive electronics. Plans also show an optional wireless link system. £8 ref FPM5

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 ref FHVMM7/TCL4

MEGA LED DISPLAYS PCB fitted with 5 seven segment displays each measuring 55 x 38mm. £5 ref LED5

MOD TRANSMITTING VALVES 5J180E £80 ref LOT112

SWITCHED MODE PSU'S 244 watt -5.32A -12.6A -5.0.2A -12.0.2A. There is also an optional 3.3v/25A rail available. 120/240V I/P. Cased, 175x90x145mm. IEC inlet suitable for PC use (8 different connectors 1 included). £15 ref LOT135

Check out our WEB SITE
full colour interactive 1997 catalogue
<http://www.pavilion.co.uk/bull-electrical>

VIDEO PROCESSOR UNITS 7/6 10AH BATT/24V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connectors on the rear. Inside 2x 6V 10AH sealed lead acid battery, p.c.s and a 8A/7.2V toroidal transformer (means in, sold as seen, may have one or two broken knobs etc due to poor storage). £15.99 ref VP2

RETRO/NIGHT SIGHT Recognition of a standing man at 300m in 1/4 moonlight, hermeticity sealed, runs on 2 AA batteries. 60mm F1.5 lens, 20mw infrared laser included. £25 ref RETRON

MAKE YOUR OWN CHEWING GUM KIT Everything you need to make real chewing gum, even the bowl and tree sap from the Sapodilla tree. £7.99 ref SC190

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphones. Designed to cover 63-106 Mhz but easily changed to cover 63-130 Mhz. Works with a common 9v (PP3) battery. 0.2W RF. £9 ref 1001

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use. 24v 3A transformer is needed to complete the kit. £14 ref 1007

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30, you will get nearly 2 watts! £15 ref 1008

FM/AM SCANNER KIT Well not quite, you have to turn the knob your self but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM.

Built in 5 watt amplifier, inc speaker. £15 ref 1013

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200 w power handling, microphone included. £17 ref 1014

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3 RF stages, microphone and audio preamp included. £24 ref 1028

STROBE LIGHT KIT Adjustable from 1-60 hz (3x lot faster than conventional strobes). Mains operated. £17 ref 1037

COMBINATION LOCK KIT 9 key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £13 ref 1114

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £9 ref 1130

ROBOT VOICE KIT Interesting circuit that distorts your voice adjustable, answers the phone with a different voice! 12vdc. £9 ref 1131

TELEPHONE BUG KIT Small bug powered by the phone line, starts transmitting as soon as the phone is picked up! £12 ref 1135

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction controlled supplied with 12 LEDs (you can fit LEDs instead to make kit mains, not supplied) 9-12vdc. £17 ref 1025

12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2a transformer also required. £8 ref 1059

HELPING HANDS Perfect for those fiddly jobs that need six hands. 6 ball and socket joints, magnifier. £7.99 ref Y057A

VOX SWITCH KIT Sound activated switch ideal for making logging tape recorders etc. adjustable sensitivity. £10 ref 1073

PREAMP MIXER KIT 3 input mono mixer, sep bass and treble controls plus individual level controls. 18vdc, input sens 100mA. £15 ref 1052

SOUND EFFECTS GENERATOR KIT Produces sounds ranging from bird chirps to sirens. Complete with speaker, add sound effects to your projects! £9 ref 1045

15 WATT FM TRANSMITTER (BUILT) 2 stage high power, preamp required 12-18vdc, can use ground plane, yaq1 or open diode. £69 ref 1021

HUMIDITY METER KIT Builds into a precision LCD humidity meter. 9 pin design, pcb, led display and all components included. £29

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration at 286, VGA, 4.1, 640k, serial port, hard drive with min 100k free. £24.99

MAGNETIC MARBLES They have been around for a number of years but still give rise to curiosity and amusement. A pack of 12 is just £3.99 ref GR22

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate: brass, steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £45 ref NK39

Miniature adjustable timers, 4 pole 0/c output 3A 240V, HY1230S, 12VDC adjustable from 0-30 secs. £4.99

HY1260M, 12VDC adjustable from 0-60 mins. £4.99

HY2405S, 240v adjustable from 0-5 secs. £4.99

HY24060M, 240v adjustable from 0-60 mins. £6.99

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1

POWER SUPPLY fully cased with mains and o.c.b leads 17v DC 500mA output. Bargain price £5.99 ref MAG6P9

COMPOSITE VIDEO KIT Converts composite video into separate H sync, V sync and video. 12v DC. £12.00 REF: MAG8P2

FUTURE PC POWER SUPPLIES These are 250x135x30mm, 4 drive connectors 1 mother board connector. 150watt, 12v fan, iec inlet and on/off switch. £12 Ref EP6

VENUS FLY TRAP KIT Grow your own carnivorous plant with this simple kit. £3 ref EP34

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimental! 30 m for £12.99 ref MAG13P1

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together believed to cause rain! £3 a pair REF EP29

3' by 1' AMORPHOUS SOLAR PANELS 14.5V, 700mA 10 WATT, aluminum frame, screw terminals. £56 ref MAG45

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needless pain to experiment with. £9 ref TP30

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £9 ref TP36

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 miles per hour! Range of over 200 metres! £8.99 ref R/S

COMPAQ POWER SUPPLIES WITH 12V DC FANS Ex equipment psus, some ok, some not but worth it for the fan, alone probably about 300 watt PC unit with IEC input. £3.50 each ref CG1

BALLON MANUFACTURING KIT Swiss made, small, biob blows into a large, long-lasting balloon, hours of fun! £3.99 ref GUESSR

9-0-8V 4A TRANSFORMERS, chassis mount. £7 ref LOT19A

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 6 on a pcb for just £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref LOT17

SOLID STATE RELAYS

CMP-DC-200P 3-32vdc operation, 0-200vdc 1A £2.50

SMT2000GS 3-24vdc operation, 26-280vac 3A £4.50

BULL ELECTRICAL
250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS).
MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3.50 P&P PLUS VAT.
24 HOUR SERVICE £4.50 PLUS VAT.
OVERSEAS ORDERS AT COST PLUS £3.50

PLEASE ALLOW 7-10 DAYS FOR DELIVERYPHONE ORDERS WELCOME (ACCESS,VISA, SWITCH, AMERICAN EXPRESS)
TEL: 01273 203500
FAX 01273 323077
E-mail bull@pavilion.co.uk

SAE FOR FREE COLOUR CATALOGUE

WE BUY SURPLUS STOCK FOR CASH
SURPLUS STOCK LINE 0802 660377

RUSSIAN BORDER GUARD BINOCULARS £1799

Probably the best binoculars in the world! For brochure
VEGARUSSIAN MULTIBAND World communications receiver, 9 wave bands, (5 short, 1 LW, 1 MW, 1 MW) external ferrite and external telescopic aerials, mains or battery. Large, typically Russian radio! £45 REF VEGA

NEW LASER POINTERS <5mw, 75 metre range, hand held unit runs on two AA batteries (supplied) £70.00 ref DEC49

MULTIBAND RADIO Compact general purpose radio receiver covering air, pb, tv, cb etc. Squelch vol and tuning £24 ref MB1

DIVINING RODS £3.99 a pair! ref EF111

MOONSHINE BIBLE 270 page book covering the production of alcohol from potatoes, rice, grains etc. Drawings of simple home made stills right through to commercial systems. £12 ref MS3

NEW HIGH POWER MINI BUG With a range of 800 metres or more and up to 100 hours use from a PP3 (this will be popular! Bug measures less than 1" square) £28 Ref LOT102

BUILD YOUR OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT61

PC KEYBOARDS PS2 connector, top quality suitable for all 286/386/486 etc £10 ref PCKB 10 for £65

TRACKING TRANSMITTER range 1.5-5 miles, 5,000 hours on AA batteries, also transmits info on car direction and motion/works with any FM radio. 1.5" square. £65 ref LOT101

ELECTRIC DOOR LOCKS Complete lock with both Yale lock and 12v operated deadlock (keys included) £10 ref LOT99

SURVEILLANCE TELESCOPE Superb Russian zoom telescope adjustable from 15x to 60x complete with metal tripod (impossible to use without this on the higher settings) 65mm lens, leather carrying case £149 ref BARR6

WIRELESS VIDEO BUG KIT Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP73, (probably not licensable)

GPS SATELLITE NAVIGATION SYSTEM Made by Garmin, the GPS38 is hand held, pocket sized, 2550, position altitude, graphic compass, map builder etc £179 ref GPS1

CCTV CAMERA MODULES 46X70X25mm, 30 grams, 12v 100mA auto electronic shutter, 3.6mm F2 lens, CCR 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a smart or video input on a tv or video. IR sensitive. £73.95 ref EF137

IR LAMP KIT Suitable for the above camera, enables the camera to be used in total darkness! £5 ref EF138

INFRA RED POWERBEAM Handheld battery powered lamp, 4 inch reflector, kryolyn bulb, gives out powerful infrared light! 4 D cells required. £29 ref PB1

MONO VGA MONITORS, Perfect condition, Compact, 14", 3 months warranty £29 ref MVGA

SUPER WIDEBAND RADAR DETECTOR Detects both radar and laser, X, K and KA bands, 360 degree coverage, front and rear wave guides, may be illegal to use! 1 1/2" 7x4 1/2" £149 ref RD2

9 WATT CHIEFTAN TANK LASERS

Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment, 7 mile range, no circuit diagrams due to MOD, new price £50,000! us? £199. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 2band, 600Hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. £199 for one. Ref LOT4

TWO WAY MIRROR KIT includes special adhesive film to make two way mirror (e) up to 60"x20" (glass not included) includes full instructions. £12 ref TW1

NEW LOW PRICED COMPUTER/WORKSHOP/HIFI/RCB UNITS Complete protection from faulty equipment for everybody! Inline unit fits in standard IEC lead (extends it by 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £6.99 each ref LOT5. Or a pack of 10 at £49.50 ref LOT6. If you want a box of 100 you can have one for £250!

WIND UP FLYING PARROT! Genuine parrot that flaps its wings and flies for up to 50 meters £6 ref EF2

RADIO CONTROLLED CARS FROM £6 EACH!!!! All returns from famous manufacturer, single channel (left, right, forwards, backwards) £6 ref LOT1. Two channel with more features £12 ref LOT2.

THOUSANDS AVAILABLE RING/FAX FOR DETAILS!
MAGNETIC CARD READERS (Stripes) £9.95 Cased with flyleads, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well? complete with control electronics PCB. just £9.95 ref BAR31

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you pursue these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

COIN OPERATED TIMER KIT Complete with consist mechanism adjustable time delay, relay output, put a consist on anything you like! TV's, videos, fridges, drinks cupboard, HIFI, takes 50p's and £1 coins. DC operated, price just £7.99 ref BAR27.

ZENITH 900 X MAGNIFICATION MICROSCOPE Zoom, metal construction, built in light, shrimp farm, group viewing screen, lots of accessories. £29 ref ANAYLT.

AA NICAD PACK Pack of 4 tagged AA nicads £2.99 ref BAR34

NIGHTSIGHTS Model T2S4 with infra red illuminator views up to 75 metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 560g weight. £199 ref BARR1. 1 years warranty

LIQUID CRYSTAL DISPLAYS Bargain prices, 16 character 2 line, 99x24mm £2.99 ref SM1623A
20 character 2 line, 83x19mm £3.99 ref SM2020A
16 character 4 line, 62x25mm £5.99 ref SMC1640A

TAL-1, 110MM NEWTONIAN REFLECTOR TELESCOPE Russian. Superb astronomical scope, everything you need for some serious star gazing! up to 169x magnification. Send or fax for further information! Ref TAL.1, £249

SOLAR ENERGY/GENERATOR PLANS For your home, loads of info on designing systems etc £7 ref PV1

SOLAR COOKERS Comprehensive guide to building solar powered cookers, includes plans, recipes, cooking times etc £7 ref SSC1

WOLVERHAMPTON ELECTRONICS STORE NOW OPEN IN WORCESTER ST TEL 01902 22039

CENTRAL POINT PC TOOLS Award winning software, 1,300 virus checker, memory optimiser, disc optimiser, file compression, low level formatting, backup scheduler, disk defragmenter, undelete, 4 calculators, D base, disc editor, over 40 viewers, remote computing, password protection, encryption, comprehensive manual supplied etc £6 ref lot 97 3 5" disks

COLOUR CCTV VIDEO CAMERAS, BRAND NEW AND, CAGED, £119.

PERFECT FOR SURVEILLANCE, INTERNET, VIDEOCONFERENCING, SECURITY, DOMESTIC VIDEO

Works with most modern video's, TV's, Composite monitors, video grabber cards etc Pal, tv P-P, composite, 75ohm, 1/3" CCD, 4mm F2.8, 500x582, 12vdc, mounting bracket, auto shutter, 100x50x180mm, 3 months warranty, 10 or more £99 ea
MICRO RADIO It's tiny, just 3/8" thick, auto tuning, complete with headphones. FM £9.99 ref EP35

HANDHELD SCANNERS 10 channel, built in charger, LCD display £119 ref B110B. 100 channel model £229 ref B110E.

SMOKE MACHINE 42.3 cubic metres a min from this means operated machine £299 ref G002B, smoke fluid £25 (5 litres) gives about 2.5 hours use. ref G002AA

Check out our
WEB SITE
full colour interactive
1997 catalogue
<http://www.pavilion.co.uk/bull-electrical>

IBM PS2 MODEL 150Z CASE AND POWER SUPPLY Complete with fan etc and 260 watt power supply. £9.95 ref EP67

1.44 DISC DRIVES Standard PC 3 1/2" drives but returns so they will need attention. SALE PRICE £4.99 ref EP68

1.2 DISC DRIVES Standard 5 1/4" drives but returns so they will need attention. SALE PRICE NOW ONLY £3.50 ref EP69

PP3 NICADS Unused but some storage means. £4.99 ref EP62

GAS HOBS AND OVENS Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob £19 ref BAR316. Basic smelt built in oven. SALE PRICE £59 ref EP73

ENERGY BANK KIT 100 6x6" 6v 100mA panels, 100 diodes, connection details etc. £59 ref EP112

PASTEL ACCOUNTS SOFTWARE, does everything for all sizes of businesses, includes word processor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual. 90 days free technical support (01342-326009 try before you buy)! SALE PRICE £9.95 ref SA12. SAVE £120!!!

PC PAL VGA TO TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in PSU, lead and software. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

YUASHA SEALED LEAD ACID BATTERIES Two sizes currently available this month. 12v 15AH at £18 ref LOT6 and 6v 10AH at just £5 ref LOT7

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc. SALE PRICE JUST £4.99 REF SA28

AUTO SUNCHARGER 155x300mm solar panel with diode and 3

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3.50 P & P PLUS VAT.

24 HOUR SERVICE £4.50 PLUS VAT.
OVERSEAS ORDERS AT COST PLUS £3.50

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS
WELCOME (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500
FAX 01273 323077

E-mail bull@pavilion.co.uk

metre lead fitted with a cigar plug. 12v 2watt. £12.99 REF AUG16P3
PROJECT STRIPPERS Small cased UNITS ideal for stripping lots of useful goodies including a smart case 120X150X50mm with feet etc., and lots of components. SALE PRICE JUST £10 FOR FIVE REF MD1 or a pack of 20 for £19.95 ref MD2

SOLAR POWER LAB SPECIAL You get TWO 6x6" 6v £30mA solar cells, 4 LEDs, waa buzzer, switch plus 1 relay or motor. Superb value kit. SALE PRICE JUST £4.99 REF SA27

13.8V 1.9A PSU cased with leads. Just £9.99 REF MAG16P3

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

SOLAR NICAD CHARGERS 4 x AA size £9.99 ref 6P47 ref 2 x C size £9.99 ref 6P477

VIEWDATA SYSTEMS made by Philips. complete with internal 1200V75 modem, keyboard, psu etc. RGB and composite outputs menu driven, auto dialer etc. SALE PRICE £12.99 REF SA18

MEGA POWER BINOCULARS Made by Helios. 20 x magnification, precision ground fully coated optics, 60mm objectives, shock resistant caged prisms, case and neck strap. £65 ref HPH11

GIANT HOT AIR BALLOON KIT Build a 4.5m circumference, 1.8m high fully functioning balloon. can be launched with home made burner etc. Reusable (until you loose it!) £12.50 ref HA1

AIR RIFLES .22 As used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets for £1.50 REF EP80

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12V DC op. Price is £25 REF: MAG15. 12v psu is £5 extra REF: MAG5P2

***MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range up to 2 km in open country. Units measure 22x5x155mm. Including cases and earpieces. 2xPP3 req'd. £37.00 p. REF: MAG30

***FM TRANSMITTER KIT** housed in a standard working 13A adaptor! the bug runs directly off the mains so lasts forever! you pay £7.00 or price is £16 REF: EP62 (kit) Transmits to any FM radio. Built and tested version now available of the above unit at £45 ref EXM54

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. By battery req'd. £14 REF: MAG14

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £14.95 Ref EF82B extra pellets (500) £4.50 ref EF80

6"X12" AMORPHOUS SOLAR PANEL 12v 155x10mm 130mA. SALE PRICE £4.99 REF SA24

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

MIXED GOODIES BOX OF MIXED COMPONENTS WEIGHING 2 KILOS YOURS FOR JUST £5.99

4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £24.95 ref R7

GYROSCOPES Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift or for educational use etc. £5 ref EP70

HYPOTHERMIA SPACE BLANKET 216x150cm aluminium foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirrors. £3.99 each ref QALD41

NICAD CHARGERS AND BATTERIES Standard universal mains operated charger, takes 4 batts + 1 PP3, £10 ref PO11D. Nicads- AA size (4 pack) £4 ref 4P44. C size (2 pack) £4 ref 4P73. D size (4 pack) £9 ref 9P12

LENSTATIC RANGER COMPASS Oil filled capsule, strong metal case, large luminous points. Sight line with magnifying viewer. 50mm dia, 86gms. £10.99 ref QM604

RECHARGE ORDINARY BATTERIES UP TO 10 TIMES! With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are charged. Automatically rejects unsuitable cells. complete with mains adaptor. BS approved. Price is £21.95 ref EP31

TALKING WATCH Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP25

RUBBER COATED HELIOS Binoculars, 10 x 25, fully coated optics. £45 ref RP1. same spec but nitrogen filled and waterproof £75 ref RP2

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU!
YOUR LICENCE! The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands. 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities. micro size just 4.25x2.5x1.75". Can pay for itself in just one day! £69 ref EP3

3" DISCS As used on older Amstrad machines. Spectrum plus's etc. £3 each ref BAR400

STEREO MICROSCOPES BACK IN STOCK Russian, 200x complete with lenses, sights, filters etc etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee!) full details in catalogue

SECOND GENERATION NIGHT SIGHTS FROM £749
RETRON Russian night sight, 1.8x, infra red lamp, 10m-Inf, standard M42 lens, 1.1kg. £349 ref RET1

LOW COST CORDLESS MIC 500' range, 90 - 105mhz, 115g, 153 x 26 x 39mm, 9v PP3 battery required. £17 ref MAG15P1

SAE FOR FREE COLOUR CATALOGUE

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

WE BUY SURPLUS STOCK FOR CASH

SURPLUS STOCK LINE 0802 660377

Edwin NC - professional EDA software for non-commercial use

Visionics UK have announced the launch of EDWin NC, a new non-commercial licenced version of their Windows-based electronic design software, EDWin. The con-commercial version is available at a fraction of the cost of the professional system, but includes all the features that have made EDWin a success worldwide.


EDWin's easy-to-use structure, running on Windows 3.1x, '95 or NT, along with its versatile, completely integrated database, have attracted engineers since it superceded Visionics' original EE Designer system.

MD Jonathan Hewer explained: "We've been led by the demands of potential customers. For years our EDA systems have been used not only in industry but in the educational sector. Students and hobby users have requested the change to buy EDWin, but the cost, which is easily justifiable to a company which will profit from productivity gains, has been prohibitive for the amateur user. Now non-commercial users can enjoy the benefits of a professional system."

Visionics recently launched EDWin NC in Belgium and Holland, where EDWin was previously little known, to test user reaction. The result, which surprised even Visionics, was over 800 systems sold within the first three weeks.

Prices now range from £49 including VAT for the basic version, which included schematics, PCB layout, 500-device library, basic autorouter, full post-processing facilities and a limit of 100 components (normal price £1163) to the de luxe 3 version at £115, which includes unlimited database, professional libraries, mixed-mode simulation and the Arizona autorouter (normal price £3513). The system comes on CD-ROM, including comprehensive manuals. Visionics FDSpice simulator, and a thermal analysis module, are also available as plug-ins.

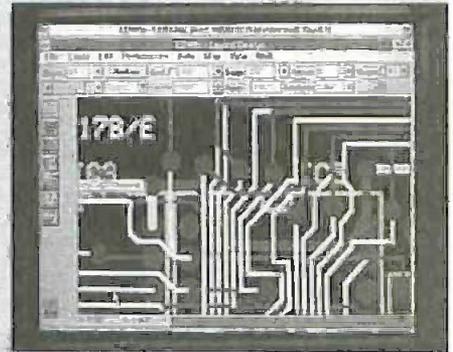EDWin NC can be purchased from Visionics' UK dealer, Swift Designs of Stevenage, Tel 01438 310133 Fax 01438 722751.



Overseas Readers

To call UK telephone numbers, replace the initial 0 with your local overseas access code plus the digits 44.

Shorts

Hitachi has doubled its production capacity of insulated gate bipolar transistors (IGBTs) in Japan to 50,000 per month. This follows increasing demand for power components, particularly in Europe. The devices are used for high-power switching in applications such as large power supplies and motor drives and are a comparatively new breed of transistor. The newest devices have lower power dissipation and more compact packaging, and the Hitachi devices range from 600V to 1200V and from 50A to 400A load currents... IBM is investing \$380 million in advances in disk drive technology, centring on magnetoresistive (MR) read heads. MR heads use changes in resistance to read magnetic data from the disk platter, instead of more conventional current-change, and have the potential to resolve smaller magnetic domains. IBM expects this innovation to make disk drives more reliable and less expensive to build, and hope to make further inroads into the commercial mass storage market... Quantum Corporation has announced 1.280 MB-per-disk versions of its Quantum Fireball TM series of 3.5-in high-performance disk drives. Offering capacities of 1.2GB (1 disk) 2.5GB (2 disks) and 3.2GB (3 disks), the drives are targeted at information-intensive commercial desktop applications. Quantum already offer Fireball drives in three 1080MB -per-disk format. The drives are designed to operate fast and provide a high level of error correction. Standard prices for the new line vary at time of writing from US \$277 for the 1.2GB set-up to US \$415 for the 3.8GB set-up. Enquiries 0171 835 1001.



You can't get enough... ..of a good thing!

Now you can have even more of your favourite magazine. As from this issue, *Electronics Today International* will be published on a four weekly cycle - which means that you get 13 instead of 12 in the calendar year.

This does mean that our normal 1st Friday publication date cannot apply throughout the year - so you will need to keep a close eye on the 'Next Month' column where the date will be prominently displayed. Furthermore, issues will not carry the 'month' of issue, but will display our Volume and issue Number. This is Volume 26 No.1. The next issue, Volume 26 No.2 will publish on 31 January. Volume 26 No.3 will be on sale 28 February. Subscriptions continue to be for twelve issues.

TRANSISTORS

PART	PRICE	PART	PRICE	PART	PRICE	PART	PRICE
BU105	80P	BU498D	75P	BUT18AF	80P	MJ15024	400P
BU108	100P	BU499	85P	BUT39V	1700P	MJ15025	700P
BU109	80P	BU426A	70P	BUT35A	100P	MJE13004	100P
BU110	90P	BU506DF	120P	IRF450	650P	MJE13005	60P
BU111	100P	BU508APH	80P	IRF520	150P	MJE13007	100P
BU124	60P	BU508AF	95P	IRF530	300P	MJE13009	100P
BU125	100P	BU508APH	80P	IRF540	300P	MJE15028	200P
BU126	65P	BU508D	90P	IRF610	150P	MJE15029	200P
BU133	125P	BU508DF	115P	IRF630	150P	MJE15030	250P
BU137	150P	BU508DR	130P	IRF640	400P	MJE15031	400P
BU180	100P	BU508V	110P	IRF730	175P	MJE16004	125P
BU184	100P	BU508VF	100P	IRF820	150P	OC28	350P
BU204	65P	BU801	70P	IRF830	225P	OC29	250P
BU205	70P	BU806	70P	IRF840	200P	OC35	350P
BU206	100P	BU807	60P	IRF930	400P	OC36	250P
BU207	150P	BU2502A	130P	IRF9540	300P	S2000A3	175P
BU208	70P	BU2508AAF	130P	IRF9510	200P	S2000AF	175P
BU208A	200P	BU2508D	150P	IRF9620	225P	S2055A	175P
BU208AT	130P	BU2508DF	150P	IRF9630	325P	S2055AF	200P
BU209	90P	BU2520AF	225P	IRF9640	375P	2N3053	18P
BU225	120P	BU2520DF	225P	IRFBC30	200P	2N3054	40P
BU226	120P	BU2525AF	325P	IRFC40	400P	2N3055	38P
BU312	90P	BUH315	200P	MJ2501	100P	2N3055H	50P
BU325	55P	BUH515	200P	MJ2855	55P	2N3440	45P
BU326A	75P	BUH517	275P	MJ15003	250P	2N3441	175P
BU405	60P	BUH715	425P	MJ15004	300P	2N3442	85P
BU406D	85P	BUT11AF	55P	MJ15015	250P	2N3771	85P
BU407	55P	BUT12	80P	MJ15016	350P	2N3772	90P
BU407D	75P	BUT13	310P	MJ15022	250P	2N3773	100P
BU408	60P	BUT18	80P	MJ15023	400P		

SATELLITE PSU REPAIR KITS

Experience shows that 50% of all receiver power supplies 'bounce' unless the correct precautionary measures are taken when being serviced. A kit of all the recommended parts is supplied for the most popular models, which when fitted should overcome this.

MAKE & MODELS	ORDER CODE	PRICE
PACE PRD800, PRD900	SATPSU1	650P
PACE SS900, 9200, 9010, 9210, 9020, 9220	SATPSU2	650P
AMSTRAD SRD510, SRD520	SATPSU3	650P
AMSTRAD SRD500	SATPSU4	650P
AMSTRAD SRX340, SRX345, SRX350	SATPSU5	650P
PACE D100/150	SATPSU6	650P
CHURCHILL D2MAC	SATPSU7	650P
PACE MSS100	SATPSU8	730P
PACE MSS200/300 APOLLO	SATPSU9	650P
PACE MSS500/1000	SATPSU10	1230P
FERGUSON SRD4	SATPSU11	835P
ECHOSTAR SR5500	SATPSU12	1735P
ECHOSTAR 6500/7700/8700	SARPSU13	3125P
AMSTRAD SRD600	SATPSU14	3125P
MIMTEC (Sorensen)	SATPSU15	775P
AMSTRAD SRD700/SR950/SRX100/302		
SRX501/502/1002/2001/SRD2000 SAT250	SATPSU16	730P

PACE 9000 SWITCH MODE TRANSFORMER
ORDER CODE: PACE9000 PRICE 800p

SERVICE AIDS

DESCRIPTION	VOLUME	CODE	PRICE
VIDEO HEAD CLEANER	75 ML	SP01	160P
VIDEO HEAD CLEANER	200 ML	SP27	250P
SWITCH CLEANER	178 ML	SP02	170P
SUPER 40	400 ML	SP15	250P
SILICONE GREASE	200 ML	SP03	210P
FREEZE IT	170 ML	SP04	300P
FREEZE IT	420 ML	SP16	600P
FOAM CLEANER	400 ML	SP05	160P
ANTI STATIC	150 ML	SP06	190P
AEROKLEANE	250 ML	SP07	220P
AERO DUSTER	150 ML	SP08	310P
AERO DUSTER	400 ML	SP17	550P
PLASTIC SEAL	200 ML	SP02	250P
GLASS CLEANER	250 ML	SP10	160P
COLDKLENE	250 ML	SP13	230P
EXCEL POLISH 50	250 ML	SP18	150P
ADHESIVE 120	400 ML	SP19	240P
LABEL REMOVER 130	200 ML	SP20	240P
REFURB 140	400ML	SP21	220P
TUBE SILICON GREASE	50 GRAMMES	SP11	220P
TUBE SILICON SEALANT WHITE	75ML	SP22	260P
TUBE SILICON SEALANT CLEAR	75 ML	SP23	260P
TUBE HEAT SINK COMPOUND	25 GRAMMES	SP12	150P
DRIVE CLEANER	200ML	SP24	150P
SCREEN CLEANER	200 ML	SP25	150P
COMPUTER CARE KIT		SP26	2100P
ANTI-STATIC FOAM CLEANER	400 ML	SP28	175P
AIR-DUSTER	400 ML	SP29	450P

ALL THE ABOVE ITEMS ARE MANUFACTURED BY SERVISOL
IF YOU PURCHASE MORE THAN ONE SERVISOL PRODUCT POSTAGE & PACKAGE WILL BE CHARGED AS FOLLOWS: 300p FOR 5 CANS 450p FOR MORE THAN 5 CANS

GRANDATA LTD

K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE
SOUTHWAY, WEMBLY, MIDDLESEX, ENGLAND HA9 0NB
Telephone: 0181-900 2329 Fax: 0181-903 6126
OPEN Monday to Saturday
Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00

FUSES

CURRENT RATING	TIME LAG (20mm)		QUICK BLOW (20mm)	
	ORDER CODE	PRICE	ORDER CODE	PRICE
100mA	FUSE36	75P	FUSE37	60P
160mA	FUSE01	75P	FUSE17	60P
250mA	FUSE02	75P	FUSE18	60P
315mA	FUSE 03	75P	FUSE19	60P
400mA	FUSE04	75P	FUSE20	60P
500mA	FUSE05	75P	FUSE21	60P
630mA	FUSE06	75P	FUSE22	60P
800mA	FUSE07	60P	FUSE23	60P
1A	FUSE08	60P	FUSE24	60P
1.25A	FUSE09	60P	FUSE25	60P
1.6A	FUSE10	60P	FUSE26	60P
2A	FUSE11	50P	FUSE27	60P
2.5A	FUSE12	50P	FUSE28	60P
3.15A	FUSE13	55P	FUSE29	50P
4A	FUSE14	55P	FUSE30	50P
5A	FUSE15	60P	FUSE31	50P
6.3A	FUSE16	60P	FUSE32	60P

CERAMIC PLUG TOP

CURRENT RATING	ORDER CODE	PRICE
3A	FUSE33	100P
5A	FUSE34	100P
13A	FUSE35	100P

20mm CERAMIC TIME LAG

CURRENT RATING	ORDER CODE	PRICE
6.3A	FUSE38	100P
8A	FUSE39	100P
10A	FUSE40	100P
3.15A	FUSE41	65P
4A	FUSE42	65P
5A	FUSE43	85P

32mm CERAMIC SLOW BLOW

CURRENT RATING	ORDER CODE	PRICE
8A	FUSE44	185P
10A	FUSE45	185P
15A	FUSE46	185P
20A	FUSE47	210P

38mm CERAMIC TIME LAG

CURRENT RATING	ORDER CODE	PRICE
10A	FUSE48	825P

ALL THE ABOVE PRICES ARE FOR PACKS OF 10 FUSES

NB. ALL FUSES ARE MADE IN THE UK AND FULLY MEET BS4265 & BS1362 SAFETY STANDARDS AND SHOULD NOT BE COMPARED WITH CHEAP IMPORTED TYPES.

SOLDERING ACCESSORIES

ANTEX SOLDERING IRONS

DESCRIPTION	CODE	PRICE
25 WATT 240 VAC (XS25W 240V)	S101	900P
15 WATT 240 VAC (XS 15W 240V)	S102	900P
25 WATT SPARE ELEMENT	S103	450p
15 WATT SPARE ELEMENT	S104	450p

SOLDERING STAND & SPONGES

DESCRIPTION	CODE	PRICE
SOLDERING STAND (MADE BY ANTEX)	S108	350p
SPARE SPONGE	S109	55p

SOLDER

DESCRIPTION	CODE	PRICE
18 SWG 500 GRAMMES	S110	500P
20 SWG 500 GRAMMES	S111	650P
22 SWG 500 GRAMMES	S112	700P

DESOLDERING AIDS

DESCRIPTION	CODE	PRICE
SOLDER MOP STANDARD GAUGE 1.2mm x 1.5 METRE	S107	80P
SOLDER MOP 1.2mm x 10 METRE	S113	400P
DESOLDERING PUMP	S105	320P
SPARE NOZZLE	S106	60P

8 way PREPROGRAMMED Universal remote Control

A single remote control to operate Televisions, Videos and Satellite Receivers. Plus Auxiliary Options!!

- Replaces up to 8 remotes with one
- Simple 4 digit setup routine
- Controls 1000's of models
- Teletext functions with Fastext
- Clear (large key) layout
- Code Search Facility
- Stylish and easy to operate
- Replace broken or lost remotes
- Original Remote not required

Order Code: 8 WAY Price: 1450P + VAT

8 way PREPROGRAMMED Universal remote Control

The Optimum 8 way universal remote control preprogrammed to operate up to 8 other remote controls for Televisions, Videos and Satellite Receivers. Plus Auxiliary Options!!

- Pre-programmed with learning capability
- Replaces up to 8 remotes with one
- Jog/ Shuttle thumb control
- Illuminated key pad
- Clear key layout
- Easy access secondary keypad
- Teletext & Fast text function
- Stylish and easy to operate
- Replace broken or lost remotes
- Original Remote not required
- Freefone, Helpline (UK Only)

Order Code: OPTIMUM 8 Price: 2100P + VAT

PLEASE PHONE US FOR TYPE NOT LISTED HERE AS WE ARE HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR LARGE QUANTITIES

Please send £1 P&P and VAT at 17.5%. Govt. Collages, etc.
Orders accepted. Please allow 7 days for delivery. Prices quoted are subject to stock availability and may be changed without notice.
TV and video parts sold are replacement parts.
Access & Visa Card accepted

WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND TDA SERIES. PLEASE RING US FOR FURTHER INFORMATION.

Electronics Industry survey confirms Engineering shortage

The Federation of the Electronics Industry (FEI) set up a task force in 1996 to address the issues of education and training in the electronics industry, from the point of view of those businesses that employ school leavers, graduates and indeed anyone with Electronics qualifications and/or experience.

The FEI, in consultation with the DTI (which provided some of the financing) commissioned a survey of 250 FEI member companies with two main objectives:

- to gather information on the education, training and skills perspectives of FEI members and other employers within the UK electronics industry, and
- to clarify FEI members' priorities in this area, in order to refine the focus of attention of the Federation's Education and Training Task Force.

In order to do this, a questionnaire was sent to FEI members. The findings were then analysed, and also compared with other recent surveys.

The questionnaire covered three main subject areas: information about the main activities of each company, and the money they allocate to training; how aware the companies are of government schemes available to help with training, and what problems the companies had with obtaining trained staff and extra training for their staff. A fourth section, requested by the DTI, asked for information on how many engineers the companies needed, and what specific classes of engineer were needed.

The questionnaire was refined in consultation with the DTI, as well as other interested bodies and a leading market research company, before being sent out to 250 member companies.

In the event, replies were received from 39 companies by the deadline. This response, of only 15%, caused a certain amount of concern, so much so that a section of the report was dedicated to examining the possible reasons.

Notwithstanding the limited statistical value of the survey's findings, the responses of genuine companies active in the electronics industry cannot fail to be of some interest to anyone working in electronics.

Firstly, nearly all the respondents are providing some training or re-training to their employees. Whether this is representative across the industry, or whether this applies only to businesses most concerned with staff training, is not known. The other side of this coin is that the majority of training seems to be either "induction training" (getting new recruits "up to speed" on the job) or product knowledge training (specific to the individual business, and not readily transferable). 21 of the 39 companies offer management training (although there is no detailed analysis of this), and 17 of the 39 offer technical training (again, without a clear distinction between "technical" and "induction/product" training, which is of necessity technical in this field). All companies were reluctant to estimate their financial input to training.

It was interesting to read that, for new recruits (including school and college leavers), the greatest need for better skills was in the area of literacy and communications, closely followed by initiative, problem solving, teamwork and "improving performance". There was far less dissatisfaction with numeracy and calculating, despite the recent publicity about poor maths results in UK schools, and concern about "other core skills" are almost non-existent.

None of these concerns is new to the 1990s, but it is significant to see them coming so squarely from within the electronics industry. There is no doubt that a sound basis in maths is important to engineering competence. There has long been a perception that technicians and engineers are to be kept in the back room and not required to communicate. Whether the new attention to literacy and communication means that managements are genuinely endeavouring to improve teamwork, or whether they are simply wishing that engineers should be easier to extract reports from is not reported by the survey. Historically, of course, engineers have always felt that it is Management needs to improve its communication and listening skills.

There is also more concern about the shortfall in non-technical skills than there is in technical skills (although only by a narrow margin), despite the fact that the most serious need for personnel is for engineers.

In recruitment, the real difficulty emerges: finding technical employees is top of the list of employers' main concerns. The industry shortfall of trained engineers and technicians is clearly reflected in the survey's results. In the category of "hard-to-fill vacancies", "Engineers" - Sales, Design, Electrical, Field, etc. - elicited 29 responses, around 75 per cent. The next category - test technicians - elicited only seven responses, and the next one after that - sales reps - only five.

In the category of Engineers, the need for Design engineers - engineers actually able to devise new equipment and new means of carrying out operations - is paramount.

"Technical Recruitment Difficulties represent the greatest need" is the conclusion of this section. In plain terms, this should mean that there are jobs there, waiting for people to fill them, at this time when there is still high unemployment throughout the UK.

The replies to many other sections are presented as comments rather than statistics, as they were felt to be individual to analyses into classes. The underlying themes, though, are pretty clear. "Providing design and applications training that bridges the gap between graduation and being effective in a commercial environment" "More vocational courses with transferable skills" "Support on development projects" "More trained engineers" "More IT training" "Higher basic educational standards" "Higher status to technical disciplines" "Competence development" "Tax incentives for individuals funding their own education" and so on.

Basically, industry is looking for people who know how to do the job, and those who understand it well enough to further develop their own skills on the job. It is felt that schools and colleges should provide basic skills, especially the "three Rs", and that government should provide more incentive to people trying to improve and extend the skill-base, whether their own or their employees'. They want more understanding of industry passed on to students in schools and universities, and more access to management skills as well as technical skills, as teamwork, time- and resource-management is necessary for everyone above the level of junior technician.

MODSMODSMODSMODSMODSMODS

Phoney Phone (November 1996)

IC1 appeared as a 7555. It should be the dual 7556, also available from Maplin.

Camplight (October 1996)

The correct wire width for winding the custom transformer is 0.20 mm insulated copper wire. This information and some extra part suggestions also appeared on page 20 of the December issue of ETI.

GMP MOS-FET POWER AMPLIFIERS
HIGH POWER. TWO CHANNEL. 19 INCH RACK

**THOUSANDS PURCHASED
BY PROFESSIONAL USERS**



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)

MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. VU meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

★ USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/4" (2U) x D11"
MXF400 W19" x H5 1/4" (3U) x D12"
MXF600 W19" x H8 1/4" (3U) x D13 1/2"
MXF900 W19" x H5 1/4" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15

SPECIALIST CARRIER DEL. £12.50 EACH

GMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable OIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with GMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE

★ ECHO & SOUND EFFECTS ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED VU meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fader, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

- TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 = 50p P&P.
 - TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 = 50p P&P.
 - TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 = 50p P&P.
 - TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 = 50p P&P.
 - TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 = 50p P&P.
- LEVEL CONTROL** Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 = 50p P&P.

IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET
FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

IBI FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR

IBI FC 12-200WATTS (100dB) PRICE £176.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair



IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99, 250W £99.99
400W £109.95 P&P £2.00 EACH

**THREE SUPERB HIGH POWER
CAR STEREO BOOSTER AMPLIFIERS**

150 WATTS (75 - 75) Stereo, 150W Bridged Mono
250 WATTS (125 - 125) Stereo, 250W Bridged Mono
400 WATTS (200 - 200) Stereo, 400W Bridged Mono

ALL POWERS INTO 4 OHMS

Features:
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

POSTAL CHARGES PER ORDER £100 MINIMUM. ORDERS
ORDERED FROM SCHOOLS, COLLEGES, GOVT. BODIES, P.L.C.s ETC.
PRICES INCLUSIVE OF V.A.T. SALES QUANTITIES 1/30A AND
ACCESS ACCEPTED BY POST, PHONE OR FAX.

GMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market (i.e. industry, leisure, instrumental and Hi-Fi etc.) When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible VU meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



GMP/MF 100 Mos-Fet Output power 110 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 45V/uS,
T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R.
-110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



GMP/MF 200 Mos-Fet Output power 200 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 50V/uS,
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
-110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



GMP/MF 300 Mos-Fet Output power 300 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 75V/uS,
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
-110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



GMP/MF 450 Mos-Fet Output power 450 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
-3dB, Damping Factor >300, Slew Rate 75V/uS,
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
-110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2
Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P



GMP/MF 1000 Mos-Fet Output power 1000 watts
R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms,
frequency response 1Hz - 100KHz -3dB, Damping
Factor >300, Slew Rate 75V/uS, T.H.D. typical
0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan
Cooled, D.C. Loudspeaker Protection, 2 Second
Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS:
STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz.
PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS
775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS



**LARGE SELECTION OF SPECIALIST LOUDSPEAKERS
AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER
GRILLES, CROSS-OVERS AND HIGH POWER, HIGH
FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E.
(80p STAMPED) FOR COMPLETE LIST.**

McKenzie and Fane Loudspeakers are also available.

EMINENCE - INSTRUMENTS, P.A. DISCO ETC

- ALL EMINENCE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE. LEAD GUITAR, EXCELLENT MID, DISCO. RES. FREQ. 72Hz. FREQ. RESP. TO 4KHz. SENS 97dB. PRICE £32.71 = £2.00 P&P
 - 10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 71Hz. FREQ. RESP. TO 7KHz. SENS 97dB. PRICE £33.74 = £2.50 P&P
 - 10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. RES. FREQ. 65Hz. FREQ. RESP. TO 3.5KHz. SENS 99dB. PRICE £43.47 = £2.50 P&P
 - 12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE. LEAD GUITAR, DISCO, STAGE MONITOR. RES. FREQ. 45Hz. FREQ. RESP. TO 6KHz. SENS 100dB. PRICE £35.84 = £3.50 P&P
 - 12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL STAGE MONITOR. RES. FREQ. 42Hz. FREQ. RESP. TO 10KHz. SENS 98dB. PRICE £36.87 = £3.50 P&P
 - 12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE. GUITAR, DISCO, VOCAL, EXCELLENT MID. RES. FREQ. 58Hz. FREQ. RESP. TO 6KHz. SENS 98dB. PRICE £46.71 = £3.50 P&P
 - 12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS. LEAD GUITAR, KEYBOARD, DISCO ETC. RES. FREQ. 47Hz. FREQ. RESP. TO 5KHz. SENS 103dB. PRICE £79.19 = £3.50 P&P
 - 15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. RES. FREQ. 46Hz. FREQ. RESP. TO 5KHz. SENS 99dB. PRICE £50.72 = £4.00 P&P
 - 15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. RES. FREQ. 39Hz. FREQ. RESP. TO 3KHz. SENS 103dB. PRICE £73.34 = £4.00 P&P

EARBENDERS - HI-FI, STUDIO, IN-CAR, ETC

- ALL EARBENDER UNITS 8 OHMS** (Except EB4-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohms)
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
 - 9" 50WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz. FREQ. RESP. TO 7KHz SENS 97dB. PRICE £8.90 + £2.00 P&P
 - 10" 50WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz. FREQ. RESP. TO 5KHz, SENS. 99dB. PRICE £13.85 = £2.50 P&P
 - 10" 100WATT EB10-100 BASS, HI-FI, STUDIO. RES. FREQ. 35Hz. FREQ. RESP. TO 3KHz, SENS 95dB. PRICE £30.39 = £3.50 P&P
 - 12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES. FREQ. 26Hz. FREQ. RESP. TO 3 KHz, SENS 93dB. PRICE £42.12 + £3.50 P&P
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
 - 5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz. FREQ. RESP. TO 20KHz. SENS 92dB. PRICE £9.90 = £1.50 P&P
 - 6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 33Hz. FREQ. RESP. TO 20KHz. SENS 94dB. PRICE £10.99 + 1.50 P&P
 - 8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz. FREQ. RESP. TO 18KHz. SENS 89dB. PRICE £12.99 = £1.50 P&P
 - 10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 35Hz. FREQ. RESP. TO 12KHz. SENS 98dB. PRICE £16.49 = £2.00 P&P

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 85-100MHz VARS-CAP CONTROLLED PROFESSIONAL PERFORMANCE. RANGE UP TO 3 MILES. SIZE 2 1/2 x 1 1/2 inches. SUPPLY 1.5V @ 8.5AMP. PRICE £14.85 = £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz VARS-CAP TUNED, COMPLETE WITH VERY SENS FET MC. RANGE 100-300m. SIZE 2 1/2 x 1 1/2 inches. SUPPLY 9V BATTERY. PRICE £9.80 = £1.00 P&P

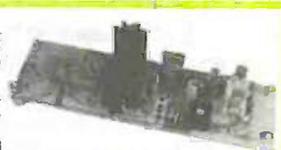


PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNIVERSITY HOUSE, 1 WAY, SOUTHFIELD ON SEA,
ESSX, SSG 6TH

TEL: 0702 527572 FAX: 0702 426049

Smart Cards by the Million

Nick Hampshire takes a look at how smart cards are developing and examines some of the problems facing this technology in the future.

If you open the Sunday papers, or one of the more heavyweight dailies, you can almost guarantee to find an article about some new application for smart cards, those credit card sized plastic cards containing an embedded integrated circuit. They are rapidly becoming another one of those technological products that we all accept as being a part of everyday life.

We use them to make phone calls, to access restricted areas, to pay for goods and services, to travel on a bus or train, and in the near future we will even be using them to prove that we are who we claim to be. Not bad for a concept which, however obvious it may seem today, is only a little over ten years old and encountered much scepticism in its early days. It is one of those products which was conceived by several people in different parts of the world at around the same time, in the early 1980s. However, most of the pioneering work, including nearly all the early commercial applications, took place in France.

It was the adoption of smart card technology by French Telecom as the basis of their phone card technology which gave smart cards the initial boost. British Telecom opted for what they regarded as the more reliable, and cheaper, holographic card technology which is only just being obsolesced. Other users opted for the magnetic stripe backed card, like the familiar credit card.

Both mag strip and smart card technologies were at that time also being used for applications such as access control, and of course magnetic stripe cards were widely used in finance in the form of credit cards and charge cards. Both of the widely used phone card technologies performed the same function. They stored a preset number relating to phone units which could be used; this number was then decremented as the card was used. When it reached zero the card was simply thrown away and a new one bought.

In the holographic cards the value was stored as an optical bar with a length equal to the number of units, as each unit was used the bar was shortened by one unit length by fusing the plastic at that point with a heater. In the smart card version, the PROM chip in the card had a fusible link blown for each unit used. Both card technologies performed the same function, both were used once and then disposed of, so why is the smart card replacing the holographic card in phone boxes across the UK?

The answer is that smart card technology has advanced to a point where it can be used for much more than simply paying for phone usage. They are no longer necessarily a disposable one-function item, but as a key part of the financial system of the future.

Smart card technology

There are three common types of smart card currently in use. The simplest is the preset stored value card such as phone cards. These cards are simply thrown away when all the stored value is used up. Then there is the rechargeable stored value

card, such as those used as utility payment cards, where the card can be reused by putting new value into it using a special terminal. Finally there is the intelligent card, such as those being used in some advanced electronic purse systems, where a microprocessor built into the card is used to give added security and additional features. There are two types of card design, those with contacts and those without. The commonest types of smartcard simply consist of an




British Telecom phone smartcard

ic mounted in a credit card sized piece of plastic sheet with a set of gold plated contacts in a fixed position on one side of the

card. In most such cards the ic is basically a one-time programmable Read Only Memory, which can either be pre-programmed to output a particular numeric value or can have the stored value decremented by the card reader as is the case with phone cards. Simple rechargeable, or

A Modex smart card

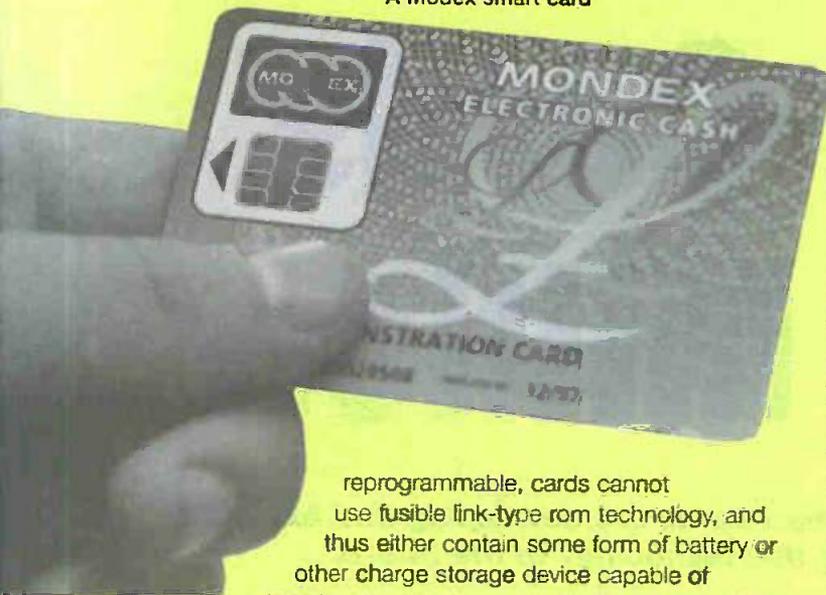

reprogrammable, cards cannot use fusible link-type rom technology, and thus either contain some form of battery or other charge storage device capable of keeping the data in a ram chip for a reasonable period, or in an eeprom. Such cards are

commonly used in access control systems to contain additional data about the authorised user and permitted access areas.

The intelligent cards may look no different, but they are infinitely more sophisticated and the reason why there is a current explosion in applications for smart card technology. Intelligent cards usually contain a fast embedded microprocessor and large memory capacity as well as some form of charge storage to ensure continuing functioning of the processor over very long periods. The embedded processor means that such cards can use advanced encryption techniques which allow them to be used in financial applications, such as the new electronic purse systems, that must be secure against fraudulent use. The smart cards of the future will be even more sophisticated. In the high tech battle against fraud they will have sufficient embedded intelligence to recognise the owner's retinal pattern or palm print. Within the next couple of years we will see the development of smart cards containing several Mbytes of memory and high speed 64bit RISC processors.

Contactless cards are favoured by the utilities, in particular the transport companies, since the card does not need to be inserted into the card reader, but only come close to it. This is important for two main reasons; firstly it allows the card checking time to be reduced to an absolute minimum, very important when faced with large numbers of commuters eager to get home. Secondly, it is more reliable, since there is no problem with contact wear on the card reader due to heavy usage.

Mitsubishi are a major designer of contactless smartcards. Those seen so far employ electromagnetic coupling to transfer data between the card and a transceiver unit at up to 25.6kbps and at a distance of up to 80cms, and an updated design is expected in 1997. The cards incorporate an 8-bit microcontroller with on-chip rom and ram, and have been designed to form part of an integrated system with transceiver units linked via a network to a host controller. Contactless cards tend to be much thicker, since they incorporate a transmitter and receiver with aerial coil, in addition to a charge-storage device. Most contactless cards are of the rechargeable intelligent variety; this is because the card's extra electronics makes them too expensive to be disposable.

Smart card applications


The development of the smart phone card over ten years ago demonstrated that the technology could be economically used as a replacement for cash. Not only does it demonstrate that the technology could be used, but it also showed that there was widespread public acceptance for the idea. The development of the smart phone card also had the effect of developing all the techniques for very low cost mass production of such cards, together with the reader technology. This in turn has led to on-going research into smart cards, research which has resulted in both the advanced card technology now in use and the multitude of applications which we see around us today.

Rather than look at all the enormous number of different applications for smart cards we will examine just three types of application in some greater depth. These are: smart cards for access control; smart cards as a ticketing system in public

transport; and smart cards as a means of transferring cash between individuals, retailers, banks, etc. These three types of application are perhaps the most important, because they will affect the lives of all of us within the next few years.

Anyone who works in a job where there is restricted access to certain areas, for safety or

A London Transport smart card reader

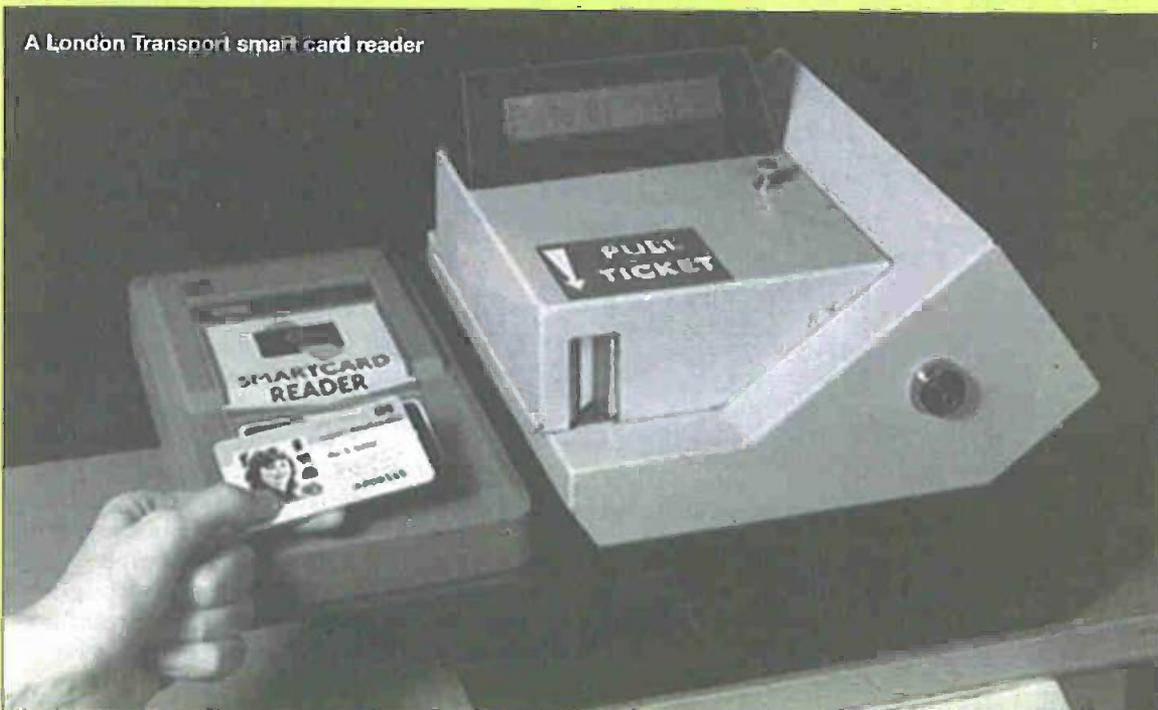

security reasons, will be familiar with the badge type systems which have been in use for many years. These credit-card sized plastic badges usually bear a photo of the individual, and some text giving name, job title, access authorisation etc. These cards usually carry a mag stripe on the back which is used together with a PIN number to gain access to restricted areas by means of a card reader and keypad controlled door lock.

The smart card version is essentially exactly the same, except that there is no mag stripe. Instead the card is a contactless smart card which can be read by the door lock system without the owner having to swipe it through a reader. So, what is the advantage of the smart card system over the mag stripe system?


One advantage is that it is more robust, mag stripes are easily damaged, and the data can be destroyed by coming in contact with a magnetic field. It is also easier to use because there is no need to physically swipe the card through the reader. However, perhaps the biggest advantage is the one that is least obvious to any user. A contactless smart card with a reasonable sensitivity across a range of several metres cannot only be used to open doors, it can also be used to track the location of the person carrying the card. In fact, card readers can be placed anywhere to provide virtually unlimited security control.

Smart card ticketing systems are basically another type of access control system, and once again basically replace the widely used mag stripe cards that are used for season tickets. The public transport operators, such as the railways, underground, and bus companies see smart cards as a replacement for the existing paper tickets which can offer the operators greater flexibility and information feedback than is otherwise possible.


Probably the biggest smart card ticketing scheme in Europe is about to be launched by London Transport. It will involve contactless cards being issued to all London Transport season ticket holders. The cards will be read by terminals on every underground station access gate, and on every bus. All terminals will be linked to a central computer systems that will give the operators an instant picture of passenger movement across the city.

The use of smart cards gives LT an increased number of ticketing options in addition to the existing one day and season travel cards. For example it will allow travellers to have pre-paid cards which will be decremented in value as they are used, in much the same way as a phone card. The LT cards will be rechargeable and passengers will be able to recharge their cards as required at terminals located in underground stations, as well as local shops, post offices, etc. London Transport see enormous advantages in such a smart card ticketing system, advantages which well outweigh the enormous cost of implementing it.

The main advantage is that will allow them to build up a very detailed analysis of exactly how passengers use the public transport network. This data will allow them to optimise scheduling to cater for the changing pattern of usage. Smart fare cards also have the advantage of reducing the need to handle large quantities of cash, something which will both reduce the enormous expenses involved. Smart cards will also help reduce ticket fraud and theft. Because the system will be able to track the position of any smart card carrying passenger on the network, it will be possible to automatically notify the police of the illegal use of a card and have the illegal user apprehended at the next stop. Also, because all records will be stored on the central control computer it will be possible to compensate the owner for any illegal use.

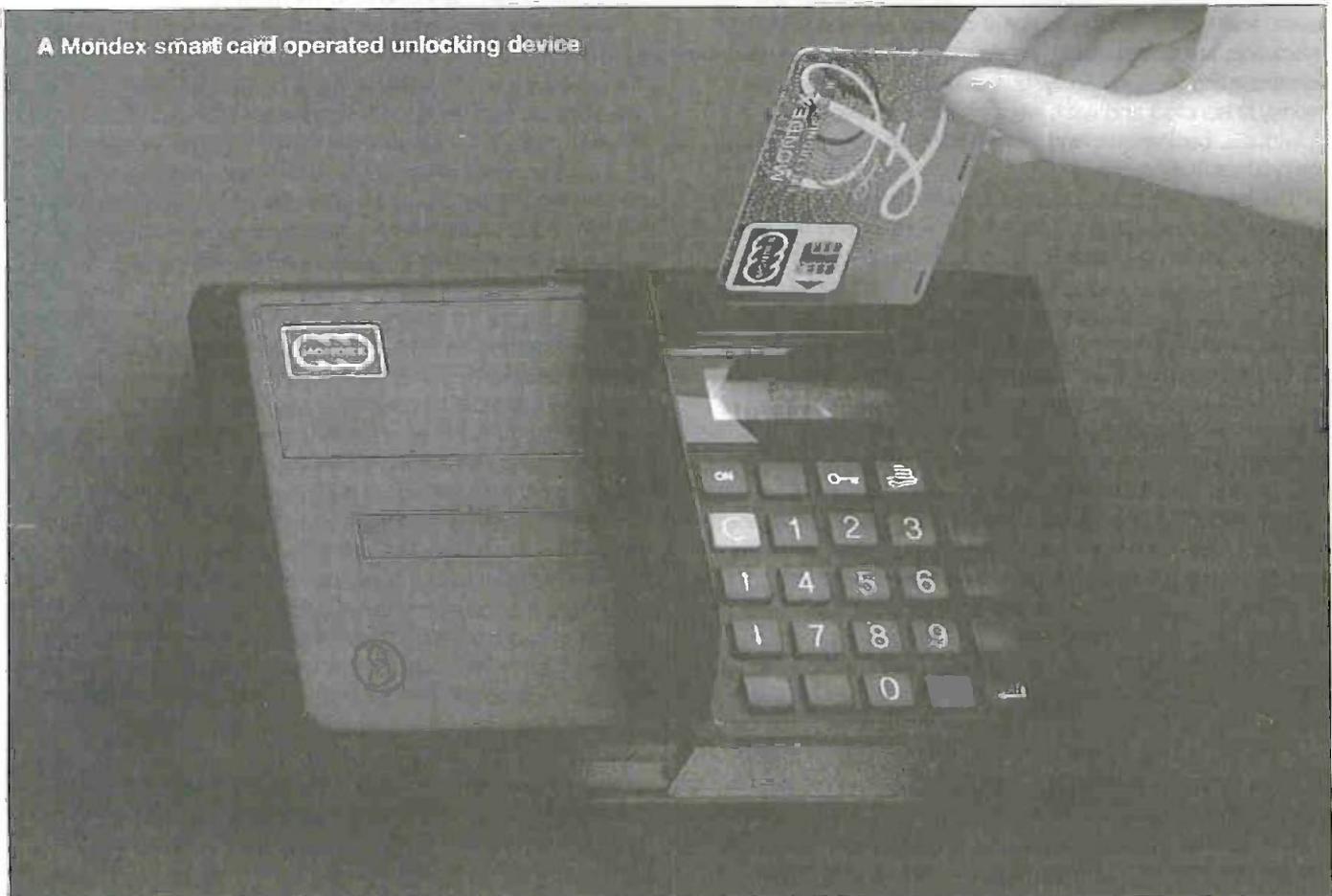

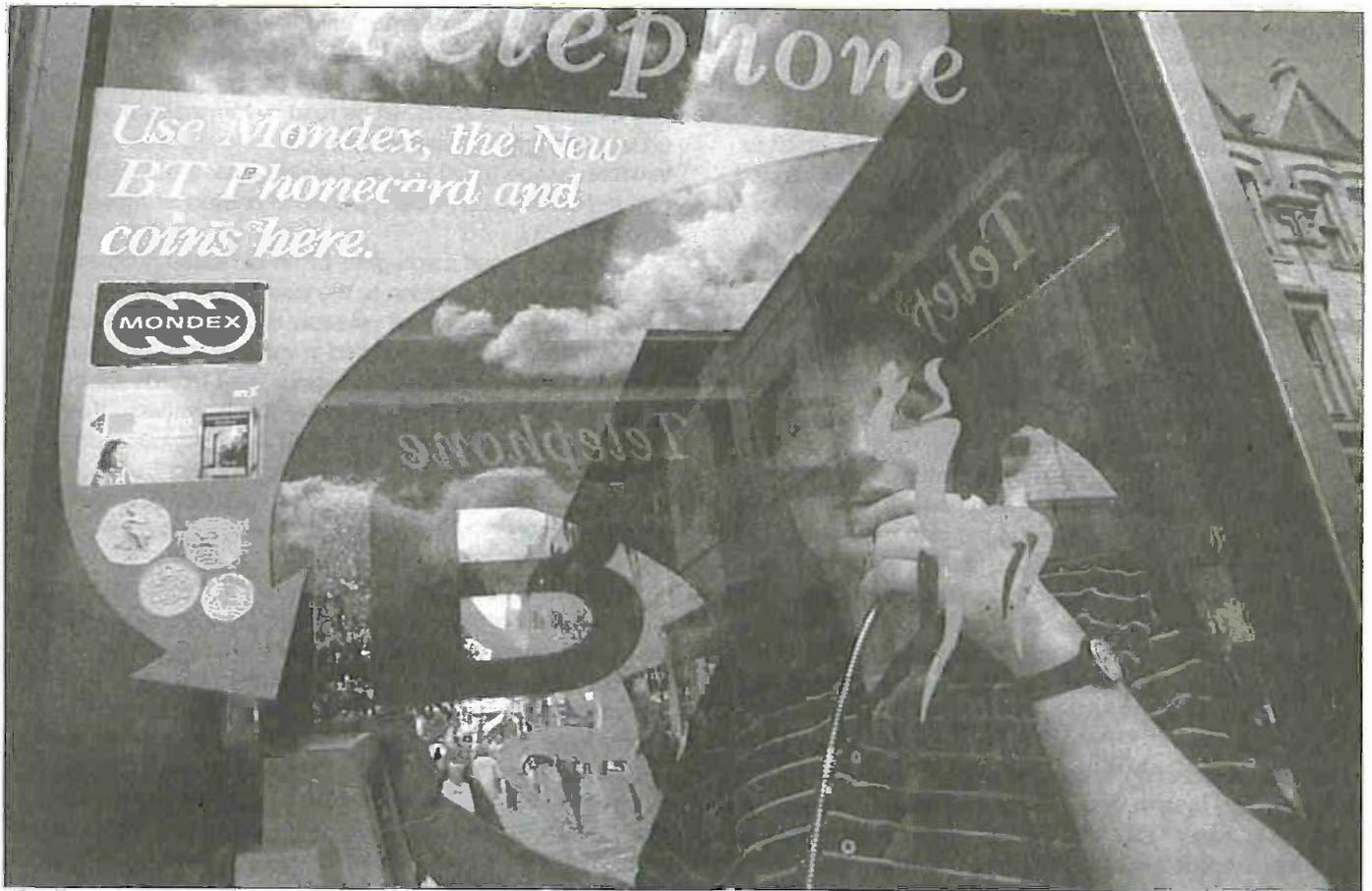A Mondex smart card operated unlocking device



The electronic purse

It is the ability to securely store monetary value within a smart card which has attracted the most interest in the last few years, and led to the development of what are known as 'electronic purse' systems. The development of this technology will according to many analysts revolutionise the way that money is handled and will have an enormous impact on individuals, businesses, and governments in the early part of the next century.

The 'electronic purse' system is based around a smart card that has stored within it a digital value representing the amount of money which has been put in the electronic purse. The card, the size of a standard credit card, locks into a special electronic wallet which makes it useless to anyone but the owner. The wallet, which looks like a small calculator with keypad and display, is accessed by a security PIN code.

Probably the most advanced 'electronic purse' system in the world is run by Mondex, a consortium of National Westminster Bank, Midland Bank, British Telecom, plus 17 other banks, and now 51% owned by the Mastercard international credit card consortium. A rival system is VisaCash, from Visa, the other main international credit card consortium. This card, which was given a test launch at the Atlanta Olympics this year, is expected to be in operation in Leeds and a couple of other UK cities within the next year. Since the middle of 1995 the Mondex system has been undergoing a large scale public test in Swindon (population 190,000). In this trial over 12,000 people were issued with Mondex cards, and over 700 retailers supplied with terminals capable of taking Mondex cards. In addition, the Mondex card can be used in many Swindon telephone boxes and via bank ATM machines.

The test has proved very successful, with customers able to use the card for buying everything from an evening paper from

a street news-vendor, to a drink in the local pub. The test has now come to an end, and Mondex are planning a UK national launch of some time in the next six months.

The survey associated with the test has shown that over 21% of the member bank's customers have taken up Mondex, this equates to a UK national figure of 2.5million people. The average user has been loading between £25 and £30 into the Mondex card, and the majority of purchases are for less than £5, with fast food, newspapers, bus fares, confectionery, and car parking tickets, being the most frequently purchased items. Supermarkets accounted for the largest value purchases and were the biggest users in terms of value, followed by department stores and petrol stations.


According to the survey, cash was previously the preferred payment method for 98% of sales in a newsagent, with Mondex card holders this has dropped to 32%, with 66% using their cards as the preferred payment method. Interestingly, 77% of users felt that the Mondex card was safer than cash, and 90% found it very easy to use. The great advantage of the Mondex system, unlike the competing VisaCash system, is its complete anonymity. It has been designed to be exactly like cash; the transactions are not logged on some central computer, the card value is simply incremented or decremented. Cash can be loaded into the card from another card, via the wallet, or from a bank ATM machine, and even a phone box can be used to transfer cash between individuals, and between an individual and the bank.

The 'electronic purse' technology is seen by the major banks of over 26 countries, including most EU member states, as the key component in a long term goal to abolish 'cash'. The abolition of cash is seen by both banks and retailers as a very important goal. Handling cash is expensive, and in the UK alone is estimated to add over £4.5billion per annum to overall

EASY-PC Professional XM

Schematic and PCB CAD

From Super Schematics

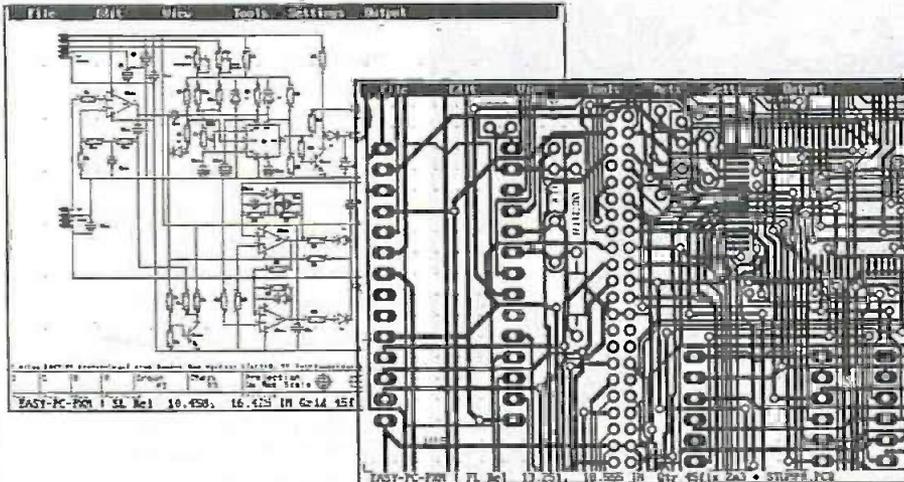


To Perfect PCB's

- Runs on:- PC/ 386/ 486 with VGA display
- Links to PULSAR (logic), ANALYSER III (analogue) & LAYAN (electromagnetic) simulators.
- Design:- Single sided, Double sided and Multi-layer boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Optional, powerful, 32 bit Multi-pass, Shape based, Shove Aside, Rip-up and Re-try Autorouter.

Simulation can even include the parasitic effects introduced by the Board Layout

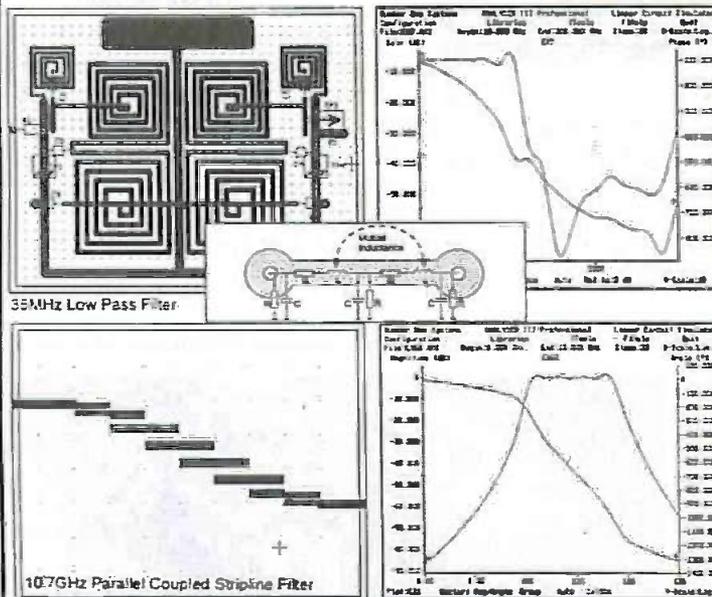LAYAN - Electro-magnetic Simulation ONLY £495



Affordable Electronics CAD

EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III, LAYAN and PULSAR.	From \$245	£145
MultiRouter: 32bit Multi-pass Autorouter	\$475	£295
LAYAN: Electro-Magnetic PCB Layout Simulator. Include the board parasitics in your Analogue simulations. Links with and requires EASY-PC Professional XM and ANALYSER III Professional	\$950	£495
PULSAR: Digital Circuit Simulator	From \$175	£98
ANALYSER III: Analogue Linear Circuit Simulator	From \$175	£98
FILTECH: Active and Passive Filter Design program	From \$245	£145
STOCKIT: New comprehensive Stock control program for the small or medium sized business	\$245	£145
EASY-PC: Entry level PCB and Schematic CAD.	\$135	£75
Z-MATCH : Windows based Smith-Chart program for RF Engineers.	From \$245	£145

*We operate a no penalty upgrade policy.
US\$ prices include Post and Packing
Sterling Prices exclude P&P and VAT.*

For full information and demo disk, please write, phone, fax or e-mail:-

Number One Systems

UK/EEC: Ref. ETI, Harding Way, St.Ives, Cambridgeshire., ENGLAND, PE17 4WR.
Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042
USA: Ref. ETI, 126 Smith Creek Drive, Los Gatos, CA 95030
Telephone/Fax: (415) 968-9306

- TECHNICAL SUPPORT FREE FOR LIFE
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

e-mail: sales@numberone.com
International +44 1480 461778





Too many cards and not enough standards

The rush to use smart card technology for a wide range of different applications is good from the standpoint of the technology developers and suppliers, but for the end user it spells chaos. This potential chaos will arise from the lack of any degree of standardisation apart from the actual card size. Take a half dozen different smart cards and you will find the contacts positioned in slightly different places, and the contact layout slightly different.

In many ways this is probably a deliberate policy. Card issuers do not, for example, want users to try using a Shell loyalty card in a BT phone box. However, do we, the users, want to end up with a wallet or purse stuffed with assorted smart cards? The trouble is that too many incompatible smart cards could end up destroying the potential offered by smart card technology, particularly as a means of electronic cash payment. If they are to replace old fashioned money as the preferred means of paying for low cost items then they need to be universally acceptable, just as conventional cash is within a specified country's borders.

For the technology to be of any value, the user of, say, a Mondex electronic purse card needs to be able to use it in the same terminals as a VisaCash card, or use it in a BT phone box, or even use it to pay for a ticket on London Transport. Otherwise we end up with the same infuriating situation

that exists with credit cards - to be sure of being able to pay for something wherever you are you need to carry a card from all three big card groups, Mastercard, Visa, and American Express. If you do not then the odds are that you will be greeted with 'I am sorry but we do not take that card'.


business costs. Currently about 90% of all transactions in the world are made using cash. Mondex have set a goal of taking over 40% of these.

The credit card companies are also becoming involved in the use of smart cards which they see as a technology which will allow them to beat card fraud as well as offering additional services. As part of the EMV and APACS projects both Visa and Mastercard have developed smart card versions of their credit cards. Starting next year the banks involved will be converting all credit cards and credit card terminals to use smart cards as opposed to conventional mag stripe cards, a process which they estimate will take between five and ten years, with hybrid cards being used in the transition period.

Uniquely in the UK, debit cards are also being converted to smart cards. This move is being paralleled by big retailers rapidly expanding their loyalty card schemes into the financial services sector, such as Tesco's Club Card scheme and Sainsbury's recent acquisition of a banking licence. As yet none of the big supermarket chains have come up with a smart loyalty card, although Shell have produced a multi vendor smart loyalty card which may well be a pointer to the future in this area.

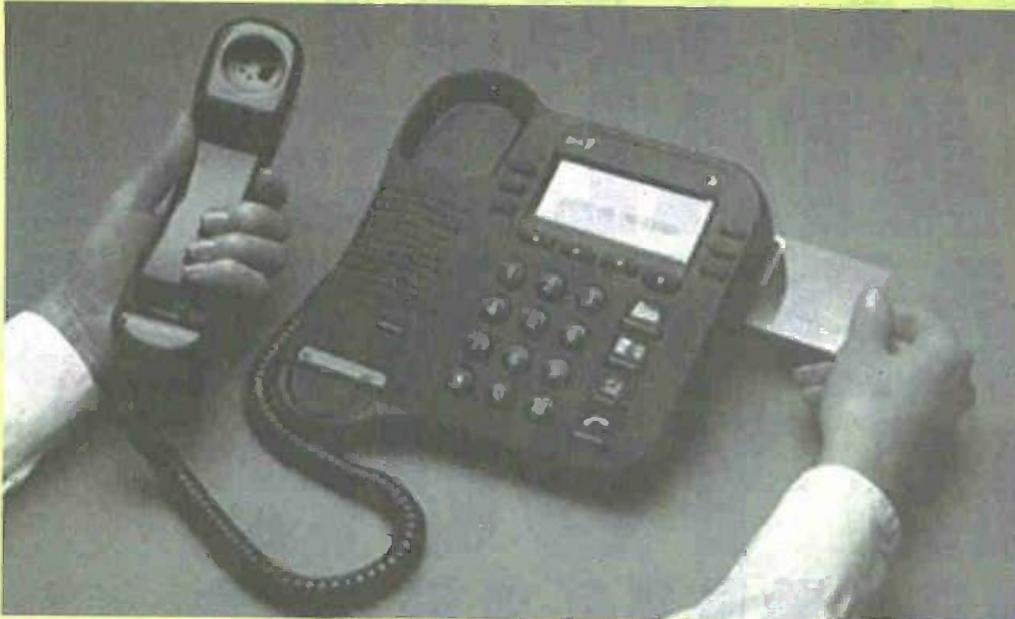This page shows two types of Mondex keyfob smartcard reader





A Mondex telephone terminal

The fact that all the main credit card groups are independently developing smart card based electronic cash technology means that we can look forward to a perpetuation of the existing credit card system. Retailers will be forced to have two or three terminals, one for each type of smart card, in addition to terminals for their own loyalty cards. It is difficult to see a street newspaper vendor investing in the means of accepting payment from two or three different electronic purse systems, and if someone like that does not accept all the competing cards then electronic cash will not be a reality. Some sort of standardisation will probably evolve over time but only after some very expensive 'terminal wars' have been fought by the main electronic purse providers.

The spectre of Big Brother?

Like a great deal of information technology the smart card has the potential to be extremely beneficial to society in general, but at the same time could also be perverted to the detriment of both individuals and society as a whole. Smart card technology gives both governments and big companies the ability to pry into our everyday lives, to check what we buy in the shops, to see where we go, to know exactly what we spend our money on, what papers we buy, what meals we eat, what films we see.

The spectre of Big Brother can easily be conjured up by the improper use of smart cards. However, we must accept that gathering data on customers is now a key element in both marketing and management. Such data allows companies to tailor their services to the needs of the customer, while at the same time maximising profitability. Indeed such data is rapidly becoming the most important asset of many companies, and it is thus hardly surprising that they are prepared to invest heavily in any technology which will increase the value of that asset.

Smart cards fall into this category, since they will allow the information gathered on each customer to be drawn from a much wider area. Although it is important that as a society we carefully look at how new technologies such as smart cards are both applied and used, so as to prevent any usage which will have a negative impact on us as individuals and the community in general, it is also important that we look at the positive side. While smart cards may make gathering data

easier, they could also be used to give back to the individual control over the data relating to that individual.

Smart cards could in the future be used, for example, to store an individual's complete medical records, data which could only be accessed via some form of security technique such as retinal scanning. A use of the technology which would be far preferable to storing all such data on a centralised computer system that could potentially be accessed by any inquisitive individual.

The future for smart cards

All around the world there are now groups of engineers developing the smart card technologies of tomorrow. They are working at building more and more intelligence into a card as well as increasing the memory capacity of cards. Indeed it is probably fair to assume that by the end of the century we will see smart cards that have a processing power equal to that of a mid range PC of today, and come complete with a megabyte or two of memory.

One of the principle security related aims for all this extra processing power is to allow smart cards to both carry and analyse biometric data. This means being able to recognise voice commands, palm prints, or retinal patterns, in addition to a conventional signature. The extra memory capacity will also be used to allow smart cards to act as personal information storage systems, containing perhaps, the owner's complete medical records.

However, as smart-cards become more intelligent so the concept of a smart card as a credit card sized piece of plastic may start to give way to the increasingly talked about concept of the 'wearable computer' - rather than carrying a smart card in a wallet or purse it may become something we wear, like a watch, and in the light of recent IBM research we will then communicate with each other via subcutaneous signals transferred by a handshake.

A Mitsubishi contactless MelCard



WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 14545 Dual Trace 100MHz Delay Storage	£1180
TEKTRONIX 2441A Dual Trace 200MHz Delay Storage	£1300
HP Type 9202A Oscilloscope 50MHz	£1150
PHILIPS 44222 Dual Trace 200MHz Delay Storage	£1050
TEKTRONIX 485 Dual Trace 200MHz Delay Storage	£1000
TEKTRONIX 485 Dual Trace 200MHz Delay Storage	£1000
TEKTRONIX 2215 Dual Trace 100MHz Delay Storage	£950
PHILIPS 3035 2-1 Ch. Storage Delay Storage	£900
PHILIPS 3037 Dual Trace 200MHz Delay Storage	£850
GOLD 0511000 Dual Trace 200MHz	£800
PHILIPS 3030A Dual Trace 200MHz	£750
GOLD 05000 Dual Trace 200MHz	£700
HP 4040 200MHz Delay Storage	£650
LEADER J20100 DMM/Scope 200MHz Dig Storage LCD display	£600
TEKTRONIX 484 Dual Trace 200MHz Delay Storage Dig Storage	£550
TEKTRONIX 484 Dual Trace 200MHz Delay Storage	£550
TEKTRONIX 484 Dual Trace 200MHz Delay Storage	£550
TEKTRONIX 484 Dual Trace 200MHz Delay Storage	£550
TEKTRONIX 484 Dual Trace 200MHz Delay Storage	£550

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

HP 8200C Sweep Gen with 82000 D - 40 & 100	£2000
HP 8200C Sweep Gen with 82000 D - 1 & 100	£2000
AVTRON 8515A Programmable Sweep Gen 1 200Hz	£1500
HP 8022A Synthesizer Sig Gen 100-1000MHz	£1150
MARCONI 2001 AMF50 Sig Gen 100Hz - 10MHz	£1000
MARCONI 2002 Synthesizer AMF50 Sig Gen 100Hz - 100MHz	£1150
MARCONI 2004 Synthesizer AMF50 Sig Gen 100Hz - 100MHz	£1150
HP 8040C Phase Lockdwn Sig Gen 100Hz - 100MHz Dig Freq	£1000
HP 8040A AMF50 Sig Gen 100Hz - 100MHz	£750
FARNELL 75520 Synthesizer AMF50 Sig Gen 100Hz - 100MHz	£1000
FARNELL 75520 Synthesizer AMF50 Sig Gen 100Hz - 100MHz	£1000
FARNELL 75520 Synthesizer AMF50 Sig Gen 100Hz - 100MHz	£1000
FARNELL 75520 Synthesizer AMF50 Sig Gen 100Hz - 100MHz	£1000
FARNELL 75520 Synthesizer AMF50 Sig Gen 100Hz - 100MHz	£1000

BRUEL & KJOER EQUIPMENT AVAILABLE PLEASE ENQUIRE


SPECTRUM ANALYSERS

HP 8445A 80MHz	£2000
ALTECH 827 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500
HP 8534 80MHz	£1500

Used Equipment - Guaranteed. Manuals supplied if possible.
This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £15. VAT to be added to Total of Goods and Carriage.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 01189 268041 Fax: 01189 351696

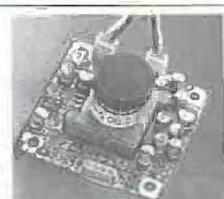HIGH QUALITY LOW COST C.C.T.V. CAMERA (12mm x 12mm) LOW LIGHT LEVEL. AUTO ELECTRONIC SHUTTER. COMPOSITE VIDEO OUT VIA BNC PLUG. SMALL DISCRETE SIZE. CAN BE USED WITH PC DIGITISER.



This super quality CCD PCB camera can be connected to your existing TV or video using the AV channel and can be used for discrete surveillance or observing your property externally using a suitable waterproof housing. Can accommodate lighting levels ranging from day light to street lighting using its built in electronic shutter. Excellent when using with an infra red source. Built in wide angle fixed focus lens the camera has a resolution of 380 TVL (Sharp CCD and IC's)

Special offer price of only **£59.95 Plus VAT (P&P £3.50) (Total £73.94).**
(£49.99 Plus VAT for 10 or more.)

For full range of CCTV products send SAE to:
Direct CCTV Limited, Direct House, Florence Street, Middlesbrough, TS2 1DR

Thinking Of Building Your Own Loudspeakers?

But struggling with all the theory & arithmetic? Help is at hand - Speaker Design is a CAD package for PC Windows that takes the pain out of all those sums. Calculate box responses, cabinet sizes & crossovers for speakers for the home, car or stage. Supplied on 3 HD disks for only **£28.95**. For more details & an order form write to:

Three
Crowns
Publishing
PO Box 5773, Laindon, Essex SS15 5FJ tel: 0410 225257

ETI READERS SERVICES

Reader offer

THE NEW TERMINATOR 10

JUST £9.95 INC P&P

TAKE THE GUESSWORK OUT OF TESTING FUSES, LIGHT BULBS, CABLES, SOCKETS, MICROWAVE OVENS AND MANY MORE ELECTRICAL ITEMS WITH THE TERMINATOR 10

Electrical faults are a major cause of domestic fires and accidents - take a few minutes to check out your appliances for safety with Terminator. You could save on repair bills or prevent an accident

The Terminator complies with BS2559 part 3 and is manufactured in accordance with VD0680 Part 6

This truly indispensable tool is supplied with easy, clear instructions and is surely one of the most versatile electrical testing devices you'll come across

Order by
Tel: 01442 665511
Fax: 01442 66998

Please supply **ROET49 @ £9.95 each (includes P&P).**
I enclose my cheque/P.O. for made payable to Nexus Special Interests or please debit my Access/Visa.

Name..... Signature..... Expiry Date.....
Address..... Post code.....

Complete details and return coupon to: Nexus Special Interests, Readers Offer, Nexus House, Boundary Way, Hemel Hempstead, Herts, HP2 7ST.
Data Protection: occasionally we may make names and addresses available to carefully vetted companies who sell services by mail order that we believe may be of interest to our readers. If you would prefer not to receive such mailings please tick this box.

ELECTRONICS TODAY INTERNATIONAL
19



Are smart cards really secure?

The smart card, a credit card sized plastic card which contains electronic circuitry capable of storing several kilobytes of data, are increasingly being viewed by banks and other financial institutions as the solution to credit card fraud. They also see smart cards as a means of generating new forms of revenue from applications such as electronic cash.

Smart cards are viewed as being immune to fraud. This is because the large memory capacity plus the incorporation of a small processor in the card's circuitry means that it can have an unique identity, an individual and totally unique electronic signature. Unfortunately, however, recent research at France Telecom, a world leader in smart card development, has shown that this may not necessarily be true.

The common card specification drawn up by the major credit card companies and known as EMV uses the RSA encryption algorithm. This algorithm relies on two keys consisting of 155 digit numbers, one public, and the other hidden in the card's memory. These keys are used to generate another number which is then used to code and decode the data stored on the card. The flaw lies in the fact that in order to either create or verify such an electronic signature requires a lot of processing, and thus a long time.

According to security experts it takes about 30 seconds for the card's RSA keys to be generated, this is deemed too long for both everyday use and card manufacture. In both cases between 1 and 2 seconds is the target. The result of this time problem is that card manufacturers are considering replacing the unique signature with one of 10,000 preset

signatures. This will of course mean that no card will be unique, indeed, there could be thousands of identical cards in circulation, a situation which lays smart cards wide open to fraudulent use.

However good the encryption techniques may be, yet further questions about smart card security have been raised by a group working at the University of Cambridge. Using a variety of different techniques these researchers claim to have broken the security of every smart card they have seen, a claim which is causing some serious redesign work to be done by smart card developers across the world.

The research group, led by Dr Ross Anderson, a lecturer at the university's computer laboratory and an expert on computer security, were able to penetrate even the most secure chips and have shown how fraud could be committed on an industrial scale. In a paper recently published on the Internet the group have outlined the techniques for cracking one of the most widely used microprocessor chips, the Dallas Semiconductor's 5002, a device which is used in about 1 million POS terminals.

The manufacturers of equipment incorporating the Dallas Semiconductor device, as well as Dallas themselves, are now working on measures to overcome the weakness identified by Dr Anderson. However, what Dr Anderson's team have shown is that any security technique can be broken, and that the developers of secure smart card systems will have to continually develop new and better security techniques if they are to stay one step ahead of the fraudsters.

(0191) 251 4363
 Fax (0191) 252 2296
ESR
ELECTRONIC COMPONENTS
 Station Road, Cullercoats,
 Tyne & Wear
 NE30 4PQ
 U.K.

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

DIL Sockets

Stamped Pin	
8 Pin DIL 0.3"	£0.06
14 Pin DIL 0.3"	£0.11
16 Pin DIL 0.3"	£0.11
18 Pin DIL 0.3"	£0.12
20 Pin DIL 0.3"	£0.12
24 Pin DIL 0.6"	£0.13
28 Pin DIL 0.6"	£0.13
40 Pin DIL 0.6"	£0.19
Turned Pin	
8 Pin DIL 0.3"	£0.11
14 Pin DIL 0.3"	£0.27
16 Pin DIL 0.3"	£0.31
18 Pin DIL 0.3"	£0.35
20 Pin DIL 0.3"	£0.39
24 Pin DIL 0.6"	£0.41
28 Pin DIL 0.6"	£0.41
40 Pin DIL 0.6"	£0.78

SIL Header Strip

1 x 36 Way Straight	£0.38
1 x 36 Way Straight	£0.72
2 x 36 Way 90°	£0.55
2 x 36 Way 90°	£0.78
20 Way Socket Strip	£0.34

Transistor Sockets

T018-4 Base Socket	£0.24
T05 Base Socket	£0.24

IDC Cable Sockets

10 Way Socket	£0.23
11 Way Socket	£0.24
16 Way Socket	£0.31
20 Way Socket	£0.26
25 Way Socket	£0.30
34 Way Socket	£0.42
40 Way Socket	£0.66
50 Way Socket	£0.75

PCB Box Headers

10 Way Straight	£0.27
14 Way Straight	£0.36
16 Way Straight	£0.36
20 Way Straight	£0.41
26 Way Straight	£0.49
34 Way Straight	£0.57
40 Way Straight	£0.63
50 Way Straight	£0.96
10 Way 90°	£0.36
16 Way 90°	£0.47
20 Way 90°	£0.53
26 Way 90°	£0.58
34 Way 90°	£0.72
40 Way 90°	£0.83
50 Way 90°	£0.99

PCB Latch Headers

10 Way Straight	£0.50
16 Way Straight	£0.70
20 Way Straight	£0.78
26 Way Straight	£1.00
34 Way Straight	£0.66
40 Way Straight	£1.50
50 Way Straight	£1.29
10 Way 90°	£0.58
20 Way 90°	£0.82
26 Way 90°	£1.06
34 Way 90°	£1.14
40 Way 90°	£1.64
50 Way 90°	£1.74

DIL Headers

14 Way DIL	£0.54
16 Way DIL	£0.59
24 Way DIL	£0.90
40 Way DIL	£1.02

Transition Headers

10 Way Transition	£0.49
14 Way Transition	£0.47
16 Way Transition	£0.47
20 Way Transition	£0.54
26 Way Transition	£0.62
34 Way Transition	£0.67
40 Way Transition	£0.90
50 Way Transition	£1.02

D Type Connectors

Solder Bucket	
9 Way Male Plug	£0.29
9 Way Female Socket	£0.30
15 Way Male Plug	£0.39
15 Way Female Socket	£0.39
15 Way D Plug	£0.49
15 Way H.D. Socket	£0.78
25 Way Male Plug	£0.49
25 Way Female Socket	£0.49
25 Way Male Plug	£0.43
25 Way Female Plug	£0.50
IDC Ribbon Mounting	
9 Way Male Plug	£1.20
9 Way Female Socket	£1.20
25 Way Male Plug	£1.26
25 Way Female Socket	£1.26
Right Angled PCB	

9 Way Male Plug

9 Way Male Plug	£0.37
9 Way Female Socket	£0.35
15 Way H.D. Socket	£0.77
25 Way Male Plug	£0.53
25 Way Female Socket	£0.51
Plastic D Covers	
9 Way Cover - Grey	£0.30
9 Way Cover - Black	£0.30
15 Way Cover - Grey	£0.33
15 Way Cover - Black	£0.34
25 Way Cover - Grey	£0.38
25 Way Cover - Black	£0.38
9 to 9 Cover / Case	£0.96
25 to 25 Cover / Case	£0.86

Audio Connectors

2.5mm Jack Plug	£0.21
2.5mm Line Socket	£0.16
2.5mm Chassis Socket	£0.09
3.5mm Mono Plug	£0.24
3.5mm Mono Line Str	£0.30
3.5mm Mono Chassis Sk	£0.13
3.5mm Stereo Plug	£0.33
3.5mm Stereo Line Sk	£0.37
3.5mm Stereo Chassis Sk	£0.34
4mm Mono Plug	£0.30
4mm Mono Line Socket	£0.35
4mm Mono Chassis Socket	£0.40
4mm Stereo Plug	£0.40
4mm Stereo Line Socket	£0.38
4mm Stereo Chassis Sk	£0.44

DIN Series

2 Pin Line Plug	£0.18
3 Pin Chassis Socket	£0.15
3 Pin Line Plug	£0.27
3 Pin Chassis Socket	£0.28
4 Pin Line Plug	£0.24
4 Pin Chassis Socket	£0.26
5 Pin Line Plug 180°	£0.30
5 Pin Chassis Sk 180°	£0.32
5 Pin Line Plug 240°	£0.24
5 Pin Chassis Sk 240°	£0.32
5 Pin Line Plug 360°	£0.24
5 Pin Chassis Sk 360°	£0.32
6 Pin Line Plug	£0.32
6 Pin Chassis Socket	£0.32
7 Pin Line Plug	£0.34
7 Pin Chassis Socket	£0.34
8 Pin Line Plug	£0.45
8 Pin Chassis Socket	£0.36

Phono Series

Red Line Plug	£0.20
Black Line Plug	£0.20
Yellow Line Plug	£0.20
White Line Socket	£0.20
Black Line Socket	£0.20
Yellow Line Socket	£0.20
White Line Socket	£0.20
Red Chassis Socket	£0.20
Black Chassis Socket	£0.20
Gold Plated Plug - Red	£0.64
Gold Plated Plug - Black	£0.64
NLR Series - metal	

3 Pin Line Plug

3 Pin Line Plug	£1.50
3 Pin Line Socket	£1.82
3 Pin Chassis Plug	£1.56
3 Pin Chassis Socket	£1.70

RF Connectors

BNC Plug 50Ω Solder	£0.93
BNC Plug 50Ω Crimp	£0.56
BNC Plug 75Ω Solder	£0.96
BNC Plug 75Ω Crimp	£0.70
BNC Chassis Socket	£0.80
F Plug - Twist	£0.27
F Plug - Crimp	£0.30
TNC Plug Solder	£1.20
TNC Plug Crimp	£0.78
UHF Plug 5mm Cable	£0.72
UHF Plug 11mm Cable	£0.66
UHF Chassis Skr - Sop	£0.45
UHF Chassis Skr - Rnd	£0.38

Terminals

All Available in - Red, Black, Green, Blue, White or Yellow	
2mm Solder Plugs	£0.15
2mm Chassis Sockets	£0.20
4mm Solder Plugs	£0.30
4mm Stackable Plugs	£0.40
4mm Chassis Sockets	£0.23
4mm Binding Posts	£0.54
3mm Crocodile Clips	£0.13

Power Connectors

DC Low Voltage	
DC Plug 0.7ID, 2.35OD	£0.40
DC Plug 1.3ID, 3.40D	£0.37
DC Plug 1.7ID, 4.60D	£0.46
DC Plug 2.1ID, 4.75OD	£0.34
DC Plug 2.1ID, 5.60D	£0.24
DC Plug 3.1ID, 6.30D	£0.46
DC Line Socket 2.1mm	£0.50
DC Line Socket 2.5mm	£0.50
DC Chassis Skt 2.1mm	£0.46
DC Chassis Skt 2.5mm	£0.46
IEC Mains G.A. 250Vac	

Sub-Minature

3A 125V 1A 250V	£0.30
5mm O Mounting Hole	
SPST 5 x 10mm	£0.58
SPDT 5 x 10mm	£0.60
SPDT C/OFF 5 x 10mm	£0.86
DPDT 0.2 x 10mm	£0.86
Miniature	
6A 125V 3A 250V	£0.40
6.2mm O Mounting Hole	
SPST 8 x 13mm	£0.66
SPDT 8 x 13mm	£0.60
SPDT C/OFF 8 x 13mm	£0.64
SPDT C/O Baised 2 way	£1.04
SPDT C/O Baised 1 way	£1.04
DPDT 12 x 13mm	£0.72
DPDT C/OFF 12 x 13mm	£0.76
DPDT C/O Baised 2 way	£1.28
DPDT C/O Baised 1 way	£1.28

Standard

10A 250V Push on terminals	
11mm O Mounting Hole	
SPST 18 x 30mm	£1.14
SPDT 18 x 30mm	£1.28
SPDT C/OFF 18 x 30mm	£1.52
DPDT 21 x 30mm	£1.78
DPDT C/OFF 21 x 30mm	£1.78

Slide Switches

Miniature	
30mA 125V	
7 x 15mm Mounting Hole	
DPDT 7 x 15mm	£0.15
Standard	
1A 125V	
5.5 x 12mm Mounting Hole	
DPDT 12 x 35mm	£0.24
DPDT C/O 12 x 35mm	£0.27

Rotary Switches

150mA 250V	
Blade before Break 22mm O	
9.8mm O Mounting Hole	
1 Pole 12 Way	£0.84
2 Pole 6 Way	£0.84
3 Pole 4 Way	£0.84
4 Pole 3 Way	£0.84

Push Switches

Miniature Round	
150mA 125V 28 x 10mm	
7mm O Mounting Hole	
Non Latching Push to Make	
Black PTM	£0.25
Red PTM	£0.25
Green PTM	£0.25
Blue PTM	£0.25
White PTM	£0.25
Non Latching Push to Break	
Black PTB	£0.25
Standard Square	
1A 250V	
39 x 15MM	
12mm O Mounting Hole	
Non Latching Push to Make	
Black PTM	£0.60
Red PTM	£0.60
Blue PTM	£0.60
White PTM	£0.60
Latching	
Black	£0.63
Red	£0.63
Blue	£0.63
White	£0.63
Rockers	
Rockers	
Miniature	
6A 250V Solder Tags	
SPST 21 x 12 x 16mm	£0.63
DPDT 21 x 24 x 22mm	£0.96
Standard	
15A 250V Push on Tags	
SPST 30 x 11 x 22mm	£0.50
DPDT 30 x 25 x 22mm	£1.12
Illuminated	
15A 250V Push on Tags	
SPST 30x14mm Red	£0.84
DPDT 30x25mm Red	£1.30
DPDT 30x25mm Amber	£1.40
DPDT 30x25mm Green	£1.46

Terminals

All Available in - Red, Black, Green, Blue, White or Yellow	
2mm Solder Plugs	£0.15
2mm Chassis Sockets	£0.20
4mm Solder Plugs	£0.30
4mm Stackable Plugs	£0.40
4mm Chassis Sockets	£0.23
4mm Binding Posts	£0.54
3mm Crocodile Clips	£0.13

Power Connectors

DC Low Voltage	
DC Plug 0.7ID, 2.35OD	£0.40
DC Plug 1.3ID, 3.40D	£0.37
DC Plug 1.7ID, 4.60D	£0.46
DC Plug 2.1ID, 4.75OD	£0.34
DC Plug 2.1ID, 5.60D	£0.24
DC Plug 3.1ID, 6.30D	£0.46
DC Line Socket 2.1mm	£0.50
DC Line Socket 2.5mm	£0.50
DC Chassis Skt 2.1mm	£0.46
DC Chassis Skt 2.5mm	£0.46
IEC Mains G.A. 250Vac	

Relays

PCB Mounting	
1A 24VDC DPDT 6V	£1.44
1A 24VDC DPDT 12V	£1.44
3A 110V SPDT 0V	£0.58
5A 110V SPDT 12V	£0.58
5A 110V SPDT 0V	£0.72
5A 110V SPDT 12V	£0.72
5A 110V DPDT 6V	£0.93
5A 110V DPDT 12V	£0.93
5A 240V DPDT 0V	£1.76
5A 240V DPDT 12V	£1.76
10A 240V SPDT 6V	£1.25
10A 240V SPDT 12V	£1.41
10A 240V SPDT 24V	£1.44

Computer Accessories

Adaptors	
9A Gender Charger	£2.33
9M Gender Charger	£2.33
25F Gender Charger	£2.80
9 Male - 25 Female	£2.51
9 Female - 25 Male	£2.67
9M - 6 Mini Din Male	£2.55
9F - 6 Mini Din Female	£2.55
SM Din - 6F Mini Din	£2.02
FF Din - 6M Mini Din	£2.25

Testers / Pin Boxes

4 Pin Tester / LEDs	£6.68
4 Pin Tester / LEDs	£7.11
Enhanced LED Switches	£15.25
25D Jumper Box M-F	£2.90
25D Patch Box M-F	£7.32
Anti-Static Wrist Strap	£5.30
RS232 Surge Protector	£5.45
Mains Surge Protector	£11.99

Leads & Cables

1.5m Printer Lead	£3.40
5m Printer Lead	£9.38
Serial Printer 25M-9F	£4.30
Serial Printer 25M-25F	£4.45
Null Modem 9F-9F	£3.45
Null Modem 25F-25F	£4.63
Null Modem 9F-25F	£5.54
Modem Lead 25M-9F	£4.08
Modem Lead 25M-25F	£4.75
Infralink Lead 25F-9F	£6.50
Infralink Lead 25F-25F	£6.50
Infralink Lead 25M-25M	£6.50
Patch Lead 25M-25M	£4.68
Patch Lead 36M-36M	£5.90
Hardy Drive Cable A/B	£4.50
Hard Disk Cable 2/IDE	£2.90
Power Cable 3/2 x 3/4	£1.88
Power Cable 5/6-2 x 3/4	£2.24
Power Cable 5/8-2 x 3/4	£2.24
Power Cable 5/8-3/4 x 3/4	£2.24

Networking

BNC T Piece FMF	£2.40
BNC T Piece FFF	£2.40
BNC Coupler M	£1.03
BNC Coupler F	£1.65
BNC Racked Crimper	£17.44
RJ45 IDC Plug	£0.39
Ternet Cable per m	£0.48

Boxes & Cases

Many more sizes available	
75 x 56 x 25mm	£0.88
75 x 51 x 22mm	£0.88
111 x 57 x 22mm	£0.90
79 x 61 x 40mm	£1.47
100 x 76 x 41mm	£1.58
118 x 98 x 45mm	£1.83
150 x 100 x 60mm	£2.31
150 x 80 x 50mm	£2.36
Diecast Aluminium	
50 x 50 x 31mm	£2.24
100 x 50 x 25mm	£2.98
112 x 62 x 31mm	£3.55
120 x 65 x 40mm	£4.02
150 x 80 x 50mm	£5.36
121 x 95 x 61mm	£5.99
Two Piece Aluminium	
133 x 70 x 37mm	£2.08

New series

Experimenting THE SYNC SEPARATOR

In the first part of his new series, Robin Abbott introduces video signals and constructs a sync separator module that can be incorporated into other circuits, for example a multi-function fader-wiper.

On recent years, with the increasing affordability of camcorders and other video sources, the operation and construction of electronic projects involving video signals has been of greater interest to electronics constructors.

Virtually all video recorders, camcorders and increasingly computer systems and video games are equipped with composite video outputs, and sometimes input connectors. In this series we shall look at the operation of the composite video signal and how it may be manipulated. We will look at some techniques for manipulating the signal, some typical video building blocks, and how to construct faders, wipers, mixers, and test equipment.

The composite video signal

The composite video signal is so named because it is a single analogue signal which contains the brightness (known as luminosity), colour, and synchronisation information necessary to display a complete colour picture. On a TV broadcast it also contains teletext signals, which are not normally visible. It is sometimes described as a baseband video signal. The signal has a bandwidth of approximately 4MHz for black and white

(monochrome), and approximately 6MHz for colour. The signal has a DC content which, as we will see, can cause us some problems.

A frame is a complete picture displayed on a monitor or a television receiver. In this series we will look only at standard TV frames in the UK video system (although foreign systems are similar, but with differing details such as number of lines, frame rate, and method of colour encoding). A complete frame is included in the composite video signal once in every 40 milliseconds, resulting in 25 frames (or cycles) per second. If we were to view a TV picture at this frame rate, however, it would flicker unpleasantly. To overcome this problem the picture frame is split into two halves, and one half is sent every 20ms to result in a 50Hz display rate.

The two frame halves are split such that one half displays odd lines of the frame, and one the even lines of the frame. The persistence of the cathode ray tube (CRT) is such that the two halves appear to come together to make a single frame at the 50Hz rate. A frame half is referred to as a field.

The frame is made up of 625 lines, and each field includes 312.5 lines. Figure 1 shows the composition of a single frame on a CRT. Each line takes 64µs.

The composite video signal must include information to signal to the monitor the start of each line, the start of each field, and whether a field forms the odd or even half of the frame. These signals are the synchronising (or sync) signals. The lowest level of the signal defines the black signal, and a signal level below the black level can be used to define the start of each line, and the start of each field. The level of the signal drops to -0.3V to indicate sync information. We will consider the black level to be 0V (in practice as we shall see this is usually not the case, although in the designs that follow the video signal is adjusted to ensure this). Figure 2 shows two complete lines of video information.

Note that the signal drops to the black level (0V) at the end of each line for 1µs. This is called the front porch. It then drops to -0.3V for a period of 4µs to allow the monitor circuits to return the electron beam to the start of the next line. There then follows a period when the signal is at the black level, defining black for the following line for the receiver. This period (called the back porch) lasts for 7µs, and then the line information starts. During the back porch, for a 2µs period a


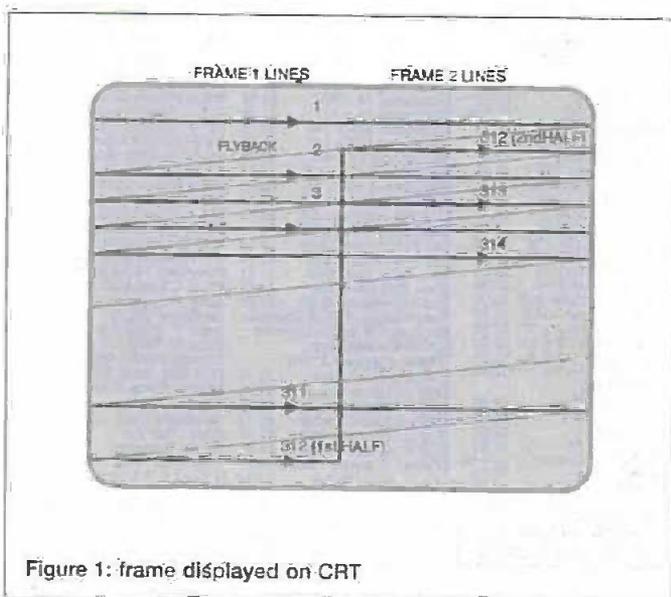


Figure 1: frame displayed on CRT

With Video **PART 1**

Figure 2: lines of picture information

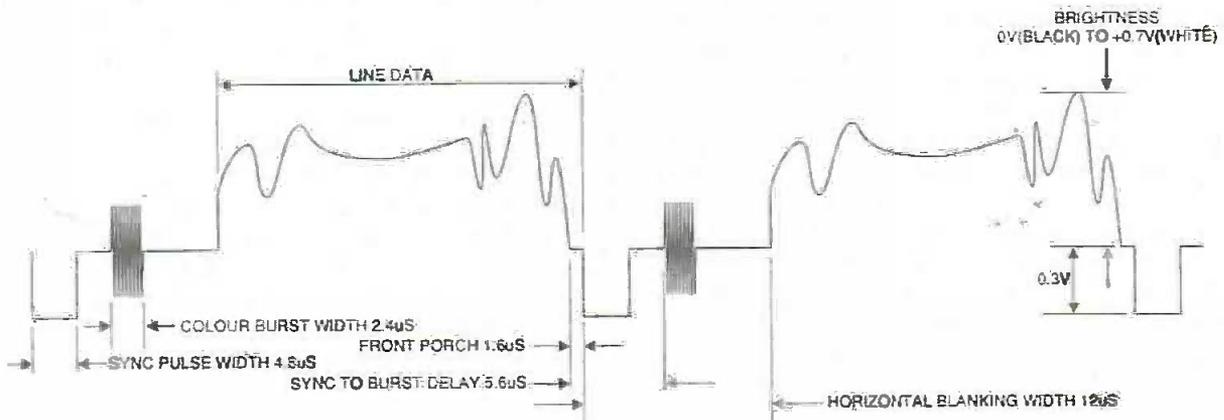

burst of the colour subcarrier is sent, which is used to lock the internal oscillator of the monitor to the colour signal and to allow the colour signals to be demodulated.

Thus the 64µs line time contains video information, and then 12µs to define the end of line, the black level, and to send the colour synchronising signal. This 12µs period is described as the line blanking interval - no information is displayed on the screen during this period.

The video information is carried as a simple brightness (or luminosity) signal, with colour modulated onto this basic signal. The luminosity signal varies from 0V (which is black), to 0.7V which represents white, with shades of grey in between. The electron beam in the receiver sweeps from the left hand side of

the CRT to the right, so the information sent immediately after the back porch is the information on the left of the screen. If you have an oscilloscope and a camcorder it is possible to test this, and careful adjustment of the trigger level can allow a reasonable display of a line. Point the camcorder at a piece of white paper and place a black card half way across the lens. The difference in the signal should be clearly visible.

Colour information is sent as a subcarrier at 4.33MHz. The composition and use of the colour signal is beyond the scope of this first article, but it is important to note its presence, and in particular it is very important to maintain the amplitude and phase of the colour burst during the back porch to ensure a stable colour picture.

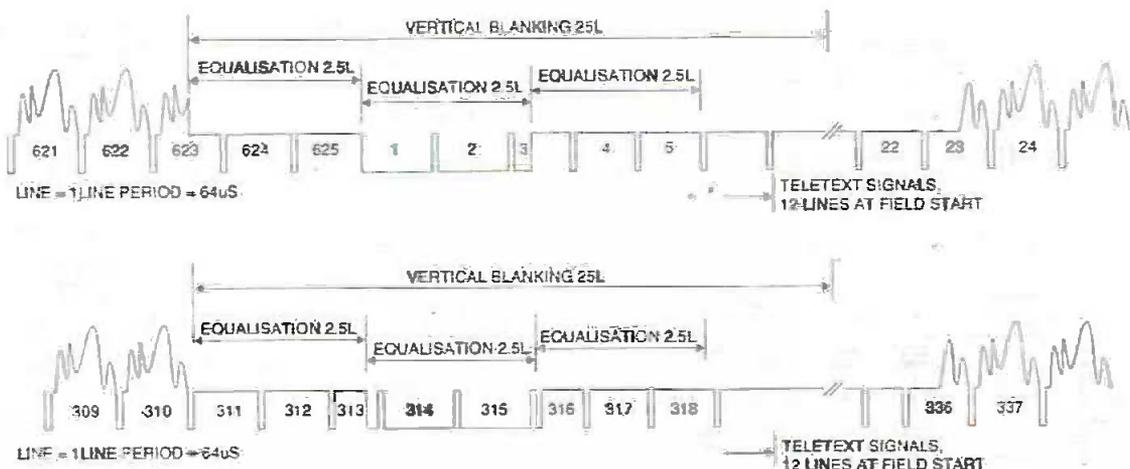


Figure 3: field synchronisation signals (for clarity, equalisation pulses are not shown)

Transform your PC

into a digital oscilloscope, spectrum analyser, frequency meter, voltmeter, data logger ... for as little as £49.00

Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement instruments or as an advanced data logger.

Hardware and software are supplied together as a package - no more worries about incompatibility and no programming required.

Pico Technology specialises only in the development of PC based data acquisition instrumentation. We have the product range and experience to help solve your test and measurement problem.

**Call for your guide on 'Virtual Instrumentation'.
We are here to help you.**



The ADC-10 supplied with PicoScope gives your computer a single channel of analog input.

ADC-10 £49
with PicoLog £59

Data Logging

Pico's range of PC based data logging products enable you to easily measure, display and record temperature, pressure and voltage signals.

TC-08 Thermocouple to PC Converter

- Supplied with PicoLog data logging software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs
- No power supply required.

TC-08 £199 TC-08 £224 with cal. Cert.
complete with serial cable & adaptor. Thermocouple probes available.



Virtual Instrumentation

Pico's PC based oscilloscopes simply plug into the parallel port turning your PC into a fully featured oscilloscope, spectrum analyser and meter. Windows and DOS software supplied.

ADC-100 Dual Channel 12 bit resolution

The ADC-100 offers both a high sampling rate 100kHz and a high resolution. Flexible input ranges ($\pm 50\text{mV}$ to $\pm 20\text{V}$) make the unit ideal for audio, automotive and education use.


ADC-100 £199 ADC-100 with PicoLog £219

ADC-200 Digital Storage Oscilloscope

- 50 MSPS Dual Channel Digital Storage Scope
- 25 MHz Spectrum Analyser
- Windows or DOS environment
- $\pm 50\text{mV}$ to $\pm 20\text{V}$
- Multimeter
- 20 MSPS also available

ADC 200-20 £359.00
ADC 200-50 £499.00

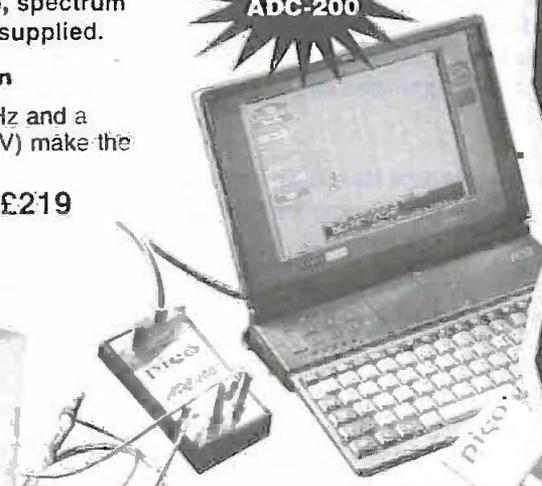Both units are supplied with cables, power supply and manuals.



Call for free demo disk and product range catalogue

Post & Packing UK £3.50, Export customers add £9 for carriage & insurance.

Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK Tel: + 44 (0)1954 211716 Fax: + 44 (0)1954 211880
E-mail: post@picotech.co.uk Web site: <http://www.picotech.co.uk/>


Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT

releasing PC potential

releasing PC potential

PICO Technology Limited

Figure 5a: waveforms from different parts of the sync separator circuit

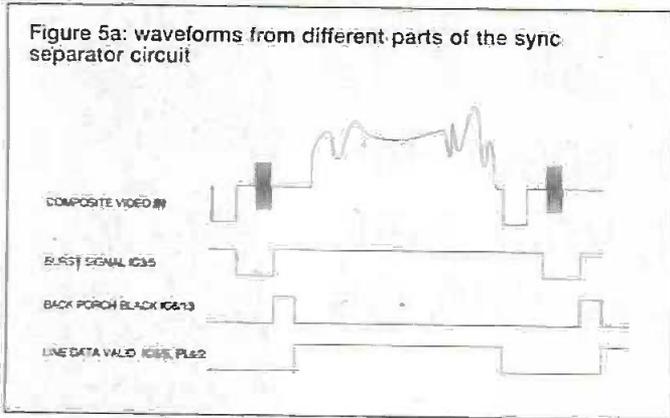

The sync separator

In this article we shall look at the design and construction of a general purpose video buffer, sync separator and regenerator. This is an essential building block of any project which is to modify the composite video signal. The sync separator provides the following functions:

Input buffer for two video signals.

DC restoration for each signal (see below).

Voltage controlled mixer to control gain of each channel and mix the channels to a common output channel. This provides fading or mixing.

Output buffer.

Synchronisation signal detection.

Line and frame valid signals which may be used to control mixing and wiping - however we manipulate the video signal we must ensure that the line and frame sync pulses are maintained because any operation which affected these sync signals would destroy the ability of a monitor to display the frames, and this function is provided on this board.

Fast switch to restore original sync signals.

We shall also look at how the circuit may be used at the heart of a fairly sophisticated multi function fader/wiper. In the next article we shall extend this to a full video mixer/fader/wiper which is digitally controlled and, apart from keyboard operation, may be controlled over a serial link from a PC or other computer to provide pre-programmed effects.

The circuit

Fortunately many useful video functions have been provided in integrated form. In this project we will be using the ELANTEC series of video buffers and control blocks.

Figure 4 shows the circuit diagram of the sync separator and regenerator. IC1a and IC1b provide unity gain buffering for the input signals. These are wide band op-amps which have a unity gain bandwidth which extends into tens of megahertz. The inputs are terminated with 75ohm resistors. If there is no signal on the B input then fading and wiping to channel B will fade and wipe to black.

From the output of IC1b (which is the buffered output from channel A), the sync circuit determines the line and frame synchronisation signals. This is achieved by IC3. This universal sync separator chip derives 4 output signals which are logic compatible. The burst signal goes low during the colour burst on each line. The vert signal goes low during the vertical sync period, and is generated on the first serration during the vertical sync period. The ODD output is high during odd fields and low in even fields. The composite sync output reproduces all the video input pulses.

Monostables


IC6 and IC7 are monostables used to derive useful signals for the rest of the circuit. IC6a is driven by the rising edge of the burst signal. It is timed to produce a pulse of about 4us which is active during the period of the back porch following the colour burst. This is used in DC restoration (see below). The falling edge of this pulse defines the beginning of the line. IC6b is triggered by the falling edge of IC6a and is set to produce a pulse of about 50us which is the same length as the data in the line. Thus the output of IC6b is a signal which is high during the line data, and low for the entire line blanking period. This is used to switch the input signal directly to the output signal during line sync data.

In similar fashion IC7 provides a signal which is high for the entire period of the field when there is no synchronisation data in the input signal. This is used to switch the input signal directly to the output signal during field sync data.

Figure 5 shows the timing of signals around this circuit.

C19 and C20 provide ac coupling from the input buffers into the next stage. Here we find the DC restoration circuit. The biggest problem with fading a video signal is that the average DC value of the composite video signal varies with the brightness of the signal. A white field will produce a video signal which has a DC level which is several hundred millivolts above the DC level of a black field. The result of this is that the black level varies with the type of picture being displayed. Any attempt to fade or wipe this signal to black (or white) will result in a blank field which will vary in shade of grey depending on the signal which is being faded. To overcome this it is

Figure 5b: waveforms from different parts of the sync separator circuit

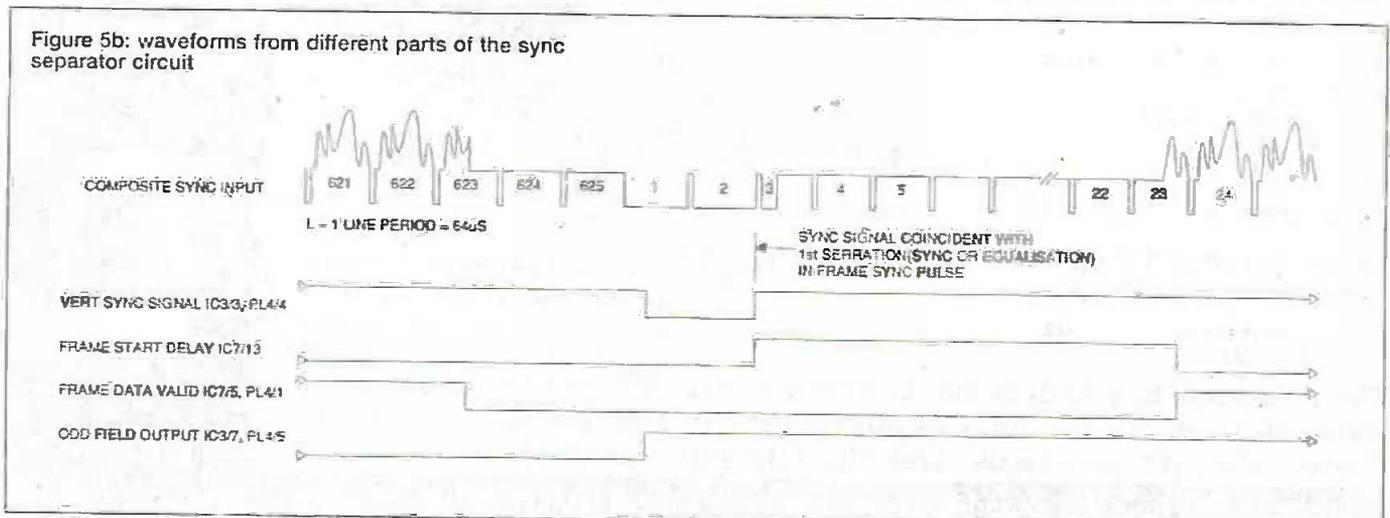

THE ONLY NEW YEAR'S RESOLUTION THAT'LL LAST!

Taking out a magazine subscription could well be the best resolution you make - and this one will last for months!

You can choose to subscribe to any of our 3 leading electronic's titles and save up to £13.00. The choice is made even easier as all subscriptions are the same price, either £25 or £50 depending on the number of issues you want.

IT COULDN'T BE EASIER

- Simply decide how much you would like to spend - £25 or £50, (overseas rates shown below) and then tick the magazine(s) that you wish to subscribe to. The longer you subscribe the more you save.
- Fill in the coupon with all your details and send with your payment to the address below.

ORDER FORM

Choose which magazine you want and simply tick the appropriate box.



Any magazine
£25

Overseas rates
£30.00 Europe & Eire
£33.00 Sterling O/Seas
U.S. \$56.00
S/C 0208

Any magazine
£50

Overseas rates
£60 Europe & Eire
£66 Sterling O/Seas
U.S. \$112.00
S/C 0209

**SAVE
£££'s
Order Today!**

	<input type="checkbox"/>	Issues	You save*
ETI	<input type="checkbox"/>	12	£3.20
HRT	<input type="checkbox"/>	13	£2.30
ARCHIMEDES WORLD	<input type="checkbox"/>	9	£6.50

	<input type="checkbox"/>	Issues	You save*
ETI	<input type="checkbox"/>	24	£6.40
HRT	<input type="checkbox"/>	26	£4.60
ARCHIMEDES WORLD	<input type="checkbox"/>	18	£13.00

*All savings are based upon purchasing the same number of copies from your newsagents.



ORDER HOTLINE: 01830 436344

Please commence my subscription(s) from the next available issue.

If renewing/extending please quote subscription number:

I enclose my cheque/P.O. for £..... made payable to Nexus Special Interests Ltd or please debit my Access/Visa



□□□□ □□□□ □□□□ □□□□

Signature Expiry /

Name: (Mr/Mrs/Miss) Initial Surname:

Address:

Postcode Telephone Number:

Photocopies of this page are acceptable. Not to be used in conjunction with any other offer. This offer is open to all readers until 30/04/97.

Please post this coupon to: Nexus Subscriptions Dept., Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leics. LE16 9EF.

Data Protection: Occasionally we may make names and addresses available to carefully vetted companies who sell services by mail order that we believe may be of interest to our readers. If you would prefer not to receive such mailings please tick this box.

necessary to bring the DC value of the black level back to a fixed level, in this case we choose ground so that an unused input appears as black.

DC restoration is traditionally accomplished using a diode clamp, however this does not guarantee restoration to ground. during the back porch (recall that the back porch defines the black level). The post burst pulse from IC6 is used to define this period and an analogue switch is used to short the signal to ground. R16 and R17 serve to pull up the signal during the period when the signal is not being clamped, and serve to make the black "blacker" which gives a better fade or wipe.

Integrated fader/mixer

IC2 is an integrated 2-channel fader/mixer IC. It has two inputs, A and B, and a gain control which defines the gain on each channel. The gain control should vary from -0.5V to +0.5V. When it is at the lowest voltage then channel B has full gain, and channel A has zero gain. When at the highest voltage then channel B has zero gain, and channel A has full gain. Thus the gain input may be used to fade the signal between channels, or when there is only one channel, to fade to black. Please note that the input impedance of the gain control is very low within IC2 (about 5K), and therefore should always be driven from a buffer.

IC2 also has an output amplifier, this is set to have a gain of +2 by R3, R4, R5 and R6 so that the output signal level (which is driven by a 75 ohm resistor) is at the right level when it is terminated correctly.

IC2 also has two inputs which force the gain to full gain on one channel and zero gain on the other. These are the force A and force B inputs. These inputs are used to force the output to channel A during sync periods by the line data valid and frame data valid signals. Whenever these signals are low (during sync periods) channel A is forced to full gain, so that sync signals are passed directly through without modification.

To achieve wiping functions, channel A is turned off and full gain is given to channel B. This is achieved by IC8. Whenever the Select B Input (pin 10 of IC8) is grounded then channel B is placed to full gain, and with no input signal to channel B, the output of the circuit will be at the black level. However IC8 also ensures that during sync periods the output of the circuit is forced back to channel A.

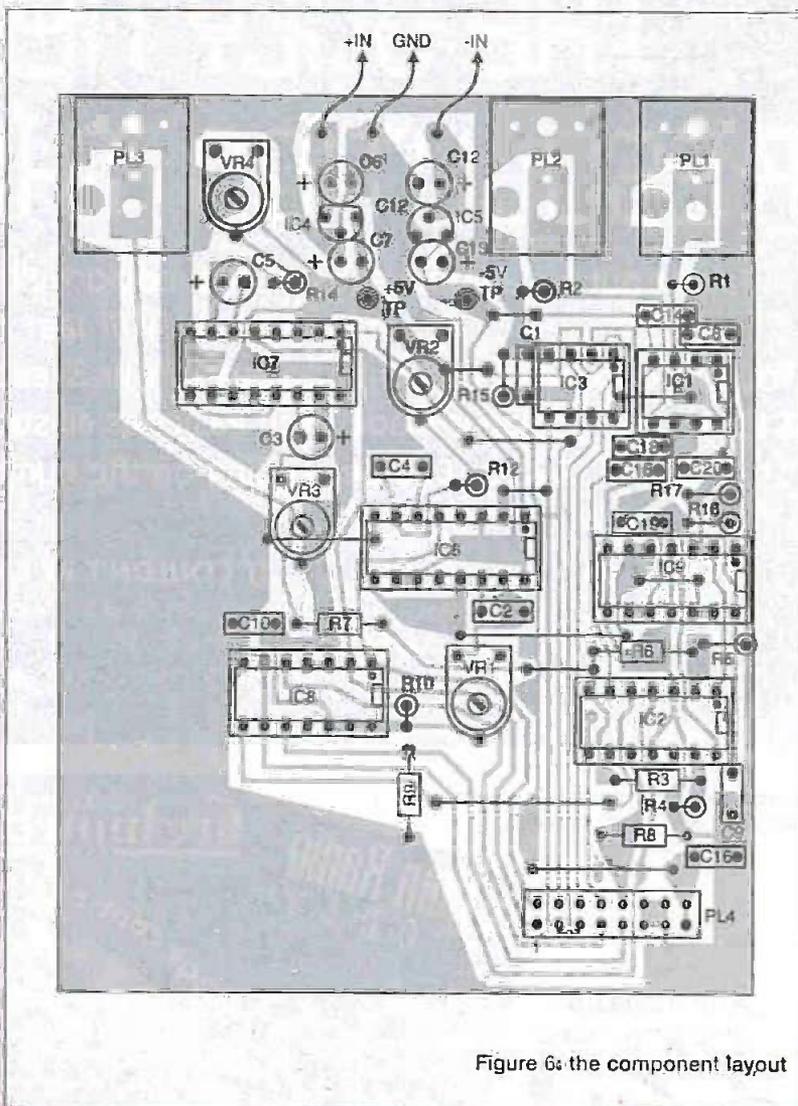


Figure 6: the component layout

- There is a 16 way control connector provided on the board. This provides the following signals:
- Burst, vertical, odd and composite sync outputs from IC3.
- Line data valid from IC6.
- Field data valid from IC6.
- Input to force the output to take its input from input A or input B directly.
- The gain input to fade between channels A and B.
- Power supplies at -5V and +5V at about 50mA drive capacity.


Construction and setting up

A PCB has been designed for this project. However, layout is not critical as most of the signals are at a high level and low impedance, and stripboard techniques could be used for the construction of this circuit. Close decoupling of the power supplies to the video chips IC1 and IC2 is very important whatever technique is used for construction. Figure 6 shows the component layout for the board.

Fit the 11 wire links first - some of these run under other components, so stripped hook up wire is recommended. Next, in order, fit the IC sockets, the resistors, the capacitors (watch for polarity here), and the remaining components. The board mounted phono sockets are sold by Maplin, other phono sockets may require a different board layout. Do not fit the ICs into their sockets yet.

The board requires a power supply at +/- 9V. Figure 8 shows a suitable circuit. To set the board up, connect the

Figure 7: simple power supply circuit

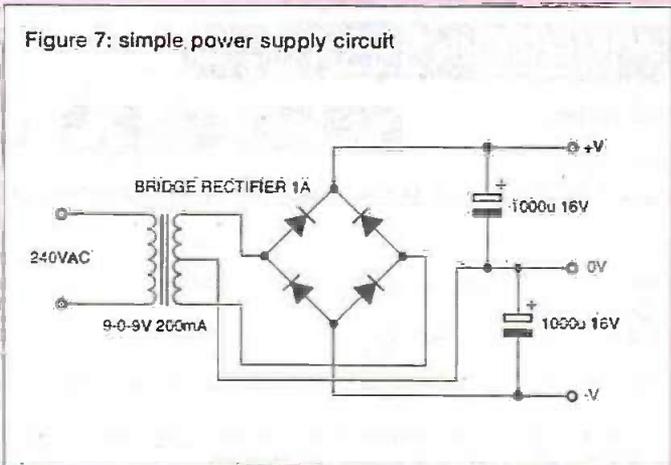

power supply and check the power supply pins of the IC sockets which should be at $\pm 5V$ as shown on the circuit diagram. Power down, insert the IC into their sockets, and power up again. Connect a composite video signal to PL2 (the A input), and monitor the output from PL3. The output can be connected directly into a TV set via a phono or SCART socket, or through a video recorder or modulator. At this point the display will be at half brightness, and will probably be rolling.

If you have a dual trace oscilloscope, trigger it from IC5 pin 7, connect channel 1 to the input on one end of R2, and channel 2 to pin 13 of IC6. Finally set the trigger delay to examine a line about 5ms into the field. Now adjust VR1 so that the output on pin 13 ends just before the line data, connect channel 2 on pin 5 of IC6, and adjust VR2 so that the signal ends just before the front porch. Now increase the timebase and monitor the outputs of IC7 to adjust VR3 and VR4.

If you do not have an oscilloscope then connect pin 10 of IC8 to +5v (connect to one end of R9 - make sure it is the signal end!). Now the display on the monitor should be blank, although the picture may show around the edges. Adjust VR1 to bring the picture onto the left of the display slowly, back off until the picture disappears and is stable. Now adjust VR2 so that the picture just disappears on the right hand side. In similar fashion use VR3 to adjust the top of the picture, followed by VR4 to make the entire screen black, and stable.

Using the sync board for a multi-function fader/wiper

In this section we will look briefly at a simple application of the sync circuit. With just two further ics and a handful of other components we can make a fader/wiper with the following functions:

- Fade picture out
- Wipe picture to left or right of screen
- Wipe picture to top or bottom of screen
- Direct switch of picture to black
- Fade, switch or wipe (effects 1-4) to black, white or any shade of grey

Any of these functions may be combined, for example the picture can be wiped off to any corner of the screen by combining the two wipe effects.

In addition any of the fade or wipe functions can fade or wipe to the picture on input B. Note that this input must be synchronised with the input on Input A. Typically this may be the output of a character or caption generator, although these devices often include their own wiper/fader functions.

Figure 8 shows the extra components needed to make the fader/wiper. This circuit can be constructed on strip board. Do not fit PL4 on the sync board, simply wire the circuits of figure 8 directly to the holes for PL4. As much or as little of this circuit can be constructed depending which functions are required. The potentiometer controls in this circuit should be slide devices.

Fade input A

Figure 8a shows the circuit for the variable gain control which can be used to fade the video input to black, white or any shade between. The potentiometer and resistors are chosen to provide a voltage from -0.6V to +0.6V to control the gain input of IC2. The unity gain buffer matches the to the low input impedance of the gain input of IC2.

The SCART socket

The SCART socket (also known as a Peritel socket), is now widely supported on video equipment, particularly in Europe. The diagram shows the layout looking down into the socket. The socket is normally 21-pin, although the final pin is usually formed from the body of the connector which forms a safety ground. All the projects in this series can be interfaced via a SCART connector, although for convenience they are all shown with phono sockets.

The pinout depends on the specific functions implemented, however certain pins such as audio and composite video are present in all implementations. For any project in this series with most videos and TV sets pins 1,2,3,4 and 6 will provide audio in and out, and pins 17,19, and 20 will provide video input and output.

The table below shows the SCART pinouts, note that where a pin is not designated as input or output (eg Blue) then it is usually an output on one device, and an input on another. Where a pin has more than one function dependant on function then these are shown in the description column. The most common function is shown first in each case

SCART connector pinout

Pin	Signal level	Impedance	Description
1	0.5V	less than 1K	Audio mono out Audio right out
2	0.5V	more than 10K	Audio mono in Audio right in
3	0.5V	less than 1K	Audio mono out Audio left out
4	0V	more than 10K	Audio ground
5	0V		Blue ground
6	0.5V	more than 10K	Audio mono in Audio left in
7	0.7V	75R	Blue in/out
8	Digital		Function select HD status in/out
9	Ground		Green ground
10	Digital		Data (2)
11	0.7V	75R	Green in/out
12	Digital		Data (1) HD vsync in/out
13	0V		Red ground
14	0V		Data ground
15	0.7V	75R	Red in/out Chrominance video in/out
16	Digital		RGB Control (High=RGB Low=Composite) HD vsync in/out
17	0V		Video ground
18	0V		RGB control ground
19	1V	75R	Composite video out
20	1V	75R	Composite video in Luminance video in/out
21	0V		Safety ground

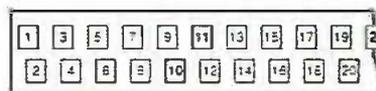


Figure 9: the SCART socket

The S-Video Connector

This type of connector is a 4 pin mini DIN plug. The composite video signal comprises the brightness signal (luminance) with the colour signals (chrominance) modulated on a 4.33 MHz sub carrier. The operation of modulating the colour signal onto the composite video signal, and then demodulating introduces noise. In addition to this high frequency variations in the brightness signal can create false colour signals (the effect can commonly be seen on small checked jackets on TV pictures).

To carry high quality video signals such as those recorded on hi-band camcorders the S video connector is used. On this type of connector the Y signal contains the brightness information with no colour burst, and no colour information, the C signal contains the colour information. This also allows

the Y signal to have a higher bandwidth than in a composite video signal, and more detail is available. It is notable that the eye can detect detail in the brightness domain with greater detail than colour, therefore increasing bandwidth of the Y signal only give the illusion of overall increase in bandwidth.

The pinout of the S-Video connector:

Pin	Function
1	Luminance Ground
2	Chrominance Ground
3	Luminance (Y)
4	Chrominance (C)

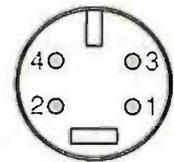


Figure 10: the Video connector

Fade/wipe shade control

Figure 8b shows a simple control to force the wipe or fade shade to any brightness between black and white. The potentiometer and resistor are chosen to produce a luminosity voltage between 0V and +0.7V which is buffered by the op-amp. As the B input is AC coupled this DC voltage cannot be directly used into input B, but must be connected to a point where DC restoration has been used, in this case the junction of R17 and IC2/1. Note that if fading or wiping to input B is to be used, then this circuit cannot be used.

An interesting effect is to set the fade control to half, and the shade to white, this gives the effect of peering through fog, although the usefulness of this function may be questioned.

Sideways wipe

Figure 8c is a sideways wiper. This operates by using a monostable triggered from the rising edge of the line data valid signal to produce a pulse which switches off the video signal during the line. The period of the monostable is controlled by the potentiometer, and the output of the monostable drives the

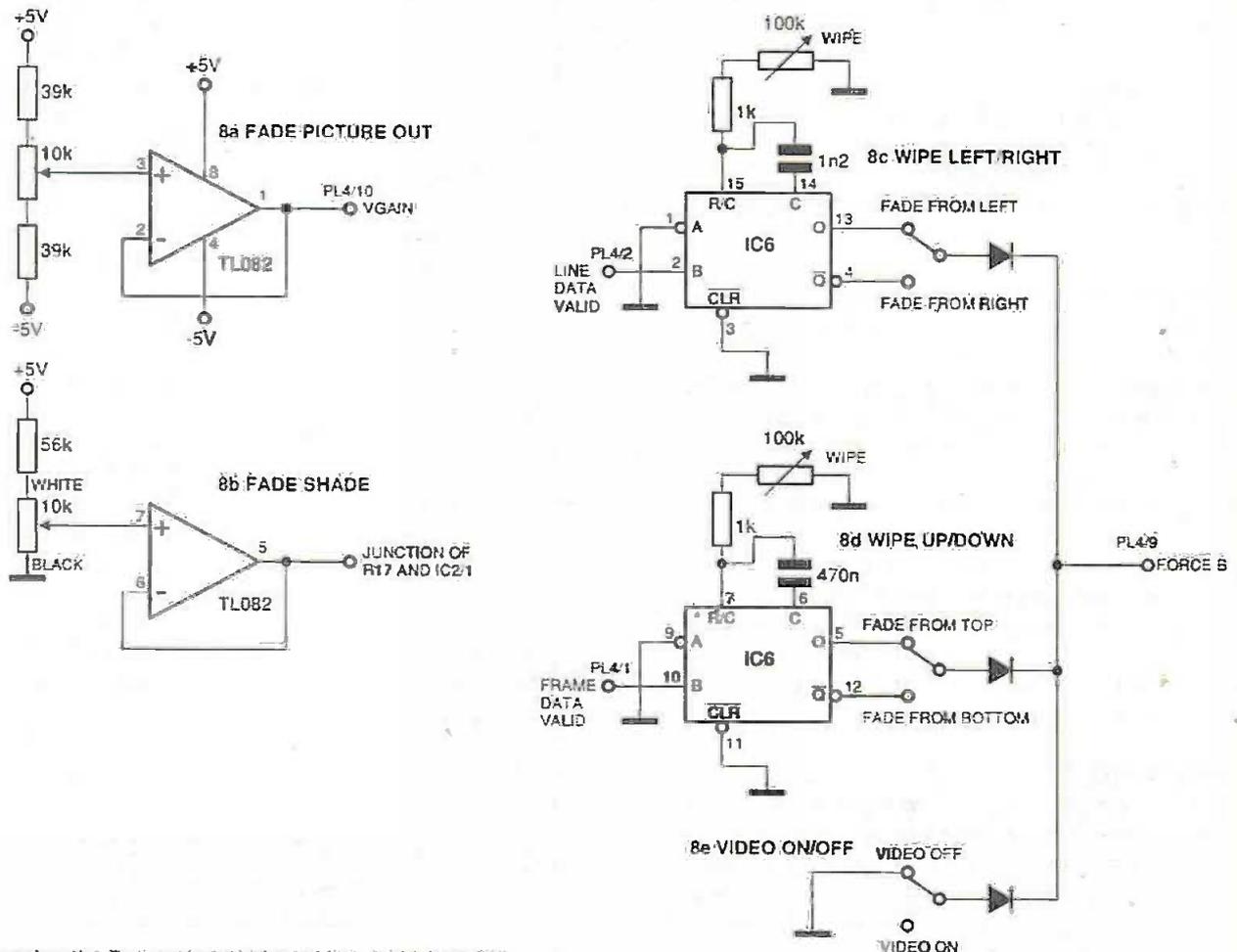


Figure 8: using the Syric separator board in a multi-function fader/wiper

force B input of the sync board. By using either the true or inverted output the wipe can be forced from the left or the right of the screen.

Note that the functions of figure 8c, 8d and 8e all drive the force B input to switch the video signal. To achieve this a simple diode OR circuit is used.

Up/down wipe

Figure 8d is the up/down wiper control which operates in the same way as Figure 8c, however it operates from the field data valid signal, and has a time constant which is much longer than the sideways wiper of frame length. Note that the on/off signal may occur during a line, and therefore the vertical fader may switch during a line causing a partial line to be displayed at the boundary of the wiped area. This is very unlikely to be

noticed, but if it is thought to be a problem then the output should be retimed by a flip flop (eg HC74) triggered by the line data valid signal to ensure that switching only occurs at the beginning of a line. The full function digitally controlled mixer to be presented in the next article uses this technique.

Video on/off

This simple switch function provides a direct on/off control for the video.

Next month

In the next article we will look at using the sync board in a full function digitally controlled fader/wiper which can be controlled from a PC, or from a keypad.

PARTS LIST

Resistors All 1% 0.25 watt

R1,2,7	75R
R3,4,5,6	1K
R8,9,10,10K	
R12	56K
R14	39K
R15	680K
R16,17	430K
VR1,2,3,4	22k horizontal preset

Capacitors

C1,8-10,14-16,18-20	0.1uF disc ceramic
C2,4	1nF disc ceramic
C3,5	1uF 10V radial electro
C6,7,12,13	10uF 25V radial electro

Semiconductors

IC1	EL2244
IC2	EL4095
IC3	EL4581
IC4	78L05
IC5	79L05
IC6,7	74HC123
IC8	74HC00
IC9	74HC4066

Miscellaneous

PL1,2,3 PCB mounted phono sockets
 PL4 16 way 0.1in IDC header
 Veropins, 2 x DIL 8 pin ic sockets, 3 x DIL 4 pin ic sockets, 2 x DIL 16 pin ic sockets
 All parts are available from Maplin and other regular suppliers.

ETI

Book of Electronics

An introduction to electronics that clearly explains the theory and principles involved. Each chapter includes a project to make. Projects include a loudspeaker divider, continuity tester, mini amplifier, a burglar alarm and more!

ETI Book of Electronics

ISBN 0 85242 928 2 **£10.95**

P&P + 10% (minimum £1)

Overseas + 20% (minimum £2)

Telephone orders (01442) 66551

I enclose my remittance of Please make cheques payable to Bailey Distribution and send to the address below.

Please charge my Mastercard/Visa

Expiry Date Signature

Name

Address

Postcode

Complete details and return to Bailey Distribution, Learoyd Road, Mountfield Road Industrial Estate, New Romney, Kent. TN28 8XU


Data Protection: Please tick this box if you do not wish to receive information from any other carefully vetted companies

THE
ETI
 BOOK
 OF
ELECTRONICS

DAVE BRADSHAW

PIC16C84 and BIM Transceiver Development Platform in one!

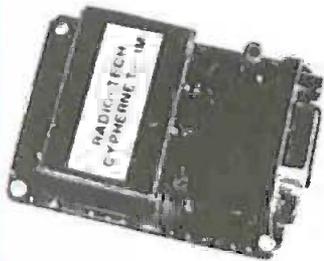A hardware development platform for exploring high speed, PC-PC, half duplex, two way Radio Data Communications!



Radio-Tech Limited CYPHERNET -1M
Measures only: 39 x 55mm x 17mm

- INCLUDES:-**
- 10MHz PIC16C84
 - BIM-418-F Transceiver
 - 9-Pin D-Type Connector
 - 2-Wire RS232 Interface
 - Transmitter On LED
 - Receiver On LED
 - 1/4 Wave Wire Antenna

Supplied with a free firmware driver the Cyphernet transceiver will permit you to link PC's and transfer data using Windows terminal mode. Only 79.95 each

Combined power and RS232 data-cable. Only 6.95 each.



Dedicated PIC16C84 programming tool for re-programming the internal control firmware, permitting the user to explore and develop applications of their own. Only £ 94.95 each.

Unit featured above is Licence Example to MPT1340 within the UK. Export Versions on 433.02MHz to ETS300-226 available with 1 and 10mW output power. Prices exclude VAT and Carriage.

Radio - Tech Limited, Overbridge House, Weald Hall Lane
Thornwood Common, Epping, Essex CM16 6NB.
Sales +44 (0) 1992 57 6107 (4-lines) Fax +44 (0) 1992 56 1994
<http://www.radio-tech.co.uk> E-Mail radtec@radtec.demon.co.uk

Smart Cards & Systems

Thousands of profitable smartcard applications are just waiting to be developed.

We can supply you with smartcard development tools, products and even with ready solutions.
Explore the smartcard technology with our NEW low cost smartcard evaluation and development kits.

Send your details NOW for our free information pack!!

EPSILON ELECTRONICS

Brynsengvn. 1a, 0667 Oslo, Norway
Tel/Fax +47 22640810

For product information, please visit our WEB site: <http://www.epsilon.no>

E-MAIL: epsilon@powertech.no
WEB: <http://www.epsilon.no>

10% DISCOUNT TO ALL ETI READERS

0-12" (300mm) Digital LCD Calipers £99.95 £89.95 inc



0-6" (150mm) Digital LCD Callipers £49.95 £44.95 inc



AUTO TURN OFF

MEASURE INSIDE, OUTSIDE AND DEPTH.
ZERO ANYWHERE ON THE SCALE. CONVERTS METRIC TO IMPERIAL AND VICE VERSA

BOTH THESE CALIPERS MEASURE TO A RESOLUTION AND REPEATABILITY OF 0.01mm/0.0005" AND ARE POWERED BY ONE STANDARD 1.5V SILVER OXIDE BATTERY. THE PRICES INCLUDE A FOAM LINED CARRY CASE, VAT, POST AND PACKING (IF YOU ARE NOT COMPLETELY SATISFIED WITH YOUR PURCHASE SIMPLY RETURN IT TO US WITHIN 30 DAYS FOR AN IMMEDIATE NO QUibble REFUND. THIS OFFER DOES NOT AFFECT YOUR STATUTORY RIGHTS)

From: KPL, 226 WHITEHORSE ROAD, CROYDON, SURREY, CR0 2LB
OR CALL TO ORDER: 0181 665 1041
FOR MORE DETAILS AND OTHER SPECIAL OFFERS.



New Free 1997 Catalogue!

Fourth International Edition

Radio - Tech Limited

Helping ManKind With Affordable Wire Free Radio Data Communications Solutions

Manufacturing EPOS Agriculture Irrigation Environmental

<http://www.radio-tech.co.uk>

Tel +44 (0) 1992 576107 (4-lines) Fax +44 (0) 1992 561994
Overbridge House, Weald Hall Lane, Thornwood, Epping

- EPOS
- Telemetry
- Security
- Metering
- Spread
- Spectrum
- Frequency
- Agile
- Modems
- Antenna
- Dev. Tools
- EMC

To Request a Copy of the Radio - Tech, Fourth Edition Radio Data Module Catalogue Contact:

Overbridge House, Weald Hall Lane
Thornwood Common, Epping, Essex CM16 6NB.
Central Office +44 (0) 1992 57 6107 (4-lines)
Fax +44 (0) 1992 56 1994
Technical Support + 44 (0) 1992 57 6114

E-Mail radtec@radtec.demon.co.uk

AN5521	1.35	STK734102	5.95	TEA2026C	4.50
AN5732	1.40	STK73605	4.50	TEA5170	1.40
AN6327	9.85	STR441	18.99	TUA2000-4	4.25
AN6577	8.50	STR451	29.99	U884B	2.35
BA5114	1.55	STR3125	5.50	UAA1008	3.00
BA6218	1.85	STR4211	5.50	UPC1178	1.05
BA6219	1.20	STR4090	11.15	UPC1162H	5.15
HA11423	1.65	STR20005	5.00	UPC1278H	2.20
HA13119	2.50	STR40090	4.00	UPC1420	4.50
KA6210	4.99	STR50103A	3.85	UPD1937	3.00
LA3220	0.60	STR54041	3.75	25A814	0.71
LA4183	1.35	STR58041	3.75	25A839	1.40
LA4445	1.90	STR80001	6.00	25A1082	1.00
LA4495	1.40	STR1706	4.75		
LA4588	2.55	STRD1806	4.50		
LA7835	2.35	STRD6008	10.00		
LB1415	2.25	TA227	1.85		
LM301	0.25	TA7271	2.50		
LM317T	1.50	TA7260	2.25		
M491BBI	4.75	TA7281	2.20		
M498BI	6.75	TA7698	5.00		
M51393	5.95	TAB200	3.50		
M58655	3.30	TAB210	3.00		
MB3739	1.70	TAB214	3.00		
MB3756	8.00	TAB215	3.00		
STK078	6.00	TAB205	3.95		
STK435	4.00	TAB659	13.00		
STK461	10.50	TA75339	13.00		
STK2250	7.45	TDA3500	4.99		
STK4121/2	7.00	TDA3645	8.00		
STK4141/2	5.50	TDA3650	8.99		
STK4142/2	6.50	TDA3850	18.99		
STK4162/2	6.25	TDA4400	1.75		
STK4171/2	8.10	TDA4500	3.50		
STK4191/2	8.50	TDA4505A	4.10		
STK4352	6.20	TDA4505B	4.10		
STK4372	5.65	TDA4505M	5.25		
STK4803	7.05	TDA4505K	6.15		
STK4843	7.05	TDA4660	4.50		
STK5315	5.85	TDA4950	1.40		
STK5332	1.80	TDA5660P	2.50		
STK5338	3.25	TDA7072	9.99		
STK5361	4.15	TDA8370	14.00		
STK5372	2.85	TDA8405	8.00		
STK5372H	4.15	TDA8732	5.95		
STK5412	3.75	TEA2018A	1.50		
STK5471	3.85				
STK6732	14.00				
STK7226	7.50				
STK7308	4.05				
STK7306	4.05				
STK7348	4.05				
STK7356	4.75				
STK7004	6.50				
STK73410	5.15				

ELECTROLYTIC CAPACITORS

250V Working	
1UF (5pack)	1.00
4.7UF (5pack)	1.50
10UF (5pack)	1.70
22UF (each)	0.40
33UF (each)	0.55
47UF (each)	0.65
100UF (each)	1.28
400V Working	
1UF (5pack)	1.10
4.7UF (5pack)	1.50
10UF (each)	0.70
22UF (each)	0.75
4.7UF (each)	1.40

IC-DATABASE ON FLOPPY DISK

The most important technical data & functions of 4500 series (20K MC's & 22K Transistors) / Track on floppy disk only £14.95 + pp & Vat

TEST CD2

This CD can be used to control CD player - 71 different test signals - Running time 30 min - Serial / Recorders & Print nodes - Complete with instruction book £12.99 each

TEST CD3

With this CD a technician can control & adjust the electrical data of CD players in a minutes or less will improve the repair results by adjusting cd player after changing the laser unit. £20.99 each

Please email us for the types not listed. Please add 5% postage packing and then add 17.5% VAT to the total. Orders by appointment only.

JAB COMPONENTS
63 THE CHASE, EDGEWARE, MIDDY HAYSON, ENGLAND
Hotlines No 081 381 1700/081 952 4631
Free Fax order Line only: 0800 318496
General Fax 061 381 1700

Peaceful Waves

BIOFEEDBACK

There is nothing so relaxing as the sound of surf on faraway sands. With a bit of imagination, and Robert Penfold's biofeedback monitor, you too could drift away from it all

In many ways Harold Macmillan was right when he said that most of us have "never had it so good", but modern life does have its down-side. Stress levels certainly seem to be on the rise, and means of combatting stress are not only of interest to high-powered executives. High tension (not the electrical kind) and anxiety now seem to trouble a substantial percentage of the population. This subject may seem to be outside the realm of electronics, but an electronic means of easing tension has been in existence for many years. The process is known as biofeedback.

Strain gauges

At one time biofeedback was not taken entirely seriously, and had a slightly zany image. However, over the years it has proved to be beneficial to most of the people that have tried it, and it can often be very effective indeed. Biofeedback is certainly taken more seriously these days, aided by the fact that it does not involve the use of any drugs which could be addictive or potentially harmful.

The basic idea is to have an electronic monitoring device that indicates how relaxed or stressed you are. You then try to relax while looking for any changes from the monitoring device. If you do something that relaxes you, the reduction in stress will be indicated by the biofeedback monitor, and you continue to do whatever it was that

produced the improvement. If you lapse, and do something that causes an increase in stress, such as thinking about problems at work, the increased tension will be indicated by the monitor. You then act on the information from the biofeedback monitor, and think about something more relaxing again.

The feedback comes in the form of a signal (the type of signal that is displayed is decided by the biofeedback unit - it

could be sound, or light, or a trace signal, for example) derived from the user's state of tension by the unit. The monitor relays the signal, and as the user responds to the information on the monitor, it is to be hoped that the signal will change in the direction of showing greater relaxation. The user is then part of a negative feedback circuit, steadily reducing tension, if the system has the desired effect.

A biofeedback monitor can be surprisingly basic. There are three common methods of monitoring the subject's state of relaxation. These are heart rate, skin resistance, and skin temperature. Heart rate tends to reduce if someone becomes more relaxed, or increase if they become more stressed. Skin resistance varies with the degree of perspiration, and we tend to perspire more when stressed. The more the subject sweats, the lower his or her skin resistance becomes. Therefore, the higher the user's skin resistance, the greater the degree of relaxation.

There may seem to be no obvious link between skin temperature and tension, but stress can cause reduced blood flow to the extremities, and reduced skin temperature. This is the opposite of what one might expect, since tension also causes increased heart rate. Apparently, stress results in less efficient circulation despite the increased heart rate. Hence someone under a lot of tension usually ends up with cold but sweaty palms.

The heart rate monitoring method is perhaps the best,

because heart rate changes relatively rapidly with changes in stress level. Its drawback is that it is relatively difficult to produce a heart rate monitor that is inexpensive, easy to use, and gives reliable results. Monitoring skin resistance is usually quite effective, has a reasonably rapid response time, and requires only the most basic of circuitry. The skin temperature method is also very simple and inexpensive, since it is only relative temperature that is of interest. A very basic temperature


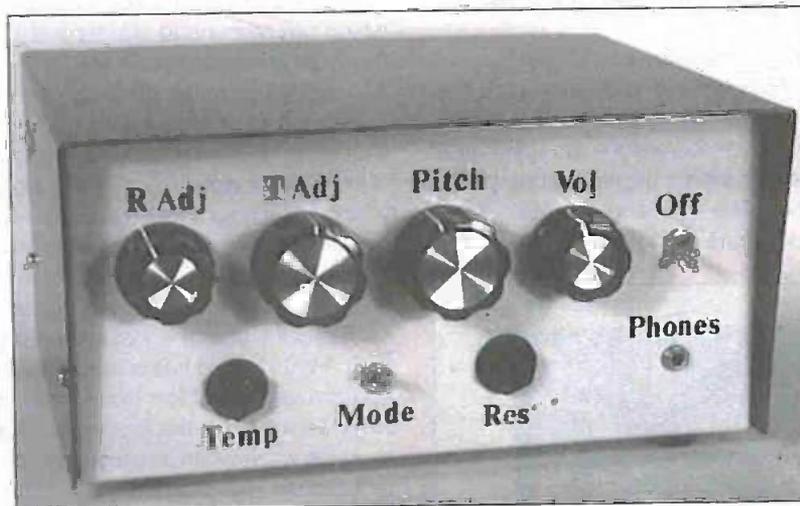


Figure 1: the circuit diagram for a minimalist biofeedback monitor which responds to changes such as skin resistance.

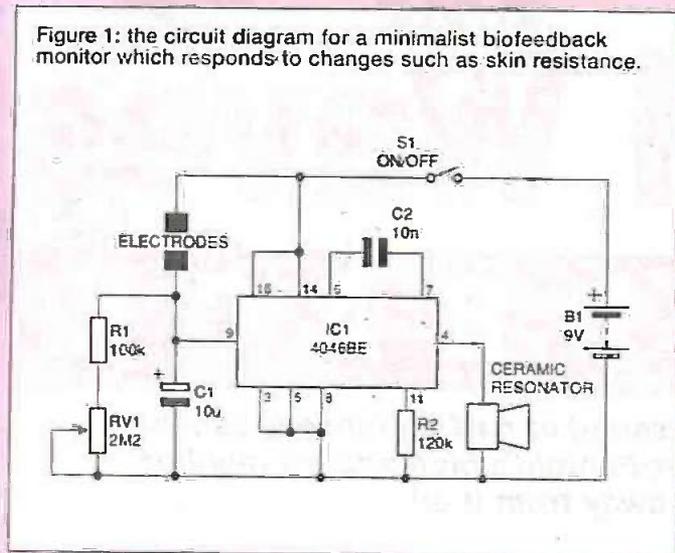


sensor such as a thermistor is perfectly satisfactory. In my experience the skin temperature method has the drawback of a relatively slow response time, and it is perhaps a little less reliable than the other two systems.

Toning it down

A biofeedback unit can be extremely basic, and anything that indicates the user's stress level can be used. Most units use a meter or some form of audio signal to indicate the user's stress level. The circuit of figure 1 is for a minimalist biofeedback monitor which can be built for a few pounds, and uses the skin resistance method. It is basically a CMOS 4046BE (IC1) used as a low frequency vco (voltage controlled oscillator). The output of the oscillator drives a ceramic resonator which produces a low frequency audio tone. The control voltage for IC1 is generated by a potential divider which has the resistance across the electrodes (in effect, the user's skin resistance) as for the upper arm, and the series resistance of R1 and VR1 as for the lower arm. C1 filters out any mains hum or other electrical noise which could otherwise produce erratic results from the circuit.

VR1 is adjusted for an output frequency that is somewhere in the middle of IC1's frequency range. If the user's skin resistance reduces, the control voltage to IC1 also reduces, and the pitch of the audio tone becomes lower. A decrease in the user's skin resistance has the opposite effect, with a higher control voltage and audio tone being produced. The user therefore tries to obtain the lowest possible audio tone from the monitor.

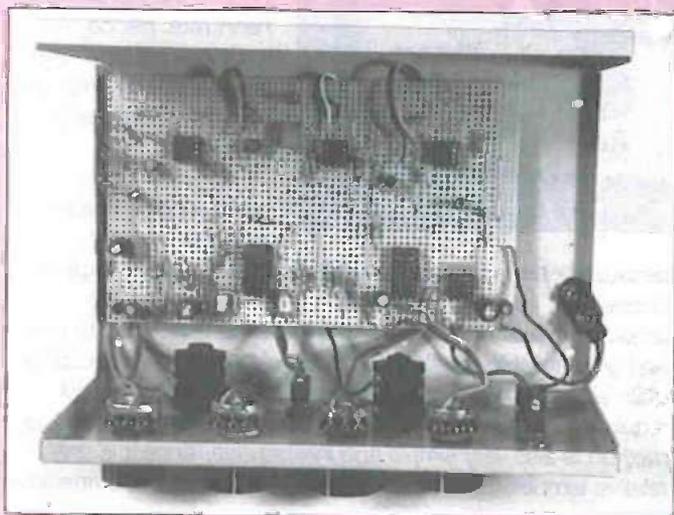

The modern trend is to use a more sophisticated form of signal to the user. This makes the system more interesting to use, and can actually aid relaxation. At its most advanced the system can have computer sound and graphics, with the onscreen action getting more pleasant if the user becomes more relaxed, or more unpleasant if the stress level increases. To some of us this seems more threatening than promising! At a less sophisticated level, the feedback could be in the form of a change in the colour of the room lighting, or via a more complex audio signal than a simple tone generator.

I suppose there is a potential flaw in any system which uses complex feedback. This is simply that the feedback which aids relaxation when things are going well could increase stress if things start to go wrong. In practice this does not seem to be a significant problem, provided a bit of common sense is used when designing the exact form of the feedback. This simply means that the feedback must not provide any sudden noises, flashing lights, or include anything which is seriously unpleasant.

Wave goodbye to stress


My experiments with various forms of feedback signal produced quite good results, and they were more fun to use than simple tone generators and meters. In general their effectiveness was not substantially better than more simple forms of feedback, but there were one or two exceptions. Some forms of sound feedback certainly seem to be above average in their efficacy. This unit, as finally developed, uses filtered noise which gives a synthesised breaking wave sound. The more relaxed the user becomes, the slower and more gentle the wave sound becomes. The sound of waves splashing onto the beach seems to have a relaxing effect on its own without any feedback element, and it is presumably this factor which aids the efficiency of the system. Sounds based on white noise tend to mask noises in the environment, and cut you off from the outside world. This possibly further accounts for the effectiveness of noise based sounds in this application.

Figure 2 shows the block diagram for the biofeedback unit, which can respond to skin temperature or skin resistance. A noise generator produces the basic "white" noise "hiss" signal. A substantial amount of signal processing is needed in order to mould this into the required breaking wave sound. Envelope shaping is needed in order to give suitable variations in the volume of the signal. The sound must build up quite rapidly in volume as the synthesised wave crashes down onto the beach, and then fall back in volume much more slowly. The pitch of the sound falls as the volume increases, and then rises again as the volume gradually falls away.

The first stage of signal processing is a simple low pass filter. "White" noise has a much stronger content at high frequencies than at low frequencies. This is the opposite of what we require in the final output signal, where the signal must be weak when it is high in pitch. The lowpass filtering reduces the high frequency content of the signal, so that it is easier for the envelope shaper to give the desired effect. The output signal from the noise generator is quite low, and it is reduced still further by the lowpass filtering. A high gain amplifier is used to boost the signal to a more useful level.

A vcf (voltage controlled filter) provides the changes in pitch, and a vca (voltage controlled amplifier) gives the required changes in the signal's volume. Both are controlled by a low frequency oscillator which provides a form of sawtooth waveform. The signal rises quite rapidly on its leading edge,

Figure 2: the block diagram for the biofeedback unit

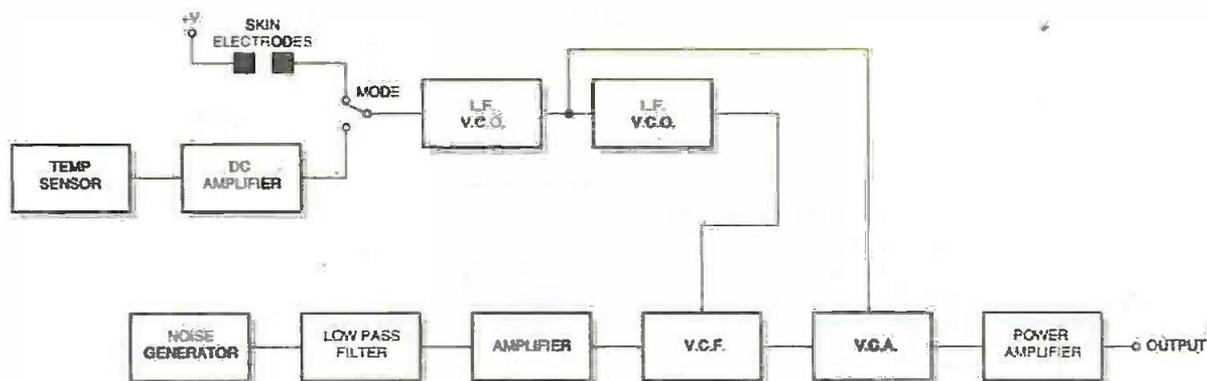

and decays much more slowly on the trailing edge. It therefore provides the required volume shaping if it is fed direct to the control input of the vca. An inverted version of the waveform is fed to the control input of the vcf. This gives the desired effect with the pitch of the noise falling rapidly as the volume quickly reaches a peak, and then rising more slowly as the volume steadily dies away.


The low frequency oscillator is voltage controlled, and the rate at which the "waves" occur is governed by the input voltage to this stage. The mode switch enables the user to select either a skin temperature or a skin resistance sensor. The skin resistance sensor uses what is essentially the same setup as the one used in figure 1, and described previously. The skin temperature sensor uses a thermistor connected in a potential divider, but the small changes in temperature involved in this application produce only minute changes in the output voltage from the potential divider. A d.c. amplifier is used to boost the voltage changes to a high enough level to drive the low frequency vco properly.

The circuit

Figure 3 shows the full circuit diagram for the biofeedback monitor. The noise generator is based on TR1, which has its base-emitter junction reverse biased by R1. This results in the junction breaking down in zener diode fashion. Also like a zener diode, TR1 generates a useful amount of "white" noise. The noise level is substantially higher than that from a zener diode, but it is produced over a much narrower bandwidth. However, in this case it is only audio frequency noise that is required, and the noise bandwidth is more than adequate for this application. Note that no connection is made to the collector terminal of TR1. TR2 operates as a common emitter amplifier which boosts the noise signal. C3 provides the lowpass filtering.

The vcf is based on IC1, which is a dual transconductance amplifier. It is used in a form of state-variable filter, giving a bandpass output from IC1a, and a lowpass output from IC1b. In this case it is bandpass filtering that gives the best results, and it is therefore the output from IC1a that is utilised. R4, R5, and C4 provide a mid-supply bias voltage for the vcf and vca circuits. The disparate values of R4 and R5 take into account the loading on the bias circuit. Strictly speaking, the filter circuit is current rather than voltage controlled. R17 has been added in series with the control inputs of IC1, and this effectively


converts the circuit from voltage to current control. IC2 is used in the v.c.a., and this is another dual transconductance amplifier. Only one section of IC2 is required, and no connections are made to the other section. R22 is used in series with the control input of IC2 so that voltage rather than current control is obtained. The output from IC2 is coupled to a small audio power amplifier (IC3) via the volume control (VR1). IC3 provides a certain amount of voltage gain, but it is included primarily as a buffer amplifier to provide the relatively high output currents required by some headphones. The circuit was designed for use with personal stereo style headphones with the two earphones wired in series. The circuit will drive practically any headphones though, and it will even give reasonable volume if used with an eight ohm impedance loudspeaker.

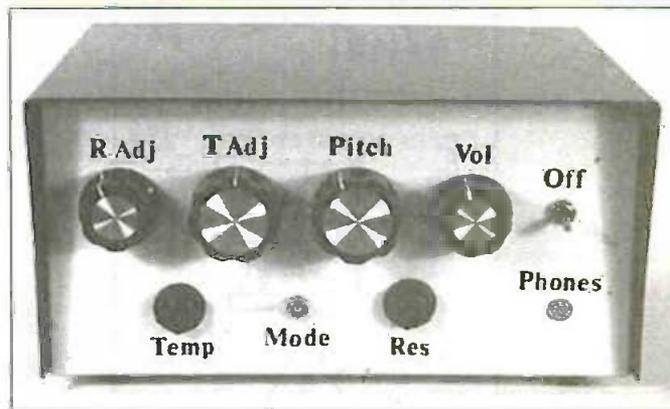

Under no circumstances should the output of the unit be coupled to a mains powered audio amplifier or any mains powered equipment.

A completely different and more stringent set of safety rules apply to a device such as this, which connects to the user via electrodes. A severe electric shock could be delivered via the electrodes if a fault should occur, and it would be very difficult for the user to remove the electrodes. It is only acceptable to use the unit with mains powered equipment if there is an

Figure 3: the full circuit diagram for the biofeedback monitor.

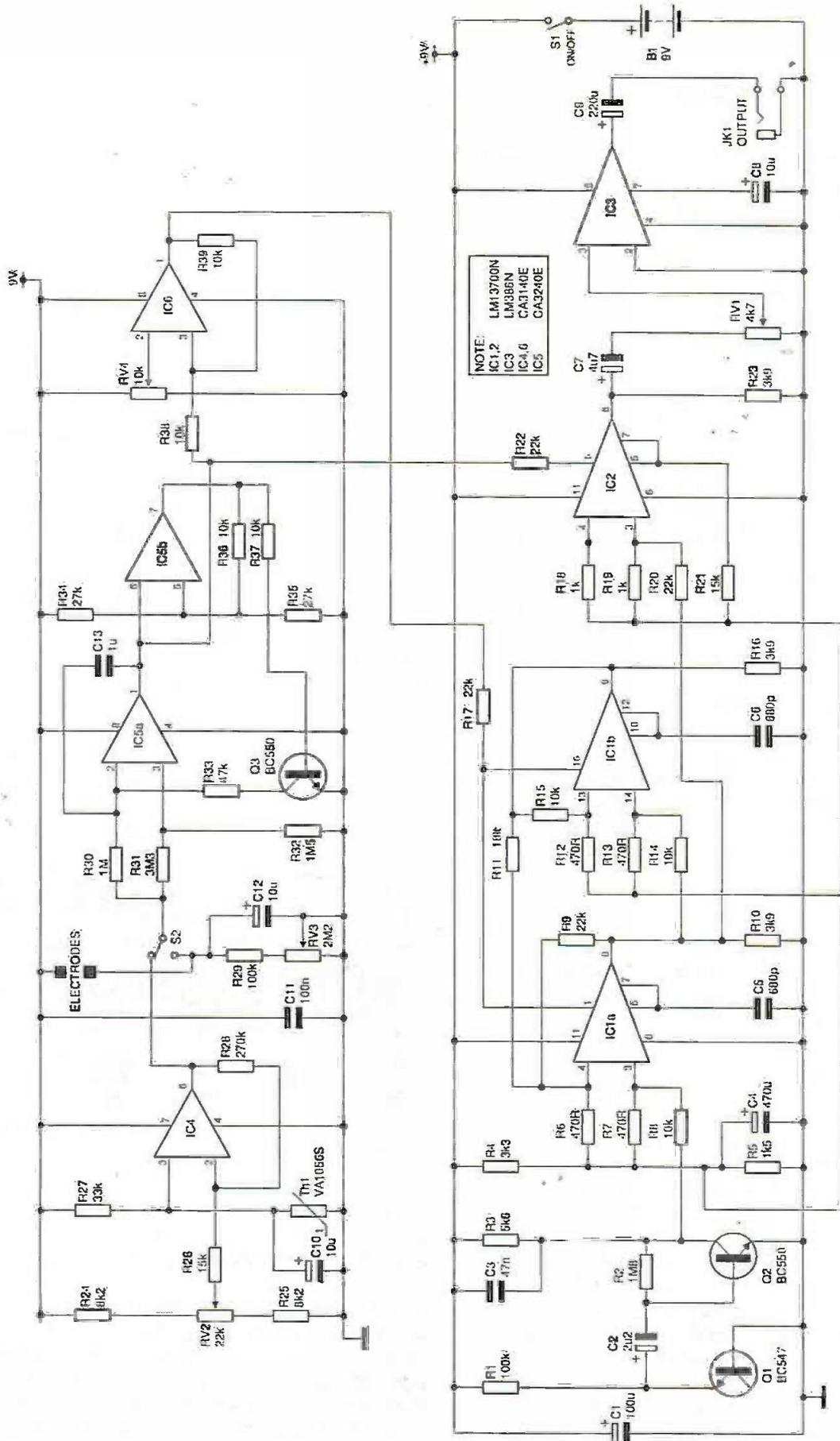


extra stage of isolation somewhere in the system (for example, to connect the audio output of the biofeedback unit to a hi-fi amplifier via a suitable opto-isolator circuit). Using battery power and headphones gives excellent results, and avoids complications.

The inverter stage uses IC6 as a standard inverting mode voltage follower circuit. VR4 enables the bias level at the non-inverting input of IC6 to be adjusted, and this provides control over the pitch range of the voc. It is simply set for the pitch range that gives the most convincing wave effect. IC5 is used in a simple vco circuit which would normally provide a

squarewave output from IC5b, and a triangular waveform from IC5a. The ratios of the resistors at the input of the circuit have been deliberately distorted from their normal figures in order to produce a suitable sawtooth waveform at the output of IC5a.

S2 enables the user to select either the skin resistance or the skin temperature sensor. The skin resistance sensor is a potential divider circuit, as used in the simple biofeedback circuit of Figure 1. The temperature sensor has thermistor Th1 connected in a potential divider circuit, and IC4 as the dc amplifier. IC4 is used as a non-inverting amplifier which has a closed-loop voltage gain of around ten times. VR2 provides an adjustable bias level to IC4, and it is adjusted to give a roughly mid-supply output voltage. C10 provides filtering of any mains hum or

Figure 4: the stripboard layout. The board measures 64 holes by 39 strips

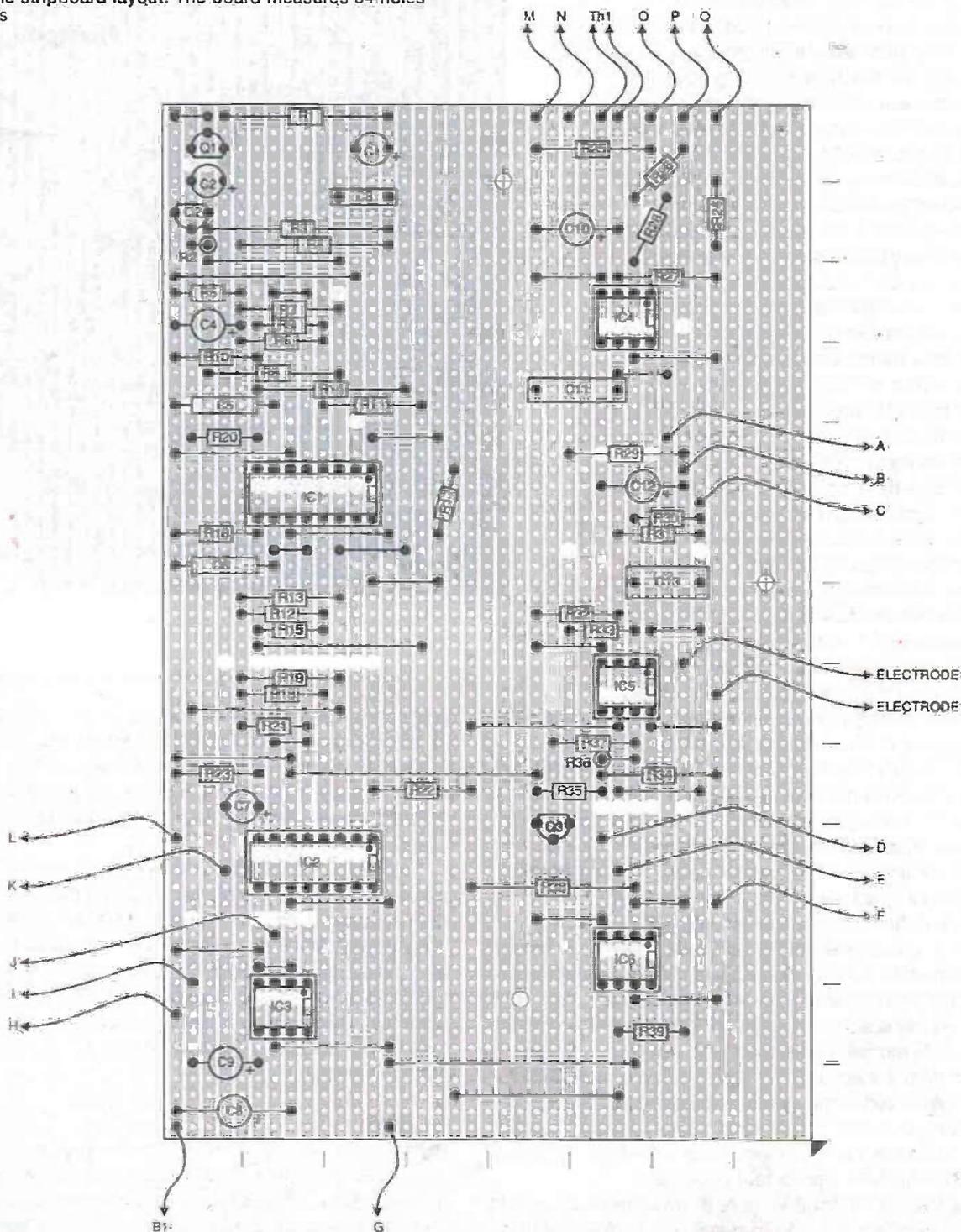

other electrical noise picked up in Th1's connecting cable.

The quiescent current consumption of the circuit is approximately 25 milliamps, but the current drain can be substantially higher than this if the unit is used at high volume levels. A high capacity nine volt battery is required, such as six HP7 size cells in a plastic holder. For the reasons explained previously, this unit must not be powered from a mains power supply.

Construction

Details of the stripboard component layout are provided in figure 4, and the underside view of the board is shown in figure 5. A board having 64 holes by 39 copper strips is required, and this can conveniently be a piece cut from a standard 300mm x 100mm board. After trimming the board to size, drill the three mounting holes and make the necessary breaks in the copper strips. The breaks can be made using the special tool, or a hand-held twist drill bit of about five millimetres in diameter will do the job quite well.


The CA3140E and CA3240E integrated circuits have PMOS input stages, and require the normal anti-static handling precautions. Both devices are operational amplifiers that will operate properly in single supply dc amplifier circuits. Most other operational amplifiers (741C, LF351N, TL071CP, etc.) will not work properly in this circuit. The circuit will work using either LM13700Ns or LM13600Ns for IC1 and IC2, or a mixture of the two. TR1 can be virtually any silicon npn transistor. There is a slight problem in that the reverse base-emitter breakdown voltage of some transistors might be a little high. This could result in the noise signal cutting off as soon as the battery voltage drops slightly due to ageing. It is probably worth experimenting with a few devices from the spares box to find one that has a low breakdown voltage.

With a large stripboard such as this I generally find things easier if the integrated circuit holders are fitted first, as they then act as markers which make it easier to navigate your way around the board. I then work my way across the board from left to right, adding the components and link-wires. I would certainly urge the use of methodical working, and not simply adding components here and there at random, which is usually a recipe for disaster. Be careful to fit the electrolytic capacitor with the correct polarity. To complete the board, fit single-sided solder pins at the points where connections to the controls, sockets, etc. will be made.

An instrument case about 200mm wide and 150mm deep will accommodate the circuit board and battery. Mount the board on the base panel of the case using 6BA or metric M3 fixings, including spacers about six to 12mm long. Position the board towards the rear of the case, and well over to the left (as viewed from the front). This keeps the board clear of the front panel mounted components, and leaves sufficient space for the battery pack to the right of the board. The front panel layout is not critical, but try to avoid long wires from the board to volume control VR1, and output socket JK1.

The hard wiring is shown in figure 6, which must be used in conjunction with figure 4. 3.5mm stereo jack sockets seem to

Figure 5: the underside of the component panel showing strip cuts

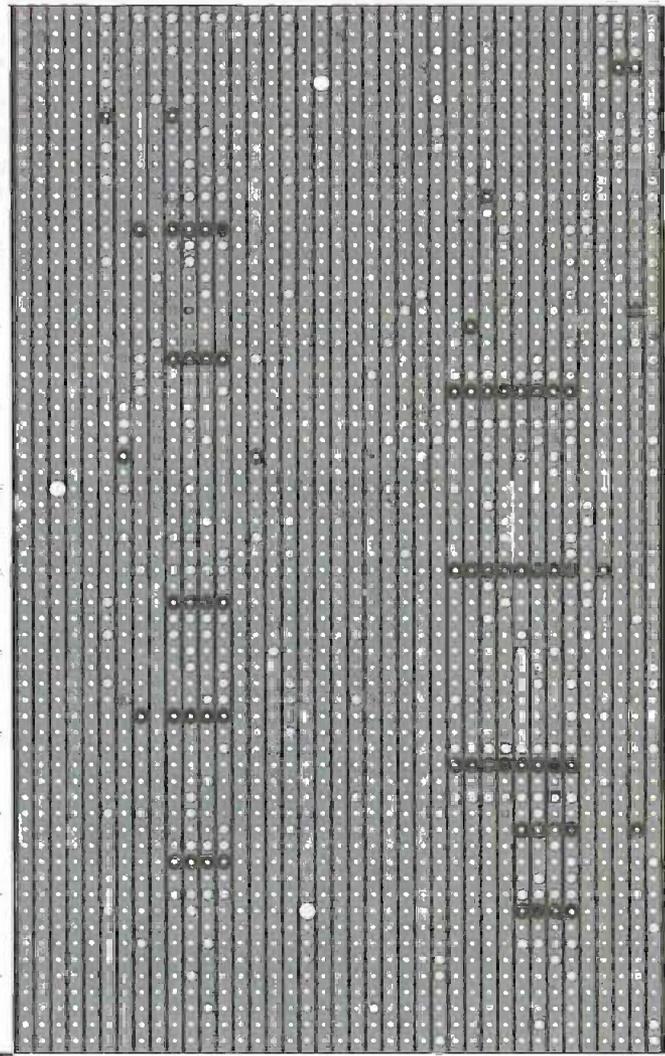


vary considerably in shape and size. On the prototype JK1 is a switched type, and it is this type of socket that is shown in figure 6. If you use a different type the wiring must be changed to suit. The earth tag is left unconnected, and the connections are made to the other two tags so that the phones are driven in series.

Thermistor Th1 and the skin electrodes can be wired direct to the circuit board, but on the prototype these connections are via standard jack plugs and sockets. It is not essential to use screened leads to make the connections to Th1 and the electrodes, since the circuit has built-in "hum" filtering. No problems were experienced when using non-screened leads about two metres or so in length. I used a VA1056S thermistor for Th1, but the circuit should work equally well using a 47k bead thermistor.

In use

Start with S2 set to the temperature mode. With Th1 in free air, adjust VR2 for a plausible wave rate, and then adjust VR4 for the best effect. The best wave sound is produced with VR4 set for a low sweep range, but not so low that the filter actually

Figure 6: details of the hard wiring (use in conjunction with figure 4)

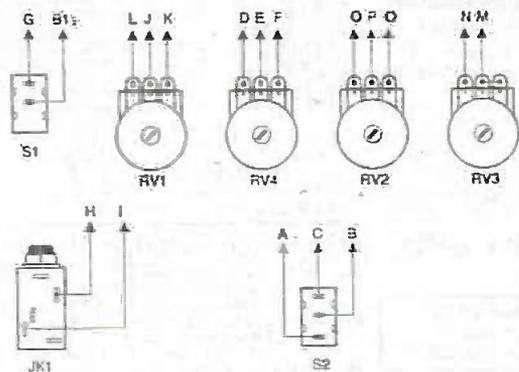

cuts off at the low frequency end of the sweep. If the temperature sensor is functioning correctly, touching Th1 should reduce the wave rate, and may bring it to a halt (a permanent wave?). In use the thermistor is simply taped to a finger, making sure that the user does not come into electrical contact with the thermistor's leads.

The skin resistance electrodes can be virtually any small pieces of sheet metal. A size of about 10mm square will suffice. It is difficult to make reliable soldered connections direct to aluminium and some other metals, but where necessary the connections can be made via solder tags bolted to the electrodes. This tends to produce rather chunky electrodes that can be difficult to use, so the direct connection method is the better one to use where it is possible. Small pieces of copper, peeled from a scrap of copper laminate board are quite effective, and can be connected direct to the leads. Whatever

you use for the electrodes, they must be kept reasonably clean and free from corrosion.

Good results seem to be obtained with the electrodes taped to finger tips or the palms of the hands. Another possibility is to have one electrode on the palm of a hand, and the other on the back of the same hand. Use the smallest amount of tape that will suffice, as there is otherwise a likelihood that the user will sweat a lot under the tape, rendering the results invalid. A fabric tape is the best type to use as it enables sweat to evaporate. Clipping the electrodes in place might be a better way of handling things. Simply holding the electrodes is ineffective, because the resistance between the electrodes varies enormously depending on how hard they are gripped.

The unit will usually respond quite rapidly if the user becomes more tense, but it takes longer to respond to a reduction in stress - just like reality, in effect. This is simply because you tend to sweat almost immediately when tension increases, but it takes time for skin moisture to evaporate. With any biofeedback system you should not be in any hurry, and must be prepared to give things time to work. Also, it is not just a matter of connecting everything up, switching on, and waiting to become more relaxed. You the user are an active part of the system, and must try to relax. This sounds like a contradiction, but it is the whole point of the exercise - once you have learned how to "become" more relaxed with the help of biofeedback, and learned what it feels like, you should be able to do it anywhere. Some things which people find help them are breathing deeply - not straining to breathe more deeply, but slowly and gently; or thinking of a place where you had a relaxing holiday and imagining how it felt to be there - not doing anything too exciting, of course. Perhaps of more importance, you must try not to think about things that produce increased stress. Biofeedback seems to work for most people, if it is given a fair chance.

PARTS LIST for Biofeedback

Resistors (all 0.25 watt 5% carbon film)

R1	100k
R2	1M8
R3	5k6
R4	3k3
R5	1k5
R6,7,12,13	470R (4 off)
R8,14,15,29,36-39	100k (8 off)
R9,17,20,22	22k (4 off)
R10,16,23	3k9 (3 off)
R11	18k
R18,19	1k (2 off)
R21,26	15k (2 off)
R24,25	8k2 (2 off)
R27	33k
R28	270k
R30	1M
R31	3M3
R32	1M5
R33	47k
R34,35	27k (2 off)

Potentiometers

VR1	4k7 log carbon
VR2	22k lin carbon
VR3	2M2 lin carbon
VR4	10k lin carbon

Capacitors

C1	100u 10V radial elect
C2	2u2 50V radial elect
C3	47n polyester (7.5mm lead spacing)
C4	470u 10V radial elect
C5,6	680p polystyrene (2 off)
C7	4u7 50V radial elect
C8,10,12	10u 25V radial elect (3 off)
C9	220u 10V radial elect
C11	100n ceramic
C13	1u polyester (10mm lead spacing)

Semiconductors

IC1,2	LM13600N or LM13700N (2 off)
IC3	LM386N
IC4,6	CA3140E (2 off)
IC5	CA3240E
TR1	BC547 (see text)
TR2,3	BC550 (2 off)

Miscellaneous

S1	spst min toggle
S2	spdt min toggle
JK1	3.5mm stereo jack socket
B1	9 volt (6 x HP7 size cells in holder)
Th1	VA1056S or similar thermistor
Case	about 200 x 150 x 100mm, 0.1 inch pitch stripboard measuring 64 holes by 39 copper strips, 8-pin dil holder (3 off), 16-pin dil holder (2 off), control knob (4 off), battery connector (PP3 type), wire, solder, leads and electrodes (see text), fixings, etc.

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

LOW COST PC's -

SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640K + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!
Order as HIGRADE 286 **ONLY £129.00 (E)**

- Optional Fitted extras: VGA graphics card £29.00
- 1.44Mb 3 1/2" floppy disk drive (instead of 1.2 Mb) £19.95
- Worperfect 6.0 for Dos - when 3 1/2" FDD option ordered £22.50
- NE2000 Ethernet (thick, thin or twisted) network card £29.00

LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd year, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256K cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable.
Many other options available - call for details. **Only £399.00 (E)**

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" or 3 1/2" from only £18.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC)

- 3 1/2" Panasonic JU363/4 720K or equivalent RFE £24.95(B)
- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GFR 1.2 Meg (for IBM post) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03-U 720K 4096 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy or HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £195.00(E)
- 8" Shugart 810 8" SS HH Brand New £195.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £250.00(E)
- Mitsubishi M2894-63 8" double sided NEW £275.00(E)
- Mitsubishi M2896-63-02U 8" DS slimline NEW £285.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only £259.00 or 2 for £525.00 (E)

- 3 1/2" FUJII FK-309-26 20mb MFM UF RFE £59.55(C)
 - 3 1/2" CONNER CP3024 20 mb IDE UF (or equiv) RFE £59.55(C)
 - 3 1/2" CONNER CP3044 40mb IDE UF (or equiv) RFE £68.00(C)
 - 3 1/2" RODIME R03057S 45mb SCSI WF (Mac & Acorn) £69.00(C)
 - 3 1/2" WESTERN DIGITAL 850mb IDE UF Brand New £185.00(C)
 - 5 1/4" MINISCRIBE 3425 20mb MFM UF (or equiv) RFE £49.95(C)
 - 5 1/4" SEAGATE ST-238R 30 Mb RLL UF Refurb £69.95(C)
 - 5 1/4" CDC 94205-51 40mb HH MFM UF RFE tested £69.95(C)
 - 5 1/4" HP 9754B 850 Mb SCSI RFE tested £89.00(C)
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00(C)
 - 8" FUJITSU M2322K 160Mb SMD UF RFE tested £195.00(E)
- Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!



TV SOUND & VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tunable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level HI FI audio output are provided as standard.

- TELEBOX ST for composite video input type monitors £36.95
 - TELEBOX STL as ST but fitted with integral speaker £39.50
 - TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
- For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Teleboxes is (B)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock. Call for info / list.

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -
At this price - Don't miss it!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched facias, test switching and LOW RADIATION: MPR specification. Fully guaranteed, supplied in EXCELLENT used condition.

Tilt & Swivel Base £475
VGA cable for IBM PC included.
External cables for other types of computers CALL

As New - Used on film set for 1 week only!
15" 0.28 SVGA 1024 x 768 res. colour monitors.
Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors.
Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed.
Dimensions: W14" x H12 1/2" x 15 1/2" **Only £95 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burn). In attractive square black plastic case measuring W10" x H10" x 13 1/2". 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 15 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

SPECIAL INTEREST ITEMS

- MITS. A. FA3415ETKL 14" Industrial spec SVGA monitors £245
- 2KW to 400 kW - 400 Hz 3 phase power sources - ex stock EPOA
- IBM 8230 Type 1, Token ring base unit driver £950
- IBM 53F5501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 2223-203-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz. IEEE £550
- Trend DSA 274 Data Analyser with GTD03(2M) 64 Kio EPOA
- Microtron 6310 Programmable 2 to 22 GHz sweep generator £6590
- HP1850B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector EPOA
- HP APOLLO RX700 system units £950
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP3081A Industrial workstation 40 Barcode swipe reader £175
- HP6264 Rack mount variable 0-20V G 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set EPOA
- HP7580A A1 B pen HPGL high speed drum plotter £1850
- EG+G Brookdeal 95035C Precision lock in amp £650
- View Eng. Mod 1200 computerised inspection system EPOA
- Ling Dynamics 2Kw programmable vibration test system EPOA
- Computer controlled 1055 x 560 mm X Y table & controller EPOA
- Kelthley 590 CV capacitor / voltage analyser EPOA
- Racal ICR40 dual 40 channel voice recorder system £3750
- Fiskers 45KV4 3 pin On Line UPS - New batch Dec 1995 EPOA
- ICI R5030UV34 Cleanline ultrasonic cleaning system EPOA
- Mann Tally MT645 High speed line printer £2200
- Intel SBC 486/133SE Multibus 486 system, 8Mb Ram EPOA
- Zeta 3220-05 AD 4 pin HPGL fast drum plotters £1150
- Nikon HFX-11 (Echigrot) exposure control unit EPOA
- Motorola VME Bus Boards & Components List. SAE / GALL EPOA
- Tri-o 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM brand printer EPOA
- Fujitsu M3041D 600 LPM printer with network interface EPOA
- Perkin Elmer 2998 Infrared spectrophotometer EPOA
- VG Electronics 1035 TELETEXT Decoding Margin Meter EPOA
- Andrews LARGE 3.1 m Satellite Dish - mount (For Voyager) £950
- Seikon SD 150H 16 channel digital Hybrid chart recorder EPOA
- TAYLOR HOBSON Tallysur amplifier / recorder £750
- System Video 1152 PAL waveform monitor EPOA
- Test Lab - 2 mbr square quitted acoustic test cabinets £300
- Kenwood 9601 PAL Vectorscope - NEW £650

Please call for further details on the above items

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels £335.00 (G)
OPT Rack 2 Rack, Less side panels £225.00 (G)

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides a IEC 3 pin Euro sockets and a 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm: 1625H x 635D x 603 W. (64" H x 25" D x 23 1/2" W)
Sold at LESS than a third of makers price !!



A superb buy at only £195.00 (G)

Over 1000 racks - 19" 22" & 24" wide
3 to 44 U high. Available from stock !!
Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232C or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc. Imagine using your finger with 'Windows', instead of a mouse !! (A driver is needed available !!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only **£145.00 (B)**
Full MICROTUCH software support pack and manuals for IBM compatible PC's £29.95 RFE - Tested

LOW COST RAM & CPUs

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95(A1)
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.
Order as: XT RAM 525K. £34.95 or 512k £39.95 (A1)

SIMM SPECIALS

- 1 MB x 9 SIMM 9 chip 120ns Only £16.50 (A1)
 - 1 MB x 9 SIMM 3 chip 80 ns £19.50 or 70ns £22.95 (A1)
 - 1 MB x 9 SIMM 9 chip 80 ns £21.50 or 70ns £23.75 (A1)
 - 4 MB 70 ns 72 pin SIMM - with parity - Only £95.00 (A1)
 - INTEL 486-DX33 CPU £55.00 INTEL 486-DX66 CPU £69.00 (A1)
- FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR LIST

FANS & BLOWERS

- EPSON DD-412 40x40x20 mm 12v DC £7.95 10 / £65
 - PAPST TYPE 612 60x60x25 mm 12v DC £8.95 10 / £75
 - MITSUBISHI MMF-06B120L 60x60x25 mm 12v DC £4.95 10 / £42
 - MITSUBISHI MMF-08C120M 80x60x25 mm 12v DC £5.25 10 / £49
 - MITSUBISHI MMF-09B120H 92x92x25 mm 12v DC £5.50 10 / £53
 - PANCAKE 12-3.5 92x92x18 mm 12v DC £7.95 10 / £69
 - EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm speed 110 or 240 V £6.95, 80 x 60 x 38 mm - speed 110 or 240 V £5.95
 - IMHOF B26 1900 rack 3U x 18" Blower 110/240V NEW £79.95
- Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

Issue 13 of Display News now available - send large SAE - PACKED with bargains!



ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET, 32 Bglgn Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath & Selshurst Park SR Rail Stations

NEW DISTEL ©
The Original
FREE On line Database
Info on 20,000 + stock items!
RETURNING SOON!

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland, UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.50, (B)=£5.00, (C)=£6.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996. E & O E, 065

ETI Remote Data Logger

Richard Grodzik has designed a PIC-driven low-voltage portable data logger that uploads to your PC.

This portable data logger has many features, including:

- 3 volt (lithium 'button' cell) operation
- 1 second or 1 minute sample intervals
- Samples stored in eeprom non-volatile memory
- Uploads at home-base to PC via 300 baud serial link
- Continuous logging mode operation when docked with a PC, enabling unlimited sampling period
- Protocol converter for importing into Lotus/Excel spreadsheets
- 8 bit +/- 0.5 bit conversion

The 5 volt Vcc power supply has been the standard for most microprocessor ics, peripherals and logic chips for many years, however, recent years have seen the introduction of Intel processors and memory operating on 3.3 volts. The advantages are obvious for portable computers - lower power expenditure with an associated reduction in heat produce a more reliable machine with a consequent extension of the primary or secondary battery life. If we take this one step further and reduce the clock frequency to a low level - kHz as opposed to MHz - power consumption by the ics is reduced to a very low level.

This is the principle of operation adopted by Microchip's low power PIC - the PIC16C54LP. Operating down to 2 volts, and with a 32.768 kHz clock, the current consumption barely reaches 10 microamps. Try measuring that with your multimeter!

Three parts, low power

The remote data logger consists of three parts.

The first section is the low power PIC with serial RS232 output, two input switches to control operations, an LED indicator and a simple jumper (J1) to select between second and minute sample times. No electrolytic capacitors are to be seen, since these capacitors have a leakage current and the object of the design was to keep current consumption down to the minimum. The power-on reset circuitry connected to the MCLR line consists of a high value resistor/diode network which provides the necessary logic low reset on switch on and consumes little current. The LED is a low current type, and with a 2k series resistor just allows a visual indication when a sample has been taken. Similarly high value (22k) pull-up

resistors for the two input switches and the jumper link (further reduce current consumption).

The second section is a serial A to D converter - the TLC5491P - with 8 bit resolution and a low power consumption of 6 milliwatts, operating on a wide supply range of between 3 and 6 volts. A reference voltage of 2.5 volts is provided by a REF25Z voltage reference device and with a 2:1 100K resistor divider network allows a 0 to 5 volt analogue input voltage range, even though the Vcc supply to the ic is only 3 volts.

The third section is a serial non-volatile eeprom 255 byte memory type 93LC56, which stores the logged data until it is retrieved by uploading via the PIC's serial link to the PC. Again, this is a low voltage device operating at voltages down to 2 volts and with a current consumption of mere microamps.

How it works

As with any embedded processor project the chip count is minimal - here only three ics are used, but the drastically reduced hardware count is at the expense of considerable expenditure in time and effort in constructing the firmware for the PIC. Let us first consider programming the ADC: for data logging, a sample is taken at a precise interval of time, in this case either every minute or every second. The conversion cycle for the TLC5491P is initiated with the 8th I/O clock pulse, so in order for a 'strobed' operation where conversion is necessary at a specific point in time, a 'dummy' conversion takes place (procedure 'RECEIVE') whereby 8 clock pulses are used to bring the hold function (of the analogue voltage) to the point in time where a conversion is required. Subsequent 8 clock input pulses (procedure 'CONV') will then clock out the conversions result starting with the MSB of the 8 bit conversion. If the dummy pulses were removed, the resulting conversion would provide data from the previous conversion,


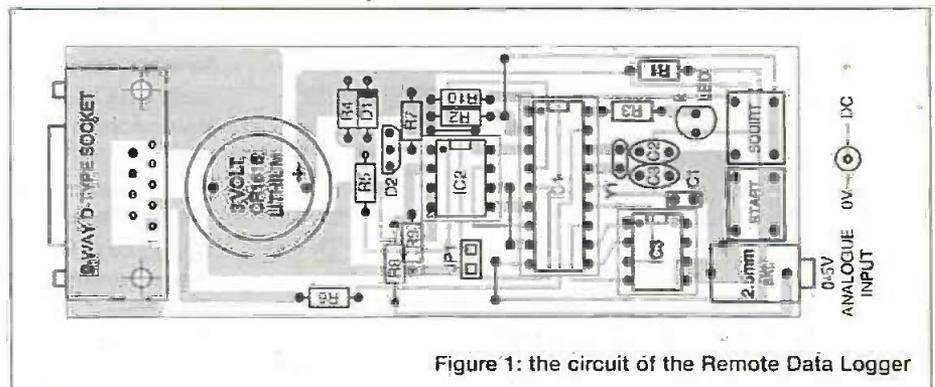


Figure 1: the circuit of the Remote Data Logger

Figure 2: the component layout

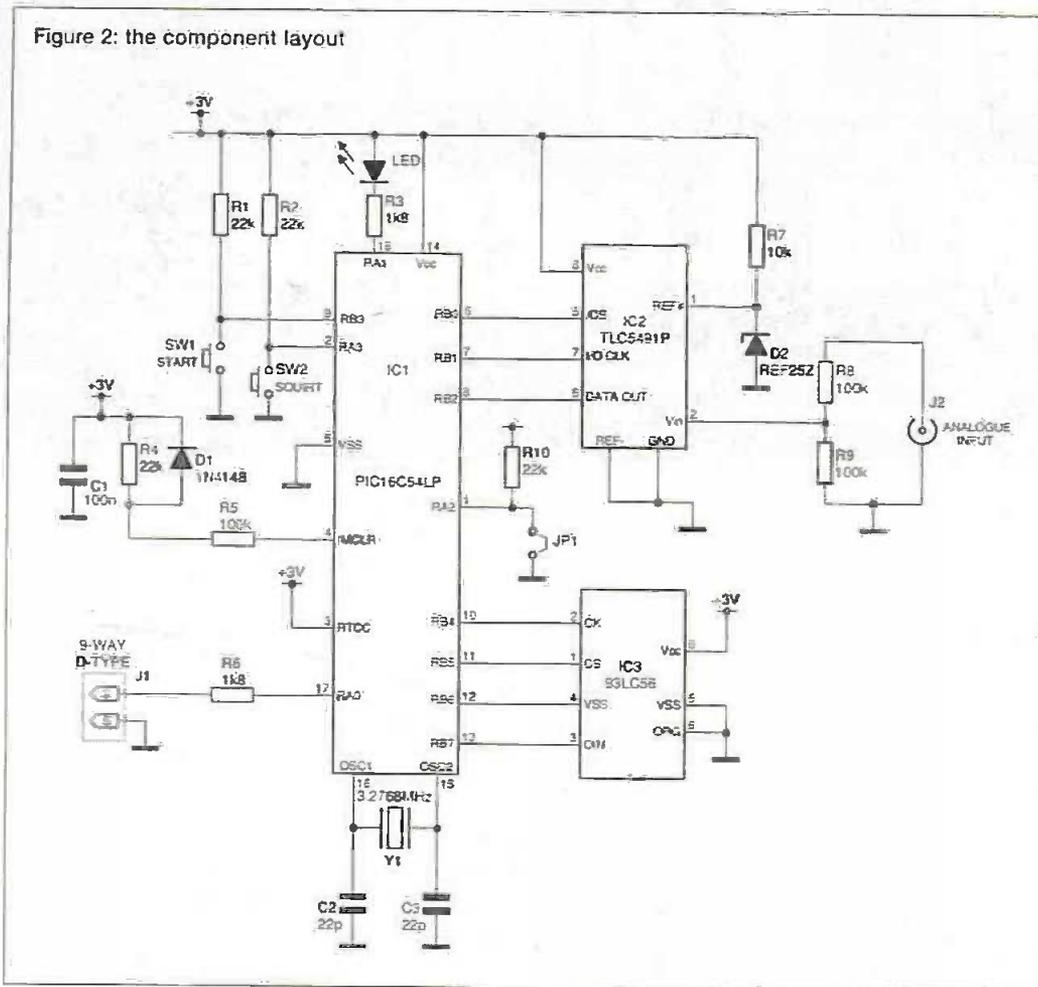

Instruction will restore the original address, to be decremented by 1 for the next write operation.

Eight data bits are then clocked into the Din line from the BUFFER register, starting with the MSB (bit 7) of the data. A 10 millisecond delay routine (DELAYEE) then allows the self timed automatic erase and write cycle by the eeprom.

When 255 conversions have taken place, the logged data is stored safely in the eeprom whose contents will be preserved (for approximately 40 years) even if the battery supply is removed. By connecting the logger to the serial port (COM1) of a PC and pressing the 'SQUIRT' switch, procedure 'FLUSH' is executed:

This consists of three sub-routines: 'READ' 'INVERT' and 'TRANSMIT'. Again, an instruction must be sent to the eeprom in order for the stored data to be read. The format is as follows:

that is, a second or minute earlier in time. As each bit is clocked out the serial data is presented to port line RB2 and shifted left-wise into buffer register 0AH.

The next part of the operation is to write this 8 bit conversion result to the eeprom. However configuring the eeprom and writing or reading data is a complex operation since the 93CLC56 is a programmable memory device. I will therefore try to explain in stages the operation of the eeprom here.

Before any writing or reading of the eeprom is possible the 'EWEN' erase/write enable and disable instruction must be sent serially to the eeprom via the Din line. This instruction has the following format:

Start bit	Opcode	Address
1	00	1XXXXXXX

Twelve clock cycle are therefore needed to clock in this information - (procedure 'EWEN').

To write data into the eeprom, the 8 bit data held in the BUFFER register is shifted out to the Din line, using register COUNTER to count the 8 data bits. The instruction to write data has the following format:

Start bit	Opcode	Address	Data
1	01	X A7 A6 A5 A4 A3 A2 A1 A0	D7-D0

Since the address (contained in register BHIGH) is clocked in serially to the eeprom Din line using the RLF BHIGH instruction, once eight address bits have been clocked in, a further RLF

Start bit	Opcode	Address	Data
1	10	X A7 A6 A5 A4 A3 A2 A1 A0	D7-D0

Procedure 'READ' shifts in the start bit, Opcode and 8 bit address into the Din pin of the eeprom. A further 8 clock pulses are then applied to the CK clock input of the eeprom to shift out the 8 data bits on the Dout line to the data register BUFFER. Procedure 'INVERT' then logically inverts the data to satisfy RS232 logic protocol. Procedure 'Transmit' shifts each data byte to the RA1 pin of the PIC for serial transmission. Note that the bits are now shifted out using the 'RRF' (shift right) instruction since the previous writing and reading of data from the eeprom had caused a reversal of bits, that is, bit 0 occupying bit 7 position and so on. Transmission of serial data at 300 baud required a bit 'cell' period of 3333.3 microseconds. Since each instruction takes 122.07 microseconds to be executed by the PIC using a 32.768 kHz crystal, the software overhead time in shifting and counting the transmitted bits is quite considerable and has to be accounted for when computing the 3333.3 microseconds delay between each data bit. It was therefore decided to use simple NOP instructions to add to the software overhead time to define an accurate 'cell' delay period.

In association with writing and reading the serial data to and from the eeprom, both the CS (Chip select) and CK (Clock) signals have to occur at precise times and in the correct order. A close examination of the firmware will show how this is done.

Construction

A 90 degree 9 way D type PCB socket allows for the unit to be

connected directly to the serial port of the PC. If necessary, an extension lead can be fabricated as follows:

9 way D type plug (to Logger) 9 way D type socket (to PC)

pin 2 pin 2
pin 5 pin 5

A battery holder is used to retain the lithium cell. This can be obtained from Electromail, Order No. 430-669. The 93LC56B IC is also available from the same source, Order No. 831-769. The other components are available from most component suppliers. Note that the press to make miniature switches have commoned connections and the 'squirt' switch must be oriented correctly to provide a 0 volt line continuity on the PCB.

Testing the unit is quite simple since the PIC software, if executing, will light the LED for an instant when the battery is inserted into its holder. A voltage check on pin 1 of the TLC549P ADC IC should be exactly 2.5 volts.

Data presentation and graphics software

The data 'squirted' from the data logger is in a binary format and has to be scaled and converted into an ASCII format in order to produce a meaningful representation of the captured data. Pascal source program '3DISC' shown below converts the binary data, scales it and writes each sample, together with a sample number in ASCII to disk to produce a file which can then be printed out or presented as a graphical XY plot using either Lotus or Excel spreadsheets. Since the ADC produces a 0 to 255 bit output for an input analogue voltage range of 0 to 5 volts a scaling factor of 51 will give a true indication of the actual voltage. An executable file, together with a real time data logging software package (VGA3) is available free of charge from the author with each pre-programmed PIC.

Continuous mode

A facility is available in the firmware so that if the data logger is docked with the PC ie connected to the serial port, continuous logging of data takes place at 1 second or 1 minute intervals. This together with PC driver 'VGA3' produces a real time graph of logged data.

```
PROGRAM 3DISC(INPUT,OUTPUT);
($f+)
($I-)

USES dos, crt;

VAR
sample:REAL;
r:real;
RO:STRING[5];
WO:STRING[20];
s:string[20];
TXT:TEXT;
BUF:ARRAY[1..5000]OF REAL;
BUFSAMPLE:ARRAY[6000..10000]OF REAL;

A:REAL;

X,Y:INTEGER;
LABEL
FINI;

PROCEDURE RECORDNAME;

VAR
NUM:INTEGER;

BEGIN
CLRSCR;
NUM:=0;

REPEAT
```

```
WRITE('ENTER FILENAME: ');
READLN(WO);
NUM:=LENGTH(WO);
CLRSCR;
UNTIL NUM>0;

ASSIGN (TXT,WO);
REWRITE(TXT);
END;

PROCEDURE LETTERS;
VAR
CODE:INTEGER;

BEGIN
repeat
WRITE('SCALING FACTOR ? ');
READLN(r0);
VAL(r0,R.CODE);
CLRSCR;
UNTIL CODE=0;
if r=0 then
r:=1;
END;

PROCEDURE WRITETEXT;

BEGIN
CLRSCR;
BUF[X]:=A;
X:=X+1;

BUFSAMPLE[Y]:=SAMPLE;
Y:=Y+1;
WRITE('Receiving
Data. . . . .',SAMPLE:2:0);

END;

PROCEDURE COM;
BEGIN
INLINE($B0);
INLINE($43);
INLINE($B4);
INLINE($00);
INLINE($EA);
INLINE($00); (* com1 *)
INLINE($00);
INLINE($CD);
INLINE($14);
END;

PROCEDURE DATA;

VAR
POLL:WORD;
hex:WORD;
realdata:real;
CODE:INTEGER;

BEGIN

REPEAT
POLL:=PORT[$3FD]; (* com1 *)
POLL:=POLL AND 1;
UNTIL POLL=1;
HEX:=PORT[$3F8]; (* com1 *)
A:=HEX/R;
sample:=sample+1;
END;

BEGIN
X:=1;
Y:=6000;
COM;
SAMPLE:=0;
RECORDNAME;
LETTERS;
WRITELN('Waiting for Data. . . . .');

REPEAT
BEGIN
DATA;
WRITETEXT;
IF SAMPLE>254 THEN GOTO FINI;
END;
UNTIL KEYPRESSED;
READLN;

FINI;
X:=1;
Y:=6000;
```

Operating instructions

1. Insert battery. Note this must be Lithium type CR1616, 3 volts.
2. Insert jumper J1.
3. Press the start switch.
4. Data will now be logged at 1 second intervals. Every time a sample is taken, the LED will light briefly. Once 255 samples have been taken, the LED will remain off. Connect in

the data logger to the COM1 serial port of the PC. Run either 3DISC.exe or VGA3.exe (VGA3_2.exe for COM2 serial port.)

5. Press the squirt switch. 255 bytes of data will now be transferred from the logger to the PC. For a 1 sample/minute interval to be selected, simply remove the jumper.

To invoke continuous logging, insert the battery while keeping the start button pressed.

PARTS LIST

Resistors

R1,R2,R4,R10	22k
R3,R6	1k8
R5,R8,R9	100k
R7	10k

Capacitors

C1	100n
C2,C3	22p

Semiconductors

IC1	PIC16C54LP
IC2	TLC5491P
IC3	93LC5 (eg Electromail O/N 831-769)
D1	1N4148

D2	REF25Z
LED1	Low current LED (eg Electromail 590-547)

Miscellaneous

Y1	32.768 kHz crystal
J1	90 degree 9-way Dtype socket
J2	2.5mm PCB-mounting jack socket
JP1	2.5mm jumper
3V CR1616 lithium button cell battery; battery holder (eg Electromail O/N 430-669); 2 x press-to-make miniature switches; 2.5mm socket; jumper leads and wire links	

PLEASE CHECK that your jack socket and miniature switch pin-outs match the PCB layout - if you use a different layout, you need to alter the position of the pin holes on your PCB foil print to fit.

```

SAMPLE:=0;
REPEAT

WRITE (TXT, BUF[X]:9.2);
X:=X+1;
write(txt, ' ');

WRITELN (TXT, BUFSAMPLE[Y]:2.0);
SAMPLE:=SAMPLE+1;
Y:=Y+1;

UNTIL SAMPLE=255;

delay (1000);

CLOSE (TXT);
CLRSCR;
WRITE('          Completed capture.....');

END.

PIC FIRMWARE LISTING: REMOTE ASM

LIST          p=16C54 ; PIC16C54 is the target
process06

32.768 KHZ          ; SC = 122.0703 FOR XTAL

EE EQU . 26        ;10 Millisecond EEPROM WRITE
TIME

TXD EQU 0          ;RA0 TRANSMIT SERIAL RS232
GREENLED EQU 1     ;RA1 LOW = ON
SELECT EQU 2       ;RA2 LOW = 1 SEC, HIGH = 1
MIN
SQUIRT EQU 3       ;RA3 SWITCH, LOW = PURGE
EEPROM

CS_ADC EQU 0        ;RB0 CHIP SELECT ADC
CK_ADC EQU 1        ;RB1 I/O CLOCK FOR ADC
DATA_ADC EQU 2      ;RB2 8 BIT SERIAL ADC DATA
START_1 EQU 3       ;RB3 START LOGGING SWITCH
CK_EE EQU 4         ;RB4 I/O CLOCK FOR EEPROM
CS_EE EQU 5         ;RB5 CHIP SELECT EEPROM
DOUT EQU 6         ;RB6 SERIAL DATA O/P FOR
EEPROM
DIN EQU 7          ;RB7 SERIAL DATA IN I/P FOR
EEPROM
    
```

```

RTCC EQU 1         ;REAL TIME TIMER/COUNTER
PC EQU 2           ;PROGRAM COUNTER
STATUS EQU 3       ;STATUS REGISTER
PORT_A EQU 5       ;PORT A
PORT_B EQU 6       ;PORT B

THIRTYTWO EQU 0FH ;MODULUS 31 COUNTER

DLYCNT EQU 8       ;TIMING LOOP COUNTER
COUNT EQU 9       ;8 BIT SHIFT REGISTER
BUFFER EQU 0AH     ;ADC CONVERSION BUFFER
COUNT EQU 0BH     ;TIMING COUNTER
INVERT EQU 0DH     ;TTL TO RS232 LEVEL
HIGH EQU 011H     ;255 SAMPLE COUNTER
SIXTY EQU 012H    ;1 MINUTE COUNTER
FLAG EQU 013H     ;
REG EQU 014H      ;RTCC VALUE
ORG 0
    
```

```

START
NOP
NOP

MOVW 0CH ;RA0SERIAL OUTPUT
;RA1 LED
;RA2 JUMPER
;RA3 SQUIRT SWITCH

TRIS PORT_A
BCF PORT_A, TXD ;RS232 START BIT LOW
BSF PORT_A, GREENLED ;LED OFF

MOVLW 040H ;RB0 CHIP SELECT ADC
;RB1 I/O CLOCK ADC
;RB2 DATA OUT ADC
;RB3 START SWITCH
;RB4 CLOCK EEPROM
;RB5 CHIP SELECT EEPROM
;RB6 DATA OUT EEPROM
;RB7 DATA IN EEPROM

TRIS PORT_B

BSF PORT_B, CS_ADC ;DISABLE ADC
BCF PORT_B, CK_ADC ;START WITH CLOCK LOW
BCF PORT_B, CS_EE ;DISABLE EEPROM
BCF PORT_B, CK_EE ;START WITH CLOCK LOW
BCF PORT_B, DIN ;AND DATA LOW
    
```

```

CALL EVEN ;INITIALISE EEPROM
CYCLE
    
```

The Low Cost Controller That's Easy To Use

Features

The K-307 Module provides the features required for most embedded applications

- Analogue • 4 Channels in 1 Channel out
- Digital • 36 Digital in or out & Timers
- Serial • RS-232 or RS-485 plus I2C
- Display • LCD both text and graphics
- Keyboard • Upto 8 x 8 matrix keyboard
- Memory • > 2Mbytes available on board
- Low Power • Many modes to choose from

Development

The PC Starter Pack provides the quickest method to get your application up & running

- Operating System • Real Time Multi Tasking
- Languages • 'C', Modula-2 and Assembler
- Expansion • Easy to expand to a wide range of peripheral cards

Other Features


Real Time Calendar Clock, Battery Back Up, Watch Dog, Power Fail Detect, STE I/O Bus, 8051 interface, 68000 and PC Interface

Cambridge Microprocessor Systems Limited



Units 17 - 18 Zone 'D'
Chelmsford Road Ind Est
Great Dunmow Essex CM6 1XG
E-mail cms@dial.pipex.com

Phone 01 371 875 644

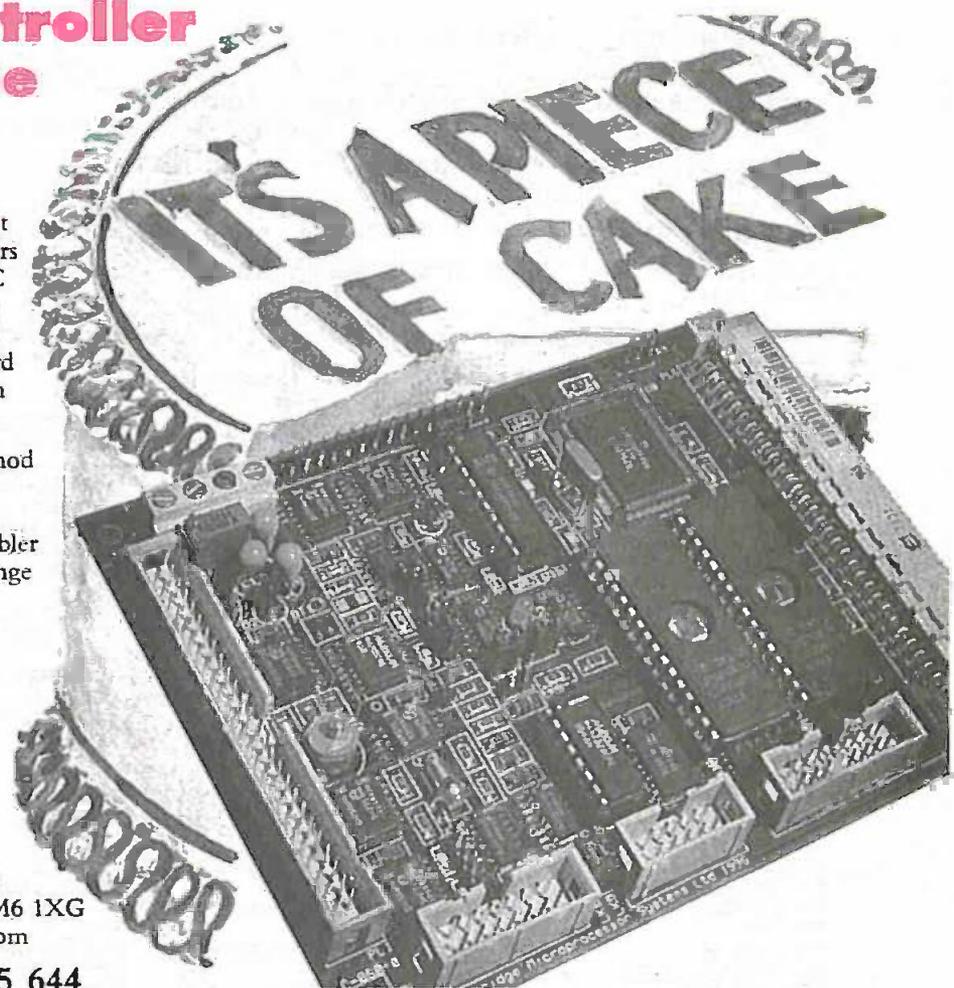

Comprehensive PIC solutions from FED

PICDESIM

PICDESIM is a fully integrated Windows PIC Simulator, to use with our Development Environment. It features: Single step, skip over, and run, Conditional breakpoints, watch variables, trace any number of variables, graphical interfaces. Up to 50 times faster than MPSIM. Wide range of stimuli including asynch serial data. Integrates with our PIC Programmer

£30.00, £25.00 if purchased with our PIC Programmer

PIC Programmer

Program 16C54/55/56/57/58, 16C62xx, 16C64, 16C71/73/74, 16C84. Uses serial link to a PC. Windows and DOS software provided. Includes PICDE, the Windows based PIC Development Environment with on-line help, project management, editing, assembler.

Kit £40.00, Ready Built £50.00

- PIC16C74JW Erasable 20MHz £24.00
- PIC 16C74-04 OTP 4MHz £8.00, 20MHz £11.00
- PIC 16C57XT/P OTP 4MHz £5.00
- PIC16C84-04P EEPROM erasable 4MHz £6.00
- 24LC65 8x8 serial EEPROM £5.00

PIC BASIC

Easy to learn BASIC in a Windows Development Environment. No need for assembler or a UV eraser to program PICs. Modules operate from a serial link to your PC. The 16C74 module has these features: 8k EEPROM, up to 2000 lines of BASIC, 27 lines of programmable I/O, 8 A/D inputs, Interrupt driven serial RS232 interface, Peripheral I2C bus interface, optional external ram.

- 16C57 Module Kit (8k, 4MHz) £30.00, Pre-built £36.00
- 16C74 Module Kit (8k, 4MHz) £35.00, Pre-built £42.00
- 16C74 Module Kit (8k, 20MHz) £40.00, Pre-built £46.00

PIC BASIC Compiler

New! A PIC BASIC compiler for the 16C74. It produces a hex code to program your 16C74 directly. Compatible with the EEPROM versions of PIC 16C74 BASIC modules.
Compiler £50.00

Serial Cable for Programmer or BASIC Modules £7.50



Forest Electronic Developments
10 Holmhurst Avenue, Christchurch,
Dorset, BH23 5PQ

Phone/fax: 01425 270191, Technical 01425 274068

Prices are inclusive, please add £3.00 for P&P and handling to each order. Cheques/POs payable to Forest Electronic Developments.



Visit our Web page at <http://www.ibmpcug.co.uk/~gmwarner/fed.htm>

```

MOVLW B'00000001' ;RTCC PRESCALE VALUE
OPTION

BTFS PORT_B, START_1 ;CONTINUOUS MODE
GOTO AUTO

BCF PORT_A, GREENLED ;TEST LED
CLR RTCC
CALL UPLOAD ;DELAY
BSF PORT_A, GREENLED ;LED OFF

MOVLW OFFH ;255 BYTE ADDRESS COUNTER
MOVWF BHIGH

POLL:
CLRWDI
BTFS PORT_A, SQUIRT ;IF SQUIRT SWITCH PRESSED
;SQUIRT DATA
GOTO STOP_FLUSH
BTFS PORT_B, START_1 ;WAIT FOR START SWITCH
GOTO POLL

RELEASE ;WAIT FOR START SWITCH TO
BE ;RELEASE
;INCLUDE DEBOUNCE TIME

CLR RTCC
DEBOUNCE CLRWDI
BTFS RTCC, 7
GOTO DEBOUNCE
BTFS PORT_B, START_1
GOTO RELEASE

;-----
;ADC CONVERSION AND WRITE TO EEPROM
;-----

CYCLE_ADC
CLR RTCC ;CLEAR TIMER
CLRWDI
BCF PORT_A, GREENLED ;GREEN LED ON
CALL RECEIVE ;PERFORM ADC CONVERSION
CLRWDI
CALL WRITE ;WRITE CONVERSION TO EEPROM
BCF PORT_B, CS_EE
CALL DELAYE ;10 MILLISECOND DELAY
;FOR SELF TIMED EEPROM WRITE
BSF PORT_A, GREENLED ;GREEN LED OFF

DECFSZ BHIGH, 1 ;NEXT EEPROM ADDRESS --1
GOTO CONT
GOTO POLL_1 ;255 SAMPLES TAKEN

CONT BTFS PORT_B, SELECT ;MINUTE SELECTED BY J1?
GOTO HIGHA ;1 MINUTE DELAY
CALL SECOND ;1 SECOND DELAY
GOTO CYCLE_ADC ;REPEAT FOR 255 SAMPLES

HIGHA CALL SECOND

MOVLW . 59 ;MINUTE COUNTER
MOVWF SIXTY
CALL MINUTE
GOTO CYCLE_ADC

POLL_1

BTFS PORT_A, SQUIRT
GOTO POLL_1

STOP_FLUSH
BCF PORT_A, GREENLED
CALL UPLOAD
BSF PORT_A, GREENLED
MOVLW OFFH
MOVWF BHIGH

FLUSH ;SQUIRT DATA AT 300 BAUD
;FROM RA0

CALL READ
MOVF BUFFER, 0
CALL CONVERT
CALL TRANSMIT

CALL UPLOAD

DECFSZ BHIGH, 1
GOTO FLUSH

GOTO CYCLE

RECEIVE ;ADC CONVERSION

```

```

MOVLW 8 ;8 DATA BITS
MOVWF COUNTR
CLRF BUFFER ;CLEAR BUFFER

BCF PORT_B, CS_ADC ;CS LOW

NEXT

BSF PORT_B, CK_ADC ;CLOCK HIGH
BCF PORT_B, CK_ADC
DECFSZ COUNTR, 1
GOTO NEXT

MOVLW 8 ;8 DATA BITS
MOVWF COUNTR
BSF PORT_B, CS_ADC ;CS HIGH

CONV
BSF PORT_B, CK_ADC ;CLOCK HIGH
BCF PORT_B, CS_ADC ;CS LOW

BCF STATUS, 0
RLF BUFFER
BTFS PORT_B, DATA_ADC;
BSF BUFFER, 0
BCF PORT_B, CK_ADC ;CLOCK LOW

DECFSZ COUNTR, 1
GOTO CONV

BSF PORT_B, CS_ADC ;CS HIGH STOP
RETLW 0

READ CALL SB ;START BIT LOGIC 1
CALL DI_1 ;OPCODE 10
CALL DI_0

CALL DI_0 ;ADDRESS A8 LOGIC X

MOVLW 8 ;8 BITS
MOVWF COUNTR

NEXT_TB
RLF BHIGH ;CLOCK IN 8 BIT ADDRESS
BTFS STATUS, 0
BSF PORT_B, DIN
BTFS STATUS, 0
BCF PORT_B, DIN

BSF PORT_B, CK_EE
BCF PORT_B, CK_EE

DECFSZ COUNTR
GOTO NEXT_TB

RLF BHIGH ;RESTORE ADDRESS
MOVLW 8 ;8 DATA BITS
MOVWF COUNTR
CLRF BUFFER ;CLEAR DATA BUFFER

CON ;CLOCK OUT 8 DATA BITS
BSF PORT_B, CK_EE ;INTO BUFFER REGISTER

BCF STATUS, 0
RLF BUFFER

BTFS PORT_B, DOUT
BSF BUFFER, 0
BCF PORT_B, CK_EE
DECFSZ COUNTR, 1
GOTO CON

BCF PORT_B, CS_EE
RETLW 0

WRITE CALL SB ;WRITE START BIT INTO EEPROM
CALL DI_0 ;OPCODE 01
CALL DI_1

CALL DI_0 ;A8 (X) BIT ADDRESS

MOVLW 8 ;8 DATA BITS
MOVWF COUNTR

NEXT_TA
CLRWDI
RLF BHIGH ;8 BIT ADDRESS
BTFS STATUS, 0 ;SHIFT ADDRESS SERIALY
BSF PORT_B, DIN ;INTO Din
BTFS STATUS, 0
BCF PORT_B, DIN

```


Is your PCB design package not quite as "professional" as you thought? Substantial trade-in discounts still available.

Board Capture

Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

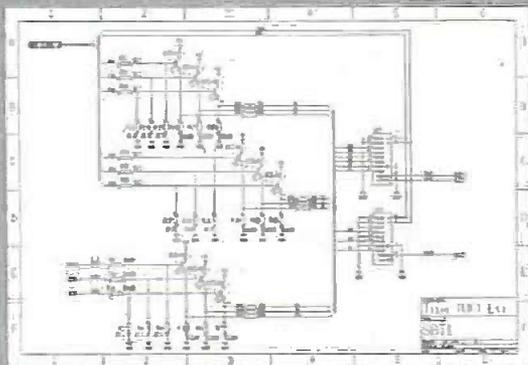

Board Maker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1
- Full netlist support- BoardCapture, OrCad, Schema, Tango, CadStar
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator- Database ASCII, BOM
- Thermal power plane support with full DRC

£395

Board Router


Gridless re-entrant autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

Output drivers - Included as standard

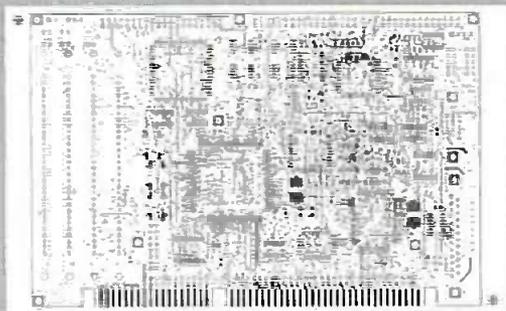- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)



For further information contact

Tsien (UK) Limited

Aylesby House


Wenny Road, Chatteris

Cambridge, PE16 6UT

Tel 01354 695959


Fax 01354 695957

E-mail Sales@tsien.demon.co.uk

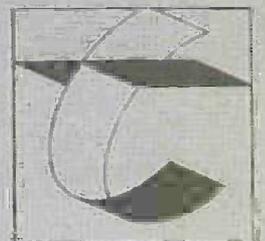

tsien



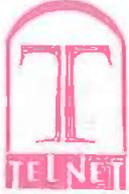

**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass In Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Cossor 3102 - 60MHz Dual Channel	£250
Gould OS 255 - 150MHz Dual Channel	£150
Gould OS 3351 - 40MHz Dual Channel	£220
Gould 5110 - 100MHz Intelligent oscilloscope	£850
Gould 1602 - 20 MHz D.S.O. with preset cursors	£1150
Hameg - 200/200-4200/5200-6 - 20 MHz Dual Channel	from £175
Hewlett Packard 1740A, 1741A, 1774A, 100MHz dual ch	from £350
Hewlett Packard 1707A, 1707B - 75MHz 2ch	from £275
Hewlett Packard 54200A - 60MHz - 2 Ch Digitizing	£1000
Hewlett Packard 54201A - 300MHz Digitizing	£1750
Hewlett Packard 54501A - 100MHz - Digitizing 4 channel	£1950
Hewlett Packard 54100D - 1GHz Digitizing	£350
Hewlett Packard 1620 - 4 channel - 100 MHz	£350
Hitachi V656F - 50 MHz Dual Channel	£350
Hitachi VC6265 - 100 MHz Digital Storage (AS NEW) GPIB	£2250
Intron 2020 - 20 MHz Digital Storage (NEW)	£750
Iwatsu SS 5702 - 20MHz Dual Channel	£175
Iwatsu SS 5121 - 100MHz Dual Channel	£425
Iwatsu SS 5710 - 60MHz Dual Channel	£375
Kikusui COS 5100 - 100MHz, 5 Channel, 12 Trace	£475
Kikusui D55 6522 - 20MHz Digital Storage	£475
Kikusui D55 6522 - 100MHz Digital Storage	£425
Meguro - M50 - 1270A - 20 MHz Digital Storage (REV)	£750
Hicolet 3091 - LF D.S.O.	£1100
Panasonic VP741A - 100 MHz D.S.O. with Digital readout + waveform analysis - TV Signal Analysis Function - G.P.I.B.	£2500
Philips 3211, 3217, 3240, 3243, 3244, 3261, 2262 (2ch + 4ch)	from £125
Philips 3219 - 50MHz with analogue storage	£400
Philips PM 3295A - 400MHz Dual Channel	£1950
Philips PM 3295 - 350MHz Dual Channel	£1500
Philips PM 3315 - 60MHz - D.S.O.	£750
Philips 3263 - 100MHz Dual Channel with Microprocessor Controlled Timing	£400
Philips 3540 - Logic Scope (25MHz Scope & Logic Analyser)	£350
Tektronix 434 - 25MHz - 2 Channel, Analogue Storage	£477
Tektronix 454 - 150MHz - 2 Channel	£750
Tektronix 466 - 100MHz - D.S.O.	£425
Tektronix 2213 - 60MHz Dual Channel	£450
Tektronix 2218 60MHz dual trace	£977
Tektronix 2235 - 100MHz Dual Channel with Counter/Timer	£750
Tektronix 2235 Dual trace 100MHz (portable)	£750
Tektronix 2445 150 MHz - 4 Channel	£1250
Tektronix 2445A - 150MHz - 4 Channel	£165
Tektronix 2225 - 50MHz dual ch	£450
Tektronix 455 - 50MHz Dual Channel	£350
Tektronix 464/466 - 100MHz An storage	from £350
Tektronix 465/465B - 100MHz dual ch	from £350
Tektronix 475475A - 200MHz/2250MHz Dual Channel	from £475
Tektronix 7713, 7603, 7613, 7623, 7633, 100MHz 4 ch	from £650
Tektronix 7704 - 250MHz 4 ch	from £650
Tektronix 7904 - 500MHz	from £850
Tektronix 7534 500MHz with storage	from £1000
Tequipment D83 - 50MHz Dual Channel	£200
Tequipment DM63 - 20MHz - 4 Channel	£150

Other scopes available too

SPECIAL OFFER

HITACHI V212 - 20 MHz DUAL TRACE	£160
HITACHI V222 - 20 MHz DUAL TRACE + ALTERNATE MAGNIFY	£200

SPECTRUM ANALYSERS

Advantest 4133A - 100kHz - 20 GHz	£6995
Eaton/Altech 757 - 10kHz - 22 GHz	£2750
Hewlett Packard 3580A - 5Hz-50kHz	£995
Hewlett Packard 3705B - Constellation Analyser with 15709A High Impedance Interface (As New).....	£3750
Hewlett Packard 182T with 6559A (10MHz - 21GHz)	£2500
HP 3582A - 25kHz Analyser, dual channel	£1000
Hewlett Packard 35601A - Spectrum Analyser Interface	£1600
Hewlett Packard 141T + 6552B + 6555A (10MHz - 18GHz)	£4000
Hewlett Packard 6565A - Network Analyser (500kHz - 1.3GHz)	£7500
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser.....	£4250
Hewlett Packard 8550A 15 10kHz-1.5 GHz	£10,000
Hewlett Packard 8552A - 50kHz - 22GHz Portable	£995
Marconi 2370 - 110MHz	£1995
Marconi 2371 - 30kHz - 200MHz	£1995
Meguro MSA 4501 - 1-300 GHz (AS NEW)	£3000
Meguro MSA 4512 - 1-11 GHz (AS NEW)	£3000
Polrad 641-1 - 10MHz - 18GHz	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz	£2500
Tektronix 2710 9 KHz - 1.8 GHz	£4250
Tektronix 7L18 with 7603 mainframe (1.5-60GHz with external mixers)	£2000

MISCELLANEOUS

AVO RM215 - L2 - AC/DC Breakdown, Leakage + Ionisation Tester	£400
ARRISU ME 4620 - DF 3 Transmission Analyser	£3000
Anritsu MG442A Pulse Pattern Generator	£1500
California 751TC - AC variable Power Source	£1200
Datolab DL 1050 Programmable Transient Recorder.....	£3500
Dyanpert TP20 Interface - Tape peel Tester - in radioactive condition	£1950
E.I.P. 549A - Frequency Counter (26.5 GHz)	£2995
EIP 331 - Frequency counter 180Hz	£700
Farnell AP70-30 Power Supply (0-70v/30A) Auto Ranging	£750
Farnell SSG-520 Signal Generator (520 MHz)	£400
Farnell TSV 70 MHz Power Supply (70V-5A or 35V-10A)	£200
Fluke 5100A - Calibrator	£3500
Fluke 5101B - Calibrator with Tape Deck	£5000
Fluke 5100B - Calibrator	£4500
Heiden 1107 - 30V-10A Programmable Power Supply (IEEE)	£650
Hewlett Packard 3437A System voltmeter	£350
Hewlett Packard 3456A Digital voltmeter	£850
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser	£3500
Hewlett Packard 3776A - PCM Terminal Test Set	EPOA
Hewlett Packard 3325A - 21MHz Synthesised Function Gen	£1500
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available)	£650
Hewlett Packard 334A - Distortion Analyser	£300
Hewlett Packard 339A - Distortion Measuring Set	£1500
Hewlett Packard 3581A Wave Analyser	£750
Hewlett Packard 3455A 6 1/2 Digit M/Meter (Autocal)	£750
Hewlett Packard 3776A - PCM Terminal Test Set	E.P.O.A.
Hewlett Packard 3779 A/C - Primary Reference Analyser	from £1000
Hewlett Packard 3779A/3779C - Primary Mix Analyser	from £800
Hewlett Packard 4273A - LCR Meter (Auto-Frequency)	£4250
Hewlett Packard 4342A - 'O' Meter	£995

Hewlett Packard 4954A - Protocol Analyser	£2995
Hewlett Packard 432A - Protocol Analyser	£2750
Hewlett Packard 448A - Power Meter (with 476A Sensor)	£275
Hewlett Packard 435A or B Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 4948A - (TMS) Transmission Impairment M/Set	£2000
Hewlett Packard 4729B - Carrier Noise Test Set	£2000
Hewlett Packard 4261A - L.C.R. Meter (Digital)	£500
Hewlett Packard 4271B - L.C.R. Meter (Digital)	£900
Hewlett Packard 5420A Digital Signal Analyser	£350
Hewlett Packard 5335A - 200MHz High Performance Systems Counter	£500
Hewlett Packard 5342A - Frequency Counter 1B GHz	£1800
Hewlett Packard 5312A - Microwave Frequency Counter (18GHz)	£1500
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter	£250
Hewlett Packard 5183 - Waveform Recorder	£2250
Hewlett Packard 5238A Frequency Counter 100MHz	£250
Hewlett Packard 5370A - 100MHz Universal Timer/Counter	£450
Hewlett Packard 5355A Frequency Counter - 1GHz - (HP 1B) with OPTS 001/003/004/005	£995
Hewlett Packard 6034 - 60V-10A System Power Supply	£1500
Hewlett Packard 6623A Triple output system power supply	£1950
Hewlett Packard 6552A - System P.S.U. 20v-25a	£1950
Hewlett Packard 6253A Power Supply 20V-3A Twin	£200
Hewlett Packard 6161C D.C. current source	£150
Hewlett Packard 6255A Power Supply 40V - 1.5A Twin	£200
Hewlett Packard 6266B Power Supply 50V-5A	£220
Hewlett Packard 6271B Power Supply 50V-3A	£225
Hewlett Packard 6002A - Autorangeing P.S.U. 50V - 10A	£500
Hewlett Packard 6034A - 0-60V-10A System P.S.U.	£1500
Hewlett Packard 4735A - 6 Pen Plotter	£250
Hewlett Packard 7590A - 6 Pen Plotter A3/A4	£450

HEWLETT PACKARD 6261B Power Supply 20v-50A £450 Discount for Quantities

Hewlett Packard 8403A - Modulator	£500
Hewlett Packard 8660D - Synthesised Sig Gen 10 KHz-2.6 GHz	£4500
Hewlett Packard 8349B - Microwave Broadband Amplifier (as new) 2 - 20GHz	£4250
Hewlett Packard 8165A - 50 MHz Programmable Signal Source	£1650
Hewlett Packard 8329B - Sweep Oscillator Mainframe (various Plug-ins available) extra	£2650
Hewlett Packard 8255A - Synthesised Signal Gen (100kHz - 500MHz)	£1750
Hewlett Packard 8683A - Microwave Signal Gen (2.4 - 6.5GHz)	£2750
Hewlett Packard 8152A - Optical Average Power Meter	£1250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011)	£1100
Hewlett Packard 83554A - Wave Source Module 26.5 to 40 GHz	£3500
Hewlett Packard 8444A - Tracking Generator	£775
Hewlett Packard 8011A Pulse gen. 0.1Hz-20MHz	£500
Hewlett Packard 8620C Sweep oscillator mainframe	£400
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 8654A 5-4GHz to 12.5GHz Sig-Gen	£2750
Hewlett Packard 8011A Pulse gen. 0.1Hz-20MHz	£500
Hewlett Packard 8620C Sweep oscillator mainframe	from £250
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 8754A - Network Analyser 4 - 1300MHz	£2950
Hewlett Packard 853A with 8559A - (0.01 - 21GHz)	£4250
Hewlett Packard 8555A - (0.01 - 22GHz)	£3750
Hewlett Packard 8634A 5-4GHz to 12.5GHz Sig-Gen	£3500
Hewlett Packard 8903A - Audio Analyser (20Hz - 100kHz)	£2500
Hewlett Packard 8958A - Cellular Radio Interface	£4000
Hewlett Packard 8901A - Modulation Analyser	£3400
Hewlett Packard P352A Variable Attenuator	£250
Hewlett Packard 11729B - Carrier Noise Test Set	£2000
Krohn-Hite 2200 Lin/Log Sweep Generator	£995
Krohn-Hite 4024A Oscillator	£250
Krohn-Hite 5500 Phase Meter	£250
Marconi 2432A 500MHz digital freq. meter	£200
Marconi - 2019A - 80kHz - 10-40MHz - Synthesised Signal Generator	£1950
Marconi 2871 Data Commms Analyser	£2000
Marconi 6530 Automatic Amplitude Analyser	£1750
Marconi 6562 (E 5910 Head) - Microwave Power Meter	£500
Marconi 2018 - 50kHz - 500MHz Synthesised AM/FM Signal Generator	£500
Philips PM 5167 10MHz function gen	£400
Philips 5190 L.F. Synthesiser (G.P.I.B.)	£800
Philips 5390 Programmable R/F Signal Gen (1020 MHz)	£1250
Philips (5518-TX) - TV Pattern Generator	£1500
Prema 4000 - 6 1/2 Digit Multimeter (NEW)	£450
Racal Dana 9242D Programmable PSU 25V-2A	£900
Racal Dana 9246S Programmable PSU 25V-10A	£1600
Racal Dana 3100 4x 150kHz synthesiser	£750
Racal 1592 - 1.3GHz Frequency Counter	£800
Racal Dana 9081 Synth. sig. gen. 520MHz	£550
Racal Dana 5034 Synth. sig. gen. 104MHz	£450
Racal Dana 9303 True RMS R/F level meter	£850
Racal Dana 9303 R/F Level Meter & Head	£950
Racal Dana 9917 UHF frequency meter 580MHz	£175
Racal Dana 9302A R/F millivoltmeter (new version)	£175
Racal Dana 9082 Synthesised am/fm sig gen (520MHz)	£500
Racal 9085 Low Distortion Oscillator	EPOA
Racal 9301A - True RMS R/F MSVometer	£300
Racal 9521 - 3GHz Frequency Counter	£450
Rohde & Schwarz AMF 2 - TV Demodulator	£1250
Rohde & Schwarz LFM 2 - 60 MHz Group Delay Sweep Gen	£1650
Rohde & Schwarz UPSF 2 - Video Noise Meter	£1400
Rohde & Schwarz - Soud Radio Code Test Set	£900
Rohde & Schwarz SUT 2 Noise Generator	£300
Rohde & Schwarz UPGS - Phosphometer	£150
Schaffner HSG 203A Line Voltage Variation Simulator	£1250
Schaffner HSG 222A Interference Simulator	£850
Schaffner HSG 223 Interference Generator	£850
Schlumberger SJL 4040 Stablock - High accuracy 1GHz Radio Test Set	£4995
Schlumberger 4923 Radio Code Test Set	£1500
Schlumberger 4031 - 1GHz Radio Comms Test Set	£7000
Schlumberger 2720 1250 MHz Frequency Counter	£500
Stanford Research DS 340 - 15 MHz Synthesised Function (NEW) and arbitrary waveform generator	£1200
Syston Donner 8030 - Microwave Frequency Counter (26.5 GHz)	£2750
Tequipment CT71 Curve Tracer	£750
Tektronix TM505 - AFG 5101 Arbitrary Function Gen	£1750
Tektronix 1240 Logic Analyser	£750
Tektronix 651 HR Monitor	POA
Tektronix DAS9100 - Series Logic Analyser	£500
Tektronix - Plug-ins - many available such as SC500, SW503, GS502, PG508, FG504, FG503, TG501, TR503 & many more.	EPOA
Tektronix 577 Curve Tracer	£1150
Tektronix AM503 - TM501 + P6302 - Current Probe Amplifier	£395
Tektronix PG506 - T0501 + SG503 + TM503 - Oscilloscope Calibrator	£1595
Tektronix CG501 - Programmable Oscilloscope Calibrator	£3995
Tektronix AA501 & TM 506 M/F - Programmable Distortion Analyser	£2500
Tektronix 577 - Curve Tracer	£1150
Time 9811 Programmable Resistance	£600
Time 9814 Voltage Calibrator	£750
Toellner 7720 - Programmable 10 MHz Function Gen (AS NEW)	£700
Wavetek 172B Programmable Sig Source (0.0001Hz-134MHz)	E.P.O.A.
Wavetek 3010 - 1 - 1GHz Signal Generator	£1250
Wilson 560 Scaler Network Analyser	£1250
Willson 6520S - Programmable Sweep Generator (3.6 - 6.5GMZ)	£650


**MANY MORE ITEMS AVAILABLE -
SEND LARGE S.A.E. FOR LIST OF EQUIPMENT
ALL EQUIPMENT IS USED -
WITH 30 DAYS GUARANTEE.
PLEASE CHECK FOR AVAILABILITY BEFORE
ORDERING - CARRIAGE & VAT TO BE ADDED
TO ALL GOODS**

Electronics Principles 3.0

For Windows 3.1, '95 & NT.

If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.

Electronics Principles 3.0 now contains fifty-eight Windows and an extended range of nearly 300 fully interactive analogue and digital electronics topics. Currently used in hundreds of UK and overseas schools & colleges to support GCSE, A-level, BTEC, City & Guilds and university foundation courses. Also NVQ's and GNVQ's where students are required to have an understanding of electronics principles.

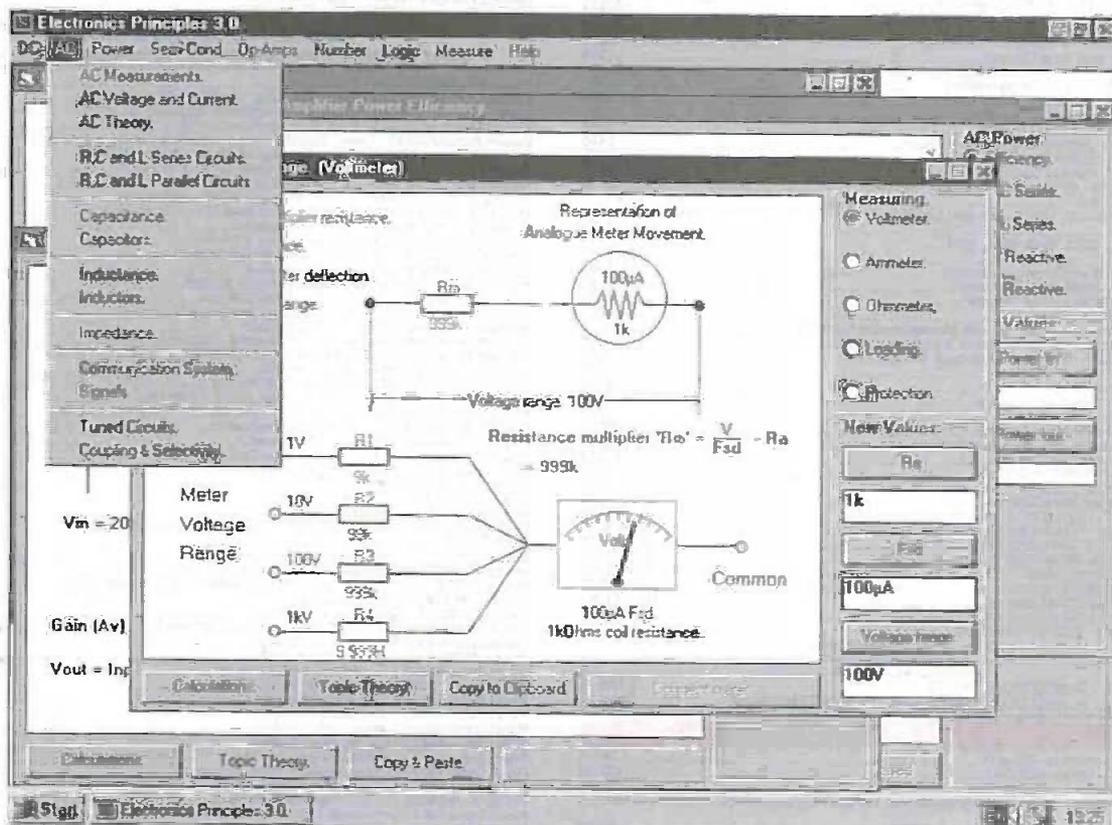

Other titles available.

Electronics Toolbox 3.0 £19.95*

Presents commonly used electronics formulae and routines in a way that makes calculations easy. Just select the topic, 'pop' in your values and find the result.

Mathematics Principles 3.0 £49.95*

Study or revise mathematics in what we believe is an interesting and enjoyable way. Nearly two hundred topics, including the GCSE syllabus with interactive, full colour graphics to enable 'learning through doing'.

Electronics Principles 4.0 £99.95*

Contains all of the extended version 3 and many more digital and analogue topics. Plus: Microprocessor & microcomputer operation, registers, arithmetic and logic unit, ROM, RAM etc. Addressing modes and full instruction set can be executed on the screen.

Inputs & outputs use electronics symbols.

Scientific notation avoided where possible to make numbers & calculations meaningful.

Experiment with standard textbook examples, even check your homework!

Hundreds of electronics formulae available for circuit investigation.

Multi-user site licence for schools & colleges.

Produce OHP slides & student handouts.

Complete Package just £49.95*

For more information, upgrades or software by return.

Telephone (01376) 514008.

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex, UK. CM8 2BJ. Tel/Fax: 01376 514008.

E-Mail sales@eptsoft.demon.co.uk Web pages <http://www.octacon.co.uk/ext/ept/software.htm>

* UK Please Add £2 per order for post & packing + VAT. Make cheques payable to EPT Educational Software.

Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date.

OVERSEAS ORDERS: Add £2.50 postage for countries in the EEC. Outside EEC add £3.50 for airmail postage.

Cupid's Arrow

Watch out - Cupid's about!

by Terry Balbirnie

The Valentine's Day party is in full swing. A smoochy CD is playing. Suddenly laughter is heard - couples are taking it in turns to try each other with Cupid's Arrow - the modern way. There are no little arrows sticking in your clothing and your hair, but if you have the potential for passion this little light-emitting dart will surely go straight to your heart - or are you secretly aiming at someone else? Are you merely a lemon-coloured lover or a red hot Romeo? Whatever you prove to be, the gales of laughter will show that you are making someone happy!

Get the message?

On the front panel of the "arrow" is a row of ten LEDs aimed in a dead-straight line. The lowest three are green, followed by two yellow, two orange, two red and, finally, a flashing red. When the button is pressed for an instant, the "reading" on the display slowly rises from the green end towards the red. After several seconds it stops. The obvious message which the colour conveys is the subject of the laughter.

It may be a disappointment to learn that operation of Cupid's Arrow is entirely random, but isn't that always the way it works out? It is impossible to predict where the display will stop - just like one of those little darts. A simpler circuit could


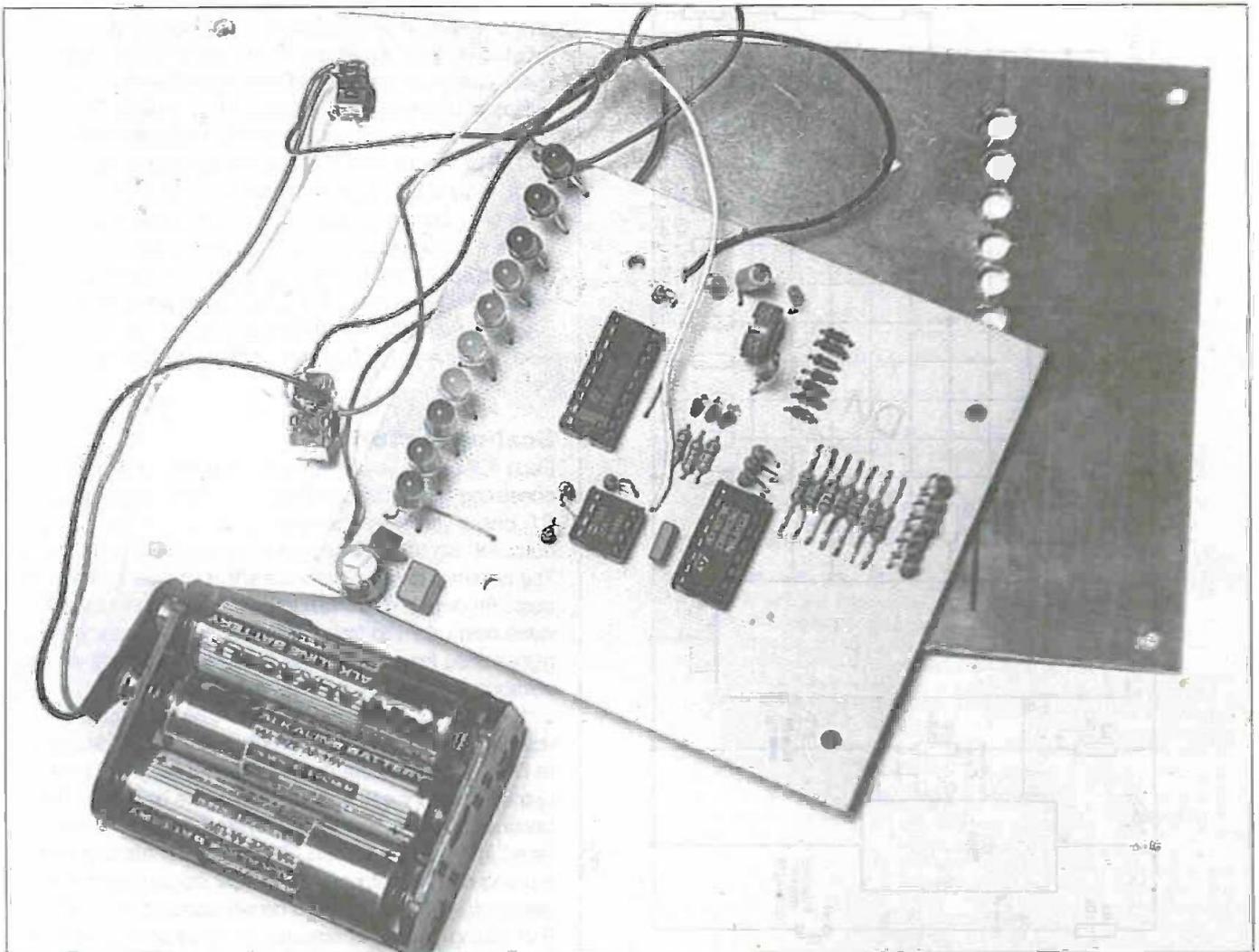


Figure 1: the circuit for Cupid's Arrow

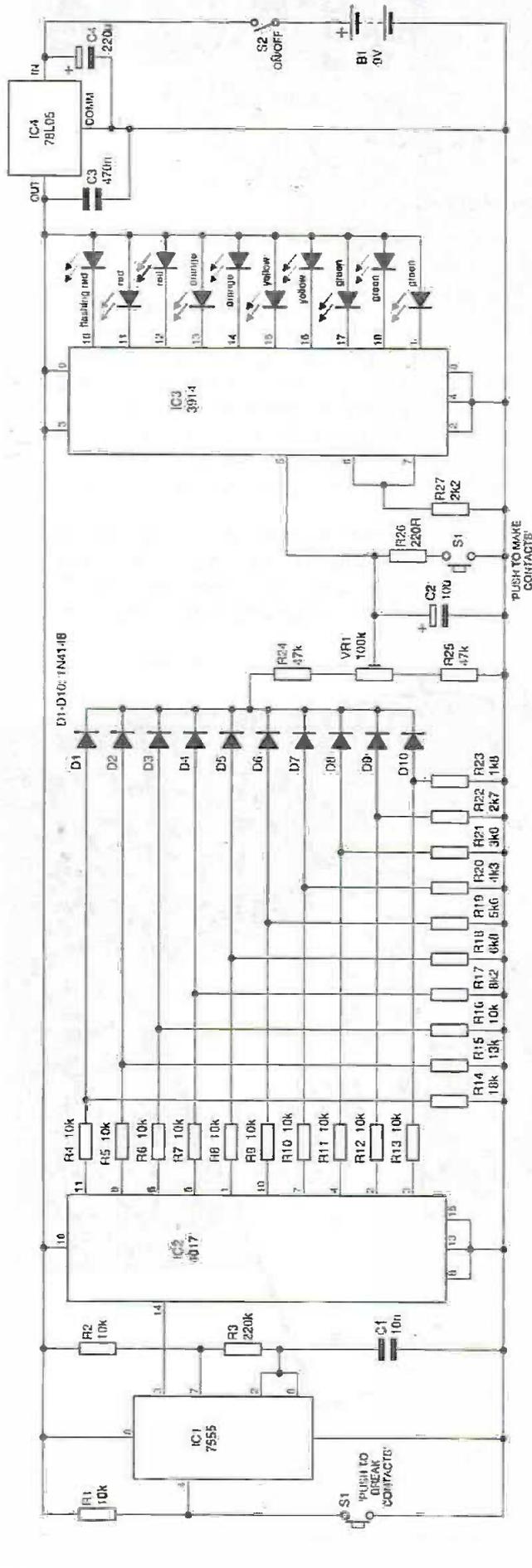

have been devised if an instant readout was considered satisfactory. However, the gradual response of this design completes the suspense.

Circuit description

The circuit diagram for Cupid's Arrow is shown in figure 1. Power is derived from the 9V battery, B1. However, this cannot be taken directly because correct operation relies on absolute voltage levels. Since the supply voltage falls as the battery ages, some stabilisation is needed. This is the purpose of voltage regulator, IC4 which works in conjunction with capacitors C3 and C4. The regulator will maintain a constant 5V output for the rest of the circuit until the battery voltage falls below 7V approximately. A battery pack consisting of six alkaline AA cells was used for the prototype power supply and this may be expected to give about 50 hours of service.

The first section of the circuit is an astable based on IC1 and associated components. Providing the reset input - pin 4 - is high (positive supply voltage), the astable provides a train of pulses at its output, pin 3. The frequency of operation (number of pulses per second) is determined by the values of resistors, R2 and R3 in conjunction with capacitor, C1. With those specified, this will be several hundred pulses per second, and since it is not critical, no adjustment is provided.

Push-to-go switch S1 is of the two-way type. In its released position, it maintains pin 4 in a low state through the push to break contacts and therefore no pulses are given. When S1 is pressed, pin 4 is made high via fixed resistor, R1 and pulses are produced until it is released. Even a momentary press will generate several tens of pulses due to the high frequency of operation. The exact number will therefore be completely unpredictable.

The pulses from the astable are applied to the clock input, pin 14, of decade counter, IC2. On the arrival of each one, the ten outputs, 0 to 9 (shown by the numbers in inverted commas), will go high in turn. On the next pulse, output 0 will go high again and the cycle will repeat until S1 is released. With a short press of S1, this cycle will therefore repeat several times. When the pulses stop, the one which happens to be high "freezes" (remains high).

Scaling factors

Each IC2 output is connected to a potential divider consisting of two fixed resistors. On each operation of S1, one of these will therefore be left active. For example, output 8 (pin 9) is connected to resistors R5 and R15. The potential dividers have the effect of scaling down the basic, 5V output by certain known factors - the lowest value being derived from output "0" and increasingly higher ones from successive outputs. Table 1 shows the voltages provided by each potential divider.

With one of the potential dividers active, a certain voltage will appear at the common cathode of diodes D1 to D10. These prevent the low state of the other nine IC2 outputs interfering with the action of the high one. This is because the diodes prevent current flowing back to "sink" into the low outputs. The voltage is applied to the top end of a further potential divider consisting of fixed resistors, R24 and R25 and preset potentiometer, RV1. If RV1 sliding contact is adjusted to mid-track position, the voltage will be divided by two. It is then applied to

capacitor, C2. This will charge slowly from zero taking several seconds to develop a steady voltage across it.

This increasing voltage is applied to the input, pin 5, of bargraph driver IC3. This responds to an analogue (smoothly changing) voltage and, according to its value, the ten outputs (labelled by the numbers in inverted commas) will go low respectively. The device is designed to respond in 0.125V increments with the corresponding output going low. When 0.125V is applied to pin 5, output "1" (pin 1), will go low. At 0.25V, output "2" (pin 18) will do so and so on. Thus, when 1.25V is reached, all ten outputs will be low. The device is configured in "bar" mode so that preceding outputs remain low as higher ones are reached.

Down the sink

The LEDs operate by allowing current to "sink" from the +5V line into the appropriate output. The first LEDs to light will therefore be the green "cold" ones followed by the "warmer" ones through yellow, orange, red and flashing red. Note that no conventional series resistors are needed for the LEDs since current limiting takes place within IC3.

Each operating voltage applied to IC3 pin 5 is calculated to exceed that required to switch on a particular LED but less than that needed to operate the next one in line. An example will help to make this clear. Suppose, when switch S1 is released, IC2 output 3 (pin 7) happens to be high. Note that this is actually the fourth output since the first one is output "0". The active potential divider will therefore be R10 and R20 and with the values specified, the voltage produced at their junction will be 1.5V approximately (see Table 1).

Table 1
IC2 Output Voltage

0	0.76
1	1.06
2	1.32
3	1.50
4	1.79
5	2.02
6	2.25
7	2.50
8	2.83
9	3.21

Taking account of the 0.45V "lost" across diode D7, there will be 1.05V at the top end of the potential divider R24/R1/R25. Note that the forward voltage drop of the diodes is much less than expected (usually taken to be 0.7V approximately). This is because they are operating under very low current conditions. If the sliding contact is at mid-track position, there will be equal values in the top and bottom arms. The voltage applied to capacitor C2 will therefore be one half of 1.05V - that is, 0.53V approximately. As the capacitor charges, the voltage applied to IC3 pin 5 will therefore rise from zero and gradually approach this value. Successive LEDs will light - the first one at 0.125V, the second at 0.25V the third and 0.375V and the fourth at 0.5V. The fifth one will not light because this would need 0.625V which is not available. The display will therefore stop at the fourth LED.

Over the threshold

Preset potentiometer, RV1, provides an adjustment to the operating voltages. This will be used at the setting-up stage to

provide correct operation. It is needed because the voltage levels may not be exactly as calculated.

Switch S1 is a single pole 2-way (SPDT) type. Its push to make contacts apply a virtual short circuit to capacitor C2 (since resistor R26 has a very low value) while the switch is pressed. This will ensure that it is completely discharged at the time it is released. The display will therefore rise from zero each time. Resistor R26 limits the discharge current which could possibly damage the switch contacts in time.

Construction

Begin by drilling the four mounting holes and soldering the three i.e. sockets in position. Follow with the two link wires then all diodes and resistors (including preset, RV1). Note that resistors R8, R12, R13, R11, R7, R6 and R10 are indicated using letters A to G for clarity. Take care to observe the polarity of the diodes. These are arranged in two sets. In the horizontal group of seven (D7, D3, D4, D8, D10, D9 and D5), the striped (cathode) end is to the right. In the vertical group of three (D2, D6 and D1), the cathode is at the bottom. Add the capacitors making sure to observe the polarity of electrolytic capacitors, C2 and C4. The slightly shorter end lead is the negative one in each case.

Solder the LEDs in position - the green ones are at the end closer to the regulator. All anode ends (those having the longer end lead) are soldered to the right-hand pads which are all connected together. Care must be taken to ensure that the LEDs stand equal distances above the panel and higher than any other component. In the prototype, the tips of the LEDs stood 20 mm above the panel. Add the regulator, again, taking care over its orientation. Using the specified component, the flat face is adjacent to the row of LEDs. Note that certain similar regulators have their outer pins interchanged. If necessary, refer to the supplier's data. Solder pieces of stranded connecting wires to the points labelled S1 "push to make contact", "push to break contact" and "common contact". Solder a similar piece of wire to the pad labelled "S2". Adjust RV1 to approximately mid-track position.

Insert the ICs into their sockets with the correct orientation. Since these are CMOS devices, they are vulnerable to damage by static charge which might exist on the body. It would be a wise precaution to touch something which is earthed - such as a water tap - before handling the pins.

Just in case

The prototype unit was built in a plastic box with an aluminium lid. This gives a good appearance. However, any case style will do as long as it can accommodate the components. Everything, except the battery pack, is mounted on the top panel. The circuit panel will be attached so that the red LEDs are at the top of the display. Measure the positions for the LED holes and drill them to a diameter of 5mm and at 7.5mm centres. The final appearance of the device depends largely on the neatness of the row of LEDs so take great care to ensure that they are equally-spaced and in a perfect straight line. Drill holes for circuit panel mounting, for on-off switch S2 and push to go switch, S1. Mount the circuit panel using plastic stand-off insulators on the bolt shanks. Cut these to such a length that the LEDs protrude through their holes by about 3 mm.

Mount the switches and referring to figure 3, complete the wiring. Take care that S1 tags are correctly connected. With the component used in the prototype unit, the tag labelled "1" is the push to make one and the one labelled "3" the push to break. This marking will be found in small lettering next to the

Figure 2: the component layout


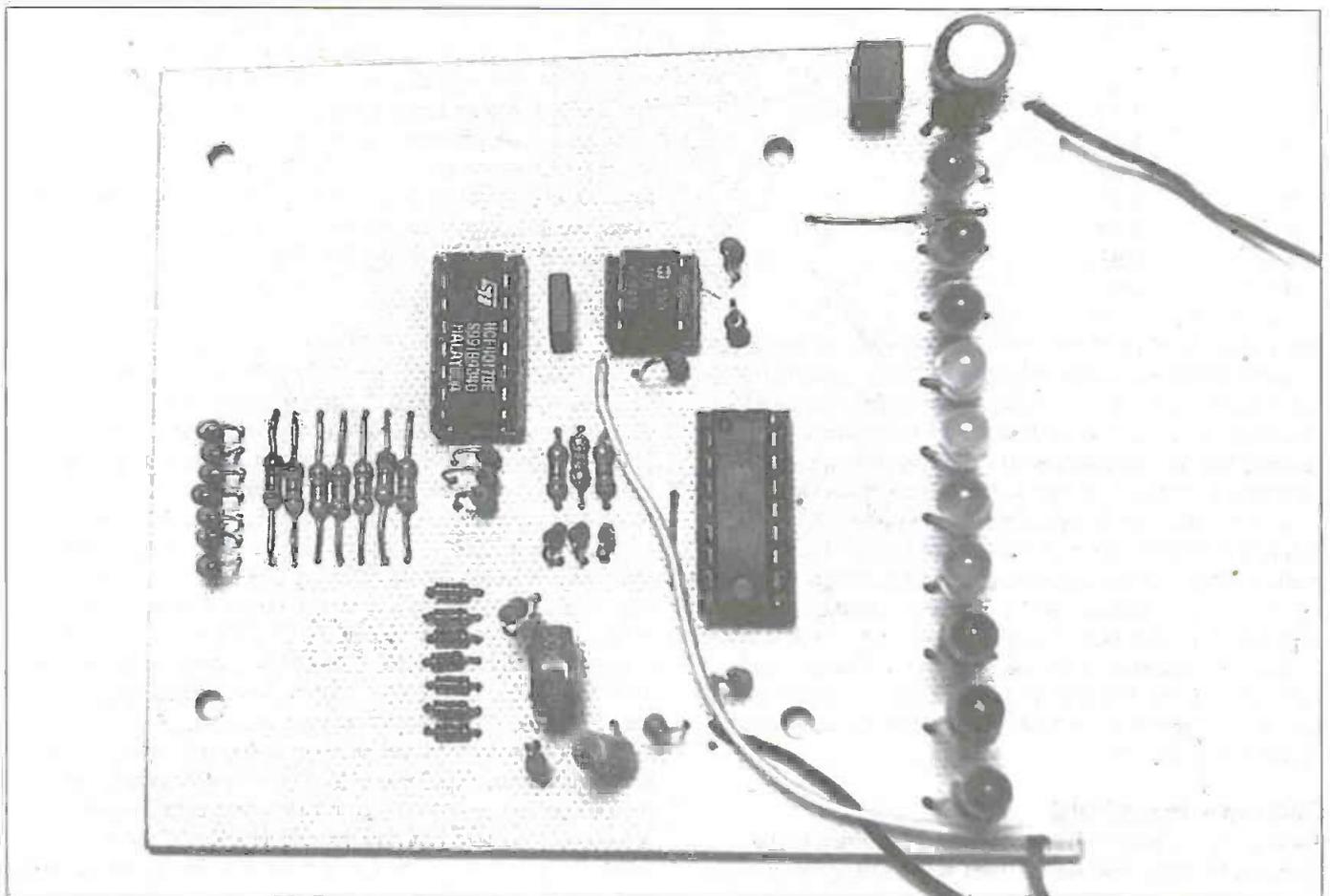
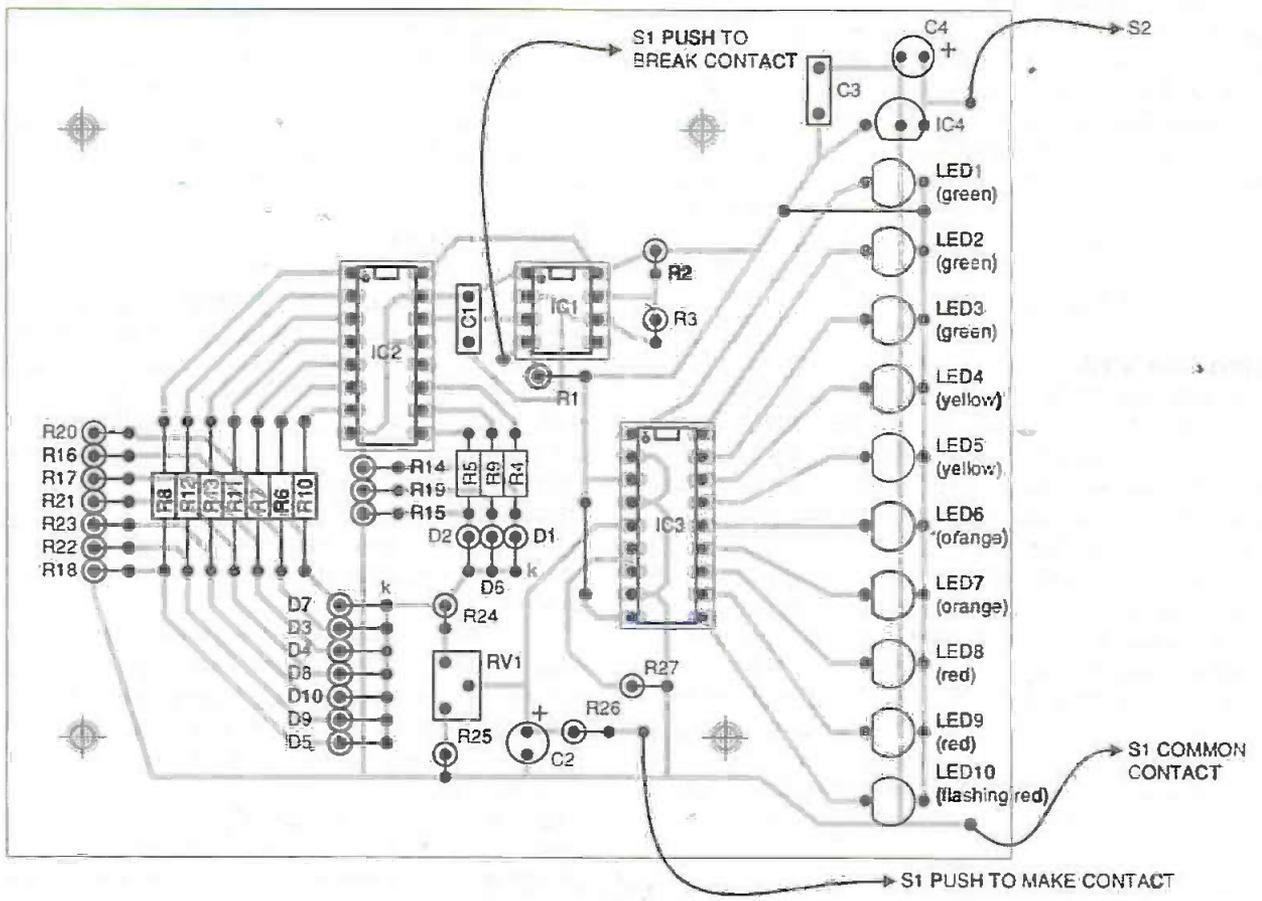


Figure 3: wiring up the arrow

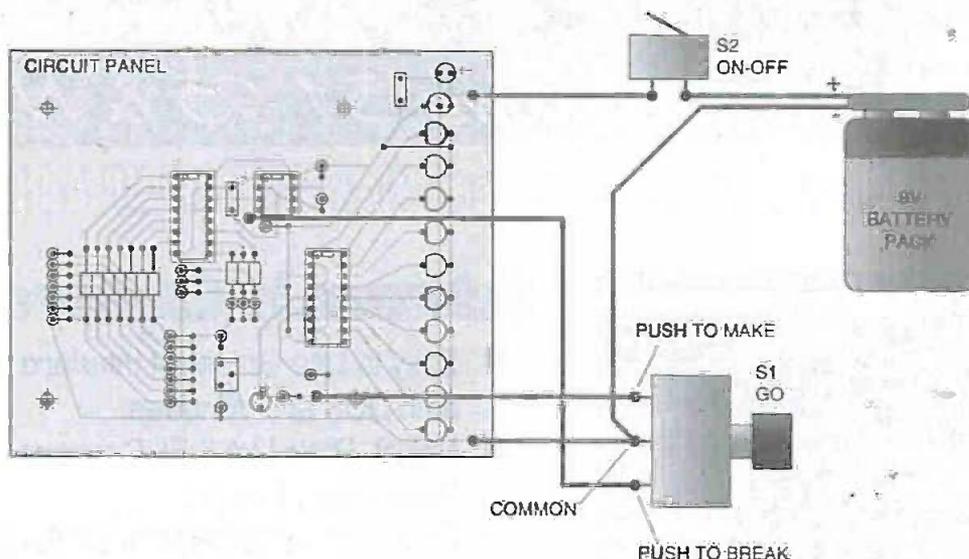

terminals themselves. The centre tag is the common one and is connected to the negative battery snap wire together with the "S1 common contact" one leading from the circuit panel as shown.

With switch S2 off, insert the batteries, snap the connector in place and secure the battery holder using a small bracket or adhesive fixing pads. Fit the lid without the screws for the moment and switch on. Some of the LEDs will light to give a random display. Press S1 for a short time. Successive LEDs should light from the green end taking several seconds to reach the final outcome. Repeat a sufficient number of times to check that each LED has a chance to operate. If it is clear that the flashing red one never comes on and there is sometimes a

result where no LED operates at all, the RV1 setting should be increased a little (by anti-clockwise rotation of the sliding contact as viewed from D8 position). If the first LED never comes on its own, the setting could be reduced. Once correctly adjusted, the preset should require no further attention and the lid may be secured. Note that the flashing red LED may not flash fully on and off. This is a consequence of the unusual way of driving it. The box may, of course, be decorated with a suitable heart motif.

The first sign that the batteries need replacing is when sometimes no LED comes on and no one ever gets the flashing red! We did warn you that this was true to life!

Press the button - you never know, you might be lucky in love!


PARTS LIST for Cupid	Resistors		Semiconductors	
	R1, R2, R4 to R13, R16	10k	IC1	7555
	R3	220k	IC2	4017
	R14	18k	IC3	3914
	R15	13k	IC4	LM78L05ACZ
	R17	8k2	LEDs	3 green; 2 yellow; 2 orange; 2 red; 1 flashing red. All 5mm.
	R18	6k8	Miscellaneous	
	R19	5k6	S1	SPDT push-button switch (Maplin BK68Y); S2 SPST miniature toggle switch; printed circuit board; box; 8-pin dill socket; 16-pin dill socket; 18-pin dill socket; holder for 6 AA size cells; six alkaline AA cells; PP3-type connector for cell holder. All components for Cupid's Arrow were obtained from Maplin.
	R20	4k3		
	R21	3k6		
	R22	2k7		
	R23	1k8		
	R24, R25	47k		
	All fixed resistors	0.6W 1% metal film		
	RV1	100k min vertical preset		
Capacitors				
C1	10n			
C2	10m 16V electrolytic			
C3	470n			
C4	220m 16V electrolytic			

PROTEUS

For DOS and Windows 3.1, 95 & NT

The Complete Electronics Design System - Now With RIP-UP & RETRY!

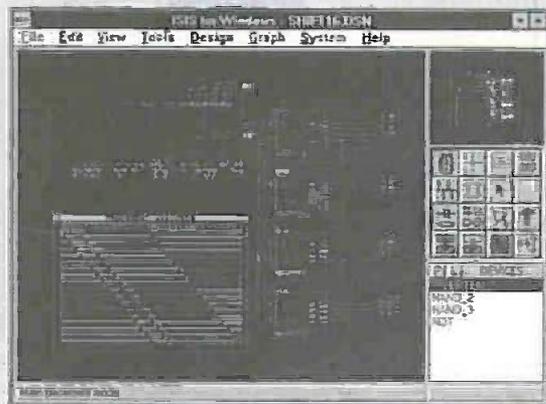NEW LOW PRICE OPTIONS AVAILABLE
Level 1 (500 pins) from £250
Level 2 (1000 pins) from £495
Level 3 (unlimited) from £995




Schematic Capture

- Easy to Use Graphical Interface under both DOS and Windows.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and



Simulation

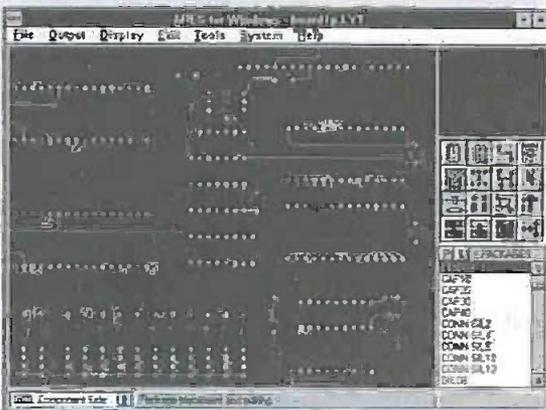- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



PCB Design

- 32 bit high resolution database.
- Multi-Layer and SMT support.
- Full DRC and Connectivity Checking.
- RIP-UP & RETRY Autorouter.
- Shape based gridless power planes.
- Output to printers, plotters, Postscript, Gerber, DXF and clipboard.
- Gerber and DXF Import capability.

labcenter
Electronics

Call now for your free demo disk
or ask about the full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857.
53-55 Main St, Grassington. BD23 5AA.

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

EMAIL: info@labcenter.co.uk
WWW: <http://www.labcenter.co.uk>

The Shake'n'Etch in operation - this shows the tilt of the tray and the approximate level (shallow) of the etching fluid.



PCB Shake'n'Etch

by Bob Noyes

Many of the messy complications of making your own PCBs at home or in a small workshop can be overcome with the help of this dedicated rocking tray for PCB etching solution.

This project was born out of total frustration: the frustration of waiting for a board to etch in an almost-cold PCB bath. When etching solution is fresh it is still hot from the hot water used to prepare it, but it soon loses its heat and takes longer and longer to work.

In the past I've used a PCB tank which has a heater and bubbles air through the solution to speed up the process, but you can't see what's happening and when the holder containing the board is withdrawn to examine the PCB it drops etching solution everywhere. Constant checks must be made to stop it from over-etching, especially when very thin tracks

are used, and consequently a mess is made and ferric chloride is a devil of a chemical to clear up.

To keep a constant eye on proceedings you can't beat the good old fashioned etching trays, but these lose their heat very quickly because the layer of ferric chloride has to be very shallow (or you can't see the board). This shallow level also means that commercial heaters on the market can't be used as they require a fair depth of solution to radiate their heat.

After years of putting up with all these problems I finally decided to do something about it, so here's the finished project, the Shake 'n Etch; it has two distinct sections and either or both can be built.

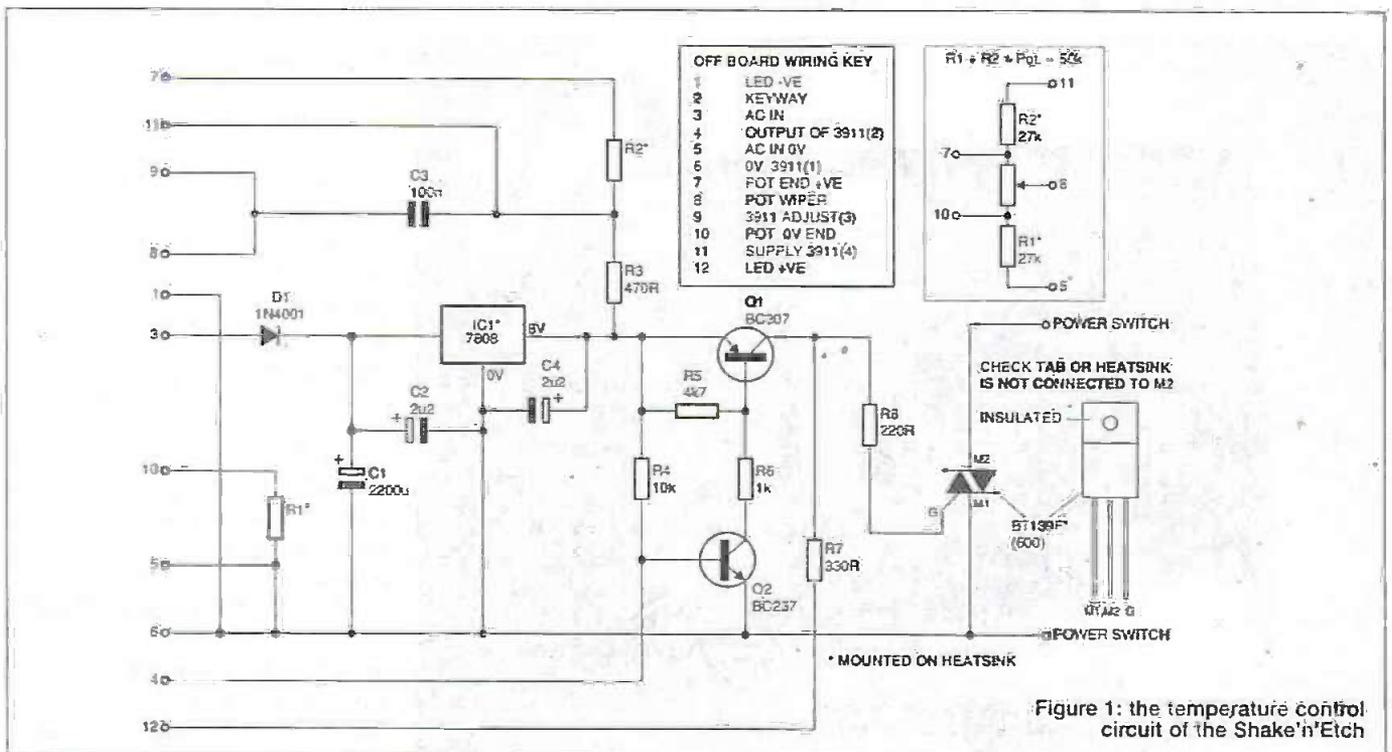


Figure 1: the temperature control circuit of the Shake'n'Etch

The heater


Because of the corrosive nature of ferric chloride it is not practicable to heat the solution directly, i.e. by putting the heater into the etching solution, so the only practical way is under floor heating - an idea borrowed from the Roman era of over a thousand years ago. In this case, it consists of a piece of aluminium at least 3mm thick, or two thinner pieces bolted together. The size is slightly larger than the PCB tray which is going to sit on it; the edges can be bent down for rigidity. A heater is bolted under the aluminium plate. The heater presented a problem at first until it struck me that large 100 watt power resistors are designed to dissipate heat to the surrounding heatsink, so two of these have been used to convert electricity directly into heat.

Now the problem was overheating; if the heaters can increase the temperature from ambient up to, say, 60 degrees C they can keep on going until either the plastic trays melt or the solution bubbles away. This problem was resolved by using an LM3911 temperature sensor IC, also bolted directly to the underside of the tray plate and used to control the heaters via a small PCB using a triac to switch the power on and off. A variable control allows precise temperature setting of the temperature of the tray plate and hence the solution.

The agitator

The second problem when using a PCB tray is that the board lies in a layer of black gunge, (although there is probably some fancy chemical name for it). In a PCB tank air is bubbled through the solution and the board sits up vertically so that the black gunge is bubbled away and drops to the bottom of the tank. This method is impractical in a PCB tray because the solution is only a fraction of an inch deep, so another approach was required. A way around this was to rock the tray slowly,

Figure 2: the component layout for the temperature control board

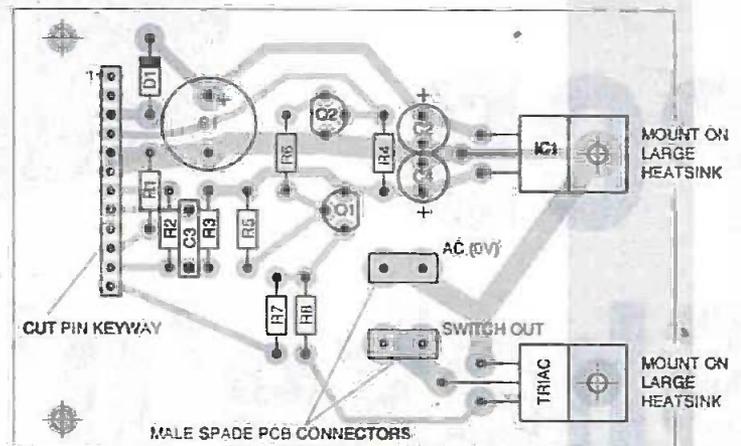

TRIAC BT139F SHOULD BE INSULATED. TAB SHOULD NOT BE CONNECTED TO MT2 IF TAB IS NOT INSULATED USE AN INSULATING MOUNTING KIT, MICA WASHER AND PLASTIC BUSH

producing a small wave; this washes over the board and removes the black gunge. When using both of these additions, the etching process is speeded up and a more even etch is achieved as well as making the solution last longer.

The heater in detail

For safety reasons a low voltage is used. Although this increases the current needed to produce the same amount of heat it is far safer; after all, a bath of liquid is going to sit on top of it when in operation. A supply of 12 volts AC was chosen as these transformers are readily available and reasonably priced. The value of the heating resistors is 4.7 ohms, 100 watts. So with no other losses the total heat generated is:

Two 4R7 resistors in parallel = 2.35R

Current = $I = V/R = 12/2.35 = 5.1$ amps

Power (heat) = $I \times V =$ watts

$5.1A \times 12V = 61.2$ watts

or 30.6 watts in each resistor.


As can be seen from the above calculation, 50 watt power resistors can be used, but 100 watt ones are larger and dissipate the heat over a bigger area and as each one is only run at 30.6 watts they are being run well within their specification.

The total power of 61.2 watts is well within the rating of the 100 watt transformer even allowing a few watts for the motor drive in the agitator unit.

To control this 60 watts of heat, a LM3911 temperature control ic is used: this remarkable little ic is again reasonable in price and contains all the electronics to switch the heating

The Shake'n'Etch box (here seen propped on its side) showing the layout of the control panel and the rocking tray.

Figure 3: the circuit of the L200 power supply board. Mount IC1, L200 on large heat sink.

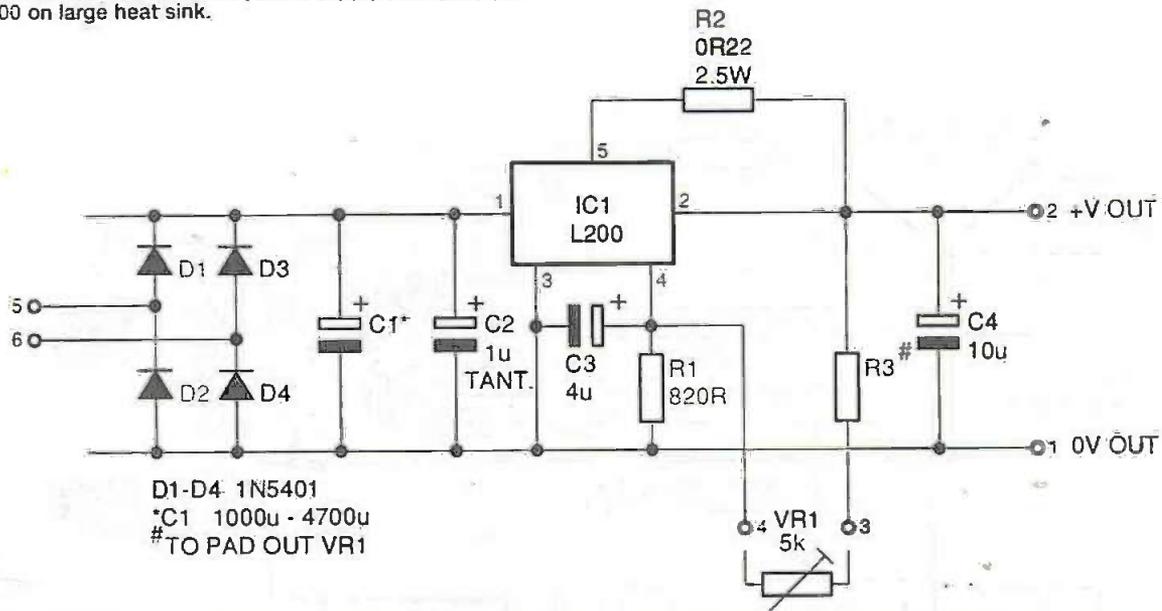

on and off digitally. Being a small DIL 8-pin device it requires an external power switch; this is because any high power switch produces heat and would interfere with the temperature being sensed by the internal thermistor. The pin out is as follows:

1. 0 volt
2. Output (open collector)
3. Temperature adjust input
4. + volts in: 6.8 volts internally regulated
- 5, 6, 7 and 8 not connected

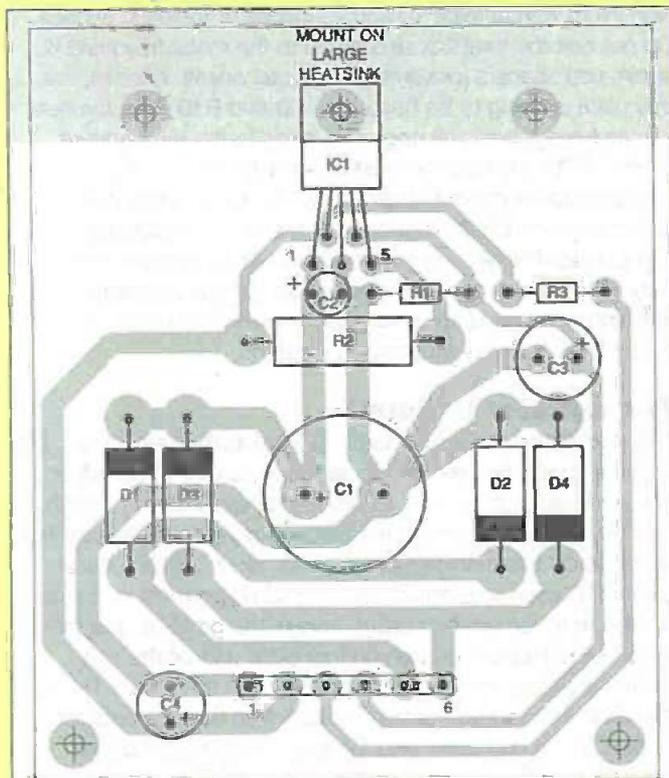



Figure 4: the component layout of the L200 power supply board. Pin 1 = 0V out; pin 2 = +V out; pin 3 = ext pot; pin 4 = ext pot; pin 5 AC in; pin 6 = AC in.

The output pin 2 takes the shape of an open collector output, so R4 is required to turn on TR2 when the temperature being sensed is lower than that set on pin 3. TR2 then turns on TR1 by drawing base current through it. TR1 then turns on the triac output device via R8 as well as a monitor LED via R7. The triac chosen, the BT139F, is a very high power device as, although in this circuit its RMS constant current is around 5 amps, its peak current is much higher. It has an insulated tab and can be mounted directly onto the heatsink without the need for an insulating set.

For correct operation the LM3911 requires a stable supply although it has a built in zener regulator. The 12 volt AC will be higher off load, i.e. the heaters off and drop to 12 volts with the heaters on. To remove this voltage change IC1, a 7808 delivers a constant 8 volts to the dropper resistor R3. Because of the low current demand of the temperature circuit control, half wave rectification is used; this also allows a common connection for MT1 of the triac and the 0V of the supply, not the case if a diode bridge was used. When the temperature being sensed is the same as the temperature set on Pin 3 (the output), pin 2 goes low. This turns off TR2 which turns off TR1 which in turn switches off the triac and the monitor LED goes out indicating that the heaters are off.

Because of the spacing of the temperature sensor IC3 between the two heaters R9 and R10 there will be a thermal delay which is caused by the heat generated in R9, R10 taking time to reach the sensor. By the time the heat reaches it the heaters have slightly overheated, that is, gone above the preset temperature, so the sensor will turn off the heaters until the sensor detects a temperature lower than that set by VR1. Then the heaters will be switched on and stay on until the sensor detects the correct temperature, so that again the temperature will vary slightly, hovering around that set. Great care must be taken when calibrating the control VR1. The LM3911 does not respond to a setting of degrees centigrade but to a voltage on Pin 3. This voltage sets the switching temperature. In both the models made here the correct maximum voltage on Pin 3 was 3.3 volts. The higher the voltage the lower the switching temperature and the lower the voltage the higher the temperature set. Because of the large number of variables no precise voltage can be given so it must be set by trial and

Figure 5: connections to the temperature control board

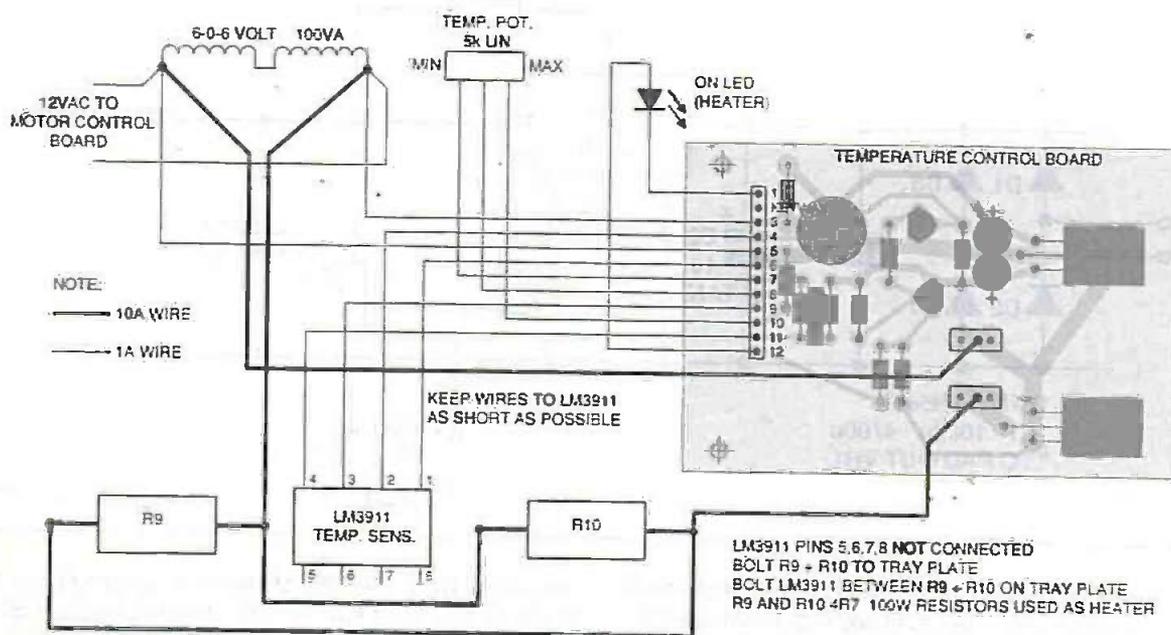

error. This should be set such that the tray plate is just touchable quickly but cannot be touched for more than an instant. The temperature of the solution will always be lower than that of the tray plate because the plastic tray acts as a kind of temperature insulator. The solution must be kept below 60 degrees C to minimise any vapour from being given off, as it has corrosive properties. Anything much above this could cause a health problem, as well as affecting the surroundings with tell-tale brown dots associated with ferric chloride.

The monitor LED will give an indication that the heaters are on. To test the circuit the base and emitter of TR2 can be shorted together, which should turn off the triac and the LED (this is simulating the effect of the temperature being sensed is above that set). If shorting these points fails to turn off the LED, re-check the circuit for errors to find out why.

As the set temperature approaches the monitor LED starts to glow less brightly; this is because the output Pin 2 of the LM3911 switches between off (high) and on (low). This is achieved by pulse width, that is, the output starts off high then pulses low with short low pulses. These pulses get wider and wider until it is low with short high pulses, and the last stage in the output goes low. This is done to provide a digital output. The triac is always hard on or hard off. This pulsing makes the use of a relay to do the power switching impractical, as the relay contacts chatter during this pulsing time. The chattering could cause the relay's contacts to pit due to the sparking of the contacts, as they would be switching the full 5.1 amps.


If the agitator section is not going to be built, the tray plate must be bolted to the box with four small-diameter bolts (3mm) and a gap of 3mm left between the metal tray plate and the external wooden box. This is to reduce the heat losses into the box as well as leave a path for any heat under the tray plate to escape. If you are going to build the agitator, only two mounting bolts are used, M4 type (4mm), and these will be used as the pivot points.

The leads from the sensor 1C3 to the temperature control PCB should be as short as possible. The best way is to mount the PCB onto the underside of the tray plate with spacers; the leads then are only a few inches long. The heatsink with the 7808 and the triac mounted on it should be a piece of aluminium with at least 10 square inches of radiating surface. Do not bolt the heatsink directly on to the metal tray plate but, again, use spacers (preferably not metal ones!). After all, the tray plate is going to be heated by R9 and R10 - not the best way to keep a heatsink cool. The leads to the temperature control PCB and heaters must be long enough to allow the tray plate to be moved up and down by the agitator without straining them. Check that none of the wires actually touch the tray plate or the heating resistors, as over a period of time this may cause the insulation to melt, with obvious problems resulting. (Always keep wires away from hot surfaces, in any case.) See the suggested layout diagram.

The agitator in detail

This part of the project is more mechanical than electronic. The object is to slowly raise and lower one end of the tray plate about half an inch in order to produce a small wave to wash over the board to dislodge the black gunge not to cause a tidal wave. To do this a small electric motor fitted with a suitable gearbox is used to produce the up and down motion. A lever is fitted to a cog on the output drive of the gearbox, this lever is connected to one end of the tray plate and as the cog rotates the lever raises and lowers on each revolution. This is shown in the diagram; care must be taken that the outside surface of the cog is flat and the lever is not fouled by the mounting bush on the axle or the axle itself. The speed of the output of the gearbox should be in the range between 10 and 40 revs per minute. A little experimenting is required to get this right. The speed of the motor, a DC model motor or similar, is controlled by the motor speed control PCB. This is basically a

Figure 6: motor speed control connections

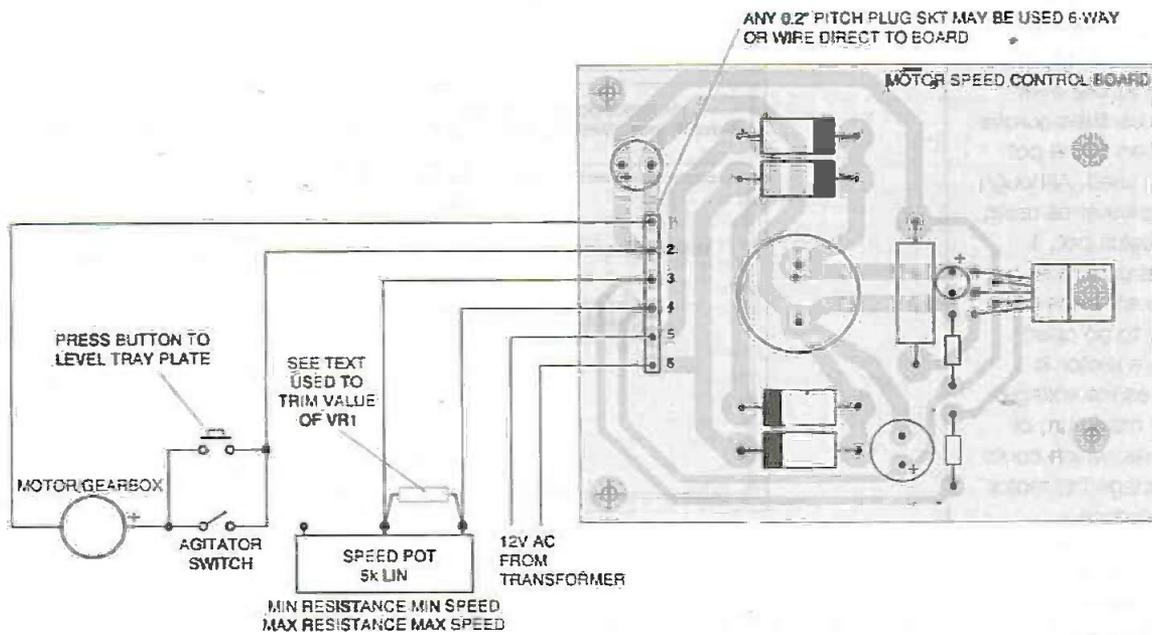

3-15 volt DC regulated supply. The motor gearbox used in the prototypes was bought as redundant stock from Greenweld but similar devices can be found from such firms as J. Bull, a frequent advertiser in ETI. The motor is basically a 12 volt DC motor and runs at 40 revs per minute at 12 volts but when the voltage is reduced it slows down.

Because of the gearbox the torque is quite sufficient at this lower voltage to raise and lower the tray plate and tray of solution. It is advised to try out the design with a tray of water rather than solution and to use a plastic sheet over the tray plate. Needless to say, while these experiments are being carried out the heater unit should be disconnected.


The final design should produce a small wave, little more than a ripple, and even at the highest speed should not cause the solution to splash.

The motor control board can produce from 3 to around 15 volts, so care must be taken if a low voltage motor is used. The circuit is the standard L200 regulated supply almost out of the reference book. R2 is the current limit resistor which causes the supply to begin to shut down when the maximum set current is approached. For most small motors a 1R 2.5 watt resistor can be used, but if more current is required this can be reduced to 0R22 2.5 watt giving well over 1 amp of output. R3 has been added so as to increase the minimum voltage out of the supply its

value can be anywhere from a short circuit, that is, a wire link to 2k2. When a motor stalls due to lack of volts it draws more current than it should, albeit not enough to turn the motor but enough to damage it over a period of time, so by fitting a suitable resistor in R3's position the minimum voltage can be increased such that the speed control, VR1, will run the motor even in the minimum speed setting. The choice of value depends on the minimum voltage required but it works out that a 330R resistor increases the minimum voltage by about 1 volt.

Once the correct voltage range has been found from experimenting say 6 -12 volts (example only). The minimum voltage has to be increased from 3 to 6 volts, that is, 3 volts at 330 ohms per volt works out to around a kilohm, so R3 is 1k.

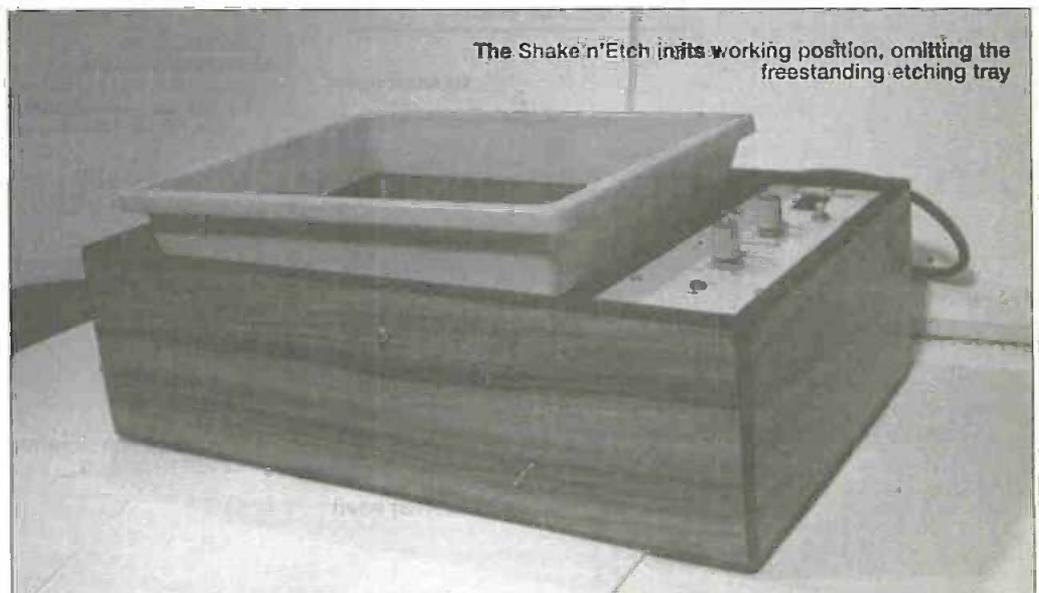
From 6 volts to 12 volts maximum is 6 volts, so again at 330 ohms per volt $6 \times 330R = 1,980$ ohms (1k980), so the



nearest value is a 2k2 potentiometer. To give full range on the control VRI, a standard 5k pot can be used, and a resistor fitted in parallel. That is, to produce a value near to 2k2 a 4k7 resistor can be fitted across the connection of the pot that is being used. Although this is not as linear as using the correct value pot, it works. Great care must be taken not to allow the pot connections to go open circuit when a motor is connected, as the voltage will go to its maximum of about 15 volts, which could possibly damage the motor as well as produce a gigantic wave of corrosive etching fluid! Once everything has been sorted out, it should be run

continuously for around half an hour without the tray in place to check everything is OK and the motor is not overheating. If bolts are used on the mechanical linkage as pivots, lock nuts must be used, or two nuts used with a shake proof washer between them, to prevent them working loose with prolonged use. Then run a final test with the tray in place, but with water in the tray instead of etching solution. Again, a full half an hour test should be carried out using the heaters and the agitator.

Figure 7: a guide to laying out the outer box

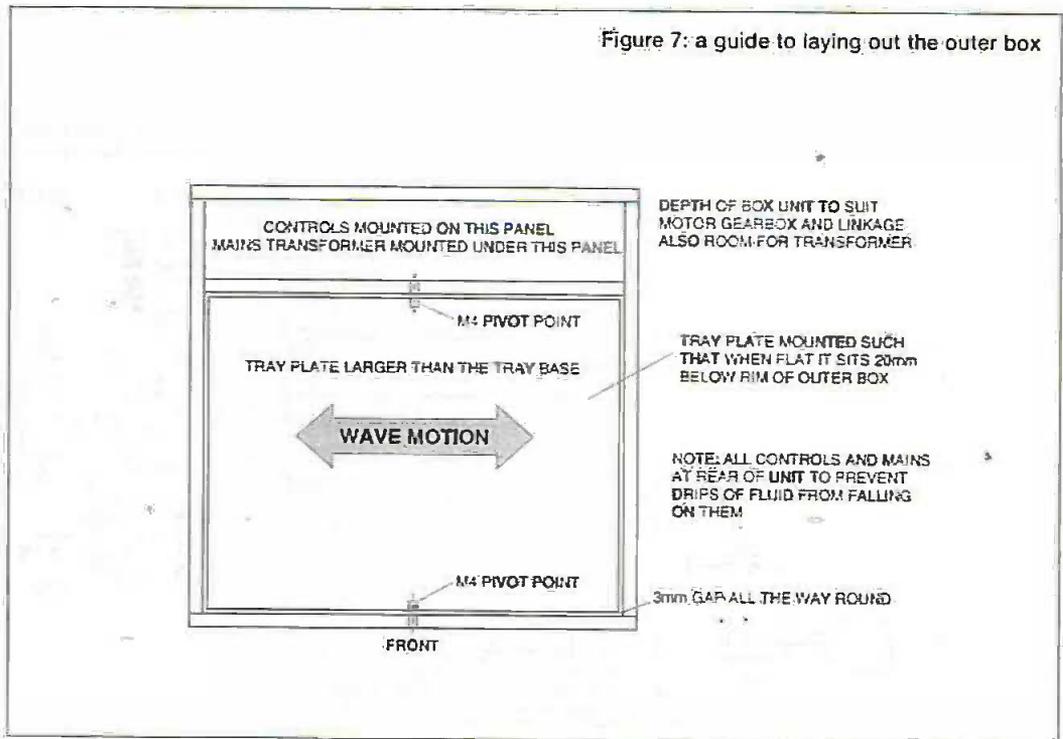

After all the testing the whole unit should be inspected for loose bolts, nuts etc. Only after these tests should solution be used. Care must be taken not to put too much liquid into the tray at once, so as to prevent splashes; also, the less fluid in the tray, the less the strain on the motor.

When in use the advantage of the press button on the agitator can be seen. It is much easier to level the tray plate with this rather than with the switch.

Figure 8: a guide to laying out LM3911, R9 and R10, and the PCB plate.


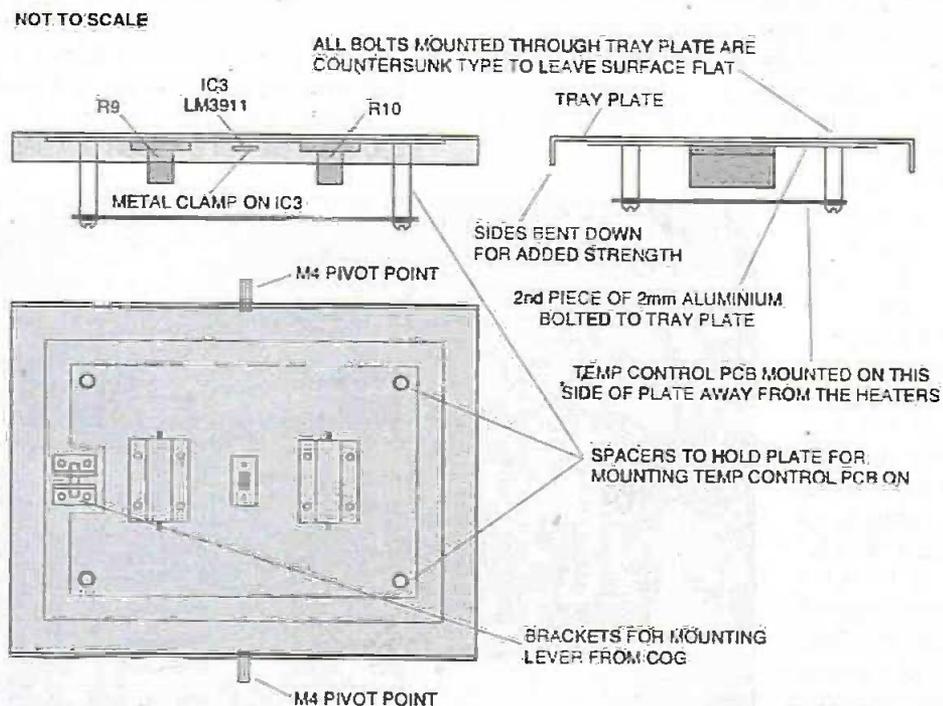


Figure 9: a guide to assembling the tray rocking plate

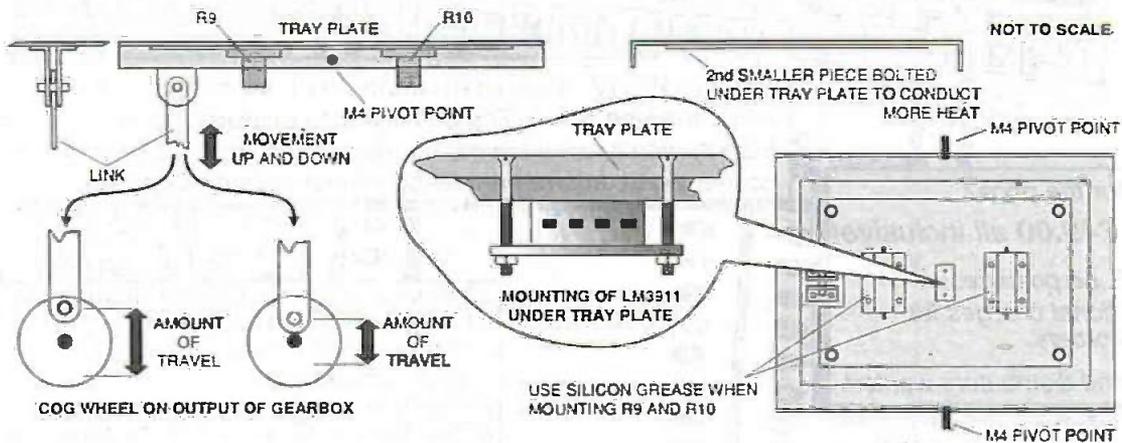

PARTS LIST For PCB Shake'n'etch

(1) The Heater

Resistors

*R1,*R2,*R3	22k
R4	10k
R5	4k7
R6	1k
R7	330R
R9,R10	4R7 100W (off board)
VR1	5k linear potentiometer

*Adjust to suit temperature range: see text.

Capacitors

C1	2200uF 16V radial
C2,C4	2u2 16V radial
C3	100n 16V disc

Semiconductors

IC1	7808 regulator
IC2	LM3911 temperature controller (off board)
Q1	BC307
Q2	BC237
D1	IN4001
TRIAC1	BT139F (Electromail 284949)
LED1	red 5mm 02 0.2in (off board)

Miscellaneous

T1 6-0-6 volt 100VA (e.g. Electromail 211351 toroidal; 207289 chassis mount; 805259 frame mount. The frame mount is suitable and cheapest.) Mains switch 2-pole on/off 3 amp; knob for temperature pot; 10amp wire for heaters; metalwork to suit (see text and diagrams); PCB.

(2) The Agitator

Resistors

R1	820R
R2	0.22R 2.5 watt for up to 1 amp from supply
R3	Link - see text

Capacitors

C1	4700uF 25V radial
C2	1uF 25V tantalum
C3	4u7 25V radial
C4	10u 25V radial

Semiconductors

IC1	L200 regulator
D1 - D4	IN5401 3 amp

Miscellaneous


Motor/gear box 3.12 volts DC motor and gearbox in the range of 10-40 revs on output. See text. (If all else fails, Maplin WC687 seems to have a suitable specification but has not been tested with the prototype.)
Speed control pot 5k linear
Knob for above
Switch - single pole on/off 1A
Switch - press-to-make 1A
Metalwork to suit; cog, etc. to fit output of gearbox
cam-lever; Vero pins or 6-way x 0.2in pin plug (e.g. Maplin JY91Y); PCB.

PCB Designer



For Windows 3.1, '95 or NT

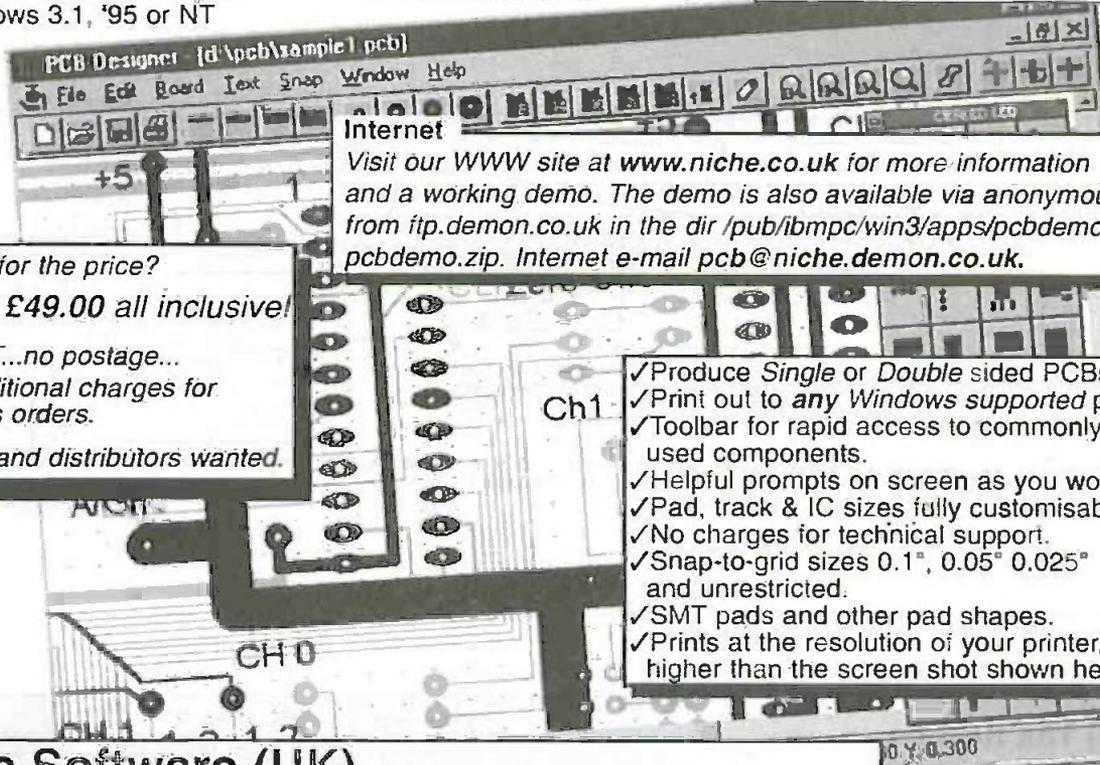Runs on any PC running Windows 3.1, Windows 95 or Windows NT with a minimum 2MB RAM
Will work with any Windows supported printer and monitor



Looking for the price?
It's just £49.00 all inclusive!
...no VAT...no postage...
...no additional charges for overseas orders.
Dealers and distributors wanted.

Internet
Visit our WWW site at www.niche.co.uk for more information and a working demo. The demo is also available via anonymous FTP from [ftp.demon.co.uk](ftp://ftp.demon.co.uk) in the dir /pub/ibmpc/win3/apps/pcbdemo/ as pcbdemo.zip. Internet e-mail pcb@niche.demon.co.uk.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to-grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Prints at the resolution of your printer, much higher than the screen shot shown here.


Niche Software (UK)

12 Short Hedges Close, Northleach, Cheltenham GL54 3PD Phone (01432) 355 414

Available in South Africa from JANCA Enterprises, PO Box 32131, 9317 Fichardtspark at R299,00

ROBOTICS!

NEW!
from the USA

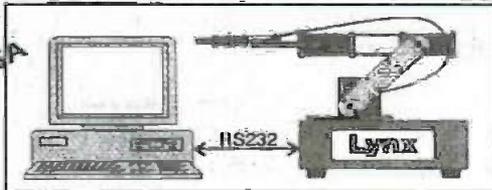


LYNX ARM

ROBOTIC ARM kit, five axis motion with gripper. Control from any serial port. Uses R/C servos for good repeatability and accuracy. Kit includes pre-cut arm components, electronics controller board, PC software (inc source listing) and detailed construction manual. \$69.95/£20.00

STAMP BUG

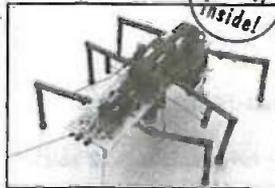'STAMP' based insect kit illustrates basic walking mechanisms. Twin levers detect objects causing back-up and turn. Preprogrammed bug with the option to re-programme (needs Stamp programming pack). Powerful 3 servo construction carries payload up to 250gms and up to 3 hours motion from the on-board NiCads. 20x15x5mm



MUSCLE WIRES

Fascinating wires that CONTRACT WHEN ELECTRICALLY HEATED producing a useful amount of force (Up to 0.9kgf for 250um wires). Require 0.3V/cm and currents from 100ma to 1amp. Choose from four gauges of wire (50,100,150 and 250 um total). Detailed Data and Project Book (128 pages) also available separately and gives Design Wire kit suitable for 13 projects.

SERVO - IR - LCD CONTROLLERS

A range of low cost controller kits: R/C servos (up to 8 servos per board - simple RS232 commands from your PC, hold servo in position until updated etc.); LCD display drivers (16 standard Hitachi controller types up to 4x20 characters - RS232 input); IR programmable receivers (7 output channels - accept any TV/IRF controller up to 25mW output per channel - programme toggle/momentary switching action)

Please call to receive further details on any of the above products

MILFORD INSTRUMENTS


Creative Products for Enquiring Minds
01977 683665, Fax 01977 681465



CHELMER VALVE COMPANY

If you need Valves/Tubes or RF Power Transistors etc. ...then try us!

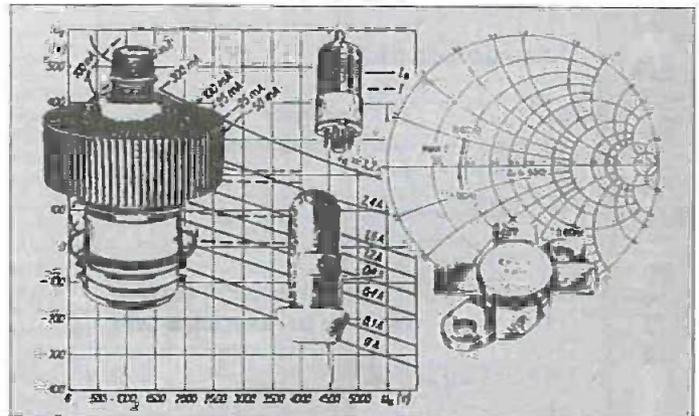We have vast stocks, widespread sources and 35 years specialist experience in meeting our customers requirements.



Tuned to the needs of the Radio Amateur


CHELMER VALVE COMPANY, 130 New London Road,
Chelmsford, Essex CM2 0RG, England

Tel: 44-01245-355296/265865

Fax: 44-01245-490064

Rectifying the Lintels

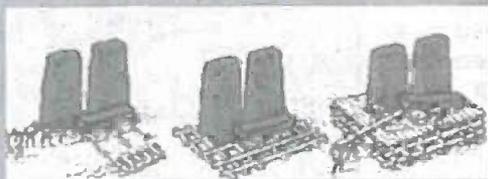A ramp of earth or wood could have been used to haul the lintels to their resting place on the bumps or tenons of the uprights.



But it has been widely accepted - that a re-erecting of timbers, along with the use of levers and wedges could have been used. Indeed, this was tried at Stonehenge in the raising of a repaired lintel some years ago.



Virtual STONEHENGE

*A Heritage site on the
World Wide Web*

Electronics has brought one of the world's oldest scientific calculating machines - Stonehenge - into virtual reality, and made an interactive, real-time reconstruction of the site accessible through the Internet.

The ancient megalithic monument on Salisbury plain in England is famous for the large size of its stone structures, the "trilithons", in which accurately cut stone slabs weighing around 7 tons each are carefully fitted onto stone uprights weighing between 25 and 50 tons apiece to form a ring of square stone arches - and the mystery of its origins. The designers and builders of Stonehenge are lost to history, but the favoured interpretation of the stone circle's use is that it was a kind of astronomical compass, to assist priests (and farmers) of a long-gone age in predicting when sunrise and moonrise would fall at certain times of year so that seasonal religious ceremonies could be carried out at the proper time.

Stonehenge as we know it is in fact a series of stone circles built at different times. The oldest stones of Stonehenge are about 4,500 years old, dating back to around 2500 BC, but there are stoneworks and other traces in the vicinity of ritual activity going back to 4000 BC and beyond.

Virtual reality

The project has been developed by virtual reality specialists Superscape VR in collaboration with the modern monolith, semiconductor giants Intel, who regard it as a fine example of how semiconductors, virtual reality and the Internet can make a dramatised and educational presentation available to a worldwide audience.

The virtual reality model has been designed to provide "scaled performance" on the Internet, so that users with a fast Pentium processor-based PC computer based on one of the faster Pentium processors can get the maximum access to all the details, and a fast frame rate, but users with an older Processor can still get into the virtual environment.

The 3D Viscap software that runs the Stonehenge program runs at the moment with Netscape Navigator 2.0 and above on Intel-based PCs with a 486 processor (or higher) running Windows 3.1, Windows 95 and Windows NT. This demonstrates the amount of processing power needed to carry a moving VR image, even one that is limited to shifting a viewpoint, rather than moving figures around independently.

EQT LTD STEVENAGE

Electronic Sub-Contract Manufacturing & Suppliers to the Electronics Industry

Do you have a requirement for any of the following services:

PCB Assembly (Conventional and Surface Mount)	Product Design/Consultation
Wave & Hand Soldering	Full Procurement Service
Complete Equipment Manufacture	PCB Test & "Burn in" Facilities
Device Programming from hand written sheets or PC 3 1/2" disc	Enclosure Design & Manufacture
Cable Harness Assembly/loom Manufacture	PCB Artwork Manufacture
Card Cage and Module Wiring	Circuits Drawn Professionally
Full Inspection	Kit Procurement & Supply
	Component Sales
	Refurbishment a speciality
	Top Quality Work at Reasonable Rates

Phone Steve on (01438) 360406 or fax details of your requirements to us on (01438) 352742

EQT LTD, Cromer House, Caxton way, STEVENAGE, HERTS, SG1 2DF

Using Windows 95 and a P150 processor, with a 28.8 modem, it still took over 5 minutes to download Viscap and the virtual world before the Stonehenge site could be viewed.

Superscape developed the virtual Stonehenge using their PC-based Superscape VRT, a VR authoring package, using photographs and illustrations taken from all around the site. The "viewing area" covers such a distance that it is quite possible to head for the mysterious grove on the horizon, and then find that you are not sure how to get back to the standing stones. You can move all round the site, and over it, gaining a full aerial view either from close to, or quite a long way up, giving a complete overview of the layout of the site.

Sometimes tourists who have come across the world to visit Stonehenge - perhaps expecting something on the scale of the pyramids - express surprise that it is not bigger. After all, it takes much longer to drive to the area from the nearest town - and park your car, buy a ticket, and walk to the wire enclosure that now surrounds the stones - than it does to walk around the immediate enclosure.

If visitors were to "walk" the entire site, perhaps from the nearest settlement, a different idea of the scale might emerge.

The virtual standing stones have been "built to scale" using photographs and photo-CD techniques to give a certain amount of texture to the stones as your viewpoint comes closer to them, and sharp showing to make the layout clearer. The display is split to give the virtual world on the right and an information display on the left, and a "Timeline" near the top of the screen allows you to scroll along and choose the age of the view that you want to explore.

Heritage

Superscape and Intel developed the Stonehenge project for English Heritage, the organisation that advises the UK Government on all matters concerning the conservation of the historic environment within England. The Chairman of English Heritage, Sir Jocelyn Stevens, has said that the project was "a fundamental part of our vision for increasing access to this mysterious monument and increasing our understanding of the enigma that is Stonehenge." Certainly "high-tech 'tourists'" will be able to "visit" the monument at any time, "day or night, present, past or future, from their own home or office".

The times that you can visit the site are split up into a series of "time bites" from various phases of the development of Stonehenge, from a speculative earliest phase when there were tall upright posts made of pine in the vicinity. One interpretation of these is that they may have been totem poles, not unlike those built by some native Americans and

Canadians in recent centuries. Other phases covered are the woodland clearances before 4000BC and the appearance of long barrows and the Neolithic causewayed enclosure, Robin Hood's Ball, the appearance of the smaller Bluestones from Wales, the erection of the famous Sarsen stones (the largest stones in the structure), and the last phase, only 3500 years ago, when the Bluestones were moved around several times, for purposes



that we can only guess at now. The most recent "redesign" seems to have remained unfinished. Perhaps this is a demonstration that even the most ambitious engineering projects must come to an end at some time.

Hypertext

Using the "intelligent links" feature of Viscap, the user can click on words in the text and "hot-link" to connected features in the virtual world, as well as related texts. This demonstrates one of the first public applications of 3D hypertext, say Superscape. The commentaries themselves are good potted histories of England's most famous ancient monument. The section under "Era 7: Phase 3: 2400-1600BC" describes how the main axis of the site is aligned to midsummer sunrise and midwinter sunset. Each time section is accompanied by a picture.

As an additional attraction, the software writers have built in the ability to observe the sunrise or moonrise over Stonehenge at each. The moonrise is a little disappointing, even on a fast processor - the full moon rises part of the way up the sky, but then seems to get stuck in the trees. The sunrise is more dramatic, with changing colours and shadows.

Virtual reality Stonehenge can be found at web site <http://www.superscape.com>.

Build your own computer

- Features:
- 16 Digital I/O's
 - 12 Analog inputs
 - 16 Timers
 - 2 High speed counters 2.5kHz
 - Direct LCD control
 - RS232 Serial interface
 - PC bus
 - One wire bus (touch memory)

Contact: Diamond Chip
 Tel: +27 12 803 6287
 Fax: +27 12 803 4350
 E-mail: stefan@dchip.com
 Internet: <http://www.dchip.com>

£12.00


excl. postage & tax

Free BASIC compiler and circuit diagram

Developers kits available

Printed Circuits in Minutes Direct from LaserPrint!

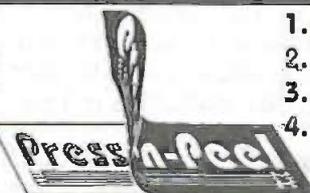8 1/2" x 11"
 * Or Photocopy
 **Use standard household iron or P-n-P Press.



1. LaserPrint*
2. Press On**
3. Peel Off
4. Etch.

Use Standard Copper Clad Board.
 5 Sheets £12.50, 10 Sheets £25.00 + VAT.
 Add £2.50 postage
PRESS-N-PEEL ETCHING SUPPLIES LTD
 18 Stapleton Road • Orton • Southgate
 Peterborough PE2 6TD • Tel: 01733 233043

LASERS

Argon ion / Helium Neon / Diode / Carbon Dioxide

Colours include red, yellow, green, turquoise, blue and infra-red. Output powers range from 0.2mW to over 20 Watts. Applications include research, light shows, image projection, medical or industrial. New and Second hand. Pictured here is a 50mW cyan/blue argon ion air cooled laser head and a miniature 1mW red HeNe laser tube only 147mm long. Second hand blue (488nm) argon ion lasers start from only £100 +VAT.



LASERTECH

Mill Road, Great Barton, Bury St. Edmunds, Suffolk, IP31 2RU
Telephone 01284 788108 Fax 01284 788135

Laser Pointers


Wavelength 660-680 nm.
Max Output < 3 mW.

Laser Range up to 200 meters.
Uses two AAA batteries (supplied).
Ideal for demonstrations and lecturing.

Also CCD Camera Modules;
b/w Standard, low lux & pinhole, £65
b/w Standard with sound, £70
Colour from £180

Nonuts Ltd.

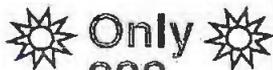2 Chase Cottages,
New Road, Aldham,
Essex CO6 3OT Tel. & Fax 01206 213322



Only
£28

inc. VAT
& postage



Purveyors of Quality
Electronic Things at
Very Friendly Prices



Crewe+Alsager Faculty

PIC MICROCONTROLLERS

Beginners Course on 16C84. One day course. Fee: £125, includes lunch, 16C84 chip and Development Board plus software.

Advanced Course on 16C84 and 16C71. One day course including look-up tables, long delays, keypads, 7 segment displays and A-D conversion. Fee: £125 includes lunch and 16C71 reprogrammable Microcontroller chip, with 4 channel A-D.

Complete Teach Yourself Package including 16C84 programmer, PSU, 16C84 chip, Switch Input Board, Keypad Board, Development Board, 7 Segment Display Board and Buzzer, LED Output Board and 86 page course book, plus software. Fee: £145.

Four-day Course - Understanding Microcontrollers Course Fee: £395, includes lunches and the complete teach yourself package. Accommodation available.

For dates and further details contact Dave Smith,
Crewe+Alsager Faculty,
The Manchester Metropolitan University,
Hassall Road, Alsager, Stoke-on-Trent, ST7 2HL
Tel: 0161 247 5437 Fax: 0161 247 6377
E-mail D.W.Smith@MMU.AC.UK

PIC DEVELOPMENT SYSTEMS

PIC PROGRAMMERS

PIC EEZE-V2 SUPPORTS 16C54/55/56/57/58/61/62/620/621
/622/63/64/71/74/84 AND SERIAL
EEPROMS ONLY £52.95

PIC EEZE-V3 IS AS ABOVE BUT WITH IN CIRCUIT
EMULATION CAPABILITY. ONLY £72.95

BOTH SYSTEMS HAVE ZIF SOCKETS ALREADY FITTED
AND EXPANSION PORTS FOR CURRENT AND
FUTURE DEVELOPMENTS.

ALL NECESSARY SOFTWARE SUPPLIED.



TRICE™

PIC REAL TIME IN CIRCUIT EMULATION

- EMULATION TO 20MHZ
- STEP/SKIP/ANIMATE/RUN ETC.
- VARIABLE SPEED SELECTION
- 8K x 16 EMULATION RAM
- TARGET PROBES INCLUDED
- SUPPORTS 18/28 PIN PIC'S
- 40 PIN PIC'S THROUGH PLUG IN MODULE

Only **£149.95**

TRUE PIC
REAL TIME
IN
CIRCUIT
EMULATION

THE
WORLD'S
FIRST
REAL TIME
PIC-ICE
THAT WON'T
BREAK THE
BANK

TEST YOUR CODE
IN A 'TRICE'

NEW

MISC

LEARNING PACK FOR
BEGINNERS £28.00
DEMONSTRATION PACK FOR
DEVELOPERS £28.00
BASIC FOR PIC'S



PLEASE ADD £2.00 P&P AND MAKE
CHEQUES PAYABLE TO LENNARD RESEARCH


29 LAVENDER GARDENS
JESMOND
NEWCASTLE UPON TYNE
NE2 3DD
TEL/FAX 0191 2818050
PRODUCT PICTURE'S/INFORMATION ON
OUR WEB SITE
<http://www.vex01.demon.co.uk/lennard.html>

ETI


ELECTRONICS
TODAY INTERNATIONAL

TOMORROW'S TECHNOLOGY TODAY


FOILS FOR THIS ISSUE

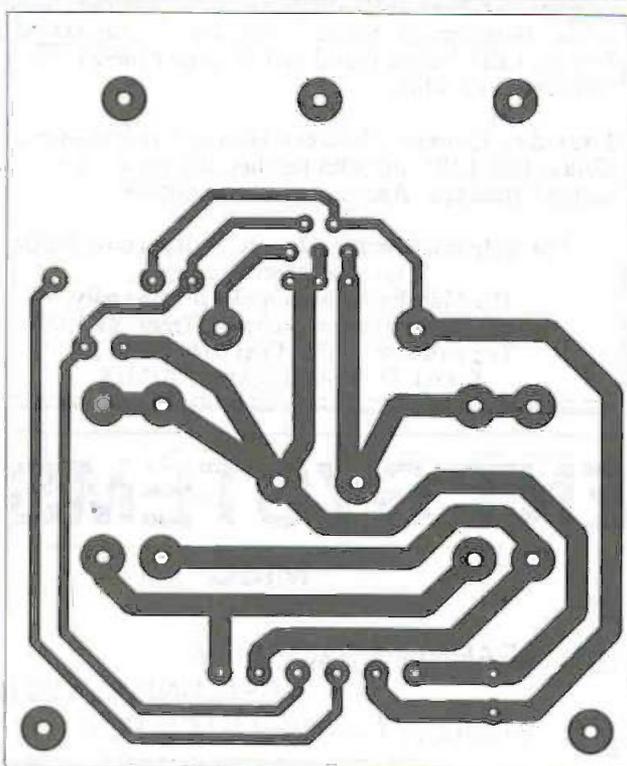


SHAKE 'N' ETCH POWER SUPPLY

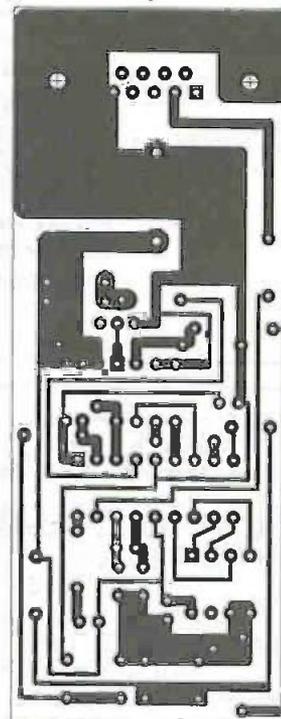


ETI REMOTE DATA LOGGER

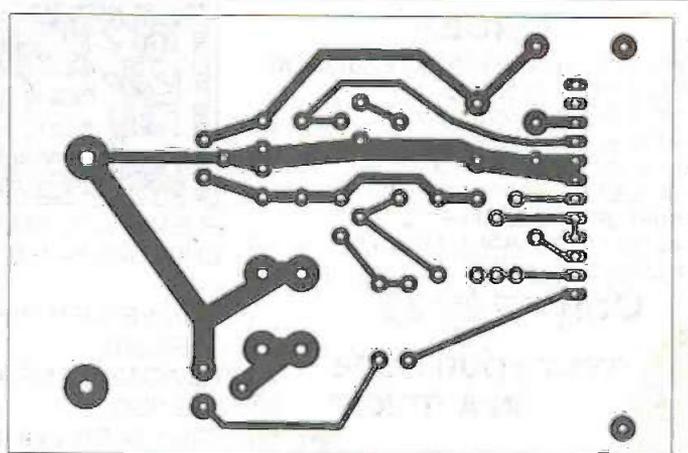

SHAKE 'N' ETCH HEATER

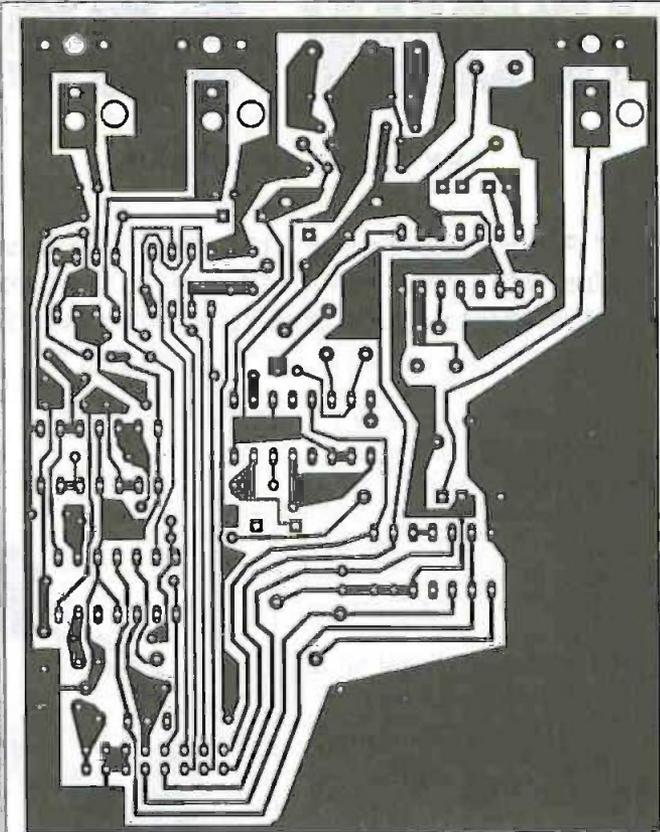

VIDEO SYNC SEPARATOR

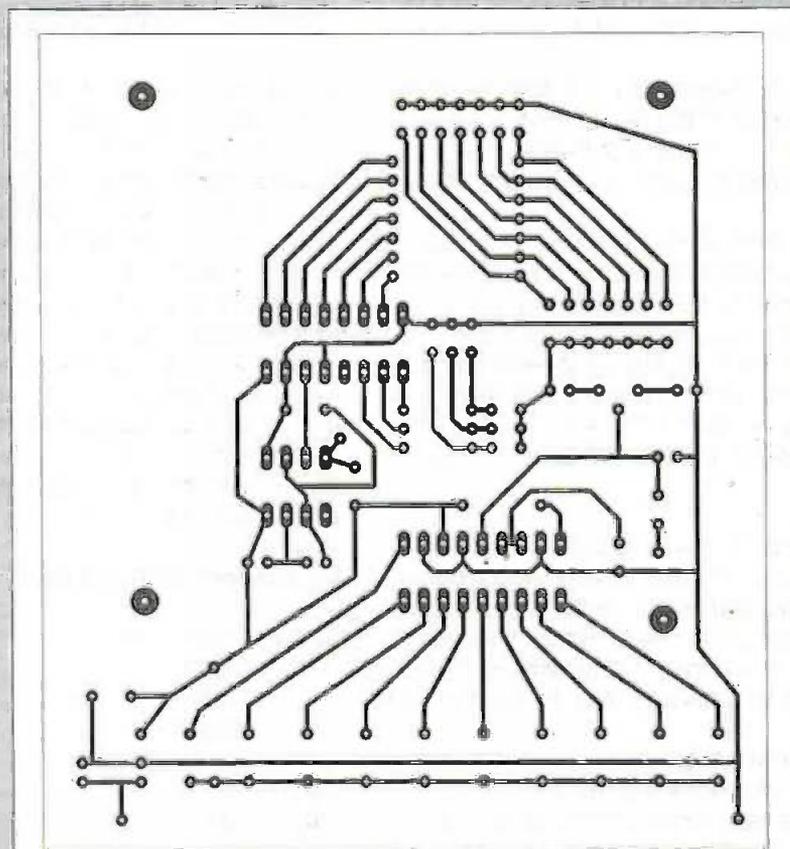

CUPID'S ARROW

Practically Speaking

BY TERRY BALBIRNIE

The last few months of Practically Speaking have been devoted to various aspects of connecting wire. This time we shall continue by looking at the way the thickness of a wire is expressed.

It would seem logical to specify the thickness of a wire as the diameter of its core. For example, a typical light-duty connecting wire may have a diameter of 0.6 mm. Remembering that the current-carrying capacity of a wire depends on the area of cross-section of its core, it might also seem to be a good idea to express it this way instead. For example, the 0.6 mm diameter wire above would have a cross-section area of about 0.28 square mm. Incidentally, this figure is obtained by regarding the cross-section of the wire as a circle of radius 0.3 mm. The formula for the area of a circle is then used:

$$A = \pi R^2 \text{ (where the constant } \pi \text{ is approximately 3.14)}$$

Illogical

However, life is not always as easy as that. A typical instruction for winding a tuning coil for a radio might read "wind 16 turns of 28 SWG enamelled copper wire on to a cardboard tube of diameter 20 mm". It is the "SWG" figure which often confuses newcomers.


The SWG (standard wire gauge) relates the diameter of the wire to some arbitrary number (in this case, 28). The picture becomes less clear when we consider that there are four or five wire gauges used around the world, all with their particular idiosyncrasies!

In Britain, SWG is the most usual system used. American readers will note that they have their own similar American Wire Gauge (AWG). In both systems, the diameter corresponding with a given wire gauge is almost arbitrary (that is, it does not follow any particular plan). However, the rule to remember is that the lower the SWG, the thicker the wire will be. In the British system, 24 SWG wire has a diameter of 0.559 mm. In the American system, 24 AWG wire has a diameter of 0.510 mm.

Thick and thin

The thickest wire likely to be encountered by the amateur is 16 SWG and the thinnest, about 42 SWG although data tables often go as low as 10 SWG and as high as 50 SWG. Very thin wire becomes extremely difficult to handle without snapping it, so its use is really limited to automatic coil winding machines. On the other hand, very thick ones are better described as rod rather than wire.

Note that it is usual for wire to be used only in the even SWG sizes. For example, although it is possible to obtain 21 SWG wire, in practice it is usual for suppliers to list only 20 SWG and 22 SWG. The table below, therefore, only shows the even SWG sizes and how they are related to the diameter of the wire. Note that the SWG figure applies to wires made of materials other than copper. They are therefore often used to

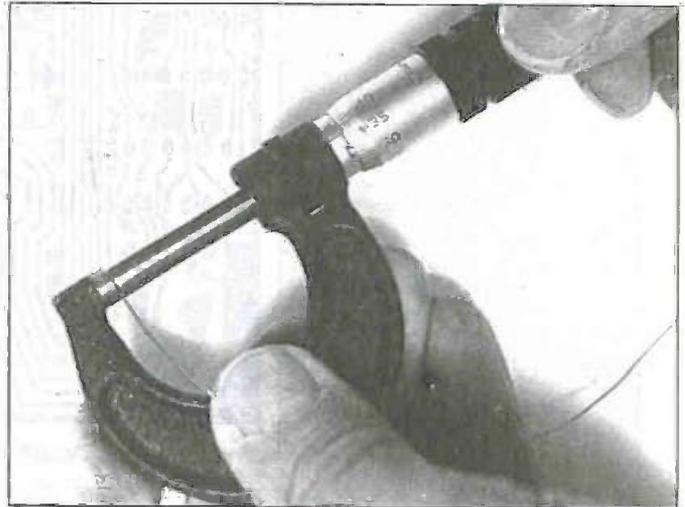

Using the micrometer to measure the diameter of a wire. Insulated wire must have the insulation stripped back first.

express the thickness of resistance wire, which will be the subject of the next Practically Speaking.


To find the SWG figure of an "unknown" wire, you will need to use a micrometer (see photograph). It is a simple matter to measure its diameter and compare this with the table. Note, however, that the diameter relates to the metal core only. With plastic insulated wire, it will be necessary to strip some of this off first. With enamelled wire, the insulation is very thin and it may be possible to make the measurement with the insulation in place. Although the diameter obtained will be slightly on the high side, when this is compared with the figures in the table, the correct SWG figure will still be found. There is a further point that the diameter of a wire is subject to a certain tolerance. Rarely will wire of a given SWG be found with its exact specified diameter.

The Standard Wire Gauge Table

SWG	Diam (mm)	SWG	Diam (mm)
16	1.63	30	0.315
18	1.22	32	0.274
20	0.914	34	0.234
22	0.711	36	0.193
24	0.559	38	0.152
26	0.457	40	0.122
28	0.376	42	0.102

That's all for this time. Next time we shall look at resistance wire.

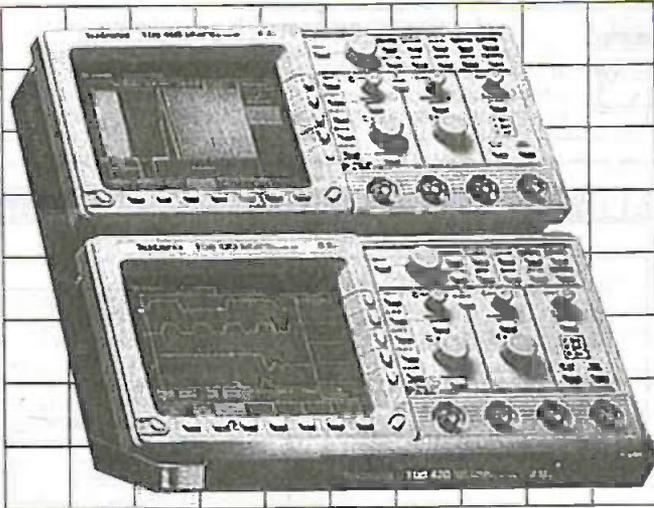SUPPLIER OF QUALITY USED TEST INSTRUMENTS




CONTACT

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
 Unit Four, Fordingbridge Site, Main Road, Barnham,
 Bognor Regis, West Sussex, PO22 0EB U.K.
 Tel: (+44)01243 545111/2 Fax: (+44)01243 542457
CATALOGUE AVAILABLE

OPERATING & SERVICE MANUALS

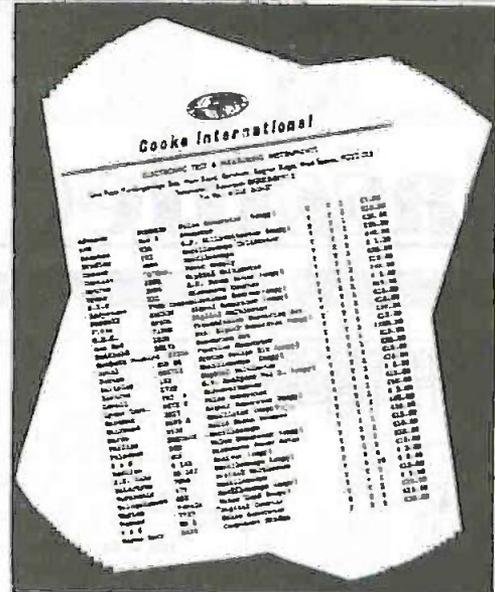

CONTACT

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
 Unit Four, Fordingbridge Site, Main Road, Barnham,
 Bognor Regis, West Sussex, PO22 0EB U.K.
 Tel: (+44)01243 545111/2 Fax: (+44)01243 542457
CATALOGUE AVAILABLE

NEW SPECIAL OFFERS

New mini waterproof TV camera 40x40x50mm requires 10 to 20 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 450 TV lines Vertical and 350 TV lines horizontal, electronic auto iris for nearly dark (1 Lux) to bright sunlight operation and a picture lens with a 90 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12v in and video out).

£93.57 + VAT = £109.95 or 10+ £89.38 + VAT = £104.95.

High quality stepping motor kits (all including stepping motors) Computer independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software.

Kit £67.00 ready built £99.00
 Software support and 4 digital inputs kit £27.00
 power interface 5A kit £36.00
 power interface 2A kit £46.00
 Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit £23.00
 Hand held transistor analyser 2 tests you which lead is the base, the collector and emitter and it is NPN or PNP or faulty £33.45
 LEDs 3mm of 5mm red or green 7p each
 yellow 11p each
 cable ties 1p each £5.95 per 1000
 per 10,000

Rechargeable Batteries

AA (HR) 500 mAh £0.99
 AA 500mAh with solder tags £1.55
 AA 700 mAh £1.75
 C (HP 11) 1.2Ah £2.20
 C 2Ah with solder tags £3.60
 D (HP2) 1.2Ah £2.60
 D 4Ah with solder tags £3.55
 PPG 3 Ah 110mAh £2.95
 1.2Ah with solder tags £1.55
 Szo C with solder tags £2.50
 AAA (HR16) 180mAh £1.75
 1/3 AA with tags (philips G1V) £1.95
 Standard charger charges 4 AA cells in 6 hours or 4Cs or Ds in 12-14 hours + 16PP3 (1, 2, 3 or 4 cells may be charged at a time) £9.95
 High power charger as above but charges the Cs and Ds in 5 hours AAs Cs and Ds must be charged in 2x 4h £10.95
 Nickel Metal Hydride AA cells high capacity with no memory, if charged at 100ma and discharged at 250ma or less 1100mAh capacity (lower capacity for high discharge rates) £3.75

Special offers please check for availability

pack of 4 x 42 x 16mm nickel batteries 171mmx18mm dia with red & black leads 4.8v £5.55
 5 button cell 6V 280mAh battery with wires (Varta 5250Dr) £2.45
 Shaded pole motor 240Vac 5mm x 20mm shaft 30 x 60 x 55mm excluding the shaft £4.95 each
 115v ac 50v dc motor 4mm x 22mm shaft 50mm dia x 60 long body (excluding the shaft) it has replaceable thermal fuse and brushes £4.95 each £3.95 100+
 7 segment common anode led display 12mm £0.45
 LM337H TO3 case variable regulator £1.95
 £1.41 100+
 GaAs FET low leakage current 66573 £12.95 each
 Microprocessor £3.50
 EL942 UHF Limbing amplifier IC 16 surface mounting £3.55 per 100
 £0.20 for 100
 BCS10A transistor £0.10 per 100, used £748
 74LS25 hex inverter £10.00 per 100, used £748
 Microprocessor £3.50
 EL942 UHF Limbing amplifier IC 16 surface mounting

package with data sheet £1.95
 PC-D4 connector Reliability model V102P5 12v in 5v 300ma out 300v input to output isolation with data £4.95 each or pack of 10 £39.50
 Hour counter used 7 digit 240v ac 50hz £1.45
 QWERTY keyboard 58 key good quality switches new £5.00
 Amps AS2203-C large stepping motor 14x 7.5 size 270mm 68mm dia body 6.3mm shaft £8.95 or £200.00 for a box of 30
 Polyester capacitors box type 22.5mm lead pitch 0.8ul 250vdc 18p each 14p 100+ 8p 1000+ 1ul 250vdc 20p each, 15p 100+ 10p 1000+ 0.22ul 250v polyester axial leads 15p each, 7.5p 100+ Polypropylene 1ul 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case 75p each 60p 100+ Philips 123 series solid aluminum axial leads 33ul 10v & 2.2ul 40p each, 25p 100+ Philips 103 series long life 22ul 50v radial 30p each 15p 100+
 Multilayer AVX ceramic capacitors all 5mm pitch 100v 100p, 150p, 220p, 10,000p (10n) 10p each, 5p 100+ 3.5p 100+
 500p compression trimmer 60p
 40 of 570vac motor start capacitor (disector type containing no pots) £5.95 or £49.50 for 10
 Solid carbon resistors very low inductance ideal for RF circuits
 270hm 2W, 68ohm 2W 25p each 15p each 100+ we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list
 P.C. 400W PSU (Intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains interlock connectors on back and switch on the top (top for lower case) dims
 212x49x145mm excluding switch £25.00 each
 £138.00 for 5
 MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor hfe 5v and 15w battery test
 £9.95
 AMD 27256-3 EProms £2.00 each, £1.25 100+
 D/F switch 3PCO 12 pin (ERG SDC-3-023) 60p each 40p 100+
 Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x258x247mm £7.95 or £49.50 for 10
 Hand held ultrasonic remote control £3.95
 CV2456 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £7.50 per 100
 Verbatim R300K-H Streamer tape commonly used on jet machines and printing presses etc. it looks like a normal cassette with a slot cut out of the top £4.95 each (£3.75 100+)
 Heatsink compound tube 95p
 HV3-2405-E5 5.24v 50mA regulator IC 16-264vac input 3 pin DIL package £3.45 each (100+ £2.25)
 LM 555 timer IC 16p 8 pin DIL socket 6p

All products advertised as new and unused unless otherwise stated. Wide range of CMOS TTL 74HC, 74F Linear Transistors kits, rechargeable batteries capacitors fuses etc. always in stock.
 Please add £1.55 towards P&P, vat inc. in all prices

PC ELECTRONICS
 E11 276-277, Chesham, Bucks Road,
 Cheshamfield S40 2BH
 Access Via Orders 01296 311102 fax 500959
 Delivery Welcome 9.30am - 5.00pm Monday - Saturday

ADVERTISERS INDEX

BK ELECTRONICS	10
BULL ELECTRICAL	5,6
CHELMER VALVE	64
COOKE INTERNATIONAL	71
COLES HARDING AND CO	72
CMS	45
C + G TRADING	73
DIAMOND CHIP COMPUTERS	66
DIRECT CCTV	19
DISPLAY ELECTRONICS	40
EPT EDUCATIONAL SOFTWARE	50
ELECTROMAIL	17
EPSILON ELECTRONICS	72
EOT	65
ESR COMPONENTS	21
FOREST ELECTRONICS	45
GRANDATA	8
JJ COMPONENTS	32
JPG	71
J & N FACTORS	72
KFL	32
LABCENTRE	56
LAZERTECH	67
LENNARD RESEARCH	67
LIGHT ENGINEERING SERVICES	72
MANCHESTER METROPOLITAN UNIVERSITY	67
MILFORD INSTRUMENTS	64
MCJ DESIGN	72
NICHE SOFTWARE	64
NO1 SYSTEMS	15
NO NUTS	67
OLSON ELECTRONICS LTD	05C
P H AGAR	72
PARTRIDGE ELECTRONICS	73
PLANCENTRE PUBLICATIONS	72
PICO TECHNOLOGY	25
PRESS AND PEEL	66
QUICK ROUTE SYSTEMS (POWERWARE)	IFC
RADIO TECH	32
RADIO AND TELECOMMUNICATIONS SCHOOL	72
SERVICE TRADING CO.	72
STEWART OF READING	19
TELNET	49
TSIEN	47
THREE CROWNS	19
VARIABLE VOLTAGE TECHNOLOGY	72
VERONICA FM	73
WILSON VALVES	72

Classified



Andy Forder
01442 66551

Send your requirements to:
ETI Classified Department, Nexus, Nexus House,
Boundary Way, Hemel Hempstead, HP2-7ST
Lineage: 75p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£10.50 + VAT per single column centimetre



Ring for information on series bookings/discounts.
All advertisements in this section must be pre-paid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60
OUTPUT 0-260V

Price P&P

Model	Price	P&P
0.5KVA 2.5 amp max	£33.00	£5.00 (£38.00 inc VAT)
1KVA 5 amp max	£45.25	£7.00 (£52.25 inc VAT)
2KVA 10 amp max	£85.00	£13.50 (£98.50 inc VAT)
3KVA 15 amp max	£95.50	£15.50 (£111.00 inc VAT)
5KVA 25 amp max	£150.00	£25.00 (£175.00 inc VAT)
10KVA 45 amp max	£300.00	£50.00 (£350.00 inc VAT)
15KVA 3 PHASE Star	£295.00	£49.00 (£344.00 inc VAT)

Buy direct from the importer. Reasonable prices in the country.
COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO (115-240V Auto transformer either cased with American sockets and mains cable or open frame type. Available for worldwide delivery).

WIDE RANGE OF XENON FLASH TUBES

Model	Price	P&P
48 40 watt £14.00 (cashiers only)	£16.45	inc VAT
28 20 watt £9.00 (cashiers only)	£10.50	inc VAT
12m 6 watt £4.80 + 75p p&p	£5.55	inc VAT
6m 6 watt £3.95 + 50p p&p	£4.45	inc VAT
6m 4 watt £3.95 + 50p p&p	£4.45	inc VAT

230V AC BALLAST KIT
For either 6m, 9m or 12m tubes £8.95 - £14.00 p&p (£9.75 inc VAT)
The above Tubes are 3500-4000 angstrom (350-400nm) useful for detecting laboratory markings, effects lighting & chemical applications.
Other Wave Lengths of U.V. TUBE available for Germaclone & Photo Sensitive applications. Please telephone your enquiries.
400 WATT BLACK LIGHT BLUE UV LAMP
GES Mercury Vapor lamp suitable for use with a 450W P.F. Ballast
Only £38.00 + £4.00 p&p (£42.00 inc VAT)

12V D.C. BILGE PUMPS
500 GPH 12v rated 3 amp £19.95
1750 GPH 12v rated 6 amp £34.95
Also now available 24V D.C. 1750 GPH 1.5 amp
£amp £28.95. All designed to be used submerged. PRICES INCLUDE P&P & VAT

SUPER HY-LIGHT STROBE KIT
Designed for Disco, Theatrical uses etc.
Approx 16 pin base. Adjustable speed £50.00 + £3.00 p&p (£53.00 inc VAT)
Case and reflector £24.00 + £3.00 p&p (£27.00 inc VAT)
SAE for further details including Hy-Light and General Strobe Kits.

SKVA ISOLATION TRANSFORMER

As New Ex-equipment fully shrouded Line Noise Suppressor. Ultra Isolation Transformer with terminal covers and Knock-out cable entries. Primary 120/240V Secondary 120/240V 50/60 Hz. 105p pf Capacitance. Size L37 x W19 x H150mm Weight 42 Kilos. PRICE £120.00 + VAT

24V DC SIEMENS CONTACTOR
Type 3TH8022 DS 2 x NO and 2 x NC 230V AC 18A contact. Screw on Din Rail fitting. Size H 120 x W 45 x 0.75mm. Brand New Price £7.63 incl. P&P and VAT.

240V AC WESTCOOL SOLENOIDS
TT2 Mod 1 6at. 1 MAx stroke 1/4 in. Base mounting 1/2 in. stroke 5/8 in. pull approx. TT8 Mod 1 Rat. 2 MAx stroke 1/8 in. Front mounting 1/2 in. Front mounting 1/2 in. stroke 1/2 in. pull approx. Price incl. p&p & VAT TT2 £5.88. TT8 £6.81. SERIES 400 £7.64.

AXIAL COOLING FAN
230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan. Price £7.29 incl. P&P and VAT. Other voltages and sizes available from stock. Please telephone your enquiries.

INSTRUMENT CASE
Brand new Modul. by Intel 131 x 118 x 190mm deep. Removable front and rear panel for easy assembly of components. Grey finish complete with case feet. PRICE £18.45 INCL. P&P & VAT 2 off £23.50 inclusive.

SEWING MACHINE MOTOR
Brand new 220/240V A.C. DC SEW-TRC 2 lead Brush Motor. Size L. 100mm x H. 70mm x W. 55mm. Spindle 1/4 in. dia x 1 in. long. £14.10 incl. P&P & VAT

GEARED MOTORS
71 RPM 200 inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £27.73

SOLID STATE EHT UNIT
Input 230/240V AC. Output approx 15KV. Producing 0.1mm spark. Built-in 10 sec timer. Easily modified for 20sec, 30 sec to continuous. Designed for trailer ignition. Dozens of uses in the field of physics and electronics, eg supplying radio or argon tubes etc. Price inc case £25.50 + £2.40 p&p (£12.51 inc VAT) NMS

EPROM ERASURE KIT
Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Kit of parts test case includes 12m 8 watt 257 Argon Tube. Ballast unit, pair of high leads, note, indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£17.00 inc VAT)

WASHING MACHINE WATER PUMP
Brand new 240V AC fan cooled. Can be used for a variety of purposes. Incl. 1/2 in. outlet 1 in. dia. Price includes p&p & VAT. £11.20 each and for £20.50 inclusive.

TURN YOUR SURPLUS TRANSISTORS, ICs ETC INTO CASH immediate settlement.

We also welcome the opportunity to quote for complete factory clearance.

Colts
COLES-HARDING & CO
Unit 58, Queens Road, Wisbech, Cambs PE13 7PO
BUYERS OF SURPLUS INVENTORY
ESTABLISHED OVER 20 YEARS
Tel: 01945 584188 Fax: 01945 475216

£50 BT INSTRUMENT FOR ONLY £7.50

We refer to the BT isolation tester and multi meter with which you can read insulation directly in megohms. AC volts up to 230V 4 ranges of DC volts up to 500V. 3 ranges of milliohms and one SA range and 3 ranges of resistance. These are in perfect condition, have had very little use, if any, tested and fully guaranteed. Complete with leads and probes £7.50. Order Ref 7.374. Carrying case which will take small tools as well £2 extra. Postage £3 unless your order is £25 and over.
J. & H. Factors
Dept. ETI, Pilgrims Works, Stairbridge Lane, Boleyn, Sussex, RH17 5PA
Telephone: (01444) 831945

OSCILLOSCOPE, Tektronix TM504, 15MHz Dual Trace, modular, DMM and Counter Timer modules, complete with manuals, £225 ono, 01389 710425 weekdays or 01436 671366 after 6pm.

COURSES

RADIO + TELECOMMUNICATIONS CORRESPONDENCE SCHOOL

12 MOOR VIEW DRIVE, TEIGNMOUTH, DEVON, TQ14 9UN

START training NOW with the SPECIALISTS for the following courses. Radio Amateur Licence C+G. Micro Processor, Telecomms, Tech C+G and Introduction to Television.

For our FREE Brochures Call 01626 779398

SMARTCARDS

STAND ALONE PIC->PIC COPIERS AND BUSTERS.
Copy/Depict PIC Smart Cards (D2mac, adult etc) with the MAC2MAC copier, NO PC REQ. £69 PIC2PIC Copier (84, 67, 71) NO PC-REQ. £67 Multi PIC programmer (1620x) £37
MCJ DESIGN
Tel: 01202 770121
Fax: 01202 770121
E-MAIL: MCJDESIGN@AOL.COM

PRINTED CIRCUIT BOARDS

PRINTED CIRCUIT BOARDS Designed & Manufactured
● Prototype or Production Quantities
● Fast turnaround available
● PCBs Designed from circuit diagrams
● Almost all computer files accepted
Easy PC / Arma / YuTraX / Cadstar Gerber / HPGL / Draw and many others.
● Fast international service
● Contract Assembly & Test available
TELEPHONE 01232 473533
INTERNATIONAL +44 1232 473533
agar FAX 01232 473533
Circuits Email: agar@argonet.co.uk
35 WOODCOT AVENUE, BELFAST BT5 5JA

SOFTWARE

SMART CARD PRODUCTS Smartcards, Readers/Encoders, Evaluation & Development Kits...
http://www.gold.net/users/cf96/epsilon.htm
E-MAIL: epsilon@powertech.no
EPSILON ELECTRONICS
Brynsengvn.1A,
0667 Oslo, Norway
TEL/FAX +4722640810

ELECTRONIC VALVES

WILSON VALVES (PROP. JIM FISH G4MH)
Over 50,000 valves stocked.
2000 different types.
vintage, military, auto, etc.
Fast service. Send SAE for list
VALVES WANTED FOR CASH
28 Banks Avenue, Golcar, Huddersfield.
West Yorks HD7 4LZ
Tel: 01484 654650
Fax: 01484 655659

PLANS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue, SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

LIGHT ENGINEERING

LIGHT ENGINEERING SERVICES (PRECISION). Machining, sheet metalwork, instrument/toolmaking etc - most engineering processes in most materials. One offs, parts, prototypes, panels, mods, figs, repairs, anything - no job too small - trade or private - for quick friendly service contact - Richard - Tel/Fax 01954 260804

TRANSFORMERS

Variable Voltage Technology Ltd
TRANSFORMERS
For valve and transistor circuits
HT Filament chokes high & low voltage
Standard and custom design
large and small quantities
Unit 24E, Samuel Whites Estate, Medina Road, Cowes, Isle of Wight PO31 7LP
Tel 01983 280592 Fax 01983 280593

Around the Corner

At first sight, the news that the Federation of the Electronics Industry - the only trade association for the electronics industry recognised by the DTI - has compiled a survey of its members' opinions on education and training should be cause for rejoicing. A major Federation is acting upon a major concern - who can supply the excellent engineers that British industry needs?

But at once a note of scepticism comes leaping in. As one colleague put it, not long ago (he was, I must hasten to add, talking about a different survey): "Lots and lots of talking. What are they actually doing?" Old hands among you will have heard (or spoken) these words many, many times.

The note of scepticism is reinforced when we read that only 39 of the 250 companies canvassed actually returned a reply by the deadline. Is this apathy? Was the survey unreadable? Or is everyone just too busy doing electronics to spend time filling in surveys?

Let me now bring on the cheerleaders: 15 percent is not a bad response. It's quite common for surveys to return a response of 10% or even 2% to paper canvassing. And electronics companies really are too busy to fill in a yet another set of forms, unless they are very clear indeed about the advantage it will bring them. This is because prices have gone down, costs have gone up, and they cannot find all the technical staff they need. They tend to be understaffed. One of the values of this survey is that the shortage of good, trained people - that we are constantly hearing about anecdotally - is amply confirmed.

The second point of interest is the desire for employees with better "literacy and communications" skills. Clearly it is felt that technical people can do their maths up to the level required, but leave something to be desired when it comes to reading, writing and discussion. Now, by and large I do not find that the

technicians and engineers I have worked with are inarticulate, or dislike reading. Of course, on ETI, most of our writers are highly self-expressive, but even outside the "tech writing" world, engineers may not spend their leisure hours writing poetry, but they usually have plenty to say and know how they want to say it.

What we do find, however, is that the finer arts of persuasion and diplomacy tend to be out-competed by the admirable tendency to call a spade a spade, and the appreciation of what the outside world finds fascinating about a product or project can become buried under the admirable art of numbered report-writing and the finer points of circuitry.

Well, the last thing we want to see is any endeavour to strangle the technical person's ability to be technical - this is after all what makes them valuable. But we also note the respondents' appeal for much more management training - significant in a technical field.

The schism between "the technical boys" and "management" has become almost axiomatic - how sales people promise new developments and fast delivery dates without consulting the engineers ... deadlines are rushed, customers (and therefore managers) are disappointed ... projects linger for months and then have to be completed in a rush ... or work is suddenly shelved half way through because the management has changed its mind, leaving the technical departments dispirited and discontented.

Managers say that engineers don't understand how important it is to reach market before the competition. Engineers say that managers don't understand how difficult it is to develop a new process, or to test it sufficiently.

So it does seem that there is a crying need for engineers who understand management concerns, and management that thoroughly understands engineering. But is it the job of schools and colleges to bridge this gap? I'll come back to this next month.

The Challenge - Things that electronics hasn't fixed yet

This month I have to pass on a passionate cry from one of our colleagues: "PROBLEMS THAT ELECTRONICS HASN'T FIXED YET - why does my modem think it is sending stuff when it isn't?"

This is not the only modem that is sometimes economical with the truth about where the data has gone. Perhaps it needs a visit from a service engineer. Perhaps it needs to be monitored to find out where the connection breaks off. Perhaps the modem software isn't accurate enough in its send/receive reports. Or is it just possible that he needs to exploit the galloping pace of technical innovation and "fix it with a new one".

Next Month

In Volume 26, no. 2 of *Electronics Today International*, arriving at your newsagent in early February, Douglas Clarkeson Returns to Mars ... look out for Experimenting with Video (Part 2) ... Dr. Pei An has a Centronics Mini Data-Lab ready to operate ... Terry Balbirnie has been checking batteries quickly and neatly, and Robert Penfold has been seen checking out an RS232C port. Mike Rhodes has found a new way of not only counting his strides, but calculating exactly how far he has walked. And more ...



EDITORIAL

Editor **Helen Armstrong**
Editorial Assistant **Lynn Bugden**
Consultant **Andrew Armstrong**

CREATIVE

Designer **Dan Sturges**
Technical Illustration **John Puczynski**
Photography **Gary Sinfield**

ADVERTISEMENT SALES

Advertisement Manager
Andrew Forder
Advertisement Copy Control
Marie Quilter

MANAGEMENT

Divisional Director
John Bridges
Production Manager
Mike Burns
Production Administrator
Theresa Davis
Business Manager
Stuart Cook
Marketing Manager
Jason Doran
Copy Sales Manager
David Pagendam



ISSN0142-7229

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Nexus Special Interests. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Nexus Special Interests and reproduction requires the prior written consent of the company c1996 Nexus Special Interests. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription rates-UK £24.75 Europe £37.10 Sterling Overseas £38.60 US Dollars Overseas \$59.00. (Air £41.80 or \$66.00.)

Published by Nexus Special Interests, Nexus House, Boundary Way, Hemel Hempstead HP2 7ST. Telephone (01442) 66551. UK newstrade distribution by Comag Magazine Marketing, Tavistock Road, West Drayton, Middlesex, UB770E. Overseas and non-newstrade sales by Magazine Sales Department, Nexus House, Boundary Way, Hemel Hempstead, HP2 7ST. Telephone (01442) 66551. Facsimile (01442) 66928. Subscriptions by Nexus Subscription Dept, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leicestershire, LE16 9EF. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. For Visa/Mastercard orders in USA - Telephone (310) 375 6258 Fax (310) 375 0543. Pacific Time: 9am-5pm Weekdays, 10am-6pm Weekends. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd, Bristol.

Nexus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (01442) 66551
Fax (01442) 66998

Get the best Universal Diagnostic tool kit on the market

**SOFTWARE
& HARDWARE
THAT REALLY
WORKS!**

Micro-Scope 6.1

UNIVERSAL DIAGNOSTIC SOFTWARE

Fully O/S independent diagnostic software

Post-Probe

Flat Error Universal P.O.S.T. Card for All PCs!

Use this Power-On-Self-test card to debug any "dead" PC that won't boot



Our servicing turn-around time has been reduced by an average of 32%. Of all the diagnostic packages tried this is the first to live up to its advertising.
Solsoft SW

We have been using Microscope and Postprobe for two months with great success. It really is as good as you have said in your publicity.

Cardiff Wales Airport.

I have spoken to our engineers about the Micro 2000 software/hardware package and received favourable reports. They say the best advantage Micro 2000 has over other packages is the fact that it is operating system independent.

Digital.

To be truthful we at Catalyst use Micro-Scope on every machine when it "walks" in or out of the door of the office.

Catalyst Computer Systems

Micro-Scope BURN-IN™

A proven way to increase quality control



Micro-Scope CLIENT™

A must-have Remote Diagnostics Tool



Micro-Scope CENSUS™

Lets you keep track of hundreds or even thousand of computers

NEW RELEASES

Call about our Tutorial and Troubleshooting Series on video cassettes! A wealth of technical help at your fingertips.

MICRO 2000



United Kingdom

Tel: +44 1462 483483
Fax: +44 1462 481484



Netherlands & France

Tel: (+31) 020 638 4433
Fax: (+31) 020 620 3437



Germany

Tel: (+49) 069 420 8278
Fax: (+49) 069 420 8270



Spain

OPEN JUNE/JULY
Call UK for details.

OLSON

®

For all your Power Distribution
Olson offer a varied choice

OLSON Distribution Units

OLSON ELECTRONICS LIMITED

OLSON DISTRIBUTION PANELS
FUSED, WITH R.F. FILTER
AND R.O.D. PROTECTION

OLSON ELECTRONICS LIMITED

OLSON FUSED WITH RCD
PROTECTION
AND DOUBLE POLY
SWITCHED SOCKETS

OLSON ELECTRONICS LIMITED

OLSON 'The Rack Range'
mains distribution panels
for 19" rack mounting

OLSON ELECTRONICS LIMITED

OLSON OFFICE FURNITURE
CABLE MANAGEMENT

OLSON ELECTRONICS LIMITED

OLSON Mains Distribution
Panels with
Non Standard Sockets

OLSON ELECTRONICS LIMITED

OLSON FUSED SUPER-SLIM
MAINS DISTRIBUTION PANELS
WITH DOUBLE POLY
SWITCHED SOCKETS

OLSON ELECTRONICS LIMITED

OLSON STRIPBLOC

OLSON ELECTRONICS LIMITED

OLSON DISTRIBUTION
UNITS

OLSON ELECTRONICS LIMITED

OLSON PANELS WITH 16AMP
GREEN/RED
SHATTERED SOCKETS
FUSED, DOUBLE POLY SW
RCD AND R.O.D. PROTECTION

OLSON ELECTRONICS LIMITED

OLSON 'The Rack Range'
WITH AMERICAN
ROCKERS 20-250V-15A

OLSON ELECTRONICS LIMITED

OLSON Mains Distribution
Panels
INTERNATIONAL RANGE

OLSON ELECTRONICS LIMITED

OLSON FUSED SUPER-SLIM
MAINS DISTRIBUTION PANELS
WITH DOUBLE POLY
SWITCHED SOCKETS
RCD AND R.O.D. PROTECTION

OLSON ELECTRONICS LIMITED

OLSON DATA PROTECTOR

OLSON ELECTRONICS LIMITED

OLSON DISTRIBUTION PANELS
WITH IEC 320 SOCKETS
INDIVIDUALLY FUSED

OLSON ELECTRONICS LIMITED

OLSON Distribution
Units

OLSON ELECTRONICS LIMITED

OLSON DISTRIBUTION PANELS
CABLES TO THE LEFT
CABLES TO THE RIGHT

OLSON ELECTRONICS LIMITED

OLSON 'The Rack Range'
GREEN/RED
SOCKETS

OLSON ELECTRONICS LIMITED

OLSON SERVICE PILLAR FOR
THE OPEN-PLAN OFFICE

OLSON ELECTRONICS LIMITED

OLSON Distribution
Units

OLSON ELECTRONICS LIMITED