DIGTAL SIGNAL PROCESSING

RIDE THE DIGITAL WAVE OF THE FUTURE

ELECTRONICS TODAY INTERNATIONAL

# TOTAL HARMONIC DISTORTION METER HIGH QUALITY NOTCH FILTER AND

AUDIO MILLI-VOLTMETER

# PLUS

GCSE GROUNDING: SOUND SWITCHER TUNEFUL TRIFLE ALPHANUMERIC MORSE TOUCHKEY AUDIBLE AND VISUAL LOW VOLTAGE TESTING AROUND THE HOME AND CAR

**313** 



Vol 26 Issue: || |0 October 1997 £2.50 USA \$4.95





# **The Autumn Collection**



Programmable Logic is one of the fastest growing areas in the Electronics Industry. This system allows you to both learn about PLDs (Programmable Logic Devices) and to implement them in practical projects. It comes complete with a Programmer (Capable of programming 16V8, 20V8 and 22V10 devices), a training module, a stand alone training course and a free copy of the industry standard CUPL for Windows, plus a Flash based device that can be reprogrammed 100s of times.



Assembler, Simulator, Book, Programmers (In System and Standalone) - All you need to give this new micro a try.

Serial EEPROMs are found in virtually every piece of programmable equipment made. From televisions, VCRs, Burglar Alarms, Mobile Phones and Microwave ovens right through to Aircraft. Worldwide over £2 Billion are sold every year and they are manufactured by over 20 companies. This, low cost, system allows you to both experiment with and implement these devices. The system allows the user to program all the popular versions including the 24, 25, 59, 93 and 17C series, both in system and standalone. The kit comprises a programming lead, programming module, Windows programming software (with integrated Hex and ASCII editors) and a comprehensive reference manual.





C is rapidly becoming the language of choice for embedded systems programming. We can now offer the professional C compiler from IAR (The acknowledged Industry Leaders) for most micros e.g. AVR Compiler = £450. Please contact us for full details. Free working Demo available on request. A full Residential Training Course is also available, ideal for INSET or enhancing your job prospects.



We have a range of low cost In Circuit Emulators (I.C.E) and development Systems available for the 51, PIC and (shortly) the AVR. Please call for details.

Switch Waster and VISA

Prices do not include VAT

Microcontroller Training Systems for PIC, AVR or 51 series micros. Includes full coursework, Hardware and Software neatly bound into an A4 Ringbinder. Starts from basics and goes step by step through to project design. A full review of this product is available in Everyday and Practical Electronics.

Introduction to the AVR book. Written by a Lecturer, this book is the perfect introduction, not only to the AVR microcontroller, but also to microcontrollers in general. Includes Official Software. Only £18.





Pendre-Hafod, Pontrhydygroes, Ystrad Meurig, Ceredigion, SY25 6DX Tel: 01974 282670 Fax: 01974 282356 Email: sales@kanda-systems.com. Website: www.kanda-systems.com

Kanda Products are also available from Maplin, Rapid Electronics and Farnell



# Volume 26 No.11



# Next issue 7th November 1997







# Regulars

News PCB foils ETI PCB Service Round the Corner

# **Digital Signal Processing**

Now used in modems, amateur radio equipment, high-end sound equipment, and in many of the fastest-developing areas of electronics, DSP is becoming more accessible and certainly more necessary to electronic design.

# Fast Fivers - A Tuneful Trifle

Would you like some light music? You can produce your own With this little light-controlled tone generator, you can make music to fit the mood with a light-dependent resistor.

# **GCSE Grounding: Sound Switcher**

Terry Balbirnie starts a series of adaptable circuits which can be incorporated or adapted for GCSE- and other projects. In this issue: a module to trigger a reaction when a sound is made.

# Alphanumeric Morse Touchkey

The Alphanumeric Morse Touchkey is designed to enable beginners learning Morse to become familiar with the dot-dash codes and their rhythmic patterns without the aid of an instructor.

# The MKII Electronic Auto-Checker

Tim Parker's original ETI Multi-checker now has a 'voice' to tell you what's going on when you are upside-down under an instrument panel, along with improved functions and straightforward one-pushbutton operation.

# Total Harmonic Distortion Meter

25

13

41

55

61

33

Robert Penfold's Total Harmonic Distortion (THD) Meter has a good quality notch filter and an audio millivoltmeter.

# Computer Radio Control for Home Automation Part 2 45

Dr. Pei An describes the Radio Mains Control System interfaces to control up to 1024 mains outlets via up to 256 radio receivers and a transmitter connected to the Centronics port.



# 3



K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE, SOUTHWAY, WEMBLEY, MIDDLESEX, ENGLAND HA9 0HB Telephone: 0181-900 2329 Fax: 0181-903 6126 OPEN Monday to Saturday. Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00 HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR LARGE QUANTITIES Please send £1 P&P and VAT at 17.5%. Govt, Colleges, etc. Orders accepted. Please allow 7 days for delivery. Prices quoted are subject to stock availability and may be changed without notice. TV and video parts sold are replacement parts. Access & Visa Card accepted WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND TDA SERIES. PLEASE RING US FOR FURTHER INFORMATION.

		TRANS	SISTORS		
PART         PRICE           AC125         30P           AC126         30P           AC127         30P           AC127         30P           AC128K         40P           AC141K         45P           AC176         22P           ACY18         48p           AD149         60P           ACY17         48p           AD149         60P           AC127         8P           BC100         8P           BC1010         8P           BC111         8P           BC160         8P           BC1610         8P           BC177         14P           BC177         14P           BC178         14P           BC179         14P           BC180         7P           BC181         7P           BC182         7P           BC184         7P           BC182         7P           BC212         7P           BC213         7P           BC214         7P           BC214         7P           BC230         20P           BC311	PART         PRICE           BD647         SOP           BD675         40P           BD676         40P           BD677         38P           BD678         40P           BD680         40P           BD681         45P           BD705         SOPP           BD707         SOP           BD707         SOP           BD707         SOP           BD733         SOP           BD828         SOP           BD829         SOP           BD731         SOP           BD733         SOP           BD827         SOP           BD733         SOP           BD7447         7SP           BDX47         TSP           BDX42         TSP           BDX4	PART         PRICE           BU419         85P           BU412         175P           BU413         175P           BU4146         250P           BU300         100P           BU300         100P           BU500         225P           BU500         225P           BU505         90P           BU505D         90P           BU505D         90P           BU506         100P           BU506         100P           BU5061         120P           BU5062         70P           BU5064         130P           BU5065         130P           BU5061         120P           BU5363         125P           BU6061         120P           BU5364         120P           BU5365         130P           BU70667         175P           BU70667         175P           BU70667         175P           BU8076         100P           BU824         450P           BU8252         100P           BU8263         120P           BU8264         120P           BU8265 <t< td=""><td>PART         PRICE           BUX84A         150P           BUX80         180P           BUX81         160P           BUX85         50P           BUX86         30P           BUX87         50P           BUX86         30P           BUX87         50P           BUX87         150P           BUY47         150P           BUY47         150P           BUY11         200P           BUZ10         65P           BUZ11         200P           BUZ20         225P           BUZ21         250P           BUZ21         250P           BUZ21         250P           BUZ21         200P           BUZ33         800P           BUZ71AF         100P           BUZ72AF         100P           BUZ73A         100P           BUZ80         200P           BU281         40P           BY111         25P           C0Y80         40P           IRF130         475P           IRF130         550P           IRF230         550P           IRF230         550P     &lt;</td><td>PART         PRICE           MPSA43         15P           MPSA43         15P           MPSA43         15P           MPSA44         40P           MPSA55         12P           MPSA56         12P           MPSA55         12P           MPSA56         12P           MPSA33         20P           MPSA33         20P           MPSU60         350P           MPSU66         400P           MPSU66         360P           OC28         250P           OC36         250P           OC36         250P           OC36         250P           OC36         250P           OC36         25P           TIP20         15P           TIP20         25P           TIP31A         22P           TIP23C         24P           TIP33C         26P           TIP33C         65P</td><td>PART         PRICE           2N3553         100P           2N3553         100P           2N3702         9P           2N3703         9P           2N3705         9P           2N3706         9P           2N3710         12P           2N3711         12P           2N3710         12P           2N3711         12P           2N3722         150P           2N3792         150P           2N3793         100P           2N3793         10P           2N3793         10P           2N3933         11P           2N3936         375P           2N4393         25P           2N4393         25P           2N4393         25P           2N4393         25P           2N4393         25P           2N4403         12P           2N4420         75P</td></t<>	PART         PRICE           BUX84A         150P           BUX80         180P           BUX81         160P           BUX85         50P           BUX86         30P           BUX87         50P           BUX86         30P           BUX87         50P           BUX87         150P           BUY47         150P           BUY47         150P           BUY11         200P           BUZ10         65P           BUZ11         200P           BUZ20         225P           BUZ21         250P           BUZ21         250P           BUZ21         250P           BUZ21         200P           BUZ33         800P           BUZ71AF         100P           BUZ72AF         100P           BUZ73A         100P           BUZ80         200P           BU281         40P           BY111         25P           C0Y80         40P           IRF130         475P           IRF130         550P           IRF230         550P           IRF230         550P     <	PART         PRICE           MPSA43         15P           MPSA43         15P           MPSA43         15P           MPSA44         40P           MPSA55         12P           MPSA56         12P           MPSA55         12P           MPSA56         12P           MPSA33         20P           MPSA33         20P           MPSU60         350P           MPSU66         400P           MPSU66         360P           OC28         250P           OC36         250P           OC36         250P           OC36         250P           OC36         250P           OC36         25P           TIP20         15P           TIP20         25P           TIP31A         22P           TIP23C         24P           TIP33C         26P           TIP33C         65P	PART         PRICE           2N3553         100P           2N3553         100P           2N3702         9P           2N3703         9P           2N3705         9P           2N3706         9P           2N3710         12P           2N3711         12P           2N3710         12P           2N3711         12P           2N3722         150P           2N3792         150P           2N3793         100P           2N3793         10P           2N3793         10P           2N3933         11P           2N3936         375P           2N4393         25P           2N4393         25P           2N4393         25P           2N4393         25P           2N4393         25P           2N4403         12P           2N4420         75P

الأرجاب والمتعاور والملار	S	ATELLITE	POWER	SUPPLY	REPAIR	KITS	Contraction of the	
AND A STATE OF A STATE	CODE	ECHOSTAR			CODE			
SAT660	SATPSU2	SR5500 EAF 6500, SR770	RLY PSU WIT 00, SR8700	H ADJ	SATPSU12 SATPSU13			
AMSTRAD SRD510, SRD520, SRD540, SRD550	), SRD550 SATPSU3 FERGUSON		CODE	9000, 9200	SATPSU2			
SRDR45 SRD500	SATPSU4		SRD 5, SRD16			NOKIA	CODE	
SRX320, SRX340, SRX345, SRX350 SATPSU5		SRDE4			SATPSU2 SATPSU11	SAT1500	SATPSU2	
SRX100 SRD600	SATPSU6 SATPSU14	FINLUX		1018W 200	CODE	PACE	CODE	
SAT250, SR950, SRD700, SRD950, SRX1002, SRX2001, SRX301,	SATPSU16	SR5700		_	SATPSU12	PRD800, PRD900, PSR800, MRD920, SS9000, SS9010,		
SRX501, SRX502	OATDOUMO	GOODMAN	S	CIT - Watter	CODE SATPSU1	SS9210, SS9220		
SRD2000	SATPSU18	ST700			SAIPSUI	D100, D150, MSS100	SATPSU6 SATPSU8	
BRITISH TELECOM	CODE	CRUNDIG	and the second		CODE	APOLLO, MSS200, MSS300 MSS500, MSS1000	SATPSU9	
SVS300	SATPSU17	STR1 GIRD200, FI	IBD3000		SATPSU1 SATPSU2	PHILIPS	CODE	
BUSH	CODE				-	STU802/05M	SATPSU1 SATPSU2	
IRD150 IRD155	SATPSU12 SATPSU19		N	and the second	SATPSU1			
		MASPRO		AND NO.	CODE	SRS4	SATPSU2	
CHURCHIL	SATPSU7	SRE250S/1,	, SRE350S/1 SRE350S, SRI	E4508	SATPSU1 SATPSU2		CODE	
D3MAC DECODER	J SAIPSU/	SHE2505, 3	5RE3303, 3RI	_4303	SAIFSUZ	SAT99, TU-SDU200	SATPSU1	
CODE	PRICE CO		PRICE	CODE	and the second s	RICE CODE PRIC		
SATPSU1 ISATPSU2		FPSU6 FPSU7	650p 650p	SATPSU1 SATPSU1		835p SATPSU16 73 735p SATPSU17 85		
SATPSU3 SATPSU4	650p SAT	TPSU8 TPSU9	730p 900p	SATPSU1 SATPSU1		3125p         SATPSU18         117           3135p         SATPSU19         65		
SATPSU4 SATPSU5		IPSU10	1230p	SATPSU1		77.5p	50	
PACE SATE		NERS			PACE SV	VITCH MODE TRANSI	ORMERS	
MODELS		CODE	PRICE	MODEL			CODE PRICE	
PRD800, MSS200 (2GHZ) (221-2077) PRD900, MSS500, MSS1000 (2Ghz)	062)	TUNER01 TUNER02	1650p 1650p	PACE90	00 ID800, PRD9	00	PACE9000 800p PRD800 550p	
PRD900, M33500, M331000 (2012)	(221-21/1012)	TONLINZ	L	METER	10000,11100			
MAX.INPUT SIGNAL: -10 DBM MAKE A MODEL Cambridge AE22/AE5 0.8dB standard 10.95 Cambridge AE14 Universal LNB 10.7-11.7/1 Cambridge AE19/AE5 Single O/P Switching Cambridge AE23/AE12 0.8dB Enhanced 10	-II.70 GHz Gold F 1.7-12.75 GHz LNB 1.0dB Stand LNB 1.0dB Enha 7-11.8GHz Gold	dard LNB2 nced LNB3 Range LNB5	SATELLI 2160p 2500p 2050p 2050p 2050p 2160p	Cambridge A Cambridge A Grundig Sup Grundig Sup	AE7 Twin O/P H AE2 Dual O/P H per Universal 'An versal 'Anis' 10.7		ORDER CODE         PRIO           LNB7         4000;           LNB8         3550;           LNB9         2600;           LNB10         2250;           LNB11         4000;	
Cambridge AE8 Dual O/P H-V Separate Ent	nanced	LNB6	4000p	050	-			
				SES				
TIME LAG		the same is not save the	(BLOW () R CODE	PRICE	CHODE	CERAMIC PLUG		
100mA FUSE36	5 75	5p FUS	SE37	60P	3A	FUSE33	100p	
160mA FUSE01 250mA FUSE02			SE17 SE18	60p 60p	5A 13A	FUSE34 FUSE35	100p 100p	
315mA FUSE03	3 75	5p FUS	SE19	60p				
400mA FUSE04 500mA FUSE05			SE20 SE21	60p 60p	CHERRE	20mm CERAMIC TIM		
630mA FUSE06			SE22	60p	6.3A	FUSE38	100p	
800mA FUSE07			SE23 SE24	60p	8A 10A	FUSE39 FUSE40	100p 100p	
IA FUSE08 1.25A FUSE08	1		SE25	60p 60p	3.15A	FUSE41	85p	
1.6A FUSE10	60	Op FUS	SE26	60p	4A 5A	FUSE42 FUSE43	85p 85p	
2A FUSE11 2.5A FUSE12			SE27 SE28	60p 60p		100240	000	
3.15A FUSE13	3 55	5p FUS	SE29	50p		38mm CERAMIC TIM		
4A FUSE14 5A FUSE15			SE30 SE31	50p 50p	10A	NT RATING ORDER COD	815P	
6.3A FUSE16			SE32	50p				
NB.						2mm CERAMIC SLO		
ALL FUSES ARE MADE	IN THE U	K AND FU	LLY MEE	т	8A	FUSE44	185P	
BS4265 & BS1362 SAFET					10A 15A	FUSE45 FUSE46	185p 185p	
BE COMPARED WITH CH		ORTED TY	PES.		20A	FUSE47	210p	
	BOVE					KS OF 10 FUS	EC**	
					TAU			

					TRANS	ISTORS					
	RICE		RICE	PART	PRICE	PART	PRICE	PART	PRICE	PART	PRIC
I.C. SOCKETS		1A/50V W01	18p	TIC116C 8A/300V	Seb	8150 8224	300p 240p	4075 4076	13 42		
PIN	AP	1A/100V		TIC116D	70p	8226	240p	4077	13	7438	
PIN	4P 5P	WO2 1A/200V	<b>1</b> 9p	8A/400V TIC126D	75p	8250 8251	750p 200p	4078	13		
PIN	6P	W04	21p	12A/400V	1 ah	8253	160p	4081 4082	13		
PIN	9P	LA/400V		TIC126M	90p	8257	220p	4085	36	7451	
PIN	10P 12P	W06 LA/600V	23p	12A/600V C106D		8271	340p	4086	30	7454	
PIN	13P	W08	28p	4A/400V	28p	8279 8283	270p 400p	4089 4093	75		
PIN	13P	1A/800V		BR103	37p	8284	440p	4094	44	7482	
PIN	15P	BR81D 2A/100V	33p	BR303 BT106	85p	8287	260p	4094	58	7485	
NER		BR82D	33p	BT119	180p 100p	8288 82C206PLCC	650p 500p	4098 4099	50 42		
DDES		2A/200V		17088	200p	8748	700p	4501	26	7495	
m	WATT	BR84D 2A/400V	37p	17089	200p	8755 8T26	800p	4502	36	74132	
TO 39V	5P	BR86D	43p	15/80H	200p 230p	8T28	95p 110p	4504 4505	35	74141 74145	
	WATT	2A/600V		15/85R	230p			4506	58	74157	
7 TO 39V	9P	BR88D 2A/800V	43p	SG 264 SG613	800p 1500p	CMOS IC	s	4507	30	74160	
VOLTAGE		BR32	43p	00010	raoop	4000	13p	4508 4510	671		HC SERIES
REGULATORS		2A/200V		COMPUTER	IC's	4001	13p	4511	30		ING DENIED
)5	25P	BR34 2A/400V	43p	Z80ACPU	100p	4002 4006	13p	4512 4514	38	74HC03	
6	25P	BR36	44p	Z80ADMA	200p	4006	34p 13p	4514	65		
8	25P 25P	2A/600V		ZBOACTC	140p	4009	20p	4516	36	74HC11	
5	25P	BR62 6a/200V	80p	Z80ASIO-1 Z80ASIO-2	210p 210p	4010	21p 13p	4517 4518	100		
8	25P	BR64	72p	75107	650	4012	130	4519	36r 28r	74HC20 74HC27	
4 5	25P 25P	6A/400V BR251		75110	75p	4013	19p	4520	36	74HC51	
6	25P 30P	25A/100V	150p	75113 75122	100p 110p	4014 4016	32p 18p	4521 4526	86r 38r		
8	30P	BR252	165p	75154	100p	4018	30p	4527	41		
2 5	30P 30P	24A/200V BR254	185p	75162	700p	4019	28p	4528	380	74HC77	
8	30P	25A/400V	leop	75183	95p 95p	4020 4021	33p 36p	4529 4532	65 48		
24	30P	BR2156	200p	75195	185p	4022	36p	4553	140	74HC107	
_05 _08	24P 24P	25A/600V BR258	240p	2114 2532	150p	4023 4024	13p 25p	4555	29	74HC123	
.12	24P	25A/800V	240p	26LS32	200p 75p	4025	25p 13p	4556 4557	36r 140r		
-15	24P	BR351	185p	2716	100p	4026	60p	4583	600	74HC132	
_18 _24	24P 24P	35V/100V BR352	200p	2732 2732A	200p 220p	4027 4028	18p 29p	4584	30r	74HC133	
_05	35P	35V/200V	LOOP	2764	150p	4029	34p	40103	40r 120r	74HC137 74HC138	
.08	35P	BR354	220p	27C64	200p	4030	17p	40105	140	74HC147	
12 15	35P 35P	35V/400V BR356	230p	27128 27256-25	150p 150p	4032 4033	52p 60p	40106 40107	35¢ 50¢	74HC153 74HC154	
309K	100P	35V/600V		27512	300p	4034	76p	40110	1700		
31 <b>7T</b> 323K	100P 350P	BR358 35V/800V	260p	4116 4164-15	40p	4035	42p	40114	180	74HC158	
09KC	800P	BY164	40p	4164-12	80p 90p	4038 4040	46p 30p	40160 40161	550	74HC160 74HC161	
12KC	700P	1.5A/100V		41256-15	80p	4041	36p	40174	480	74HC162	
IGKC	800P	BY176 1.5A/800V	40p	41256-12 41256-10	100p 110p	4042 4043	30p 36p	40192 40193	48r 48r	74HC163 74HC164	
L.E.D.'s 3mm				41464-12	150p	4045	72p	40194	40, 58¢		
)	5p	TRIACS		6116 6264-10	80p 210p	4046 4047	42p 45p	40257	120	74HC166	
LOW	8p	TIC206D	60p	62256-12	210p 300p	4048	45p 26p		74 SERIES	74HC174 74HC175	
EN	8p	4A/400V		6502A	360p	4049	18p			74HC190	
n		TIC225D 6A/400V	69p	65C02 6522	930p 280p	4050 4051	20p 38p	7400 7401	20p 16p		
	5p	TIC226D	68p	6800	210p	4052	35p	7402	18		
LOW	8p	8A/400V		6802 6803	2200	4053	35p	7403	200	·74HC195	
EIN	8p	TIC235D 12A/400V	85p	6803 6808	500p 500p	4054 4055	53p 52p	7404 7405	35p 10p	74HC221 74HC238	
RECTANGULAR		TIC246D	105p	6809	500p	4056	52p	7406	30p	74HC240	
LED's		16A/400V	400-	6810	150p	4060	40p	7407	300	74HC241	
n x 2.5mm		TIC253D 20A/400V	190p	6818 6821	380p 130p	4063 4066	52p 20p	7408	25r 20r	74HC242 74HC243	
	5p	TIC263D	205p	6840	2900	4067	120p	7413	30p	74HC245	
LOW	8p	25A/400V		6845 6850	200p	4068	13p	7414	450	74HC251	
	8p	THYRISTORS		74F244	90p 35p	4069	13p 13p	7416	32c 32c		
BRIDGE			- 0	8085A	300p	4071	13p	7420	20p	74HC273	
RECTIFIER 05	16p	2N5061 0.8A/60V	20p	8086	500p 480p	4072	13p 13p	7421 7425	25p 15p	74HC280 74HC283	
	100	0.0.7001		1	4000		1.00		1.91	14110203	

# SERVICE AIDS

DESCRIPTION	VOLUME	CODE	PRICE	DESCRIPTION	VOLUME	CODE	PRICE
VIDEO HEAD CLEANER	75ML	SP01	180p	EXCEL POLISH 80	250ML	SP18	150p
VIDEO HEAD CLEANER	200ML	SP27	250p	ADHESIVE 120	400ML	SP19	190p
SWITCH CLEANER	176ML	SP02	180p	LABEL REMOVER 130	200ML	SP20	240p
SUPER 40	400ML	SP15	250p	REFURB 140	400ML	SP21	240p
SILICONE GREASE	200ML	SP03	210p	TUBE SILICON GREASE	50 GRAMMES	SP11	220p
FREEZE IT	170ML	SP04	320p	TUBE TUBE SILICON		1.1	
FREEZE IT	400ML	SP16	600p	SEALANT WHITE	75ML	SP22	280p
FOAM CLEANER	400ML	SP05	200p	TUBE SILICON SEALANT			
ANTI STATIC	200ML	SP06	190p	CLEAR	75ML	SP23	280p
AEROKLEANE	200ML	SP07	220p	TUBE HEAT SINK COMPUND	25 GRAMMES	SP12	150p
AERO DUSTER	150ML	SP08	310p	DRIVE CLEANER	200ML	SP24	150P
AERO DUSTER	400ML	SP17	550p	SCREEN CLEANER	200ML	SP25	150p
PLASTIC SEAL	200ML	SP09	250p	COMPUTER CARE KIT	N 10-	SP26	2100p
GLASS CLEANER	250ML	SP10	160p	ANTI STATIC FOAM CLEANER	400ML	SP28	175p
COLDKLENE	250ML	SP13	230p	AIR DUSTER	400ML	SP29	450p

# ALL THE ABOVE ITEMS ARE MANUFACTURED BY SERVISOL

IF YOU PURCHASE MORE THAN ONE SERVISOL PRODUCT POSTAGE & PACKING WILL BE CHARGED AS FOLLOWS: 300P FOR 5 CANS

SUUP TOR S CANS

450p FOR MORE THAN 5 CANS

**GRANDATA LTD** K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE, SOUTHWAY, WEMBLEY, MIDDLESEX, ENGLAND HA9 0HB Telephone: 0181-900 2329 Fax: 0181-903 6126 OPEN Monday to Saturday. Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00 PLEASE PHONE US FOR TYPE NOT LISTED HERE AS WE ARE HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR LARGE QUANTITIES Please send £1 P&P and VAT at 17.5%. Govt, Colleges, etc. Orders accepted. Please allow 7 days for delivery. Prices quoted are subject to stock availability and may be changed without notice. TV and video parts sold are replacement parts. Access & Visa Card accepted WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND TDA SERIES. PLEASE RING US FOR FURTHER INFORMATION.



# **OVERSEAS READERS**

To call UK telephone numbers, replace the initial 0 with your local overseas access code plus the digits 44.



Ivex Design International's WinDraft CAD package for Windows will now have the capability to act as a "schematic viewer" and view any size of sheet. The facility applies to all versions, including the 100pin capacity shareware version.

WinDraft's view mode is analogous to Microsoft's Word 6 viewer, and allows the user to view a document without having to purchase a "full" version of the software. According to Ivex, WinDraft V1.26 will give engineers the ability to distribute schematics freely in a standardised

# Update to WinDraft for schematic design

format, including over the Internet.

Features available with V1.26 include the ability to view any size of sheet created with a licensed copy of WinDraft Schematics; added printing functionality to allow x and y offsets in the print dialog box; user definable attribute fields to include in the Bill of Materials (the user can include information such as the module name, part stock number or any other attribute); an improved Library Editor to allow easier pin mobility when creating or editing parts and changed configuration to speed up use; added default module footprints of hundreds of additional parts to facilitate PCB layout; user-request to view pin numbers on power pins; revised Getting Started Guide which includes netlist information and important PCB layout information; revised on-line Help with up to date

information.

WinDraft is the ideal front end for WinBoard PCB layout software. Prices range from £19.95 (including VAT) to £350 plus VAT, depending on the pin capacity. Version 1.26 is a free upgrade to existing customers.

A free shareware version of both WinDraft and WinBoard can be obtained from the Web at http://www.ivex.com by downloading wdshare.exe and wbshare.exe on the anonymous FTP service. These shareware versions are complete, fully functional programs with an 100pin/pad limitation, and will now view any size of schematic.

For more information contact The PC Solution, 2a High Road, Leyton, London E15 2BP. Tel 0181 926 1161 Fax 0181 926 1160 email: info@The PCSol.Demon.co.uk.

# Shorts

Author Bill Davies has produced a substantial first volume in a series covering all areas of applied robotics, Practical Robotics. For information about the contents, price, delivery costs etc. please contact the author at WERD Technology Inc., Unit 35B, Suite 155, 10520 Yonge St., Richman Hill, Ontario L4C 3C7, Canada. Information may also be available from CPIC Technical Books email cpic@idirect.com

The Federation of Electronics Industry has appointed a new President for 1997-1998, Barry Wood, chairman and MD of Celab Ltd., specialists in power conversion for defence, telecomms and cable TV. Speaking to the FEI annual dinner, Barry Wood said, "Well over 80 percent of the 50,000 companies in the electronics and related industries employ less than 20 people and over 95 percent less than 200 people. Successful partnerships between large and small enterprises are crucial to the economic success of national and European industry. Without innovative and flexible small firsm the industry will not prosper." IT, electronics and telecommunications is set to represent 10 percent of all

# Yes, There are 5 prizes to win!

But no prizes for spotting that we only printed one question last month, instead of the three questions needed to enter our RD Research/B2Sprice competition. Technical details: it was right when it left our end of the phone lines, and different when it came out at the other end, burying the all-important questions under the answer coupon.

The three questions are:

Question 1 What is the latest SPICE ENGINE used in B2 Spice V2?

Question 2: Which university developed it? Question 3: What does SPICE stand for?

The competition is open to purchasers of ETI Issue 10 1997 (last month's issue) who are not empolyees of Nexus Special Interest Ltd. or RD Research. Please send your entries on the coupon in Issue 10, or a neat copy of it, to: Spice Competition, ETI Magazine, Nexus Special Interests, Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST. Terms are as published in ETI issue 10 1997, and the final date for entries has been extended to October 30th 1997.

# **B<sup>2</sup> Spice &** Not Just a Pretty Interface **B<sup>2</sup> Logic**

 Design and test analogue and digital circuits quickly and easily

£199

- Incorporates a dedicated model editing package
- Fast 32 bit SPICE 3F5 engine
- Windows 3.1/95/NT
- Mac version also available
- CD ROM or 3.5" disk

## Fully Integrated and Interactive Build the circuit on the screen and set up the

Build the circuit on the screen and set up the simulations by choosing options from menus and dialogues. Then run the simulation and view your results.

# Flexible Visualisationof Results

In B<sup>2</sup> Spice results can be displayed in graphs, tables or directly in voltmeters and ammeters. Change from typical to worst case analysis and include the effects of temperature on components. You can customise everything, right down to the colour of an individual trace so you see just what you need. B Spice and B<sup>2</sup> Logic let you export data to other applications.

# Versatility

A plethora of components include resistors, capacitors, inductors, mutual inductors / transformers, controlled sources, bipolar junction transistors, zener diodes, power MESFETS, JFETS, MOSFETS, voltage regulators, operational amplifiers, optocouplers, voltage comparators, quartz crystals, IBIS I/O buffers and switching matrix connectors and much more *All devices and model parameters can be edited to suit your needs*. Implement hierarchical circuits in your designs quickly and easily

# No Limits

With B<sup>2</sup>Spice and B<sup>2</sup> Logic there is no limit on the number of components in the circuit.

# Models

There are literally thousands of them... The complete Berkeley SPICE model library as well as commercial libraries from manufacturers such as. Motorola, Texas Instruments, Burr-Brown, Maxim, National Semi, APEX Comlinear, AMP, Elantec, Linear Tech, and many more. Included with BSpice is a full model and symbol editing package so you can create. Import and edit custom models.

# Commands

B<sup>2</sup> Spice supports AC frequency sweep. DC operating point, transient analysis, fast founer Noise, sensitivity distortion, Tf small signal transfer.

# Simulation Options

Added facility for sub-circuits (macro-models). You can set all simulation options. Allows you to set initial conditions at all nodes. Allows you to set initial guess at nodes for simulation.

Allows "not given" state for all values

# Total Control

B<sup>2</sup> Spice gives full access to Berkeley SPICE simulation control options. For example you can set global defaults for transistor channel lengths and widths! Plus much more.

AQ 2

ROM 255KG ROM 255KG ROM 4Kd S' R' Latch

T Flip Flop

leg Dis

# Waveform Analysis

Display and compare multiple response curves in a single graph at the same time. BSpice simulation results can be selectively displayed and analysed graphically and in numerical format as well as exported to other applications. All of BSpice and B' Logic's display capabilities are completely flexible.

# Devices & Stimulus for Simulation

In B<sup>2</sup> Spice sinusoidal, constant, periodic pulse, exponential, single frequencyFM, AM, DC voltage, AC voltage, VCO, Vcc, piecewise linear, exponential, polynomial /arbitrary source. voltage-controlled voltage, voltagecontrolled current, current-controlled voltage, current-controlled current, Lossy and ideal transmission line, MESFET uniform RC. current and voltage switches are all available.

# Cross Probing

Cross probing allows you to display waveform results simply by marking pins, wires and devices on the circuit drawing. Monitor results while the simulation is in progress then plot analogue results on linear or log scales.

# Graphs

In B<sup>2</sup> Spice analogue traces may be displayed as raw voltages and current values or further processed using arithmetic expressions, functions and Fast Fourier Transforms.High quality graphs let you see just what you need to, clearly and easilyYou can also display multiple simulations in one graph. Multiple graphs can then be alkaned and compared.

# Data Analysis

Position detection with mouse for data points Import and export data to and from other industry standard SPICE programs. B Spice supports Polar, Smith and Nyquist charts.

# Digital Options.

B<sup>2</sup> Logic is completely flexible. Set up ROM, RAM and PLA to your own requirements. Shrink a whole circuit to a block and use it as a component in a new design. Run the simulations in real time or step by step. Customise rise and fall time of all components. Results displayed in a logic analyser or table. Select parts from all major logic families. Create your own custom libraries. Create and run pre-programmed simulations. Design engineers need software that produces results they can rely on. Anything less is a liability.  $B^2$  Spice &  $B^2$  Logic will give you the accurate results you need fast.

The best way to find out if a package is really what you need is to try it, which is what we're giving you the chance to do... risk free for 30 days.

We guarantee you will be 100% satisified with the results or your money back.

# To order your copies to try for 30 days call:

# 01603872331

http://www.paston.co.uk/spice email: rd.research@paston.co.uk





# **RD Research** Research House, Norwich Road, Eastgate, Norwich. NR10 4HA Postage & packing £4.50. Prices quoted are ex VAT. All trademarks are acknowledged



# **Electrical recycling charges up in Yorkshire**

Businesses in Yorkshire have been invited to attend two seminars on electronic waste in Hull and Bradford in September as part of a trial collecting project to target the region's share of the 6 million or so pieces of electronic waste discarded annually in the UK. Equipment like computers, printers, telephones, fax machines and monitors contain valuable materials and components which can be collected for reuse and recycling.

The seminars were arranged by Save Waste and Prosper (SWAP) in conjunction with Leeds Environment Business Forum, Bradford Business and Environment Forum and the Humber Resource Efficiency Centre, with attendance by representatives from the Industry Council for Electronics Recycling and the Corporation of London. The main theme was a survey carried out by SWAP which revealed widespread uncertainty in local companies about how to dispose of obsolete electronic and electrical equipment. The 200 Leeds companies surveyed tackled the problem in a variety of ways from long-term storage, donation to schools, selling off to staff and disposal with general waste. Leeds-based collection company Silver Lining Ltd. began a trial collection service in July, to continue till January 1998 in the Leeds, Bradford and Humber areas. Considerable interest is expected from businesses that do not yet know about the scheme.

Few businesses know that they can pay to have specifically electronic waste removed; some items, such as nicad batteries, should by law be disposed of (by businesses) through specialist commercial waste collection, not via normal rubbish collection.

The seminars are part of a project funded by Cleanaway Ltd. through the Landfill Tax mechanism, which was one of the first to gain support in this way. Support has also come from the Government Office for Yorkshire and Humber.

Businesses that have electronic waste they want collected can contact the organisations listed below - please note that companies will be charged for collection according to the amount and weight of waste.

Paul Twiddy at Business Link Bradford tel. 01274 751399; John Frank at Leeds Environmental Business Forum, tel. 0113 2470000; Terry Lander, Humber Resource Efficiency Centre, tel. 01482 228580.

For further information, contact Elaine Kerrell or Rebecca Shannan at Save Waste and Prosper Ltd., tel. 0113 243 8777 fax 0113 234 4222.

# **Reclaim and recovery gathers pace in Scotland**

A new electronics recycling plant is being opened at the Dumfries site of R Frazier Reclamation, Scotland's Waste, Electrical and Electronic Equipment (WEEE) Recycler. R Frazier Reclamation specialises in the recycling of computers, telecoms and office equipment, including the reclamation of components and parts, and the recycling of materials.

MD Gary Griffiths said, "The purpose-built recycling plant has been designed to process electrical and electronics equipment and related plastics. Sophisticated mechanical separation equipment will reduce electronic parts such as computer boards to small particles, enabling separation of metals from plastics and other materials more effectively than existing processes. The recovered material will them be recycled into new products." He also adds, "R Frazier's asset management approach maximises revenue earning potential as re-used equipment earns more than recycled material."

The company acknowledges openly (not all reclaiming operations do this) that a proportion of waste electronics will be recovered and resold for reuse in its original function. Product handling by the company is prioritised on the basis of re-use, reclaiming components and materials recycling. Trained operators sort incoming equipment to identify any products that can be sold for re-use. The remainder is dismantled and reusable components recovered for re-sale. Hazardous parts such as capacitors, VDUs and batteries are safely disposed of. The company states that security-sensitive equipment is guaranteed destruction - a reassurance that may be necessary as companies frequently forget to clean or overwrite company information on hard disks before parting with their obsolete computers. All products will be tracked and clients will receive reports on how and where materials end up.

"This offers clients the opportunity to turn waste management costs into possible revenue in a process offering both commercial and environmental benefits", says Chairman Liam McKenna.

The company is aiming for zero landfill at the end of the process, and reckons that it has already achieved 99 percent recovery on IT products and 97 percent on telecoms products. The company aims to work with organisations to improve the commercial viability of electronic and electrical equipment recycling, rather than have such recyclable material dumped at cost into landfill.

For further details, contact Gary Griffiths or Katie Martin tel. 01387 721513.



ORDERING INFORMATION - Carriage £1.25+Vat, Prices Exclude Vat (171/2%), Add Carriage & Vat to all orders. Payment with Order. PO/Cheques payable to ESR Electronic Components. ALL Credit Card Orders Accepted. NO Credit Card Surcharges. Trade discount for Schools & Colleges.

# TELNET



(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES	
Beckman 9020 - 20MHz - Dual Channel	
Cossor 3102 – 60MHz Dual Channel	£250
Gouid OS 245A/250/255/300/3000/3351/4000	
Hameg 203/203-5 - 20MHz - Dual Channel	from £150
Hewlett Packard 180A/180C/181A/182C	from £200
Hewlett Packard 1740A. 1741A. 1744A. 100MHz dual ch	from £350
Hewlett Packard 54100D – 1GHz Digitizing	£2995
Hitachi V650E – 60MHz Dual Channel	£350
Hitachi V152F/V302B/V302F/V353F/V550B/V650F	from £125
Intron 2020 – 20MHz Digital Storage (NEW)	£650
watsu SS 5710/SS 5702 - 20MHz.	
Kikusui COS 6100 – 100MHz, 5 Channel, 12 Trace	£475
Kikusul 5100 – 100MHz – Dual Channel	£350
Meauro – MSO 1270A – 20MHz Digital Storage (NEW)	6850
Nicolet 310 – L.F. D.S.O. with twin Disc Drive	2550
Nicolet 3091 – L.F. D.S.O.	0003
Lecrov 9450A - 300MHz/400 Ms/s D.S.O. 2 ch	£2250
Philips PM 3211/PM 3212/PM 3214/PM 3217/PM 3234/PM 3240/PM 3243/PM	3244/PM 3261/
PM 3262/PM 3263/PM 3540	from £125
Philips PM 3295A - 400MHz Dual Channel	£1750
Philips PM 3335 - 50 MHz/20Ms/s D.S.O. 2 ch	£1500
Philips PM 3055 - 50 MHz DUAL Timebase	CASO
Tektronix 434 - 25MHz - 2 Channel Analogue Storage	6250
Tektronix 454 - 150MHz - 2 Channel	6400
Tektronix 468 – 100MHz D.S.O.	
Tektronix TDS 520 - 500 Mhz/500Ms/s D.S.O. 2 Ch	CADOO
Tektronix 2213 - 60MHz Dual Channel	
Tektronix 2221 - 100MHz Digital Storage 2 Channel.	
Tektronix 2221 - 60MHz Digital Storage 2 Channel.	C1500
Tektronix 2235 - 60MHz Dual trace	C4E0
Tektronix 2235 – 100MHz Dual trace	
Tektronix 2335 – Dual trace 100MHz (portable)	\$750
Tektronix 2225 – 50MHz duai ch	C/50
Tektronix 2440 - 300 MHz/500 Ms/s D.S.O. 2 Ch	CADEA
Tektronix 455 – 50MHz Dual Channel	
Tektronix 464/466 – 100MHz An storage	
Tektronix 465/465B – 100MHz dual ch.	
Tektronix 475/475A - 200MHz/250MHz Dual Channel	from £475
Tektronix 485 – 350MHz – 2 channel	
Tektronix 5403 – 60MHz – 2 or 4 Channel	
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch.	from \$200
Tektronix 7313, 7003, 7013, 7023, 7033, 100MHz 4 Gil	
Tektronix 7704 – 200MHz 4 01	
Tektronix 7904 – 500MHz with storage	
Trio CS-1022 – 20MHz – Dual Channel	
Other scopes available too	£125
Other scopes available too	

## пот асороа атвларие

SPECIAL OFFER	
HITACHI V212 – 20MHZ DUAL TRACE	L
HITACHI V222 - 20 MHZ DUAL TRACE + ALTERNATE MAGNIFY	

## SPECTRUM ANALYSER

Advantest 4131 – 10KHz – 3.5GHz (G.P.I.B.)	£4500
Advantest 4133B - 10KHz - 20GHz (60GHz with external mixers) + Ext. Keyboard	£7250
Ando AC8211 - Spectrum Analyser 1.7GHz	
Avcom PSA65 S - 1000MHz - portable.	£1500
Eaton/Alitech 757 - 10KHz - 22GHz	£2750
Hewlett Packard 3580A - 5Hz-50KHz	6005
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
Hewlett Packard 35601A - Spectrum Analyser Interface	
Hewlett Packard 141T + 8552B + 8555A - (10MHz - 18GHz)	£1800
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser	£7500
Hewlett Packard 8505A - Network Analyser 500KHz - 1300MHz	£2050
Hewlett Packard 853A + 8558B - 0.1 to 1500MHz.	
Hewlett Packard 182T + 8558B - 0.1 to 1500MHz	C2750
Hewiett Packard 8754A - Network Analyser 4-1300MHz	£2000
Hewlett Packard 8591E (HP - 1B) - 9KHz - 1.8GHz (calibrated)	
Marconi 2370 - 110MHz	
Marconi 2371 – 30KHz – 2000MHz	C1050
Meguro MSA 4901 – 1-300GHz (AS NEW)	£1250
Meguro MSA 4912 - 1-1GHz (AS NEW)	£1993
Poirad 641-1 - 10MHz - 18GHz	£1500
Rohde & Schwarz – SWOB 5 Polyskop 0.1 – 1300MHz.	£1800
Takeda Riken 4132 - 1.0GHz Spectrum Analyser	
Tektronix 7L18 with mainframe (1.5-60GHz with external mixers)	£2000

## **MISCELLANEOUS**

Adret 740A - 100KHz - 1120MHz Synthesised Signal Generator	£2000
ANRITSU ME 462B DF/3 Transmission Analyser	£3000
Danbridge JP30A – 30KV Insulation Tester	£1500
Anritsu MG642A Pulse Pattern Generator	£1500
Dranetz 626 – AC/DC – Multifunction Analyser	£850
EIP 331 – Frequency counter 18GHz	£700
EIP 545 - Frequency counter 18GHz	£1500
EIP 545A - Frequency counter 18GHz	£1600
FIP 575 - Frequency counter 18CHz	£17E0
Farnell TSV-70 MKII Power Supply (0-70v/30A) Auto Ranging Farnell TSV-70 MKII Power Supply (70V – 5A or 35V – 10A)	£750
Farnell TSV-70 MKII Power Supply (70V - 5A or 35V - 10A)	£200
Farnell DSG-1 Synthesised Signal Generator	£125
Farnell DSG-1 Synthesised Signal Generator Farnell ESG-1000 Synthesised Signal Generator 1GHz (as new)	£1650
Flure 5100A - Calibrator	£2500
Flure 5100B – Calibrator	£3500
Gigatronics 8541 - Universal Power Meter	£1500
Guildline 9152 - T12 Battery Standard Cell	\$550
Hewlett Packard 333A – Distortion Analyser	£300
Hewlett Packard 3314A – Function Generator	£2250
Hewlett Packard 3336C - Synthesised Signal Generator (10Hz - 21MHz)	£1000
Hewlett Packard 3437A System voltmeter	\$350
Hewlett Packard 3456A Digital voltmeter	2850
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 35600A Dual Ch. Dynamic Signal Analyser	£3750
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser	£2250
Hewlett Packard 3776A - PCM Terminal Test Set	EPOA
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen	£1500
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available)	
Hewlett Packard 334A - Distortion Analyser	
Hewlett Packard 3455A 6% Digit M/Meter (Autocal)	\$750
Hewlett Packard 3478A – Multimeter (5½ Digit) + HP – 18 Hewlett Packard 3776A – PCM Terminal Test Set	\$550
Hewlett Packard 3776A - PCM Terminal Test Set	EPOA
Hewlett Packard 3779A/3779C - Primary Mux Analyser Hewlett Packard 436A + Sensor	from £600
Hewlett Packard 436A + Sensor	from £1000
Hewlett Packard 4275A – LCB Meter (Multi-Frequency)	£3950
riewiett Packard 4338A - Millionmeter (As New)	
Hewlett Packard 4342A 'Q' Meter	£995
Hewlett Packard 4342A 'Q' Meter Hewlett Packard 4952A - Protocol Analyser (with interfaces)	£2500
Hewlett Packard 4953A - Protocol Analyser	£2750
Hewlett Packard 432A Power Meter (with 478A Sensor)	£275

Hewlett Packard 435A or B Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 4271B – L.C.R. Meter (Digital) Hewlett Packard 4278A – 1KHz/1MHz Capacitance Meter	0003
Hewlett Packard 4278A - 1KHz/1MHz Capacitance Meter	£3750
Hewlett Packard 4279A – 1MHz C-V Meter	£6500
Hewlett Packard 4948A - (TIMS) Transmission impairment M/Set	£2000
Hewlett Packard 4972A - Lan Protocol Analyser	£2000
Hewlett Packard 5420A Digital Signal Analyser.	£350
Hewlett Packard 5335A - 200MHz High Performance Systems Counter	0083.
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter	
Hewlett Packard 5183 - Waveform Recorder	£2250
Hewlett Packard 5238A Frequency Counter 100MHz	£250
Hewlett Packard 5370A – 100MHz Universal Timer/Counter	£450
Hewlett Packard 5384A – 225 MHz Frequency Counter	£950
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP18) with OPTS 001/003/	004/005£995
Hewlett Packard 6031A - 1000W Autoranging p.s.u. (20v - 120A)	£1550
Hewlett Packard 6034 ~ 60V - 10A System Power Supply	
Hewlett Packard 6253A Power Supply 20V - 3A Twin	£200
Hewlett Packard 6255A Power supply 40V - 1.5A Twin	
Hewlett Packard 6266B Power Supply 40V - 5A	
Hewlett Packard 6271B Power supply 60V - 3A	£225
Hewlett Packard 6034A - 0-60V - 10A System P.S.U.	£1500
Hewlett Packard 7475A – 6 Pen Plotter	
Hewlett Packard 7550A - 8 Pen Plotter A3/A4	

# HEWLETT PACKARD 6261B Power Suppiy 20V-50A £450 Discount for Quantities

Power Supply 20V-50A £450 Discount for Quantities	
Hewlett Packard 8349B – Microwave Broad Band Amplifier Hewlett Packard 83555A – Millimeter – Wave source Module 33-50GHz	£350
Hewlett Packard 83555A – Millimeter – Wave source Module 33-50GHz	£425 £75
Hewlett Packard 8405A - Vector Voltmeter	£50
Iswiett Packard 8015A – 50MHz Pulse Generator Iswiett Packard 8405A - Vector Voltmeter Iswiett Packard 8165A - 50MHz Programmable Signal Source Iswiett Packard 8150B - Sweep Oscillator Mainframe (various Plug-ins available) Iswiett Packard 8152A - Optical Average Power Meter Iswiett Packard 8152A - Optical Average Power Meter Iswiett Packard 8150A - Optical Average Toward (OPTS 002 + 011) Iswiett Packard 8180A - Data Generator	£165
Hewlett Packard 83500 - Sweep Oscillator Maintrame (vanous Plug-ins available)	extra£265 £125
lewiett Packard 8158B - Optical Attenuator (OPTS 002 + 011)	£110
Newlett Packard 8180A - Data Generator.	£150
Tewlett Packard 810A – Data Generator Hewlett Packard 8182A – Data Analyser. Hewlett Packard 83554A – Wave Source Module 26.5 to 40GHz Hewlett Packard 8305 Sweep oscillator mainframe Hewlett Packard 8656B – Synthesised Signal Generator Hewlett Packard 8556B – Synthesised Signal Generator	£150 £350
Hewlett Packard 8684A 5.4GHz to 12.5GHz Sig-Gen	£275
lewiett Packard 8620C Sweep oscillator mainframe	from £25
tewlett Packard 8656B - Synthesised Signal Generator	£295
Hewitet Packard 8568 – symmesised signal Generator	£200
lewlett Packard 8903A - Audio Analyser (20Hz - 100KHz)	£260
Hewlett Packard 8958A - Cellular Radio Interface	£200
Hewlett Packard 8920A - R/F Comms Test Set	
lewiett Packard P382A Variable Attenuator	£25
lewlett Packard 1630D - Logic Analyser (43 Channels)	£65
rewiett Packard 16500A - Filled will 16510A/16515A/16530A/16531A - Logic Ani lewiett Packard 11729B - Carrier Noise Test Set	alyser£400 6200
(rohn-Hite 2200 Lin/Log Sweep Generator	
(rohn-Hite 4024A Oscillator	£25
(rohn-Hite 5200 Sweep, Function Generator	£35
Ironn-rine 6500 Phase Meter	£25 ¢185
Aarconi 2019A - 80KHz - 1040MHz - Synthesised Signal Generator	£195
tewiett Packard 8920A – R/F Comms Tesi Set tewiett Packard P382A Variable Attenuator	£200
Aarconi 2432A 500MHz digital freq. meter	£20
Aarconi 2010 - True rimo volutieter	£85 ¢100
Aarconi 2955 - Radio Comms Test Set	£300
Aarconi 2022A - 10KHz - 1GH2 AW/FM Signal Generator Aarconi 2023A 500MHz digital freq meter Aarconi 2610 - True RMS Voltmeter Aarconi 2617 Data Comms Analyser Aarconi 2955 - Radio Comms Test Set Harconi 2950A - Radio Comms Test Set with Cellular Adaptor Jarconi 6960 - Power Meter & Sensor Jarconi 6960 - Dower Meter & Sensor	£350
Aarconi 6960 – Power Meter & Sensor Iarconi 6960A – Power Meter & Sensor	from £95
Marconi 6960 – Power Meter & Sensor	Trom £105 ¢40
hilips 5190 L.F. Synthesiser (G.P.I.B).	280
Philips PM5519 – TV Pattern Generator	£35
hilips PM5667 - Vectorscope	£50
Thilps PM5/16 - SUMHZ PUISE Generator	£52
Philips PM6670 - 120MHz High Resolution Universal Counter	£35
hillps PM6673 – 120MHz High Resolution Universal Counter	£43
Prema 4000 – 6 % Digit Multimeter (NEW)	£45
Recei Dana 9081/9082 Synth sig gen 520MHz	£80
Racal Dana 9064 Synth. sig. gen. 104MHz	£45
tacal Dana 9303 R/F Level Meter & Head	£65
tacal Dana 9917 UHF frequency meter 560MHz	£17
acal Dana 9082 Synthesised am/fm sig gen (520MHz)	£50
tacal 9301A - True RMS R/F Multivoltmeter	£30
tohde & Schwarz LFM2 – 60MHz Group Delay Sweep Gen	£160
Ionde & Schwarz SMFP2 - 1GHZ Hadio Comms 1/Set	
lohde & Schwarz URE – RMS Voltmeter (10Hz-25MHz)	£50
tohde & Schwarz Scud Radio Code Test Set	£30
Tohde & Schwarz SUF 2 Noise Generator	£30
Nohde & Schwarz SUF 2 Noise Generator Nohde & Schwarz SMDU – 15MHz to 525MHz Signal Gen (FM & AM). Schaffrer NSG 203A Line Voltage Variation Simulator. Schaffrer NSG 222A Interference Simulator.	£50
Schaffner NSG 222A Interference Simulator	
Schaffner NSG 223 Interference Generator	£85
Schaffner WSG 431 Electrostatic Discharge Simulator	£125
schlumberger 4923 Hadio Code Test Set	£95
Schlumberger 4031 – TGHZ Haulo Comms Test Set	
Schlumberger 7060/7065/7075 Multimeters	from £35
ichaffner NSG 222A Interference Simulator ichaffner NSG 223 Interference Generator ichaffner WSG 431 Electrostatic Discharge Simulator ichlumberger 4923 Radio Code Test Set ichlumberger 4031 – 1GHz Radio Comms Test Set ichlumberger 7080/7065/7075 Multimeters ichlumberger 7080/7050/7050/705 ichlumberger 7080/7050/7050/7050/705 ichlumberger 7080/7050/7050/7050/7050/7050/7050/7050/	£250
Stanford Research DS 340 – 15MHz Synthesised Function (NEW) and arbitrary	6120
Systron Donner 6030 – Microwaye Frequency Counter (26 5GHz)	£120 £250
elequipment CT71 Curve Tracer	£25
ektronix TM5003 + AFG 5101 Arbitrary Function Gen.	£175
ektronix 1240 Logic Analyser ektronix DAS9100 – Senes Logic Analyser ektronix Plug-ins – many available such as SC504, SW503, SG502, G508, FG504, FG503, TG501, TR503 + many more ektronix PC Curpe Tracer extreme FZ Cu	£50
ektronix - Plug-ins - many available such as SC504 SW503 SG502	
G508, FG504, FG503, TG501, TR503 + many more	£PO
ektronix AM503 + TM501 + P6302 – Current Probe Amplifier ektronix PG506 + TG501 + SG503 + TM503 – Oscilloscope Calibrator	
ektronix AA5001 & TM5006 W/F - Programmable Distortion Analyser	£250
aktronix 577 - Cupya Tracer	C115
Time 9811 Programmable Resistance	£60
Ime 9814 Voltage Calibrator	£75
continer 7720 - Programmable 10MHz Eusetion Can (AS NEW)	£PO 4
Toeliner 7720 – Programmable 10MHz Function Gen (AS NEW)	
Toeliner 7720 – Programmable 10MHz Function Gen (AS NEW) /alhalia Scientific – 2724 Programmable Resistance Standard	£995
cellner 7720 – Programmable 10MHz Function Gen (ÅS NEW) falhalla Scientific – 2724 Programmable Resistance Standard Vandel & Gottermann PCM4 (+ options) Vayne Kerr 4225 – LCR Bridge	£995 
cellner 7720 – <sup>1</sup> Frogrammable 10MHz Function Gen (AS NEW) <b>⊲lnhalla Scientifto –</b> 2724 Programmable Resistance Standard <b>vandel &amp; Gottermann PCM4</b> (+ options) <b>vayne Kerr 4225 –</b> LCR Bidge Wayne Kerr 4425 – Precision Component Analyser	£995 £60 £27
Wayne Kerr 6425 – LCH Dhoge Nayne Kerr 6425 – Precision Component Analyser	£50 £27 £85
Time 9811 P rogrammable Resistance Time 9814 Voltage Calibrator Seeliner 7720 – Programmable 10MHz Function Gen (AS NEW) /alhalla Scientific – 2724 Programmable Resistance Standard Wayne Kerr 4225 – LCR Bridge Wayne Kerr 4225 – LCR Bridge Wayne Kerr 8056 – Precision LCR Meter Mayre Kerr 8056 – Precision LCR Meter Waytek 171 – Synthetised Function Generator Wavetek 171 – Synthetised Function Generator Wavetek 172 B Programmable Sig Source (0.0001Hz – 13MHz)	£50 £27 £85 £25
Wayne Kerr 4/20 – LCH broge Wayne Kerr 8905 – Precision Component Analyser Wayne Kerr 8905 – Precision LCR Meter Wavetek 171 – Synthetised Function Generator Wavetek 178 Programmable Sin Source (0.0001Hz – 13MHz)	£50 £27 £85 £25
Wayne Kerr 925 - CCH Dhoge Nayne Kerr 925 - Precision Component Analyser	£50 £27 £85 £25

MANY MORE ITEMS AVAILABLE -SEND LARGE S.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED -WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING – CARRIAGE & VAT TO BE ADDED TO ALL GOODS

# Digital Signal Processing

Signal processing in a chip, DSP will soon become as ubiquitous as the general purpose microprocessor.

igital signal processing (DSP) is used in modems, amateur radio equipment, high-end sound equipment, and in many areas where you might not at first expect to find it. Although it is difficult to design a complicated DSP system, the principles on which DSP works are accessible to anyone. It is only the mathematics and coding for complex systems which present a challenge.

Apart from fashion, why should DSP be used in preference to other filtering techniques? There are many reasons, but one of the most important is that DSP can do things that are not achievable with conventional signal processing (see finite impulse response filters below), or that are too expensive or complicated to be practical with other techniques.

A DSP system is controlled by software, so that the same system can be dynamically reconfigured for different functions (for instance, for different modem speeds) or can even be self-adapting. Depending on

speed of signal and the speed of the DSP system, the same DSP chip may be able to carry out several functions at once, or perhaps to control a user interface with controls and displays in addition to its real-time signal processing task. For these and other good reasons, DSP is becoming widely used.

Digital signal processing, once the signal is in digital form, requires adders, subtractors, multipliers and dividers. It also needs time delays, which can normally be provided by the use of memory.

# **Digitisation**

In order to use a digital filtering system, the first requirement is to digitise the signal (unless, as with the data stream from a CD, it has already been digitised). In order to implement a high quality DSP function, the digitisation of the signal must be carried out to a high standard. Otherwise, even if the rest of the system is well designed, the overall performance will be disappointing. Since the aim of this article is to cover DSP itself, I shall cover only the highlights of digitisation.

An analogue signal, which may also be called a continuous time sequence, may be converted into a digital signal or discontinuous time sequence by sampling at regular intervals and assigning a digital value corresponding to the voltage of the signal at the



instant of sampling. This principle is illustrated in figure 1.

In some cases the voltage to be measured will always be positive, in which case a binary representation starting at all zeros for the lowest voltage to be represented to all ones for the highest voltage will be suitable. However, in many cases positive and negative values must be represented, as in an audio signal. There are two major methods of using binary numbers to represent such voltages, offset binary, and twos complement.

Offset binary is straightforward to understand. If 8 bits are used to represent the signal than the zero point is set to 127





(01111111 in binary, 7F in hexadecimal). A simple way to do this is illustrated in figure 2. Here a signal with a range of +/-2.5V is halved and added to a halved copy of the 2.5V reference, converting it to a signal having a range from zero to -2.5V. An inverter converts this to an equivalent positive range, which matches the voltage reference of the analogue to digital converter. This provides offset binary independent of the number of bits.

This can be useful for such things as data logging on a PC, where the data logging program can do the necessary calculations for offset and scaling. It is less useful for real time digital signal processing, where calculations must be done with maximum speed. For this purpose "two's complement" is more useful. This is a means of representing positive and negative values with a single binary sequence, in a manner compatible with binary arithmetic operations, so that if a positive and a negative number are added, the resulting number is correct.

To convert a number to two's complement, invert all the bits and add 1. This is the same as saying that the most significant bit is the sign bit, with 0 representing positive numbers and 1 representing negative ones. It is also necessary to ignore the carry bit.

Here are some examples of additions:

00010110 (+0010110) 11111101 (-0000011)

100010011 (+0010100) (Disregard the carry bit, and the sign bit is 0, meaning positive)

00000011 (+0000011) 11101010 (-0010100)

11101101 (Two's complement for -0010011)

Most analogue to digital converters intended for use in DSP can output data in two's complement mode. Often the converter itself cannot accept negative input voltages, but can use an analogue ground offset of half the reference voltage. In this case a voltage of half the reference is added to the signal in a manner similar to that shown in figure 2 for the offset binary conversion.

# **Conversion techniques**

There are a number of ways to convert a voltage to a binary number. The fastest is the flash converter, in which, for an eight-bit conversion, 255 comparators are used with a reference chain and the output is encoded into binary. This principle is illustrated in figure 3, which shows a two-bit flash converter.

Two bits of binary can have a total of four states: 00, 01, 10, 11. To split an input voltage into four states requires three comparators, with the states being: all comparators off, one on, two on, and all three on. In general, one comparator less than the number of states is needed, so 255 comparators would be needed for an eight-bit conversion. For video encoding, six bit flash converters are sometimes used, with one converter for each of the colour signals (RGB).

The advantage of a flash converter is that it is as fast as a single comparator, faster than any other technique.



Disadvantages include the large number of comparators needed, and the power dissipation of the resistor chaln. It is normally only considered practical to use integrated flash converters.

Perhaps the most accurate, and slowest, is the dual slope converter, used widely in digital multimeters. However, the majority of converters for medium frequencies (including audio) use a variety of successive approximation technique. The idea is illustrated in figure 4.

The procedure is to start with all bits set to 0, then set the most significant to 1 (that is, half scale). If the comparator switches, then the most significant bit gives too high a voltage, so it is set to 0 and the next most significant bit is set to 1. This



process continues until all the bits have been tested. Thus a sixteen-bit conversion takes sixteen comparisons.

Normal digital to analogue converters use a series of resistors, either weighted in the sequence 1, 2, 4, 8 etc. or the widely used R-2R network.

It is difficult to integrate precision resistors of the quality required for accurate conversion using normal chip fabrication technology. Even for a 12-bit conversion, the most significant bit resistor must be accurate to one part in 4096. A 16-bit conversion requires an accuracy of one part in 65536.

Another interesting technique used in some A to D converters is to use capacitors instead of resistors, with analogue switches to sample and integrate the charge. Capacitor errors can be corrected by comparing larger value capacitors in the chain with all the smaller ones, and averaging the errors. Correction figures are stored in registers and used to correct the output for calibrated linearity errors. A detailed discussion of this is beyond the scope of this article, but various semiconductor manufacturers literature explains it in more detail.

It is worth noting that, in order to design a good quality DSP-based system, the analogue signal conditioning must be of an adequate standard. If the noise and offsets of the signal conditioning exceed one least significant bit, then the signal conditioning is probably degrading the overall result significantly.

# Aliasing

When converting an analogue signal to a digital form, it is sampled at fixed times. It must be sampled sufficiently often that the instantaneous signal value has not changed too much since the last sample. Sampling less than once per half cycle of the maximum input frequency causes a particular problem, that of the generation of non-existent lower frequency signals as a result of a beat between the sample rate and the input frequency. This is illustrated in figure 5.

The resulting frequency in this example is in the audible range, and would definitely interfere with the sound of a CD if this effect were present on the recording. A sampling rate of exactly two samples per cycle is called the Nyquist frequency. This sample rate is the lowest possible one that avoids aliasing.

Clearly, it is better to sample at well above the Nyquist frequency if possible. There are several reasons for this. One is that, to avoid aliasing, the analogue signal must be filtered to remove all frequency components above half the sampling frequency. A higher sampling frequency permits the filter cutoff frequency to be well above the maximum frequency of interest, which improves the phase response in band. This is of interest in audio applications, where the effects of very sharp filters can be heard.

In addition, sampling generates noise power spread evenly over the spectrum. If the sampling rate is higher, the spectrum over which the noise power is spread is greater, so the proportion in the band of interest is less.

A digitisation technique particularly well suited to audio applications is called sigma-delta conversion. The sampling rate



is much higher than the Nyquist rate, but the conversion is only one bit. In effect, the one bit says whether the signal went up or down during the preceding sample period. Figure 6 shows the block diagram of a sigma-delta analogue to digital conversion. The loop here acts as a low pass filter for the input signal and a high pass filter for the quantisation noise. This noise shaping suits audio requirements well.

After the one-bit conversion is a decimation filter, which







lowers the data rate and increases the accuracy. Figure 7 shows the effect of the decimation filter.

# Simple filters - FIR and IIR

The first point to note is that almost all other filter technologies give an infinite impulse response. This is easily illustrated by the simplest possible low pass filter, using one resistor and one capacitor, as shown in figure 8. The output voltage from this filter is affected by all previous inputs back to the time it was built, because the charging and discharging of the capacitor is exponential. The voltage on the capacitor approaches its aiming point more and more closely, but never actually reaches it. The exact voltage at any given point on a charge or discharge waveform is affected by the starting voltage, which is itself affected by the starting voltage of previous charge and discharge waveforms.

Equally, a tuned circuit will ring forever, with decreasing amplitude, after being excited with one impulse. So, the defining characteristic of an infinite impulse response filter is that its output is dependent on all the inputs it has ever received, and its output for a given input will persist theoretically to infinity. In real systems, the output will decline to a negligible level after a short time, but this level, though too small to measure, is not zero.

The infinite impulse response of analogue filters is not always brought out in mathematical descriptions. When Laplace transforms are used to analyse the filter response, there is normally an implicit assumption that the starting state of charge of all capacitors is zero, and that the initial inductor current is also zero. A rigorous Laplace transform would have to include the initial conditions of the system being analysed.

By contrast, a transversal filter using surface acoustic wave technology, shown in figure 9 is, apart from any imperfections, a finite impulse response filter. Different parts of the input signal are fed to the output with different amplitudes and delays, and after the input signal ceases, and has passed through the filter, its output is zero except for the effects of stray reflections from the acoustic absorbers.



Figures 10 and 11 show examples of FIR and IIR filters. Note that the FIR filter has no feedback paths, and that the feedback paths are what make the filter infinite impulse response. Signals can be fed round and round the loop, being modified (probably attenuated) each time, but theoretically persisting forever. In practice, of course, the amplitude of the recirculating signal in a practical IIR filter will rapidly fall below one least significant bit.

DSP is often thought of as something only esoteric, but, although the term is not often used in this context, the averaging of a series of readings (to

average out the noise) in a microprocessor based control system, is a simple form of digital signal processing.



Figure 10: a simple finite impulse response filter



# **Characteristics of FIR and IIR filters**

FIR filters can be linear phase and cannot oscillate. They also need a lot of stages to achieve a sharp cutoff.

IIR filters could oscillate if badly designed, and normally have a non-linear phase response, but a much sharper cut off than a similar order of FIR filter.

# **DSP** chip major functions

As may already have become apparent, digital signal processing can be carried out on any microprocessor. The basic mathematical functions used - addition, multiplication etc. - are just the same. The reason for having specific chips or whole dedicated chip sets is because the arithmetical functions required involve a great deal of repetitive computation which is usually done in real time. A general-purpose microprocessor, while being capable of performing such 'number crunching', in practice would not be able to provide sufficient signal bandwidth to be useful. To overcome this, the chip designers have taken some of the software functions - such as





multiplication - and provided a dedicated hardware multiplier that will provide the product of two digital numbers very quickly while the DSP processor is performing another task. The advantages of this are that a multiplication task is performed faster than the processor could do it, but at the expense of cost because the chip includes extra hardware.

On the other hand, it is optimised for the job, and in many cases a cheap dsp chip could perform dsp better than a Pentium.

The techniques of DSP have been around for a considerable time, but have been used much slower than real-time on previous generations of computers. For example, an audio recording could be digitally reprocessed to remove clicks and noise, and a new recording made to a quality more suitable for broadcast. Even if the process took several hours to improve a five-minute recording, the quality of the result was good enough to be worth the effort.

Nowadays, however, the term DSP is used to refer to realtime processing, often on audio or video frequency signals. Instead of the microprocessor carrying out multiplications using successive additions with shifts in between (shift and add), a hardware multiplier is used to do what is otherwise a software function. It is this approach that enables DSP chips to keep up with the real world signals that they are required to process.

Equally, time can be saved in fast Fourier transforms by incorporating a special addressing mode in the DSP chip (bitswapped addressing). This permits samples to be stored in the order in which they occur, and be addressed in the order in which they are required, without doing any extra address calculations.

A major function of DSP chips is to carry out Fourier transforms. The reason is that the Fourier transform is a representation of a waveform in terms of frequency instead of time. In this representation, it is simple to remove a frequency component from the signal to generate a notch, or to make any other modification to the frequency response. To understand this, it is unavoidably necessary to look at the mathematics to a certain extent.

# **Fourier transforms**

All complex (non-sinusoidal) signals are made up of various component frequencies. Viewing a square wave on an oscilloscope will show an easily recognisable trace, but feeding that same waveform into a spectrum analyser gives a very different picture indeed. The spectrum analyser, through the use of linear filters (or, if it's more **modern**, DSP), breaks the square wave up into its component **frequencies** and displays them as relative amplitudes. It is **import**ant to note that they are both giving the same information but in different domains. The oscilloscope shows the signal in the time domain with the horizontal axis representing time as defined by the timebase control. The spectrum analyser displays the signal in the frequency domain where the horizontal axis shows the frequency range over which the instrument is working. But note: the spectrum analyser does not give phase information of the displayed frequencies, which is vital to reconstituting the original signal from the displayed data.

In order to understand how a software program can calculate the frequency spectrum of a signal it is necessary to simplify for a moment by leaving out the effect of the sampling, and by using a repetitive signal such as a square wave. The Fourier transform converts between the time domain and frequency domain according to the following formula:

# $X(\omega)=1/2\pi$ . $\int^{+\infty} X(t) e^{-j\omega t} dt$

Where X(t) is the time waveform; X(( $\omega$ ) is all the component frequencies that go to make up the time waveform; 1 / 2 $\pi$ s converts between radians and hertz; e-j $\omega$ t is a phasor representation of both sine and cosine terms represented as a time dependent waveform; and dt is the differentiation of the time waveform (X(t)) with respect to time (t), which extracts the rate of variation of the time waveform in time.

Examining this formula shows that it encompasses minus infinity to plus infinity, which means that it can cover random signals. The square wave, because it is repetitive does not need to solved over this range, only the period over which one complete cycle exists.

If a single frequency is represented by a sine wave and, as described above, the square wave contains many different frequencies, then the formula must describe the shape of the waveform in order to be able to extract the frequency data. Therefore to convert the square wave from a time domain waveform to a composite set of frequencies and phases, we modify the Fourier transform formula as follows:

For a square wave of amplitude (V and duration at each level T (that is, the total period 2T), the Fourier series is:

# $X(\omega)=1/2\pi_{0}\int t(+V)e^{-j\omega t} dt + 1/2\pi_{1}\int 2t(-V)e^{-j\omega t} dt$

# Where ∫ indicates integration.

This formula describes the basic shape of the waveform mathematically over the various time periods that go to make up the overall signal, a positive DC level which lasts for T seconds followed by a negative DC level which also lasts for T seconds. In fact any repetitive waveform can be described in this manner and the associated frequency spectrum derived accordingly.

When the data describing the waveform is entered into the formula it was presented in the form "over the time period 0 to X, the waveform was a DC level of +V volts", "over the time period X to Y the waveform was a DC level of -V volts". Examining the form of the data entry shows that we have described the shape of the waveform completely in a theoretical manner. In effect we have looked at the waveform outside of time and described how it **varies** with respect to time.

ELECTRONICS TODAY INTERNATIONAL .

ł

DIFFERENTIAL THERMOSTAT KIT Perfect for hestrecovery, solar systems, boiler efficiency etc. Two sensors will operate a relay when a temp difference (adjustable) is detected. All components and pcb. £29 re LOT93 SOLAR WATER HEATING PLANS 25 REF SOLP

# PC POWER SUPPLIES **PACK OF 8 FOR £9.95**

Thats right! 8 power supplies for £9.95! These are all fan cooled (usually 12v) our choice of specs etc, and are sold as seen. But worth it for the fans alone! ref XX17

MAINS POWER SAVER UK made plug in unit, fitted inseconds, can reduce your energy consumption by 15%. Works with fridges, soldering irons, conventional buils etc. Max 2A rating, £9 each ref LOT71, pack of 10 £69 ref LOT72

# DC TO DC CONVERTERS

é

1

DRM58 input 10-40vdc output 5v 8A £15 DRM128 input 17-40vdc output 12v 8A £18 DRM158 input 20-40vdc output 15v 8A £18 DRM248 input 29-40vdc output 24v 8A £12 DRS123 input 17-40vdc output 12y 3A £10 DRS153 input 20-40vdc output 15y 3A £20 DRS243 input 29-40vdc output 24v 3A £8

HITACHI LM225X LCD SCREENS 270x150mm, standard 12 way connector, 640x200 dots, tec spec sheet, £15 each ref LM2 HOME DECK CLEARANCE These units must be cleared!

leads, a n infra red remote qwerty keyboard and receiver, a standard UHF modulator, a standard 1200/75 BT approved modem and loads of chips, capacitors, diodes, resistors etc all for just £10 ref BAR33. PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/set. Ref F/XP1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks vet produces positive motion and effect. Excellent for science projects magic shows, party demonstrations or serious research & develops of this strange and amazing phychic phenomenon. £4/set Ref F/TKE 1.

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set. Ref F/EH2.

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of materials and without any visible means- cause it to levitat 10/set Ref F/GRA1

WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, 'Plasme in a jar', St Elmo's fire, Corona, excellent science project or conversation piece. £5/set Ref F/BTC1/LG5.

COPPER VAPOUR LASER PLANS Produces 100mm of visible green light. High coherency and spectral quality similar to Argon aser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commision of NEGEV in Israel. £10/set Ref F/CVL1.

VOICE SCRAMBLER PLANS Minature solid state system tums speech sound into indecipherable noise that cannot be understood ithout a second matching unit. Use on telephone to prevent third party listening and bugging, £8/set Ref F/VS9.

PULSED TV JOKER PLANS Little hand held device utilises echniques that will completely disrupt TV picture and sound! on FM too! DISCRETION ADVISED, £8/set Ref F/TJ5. pulse techniqu

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent s or very interesting science project. £8/set Ref F/BHT1 curity d

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is eas ble to burning and etching wood, cutting, plastics, textiles etc £12/set Ref F/LC7

DVNAMO FLASHLIGHT Interesting concept, no batteries needed just squeeze the trigger for instant light apparently even works under rater in an emergency although we haven't tried it yet! £6.99 ref SC152 ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquides. Many cleaning uses for PC boards, jewliery, coins, small parts etc. £6/set Ref F/ULB1.



Water pump motors, mains powered, 165x75mm, 5mm shaft. £6 ea ref MM10. Pack of 3 for £12 ref MM11.

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of accoustical energy that dogs cannot tolerate £6/set Ref F/DOG2

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to be ar sounds from a premises without gaining access. £12/set Ref F/ LLIST1

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with ext controls. £6/set Ref F/PSP4

INFINITY TRANSMITTER PLANS Telephone line grabber/ room monitor. The ultimate in home/office security and safetyl simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. Ref F/TELEGRAB

BUG DETECTOR PLANS is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Shiffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies, £5/set Ref F/ BD1

ELECTROMAGNETIC GUN PLANS Projects a metal object stance-requires adult supervision £5 ref F/EML2 ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HANDI £5/set Ref F/EMA

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant so ounde us them to our ultra sensitive electronics I wireless link system. £8/set ref F/PM5 nd foc cs. Plans also show an

**2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND** HIGH DC VOLTAGE. SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 Ref F/HVM7/

MEGALED DISPLAYS PCB fitted with 5 seven segment displays h measuring 55 x 38mm. £5 ref LED5. MOD TRANSMITTING VALVES 5J180E £80 ref LOT112

SWITCHED MODE PSU'S 244 watt. +5 32A, +12 6A, -5 0.2A, -12 0.2A. There is also an optional 3.3v 25A rail available. 120/240v l/ P. Cased. 175x90x145mm, IEC inlet Suitable for PC use (6 d/drive connectors 1 m/board). £15 ref LOT135





# VIDEO PROCESSOR UNITS?/6v 10AH BATTS/24V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390X320X120mm, on the front are

controls for scan speed, acan delay, scan mode, loads of connections on the rear. Inside 2 x 6v 10AH sealed lead acid batts, pcb's and a 8A? 24v torroidial transformer (mains in), sold as seen, may have one or two broken knobs etc due to poor storage. £15.99 ref VP2

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 68-108 Mhz but easily changed to cover 63-130 Mhz. Works with a common 9v (PP3) bettery. 0.2W RF. £9 Ref 1001.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 Ref 1007. 1 WATT FM TRANSMITTER KIT Supplied with piezo e

8-30vdc. At 25-30v you will get nearly 2 watts! £15 ref 1009. FM/AM SCANNER KIT Well not quite, you have to turn the knob your self but you will hear things on this radio that you would not hear on

n ordinary radio (even TV). Covers 50-160 mhz on both AM and FM. uitt in 5 watt amplifier, Inc speaker. £18 maf 1013. 3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains

ted, separate sensitivity adjustment for each channel, 1,200 w



power handling, microphone included. £17 Ref 1014.

# Install a coin box telephone at

# home

# for less than £5

By using our phone box, you get everything you need to convert any standard telephone into a coinbox telephone. You simply open the box, plug your telephone into a connector inside and then plug the coinbox nto your telephone socket, it's that simple! There a e one or two tches however

Catch one is that the lock and hinges my be damaged/broken, this doesn't really matter because you could replace the hinges easily and change the lock or you could refit the front panel onto a box of your own choosing.

Catch two is that the three coinslots accept £1, 50p and 10p's this is fine except that the 10p slot is for the older 10p piece so you would need to glue a small piece of plastic across the bottom of the slot on the inside to reduce the hole size. Full programming instructions are included with every combox Bargain price £4.99 ref\_CBT1

4 WATT FM TRANSMITTER KIT Small but powerful FM nitter, 3 RF stages, microphone and audio preamp included. £24 Ref 1028. STROBE LIGHT KIT Adjustable from 1-60 hz (a lot faster than

conventional strobes). Mains operated, £17 Ref 1037. COMBINATION LOCK KIT9 key, programmable, complete with

keypad, will switch 2A mains, 9v dc operation, £13 ref 1114 PHONE BUG DETECTOR KIT This device will warm you if

ebody is eavesdropping on your line. £9 ref 1130. ROBOT VOICE KIT Interesting circuit that distorts your voice!

ver the phone with a different voice! 12vdc£9ref 1131 TELEPHONE BUG KIT Small bug powered by the 'phone line, starts transmitting as soon as the phone is picked upl £12 Ref 1135. 12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2a transformer also required. £8 ret 1069

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recorders etc. adjustable sensitivity. £10 ref 1073. SOUND EFFECTS GENERATOR KIT Produces sounds

ranging from bird chips to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045. 15 WATT FM TRANSMITTER (BUILT) 4 stage high power,

preamp required 12-18vdc, can use ground plane, yagi or open dipole. 660 mf 1021

HUMIDITY METER KIT Builds into a precision LCD humidity ign, pcb, lcd display and all components included. £29 PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want Minimum system configeration is 286, VGA, 4.1,640k, senal port, hard drive with min 100k free. £24.99

NICKEL PLATING KIT Profesional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal,copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £45 ref NIK39.

Minature adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12vDC adjustable from 0-30 secs. £4.99 HY1260M, 12vDC adjustable from 0-60 mins. £4.99 HY2405S, 240v adjustable from 0-5 secs. £4.99 HY24060m, 240v adjustable from 0-60 mins, £6.99 BUGGING TAPE RECORDER Small voice activated recorder, nicro cassette complete with headphones. £28.99 ref MAR29P1 POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9 COMPOSITE VIDEO KIT. Converts composite video into sepa-

and video. 12v DC. £12.00 REF: MAG8P2. VENUS FLY TRAP KIT Grow your own carnivorous plant with this simple kit £3 ref EF34

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 30mA. Bargain price just £5.99 ea REF MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4,99. ref MAG5P13 ideal for experimenters 30 m for £12.99 ref MAG13P1 ELECTRONIC ACCUPUNCTURE KIT Builds into an ele ctronic version instead of needles| good to experiment with, £9 ref 7P30

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £9 ref 7P36. HIGH POWER CATAPULTS Hinged arm brace for stability, pered steel yoke, super strength latex power bands. Departure ed of ammunition is in excess of 200 miles per hourl Range of over 200 metres| £8.99 ref R/9.

COMPAQ POWER SUPPLIES WITH 12V DC FANS Ex equipment psu's, some ok some not but worth it for the fan alone! obably about 300 watt PC unit with IEC input. £3.50 each ref CQ1 9-0-9V 4A TRANSFORMERS, chassis mount. £7 ref LOT19A. FRESNEL PERSPEX SCREENS 11"x11"x316" as used in overhead projectors etc. New. £19 ref FRESN

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb forjust £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref OT17

SOLID STATE RELAYS CMP-DC-200P 3-32vdc operation, 0-200vdc 1A £2.50 SMT20000/3 3-24vdc operation, 28-280vac 3A £4.50



WE BUY SURPLUS STOCK FOR CASH SURPLUS STOCK LINE 0802 660335

# **Discrete transforms**

If a dsp processor analyses a waveform it cannot "look ahead" to examine the whole waveform, all it can do is look at the signal level now plus a data array of historical values which describe the shape of the waveform over a specific period. To be able to analyse the signal fully, the dsp must be able to process sufficient sampling points to cover the entire square wave from its start point to the end point. Obviously the more complex a waveform is, the more sampling points are necessary and the larger the number of computations the processor has to cope with. Equally the samples must accurately describe the waveform shape without missing any fast transient edges.

All this applies to repetitive waveforms but not to the more random waves that dsp is really targeting. If a single sentence of speech is considered, there is virtually nothing within it that can obviously be described at repetitive, yet the sentence is rich with fundamental frequencies and associated harmonics, all of which can be extracted and either displayed or mathematically adapted.

Try connecting a microphone to a spectrum analyser and looking over the range 50Hz to 20kHz. Speaking into the microphone will show a continually varying display of frequencies. This is an important aspect of the digital processing of a real time signal - the information is not constant as in the square wave analysed above. Thus a modification to the Fourier transform is needed, one that can cope with real world signals with time varying frequency components. The discrete Fourier transform is used to do this, and it works on a range of data samples during a discrete time period that can be used to interpret a portion of the incoming waveform and extract the frequency and phase information. Thus the dsp processor has to extract information from a small time window that contains a limited number of digitised samples of data. The more samples in a given window means a more accurate frequency description equally a bigger window will also increase the accuracy.

The easily understood means to carry out a Fourier transform on a set of sampled data is to generate data points for sinewaves of different frequencies which fit exactly into the length of the sample. The lower frequency limit is where one cycle fills the available space, while the upper limit is either the highest frequency of interest, or when there are only two samples per cycle.

These sinewaves are multiplied by the data samples point by point, and the amplitude of the resulting signal is computed. The same is done with cosine waves. Then, for each frequency computed, there is a sine and a cosine amplitude. This defines the amplitude and the phase, necessary to reconstitute the signal in time from frequency information.

Of course, to be useful the process is continuous, and as soon as one set of sampled data has been computed a further set is processed, to give a time varying set of frequency and phase components, like a spectrum analyser but with the addition of phase information. Often successive sets of data will overlap, to give a better representation of the waveform being processed.

This can be useful if, for example, a very sharp cutoff filter is required. For a lowpass filter, all that is necessary is to ignore frequencies above the cutoff point, then reconstruct the time varying waveform from the sine and cosine components from below the cutoff point. This would appear to be a perfect filter, but it is not because of the finite number of samples in a given window, and because not every frequency component in the



input signal has a whole number of cycles fitting within the set of samples used.

Also, it is fundamental to the principle of a Fourier transform that it is carried out on a waveform that repeats. Clearly speech or music waveforms do not fit this criterion, so that the answer is an approximation to the truth rather than being perfect. One way to improve this situation is to use a windowing function before the Fourier transform. This is effectively a means of scaling the data samples so that the ones at the beginning and end of the sequence are reduced in amplitude relative to the ones at the centre. This artificially makes the samples seem to contain only waves with whole numbers of cycles fitting in the window. Then the data is moved along by one sample and the whole process is carried out again.

This all takes a great deal of processing, and a typical DSP chip might only be able to deal with signals up to a few tens of hertz using the straightforward approach to the Fourier transform. However, looking at the maths carefully, it is discovered that the straightforward approach involves much duplication. An improved numerical technique called the fast Fourier transform has been developed. This reduces the computation to a series of pairs of additions, for which the only difficulty is that they are not done on consecutive addresses. Therefore many DSP chips have a special addressing mode called bit swapped addressing which automatically addresses the correct data points without extra machine samples. The fast Fourier transform is then a rapid and practical means to process signals, and it is widely used.

# Image processing

There are a number of ways to process images so that they can be transmitted in less bandwidth. A widely used technique, typical of the field, is the discrete cosine transform. This analyses blocks of pixels to extract their frequency components, after which the higher frequency parts can be processed to reduce the total bandwidth requi**rement.** There are two major approaches to this: one is simply to **ignore** high frequency components, perhaps below a certain **ampli**tude. The other is to make use of the fact that the high frequency components are almost always of a lower amplitude than the rest of the signal and assign reduced length bit sequences to them. This is just a sample of what dsp is and can do. As mentioned in a previous editorial, dsp chips are now available to carry out all the functions of television intermediate frequency GAS HOBS Standard domestic units, new and boxed, 3 burner, household gas, brown. Bargain at just £12.95 ref BAR318

INFRA RED FILM 6" square piece of flexible infra red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc to infra red output only using standard light bulbs Easily cut to shape. 6" square £15 ref IRF2

HYDROGEN FUEL CELL PLANS Loads of information on hydrogen storage and production. Practical plans to build a Hydrogen fuel cell (good workshop facilities required) £8 set ref FCP1

STIRLING ENGINE PLANS Interesting information pack covering all aspects of Stirling engines, pictures of home made engines made from an aerosol can running on a candlel £12 ref STR2 12V OPERATED SMOKE BOMBS Type 3 is a 12v trigger and 3 smoke cannisters, each cannister will fill a room in a very short space of timel £14.99 ref SB3. Type 2 is 20 smaller cannisters (suitable for simulated equipment fires etc) and 1 trigger module for £29 ref SB2 Type 1 is a 12v trigger and 20 large cannisters £49 ref SB1

HI POWER ZENON VARIABLE STROBES Useful 12v PCB fitted with hi power strobe tube and control electronics and speed control potentiometer. Perfect for interesting projects etc 70x55mm 12vdc operation. £6 ea ref FLS1, pack of 10 £49 ref FLS2

NEW GEIGER COUNTERS IN STOCK Hand held unit with LCD screen, auto ranging, low bettery alarm, audible 'click' output. New and guaranteed, £129 ref GE1

RUSSIAN BORDER GUARD BINOCULARS £1799 Probably the best binoculars in the world! ring for colour brochure.

RUSSIAN MULTIBAND WORLD COMMUNICATIONS RECEIVER, Exceptional coverage of 9 wave bands, (5 short, 1 LW, 1FM, 1MW) internal fertile and external telescopic aerials, mains/ bettery. E45 ref VEGA

NEW LASER POINTERS 4.5mw, 75 metre range, hand held unit runs on two AA batteries (supplied) 670nm. £29 ref DEC49 HOW TO PRODUCE 35 BOTTLES OF WHISKY FROM

HOW TO PRODUCE 35 BOTTLES OF WHISKY FROM A SACK OF POTATOES Comprehensive 270 page book covers all aspects of spirit production from everyday meteriets. Includes construction details of simple stills etc. £12 ref MS3

NEW HIGH POWER MINI BUG with a range of up to 800 metres and a 3 days use from a PP3 this is our top selling bugi less than 1" square and a 10m voice pickup range. £28 Ref LOT102.

BUILD YOU OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators and propellors. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81 PC KEYBOARDS PS2 connector, top quality suitable for all 286/

386/486 etc £10 ref PCKB. 10 for £65. NEW LOW COST VEHICLE TRACKING TRANSMITTER

KIT £29 range 1.5-5 miles, 5,000 hours on AA betteries, transmita info on car direction, left and right turns, start and stop information. Works with any good FM radio, £29 ref LOT101a HIGH SECURITY ELECTRIC DOOR LOCKS Complete

HIGH SECURITY ELECTRIC DOOR LOCKS Complete brand new Italian lock and latch assembly with both Yale type lock (keys inc) and 12v operated deadlock. £10 ref LOT99

\*NEW HIGH POWER WIRELESS VIDEO AND AUDIO BUG KIT 1/2 MILE RANGE Transmits video and audio signals from a minsture CCTV camera (included) to any standard television! Supplied with telescopic aerial. £169

CCTV PAN AND TILT KITMotorize your CCTV camera with this simple 12vdc kit. 2 hermentically sealed DC linear servo motors 5mm threaded output 5 secs stop to stop, can be stopped any where, 10mm travel, powerful. 812 crd LOT125

CCTV CAMERA MODULES 46X70X29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video utput is 1v pp (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

IR LAMP KIT Suitable for the above camera, enables the camera to be used in total darkness! £6 ref EF138

UK SCANNING DIRECTORY As supplied to Police, MOD,M15 and GCHQI coverers everything from secret government frequencies, eye in the sky, prisons, multitary avised on etc 216.50 ref SCANB INFRA RED POWERBEAM Handheid battery powered lamp, 4

INFRA RED POWERBEAM Handheld battery powered lamp, 4 inch reflector, gives out powerful pure infrared light! perfect for CCTV use, nightstights etc. £29 ref PB1.

SUPER WIDEBAND RADAR DETECTOR Detects both radar and laser , X K and KA bands, speed cameras, and all known apeed detection systems. 360 degree coverage, front & an waveguides,

# 1.1"x2.7"x4.8" fits on sun visor or death £149 ref CHIEFTAN TANK DOUBLE LASERS 9 WATT+3 WATT+LASER OPTICS

Could be adapted for laser listener, long range communications etc Double beam units designed to fit in the gun barret of a tank, each unit has two semiconductor lasers and motor drive units for alignement. 7 mile range, no circuit diagrams due to MOD, new price £50,000° us? £199. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x3 watt, 900m wavelength, 28 vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from transfer. E109 for one. Berl L 074.

Augusta, E. 159 for one, Ref 2014. NEW LOW PRICED COMPUTER/WORKSHOP/HI-FI RCB UNITS Complete protection from faulty equipment for everybody! Inline unit fits in standard IEC lead (extends it by 750mm), fitted in less than 10 seconds, reservices button, 10A rating, E6, 99 each ref LOT5. Or a pack of 10 at £49,90 ref LOT6. If you want a box of 100 you can have one for £250!

TWO CHANNEL FULL FUNCTION B GRADE RADIO CONTROLLED CARS From World famous manufacturer these are returns so they will need attention (usually physical damage) cheap wey of buying TX and RX plus servos etc for new projects etc. £12 each sold as seen rof LOT2.

MAGNETIC CREDIT CARD READERS AND ENCODING MANUAL £9.95 Cased with flyleads, designed to read standard credit cards! complete with control elctronics PCB and manual covering everything you could want to know about whats hidden in that magnetic strip on your card! just £9.95 ref BAR31

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74



HIGH POWER DC MOTORS, PERMANENT MAGNET 12-24v operation, probably about 1/4 horae power, body measures 100m X75mm with a 60mm x5mm output shaft with a machined flat on it. Foing is simple using the two threaded bolts protunding from the front of the motor 4mm x 12mm). These motors are perfect for model engineering etc:they may even be suitable as a cycle motor? We expect high demand so if you would like one or think you may require one in the future place your ordertoday! E22 ref MOT4 10 pack£185 ref MOT55 ELECTRONIC SPEED CONTROLLER KIT For the above motoris £19 ref MAG17. Save£5 if you buy them both together, 1 motor plus aboed controller mp is £41. offer price £36 ref MOT5A

RUSSIAN 900X MAGNIFICATION ZOOM MICROSCOPE metal construction, built in light, mirror etc. Russian shrimpfarm1, group viewing screen, lots of accessories. £29 ref ANAYLT.

AA NICAD PACK Pack of 4 tagged AA nicads £2.99 ref BAR34 RUSSIAN NIGHTSIGHTS Model TZS4 with infra red illuminator, viewa up to 75 metres in full darkness in infrared mode, 150m range, 45mm iens, 13 deg angle of view, focussing range 1.5mto infinity, 2AA betteries required. 550g weight, £199 ref BAR51.1 years werranty LIQUID CRYSTAL DISPLAYS Bargain prices, 20 character 2 line, 63x19mm £3.99 ref SMC2024A 16 character 4 line, 62x25mm £5.99 ref SMC1640A TAL-1, 110MM NEWTONIAN REFLECTOR TELESCOPE Russian. Superb astronomical 'scope, everything you need for some serious star gazingl up to 169x magnification. Send or fax for further

serious star gazingi up to 169x magnification. Send or fax for further information.20kg, 885x80x1650mm ref TAL-1, £249 YOUR HOME COULD BE SELF SUFFICENT IN ELECTRICITY Comprehensive plans with loads of info on designing

systems, panels, control electronics etc £7 ref PV1



COLOUR CCTV VIDEO CAMERAS, BRAND NEW AND, CASED, FROM £99. Works with most modern video's, TV's, Composite monitors, video grabber cards etc Pal, 1v P-P, composite, 750hm, 1/3" CCD, 4mm F2.8, 500x582, 12vdc, mounting bracket, auto shutter, 100x50x180mm, 3 months warranty,1 off price £119 ref XEF150, 10 or more £99 ea 100+ £89

YUASHA SEALED LEAD ACIDS FROM £2.50 12v 6.5Ah ex equipment batteries to clear at just £9.99 for a pack of fourt ref XX1

# A MAGNET THAT LIFTS 33 KILO'S! Just in this week are these incredible magnets that lift 33

kilo's! Price is £14.99 ref MAG33 25 SQUARE FOOT SOLAR ENERGY BANK KIT 100 6"x6"

5v Amorphous 100mA panels, 100 diodes, connection details etc to build a 25 square foot solar cell for just £99 ref EF12. CONVERT YOUR TV INTO A VGA MONITOR FOR £25! Converts a colour TV into a basic VGA screen Complete with built in

Converts a colour TV into a basic VGA screen. Complete with built in peu, lead and swere... Idealfor laptops or a cheap upgrade. Supplied in kill form for home assembly. SALE PRICE 225 REF SA34 "15 WATT FM TRANSMITTER Already assembled but some

RF knowledge will be useful for setting up. Preamp reg d, 4 stage 80-108mbz, 12-18vdc, can use ground piane, yagior dipole £69 ref 1021 \*4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter kit. 3 RF stages, mic & audio preamp included £24 ref 1028 YUASHA SEALED LEAD ACID BATTERIES 12v 15AH at \$18 ref | 0.78 and below parc fv 10AH at \$5 a pair

£18 refLOT8 and below spec 6v 10AH at £5 a pair ELECTRIC CAR WINDOW DE-ICERS Complete with cable plug etc SALE PRICE JUST £4.99 REF SA28

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2wett. £12.99 REF AUG10P3. SOLAR POWER LAB SPECIAL You get 2 6\*86\* 6v 130mA cells, 4LED's wire, buzzer, switch +1 relay or motor. £7.99 REF SA27 SOLAR NICAD CHARGERS 4 x AA size £9.99 ref 6P476, 2 x



C size £9.99 ref 6P477

GIANT HOT AIR BALLOON KIT Build a 4.5m circumfrence, fully functioning balloon, can be launched with home made burner etc. Reusable (until you loose it!) £12.50 ref HA1 AIR RIFLES. 22As used by the Chinese army for training puppees.

AIR NIFLES .22.48 used by the Chinese army for training pupples, so there is a lot about 13.99.5 Ref EFR. 500 pellets £4.50 ref EFR0. \*NEW MEGA POWER VIDEOAND AUDIO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 500m rangel (tune TV to channel 31) 12 v DC op. Price is £65 REF: MAG15 12v psu is £5 extra REF: MAG522

op. Proc is £65 REF: MAG15 12v psu is £5 extra REF: MAG5P2 \*MINATURE RADIO TRANSCEIVERS A pair of walkie talkies with a range up to 2 km in open country. Units measure 22x52x155mm. Including cases and earpices. 2xPP3 red(4.£37.00 pr.REF: MAG30 \*FM TRANSMITTER KIT housed in a standard working 13A adaptent the bug runs directly off the mains so lasts forevert why pay £700? or price is £18 REF: EF62 (kit) Transmits to any FM radio. Buit and tested version now available at £45 ref EXM34

\*FM BUG BUILT AND TESTED superior design to kit. Supplied to detective agencies. 9v battlery reg'd. £14 REF: MAG14

GAT AIR PISTOL PACK Complete with pistol, darts and pelleta £14.95 Ref EF828 extra pellets (500) £4.50 ref EF80.

HEAT PUMPS These are mains operated air to air units that consist of a aluminium plate (cooling side) and a radiator (warming side) connected together with a compressor. The plate if inserted into water will freeze it. Probably about 3-400 watts so could produce 1kw in ideal conditions. £30 ref HP1

3 FOOT SOLAR PANEL Amorphous silicon, 3' x 1' housed in an aluminium frame, 13v 700mA ouput. £55 ref MAG45

SOLAR/WIND REGULATOR Prevents batteries from over charging. On reaching capacity the regulator diverts excess power into heat avoiding damage. Max power is 60 watts. £27.99 ref S/CA11-/05 4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £24.95 ref R/7.

NICAD CHARGERS AND BATTERIES Standard universal mains operated charger, takes 4 batts + 1 PP3, £10 ref PO11D, Nicads-AA size (4 pack) £4 ref 4P44, C size (2 pack) £4 ref 4P73, D size (4 pack) £9 ref 9P12.

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE! The new multiband 2000 rader detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka banda, 3 mile range, lover the hilf 'around bends' and 'rear trap facilities, micro size just 4.25"x2.5"x.75",

Can pay for itself in just one day! £89 ref EP3. **STEREO MICROSOPES BACK IN STOCK** Russian, 200x complete with lenses, lights, filters etc etc very comprehensive microscope that would normally be around the £700 mark, our price is just £290 (full money back guarantee) full details in catalogue. **SECOND GENERATION NIGHT SIGHTS FROM £748** 

RETRON Russian night sight, 1.8x, infra red lamp, 10m-inf, standard M42 lons, 1.1kg, 5349 ref RET1

MAINS MOTORS 180 RPM 90X70mm, 50X5mm 50X5mm output shaft, start cap included. £22 ref MGM1

# PC POWER SUPPLIES, CUSTOMER RETURNS, ALL FAN COOLED, OUR CHOICE, BARGAIN AT 8 PSU'S FOR £9.99 REF XX16

LOW COST CORDLESS MIC 500' range, 90 - 105mhz, 115g, 193 x 26 x 39mm, 9v PP3 battery required. £17 ref MAG15P1 JUMBO LED PACK 15 10mm bicolour leds, plus 5 giant (55mm) seven segment displays all on a pcb £8 ref JUM1. Pack of 30 55mm seven seg displays on pcbs is £19 ref LED4, pack of 50 £31 ref LED50 12VDC 40MM FANS MADE BY PANAFLO, NEW.£4. REF FAN12



WIND GENERATORS 380 WATT

1.14 metre dia blades, carbon matrix blades, 3 year warranty, 12vdc output, 24v version available, control electronics included, brushless neodymlum cubic curve alternator, only two moving parts, maintenance free, simple roof top installation, start up speed 7mph, max output (30mph) 380w. £499 ref AIR1

Check out our WEB SITE

full colour interactive 1997 catalogue

http://www.pavilion.co.uk/bull-electrical

FREE COLOUR CATALOGUE WITH EVERY ORDER

SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK WE BUY SURPLUS STOCK FOR CASH SURPLUS STOCK LINE 0802 660335 amplifiers, with very good filter response. This has for some years been done using surface acoustic wave devices, but inevitable dsp will take over in an increasing number of television sets.

Digital television will only be practical because of the substantial bandwidth reduction possible due to dsp, thought the actual processing used will be multi-stage and more complex than just a discrete cosine transform.

Another function available from dsp is to correct for unpleasant frequency and phase responses by applying the reverse function. Thus it is possible to cancel the effects of room resonance etc much more accurately with DSP then with a graphic equaliser. It is also possible to do this automatically, so that the correction characteristics can adapt to a dance floor filling up during the evening.

Echo cancellation can be carried out conveniently using DSP. An algorithm analyses the time delay, amplitude, and frequency response of any echo on, for example, a telephone line, and subtracts a suitable signal to cancel the echo. This is important to permit modems to run at higher speeds.

As time goes on, more signal processing previously done by analogue electronics will instead be carried out using DSP. In most respects this will result in improved performance for less cost. The slight downside, which it is wise to try to avoid, is to put too trivial functions into DSP, so that a signal may be digitised, processed, and turned back into analogue, all to do what could be done just as well with one op-amp and four passive components.

DSP is not a panacea, but it is an increasingly important aspect of signal processing, enabling otherwise impossible functions to be carried out cheaply. Like the conventional microprocessor, DSP chips will soon be widely found in consumer electronics.

# In the market

I have selected three examples from major semiconductor manufacturers to give an outline of what is happening in the field. The manufacture of dsp chips is now a widespread field undertaken by many semiconductor companies.

Texas Instruments have introduced a new dsp chip, the TMS320C6x, which is aimed at the digital cellular telephone market - not the handsets but base stations! The high points are the 200MHz operation, and an architecture called Very Long Instruction Word, which packs up to eight 32-bit instructions into a cycle. The performance is rated at 1600 mips, and it is able to carry out a 1024 point complex fast Fourier transform in 70ns.

The chip includes dual buffered serial ports intended to interface to standard telecommunication systems, and can implement a base station with 30 full GSM channels with a single dsp chip.

Another chip in the Texas range, the TMS320C54x, is used in a well-known range of 33.6kbps modems designed to be upgradable to 56kbps.

Analog Devices have recently added a lower cost dsp device to their high-power family, named SHARC (presumably from the Super Harvard Architecture). This is intended for applications such as home theatre, professional audio mixers, office scanners and printers among many others. Harvard architecture machines store code and data in separate memory banks with separate busses to speed access to program and data.



This is no device for the amateur, though. Costing \$49 in quantity, the chip is supplied in a 240 lead quad flat pack.

The ADMC300 series is aimed at a very different function, that of motor control. By measuring various electrical parameters it is possible to determine the speed of an ac motor, how close it is to stalling, and so on, but to do this without sensors on the motor a dsp chip is needed. The ADMC incorporates five channels of 12-bit sigma-delta analogue to digital conversion for the necessary measurements, with an interface designed for position encoders for applications requiring this function.

Analog Devices even have a chip (the ADSP-2104) whose applications include use in toys. Other uses include telephone answering machines and music synthesisers. The chip provides 20 mips for \$4.50 in quantity

Another semiconductor giant, Motorola, has recently released their DSP56300 family, whose features include one instruction per clock cycle, a low power consumption per MIPS, and carefully chosen instruction sets to give enhanced performance per mips. The chip is designed to carry out in one instruction what many chips must do in two.

The chip runs at 81MHz, but uses an internal phase locked loop frequency multiplier to permit the use of a lower frequency crystal. Applications at which the chip Is aimed include DVD (digital versatile disc), HDTV, and receivers incorporating Dolby AC3, for which Dolby labs have certified it.

# In the market

I have selected three examples from major

semiconductor manufacturers to give an outline of what is happening in the field. The manufacture of dsp chips 'is now a widespread field undertaken by many semiconductor companies.

Texas Instruments have introduced a new dsp chip, the TMS320C6x, which is aimed at the digital cellular telephone market - not the handsets but base stations! The high points are the 200MHz operation, and an architecture called Very Long Instruction Word, which packs up to eight 32-bit instructions into a cycle. The performance is rated at 1600 mips, and it is able to carry out a 1024 point complex fast Fourier transform in 70ns.

The chip includes dual buffered serial ports intended to interface to standard telecommunication systems, and can implement a base station with 30 full GSM channels with a single dsp chip.

Another chip in the Texas range, the TMS320C54x, is used in a well-known range of 33.6kbps modems designed to be upgradable to 56kbps.

Analog Devices have recently added a lower cost dsp device to their high-power family, named SHARC (presumably from the Super Harvard Architecture). This is intended for applications such as home theatre, professional audio mixers, office scanners and printers among many others. Harvard architecture machines store code and data in separate memory banks with separate busses to speed access to program and data.

This is no device for the amateur, though. Costing \$49 in quantity, the chip is supplied in a 240 lead quad flat pack.

The ADMC300 series is aimed at a very different function, that of motor control. By measuring various electrical parameters it is possible to determine the speed of an ac motor, how close it is to stalling, and so on, but to do this without sensors on the motor a dsp chip is needed. The ADMC incorporates five channels of 12-bit sigma-delta analogue to digital conversion for the necessary measurements, with an interface designed for position encoders for applications requiring this function.

Analog Devices even have a chip (the ADSP-2104) whose applications include use in toys. Other uses are telephone answering machines and music synthesisers. The chip gives 20 mips for \$4.50 in quantity

Another semiconductor giant, Motorola, has recently released their DSP56300 family, whose features include one instruction per clock cycle, a low power consumption per MIPS, and carefully chosen instruction sets to give enhanced performance per mips. The chip is designed to carry out in one instruction what many chips must do in two.

The chip runs at 81MHz, but uses an internal phase locked loop frequency multiplier to permit the use of a lower frequency crystal. Applications at which the chip is aimed include DVD (digital versatile disc), HDTV, and receivers incorporating Dolby AC3, for which Dolby labs have certified it.



# **Electronics Principles** 4.0

For Windows 3 95 8 NT of studying or If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.



# The popular Electronics Principles 3.0

£49.95\*

A comprehensive Introduction to ac & dc circuit theory. Ohm's law, voltage, current. Phase angles, alternating voltages and currents, RCL series and parallel networks, reactance and Impedance. Active devices - diodes, bi-polar and field effect transistors, SCR's and OP-Amps. Logic gates, counters, shift registers and binary, octal and hex number conversions.

There are nearly three hundred analogue and digital main topics, all with fully interactive graphics in colour, with supporting calculations that reflect your inputs along with notes to explain each topic.

- All Inputs & outputs use electronics symbols.
- Hundreds of electronics formulae available for circuit nvestigation.
- Ideal for students and hobbyists who require a quick and easy way to get to grips with a particular point.
- Explore the subject as the interactive graphics are redrawn showing phase angles, voltage and current levels or logic states for your chosen component values.
- Generate hard copies of graphics, text and calculations.

# Schools and Colleges. A fully interactive 'electronics textbook' on the screen.

OHP slides and student handouts within minutes. Multi-user network version available.

Electronics Principles 4.0 now has on extended range of fully Interaction analogue and digital topics. From current flow, and, do circuits flyouary switching and transistor operation to passive and active fillers Logic begins with simple gates through bihary hex and octal number conversion, addition, and subtraction to Boolean algebra. Plus micropiocessor and microcomputer operation, registers, arithmètic and logic unit, ROM, RAM. Addressing modes and full instruction set which can be simulated on the screen, All version 3.0 topics are included within this program.

Currently used in hundreds of UK and overseas schools & colleges to support GCSE, A-level, BTEC, City & Guilds and university foundation courses. Also NVQ's and GNVQ's where students are required to the ve an understanding of electronics principles.



# Series Resistors.

- Total 'R' = 4700 + 2500 + 100 = 7300 = 7.3
- V = 3.424658E-03 × 7300 ≈ 25 = 25V
- $1 = \frac{25}{7300} = 3.424658E \cdot 03 = 3.4247 mA$
- $Total 'R' = \frac{25}{3.424658E \cdot 03} = 7300 = 7.3k$
- V1 = 4700 × 3.424659E-03 = 16.09589 = 16.0959V V2 = 2500 × 3.424658E-03 = 8.561644 = 8.5616V
- $V_2 = 2500 \times 3.4246562 + 0.3 = 6.361644 = 6.56164$  $V_3 = 1.00 \times 3.424658E + 0.3 = .3424658 = 342.4658mV$
- V3 = 100 × 3.424658E-03 = .3424658 = 342.4658mV

EPT Educational Software. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ. Tel/Fax: 01376 514008. e-mail sales@eptsoft.demon.co.uk \* UK & EC countries add £2 per order for post & packing. VAT should be added to the total. Outside Europe £3.50 for air mail postage by return. Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date. Cheques & Postal Orders should be made payable to EPT Educational software.

24-

# A Total Harmonic Distortion Meter

For testing audio amplifiers, Robert Penfold's Total Harmonic Distortion (THD) meter incorporates a good quality notch filter and an audio millivoltmeter

hen dealing with audio equipment there are several important parameters that often need to be measured. Most of these, such as frequency response and voltage gain, can be measured using just a sinewave generator and some form of audio millivolt meter. Total harmonic distortion (THD) is slightly more difficult to measure as it also requires a high quality audio notch filter. Furthermore, the quality of the audio signal generator is much more important for distortion measurement than it is for frequency response testing, etc. There is no point in trying to measure 0.1 percent distortion using a signal generator that itself has about 1 percent distortion on its sinewave output signal. Fortunately, most modern signal generators have very low distortion levels, and even some quite low cost units have a distortion figure of only about 0.01 percent at middle audio frequencies. This is more than adequate to measure the THD of all but the highest quality audio equipment. Note, though, that most function generators do not have low distortion output signals and are unsuitable for distortion measurements on all but the cheapest of audio equipment. Sinewave distortion figures of around 0.5 to 2 percent are quite common for this type of equipment.

The THD meter featured here consists of a high quality notch filter and an audio millivolt meter. The filter is tunable from about 100Hz to 10kHz in two ranges. The audio millivolt meter has four ranges with full scale values of 1mV, 10mV, 100mV, and 1 volt rms. These correspond to full scale distortion levels of 100 percent, 10 percent, 1 percent, and 0.1 percent. A separate signal generator is required, and any good quality Wien type audio generator should suffice.

# THD basics

The two main forms of audio distortion are total harmonic and intermodulation distortion. Intermodulation distortion is where two frequencies are mixed to produce sum and difference frequencies (for example, signals at 1kHz and 3kHz would produce new signals at 2kHz and 4kHz). Total harmonic distortion is the more simple form, and it results in the generation of harmonics (multiples of the input frequency). For example, with a 1kHz test signal the harmonics will be at 2kHz, 3kHz, 4kHz, etc. This is the type of distortion normally specified in data sheets, amplifier specifications, etc. It is relatively easy to measure, and the block diagram of figure 1 shows the basic arrangement used.

The amplifier under test is fed with a high quality sinewave signal. The salient point here is that a sinewave signal consists of just the fundamental frequency, and has no harmonic content. The signal generator is set to provide the required output level from the







amplifier, and if necessary a dummy load resistor is used at the output of the amplifier. When testing a preamplifier it may not be necessary to include this load resistor, but it will invariably be required when testing power amplifiers. This is due to the fact that power amplifiers provide greatly reduced performance when driving a low impedance load, which is of course the way that they will operate in normal use. Without the dummy load resistor the test will give a highly flattering account of the amplifier's performance.

A variable attenuator at the output of the amplifier enables the signal voltage to be reduced to a convenient reference level. This distortion meter is designed to operate at an input level of 1 volt rms, and the output of the attenuator is switched direct to the input of an audio millivolt meter so that the correct signal voltage can be set. The meter is then switched to monitor the output of the amplifier via a high quality notch filter. The tuning control of the notch filter is carefully adjusted to the test frequency so that the signal from the audio generator is removed. In practice it requires some careful adjustment of tuning and balance controls in order to obtain a really high degree of attenuation, but the fundamental signal can be reduced by about 80 dB. This application requires a very high quality filter as it must provide around 80 dB of attenuation in the notch, but it must provide no significant attenuation at twice the notch frequency or it will significantly reduce any second harmonic component in the signal.

With the fundamental signal removed, all that remains are the harmonics generated by distortion in the amplifier, plus any noise generated by the amplifier. This gives a figure for the noise and distortion of the amplifier, and this is called the distortion factor. The total harmonic distortion is equal to the distortion factor minus the noise level. The noise revel can be determined by disconnecting the signal generator from the input of the amplifier, short-circuiting the amplifier's input, and then measuring the noise using the audio millivolt meter. We are assuming here that the

signal generator is perfect, and that it does not produce any noise or distortion of its own. In reality the noise and distortion from the signal generator will sometimes be a significant factor, and must be determined by initially measuring the direct output from the generator. Where necessary, the noise and distortion level of the signal generator itself can then be deducted from the figure obtained when testing an amplifier.

When you start testing modern audio equipment you soon discover that it is quite common for low cost equipment to have more mains hum on the output signal than general background noise and distortion. In fact the hum level can sometimes be many times higher than the harmonic distortion, resulting in the distortion products being swamped by the hum. In such cases it is only possible to make an accurate assessment of the distortion level if a hum filter is added ahead of the distortion meter circuit. Such a filter should be regarded as an essential item rather than as an optional extra if you intend to test a lot of "budget" audio equipment.

# **Circuit operation**

The circuit diagram for the filter section of the unit appears in figure 2. The filter is based on a Wien network, which is the same type of network that is used as the basis of most high quality audio signal generators. In this case the two sections of the Wien network are fed with anti-phase signals, as shown in the skeleton circuit of figure 3. At a certain frequency there will be zero phase shift through both sections of the network, And precise cancelling of the two signals will result provided the signal levels are accurately balanced. This balancing is achieved by having the gain of the inverting amplifier variable, so that it can be adjusted to precisely match the amplitudes of the two signals. This produces a notch of very high attenuation at the frequency where zero phase shift occurs, but at other frequencies the amount of phase shift is unequal, and little cancelling of the signals occurs.

If we now consider the circuit of figure 2, VR1 is the variable input attenuator. From here the signal is coupled to a buffer amplifier which is based on IC1 and operates in the inverting mode. The signal is then applied to the main filter circuit which has IC2 as the non- inverting buffer stage and IC3 as the inverting mode amplifier. VR3 and VR4 enable the voltage gain of the inverting mode amplifier to the varied, and these two potentiometers respectively act as the fine and course balance controls. The restive elements in the Wien network are R5 plus VR2a, and R10 plus VR2b. VR2 is, of course, the tuning control. S1 enables either C4 and C7, or C5 and C8 to be used as the capacitors in the main network. This gives the unit its two tuning



ELECTRONICS TODAY INTERNATIONAL



ranges of approximately 100Hz to 1kHZ (C5-C8) and 1kHz to 10kHz (C4 and C7). IC4 simply acts as a buffer stage at the output of the filter. Either the direct output of the input attenuator or the filtered signal can be selected using S2.

There is a slight problem with the basic filter circuit in that it provides about 6dB of attenuation at twice the notch frequency, which means that it would tend to reduce any second harmonic distortion and produce an unrealistically low total harmonic distortion figure. This problem is overcome by introducing some overall negative feedback to the circuit, and this feedback is provided by R11. As one would expect, the negative feedback reduces the voltage gain of the circuit and tends to flatten the frequency response. The reduced voltage gain simply brings the gain down to the required level of unity, and the flattening of the frequency response results in losses at double the notch frequency being reduced to about 1 dB. This level of attenuation is not high enough to significantly affect results and is therefore perfectly acceptable. One slight drawback of using the negative feedback is that it also tends to reduce the amount of attenuation in the notch, but this does not prevent the circuit from achieving some 80 dB or more of attenuation if the tuning and balance controls are carefully adjusted. Anyway, it is a price that has to be paid in order to obtain low levels of attenuation at the frequencies of the harmonics. Figure 4 shows the frequency response of the prototype filter when set for a notch frequency of 1 kilohertz.

Figure 5 shows the circuit diagram for the millivolt meter section of the unit. IC5 is used as a non-inverting buffer stage that provides the circuit with a high input impedance of 500 kilohms. A high input impedance is essential as the millivolt meter circuit will otherwise significantly load the input attenuator when S2 is switched to the direct mode. This would give a jump in the input level when S2 was set back to the filter mode. An input impedance of 500 kilohms is more than adequate to ensure that there is no significant change in the signal level when S2 is operated. The output from IC5 is coupled into a conventional four





step attenuator which provides attenuation levels of zero, 20, 40, and 60dB. The basic sensitivity of the circuit is 1 millivolt rms, and the attenuator therefore provides additional ranges of 10 millivolts, 100 millivolts, and 1 volt rms. These correspond to full scale distortion figures of 0.1 percent, 1 percent, 10 percent, and 100 percent. Having the attenuator in a low impedance part of the circuit enables fairly low values to be used, thus avoiding the need for any frequency compensation capacitors.

IC6 is used as a simple non-inverting amplifier which has a voltage gain of about 40dB and an input impedance of 470 kilohms. This high input impedance ensures that there is no significant loading on the attenuator and that its accuracy is not impaired. SK2 enables the filtered signal to be monitored using an oscilloscope, or the signal can be monitored via a crystal earphone (but do not connect any other type of headphones or earphone to SK2). Testing the filtered signal "by ear" or using an oscilloscope can be quite revealing as it will show the nature of the noise and distortion signal. If the signal is predominantly mains hum or "hiss" type noise, it will be immediately obvious. The meter only shows you the level of the noise and distortion, with no hint as to its exact nature. You may also find that it is easier to null the fundamental signal "by ear" rather than using the meter as a signal level indicator.

IC7 is used in a conventional full-wave precision rectifier. A passive rectifier circuit based on semiconductor diodes gives inadequate performance due to the non-linearity of the diodes. In the case of ordinary silicon diodes this non-linearity is very severe



indeed, and a forward voltage of about 0.5 volts or so is needed before any significant current starts to flow. Germanium diodes have much better performance in this respect, but they still provide something well short of good linearity. The standard approach to counteracting this non-linearity is to use the diodes in the negative feedback circuit of an amplifier. The general idea is to have non-linear feedback that counteracts the distortion through the diodes. This distorts the output signal of the amplifier in such a way that it accurately balances the non-linearity of the diodes and gives linear scaling on the meter.

In this precision rectifier circuit diodes D1, D2, D5, and D6 form a conventional bridge rectifier. Germanium diodes are used in the rectifier circuit as their better linearity places less demand on the amplifier, and provides better performance at high frequencies

Resistors	
	ercent metal film)
R1,5,6,10,15,22	10k
R2,3,7,8	33k
R4	27k
R9	12k
R11	15k
R12	4k7
R13,14	1M
R16,24	1k
R17,23	100R
R18	11R
R19,20	39k
R21	470k
R25	150R
	resonation from the rest will a net
Potentiom	
VR1	10k log rotary
VR2	100k lin dual gang rotary
VR3	1k lin rotary
VR4	10k lin rotary
VR5	220R min hor preset
Capacitors	and the second
C1	100u 25V radial elect
C2	1u 50V radial elect
C3,6	4u7 50V radial elect
C4,7	1n5 polyester
C5,8	15n polyester
C9	100n ceramic
C10,14	10u 25V radial elect
C11	47n polyester
C12	2u2 50V radial elect
C13	100n polyester
C15,16	100u 16V radial elect
Semicondu	ictors
IC1,2,3,4,5,7	LF351N
IC6	NE5534AN
D1,2,5,6	OA91
D3,4	1N4148
Miscellane	ous
B1,2	9 volt (PP3 size)
S1	DPDT min toggle switch
S2	SPDT min toggle switch
S3	12 way 1 pole rotary with
	adjustable end-stop
S4	SPST min toggle switch
ME1	1mA moving coil panel meter
SK1,2	Phono socket
	about 246 x 220 x 100mm printed
	pin DIL holder control knob,

battery connector, wire, solder, etc.

**ARTS LIST for the THD Meter** 

where the open loop gain of the amplifier is relatively low. The meter (ME1) is driven from the output of the rectifier via series resistor R25. D3 and D4 provide overload protection for ME1. IC7 is used in the non-inverting mode, and the rectifier circuit is connected in a negative feedback network which has VR5 and R24 as the other elements. The closed loop voltage gain of the rectifier circuit is controlled via VR5, and this is adjusted to give the circuit the correct sensitivity. The millivolt meter circuit has a -3dB point at about 100kHz,

The circuit requires a supply voltage of at least 18 volts, and this is provided by two nine volt batteries connected in series. On the face of it a supply potential of 9 volts would be adequate, since the circuit is handling a maximum input level of 1 volt rms (about 2.8 volts peak-to-peak). However, at some points in the filter circuit the signal level is very much higher than this, and the operational amplifiers provide better performance with a higher supply voltage anyway. The current consumption of the circuit is about 12 to 14 milliamps. Two PP3 size batteries are just about adequate to supply this, but it would probably be more economic to use higher capacity batteries if the unit is likely to receive a great deal of use.

A mains power supply unit can be used, but this should have a well smoothed output. Obtaining really good results using a mains power supply can be difficult though, with the general hum and noise level severely compromising results on the one millivolt range of the unit. In many areas the mains supply seems to be contaminated with a fair amount of noise, and it can be difficult to effectively screen sensitive audio circuits from this interference. Also, using a mains power supply unit is likely to introduce problems with hum loops unless you are very careful. Using a battery supply is an easy way of ensuring that a high level of performance is attained.

# Construction

The component overlay for the printed circuit board is provided in figure 6. None of the integrated circuits are static sensitive types, but it is still advisable to fit them in DIL holders. Do not overlook the to link-wires (one just to the right of IC2, and the other above and to the right of IC4). D1, D2, D5, and D6 are all germanium diodes, and as such they are more easily damaged by overheating than silicon types. Take due care when soldering these components to the board, and try to complete each soldered joint reasonably quickly. In other respects construction of the board is perfectly straightforward.

Although the printed circuit board and batteries require only a modest amount of space, it will almost certainly be necessary to use a fairly sizeable case in order to accommodate the controls, sockets, and meter on the front panel. The prototype is housed in a metal and plastic instrument case which has a front panel measuring about 235mm by 90mm. This represents about the



minimum size that will comfortably accommodate everything, although a slightly smaller panel will be acceptable if the two sockets are relegated to the rear panel. With sensitive test equipment such as this there is some advantage in using an all metal case which will provide screening of the components and wiring. No significant problems with stray pickup were experienced



with the prototype equipment, but it is clearly not a good idea to operate the unit close to any likely sources of interference if it is housed in a non-metallic case.

Use a front panel layout that will make the unit reasonably straightforward to use, but also use one that will avoid too many long collecting wires, especially in the millivolt meter section of the unit. I used phono input and output sockets, but it is acceptable to use BNC sockets or any other type that will fit in better with your other equipment. Mounting the meter on the front panel can be slightly awkward as it requires a large circular cut-out which is 38 millimetres in diameter for a standard 60 by 45 millimetre panel meter. This can either be cut using a special hole cutting tool, or using something like a coping saw or an Abrafile. Once the large cut-out has been made the meter itself can be used as a sort of template to help locate the positions of the four small mounting holes. These are for the four threaded mounting rods that are built into the meter. These rods require three millimetre diameter mounting holes.

A substantial amount of hard wiring is required, and details of this wiring are provided in figure 7 (which should be used in conjunction with figure 6). Resistors R15 to R18 are mounted on S3, which helps to avoid problems caused by stray capacitance in the wiring. S3 is a standard 12 way 1 pole rotary switch having an adjustable and-stop, and in this case it is obviously set for four way operation. Fitting the resistors on the switch should be very easy provided the ends of the leadout wires and the tags of the switch are tinned with solder first. The rest of the wiring is perfectly straightforward, but with so much hard wiring it is obviously necessary to proceed carefully and to check everything very thoroughly once the wiring has been completed.

The 0-1 scaling of the meter is correct for the 1 percent range, and it is not difficult to convert readings into the corresponding distortion figures on the other ranges. Consequently, it is probably not worthwhile bothering with any recalibration of the meter's scale. If you should decide to do this, the front of the meter simply unclips, and removing two small screws then enables the scale plate to be slid clear of the meter movement. Rub-on transfers can then be used to add further numbers to the meter's scale, after which the meter is reassembled. Moving coil meter movements are very delicate mechanisms, and great care must be taken or the meter could be irreparably damaged.

# **Calibration and use**

The millivolt meter must be calibrated before the unit can the be used in earnest. In order to do this the unit must be fed with an audio sinewave signal having an amplitude of 1 volt ms. Most ready-made audio signal generators have accurately calibrated output attenuators that make it easy to set the required output level. This feature is absent on most home constructed generators, and with these it will be necessary to measure the output level so that it can be set with a fair degree of accuracy. Most multimeters can measure a potential of 1 volt ms with moderate accuracy, but note that many multimeters (especially the digital variety) have very restricted bandwidths and will only give accurate results if the signal generator is set at a frequency of no more than a few hundred hertz. Fortunately, any error in the calibration will not impair the accuracy of results, it will simply mean that the unit is operating at a signal level which is not precisely 1 volt ms.

Start with VR5 at a roughly middle setting, and VR1 set in a fully clockwise direction. S2 should be set so that the millivolt meter is fed direct from the wiper of VR1, and S3 is set to the 1 volt position. With a suitable test signal applied to SK1,VR5 Is then adjusted to provide a full scale reading on the meter. The unit is then ready for use.



Before making any meaningful distortion measurements it is necessary to determine the distortion level of the signal generator you will be using. This is basically just a matter of making a normal distortion measurement, but the input of the distortion meter is fed direct from the signal generator rather than via an amplifier. The distortion performance of signal generators often varies guite significantly with changes in the output frequency, and it is therefore advisable to check the distortion figure of the generator at 100 hertz, 1 kilohertz, and 10 kilohertz. In each case it is a matter of first setting the signal generator to the correct output frequency, switching S2 to the direct mode, and setting S3 to the one volt range. VR1 and the output level controls of the generator are then adjusted to produce a full scale reading on the meter.

With S2 switched to the filter setting, the tuning and balance controls of the distortion meter are carefully adjusted to produce the lowest possible reading from the meter. The millivolt meter should be set for progressively higher sensitivities as the signal level is reduced.

There is no well defined distortion level at which the audio generator becomes unusable. A distortion level of 0.1 percent may be perfectly acceptable if you will only be testing low and medium fidelity equipment, but it will be of little use for testing "state of the art" hi-fi equipment having distortion levels of around 0.01 percent. The lower the distortion factor of your audio generator, the greater the scope of the distortion meter.

# Microchip PIC and Motorola HC11 based development Tools

PIC Microcontroller Programmers Original - This is our original programmer for 16C5X, 16C5X, 16C6X, 16C7x, 16C8x, 16F8X devices. Price: £40 for the kit, or £50 ready built. Serial - This programmer programs the newest PIC devices in a single 40 pin multi-width ZIF socket. Will program: 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, PIC 14000. Also In-Circuit programming. Price : £40 for ZIF socket. Will program: 16C55X, 16C6X, 16C7X, 16C8X, 16C8X, 16C8X, 12C508, FIC 14000. Also informating programming. Finde . 240 for the kit, or 250 ready built. Introductory - Will program 8 pin and 18 pin devices : 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508, and 12C509. Price 222 for the kit (not available ready built). Note : All our programmers operate on a PC, using a standard RS232 serial interface (COM1, 2, 3, or 4). No hard to handle parallel cable swapping ! All programmers are supplied with instructions, Windows programming software, MPASM, MPSIM and PICDE (Windows based PIC assembler) **PIC or HC11 Windows Based Development:** PICDESIM and HC11DE allows assembly and simulation of your PIC or HC11 projects in

one Windows program. Incorporate multiple files, view help file information directly from the code, edit within project, build and track errors directly in the source, then simulate. Simulator allows 3 breakpoint types, follow code in the source window, set breakpoints directly in code. Run programs, or single step, or step over subroutines. Track variable values and trace for display on the Trace Analyser. Input stimuli include clocks, direct values and asynchronous serial data. Profile your program - examine frequently called routines which are timed and use the information to optimise out bottle necks. PIC Version Simulates up to 50 times faster than MPSIM ! NEW ! - 32 bit version allows full use of Windows '95/NT4.0 facilities. Cost £30.00, or £25.00 for existing and new purchasers of any of our programmers. Please specify Windows 33.1, or Windows '95 (32 bit) and either PIC or HC11 version PIC BASIC FED's PIC BASIC products - straightforward, capable, powerful, rapid development. Operating in a Windows

Development Environment our modules need no assembler or UV eraser to program your PIC's, and operate from a serial link to your PC. The 16C74 module features - 8k EEPROM, up to 2000 lines of BASIC, 27 lines of programmable I/O, 8 A/D inputs, Interrupt driven serial RS232 interface, Peripheral I2C bus interface, LCD display driver routines, up to 178 bytes for variables and stack, extendible with optional external RAM and all the standard 16C74 features. Ask about the 16C57 version.

Compiler - The FED PIC BASIC compiler for the 16C74. It produces hex code to program your 16C74 directly with no need for external EEPROM. Compatible with the EEPROM versions of PIC 16C74 BASIC modules - develop on an EEPROM based module then compile and

program your PIC chips directly. 16C57 Module Kit (8k EEPROM, 4MHz) £25.00, Pre-built £30.00 16C57 Module Kit (8k EEPROM, 10MHz) £31.00, Pre-built £37.00 16C74 Module Kit (8k EEPROM, 4MHz) £35.00, Pre-built £42.00 16C74 Module Kit (8k EEPROM, 20MHz) £40.00, Pre-built £46.00 16C74 Module Kit (8k EEPROM, 4MHz) £35.00, Compiler - £60.00, or £50.00 when ordered with a module 16C84 chip programmed with BASIC - £25.00 Compiler - £60.00, or £50.00 when ordered with a module PIC and HC11 devices

				FIC AND ACTI DEVICES			
PIC16C74/JW	Erasable	20MHz	£24.00	PIC16C558			£5.00
PIC16C74-04P	OTP	4MHz	£8.00	PIC16C74-20P	OTP	20MHz	£11.00
PIC16C57-04P	OTP	4MHz	£5.00	PIC16C57-10P	OTP	10MHz	£6.00
PIC16C84-04P		4MHz	£6.00	PIC16C84-10P		10MHz	£8.00
PIC16F84-04P		4MHz	£6.00	PIC12C508-04P	OTP	4MHz	£2.20
PIC14000-04P	OTP	4MHz	£10.00	PIC14000/JW		Erasable	£23.00
PIC12C508-04P	OTP	4MHz	£2.70	Motorola MC68HC811E	2	Ring for de	tails
				Ask about other chips!		9	

# Forest Electronic Developments

VISA 10 Holmhurst Avenue, Christchurch, Dorset, BH23 5PQ 01425-270191 (Voice/Fax) . http://www.lakewood.win-uk.net/fed.htm e-mail: fed@lakewood.win-uk.net Prices are inclusive, please add £3.00 for P&P and handling to each order. Cheques/POs payable to Forest Electronic Developments, or phone with credit card details. Serial Cables - £7.50



# NON COMMERCIAL **ELECTRONIC DESIGN FOR WINDOWS**

# **TEACHERS... STUDENTS...** HOME USERS... etc.

# Your opportunity to save fffff's

With this non commercial version of our software produced for single users, this is your dream come true!

Software as you are probably aware has no real material value, but is priced to recover the enormous costs of development. The software house tries to evaluate how many units will sell at a specific price to generate the amount needed and produce a healthy profit.

As the electronics marketplace shrinks, due to expanding competition, it means that, in reality, powerful user friendly software, such as EDWin, must be very highly priced and therefore remains inaccessible to the individual and small businesses.

Until today ... Norlinvest, one of the biggest software houses in the electronics sector, has decided to put onto the market a "Non Commercial" version of their EDWin software, which is known worldwide.

This is the first truly seamlessly integrated suite of software running in all Windows formats . simulation, schematics and PCB design. At last allowing amateurs, teachers, students, ... in a work "individual" to take advantage of current technology, without any restriction.

To avoid misunderstanding - there is no difference between the industrial version of the software and our Non-commercial version, except the price. In other words; industry is subsidising the development cost and now the individual can take full advantage of this.

# **Computer Compatibility**

To run the program you will need:

- Windows 3.x, Win95 or Win NT,
- a min. 386 processor (486+ rec.)
- 8mb of RAM
- CD-ROM Drive



with Basic Autorouter and Postprocessing. Max. 100 component database and 500 symbol Device Library. £49.00

The De Luxe 1 version has the above, but also includes Professional Libraries and unlimited database components. £79.00

De Luxe 2 is the same as the basic version, but with Professional Libraries and adds Mix-mode Simulation, £79.00

De Luxe 3 all the above plus the Arizona Autorouter. £114.00

**Options: Professional Libraries £24.00 Professional Database** (Unlimited components) £24.00 Mix-mode Simulation £24.00 Arizona Autorouter £24.00 EDSpice Simulation £49.00 Thermal Analysis £19.00

Post and Packing £5.00 UK. Overseas £10.00 Prices include VAT

VISA All Major Credit Cards Accepted





YES! Please Rush Me My EDWIN NC Program. Swift Designs Ltd., Dept.ETI, Business & Technology Centre, Bessemer Drive, Stevenage, Herts, SG1 2DX.
Name:
Address:
Postcode:
Tel: (Day)
(Evening)
Version Required: Basic De Luxe 1 2 3 (please circle)
I enclose £+ p.p. £5.00 UK (p.p. £10.00 outside UK)
Cheque/P.P./Credit Card: Visa/Access/Mastercard:
N°: Expiry Date:
Signature:
PLEASE ALLOW 10-15 DAYS FOR DELIVERY.

System Features

Complete End-to-End CAE/CAD system. Simultaneous Schematic and Layout generation. Automatic Front and back annotation. Intuitive hierarchical menu structure. Mouse or keyboard commend activation. Macro operations. Real-time display of: ratsnest, active nodes, single line or true trace width. On-line help Auto reconnect. Full Integration of Schematic and Layout. Automatic file backup. User definable text sizes. DXF in and output. Screen hardcopy. Library viewer with editing possibility. Switching on/off possibility for tool and scroll bars Visible schematic and PCB symbols by editing. Monochrome mode for better print resolution. Bitmap support for loading logos, documentation, etc. Can be used in hierarchical as well as in simple schematic or PCB design. Maximum number of nets: 16,000. Maximum number of nodes: 32,000 Maximum number of bend points: 64,000. Maximum number of connections: 64,000. Maximum number of symbols: 32,000. Maximum number of components: 32,000 Maximum number of multi-segment traces: 32,000, with a total of 64,000 trace segments. ANSI/IEC libraries Full Gerber, NCD, pic and place output

# Schematic Capture

Up to 100 schematic sheets. Up to 64" x 64" sheet size. Industry standard sheet sizes Rotate, scale and mirror symbols. Real-time dragging of components and wires. Automatic package and pin assignment Orthogonal and free mode manual routing. Automatic bus annotation. Block save, load, move and delete Direct access to mixed mode simulation. Autorouting of connections. Merging and splitting of nets possibility. Definable line width, also for bus-lines Swapping of component positions. Automatic component renumbering by swapping.

# PCB Lavout

32 layers (28 route layers, 2 silk-screen layers (front and back), 2 soldermask layers (front and back)) User definable trace sizes. User definable pads. Curved traces. 1 mil grid resolution - Fine grid 10 micron. SMT, fine line, analog support. Component repeat, rotate and mirror. Components "Move by name" Component, gate and pin swap. Automatic component renaming. Trace repeat On-line, multi-layer routing with automatic via insertion. Pin-to-pin, free or 45 degree routing. Change segment side and width, trace side and width. Fast interactive generation of ground planes with user definable cross-hatch or solid fill. Automatic ground plane with thermal relief insertion Automatic DRC with user specified parameters. Electrical connectivity checking. Linear rotation of symbols. Gerber input read and use possibility. Built-in interface for Spectra 6.0, Max route 6.0 and Arizona Autorouter. Bitmap functions (logos, drawings, ...). Sophisticated database viewer Mixed Mode Simulation AC analysis (Frequency domain). DC analysis (Linear/non-linear) TD analysis (Time domain).

Diagram generator. Dynamic parameter definition of active and passive components

Output graphs displayed on screen, hardcopy or placed on schematic.

Oscilloscope function. DLL based analog/digital simulation primitives, modelling language and library creation tools. Built-in model generator for discrete devices.

Please Note: Some of the above are ONLY provided on the De Luxe 3 Version. EdSpice and Thermal Analysis are available as bolt-on extras.

Fax: 01438 722751 Email: designs@swiftdesigns.co.uk Web: www.swiftdesigns.co.uk Tel: 01438 310133

Data Acquisition Virtual Instrumentation

Environmental Monitoring

# 'Pico's PC Converters monitor and record temperature and humidity'.

# *Enviro Mon* Temperature / Humidity Logger & Alarm System

EnviroMon has many applications in: food processing - storage and distribution, energy management - waste energy, heating and processing, agriculture - monitoring humidity in greenhouses, and in hospitals - accurate monitoring of temperature sensitive items.

Pico Technology

Monitors up to 30 channels of temperature over a 400 m. distance.

- ▼ -55 to 100°C temperature range (typical accuracy ±0.2°C).
- ▼ Data can be downloaded to PC.

# Enviro Mon

pico

TC-08

Starter Kit from £393.00 3 temperature Sensors on 5m lead, 3 channel Converter, Enviromon Logger, cables & fittings. Expandable at any time for around £50 / channel

# TC-08

# 8 channel Thermocouple to PC Converter

Simple to use thermocouple to PC interface.

- Connects to serial port no power supply required.
- Supplied with PicoLog data logging software.
- ▼ Resolution 0.1<sup>o</sup>C.

# **TC-08** £199.00

Supplied with serial cable and adaptor. Calibration certificate £25.00. Thermocouple probes available.

# TH-03 3 channel Thermistor to PC Converter

- Connects to serial port -
- no power supply required. PicoLog data logging software.
- ▼ -55 to 105°C temperature range
- ▼ Resolution 0.01<sup>o</sup>C.

**TH-03** £79.00 Supplied with serial cable and adaptor. Thermistor sensors available.



echnolog]

Call for free demo disk or download our web site: http://www.picotech.com All prices exclusive of VAT.

Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK Tel: (0)1954 211716 Fax: (0)1954 211880 E-mail: post@picotech.co.uk Environmental Monitoring Virtual Instrumentation

**Data Acquisition** 

Pico

400-200

# 'Pico's Virtual Instrument is the most powerful, flexible test equipment in my lab.'

Pico's virtual instruments emulate the functions of traditional instruments such as **Oscillscopes**, **Spectrum Analysers and Multimeters.** Controlled using the standard Windows interface, the software is easy to use with full on line help.



# ADC-200 Dual Channel High Speed

- 100, 50 or 20 MS/s sampling.
- 50, 25 or 10 MHz spectrum analysis.
- S0, 25 or 10 MHz spectrum analysis
   Advanced trigger modes capture
- intermittent one-off events.
- Less than half the cost of a comparable benchtop scope.

 ADC 200-100
 £549.00

 ADC 200-50
 £499.00

 ADC 200-20
 £359.00

 Supplied with cables and power supply.

# ADC-100

# **Dual Channel 12 bit resolution**

The ADC-100 offers both a high sampling rate 100kS/s and a high resolution. Flexible input ranges ( $\pm$ 50mV to  $\pm$ 20V) make the unit ideal for audio, automotive and education use.

ADC-100 with PicoScope software £199.00 with PicoScope & PicoLog software £219.00

# ADC-40/42

**Single Channel - low cost** 

- ▼ 20 kS/s sampling.
- 10 kHz spectrum analysis.
- ± 5V input range.

ADC-40 8 bit resolution £59.00 ADC-42 12 bit resolution £85.00



sy'

echnolo

Call for free demo disk or download our web site: http://www.picotech.com All prices exclusive of VAT.

Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK Tel: (0)1954 211716 Fax: (0)1954 211880 E-mail: post@picotech.co.uk

# MKII Electronic Auto-Checker

# Tim Parker has updated the original multi-purpose Multi-checker to be a new, improved audible/visible low voltage tester, with a special relevance to cars

egular readers will remember the Multi-checker from the August 1995 issue of ETI. Excellent piece of handy test gear though it was, it only had a visual indicator, lacking any audible feedback to the user. This made testing for voltages in awkward places a little difficult, since the user had to be able

to actually see the tester in order to check the states of the two LEDs. The scenario which immediately comes to mind will be recognised by anyone who has tried to find a supply line, or install even the simplest pieces of equipment anywhere near the dashboard of a motor vehicle: lying on your back in either the driver's or the front passenger footwell, with your feet and lower leg portions either on, or up the back of the seat! As if that wasn't uncomfortable enough, if it's the drivers side, you also have the added pain in the neck - literally - from the control pedals folding up your skin like a baker kneading dough!

Once you have managed to get into this position, you then have to start the testing, prodding around with the test leads in the hopes of finding a 'live' wire, only to discover you cannot see the test equipment without inducing excruciating cramp in your neck or your stomach, or both. By this time you are in no position to manoeuvre your body to ease the pain.

To overcome this problem, and also in response to numerous requests from constructors for some form of audible indication, the original Multi-checker has now acquired a 'voice' - well, a buzzer at least. The overall operation of the original tester has also been made much simpler, converted from a (slightly tedious) three position slide switch, to a simple, one-press pushbutton operation. Given the above scenario, and because the majority of enquiries related to motor vehicle work, the new tester is known as the Auto-Checker.

As a reminder, figure 1 shows the circuit diagram of the original Multi-checker. This has two basic modes or functions: a voltage finder with polarity indicator, and a continuity/component tester. We won't ponder on the original circuit for long, because it was explained fully in the earlier issue of ETI, but a brief recap of how it works, using the new circuit in figure 2, will benefit new readers. We should point out that the Auto-Checker is not aimed solely at motor vehicles; it should satisfy the majority of basic 'good/no good' testing requirements for a range of low-volt electrical and electronic



components, where just a simple indication of whether or not a device is working will do, or whether a low voltage connection has a potential on it or not.

The Auto-Checker uses two LEDs and a piezo buzzer to indicate the status of its two test points, to which a pair of test leads can be attached if required. A third LED is provided to warn you that the internal battery is being used, and serves as a reminder to switch off the tester afterwards. The test pads shown in figure 1, and which were fitted to the front of the original unit have been removed, because it was possible for either or both these to come into contact with (earthed) metal body parts during testing and, since they were connected directly to the test probe sockets, this was perhaps an undesirable situation with respect to motor vehicle testing, whereby a test pad in contact with the chassis of the vehicle might just happen to be the one corresponding to the particular test probe you have connected to the 'live' wire!

Note: This equipment is not for use on mains voltages.





# **Auto-Checker Modes**

Mode 1 is a simple, low voltage indicator with an input level of up to about 25 volts. This is the default mode when the pushbutton is 'out', and the internal battery is on standby for the buzzer only. The test leads are not polarised, but are simply labelled 'A' and 'B', and you don't even have to worry about which way round to connect them to your circuit, since the Auto-Checker will light the LED(s) and sound the buzzer when a voltage is detected. The states of the LEDs and the type of sound from the buzzer indicate whether that voltage is AC, DC, or pulsing (on/off) DC up to about 20Hz. Furthermore, the Auto-Checker provides polarity indication for DC voltages, by showing which of the two test probes is connected to the positive terminal - ideal if you're looking for power when installing in-car accessories.

Mode 2 is enabled by depressing the pushbutton to the 'in' position. The Auto-Checker now becomes a simple

audible/visual continuity tester, giving good or bad indication of fuses, light bulbs, switch contacts, transformer windings, speaker coils and heating elements, etc. - in fact, anything which has a relatively low resistance. This mode also provides a very useful facility for 'good/no good' testing of diodes and LEDs. By connecting them either way round across the test probes, the Auto-Checker will show which of the two probes is connected to the cathode of the device. Furthermore, if a good LED is being tested, not only will the cathode be identified, but it will also light up in a flashing manner, giving visual confirmation that it does actually work.

# The circuit

With SW1 in position <sup>1</sup>/<sub>1</sub> (out), R5 is connected in series with the test points and LEDs 2 and 3. With a low voltage DC potential applied to the test points, the buzzer will sound and one of the LEDs will light, which also indicates the polarity of the voltage.<sup>1</sup> If test point 'A' is connected to the positive connection then LED2 will light up. If the positive is on test point 'B' then LED3 will light up. If the voltage is pulsing at a frequency below about 20Hz, then the buzzer will pulse at the same rate, and either LED2 or LED3 will flash at this frequency, depending on which test point is connected to the pulsing line. At frequencies above 20Hz it will be difficult to detect the flashing and buzzer pulsing, which may give the (wrong) impression that the voltage is constant.

With a low voltage AC input, the buzzer sounds continuously and both LEDs light up, but each one on opposite half cycles of the input signal. Again, frequencies below about 20Hz should produce a noticeable pulsing. How apparent this is depends on the rise and fall times of the input waveform, a sinewave input will produce less flashing effect than a squarewave input, for instance.



Pressing SW1 (in) connects R4 and R6 in series with the test leads and the LEDs, and power is applied to IC1. D1 protects against reverse polarity, just in case the battery makes reverse contact with its connector clip when being replaced while SW1 is depressed. C1 and C2 provide supply rail decoupling and LED1 serves as a power on indicator, this helps to remind you to turn it off.

IC1, R2 and C3 form a low frequency squarewave oscillator with complimentary outputs on pins 10 and 11, which are connected in series with the test points, LEDs and current limiting resistors R4 and R6. With pin 10 high, and continuity or a low resistance across the test points - such as a good fuse or light bulb, current flowing through the load across the test points will light up LED3. With pin 11 high, LED2 will light up.

# The buzzer circuit

Many constructors of the original Multi-checker attempted to connect a buzzer driver circuit of their own, usually by driving the base of a transistor from one of the test points via a suitable resistor (which, initially, seems the logical way to do it), only to discover it was not possible using a simple transistor switch, due to the fact that the test point terminals were bi-directional, and they also cannot have a current path to 0V. When they did manage to get it to work in a fashion, it would only respond to unipolar signals, and wouldn't work in the voltage test mode at all unless the buzzer was tied permanently to the positive supply rail. This was fine until they touched the test point terminal with just their fingers, which produced sufficient base drive to turn on the transistor and sound the buzzer, even with the Multichecker turned off!

# **Bridge rectifier**

In reply to all those who questioned the possibility of adding a buzzer, here's how it's done. The answer is to detect current flowing in either direction through either of the two status LEDs. This is achieved by connecting the AC input of a bridge rectifier - formed by D2 to D5 - across the LEDs themselves, and making use of the unipolar output from the bridge. Simple as this may seem in theory, it's a little more difficult to put into practice, because the voltage drop across an LED and the voltage losses through a bridge rectifier are pretty similar, the overall result being not enough usable voltage at the output of the bridge rectifier. To overcome this, D6 and D7 have been added in series with each LED to increase the amount of voltage drop across them.

On its own, the bridge rectifier hasn't overcome the problem of having a current path to 0V. For this, an optoisolator with NPN transistor output is used - OP1. Only C4 and the internal LED of the opto-isolator are connected across the output of the bridge rectifier, which eliminates any current flow to 0V. The voltage drop across either LED can now be used to drive the LED of the opto-isolator. The transistor output from this, together with Q1 forms a darlington driver which is used to turn on the buzzer. By connecting the positive lead of the buzzer permanently to the internal battery's positive supply rail, the buzzer will sound whenever either of the test LEDs light up, which means the buzzer is functional in both voltage finder and continuity modes. To ensure negligible drain on the battery, R3 keeps Q1 turned off in the event of no input signal, and also prevents instability which is always present in open base high gain darlington driver circuits such as this.



# Construction

Compared to the original multi-checker, the overall construction of the Auto-Checker has been made much simpler. So much so, that everything is mounted ón the board, which in turn is held in place by the test sockets and a double sided self adhesive foam pad. The PCB component layout is shown in figure 3. The first items to solder in place should be the solder tags supplied with the 4mm test sockets, since these are soldered to the underside of the PCB, and are used to hold the board in



place. Also, they are not accessible with the board in place. Only solder about 3mm of the tag to the A and B copper pads, leaving sufficient to bend and form the remainder of the tag to facilitate the final mounting position of the board. Solder all components except the LEDs in a low-to-high profile sequence, taking care with the orientation of all the polarised ones - capacitors, diodes, ics etc. - and don't forget the leads from the battery clip.

In order to make fitting the LEDs easier, it is best to crop the leads to the correct length prior to soldering them in


•	Resistors	
	B1	1k
	R2	4M7
•	R3	47K
	R4, R6	470B
H	R5	1k5 him i grantel ladob reat al
	Capacitor	
	C1	10uF/35V sub-miniature
		radial electro
2	C2, C3, C4	100nF polyester or ceramic
	02,00,04	form polyester of certaining
4	Semicond	uctors
	D1 - D7	1N4148 signal diode
	IC1	CD4093B guad nand Schmitt
		trigger
	LED1	3mm Green LED
	LED2, 3	5mm high intensity red LED
	OP1	SFH610-2 opto isolator
	Q1	BC547 NPN transistor (or similar)
	Miscellan	eous
	BZ1	5V miniature PCB mounting
		peizo buzzer
	SK1,SK2	4mm panel mounting sockets
	SW1	4 pole changeover PCB push
	JUAT.	switch
	Battery clip	PP3 battery clip
	Fixings	M3 nuts, bolt and washers
	Case	Plastic box 56mm x 110mm x
	0000	21mm
	B1	9V PP3 battery *
	Probes	Pair of 4mm Test Leads & Probes
	PCB	DTE "AC101 - Auto-check PCB
		The rest and the shock I of

INNI EIGCHUING AUGUNGAN

place, otherwise you will have to keep re-soldering them at different heights until you get them right. To do this, turn each one upside down and place the top face of the LED on the inside bottom of the case as shown in the diagram, then crop the leads level with the outer edge of the case. These can now be soldered into the PCB with about 1mm of lead protruding through to the copper side of the board, and they should be at the correct height when the PCB is finally secured in place. Note that the LEDs all face in different directions, so take care with their polarities. They won't be damaged if they are soldered the wrong way round, they just won't light up. However, if you also get one of the diodes back-to-front, then you will have the oddest results displayed when using the tester, so please pay take great care with the orientation of them all.

The front panel suggestion in figure 6 can be used as a drilling template for the three LED hole positions to ease the process of ensuring the various holes needed in the lid of the case are lined up relative to the component positions on the PCB. Only the rounded top face of the LEDs should - protrude through the case, with none of the body showing, so drill undersized holes for them, and taper the insides to provide a tight fit, allowing for about 1mm of the LEDs showing externally. The shorter body length of the 3mm power on LED (LED1) means that most of it is taken up by the thickness of the case lid, so the hole diameter for this one can be full size. For a louder buzzer sound, drill a hole in the lid of the case to accept 4mm test sockets, and a final hole in the side of the case for the switch button.





Figure 7: the pattern for the Auto-Checker front panel. Our original is white on black

#### Enclosure

The new Auto-Checker is designed to fit the same pocket sized plastic case as the original Multi-checker. Prior to final installation, it's a good idea to power up and test the board for correct operation by connecting test pieces across the solder tags. Once you're satisfied everything is operational, the board can be secured in place according to the details shown in figure 5.

The inset of figure 5 shows how the 4mm test sockets would normally be used, particularly in the case of metal enclosures, whereby the insulating bush is inserted from the outside of the case, so as to isolate the socket from any other metal parts. For our purposes, not only because we're using a plastic case, but also to increase the testing area so that fuses and the like can be tested directly on the unit without inserting the test probes, the metal washer is used

on the outside of the case, and the two bushes are both slotted onto the shaft of the socket from the inside of the case. This forces the solder tag to be slightly further away from the edge of the case to where it would normally sit, which benefits us by preventing the PCB being too close to the test socket, where it might be more awkward to finally secure it in place, especially if the solder tags are a touch on the short side.

#### In use - voltage mode

This mode is used to locate or detect low voltages between about 3 and 30 volts, and is selected when the mode switch is in the out position. This mode can be used without an internal battery fitted to the Auto-Checker, and the status LEDs will function normally, but no sound will be produced

A	В	BLEEPER	POSSIBLE DIAGNOSIS
OFF	OFF	NO SOUND	NO VOLTAGE POTENTIAL ACROSS A AND B. ALSO OCCURS IF BOTH LEADS CONNECTED TO THE SAME POSITIVE OR NEGATIVE VOLTAGE
ON	OFF	CONSTANT	DC VOLTAGE PRESENT. POSITIVE ON A, NEGATIVE ON B
OFF	ON	CONSTANT	DC VOLTAGE PRESENT. POSITIVE ON B, NEGATIVE ON A
ON	ON	CONSTANT	AC VOLTAGE PRESENT AT 20Hz OR GREATER FREQUENCY*
FLASHING	OFF	PULSING	PULSING DC VOLTAGE PRESENT. POSITIVE PULSES ON A*
OFF	FLASHING	PULSING	PULSING DC VOLTAGE PRESENT. POSITIVE PULSES ON B*
FLASHING	FLASHING	CONSTANT OR PULSING	AC VOLTAGE PRESENT AT 20Hz OR LOWER FREQUENCY*

Та

A	В	BLEEPER	POSSIBLE DIAGNOSIS
OFF	OFF	NO SOUND	BAD CONNECTION - OPEN CIRCUIT, SWITCH CONTACTS OPEN, BLOWN FUSE OR LAMP, OR HIGH RESISTANCE (> 47 KILOHMS)
FLASHING BRIGHTLY	FLASHING BRIGHTLY	CONSTANT	GOOD CONNECTION - SHORT CIRCUIT, SWITCH CONTACTS CLOSED, FUSE OR LAMP OK, OR A LOW RESISTANCE (< 1 KILOHM)
FLASHING BUT DIMLY		CONSTANT (MAYBE POOR)	POOR CONNECTION - RESISTANCE GREATER THAN 10 KILOHMS, OR LOW INTERNAL BATTERY VOLTAGE - CHECK / REPLACE BATTERY
2 DO N	YS DISCONNED	TO CHECK FOR VOLT	TEST ITEM BEFORE TESTING. DO NOT CARRY OUT 'IN SITU' TESTING AGES WHEN THE AUTO-CHECKER IS SET TO <b>CONTINUITY</b> MODE THE OUT POSITION AFTER USE TO CONSERVE THE INTERNAL BATTERY POWER

COMPONENT	DESCRIPTION OF MULTI-CHECKER STATUS
DIODE OR >10V ZENER DIODE	FLASHING A OR B (BUT NOT BOTH). PULSED BLEEPER TONE. WHICHEVER STATUS LED IS FLASHING DENOTES THE CATHODE OF THE DIODE UNDER TEST.
SINGLE (ONE) COLOUR LED	FLASHING A OR B (BUT NOT BOTH). LED UNDER TEST FLASHING AT SAME RATE. PULSED BLEEPER TONE. WHICHEVER STATUS LED IS FLASHING DENOTES THE CATHODE OF THE LED UNDER TEST
BI AND TRI COLOUR LED	FLASHING A AND B. ALTERNATING COLOURS OF LED UNDER TEST. CONSTANT BLEEPER TONE. THE CATHODE IS IDENTIFIED BY THE STATUS LED WHICH FLASHES WHEN THE TEST LED IS RED
TRANSISTOR (NPN)	FLASHING A OR B (BUT NOT BOTH). PULSED BLEEPER TONE. THE BASE TERMINAL OF THE NPN TRANSISTOR IS IDENTIFIED BY THE STATUS LED WHICH DOES NOT FLASH
TRANSISTOR (PNP)	FLASHING A OR B (BUT NOT BOTH). PULSED BLEEPER TONE. THE BASE TERMINAL OF THE PNP TRANSISTOR IS IDENTIFIED BY THE STATUS LED WHICH DOES FLASH

by the bleeper. The conditions given in both Table 1 and Table 2 assume there is a battery fitted. For testing purposes, the test leads, although red and black, can be fitted and used either way round, since the test sockets are not polarised.

#### In use - continuity mode

This is selected when the mode switch is in the 'in' position and the power indicator is lit. This mode can be used for testing fuses, lamps, coils, switch contacts, diodes and other electronic components.

#### **Component testing**

When testing electronic components on the Auto-Checker, in all cases they may be connected any way round across the test leads. Transistors are tested two legs at a time and may require up to three configurations before the base terminal is identified. The 'good' states of the two status LEDs are given in Table 3. Any conditions other than these states could represent a possible fault, which should be investigated further.

Finally, a word of caution. The Auto-Checker makes an ideal piece of tackle to have around the home, garage, workshop or in the tool box, and when used for its intended purposes should provide many years of trouble-free use, as long as it is not abused. When checking for voltages, make sure that you have selected mode 1 (switch in the out position) prior to starting, otherwise permanent damage to IC1 could result if the continuity mode is selected with top much voltage applied to the inputs.

A complete kit of parts which includes the case, PCB, and a pair of test leads and probes (\* battery not included) is available from the author by mail order only from:

DTE Microsystems, 112 Shobnall Road, Burton-on-Trent, Staffs DE14 2BB, UK Tel 01283 542229

The price for the complete kit of parts is  $\pounds 17.93$ . The PCB is also available separately at  $\pounds 5.30$ . (It is included in the kit).

Please.add postage & packing (per order):  $\pounds 2.00$  for the UK,  $\pounds 4.00$  elsewhere.

Please make Cheques/postal orders payable to 'DTE Microsystems'. If ordering from overseas, payment must be in Pounds Sterling  $(\mathfrak{L})$  and cheques must be drawn on a British bank. Goods will normally be dispatched within five working days from receipt of order (subject to availability and cheque clearance), but please allow up to 28 days for delivery.

DO NOT under any circumstances, or for any reason whatsoever, subject the Auto-Checker to mains voltage potentials. This piece of equipment is not designed for mains voltage purposes and any such misuse would be extremely dangerous and could prove fatal.



The TI Technical Bookshop currently stocks over 80 Data Books, Design Manuals and User's Guides. They cover the entire spectrum of semiconductors from Texas Instruments - the company with one of the world's broadest S/C product ranges, and the acknowledged leader in Digital Processing Solutions. If you are a system designer or product specifier you cannot afford to be without ready access to this invaluable data bank.

Now, you can once again order this complete range of reference books from a UK supplier.

Contact the TI Technical Bookshop (UK) for the full list of books, prices and ordering information, or visit our web site at: http://www.ti-techbooks.co.uk

Or write/fax to: TI Technical Bookshop (UK) PO Box 712 Milton Keynes MK17 8ZH Tel: 01908 282121 Fax: 01908 585660







Adaptable, affordable - handy circuits for around £5. By Owen Bishop 6. A tuneful trifle

ould you like some light music? You can produce your own with this light-controlled tone generator. This is a toy for budding young musicians in which the pitch of the note depends on the amount of light falling on the instrument. The light sensor is a lightdependent resistor (LDR) which consists of a block of semiconductor material, often cadmium sulphide. Because of this, the LDR is sometimes known as a cadmium sulphide cell (CSC). It is also known as a photoconductive cell (PCC).

The principle of the LDR/CSC/PCC is that, when the material is exposed to light, the energy of the light causes free charge carriers to be produced. The more light, the more charge carriers. And the more charge carriers, the less the electrical resistance of the material.

The LDR has a pair of electrodes deposited on its exposed surface and, as the light level increases, the amount of current flowing from one electrode to the other increases roughly in proportion. In this circuit the LDR forms half of a potential divider network, with R1 as the other resistor. As light increases, the resistance of LDR1 becomes smaller in





proportion to that of R1, which is fixed at 15 kilohms. As a result, the voltage across LOR1 is reduced in proportion to that across R1. Since the total voltage across the pair is fixed at 9V, the voltage at the junction of LDR1 and R1 must increase. By varying the amount of light falling on LDR1 we can vary the voltage at pin 9 of IC1.

IC1 is actually a phase-locked loop ic, but we are using only a part of it, the voltage-controlled oscillator (VCO). Now, that's enough TLAs! (Three-letter abbreviations.) The higher the voltage applied to pin 9 the higher the frequency of the tone produced. Frequency also depends on the values of C1 and R2, higher values giving lower tones. The frequency produced when the input voltage is half the supply (4.5V in this case) is  $f = 1/(C1 \times R2)$ . Resistor R3 also affects the frequency by producing an offset which determines the lowest and highest frequencies produced as the voltage is swept from 0V to 9V. R3 should be greater

than R2, and the bigger R3 the bigger the range of tones. The capacitor and resistor values given in figure are suitable for producing a useful range of audio frequencies.

The output from IC1 appears at pin 4 and this is fed through R4 to Q1, which amplifies the signal and causes sound to be emitted from the loudspeaker, LS1.

#### Construction

Although the circuit could be housed in an opaque box with a hole cut to allow light to reach LDR1, we decided to build it in a transparent box with the circuit totally enclosed. Only the push-button S1 is accessible when the lid of the box is screwed down. Drill a hole in one end of the box (figure 3) to take the pushbutton. Drill several small holes in the box in the region where the speaker is to be mounted.

The circuit is assembled on a piece of stripboard (figure 2). Note that the strips are cut across at D8, E5, B13 to J13 and C17. There are blobs of solder joining adjacent strips at Al5/B15 and J12/K12. There are many different types of LDR suitable for this project. You can use the popular ORPI2 or one of the less expensive LDRs which have a resistance of a few tens of kilohms in normal indoor



daylight levels. If in doubt, measure the voltage at pin 9 when the circuit is assembled and the power is on. It should be around 4.5V when the LDR is partly shaded. If it tends to be much lower of higher, substitute a higher or lower resistor for R1. Similarly, when you test the operation of the circuit you may decide that the notes are too low-pitched (perhaps even separating out to a rapid series of 'ticks') or too high-pitched. If so, alter the value of R2. You can increase R3 to obtain a wider range of pitch.

It is easier to connect the off-board items to the board *before* mounting everything inside the box. The circuit is powered by a 9V PP3 battery which can be fixed to the lower side of the box by a piece of doublesided adhesive tape or a 'Sticky Fixer' (figure 3). We wanted to mount the circuit board just below the upper



surface of the box and found that it is sufficiently secure to attach it using double-sided tape applied to the upper surface of IC1. The loudspeaker is glued in position using clear adhesive (Uhu, for example) applied to its rim.

#### **Playtime**

The circuit is silent when S1 is not pressed, and uses no current. Press S1 to produce a note, but first position your hand so as to shade LDR1 to a greater or lesser extent. The more shading, the lower the pitch. Pressing and releasing the button for each position of your shading hand gives distinct notes. Or you can hold the button down as you vary the shading to obtain what musicians term a *glissando* effect. Waggling your fingers gives *vibrato*. Take it away, *Maesto*!



## THE ELECTROMAIL CD-ROM CATALOGUE What will you get out of yours?

#### A virtual technical superstore

ducts ranging from batteries to bearings, fuses to fans, to semi-conductors, hand tools to health & safety3

#### A technical encyclopaedia

änge, Plus a full selection of over 400 mänufacturers

#### Professional advice and technical back-up

hatever your requirement, we have a range of technical

#### **Round the clock service**

Place your order anytime; we're open 24 hours a day,

oducts, more information, more service than you ever thought possible. And for-just £5.00 can your business, our hobby of even your home really manage

#### How to order

© 01536 204555 FAX 01536 405555 When ordering by fax or phone quote Stock No. 263-7519, along with your card T 01536 204555 number and expiry date.

SEE OUR WEBSITE

bee Jun weboile

- 375- 1754 - VISA

ELECTROMAIL, P.O. Box 33, Corby, Northauts, NN17 9EL Tel= 01536 204555 Fax: 01556 405555

## The Low Cost Controll hat's Easy To Use

CATALOGUE JULY-OCT

insc

#### Features

The K-307 Module provides the features required for most embedded applications

87,000

RODUCTS

ECTROMAIL

Analogue 4 Channels in 1 Channel out Digital 36 Digital in or out & Timers Serial RS-232 or RS-485 plus I2C Display LCD both text and graphics Keyboard Upto 8 x 8 matrix keyboard Memory > 2Mbytes available on board Low Power Many modes to choose from

#### Development

The PC Starter Pack provides the quickest method to get your application up & running

- Operating System Languages
- Expansion
- Real Time Multi Tasking 'C', Modula-2 and Assembler Easy to expand to a wide range of peripheral cards

#### **Other Features**

Real Time Calendar Clock, Battery Back Up, Watch Dog, Power Fail Detect, STE I/O Bus, 8051 interface, 68000 and PC Interface

#### **Cambridge Microprocessor** Systems Limited



Units 17 - 18 Zone 'D' Chelmsford Road Ind Est Great Dunmow Essex CM6 1XC E-mail cms@dial.pipex.com

Phone 01 371 875 644



## **Computer Radio Control for Home Automation Part 2** Mains socket Figure 1: A PC-controlled radio digital home automation system Controlled output mains Incoming mains MAINS CONTROLLER Mains socket up to 1024 mains controllers 418MHz radio signal MAINS CONTROLLER Connected to the Centronics port of the PC Transmitte e Radio Mains **Control System**

## 1024 mains outlets can be computer-controlled by Dr. Pei An's home automation interfaces. Part 2 describes the mains control modules

he article describes a radio digital data control system which can be used for home automation applications. The complete system consists of one radio transmitters and 256 receivers with different addresses. The transmitter is connected to the Centronics port of a computer, and four bits of data issued by the computer can be transmitted to any one of the receivers. One of the four bits is used to control the ON/OFF of the mains of a socket. So a total of 1024 mains sockets can be controlled by one computer. The transmitting distance is about 50 meters in buildings and 200 meters in open fields. The system is illustrated in figure 1.

In the first part of this series, ETI issue 3 1997, I described how to construct radio transmitter and receiver modules and how to write a Turbo Pascal 6 software driver. In this article, I will show how to use the modules in a remote mains control application. I will also present a Windows Visual Basic software driver for the system.

## A summary of the 418MHz radio transmitter and receiver

Inside the transmitter, an encoder (HT-12E) converts a 12-bit parallel data into a serial encoded data. The 12 bits are supplied to the HT-12E by a computer via the Centronics port. The first 8 bits of the data represent an address and the other 4 bits are the data to be sent. The encoded serial data modulates a 418 MHz radio frequency signal using an FM modulation scheme. The radio frequency signal is then transmitted to the surroundings. The modulation is facilitated by an FM radio transmitter, TMX-418-A. The assembly of the module is shown in figure 2.





Inside a receiver, the radio signal picked up by the antenna is demodulated by an FM radio receiver module, SILRX-418-A. The demodulated serial data is fed into the serial-to-parallel decoder (HT-12D), which converts the serial data back to the parallel data. The address bits are compared with the pre-set address of the decoder. If they match, the 4-bit data is latched to the outputs. If the address does not match, the decoder ignores the data. As an 8-bit binary data has 256 possible combinations, the maximum number of receiver's address is 256. The assembly of the module is shown in figure 3.

The transmitter is type-approved to the Radiocommunications Authority specification MPT 1340 in the UK. This avoids the need to submit the final project for approval.

## The radio mains control system

The radio transmitter unit The radio transmitter module is housed in a plastic box. The assembled unit has a 36-way female Centronics-type connector, an LED indicator, a power switch and a power socket. The antenna

is a whip type, the total length of which is 160 mm. Figure 4 shows the cutting of the box. Figure 5 shows the assembly of the radio transmitter unit.

#### The mains controller unit

The circuit diagram of the mains controller unit is given in figure 6. Euro chassis plugs and sockets are used for the mains input and the controlled mains output. The incoming 240V is converted into 12V AC by T1, which is a mains transformer with an internal fuse. The AC voltage is rectified by BR1 and smoothed by C1. It is then fed into the 7812 voltage regulator where a +12V DC is produced. This is the supply voltage for other circuits. The radio receiver module is mounted on the controller PCB board. One of the outputs of the module is connected to J6. This signal is amplified by Q1 and it controls the on/off of the relay. SW1 is used to select the automatic mode and override mode. In the automatic mode, the mains controller is controlled remotely by the computer. In the override mode, the relay is permanently energised. Two LEDs indicate the power on and off.

Important note: This project involves mains voltage. Constructors should be very careful in constructing it, in testing it and in using it in practice. Seek assistance if you are not experienced in constructing with mains voltages.





Figure 7 shows the assembly of the PCB board of the unit. The PCB board is fixed inside a plastic box. The cutting of the box is shown in figure 8 and the assembly of the unit is shown in figure 9.

#### The software driver

The Turbo Pascal 6 program which was listed in the previous article can be used to control the main switches.

In this article, a Windows Visual Basic software driver is described. Visual Basic allows users to develop user friendly graphic interfaces in Windows environment with ease. Although it offers a wide range of program supports for user interfaces, Visual Basic does not provide functions for direct I/O access and memory access. Dynamic link libraries (DLLs) are used to supply Visual Basic programs with functions. DLLs can be easily written using other Windows programming languages such as Turbo Pascal for Windows, Windows C, etc..

The first program list is the DLLs for the radio mains control system written in Turbo Pascal for Windows. It contains several functions. Three of them which are related to the hardware control are explained below: Centronic(x:integer):integer is a function. Centronic(0) returns the number of number of Centronics ports installed on your PC. Centronic(1) returns the port address of LPT1 and Centronic(2) returns the address of LPT2, etc. send\_data (P\_address, address, data :integer) :integer sends the address and data to the 74LS164 shift register. The Centronics address should be supplied. When sending the address and data, the Transmit Enable (-TE) must



The assembly of the radio control mains unit in its box

be high to stop transmission. Transmit (P\_address,flag:integer):integer starts (flag=1) or stops (flag=0) the transmission of the encoded data. DLLs are generated by MAKE or BUILD functions in the COMPILE pulldown manual in the editor. They are executable files, but they cannot be run on their own.

#### Listing one. WHDLL.PAS

library radio\_mains\_controller; {Window DLL for the Smart Radio Mains Control System designed by Dr. Pei An, 4/5/97} {74LS164 latches the data sent serially by the computer's Printer port.

DB0, DB1, DB2 and DB3 are loaded with address A0, "A1, A2 and A3 DB4, DB5, DB6 and DB7 are loaded with data D0, D1, D2 and D3}

#### uses

wincrt, windos;

#### var

address,i,j,swaddress,sdata:integer; delaytime,lighttime:real; dummy,P\_address:integer; input\_char:char;

Function Centronic(x:integer):integer; export; (\* \$000:\$0408 holds the printer base address for LPT1

000:040A holds the printer base address for LPT2

\$000:\$040C holds the printer base address for LPT3

\$000:\$040e holds the printer base address for LPT4

\$000:\$0411 number of parallel interfaces in binary format \*)
var

number\_of\_LPT, LPT1, LPT2, LPT3, LPT4 :integer; begin

number\_of\_LPT:=mem[\$40:\$11]; (\* read number of
parallel ports \*)

```
number_of_LPT:=(number_of_lpt and (128+64)) shr
6;
```

lpt1:=0; lpt2:=0; lpt3:=0; lpt4:=0;

```
LPT1:=memw[$40:$08];(* Memory read procedure *)
LPT2:=memw[$40:$0A];
LPT3:=memw[$40:$0C];
LPT4:=memw[$40:$0E];
```

```
case x of
```

0: centronic:=number\_of\_LPT; 1: centronic:=lpt1;

- 2: centronic:=lpt2;
- 3: centronic:=1pt3;
- 4: centronic:=lpt4

```
end;
end:
```

```
procedure delay;
var
    ij:integer;
begin
    for ij:=1 to 10000 do ij:=ij;
end;
Function bit_weight(bit:integer):integer; export;
var
    i,dummy:integer;
begin
    if bit=1 then bit_weight:=1
```

```
else begin
  dummy:=1;
```

for i:=1 to bit-1 do dummy:=2\*dummy;









```
bit_weight:=dummy;
end;
```

#### end;

```
Function
send_data(P_address, address, data:integer):integer;
export; (Send the address to the 74LS164 shift
register}
(When sending the address, the Transmit Enable (-TE)
must be high to stop transmit}
(During loading, (1) DBO is loaded with the data
sw[i],
                   (2) DB1 (CLOCK) is made from low-
to-high-then-low
                   (3) DB2 (-transmit enable) is kept
high all the time}
var
  sw:array[1..12] of byte;
begin
  for i:=8 downto 1 do
   begin
    sw[i]:=0:
    if address>=Bit_weight(i) then begin
      address:=address-bit_weight(i);
      sw[i]:=1;
         end;
```

```
end;
  for i:=4 downto 1 do begin
    sw[8+i]:=0;
    if data>=bit_weight(i) then begin
      data:=data-bit_weight(i);
      sw[8+i]:=1;
      end:
   end;
(loading address and data into the 74LS164
registers}
for i:=12 downto 1 do
  begin
    port[P_address]:=sw[i]+4; {DB0=sw[i], DB1=0,
DB2=-TE=1
              {a delay}
      delay;
      port[P_address]:=sw[i]+2+4; {DB0=sw[i],
DB1=1(loading into register), DB2=-TE=1}
      delay; {a delay for loading the bit}
      port[P_address]:=sw[i]+4; {DB0=sw[i], DB1=0,
DB2=-TE=1}
   end;
end;
Function
transmit(P_address,flag:integer):integer;export;
(Start or quit the encoded data transmitting
```

depending on FLAG} begin if flag=1 then port[P\_address]:=0 else port[P\_address]:=4; end;

Exports Centronic

ARTS LIST for the Radio Control Syste

index 1,



#### The radio transmitter unit in the box

	To be	ox the transmitter module
	Box	T4 box (Maplin stock number KC93B)
	SK1	2.5 mm power socket
ł	SK2	36-way female Centronics connector
		(Maplin stock number FV87U)
	SW1	SPDT toggle switch
	LED	5mm red standard LED
	Main	s Control Units
I	Resis	stors
I	All 1 pe	rcent metal film
	R1	1k
	R2	1k2
	R3	390R
		WCo III
	Capa	citors
	C1	2200 uF/25V electro
	C2	100nF ceramic disk
		E
		conductors
	IC1	7812 1A +5V voltage regulator
	Q1	ZTX300
	D1	1N4001
	D2	1N4148
	LED1	5mm red LED
	LED2	5mm green LED
	BR1	1A rectifier
	Relay	12V coil, 240V and 3A contact (Maplin stock number JM18U)
	T1	240V primary, two 6VA transformer with
	Contraction of the	internal fuse. (Available from author -
		see above.)
	Conr	nectors
	J1, J2	3-way terminal blocks
	J3,J5	2-way PCB connectors
	J6,J7	2-way terminal blocks
	J4	3-way PCB connectors
	SK1	Male mains socket (Euro chassis plug,
		Maplin stock number MK19V)
	SK2	Female mains socket (Euro chassis
		socket, Maplin stock number MK17T)
	SW1	toggle switch
	Box	H2851 box (Maplin BZ74R)

Bit_weight	index 2,	
send_data	index 3,	
transmit	index 4;	
*******************Main		
rogram************************************	*}	
egin		
end.		

The graphic interface of the Visual Basic software driver is shown in figure 10. The program first reports the number of LPTs installed on your PC, then it asks users to select an LPT port to be used. Next the control panel appears on the screen. Users need to input the address of the mains switch and the data to be sent. If D0 of the radio receiver module is used to control the mains switch, input 1. Then users need to input the period of ON and the period of OFF of the mains switch. Clicking the Start button using the mouse starts the remote control. Clicking the Stop button any time will terminate the remote control.

The complete VB3 program listing is shown in listing 2. The VB program is very simple, but it shows the basics in Visual Basic programming. At the beginning of the program, declare functions declare four DLL functions. All the functions can be called elsewhere within the VB3 program.

Declare Function Centronic Lib "c:\project\home\whdll.dll" (ByVal X As Integer) As Integer

Declare Function Bit\_weight Lib "c:\project\home\whdll.dll" (ByVal X As Integer) As Integer

Declare Function send\_data Lib "c:\project\home\whdll.dll" (ByVal P\_address As Integer, ByVal address As Integer, ByVal datax As Integer) As Integer

Declare Function transmit Lib "c:\project\home\whdll.dll" (ByVal P\_address As Integer, ByVal flag As Integer) As Integer

It should be pointed out that the dynamic link library, WHDLL.DLL, should be stored in the directory c:\project\home. Using the Windows DLLs provided, uses can write more sophisticated and more adventurous software for controlling the mains controllers.

#### Listing two WINHOME

```
Declare Function Centronic Lib
"c:\project\home\whdll.dll" (ByVal X As Integer) As
Integer
Declare Function Bit_weight Lib
"c:\project\home\whdll.dll" (ByVal X As Integer) As
Integer
Declare Function send_data Lib
"c:\project\home\whdll.dll" (ByVal P_address As
Integer, ByVal address As Integer, ByVal datax As
Integer) As Integer
Declare Function transmit Lib
"c:\project\home\whdll.dll" (ByVal P_address As
Integer, ByVal flag As Integer) As Integer
Dim address, datax, Onstatus, centronic_address As
Integer
Dim ontime, offtime As Integer
Sub Command1 Click ()
 'assign variables
 address = Val(text1.Text) 'address of the mains
controller
 datax = Val(text2.Text) 'data sent to the mains
controller
 ontime = Val(text3.Text) * 1000'period of ON
offtime = Val(text4.Text) * 1000'period of OFF
 timer1.Interval = ontime
 timer1.Enabled = True
 Onstatus = 1
```

```
End Sub
Sub Command1_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
  label9.Caption = "Start the automatic control"
End Sub
Sub Command2_Click ()
 timer1.Enabled = flase
End Sub
Sub Command2_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
 label9.Caption = "Stop the automatic control"
End Sub
Sub Command3 Click ()
End
End Sub
Sub Command3_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
  label9.Caption = "Quit the program"
End Sub
Sub Form_Load ()
dummy = MsgBox(Str(Centronic(0) - 1) & " Centronic
ports are installed on your PC. Their base
addresses are: " & Format$(Centronic(1), "###") & "
" & Format$(Centronic(2), "###") & " " &
Format$(Centronic(3), "###") & " &
Format$(Centronic(4), "###") & "Decimal", 48,
"Centronic ports on your PC")
Centroic_number = Val(InputBox$("Input 1, 2, 3 or
4 to select a Centroic port (Centroic) for the
Mini-Lab Data Logger/ Controller", "Select Centroic
ports"))
 centronic_address = Centronic(Centroic_number)
 centronic_address = 632
 timer1.Enabled = False
End Sub
Sub Label9_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
 label9.Caption = "On-line help window"
End Sub
Sub Text1_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
 label9.Caption = "Input address of controller, 0
to 255"
End Sub
Sub Text2_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
  label9.Caption = "Input the 4-bit data 1,2,4 or
8"
End Sub
Sub Text3_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
  label9.Caption = "Input the ON period in second"
End Sub
Sub Text4_MouseMove (Button As Integer, Shift As
Integer, X As Single, Y As Single)
 label9.Caption = "Input the OFF period in second"
End Sub
Sub Timer1_Timer ()
 If Onstatus = 1 Then
  timer1.Enabled = flase
  dummy = transmit(centronic_address, 0)
  dummy = send_data(centronic_address, address,
datax)
   dummy = transmit(centronic_address, 1)
   For i = 1 To 100000
   i = i
   Next i
```

Onstatus = 0

timer1.Interval = offtime

```
timer1.Enabled = True
Else
timer1.Enabled = flase
dummy = transmit(centronic_address, 0)
dummy = send_data(centronic_address, address, 0)
dummy = transmit(centronic_address, 1)
For i = 1 To 100000
i = i
Next i
Onstatus = 1
timer1.Interval = ontime
timer1.Enabled = True
End If
End Sub
```

#### **Final words**

A number of mains switches can form a mains control network which is fully controlled by one computer. To make a good control of mains, you need a good software driver. As the radio transmitter is connected to the printer port, any type of computer can be used. Have you ever thought about using your Mac, your Amiga or your Psion organiser to control such a radio mains control system? Here imagination is unlimited.

#### Components

The parts lists for the radio transmitter and receiver modules were given in Part 1 of this series (ETI Volume 26 Issue 3).

#### Part 1

For anyone who missed Issue 3 this year, Back issues of ETI are available for £3.05 each from Nexus Subscription Services, ETI, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leicestershire LE16 9EF. Backissue enquiries 01858 435322. Please make cheques payable to Nexus Special Interest.

#### **Technical support**

Constructors should be able to obtain most of the components from Maplin or Electromail. The VB3 software driver (source code and EXE files) and DLLs are available at a price of £15.00 UK from me. The PCB boards for a pair of radio transmitter and receiver module is £12.00. The PCB board for the mains switch is £8.00. The mains transformer is avialable for £3.90. I also have a limited number of kits which put everything together in a package. Please direct your enquiry to Dr. Pei An, 11 Sandpiper Driver, Stockport, SK3 8UL UK. My telephone and answer phone number is 0161 477 9583 and my e-mail is PAN@FS1.ENG.MAN.AC.UK



Figure 10: a Visual Basic control panel for testing the radio mains control system







Call for educational, multi-user and dealer pricing - new dealers always wanted. Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

c t

оп

C

# Sound Switcher Circuit

## Terry Balbirnie starts a series of adaptable circuits for GCSE- and similar-level projects with a module to trigger a reaction when a sound it made.

very so often during your school or college course in Electronics or Technology, you will be asked to undertake a project. Some teachers and lecturers give a fairly specific idea of what the finished device should do and what components it should

contain. Some examinations boards require you to make a project with a specification set by them. However, for midcourse assessments and for many other examinations you will have to work on a project of your own choice.

#### Making a start

So, where do you begin? It is always best if the project reflects some specific interest which you have, such an another hobby or voluntary activity. It may be related to some other person such as an aid for the disabled, a child's toy and so on. This type of personal interest will show through when you come to write up your report. Also, since the finished device will probably be given back to you at the end of the course or module, you will have something else useful for your hard work!

Over the coming months (although not every month), we shall provide some basic projects which cater for a variety of interests. You will be able to use a circuit as it stands or modify it for the purpose you have in mind. All the designs will be fairly basic so no one should have too much trouble understanding how their chosen circuit works or how to construct it. Any modifications and experimental work is left up to you. The designs are open-ended, so that there will be plenty to make the more able student think - in fact, there are one or two slightly off-beat features built into each one for this very purpose. The end product in each case will be a circuit panel which "does something".

All the devices are given in the form of a circuit diagram and a stripboard (Veroboard) layout. This will be useful for anyone who does not have the facility for making actual PCBs. Also, the "in-line" stripboard arrangement more resembles the circuit diagram than a true PCB and is more easily followed by some people. Of course, some students will wish to translate the circuit diagram into true PCB form.

#### **Down, Rover**

This month we shall look at a sound-operated switch which may be used to operate a toy - such as a cardboard dog which jumps out of a kennel when you whistle. It could also be used for environmental studies work where a light is meant to come on when the sound reaches a certain level. Another idea would be to use it to trigger a photographic flash gun. By setting up the camera in darkness with the shutter open, a photograph would be taken of anything that made a sound. Anyone want to try Ghost Busting?

The circuit terminates in a relay output so that it may be used to operate a wide variety of devices, including other electronic circuits, by means of a separate battery. For high-powered lamps, motors and solenoids it will be necessary to upgrade the relay to an appropriate heavyduty type. Another idea would be to use the relay on the PCB to operate the coil of the up-rated one "piggy back' fashion.



#### Sound circuit

The circuit for the sound switch is shown in figure 1. Power is obtained from a 9V PP9 battery or six "M" size cells in a suitable holder. A PP3 battery is not really up to the job. Diode DI allows current to pass and charge up capacitor C4 which then gives a supply for most of the circuit. The capacitor provides a reserve of charge and helps to promote stable operation. The relay coil is powered direct - that is, before DI and C4. Its power supply needs no special treatment.

Microphone MIC1, picks up the

	Resis	stors
	RI	1k
	R2	2M2
	R3	4k7
	R4	33k
	R5	10k
1	R6	470k
	R7	560R
	R8	47k
	R9	100k
1	R10	3k9
	RV1	47k mm vertical preset
	RV2	1M mm vertical preset
and the		
		citors
and all	C1, C3	10p 16V electrolytic
er+-	C2	100n mm metallised polyester
5	C4	1000u 16V electrolytic
Ø	a serie	Monodoso oto Sentesteras da atomis
	General Conterna	conductors
(UP)	IC1	CA3140E
O	IC2	7555
	Q1	BC108C
	Q2	ZTX300
2	D1	1N4001 Selection and even selection
	D2	1N4148
50	LED1	3mm red LED
PARTS LIST for the Sound Switcher	Misc	ellaneous
	RLAT	Mm relay with 6V coil and 2A "make"
9		contacts
	MIC1	Mm electret microphone insert (2-pin type)
O I	1 in ma	trix stripboard; PP9 battery and connectors;
	8-pin d	Il sockets. The relay used in the prototype
	was typ	be FM9IY from Maplin.

sound and converts it into electrical signals. These take the form of very weak ac which changes in frequency and amplitude to represent the sound being received. The type of microphone specified contains a FET (field effect transistor) pre-amplifier which boosts the signal given at the output. Resistor R1 provides the supply to the pre-amplifier from the positive line. Note that the pre-amplifier supply input and the signal output are the same pin.

The signals, which are still very weak, are passed from the output via capacitor, C1, to the base of transistor, Q1. This amplifies them further. Resistors R2 and R3 provide bias with some negative feedback so that the transistor is partially turned on. It is then found that about one half of battery voltage appears across the collector resistor R3. The other half exists between Q1 collector and emitter. These points could be checked using a voltmeter at the end. Capacitor C1 allows the ac signal to flow from the microphone output to Q1 base while blocking the standing dc voltage which exists there. This would otherwise upset the bias of Q1 because the two voltages would be different.

When sound is received by the microphone, the steady voltage existing between QI collector and emitter will rise and fall in sympathy. Whistling at a distance of 1m from the microphone in the prototype unit provided a 1V change approximately. At the end of construction and particularly if the unit fails to work, this could be checked using an oscilloscope. Preset potentiometer RV1 behaves as a potential divider and scales down the voltage between Q1 collector and emitter. This will be used as a sensitivity control and the way in which it works will be explained presently.

#### **Voltage comparator**

The next section of the circuit is a voltage comparator and is based on operational amplifier (op-amp), IC1. The rule is this: if the voltage applied to the non-inverting input (pin 3) exceeds that at the inverting one (pin 2) then the output, pin 6, will be high otherwise it will be low. Pin 2 receives a fixed voltage equal to about one-quarter that of the supply due to the potential divider action of resistors R4 and R5. RV1 will be adjusted so that the voltage applied to pin 3 is slightly less than that at pin 2. Since there is about one-half of supply voltage existing across the outer terminals of RV1, the balance point will be found at about the mid-point of the track. With the voltage at pin 3 being less than that at pin 2, the op-amp output, pin 6, will be low and LED1 off. The LED will be used as an aid to setting-up RV1 correctly at the end. Resistor R7 limits its operating current to I2mA approximately. When sound is detected, the rising parts of the waveform appearing at Q1 collector will be reflected in a rising voltage at IC1 pin 3 and, if is loud enough, will rise above the voltage at pin 2 on the peaks. Pin 6 will therefore go high and low as the wave rises and falls. This is passed on to the next section of the circuit which is a monostable based on the 7555 timer, IC2. Resistor R6 applies a little positive feedback to the system and this sharpens the switching action.

#### **Good timing**

When the first low pulse is received at IC2 trigger input, pin 2, the output (pin 3) will go high for a certain time then revert to low. The time during which it does this depends on the values of capacitor C3, fixed resistor, R9 and preset variable, RV2. With the specified components, the timing will lie between 1 second and 10 seconds approximately with RV2 providing the adjustment. The timing could be increased by raising the value of C3 in proportion and vice versa and this could be the subject of experiment at the end. In the absence of sound, the





## GAL PROGRAMMER £89.95

#### 16V8 / 16V8A / 16V8Z / 20V8 / 20V8Z / 20V10

- Works on IBMPC / compatible / laptops / Notebooks
  Plugs into Centronics printer port.
  - Fast and reliable programming using manufactures algorithims.
  - Program protection fuses prevent unauthorised copying
  - · Easy to use software load/save in JEDEC format
  - Supplied with PLAN logic compiler software
  - Stylish compact case with quality ZIF
  - Complete with examples, connection lead and PSU
  - Full 12 months parts and labour guarantee

#### (P87C51/2 PROGRAMMER) £79.95

Programs all makes of **P87C51/2** and **Amtel 89C51 Flash types** Cased as above, this unit plugs into the serial port on any IBM PC or compatibles and is complete with software, connection lead, PSU, and 12 months guarantee

#### EPROM PROGRAMMER

#### EPROMS / EEPROMS / FLASH EEPROMS / 12C BUS EEPROMS Covers all devices from 2K to 8MEG



The Megaprom Eprom Programmer plugs into the Centronics port on any IBM PC or compatible. The easy-touse software supports Bin, Intel Hex, Motorola S, and ASC file formats. Read / Edit / Verify / Reprogramme etc - very fast programming and verification. Requires 12-18V AC/DC PSU. The megaprom comes with

Requires 12-18V AC/DC PSU. The megaprom comes with full 12 months guarantee

#### SMARTCARD READER / PROGRAMMER

£79.95

Read/Program 1,2,3 chip D2MAC, Wafer, new Digital 'Gold', ISO7816 (Videocrypt, GSM, Telephone, etc) cards.



This powerful unit reads and programs an amazing variety of smartcards, Easy to use software allows you to simply load in codes and program them to the card of your choice. The type of card is selected by setting the on-board jumpers. In ISO mode (Videocrypt, GSM, etc) you can send single or multiple bytes to the card and 'log' it's response. Knowledge of correct codes can result in cards being altered (eg serial number change, revival of dead cards, altering of unit amounts). Ideal for 'educational' use and 'investigation' into smart card

technology the unit also allows the 'in circuit' programming of PIC 84 chips. Unit comes with 'interesting' text files relating to smartcard encryption, software, current D2MAC codes, connection lead details and full 12 months guarantee. Note: This unit **must not** be used to copy Videocrypt, GSM, or Telephone cards.

## **EPROM EMULATOR**

#### £89.95

This is the ideal way to test / change 'running' code on CPU based systems. It plugs directly to the printer lead of an IBM compatible computer. There are no internal cards so it is ideal for laptops etc. The unit emulates ALL Eproms from 24 pin 2716 (2k) to 32 pin 27C0]0 (128k). The memory can be configured as 128k by 8 bits or 2x64k by 8 bits. A CPU reset line is provided and the user can select, high/low or low/high reset signals. Software supplied has full screen editing and allows you to save and load code with offsets. Full 12 month guarantee.



£99.95

ELECTRONICS TODAY INTERNATIONAL

57

#### **£1 BARGAIN PACKS** - List 1

1,000 items appear in our Bargain Packs List - request one of these when you next order.

1 x 12V Stepper Motor. 7:5 degree. Order Ref; 910. 1 x 10 pack Screwdrivers. Order Ref: 909. 2 x 5 amp Pull Cord Celling Switches. Brown. Or-

2 x 5 amp Puil Cord Celling Switches. Brown. Or-der Ref: 921. 5 x reels Insulation Tape. Order Ref: 911. 4 x 14mm Bull-races. Order Ref: 912. 2 x Cord Grip Switch Lamp Holders. Order Ref: 913 913

1 x DC Voltage Reducer. 12V-6V. Order Ref: 916. 1 x 10 amp 40V Bridge Rectifier. Order Ref: 889. Lightweight Stereo Headphones. Moving coil so superior sound. Order Ref: 896.

2 x 25W Crossovers. For 4ohm loudspeakers. Order Ref; 22.

2 x NiCad Constant Current Chargers. Easily adaptable to charge almost any NiCad battery. Order 18V-0-18V 10VA mains transformer. Order Ref: 813.

18V-0-18V 10VA mains transformer, Order Ref: 813. 2 x White Plastic Boxes. With lids, approx. 3" cube. Lid has square hole through the centre so these are ideal for light operated switch. Order Ref: 132. 2 x Reed Relay Kits. You get 8 reed switches and 2 coil sets. Order Ref: 148. 12V-0-12V 6VA mains transformer, p.c.b. mounting. Order Ref: 938.

Groer Hef: 938. 1 x Big Puil Solenoid. Mains operated. Has ½" pull. Order Ref: 871. 1 x Big Push Solenoid. Mains operated. Has ½" push. Order Ref: 872. 1 x Mini Mane

push. Order Ref: 872. 1 x Mini Mono Amp. 3W into 4 ohm speaker or 1W into 8 ohm. Order Ref: 495. 1 x Mini Stereo 1W Amp. Order Ref:870. 15V DC 150mA p.s.u., nicely cased. Order Ref: 942. 1 x In-Flight Stereo Unit is a stereo amp. Has two most useful mini moving coll speakers. Made for BOAC passengers. Order Ref: 29. 1 x 0-1mA Panel Meter. Full vision fact 70mm square. Scaled 0-100. Order Ref: 756. 2 x Lithlum Batterles. 25V penioht size. Order Ref:

2 x Lithlum Batteries. 2.5V penlight size. Order Ref: 874

8/4. 2 x 3m Telephone Leads. With BT flat plug. Ideal for phone extensions, fax, etc. Order Ref: 552. 1 x 12V Solenoid. Has good ¼<sup>\*</sup> pull or could push if modified. Order Ref: 232. 3 x In-Flex Switches. With neon on/off lights, saves

3 x In-risk Switches, with head on Order Ref: 7. 2 x 6V 1A Mains Transformers. Upright mounting with fixing clamps. Order Ref: 9. 2 x Humidity Switches. As the air becomes damper, the membrane stretches and operates a micro switch. Order Ref: 32.

4 x 13A Rocker Switch. Three tags so on/off, or changeover with centre off. Order Ref: 42. 1 x Suck or Blow-Operated Pressure Switch. Or it

can be operated by any low pressure variation such as water level in tanks. Order Ref: 67. 1 x 6V 750mA Power Supply. Nicely cased with mains input and 6V output lead. Order Ref: 103A.

x &V 750mA Power Supply. Nicely cased with mains input and 6V output lead. Order Ref: 103A.
 x Stripper Boards. Each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc. Order Ref: 120.
 Very Fine Drills. For PCB boards etc. Normal cost about 80p each. Order Ref: 128.
 x Motors for Model Aeroptanes. Spin to start so needs no switch. Order Ref: 134.
 x Microphone Inserts. Magnetic 400 ohm, also act as speakers. Order Ref: 139.
 x Neon Indicators. In panel mounting holders with lens. Order Ref: 180.
 x In-Flex Simmerstat. Keeps your soldering iron etc always at the ready. Order Ref: 199.
 x Mains Solenoid. Very Powerful as ½" pull, or could push if modified. Order Ref: 211.
 x 12 Valarms. Makes a noise about as loud as a car hom. All brand new. Order Ref: 211.
 x (6" x 4") Speakers. 16 ohm 5 watts, so can be joined in parallel to make a high wattage column. Order Ref: 243.
 x Panostat. Controls output of boiling ring from simmer up to boil Order Ref: 252

Order Ref: 243.
1 x Panostat. Controls output of boiling ring from simmer up to boil. Order Ref: 252.
2 x Oblong Push Switches. For bell or chimes, these can switch mains up to 5A so could be foot switch if fitted in pattress. Order Ref: 263.
50 x Mixed Silicon Diodes. Order Ref: 293.
1 x 6 Digit Mains Operated Counter. Standard size but counts in even numbers. Order Ref: 28.
2 x 6V Operated Reed Relays. One normally on, other normally closed. Order Ref: 824.
1 x Cabinet Lock. With two keys. Order Ref: 55.
6½ 8Ω 5 Watt Speaker. Order Ref: 824.
1 x Shaded Pole Mains Motor. 34" stack, so quite powerful. Order Ref: 85.
2 x 5 Aluminium Fan Blades. Could be fitted to the

2 x 5 Aluminium Fan Blades. Could be fitted to the above motor. Order Ref: 86. 1 x Case, 3½ x 2¼ x 1¾ with 13A socket pins. Order

Ref: 845 2 x Cases, 21/2 x 21/4 x 13/4 with 13A pins. Order Ref:

565 4 x Luminous Rocker Switches, 10A mains. Order

Ref: 793 4 x Different Standard V3 Micro Switches. Order Ref: 340.

4 x Different Sub Min Micro Switches. Order Ref:

313

#### **BARGAINS GALORE**

INSULATION TESTER WITH MULTIMIETER. Internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges, AC/DC volts, 3 ranges miliarnes, 3 ranges resistance and 5 amp range. These instruments are werken that hele-com but in very good condition, tested and guaranteed CK, probably cost at least ES0, yours for only £7.50 with leads, carrying case £2 extra, Order Rei 7.574. THIS INSTRUMIENT but signify faulty – you should be able to repair it. We supply circuit diagram and notes, £3, Order Rei 7.8176. 12Y 10A SWITCH MIODE POWER SUPPLY. For only £9.50 and a little bit of work because you have to convert our 135W PSU. Modifications are relatively simple – we supply instructions. Simply Order PSU Rei : 9.5P2 and request modification details. Price still £9.50. MEDICINE CUPBOARD ALARML Or it could be used to warn when any cupboard door is opened. The light shining on the unit makes the bell ring. Completely built and neally cased, requires only a battery, £3, Order Rei : 39152. INSULATION TESTER WITH MULTIMETER. Internally general instance which enable you to read insulation directly in megohins. T

L1, Otter Her. Str 133: DOM'T LET IT OVERRLOWI Be it bath, sink, cellar, sump or any other thing that could flood. This device will tell you when the water has risen to the preset level. Adjustate over quite a useful range. Neally cased for well mounting, ready to work when battery fitted, £3, Order Ref: for wa 3P156

SP156. VERY POWERFUL MAINS MOTOR. With extra long (21/5) shafts extending out each side. Makes it ideal for a reversing arrangement for, as you know, shaded pole motors are not reversible, £3, Order Ref. 39157.

SOLAR PANEL BARGAIN, Gives 3V at 200mA, 52, Order Ref: 2P324.=

E1 SUPER BARGAIN 12V axial tan tor only £1, ideal for equipment cooling, brand new, made by West German com-pany. Brushless so virtually everlasting. Needs simple transistor drive circuit, we include diagram. Only £1, Order Ret 191. When we supply this we will include a list of approximately 800 of our other £1, bargains.

LIGHT DIMMERS. On standard plate to put directly in place of flush switch. Available in colours, green, red, blue and yellow, £2.50, Order

Ref: 25-P9. 45A DOUBLE POLE MAINS SWITCH. Mounted on a 6" x 3% aduminium plate, beautifully finished in gold, with pilot light. Top quality, made by MEM, 52, Onder Ref: 29316. DON'T STAND OUT IN THE COLD. Our 12m telephone extension lead has a flat BT socket one end and flat BT plug other end, 52, Order Ref: 29338. 20W 4 OHM SPEAKER. 53, Order Ref: 3P145. Matching 4 ohm 20W tweeter on separate baffle, 51:50, Order Ref: 1.5P9.

LCD 3% DIGIT PANEL METER

This is a multi-range voltmeter/ammeter using the A-D converter chip 7106 to provide 5 ranges each of volts and amps. Supplied with full data sheet. Special ship price of £12, Order Ref: 12P19.

TELEPHONE EXTENSION WIRE. 4 core correctly colour coded, in-tended for permanent extensions, 25m coll, 12, Order Ref. 2P339. PHILIPS 9 HIGH RESOLUTION MONITOR. Black and while in metal

PHILIPS IF HIGH RESOLUTION MONITOR. Black and white in metal frame for easy mounting. Brand new, still in maker's packing, offered at less than price of tube alone, only £15, Order Ref: 15P1. HIGH CURRENT AC MAINS RELAY. This has a 230V coll and changeover switch rated at 15A with PCB mounting with clear plastic cover, £1, Order Ref: 955. ULTRA THIN DRILLS. Actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per Jack. Tother Ref: 7978. YOU CAN STAND on ITT Made to house GPO telephone equipment.

TUE LAW STARE UNITT Made to house GPO telephone equipment, this box is extremely lough and would be ideal for keeping your small tools in, internal size approx. 10½ x 4½ x 6° high. Complete with carrying strap, price £2, Order Ref: 2P2338. ULTRA SONIC TRANSDUCERS. Two metal cased units, one trans-mits, one receives. Built to operate around 40kHz, price £1.50 fle pair, Order Ref: 1.5P4.

Order Ref: 1.5P4. POWER SUPPLY WITH EXTRAS. Mains input is fused and fillered and the 12V DC output is voltage regulated, intended for high class equipment, this is mounted on a PCB and also mounted on the board but easily removed, are two 12V relays and Piezo sounder. Price £3, Order Ref: 3P808. MAINS ISOLATION TRANSFORMER. Stops you getting "to earth" shocks, 230V in and 230V out, 150W, (7.50, Order Ref: 7.5P5, and a 250W version is £10, Order Ref: 10P97. MAINS 230V FAN. Best make "PAPST", 4½" square, metal blades, E8, Order Ref: 8P8.

MAINS 200V FAIL best make "PAPSI", 4½ square, metai backs, £3, Order Ref: 8P8. 201W LASER. Helium neon by Philips, full spec., £30, Order Ref: 30P1, Power supply for this in kit form with case is £15, Order Ref: 15P16, or in larger case to house tube as well, £18, Order Ref: 18P2. The larger unit, made up, tested and ready to use, complete with taser tube, £59, Order Ref: 63P1.

#### 10% FREE If you order ten of an item we will add an eleventh one free.

AIR SPACED TRIMMER CAPS. 2-20pl, ideal for precision tuning UHF

Am STACED Triament GATS, 2-200, Use in proceed using orm circuits, 4 for 11, Order Reit 8188. MODEM AMSTRAD FM240. As new condition but customer return so you may need to fault find, 50, Order Reit 6734. AMSTRAD POWER UNIT. 13.5V at 1.9A or 12V at 2A encased and

AMSTRAD POWER UNIT. 13.5V at 1.9A or 12V at 2A encased and with leads and output plug, normal mains input, 85, Order Rei: 6P23. 80W MAINS TRANSFORMER. Two available, good quality, both with normal primaries and upright mounting, one is 20V 4A. Order Ref: 3P106, the other 40V 2A, Order Rei: 3P107. PROJECT BOX. Size approx. 8 x 4 x 4½° metal, sprayed grey, lourved ends for vernilation otherwise undrilled. Made for GPO so best quality, only 25 acch, Order Ref: 3P74. SENTWEL COMPONENT BOARD. Amongst hundred of other parts, this has 15: cs., all plug ins o do not need soldering. Cost well over £100, yours for £4, Order Ref: 4P67. 15W 8 Orlin 8' SPEAKER & 3' TWEETER. Made for a discontinued high quality music centre, gives real hi-fl and only £4 per pair, Order Ref: 4P57.

WATER PUMP. Very powerful, mains operated, £10, Order Ref: 10P74

WATER FOWE, very powerus, mains operated, and construct 10P74.
0-1mA FULL VISION PANEL METER, 2.34° square, scaled 0-100 but scale assily removed for re-writing, 15 each, Order Ref: 756.
AMSTRAD KEYBOARD MODEL KB. This is a most comprehensive keyboard, having over 100 keys including, of course, full numerical and gwerty. Brand new, still in malker's packing, order Ref: 5P202.
4 RPM MOTOR. This is only 2W so will not cost much to nur. Speed is ideal for revolving mirrors or lights, £2, Order Ref: 2P288.
UNUSUAL SOLENOID. Sciencide normally have to be energised to pull in and hold the core, this is a disadvantage where the appliance is left on for most of the time. We now have magnetic solencids which hold the core until a voltage is applied to release it. £2, Order Ref: 2P327.

2P327. MAINS FILTER. Resin impregnated nicely cased, p.c.b. mounting, £2, Order Ref: 2P315.

ELECTRONICS TODAY INTERNATIONAL 58

#### **£1 BARGAIN PACKS** - List 2

This is the  $\pounds$ 1 Bargain Packs List 2 – watch out for lists 3 and 4 next month.

3 x Battery Model Motors, tiny, medium and large, Order Ref: 35 Order Ref: 35. 2 x Tuning Capacitors for super-het wave radios, Or-der Ref: 36.

oer Her. so. Miniature 12V Relay with low current consuming coil, 2 x 3A changeover contacts, Order Ref: 51. 2 x Ferrite Stab Aerials with medium wave coils. Ideal

oudspeaker volume control, Order Ref: 69. istors. Ideal for

2 x Wirewound Variable Resistors in any of the fol-lowing values, 18, 35, 50, 100 ohms, your choice, Order Ref: 71.

4 x 30A Procelain Fuse Holders. Make your own fuse board, Order Ref: 82. 1 x 5½" Metal Fan Blades for 5/16" shaft, Order Ref:

86/61/5

86/6%. Mains Motor to suit the 6½" blades, Order Ref: 88. 1 x 4.5V 150mA DC Power Supply. Fully enclosed so quite safe, Order Ref: 104. 10 each red and black small size Crocodile Clips, Order Ref: 116. 15m Twin Wire, screened, Order Ref: 122A.

15m I win wire, screened, Order Hei: 122A.
100 Plastic Headed Cable Clips, nail in type, several sizes, Order Ref: 123.
4 x MES Batten Holders, Order Ref: 126.
4 x 2 Circuit Micro Switches (Licon) Order Ref: 157.
1 x 13A Switch Socket, quite standard but coloured, or the standard but coloured.

Order Ref: 164. 1 x 30A Panel Mounting Toggle Switch, double-pole, Order Ref: 166. 2 x Neon Numicator Tubes, Order Ref: 170. 100 x 3/8 Rubber Grommets, Order Ref: 181

2 x ex-GPO Speaker Inserts, ref 4T, Order Ref; 352 100 x Sub Min 1F Transformers. Just right if you want coil formers, Order Ref: 360. 1 x 24V 200mA PSU, Order Ref: 393. 1 x Heating Element, mains voltage 100W, brass en-cased, Order Ref: 8.

1 x Mains Interference Suppressor, Order Ref: 21. 3 x Rocker Switches, 13A mains voltage, Order Ref:

1 x Mini Uni-Selector with diagram for electronic jigsaw, Order Ref: 56. 2 x Appliance Thermostats, adjustable 15A, Order Ref: 65.

1 x Mains Motor with gearbox giving 1 rev per 24 hrs, Order Ref: 89. 10 x Round Pointer Knobs for flatted 1/4" spindles,

1 x Ceramic Wave Change Switch, 12-pole, 3-way with ¼' spindle, Order Ref: 303. 1 x Tubular Hand Mike, suits cassette recorders, etc. Order Ref: 305 2 x Plastic\_Stethosets, take crystal or magnetic in-

seris, order Ref: 331. 20 x Pre-eet Resistors, various types and values, Or-der Ref: 332. 6 x Cer Type Rocker Switches, assorted, Order Ref:

1 x Reversing Switch, 20A double-pole or 40A single-pole, Order Ref: 343. 4 x Skirted Control Knobs, engraved 0-10, Order Ref:

335. 3 x Luminous Rocker Switches, Order Ref: 373. 2 x 1000W Tubular Heating Elements with terminal ends, Order Ref: 376. 1 x Mains Transformer Operated NICad Charger, cased with leads, Order Ref: 385. 2 x Clockwork Motors, run for one hour, Order Ref:

389. MINI AM/FM TUNING CAPACITOR. Only 1" square but has a good length of 1/" diameter spindle with 4 variable preset caps for fine tuning. Price £1, Order Ref: D202. ANOTHER 7" FERRITE ROD AERIAL. This is an extra special 1/2" diameter with long and medium wave coils. Price £1, Order Ref: D203.

TERMS

Send cash, PO, cheques or quote credit card number --orders under £25 add £3 service charge.

**J&N FACTORS** 

**Pilgrim Works (Dept. E.E.)** 

Stairbridge Lane, Bolney, Sussex RH17 5PA

Telephone: 01444 881965

Order Ref: 295.

333

355

389

100 x 3/8 Rubber Grommets, Order Ref: 181. 4 x BC Lamp Holder Adaptors, Order Ref: 191. 8 x Superior Type Push Switches. Make your own keyboard, Order Ref: 201. Mains Transformer 8V-0V-8V ½A, Order Ref: 212. 2 x Sub Min Toggle Switches, Order Ref: 214. High Power 3" Speaker (11W 80hm) Order Ref: 246. Medium Wave Permeability Tuner. Its almost a com-plete radio with circuit, Order Ref: 247. 6 x Screwdown Terminals with through panel in-sulators, Order Ref: 269. 10 x Push-On Long Shafted Knobs for ¼" spindle, Order Ref: 339. 2 x ex-GPO Speaker Inserts, ref 4T, Order Ref: 352.

trigger input, pin 2, is kept high through resistor R8 and this prevents possible false operation. Note that if sound continues to be picked up, IC2 will receive repeated triggering pulses and the output will remain high.

If the unit needs to be more sensitive, you will need to adjust RVI so that the standing voltage at ICI pin 3 is only slightly less than that at pin 2. The monostable will then be triggered with only a very small sound.

With the monostable output high, current flows through resistor R10 to the base of transistor Q2. This turns it on and collector current flows through the coil of relay, RLA1. The "make" contacts of this component then act as a switch for any device requiring less than 2A which is the maximum current rating of the contacts. Diode D2 allows the high-voltage reverse pulse which appears across the coil when it switches off to be bypassed. This prevents possible damage to other semiconductor components in the circuit. The external device must be powered using a separate battery - do not try to use the battery which is used to operate the circuit. If you did, the sudden increase in current would cause a dip in the supply voltage. This would probably interfere with correct operation of the main section.

#### Construction

Note that an electret microphone insert is used for this project. This is the working part of the microphone without the case, lead, etc. This is much cheaper than a complete microphone. Some microphone inserts have pads on the base and other have short end wires. On the whole, wires are more convenient. If the microphone used is of the "pad" type, small bare wire "stalks" will need to be soldered to them before proceeding. Some microphones are of the three-wire type but the two-wire variety is used here. transistors, microphone insert and capacitors C1, C3 and C4 the correct way round. Look at the underside of the microphone - the pad which connects to the case is soldered to the 0V line. Solder PP9-type battery connectors or as required to the "+9V" and "0V" tracks as indicated. Solder wires to the relay contact tracks. Adjust RV1 to about midtrack position and RV2 fully clockwise (as viewed from 1C2 position) which will give minimum timing. Insert the ic taking care over the orientation. Both of them are CMOS components and could be damaged by static charge which might exist on the body. Earth yourself by touching the bare metal of a water tap first.

#### Testing

It is necessary to test the circuit in a quiet room! Connect up the battery. The circuit generally self-triggers on powering-up and the relay will probably be heard to operate. It will then click off again after about one second. Adjust RV1 until the LED is off. Clap your hands near the microphone. The LED should come on momentarily and the relay should click on and off again. If this does not work, adjust RV1 a little and try again. Try increasing the sensitivity noting that if RV1 is set too finely, the circuit will go unstable and the LED will flash on and off repeatedly. The circuit will work if the LED is normally just on instead of just off. However, this tends to be a less stable arrangement.

#### **Ideas for experiments**

This circuit must not be used to operate mains appliances. It is not designed to control mains and would be extremely dangerous. The relay "break" (normally closed) contacts could be used to switch an item off during the monostable timing period although this is probably less useful than switching it



The topside stripboard layout (component side view) for the Sound Switch is shown in figure 2. Note that there are a large number of track breaks and several inter-strip links needed. Make the track breaks first using a proper spot face cutter. *Most causes of malfunction are due to strips not being broken completely, a break or "bridge" being left out, a break in the wrong place or a small blob of solder or sliver of copper bridging adjacent tracks.* Some of these are invisible to the naked eye. You have been warned! Make the inter-strip links and follow by soldering the ic sockets in position, and then all the remaining components. Take care to mount the on. For more sensitive operation, the supply voltage might need to be stabilised. Set the monostable time period as required. If necessary use an alternative value for C3.

A small motor at the output could be used to make something turn or move, possibly for a toy. A solenoid could give a pushing or pulling effect to make "Rover" jump out of his kennel. Motors require a much higher current than their running value while they speed up. Also, other components such as solenoids and filament lamps require more current at the instant of switching on. All this must be taken into account when choosing a suitable relay.



#### A slimline storage oscilloscope and digital voltmeter with a sampling rate of up to 20 MHz. Inclusive software enables the recorded signals to be displayed simultaneously on a PC screen.

Sample Rates: From 50 ns to 1 ms. Purveyors of Quality Input Voltage: 1 V, 10 V, 100 V. Trigger: ±Internal, ±External, Auto. Voltmeter: AC and DC.

Electronic Thingles at Very Friendly Prices

Supply Voltage: 9 V to 13 V DC, 13 mA, external. Trigger, ground, power & serial cables included.

Also Available; 3 mW Laser Pointers £26 CCD Camera Modules from £60 Pinhole camera in wall clock £80 Colour CCD modules from £170 Please add £2 p&p to all orders.

Crewe+Alsager Faculty

#### PIC MICROCONTROLLERS

Beginners Course on 16C84. One day course. Fee: £125, includes lunch, 16C84 chip and Development Board plus software.

Advanced Course on 16C84 and 16C71. One day course including look-up tables, long delays, keypads, 7 segment displays and A-D conversion. Fee: £125 includes lunch and 16C71 reprogrammable Microcontroller chip, with 4 channel A-D.

Complete Teach Yourself Package including PSU, Switch Input Board, Keypad Board, Development Board, 7 Segment Display Board and Buzzer, LED Output Board, Analog Development Board and 115 page course book, plus software. Fee:  $\pounds 145 + \pounds 6 p + p + VAT$ .

Four-day Course - Understanding Microcontrollers Course Fee: £395, includes lunches and the complete teach yourself package. Accommodation available.

For dates and further details contact Dave Smith, Crewe+Alsager Faculty, The Manchester Metropolitan University, Hassall Road, Alsager, Stoke-on-Trent, ST7 2HL Tel: 0161 247 5437 Fax: 0161 247 6377 E-mail D.W.Smith@MMU.AC.UK

Mini waterproof TV camera 40x40x15mm requires 9 to 13 5 button cell 6V 280mAh battery with wires (Varta vots at 120mA with composite video output (to feed into a 5x2500K) f22.45 video or a TV with a SCART plug) it has a high resolution Orbitel 866 battery pack 12v 1.0AH contains 10 sub C of 450 TV lines Vertical and 380 TV lines horizontal, cell sub solid rags (the size most commonly used in electronic auto Iris for nearly dark (1 LUX) to bright cordless screwdrivers and drills 22 dia x 42mm tail). It is sunight operation and a small aller with a 3 tar.77 each or t110.50 per box of 14 wire lead (1/V) in grid and video out). Now allow available CD box 190x10650mm with batts to house a pcb the lid with wall mount fill and swivel case (at the same prob.) contains an edge connector (12 way 8mm pitch) and 523 57 varts = 1009.56 or 10.459.32 via 2 = 104.35 box 100 to common anode led display 12mm E0.45 to be housed in your own enclosure and have fragile GaAs FET (sw leakage cument S8073 112.95 each 129 so with 6 in arcs and is mall allow 150 and 100 to 77 Amms on the second set of the 100 to 77 Amms on the second set of the 100 to 77 Amms on the 100 to 1

speaker dia	15"	2"	8"
oower rating	250WRMS	175WRMS	100WRMS
impedance	8ohm	8ohm	8ohm
frequency range	40hz-20khz	45hz-20khz	60hz-20khz
sensitivity(1W/1M)	97dB	94dB	92dB
size in mm	500x720x340	450x640x345	315x460x230
weight	21.1kg	16.8kg	7.4kg
price each for:	•	9	5
black viny! coating	£139.95	£99.99	£54.94
grey felt coating	£159.97**	£119.97**	£64.99
(** = not normall	y in stock alio	w 1 week for d	elivery)
Power amplifiers	s 19" rack me	ount with oain	controls & VI

C = RUCHOMEN, stack mount with gain controls & VU meters STA300 2x490Wms (4ohm load) 11kg £339.00 STA900 2x490Wms (4ohm load) 11kg £365.00 LEDs 3mm or 5mm red or green ...7 peach yellow 11p each cable ties 1p each £5.95 per 1000 £49.50 per 10,000 Rechargeable Batteries AA(HP7) 500mAH 60.99 AA 500mAH with solder tags £1.55 AA 590mAH 61.75 C(HP11) 12AH £2.20 C 2AH with solder tags £1.85 C(HP11) 12AH £2.20 C 2AH with solder tags £1.95 PP3 8.4V 10mAH £4.95 1/2AA with solder tags £1.55 Sub C with solder tags £2.50 AAA (HP16) 180mAH £1.75 1CA A with tags (philpsCTV) £1.95 Nickei Metal Hydride AA cells high capacity with on emony, (I charged at 100mAH capacity (lower capacity) for high discharge rates) £3.75 Special offers please check for availability stick of 4.2 x 16mm nicad batteries 171mmx16mm dia. with red & black leads 4.8v £5.95

stock Please add £1.95 towards P&P (orders from the Scottish highlands, Northern Ireland, Isle of Man, Isle of Wight and overseas may be subject to higher P&P for heavy items), VAT included in all prices



ETI 276-278 Chatsworth Road. Chesterfield S40 2BH ccess Visa Orders (01246) 211202 fax 550959



Includes software to run from PC. KITS FROM £85.00

All prices exclude VAT and shipping For a full catalogue of the above items and other products, please call or fax Milford Instruments at 01977 683665; Fax 01977 681465.



#### Roy Bebbington's dot-dash tone touchpad can be used for Morse or for music.

he Alphanumeric Morse Touchkey is designed to enable beginners learning Morse to become familiar with the dot-dash codes and their rhythmic patterns without the aid of an instructor. The touchpad consists of a metallic baseplate

covered by a plastic overlay template with hole patterns representing the alphanumeric Morse characters. These characters can be sounded and visually displayed by drawing a finger across them at an even speed. As experience grows, students can graduate to a finger-tapping proficiency pad, to emulate the movement of a Morse key.

Merely looking at a list of dots and dashes and learning it off by heart, or by head as the Dutch say, is not the way to learn Morse. While it is comparatively easy to make a mental translation from the code to alphanumeric characters at slow speeds, in a 12 wpm test there simply isn't the time for this! With characters arriving in quick succession, each must be identified by its unique sound pattern. The touchpad method ensures that even beginners can immediately send and hear characters that are formed correctly. This would appear to have wide appeal for radio amateurs, sea cadets, scouts and sailing clubs where a knowledge of Morse code is required. With two of these pads linked to a common circuit, students would be able to send and receive rhythmically correct



messages at a very early learning stage. And talking of 'rhythmical', music students could also benefit from a suitable plastic overlay to bone up on a few basic rhythms or to sort out a few awkward syncopated bars - always a problem for beginners.

For compactness, characters that are mirror images (for example, N is the same as A in reverse) have been combined. For instance, B is sounded by a left to right movement, and the same hole pattern sounds a V by a right to left movement.

The circuit and PBD uses two 555 timer ICs. Alternatively, these could be replaced by one 556. (This would require a different PCB or stripboard layout, which we leave to the reader's ingenuity.) There are two simple stages:

-A finger touch switch operating the first 555 in monostable mode, which triggers a tone generator formed by the second 555 in astable mode.

-A LED indicator and a loudspeaker provide visual and audible output.

#### The circuit

In the circuit (figure 1), IC 1 acts in the monostable mode as a touch switch. It is preferable to mount IC1 in an ic socket. When pin 2 and the 0V rail are bridged by a resistance; the body resistance in this application, a negative-going trigger pulse is applied to IC1 that turns off an internal transistor that is normally short-circuiting pin 7 to the 0V rail. This allows capacitor C1 to charge via R1, consequently, a positive-going output pulse is produced on pin 3. Light-emitting diode DI with its current-limiting resistor R2 provides a visual indication of the applied input signal. R3 feeds these long and short positive-going pulses that represent the alphanumeric characters to pin 7 of 1C2. C3 repeatedly charges via R3 and R4, and discharges via R4, oscillating at a frequency dependent on the RC values.

Frequency = 1.44/(R3 + 2R4)C3

Rectangular pulses on pin 3 practice an audible output at a frequency of approximately 1kHz in LS1. Variable resistor RVI



Did you know that there is an organisation which has 30,000 research assistants at your disposal?

Members with creative ideas - they've done it - not just talked about it! Valuable resource information *including*:

> EMC advice Propagation forecasting Technical data Recruitment adverts

Plus, a comprehensive list of specialist publications and much, much more!

As a member you would receive RadCom, the 100 page colour magazine delivered to your door every month

Who are we? We are the national society for radio amateurs and if you are interested in electronics we can help you

RSGE

Radio Society of Great Britain (Dept ET19) Lambda House Cranborne Road Potters Bar Herts EN6 3JE Tel: 01707 659015 Fax: 01707 645105; e-mail: sales@rsgb.org.uk



provides a series volume control to mute the loudspeaker if only visual signalling is required. A potentiometer with a switch could replace the separate on/off switch.

#### Construction

The prototype was built on a small piece of 0.1 in stripboard, but a suitable layout for a printed circuit board using two 555s is given in figure 5. Alternatively, a composite PCB could be made to include both the layout of the characters and the circuit.

A generous A4-sized baseplate is preferable to prevent fingers bridging the small spaces between the dots, and in the overlay, which would result in continuous sounds. Alternatively, a metal paper-clip held between the fingers can serve as a useful stylus.

The baseplate can be a sheet of polished aluminium or baking foil glued to thick card or plastic. Cut the holes in the plastic overlay with a sharp knife and tape or glue it to the metallic base. Use rub-down lettering for the alphanumeric characters or print them on the plastic overlay. A suggested layout for the plastic overlay is shown in figure 3.

The baseplate can either be free-standing or form the upper-side of the case that houses the circuit. Otherwise, you can house the loudspeaker and battery in a small case wired up to the baseplate, or even leave the loudspeaker "adrift" and the battery tacked to the baseplate with a battery holder or some double-sided tape. The left thumb touchpad can be an isolated part of the baseplate or a separate contact somewhere convenient on the case.

#### **Musical coda**

A suitable plastic overlay for sounding basic music rhythms is given in figure 4. Any other problematic rhythmic figures could also be stencilled on to a plastic overlay. However, a better solution for a teaching aid could be made up by mounting pieces of copper clad board into a multiway



## EASY-PC Professional XM Schematic and PCB CAD



For full information and demo disk, please write, phone, fax or email:-

## **Number One Systems**

UK/EEC: Ref. ETI, Harding Way, St.Ives, Cambridgeshire., ENGLAND, PE17 4WR. Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042 Ref. ETI, 126 Smith Creek Drive, Los Gatos, CA 95030 USA: Telephone/Fax: (415) 968-9306 http://www.numberone.com

e-mail: sales@numberone.com International +44 1480 461778

PROGRAMS NOT COPY PROTECTED.

SPECIAL PRICES FOR EDUCATION.

VISA

64



	1. 1. 1. 1. 1. 1. 1. 1.			
	No. of Contents	·····································		
-	A CONTRACTOR			
	The station of the	A STATE OF THE REAL PROPERTY O		
	Resistors	STATE PLANE PLANE		
	R1	68k		
	B1 B2			
$(\mathbf{I}_{\mathbf{i}})$		1k		
	R3	68k		
-	R4	18k		
		The second states of the second states		
No.	Potentiom	leters		
	RVI	5k log (see text)		
PARTS LIST for the Morse Touchkey	and the second second	REAL PROPERTY AND INC.		
	Capacitor	S		
	C1,C2	10nF		
	C3	20nF		
	C4	4.7u 10V elect		
	C5	47u 10V elect		
e	A STATE OF	and the second second second second		
	Semiconductors			
3	IC1	555 timer		
0	102	555 timer		
10	DI	LED		
6	Car was I			
	Miscellaneous			
	LSI	8R miniature		
2	Switch			
6	State of Association of Concession, State of State	spst (on/off)		
		clip, touchpad base and overlay,		
*	connecting wir	e, solder, etc.		
P	· 当、冬川、山、竹	and set of a little set of a set of the		
		a lot and the second second second second		
2 - 75		A March		

Figure 3: musical rhythm overlay

socket as shown in the musical rhythm simulator of figure 5, using it to activate the touch circuit of figure 1. All pins of the socket must be soldered together and taken to the 0V rail. Several pieces of copper board board are needed for each type of note; quaver, crochet, etc., the widths of these depending upon the particular note values. As indicated in the diagrams, the physical widths of the notes correspond with their relative time duration; ie a crochet has a duration

of two quavers, so is twice as wide as a quaver. A minim is equal to two crochets, so is twice as wide, and similarly, a semibreve is twice as wide as at minim.

The copper clad side is deleted for the notes; the reverse side (or a piece of plain board) could be selected for an equivalent rest. Slightly space the notes in the socket to allow them to sound separately; butt any pieces together that need to sound continuously (ie as tied notes).



# ELECTRONICS ID DAY INTERNATIONAL PCB Service

**ETI** can supply printed circuit boards for most of our current projects - see the list below for boards available. For recent boards not listed, check the constructional article for an alternative supplier.

Please use this order form or a copy of it. Check that all relevant information is filled in, including the Unit Order Code, and that you have signed the form if sending a credit card number. Overseas customers please add postage appropriate to the number of units you are ordering. Make cheques/POs/money orders, in £ sterling only, payable to Nexus Special Interest Limited. Please allow 28 days for delivery. Access/Visa orders may be made on 01442 66551 (ask for Readers Services).

Only boards listed here are available from our PCB Service. For past issues of magazines, copy articles or binders, please see the admin panel (page 74) or contact Readers Services (see below) for information.

and and and and		STREED B
Name and issue of project	Unit code	Price
CTI Incurs 11 1007		
ETI Issue 11 1997 Total Harmonic Distortion Meter	E/1197/1	£13.43
Alphanumeric Morse Touchkey	E/1197/2	£5.09
Mighty Midget	E/1197/3	£8.99
PC Phonecard Reader - ITT Cannon	E/1197/4	£6.22
Minute Minder	E/1197/5	£13.98
	and the second	
ETI Issue 10 1997	ST. COLUMN	A STATE
The IQ Tester	E/1097/1	£5.64
Fake Flasher	E/1097/2	£5.09
DC Motors (Part 2)	E/1097/3	£6,77
Valve Tester Main Board	E/1097/4	£21.22
Valve Tester - Socket Board	E/1097/5	£5.09
Valve Tester - Heater Regulator	E/1097/6	£5.09
All three Valve Tester boards	E/1007/4/5/6	£30.30
(Due to price breaks there is a small discount on thi	and the second se	同志(同)(同)(1)
The IQ Tester (previously E/897/20	E/1097/7	C5 64
ETI Issue 9 1997		212.10
Eprom Emulator	E/997/1	£16.49
The Power Supply	Ę/997/2	£5.09
Electronic Door Chimes	E/997/3	£5.09
Digital Power Supply	E/997/4	£10.11
	and the second s	-
ETI Issue 8 1997	F (00714	05.00
The Brake Light Tester	E/897/1	£5.09
DC Motors (3 experimental boards)	E (007/0	05.00
DC Motors: The first Control Unit	E/897/3 E/897/4	£5.09
DC Motors: The 4046 Circuit		£5.09
DC Motors: The Crystal Drive Circuit	E/897/5 E/897/3/4/5	£5.09 £11.50
All three DC Motors boards	E/891/3/4/5	211.00
CTI Inc. 2 1007	1. 1.	
ETI Issue 7 1997	E797/1	£13.32
Eprommer: main board (double sided)	E797/2	£13.32 £5.64
Eprommer: PSU board	LIGHZ	20.04
Eprommer: personality modules	E797/3	
(double sided): Any ONE module board	E19110	£5.09
		£5.09 £7.90
Any two modules		£11.85
Any three modules		211.00

Any four modules	£15.80
Any five modules	£19.75
All six modules	£23.70
Please specify which Epro. modules you require. Modules are for 2 27128, 27256 or 27512. One order code/overseas postal charge a selection or all six personality module boards are ordered.	2716, 2732, 2764, applies whether a

Are Your Lights On?	E/797/4	£5.09
Peak Reading VU Meter	E/797/5	£5.09

#### Terms of trade

Terms strictly payment with order. We cannot supply credit orders, but will supply a proforma invoice if requested. Proforma orders will not be processed until payment is received. All boards are manufactured from the foils that appear in the ETI Foils Pages for the appropriate issue. Please check that our foils are suitable for the component packages you intend to use before ordering as we cannot supply modified boards or replace boards that have been modified or soldered. Boards are only supplied in the listed units. Sorry, we cannot break units. Prices and stock may be altered without prior-notice. Prices and stock listed in this issue supersede prices and stock appearing in any previous issue. ET, Nexus Special Interests and their representatives shall not be liable for any loss or damage suffered howsoever arising out of or in connection with the supply of printed circuit boards or other goods or services by ETI, Nexus Special Interests or their representatives other than to supply goods or services offered or refund the purchase may money paid in respect of good not supplied.

# **Picketts Lock '97**

LARCCR **TAKE 2** 

Picketts Lock Lane Edmonton Last year London **RadioSport** N9 OAS introduced their all-new LONDON **AMATEUR RADIO & COMPUTER CHRISTMAS RALLY, a** traditionally styled event with bargains galore.

Saturday

November 15th

& Sunday

November 16th

10am - 5pm

each day

This year, by popular demand, the event is being expanded to two days.

With around 100 exhibitors, special interest groups, a huge Bring & Buy

stand disabled facilities, bars and restaurants, it's the event with something to interest every radio and computing enthusiast.

What's more, you could bring the family and leave them at the 12 screen cinema while you look around.

Venue:

Lee Valley

Leisure Centre,

As those of you who have been to Picketts Lock before know, there's something about the events which take place here that just feels good.

If you're only going to visit one rally this Christmas, make sure it's this one.

RadioSport Ltd, 126 Mount Pleasant Lane, Bricket Wood, Herts AL2 3XD TEL: 01923 893929 FAX: 01923 678770 Presented in association with Southgate Amateur Radio Club

Admission:

Adults

£2.50

Pensioners

£1.50

Under 14's

£1.50

For the latest list of exhibitors, detailed directions on how to get there, etc. visit our website www.sadiosport.co.uk

Now

By car on the A1055. Follow the signs from junction 25 of the M25. Free parking for all By public transport: bus W8 from Edmonton Green B. R. station

with the major Japanese importers!



# FOILS FOR THIS ISSUE











THE BOOK OF ELECTRONICS	<section-header>         Bit Book of Electronics         Are book is both a theoretical and practical introduction to electronics. It clearly the beginner to make. The projects are a loudspeaker divider, continuity tester, to won-our alarm, treezing alarm, loudspeaker, mini-amplifier and a burglar alarm.         Book and theoretical and practical introduction to electronics. It clearly the beginner to make. The projects are a loudspeaker, mini-amplifier and a burglar alarm.         Book and theoretical and practical introduction to electronics. It clearly the beginner to make. The projects are a loudspeaker, mini-amplifier and a burglar alarm.         Book and theoretical and practical introduction to electronics. It clearly to the beginner to make. The projects are a loudspeaker, mini-amplifier and a burglar alarm.         Book and the complex and principles of electronics and pace to thouse the preformance of scanners provides even the information to the use of MFG and UHG communication bands and gives details on how to construct accessories to alarme to prevent and the top pace to the prevent accessories for alarme to pace to scanner on the use of the four on the use of MFG and UHG communication bands and gives details on how to construct accessories to alarme to beak in the top pace to the prevent accessories for all these ID regions, including acunty-by-county-oracitants. Not alarmed to the prevent and and and gives details on how to construct accessories to alarme to beak is the top pace to the prevent accessories to alarmed to the pace to t</section-header>
DIVE BRADSHAW	Telephone orders: 01322 616300 ask for Nexus Direct:
	Please send mecopies of NB@
Expiry DateSignature	
Name	Trease send me
AddressPost code	
Telephone Number	
Complete details and return coupon to: Nexus Direct, Nexus House, Boundary Way, Hemel Hempstead, Herts, HP2 7ST, If you do not wish to receive mailing from other companies, please tick box.	or please debit my Access/Visa.

## **NEW FROM NEXUS!** An Introduction to Robotics

A fascinating and unique book that breaks new ground by exploring the exciting world of robotics in a clear and concise way. Both the theoretical and practical aspects are presented in an uncomplicated fashion using everyday English, which makes this an ideal book for the amateur. Divided into two sections, the first part explains how and why robots work and are controlled, while the second shows you how to make a simple two legged humanoid robot that can be programmed to walk. There are no complicated formulas or equations to grapple with or incomprehensible circuit diagrams to decipher, - this robot can be built on your kitchen table and can be run from any personal computer! All you need are model aeroplane servos, a controller, a power supply and some plywood - and all parts are easily available in the UK and the USA. This is a book that will be of interest to modellers and everyone with a fascination for things mechanical and electronic.

This is the way of the future, stay one step ahead and order your copy today!

Only £11.50 UK & £12.50 Overseas (Includes Postage & Packing).

Telephone orders: 01442 266551 and ask for Nexus Direct

Please send me..... copies of NB299 @.....

nclose my cheque/PO for £ made payable to Nexus Special Interests OR ease debit my Access/ Visa.	
piry date Signature Name	
ddress	
ost code Telephone No	
omplete details and return coupon to: Nexus Special Interests, Nexus House, Boundary	Way,
emel Hempstead, Herts, HP2 7ST. If you do not wish to receive mailing from other companies, please tick bo	





VISA

Tuned to the needs of the Radio Amateur

Chelmer Valve Company, 130 New London Road, Chelmsford, Essex CM2 ORG. England. Tel: 44-01245-355296/265865 Fax: 44-01245-490064

ELECTRONICS TODAY INTERNATIONAL

GRANDATA......4, 5, 6, 7

**GREENWELD ELECTRONICS** ....62



LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the mother-board, PSU and EGA video card with single 5% 1.2 Mb (flopp) disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run 1 Order as HIGRADE 286 ONLY £129.00 (E)

Optional Fitted extras: VGA graphics card 1.4Mb 3½\* floppy disk drive (instead of 1.2 Mb) Wordperfect 6.0 for Dos - when 3½\* FDD option ordered £29.00 £19.95 NE2000 Ethernet (thick, thin or twisted) network card £29.00

OW COST 486DX-33 SYSTEM Limited quantity of this 2nd user, supurb small size desktop unit. Fully leatured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5\* floppy disk drive. Fully tested and guaranteed. *Fully expandable* Many other options available - call for details. **£399.00** (E)

## FLOPPY DISK DRIVES 31/2" - 8"

#### 51/4" or 31/2" from only £18.95 !

Massive purchases of standard 5¼° and 3½° drives enables us to present prime product at industry beating low prices! All units (unless stated) are **BRAND NEW** or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3%\* supported on your PC). 3½" Panasonic JU363/4 720K or equivalent PEE

31/2" Panasonic JU363/4 720K or equivalent RFE	£24.95(B)
31/2" Mitsubishi MF355C-L. 1.4 Med. Laptops only	£25.95(B)
31/2" Mitsubishi MF355C-D, 1.4 Meg, Non laptop	£18.95(B)
5¼* Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE	£18.95(B)
51/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE	£29.95(B)
51/4" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
Table top case with integral PSU for HH 51/4" Flopp or HD	£29.95(B)
8" Shugart 800/801 8" SS refurbished & tested	£195.00(E)
8" Shugart 810 8" SS HH Brand New	£195.00(E)
8" Shugart 851 8" double sided refurbished & tested	£250.00(E)
Mitsubishi M2894-63 8" double sided NEW	£275.00(E)
Mitsubishi M2896-63-02U 8" DS slimline NEW	£285.00(E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00(E)

#### HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD Interface, replaces Fujitsu equivalent model. Full manual. Only £299.00 or 2 for £525.00 (E)

3½" FUJI FK-309-26 20mb MFM I/F RFE	£59.95(C)
31/2" CONNER CP3024 20 mb IDE I/F (or equiv )RFE	£59.95(C)
31/2" CONNER CP3044 40mb IDE I/F (or equiv.)RFE	£69.00(C)
3½" RODIME RO3057S 45mb SCSI I/F (Mac & Acorn)	£69.00(C)
31/2" WESTERN DIGITAL 850mb IDE I/F Brand New	£185.00(C)
51/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE	£49.95(C)
51/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95(C)
5¼" CDC 94205-51 40mb HH MFM I/F RFE tested	£69.95(C)
51/4" HP 9754B 850 Mb SCSI RFE tested	£89.00(C)
5¼" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00(C)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00(E)

Hard disc controllers for MFM , IDE, SCSI, RLL etc. from £16.95

#### THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TVII



The TELEBOX is an altractive fully cased mains powered unit, con-taining all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANVO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug direcity into most video recorders, allowing reception of TV channels not normally receivable on most televi-sion receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 luty tuneable 'off air' UHF colour television recare to a flug tuneable 'off air' UHF colour television recentres. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors with audio output are provided as standard. TELEBOX ST for composite video input type monitors tor overseas PAL versions state 5.5 or 6 mHz sound specification. "For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Teleboxe's is (B) The TELEBOX is an attractive fully cased mains powered unit,

#### **DC POWER SUPPLIES**

Virtually every type of power supply you can imagine.Over 10,000 Power Supplies Ex Stock Call for info / list.

VISA





Mitsubishi FA3415ETKL 14" SVGA Mutlisync colour monitor with fine 0.28 dot prich tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of comput-ers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-LENT little used condition.

Only £119 (E) Order as Tilt & Swivel Base \$475 VGA cable for IBM PC included.

External cables for other types of computers CALL

As New - Used on film set for 1 week only!! 15" 0.28 SVGA 1024 x 768 res. colour monitors. Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for Info

Good SH condition - from £299 - CALL for into PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 Khz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed Dimensions: W14" x H12%" x 15½" D. Only £95 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with stan-dard composite 15.625 Khz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attrac-tive square black plastic case measuring W10" x H10" x 13%" D. 240 V AC mains powered. Only £79.00 (D) Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot KME 10° 15M10009 high definition colour monito pitch. Superb claritly and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorr Archimedes & BBC. Measures only 13½\* x 12° x 11° Good used condition

11". Good used condition. Only £125 (E)

#### 20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors complete with composite video & *optional* sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc.In EXCELLENT little used condition with full 90 day guarantee. Clubs, etc.In





#### Surplus always wanted for cash!

#### 19" RACK CABINETS Superb quality 6 foot 40U

Virtually New, Ultra Smart Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully and lowered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stack side by side and therefore

require only two side panels to stand singly or in multiple bays Overall dimensions are: 77½" H x 32½" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels. £335.00 (G) OPT Rack 2 Rack, Less side panels £225.00 (G)

#### 32U - High Quality - All steel RakCab

**32U - High Quality - All steel RakCab** Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with its socures 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struits (extras available) are pre punched for standard cage nuts'. A mains distribution panel internal-ly mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for rable (competor access etc. Swinglied in excellent silothy used



castors and floor levelers, prepuncted utility panel at lower rear for cable / connector access etc. Supplied in **excellent**, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 234" W)

Sold at LESS than a third of makers price !!

#### A superb buy at only £195.00 (G) Over 1000 racks - 19" 22" & 24" wide 3 to 44 U high. Available from stock !! Call with your requirements.

#### TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts MicroTouch - but sold at a price below cost II System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a linger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct con-nection to a PC for a myriad of applications including: control pan-els, pointing devices, POS systems, controllers for the disabled or computer un-trained etc etc. Imagine using your tinger with 'Windows', instead of a mouse !! (a driver is indeed available !) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an Incredible price of only: *Full MICROTOUCH software support pack* and manuals for IBM compatible PC's £9.95 RFE-Tested MicroTouch - but sold at a price below cost II System consists of

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. E59.95(A1) Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data. Order as: XT RAM UG, 256K, £34.95 or 512k £39.95 (A1)

SIMM SPECIALS					
1 MB x 9 SIMM 9 chip 120ns		16.50 (A1)			
1 MB x 9 SIMM 3 chip 80 ns £19.50		22.95 (A1)			
1 MB x 9 SIMM 9 chip 80 ns £21.50	or 70ns £				
4 MB 70 ns 72 pin SIMM -with parity-	Only £	95.00 (A1)			
INTEL 486-DX33 CPU £55.00 INTEL 486-DX66 CPU £69.00 (A1)					
FULL RANGE OF CO-PROCESSOR'S E	K STOCK - CAL	L FOR ÉEE			

#### FANS & BLOWERS

£7.95 10 / £65 EPSON DO412 40x40x20 mm 12v DC PAPST TYPE 612 60x60x25 mm 12v DC PAPST TYPE 612 60x60x25 mm 12v DC MITSUBISHI MMF-D6012DL 60x60x25 mm 12v DC MITSUBISHI MMF-06812DM 92x92x25 mm 12v DC MITSUBISHI MMF-09B12DH 92x92x25 mm 12v DC £8 95 10 / £75 £8.95 10 / £75 £4.95 10 / £42 £5.25 10 / £49 £5.95 10 / £53 £7.95 10 / £69 PANCAKE 12-3.5 92x92x18 mm 12v DC £7.95 10 / £6 EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm specify 110 or 240 v £6.95. 80 x 80 x 38 mm - specify 110 or 240 v £5.95 IMHOF B26 1900 rack mnt 3U x 19' Blower 110/240v NEW £7.9.95

£79.95 Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL



All prices for UK Mainland, UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10, Bona Fide account orders accepted from Government, Schools Universities and Local Authonities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (E)=£18.00, (G)=£18.00, 25 YEARS





FOR SALE

Boundary Way, Hemel Hempstead, HP2 7ST Lineage: 85p per word (+VAT) (minimum 20 words) Semi display: (minimum 3cms) £12.50 + VAT per single column centimetre Ring for information on series bookings/discounts All advertisements in this section must be pre-paid.

ETI Classified Department, Nexus, Nexus House,

01442 66551 Send your requirements to:

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).



To Advertise in the next issue of ETI phone our friendly sales team on: 01442 66551

or fax your advert to us on: 01442 66998



18 Victoria St, Queensbury, BRADFORD, BD13 1AR Tel 01274 816200 Email veronica@legend.co.uk



#### £50 BT INSTRUMENT FOR ONLY £7.50

We refer to the BT insulation tester and multi-meter with which you can read insulation directly in megahns, AC volts up to 230, 4 ranges of DC volts up to 500, 3 ranges of milliamus and one 54 range and 3 ranges of resistance. These are in particle condition, have had very little use, if any, tested and fully guaranteed. Complete with leads and prods \$7.50, Order Ref 7.594. Carrying case which will take small leads as well, 52 extra. Pastage £3 unless your order is £25 and over. J & N Factors Dept ETI, Pilgrim Works, Starkridge Lune, Bolney, Sessex, RH17 5PA Telephone: (01444) 881965











VISA

Ample Parking Sp





For more information and rates contact: Wise Owl Worldwide Publications 4314 West 238th Street, Torrance, CA 90505 4509 Tel: (310) 375 6258

alking of chucking old computers in skips - this is no longer the politically correct thing to do, now that the European Commission is close to publishing a draft directive on ways to recycle Europe's rocketing quantities of waste electrical and electronic equipment (WEEE for short).

**Around the** 

Jorner

You may profoundly wish to hear that your younger brother/sister/offspring's double-audio-power-blast CD-rom multimedia games PC is on its way to a landfill somewhere, but this won't be on the cards for much longer. It's more likely that the new waste directive will eat it up and spit it out as a refurbished, recycled, lowercost, not-so-neat but just-as-loud games PC - two for the price of one! Whoopeee!

More seriously, there has been concern for some time about the future pollution potential of the increasingly large quantities of plastics, batteries, electronic components and solder and other heavy metal products being discarded as they fall out of use. Behind this concern is the wider one of waste disposal as a whole. Currently only a few materials (such as aluminium, a genuinely valuable recycling product) can be recycled with real cost-effectiveness, but landfills and other waste sites are filling up ever-faster, and local waste collection services in the UK are more and more strained. (Some people blame it on Wheelie bins tempting us to throw more in them, and others on Government spending cuts tendering out refuse collection to the lowest bidder.) And looking at the longer term, recycling is a habit that it would be good for all of us to get into, even though common materials like glass and paper are borderline in cost terms at the moment.

Once retrieval and recycling of used-up electronics becomes general, someone will have to pay for it, and it is expected that various parts of the electronics industry will pay a levy towards recycling, or arrange recycling themselves.

Already as we saw in the news pages of this issue of ETI, and the previous one, organisations with a track record in recycling electronics, or running pilot schemes, are on the move all over the UK. This will no doubt be a growth area for a while.

Some waste managers are inclined towards dismantling, separating materials and recycling as salvage, and some towards refurbishing and moving equipment (especially computers) into the second-user market, depending how viable they are. Properly organised, businesses updating quantities of equipment should be able to get a reasonable price for their old machines, while others will have to pay to get their junk removed.

Already businesses with rechargeable batteries to discard are expected to pay for removal, usually without even the option of delivering the waste themselves to collection points. It is high time the controlled collection of used batteries containing cadmium or lead was made easy, and mandatory, for everyone, including households.

As far as genuine "recycling" goes, talking to electronics constructors is preaching to the converted. Computer out of date? Cannibalise some parts, swap something with something else, add a couple of cards (wrestling with the compatibility problems - but so do people buying all-new systems) and an upgraded hard disk, and you have a new computer, with not a lot left over but a handful of screws and tags and a superannuated disk module which a mate somewhere could probably use. Dead mobile phone? There should be a card for it ... Walkman? Fit a new motor and give it to the kids. Radio? No-one ever gives up on a radio. TV? Fred's experimenting with one of those whole-wall display drivers in his garage ... and then there's the spare parts box.

It look as though industry will soon be doing all this on a Europe-wide scale.

#### Next Month...

Volume 26 no. 12 of Electronics Today International will be in your newsagent on 7thth November 1997 ... Mike Bedford will be looking at new electronic products that can stand tough treatment ... Ray Haigh has designed a dedicated classic medium wave receiver with high-sensitivity and reception to please the discerning ear ... Robert Penfold has been working on an Infra-red remote controller ... all the regulars, and more.

Contents are in preparation but are subject to space and availability.



Published by Nexus Special Interests Limited Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST Tel: 01442 266551 Fax: 01442 266998

#### EDITORIAL

Editor Helen Armstrong Administration Assistant

**Beverley Walden** Consultant Andrew Armstrong

PRODUCTION

#### Designer Mark Dodgson

Technical Illustrator John Puczynski

**Production Executive** (Copy control) Marie Quilter

Printed By Wiltshire Ltd., Bristol **Origination** by

Ebony, Liskeard

#### SALES

Advertisement Manager Alison Weatherill 01442 266551x322

Group Sales Manager Jason Wollington

#### MANAGEMENT

Divisional Managing Director John Bridges

**Business Manager** Stuart Cooke

Senior Editor David Watkins

**Circulation Manager** William Pearson

Marketing Manager Jason Doran

Copy Sales Manager David Pagendam

#### SUBSCRIPTIONS

UK:Orders 01858 435344 Enquiries 01858 435322 USA: Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. For VISA/Mastercard orders phone: (310) 375 6258. Fax: (310) 375 0548, Pacific Time: 9am - 9pm weekdays 10am - 6pm weekends. Visa/MC/Discover accepted.

#### **READERS SERVICES**

READERS SERVICES Back issues(last 12 months) £3.20 per issue if available. Older issues: photocopies of older articles often available. Write to The Photocopy Service, Readers Services Department, at Nexus House. Boundary Way, Hemel Hempstead, Herts HP2 75T. Binders for ETI: £7.50 each including UK post and packing. Overseas please add £1.50. Cheques to Nexus Special Interest at Nexus House, or phone VISA/Mastercard orders to Readers Services Department 01442 266551



© Nexus Special Interests Limited 1997 All rights reserve ISSN 0142-7229

The Publisher's written consent must be obtained before any part of this publication may be reproduced in any form whatsoever, including photocopiers, and information retrieval systems, While reasonable care is taken in preparation of magazine contents, the publishers, editors and their agents cannot be held legally responsible for loss howsoever arising from errors or other published material.

## MIGRO-PRO The Ultimate 8051 Microcontroller Programmer

Supports Atmel FLASH 89C +895, Generic 87C51/52/FA/ FB/FC microcontroller derivatives FLASH & E2 libraries also £149.00 Order Code: MPW-SYS available as chargeable update

Code Size : Bla

Start End :



The above software is now available with all our programmers featured in this ad

## Profession /ABm Starter Syste

#### **Features:**

Supports programming of Atmel 90S(AVR) microcontroller families

Supports both Paral el and Serial programming modes

**Comes complete with:** 

Serial program ing cable, AT90S1200 microcontroller, assembler, Co ROM Databook, Parally able and Power supply

£59.95 Order Code: AVR-ST

MICRO-ISP

## Serial Programming System "Now you can program the 8051



£39.95 Order Code: UISP-V2-SYS

without removing the device from the socket!"

#### **B95 Socket Stealer Module**

Simply plug this into your existing 8051 or AVR socket for INSTANT In-System Programming NO £49.00 Order Code: SS-895-DIL40 Target System redesign required.



GD Technik +44 1734 342277, Rapid Electronics +44 1206 Farnell Components +44 1132 790101 INOX DISTRIBUTORS: BELGIUM Alcom Electronics Nv/sa +32 3 458 30 33 751166, Quarndon Electronics +44 1332 332651 FRANCE Newtek +33 1 4687 2200 GERMANY Ineltek GmbH +49 7321 93850, MSC Vertriebs GmbH +49 08 9945532 12 GREECE Micrelec +30 1 5395042 4 ITALY Grifo Italian Technology +39 51 89 20 52, Newtek Italia +39 2 33 10 53 08 NETHERLANDS Alcom Electronics BV +31 10 4519533, NORWAY ACTE NC Norway +47 63898900, Jakob Hatteland Electronic Anatronic +35 119 371 834 SPAIN Anatronic SA +34 1 366 01 59 SWITZERLAND Anatec Ag +41 41 748 32 41 USA Hitools Inc +1 408 298 9077, Peachtree Technology +1 770 888 4002

Equinox reserves the right to change prices & specifications of any of the above products without prior notice. E&OE. All prices are exclusive of VAT & carriage AVR<sup>TM</sup> is a trademark of the Atmel Corporation

The Embedded Solutions Company

# )]]/[[ SOLUTIONS R

For product information visit our web site at: www.equinox-tech.com E-mail: sales@equinox-tech.com 229 Greenmount Lane Bolton BL1 5JB UK



A comprehensive range of 51 Starter & Development Systems are also available

## STILL THE WORLD'S MOST POWERFUL PORTABLE

## PROGRAMMERS?

NEW MODEL

Dataman

......

SURELY NOT.

INTELLIGENT UNIVERSAL PROGRAMMER

SURELY SOMEONE SOMEWHERE HAS DEVELOPED A PORTABLE PROGRAMMER THAT HAS EVEN MORE FEATURES, EVEN GREATER FLEXIBILITY AND IS EVEN

ACTUALLY, NO. BUT DON'T TAKE OUR

MANUFACTURERS' PRODUCTS COMPARE.

WORD FOR IT. USE THE FEATURE SUMMARY BELOW TO SEE HOW OTHER

BETTER VALUE FOR MONEY.

DATAMAN-48LV

£495+VAT

(F

- Plugs straight into parallel port of PC or laptop
- Programs and verifies at 2, 2.7, 3.3 & 5V
- True no-adaptor programming up to 48 pin DIL devices
- Free universal 44 pin PLCC adaptor
- Built-in world standard PSU for goanywhere programming
- Package adaptors available for TSOP, PSOP, QFP, SOIC and PLCC
- Optional EPROM emulator

### DATAMAN S4

- Programs 8 and 16 bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 microcontrollers and more
- EPROM emulation as standard
- Rechargeable battery power for total portability
- All-in-one price includes emulation leads, AC charger, PC software, spare library ROM, user-friendly manual
- Supplied fully charged and ready to use

## S4 GAL MODULE

- Programs wide range of 20 and 24 pin logic devices from the major GAL vendo s
- Supports JEDEC files from all popular compilers

### SUPPORT

- 3 year parts and labour guarantee
- Windows/DOS software included
- Free technical support for life
- Next day delivery always in stock
- Dedicated UK supplier, established 1978

**Still as unbeatable as ever.** Beware of cheap imitations. Beware of false promises. Beware of hidden extras. If you want the best, there's still only one choice - Dataman.

Order via credit card hotline - phone today, use tomorrow.

Alternatively, request more detailed information on these and other market-leading programming solutions.

### MONEY-BACK 30 DAY TRIAL

1000

Brut Cots aprils

£795+VAT

If you do not agree that these truly are the most powerful portable programmers you can buy, simply return your Dataman product within 30 days for a full refund



Orders received by 4pm will normally be despatched same day. Order today, get it tomorrow!



Dataman Programmers Ltd, Station Rd, Maiden Newton, Dorchester, Dorset, DT2 0AE, UK Telephone +44/0 1300 320719 Fax +44/0 1300 321012 BBS +44/0 1300 321095 (24hr) Modem V.34/V.FC/V.32bis Home page: http://www.dataman.com FTP: ftp.dataman.com Email: sales@dataman.com