



## VHF INTERFERENCE FILTER

For High-Band Receiving Antennas  
- Keep Radio-Pager Signals Out

## THREE RANGE INDUCTANCE METER

Measures high value audio filters down to many of the small chokes

## BB RANGER

An Electronic Self Scoring Target For Lightweight Pellet Guns

# UNDERSTANDING ROBOTS

Every Second Counts For The Mechanical Manipulators

## PLUS

- GCSE Sound Effect Module
- LED Battery Check
- Spiced Circuits: Logic Simulation and Maths






# Contents

Volume 27 No.4

## & Features & Projects

Next Issue 24th April 1998

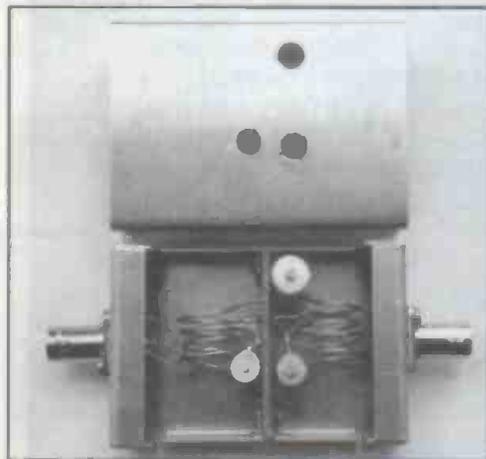

## Regulars

News	4,5,7
ETI PCB Service	67
PCB foils	66, 68, 69
Round the Corner	74

**Understanding Robots** 8  
Harprit Sandhu introduces the expanding family of "programmable general purpose manipulators" and the mechanisms and control loops that make them function.

**Three-Range Inductance Meter** 19  
To partner last month's Capacitance Meter, Robert Penfold's Inductance Meter has three ranges of full-scale value 1mH, 10mH, and 100mH.

**Radio Interference Filter for VHF** 24  
Strong legal transmissions, particularly the ever-expanding range of radio-paging signals, can swamp VHF reception. E Chicken MBE's filter is designed to reduce swamping and clear reception.

**LED Voltmeter for 12V battery check** 29  
Twelve-volt lead-acid "leisure" batteries are designed to run down significantly before re-charging. Terry Balbirnie's four-LED battery checker indicates the charge state.

**BB Ranger** 35  
The Ranger is an eeprom-driven electronic score-board for a BB pellet-gun shooting range. A specially-built set of fall-down targets enable an instant readout of the accumulated score.

**GCSE Grounding: Sound Effects Module** 46  
Terry Balbirnie continues his circuits for GCSE students. In this issue: a six-sound effect module which can be adapted.

**The Orphan Decibel** 51  
The Decibel is an unusual unit of measurement - it describes a thing not by what it is, but by what it does. E.Chicken MBE FIEE describes how to calculate power with decibels.

**Spiced Circuits: Logic Simulation and Maths** 56  
In the last of Owen Bishop's series on Spice-based circuit simulation, he looks at logic simulation, including B2Logic V3.0

**Digital Tic Tac Toe** 60  
An electronic game of Noughts and Crosses which allows you to play against a PIC 16C64 microcontroller. By Rose and Andy Morell.

**Line-Up Oscillator With Glitch** 63  
When you are sending an audio signal to a remote destination, it is necessary to know which stereo channel you are monitoring. Tony Sercombe's glitch will tell you.

**Review: Peak DCA50 Component Analyser** 73  
An advanced new meter for the identification of component types, pin-outs and functions.

  
SUBSCRIPTIONS  
& BACK ISSUES HOTLINES:  
01858 435344  
ORDERS  
& ENQUIRIES:  
01858 435322  
Lines Open 9am - 6.30pm

**Subscribe & Save**  
Phone the hotline and take advantage of our special offer detailed on page 45

## Advanced IBM Disk Technology Loads More Than Before

"Giant Magnetoresistive (GMR)" disk drive heads, pioneered by IBM Research scientists, are the essential component behind the world's highest capacity desktop PC disk drives. The IBM Deskstar 16GP is a 16.8-gigabyte drive capable of holding eight times more information than today's average desktop hard drive. The 16GP can hold eight hours of full-motion video (MPEG-2 quality video), or, according to IBM, sufficient information to fill more than 16 pick-up trucks if printed out as hardcopy (presumably on USA standard 11 x 8.5-in paper stock).

A pickup truck is a traditional North American lightweight open-backed flatbed van with low sidings. Goods and passengers are either stacked loose or lashed in place, usually accompanied by a dog. Not generally robust enough for full commercial loading, pickups are widely used for local deliveries, general agricultural transport and riding around. Loading capacity (depending on age and condition, and taking into account the low compressibility of paper) may be approximately compared to one "transit" van, half a Luton box van, or a reasonable fraction of a corporation dustcart.

For large companies like IBM, mass storage of this kind once promised the "paperless office", but the comparatively slow spread of electronic documentation, and paper hardcopy's flexibility and freedom from compatibility problems, has tended to increase the amount of paper in circulation, rather than decrease it. In the future, mass storage by removable hard disk may help to reduce the physical need for filing space.

The GMR disk head is no bigger than the head of a pin and is the world's most sensitive sensor for reading data on



hard disks. According to IBM, the massive storage capabilities of the Deskstar 16GP allow television-like sound and picture-quality multimedia programs on a suitable computer.

GMR technology expects to be able to provide storage of more than 10 million bits per square inch on the disk platter by 2001.

The Deskstar range has 10 disk capacities to choose from. For high performance as opposed to maximum capacity, The Deskstar 14GXP family has a choice of three different capacities from 10 gigabytes to 14.4 gigabytes running at 7200 revs per minute. The 5400 RPM 16GP drive family has seven capacities from 3.2 to 16.8 GB.

For more information see IBM Storage Systems Division's web page: [www.ibm.com/storage](http://www.ibm.com/storage), Dept. Star 30, or contact IBM UK Ltd., South Bank 76 Upper Ground, London SE1 9PZ, UK. Tel 0171 202 3744, fax 1071 202 3792.

## BULL ELECTRICAL'S EMPORIUM

SOLAR PANELS  
RADIO CONTROL  
WIND GENERATORS  
ROCKETS  
HYDROPONICS  
WORMS  
BAGS  
NIGHTSIGHTS  
KITS  
ELECTRONICS  
MAGNETS



ESTABLISHED FOR  
MORE THAN 50 YEARS

## New Bulls On The Loose!

Bull Electrical's latest catalogue is now out. It features remote control systems, telescopes and microscopes, batteries and battery chargers, surveillance bugs and camera accessories, video cameras, solar panels and a complete wormery with 1000 worms to convert kitchen waste into organic compost.

Bull have also started a new catalogue concentrating on the scientific hobby of hydroponic gardening. The catalogue includes nutrients, heaters, pumps, lighting, accessories and how-to books. An ideal way to utilise the rich organic nutrients from your wormery!

For more information and copies of their catalogue, contact Bull Electrical, 250 Portland Road, Hove, Sussex BN3 5QT, UK. Tel. 01273 203500, fax 01273 323077.

## BULL Hydroponics Catalogue

NUTRIENTS  
NFT SYSTEMS  
HEATERS  
PUMPS  
FITTINGS  
BOOKS  
LIGHTS



ESTABLISHED FOR  
MORE THAN 50 YEARS IN MAIL ORDER

## All Micro Show at Bingley Hall in April

The SAMS'98 Spring All Micro Show will take place on Saturday 18th April at Bingley Hall, Staffordshire Showground, Weston Road, Stafford. The show will be open from 10am to 4pm, with plenty of free parking. Entrance is £3.00 for adults, 50p for children under 14, £2.00 for concessions: OAPs, RSGB members, student cards, UB40. Advance tickets are also £2.00 plus a stamped, self-addressed envelope.

The Showground is on the A518 Stafford-Uttoxeter Road, signposted from junction 14 on the M6. There is a bus shuttle from Stafford railway station.

This is the 10th consecutive year of the All Micro Show at Bingley Hall. Last year saw 3,000 people and 100 trade stands covering all formats computing, including PC, Sinclair, Einstein, Amiga, Atari St and Atari 8-bit computing supported by various user groups, along with stands selling accessories, software, books, components, shareware, media, hardware, radio, satellite and a big Electronics Bring and Buy Stall. There are refreshments, a cafeteria and a licensed bar from 11 am.

There will be another All Micro Show in Bingley Hall on November 14th.

For further details, advance tickets etc. contact Sharon Alward at Sharward Promotions, Knightsdale Business Centre, 30 Knightsdale Road, Ipswich, Suffolk IP1 4JJ. Tel 01473 741533, fax 01473 741361. Email: [services@sharward.co.uk](mailto:services@sharward.co.uk)

## Electronic Recycling Guidelines from Industry Council


ICER - the Industry Council for Electronic Equipment Recycling - has set up a Recycling Directory for use in industries looking for serious suggestions about what to do with unwanted electronic equipment.

The directory lists some 30 UK companies which specialise in recycling different kinds of electronic and electrical equipment, ordered by category of equipment and the recyclers who handle it, as well as an alphabetic list of recyclers giving more information about the companies. A website giving access to the directory is also planned.

Anticipating that an EU directive will eventually require that recycling is carried out by "approved recyclers", ICER has produced a summary of "best practice", "for defining the criteria for approved recyclers", according to Gary Griffiths of R Frazier, who chairs the ICER recycling group. This includes points such as:

"A recycler will need to: show the company has appropriate licences or exemption certificates for all sites in accordance with waste regulations, and uses waste transfer notes and authorised transport operations", and "..." classify any waste from processes (eg Controlled Waste, Special Waste) and dispose of it properly."

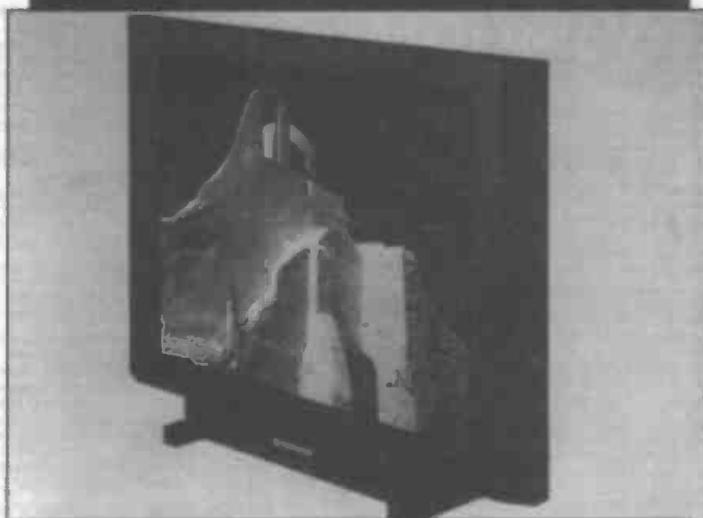An ICER publication, *ICER Guidelines: Design for Recycling Electronics and Electrical Equipment* is available, price £20 plus postage and packing (depending on destination) from Pam Gibson, ICER, 6 Bath Place, Rivington Street, London, EC2A 3JE. Tel 0171 457 5038.



## New Plasma Screen Technology Ready to Hang on the Wall

Pioneer's new television monitors are using new plasma technology that allows them to be slimmed down to just 9 cm (88mm, in fact) deep.

The immediate result of this ultra-slim profile is likely to be more "Public Information Screens" in public places. The plasma screens are thin enough to be hung on the wall like a picture, making them useful in areas normally too small or inaccessible for normal screens. For example, all the lifts at major airports could be fitted with plasma screens giving the latest departure, arrival and check-in information.

Pioneer's innovative 40-in colour plasma display screens can be linked to video, PC CD-rom, a normal television tuner, even DVD, making them a versatile choice for conference organisers and marketing organisations.

In due course the plasma screens are expected to cross over into homes for use with a TV tuner, to hang on the wall or sit on slimline stands, far less bulky than current TV tubes. The plasma screens' high brightness (400 candela per square meter - the highest level in the world) and a 160-degree vertical and horizontal viewing angle ensure that the screen is a screen that's seen - a flat, non-glare surface makes the screens suitable for bright environments (no more need to turn all the room lights down to cut off the glare and screen washout), while their long lifespan (20,000 hours) and optional rain-proof housing making them durable enough for indoor or outdoor use.

The base-model screens are available from April 1998 and have built-in compatibility with TV tuners, amplifiers, SPs, external CPUs and DVD players, and are compatible with PAL, NTSC and VGA video standards.

For more information, contact Kate Moir or Julia Savage, Storm Communications (Pioneer Multimedia Press Office) tel. 01494 670444. Email: [stormcomm@compuserve.com](mailto:stormcomm@compuserve.com)

Surplus always wanted for cash!

# THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

## LOW COST PC's

### SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram



Industrial grade 12MHz HI GRADE 286 systems Made In The USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard. 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!

Order as HIGRADE 286 **ONLY £99.00** (E)

Optional Fitted extras: VGA graphics card £29.00  
1.44Mb 3 1/2" floppy disk drive (instead of 1.2 Mb) £19.95  
Wordperfect 6.0 for Dos - when 3 1/2" FDD option ordered £12.50  
NE2000 Ethernet (thick, thin or twisted) network card £29.00

## INTEL 486DX-33 SYSTEMS

Limited quantity of this 2nd year, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable.

Only **£199.00** (E)

## FLOPPY DISK DRIVES 3 1/2" - 8"

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call for over 2000 unlisted drives for spares or repair.

- 3 1/2" Panasonic JU3634 720K or equivalent RFE £24.95(B)
- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GFR 1.2 Meg (for IBM PCs) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for MH 5 1/4" Flopp or HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS HH Brand New £195.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

## HARD DISK DRIVES

- 2 1/2" TOSHIBA (19 mm H) MK2101MAN 2.16 Gb. New £199.00
  - 2 1/2" TOSH (12.5 mm H) MK1002MAV 1.1 Gb laptop. New £115.00
  - 2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £15.95
  - 3 1/2" FUJII FK-309-28 20mb MFM VF RFE £59.95
  - 3 1/2" CONNER CP3024 20 mb IDE VF (or equiv.) RFE £59.95
  - 3 1/2" CONNER CP3044 40mb IDE VF (or equiv.) RFE £69.00
  - 3 1/2" RODIME R303057S 45mb SCSI VF (Mac & Acorn) £69.00
  - 3 1/2" QUANTUM 40S Prodrive 42mb SCSI VF, New RFE £49.00
  - 3 1/2" WESTERN DIGITAL 850mb IDE VF New £185.00
  - 5 1/4" MINISCRIBE 3425 20mb MFM VF (or equiv.) RFE £49.95
  - 5 1/4" SEAGATE ST-238R 30 mb RLL VF Refurb. £69.95
  - 5 1/4" CDC 94205-51 40mb HH MFM VF RFE tested £69.95
  - 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
  - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
  - 8" NEC D2245 85 Mb SMD interface. New £199.00
  - 8" FUJITSU M2322K 160Mb SMD VF RFE tested £195.00
  - 8" FUJITSU M2392K 2 Gb SMD VF RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (D)

## THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!



TV SOUND & VIDEO TUNER  
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

- TELEBOX ST for composite video input type monitors £36.95
  - TELEBOX STL as ST but fitted with integral speaker £39.50
  - TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
- For overseas PAL versions state 5.5 or 6 MHz sound specification. \*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

## DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock. Call for info / list.

## IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK  
6,000,000 Items EX STOCK  
For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

## VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -  
At this price - Don't miss it!!

Mitsubishi FAM15ETKL 14" SVGA Multisync colour monitor with the 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes. BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched bezel, text switching and LOW RADIATION MPPR specification. Fully guaranteed, supplied in EXCELLENT like used condition.

TB & Serial Base £475 **Only £119** (E) Order as MITS-SVGA  
VGA cable for IBM PC included.  
External cables for other types of computer CALL.

As New - Ex Demo  
17" 0.28 SVGA Mitsubishi Diamond Pro monitors  
Full multisync etc. Full 90 day guarantee. £325.00 (E)

Just in - Microvitec 20" VGA (800 x 600 res.) colour monitors.  
Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed.  
Dimensions: W14" x H12 1/2" x 15 1/4" D.  
**Only £99** (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, as-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.  
**Only £79.00** (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.  
**Only £125** (E)


## 20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive sleek style case. Perfect for Schools, Shops, Disco, Clubs, etc. in EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)
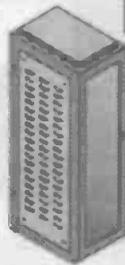
## SPECIAL INTEREST ITEMS

- MITS. J. FA3445ETKL 14" Industrial spec SVGA monitors £245
- 11kW to 400 kW - 400 Hz 3 phase power source - ex stock EPOA
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM 53P5501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8226-23-5060N £95
- AIM 501 Low distortion Oscillator 0Hz to 330KHz, IEEE £550
- Trend DSA 274 Data Analyser with G703(2M) 64 I/O EPOA
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £6500
- HP1650B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector EPOA
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP8264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set EPOA
- HP7880A A1 8 pan HPGL high speed drum plotter £1850
- F&B Wardrobe case, insurance spec 1 hour rated fire safe £650
- Edo-G Brookdale 8953CS Precision lock in amp VEG Eng. Mod 1200 computerised inspection system £650
- Sony DRG-3000A High quality CCD colour TV camera CSZ VERY Large 3 cavity thermal shock chamber EPOA
- Phillips PW1730/10 XRAY generator with accessories EPOA
- Kelthley 590 CV capacitor / voltage analyser EPOA
- Racal ICR40 dual 40 channel video recorder system £3750
- Flakers 45KV4 3 ph On Line UPS - New batteries £9500
- ICI R5030UH34 Cleanline ultrasonic cleaning system EPOA
- Mann Tally MT645 High speed line printer £2200
- Intel 58C 486/133SE Multibus 486 system. RAM Rom £945
- Intel SBC 486/125C08 Enhanced Multibus (MSA) NEW £1450
- Zeta 3220-05 A0 4 pan HPGL fast drum plotters £1150
- Nikon HFX-11 (Epiphot) exposure control unit £1450
- Motorola VME Bus Boards & Components List. SAE / CALL EPOA
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM bend printer £1950
- Fujitsu M3041D 600 LPM printer with network interface £1250
- Pertin Elmer 2998 infrared spectrophotometer £500
- Pertin Elmer 597 infrared spectrophotometer £3500
- VG Electronics 1035 TELETEXT Decoding Margin Meter £3750
- LightBand 60 output high spec 2u rack mount Video VDA's £495
- Sekonic SD 150H 18 channel digital hybrid chart recorder £1995
- Taylor Hobson Tallysurf amplifier / recorder £750
- System Video 1152 PAL waveform monitor £485
- Siemens K4400 84Kb to 140Mb demux analyser £2950



## 19" RACK CABINETS

Superb quality 6 foot 40U  
Virtually New, Ultra Smart  
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

- OPT Rack 1 Complete with removable side panels. £345.00 (G)
- OPT Rack 2 Rack, Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories  
19" 22" & 24" wide 3 to 46 U high.  
Available from stock !!

## 32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure B lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm-1625H x 835D x 803 W ( 64" H x 25" D x 23 1/4" W)  
Sold at LESS than a third of makers price !!



A superb buy at only **£245.00** (G)  
42U version of the above only £345 - CALL

## BATTERY SCOOP - 50% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SB515 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS4290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each!  
**Our Price £35 each (C) or 4 for £99 (D)**

## RELAYS - 200,000 FROM STOCK

Save £££'s by choosing your next relay from our massive stocks covering types such as - Military, Octal, Cradle, Hermetically Sealed, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting, CALL US WITH YOUR NEEDS. Many obsolete types from stock. Save £££'s

## LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (288 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95  
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.  
Order as: XT RAM UQ. 256k. £34.95 or 512k £39.95

## SIMM SPECIALS

- 1 MB x 9 SIMM 9 chip 120ns Only £8.50
  - 1 MB x 9 SIMM 3 chip 60 ns £10.50 or 70ns £11.95
  - 1 MB x 8 SIMM 9 chip 80 ns £10.50 or 70ns £11.75
  - 4 MB 70 ns 72 pin SIMM - with parity - Only £35.00
  - INTEL 486-DX33 CPU £19.95 INTEL 486-DX66 CPU £59.00
  - FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR LIST
  - MOTOROLA 25 Mhz 68040 (XC68040RC25M) CPU'S £59.00
- shipping charges for RAM / CPU upgrades is code B

## SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged.  
Special Price ONLY £99.00  
Microsoft - Windows for Workgroups 3.11 & DOS 6.22. Supplied on 3 1/2" disks with license & documentation documentation. £39.95  
DOS 5.0 on 3 1/2" disks with concise books c/w 0Basic. £14.95  
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95  
shipping charges for software is code B

Visit our London shop for a full range of Test Equipment and other bargains

DISPLAY  
-ELECTRONICS-

ALL MAIL & OFFICES  
Open Mon - Fri 9.00 - 5.30  
Dept ET1, 32 Bllgyn Way  
Upper Norwood  
LONDON SE19 3XF

LONDON SHOP  
Open Mon - Sat 9.00 - 5.30  
215 Whitehorse Lane  
South Norwood  
On 66A Bus Route  
R. Thornton Health & Salford Park SR Rail Stations

NEW DISTEL ©  
Visit our web site  
www.distel.co.uk  
email admin@distel.co.uk

ALL ENQUIRIES  
**0181 679 4414**  
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bonus Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)-£3.00, (AT)-£4.00, (B)-£5.50, (C)-£8.50, (D)-£12.00, (E)-£15.00, (F)-£18.00, (G)-CALL. Allow approx 6 days for shipping - better CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All quantities on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. TOP CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1997. E & O.E. 018



## Construction Toolkits Get A Free Upgrade

The new versions of the Minicraft 12-volt kits now come with extra power and accessories. The Hobby Kit (MB 1000), designed for the beginner, now has a more powerful



30-watt motor and heavy duty single-speed MB714 transformer. The list price is £44.99. The Precision Drill Kit (MB5001) is designed for the person with system-expansion in mind, and also has a more powerful 30-watt motor. The list price is £68.99. The High Precision Drill Kit (MB8571) is designed for the serious enthusiast and is upgraded with 40 accessories instead of 15. The list price is £84.99. Particularly recommended for Minicraft's lathe attachment (MB850).

The new features have been added to the kits at no extra cost. All kits come in a useful plastic carrying case.

For more information, catalogue or list of stockists, call Minicraft on 07000 646427238.

## Adaptable 8-Output Metrabyte KPCMCI-8AO Cards from Keithley

Keithley Instruments has released a Metrabyte KPCMCI-8AO 12-bit analogue output PCMCI card for use with notebook and PCMCI-equipped PCs. The KPCMCI-8AO is "uniquely capable" of updating eight independent bipolar or unipolar outputs simultaneously at 100kHz. Because the card has an onboard event timer that permits it to interrupt a PC's CPU at software-programmable intervals, it can generate waveform-quality outputs. In addition, the card offers eight channels of TTL-compatible digital I/O.

The Metrabyte card is available in two versions: the KPCMCI-8AOU with eight unipolar outputs with a range of 0 to +5V, and the KPCMCI-8AOB, with eight bipolar outputs with a range of +/- 5V. The KPCMCI-8AO is PCMCI standard 2.1 compliant, supports hot swapping, and accommodates external interrupt inputs. The card can update multiple outputs simultaneously under software control or with an external event. Each of its eight I/O channels are software configurable as an input or output, providing for control or monitoring of digital information. The KPCMCI-8AO is fully programmable and Windows '95 compatible, and is shipped with cabling.

The KPCMCI-8AO's small size and low power consumption make it suitable for an array of portable and field applications in laboratory and industrial settings. It is especially suitable for product testing and control applications where an input stimulus is required to generate a variable-output control signal, such as in the control of a proportional solenoid. It is also useful for waveform generation and voltage sourcing, which are important elements of many laboratory applications.

## MODMODMODMOD

In ETI 2, 30th January 1998, Smartcam: In figure 1, the circuit diagram, an erroneous wire link is shown between IC5 (7806) and Video Out. This was intended to represent pointers to two wire links: one between IC4 pin 1 and a 75-ohm resistor (R6, also omitted) just before Video Out, and one between IC5 (7806) Vi and +12V/IC6 (7805)-Vi. The component layout, figure 3, shows the links correctly.

On the component layout, figure 3, R13 has been omitted. JP2 should move one pad to the left, and R13 inserted between IC1 pin 14, and IC1 pin 16/C13. The pads appear correctly on the PCB foil.

JP1-4, omitted from the Parts List, are option pin/pin jumpers, available from Maplin.

The author advises us that 0.25-watt resistors will work as well as 0.5-watt.

A query raised about the connections from IC7 and the opto-module board is still outstanding and any correction will be added to the MODs sheet as soon as possible.

The KPCMCI-8AO supports Windows '95 and comes with the Daqware (tm) standard software package, which includes Testpoint driver software. Labview drivers are also available.

Daqware includes everything the user needs to install, configure, test, calibrate and program a The KPCMCI-series card, including example programs for all supported languages. Testpoint, available as an option, allows the user to create applications without programming. It provides a drag-and-drop interface for data acquisition. Testpoint incorporates most commonly used mathematical, analysis, report generation and graphics functions, and includes features for controlling external devices, responding to events, processing data, creating report files and exchanging information with other Windows programs. Testpoint is Keithley's preferred "packaged software".

Optional Labview driver software provides an interface to National Instruments' Labview application software, allowing the Labview programmer to take advantage of software previously developed using Labview for National Instruments boards without expensive reprogramming.

For more information contact Keithley Instruments Ltd., The Minster, 58 Portman Road, Reading, Berks RG30 1EA. Tel 0118 9575666, fax 0118 9596469



# Robots

## Understanding

**This introduction to robotics by Harprit Sandhu explains what robots are and the basic conditions needed to make them functional.**

**A** robot can be described as a programmable manipulator doing work that otherwise a human would have to do, in a manner at least somewhat similar to the way a human would do it. A washing-up machine, for instance, is not normally considered a robot. It washes dishes, but it does not place the dishes in a sink, use a mop, or stack them in the drying rack afterwards. The robot of popular fiction is a mechanical person; more often today, a robot resembles a part of a mechanical person. Most shop-floor robots are the emulation of one arm of a human being.

Robot arms are used to weld, package, paint, position and assemble a host of everyday products. Parts from integrated circuits to printed circuit boards and VCR tapes to automobiles are now wholly or partly made and assembled by robots.

There are three distinct component groups within any sophisticated robot(ic) system. They parallel human functions:

1. Hardware: the body  
Robot arm and gripper: the arm and hand  
Vision system: eyes
2. The computer electronics: the brain
3. The software programming: the education

The mechanical part of the robot that does the physical work is designed to perform a specific family of tasks within a specified envelope determined by the physical size of the robot. The majority of the mobile robot population are Automatically Guided Vehicles (AGVs). Their main use is the delivery of raw material components. They provide an intelligent, mobile, programmable conveyor function.

A robot arm is a series of linkages connected up to work as a manipulator or arm. A motor controls each joint or movement. The operation of each joint does not have to be independent, but there are advantages to independent operation. If operation is not independent, the computer can be programmed so that for our purposes operation is virtually independent. However, this makes the task more computer-intensive, because calculations may have to be made before every move, and this computing time is no longer available for other computations. Even so, the mechanism is nowhere near as complex or flexible as the human arm.

The modern robot arm is a six-axis device fixed to the shop floor or to the machine it serves. It is controlled from a powerful computer, usually nearby. The computer cabinet contains all the logic components and amplifiers needed to run the robot. Shop floor robots can pick up pieces that weigh over 100

kilograms (220 pounds) and place them within about 1 mm (0.040 inches) of a desired location with ease. They can move loads at about 1 meter (3 feet) per second and put them down as softly as you please. Grippers or robot hands of many kinds can manipulate and control all manner of things.

### Types of robots

Robots can be divided into families according to the type of work they do. The major divide is between mobile and stationary robots. (See Table 1.)

### Defining a robot

In some ways, a "robot" is whatever we agree to call a robot. We tend to use "robotic" to describe machines designed to act automatically or autonomously. We might call an automated vehicle a robotic jeep. Industrial robots are called robotic arms, and machine vision is referred to as robotic vision.

Robots in general:

Are normally computer-controlled.  
Have components that move in some way  
Have servo-motors incorporated  
Have a user interface to allow us to interact with them.  
The interface may consist only of a start button or a keyswitch  
Can be programmed to do tasks  
Interact with their environment with input and output signals  
Handle or examine something external to themselves in some way



An AGV (Automatically Guided Vehicle) transporting paper rolls automatically in a factory environment. Note the hand-held pendant on the right, used for controlling the AGV manually. (Picture courtesy of Rocla (Finland)/Mentor (USA).)

It is worth noting that though playing chess is very "human", we do not call chess-playing computers robots. If, however, we were to add a rudimentary robot arm to manipulate the chess pieces, a mundane task compared to the ability to play chess, we would all agree that this was indeed a chess-playing robot. This shows that manipulation is an important element in our perception of a robot. Yet we often call vision systems "robotic vision" even though no manipulations are involved.

## Conclusions

We conclude that a robot is a programmable, computer-controlled machine that manipulates products and/or tools to do work. It can make decisions and interact intelligently with its environment. It can receive and send information to its environment. It may or may not be mobile.

This is not the official definition of a robot stipulated by the RIA, but it sums up what the the official definition conveys:

"A re-programmable, multi-functional manipulator designed to move materials, parts, tools, or specialised devices through various programmed motions for the performance of a variety of tasks." Robot Institute of America, 1979

A broader definition is: "An automatic device that performs functions normally ascribed to humans or a machine in the form of a human." Webster.

## Robots as workers

We humans have an overwhelming interest in doing as little as we can to get the job done. We design robots to improve on the positive attributes and eliminate the negative attributes of humans. Almost the total effort is in this direction. The essential difference between the automatic machines of today and yesterday is that today's machines are programmable. Today, what they do depends on the information that we put into them. Tomorrow, they will add intelligence, eventually massive intelligence. They will be able to optimise their work and react intelligently to all predictable and most unpredictable disturbances. Gross unpredictable disturbances can be handled by shutting down, sounding an alarm, summoning a human supervisor, or rejecting the part. Minute changes from cycle to cycle and part to part are harder to handle. They are subtle and hard to define, detect and react to appropriately.

## Intelligence

In machines, intelligence is the implementation of sophisticated "If... Then..." strategies in which action depends on what has already happened. This looks intelligent, but it is really rigid logic, perhaps with some randomness, range and flexibility added to the decision-making process. "If... Then..." strategies can be made extremely complex - this is what makes them useful. Today, most robot language programming is done in the programming language C. C has around 28 instructions in it. I say "around 28", because 28 instructions are defined although not all are used. There is little limit to what can be built up with these 28 kernels, and there are many sophisticated versions of the language. (Separate instruction sets address different tasks). A language with only 28 instructions is relatively easy to write (or port over) for a new computer design. All that has to be done is to implement these 28 instructions.

## Robot geometry


Two basic factors govern the motion and abilities of the robot: the geometry of the design and the sophistication of the

software. Robots come in many shapes and sizes, and the software is optimised to the needs of the specific robot. In "three-space", our everyday three-dimensional environment, there are various ways to design a robot that will reach all points in its work environment. As a rule you need one motor for each degree of freedom that you want to specify. So, at least three motors are needed to reach a location in three-space (X, Y and Z coordinates). Another three motors are needed to orient the hand in the three possible orientations (roll, pitch and yaw). This is the basic universal six-axis robot.

There are some mechanical design aspects of the human arm that we should observe:


The distance from shoulder to elbow is greater than the distance from elbow to wrist; which is greater than the distance from wrist to knuckles; which is greater than the distance from the first finger joint to the second finger joint. The distance from the second finger joint to the fingertip is the smallest distance on the mechanism.

The resolution of the system gets finer as we get closer to the gripper and the work. There are also increasing numbers of nerves in the human arm as we move from the shoulder to the fingertip. After the wrist, flexibility is provided by splitting the palm, by opposing the thumb to the fingers, by removing one digit from the thumb and by duplicating the fingers. Providing fingers of different lengths is a further refinement.

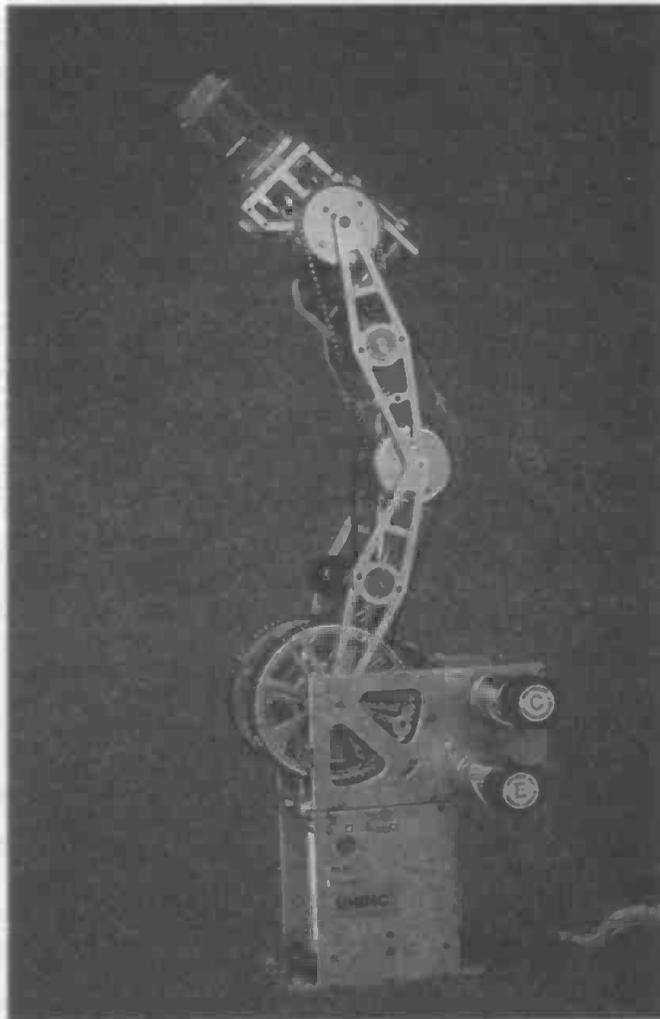

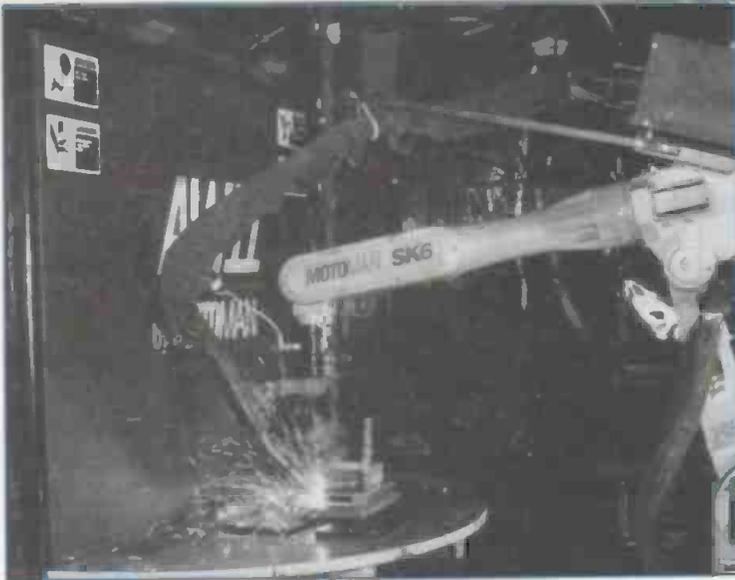A 5-axis, 6-motor robot arm that can lift about 1kg and run at about 1 foot per second. This 32-inch high Rhino XR-4 robot was designed to mimic larger industrial robots in a teaching environment





A Motoman SK6 robot arc-welding. The welding rod is fed in automatically, and co-ordinated by the robot controller. All aspects of welding (arc detection, puddle size, depth of weld, welding current, etc.) can be detected and controlled by the robot controller. (Picture courtesy of Motoman USA.)

This should give us a framework in which to think of the human arm as a robotic mechanism. This arm has done most of what we need for millions of years. What does it tell us about robot arms?

### Industrial robots

The moves we want our robot to make are dictated by the work we want it to do. The design will be an expression of the minimum capabilities needed to get that work done. The reach of each axis, the number of axes, the capabilities of the computer, the memory needed and the number of sensors (to mention just some of the major design parameters), will all be minimised to produce the most economical robot possible (figure 1).

Robot geometries are defined by the shapes that the robot's design mimics. The most common robot configurations are:

**Articulated:** Articulated robot arms act like the human arm. This is a flexible design that allows the most humanoid arm movements.

**Cylindrical:** A cylindrical configuration dictates a robot whose axes are designed to be specified as cylindrical co-ordinates. This usually means an axis that moves up and down like a cylinder, and another axis that moves in and out like a radius vector.

**Spherical:** In a spherical co-ordinate robot the two angles and a radial specification specify the point in space.

**XYZ or Orthogonal:** An orthogonal robot is an XYZ machine. It has three sides that are arranged at

right angles to one another.

**Gantry robots:** Gantry robots have a robot gripper suspended from a gantry that covers a large space.

### Grippers

The design of robotic grippers is a discipline in itself. Sophisticated grippers have microprocessors dedicated to their control. Almost all grippers fall into the following three categories:

**Vacuum Operated Grippers:** these allow the robot to pick up parts that have a flat surface. Small, delicate parts or large flat sheets often need vacuum grippers.

**Pneumatic Operated Grippers:** these allow simple open-close control. The fingers can have many shapes and configurations, including two-, three- and four-finger units.

**Electrically Operated Grippers:** these are the most sophisticated type. They allow the greatest flexibility of use and need the most sophisticated software. They also need the most maintenance.

### Software

The most important part of the robot is the software. Software determines what can be done with existing hardware and how it is done. Of course, if the appropriate hardware for a task does not exist, the task cannot be carried out, and if the software does not address the hardware in an appropriate way, even appropriate hardware is useless.

### Sensors and transmitters

Sensors that the robot employs can be located either on the robot itself, on the gripper, or in the robot's immediate environment. Sensors tell the robot controller about the robot itself, or its immediate environment, or about what is currently in the gripper. The robot can only take in information for which

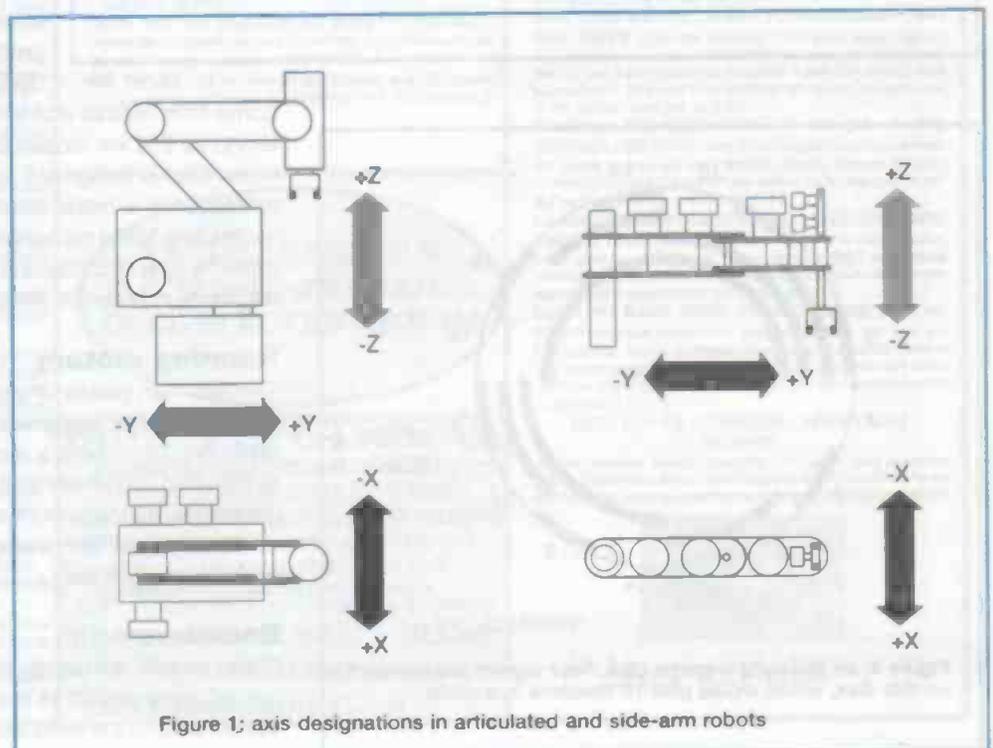


Figure 1; axis designations in articulated and side-arm robots

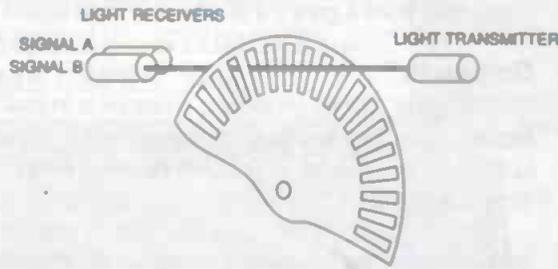


Figure 2: an optical encoder construction. Signals A and B will be 90 degrees out of phase. Here, signal B is On and signal A is Off.

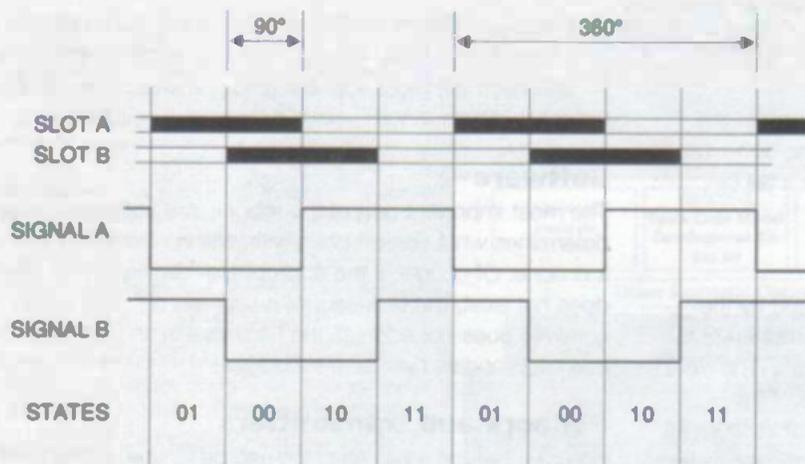


Figure 3: incremental optical encoder signals shown 90 degrees out of phase

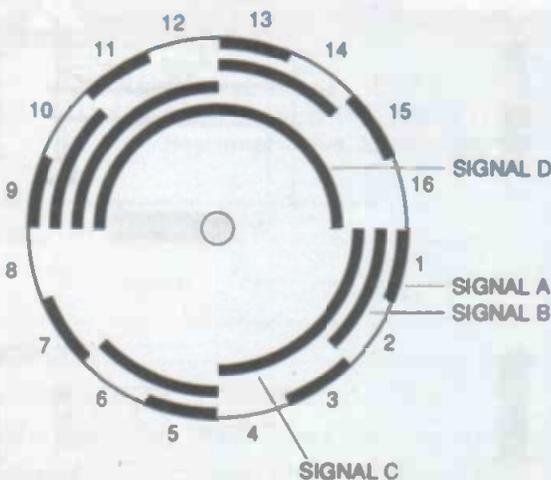


Figure 4: an absolute encoder disk. Four signals are shown on this disk, which would give 16 divisions in a circle.

it has the appropriate sensors, and only transmit information for which it has appropriate transmitters. Only those things that affect the robot and its operations are of interest to the robot operating system. All other phenomena are ignored.

Sensors used with robots fall into the following categories. These are listed in "distance to robot" categories. A robot can only receive signals from its environment through its sensor systems. The robot emits signals to send information to its environment. These can be electrical signals by wire, the physical closing and opening of relays, specific light, sound and radio signals or some other form of signal.

### Robotics and sound

Sound is easy to generate, detect and record. Using sound to detect distance involves emitting a specific frequency in short bursts and waiting for the sound to bounce back from surrounding objects. Emission and detection are relatively time-consuming, so this can be done only 20 to 50 times a second.

Sound moves across a space as a series of pressure waves. If we sample a sound 40,000 times a second (twice the highest frequency we can hear), we can re-transmit that sound, and the human ear will find the reproduction completely faithful. However, less than 20,000 Hz is sufficient for robotics.

Signal noise (such as a bad connection, or distortion) can be a problem, but the biggest problem is normal acoustic background noise - the kind of noise that makes conversation in a noisy factory impossible. Noise problems can be minimized by using high frequencies and modulating them so that the signal can be more easily distinguished.

Having our 20,000 bytes per second, we must analyse it. The analysis is complex and time-consuming. It is pretty certain that the sound will not be deciphered neatly one byte at a time.

Some form of front end filtering is used to sort out the correct sound so that we receive the information efficiently. Once we know what is being said, we must decipher what it means. In robotics, this is made easier by limiting the machine's vocabulary. Voice recognition is already available for quite small systems (one of ETI's contributors uses it on a PC), and telephone companies are using it to some extent.

### Running motors

The two main pieces of equipment needed to control a motor with a computer are optical encoders and power amplifiers. Encoders tell us what a motor is doing in terms of its rate of motion and overall revolutions, and amplifiers allow us to control the motor by controlling the energy supplied. By combining these with the speed of a computer, we can control a motor very precisely.

### Encoders

Robot motors are usually linked to optical encoders using an optical signal system to provide motion information. The signals sent to the computer are usually of the type that switch

## WIND GENERATORS 380 WATT

1.14 metre dia blades, carbon fibre blades, 3 year warranty, 12vdc output, 24v version available, control electronics included, brushless neodymium cubic curve alternator, only two moving parts, maintenance free, simple roof top installation, start up speed 7mph, max output (30m/s) 380w, £495 ref AR1

## HYDROPONICS

### DO YOU GROW YOUR OWN?

We have a full colour hydroponics catalogue available containing nutrients, pumps, fittings, environmental control, light fittings, plants, test equipment etc

Ring for your free copy.

**PORTABLE X RAY MACHINE PLANS** Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £8/SET Ref FXP1.

**TELEKINETIC ENHANCER PLANS** Mysterly and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon £4/SET Ref FTK1.

**ELECTRONIC HYPNOSIS PLANS & DATA** This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously, it is for use as entertainment at parties etc only, by those experienced in its use £15/SET Ref FIE/2.

**GRAVITY GENERATOR PLANS** This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means- cause it to levitate £10/SET Ref FGRA1.

**WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS** Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects. "Plasma in a jar", St Elmo's fire, Corona, excellent science project or conversation piece. £5/SET Ref FBTCLG5.

**COPPER VAPOUR LASER PLANS** Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/SET Ref FICV1.

**VOICE SCRAMBLER PLANS** Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/SET Ref FVSB.

**PULSED TV JOKER PLANS** Lite hand held device utilises pulse techniques that will completely disrupt TV picture and sound! works on FM too! DISCRETION ADVISED. £8/SET Ref FIT5.

**BODYHEAT TELESCOPE PLANS** Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £6/SET Ref FIBHT1.

**BURNING, CUTTING CO2 LASER PLANS** Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a worthwhile in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may vary well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc. £12/SET Ref FALC7.

**DYNAMO FLASHLIGHT** Interesting concept, no batteries needed just squeeze the trigger for instant light apparently even works under water in an emergency although we haven't tried it yet! £8.95 ref 9C152

**ULTRASONIC BLASTER PLANS** Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £6/SET Ref FALB1.

**ANTI DOG FORCE FIELD PLANS** Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £6/SET Ref FIDOG2.

**LASER BOUNCE LISTENER SYSTEM PLANS** Allows you to hear sounds from a premises without gaining access. £12/SET Ref FILL1.

**PHASOR BLAST WAVE PISTOL SERIES PLANS** Handheld, has large transducer and battery capacity with external controls. £6/SET Ref FIPBP4.

**INFINITY TRANSMITTER PLANS** Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phasor, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref FITELEGRAB.

**BUG DETECTOR PLANS** Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £5/SET Ref FBD1.

**ELECTROMAGNETIC GUN PLANS** Projects a metal object a considerable distance-requires adult supervision £5 ref FEMG2.


**ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND!** £5/SET Ref FEMAL.

**SOLAR POWERED WIND UP RADIOS BACK IN!** These F/M/AM radios have a solar panel and a hand operated charger! £17.95 ref SOLRAD.

**PARABOLIC DISH MICROPHONE PLANS** Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or

hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £6/SET ref FFP1/5.

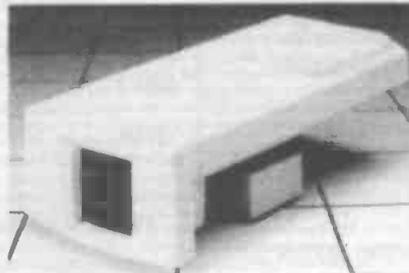**2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS** Operates on 0-12vdc, many possible experiments. £10 Ref FFM/71 TCLA.



## COLOUR CCTV VIDEO CAMERAS,

BRAND NEW AND, CASED, FROM £99.

Works with most modern video's, TV's,

Composite monitors, video grabber cards.

Pal, 1v P-P, composite, 78ohm, 1/3" CCD, 4mm F2.8,

500x582, 12vdc, mounting bracket, auto shutter,

100x50x180mm, 3 months warranty, 1 off price £119

ref XEF190, 10 or more £99 ea 100+ £89

**CIRCUIT PACKS** Packs of 35 circuit diagrams covering lasers, SW radio, gauges, bugs, car etc. Pack1, Pack2, Pack3 £4.99 each.

**SMOKE ALARMS** Mains powered, made by the famous Gent company, easy fit next to light fittings, power point. £4.99 ref SMOX.

**CONVERT YOUR TV INTO A VGA MONITOR FOR £26!**

Converts a colour TV into a basic VGA screen. Complete with built in pass, lead and swerve. Ideal for laptops or a cheap upgrade! Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

**\*16 WATT FM TRANSMITTER** Already assembled but some RF knowledge will be useful for setting up. Preamp req'd, 4 stage 60-100MHz, 12-18vdc, can use ground plane, yagi or dipole £69 ref 1021

**\*4 WATT FM TRANSMITTER KIT** Small but powerful FM transmitter kit, 3 RF stages, mic. & audio preamp included £24 ref 1026

**YUASHA SEALED LEAD ACID BATTERIES** 12v 15AH at £18 ref LOT8 and below spec 6v 10AH at £5 a pair

**ELECTRIC CAR WINDOW DE-ICERS** Complete with cable, plug etc. SALE PRICE JUST £4.99 REF SA26

**AUTO SUNCHARGER** 156x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £12.99 REF AUG10P3.

**SOLAR POWER LAB SPECIAL** You get 2 6v's 6v 130mA cells, 4 LEDs, wire, buzzer, switch + 1 relay or motor. £7.99 REF SA27

**SOLAR NICAD CHARGERS** 4 x AA size £9.99 ref 6P476, 2 x C size £9.99 ref 6P477

**GIANT HOT AIR BALLOON KIT** Build a 4.5m circumference, fully functioning balloon, can be launched with home made burner etc. Reusable (until you loose it!) £12.50 ref HA1

**AIR RIFLES** .22 As used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78 500 pellets £4.50 ref EF80.

REGISTER FOR OUR  
ELECTRONIC NEWSLETTERS  
BULL-ELECTRICAL.COM

## BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3.50 P&P PLUS VAT.

24 HOUR SERVICE £5.00 PLUS VAT.

OVERSEAS ORDERS AT COST PLUS £3.50

(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

phone orders : 01273 203500

FAX 01273 323077

Sales@bull-electrical.com

**INFRA RED FILM** 6" square piece of flexible infra red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc to infra red output only using standard light bulbs. Easily cut to shape. 6" square £16 ref IRF2.

**HYDROGEN FUEL CELL PLANS** Loads of information on hydrogen storage and production. Practical plans to build a Hydrogen fuel cell (good workshop facilities required) £8 set ref FCP1.

**STIRLING ENGINE PLANS** interesting information pack covering all aspects of Stirling engines, pictures of home made engines made from an aerosol can running on a candle! £12 ref STR2.

**12V OPERATED SMOKE BOMBS** Type 3 is a 12v trigger and 3 smoke canisters, each canister will fill a room in a very short space of time! £14.95 ref SB3. Type 2 is 20 smaller canisters (suitable for simulated equipment fires etc) and 1 trigger module for £29 ref SB2.

Type 1 is a 12v trigger and 20 large canisters £49 ref SB1.

**HI POWER ZENON VARIABLE STROBES** Useful 12v PCB fitted with hi power strobe tube and control electronics and speed control potentiometer. Perfect for interesting projects etc. 70x55mm 12vdc operation £6 ea ref FLB1, pack of 10 £49 ref FLB2.

**RUSSIAN BORDER GUARD BINOCULARS** £1799

Probably the best binoculars in the world! ring for colour brochure.

**NEW LASER POINTERS** 4.5mw, 75 metre range, hand held unit runs on two AA batteries (supplied) 670nm £29 ref DEC49.

**HOW TO PRODUCE 35 BOTTLES OF WHISKY FROM A SACK OF POTATOES** Comprehensive 270 page book covers all aspects of spirit production from everyday materials. Includes construction details of simple stills etc. £12 ref MS3.

**NEW HIGH POWER MINI BUG** With a range of up to 800 metres and a 3 days use from a PP3 this is our top selling bug! less than 1" square and a 10m voice pickup range. £26 Ref LOT102.

**BUILD YOUR OWN WINDFARM FROM SCRAP** New publication gives step by step guide to building wind generators and propellers. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81.

**NEW LOW COST VEHICLE TRACKING TRANSMITTER** KIT £29 range 1.5-5 miles, 5,000 hours on AA batteries, transmits info on car direction, left and right turns, start and stop information. Works with any good FM radio. £29 ref LOT101a.

**CCTV CAMERA MODULES** 40x70x20mm, 30 grams, 12v 100mA auto electronic shutter, 3.6mm F2 lens, COIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

**IR LAMP KIT** Suitable for the above camera, enables the camera to be used in total darkness! £6 ref EF138.

**UK SCANNING DIRECTORY** As supplied to Police, MOD, M15 and GCHQ covers everything from secret government frequencies, eye in the sky, prisons, military aviation etc. £16.50 ref SCANS.

**INFRA RED POWERBEAM** Handheld battery powered lamp, 4 inch reflector, gives out powerful pure infrared light! perfect for CCTV use, nightlights etc. £29 ref PB1.

**SUPER WIDEBAND RADAR DETECTOR** Detects both radar and laser, X K and KA bands, speed cameras, and all known speed detection systems. 380 degree coverage, front beamsteering. £192.7x4.5" fits on sun visor or dash. £149 ref

**CHIEFTAN TANK DOUBLE LASERS 9 WATT+3 WATT+LASER OPTICS**

Could be adapted for laser listener, long range communications etc. Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, no circuit diagrams due to MOD, new price £50,000? £195. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 20vdc, 800Hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. £199 for one. Ref LOT4.

**NEW LOW PRICED COMPUTER/WORKSHOP/HI-FI PCB UNITS** Complete protection from faulty equipment for everybody! In-line unit fits in standard IEC lead (extends 8" by 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £9.50 each ref LOT5. Or a pack of 10 at £49.90 ref LOT6. If you want a box of 100 you can have one for £250!


**DIGITAL PROPORTIONAL B GRADE RADIO CONTROLLED CARS** From World famous manufacturer these are returns to they will need attention (usually physical damage) cheap way of buying TX and RX plus servos etc for new projects etc. £20 each sold as seen ref LOT2DP.

**MAGNETIC CREDIT CARD READERS AND ENCODING MANUAL** £9.95 Cased with flyleads, designed to read standard credit cards! complete with control electronics PCB and manual covering everything you could want to know about what's hidden in that magnetic strip on your card! Just £9.95 ref BAR31.

**WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA?** We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the test editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74.

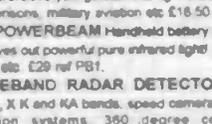**HIGH POWER DC MOTORS, PERMANENT MAGNET**

12-24v operation, probably about 1/4 horse power, body measures 100mm x 75mm with a 60mm x 5mm output shaft with a machined flat on it. Firing is simple using the two threaded bolts protruding from the front.



£22ea REF mot4

on and off with respect to time. The information is in the timing, and there are often millions of zeros and ones to read and sort out.

The position of a motor shaft must be measured precisely to be controlled accurately. These measurements can be taken with measuring devices that divide the position of the motor into thousands of counts per revolution. Optical encoders can divide a circle into over 1000 divisions. Combining this with appropriate gearing to the robot arm achieves the necessary accuracy.

Optical encoders come as incremental and absolute encoders.

### Incremental encoders

Incremental encoders (figures 2 and 3) provide two signals 90 degrees out of phase. Each signal is assumed to switch on and off for equal periods of time during each cycle, as shown below. The convention states that one complete on/off signal cycle represents a 360-degree rotation.

When a motor moves in one direction, one signal leads; when it moves in the other direction, the other signal leads. This tells the computer which way the motor is turning, and allows it to determine the progress and position of the motor even after many revolutions. Speed is determined by taking two encoder counts a known time apart, and dividing the positional difference by the elapsed time.

### Absolute encoders

Absolute encoders give the position of the axis they are connected to within a single revolution; therefore, they are usually fixed not to the motor but to a robot arm joint. Whereas incremental encoders must have a known starting point to count from, absolute encoders can provide the arm position at all times without reference to a known start-point (see figures 4 and 5). Each ring on the encoder is divided into alternate dark and light segments to give a binary signal. Each ring has twice as many segments as the previous ring, providing finer and finer positional information moving away from the centre. The rings must be read simultaneously. Eight rings provide a resolution of 1.41 degrees, or 1 part in 256 in a circle. Sixteen rings provide a resolution of one part in 65,536 (256 x 256), or 0.0055 degrees.

### Motors

Now that we have an understanding of how positional

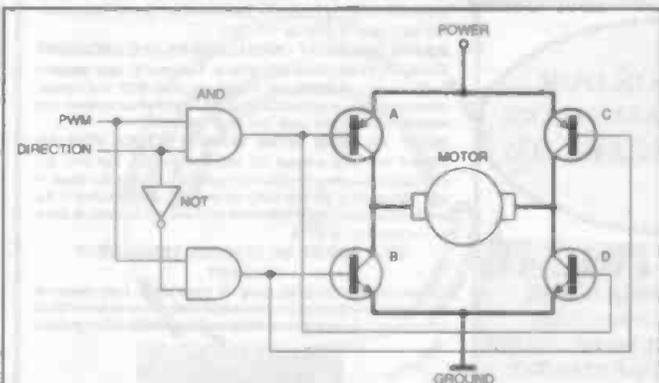


Figure 7: a basic "H" Bridge amplifier. In this A, B, C and D are large transistors that act as switches. Either A and D or B and C can be turned on at one time. Power wiring is shown as heavy lines.

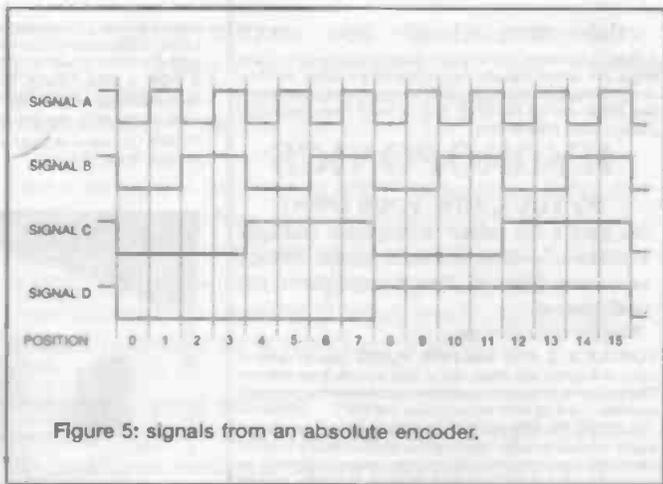


Figure 5: signals from an absolute encoder.

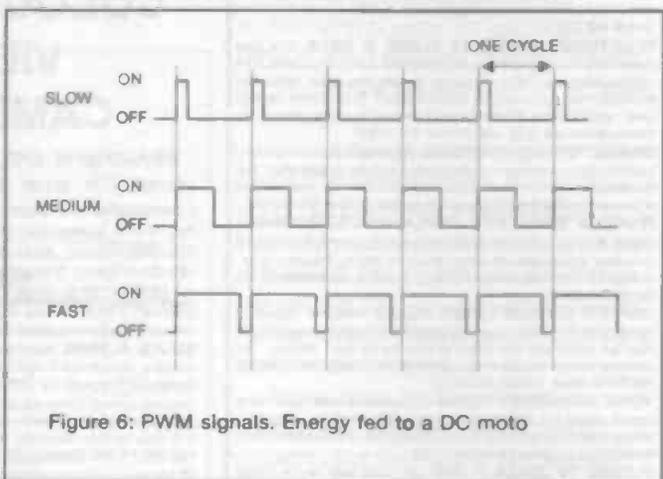


Figure 6: PWM signals. Energy fed to a DC motor

information can be obtained with the desired accuracy, we need to understand how a motor is positioned to exactly the position we are interested in.

With regard to the motor, there are two things you need to know over a period of time: how fast is it running and how long has it been running. With this information we can determine what the motor has done and what it is currently doing. Add to this the very accurate clock in the computer, and we can do the following:

Start a motor when we want; accelerate it at a desired rate; reach any velocity reasonable for the application; maintain the velocity under varying loads; slow the motor down as we want; slow down the motor at a desired rate; stop the motor at the exact point that we want; base the stopping point on time or on revolutions turned; base the control on internal or external events; change the control algorithm at will and as often as we want.

The speed of a DC motor can be controlled by changing the amount of energy supplied to it. Changing the load on a DC motor also changes its speed. The motor is stabilised by monitoring it and modifying the energy supplied to maintain the desired speed. In a robot with an ever-changing load on the motor, these energy corrections must be made hundreds of times a second.

There are two basic ways of controlling motor speed electrically: to control the voltage to the motor by an analogue method, or to turn a fixed voltage rapidly on and off. In a digital system it is easier to turn the signal on and off to vary the amount of energy sent. This technique is called Pulse Width

**PINHOLE CAMERA MODULE WITH AUDIO!** Superb board camera with on board sound! extra small just 28mm square (including microphone) ideal for covert surveillance. Can be hidden inside anything - even a matchbox! Complete with 15 metre cable, psu and tvrc connectors. £73.95 ref CC8

**BBC SELECTORS WITH SMART CARD SLOT AND VIDEO CRYPT** interesting new item in this week is the Selector. Originally made for the BBC to send encrypted video films to your VCR at night time. The project seems to have failed. Very complex units consisting of a smart card slot in the front plus several switches and an IR receiver. Fully cased and measuring 230 x 430 x 90mm, new and boxed. On the back of the unit is a smart socket plus a UHF input and output. A channel tuning control numbered 26 to 40 and an IR socket. Inside is a comprehensive tuner section, smart card reader mechanism and control electronics plus a power supply section. These units are sold as strippers but we imagine you could use one to convert a monitor into a TV or maybe use the video crypt side of things for something else. Supplied complete with manual and mains lead. Clearance price just £9.95 ref BBC1X

**IN-LINE RCB UNIT** This in-line earth leakage unit instantly shut off the mains supply in the event of any current flowing between live and earth thus preventing a potentially lethal shock. IEC plug one end, socket the other, fitted in seconds, reset button. The ultimate safety aid when working on electronic equipment, computers etc. As these units are fitted with an in-line IEC plug on one end and socket on the other than could even be used to extend standard IEC computer leads. Pack of 3 £9.95 ref LOTS4

**THE ULTIMATE ENCLOSURE** for your projects must be one of these! Well made ABS screw together beige case measuring 120 x 150 x 50mm. Already fitted with rubber feet and front mounted LED. Inside is a pcb fitted with other bits and pieces you may find useful. Sold either as a pack of five for £10 ref MO1, pack of 20 for £19.95 ref MO2

**17 WATT 12V SOLAR PANEL** A solar panel designed to give a nominal 12v. The solar cells are laminated within a high quality resin material which offers excellent protection against UV and moisture. Mounted on tempered glass in an aluminium frame. The panel is ideal for charging sealed lead acid batteries and a protection diode in the circuit prevents reversed current flow. Mounting is by four adjustable hooks and connection is by screw terminals. Max power 17 watts, 35 cells, 17vdc peak, 433x402x15mm, 1000mA max, 1.9kg. Solar panel £115 ref SOL4

**SOLAR POWERED AM/FM RADIO** A compact, AM/FM mono radio complete with earphone and a solar panel that recharges the built-in battery when placed in direct sunlight or under a strong lamp. It features a rotary Volume/On/Off control (which must be set to 'Off' for recharging), AM/FM selector switch, rotary tuning control, metal belt clip and socket for external 3V DC supply. Solar Radio £7.95 ref SR23

**MOTOR CYCLISTS RADAR DETECTOR** Now in is the Whistler 1590 Laser/Radar detector complete with a speaker for motorcycle helmets. Super wide band covering X, K and Ka plus lasers at 950nm +/- 10nm, 380 deg total parimeter protection, detects laser, radar and V0-2 wherever they come from. £158.95 ref RD4

**MAGIC EAR** Unlike previous 'sound-magnifiers' we have offered, Magic Ear fits unobtrusively behind the ear itself. Magic Ear's micro technology is very advanced. Its built-in microphone is extremely sensitive and there's also a volume control to help you adjust to all conditions in use. Magic Ear is startlingly effective. It'll help you to follow every word of conversation even at a distance, and enjoy theatre, cinema or live music with stunning new sound. Comes fitted with 3 long life batteries, a free travel pouch, plus a choice of 3 different ear pieces designed to fit all shapes of ear. Magic ear £16.95 ref MAGE3

**RADIO METER** Perhaps the best of the scientific knock-knocks of the past and well overdue for revival! Fascinating, soothing and educational in the vacuum inside the inverted bulb contains the vases revolve, driven round by light particles alone! (each vase is black on one side white on the other) Radiometer £9.95 ref SC120B

**SATELLITE NAVIGATION £119** The GARMIN- GPS 36 is the one navigational tool for the great outdoors that offers big features in a small, lightweight package - all at a truly affordable price. Mark your favorite fishing spots, tree stand or camp site. Or trace your steps back to the safety of your starting point using our all-new TrackBack feature. The GPS 36 shows you exactly where you are, where you've been and where you're going. The GPS 36 features easy, one-thumb operation and weighs only 255g. There's a resettable trip odometer, graphic compass and high way steering guidance. And it provides up to 20 hours of use on a set of 4 AA batteries. The GARMIN GPS 36. The affordable way to bring you back. £119 ref GPS1

**DIFFERENTIAL THERMOSTAT KIT** An electronic self assembly kit designed for use in solar heating systems, heat recovery systems etc. The principle of the kit is that it has two thermostats that are placed on the same to be measured (typically a solar panel and a water storage tank) the controller then operates a relay all the time one temperature is higher than the other. The temperature difference is adjustable. A typical use would be to operate a pump all the time a solar panel was at a higher temperature than the water storage tank. Differential thermostat kit £29 ref LOTS3

**10 WATT SOLAR PANEL** Amorphous silicon panel fitted in a anodized aluminium frame. Panel measures 3' by 1' with screw terminals for easy connection. One of these panels will run our solar water pump in full sunlight although we would recommend that for optimum performance two panels would be preferable. 3' x 1' solar panel £56 ref MAQ45

**12V SOLAR POWERED WATER PUMP** Perfect for many 12v DC uses, ranging from solar fountains to hydroponics! Small and compact yet powerful! Will work direct from our 10 watt solar panel in bright sunlight. Max head 17 ft Max flow rate: 8 lpm Current: 1.5A (Ref ACB) £18.95

**BOOST CELL PHONE RECEPTION ON THE MOVE!** Compared to high-powered carbonates, hand-portable mobile phones don't always work too well in moving vehicles. Sometimes the signal 'drops out' during a call, other times there's too much interference to get through at all. However, the affordable Cell Patch provides a major improvement, dramatically boosting signal reception without wires or batteries. The 9.5 x 9.5cm (3.7" x 3.7") microthin antenna adheres to your car window/sunvisor, ideally within 61-122cm (2-4') of the handset, or can be carried in a pocket. Works with all types of portable cellular phone. Cell Patch £11.95 ref CEL1

**CAT SCARER** produces a blend of high sonic and low ultrasonic sound, which is inaudible to humans, birds and fish - so it is ideal where you want to protect your bird table or fish pond against feline predators. It will deter cats from your garden and other protected areas. It will also deter feral cats, mains operated, 10 m of cable. Running cost will be approximately 1 p per day, Garden watcher £42.45 ref GW2

**VIDEO PROCESSOR UNITS 78v 10AH BATT/24V BA TX** Not too sure what the function of these units is but they certainly make good strippers! Measures 300x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear, inside 2x 6v 10AH sealed lead acid batts, pcb's and a BA? 24v toroidal transformer (mains in) sold as seen, may have one or two broken knobs etc due to poor storage. £9.95 ref VP2X

**SOLAR MOTORS** Another new line for us are these tiny motors which run quite happily on voltages from 3-5Vdc. We have tried one on our 6v amorphous 6" panels and you can run them from the sun! 32mm dia 20mm thick. £1.50 each

**TELEPHONES** Just in this week is a huge delivery of telephones, all brand new and boxed. Two piece construction with the following features: illuminated keypad, nice clear easy to use keypad, tone or pulse (switchable), recall, redial and paste, high/low end of ringer switch and quality construction. Each telephone is finished in a smart off white colour and is supplied with a standard international lead (same as US or modern card sockets) if you wish to have a BT lead supplied to convert the phones these are also available at £1.55 each ref BTUX. Phones £4.99 each ref PH2

**INFRARED CAR PHONE KIT £7.99** interesting box of goodies! this kit was designed to convert car phones to enable hands free dialling, the kit contains the following items: 1) A keypad designed to mount in the centre of the steering wheel. It requires a 9v PP3 battery and transmits the numbers using three on board high power infra red LEDs 140 x 120mm. 2) An infra red receiver module containing a IR photo diode, IR filter and control electronics. 60 x 30 x 15mm (cased). 3) Control box (nice case) 100 x 170 x 35mm which we understand is the interface between the infra red and the car phone. It is also supposed to adjust the volume of your car stereo at the same time made for Philips car phones (but we don't know the model) Complete kit is £7.99 ref CP1

**Hi power 12v xenon strobe** variable rate flasher modules and tubes £8. Useful 12v PCB fitted with control electronics and a powerful Xenon tube! Just apply 12v DC to the input and the tube will flash. On the board is a small potentiometer which can be used to vary the flash rate. PCB measures just 70x 55mm and could be incorporated into many interesting projects. £8 ref FLS1. Pack of 10 is £49 ref FLS2

**WANT TO MAKE SOME MONEY?** Stuck for an idea? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is a certificate enabling you to reproduce the manuals as much as you like! £14 ref EP74

**TALKING WATCH** Yes, it actually tells you the time at the push of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £8.99 ref EP26A

**POWERBEAM INFRARED Lamp** All this lamp gives out is infra red light, and loads of it! perfect for supplementing night sight and surveillance equipment. Most mono CCTV video cameras are infra red sensitive so used in conjunction with this lamp would greatly enhance their operating performance. Water resistant case and rubber covered switch make this unit perfect for all weathers. Krypton bulb. 4 D cells required. Powerbeam lamp £29 ref PB1

**GIANT SCREEN VIEWER!** Turn your TV picture into a super size screen! This high precision Fresnel lens converts even the smallest screen up to a massive 26", giving a crystal clear picture at a fraction of the cost of a big TV. Easily fitted in minutes. Also ideal for PC monitors etc. £26.95 ref SVGA2

**NOGALIGHT NIGHT VISION £129** Open up a new world of adventures and experiences. Wildlife enthusiasts and adventurers in the wilderness, amateur astronomers, hunters, war gamers, private eyes on surveillance, all find Nightguy indispensable for their use. Nightguy's unique features include a special tube protection device, to eliminate over exposure, and infrared illuminator used in total darkness, such as in cave exploration and operations in dark rooms. The Nightguy is light and hand held, or can be mounted on a standard tripod. It uses two standard AA batteries and can be operated by left or right hand users, with or without optical glasses. Optical Magnification X 1.7 Field of View 10 Degrees Focusing Range 25cm to infinity objective Focal Length: 50 mm FN 1.6 Diopter Range: +/- 3 Mechanical Length: 182 mm Width: 65mm Height: 100 mm Weight: 700 gr. Electrical Power Source: 3 VDC, 2AA batteries Battery Life: 40 hours Infra-red illuminator, built-in Imaging Detector: Night Vision Image Intensifier Tube £129 ref NOGA

**Register with us at  
www.bull-electrical.com  
for your free e-mail  
NEWSLETTERS!**

**DRILL OPERATED PUMP** Fits to any drill in seconds, uses standard garden hose, will pump up to 40 gallons per hour! £8.99 ref DRL3

**BULL ELECTRICAL**  
250 PORTLAND ROAD, HOVE, SUSSEX.  
BN1 5QT. (ESTABLISHED 50 YEARS).  
MAIL ORDER TERMS: CASH, PO OR CHEQUE  
WITH ORDER PLUS £3.50 P&P PLUS VAT.  
24 HOUR SERVICE £5.00 PLUS VAT.  
OVERSEAS ORDERS AT COST PLUS £3.50  
(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)  
phone orders : 01273 203500

FAX 01273 323077  
Sales@bull-electrical.com

**STEREO MICROSCOPES BACK IN STOCK** Russian, 200x complete with lenses, lights, filters etc etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee) full details in catalogue

**SECOND GENERATION NIGHT SIGHTS FROM £748**

**RETRON** Russian night sight, 1.6x, infra red lamp, 10m-Inf. standard M42 lens, 1.1kg. £349 ref RET1

**MAINS MOTORS** 180 RPM 90X70mm, 90X55mm 50x50mm output shaft, start cap included. £22 ref MGM1

**PC POWER SUPPLIES, CUSTOMER RETURNS, ALL FAN COOLED, OUR CHOICE, BARGAIN AT 8 PSU'S FOR £9.99 REF XX17**

**LOW COST CORDLESS MIC** 500 range, 90 - 105mhz, 115g, 103 x 26 x 30mm, 9v, PP3 battery required. £17 ref MAG15P1

**JUMBO LED PACK** 15 10mm bicolor leds, plus 6 giant (56mm) seven segment displays all on a pcb £8 ref JUM1. Pack of 30 55mm seven seg displays on pcb's to £19 ref LED4, pack of 50 £31 ref LED50

**12VDC 40MM FANS MADE BY PANAFLO, NEW. £4 REF FAN12**

**ELECTRONIC SPEED CONTROLLER KIT** For the above motor is £19 ref MAG17. Save £5 if you buy them both together, 1 motor plus speed controller rrp is £41, offer price £36 ref MOT5A

**RUSSIAN 900X MAGNIFICATION ZOOM MICROSCOPE** metal construction, built in light mirror etc. Russian shrimp farm, group viewing screen, lots of accessories. £29 ref ANAYLT.

**AA NICAD PACK** Pack of 4 tagged AA nicads £2.99 ref BAR34

**RUSSIAN NIGHTSIGHTS Model TZS4** with infra red illuminator, views up to 75 metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focusing range 1.5m to infinity. 2AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty

**LIQUID CRYSTAL DISPLAYS** Bargain prices, 20 character 2 line, 63x19mm £3.99 ref SMC2024A

**16 character 4 line, 62x25mm £5.99 ref SMC1640A**

**TAL-1, 110MM NEWTONIAN REFLECTOR TELESCOPE** Russian Super astronomical 'scope, everything you need for some serious star gazing! up to 160x magnification. Send or fax for further information 20kg, 885x500x1650mm ref TAL-1, £249

**YOUR HOME COULD BE SELF SUFFICIENT IN ELECTRICITY** Comprehensive plans with loads of info on designing systems, panels, control electronics etc £7 ref PV1

**PHOTOMULTIPLIER TUBES** Based and unused straight from the ministry of defence. Made by EMI with a MOD part no of 100CV/5114 and packed almost 30 years ago. I do you have a use? do you want to count light particles? They would look nice on the mantle piece! Offered to you at £15 each (we think the MOD paid more than this is 1956! £15 each ref PM2)

**CLOCK CAMERA WITH AUDIO** Discreetly monitor living rooms, reception, offices, etc or any other area. Fully working clock houses an invisible spy camera complete with audio. Complete setup includes clock, camera, microphone, clock battery, 15 metres of cable, power supply, adapter for either scart or phono. Everything you need, no soldering required. Full instructions included. Easily installed in just a few minutes. Plugs straight into VCR or TV (scart or phono) Clock camera with audio £99.95 ref CC3

**AUTO RECORD KIT** This automatic system will instruct your VCR to start recording when movement is detected via the PIR. Recording will stop 30 seconds after your visitor has left which saves hours of tapes as the video only records what you want to see. Complete system with PIR, will work with all remote control video recorders. £39 ref CV2

**TELEPHONE VOICE CHANGER** Changes your voice to a male or unfamiliar one. Simply place over the telephone mouth piece and speak into the changer. Fully adjustable for different voices. Supplied complete with batteries, ready to go. Unit measures 90 x 80 x 20mm Telephone voice changer £14.95 ref CC3

**EXTERNAL CAMERA** Introducing the Bulldog model 4 vandal resistant camera in heavy steel case for interior or exterior use. Top quality case housing a 420 line camera module. Each camera is supplied with a 15m cable terminating in Scart and phono plugs. Multi angle bracket for easy installation in any situation. A 12vdc psu is also included. Easily installed in a few minutes, plugs straight into VCR or TV (phono or scart). Bargain price £39.95 ref CC1

**GIANT INSULATORS** Just in this week are some giant ceramic insulators, each one measures 130mm high and about 170mm diameter. Finished in a high gloss brown and black glaze. In the base of each insulator is a threaded hole approx 1" diameter, rather like a mop/broom head thread. If you are into shortwave radio, crystal sets or high voltage experiments then these are for you. (We've got one as a door stop) Not too sure what their original purpose was, all we know is they were made for export about 25 years ago, never imported and been in store since then. Price is £8 each ref INS1.

**NATO RADIATION MONITORS** interesting new line! - These are small modules that strap on your wrist (strap supplied) and monitor radiation. We have stripped one apart and they contain a small piece of "crystal" this could be something like Naphthalene or any other rare radiation sensitive crystal. When radiation strikes the crystal, it scintillates and a small amount of light is produced in the crystal in reaction to the radiation exposure. This light is then picked up by a micro pv cell measuring about 2mm square! Also in the unit is a sheet of foil, a circular metal plate (insulation between the two) and a small pair of additional parallel metal plates. NATO part no is 6885-80-225-2314 any information gratefully received! Alternatively if you wish to buy one they are just £3 each ref NATOX

**WE HAD 38,000 'HITS' ON OUR WEB SITE IN FEBRUARY '98....**  
**BULL-ELECTRICAL.COM**  
See our live camera!

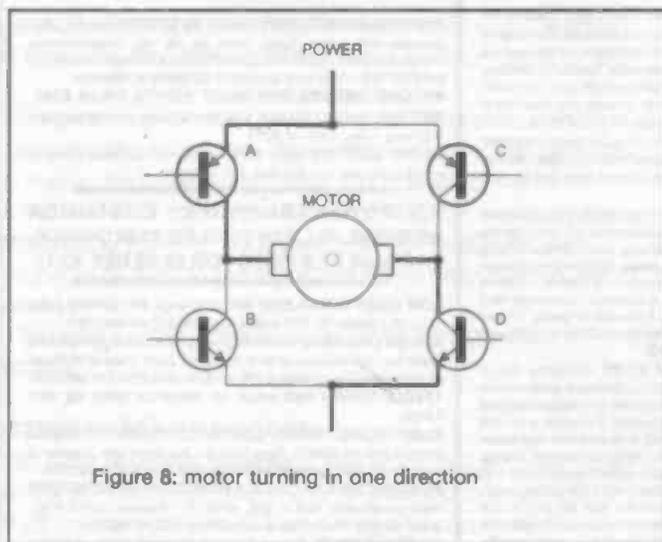


Figure 8: motor turning in one direction

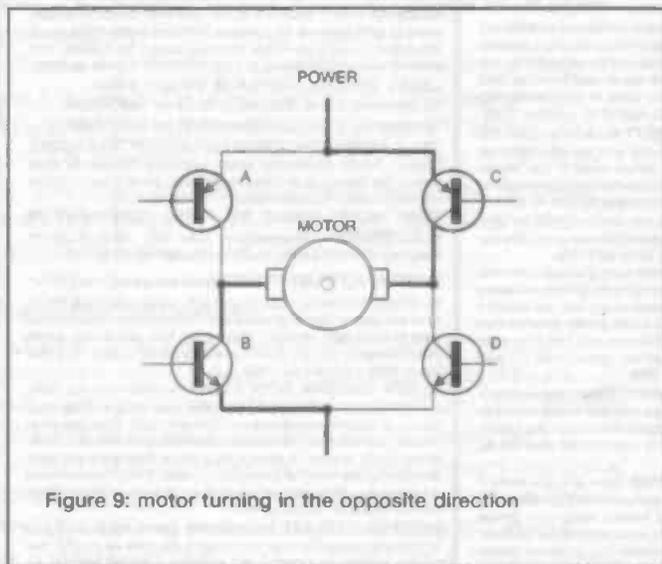


Figure 9: motor turning in the opposite direction

Modulation (PWM). The length of the energy pulse is modified in each cycle (see figure 6). If the signal is on all the time, the pulse width is long, and the motor runs at a high speed. If it is on half the time, the pulse width is 50 percent and the motor runs at about half speed. If it is on none of the time, the pulse width is zero and the motor remains off.

The motor must be switched very rapidly for smooth operation. About 200 times a second (Hz) is enough for most motors, because the mass of the motor and its attached components averages out the speed. However, these are frequencies that human beings find very annoying when something loose in the motor windings starts to vibrate. An off frequency above 20,000 Hz is usually chosen. 40,000 Hz takes it above the hearing range of most domestic animals as well.

### The PWM amplifier

The basic PWM motor amplifier is an H bridge (see figure 7). In this bridge, if transistors A and D are turned on, current flows in one direction in the motor windings, and the motor runs in one direction. If A and D are turned off and transistors B and C are turned on, the current flows in the other direction and the motor runs the other way (figures 8 and 9). If transistors A and C or B and D come on together, there is a direct short circuit from power to ground, destroying the amplifier. It is crucial that one set of transistors is shut completely before the other set comes on. Because the

switching of the transistors is very rapid but not instantaneous, overlap is a risk. Logic circuits in the amplifier should ensure that this does not happen.

A servo-motor must respond to commands within certain parameters to be useful in a robotic application. A motor would not be performing its job if any of the following happened:

It does not turn on immediately when power is applied; it does not stop immediately when power is removed; it does not move as fast as it needs to; it moves faster than told to; its operation is not repeatable.

Motor control schemes should ensure that none of this occurs. Otherwise, the system should detect it and warn the operator. Usually, when the error between what the motor is supposed to do and what it does exceeds a certain number of encoder counts, the condition is flagged as a performance error. Nevertheless, there are always delays between an event, the taking of readings, their interpretation, and initiating corrective action.

### Speed control

The control of motor speed by the percentage of time the motor is switched on (figure 10) is done with software. As the motor turns, the encoder counts go to a counter that the computer reads whenever it needs to. The computer uses that information, and the time from its internal clock, to change the pulse width to the amplifier to maintain the speed and position of the motor.

What follows here is an English-language-like program to maintain a motor speed with the integrative function only:

```

Label 1
Read the position counter
Compare it with the last
reading
Calculate the motor speed
If it is faster than desired, lower
the current
If it is slower than desired,
increase the current
Take care of other functions
Go to Label 1

```

The computer code will look less like English, but will fulfil the same function.

The control loop consists of a series of expressions representing the proportional, integrative and derivative components of the energy needed by the motor. This is a PID

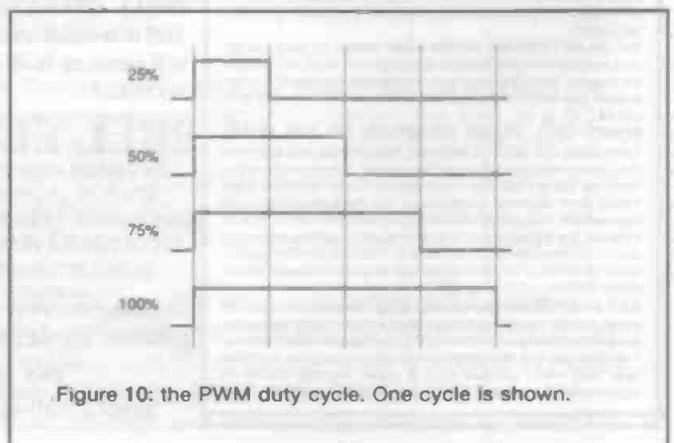


Figure 10: the PWM duty cycle. One cycle is shown.

equation, and we often refer to this form of control as PID control. It is important to know that having three components allows better control of a motor.

The motors used to control robots are called servo-motors (see figures 11 and 12). "Servo" (derived from Latin *servus*, a slave) expresses the idea that the motor takes orders from a changing signal, here called an error signal. In effect, the motor responds to an error signal by trying to make the signal disappear. Whatever the motor is connected to affects the magnitude of the error signal, and the motor is made to work or move in the direction that will reduce the error signal. An external (to the motor-load) device is also able to manipulate the error signal. Since the motor is designed to follow the signal, we can make the motor do useful work by programming the error signal.

We can now tell the motor exactly when to start, how fast to speed up, how fast to run, how long to run, how to slow down and exactly when and where to stop. We can tell the motor to repeat the cycle as often as we like, we can cycle it just once, and we can modify the cycle at will while the cycle is in progress. This allows us to make the operation of the motor dependent on any condition within the controlling computer or on any signal that can be read by the computer.

In current technology, electric motors are put into motion by creating opposing and attracting magnetic fields. The magnetic fields are manipulated sequentially to rotate a shaft attached to the rotating armature. Since at least one of the magnetic fields is created by passing an electric current through a winding, and we can control electricity, we can control the motor by controlling the electricity through its windings.

The following motor designs are suitable for robots:

**Rotating Servo-motors:** these are usually DC motors with a position encoder attached to the motor shaft, usually an incremental optical encoder, to provide a feedback signal giving the position and speed of the motor.

**Linear servo-motors:** these use the same technology as rotating motors, except that their armatures and fields are arranged in a straight line rather than a circle. Imagine cutting a regular motor along a radial plane, opening it up and laying it flat on the table. (Don't try this at home!) The field, the armature and the commutator are in straight lines, and the motor armature moves across the field in a straight line. (Appropriate physical constraints and guides are added.)

**Stepper motors:** these move through a small segment of a circle each time the current to the motor is changed. There are several independent windings in the motor, and usually a sequence of four electrical changes. The motor moves a step during each change. There are also half steps and micro steps, created electronically. Stepper motors usually move between

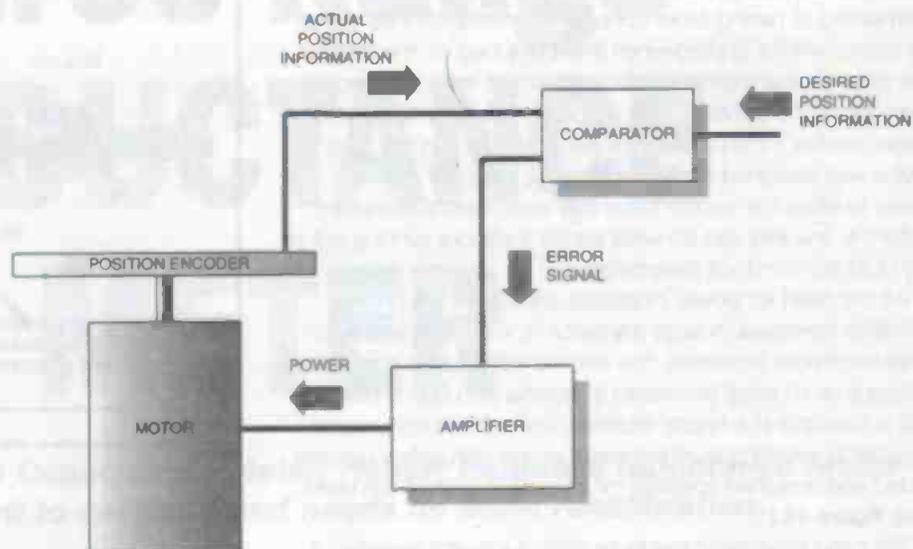


Figure 11: motor feedback scheme schematic

0.9 and 15 degrees per step, and they do not normally need feedback encoders, as we can count the motor's steps as we send them. However, if the motor is overloaded, it can slip, and the count will be compromised. Stepper motors usually have low speed and low torque characteristics. Their main use is in office machinery and other low power applications.

For the motor movement to be predictable, it is made to follow a trapezoidal profile (figure 13): the motor accelerates at a fixed rate until it reaches its operational velocity. It then decelerates at a fixed rate until it stops. The computer calculates the energy needed by the motor to do its work in the time required. Motors operating in synchronisation with another motor must accelerate and decelerate for the same length of time as the lead motor to keep their encoder counts in synch.

For very short moves, there is no constant speed operation. The motor accelerates, decelerates and stops, never getting up to the running speed. This move profile is called a triangular (three-point) move.

It is very hard to run a motor at a very slow speed. Imagine trying to run a motor at one revolution per day (gears not allowed). If we wanted to adjust the speed every second we would need  $24 \times 60 \times 60 = 86,400$  encoder counts per revolution to get one count per second, and we probably need 1000 thousand times that for smooth motion. Let's assume an encoder that gives the minimal 86,400,000 counts: if we also wanted to run this motor at 3000 revolutions per minute at its top speed, we will need encoder counts for  $3000/60 \times 86,400,000$ , or 4,320,000,000 counts per second. Though not impossible, this causes problems. Minimum speed, maximum speed and encoder counts are interrelated.

For a motor in a servo application, we want to define a top speed that will use less than the maximum energy the motor can accept. For example, if we want to run a device at 100 rpm and we have geared the motor to the device with a 20:1 ratio, the full speed of the motor will need to be 2000 rpm to achieve the speed we want. It is desirable that this full speed

be attained when the motor is being given as little as 25 percent of the energy that it can readily accept (without overheating or having other operational problems). The rest of the energy will be applied when there is a load on the device. This gives us the reserve power we need to meet the load demands of the application. A 25 percent duty cycle is not a magic number - the percentage would depend on the load the device was designed for. There must be plenty of reserve power to allow the system to be fully compliant; a compliant system is one that can do what we tell it without running out of any of its performance parameters.

As the need for power increases, the size of the driving transistor increases. A large transistor is, very roughly, a lot of small transistors in parallel. You can control a larger current by putting 8 or 10 small transistors in parallel with one another. This is tolerable in a hobby situation, but not in a commercial application, where special transistor arrays with safety features added and designed specially for controlling motors are used. (See figure 14.)

We need three basic inputs to control a motor amplifier: a signal to enable the motor amplifier; a signal to select direction of motion

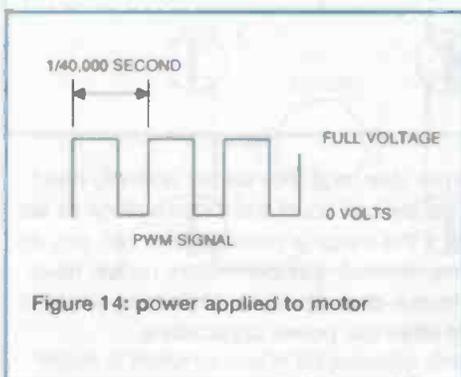


Figure 14: power applied to motor

(forward or backward); and a signal to determine the percentage of full power applied (the pulse width).

A signal to enable the motor amplifier is important to ensure that the

amplifier will remain turned off till the computer has come up to a stable condition and is ready to control the motor. This is specially important with a robot motor, because the motor must not move until we are absolutely ready for it, or damage may be done. This is achieved with fail-safe electronics and tying other signals to ground potential until they are ready to be released.

### Model aircraft servo motors

Radio-controlled model aircraft use tiny servo motors, positioned by converting the length of pulse fed to them into the position of the servo's output shaft. These servo motors consist of motor, a gearbox, a potentiometer and a small integrated circuit. The ic converts the length of the incoming pulse to a desired output shaft position (represented by a shaft-mounted potentiometer). If the position of the pot does not match the desired shaft position, the motor is turned forwards or backwards till the pot reaches the desired position. The current to the motor is then turned off. The situation is monitored constantly, so that correction is taking place all the time. (See figure 15.)

The positioning accuracy depends on the accuracy of both the pot and the pulse length. A resolution of about half a degree can be achieved with most model aircraft servos.

These servo motors run on three wires: the power line, the pulse signal line and a common ground. As model aircraft servos operate by converting a known pulse width to a motor output shaft position, they are relatively easy to use if a source of short pulses can be created. This is quite easy with the

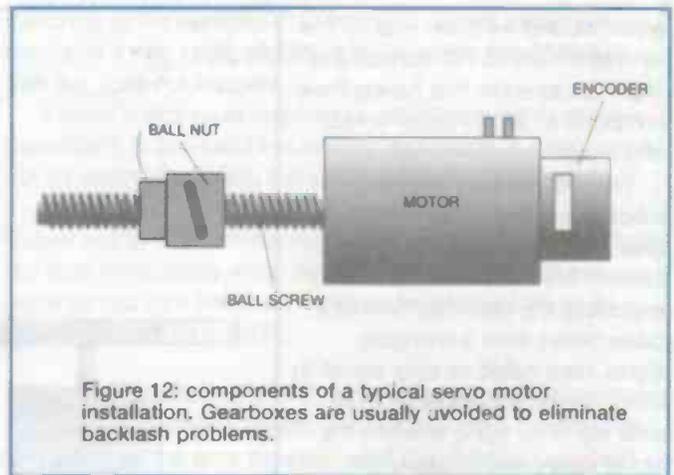


Figure 12: components of a typical servo motor installation. Gearboxes are usually avoided to eliminate backlash problems.

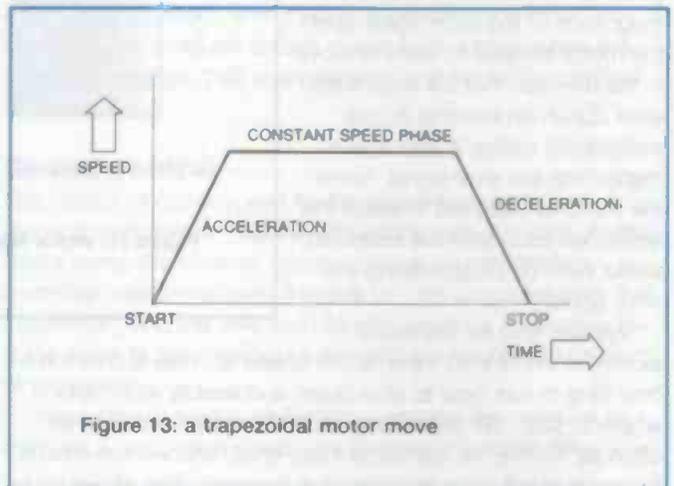


Figure 13: a trapezoidal motor move

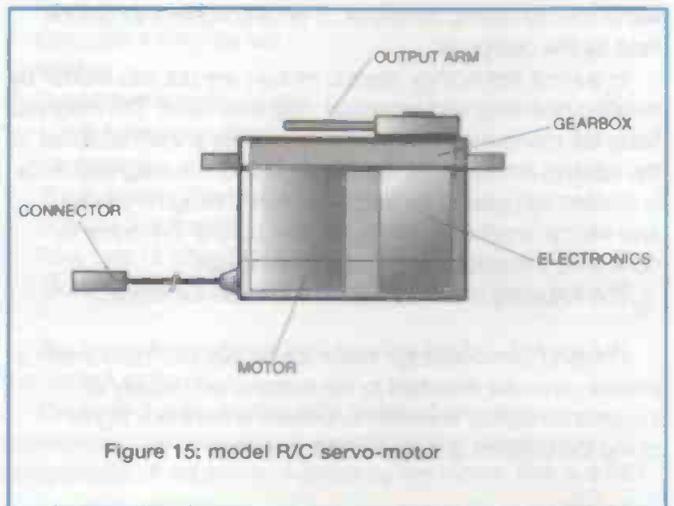


Figure 15: model R/C servo-motor

small single chip microcomputers now on the market. These inexpensive units are suitable for robotic experimentation.

(My book "Introduction to Robotics" from Nexus gives detailed plans and instructions on how to build and program a walking robot with such motors.)

Cover: The Mitsubishi RV-E2M Movemaster, a small sophisticated table-top robot with a positioning "teach" pendant and controller. (Courtesy: Rixan, US Mitsubishi distributor.)


# Three-Range INDUCTANCE METER

*A partner to last month's Capacitance Meter, Robert Penfold's Inductance Meter is straightforward to calibrate and needs no scale recalibration.*

**T**his inductance meter is a companion project to the capacitance meter published last month. Like the capacitance meter, it is very easy to calibrate and use. Only one inductor is needed to calibrate the unit, and no recalibration of the meter's scale plate is needed, because the unit has linear scaling. The three ranges have full-scale values of 1mH, 10mH, and 100mH, which enables a wide range of inductors to be checked. This includes high value components for use in audio filters, medium value inductors as used in switch mode power supplies, and many of the small chokes used in radio frequency circuits. The unit cannot be used to measure accurately very low value chokes of less than about 22uH in value, but these are little used in practice. They are difficult to measure accurately because the inductance in the leadout wires and test leads is quite significant in relation to the value of the components under test. In fact, the inductance of a very small choke can be considerably less than the inductance of its leadout wires!

It is only fair to point out that there is a slight problem when trying to test inductors, which is that their inductance is invariably frequency dependent. Most inductors are designed with a specific frequency range in mind, and tend to have generally lower values outside that frequency range. In this case, the inductance is measured at a frequency of just over 10kHz, which gives good results with medium to high value inductors as they are usually designed for optimum results at low to medium frequencies. Results with radio frequency chokes may seem to lack accuracy because the unit is measuring the inductance at a frequency that is below their designed operating range. The meter is giving accurate results, but at an inappropriate frequency. Readings obtained when measuring high frequency chokes must therefore be treated with a degree of caution. This is a problem that is common to most inductance meters and bridges incidentally, and it is not a shortcoming specific to this particular unit.



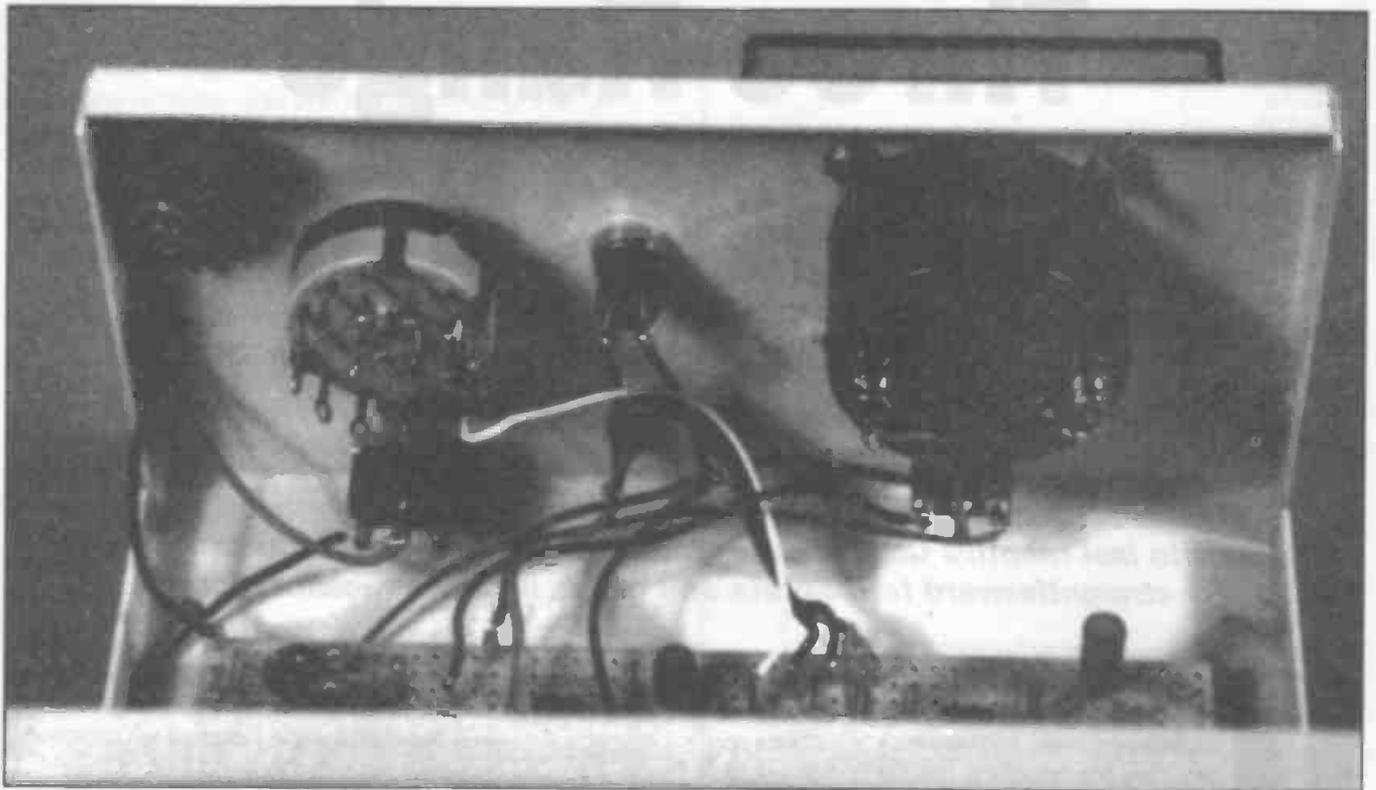

### System Operation

As can be seen from the block diagram in figure 1, the general make-up of the unit is quite similar to that of the companion capacitance meter project. It operates in essentially the same manner, but things have to be swapped around slightly in the amplifier stage at the heart of the circuit. This compensates for the fact that the impedance of an inductor rises with increased value, whereas the impedance of a capacitor reduces with increased value.

The oscillator stage of this circuit is simpler than the equivalent stage of the capacitance meter. As before, the accuracy of the unit depends on the oscillator providing a reasonably pure sinewave signal. In the capacitance meter, the oscillator operated at about 100Hz, and the sinewave signal was generated using a triangular waveform generator plus some lowpass filtering. In this case a much higher frequency of about 10kHz or so has to be used, because the impedance of the test components are impracticably low at lower frequencies. There is potentially some advantage in using a higher test frequency, but the operational amplifiers in the circuit do not perform well at much more than about 10kHz, and this was found to be a good compromise figure. The signal is generated by a Wien oscillator, which has the usual

thermistor stabilisation to ensure good results. Although simpler than the filtering method, using a Wien oscillator is more expensive. However, at the higher test frequency of 10kHz a Wien oscillator seems to give more consistent results.

An inverting amplifier receives the sinewave signal, and a negative feedback network governs the closed loop gain of this circuit. This is a two-section network that has one of three switched resistors forming the input arm. These resistors provide the unit with its three measuring ranges. The inductor under test provides the other arm of the negative feedback network. The voltage gain of the circuit is equal to the impedance of the test inductor divided by the resistance of the input resistor. At a fixed test frequency, the impedance of an inductor is proportional to its value. For example, if a 10mH inductor has an impedance of 10k, a 5mH inductor would have an impedance of 5k, and a 1mH inductor would have an impedance of 1k. Suppose the input resistance has a value of 10k, this would equate to voltage gains of 1, 0.5, and 0.1 with test values of 10mH, 5mH, and 1mH. Of more importance, if the output voltage were 1 volt with a 10mH choke, it would respectively be 0.5 volts and 0.1 volts with 5mH and 1mH chokes. In other words, the AC output potential is proportional to the value of the test component.

The output signal from the amplifier is fed to a precision half-wave rectifier and a moving coil meter. These form a simple but accurate AC voltmeter circuit that has good linearity. The meter responds to the output voltage from the amplifier, but as already explained this voltage is proportional to the value of the test component. With the right voltmeter sensitivity, test frequency, and so on, the meter will read directly in terms of inductance, and the scaling will be linear. This avoids the need for any

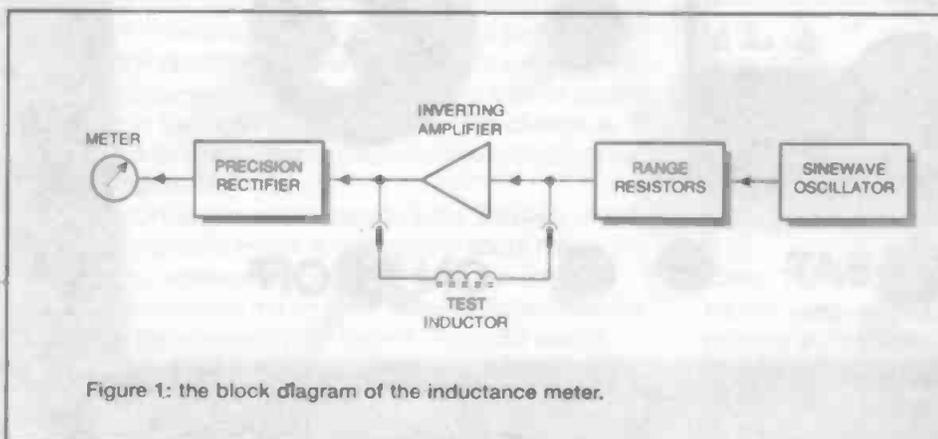


Figure 1: the block diagram of the inductance meter.

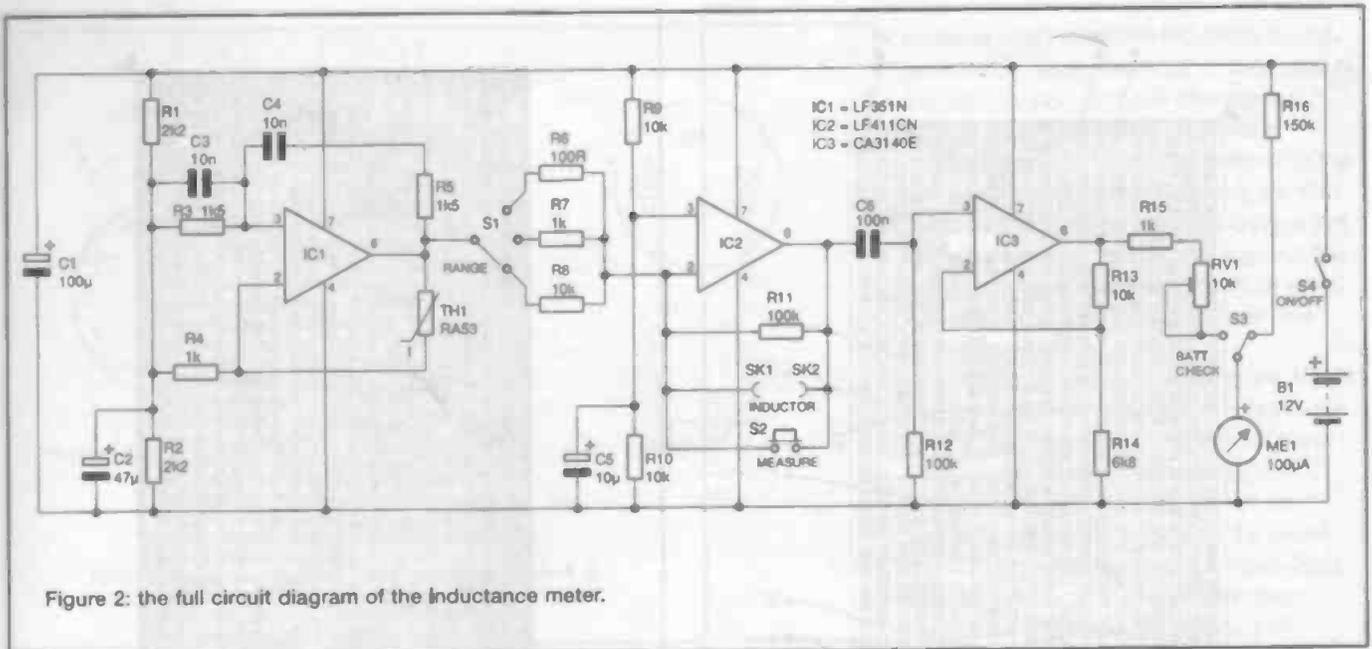


Figure 2: the full circuit diagram of the inductance meter.

recalibration of the meter's scale plate, and renders the calibration process very easy indeed.

### Circuit operation

The full circuit diagram for the inductance meter is in **figure 2**. The Wien oscillator uses IC1 in the conventional arrangement with the positive feedback provided by R3, R5, C3, and C4. These set the operating frequency of the sinewave oscillator at about 10.7kHz. Negative feedback is provided by R4 and TH1, with TH1 stabilising the output level of the oscillator. Precise control of the negative feedback is essential if a low distortion output signal is to be obtained. Slightly too little feedback results in strong oscillation, and the output signal becoming heavily clipped. Fractionally too much feedback causes the oscillator to stall and the output signal to cease.


Thermistor TH1 is the usual negative temperature coefficient type, which means that its resistance falls as its temperature increases. Unusually, it is a self-heating thermistor that is contained in an evacuated glass envelope so that it is, as far as possible, isolated from the ambient temperature. At switch on TH1 has a low temperature and therefore exhibits a high resistance. This gives relatively little negative feedback, high closed loop voltage gain from IC1, and strong oscillation. A strong current flow through TH1 results, causing its temperature to rapidly increase. This produces a reduction in IC1's voltage gain, and the oscillation decays to a low level. Now there is reduced current flow through TH1, its

temperature decreases, and the circuit oscillates more strongly. After a certain amount of seesawing, the output level tends to settle down and stabilise due to what is really a simple form of negative feedback action. The negative feedback stabilises the output level very efficiently, counteracting changes in output loading, the supply voltage, and so on. An output level of approximately one-volt RMS is produced at the output of IC1.

IC2 is the operational amplifier that forms the basis of the inverting amplifier stage. R6 to R7 are the three range resistors and S1 is the range switch. R6 to R8 respectively provide the 1mH, 10mH, and 100mH ranges. Using an inductor in the negative feedback of an operational amplifier tends to produce problems with instability, and can easily lead to strong high frequency oscillation. There are no major instability problems with this circuit, but it is necessary to include R11 to damp the test inductor slightly. Otherwise the circuit is apt to break into oscillation on the 100mH range. IC2 operates open loop with no test component in circuit, taking the meter beyond its full-scale reading. While this is unlikely to cause any damage to the meter, it is a possibility can not be completely ruled out. Therefore, S2 is used to place a short circuit across the test sockets until a test component has been connected across SK1 and SK2. S2 is then operated, removing the short circuit so that a reading can be taken.

The precision half wave rectifier is a very simple type that uses IC3 as a non-inverting amplifier. The circuit is basically just a standard DC non-inverting circuit, but IC3 does not have a negative supply rail. Consequently, positive input half cycles appear amplified at the output of IC3 in the normal way, but negative half cycles are not produced because the output of IC3 can not go negative of the 0 volt supply rail. The output signal from IC3 is therefore a slightly amplified and half-wave rectified version of the input signal. This signal is used to drive a simple voltmeter formed by R15, RV1, and ME1. RV1 enables the sensitivity of the voltmeter to be varied, and this enables the unit to be calibrated.

With S3 set to the right hand position ME1 operates as a simple voltmeter which measures the battery voltage. The full-scale sensitivity of this circuit is nominally 15 volts. This provides a simple battery check facility, and the unit will only produce accurate results if the supply potential is more than about 10 volts. The current consumption from the 12-volt

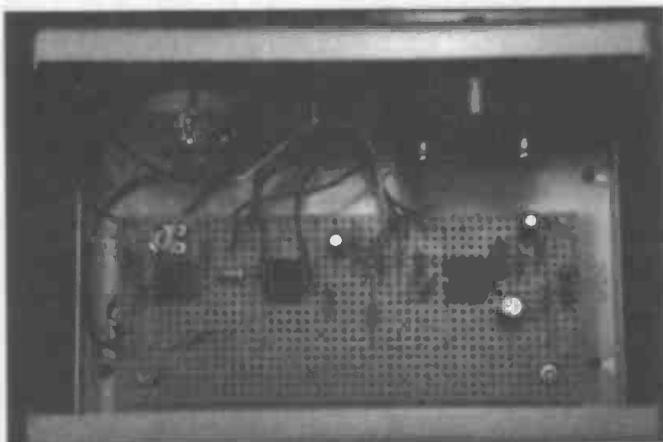

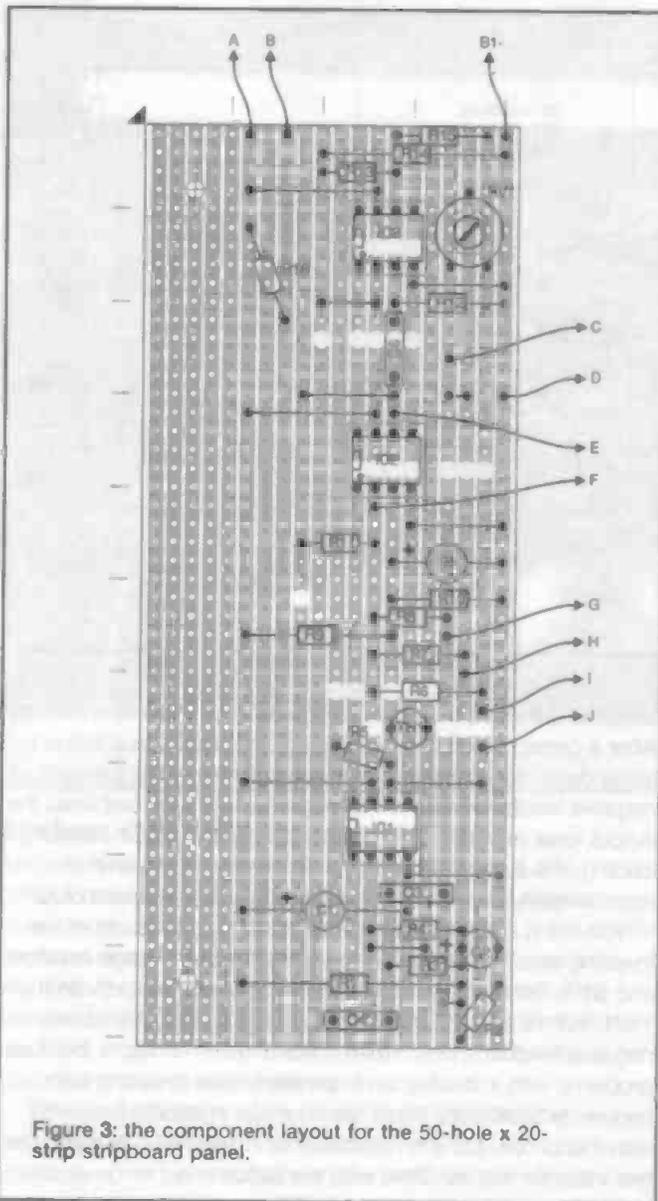


Figure 3: the component layout for the 50-hole x 20-strip stripboard panel.

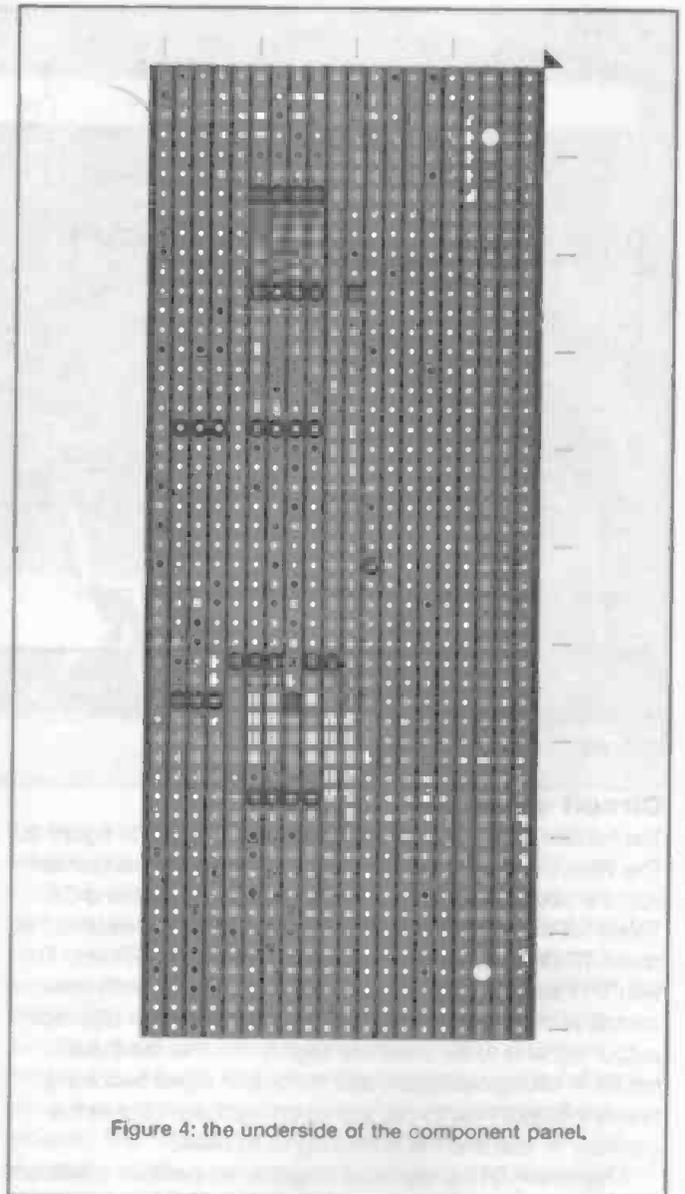


Figure 4: the underside of the component panel.

battery supply is about seven or eight milliamps, which gives an extremely long battery life. Note that a regulated supply is unnecessary because the thermistor stabilisation prevents the output level from IC1 changing significantly with variations in the supply voltage, and the closed loop voltage gains of IC2 and IC3 are also independent of the supply potential.

Constructors of this project should note that the operational amplifiers used in this device were chosen after careful consideration, and are not random choices. The device used for IC1 must be capable of providing a good quality sinewave signal at 10kHz into a fairly low load impedance. The amplifier used in the IC2 position must have high enough performance to give good results, but should not be so lively that instability becomes a major problem. It must also be capable of stable operation with less than unity voltage gain. The device used for IC3 must be a type that is suitable for use in a single supply rail DC amplifier circuits. Using alternative devices for any of the operational amplifiers in this circuit is likely to result in it failing to work properly.

### Construction

This circuit is simple enough for stripboard construction, and a suitable layout is provided in figures 3 and 4. These respectively show the component and copper side views of the

board, which measure 50 holes by 20 copper strips. Construction of the board follows along the normal lines, with a board of the correct size being cut out, the necessary breaks being made in the copper strips, and the two 3.2 millimetre diameter mounting holes being drilled. The components and link-wires are then fitted. The CA3140E used for IC3 is the only static-sensitive component, but I would recommend using holders for all three integrated circuits. Resistors R6, R7 and R8 should have a tolerance of 1 percent so that good accuracy is provided on all three ranges. Thermistor TH1 has a glass encapsulation that makes it relatively fragile, and it should therefore be handled with care. It is probably best to fit this component last of all. The RA53 thermistor is also available as the R53, and either will work properly in this circuit. It is quite an expensive component, and it seems to be worthwhile shopping around to find the best price.

The prototype is built into a small metal instrument case of the same size and type that was used for the capacitance meter project. The general layout of the unit is much the same as for the capacitance meter project, and the front panel layout is virtually identical. The only difference is that pushbutton switch S2 has been added between the range switch and the panel meter (see the accompanying photographs). Note that S2 is a push-to-break switch, and not the more common

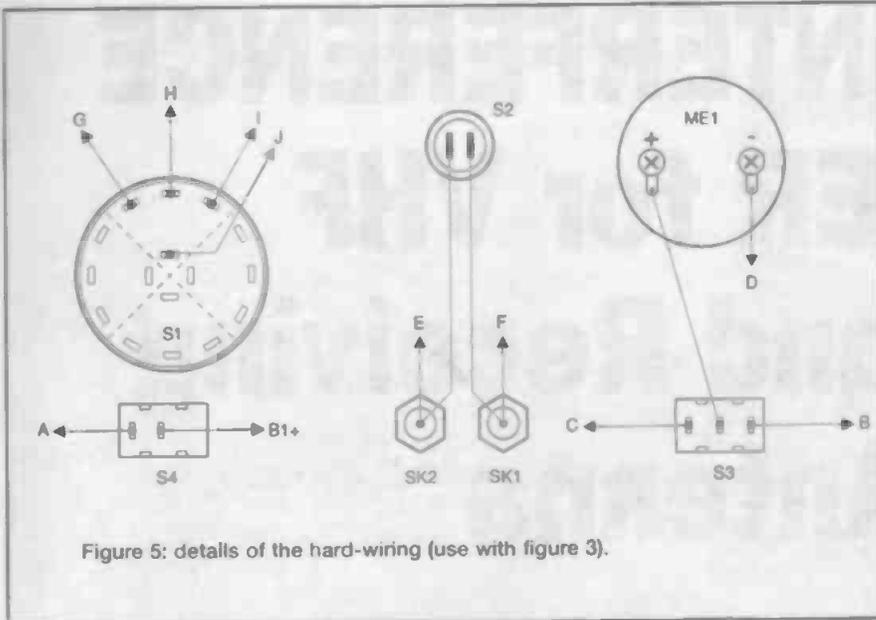


Figure 5: details of the hard-wiring (use with figure 3).

push-to-make variety. In general the exact layout used is not critical, but try to keep the leads from the circuit board to the test sockets (SK1 and SK2) as short as possible.

Details of the hard wiring are provided in figure 5, which should be used in conjunction with figure 3 (for example, point "A" in figure 3 connects to point "A" in figure 5). This wiring is straightforward and should not present any problems. S1 is a standard three-way four-pole rotary switch, but in this circuit only one pole is used and 12 of its tags are left unconnected. The battery pack consists of eight HP7 (AA) size cells fitted in a plastic holder. There is just about enough space for the batteries inside the case, but the holder will probably have to be fixed to the rear panel or top of the case using double-sided adhesive pads. Do not simply leave the battery pack rattling around inside the case, as it would probably damage thermistor TH1. Connections to the battery holder are via an ordinary PP3 size battery clip.

Many inductors will connect direct to SK1 and SK2 without any difficulty, but some components have very short pins rather than leads. It can be quite difficult to make the connections to these, and the best solution is to make up a pair of test leads fitted with the smallest crocodile clips you can obtain. Alternatively small probe-clips can be used. The test leads should be as short as reasonably possible so that they add a minimal amount of inductance in series with the test components.

It is not difficult to remove the scale-plate of the meter and add figures to suit the 1mH and 10mH ranges (the existing 0-100 scale is correct for the 100mH range). Normally the front cover of a panel meter simply unclips, and removing two tiny screws then frees the scale-plate. Rub-on transfers can then be used to add the new numbers. As it is not difficult to mentally convert readings on the 1mH and 10mH ranges into measured values, and moving coil meters are easily damaged, it is probably not worth the risk and effort involved in altering the scale-plate. If you do decide to modify the scale-plate, proceed very carefully. In particular, avoid touching the meter's pointer and try not to get any dust into the meter movement.

### Calibration and use

Ideally the unit should be calibrated against a precision inductor having a tolerance of one percent or better. In practice a lower tolerance component will probably have to be used

because close tolerance inductors do not seem to be readily available. In fact most of the inductors currently on offer have a tolerance rating of some 10 percent. Probably the best choice for calibrating the unit is a 10mH type 8RB inductor (as sold by Cirkit Distribution Ltd.). This component has a five percent tolerance rating, but five percent is the guaranteed maximum error. Actual components tested were all well within the tolerance limits.

To calibrate the unit set S1 to the 10mH range (the middle setting) and connect the 10mH calibration component to SK1 and SK2. With S3 set to the "inductance" position, press S2 and adjust RV1 for precisely maximum reading on the panel meter. The unit is then ready for use. Bear in mind the warning given earlier about testing high frequency inductors. With these components the measured value at

10kHz is likely to be slightly different to the marked value.

## PARTS LIST for the Inductance meter

### Resistors

All 0.25W 5 percent metal film-unless noted otherwise

R1,2	2k2
R3,5	1k5
R4,15	1k
R6	100R 1 percent
R7	1k 1 percent
R8	10k 1 percent
R9,10,13	10k
R11,12	100k
R14	6k8
R16	150k
RV1	10k min hor preset
TH1	RA53 or R53 thermistor

### Capacitors

C1	100u 16V radial elect
C2	47u 16V radial elect
C3,4	10n polyester
C5	10u 25V radial elect
C6	100n polyester

### Semiconductors

IC1	LF351N
IC2	LF411CN
IC3	CA3140E

### Miscellaneous

S1	3-way 4-pole rotary (one pole used)
S2	Push-to-break switch
S3	SPDT min toggle switch
S4	SPST min toggle switch
B1	12 volts (8 x AA size cells in holder)
ME1	100uA moving coil panel meter
SK1,2	1mm or 2mm sockets
Metal instrument case about 152 x 105 x 75mm, 0.1 inch stripboard with 50 holes by 20 copper strips, battery connector (PP3 type), control knob, 8-pin DIL holder, wire, solder, etc.	

# RADIO INTERFERENCE FILTER for VHF High-Band Receiving Antenna

**Reception can easily be swamped by legitimate strong transmissions nearby, particularly by radio-paging. This filter has reduced the problem dramatically for designer E Chicken MBE F1EE G3BIK.**


**T**his article describes a low-cost filter of straightforward construction, designed to remove or substantially reduce destructive interference from strong local transmissions in the 120-150MHz range, such as interference to amateur radio reception in the 2-metre band, or to reception of weather-satellite or air-traffic signals.

## "Swamped"

In some parts of the UK, legally authorised radio transmissions on frequencies close to the edge of the 144MHz amateur band can make reception of amateur transmissions difficult due to close-proximity swamping effects. For example, in my own locality, reception of 2-metre low-level signals from the Russian space-craft MIIR suffers badly from a nearby Home-Office radio tower. This does not imply that such transmissions are in any way at fault. It is simply a technological fact of life that the rf input stages of even the best receivers can be swamped by strong local transmissions, especially on adjacent frequency bands. Similar problems can also be encountered if you enjoy listening to air-traffic signals. And if you were to mention the word "radio-pager" in the presence of the 2000 or more UK weather-satellite receiving enthusiasts, you might be told in no uncertain terms to go wash your mouth out!

The reason for this powerful aversion to modern paging systems among 137-MHz weather buffs is that since that band was assigned to digital paging in the UK, weather picture signals from low-orbit satellites have been suffering severe interference throughout the UK. The very nature of the pager transmissions, coupled with the nationwide distribution of their radio-sites, has made this a very difficult problem to deal with, to the point where NASA may have to change a frequency on its proposed new weather satellite.

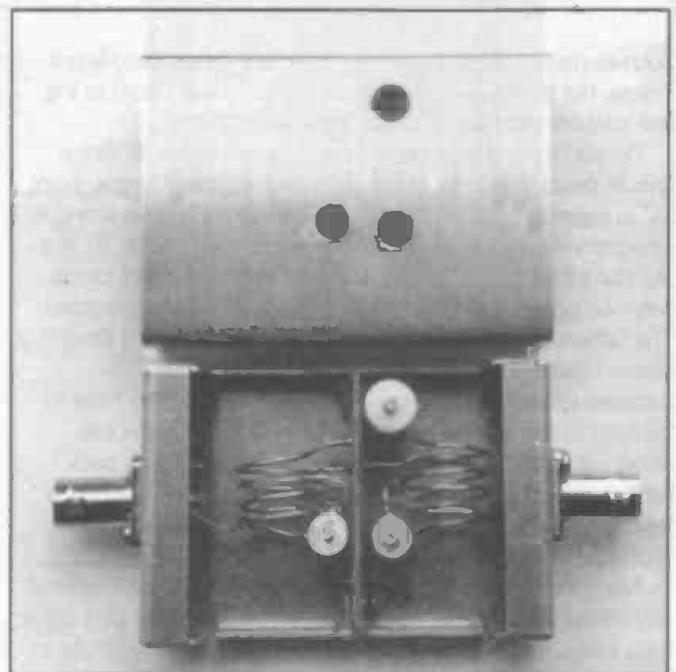Many long-established weather-satellite receivers have had




The interior of the interference Filter

to be redesigned to combat this new and destructive interference. In truth, my own receiving set-up does not suffer too badly, but only because it is a modified ex-pmr commercial receiver of very high technical specification with a highly selective multi-stage tuned rf input circuit and very narrow IF bandwidth. Although its narrow bandwidth causes some loss of detail on the received images, in practice the definition of cloud and land has up to now been adequate for my purposes.

Recently, however, following the announcement of extra frequencies for further planned satellites, and bearing in mind the cost of extra crystals for my ex-pmr set, I decided as an experiment to modify a domestic VHF FM radio-tuner bought as a bargain at the local car-boot sale. I re-tuned it to receive 137-MHz weather satellite transmissions.

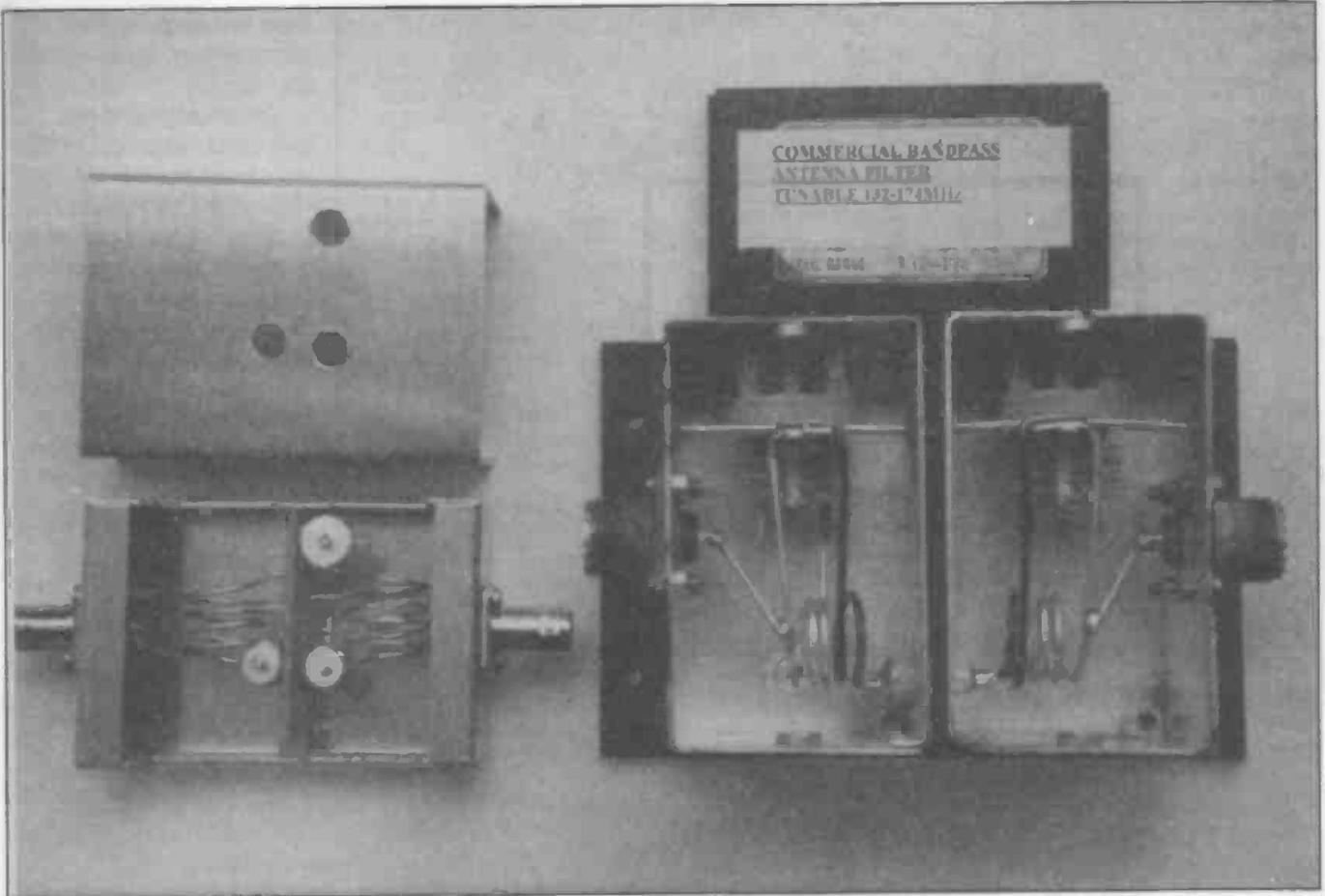It was a quality product with a tuned rf stage preceding the tuned mixer, and the usual upper limit of 108 MHz prior to modification. Results were encouraging, with sensitivity sufficient to give full background quietening by the satellite fm signals, but, alas badly disrupted by radio-paging



A good commercial filter beside the Interference Filter giving a size comparison. An unusual feature of our design is the third trimmer capacitor, which can resonate the link-loop itself for optimum signal transfer at the required frequency.

transmissions even though my nearest tower is some 1.5km away! Now I knew how my fellow Wefax enthusiasts really felt!

The problem of co-channel interference is not in itself new. It is and has always been of major proportions on commercial radio-communication sites, where receiving antennas have to share the same tower as transmitting antennas on adjacent frequencies. One effective and often-used cure to that problem is the installation of a sharply tuned band-pass filter such as that illustrated in figure 1, in line with the receiving antenna's coaxial feed-cable at the point where it connects to the receiver. Based on that knowledge from my professional experience, a similar filter was constructed using readily available low-cost components at a total outlay of about £6 at 1998 prices. This totally cleaned up reception on my

2metre amateur-band receiver.

The filter also removed the last vestige of radio-pager interference to weather image reception on my modified ex-prmr receiver, and it even allows reception of acceptably clean weather images from my bargain-priced retuned domestic fm receiver. As with all filters, there is some slight insertion loss on the signals of interest, but not enough to cause concern, as the advantage far outweighs any disadvantage.

### The circuit

Figure 1 gives the circuit diagram of the filter, which is fully reversible, with the antenna coax feed-line connecting to one end and the receiver to the other via a short coaxial jumper-lead with suitable plugs. It consists of two separate but identical parallel-resonant LC circuits each tuned to, for example, 145MHz for use on the 2-metre amateur band, or 137.5MHz, which is about mid-band for weather-satellites and is one of the most used frequencies. A metallic screen electrically separates the two tuned circuits L1/C1 and L2/C2, and the required incoming signal is transferred from one to the other by means of a closed loop. This consists of two single-turn link-coils L3 and L4 connected in series, each of which is inductively close-coupled to one of the resonant circuits.

An unusual feature of this design, which makes it different from a typical commercial version, is the addition of a third trimmer capacitor C3 whereby the link-loop itself can be resonated for optimum signal transfer at the required frequency. This also ensures maximum rejection of the radio-pager or other interfering signals.

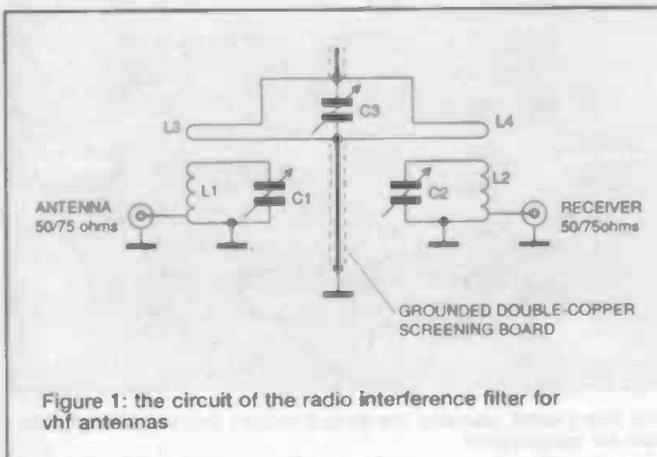


Figure 1: the circuit of the radio interference filter for vhf antennas

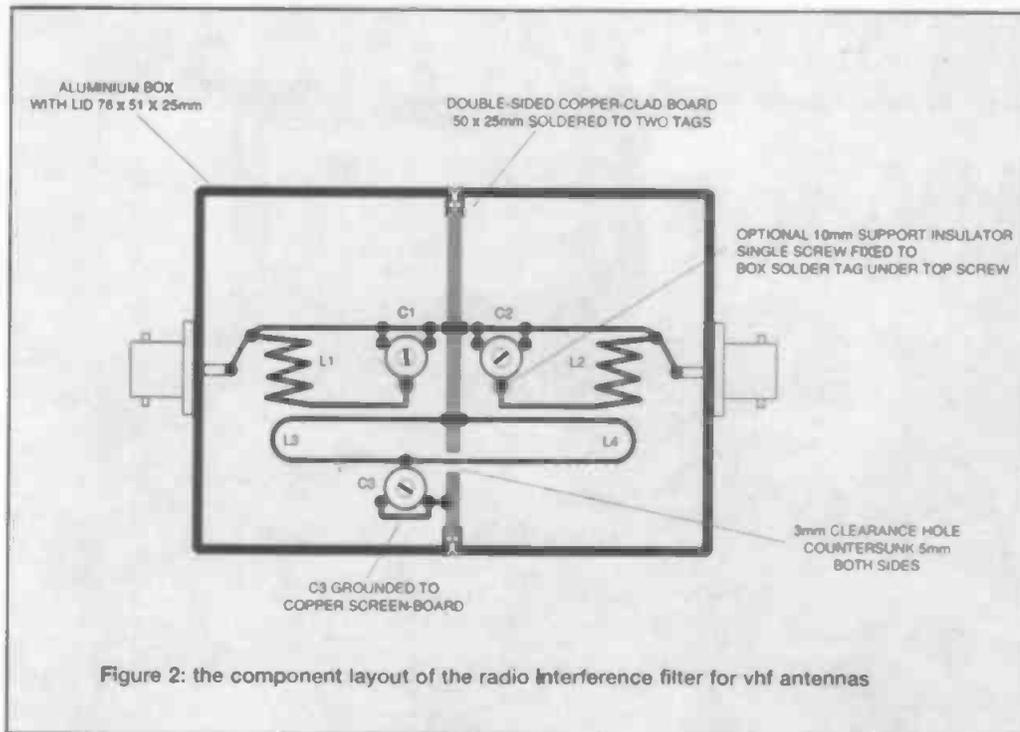


Figure 2: the component layout of the radio interference filter for vhf antennas

The design of the filter assumes that the receiving antenna for the vhf high-band receiver uses coaxial cable of characteristic impedance in the order of 50 to 75 ohms. This is impedance-matched into and out of the filter by tapping onto the tuned-coil at a low-impedance position close to its grounded end. The actual position of the tap is not unduly critical.

## Construction

Drills of sizes 1, 2, 3, 5, and 7mm are needed. The prototype filter was contained in an aluminium box of size 76 x 51 x 25 mm (3 x 2 x 1 inches) with a removable lid. Mounted centrally on each end face of the box is a 50-ohm BNC or uhf coaxial socket chosen by you to suit your own receiver.

A 50 x 25-mm piece of double-sided copper-clad pcb laminate board serves both as the inter-screen for the tuned circuits, and the mounting-plate for the coils and capacitors. The board is secured and grounded at its two bottom corners by soldering each to a pair of solder-tags on the box sides. These tags are longer than their 6mm fixing-bolts, which allows the board to be gripped between them before soldering to both copper faces. Countersunk bolts are used to avoid mechanical conflict with the lid. Fixing of the lid is provided by drilling 2-mm holes through the lid and side-plates of the box to accommodate self-tapping screws. Two screws should be sufficient, one at each diagonal side.

Before soldering the screening board into the box, the component fixing-holes must be drilled as described in figure 3 using a 1-mm drill which provides a neat fit for the 20swg wires, and then the four coils and three trimmer capacitors fitted onto the board and soldered into place. Figure 2 gives guidance for mounting of the components, but positioning is not critical, as the wire tails of the coils can easily be bent in situ to suit your particular layout.

Four coils of 12-mm inside-diameter need to be wound with 20swg tinned copper wire, after first having straightened the wire by pulling it through a soft cloth. Coils L1 and L2 are each of three turns plus tails of about 25mm, with the turns spaced to give a span of 12mm. Link-coils L3 and L4 are

each one single 12-mm diameter turn, again with 25-mm tails.

Temporarily bend one wire tail of coil L1 out of the way, insert its other tail through the appropriate hole with the coil horizontal, and solder the wire to the copper on both sides of the board. Cut off any surplus tail wire. From the opposite side of the board, do the same with the other coil L2.

Solder the two common-tags of the green-coloured 22pF trimmer capacitor C1 to the grounded tail of coil L1, with the adjusting slot facing upwards and the centre-tag pointing inwards. With fine-nosed pliers, carefully bend the free tail of coil L1 and cut it to length such that it can then be

soldered to the centre-tag of trimmer C1. Do the same with the trimmer C2 and coil L2 on the other side of the board.


This self-supporting coil capacitor method is mechanically adequate. Optionally but not really necessary, extra mechanical support for each centre-tag/coil junction can be provided by means of a 10-mm insulated-spacer, single-hole fixed to the bottom of the box by an M3 bolt. A solder-tag bolted to the spacer's free end would then serve as a firm anchor point for the solder joint.

One tail of each single-turn coil coupling-loop L3 and L4 is grounded by passing it through a hole in the board, and soldering it to both copper faces. Note that the 3-mm clearance-hole, through which the other tail of each loop passes, is countersunk with a 5-mm drill on both sides of the board to trim back the copper-plane so as to prevent the wires from touching it. These two tails are soldered together on each side of the hole, but not to the board itself. Each loop is then physically adjusted to be closely parallel to, but not touching, its associated coil L1 or L2.

Now solder the yellow-coloured 65pF trimmer capacitor C1 into position on one side of the screen. The choice of side



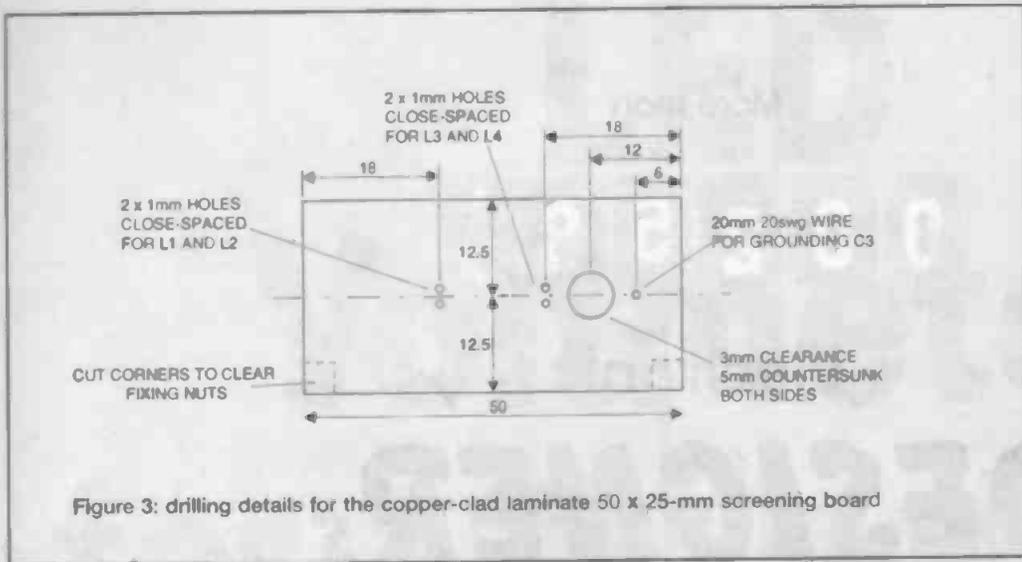The filter boxed, showing the three trimmers and an old-style 50pF coin for comparison!



It should be noted that, because of the filter's very high selectivity, it may not be possible at first to hear the off-air signal through the filter before it has been tuned, so using a signal generator may be the best option. However, if a signal generator is not available, adjustment of the filter on an incoming radio signal in the band 120.450MHz can be simplified as follows:

Remove the filter-lid. Set all three trimmer vanes to mid-mesh. Connect the antenna to the receiver and listen for,

is not important, but the trimmer should sit snugly against the copper with its adjusting slot upwards, and the centre-tag facing inward. The trimmer's two common-tags are soldered to the short piece of 20swg grounding wire which is soldered through the board at 6mm from the edge, as shown in figure 3. The centre-tag should be in contact with and soldered to the union of the two link-loops, close to where they pass through the clearance-hole in the board.

Fit the assembled screening-board into the box with each corner gripped between a pair of solder-tags, then solder the tags to both copper faces. It will be necessary to snip each corner to clear the solder-tag fixing nut. If necessary, shorten the two socket-pins to avoid unintended contact with the coils, then solder a wire link from each pin to the turn nearest the earth end of its own coil.

Finally, drill three 7-mm diameter holes in the top face of the lid located so as to give clearance-access to the adjusting slot of each trimmer. An easy way to determine the drilling points is to press a thin layer of Plasticine or wax on to the inner surface of the lid and to gently press it down on the trimmers. This leaves a clear impression of the trimmer adjusting-slots in the Plasticine, which can then be used as a drilling template. After drilling the trimmer adjustment-holes, set the moving plates of each trimmer capacitor to about mid-way, then fasten the lid into place.

### Installing and tuning the filter

The filter must be connected between the antenna and the receiver, as close to the receiver's antenna input socket as possible. The antenna's coaxial lead plugs into either end of the filter. A short length of 50-ohm coaxial cable fitted with an appropriate 50-ohm plug at each end is required to make the connection between filter and receiver. The only adjustment necessary, is to tune each of the three trimmer capacitors for maximum received signal strength with the receiver set to say the local repeater channel for 2 metres, or to 137.5MHz for weather-satellite use. For convenience, a signal-generator should be used as the signal source. It should preferably be a tone-modulated vhf fm signal generator of 50-ohm output impedance, but a dip-oscillator would suffice. Alternatively, the 2-metre repeater or weather-satellite signal itself could be used.

It is very important that an insulated trimming tool is used on the trimmers, not a screwdriver. When tuning is completed, label one socket as Antenna and the other as Receiver.

say, the 2-metre repeater signal, or air-traffic signals on or about 120MHz, or weather satellite signal on 137.5MHz. The latter would best be done during an overhead pass, when the satellite can be heard for 15-20 minutes. While the required signal is present, disconnect the antenna from the receiver, leaving the antenna cable unconnected. Connect the filter to the receiver, then touch the free antenna plug onto the adjusting slot of the yellow 65pF trimmer, allowing the signal to be heard. Adjust the green 22pF trimmer nearest the receiver socket for maximum signal. Now touch the antenna plug on to the adjusting slot of the other green 22pF trimmer, and adjust the yellow 65pF loop-trimmer for maximum signal. Connect the antenna plug to its own socket on the filter, and adjust its nearest green 22pF trimmer for maximum signal. Refit the lid and give a final adjustment for maximum signal to each of the three trimmers.

## PARTS LIST

### Radio Interference Filter

C1	5-65pF miniature film*trimmer Maplin WL72P
C2, C3	2-22pF miniature film trimmers Maplin WL70M (Adjust each for maximum required signal.)
L1, L2	12-mm dia. 20swg tinned-copper wire single-turn links
L3, L4	12-mm dia. 20swg 3 turns each, spaced to 12-mm span
SK1, SK2	50-ohm square socket, bnc or uhf 50239 Maplin YW00A or BW850

2 x 50-ohm twist-on plug, bnc or PL259 to suit receiver, Maplin JK21X or HL9SD; 2 x M3 6mm bolt and nut, countersunk, Maplin BF36P; 4 x M3 20-mm bolt and nut, pan-head, Maplin JY22Y; 6 x M3 solder tag, Maplin LR64U; 2 x 10-mm insulated spacer (optional), Maplin FS36P; 0.5-m 50-ohm 5-mm UR76 coax cable, fitted each end with appropriate 50-ohm plug; 50mm x 25mm double-sided copper-clad laminate pcb board, Maplin FA5SK; 0.5m 20swg tinned copper wire, Maplin BL13P; aluminium box with lid, 6 x 51 x 25mm (3 x 2 x 1 in), Maplin AB12; preset trim-tool, Maplin BR491.

Maplin catalogue numbers are given for guidance only, and any suitable alternatives can be used with confidence.

More than

0 0 2 5 8

Electronic

**DESIGNERS**

know how to get their

**PROTOTYPE PCBs**

from their **usual manufacturer** for a

**FRACTION** of the **COST!**

DO YOU ?

STOP WASTING YOUR MONEY!

CALL NOW: 00353 65 66500

**Beta**  
LAYOUT  
**PCB-POOL®**

**get**  
**connected**

pcbpool@betalayout.ie  
<http://www.pcb-pool.com>



**FAX**  
on-Demand  
66515

**EURO**  
File-Transfer  
66520

**analog**  
BBS  
66516

**ISDN**  
BBS  
66518

☎ 00353 65 66500  
FAX 66514

# LED Voltmeter for 12V battery


*If 12-volt leisure batteries are run down very far, their life-span decreases dramatically. Terry Balbirnie's four-LED charge-state indicator helps to monitor battery health.*

**T**welve-volt "leisure" batteries are the standard power source for equipment in a caravan or boat. They are used to operate the low-voltage appliances such as lights, water pump, television, etc. This type of battery is also used by radio amateurs to operate transmitting equipment in remote locations and by those taking environmental measurements in the field. When used in conjunction with an inverter, they also serve to provide a 240V 50Hz supply for mains equipment, such as computers, where no actual mains supply is available.
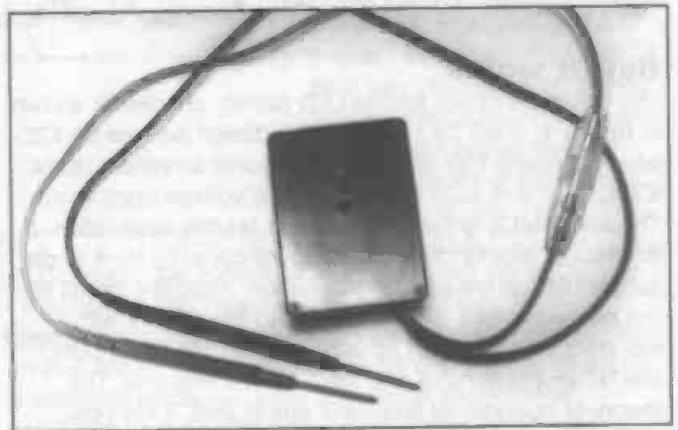
## How to kill a battery

Leisure batteries are a member of the lead-acid family. The most familiar one is the car battery. However, leisure batteries are specially designed for cyclic use, whereas a car battery is used chiefly in float mode. Cyclic means that the battery is run down significantly before re-charging. In float mode only a small fraction of the total charge is drawn at any time. The battery is then re-charged at a low rate and over a prolonged period - even continuously - as in the back-up supply for a burglar alarm. Batteries designed for float applications may be cycled occasionally, such as when the car fails to start in the winter and it runs flat. Car batteries, however, are not designed for cyclic use and will fail fairly quickly under such conditions - hence the need to buy the correct product and to avoid using a cheap car battery for any of the purposes mentioned earlier.

Even a leisure battery will fail much more quickly if it is regularly discharged to its rated low point. Typically, if a battery is only run down by one-third of its total charge, it may be expected to cycle some 1000 times. If the depth of discharge is 50%, this figure falls to some 500 times. If it is run down to its low point, the life may be expected to drop to some 100 to 200 cycles only. This is not always appreciated by users.



## Deep discharge

Lead-acid batteries suffer from one major disadvantage: they must always be maintained in a satisfactory state of charge. If they are allowed to run down below the rated low point, permanent damage is likely to occur. The battery will then fail to accept a full charge. Under extreme conditions of "deep" discharge such a battery will be completely ruined, especially if it has been left that way for some time. It is interesting to note that a battery left with a terminal voltage of less than about 12.3V (50 percent charge) will slowly deteriorate anyway.

Although leisure batteries are described as having a 12V output, this is only an average figure. A fully-charged battery will develop an off-load voltage of some 13V irrespective of size or manufacturer. As the battery is run down, the terminal voltage falls. At 12.3V, some 50 percent of the charge remains. At about 11.7V it may be considered flat, even though some charge still exists. Below about 11.5V the battery is in a dangerously low state and must be re-charged as soon as possible. The state of a battery could therefore be found by using a digital voltmeter. However, some non-technically minded

people would find difficulty interpreting the readings, and many would not wish to use their expensive instrument for this purpose anyway.

### Thermometer display


Most of the time, the user simply wishes to know the approximate state of the battery, and this battery check circuit fulfils that need. On the front panel of the unit are four LEDs (light-emitting diodes) arranged thermometer-fashion. The colours used are green, yellow, orange and red to indicate "good", "serviceable", "poor" and "flat" respectively. These will operate in turn when predetermined voltages are applied to the input. There is, of course, a further state where none of the LEDs are on. This indicates the point when the type of rapid damage referred to above is likely to occur.

The circuit is powered from the battery being monitored, drawing about 1.5mA plus a further 15mA for each illuminated LED. Thus, when all four LEDs are glowing (battery fully charged) the total requirement is a little over 60mA. The device should not be left connected permanently to the battery because even this small drain would eventually run it down. A large battery of 60Ah capacity would take several weeks to do so but a small one of, say, 1Ah capacity would take only a few hours. The intention is that the meter is used every now and again to monitor the condition of the battery.
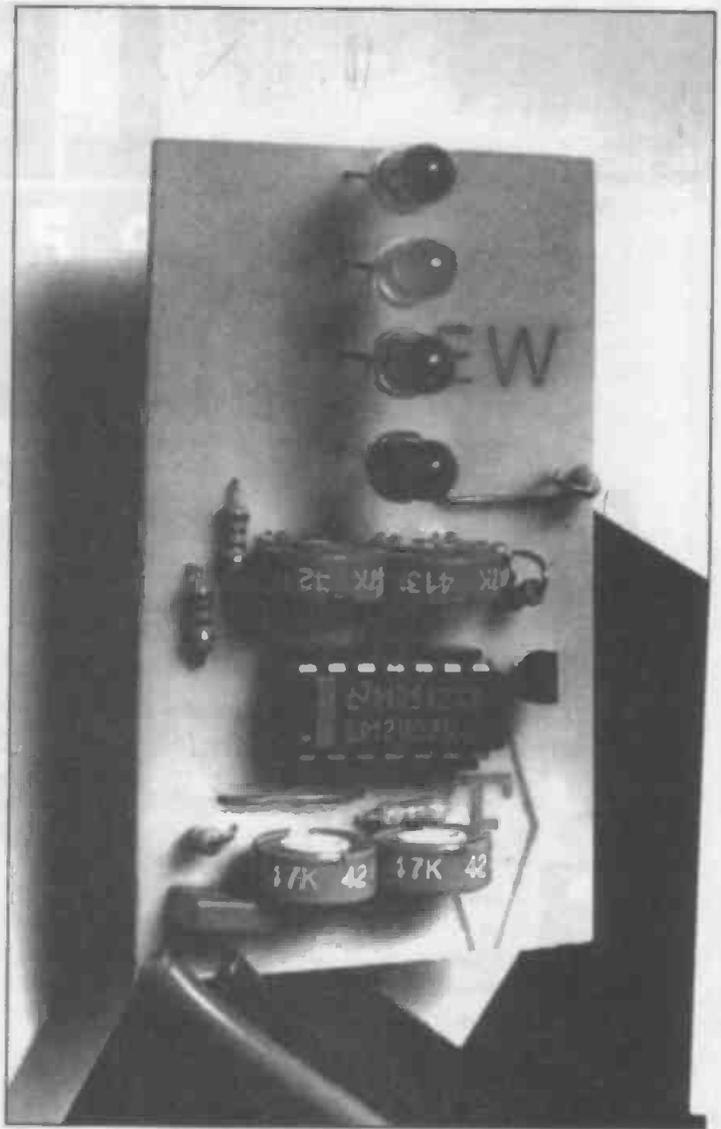
### How it works

The complete circuit for the LED battery checker is shown in figure 1. It will be seen that the design centres on IC2, which contains four identical operational amplifiers, IC2a, IC2b, IC2c and IC2d each used as a voltage comparator. The specified ic is particularly good for this application. It is a robust bipolar device and works correctly from single supply rails as are used in this circuit. Also, the circuit will not be damaged if it is connected to the battery with incorrect polarity. Each op-amp section has two inputs, the "+" (non-inverting) and the "-" (inverting) one. The theory of operational amplifiers states that, if the non-inverting input voltage at any unit exceeds the inverting one, the appropriate output will be on.

The circuit is connected to the nominal 12V battery through fuse, FS1. A supply is then provided to the 5V reference device, IC1. This operates in conjunction with load resistor, R3, to give a precise 5V between its ends. IC1 may be regarded as a superior type of zener diode and is represented by the same symbol. This reference voltage is connected to the inverting inputs of all four op-amps (pins 2, 6, 9 and 13). Meanwhile, each non-inverting input (pins 3, 5, 10 and 12) receives a voltage dependent on the adjustment of presets RV1, RV2, RV3 and RV4 respectively. These are connected as potential dividers and they operate in conjunction with fixed resistors, R1 and R2 which are common to all units. The purpose of these resistors is to narrow the range of adjustment of the presets so that they are more easily adjusted at the end. To make the operation clear, suppose RV1 is adjusted so that exactly 5V exists at IC2d non-inverting input, pin 3, when the battery supply is 11.8V (i.e. a poorly-charged battery). Suppose also that the other presets are adjusted so that each non-inverting input develops 5V with supply voltages of 12.2V (IC2c), 12.5V (IC2b) and 12.8V (IC2a) - that is, increasing states of charge.



Suppose the battery is in a very poor state of charge and only 11.5V exists between its terminals. It will be seen that all the non-inverting input voltages are less than 5V. None of the op-amp outputs will be on and therefore all LEDs will be off. Now suppose that the battery voltage just exceeds 11.8V. The voltage at pin 3 rises above the 5V reference at pin 2 so IC2d output, pin 1 is high. Thus, the red light-emitting diode, LED1, will operate via current-limiting resistor, R4. In a similar way, as the battery voltage rises above 12.2V, 12.5V and 12.8V, the non-inverting inputs of IC2c, IC2b and IC2a will exceed the 5V reference existing at the inverting ones. Thus, orange, yellow and green light-emitting diodes LED2, LED3 and LED4 will operate in turn via the appropriate current-limiting resistor. By adjusting the presets to the required working voltages at the end of construction, the colours will show at predetermined points and the device will behave as a narrow-scale voltmeter.

The op-amps are used without positive feedback. This means that the switching action will not be sharp. In other words, the LEDs will come on and go off gradually over a small range. For the present purpose, this does not matter.

### Construction

Construction is based on a single-sided printed circuit board (PCB) and the component overlay is shown in

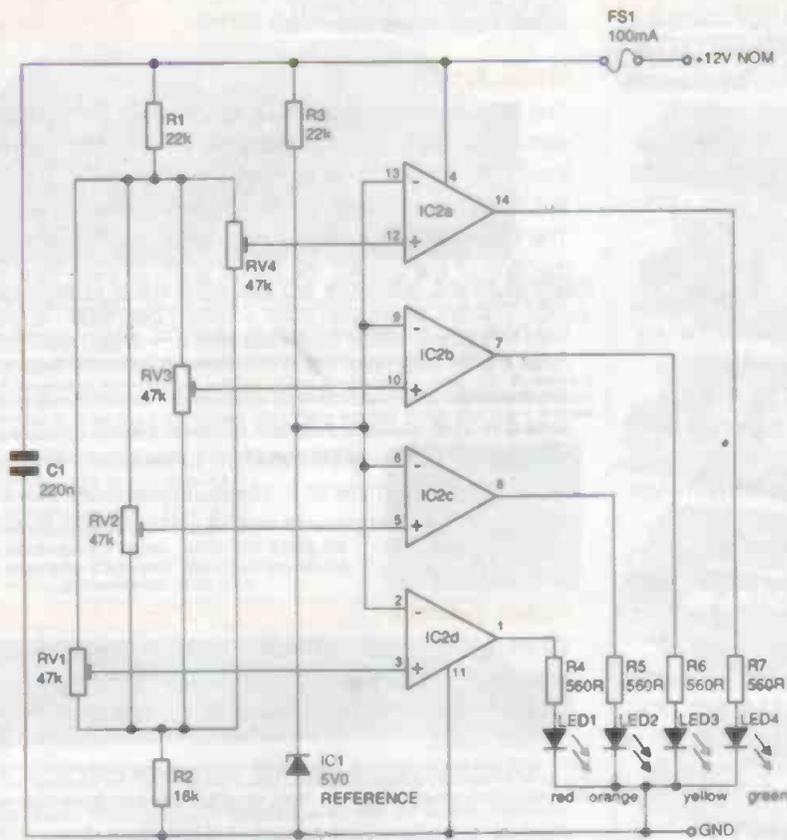


Figure 1: the circuit of the LED voltmeter battery checker

they appear neat in the finished device. Take IC1 and, holding it so that the flat face is towards you and with the leads pointing upwards, cut off the right-hand end one close to the body. This lead is connected to the substrate and has no effect if left unused. Solder the two remaining leads in position with the flat face of the ic towards the lower edge of the PCB.

Solder test probes to the points labelled "+12V nom" (nominal) and "gnd". The +12V one should be red and the "gnd" one, black. These could be easily made. However, in the prototype unit, a pair of inexpensive meter leads was used with the 4mm plugs cut off the other end. These give a more professional appearance. Connect the in-line fuseholder in the positive lead as shown in the photograph. Adjust the presets as follows: RV1 and RV2 fully clockwise; RV3 and RV4 fully anti-clockwise. These adjustments are as viewed from the edges of the circuit panel (that is, not from IC2 position)

**figure 2.** Begin by soldering the ic socket and two link wires in position. Follow with all the resistors (including the four presets) and capacitor. Solder the LEDs in place taking care over their orientation (the cathode end is marked "k" in figures 1 and 2). Note that with LEDs 1 and 4, the cathode end is connected to the lower track on the PCB whereas with LEDs 2 and 3 it is the upper one - If the polarity is incorrect, the LED will not work. The tips of the LEDs should stand approximately 20mm above the circuit panel and should all have exactly the same height so that

Complete the construction of the circuit panel by inserting IC2 into its socket, taking care over the orientation. Insert the fuse into its holder. This should have a value not exceeding 100mA. Note that the use of a fuse is essential because, under accidental short-circuit conditions, a lead-acid battery can deliver an enormous current. This could cause wires to become red hot and result in burns or even fire. Also, in the event of connecting the probes to the battery with incorrect polarity, a larger current than normal will flow. If left for more than a second or so, the fuse will blow. The op-amp and voltage reference ic seem to survive, however.

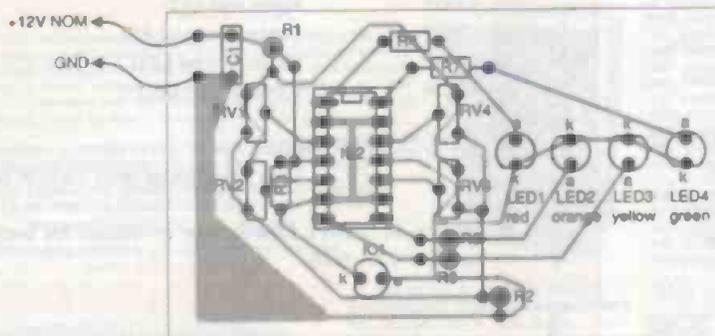


Figure 2: the component layout of the LED voltmeter battery checker

more than a second or so, the fuse will blow. The op-amp and voltage reference ic seem to survive, however.

### Adjustment and testing

If you have a continuously variable power supply unit and a digital voltmeter available, you could adjust the circuit with the aid of these. If you do not have this equipment, adjustments may be made by discharging the battery under controlled conditions. This takes longer but will probably produce better results because they are based on real experience.

If you are using the power supply method, connect its output (observing the polarity) to the input

probes on the unit and also to the voltmeter. Set the output of the power supply unit to 12.8V and adjust RV4 using a trimming tool or small screwdriver so that the green LED is just completely off. Reduce the voltage to 12.5V and repeat with RV3 until the yellow LED is just off. Repeat at 12.2V adjusting RV2 so that the orange LED is just off. Finally, do the same at 11.8V adjusting RV1 so that the red is just off. Slowly increase the voltage again and note that each LED comes on in turn over a small range.

### Absent voltmeter

In the absence of the above equipment, charge the battery fully and connect a suitable bulb to act as a load. Do not draw too large a current in an effort to speed up the process. Aim to run the battery down over a period of at least 20 hours. This may be done in more than one operation so it will not be necessary to get up in the middle of the night to adjust a preset!

Start by finding the Ah (amp-hour) capacity of the battery - this will be printed on it somewhere. A leisure battery will have a typical capacity of 60Ah. This means, in theory, that it could supply 1A for 60 hours, 2A for 30 hours, 3A for 20 hours and so on. With a small load connected, it will appear to have a larger capacity. For example, it would supply one amp for more than 60 hours. Conversely, the capacity will be less with a large load so it would not maintain a load of 60 amps for a full hour.

With the amp-hour capacity known, divide it by 20. This will give the approximate current that must be drawn to run the battery down in 20 hours. For example, the 60Ah leisure battery would need a load of 3A to do this but a small battery, of say 6Ah capacity, will need only 0.3A or 300mA. Now choose a 12V bulb, or bulbs to roughly provide this load. To find the current needed by a bulb, divide the wattage figure by 12 (the nominal voltage of the supply). For an approximate result, you could divide by 10 instead. For example, a 10W car-sidelight bulb could be considered to draw 1A or a 21W flashing indicator lamp, 2A. If you applied the 21W bulb to the 60Ah battery, it would take some 30 hours to discharge and this would be a suitable time. For the smallest batteries, you would need a panel light bulb. These are available in a range of power ratings from car accessory shops. A typical one is rated at 2.2W which works out at about 0.2A. This would be a suitable load for the 6Ah battery mentioned above. One practical point - since filament bulbs become very hot in use, care must be taken that they do not cause burning. They must be placed on a suitable heat proof surface or (better) suspended in the air.

Connect the bulb to the battery and note how many hours it has been alight to the point where it begins to dim noticeably or until a voltmeter shows 11.8V. This time will probably not be the same as the theoretical value. Remember, this does not need to be done in one continuous session. Re-charge the battery. Now decide on suitable timings which will be used to decide "good", "serviceable", "poor" and "flat" states. Suppose it took 30 hours for the bulb to go slightly dim. It may be decided to regard times greater than 20 hours to be "good" (green just off after this time) down to 15 hours, "serviceable" (yellow just off), down to 10 hours, "poor" (orange just off) down to 5 hours "flat" (red just off). Less than 5 hours (all LEDs off) will indicate a dangerously discharged condition. In actual use, the unit will be used with the battery off-load. It is therefore best if the bulb is disconnected before making an adjustment. Wait for

10 minutes or more so that the voltage stabilises before adjusting the corresponding preset.

### Hole truth

The circuit panel may be built in any small plastic box which can accommodate it. Measure the positions of the LEDs on the PCB and drill holes in the lid to correspond. Take care to drill them in a perfect straight line and make them a tight fit. The PCB will then require little extra support. Drill a hole in the side of the box for the probe leads to pass through. You will need to remove them from the PCB, pass them through the hole and re-solder them in position. Apply some strain relief by, for example, tying a knot in the wires. Leave some slack inside the case and check that the wires cannot be pulled free in service. A piece of foam plastic on the base of the box will probably be sufficient to support the circuit panel. Check with the lid in place. If necessary, make adjustments to the presets over a period of use to obtain the desired effect.

### Final points

When using the LED voltmeter, make the test with the battery off-load and preferably after it has rested for a while. This will enable the terminal voltage to settle down to the correct value.

If a routine test reveals that the yellow LED is off (indicating about 12.5V), the battery should be charged as soon as possible. This will prevent the slow deterioration referred to earlier. In service, this will not always be possible but the battery should certainly be charged before the red LED has gone off.

## PARTS LIST

for the LED Voltmeter for 12V batteries

### Resistors

R1, R3	22k
R2	18k
R4-R7	560R
RV1-RV4	47k

### Capacitor

C1	220n
----	------

### Semiconductors

IC1	LM2902
IC2	REF50Z
LED1	5mm red LED
LED2	5mm orange LED
LED3	5mm yellow LED
LED4	5mm green LED

### Miscellaneous

FS1	Line fuseholder with 100mA fuse to fit
14-pin dil socket; plastic box; materials for test probes (see text).	

**OMP MOS-FET POWER AMPLIFIERS**  
HIGH POWER TWO CHANNEL 19 INCH RACK

**THOUSANDS PURCHASED BY PROFESSIONAL USERS**



**THE RENOWNED MXF SERIES OF POWER AMPLIFIERS**  
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)  
MXF600 (300W + 300W) MXF900 (450W + 450W)  
ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

**FEATURES:** Independent power supplies with two toroidal transformers • Twin LED VU meters • Level controls • Illuminated on/off switch • XLR connectors • Standard 775mV inputs • Open and short circuit proof • Latest Mos-Fets for stress free power delivery into virtually any load • High slew rate • Very low distortion • Aluminium cases • MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

**SIZES:-** MXF200 W19"xH3 1/4" (2U)xD11"  
MXF400 W19"xH3 1/4" (3U)xD12"  
MXF600 W19"xH3 1/4" (3U)xD13"  
MXF900 W19"xH3 1/4" (3U)xD14 1/2"

**PRICES:-** MXF200 £175.00 MXF400 £233.85  
MXF600 £329.00 MXF900 £449.15  
SPECIALIST CARRIER DEL £12.50 EACH



**OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER**



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/6KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

**STEREO DISCO MIXER SDJ3400S** ★ ECHO & SOUND EFFECTS ★

**STEREO DISCO MIXER** with 2 x 7 band L & R graphic equalisers with bar graph LED VU meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 8 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 8 Line for CD, Tape, Video etc.



Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

**PIZZO ELECTRIC TWEETERS - MOTOROLA**

Join the Pizzo revolution! The low dynamic mass (no voice coil) of a Pizzo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

- TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
  - TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
  - TYPE 'C' (KSN1016A) 2 1/2" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
  - TYPE 'D' (KSN1025A) 2 1/8" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
  - TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
- LEVEL CONTROL** Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

**IBI FLIGHT CASED LOUDSPEAKERS**

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.




**POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET**  
FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

IBI PC 12-100WATTS (100dB) PRICE £189.00 PER PAIR  
IBI PC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL £12.50 PER PAIR  
OPTIONAL STANDS PRICE PER PAIR £49.00  
Delivery £8.00 per pair

**IN-CAR STEREO BOOSTER AMPS**

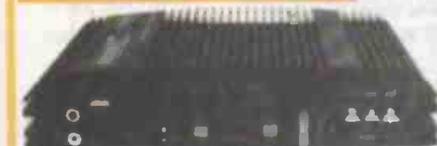

PRICES: 150W £49.99 250W £69.99  
400W £99.95 P&P £2.00 EACH

**THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS**  
150 WATTS (75 + 75) Stereo, 150W Bridged Mono  
250 WATTS (125 + 125) Stereo, 250W Bridged Mono  
400 WATTS (200 + 200) Stereo, 400W Bridged Mono  
**ALL POWERS INTO 4 OHMS**  
**Features:**  
• Stereo, bridgeable mono • Choice of high & low level inputs • L & R level controls • Remote on-off • Speaker & thermal protection.

**OMP MOS-FET POWER AMPLIFIER MODULES**

SUPPLIED READY BUILT AND TESTED.

These modules meet today's professional reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible VU meter. All models are open and short circuit proof.

**THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS**



**OMP/MF 100 Mos-Fet Output power 110 watts**  
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz  
-3dB, Damping Factor > 300, Slew Rate 45V/uS,  
T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R.  
-110 dB. Size 300 x 123 x 60mm.  
PRICE £40.85 + £3.50 P&P



**OMP/MF 200 Mos-Fet Output power 200 watts**  
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz  
-3dB, Damping Factor > 300, Slew Rate 50V/uS,  
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.  
-110 dB. Size 300 x 155 x 100mm.  
PRICE £64.35 + £4.00 P&P



**OMP/MF 300 Mos-Fet Output power 300 watts**  
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz  
-3dB, Damping Factor > 300, Slew Rate 60V/uS,  
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.  
-110 dB. Size 330 x 175 x 100mm.  
PRICE £81.75 + £5.00 P&P



**OMP/MF 450 Mos-Fet Output power 450 watts**  
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz  
-3dB, Damping Factor > 300, Slew Rate 75V/uS,  
T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.  
-110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2  
Second Anti-Thump Delay. Size 385 x 210 x 105mm.  
PRICE £132.85 + £5.00 P&P



**OMP/MF 1000 Mos-Fet Output power 1000 watts**  
R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms,  
frequency response 1Hz - 100KHz -3dB, Damping  
Factor > 300, Slew Rate 75V/uS, T.H.D. typical  
0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Fan  
Cooled, D.C. Loudspeaker Protection, 2 Second  
Anti-Thump Delay. Size 422 x 300 x 125mm.  
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS:  
STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz.  
PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS  
775mV, BAND WIDTH 80KHz. ORDER STANDARD OR PEC.

**LOUDSPEAKERS**

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

**EMINENCE- INSTRUMENTS P.A. DISCO ETC**

- ALL EMINENCE UNITS 8 OHMS IMPEDANCE
- 8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB. PRICE £32.71 + £2.00 P&P
- 10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB. PRICE £33.74 + £2.80 P&P
- 10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB. PRICE £43.47 + £2.80 P&P
- 12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB. PRICE £35.64 + £3.80 P&P
- 12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.67 + £3.80 P&P
- 12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 96dB. PRICE £44.71 + £3.80 P&P
- 12" 300 WATT R.M.S. ME12-300HP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB. PRICE £70.19 + £3.80 P&P
- 18" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB. PRICE £80.72 + £4.00 P&P
- 18" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB. PRICE £73.34 + £4.00 P&P

**LADDERS- IN-CAR STUDIO, IN CAR ETC**

- ALL LADDERS UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohms)
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
- 8" 50Watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS 97dB. PRICE £8.90 + £2.00 P&P
- 10" 60Watt EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 99dB. PRICE £13.08 + £2.80 P&P
- 10" 100Watt EB10-100 BASS, HI-FI, STUDIO. RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB. PRICE £30.39 + £3.80 P&P
- 12" 100Watt EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES. FREQ. 26Hz, FREQ. RESP. TO 3KHz, SENS 93dB. PRICE £42.12 + £3.80 P&P
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
- 5 1/2" 60Watt EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB. PRICE £9.99 + £1.50 P&P
- 8 1/2" 60Watt EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB. PRICE £10.99 + 1.80 P&P
- 10" 60Watt EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 95dB. PRICE £12.99 + £1.80 P&P
- 10" 60Watt EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB. PRICE £16.49 + £2.00 P&P

**TRANSMITTER HOBBY KITS**

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

- 3W TRANSMITTER BS-100MHz, VARCAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 58 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P
- 5W MICRO TRANSMITTER 100-108MHz, VARCAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 54 x 62mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W PM TRANSMITTER

**B.K. ELECTRONICS**

UNITS 1 & 2 COMET WAY SOUTHEND ON SEA

ESSEX SS5 2TR

Tel 01702 527572 Fax 01702 420243

POSTAL CHARGES £25 GROUP £100 MINIMUM OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ



All Major Credit cards Accepted. Prices Exclude Vat @17.5%. Add £1.25 carriage & Vat to all orders. Cheques / Postal orders payable to ESR Electronic Components.

See Next / Last Months Ad. for COMPONENT ACCESSORIES

Table listing various electronic components such as resistors, capacitors, and diodes with their respective part numbers and prices.

Table listing electronic components including diodes, transistors, and integrated circuits with their part numbers and prices.

Table listing electronic components including diodes, transistors, and integrated circuits with their part numbers and prices.


Table listing electronic components including diodes, transistors, and integrated circuits with their part numbers and prices.

Table listing electronic components including diodes, transistors, and integrated circuits with their part numbers and prices.

Tel: 0191 2514363 Fax: 0191 2522296 Email: sales@esr.co.uk http://www.esr.co.uk
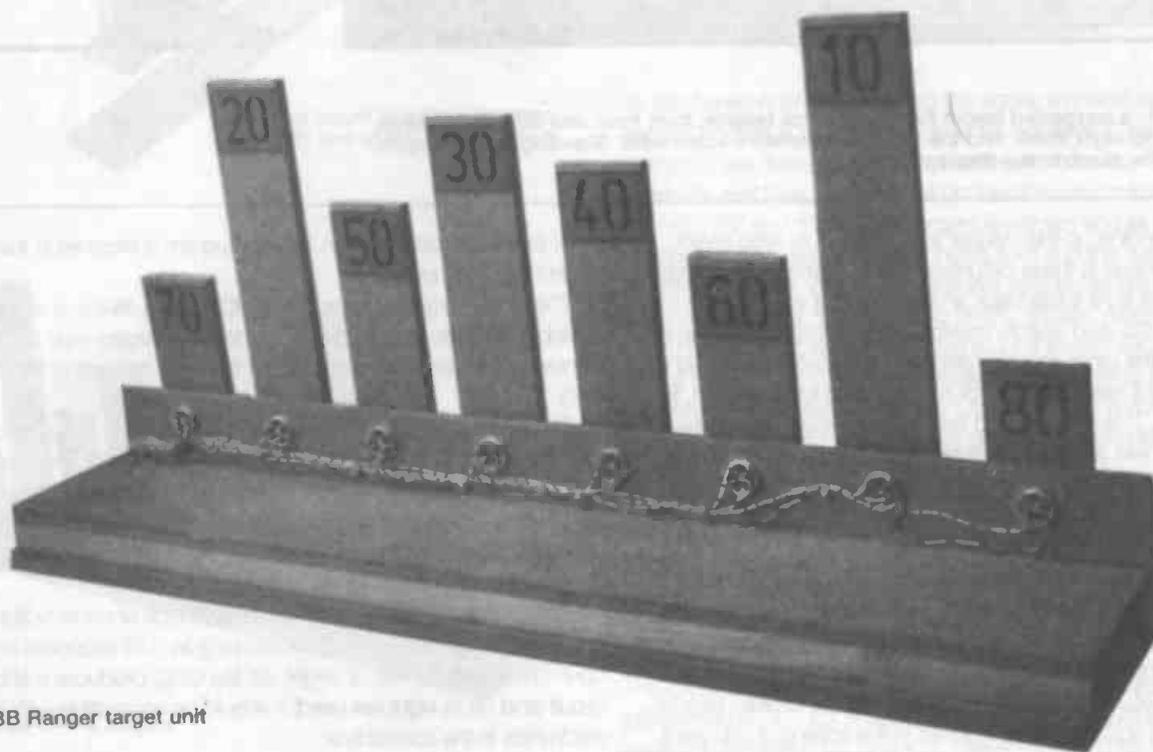
# BB Ranger

This is a combination of an eprom-driven control box, a custom-built fall-down target and an LED scoreboard for BB and other lightweight pellet guns, by Bob Noyes



The BB Ranger target unit

**T**his project was designed as an electronic scoreboard for a BB shooting range. Both of my sons have gone through the BB gun fad, starting with small, lightweight, very low power guns and working up to quite accurate pieces, some of which look similar to real guns although their plastic appearance ensures they can't easily be confused with the real things.

For target practice and in order for the boys to pit their skills against those of their friends I decided that some kind of electronic score board was required to give an instant read-out of the accumulated score. There was nothing on the market that would do so this project, BB Ranger, was born.

For those of you not familiar with BB guns, they are, in many ways, similar to air guns, using a powerful spring or puff of air, or both, to propel a small 6mm round plastic pellet - originally it was a small ball bearing, hence "BB". Unlike real guns, there is no explosive element in BB guns and licences aren't required for ownership; they are not lethal weapons although, as a precaution, eye protection should always be worn by everyone around when the guns are in use. This project is suitable for air guns as well as BBs, but air rifles are too powerful and may damage the targets.

Although a bullseye type target would have been preferable, it

was not easy to construct one on which switches could be mounted to detect the score. As a convenient compromise, instead of a conventional target with the smallest ring being the highest score and the larger rings the lowest, we used separate individual fold-back targets (figure 1). There are eight targets, with scores ranging from 10 to 80 points. It goes without saying that the smaller ones carry higher scores. In the prototype, the 80-points score target measured 25mm high by 63.5mm wide; 70 points, 51mm by 63.5mm, each target thereafter being 25mm taller than the one before but scoring 10 points less, until the 10-points target, which was 203mm high. These eight targets were mounted in a straight line, but you can choose whether to mount them in ascending order, or all mixed up with a gap of about 38mm between each one. As can be seen in figure 2, they are mounted in such a way that, when hit, they fall backwards.

Out of sight behind the body of the assembly, a magnet is mounted in each of the targets. The type used was a door switch like those used in alarm systems - it is readily available and easy to mount, as a flange with countersunk holes is built into the magnet and the reed switches.

The magnet is mounted into the fall-back part of the target, and the reed switch into the body of the target assembly, so that when

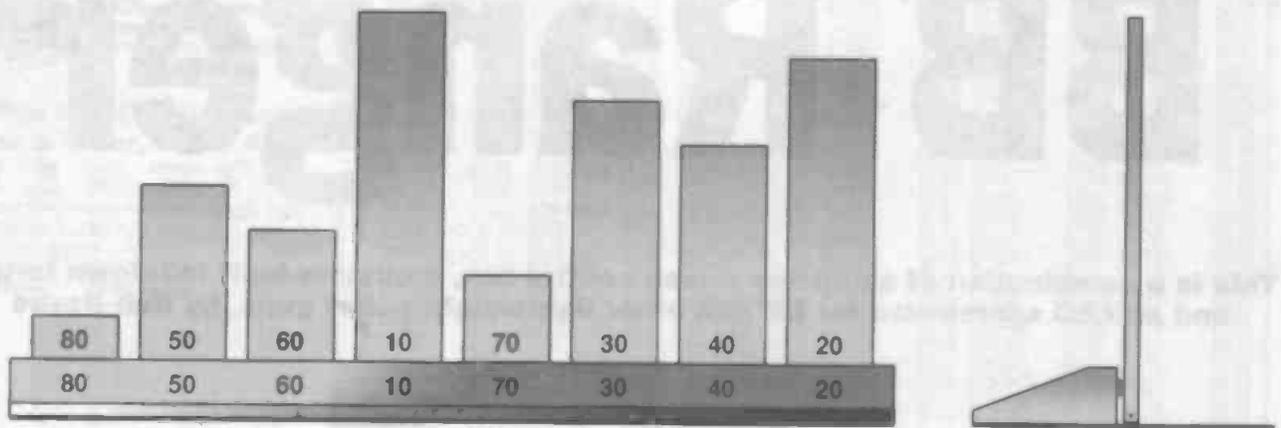


Figure 1: a suggested layout for the fall-back targets, from front and side. Each player has up to eight shots, and the highest cumulative score wins. Standing up the targets resets the score in the display.

the target is standing up the magnet is in range of its reed switch. The switch is closed in these circumstances but when the exposed part of the target is hit it falls back and the magnet mounted on it is out of range of the reed switch, making an open circuit. The same is repeated for the other seven targets. A 9-way cable was used to connect the eight reed switches, plus a common to all of them, to the control box. This cable should be several metres long to keep the control box well away from the target area. A plug and socket was used to connect the cable to the control box.

### Board and paint

You don't have to construct eight fold-back targets if you don't want to. So long as the ones used score in the range 10, 20, 30, 40, 50, 60, 70 and 80 the circuit will work, although wire links must be used to connect the unused connections permanently from the control box to 0V. This just kids the control that the unused targets are still standing and don't play any part in the scoring. If you want

more than eight targets, then a new program is required in the control box. See below.

The whole target is made out of MDF board as this is readily available and reasonably priced. The finished targets may be painted or varnished to protect them from the ravages of time (and kids).

The exposed parts of the target were covered in sticky-backed foam, the sort of stuff that pipes can be covered with. This absorbs the impact of the pellet hitting the target and helps prevent it rebounding to the firing position. The front of the body of the target assembly slopes back, again to deflect the pellet. This surface is used to show the score for each target.

This Ranger project is just one possible type of construction. Any similar type may be built, and so long as a hit produces an open circuit and a miss, or target still standing, produces a short circuit (and up to eight are used) it should be compatible with the electronics in the control box.

A very large cardboard cover was made to go over the target assembly in order to trap the pellets so they could be used again. The original was well over a metre long, 53cms high and 53cms deep, which allowed enough room to reset the targets, that is, to stand them up again. It also retained about 95 percent of the pellets used. The inside of the box was covered with canvas from an old tent to stop the pellets embedding themselves into the soft cardboard. I used wallpaper paste to stick the canvas to the cardboard. To reset the display, just stand up all the fallen targets and it will read zero.

### The 2716 eprom

At the heart of the control PCB is an eprom or erasable programmable read only memory. The one used is the 2716, which is the smallest in the 27xx range



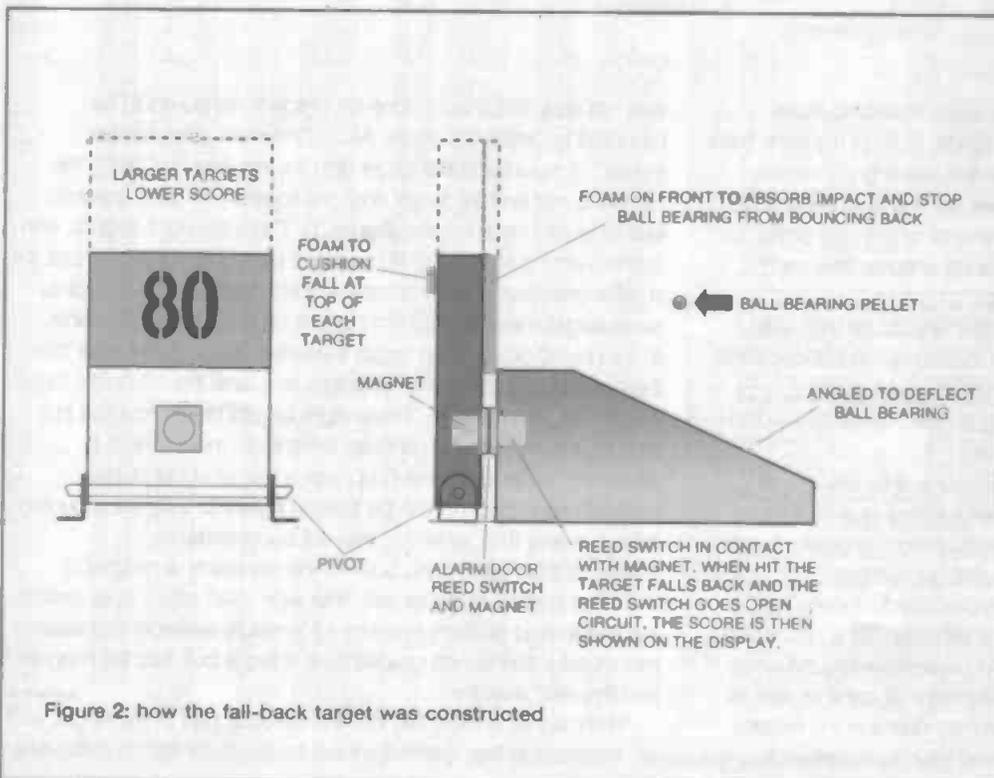


Figure 2: how the fall-back target was constructed

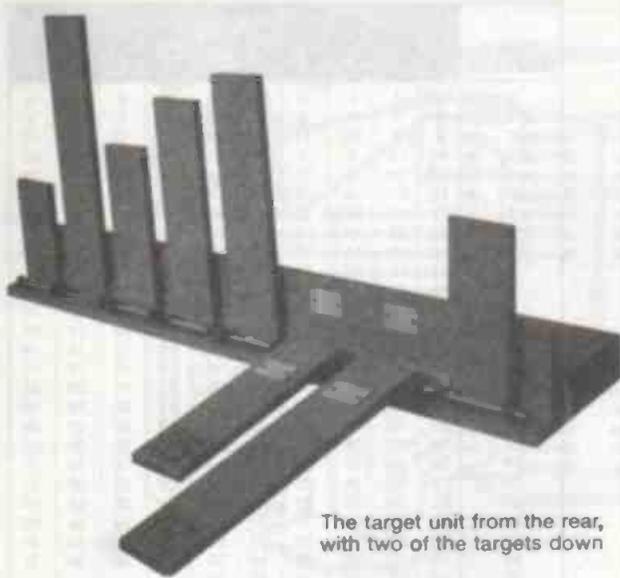

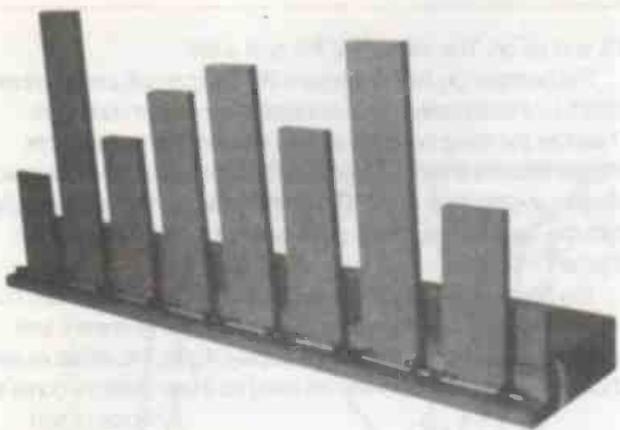The target unit from the rear, with two of the targets down



The rear of the targets

of eproms, and can be picked up very cheaply as surplus stock. Larger memories such as 2732 and 2764 can be used so long as their control signals and extra address lines are catered for. However, the PCB in this project is designed for the 2716 only. (See figure 3.)

For some reason, eproms are often considered only as a part of a computer system containing software for the operating system, but it is just another component with a specification. In this case we are using its memory, even when the power is removed, to hold every combination of score from the eight targets. There is a total of 256 combinations of score from all targets up, that is, no score or zero to all eight targets down and a score of 36 points. The eight inputs from the targets' reed switches go to the 8 lowest address lines of the eprom, that is, the "10" goes to A0 (note A0 not A1), "20" goes to A1, "30" to A2 and so on. The remaining address lines, A8, A9 and A10 are connected to zero. If a larger 2732 is used, A11 must also be grounded. Now every combination of score sets its own address, i.e. with the "10" and "20" and "30" down but all the others up the address is as follows:

A7 A6 A5 A4 A3 A2 A1 A0  
0 0 0 0 0 0 0 0

At this address a score of "6" is stored in the memory; this takes the form of D0, D1, D2, D3 which holds the tens or next most significant decade:

D0 D1 D2 D3  
1 2 4 8

so data stored is:

D0 D1 D2 D3  
0 1 1 0

and D4, D5, D6 and D7 hold the most significant decade:

D4 D5 D6 D7  
1 2 4 8

As can be seen when adding up the score, the least significant decade or units is always zero, so does not have to be held in memory. Only the most significant and next most significant, or hundreds and tens, must be held in memory. So, in the case where the "10", "20" and "30" points targets are down and all the others are up, the most significant digit holds zero and the next most significant holds 6. With the permanent zero in the least significant decade, a score of "60" will show on the display. When you buy the 2716 eprom, it will either be blank, or, if it has been reclaimed from a circuit, it will contain a useless program. In that case the old program must be removed with a UV eraser. The eprom is usually exposed to UV light for 10 minutes or so, which should blank the eprom's memory:

The program for this project can then be loaded in via an eprom programmer, or a ready-programmed 2716 can be obtained ready me, for £16 including postage and packing (see the end of this article). The program is listed in figure 4.

### The circuits

The circuit diagram of the BB Ranger appears in figure 5. The information in D0 - D7 is decoded by two 4511 BCD to seven-segment decoders, IC2 and IC3. These ics give outputs suitable for switching on the separate elements in the seven-segment LED displays. If only a small readout is required, DIL1 and DIL2 supply the current limiting resistors required for the two decades of common cathode displays. The third least significant decade display is wired so that all segments but the "g" segment are on, so that it reads zero. This takes the form of 6 x 270Ω resistors from each segment: a, b, c, d, e and f connected to +5V, and the common connected to 0V. Any small seven-segment common cathode displays will do, but they all have different pin outs. The pin


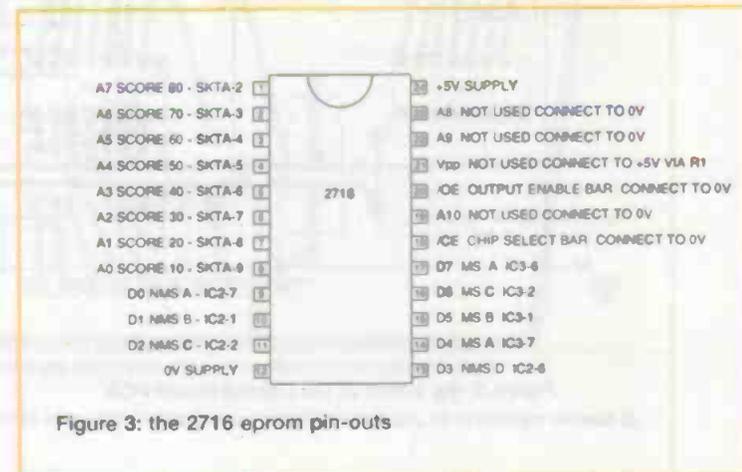


Figure 3: the 2716 eprom pin-outs

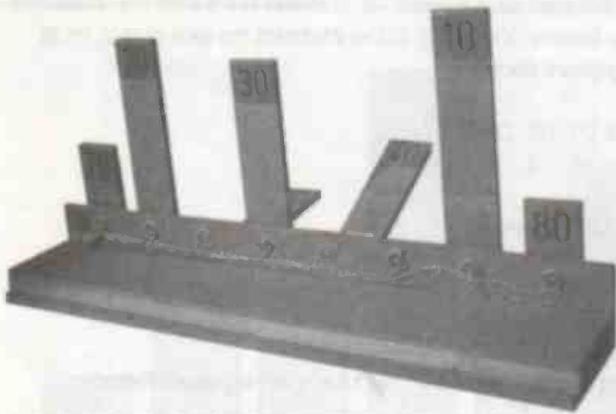

The target unit from the front, with two of the targets falling

out must be obtained for the ones used, and the common connected to 0V. The problem with these small LED displays is that they have a very limited readability range. To see the display from several metres away, larger displays are required.

As can be seen from the PCB layout in figure 6, although it is supplied with 12 volts, the circuit works from 5 volts via the on-board 104 regulator, which must be compatible with the eeprom. 5 volts presents a problem with larger displays, as it only allows two round 5mm LEDs to be wired in series as each drops around 2.2 volts. In order to build up a larger display, 4 x 5mm LEDs are used to make each segment of the three seven-segment displays. Having four LEDs in series, each dropping around 2.2 volts, requires a supply in excess of 10 volts to allow for the LEDs plus the darlington voltage drop, and so on. To switch each of these segments on, DIL power darlings are used, one for each active decade: the most significant or hundreds decade and the middle display or tens decade. The units decade is again permanently wired to read zero. If you are going to build a larger display, DIL1 and DIL2 can be linked across, that is, pin 1 to pin 14, pin 2 to pin

TENS & HUNDREDS	UNITS									
	0	1	2	3	4	5	6	7	8	9
0	0	1	2	3	3	4	5	6	4	5
1	6	7	7	8	9	10	5	6	7	8
2	8	9	10	11	9	10	11	12	12	13
3	14	15	6	7	8	9	9	10	11	12
4	10	11	12	13	13	14	15	16	11	12
5	13	14	14	15	16	17	15	16	17	18
6	18	19	20	21	7	8	9	10	10	11
7	12	13	11	12	13	14	14	15	16	17
8	12	13	14	15	15	16	17	18	18	17
9	18	19	19	20	21	22	13	14	15	16
10	16	17	18	19	17	18	19	20	20	21
11	22	23	18	19	20	21	21	22	23	24
12	22	23	24	25	25	26	27	28	08	09
13	10	11	11	12	13	14	12	13	14	15
14	15	16	17	18	13	14	15	16	16	17
15	18	19	17	18	19	20	20	21	22	23
16	14	15	16	17	17	18	19	20	18	19
17	20	21	21	22	23	24	19	20	21	22
18	22	23	24	25	23	24	25	26	26	27
19	28	29	15	16	17	18	18	19	20	21
20	19	20	21	22	22	23	24	25	20	21
21	22	23	23	24	25	26	24	25	26	27
22	27	28	29	30	21	22	23	24	24	25
23	26	27	25	26	27	28	28	29	30	31
24	26	27	28	29	29	30	31	32	30	31
25	32	33	33	34	35	36				

Figure 4: the BB Ranger eeprom program 0 - 255 for the 2716 eeprom

13, and so on. This will reduce the cost a little.

The heatsink on the prototype is RS (Electromail) part number 263251. Unfortunately, this is not available in single quantities. Therefore the fitting holes have been left undrilled so that other suitable heatsinks can be used. The heatsink must have solderable tabs, to give support to the IC. Drill the holes for the tabs carefully from the copper side, taking great care not to cut through the adjacent PCB track.

The power darlington ics are ULN and 2003A. These have built in base resistors, but 100n resistors are required to current limit each of the segments of the large display. Again, DIL resistors were chosen. Here, 16-pin sockets are used as these resistors come in

a choice of two packages: although the circuit only required the 14-pin package, the 16-pin package will also fit. Care must be taken when wiring up the display PCB to the control PCB, because although they share a common 0V, their power supplies are different. The +12 volts of the display board must not be connected to the +5V on the control PCB. A table of the control board connections follows:

- A Inputs
- To targets
- 1 +5V
- 2 Score 8
- 3 Score 7


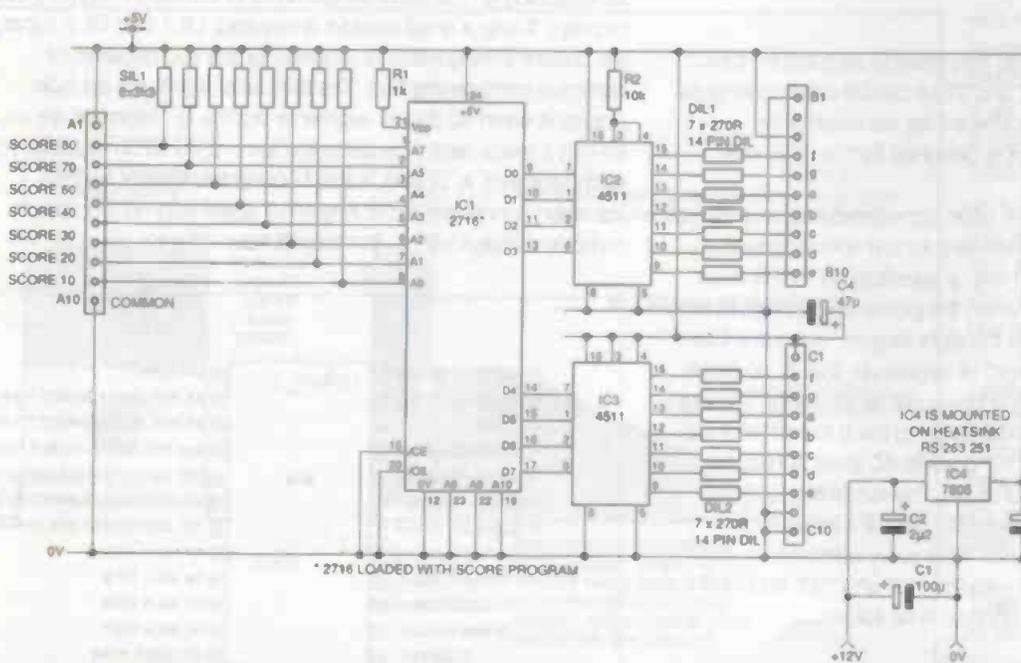


Figure 5: the circuit of the Control Board PCB

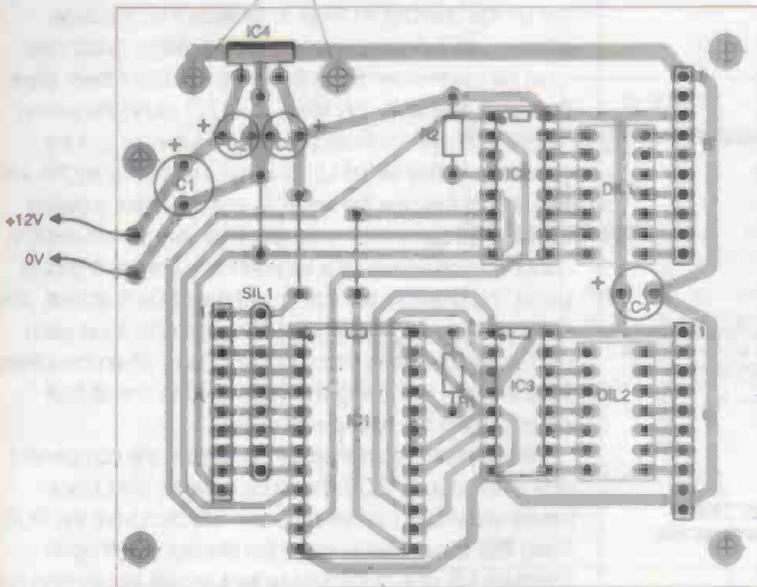HOLES TO FIT HEATSINK RS PART NO. 263 251



NOTE: SOCKETS A, B, C 10 x 0.1" CONNECTORS

Figure 6: the component layout of the Control Board PCB


- 4 Score 6
- 5 Score 5
- 6 Score 4
- 7 Score 3
- 8 Score 2
- 9 Score 1
- 10 0V common

Outputs

- To large display
- |    |             |     |
|----|-------------|-----|
| B  | Function To |     |
| 1  | 0V          | E10 |
| 2  | Keyway      |     |
| 3  | +5V         |     |
| 4  | NMS f       | E5  |
| 5  | NMS g       | E2  |
| 6  | NMS a       | E7  |
| 7  | NMS b       | E6  |
| 8  | NMS c       | E4  |
| 9  | NMS d       | E3  |
| 10 | NMS e       | D2  |


Outputs

- To large display
- C Function To

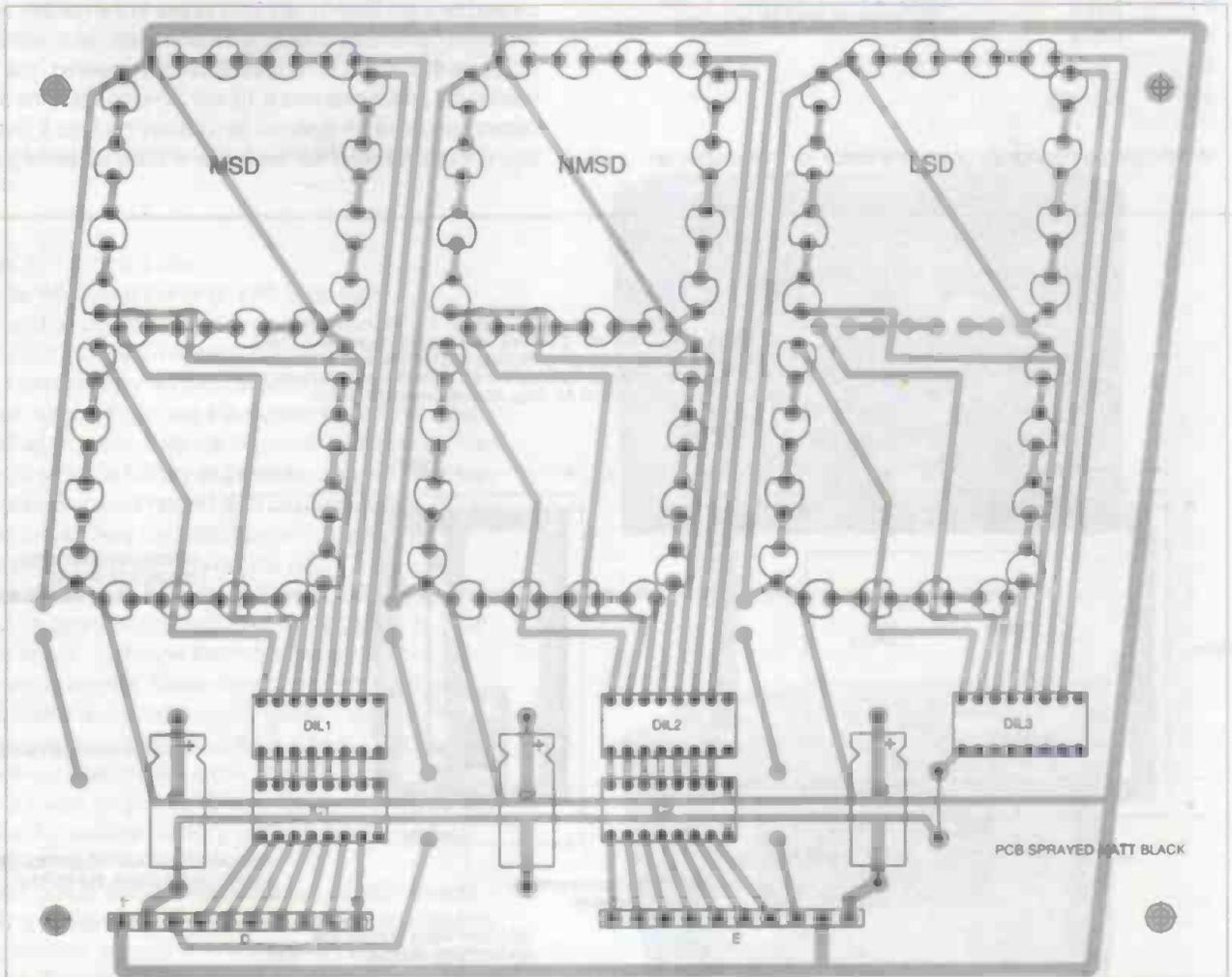

SOCKETS D AND E ARE 10-WAY 0.156" RIGHT-ANGLE PCB HEADERS DIL 1, 2 AND 3 ARE 14 OR 16-PIN. ONLY 14-PIN REQUIRED FOR 100R RESISTORS

Figure 7: the layout of the Display Board. The centre bar is not required in the lowest significant digit, as it always shows 0. 80 identical 0.2-in LEDs are used

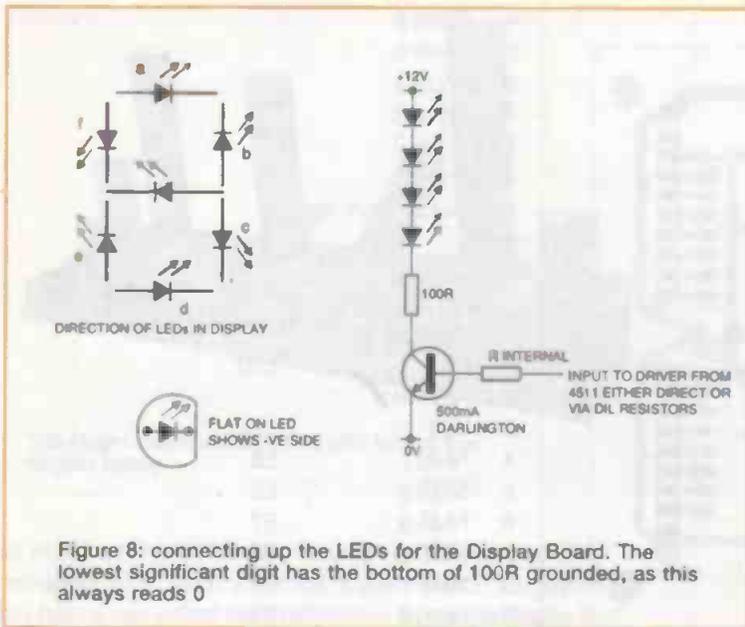

- |    |        |     |
|----|--------|-----|
| 1  | +5V    |     |
| 2  | MS f   | D8  |
| 3  | MS g   | D5  |
| 4  | MS a   | D10 |
| 5  | MS b   | D9  |
| 6  | MS c   | D7  |
| 7  | MS d   | D6  |
| 8  | MS e   | D4  |
| 9  | 0V     | D2  |
| 10 | Keyway |     |


When using a darlington, or any transistor for that matter, an

inversion takes place as a high on the base will produce a low on the collector. In order to facilitate this, the large displays use a common anode configuration. Great care must be taken when fitting the LEDs - all 80 of them (see figures 7 and 8). It only takes one LED round the wrong way to stop the whole segment from illuminating. It's a good idea to buy all the LEDs at the same time, as this will ensure that they are the same type; it will make a clearer display than using odd ones, as LEDs vary considerably in colour and brightness. If a segment is out when it should be on, the chances are that one of the LEDs is at fault. The easiest way to find out which LED is out is to short each LED on the offending segment out in turn. When the others illuminate, the one being shorted out is the one at fault - either dead or the wrong way round.

To enhance the contrast of the display, the component side of the display PCB should be sprayed matt black before assembly; this prevents any reflection from the PCB. A red filter is required to cover the display, which again improves the look of the final project as well as blanking out everything but the illuminated LEDs.

### The battery supply

The power supply to the display must be capable of producing in excess of 500mA, so a rechargeable battery is a must. Because this project can only be safely used out of doors, it **must not be mains powered for obvious reasons**. Too many accidents are caused by the misuse of electrical power in the garden, from excessive dampness to faulty extension leads, so to eliminate these problems this project is completely battery powered. The battery used in the prototypes was a 12-volt 2.3-amp hour, the sort of battery used in alarm systems as a battery backup. It goes without saying that it will need recharging, so a fused socket is provided for

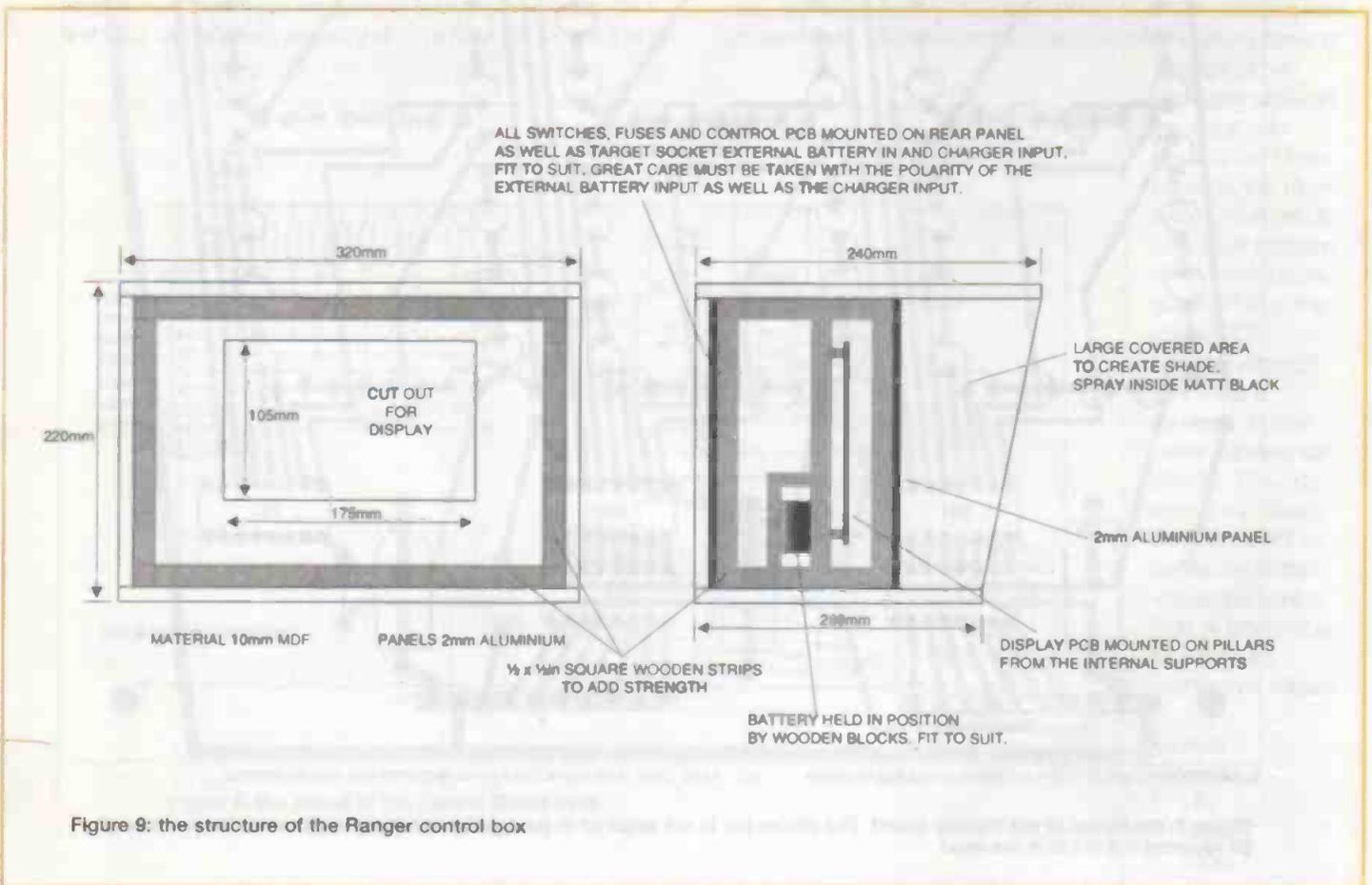

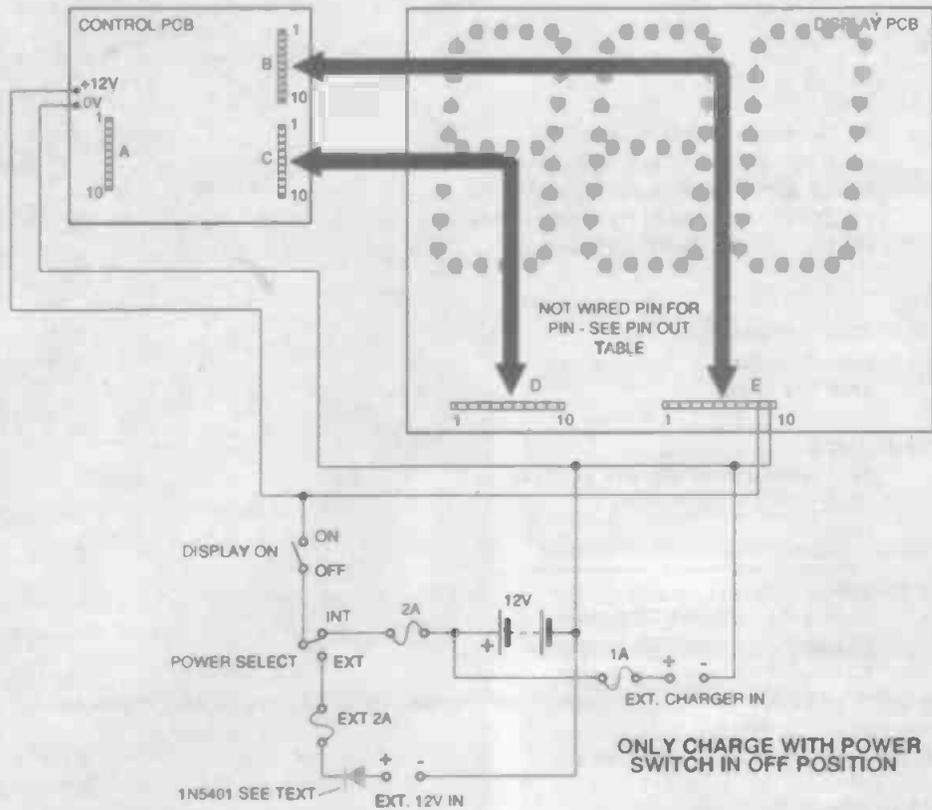



Figure 10: the external connections for the BB Ranger system

this on the rear of the control box.

The batteries will differ depending upon type, style, manufacturer and so on, so no precise charging currents or times can be given. Manufacturers' information must be followed. Although the internal battery will provide several hours of continuous use, for prolonged use it is recommended that a car battery is used as an external source of power. This must be fused at 2 amps as close to the battery as possible, using an inline fuse holder. If it is going to be connected by a plug and socket, the lead from the battery must have shrouded female contacts. This eliminates the possibility of shorting out the pins.

A selector switch should be used to make sure that this external battery cannot be connected across the internal battery, as great damage may result. Only one battery source can be selected at any one time. Great care must be taken to ensure the polarity is correct, as, although fuses are fitted, a lot of damage can result before a fuse blows. A diode can be fitted in series; this must be the 1N5401 type. Although it will add a 0.7-volt drop, this should be compensated by the fact that a 12-volt car battery, when fully charged, is well above 12 volts.

The control box is also constructed out of MDF board (figure 9). The design should include a lip over the display to provide a shaded area so that the display can be seen in bright daylight. The size of the box is not important so long as it is large enough to contain all the parts: the main control PCB, the large display and the battery. Again, only recommendations are given as the type of battery and other details will differ from one to another. The power set-up for

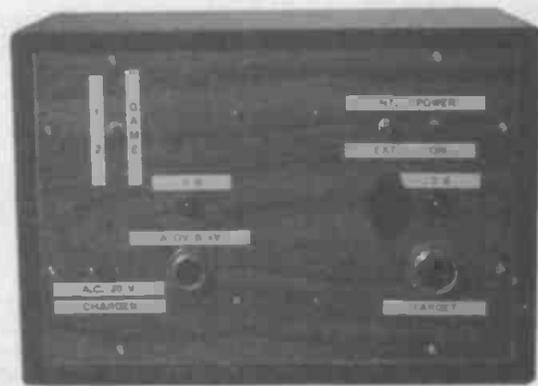

The control box from the rear, showing connections



The control box from the front, showing the score display

## The Control Board

### Resistors

R1	1k
R2	10k
SIL1	8 x 3k3 single-in-line resistor unit
DIL1	7 x 270R 14-pin dual in line resistor unit OR 7 x 270R one-third watt resistors
DIL2	7 x 270R 14-pin dual in line resistor unit OR 7 x 270R one-third watt resistors

### Capacitors

C1	100uF 16V radial
C2, C3	2u2 16V radial
C4	47uF 16V radial

### Semiconductors

IC1	2716 programmed eprom - see text
IC2, IC3	4511
IC4	7805

### Miscellaneous

SKTA	10-way 0.1 vertical PCB header
SKTB	10-way 0.1 vertical PCB header
SKTC	10-way 0.1 vertical PCB header

The heatsink on the prototype was RS (Electromail) part number 263251. Other suitable heatsinks can be used if holes are drilled - see text.

Suitable casing (see text); link wire, solder, etc.

## The Display Board

### Resistors

DIL1, 2, 3	14- or 16-pin 100R dual in line resistor units of 7 or 8 100R resistors. Only 14 pins are required, but 16 pins will fit.
------------	---

### Capacitors

C1, C2, C3	100uF 16V
------------	-----------

### Semiconductors

IC1, IC2	ULN 2003A
----------	-----------

LEDs: 80 x 0.2-in red LEDs: all the same type to make an even display

### Miscellaneous

Sockets D, E: 10-way 0.156 right-angled PCB headers

Matt black-paint for PCB and pellet-retaining cowling.

Wire, solder, etc.

### The Target

10-pin 100R board for construction; door-alarm type reed switch and magnet combinations for each fall-back target; 80 x 0.2-in red LEDs; small pivots for individual fall-back targets; sticky-backed foam strip (see text); insulated connection wire; strong cardboard to make pellet-retaining cowling.

### Batteries

Rechargeable or external rechargeable battery source. Fuses, fused socket, selector switch etc. as appropriate for batteries (see text).

the Ranger is shown in figure 10.

Since the original was built a couple of years ago, the control box has found other uses. One, for instance, was used in a Roll the Ball game at a fete where light-dependent cells were used under holes in the game. When a ball lodged in the hole, it shut out the light to the LDR and a score was registered on the display. Again, there were eight holes with scores 10 - 80; the object was to roll five balls down a short runway and get them to lodge in the various holes, the winner to score 210 points and win a prize.


For a pre-programmed 2716 send a cheque or postal order for £16 to me, Bob Noyes, 13 Bowfell Close, Tilehurst, Reading RG31 6QR.

Blank 2716 eproms from Farnell Electronic Components: Canal Road, Leeds, LS12 2TU. Tel 0113 263 6311 or other sources. Second user ICs are often available as salvage from Greenweid Electronic Components Tel. 01703 236363.

# PROTEUS


## Schematic Capture

NEW Version IV

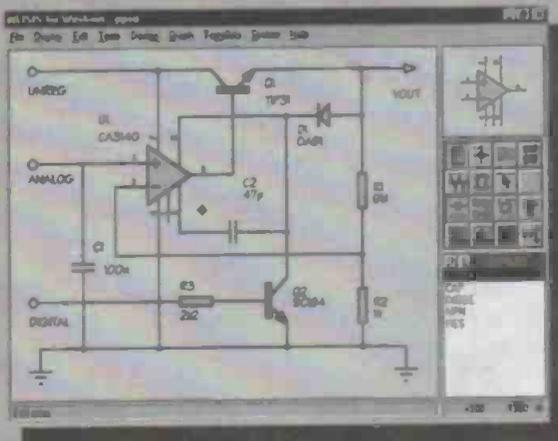

- Produces attractive schematics like you see in the magazines.
- Netlist, Parts List & ERC reports. ● Hierarchical Design. ● Full support for buses including bus pins. ● Extensive component/model libraries. ● Advanced Property Management.
- Seamless integration with simulation and PCB design.

## Simulation

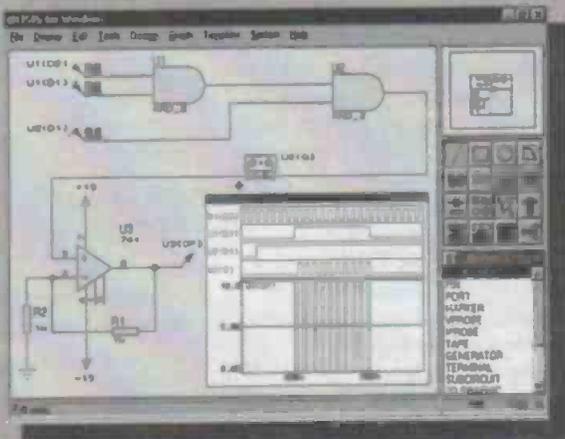

- Non-Linear & Linear Analogue Simulation. ● Event driven Digital Simulation with modelling language. ● Partitioned simulation of large designs with multiple analogue & digital sections. ● Graphs displayed directly on the schematic.

**FREE**  
SOFTWARE

ISIS & ARES Lite  
Schematic & PCB  
Design

**SHAREWARE VERSIONS  
AVAILABLE TO DOWNLOAD  
FROM OUR WEBSITE**

<http://www.labcenter.co.uk>

labcenter  
Electronics

# The IV<sup>th</sup> Generation


## New Features

- Component Auto-Placer
- Pinswap/Gateswap Optimizer
- Background Regeneration of Power Planes
- Enhanced Autorouting with Tidy Pass
- Full Control of Schematic Appearance
- Extensive New Component Libraries

Available in 5 levels - prices from £295 to £1625 + VAT.  
Call now for further information & upgrade prices.

## PCB Design

NEW Version IV

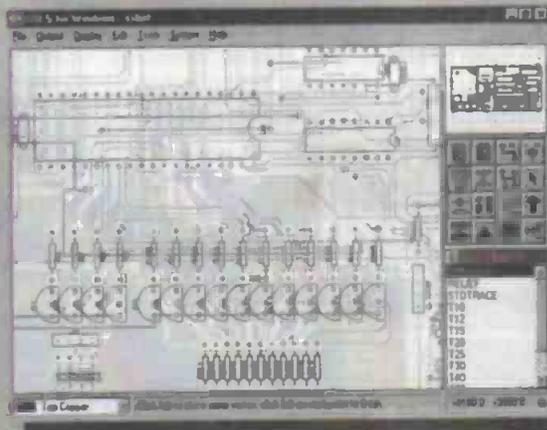

- Automatic Component Placement. ● Rip-Up & Retry Autorouter with tidy pass. ● Pinswap/Gateswap Optimizer & Backannotation. ● 32 bit high resolution database. ● Full DRC and Connectivity Checking. ● Shape based gridless power planes. ● Gerber and DXF Import capability.

**"PROTEUS  
is particularly good  
with its rip-up-and-retry  
autorouter"** EWW January 1997

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.  
Tel: 01756 753440. Fax: 01756 752857. EMAIL: [info@labcenter.co.uk](mailto:info@labcenter.co.uk)  
53-55 Main St, Grassington, BD23 5AA. WWW: <http://www.labcenter.co.uk>

Fully interactive demo versions available for download from our WWW site.  
Call for educational, multi-user and dealer pricing - new dealers always wanted.  
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

# Video Surveillance



Pinhole Board Camera (B&W) 12v  
DC, 0.1LUX,  
380 TV Resolution  
Size: 35mmx35mm **£35.00**

Pinhole Board Camera (Color) 12v  
DC, 0.5 LUX,  
420 TV Resolution  
2 board foldable  
Size: 40mmx40mm **£190.00**

Audio/Video Transmitter module  
12v DC, 4 Channel Selection  
900MHz-1200MHz, FM Modulation  
**£120.00**



4 Channel Receiver + Switcher  
12v DC, Composite Audio/Video  
Output **£150.00**



TFT 4" Colour Monitor  
12v DC **£150.00**

We also stock:  
Time & Date Generator, Miniature PIR etc.

## Confidential Communications Limited

344 Kilburn Lane, Maida Vale  
London W9 3EF

Tel (44)(0) 181 968 0227 Fax: (44)(0) 181 968 0194

Email: 106075.276@Compuserve.com

## osziFOX

**£75**  
Inc.

A universal 20 MHz  
storage oscilloscope



A slimline storage oscilloscope and digital  
voltmeter with a sampling rate of up to 20 MHz.  
Inclusive software enables the recorded signals to  
be displayed simultaneously on a PC screen.

Sample Rates: From 50 ns to 1 ms. Purveyors of Quality

Input Voltage: 1 V, 10 V, 100 V. Electronic Thingsies at

Trigger: ±Internal, ±External, Auto. Very Friendly Prices

Voltmeter: AC and DC.

Supply Voltage: 9 V to 13 V DC, 13 mA, external.

Trigger, ground, power & serial cables included.

**No  
Nuts  
Limited**

2 Chase Cottages,  
New Road, Aldham,  
Essex CO6 3QT Tel. & Fax 01206 213322

**Also Available;**  
CCD Camera Modules from £60  
Complete CCD Kits, with housing,  
cable and connectors. Ready to run.  
B/W + Audio CCD Kit £85  
Colour + Audio CCD Kit £150  
Please add £2 p&p to all orders.

# ELECTRONICS DIRECT

## SUBSCRIBE & SAVE WITH ELECTRONICS DIRECT

Our subscription deals just get better and better - now  
you can save almost £20 if you subscribe today!

### ETI, code: 0215

Electronics Today International - The Project Magazine for all  
Electronics Constructors.

The single source guide to electronics for today and tomorrow,  
packed with numerous projects for enthusiasts of all abilities.  
The detailed features and up-to-the-minute news items keep all  
readers fully informed of the latest, exciting developments in  
this ever changing hobby, whilst the equipment reviews ensure  
that you always know exactly what to buy.

15 issues for the price of 13


UK: NOW ONLY £35.75 YOU SAVE £5.50

Europe: £44.59, Overseas: £47.84, USA: \$74.00

30 issues for the price of 26

UK: NOW ONLY £71.50 YOU SAVE £13.75

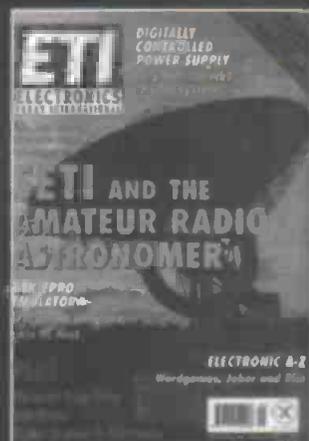Europe: £89.18, Overseas: £95.68, USA: \$148.00



### ACORN ARCHIMEDES WORLD, code: 0215

In the constantly changing world of IT, it is vital to keep  
abreast of all the latest trends and developments. Of course,  
this is easier said than done. However, you CAN keep fully  
informed by reading Acorn Archimedes World, Britain's most  
respected computing magazine devoted to all Acorn 32 bit  
RISC OS systems. The wide ranging editorial brings you in-  
depth hardware and software reviews, evaluates new products  
and forecasts what will happen next, and includes a dedicated  
educational section. Each issue also comes with a free cover-  
mounted disc, often containing complete, usable programs as  
well as workable and playable demos.

15 issues for the price of 13

UK: NOW ONLY £51.35 YOU SAVE £7.90

Europe: £62.40, Overseas: £66.56, USA: \$103.00

31 issues for the price of 26

UK: NOW ONLY £102.70 YOU SAVE £19.75

Europe: £124.80, Overseas: £133.12, USA: \$206.00



REMEMBER, it's always cheaper to subscribe - and you avoid future cover price increases!

All savings are based upon buying the same number of issues from your newsagent, UK only.

## BINDERS

Keep your favourite magazines in mint condition in one of  
our sturdy binders.

Each binder will hold up to 13 issues.

**Code: bind 02**

**£7.50 U.K. £8.00 Overseas**

BINDERS AVAILABLE

● ETI ● ARCHIMEDES WORLD




'Electronics Direct' is the One Stop Shop for all your computing, electronics and amateur radio needs from Nexus Direct. We are offering some sensational deals on Subscriptions, Books & Reader Offers - all available direct by mail order. Remember, all our prices include postage and packing - so there are no hidden extras to add! You can order by phone, fax or use the coupon.

# ELECTRONICS DIRECT

Please order all your goods using the coupon below ensuring you fill in all sections OR simply use our order hotline. Thank you.

## SAVINGS ON BOOKS

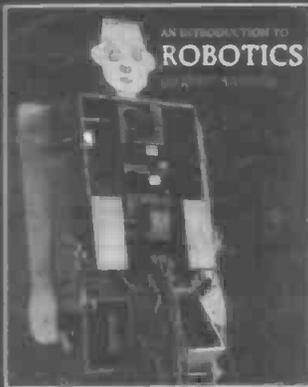


### AN INTRODUCTION TO ROBOTICS.

A fascinating and unique book that breaks new ground by exploring the exciting world of robotics in a clear and concise way. Both the theoretical and practical aspects are presented in an uncomplicated fashion using everyday English, which makes this an ideal book for the amateur. Divided into two sections, the first part explains how and why robots work and are controlled, while the second shows you how to make a simple two legged humanoid robot that can be programmed to walk. There are no complicated formulas or equations to grapple with or incomprehensible circuit diagrams to decipher - this robot can be built on your kitchen table and can be run from any personal computer! All you need are model aeroplane servos, a controller, a power supply and some plywood - and all parts are easily available in the UK and the USA. This is a book that will be of interest to modellers and everyone with a fascination for things mechanical and electronic.

Code: NB299

ONLY £11.95 UK £12.95 Overseas

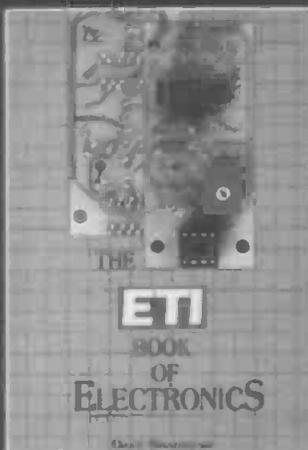


### ETI BOOK OF ELECTRONICS

This is the perfect book for beginners, offering a clear and concise introduction to both the theories and principles of electronics. Each chapter also allows you to put this theory into practice with an easy to follow project to make, including a loudspeaker divider, continuity tester, 'brown out' alarm, freezing alarm, loudspeaker mini-amplifier and a burglar alarm.

Code: NB214

ONLY £12.95 UK £13.95 Overseas

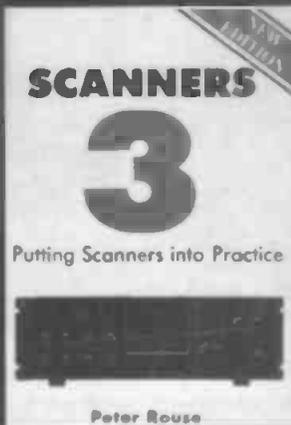

### SCANNERS 3 - PUTTING SCANNERS INTO PRACTICE

This is the fourth revised and completely updated edition of Scanners, the complete VHF/UHF radio listeners guide, containing everything you need to know to put your scanner to better use. There is a great deal more information than ever before on frequency listing; in particular, actual frequencies used by coastal stations, airfields and the emergency services. Also included for the first time is a section on the HF (short wave) band as many scanners now cover this range.

Code: NB217

ONLY £11.95 UK £12.95 Overseas



### SCANNERS 2 INTERNATIONAL

The companion book to 'Scanners' provides even more information on the use of VHF and UHF communication bands, and gives details on how to construct accessories to improve the performance of scanning equipment. The book is international in its scope and contains frequency allocations for all three ITU regions, including country-by-country variations.

Code: NB216

ONLY £11.95 UK £12.95 Overseas

### SUBSCRIPTIONS

Magazine	Code	No. of Issues	Price
.....	.....	.....	£.....
.....	.....	.....	£.....
.....	.....	.....	£.....
Total Subscription Value			£.....

Subscription No. if renewing .....

### READERS OFFERS/BOOKS/BINDERS

Title	Code	Qty	Price
.....	.....	.....	£.....
.....	.....	.....	£.....
.....	.....	.....	£.....
.....	.....	.....	£.....
.....	.....	.....	£.....

Total Order Value £

### METHOD OF PAYMENT

The total value of my order is £ .....  
I enclose a Cheque/P.O. made payable to  
**Nexus Special Interests Ltd.** or please debit my  
Mastercard/Visa/AMEX account

Card No. [.....]

Expiry ...../..... Signature .....

### Your Details

Name: (Mr/Mrs/Miss) .....

Initial ..... Surname .....

Address: .....

Postcode/Zipcode ..... Country .....

Telephone: .....

### Send to:

**Electronics Direct**  
Nexus House  
Boundary Way  
Hemel Hempstead  
Herts. HP2 7ST.

### Please Note

All prices include P&P where appropriate. All subscriptions start with the first available issue. Every effort will be made to despatch your order within 14 days but please allow up to 28 days for delivery. Individual items may be dispatched separately. These offers are not to be used in conjunction with any other promotion.

Please tick this box if you do not wish to receive direct mail from other companies



# ELECTRONICS DIRECT

## Express Order Hotline

# 01442 266551

9am - 5pm Monday - Friday


Fax order line: 01442 266998

Closing date: 30/06/98

# BOOKS DIRECT
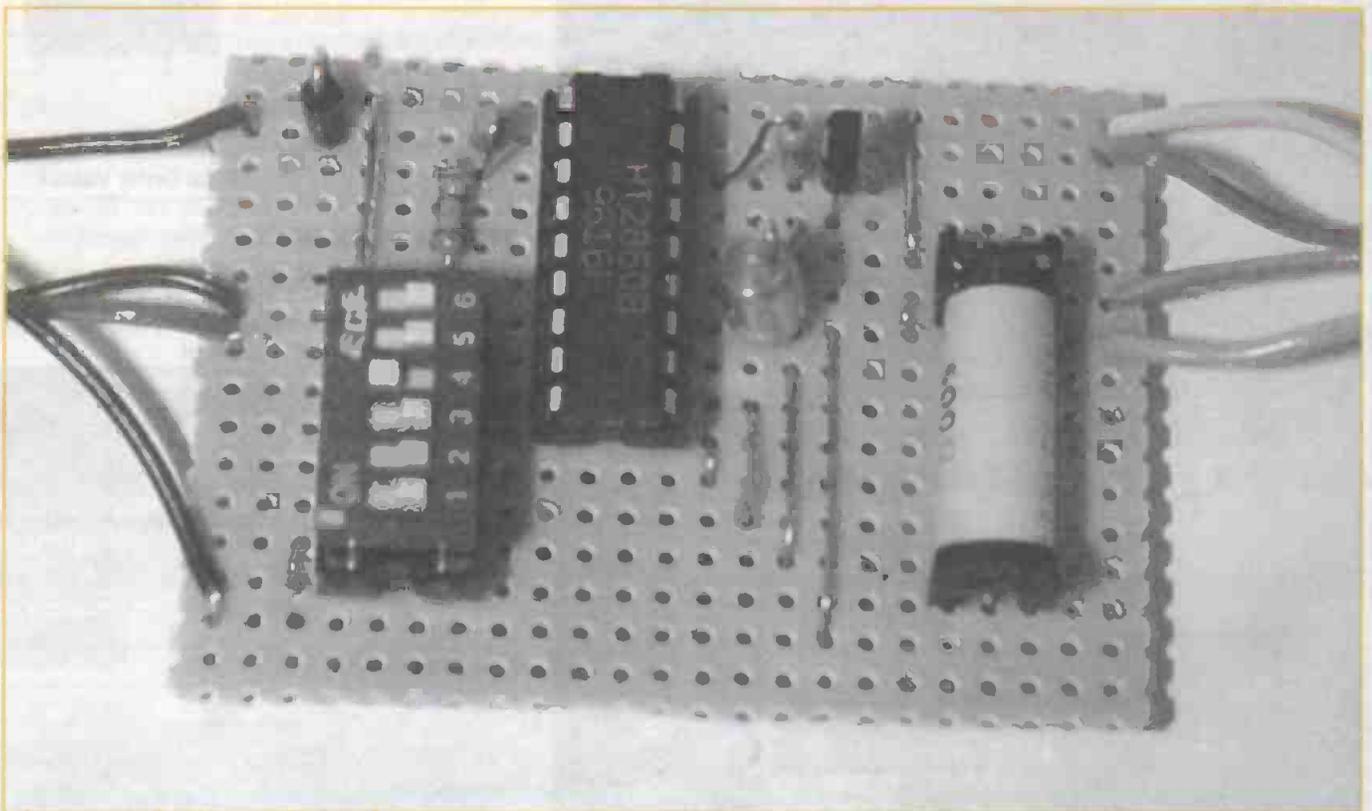
# Sound Effects Module

*Terry Balbirnie continues a series of adaptable circuits for GCSE projects with a module based on the HT2860, a three-oscillator sound effect chip*



**B** In this series we are describing some electronic modules which could be useful to students of GCSE Technology or similar courses at school or college. The circuits may be used in whole or in part for practical projects. All circuits have the potential for further investigative work built in, which could be useful for the more adventurous student. But you can use the circuits as they stand or with only "cosmetic" modifications.

All the designs are laid out on Veroboard. This has the advantage of being similar in layout to the circuit diagram. Some students find PCB layouts difficult to relate to the circuit diagram. Such details as exactly what the circuit is to be used for and how it will be housed are left to the constructor.

### Just for effect

The circuit this month is a Sound Effects Module. This will

provide a effects of four alarms plus a horn and an ambulance sound, and the effect is determined by the setting of a set of miniature switches on the circuit panel. An external push-button or other type of switch is then used to activate the circuit and the sound will be given as long as it is operated. Alternatively, the unit can be operated by some other circuit or system using a reed relay to provide isolation between the parts. In this way, no particular care need be taken to make the two sections "match" - for example, if the two circuits use different supply voltages. Any source of between 5 and 12V and capable of giving 10 to 20 milliamps will be sufficient to drive the coil of the reed relay and hence operate the new circuit.

The Sound Effects Module may be made into part of a toy or a game. It could be used to provide a different sound with each aspect of the game, or for different functions of a toy. It

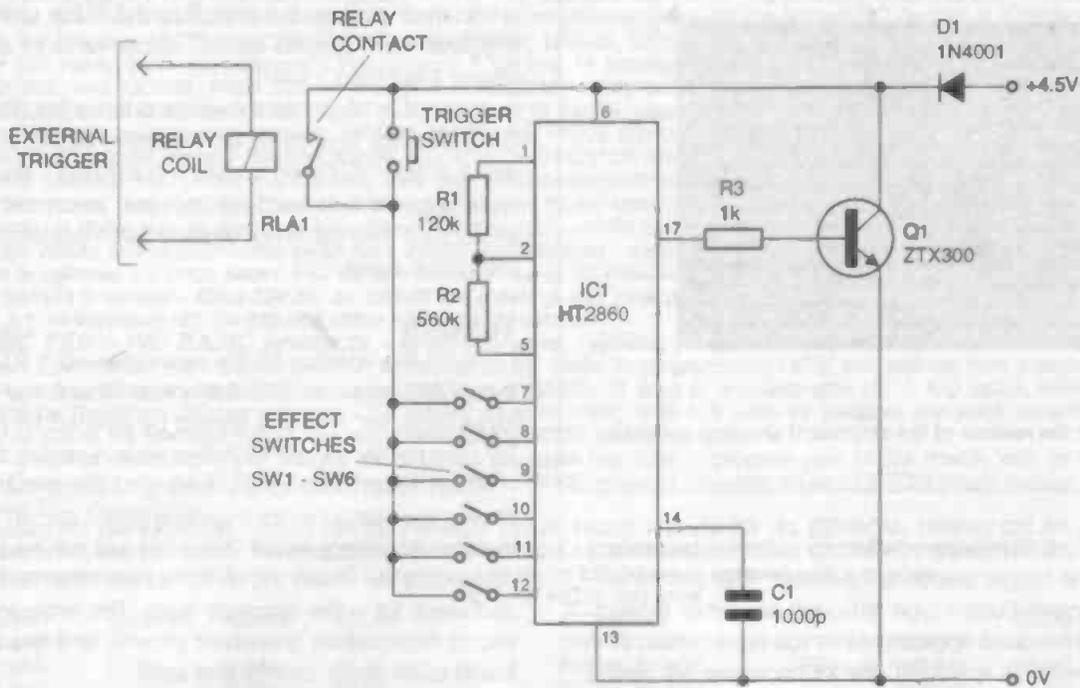


Figure 1: the circuit of the Sound Effects Module

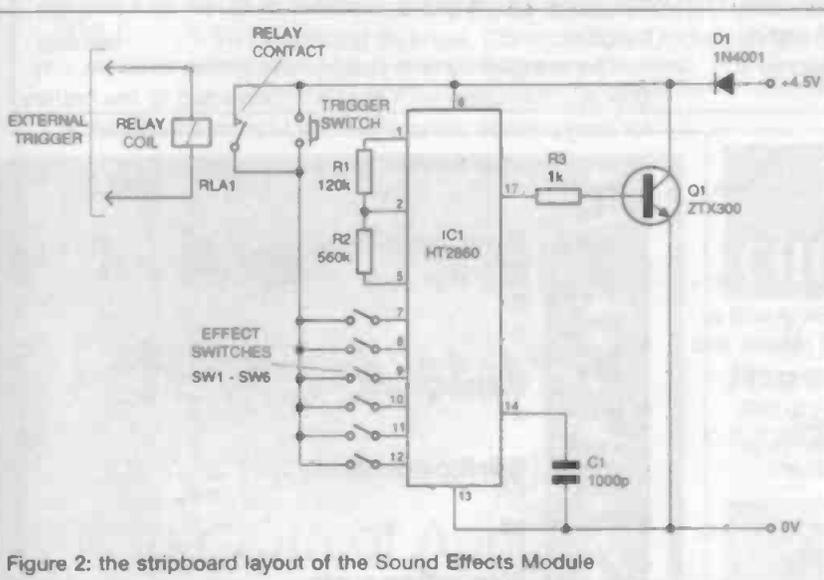


Figure 2: the stripboard layout of the Sound Effects Module

may be that, once the sounds have been heard, a little imagination could be used. They could be called "laser gun" or "phaser missile" for example! By adding a suitable amplifier, the module could be used as the basis for a burglar alarm system or another high-powered warning device.

### Circuit description

The circuit for the Sound Effects Module is shown in figure 1. The circuit requires a supply voltage between 3V and 4.5V. Here, it is provided by three "AA" size alkaline cells in a suitable holder, giving a nominal 4.5V. Diode D1 provides protection to the circuit should the battery be connected in the wrong polarity, since then it would not conduct and no current would flow. In fact, the voltage applied to the circuit is only 3.8V or thereabouts due to the forward voltage drop of this diode.

The circuit centres on IC1, which is a sound effects chip. The effects are pre-programmed into it, so very few additional components are needed to make a working system. The quality of the sounds are controlled by three built-in oscillators (referred to as OSC 1, 2 and 3) and these require two external resistors and one capacitor to make them work. R1 is connected between pin 1 (OSC2) and pin 2 (OSC 1). The other resistor, R2, is connected between pin 2 and pin 5 (OSC3). The capacitor is connected between pins 13 (the 0V "negative" supply input) and 14. Pin 4 could be used to operate an LED while the system is working, but there did not seem to be any point in using it. In addition, the ic has several "test" pins (3, 15, and 16) and, again, these are not used. The positive of the supply (connected via diode D1) is applied to pin 6. The output signal is provided between pin 17 and the 0V line but it

can only give a small current. Some students might like to try a piezo transducer connected to these pins direct. However, most people will wish to use a small loudspeaker. This needs a simple amplifier to provide sufficient current to operate it. This is the purpose of transistor Q1. Current from pin 17 enters its base via current-limiting resistor R3. The much larger collector current then flows through the speaker. Note that the speaker must be of the high impedance type as specified. Do not use an 8-ohm speaker which is the most common type. Note that, even with the amplifier, the sound will not be very loud but should be sufficient for many purposes.

The required effect is obtained by making one of the "effect pins" 7, 8, 9, 10, 11, or 12 high (that is, connecting it to supply positive). This is achieved by pre-selecting it using one of the miniature switches, SW1 to SW6 ("effect switches"). These switches are in a plastic case exactly the same shape as an

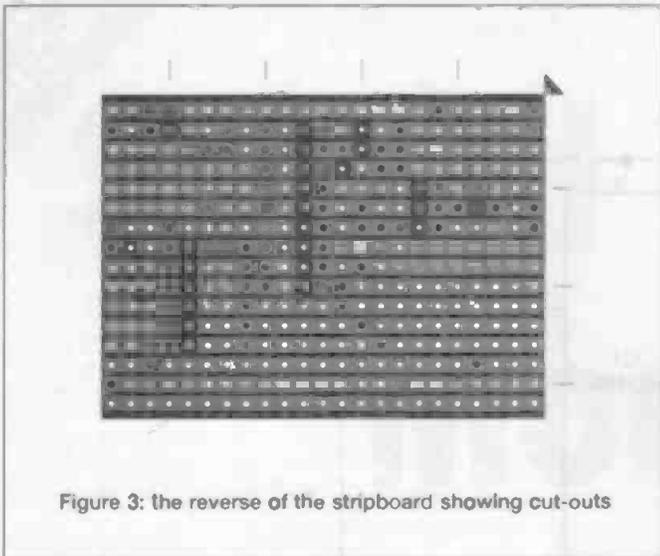


Figure 3: the reverse of the stripboard showing cut-outs

integrated circuit. The required effect pin will then be made high when the trigger switch is operated. This switch is shown as a push-button type although any other type of switch could be used appropriate to the application. When the trigger switch is actuated, the loudspeaker will sound with the desired effect. Some students will wish to provide individual connections to the effect pins so that different switches can be used to give the various effects.

The alternative triggering method is via the "make" contacts of reed relay, RLA1. Its "make" (normally-open) contacts, connected in parallel with the "trigger" switch works in the same way. Its coil could be energised by a signal from another circuit as described earlier.

### Construction

If the circuit is going to be triggered by an external switch, there is no point in including RLA1. Use this only if the circuit is to be operated by some other system.

The topside stripboard layout (component side view) is shown in figure 2. There are several inter-strip links and a number of track breaks needed. Make the track breaks first then solder the link wires in place. If the circuit does not work at the end, it is almost certainly due to a strip not being properly broken, a break or link wire being left out or a blob of solder or sliver of copper bridging adjacent copper tracks - you have been warned!

Solder the ic sockets (one for IC1 and one for the effect switches) and all other components in position. The switches could be soldered to the PCB direct but it is better to use a 12-pin dill socket for them. This size of socket is not readily available. However, it is an easy matter to file a 14-pin unit to size. Alternatively, a 14-pin socket could be simply soldered to the PCB with the extra two pins at the bottom left unused as shown in the photograph. The reason for using an ic socket for the effect switches is because all strips to the left-hand side of them are connected together using a piece of bare copper wire on the copper strip side of the circuit panel. While soldering this wire, considerable heat will be generated and this could damage the switches. Using an ic socket disperses the heat and avoids any likely damage. When soldering this wire, make sure it does not touch anything else and cause a short circuit. Take care to mount diode D1 and the transistor with the correct orientation. Solder the PP3-type battery connector to the "+4.5V and the "0V" points.

Solder short pieces of wire to the trigger ("trigg") positions. Set all but one of the effect switches off (the "on" direction is clearly shown on the switch body). If the unit is to be triggered from another circuit, solder wires to external trigger ("ext trigg") points.

Insert IC1 taking care over its orientation. This is a CMOS device and could be damaged by static charges. To avoid problems, touch something earthed - such as a water tap - before handling the pins. Insert the effect switches if they have not already been soldered direct to the circuit panel.

### Testing

Connect the speaker to the wires marked "LS1". Insert the three "AA" size cells into the holder. Touch the two "trigg" wires together. A sound should be emitted by the speaker. Try using other trigger switches while keeping the rest off.

There is an interesting property of the circuit which shows itself when more than one effect switch is on when the circuit is triggered. If this is tried, it will be found that the effects for which the switches are responsible sound in sequence for a few seconds each. The order in which they sound depends on an in-built priority, and this may be found quite easily by trial and error.

More adventurous candidates may wish to try increasing the volume emitted by the speaker by splitting the supply into 4.5V to the actual circuit and a higher voltage for the transistor section. It would also be possible to add an integrated circuit power amplifier or to use an external amplifier.

The standby current requirement of this circuit is only 8uA approximately so it may be connected to the battery for long periods without the need for an on-off switch.

## PARTS LIST

for the Sound Effects Module

### Resistors

R1	120k
R2	560k
R3	1k

### Capacitors

C1	1000pF
----	--------

### Semiconductors

IC1	HT2860
D1	1N4001

### Miscellaneous

SW1-6	Set of six SPST sub-miniature PCB-mounting switches
LS1	Miniature 60 - 70 ohm loudspeaker
RLA1	Reed relay with SPST contacts and 5V 500 ohm coil - if required (see text)

0.1 in matrix stripboard; holder for three "AA" cells and alkaline cells to fit; PP3-type battery connector; 18-pin dill socket; socket for PCB-mounting switches if required - see text.

IC1 and all other components are available from Maplin. The reed relay is order code JH12N.

## Microchip PIC and Motorola HC11 based development Tools

**PIC Microcontroller Programmers Original** - This is our original programmer for 16C5X, 16C55X, 16C6X, 16C7x, 16C8x, 16F8X devices. Price : £40 for the kit, or £50 ready built. **Serial** - This programmer programs the newest PIC devices in a single 40 pin multi-width ZIF socket. Will program: 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, PIC 14000. Also in-Circuit programming. Price : £40 for the kit, or £50 ready built. **Introductory** - Will program 8 pin and 18 pin devices : 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508, and 12C509. Price £22 for the kit (not available ready built). **Note** : All our programmers operate on a PC, using a standard RS232 serial interface (COM1, 2, 3, or 4). No hard to handle parallel cable swapping ! All programmers are supplied with instructions, Windows programming software, MPASM, MPSIM and PICDE (Windows based PIC assembler )

**PIC or HC11 Windows Based Development:** PICDESIM and HC11DE allows assembly and simulation of your PIC or HC11 projects in one Windows program. Incorporate multiple files, view help file information directly from the code, edit within project, build and track errors directly in the source, then simulate. Simulator allows 3 breakpoint types, follow code in the source window, set breakpoints directly in code. Run programs, or single step, or step over subroutines. Track variable values and trace for display on the Trace Analyser. Input stimuli include clocks, direct values and asynchronous serial data. Profile your program - examine frequently called routines which are timed and use the information to optimise out bottle necks. PIC Version Simulates up to 50 times faster than MPSIM ! **NEW !** - 32 bit version allows full use of Windows '95/NT4.0 facilities. **Cost £30.00, or £25.00 for existing and new purchasers of any of our programmers. Please specify Windows 3.1, or Windows '95 (32 bit) and either PIC or HC11 version**

**PIC BASIC FED's PIC BASIC products** - straightforward, capable, powerful, rapid development. Operating in a Windows Development Environment our modules need no assembler or UV eraser to program your PIC's, and operate from a serial link to your PC. The 16C74 module features - 8k EEPROM, up to 2000 lines of BASIC, 27 lines of programmable I/O, 8 A/D inputs, Interrupt driven serial RS232 interface, Peripheral I2C bus interface, LCD display driver routines, up to 178 bytes for variables and stack, extendible with optional external RAM and all the standard 16C74 features. Ask about the 16C57 version.

**Compiler** - The FED PIC BASIC compiler for the 16C74. It produces hex code to program your 16C74 directly with no need for external EEPROM. Compatible with the EEPROM versions of PIC 16C74 BASIC modules - develop on an EEPROM based module then compile and program your PIC chips directly.

**16C57 Module Kit (8k EEPROM, 4MHz) £25.00, Pre-built £30.00** **16C57 Module Kit (8k EEPROM, 10MHz) £31.00, Pre-built £37.00**  
**16C74 Module Kit (8k EEPROM, 4MHz) £35.00, Pre-built £42.00** **16C74 Module Kit (8k EEPROM, 20MHz) £40.00, Pre-built £46.00**  
**16C84 chip programmed with BASIC - £25.00 Compiler - £60.00, or £50.00 when ordered with a module**

### PIC and HC11 devices

PIC16C74/JW	Erasable	20MHz	£24.00	PIC16C558			£5.00
PIC16C74-04P	OTP	4MHz	£8.00	PIC16C74-20P	OTP	20MHz	£11.00
PIC16C57-04P	OTP	4MHz	£5.00	PIC16C57-10P	OTP	10MHz	£6.00
PIC16C84-04P		4MHz	£6.00	PIC16C84-10P		10MHz	£8.00
PIC16F84-04P		4MHz	£6.00	PIC12C508-04P	OTP	4MHz	£2.20
PIC14000-04P	OTP	4MHz	£10.00	PIC14000/JW		Erasable	£23.00
PIC12C508-04P	OTP	4MHz	£2.70	Motorola MC68HC811E2		Ring for details	

Ask about other chips!



## Forest Electronic Developments

10 Holmhurst Avenue, Christchurch, Dorset, BH23 5PQ 01425-270191 (Voice/Fax)

<http://www.lakewood.win-uk.net/fed.htm> e-mail: [fed@lakewood.win-uk.net](mailto:fed@lakewood.win-uk.net) Prices are inclusive, please add £3.00 for P&P and handling to each order. Cheques/POs payable to Forest Electronic Developments, or phone with credit card details. Serial Cables - £7.50



# Advertisers Please note

copy date for issue 6  
is the 15th of April 98'

## LASERS

Argon ion / Helium Neon / Diode / Carbon Dioxide

Colours include red, yellow, green, turquoise, blue and infra-red. Output powers range from 0.2mW to over 20 Watts. Applications include research, light shows, image projection, medical or industrial. New and Second hand. Pictured here is a 50mW cyan/blue argon ion air cooled laser head and a miniature 1mW red HeNe laser tube only 147mm long. Second hand blue (488nm) argon ion lasers start from only £100 +VAT.



### LASERTECH


Mill Road, Great Barton, Bury St. Edmunds, Suffolk, IP31 2RU  
Telephone 01284 788108 Fax 01284 788135


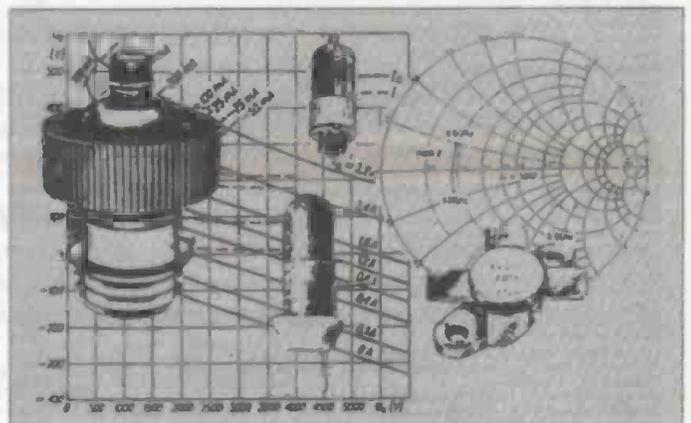
## CHELMER VALVE COMPANY

*If you need Valves/Tubes or RF  
Power Transistors etc. ...then try us!*

We have vast stocks, widespread sources  
and 35 years specialist experience in meeting our  
customers requirements.



*Tuned to the needs of the Radio Amateur*

Chelmer Valve Company, 130 New London Road,  
Chelmsford, Essex CM2 0RG, England.

Tel: 44-01245-355296/265865

Fax: 44-01245-490064



**8 CAVANS WAY,  
BINLEY INDUSTRIAL ESTATE,  
COVENTRY CV3 2SF**  
Tel: 01203 650702  
Fax: 01203 650773  
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

## OSCILLOSCOPES

Beckman 9020 - 20MHz - Dual Channel	£150
Coscor 3102 - 80MHz Dual Channel	£300
Gold OS 245A/250/255/300/335/14000	from £125
Hewlett Packard 180A/180C/181A/182C	from £200
Hewlett Packard 1740A, 1741A, 1744A, 100MHz dual ch	£350
Hewlett Packard 54100B - 1GHz Digitizing	£2995
Hewlett Packard 54300A - 50MHz Dual	£650
Hewlett Packard 54201A - 200MHz Digitizing	£1500
Hitachi V650F - 60MHz Dual Channel	£350
Hitachi V152F/302B/V302F/353F/550B/V650F	from £125
Intron 2020 - 20MHz Digital Storage (NEW)	£850
hwaesu SS 5710/SS 5702 - 20MHz	from £125
Kikusui COS 6100 - 100MHz, 5 Channel, 12 Trace	£475
Kikusui 5100 - 100MHz - Dual Channel	£350
Meguro - MSO 1270A - 20MHz Digital Storage (NEW)	£650
Nicolet 310 - L.F. D.S.O. with twin Disc Drive	£550
Nicolet 3091 - L.F. D.S.O.	£900
Leeroy 8450A - 300MHz/400 Mts D.S.O. 2 ch	£2250
Philips PM 3211/PM 3212/PM 3214/PM 3217/PM 3234/PM 3240/PM 3244/PM 3261/PM 3262/PM 3263/PM 35	from £125
Philips PM 3295A - 400MHz Dual Channel	£1750
Philips PM 3335 - 50 MHz/20Mts D.S.O. 2 ch	£1500
Philips PM 3055 - 50 MHz DUAL Tracebase	£450
Tektronix 434 - 25MHz - 2 Channel Analogue Storage	£250
Tektronix 454 - 150MHz - 2 Channel	£400
Tektronix 468 - 100MHz D.S.O.	£750
Tektronix 2213 - 60MHz Dual Channel	£425
Tektronix 2221 - 60MHz Digital Storage 2 Channel	£1500
Tektronix 2218 - 60MHz Dual trace	£450
Tektronix 2235 - 100MHz Dual trace	£900
Tektronix 2335 - Dual trace 100MHz (portable)	£750
Tektronix 2225 - 50MHz dual ch	£450
Tektronix 2440 - 300 MHz/500 Mts D.S.O. 2 Ch	£3750
Tektronix 455 - 50MHz Dual Channel	£350
Tektronix 464/466 - 100MHz An storage	from £350
Tektronix 465/465B - 100MHz Dual ch	from £350
Tektronix 475/475A - 200MHz/250MHz Dual Channel	from £475
Tektronix 485 - 350MHz - 2 channel	£900
Tektronix 5403 - 60MHz - 2 or 4 Channel	from £250
Tektronix 7313, 7603, 7613, 7823, 7833, 100MHz 4 ch	from £300
Tektronix 7704 - 250MHz 4 ch	from £650
Tektronix 7904 - 500MHz	from £850
Trio CS-1022 - 20MHz - Dual Channel	£125

Other scopes available too

## SPECIAL OFFER

HITACHI V212 - 20MHz DUAL TRACE	£180
HITACHI V222 - 20 MHz DUAL TRACE + ALTERNATE MAGNIFY	£200

## SPECTRUM ANALYSERS

Advantest 4133B - 10KHz - 20GHz (80GHz with external mixers) + Ext. Keyboard	£7250
Advantest 4131B - 10KHz - 3.5GHz	£4950
Ando AC8211 - Spectrum Analyser 1.7GHz	£2950
Anritsu MS610B - 10KHz - 20Hz - (Mini)	£4750
Anritsu MS341A - MS3401B - (10Hz - 30MHz)	£3995 + £4995
Anritsu MS62B - 10KHz - 1700MHz	£2500
AVCOM PS465 S - 500MHz - portable	£995
Hewlett Packard 3580A - 3Hz-800KHz	£3750
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£1000
Hewlett Packard 35601A - Spectrum Analyser Interface	£2500
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser	£900
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser	£900
Hewlett Packard 653A + 8558B - 0.1 to 1500MHz	£3250
Hewlett Packard 182T + 8558B - 0.1 to 1500MHz	£2750
Hewlett Packard 8754A - Network Analyser 4-1300MHz	£2000
Hewlett Packard 8591A - 9KHz - 1.7GHz	£4995
Hewlett Packard 8594E - 9KHz - 2.9GHz	£7000
Hewlett Packard 3582A - 0.02Hz - 25.8KHz (dual ch.)	£2000
Hewlett Packard 3585A - 20Hz - 40MHz	£4995
Hewlett Packard 8754A (opt. H2B) - 4MHz - 2.8GHz	£2950
IFR 7750 10KHz - 1GHz	£3250
Marconi 2370 - 110MHz	£995
Marconi 2371 - 30KHz - 2000MHz	£1250
Meguro MSA 4901 - 1.300GHz (AS NEW)	£1500
Meguro MSA 4912 - 1.10GHz (AS NEW)	£1995
Poird 641-1 - 10MHz - 18GHz	£1500
Rohde & Schwarz - SWOB 5 Polystop 0.1 - 1300MHz	£1800
Takeda Rilken 4132 - 1.0GHz Spectrum Analyser	£2500
Tektronix 7L18 with mainframe (1.5-80GHz with external mixers)	£2000
Tektronix 495P - 100Hz - 1.8GHz programmable	£4950

## MISCELLANEOUS

Adret 740A - 100KHz - 1120MHz Synthesised Signal Generator	£800
ANRITSU ME 462B DF3 Transmission Analyser	£3000
Danbridge JP30A - 30KV Insulation Tester	£1500
Anritsu IQ642A Pulse Pattern Generator	£1500
Dranetz 626 - AC/DC - Multifunction Analyser	£850
EIP 331 - Frequency counter 18GHz	£700
EIP 545 - Frequency counter 18GHz	£1500
EIP 545A - Frequency counter 18GHz	£1600
EIP 575 - Frequency counter 18GHz	£1750
Farnell AP70-30 Power Supply (0.7-70V/30A) Auto Flanging	£750
Farnell TSV-70 MKII Power Supply (70V - 5A or 35V - 10A)	£250
Farnell DSG-1 Synthesised Signal Generator	£125
Farnell ESG-1000 Synthesised Signal Generator 1GHz (as new)	£1650
Fluke 5100A - Calibrator	£2500
Guidline 9152 - T12 Battery Standard Cell	£550
Hewlett Packard 331A - Distortion Analyser	£300
Hewlett Packard 3336C - Synthesised Signal Generator (10KHz - 21MHz)	£1000
Hewlett Packard 3437A System Voltmeter	£350
Hewlett Packard 3456A Digital Voltmeter	£850
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 3488A - Switch Control Unit	£850
Hewlett Packard 35600A Dual Ch. Dynamic Signal Analyser	£3750
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser	£2250
Hewlett Packard 3325A - 21MHz Synthesised Function Gen	£1500
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available)	£999
Hewlett Packard 3455A 8 1/2 Digit M-Meter (Audlocal)	£550
Hewlett Packard 3476A - Multimeter (5 1/2 Digit) - HP - 1B	£1000
Hewlett Packard 3585A - Selective Level Meter	£999
Hewlett Packard 3776A - PCM Terminal Test Set	£1500
Hewlett Packard 3779A/3779C - Primary Mux Analyser	from £800
Hewlett Packard 3784A - Digital Transmission Analyser	£4995
Hewlett Packard 37900D - Signalling Test Set (No 7 and ISDN)	£6000
Hewlett Packard 4262A - Digital LCR Meter	£1350
Hewlett Packard 4275A - LCR Meter (Multi-Frequency)	£3950
Hewlett Packard 4338A - Milliammeter (As New)	£2000
Hewlett Packard 4342A $\Omega$ Meter	£995

Hewlett Packard 435A or B Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 4279A - 1MHz C-V Meter	£999
Hewlett Packard 4948A - (TMS) Transmission Impairment M-Set	£1500
Hewlett Packard 4972A - Lan Protocol Analyser	£1750
Hewlett Packard 5420A Digital Signal Analyser	£350
Hewlett Packard 5335A - 200MHz High Performance Systems Counter	£600
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter	£250
Hewlett Packard 5318A - Universal Counter (IEEE)	£500
Hewlett Packard 5183 - Waveform Recorder	£1750
Hewlett Packard 5238A Frequency Counter 100MHz	£250
Hewlett Packard 5370A - 100MHz Universal Timer/Counter	£450
Hewlett Packard 5384A - 225 MHz Frequency Counter	£650
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/008	£995
Hewlett Packard 6253A Power Supply 20V - 3A Test	£200
Hewlett Packard 6255A Power supply 40V - 1.5A Test	£200
Hewlett Packard 6268B Power Supply 40V - 3A	£220
Hewlett Packard 6271B Power supply 60V - 3A	£225
Hewlett Packard 6622A - Power Supply, Dual O/P	£1650
Hewlett Packard 6623A - Power Supply, Triple O/P	£1750
Hewlett Packard 6652A - Power Supply (0 - 20V, 0 - 25A)	£1250
Hewlett Packard 6264B - Power Supply (0 - 20V, 0 - 25A)	£400
Hewlett Packard 7475A - 6 Pen Plotter	£999
Hewlett Packard 7550A - 6 Pen Plotter A3/A4	£450

## HEWLETT PACKARD 6261B Power Supply 20V-50A £450 Discount for Quantities

Hewlett Packard 83555A - Millimeter - Wave source Module 33-50GHz	£4250
Hewlett Packard 8015A - 50MHz Pulse Generator	£750
Hewlett Packard 8405A - Vector Voltmeter	£350
Hewlett Packard 8165A - 50MHz Programmable Signal Source	£1950
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various Plug-ins available) extra	£2850
Hewlett Packard 8152A - Optical Average Power Meter	£1250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011)	£1100
Hewlett Packard 8160A - Data Generator	£1800
Hewlett Packard 8182A - Data Analyser	£1500
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various plug-in options available)	£2500
Hewlett Packard 8354A - Wave Source Module 26.5 to 40GHz	£3500
Hewlett Packard 8620C - Sweep oscillator mainframe	from £250
Hewlett Packard 8656A - Synthesised Signal Generator (900MHz)	£2000
Hewlett Packard 8656B - Synthesised Signal Generator	£2000
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 8750A - Scalar Network Analyser	£1500
Hewlett Packard 8757A - Scalar Network Analyser	£2250
Hewlett Packard 8903A - Audio Analyser (20Hz - 100KHz)	£2800
Hewlett Packard 8903E - Distortion Analyser (Mini)	£2000
Hewlett Packard 8958A - Cellular Radio Interface	£2000
Hewlett Packard 8901A - Modulation Analyser	£3400
Hewlett Packard 8920A - R/F Comms Test Set	£6000
Hewlett Packard 8922b - GSM Radio Comms Test Set	£9995
Hewlett Packard P382A Variable Attenuator	£250
Hewlett Packard 16300 - Logic Analyser (43 Channels)	£850
Hewlett Packard 16500A - Fitted with 16510A/16515A/16530A/16531A - Logic Analyser	£4000
Hewlett Packard 11729B - Carrier Noise Test Set	£999
Krohn-Hite 2200 Lin/Log Sweep Generator	£300
Krohn-Hite 4024A Oscillator	£250
Krohn-Hite 5200 Sweep Function Generator	£350
Krohn-Hite 6500 Phase Meter	£250
Leader 3216 - Signal Generator (100KHz - 140MHz) AM/FM/CW with built-in FM stereo modulator (mini)	£995
Marconi 2019 - 80KHz - 1040MHz Synthesised Sig Gen	£1450
Marconi 2019A - 80KHz - 1040MHz - Synthesised Signal Generator	£1600
Marconi 2022A - 10KHz - 1GHz AM/FM Signal Generator	£2000
Marconi 2041 - (10KHz - 2.7GHz) Low Noise	£7500
Marconi 2305 - Modulation Meter	£1995
Marconi 2610 - True RMS Voltmeter	£850
Marconi 2671 Data Comms Analyser	£1000
Marconi 2955 - Radio Comms Test Set	£2000
Marconi 6950 - Power Meter & Sensor	from £950
Philips PM 5167MHz function gen	£400
Philips 5190 L.F. Synthesiser (G.P.I.B.)	£800
Philips 5193 Synthesised Function Generator	£1500
Philips 5518 Synthesised Function Generator	£1500
Philips PM5518 - TV Pattern Generator	£350
Philips PM5718 - 50MHz Pulse Generator	£525
Philips PM6652 - 1.5GHz Programmable High Resolution Timer/Counter	£900
Philips PM6673 - 120MHz High Resolution Universal Counter	£430
Prema 4000 - 6 1/2 Digit Multimeter (NEW)	£450
Racal 1992 - 1.3GHz Frequency Counter	£800
Racal Dana 9061/9082 Synth sig gen 520MHz	from £500
Racal Dana 9084 Synth sig gen 104MHz	£450
Racal Dana 9303 R/F Level Meter & Head	£999
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9302A R/F multivoltmeter (new version)	£375
Racal Dana 9082 Synthesised am/fm sig gen (520MHz)	£500
Racal 9301A - True RMS R/F Multivoltmeter	£300
Racal 6111/6151 - GSM Radio Comms Test Set	£POA
Rohde & Schwarz LFM2 - 60MHz Group Delay Sweep Gen.	£1600
Rohde & Schwarz Scud Radio Code Test Set	£300
Rohde & Schwarz CMS 54 Radio Comms Monitor	£6250
Rohde & Schwarz CMTA 94 GSM Radio Comms Analyser	£7500
Schaffner NSG 203A Line Voltage Variation Simulator	£950
Schaffner NSG 222A Interference Simulator	£850
Schaffner NSG 223 Interference Generator	£850
Schaffner W50 431 Electrostatic Discharge Simulator	£1250
Schlumberger 4031 - 1GHz Radio Comms Test Set	£4995
Schlumberger 2720 1250MHz Frequency Counter	£500
Schlumberger 7060/7065/7075 Multimeters	from £350
Schlumberger Stabilock 4040 Radio Comms Test Set	£3500
Solartron 1250 - Freq. Response Analyser	£2500
Stanford Research DS 340 - 15MHz Synthesised Function (NEW) and arbitrary waveform generator	£1200
Syston Donner 6030 - Microwave Frequency Counter (26.5GHz)	£2500
Tequipment CT71 Curve Tracer	£350
Tektronix TM5003 + AFG 5101 Arbitrary Function Gen.	£1800
Tektronix 1240 Logic Analyser	£500
Tektronix DAS9100 - Series Logic Analyser	£500
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PG508, FG504, FG503, TG501, TR503 & many more	£POA
Tektronix AM503 + TM501 + PG302 - Current Probe Amp/Probe	£995
Tektronix PG506 + TG501 + SG503 + TM503 - Oscilloscope Calibrator	£1995
Tektronix AA5001 & TM5006 M/F - Programmable Distortion Analyser	£1995
Tektronix 577 - Curve Tracer	£1150
Time 9811 Programmable Resistance	£400
Time 9814 Voltage Calibrator	£550
Toelner 7720 - Programmable 10MHz Function Gen (AS NEW)	£999
Valhalla Scientific - 2724 Programmable Resistance Standard	£POA
Wandel & Goettermann PF-J-8 - Error/Jitter Test Set	£12500
Wandel & Goettermann PCM4	£11000
Wandel & Goettermann PCM4 (+ options)	£9950
Wayne Kerr 4226 - LCR Bridge	£999
Wayne Kerr 6425 - Precision Component Analyser	£275
Wayne Kerr 8905 - Precision LCR Meter	£850
Wavetek 171 - Synthesised Function Generator	£250
Wavetek 172B Programmable Sig Source (0.0001Hz - 13MHz)	£POA
Wavetek 184 - Sweep Generator - 5MHz	£250
Wavetek 3010 - 1-1GHz Signal Generator	£1250
Wiltron 6409 - RF Analysers (1MHz - 20GHz)	£POA
Wiltron 6620S - Programmable Sweep Generator (3.6 - 6.5GHz)	£650

MANY MORE ITEMS AVAILABLE -  
SEND LARGE S.A.E FOR LIST OF EQUIPMENT  
ALL EQUIPMENT IS USED -  
WITH 30 DAYS GUARANTEE  
PLEASE CHECK FOR AVAILABILITY BEFORE  
ORDERING - CARRIAGE & VAT TO BE ADDED  
TO ALL GOODS

# The Orphan Decibel

**Power variations are better represented in a logarithmic rather than a linear manner. This is accomplished by the use of the decibel - but what is a decibel?**

**By E.Chicken MBE FIEE**

"Decibel" clearly means one tenth of a bel, but have you wondered why one never hears of a "bel", or for that matter a millibel, megabel or kilobel? Well, the truth is that they do not exist. This is not quite the truth, perhaps, because in theory the "bel" is still out there somewhere but its story is rarely told - or perhaps that should be "told", as the bel lost one "l" when it first appeared more than 70 years ago. The lone bel was doomed to disappearance because of its inconvenient dimension, somewhat like (and likewise despite its eminent inventor) the farad.

Named after Alexander Graham Bell, inventor of the telephone, the bel replaced in 1924 the "transmission unit" which had been introduced the year before into the field of line telephony by the American Telephone and Telegraph Company (ATT). The bel was intended to equal 10 of ATT's "transmission units".

The "transmission unit" itself had replaced an even earlier concept based on the ratio between the decrease in signal power produced by a given telephone cable and that produced in one mile of standard cable. In 1924, an international advisory committee on long distance telephony in Europe, in cooperation with American representatives of the Bell telephone system, agreed to recommend the adoption as standard of either the *bel* or the *neper*, both of which were loosely referred to as units.

The bel was to be a unit based on logarithms to the base 10, while the neper (named after Napier) would be based on Napierian logarithms to the base 2.71828. The neper was later used to some extent in Europe, but is not often met today. Both units were intended as a means of expressing power ratios, and gain or loss of power-related quantities such as voltage and current. But in practice, one bel was too large, so it was scaled down some 5 years later to one tenth of a bel, becoming the *decibel*, abbreviated to *dB*. (And in retrospect, it looks remarkably like the equivalent of the earlier "transmission unit" that it sought to replace.) But since then, the decibel (dB) has become a very useful and much used mathematical tool, particularly in electrical engineering and acoustics, although I will only consider the former here.

## Power

Strictly speaking, the original mathematical expression for bel relates only to power ratios. Two powers (say  $P_1$  and  $P_2$ ) are said to differ by  $N$  bels (where  $N$  is a number), when:

$$\text{their power ratio } P_1 / P_2 = 10^N$$

which when converted into logarithm form becomes:

$$N \text{ bels} = \log_{10} (P_1 / P_2)$$

and because 1 bel = 10 decibels, this becomes:

$$N \text{ decibels} = N \text{ dB} = 10 \log_{10} (P_1 / P_2)$$

It is important to note that this expression defines a *number* of decibels, not the decibel as a *unit*, so, strictly speaking, one can refer to a decibel or to one decibel, but not to the decibel. Nor is decibel a metric unit of measurement or quantity, which is why it does not appear in the Systeme International d'Unites or SI System. In that metric system, the product or quotient of any two quantities is the unit of the resultant quantity: for example, volt x ampere = watt, each of which can be expressed in decimal multiples or sub-multiples such as mega-, milli-, and so on.

Decibel however, cannot be multiplied or divided by any SI Unit to produce another SI Unit, nor can it adopt other decimal multiples or sub-multiples in place of deci-. It is an orphan in the field of electrical engineering measurement, because it is really no more than a mathematical tool (as is the logarithm), whereby the products or quotients of large numbers can be more simply handled by the addition or subtraction of dB quantities. Examples of this are given later.

Note that a ratio such as 2/1 produces a positive number of decibels, whereas a 1/2 ratio would produce a negative logarithm and a negative number of decibels. Positive decibels add to simulate multiplication, whereas negative decibels subtract to simulate division, for example:

$$(+10\text{dB} - 3\text{dB}) = (x 10/2) = x 5 = 7\text{dB}$$

But for convenience of use, rather than referring to power ratios, it is better to refer to power gain or loss. In which case, +dB represents a power gain, and -dB a power loss or attenuation.

## Voltage

As said earlier, dB can also be applied to derivatives of power such as voltage and current, but using a slightly modified expression based on the relationship power  $P = E^2 / R$ , as follows:

$$N \text{ dB} = 10 \log_{10} (P_1 / P_2)$$

now re-written as:

$$N \text{ dB} = 10 \log_{10} \frac{(E_1)^2 / R}{(E_2)^2 / R}$$

and cancelling the  $R/R = 10 \log_{10} (E_1^2 / E_2^2) = 10 \log_{10} (E_1 / E_2)^2$

## £1 BARGAIN PACKS

If you would like to receive the other four £1 lists and a lot of other lists, request these when you order or send SAE.

**TEST PRODS FOR MULTIMETERS** with 4mm sockets. Good length very flexible lead. Ref: D86.

**8 OHM PM SPEAKERS**, size 8" x 4", pack of two. These may be slightly rusty and that is why they are so cheap but are electrically OK. Ref: D102.

**PAXOUN PANELS**, size 8" x 6", approximately 1/18" thick, pack of two. Ref: D103.

**13A SOCKET**, virtually unbreakable, ideal for trailing lead. Ref: D95.

**PIEZO BUZZER** with electronic sounder circuit, 3V to 9V D.C. operated. Ref: D76.

**DITTO** but without internal electronics, pack of two. Ref: D75.

**LUMINOUS ROCKER SWITCH** approximately 30mm sq. pack of two. Ref: D64.

**ROTARY SWITCH**, 9-pole, 5-way, small size 77 spindle, pack of two. Ref: D54.

**FERRITE RODS**, 7" with coils for Long and Medium waves, pack of two. Ref: D52.

**DITTO** but without coils, pack of three. Ref: D52.

**MAINS DP ROTARY SWITCH** with 1/4" control spindle, pack of five. Ref: D49.

**ELECTROLYTIC CAP**, 800µF at 6.4V, pack of 20. Ref: D48.

**ELECTROLYTIC CAP**, 1000µF + 100µF 12V, pack of 10. Ref: D47.

**MINI RELAY** with 5V coil, size only 26mm x 19mm x 1mm, has two sets of changeover contacts. Ref: D42.

**MAINS SUPPRESSOR CAPS** 1µF 250V A.C., pack of 10. Ref: 1050

**TELESCOPIC AERIAL**, chrome plated, extendable and folds over for improved F.M. reception. Ref: 1051.

**MES LAMP HOLDERS**, slide on to 1/4" tag, pack of 10. Ref: 1054

**PAXOUN TUBING** 3/16" internal diameter, pack of two, 12" lengths. Ref: 1056.

**ULTRA THIN DRILLS**, 0.4mm, pack of 10. Ref: 1042.

**20A TOGGLE SWITCHES**, centre off, part spring controlled, will stay on when pushed up but will spring back when pushed down, pack of two. Ref: 1043.

**HALL EFFECT DEVICES**, mounted on small heatsink, pack of two. Ref: 1022.

**12V POLARISED RELAY**, two changeover contacts. Ref: 1032.

**PAXOUN PANEL** 12" x 12" 1/16" thick. Ref: 1033.

**MINI POTTED TRANSFORMER**, only 1.5VA 15V-0V-15V or 30V. Ref: 964.

**ELECTROLYTIC CAP**, 32µF at 350V and 50µF section at 25V, in aluminium can for upright mounting, pack of two. Ref: 995.

**PRE-SET POTS**, one megohm, pack of five. Ref: 998.

**WHITE PROJECT BOX** with rocker switch in top left-hand side, size 78mm x 115mm x 35mm, unpainted. Ref: 1006.

**5V SOLENOID**, good strong pull but quite small, pack of two. Ref: 1012.

**FIGURE-8 MAINS FLEX**, also makes good speaker lead, 15m. Ref: 1014.

**HIGH CURRENT RELAY**, 24V A.C. or 12V D.C., three changeover contacts. Ref: 1016.

**LOUDSPEAKER**, 8 Ohm 5W, 3.7" round. Ref: 962.

**NEON PILOT LIGHTS**, oblong for front panel mounting, with internal resistor for normal mains operation, pack of four. Ref: 970.

**3.5MM JACK PLUGS**, pack of 10. Ref: 975.

**PSU**, mains operated, two outputs, one 9.5V at 550mA and the other 15V at 150mA. Ref: 968.

**ANOTHER PSU**, mains operated, output 15V A.C. at 320mA. Ref: 969.

**PHOTOCELLS**, silicon chip type, pack of four. Ref: 939.

**LOUDSPEAKER**, 6" 4 Ohm 5W rating. Ref: 939.

**LOUDSPEAKER**, 7" x 6" 4 Ohm 5W. Ref: 949.

**LOUDSPEAKER**, 4" circular 6 Ohm 3W, pack of 2. Ref: 951.

**FERRITE POT CORES**, 30mm x 15mm x 25mm, matching pair. Ref: 901.

**PAXOUN PANEL**, 8 1/2" x 3 1/2" width electrolytics 250µF and 100µF. Ref: 905.

**CAR SOCKET PLUG** with P.C.B. compartment. Ref: 917.

**FOUR-CORE FLEX** suitable for telephone extensions, 10m. Ref: 918.

**PROJECT CASE**, 95mm x 66mm x 23mm with removable lid, held by four screws, pack of two. Ref: 876.

**SOLENOIDS**, 12V to 24V, will push or pull, pack of two. Ref: 877.

**2M MAINS LEAD**, 3-core with instrument plug moulded on. Ref: 879

**TELESCOPIC AERIAL**, Chrome plated, extendable, pack of two. Ref: 884.

**MICROPHONE**, dynamic with normal body for hand holding. Ref: 886

**CROCODILE CLIPS**, superior quality flex, can be attached without soldering, five each red and black. Ref: 886

**BATTERY CONNECTOR FOR PP3**, superior quality, pack of four. Ref: 887.

**LIGHTWEIGHT STEREO HEADPHONES** Ref: 888.

**PRESETS**, 470 Ohm and 220 kilohm, mounted on single panel, pack of 10. Ref: 849.

**THERMOSTAT** for ovens with 1/4" spindle to take control knob. Ref: 857.

**12V-0V-12V 10W MAINS TRANSFORMER**. Ref: 811.

**18V-0V-12V 10W MAINS TRANSFORMER**. Ref: 813.

**AIR-SPACED TRIMMER CAPS**, 2pF to 20pF, pack of two. Ref: 818.

**AMPLIFIER**, 9V or 12V operated Multitard 1153. Ref: 823.


**2 CIRCUIT MICROSWITCHES**, Ikon, pack of 4. Ref: 825.

**LARGE SIZE MICROSWITCHES** changeover contacts, pack of two. Ref: 825.

**MAINS VOLTAGE PUSH SWITCH** with white dolly, through panel mounting by hexagonal nut. Ref: 829.

**POINTER KNOB** for spindle which is just under 1.4", like most thermostats, pack of four. Ref: 833.
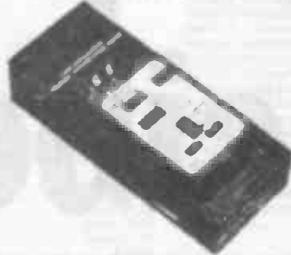
## CAMCHARGER CAMCORDER BATTERY QUICK CHARGER (WITH RECONDITIONER & TESTER)



Brand new and boxed. Normal price £35, yours for £18. Order Ref: 15P73.

## TOROIDAL MAINS TRANSFORMERS

All with 220/240V primary winding. 0.30V + 0.30V at 120VA, would give you 30V at 4A or 60V at 2A, price £8. Order Ref: 8P2. Order Ref: 8P2. 0.110V + 0.110V at 120VA would give you 110V at just over 8A or 220V at 1/2A, price £8. Order Ref: 8P3. 0.35V + 0.35V at 150VA would give you 35V at 4A or 70V at 2A. Price £8. Order Ref: 8P6. 0.35V + 0.35V at 220VA would give you 35V at 6 1/2A or 70V at 3 1/4A, price £9. Order Ref: 9P4. 0.110V + 0.110V at 220VA would give you 110V at 2A or 220V at 1A, price £10. Order Ref: 10P6. 0.45V + 0.45V at 500VA would give you 45V at 11A or 90V at 6 1/2A, price £20. Order Ref: 20P7. 0.110 + 0.110V at 500VA would give you 110V at 5A or 220V at nearly 3A, price £25. Order Ref: 25P7.



**SUPER WOOFERS**. A 10" 4ohm with a power rating of 250W music and normal 150W. Normal selling price for this is £85 + VAT, you can buy at £29 including VAT and carriage. Order Ref: 29P7. The second one is a 8" 4ohm, 200W music, 200W normal. Again by Challenger, price £18. Order Ref: 18P9. Deduct 10% from these prices if you order in pairs or can collect. These are all brand new in maker's packing.



## SOLDERING IRON

Super mains powered with long life ceramic element, heavy duty 40W for that extra special job. Complete with plated wire stand and 245mm leads, £3. Order Ref: 3P221.

## YOU SAVE £40

THE JAP MADE 12V 12A SEALED BATTERY from regular suppliers costs £50, you can have one from us for only £10 including VAT if you collect or £12 if we have to send. Being sealed it can be used in any position and is maintenance free. All in tip top condition and fully guaranteed. Order Ref: 12P32. Or if you want a smaller one we have 12V 2.3AH, regular price £14, yours for only £3.50. Order Ref: 3.5P11.



**FLASHING BEACON**. Uses an XENON tube and has amber-coloured dome with separate bracket. 12V operated. Price only £5. Order Ref: 5P 267.

**HIGH RESOLUTION MONITOR**, 9" by Philips, in metal frame for easy mounting. Brand new, offered at less than the price of the tube alone. £15. Order Ref: 15P1.

**15W 8" SPEAKER AND 3" TWEETER**. Amstrad, made for their high quality music centre. £4 per pair. Order Ref: 4P57.

**INSULATION TESTER WITH MULTIMETER**. Internally generates voltages which enables you to read insulation directly in megohms. The multimeter has four ranges, AC/DC Volts, 3 ranges millamps, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P4.

We have some of the above testers but slightly faulty, not working on all ranges, should be repairable, we supply, diagram, £3. Order Ref: 3P176.

**250W LIGHT DIMMER**. Will fit in place of normal wall switch, only £2 each. Order Ref: 2P380. Note these are red, blue, green or yellow but will take omission to suit the colour of your room. Please state colour required.

**LCD 3 1/2" DIGIT PANEL METER**. This is a multi-range voltmeter/ammeter using the A-D converter chip 7106 to provide five ranges each of volts and amps. Supplied with full data sheet. Special snap price of £12. Order Ref: 12P19.

**MINI BLOW HEATER**, 1kW, ideal for under desk or airing cupboard, etc. Needs only a simple mounting frame, £5. Order Ref: 5P23.

**MEDICINE CUPBOARD ALARM**. Will warn when cupboard door is opened. Light makes the bell ring. Neatly cased, requires only a battery, £3. Order Ref: 3P155.

**DON'T LET IT OVERFLOW**. Be it bath, sink, cellar, sump, etc., this device will tell you when the water has risen to the pre-set level. Adjustable, neatly cased for wall mounting, £3. Order Ref: 3P156.

**DIGITAL THERMOMETER**. Suitable for outdoors or indoors, has an extra wide temperature range -50° to +70°C, complete with heavy duty battery which should last several years. Its sensor can be outside, but with the read-out inside, £4. Order Ref: 4P104.

## SMART HIGH QUALITY ELECTRONIC KITS

All kits are complete with PCB and other components in a blister pack. If you want more information about them, we have copies of the illustrated Smart catalogue available price £1.

Cat. No.	Description	Price £	Cat. No.	Description	Price £
1003	5 watt electronic siren	2.55	1089	L.E.D. Flasher/555 tester	1.61
1005	Touch switch	2.87	1090	Stress meter	3.22
1008	SF function generator	6.90	1093	Windscreen wiper controller	3.68
1010	5-input stereo mixer, with monitor output	19.31	1094	Home alarm system	12.42
1016	LOUDspeaker protection unit	3.22	1095	Lead acid battery charger	3.45
1017	Linear CB 30W amp	4.70	1100	2 x 18 watt integrated amplifier	18.39
1020	0.5 min. time switch	4.70	1101	Dollar tester	4.70
1023	Dynamic headphone preamp	2.50	1103	L.E.D. power meter	1.84
1025	7 watt hi-fi power amplifier	2.53	1106	Thermometer with L.e.d.s.	6.90
1026	Running lights	4.60	1107	Electronics to help win the pools	3.88
1027	NiCad battery charger	3.91	1112	LOUDspeaker protection with delay	4.60
1030	Light dimmer	2.53	1113	2 x 18 watt power amplifier	5.98
1032	Stereo tone control	3.55	1115	Courtesy light delay	2.07
1035	Space sound effects	2.30	1118	Xmas-switch, with triac, 0.10 mins	4.14
1039	Stereo VU meter	4.60	1119	Telephone line recording device	5.25
1042	AF generator 250Hz-16kHz	1.70	1123	Morse code generator	1.84
1043	Loudness stereo unit	3.22	1124	Electronic bell	2.76
1047	Sound switch	5.29	1125	Telephone lock	2.68
1048	Electronic thermostat	3.68	1126	Microphone preamplifier	4.60
1050	3-input hi-fi stereo preamplifier	12.42	1127	Microphone tone control	4.60
1052	3-input mono mixer	6.21	1128a	Power flasher 12V d.c.	2.53
1053	Electronic metronome	3.22	1133	Stereo sound-to-light	5.26
1054	4-input instrument mixer	2.76			
1056	8V-20V 8A stabilised power supply	12.42			
1057	Cassette head preamplifier	3.22			
1059	Telephone amplifier	4.60			
1060	+40V B A power supply	8.28			
1061	12V 1/2A stabilised power supply	3.38			
1062	5V 0.5A stabilised supply for TTI	2.30			
1063	12V 2A power supply	2.30			
1064	+12V 0.5A stabilised supply	3.22			
1067	Stereo VU meter with leads	9.20			
1068	18V 0.5A stabilised power supply	2.53			
1070	Hi-Fi preamplifier	7.47			
1085	D.C. converter: 12V to 6V or 7.5V or 9V	2.53			
1086	Music-to-light for your car	4.60			

### TERMS

Send cash, PO, cheque or quote credit card number - orders under £25 add £3.50 service charge.

**J & N FACTORS**  
Pilgrim Works (Dept. E.T.I.)  
Stairbridge Lane, Bolney,  
Sussex RH17 5PA  
Telephone: 01444 881965

which, by using the mathematical expression  $\log_{10}(x^2) = 2\log_{10}(x)$ , can be re-written as:

$$2 \times 10 \log_{10}(E_1/E_2)$$

hence, in terms of voltage E:

$$N \text{ dB} = 20 \log_{10}(E_1/E_2)$$

**Current**

Similarly in terms of current I, using the relationship power  $P = I^2 R$ , yields:

$$N \text{ dB} = 20 \log_{10}(I_1/I_2)$$

Some examples follow. Note that all examples deliberately use approximated numerical values:

In power terms:

a power-gain of x2 (ratio 2/1), gives:

$$N = 10 \log_{10}(2) = 10 \times 0.3 = 3 \text{ dB}$$

a power-gain of x5 (ratio 5/1), gives:

$$N = 10 \log_{10}(5) = 10 \times 0.7 = 7 \text{ dB}$$

a power-gain of x10 (ratio 10/1), gives:

$$N = 10 \log_{10}(10) = 10 \times 1.0 = 10 \text{ dB}$$

In voltage terms:

a voltage-gain of x1.4 (ratio 1.4/1), gives:

$$N = 20 \log_{10}(1.4) = 20 \times 0.15 = 3 \text{ dB}$$

a voltage-gain of x2 (ratio 2/1), gives:

$$N = 20 \log_{10}(2) = 20 \times 0.3 = 6 \text{ dB}$$

a voltage-gain of x3 (ratio 3/1), gives:

$$N = 20 \log_{10}(3) = 20 \times 0.5 = 10 \text{ dB}$$

a voltage gain of x10 (ratio 10/1), gives:

$$N = 20 \log_{10}(10) = 20 \times 1 = 20 \text{ dB}$$

Applying the above dB values to obtain an acceptably near approximation of power or voltage gain:

Example 1: Power-gain of 33dB is here converted to its numerical power gain.

$$\begin{aligned} 33\text{dB} &= 10\text{dB} + 10\text{dB} + 10\text{dB} + 3 \text{ dB} \\ &= 10 \times 10 \times 10 \times 2 \\ &= \text{power gain of } x2000 \text{ (cf } x1995 \text{ true)} \end{aligned}$$

Example 2: Power-gain of 67dB is here converted to its numerical power gain.

$$\begin{aligned} 67\text{dB} &= (10+10+10+10+10+10+7) \text{ dB} \\ &= (10 \times 10 \times 10 \times 10 \times 10 \times 10 \times 5) \\ &= \text{power gain of } 5 \times 10^6 \text{ (cf } 5.01 \times 10^6) \end{aligned}$$

Example 3: Voltage-gain of 36 dB is here converted to its numerical voltage gain.

$$\begin{aligned} 36\text{dB} &= 20\text{dB} + 10\text{dB} + 6\text{dB} = 10 \times 3 \times 2 \\ &= \text{voltage gain of } x60 \text{ (cf } x63.1 \text{ true)} \end{aligned}$$

Example 4: Voltage-gain of 126dB is here converted to its numerical voltage-gain.

$$\begin{aligned} 126\text{dB} &= (20+20+20+20+20+20+6) \text{ dB} \\ &= (10 \times 10 \times 10 \times 10 \times 10 \times 10 \times 2) \\ &= \text{voltage-gain } 2 \times 10^6 \text{ (cf } 1.995 \times 10^6 \text{ true)} \end{aligned}$$

It is clear from the above that:

In terms of power:

3 dB means a multiplication by 2, ie twice the original power  
10dB means a multiplication by 10, ie ten times the original power

Similarly, a negative dB figure implies division:

-3dB means a division by 2, ie half the original power  
-10B means a division by 10, ie one tenth the original power

And in terms of voltage:

6dB means a multiplication by 2, ie twice the original voltage  
20dB means a multiplication by 10, ie ten times the original voltage

Similarly, a negative dB figure implies division:

-6dB means a division by 2, ie half the original voltage  
-20dB means a division by 10, ie one tenth the original voltage

In amateur electronics and radio, decibel usage leans more to power and voltage and rarely to current. Now, bear in mind that to produce a two-fold increase in received radio-signal voltage (considered by some to be = one S-point) requires not just doubling, but quadrupling of transmitted power (=+3dB+3dB)! It is then obvious that 1dB (= x1.26 power or x1.2 voltage) and even 2dB (= x1.6 power or x1.3 voltage) represent not very significant gains/losses either in power or voltage terms, hence can be ignored for many-practical purposes, especially if only approximate values are sought.

In this case, it is possible to 'guesstimate' quite easily the power or voltage gain/loss equivalent to a given number of dB, by committing to memory the following six relationships:

Power:

- 3dB = multiply or divide by 2
- 7dB = multiply or divide by 5
- 10dB = multiply or divide by 10

Voltage:

- 6dB = multiply or divide by 2
- 10dB = multiply or divide by 3
- 20dB = multiply or divide by 10

Example 5:

Antenna gain of 16dB:  
 = (power) 10dB + 3dB + 3dB  
 = x 10 x 2 x 2 = x40 gain (cf 39.8 true).

or:

$$\begin{aligned} &= (\text{voltage}) 10\text{dB} + 6\text{dB} \\ &= x3 \times 2 = x6 \text{ gain (cf 6.3 true)} \end{aligned}$$

Example 6:

$$\begin{aligned} &\text{Power gain of } 47\text{dB} \\ &= 10\text{dB} + 10\text{dB} + 10\text{dB} + 10\text{dB} + 7\text{dB} \\ &= x10 \times 10 \times 10 \times 10 \times 5 \\ &= 5 \times 10^4 \text{ (cf } 5.01 \times 10^4) \end{aligned}$$

Example 7:

A coaxial cable is quoted as having attenuation of 6dB per 100metres at 100MHz. This means a power loss of 6dB/100m = (-3dB-3dB)/100m = (72)/100m = 74/100metre. Signal power is thereby reduced progressively by cable losses, to one quarter of its former value for each 100m of the cable's length, or to one half power per 50m of cable, and so on.

### Absolute power, voltage, or current

The previous section showed decibel or decibels as applying to power or voltage ratios, that is, to relative power or voltage, and not to absolute values in watts or volts.

This difference is important in practice. For example, if a radio amateur were to say "I have increased my power by 20 watts", that would be of no significance if his original power was 1000W, but very significant if he had increased from 1 watt to 21W. Similarly, a 3dB increase in power could mean a change from 2watts to 4watts, or from 4kW to 8kW, so to be meaningful in absolute terms one would need to also state the original reference power level. There is however a way around this, and that is to express the ratio in +/-dB relative to some arbitrarily chosen datum or 'zero level'. Datum levels have been internationally adopted to suit different purposes, three of which are given below as being of direct interest to the radio amateur:

**dBm** = dB relative to one milliwatt (mW) of electrical power, whereby 0dB = 1mW

**dBW** = dB relative to one watt (W) of electrical power, whereby 0dB = 1W

**dBd** = dB power or voltage gain (typically of a beam antenna) relative to a half-wave dipole antenna.

Note that dBd as applied to antenna gain is still only relative, in that it does not provide an absolute power in watts or level in volts. It implies an increase in power or voltage over whatever is expected from the major lobe of a dipole antenna in a similar location, and that applies equally to either reception or transmission.

Example 8

33dBm = power increase of x2000 above 1 milliwatt = (1/1000 W) x 2000 = 2 watts

-33dBm = power decrease of 2000 below 1 milliwatt = (1/1000W) / 2000 = 0.5 microwatt

33dBW = power increase of x2000 above 1 watt = (1W) x 2000 = 2000 watts

-33dBW = power decrease of 2000 below 1 watt = (1W) / 2000 = 0.5 milliwatt

26dBW = power increase of x400 above 1 watt = (1W) x 400 = 400 watts

16dBd = power gain of x40 relative to main lobe of dipole antenna

16dBd = voltage gain of x6 relative to main lobe of dipole antenna

In electrical engineering, 0dBm is taken as being 1 milliwatt into 600 ohms (hence 0dB=0.775V rms pd), whereas in radio it is more

likely to be 1mW into 50 ohms (hence 0dB = 0.224V rms pd). This is important, for example when using a signal generator the output attenuator of which is calibrated in dB, and you might wish to convert that into microvolts pd to determine the sensitivity of a receiver.

Some other dB terms of radio interest are:

**dBV** = +/-dB relative to 1 volt

**dBuV** = +/-dB relative to 1 microvolt

**dBi** = antenna gain relative to the theoretical "isotropic" (equal response in all directions) radiator

**dBc** = dB relative to carrier level, for use in spectrum analysis to quantify noise, spurious signals and distortion products such as harmonics

Other applications of dB in radio include the measurement of receiver sensitivity, adjacent channel selectivity, squelch sensitivity, intermodulation rejection, image rejection and S-meter linearity.

### Power v voltage gain

Voltage (or current) gain of an amplifier can correctly be quoted in dB, even if the input and output impedances are not equal. If however the input and output impedances really are equal, then voltage dB will numerically equal power dB and vice-versa, that is, 3dB voltage-gain = 3dB power-gain, but only when  $Z_{in} = Z_{out}$ . That is because there can only be a direct relationship between voltage dB and power dB if the impedances across which the voltages are measured are equal, to cancel out in the previously stated dB formula based on  $P=E^2/R$ . But in real life, amplifier voltage-gain is often quoted in dB, even when the input and output impedances are unequal, so it must be treated with due care.

Antenna gain is often quoted in dB. This is an example of where  $Z_{in} = Z_{out}$  because the feed impedance is a constant, so that the dB figure applies equally to power-gain or voltage-gain.

Example 9:

A 16dB gain antenna would produce:

$$\begin{aligned} &\text{a power-gain of } 16\text{dB} = (10\text{dB} + 3\text{dB} + 3\text{dB}) \\ &= (x10 \times 2 \times 2) = x40 \end{aligned}$$

or,

$$\begin{aligned} &\text{a voltage-gain of } 16\text{dB} = (10\text{dB} + 6\text{dB}) \\ &= (x3 \times 2) = x6. \end{aligned}$$

### Conclusion

It is useful for all radio and electronics enthusiasts to have at least a basic understanding of decibels, even if only to appreciate the meaning of those mystical figures that appear in antenna adverts and equipment reviews, or to translate into watts the 26dBW given as permitted transmitter output power in the UK Amateur Radio Licence. Of course, the full utility of decibels really comes into its own in complex calculations such as those for radio link-paths for earth-moon-earth or meteor-scatter communications. But whether it be for simple or complex calculations, a pocket scientific calculator makes light work of conversion from numerical gain or loss into +/-dB and vice-versa, by using the log key when converting from gain to dB, and the inv. log key for dB to gain - not forgetting of course to multiply or divide by 10 for power and 20 for voltage.

# CROWNHILL ASSOCIATES LIMITED

The Old Bakery, New Barns Road, Ely, Cambs. CB4 7PW

Tel:+44 (0)1353 666709 Fax:+44 (0)1353 666710

## CHIP DRIVE - PROFESSIONAL Smart Card Programming System

Intelligent programmer for Smart Cards using the International Standard T=0 or T=1 protocols also Memory and Secure Memory using 1'C, 2-wire & 3-wire interfaces. Supplied with software to read and write to most popular secure smart cards, inc GSM, PHONE and ACCESS-CONTROL cards.

T=0 or T=1 @ 3.579MHz  
RS232 @ 9600 - 11500 bps  
Internal Supply / Ni-MH  
Size: 100x70x80 mm  
Weight 660 Gram  
CE compliant



£79.95



www.towitoko.co.uk  
Crownhill Associates Limited  
Sole UK Distributor



### CHIPDRIVE starter kit

All you need to develop applications for the CHIPDRIVE terminal family containing:

- ◆ CHIPDRIVE (see left)
- ◆ WINDOWS driver software with detailed documentation, many sample routines with source code
- ◆ a selection of Smart Cards

£125.00



### Crownhill Associates Research & Development - The Smartest Solution -

Crownhill stock a full range of Smartcards, Smartcard Programmers and Accessories. From 256 bit memory cards through to RISC processor cards, from Towitoko professional CHIPDRIVE systems to OEM ISO interfaces. Crownhill offer the widest range of cards at some of Europe's lowest prices - full spec ISO smartcard sockets from just £1.45 each and RISC processor based Smartcards from just £3.45 each. Crownhill offer design services for both Hardware and Software, from feasibility through prototype to production. (volume production facilities are based outside of EC)

### PIC Microchip™ Development Systems & Components

**PIC Programmer KIT** £15.00  
components and high quality PCB with instructions & circuit diagram. Complete Microship™ library on CD-ROM, assembler, simulator and program driver. Programs 16C84, 16F84 & 24xx

PIC16C84 - £2.00 each  
PIC16F84 - £2.10 each  
PIC12C508/509 from 90p

Smart Cards  
PIC16x84 10MHz  
PIC16x84 & 24c16  
24c01 - 65  
Phase II phone cards

**PIC12C508 Development System**  
Real Time In Circuit Emulator. Programmer, Editor/Assembler. 10 fully sample programs including source code  
Fully Cased with Manual, Leads and AC Power Supply Unit  
£59.95

**Universal Programmer**  
programs all PIC Devices  
12c, 16c, 16F, 17c, 24c  
Includes assembler/editor  
High Quality PCB inc ZIF  
Ski  
£49.95

All prices exclude P&P + VAT @ 17.5%

**FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!**

**FREE! FREE! FREE! FREE! FREE! FREE!**  
**OUR 1998**  
**CATALOGUE**  
**AND LATEST**  
**BARGAIN LIST**  
**ABSOLUTELY**  
**FREE!**  
**FREE! FREE! FREE! FREE! FREE! FREE!**

**PHONE, FAX OR WRITE TODAY!**

**GREENWELD**  
**ELECTRONIC COMPONENTS**

27E Park Road · Southampton · SO15 3UQ  
TELEPHONE: 01703 236363 FAX: 01703 236307  
E-Mail: greenweld@aol.com INTERNET: http://www.greenweld.co.uk

# SPICED CIRCUITS

**Circuit simulation with software, by Owen Bishop. This month, part 7 - Logic simulation and a maths package.**

**I**n the previous part (Vol 27 Issue 1) we looked at simulation of logic circuits by conventional SPICE-based simulators. But even SPICE cannot be expected to be all things to all designers. It was written for designing integrated circuits. Subsequently it has been very useful in numerous applications relating to discrete analogue circuits, but it has limitations with logical circuits. When we describe a logic circuit, we do it in terms of gates, and assemblies of gates (such as flip-flops, counters and registers). Logical analysis is based on truth tables.

When we simulate a logical circuit using SPICE, the nature of SPICE makes it operate at a more fundamental level, calculating the currents through the transistors and resistors that go to make up each gate. Analogue analysis is based on Ohm's Law, Kirchoff's Laws and transistor output characteristics, plus a great deal more. This is slow if the circuit contains more than a few dozen components. Logic gates usually consist of several transistors and other components, so that they perform in a very robust and repeatable way. Analysing them by analogue methods involves many time-consuming calculations for which, in practice, there is no need.

For instance, if the voltage at the input of a CMOS gate is greater than half the supply voltage, it rates at a high input. With a 5V supply, it does not matter if the voltage is 3V, 4V, or 5V or something in between. So there is no point in making the simulator iterate around a resistor/transistor gate circuit to calculate the voltages to 12 decimal places. A logic gate can be taken as a black box; given certain inputs, it gives a predicted output, with various but small and dependable time delays. The whole approach to modelling digital circuits is different.

The completely SPICE-modelled gate has uses for simulating mixed-mode circuits but the time that this takes limits the number of gates that can be included in a circuit. And we are talking about gates, which is still a long way from modelling logic circuits with counters, shift-registers, arithmetic units, and even further from LSI and VLSI devices. There is another reason why SPICE is inherently unsuitable for simulating logic circuits. Logic gates change state in a few nanoseconds but, once changed, may remain in the same state for microseconds or milliseconds. These are periods several thousand or million times longer than the period of change. It makes no sense to repeatedly calculate voltages and currents for these static periods. The simulator

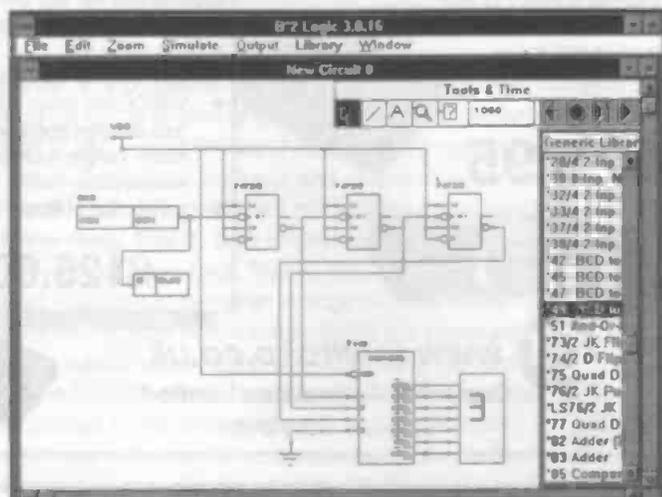


Figure 1: this version of the JK ripple counter uses a 7449 decoder and a 7-segment display to read the output states

must be event-driven, leaping from one voltage change to the next. The iterating procedures of SPICE do not fit in with logic gate timings.

Simulators such as SpiceAge, on which we based the first five parts of this series, minimise these disadvantages by breaking away from SPICE in certain respects. SpiceAge has recently added logic gate primitives and other function blocks to its range of 'components'. It also has algorithms for automatically calculating the size of the time step, to produce longer time steps when feasible and so decrease analysis time. Going even further, some simulators have started again from scratch and use a purely logic-based approach to digital analysis. One such simulator is described below.

## B2 LOGIC, V3.0

B2 Logic 3.0 is published by Beige Bag Software, of Ann Arbor, Michigan, who also publish the analogue simulator B2 SPICE which we looked at in the previous article. B2 LOGIC is available in Windows and Macintosh versions, and is an impressive piece of software which is very easy to use.

The first stage in setting up a logic circuit is to draw its schematic on the screen. As a simple demonstration, we set up a ripple counter, one of the logic circuits that we analysed last month. Logic elements are selected from the device library (right of screen in figure 1, though it can be moved around). There is a very extensive library including everything from a plain inverter gate, through all kinds of registers and

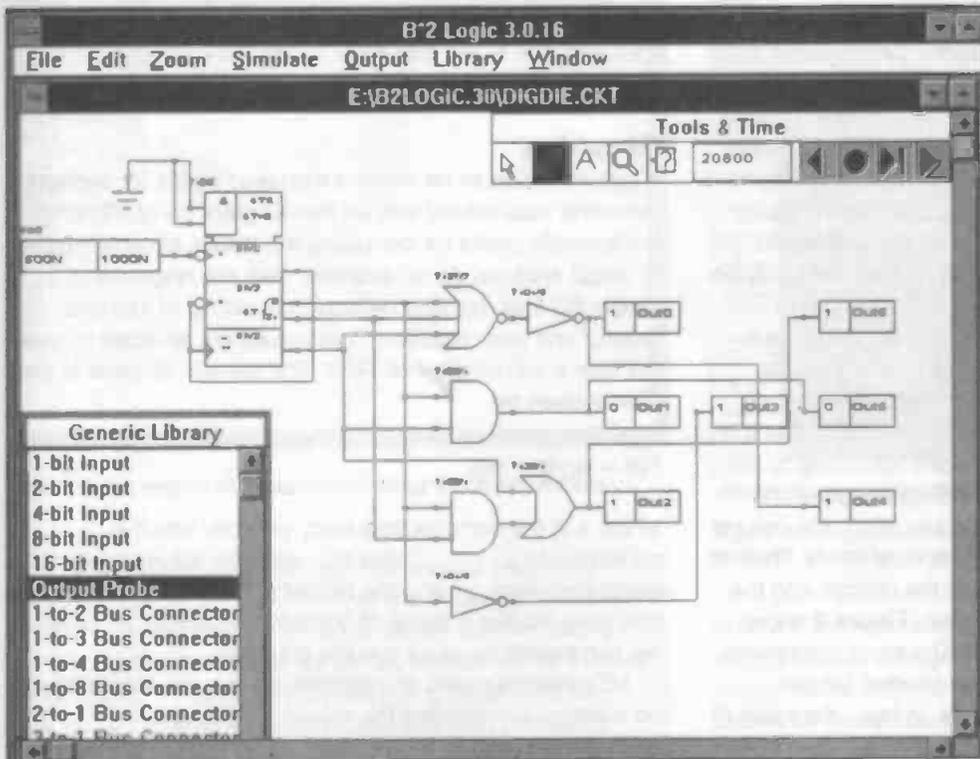


Figure 2: a simulation of one of many possible simulations of a digital die. The operator has just 'thrown' a five

flip-flops to a 74646 octal bus transceiver and register. The devices are displayed as standard IEC (International Electrotechnical Committee) symbols. There are several libraries to choose from, including Generic devices, TTL, LSTTL and CMOS technology. For this analysis we selected from the Generic library and built a three-stage ripple counter (it was two-stage a few months ago, but we can be a bit more ambitious with a dedicated digital simulator). B2 Logic has a useful set of input and output devices. The high voltage device (Vcc) provides logic high to inputs that need it, such as the J, K and reset inputs. Another device, a clock, is set to have a period of 80ns, with a pulse width (length of time for which it is high) of 40ns.

A probe is a handy device for reading output levels. We attached one to the clock and set it to display '0' for logic low and '1' for logic high (you can also make it display 'L' or 'H'). We could have done the same with the outputs from the counter but, if we have a ready-to-use 7449 decoder handy, why not use this instead? The 7449 is a BCD to 7-segment decoder and the library also has a 7-segment LED display which is easily attached (by dragging it with the cursor - simulation has that big advantage over real life). All we have to do now is to run the simulation and watch the display. The 'Tools and Time' window has buttons like those on a tape player for reset to zero time, stop, single step forward, and continuous run. Single-stepping (for presettable time intervals) shows the clock alternating between high and low and the 7-segment display goes through this sequence repeatedly:

0 1 (0) 2 3 (2) (0) 4 5 (4) 6 7 (6) (4) 0 1 etc

With 10ns steps, the numerals in brackets are displayed for a relatively short time. They are the glitches on a ripple counter that we explained last month. A continuous run makes the glitch periods so short that you can hardly notice them and the counter appears to be running correctly. At the

end of the run we can ask for a trace, which plots the levels detected by probes. To examine these we first need to attach probes to the three counter output lines. The 10ns delay in each flip-flop is then clearly seen. Alternatively we can call up a table of probe logic levels at preselected time intervals during the run.

This circuit demonstrates how a counter can be built up from flip-flops and then analysed. If you need counters in other circuits, you would dig into the Library and use complete counter devices ranging from the 7493 binary ripple counter to the 74169 synchronous up/down binary counter with parallel load.

### The ultimate simulation

In the world of simple circuits there are probably more

designs for egg-timers than for any other function. Second on the list comes the digital simulation of rolling a die, with LEDs displaying a random count from 1 to 6 when you press the stop button. Figure 2 is a simulation of one of the many digital die circuits. This is a simulation of a simulation - but it works. The circuit is driven by the clock we used in figure 1: but this time its output goes to a counter, a model of the 74LS92 counter wired to count repeatedly from 0 to 5.

The output is decoded by various logic gates, to which seven probes are connected. We have arranged these so that, if you look for the '1's, they produce the conventional patterns of spots on the face of the die. The number of gates is fewer than would usually be the case because it would be uneconomic to use four different kinds of gate, when building a real circuit. We would probably manage it just with NANDs and NORs and the simulator could be used to check out the slightly more complicated logic involved.

To start the die rolling, click on the continuous run arrow. When you click on stop the display shows the score. In the figure, the pattern of '0Ns' displays 'five'. Here we must reluctantly leave B2 Logic, which has in fact shown us the last simulation of this series, and move on to something entirely different.

### MEXPRESS 1.1

This is one of the newer maths packages, and has a lot to offer the electronics designer. The simplest way to use it is as an on-screen calculator. For example, type  $25 \cdot \sin(1.2) + 3.27$  at the prompt, press ENTER, and back comes the result, 26.570. It can handle imaginary numbers too. For example  $3.4 + 0.2i$  multiplied by  $2.1 - 5.67i$  gives the result,  $8.274 - 18.858i$ , although entering the calculation is slightly more involved. The package has a range of over 250 functions, including matrix algebra, statistical functions and equation solving. Another strong feature of this package is its flexible system of plotting graphs, both 2D and 3D, and its ability to produce real-time animations. Before we look at

its graphics we will consider how the mathematical functions can be of use to the electronics designer. Although MExpress probably could simulate whole electronic circuits, we are not likely to use it for this purpose because it would take too long to set up the equations and plotting routines required. Regular simulators have all the required functions built in already. But there are numerous instances of design calculations that we need to perform over and over again, yet are that bit more complicated than can be handled easily on an ordinary calculator.

To take one very simple example as an illustration, we often need to find suitable resistor values for a potential divider. For instance, there is a need for this when we are trying to bias a transistor. You can, of course just make this a one-off calculation, type in the variables according to the formulae and obtain the results. But MExpress goes one better (actually two better, as we shall see later). We can set up the calculation plus a few frills in a special .X file. Then all we do is type the name of the .X file at the prompt and the routine is automatically called into action. **Figure 3** shows the notepad with the routine entered. The input statements ask the user to key in the three values needed for the calculation. Then the routine calculates 'oures', the value of the output resistor, and also the current through the network. After printing a heading, the calculated values are displayed. The contents of Notepad are then saved in a file called potdiv.X.

**Figure 4** shows the outcome when, back in MExpress, we type the file name 'potdiv' and press Enter. We are asked to enter the values of input and output voltage and also the intended total resistance of the chain. The displayed results show that the output resistor should be 2.2k and the other resistor 7.8k. Probably the nearest E24 value, 7.5k? would be acceptable. Current through the network is 9mA. To recall the routine for another calculation, simply press the cursor 'up-arrow' key a few times until the original 'potdiv' command reappears at the prompt. Key 'Enter' and repeat the calculation with new values.

This is only the barest routine. Several refinements are possible, including routines to select the nearest E24 values. As an illustration of what can be done we have added a 'message screen'. This comes up on the screen as a typical Windows message, to warn you if by accident you have typed in the input and output voltages the wrong way round. The message screen can be tailored to fit your needs. This one has a bold exclamation mark on it and an 'OK' button for acknowledging the message.

We said we could go two better, and the next step could be to compile the potdiv routine to produce a free-standing program. You need a C++ compiler for this. MExpress translates your .X file into C++, to which you can add any C++ code of your own, and compile the lot to produce your faster-running and more sophisticated potdiv software. Whether you compile or not, you can quickly write a number of variants of the potdiv routine. Another variant could ask for voltages and network current and calculate both resistor values. Another could ask for both resistor values

and input voltage and calculate output voltage. Then, turning your attention to the 555 timer ic, there are several more routines which would be very useful to have handy.

## Graphics

A picture is said to be worth a thousand words (or perhaps a thousand data values) and so the 3D graphics of MExpress are specially useful for portraying the results of certain types of circuit analysis. As an example, take the response of a simple RC lowpass filter network, consisting of just one resistor and one capacitor. Their values are selected to give the filter a cut-off point of 1kHz. The transfer function of the filter is given by:


$$F(s) = \omega_0 / (s + \omega_0)$$

where s is the complex frequency variable, which is equivalent to  $(\sigma + j\omega)$ . These two variables are measures of signal frequency ( $\omega$ ) and the rate at which amplitude is changing ( $\sigma$ ). For a signal of constant amplitude,  $\sigma = 0$ , and we can substitute  $j\omega$  for s in the equation.

MExpress is based on matrices, so the first step is to set up a matrix s containing the values of s for which we want to plot values of F(s). This will be a 2-dimensional matrix with rows for each value of  $\sigma$  and columns for each value of  $j\omega$  (actually  $j\omega$  because MExpress uses the symbol j instead of j). Values of  $\sigma$  are 0 to -8000 in steps of 2000, and values of  $j\omega$  from 0i to 3i in steps of 1i. We then form a matrix t, holding of values of F(s) by using the command:  $t = \text{abs}(6283 / (s + 6283))$ . The term 'abs' gives the absolute value of the expression, since we are concerned here only with the amplitude of the output signal, not its phase. The value  $\omega_0 = 6283$ , is obtained from:

$$\omega_0 = 2\pi f_0$$

when  $f_0 = 1\text{kHz}$ . All that remains is to type MPlot(t), to obtain the 3D graph shown in **figure 5**. The axis running off to the left is frequency ( $j\omega$ ) and the axis running to the right is the

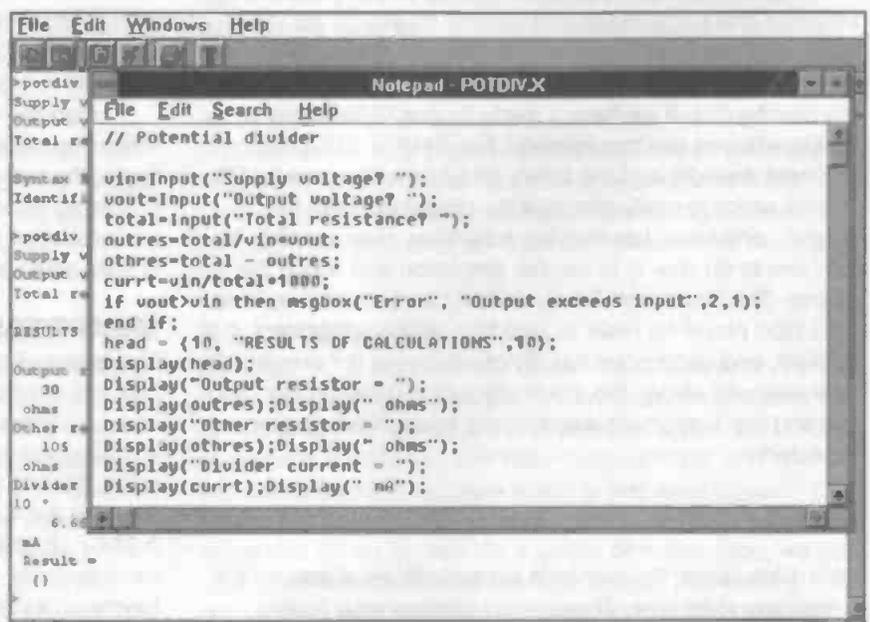

**Figure 3:** In MExpress, users can type often-used routines into Notepad and save them for instant use later. This is 'potdiv', a routine useful for calculating values for transistor biasing resistors

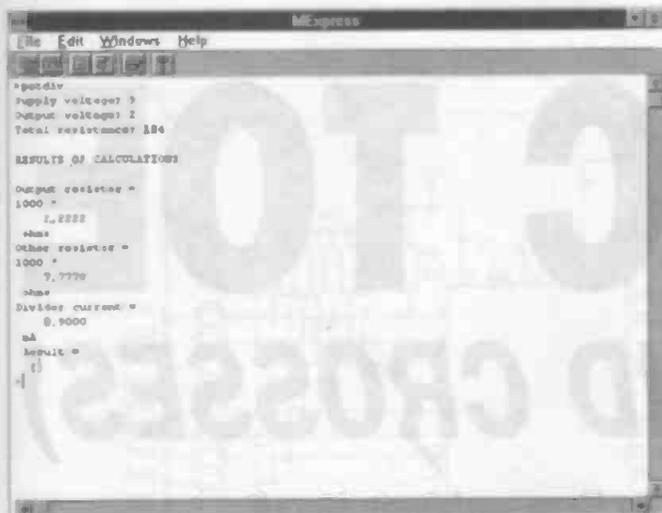


Figure 4: the results of a calculation using the potdiv routine

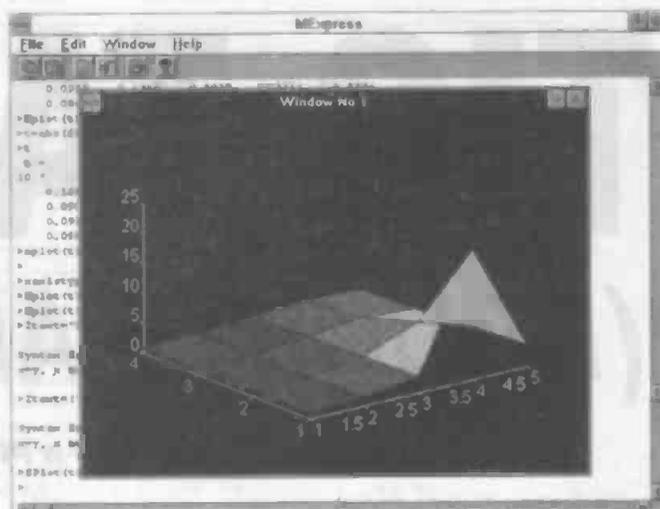


Figure 5: the gain of a lowpass RC filter plotted against frequency and rate of change of amplitude

rate of change of amplitude ( $\sigma$ ). The vertical axis is the transfer function, or gain, ( $F(s)$ ). At the origin (centre front) the gain is 1, as is expected for a DC signal. Running along the left-hand edge of the plot we have the response of the filter to increasing frequency at constant amplitude - the usual plot of gain against frequency. Gain falls with increasing frequency, as would be expected in a low-pass filter, but this does not show up on the graph because the vertical scale is too large. The reason for this is the tall peak we have discovered at the point where  $s = -6000 + 0i$ . Substituting this value into the equation gives  $F(s) = 6283/283 = 22.2$ . If we made  $s$  equal to 6283, the result would be infinitely large, and project infinitely upward. We call this a pole. The pole and its surrounding region represents a set of conditions

at which the filter enters a resonant state, perhaps briefly, and its output voltage exceeds its input voltage by a considerable amount. Looking for poles is an important aspect of design because, if there is a chance of the circuit operating in the region of a pole we can expect severe distortion. Plots such as figure 5 can help in locating poles.

This ends our brief survey of software useful to the electronics designer. New programs are coming onto the market all the time, but we hope that the examples we have used here will help you think clearly about simulation and to choose one most suited to your needs.

**T.I.S.**

2 John Street, Larkhall, Lanarks, ML9 1HE  
Tel: 01698 883334 / 884585 Fax: 884825  
Send a S.A.E. for your **FREE** Catalogue & Quote.

**T.I.S.**

Unconditional replacement or refund on any item if not as requested

**TOP SELLING BOOKS**

- Pract' TV or VCR Repairs - £16.95 (Both £30)
- Buy/Sell/Serv/Repair Used Equipment -
- CD, TV or VCR - £10.95 each (All 3 £27)
- 6 Giant IC Ref' Manuals - £12.95 each
- Data Ref' Guide - identifies/ prices/ cross-ref's data for most models - £9.95 (3.5" Disk £5)
- Microwave Energy & Ovens - £9.95
- 3.5" Disk Drives - £9.50
- The Giant Fault-Finding Guides:-
- CTV's £16.95 / VCR's £16.95

**SERVICE MANUALS**

- DESIGNER COLLECTIONS**
- Comprehensive Circuits Collections of any make of CTV as requested, prices from £8 to £49 (IE. Alba/Bush £20) Full list in Free Catalogue.
  - Amateur Kit: 10 Service Manuals (as needed), Data Ref', Pract' TV & VCR Repairs, Radio Repairs, Thom Serv' Set & any 3 CTV Circ Collections. £199
  - Professional Kit: As above + 10 Serv' Man's, Microwave E&O, Buy/Sell/Serv' Collection & 2 More CTV Circ's. £370

**3 UNIQUE SERVICE MANUAL OFFERS**  
GUARANTEED SAVINGS TO YOU **NOW!!**

- \***LIBRARY** Joining fee £65.00  
You receive any Service Manuals, no matter how expensive, for £10 each, and you get a £5 credit for any you return.
- \***PRE-PAY MANUALS**  
You get 20 Service Manuals, as and when you need them; as many or few at a time as you want, for a one-off payment of £185.
- \***SERVICE MANUAL EXCHANGE**  
If you have a Service Manual we **don't** have and need another manual (ie. TV for TV, VCR for VCR), we will exchange it for **FREE**.

Please add £2.50 to all orders to cover Postage & Handling

**WORLD'S LARGEST SERVICE MANUAL COLLECTION**

Normal Prices Given (Some Manuals may be Cheaper or more Expensive)



VCR/VIDCAM - FULL MANUALS £16.50 - CIRCUITS £8.00 COMPLETE  
CTV's / CD's - FULL MANUALS £12.50 - CIRCUITS £6.00 COMPLETE



AUDIO, CD, COMPUTERS, MONITORS, DOMESTIC / TEST EQUIP', ETC.. FROM £4.00

# TIC TAC TOE

## (NOUGHTS AND CROSSES)

*A game-in-a-box with a PIC, by Rose and Andy Morell*



This is an electronic game of Noughts and Crosses which allows you to play against the 'computer', that is, the PIC 16C64 microcontroller.

The PIC contains a long program designed to allow one or two players to play the game. The source code is available (see below). The 16C64 is the "intelligence" of the unit, and the playing board consists of nine 5mm tricolour leds (LED1 to LED9). In this way, the lights can be either green or red when selected, depending on whose turn it is, as the colour changes automatically. There are also two further leds, LED10 and LED11, which indicate whose turn it is. The eventual winner is heralded by a tune, which plays when a game has been won (or lost!), while the winning line flashes on and off. There are ten pcb-mounted push switches, including one reset switch. The position of the buttons corresponds to the position of the tri-colour leds, that is, it is a 3 x 3 matrix.


### How to play

With the power on, select either push-switch 1, push-switch 2, or push-switch 3. To play against an opponent, select switch 1, and to play against the computer, select switch 2 or switch 3. Switch 3 will allow the computer to make the first move, and Switch 2 leaves you to make the first move. After that, you can press any one of the nine switches to commence play and make your move. Should you opt to play against the PIC, be prepared for a rapid response!

If there is stalemate in the game, you will have to press Reset to start a new game. If, on the other hand, you or the PIC should win a game, you will hear a tune (exactly which one depends on your choice of the sound generator chip during the construction stage). No further moves will be possible once the winning move is made. To stop the tune and start a new game, press 'reset'.
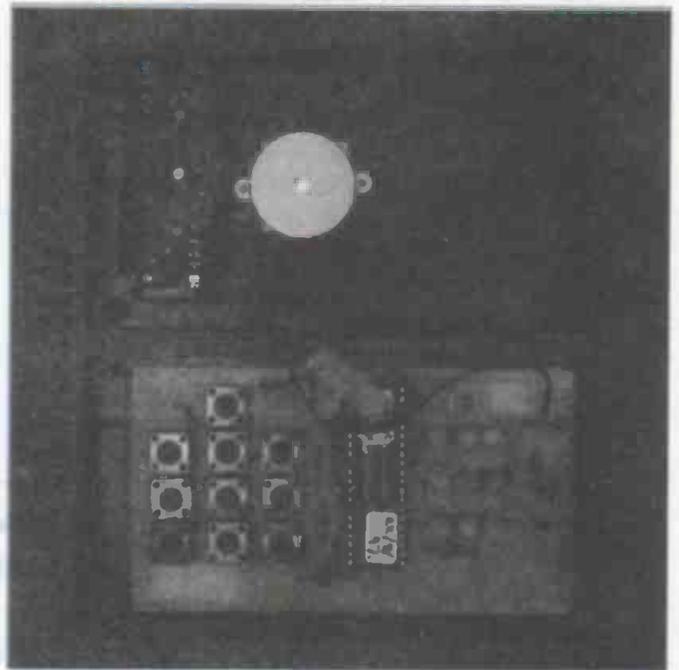
### How the software works

There are nine memory locations representing the nine leds. On reset or power-up, the nine memory locations are filled with the number '8'. The software uses this information to determine what move to make. Now the game is being played, and you have just made the first move. Next, it's the PIC's turn, so the computer scans all three rows of leds, followed by the three columns, and lastly, the two diagonals, looking for a 'good move'!



It does this by looking at the nine memory locations that represent the nine leds. Once a move has been made, the PIC puts a '1' in the chosen location for an 'X', or a '2' for an 'O', while a space remains an '8'. (The microcontroller is always the 'O'.) On subsequent moves, the computer scans the memory locations and adds up the numbers in each row, column, and diagonal, looking for a line that contains two 'O's to win, or two 'X's so that it can block the third 'X' and at least not lose. To summarise:

- 1) A win in one move: the PIC only has to put its 'O' in the appropriate space to win.
- 2) A lose in one move: the PIC must block the 'X's' next move to avoid losing.
- 3) Neither is possible yet: the PIC will check the centre led to see if it has been occupied. If it has, it will look for 'any space', and if not it will bag the centre led!

For the 'computer' to find a win in one move, there must be three consecutive locations resulting in a total count of '12 decimal', that is, two 'O's, and one space:  $2 + 2 + 8 = 12$ . Therefore, if any row, column and diagonal totals 12, a win in



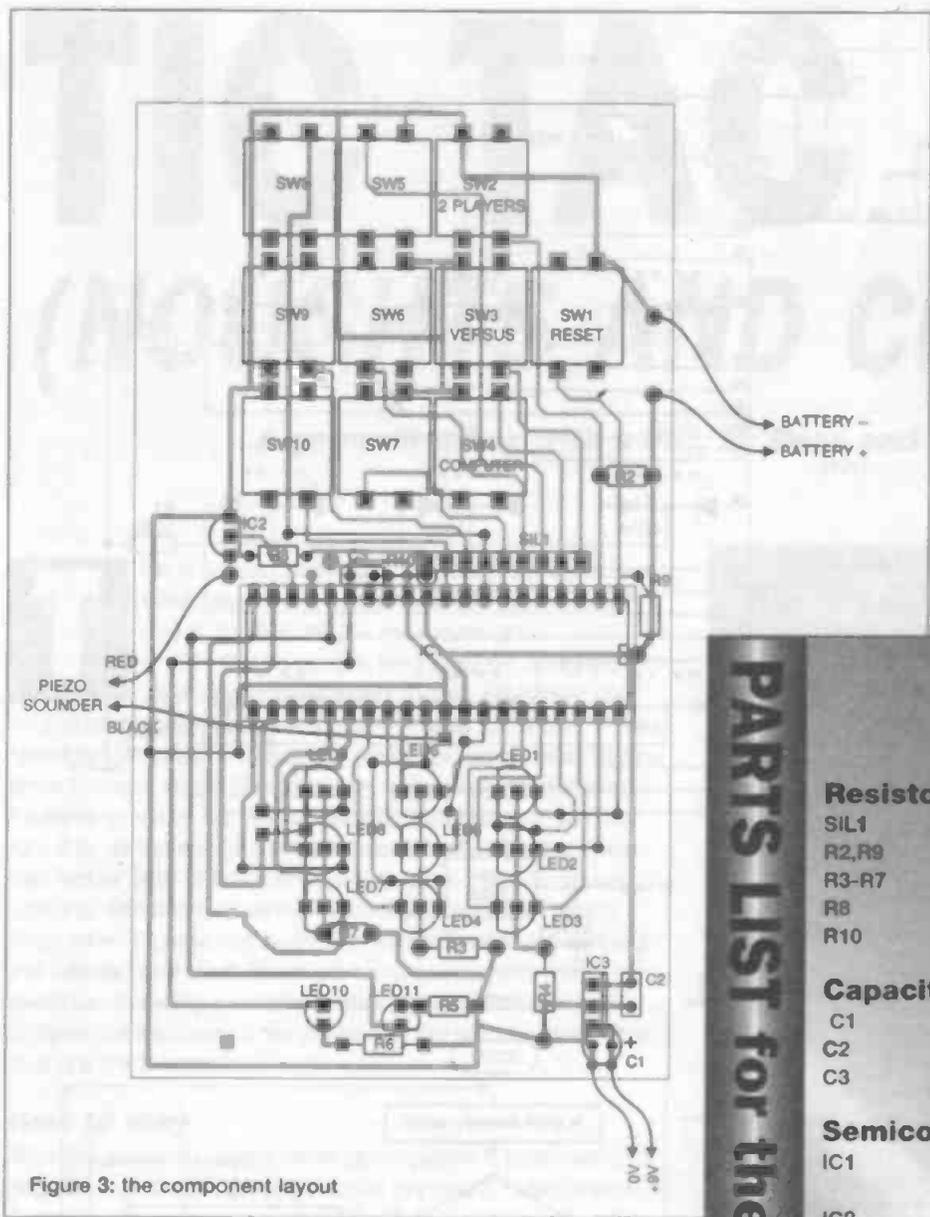


Figure 3: the component layout

sound generator, IC2, the correct way round with the 'flat' side facing the keys. There are three capacitors, of which one (C1) is polarised (and optional). The voltage regulator (also optional) is fitted next with the 'curved' side facing the leds. A battery clip or power socket can be fitted to the Veropins, perhaps with a 9V battery providing the power. A good dc power supply can be used instead, if required, but please consult the section 'Using the unit'.

Crystals are not used for the timing components. To keep costs down, a resistor/capacitor network (R10,C3) is used instead. C3 is from 20 pF upwards, but it is not definitely needed. The oscillator operated quite happily with a 100k resistor on its own on the prototype.

Finally, a piezo speaker is fitted. A suitable one can be obtained from Maplin.

### Casing the unit

The pcb was found to fit neatly in a small box, with the two halves held together by a 'hinge' made of adhesive electrical tape. Real hinges could have been used, if they are small enough. We stuck the pcb down with double sided tape inside one-half of the box, with the other half holding the batteries (side by side), and the piezo sounder stuck there also. So the components are then protected from damage, and the box

easily opens when it is required. The box we used was from Maplin and measured 145mm x 80mm x 32mm.

### Using the unit

Once the PIC has been programmed and the hardware constructed satisfactorily, the game can be played. At the start of the game select one push-switch 1, 2 or 3. This determines play (see above). Press the buttons gently. The game provides endless hours of enjoyment for children or adults.

Batteries can be used, but we found that while the unit (including the PIC) worked quite happily on a 3-volt battery, without the voltage regulator, the display is not so bright.

## PARTS LIST for the Pic Tic Tac Toe

### Resistors

SIL1	4k7 sil resistor, Maplin RA296
R2,R9	4k7
R3-R7	300R
R8	270R
R10	100k

### Capacitors

C1	(see optional regulator below)
C2	100 nF capacitor, ceramic.
C3	See text

### Semiconductors

IC1	PIC 16C64 (see below) Write for prices
IC2	Sound generator chip: choice of music chips from Maplin (M66T Series, eg GX55K)
LED1-LED9	5mm tri-colour LEDs (common cathode)
LED10	3mm red led
LED11	3mm green led

### Miscellaneous

Z1	Piezo sounder PCB, battery clip, battery box, solder, wire, Vero-pins.
----	--

### Optional (for regulator)

C1	1uF 16v elect radial
IC3	7805 100mA voltage regulator

A 3.5-inch disk containing the source code is available for £5 (inc. postage and packing) payable to A J Morrell, 12 Boscobel Road, Winchester, Hants SO22 6RY. Postal only - please do not call. Programmed PICs may be available if demand is sufficient - please write (enclosing an SAE) and enquire.

# Line-Up Oscillator with Glitch

*A glitch is a good thing if it tells you which channel you are in, according to Tony Sercombe.*

**W**hen sending an audio signal to a remote destination, or to a tape recorder, it is necessary to know the average sending levels, and also, in the case of a stereo signal, to know which leg is stereo right and which is left. The following circuit fulfils both these criteria.

The circuit is intended to be included within existing audio equipment, and as such a separate power supply is not provided, since its requirements are very modest, and it can be run from various voltages.

## The circuit

The oscillator consists of a single transistor, working at 1 kHz. The output is fed to Q2, which is an N-channel fet connected as a buffer. This is necessary to prevent loading of the oscillator, which would lead to severe distortion of the

waveform. The output of the buffer is fed to a resistor network consisting of three resistors. The two series resistors have the same total value as the single resistor in parallel. However, at the junction of these resistors is the point at which the glitch in the output of one leg takes place. The 220 uF capacitor in series with a P-channel fet and a 1k2 resistor form a switch from this output feed to earth, controlled by IC1. Under non-glitch conditions, the two output resistances are equal. When a glitch is applied, the resistance of the fet Q3 is reduced, effectively reducing the signal by the potential divider action of R12 and R11, the resistance of the fet being negligible.

IC1 operates in the astable mode. R7 and R8, connected between pins 8, 7 and 6, charge C6, which is connected between pins 2 and 6, and ground. When this charge reaches two-thirds of the supply voltage, C6 discharges via R8 into pin 7. The standing voltage on pin 3 feeding the gate of Q3 now

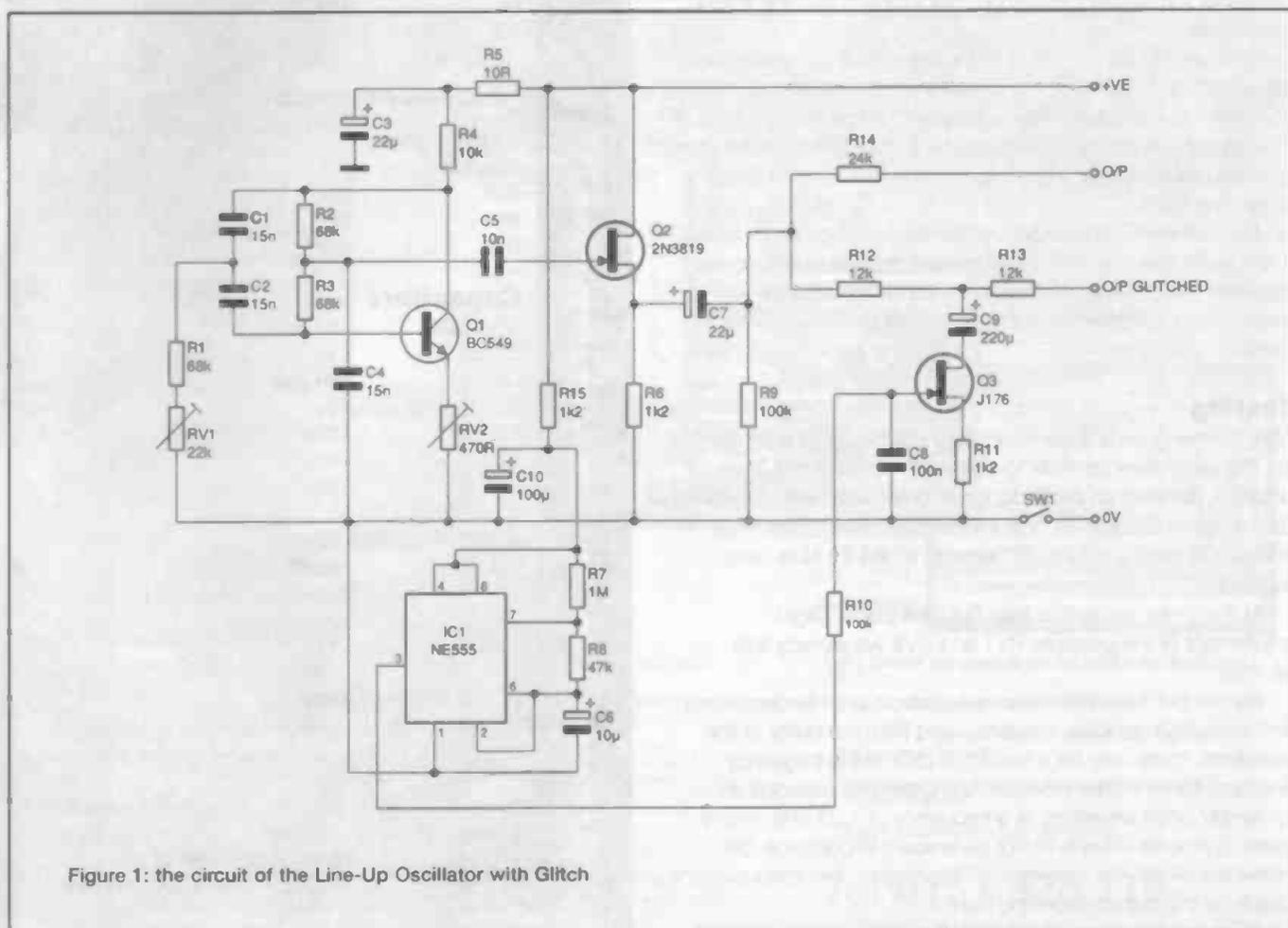


Figure 1: the circuit of the Line-Up Oscillator with Glitch

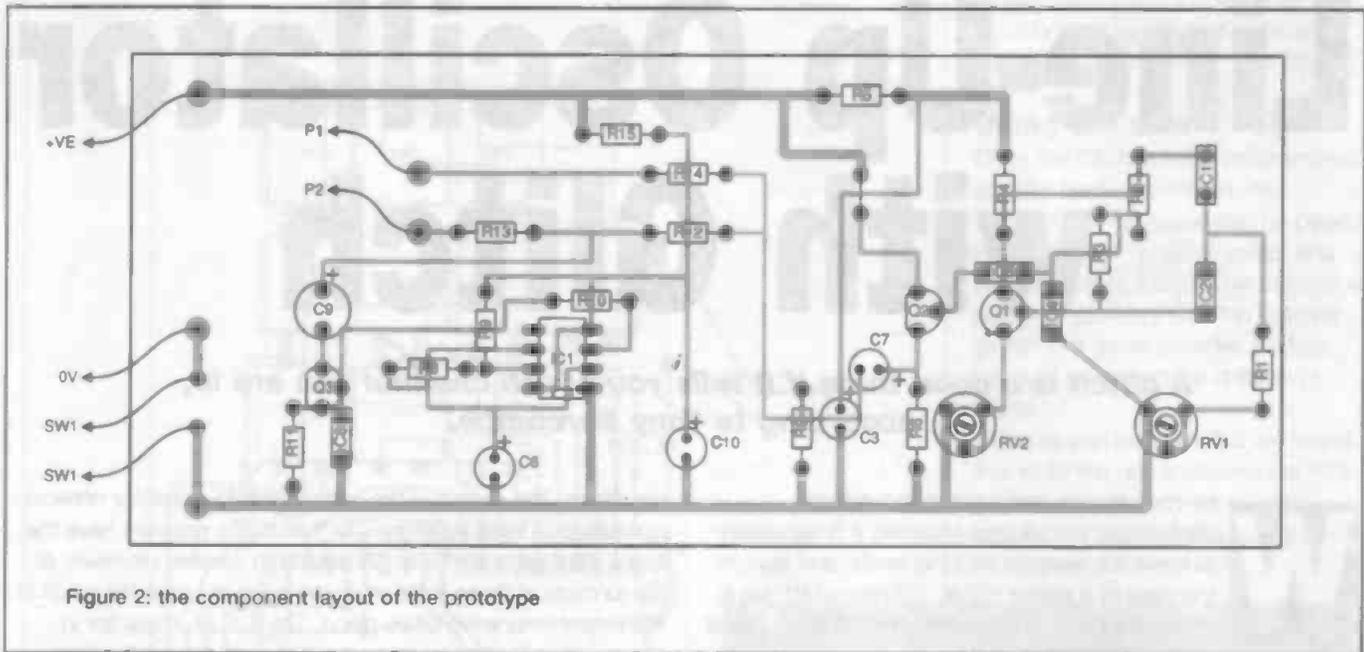


Figure 2: the component layout of the prototype

ramps low-switching Q3 to the low (resistance) state, thus producing the glitch. The IC is a standard NE555 timer. The somewhat heavy decoupling on pins 4 and 8 prevents disturbance on the supply line. The component values shown at IC1 provide for a half-second glitch every 10 seconds. If desired, these times may be modified to suit individual needs, and the values changed accordingly. However, the values shown seemed to be about right in the prototype. It is important that the glitch should not take place too frequently, otherwise the frequent repetition may interfere with the line-up procedure.

In the prototype the signal output level was 150 millivolts, measured as 146 mV with a 15-volt supply, dropping to 130 mV with a 9-volt supply. The outputs should be fed to a load of 10k. Much less than this will produce a disturbance of the unglitched output. If this is unavailable, you may have to resort to buffer amplifiers.

A circuit layout is provided. When construction is complete, it is a good idea not to fit the ic immediately, so that the oscillator may be adjusted more conveniently. I always recommend the use of ic sockets, so that this is a minor matter.

### Testing

After checking for any construction mistakes, dry joints, etc., set the two preset controls to their midway positions. If possible, connect an oscilloscope to one of the outputs. Failing this, a pair of medium to high impedance headphones may suffice. Connect a voltage of between 9 and 15 volts, and switch on.

At this point, oscillation may not take place. Slight adjustment of the presents RV1 and RV2 will remedy this situation.

Remember here that these two controls are interdependent, and since RV1 sets the frequency, and RV2 the purity of the waveform, there may be a small compromise in frequency accuracy to be made. However, the prototype provided an extremely good waveform at a frequency of 1.02 kHz. In any event, a precise value is not of paramount importance, but rather a well-defined waveform. If listening on headphones, check for the purest-sounding note.

Once this has been completed, the glitch can be checked.

Remove the supply and put the ic into its socket. After restoring the supply, the glitch should be noticed as a sharp dip in output of half a second, every 10 seconds.

## PARTS LIST for the Line Up Oscillator

### Resistors

R1,R2,R3	68k
R4	10k
R5	10R
R6,R11,R15	1k2
R7	1M
R8	47k
R9,R10	100k
R12,R13	12k
R14	24k
RV1	22k
RV2	470R

### Capacitors

C1,C2,C4	15n poly
C3,C7	22u
C5	10n poly
C6	10u
C8	100n
C9	220u
C10	100u

### Semiconductors

IC1	NE555
Q1	BC549 (or 108/9, etc.)
Q2	2N3819
Q3	J176*

### Miscellaneous

This project is designed to be fitted in existing equipment. PCB, ic socket, wire, solder, etc.

\*The J176 can be obtained from Cirkuit Distribution Ltd., Park Lane, Broxbourne, Hertfordshire EN10 7NQ. Tel\*01992 448899 stock no. 59-02176, or another suitable P-channel device may be used.

# HOW DOES YOUR EQUIPMENT MEASURE UP? AT STEWART OF READING THERE'S ALWAYS 'SCOPE' FOR IMPROVEMENT!



PHILIPS PR3217 (This is a Proper Scope)  
Dual Trace 50MHz Delay Sweep Int'l 2 Probe DMM



MARCONI 2018A Syn AM/FM Signal Gen 80MHz-100MHz £1800  
MARCONI 2018 Syn AM/FM Signal Gen 80MHz-100MHz £1500  
MARCONI 2018 Syn AM/FM Signal Gen 80MHz-100MHz £900  
MARCONI 2017 AM/FM Signal Gen 10MHz-100MHz £1750



HCS888  
Dual Trace 20MHz 5mV/20V Div. 0.2µSec-0.5Sec/Osc. 1-P; IS Magnifier; TV Sync etc.  
Hardly used £150 Un-Used £200



FAIRWELL P5G520 Syn AM/FM Signal Gen 10-50MHz £325  
FAIRWELL P5G520 Syn AM/FM Sig Gen 10-50MHz Portable £450

MARCONI 6111 Programmable Sweep Gen 10MHz-200MHz £650  
MARCONI 2222C AM/FM Signal Gen 10MHz-100MHz £2000  
H.P. 8056A Syn Signal Gen 0.1-100MHz £700  
H.P. 8048 Phase-Lock Syn Sig Gen 5000Hz-512MHz £750  
H.P. 8048A AM/FM Signal Gen 5000Hz-100MHz £650  
PHILIPS PR3180 Programmable Syn Func Gen 0.1MHz-30MHz £1800  
PHILIPS PR3180 Programmable Syn Func Gen 0.1MHz-20MHz £1200  
H.P. 3225A Syn Function Gen 2MHz £1250  
PHILIPS PR3134 Sweep Func Gen 0.2MHz-25MHz Sine/Sqr/Tri etc. £400  
PHILIPS PR3132 Sweep Func Gen 0.1Hz-20MHz Sine/Sqr/Tri etc. £250




CLASSIC AV81 MS in Case with Batteries & Leads £50



FLUKE 77 DMM 2 1/2 dig with Carrying Case & Leads £80



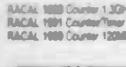RACAL COUNTERS  
8918 1MHz-50MHz £125  
8916 1MHz-20MHz £150  
8904 DC-50MHz £90



RACAL 1088 Counter 1.5MHz GPB £850  
RACAL 1091 Counter/Preamplifier 100MHz £650  
RACAL 1089 Counter 120MHz £300



SOLARTRON 7151 DMM 2 1/2 dig IEEE £400  
SOLARTRON 7150 DMM 1 1/2 dig IEEE £300

## THE CLASSIC TEKTRONIX 400 SERIES



448 Digital Storage Dual Trace 100MHz Delay £850  
446 Analogue Storage Dual Trace 100MHz Delay £385  
475 Dual Trace 200MHz Delay Sweep £500  
488 Dual Trace 100MHz Delay Sweep £400

FLUKE PROBE 20-200 100MHz Delay TB Carriers £1200  
PHILIPS PR3285A Dual Trace 400MHz Dual TB Delay Carriers IEEE £1750  
TEKTRONIX 7455A 4 Trace 50MHz Delay Surobit etc. £2500  
TEKTRONIX 1A548 Dual Trace 100MHz Delay Surobit £300  
TEKTRONIX 1054A Dual Trace 100MHz 100MHz Surobit Dig Storage £1300  
TEKTRONIX 2715 Dual Trace 60MHz Delay Sweep £400  
PHILIPS 3055 2-1 Ch 50MHz Delay TB £105  
PHILIPS PR317 Dual Trace 50MHz SCOPOMETER Dig Storage £800  
GOLD 05106 Dual Trace 50MHz £240  
GOLD 05106 Dual Trace 20MHz £200

AND REMEMBER ALL OUR EQUIPMENT IS TESTED PROPERLY

## LOOK!! BRAND NEW OSCILLOSCOPES - NEVER USED LIMITED STOCK




DMS 3054A DIGITAL STORAGE OSCILLOSCOPE  
Hardware LCD Display 2 Channel 50MHz Auto range 4 digit Dual Channel Frequency Counter Battery Operated or internal 7.5-4VDC or AC Adapter (not supplied). RS232 Comes in Back Carrying Pouch complete with 2 scope probes, DMM leads, Manual FOR ONLY £480



DTS 40 DIGITAL STORAGE OSCILLOSCOPE  
Dual Trace 40MHz 20MHz Storage Cursor - On Screen Readout, Sweep Delay, Interface etc. etc. Supplied Un-used in original box complete with 2 Probes & Manual  
AMAZING VALUE AT £400



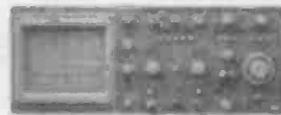DTA 204096 DUAL TRACE OSCILLOSCOPE  
with All Magnification TV Trig etc. etc. Lists of Specification  
DTA20 Dual Trace 20MHz £225  
DTA40 Dual Trace 40MHz-120V EHT £300  
DTA80 Dual Trace 80MHz-120V EHT £375  
All unused & boxed supplied with 2 probes & Manual




DTV 100 3 Channel 100MHz Sweep Delay etc. £425  
DTV 80 3 Channel 80MHz Sweep Delay etc. £375  
DTV 60 Dual Trace 20MHz £200
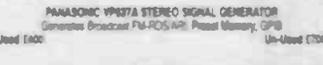
## NEW & HARDLY USED



PANASONIC VP177A PFM/SIGNAL GENERATOR  
1000Hz-100MHz FM 0-1000Hz Output -10dB-20dB AM 0-40%, 32 Preset Memory, Digital Display Frequency & Output  
Used £450 Un-Used £750



PANASONIC VP174A STEREO SIGNAL GENERATOR  
Generates Broadcast FM-RDS/RRI, Preset Memory, GPB  
Used £400 Un-Used £700




KENWOOD FL164A WAVEFORM METER  
0.005%-10% Freq 30kHz-150kHz RMS AVERAGE PEAK, Weighted Filters, Digital Display or rpm, 4 digit Peak Counter 0.01Hz-4.999Hz 0.1Hz-250kHz-250kHz  
Used £80 Un-Used £300



POWER SUPPLY MODEL HSP1614  
0-30 Volts, 0-10 Amps, Current Limiting, 2 Meters  
Used £70 Un-Used £200



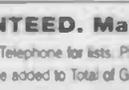GOODWILL GAC-600 AUDIO GENERATOR  
Sine/Square 10Hz-100kHz to 5 Ranges 0.1% Low Distortion 5 Steps Output Attenuator  
Un-Used £38



GOODWILL GFC 10196 FREQUENCY COUNTER  
Range 1Hz-120MHz  
8 Digit Display 15MHz RMS Sensitivity  
Un-Used £75



ANALOGUE MULTIMETER Beam HC8087R AC/DC Volts, DC Current 10Amps, 17 Ranges, Continuity Buzzer, Transistor Tester  
Un-Used £75



STEREO AUDIO BALANCE to UNBALANCED CONVERTOR for Car Radio: Sensitive Un-Used £28

**STEWART of READING**  
110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
Telephone: (0118) 9268041, Fax: (0118) 9351696  
Callers Welcome 9 am - 5.30 pm Monday to Friday (other times by arrangement)

**Used Equipment - GUARANTEED. Manuals supplied**  
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

## Electronic CAD

**WINDRAFT**  
Schematics

**WINBOARD**  
PCB Layout


**cadence SPECCTRA**  
Autorouter

*The complete, powerful schematic and PCB layout tools for Windows.*

- Design your schematic with WinDraft...
  - Choose from over 10,000 parts in WinDraft's complete library of components.
  - All the utilities you need are included in the package with an Electrical Rules Checker to netlist output to printing and plotting outputs.
  - Cut and Paste into other Windows applications such as Microsoft Word. Makes it easy to document your projects!
- Create the artwork for the PCB with WinBoard...
  - Quickly route boards on up to 16 layers.
  - Use SMD or through-hole components — or mix them for maximum flexibility.
  - Unique pad-stack editor can create pads of virtually any size or shape.
  - Rotate components in 0.01° increments.
- Create a Gerber photoplot, NC Drill, pick and place, and other manufacturing outputs!

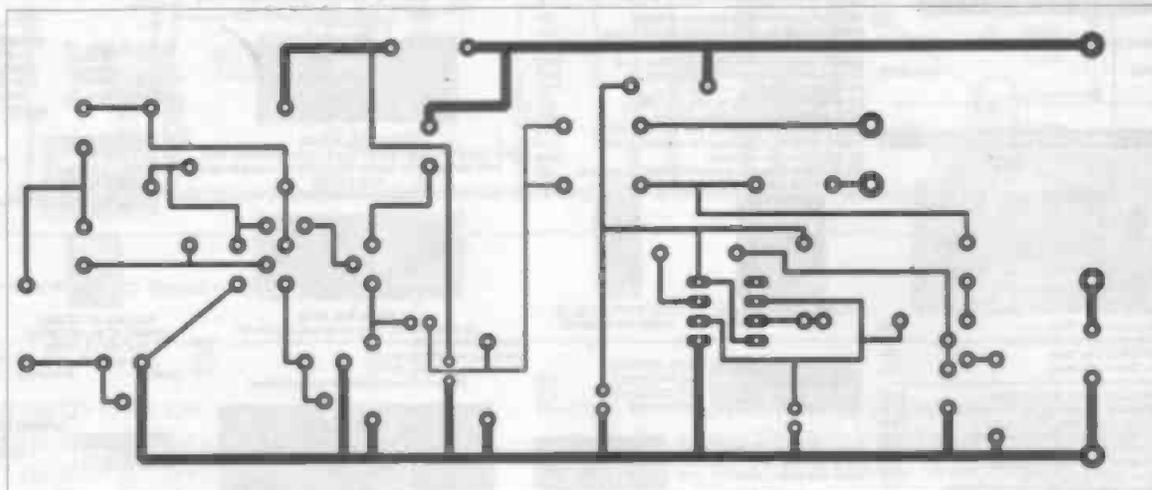
**Tel 0181 926 1161**

The PC Solution, 2a High Road Leyton, London, E15 2BP. Fax 0181 926 1160 <http://www.thepcsol.demon.co.uk>



Line Up Oscillator with Glitch

## Easy-PC for Windows 95 and NT!

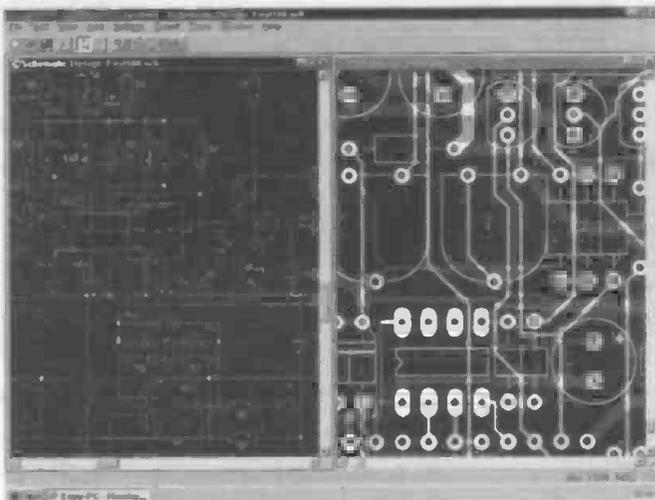

- 4th Generation Schematic Design and Printed Circuit Layout.
- By Engineers, for Engineers.
- Full links to our Analogue, Digital and Electromagnetic simulators.
- NO pin, net or layer limits!
- Fast, Intuitive Operation!
- Track and Component editing - a dream!
- Superb User Interface!
- *Competitive pricing!*

### Number One Systems

Write, fax, phone or e-mail for full information.


UK/EEC: Ref: ETI, Harding Way, St.Ives, Cambridgeshire, ENGLAND, PE17 4WR.  
Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042

e-mail: [sales@numberone.com](mailto:sales@numberone.com)  
International +44 1480 461778/494042


USA: Ref: ETI, 126 Smith Creek Drive, Los Gatos, CA 95030  
Telephone/Fax: (408) 395-0249

<http://www.numberone.com>




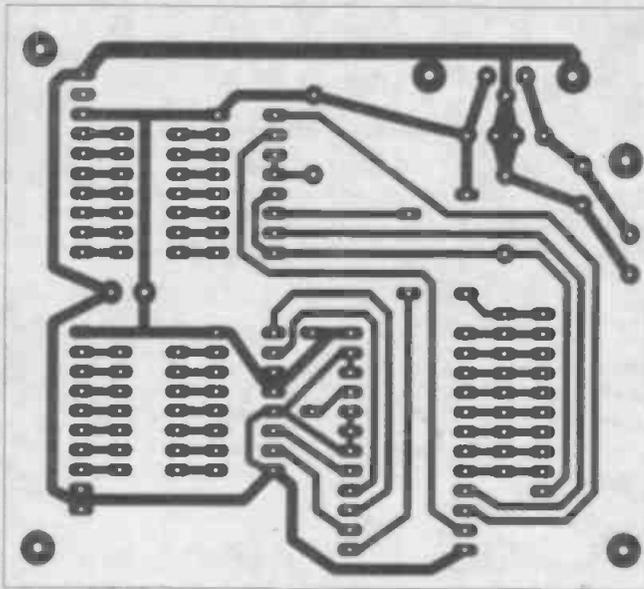


BB Ranger Control Board

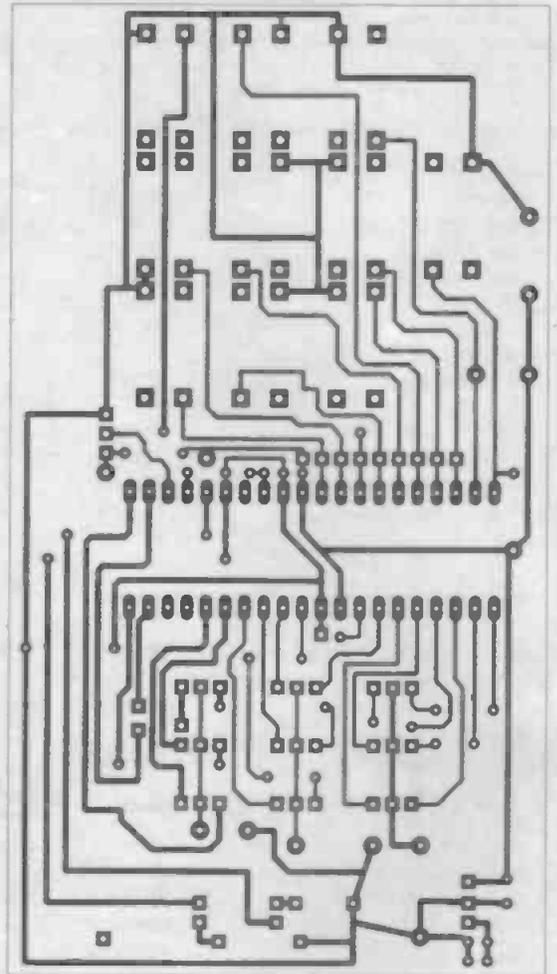


Tic Tac Toe

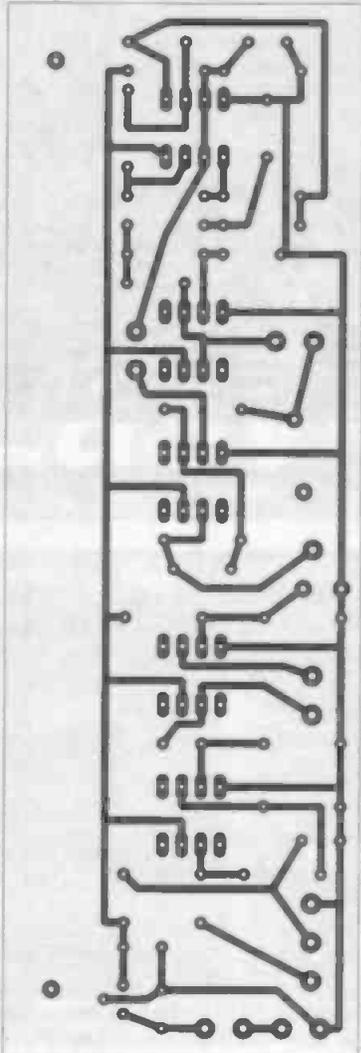

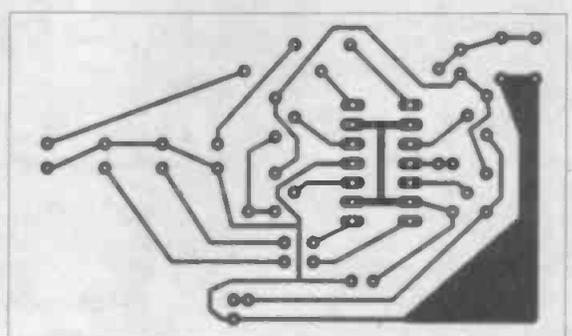5 Range Capacitance Meter  
ETI Issue 3 1998  
corrected print out



LED VOLTMETER

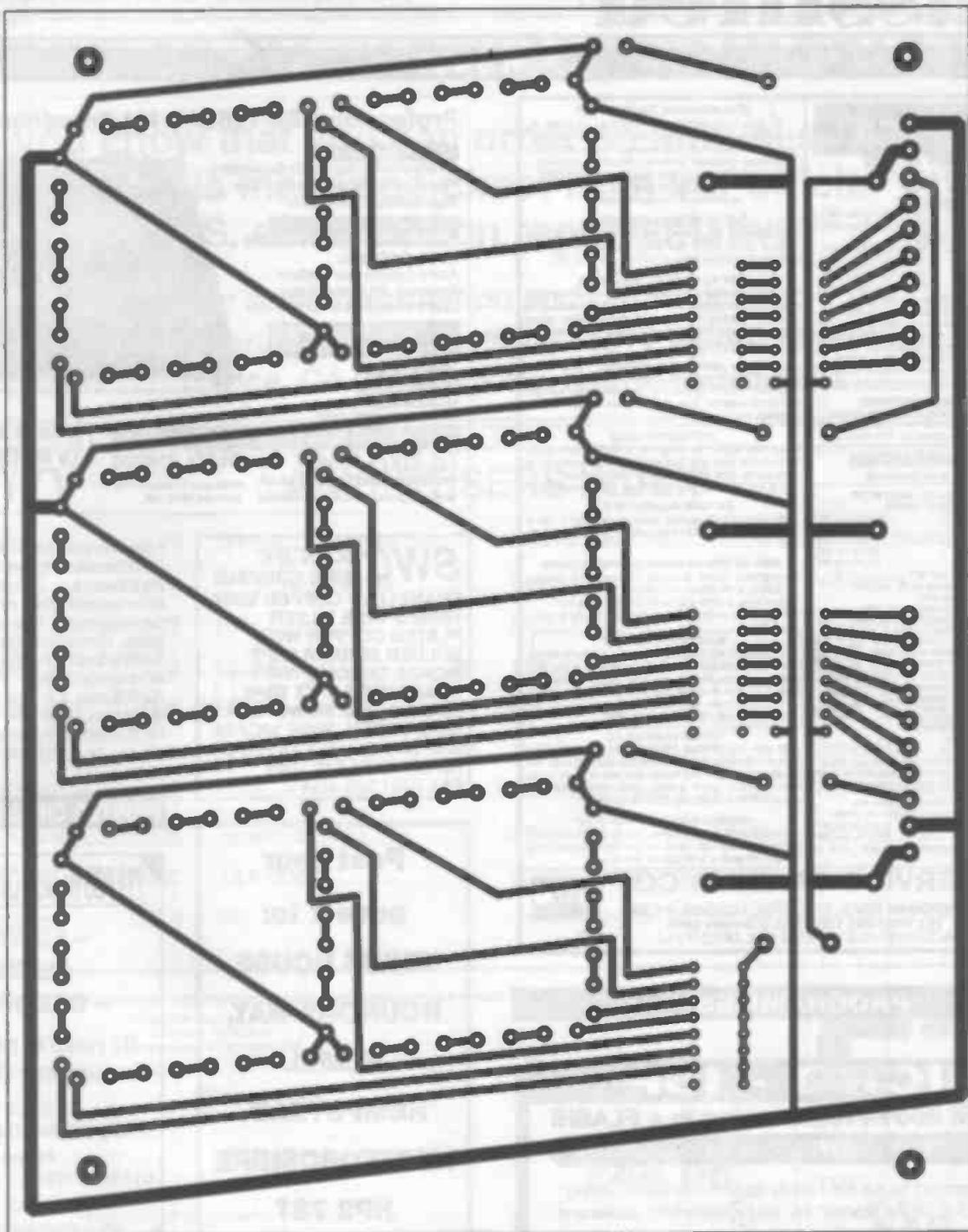

BB Ranger Score Board:



# Classified



## Andy Forder 01442 266551

Send your requirements to:  
ETI Classified Department, Nexus, Nexus House,  
Boundary Way, Hemel Hempstead, HP2 7ST  
Lineage: 85p per word (+VAT) (minimum 20 words)  
Semi display: (minimum 3cms)



£12.50 + VAT per single column centimetre  
Ring for information on series bookings/discounts.  
All advertisements in this section must be pre-paid.  
Advertisements are accepted subject to the terms and conditions  
printed on the advertisement rate card (available on request).

## FOR SALE

### VARIABLE VOLTAGE TRANSFORMERS

INPUT 220-240V AC 50/60

OUTPUT 0-260V

Price P&P

	Price	P&P
0 SKVA 2.5 amp max	£33.00	£3.00 (E45.83 inc VAT)
1 SKVA 5 amp max	£46.25	£7.00 (E53.25 inc VAT)
2 SKVA 10 amp max	£64.00	£10.00 (E74.00 inc VAT)
3 SKVA 15 amp max	£89.50	£13.00 (E102.50 inc VAT)
5 SKVA 25 amp max	£150.00	Plus Carriage & VAT
10 SKVA 45 amp max	£250.00	Plus Carriage & VAT
6 SKVA 3 PHASE Star	£280.00	Plus Carriage & VAT

Buy direct from the importers. Lowest prices in the country  
**COMPREHENSIVE RANGE OF TRANSFORMERS-LY-ISOLATION & AUTO**  
(110-240V Auto transfer either casted with American sockets and brass lead of open frame type. Available for immediate delivery.

### 500VA ISOLATION TRANSFORMER

New standard, surplus 'C' Core, incorporated with top plate and spider connections. 0.24V AC Pkts. 5-0-100-100-120V & 500VA. Size: 100 x 100 x 135mm. Price: £39.00. Cost: £27.50 (E46.50 inc VAT)

### RANGE OF XENON FLASH TUBES

Write/Phone your enquiries

### ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft 40 watt	£14.00 (eachers only)	£18.45 inc VAT
2ft 20 watt	£9.00 (eachers only)	£10.98 inc VAT
12in 8 watt	£4.80 + 75p p&p	£5.52 inc VAT
6in 4 watt	£3.95 + 50p p&p	£4.24 inc VAT
6in 4 watt	£3.95 + 50p p&p	£4.24 inc VAT

### 230V AC BALLAST KIT

For either 8in, 6in or 12in tubes. £9.05 + £1.40 p&p (E10.75 inc VAT)  
The above Tubes are 3500-4000 angst. (280-400nm) ideal for detecting security markings, effects lighting & Chemical applications.  
Other Wave Lengths of UV TUBE available for Germicidal & Photo Sensitive applications.  
Please telephone your enquiries.

### 400 WATT BLACK LIGHT BLUE UV LAMP

QES Mercury Vapor lamp suitable for use with 400W P.F. Ballast. £39.95 INCL. P&P & VAT

### 12V D.C. BILGE PUMPS

500 GPH 1 1/2" head 3 amp £18.95  
1700 GPH 1 1/2" head 3 amp £34.55  
Also now available 24V D.C. 1750 GPH 1 1/2" head 3 amp £35.55  
All designed to be used submerged. PRICES INCLUDE P&P & VAT

### SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical uses etc.  
Approx 18 pulses. Adjustable speed £30.00 + £3.00 p&p (E33.00 inc VAT)  
Case and reflector £24.00 + £3.00 p&p (E27.00 inc VAT)  
SAE for further details including Hy-Light and industrial Strobe Kits.

## SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB  
TEL 0181-995 1560 FAX 0181-995 0549  
ACCOUNT CUSTOMERS MIN, ORDER £10



Accepts Parking Space

### 5KVA ISOLATION TRANSFORMER

As New Ex-equipment fully shrouded Line Noise Suppression. Ultra Isolation Transformer with terminal covers and Knock-out cable entries. Primary 120/240V Secondary 120/240V 50/60 Hz. 508 pF Capacitance. Size L:37 x W:19 x H:18cm Weight 42 Kilos. PRICE: £120.00 + VAT  
ex-equipment. Carriage on request

### 24V DC SIEMENS CONTACTOR

Type 3TH4022 DB 2 x NO and 2 x NC 230V AC 10A contacts. Screw or Din Rail fitting. Size H 120 x W 45 x D 75mm. Brand New Price £7.63 incl. P&P and VAT.

### 240V AC WESTCOOL SOLENOIDS

TT2 Mod 1 1/2in. 1 MA. stroke 1/4 in. Base mounting 1/2in. stroke 5/8 in. pull approx. TT6 Mod 1 1/2in. 2 MA. stroke 1/8 in. Front mounting 1/2in. Front mounting 1/2 in. stroke 15/8 in. pull approx. Price incl. p&p & VAT TT2 £5.88, TT6 £8.81. SERIES 400 £7.64.

### AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan. Price £7.29 incl. P&P and VAT. Other voltages and sizes available from stock. Please telephone your enquiries.

### INSTRUMENT CASE

Brand new Manuf. by Imhof L31 x H18 x 10cm deep. Removable front and rear panel for easy assembly of components. Grey finish complete with case fast. PRICE £16.45 INCL. P&P & VAT 2 of £28.20 inclusive

### DIE CAST ALUMINIUM BOX

with internal PCB guides. Internal size 265 x 165 x 50mm deep. Price £9.93 incl. p&p & VAT 2 of £17.80 incl.

### 230V AC SYNCHRONOUS GEARED MOTORS

Brand new Onrod Gearbox. Crouzet type motors. H 55mm x W 55mm x D 35mm. 4mm dia shaft x 10mm long. 6 RPM and 6 RPM. Price £9.99 incl. p&p & VAT. 20 RPM and 6 RPM. Price £11.16 incl. p&p & VAT.

### SOLID STATE EHT UNIT

Input 230/240V AC, Output approx 15kV. Producing 0mm spark. Built-in 10 sec timer. Easily modified to 20sec. 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (E10.90 inc VAT) HMS

### EPROM ERASURE KIT

Build your own EPROM ERASURE KIT for a fraction of the price of a made-up unit. Kit of parts less case includes 12in x 8 inch 2537 Argon Tube Ballast unit, pair of 8-pin leads, neon indicator, erasol switch, safety microswitch and circuit £15.00 + £2.00 p&p (E17.00 inc VAT)

### WASHING MACHINE WATER PUMP

Brand new 240V AC, fan cooled. Can be used for a variety of purposes. Inlet 1 1/2 in. outlet 1 in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

## Professional 88-108MHz FM Broadcasting Kits

All our kits include:  
Detailed Instructions with Schematics  
High Quality Screen Printed PCBs  
High Quality Components

Our Product Range Includes:  
Transmitters from 0.05W to 220W  
FM Stereo Coders  
Audio Compressor Limiters  
Antennas RF Power Amps  
Link Transmitters and Receivers

Our Kits Are Also Available Fully Assembled And Tested




WE DELIVER WORLD-WIDE AND ACCEPT MAJOR CREDIT CARDS

Contact Us Now For A Free Brochure

Tel 01274 883434 Fax 01274 816200

email veronica@legend.co.uk

www.legend.co.uk/veronica/

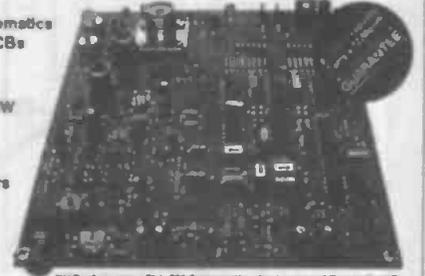

Professional PLL PCB Transmitter for Licensed Use in the UK

16 Veronicas St. Occidentary

Reister, E. HD 13 1AR



## SWC SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE  
TINNED WIRE SILVER  
PLATED COPPER WIRE  
SOLDER EUREKA WIRE  
NICKEL CHROME WIRE  
BRASS WIRE LJ TZ WIRE  
BIFILAR WIRE MANGANIN  
WIRE TEFLON WIRE NICKEL  
SAE BRINGS LIST 18 RAVEN  
RD LONDON E18 1HW  
FAX 0181 559 1114

<http://www.dontronics.com> Is DonTronics Home Page.  
Hardware: Atmel and PIC Microcontroller prototype and development boards, Programmers, SimmStick (tm).  
Software: Basic Stamp II Windows 95 Front End, AVRBasic for the AT90S1200, BascomLT for the AT89C2051, Multi-media "Pacman-like" Tutorial for the PIC16F84 and lots more

## PRINTED CIRCUIT BOARDS

### ??? PCB DESIGN OVERLOAD ???

- EDWIN -
- EED3 -
- CADSTAR -

WE COULD BE THE ANSWER.  
CONTACT SWIFT DESIGNS LTD

Email: Designs@SwiftDesigns.co.uk  
Phone: 01438 310133 - 01438 821811  
Web: www.swiftdesigns.co.uk

PRINTED CIRCUIT BOARDS  
DESIGNED & MANUFACTURED  
• PROTOTYPE OR PRODUCTION QUANTITIES  
• FAST TURNROUND AVAILABLE  
• PCBs DESIGNED FROM CIRCUIT DIAGRAMS  
• ALMOST ALL COMPUTER FILES ACCEPTED  
• EasyPC / Ares / Vutrax / CadStar  
Gerber / HPGL / IDeas and many others.  
• ASSEMBLY & TEST AVAILABLE  
TELEPHONE 01232 738897  
INTERNATIONAL +44 1753 708897

agar  
Circuits  
FAX: 01232 738897  
Email: agar@agarprint.co.uk  
Unit 6, East Belfast Enterprise Park,  
308 Altoncherry Road, Belfast, BT5 6GX

## PROGRAMMES

## MICRO - ISP

### In-system 8051 Programming in a FLASH!

Now supports the AVR Microcontroller Family

Code development for the 8051 family could not be easier. Simply plug the "Socket Stealer Module" into your existing 8051 socket and then use the Micro-ISP Programmer to download code (and data) to your target microcontroller without even removing it from the target socket.

## EQUINOX TECHNOLOGIES

The Embedded Solutions Company

Sales: 01204 492010 Technical: 01204 491110 Fax: 01204 494883

Visit our web page at: [www.equinox.tech.com](http://www.equinox.tech.com)

Email: [sales@equinox.tech.com](mailto:sales@equinox.tech.com)

**TRANSFORMERS**

**WVT** Variable Voltage Technology Ltd  
**TRANSFORMERS**  
 For valve and transistor circuits  
 HT Filament chokes high & low voltage  
 Standard and custom design  
 large and small quantities  
 Unit 24E, Samuel Whites Estate, Medina Road, Cowes, Isle of Wight PO31 7LP  
 Tel 01983 260592 Fax 01983 260593

**VALVES**

**WILSON VALVES**  
 (PROP JIM FISH GMBH)  
 Over 50,000 valves stocked,  
 2000 different types,  
 vintage, military, audio, etc.  
 Fast service. Send SAE for list  
**VALVES WANTED FOR CASH**  
 26 Banks Avenue, Golcar, Huddersfield,  
 West Yorks HD7 4LZ  
 Tel: 01484 654650  
 Fax: 01484 655699  
 Email: wilsonvalves@surlink.co.uk

**PLANS**

**ELECTRONIC PLANS**, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and com-puter graphics tablet. 150 projects. For catalogue, SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

**QUARTZ CRYSTALS**

**QUARTZ CRYSTALS** 100 KH2 - 100 MHZ at low cost. Full list available and technical advice. Electronic Design Associates. Tel: 0181-391-0545. Fax: 0181-391-5258.

**CALL ANDY TO PLACE YOUR ADVERT ON 01442 266551**

**ATTENTION ALL NORTH AMERICAN READERS!**

**Did you know that you can order an annual subscription to this magazine direct from our official U.S. subscription representative?**

*For more information and rates contact:*

**Wise Owl Worldwide Publications 4314 West 238th Street, Torrance, CA 90505 4509 Tel: (310) 375 6258**

**ADVERTISERS INDEX**

Agar Circuits . . . . .70	Electronic Design Association .71	Labcenter Electronics . . . . .43	Stewarts of Reading . . . . .65
Ambyr Ltd . . . . .70	EPT Educational Software . . . . IFC	Lasertech . . . . .49	Swift Designs . . . . .10
BETA Layout . . . . .28	EQT . . . . .72	Milford Instruments . . . . .72	Techno Info Services . . . . .59
B.K. Electronics . . . . .33	Equinox . . . . .IBC	NCT . . . . .72	Telnet . . . . .50
Bull Electrical . . . . .13,15	ESR Electronic Components . . .34	No1 Systems . . . . .66	Variable Voltage Technology Ltd .71
Chelmer Valves . . . . .49	Forest Electronics . . . . .49	No Nuts . . . . .44	Veronica FM . . . . .70
Confidential Communications . .44	Greenweld Electronics . . . . .55	Plancentre Publications . . . . .71	Wilson Valves . . . . .71
Crown Hill Associates . . . . .55	Harrison Electronics . . . . .72	PC. Solution . . . . .65	
Dataman Programmer Ltd . . .OBC	J & N Factors . . . . .52	Scientific Wire Co. . . . .70	
Display Electronics . . . . .6	JPG . . . . .72	Service Trading Co . . . . .70	

All adverts must be prepaid.  
 Cheques payable to:  
**Nexus Special Interests Ltd.**

Name . . . . .  
 Address . . . . .  
 Daytime Tel. No. . . . .  
 Signature . . . . .  
 Date . . . . .

PLEASE DEBIT MY ACCESS/BARCLAY CARD No.

EXPIRY DATE

FOR SALE COMPONENTS PLANS OTHER—PLEASE STATE  
 Please ring the required heading.

**ETI**

3 x 1  
**£44.06**  
 inc vat

20 words lineage  
**£19.97**  
 inc vat

**ELECTRONIC TODAY INTERNATIONAL**  
 CLASSIFIED ADVERTISEMENT DEPARTMENT,  
 NEXUS HOUSE, BOUNDARY WAY, HEMEL HEMPSTEAD HP2 7ST




## DISTANCE LEARNING COURSES in:

Analogue and Digital Electronic Circuits, Fibres & Opto-Electronics Programmable Logic Controllers Mechanics and Mechanisms Mathematics

- Courses to suit *beginners* and those wishing to *update* their knowledge and practical skills,
- Courses are delivered as self-contained kits
- No travelling or college attendance
- Learning is at your own pace
- Courses may have BTEC Certification and Tutoring


For Information contact:  
NCT Enterprises  
Barnfield Technology Centre  
Enterprise Way, Luton LU3 4BU  
Telephone 01582 569757 • Fax 01582 492928
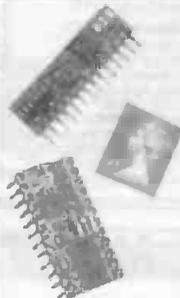
# CONTROL & ROBOTICS from Milford Instruments



**BASIC Stamps**  
reprogrammable stamp sized computers  
Easy to use BASIC language

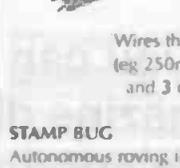- 8 or 16 Input/Output lines each 20mA capability
- 80 or 500 Program lines
- Re-programmable thousands of times from PC or Mac ● 5-12VDC Supply. Stamps from £25.00 each. Development Kits including programming software, Stamp, Cable, Project Board and 25+ Application notes from £79.00.



**MUSCLE WIRES**  
Wires that contract approx 5% when heated (eg 250mA current) -120 page Project book and 3 one metre lengths of wire. £40.00

**STAMP BUG**  
Autonomous roving insect using the BASIC Stamp as its "brain". Approx 300mm overall length.  
KITS FROM £29.00



**LYNX ARM**  
5 Axis robot arm kit; approx size 300mm. Control from any serial comms port or Stamp. Includes software to run from PC. KITS FROM £85.00



All prices exclude VAT and shipping.  
For a full catalogue of the above items and other products, please call or fax Milford Instruments at 01977 683665; Fax 01977 681465.

## Surplus Electronic Components

Example price each for 25 off quantity:

27256-2	.75	78M09	.20
27C256-120	.75	78M12	.20
27C512-2	1.80	7812	.20
27C1001-20	2.60	7815	.20
CD4046BCN	.20	7906	.20
CD4066BCN	.10	4N25	.10
MC74HC373	.16	LM339N	.09

Write, FAX, Phone or e-mail for full list

### Harrison Electronics

Century Way, March, Cambs. PE15 8QW  
email: harrison.electronics@mcmall.com  
Tel/Fax:(01354) 651289

Mini waterproof TV camera 40x40x15mm requires 9 to 13 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) It has a high resolution of 450 TV lines Vertical and 380 TV lines horizontal, electronic auto iris for nearly dark (1 LUX) to bright sunlight operation and a small lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12v in gnd and video out). Now also available with seal mount kit and velvet case (at the same price). £93.57 - vat = £109.95 or 90+ £89.32 - vat = £104.88

Board camera kit with 512x582 pixels 4.4x3.3mm sensor 9-13 volts power supply and composite video out. All housed to be housed in your own enclosure and have fragile exposed surface mount parts. 47MR size 80x36x27mm with 6 infra red leds (gives the same illumination as a small torch would) £50.00+vat = £58.78 40MP size 30x36x23mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole. £57+vat = £66.98 40MC size 30x36x28mm camera for C mount lens this gives a much clearer picture than with the small lenses £68.78+vat = £80.63 standard C mount lens F1.6 16mm for 40MC £28.43+vat = £31.68

High quality stepping motor kits (all including stepping motors) "Comet" independent control of 2 stepping motors by PC (through the parallel port) with 2 motors and software. Kit £87.00 ready built £96.00 software support and 4 digital inputs kit £27.00 power interface 4A kit £38.00 power interface 6A kit £46.00 Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit £23.00

DTA30 Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty (NEW VERSION does not say PETS & SCRs are transistors) DTA30 £38.34

HMA20 hand held MOSFET analyser identifies gate drain and source and I/P or N channel HMA20 £38.34

Speaker cabinets 2 way speaker systems with Motorola tweeters

speaker dia	15"	2"	8"
power rating	2200W RMS	1750W RMS	1000W RMS
impedance	8ohm	8ohm	8ohm
frequency range	40Hz-20kHz	40Hz-20kHz	40Hz-20kHz
sensitivity 1W/1m	91dB	94dB	92dB
size in mm	502x720x40	450x402x45	315x482x20
weight	21.1kg	16.8kg	7.4kg

price each kit  
black vinyl coating £139.95 £99.99 £54.84  
grey felt coating £159.97\*\* £119.97\*\* £64.99  
(\*\* = not normally in stock allow 1 week for delivery)

Power amplifiers 15" rack mount with gain controls & VU meters

STA300 2x150W RMS (4ohm load) 11kg	£339.00
STA600 2x400W RMS (4ohm load) 15kg	£585.00

LED's 3mm or 5mm red or green . 7ip each yellow 11p each cable fits 1p each £3.95 per 1000 £48.50 per 10,000

Rechargeable Batteries

AA (HP7) 500MAH £0.99	AA 500MAH with solder tags £1.55	AA 950MAH £1.75	CD (HP11) 1.2AH £2.20
2AH with solder tags £3.60	DH (P2) 1.2AH £2.60	D 4AH with solder tags £4.95	PP3 3.6V 110MAH £4.95
1/2AA with solder tags £1.58	Sub C with solder tags £2.50	AAA (HP16) 100MAH £1.75	1/3 AA with tags (philips) £1.85

Nicad Metal Hydrate AA cells high capacity with no memory if charged at 100ma and discharged at 250ma or less 1100MAH capacity (lower capacity for high discharge rates) £3.75

Special offers please check for availability stock of 4.42 x 16mm nicad batteries 171mmx10mm dia with red & black leads 4.8v £5.95

8 button cast 6V 280mAh battery with wires 5x2500K £2.45

Orbital 666 battery pack 12v 1.6AH contains 10 sub C cells with solder tags (the size most commonly used in cordless screwdrivers and drills 22 dia x 42mm tall) It is easy to crack open and was manufactured in 1994. £8.77 each or £116.50 per box of 14

BCI box 100x100x50mm with slots to house a pcb the lid contains an edge connector (12 way 6mm pitch) and screw terminals to connect to wires and 5 slides in cable banna. £2.95

7 segment common anode led display 12mm £0.45

GAAs FEY low leakage current S8873 £12.95 each £9.95 10+ £7.95

BC547A transistor 20 for £1.00

SL952 UHF limiting amplifier LC 16 surface mounting package with data sheet £1.95

DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output isolation with data £4.95 each or pack of 10 £38.99 Arpaas A82903-C large stepping motor 14v 7.5' step 270mm 68mm dia body 6.3mm shaft £8.95 or £200.00 for a box of 30 Polyester capacitors box type 22.5mm lead pitch 0.5uF 250vdc 18p each 14p 100+ 9p 1000+ 1uF 250Vdc 20p each 15p 100+ 10p 1000+ 1uF 50v bipolar electrolytic axial leads 18p each 7.5p 1000+ 0.22uF 250v polyester axial leads 15p each 7.5p 100+ Polypropylene 1uF 400Vdc (Wima MKP10) 27.5mm pitch 32x28x17mm case 75p each 95p 100+

Philips 123 series solid aluminium axial leads 33uF-10v & 2.2uF 40v-40p each, 25p 100+ Philips 18B sense long life 22uF 63v axial 75p each 15p 1000+ 500uF compression trimmer 60p Solid carbon resistor very low inductance ideal for RF circuits 27ohm 2W, 744C 2W 25p each 15p each 100+ we have a range of 0.25m 0.5m 1m and 2m solid carbon resistors please send SAE for list

PC. 400W PSU (Intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains interlock connectors on back and switch on the side (top for lower case) dms212x140x140mm excluding switch, £26.00 each £138.00 for 6 MX180 Digital multimeter 17 ranges 1000vdc 750vac 2kOhm 200mA transistor hfe 9v and 1.5v battery test £9.95

Hand held ultrasonic remote control £3.95 CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £8.50 per 100 Verbatim R300H4 Streamer tape commonly used on rd machines and printing presses etc it looks like a normal cassette with a slot cut out of the top £4.95 each (£3.75 100+) Heatsink compound tube £0.80

HV3-2405-ES 5-24v 50mA regulator ic 16-264vac input 8 pin DIL package £3.49 each (100+ £2.35)

LM 555 timer ic 18p, 8 pin DIL socket tip all products advertised are new and unused unless otherwise stated wide range of CMOS TTL 74HC 74F Linear Transistors plus rechargeable batteries capacitors tools etc always in stock

Please add £1.95 towards P&P (orders from the Scottish Highlands, Northern Ireland, Isle of Man, Isle of Wight and overseas may be subject to higher P&P for heavy items) VAT included in all prices

### JPG ELECTRONICS

ETI 276-278 Chatsworth Road  
Chosserfield S40 2BH  
Access Via Orders (01246) 211202 ext 550959  
Callers Welcome 9.30am-5.30pm Monday-Saturday

## EQT LTD STEVENAGE

Professional Sub-Contract Manufacturing & Suppliers to the Electronics Industry

- Do you have a requirement for any of the following services:
- PCB Assembly (Conventional and Surface Mount)
  - Wave & Hand Soldering
  - Complete Equipment Manufacture
  - Device Programming from hand written shits or PC 3 1/2" disc
  - Cable Harness Assembly/loom Manufacture
  - Card Cage and Module Wiring
  - Full Inspection
  - Product Design/Consultation
  - Full Procurement Service
  - PCB Test & "Burn in" Facilities
  - Enclosure Design & Manufacture
  - PCB Artwork Manufacture
  - Circuits Drawn Professionally
  - Kit Procurement & Supply
  - Component Sales
  - Refurbishment a speciality
  - Top Quality Work at Reasonable Rates

Phone Steve on (01438) 360406 or fax details of your requirements to us on (01438) 352742  
EQT LTD, Cromer House, Caxton way, STEVENAGE, HERTS, SG1 2DF

## Peak Electronic DCA50 Component Analyser

*A neatly made analyser than can identify transistors, diodes and LED and give the pin-outs quickly and without fuss.*

**T**he DCA50 is an analyser designed to identify discrete semiconductors and their connections. It can test a variety of two-terminal or three-terminal devices, chiefly diodes, mosfets and bipolar transistors. Three-terminal diode networks can be tested for the presence of diode junctions, and the individual junctions can be identified.

The analyser has three leads - in red, green and blue for quick identification - each terminated in a miniature crocodile clip. The readout is a two-line liquid crystal dot matrix display. The heart of the instrument is a PIC16C64.

Components are tested simply by connecting each of the two or three connections of the component to the crocodile clips in any order and operating the one button on the front panel. For a couple of seconds, the unit displays the message "DCA950 Component Analyser (R1010)", and then the analysis, such as "NPN Transistor RGB=>BEC Hfe=460", appears. This message was displayed when testing a BC109 transistor. The second time I tested the same device, the Hfe reading came up as 445.

The tester can identify signal diodes, rectifier diodes, zeners and also identify the terminals of a light emitting diode, and flash the component for a visual indication that it is functioning (regardless of which way round it is).

At more length, the main components that can be tested are P- and N-channel enhancement mosfets; NPN and PNP transistors; diodes and diode networks, and LEDs. It can indicate Hfe for bipolar transistors in the range 5 to 955, with an error of 5 Hfe and +/- 4 percent of the reading. Darlington transistors can be tested, but are likely to exceed the maximum range of measurement, in which case a reading of 955 is displayed.

The DCA50 cannot, apparently, test depletion mode mosfets and junction fets (which are inevitably depletion devices, and therefore not supported. They are, in any case, not in such widespread use as they used to be) but it will indicate the anode and cathode of any diode junctions, which effectively identifies the gate, and determines whether the device is N-channel or P-channel. The same method is used to read faulty transistors (if they are readable at all). If the current gain is very low or non-existent, the DC50 should be able at least to identify one or both diode junctions. Some diode-protected transistors cannot be accurately identified.

The analyser's crocodile clips are small, but they are not small enough to make easy contact with the thin wires of TO92 transistors. Surface mount devices are even harder to connect to.

It is very useful in that it can identify the pin connections of unknown devices, including the determination of which is the collector and which the emitter in junction transistors. It is easy enough to identify the base by using an ordinary multimeter on the

diode test range, but to identify collector and emitter automatically saves a lot of effort.

### Black and blue

The black case feels robust enough for general use, and fits neatly in the hand. The stylish metallic blue lettering on the case is more eye-catching than easy to read, but this may actually be an advantage, as it does not distract from the display.

The unit is specifically for examining components out of circuit, and includes a warning against trying to test components in a powered circuit, as damage to the analyser and possibly the test circuit may occur.

It will be a useful aid in replacing components in equipment which incorporates discrete semiconductors, particularly semiconductors with indecipherable markings. It will also help in making sure that semiconductors are connected up correctly in prototypes.

In operation, it is handy and trouble-free. You simply connect it up to the component, press the single button, and it gives you a readout. The readout is clear, and as long as you have read the instruction booklet to make sure that you understand the correspondences on the readout, you should know at once which leads are the collector, base and emitter, or cathode (k) and anode (a), depending on the kind of readout given.

The instructions give a table of testable component types and the parameters within which they can be tested accurately. The makers say that the analyser is optimised for the vast majority of supported component types; a minority will fall outside the required operating conditions.

Maintenance on the component analyser amounts to making sure that the PP3 or equivalent battery is changed at least every 18 months to guard against inadvertent battery leaks. A battery warning appears when the battery is nearing the end of its life.

Although it may be more than the hobby user would spend in order to identify the occasional recalcitrant transistor, the DCA50's basic list price of £49 is good for a PIC-driven instrument with this much functionality, and is well worth considering if there is much component identification to be done. We found it particularly useful for quick-testing diodes from the diode box before using in displays or prototypes.

The 8-page instruction booklet is easy to follow and clearly illustrated, and includes the parameter list for components capable of being tested accurately.

For information, prices etc. contact Peak Electronic Design, 70 Nunsfield Road, Buxton, Derbyshire SK17 7BW, UK.



Published by  
Nexus Special Interests Limited  
Nexus House, Boundary Way,  
Hemel Hempstead, Herts HP2 7ST  
Tel 01442 266551 Fax 01442 266996  
Sorry, we cannot answer queries about projects or other  
technical question on the phone. Please write to the address  
above. Our admin assistant can often help with other queries  
about this issue.

## Fine lines and slim salaries

**A** team of graduate students from the University of Texas in the USA, working with DuPont Photomasks Inc., has made a major

breakthrough in semiconductor production design in a way that nobody thought possible with the current technology.

The student team, led by chemistry and chemical engineering professor Grant Willson, produced a semiconductor wafer print etched with features 0.08 micron in width, the thinnest etching yet achieved, and not expected before around 2008. Further, the etching was achieved with the 193-nanometre wavelength of light, rather than the much finer beams used in more experimental research. It had been expected that technology still in very early stages of development, such as extreme ultraviolet or x-ray lithography, would be needed to achieve such small lines, but instead it has been done with the same sort of optical technology used for the current generation of 0.25 micron semiconductors.

It is not yet known whether this will turn out to be a commercially viable process, and it is likely to be several years before this is determined. One interesting thing is that, using the 193-nanometre wavelength of light, the features etched are effectively finer than the etching beam used.

But beside this dramatic progress, in the USA, as in the UK, there is a shortage of technical skills. American companies have asked the government to increase the number of foreign workers who can be given temporary visas. Companies as reputable as Microsoft, Cypress Semiconductor, and Texas Instruments are all reported to be lamenting the skills shortage.

Texas Instruments' Stephen Leven is reported to have found evidence that the image of high tech workers is distinctly uncool with American youth. "Recently, I was shown a drawings by children asked to

envision someone in the high technology

industry," said Leven. "Their images of the folks who work in our companies are unflattering ... men with pocket protectors, crooked glasses and rumpled clothing ..." Dilbert rules.

Too often it seems that the engineering image in Britain is even more comic. The difference is that the American response has been to offer higher salaries to attract the people who are available, while in Britain, although salaries are not too bad for technical people, they are not in the same range. As an example, \$40,000 (about £25,000) was offered for graduates with a very modest bachelor's degree from an average college.

Britain's attitude is compounded by some of the great and the good who think that the ability to understand anything technical means an inferior intellect. There is certainly a difference in outlook between engineers and politicians. As we know, engineers tend to regard facts as reasonably fixed and verifiable, while politicians sometimes seem to regard them as infinitely mutable.

The attitude is typified by an MP on the first day TV cameras were used in the House of Commons. The interviewer asked whether he would watch his performance on video afterwards, and he replied, with pride ringing in his voice, that although they had a video recorder, neither he nor his wife knew how to operate it.

This was an extreme indication of the ignorance of the true economic significance of science and technology. Despite, or perhaps even because of this, governments the world over react slowly to most technological advances.

Speaking of which, we hope to have an ETI page on the World Wide Web soon. The url will be published as and when it is set up. If you try a search engine, you may get a preview before the magazine containing the url is published.

## EDITORIAL

Editor

Helen Armstrong

Administration Assistant

Sandra Ballantyne

Consultant

Andrew Armstrong

## PRODUCTION

Designer

David Rice

Technical Illustrator

John Puczynski

Production Executive

Marie Quilter

Printed By

Wiltshire Ltd., Bristol

Origination by

Atelier, St. Austell

## SALES

Midland and Southern Area Sales

Andrew Forder

01442 266551

Northern Area Sales

Denise Barrow

0161 776 4460

Group Advertisement Manager

Diana Farnham

## MANAGEMENT

Divisional Managing Director

Tony DeBel

Business Manager

Stuart Cooke

Circulation Manager

William Pearson

Copy Sales Manager

David Pagendam

## SUBSCRIPTIONS

UK Orders 01858 435344

Enquiries 01858 435322

USA: Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA 90505-4509, USA. For VISA/Mastercard orders phone (310) 375 6258. Fax (310) 375 0548. Pacific Time: 9am - 9pm weekdays 10am - 6pm weekends. Visa/MC/Discover accepted.

READERS SERVICES

Back issues (last 12 months) £3.20 per issue if available. Older issues photocopies of older articles often available. Write to The Photocopy Service, Readers Services Department, at Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST. Binders for ETI: £7.50 each including UK post and packing. Overseas please add £1.50. Cheques to Nexus Special Interests at Nexus House, or phone VISA/Mastercard orders to Readers Services Department 01442 266551.



© Nexus Special Interests Limited 1998

All rights reserved

ISSN 0142-7229

The Publisher's written consent must be obtained before any part of this publication may be reproduced in any form whatsoever, including photocopies, and information retrieval systems. All reasonable care is taken in preparation of magazine contents, but the publishers, editors and their agents cannot be held legally responsible for loss howsoever arising from errors or other published material.

## Next Month

Volume 27 no. 4 of Electronics Today International will be in your newsagents on 24th April 1998 ... Geoff Pike GI0GDP's unusual UHF model radio controller looks set to take off ... Robert Penfold is working on a noise limiter for music systems ... Robin Abbott starts a new introduction to PIC programming with emphasis on more advanced microcontrol ... we have some more electronic games ... plus all the regulars, and more.

Contents are in preparation but are subject to space and availability.

# The Ultimate 8051 Microcontroller Programmer

- Supports Atmel FLASH 89C +89S, Generic 87C51/52/FA/FB/FC microcontroller derivatives
- FLASH & E<sup>2</sup> libraries also available as chargeable update

**NOW £125.00**

▲ £125.00 Order Code: MPW-SYS


## 8051 2K Starter System

For C51 Project Development...in a FLASH  
Includes: Programmer, Evaluation module and PK51-2K ▶

▲ £199.00 Order Code: AT-89C-2K-ST
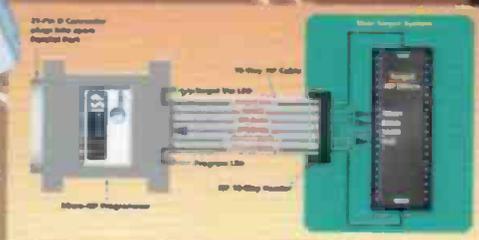
## MICRO-ISP In-System Programming (ISP)

"Now you can program the 8051 or the AVR™ without removing the device from the socket!"



▼ Order Code: AVR-ST £59.95

£39.95 Order Code: UISP-V2-SYS ▲

# AVR™ Professional Starter System

### FEATURES

- Supports Atmel 90S (AVR) RISC microcontroller family
- Supports Parallel Programming mode in ZIF socket
- Supports In-System Programming via ribbon cable (provided)
- Equinox FAST ISP Programming Algorithm
- All on-chip facilities supported e.g. RC Osc.

### SYSTEM CONTENTS

- Professional Device Programmer
- Atmel AVR™ Assembler
- AVR™ Basic Lite Compiler (NEW)
- Atmel Databook on CD ROM
- Power Supply
- ISP Ribbon Cable (to target)
- Serial Cable (to host PC)

**NOW SUPPLIED AVR BASIC LITE**

## Write in BASIC, Run in a FLASH

**NEW**

- Compiled BASIC generates tight AVR™ machine code
- Not a Run-Time Interpreter; NO code overhead
- Target speeds comparable with assembler
- Breaks the cost barrier for small projects
- Ideal for educational, hobbyist and professional use


From Only £24.95!

## AVR BASIC LITE

- AVR™ BASIC LITE only supports the AT9012LH (\$12 words total)
- BK version also available

Order Code: AVR-BAS-LIT £24.95

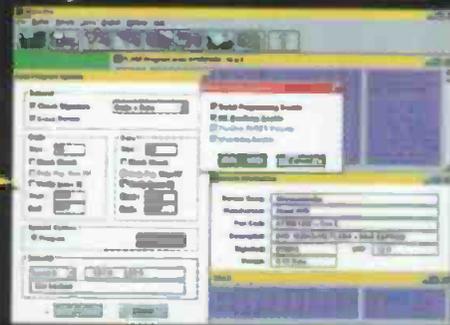▼ Programmer Interface Software for Windows™



▲ Keil 8051 C compiler, Assembler, Simulator (2K code), Windows™ IDE

▲ £99.00 Order Code: PK51-2K

## 89S Socket Stealer Module

Simply plug this into your existing 8051 or AVR™ socket for INSTANT In-System Programming

NO Target System redesign required.



▲ £49.00 Order Code: SS-89S-DIL40



The Embedded Solutions Company

# PROVIDING THE SOLUTIONS TO YOUR PROBLEMS!

Tel: +44 (0) 1204 529000  
Fax: +44 (0) 1204 535555

For product information visit our web site at:

[www.equinox-tech.com](http://www.equinox-tech.com)

E-mail: [sales@equinox-tech.com](mailto:sales@equinox-tech.com)

3 Atlas House, St Georges Square, Bolton, BL1 2HB UK




EQUINOX DISTRIBUTORS: AUSTRALIA Farnell +61 2 9645 8888 AUSTRIA Farnell +43 0660 87 75 BELGIUM Alcom Electronics Nvha +32 3 227 36 47 Farnell +32 03 227 36 47 BRAZIL Mastec +55 11 522 1799 Anacom +55 11 453 5588 DENMARK Farnell +45 44 53 66 44 EIRE Farnell +353 1 8309277 FINLAND Farnell +358 9 3455 400 FRANCE Farnell +33 474 65 94 66 Hewlett +33 1 4687 2200 GERMANY Farnell +49 89 61 39 39 39 Inhatel GmbH +49 7321 93850 MSC Vertretis GmbH +49 08 9945532 12 GREECE Microtec +30 1 5395042 & HONG KONG Farnell 800 968 280 OK Direct Toll Free ITALY Farnell +44 113 231 1311 Grifo Italian Technology +39 51 89 20 52, Newtek Italia +39 2 33 10 53 08 MALAYSIA Farnell +60 3 773 8000 NETHERLANDS Alcom Electronics BV +31 10 4519533 Antratek +31 10 450 4949 Farnell +31 30 241 2323 NEW ZEALAND Farnell +64 9 357 0646 NORWAY ACTE NC +47 63009000 Jakob Husterland Electronic AS +47 53763000 PORTUGAL Anacom +35 119 371 834 Farnell +44 113 289 0040 SINGAPORE Farnell +65 788 0200 SPAIN Anacom SA +34 1 366 01 59 Farnell +44 113 231 0447 SWEDEN ACTE NC +46 8 445 28 70 Farnell +46 8 730 50 00 SWITZERLAND Anacom Ag +41 41 748 32 41 Farnell +41 1 204 64 64 UNITED KINGDOM Alcom Electronics +44 1206 751166 Quamdon Electronics +44 1332 332651 USA Hitco Inc +1 408 298 9077 Newark Electronics +1 800 718 1997 Peachtree Technology +1 770 888 4002 Pioneer Standard +1 888 832 2976

Equinox reserves the right to change prices & specifications of any of the above products without notice. E&OE. All prices are exclusive of VAT & carriage. AVR™ is a trademark of the Atmel Corporation

# STILL THE WORLD'S MOST POWERFUL PORTABLE PROGRAMMERS?

£495+VAT

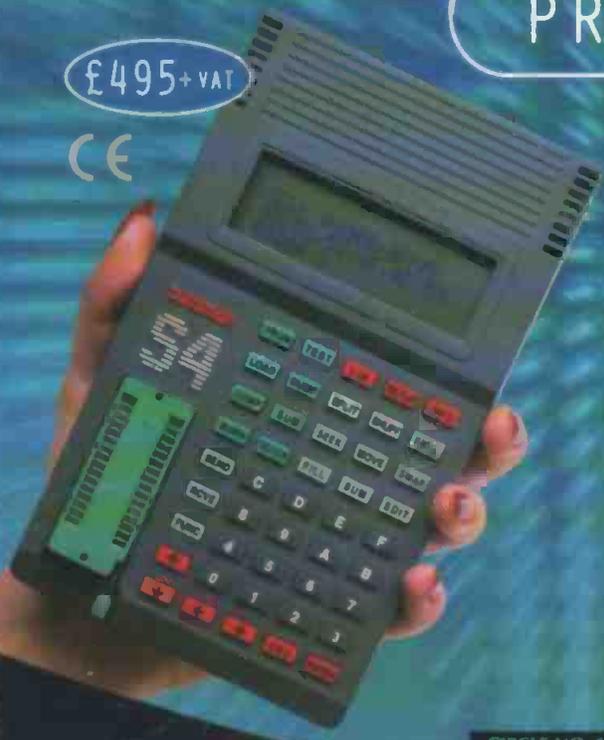

CIRCLE NO. 103 ON REPLY CARD

NEW MODEL



£795+VAT

SURELY NOT.  
SURELY SOMEONE SOMEWHERE HAS  
DEVELOPED A PORTABLE PROGRAMMER  
THAT HAS EVEN MORE FEATURES, EVEN  
GREATER FLEXIBILITY AND IS EVEN  
BETTER VALUE FOR MONEY.

ACTUALLY, NO. BUT DON'T TAKE OUR  
WORD FOR IT. USE THE FEATURE  
SUMMARY BELOW TO SEE HOW OTHER  
MANUFACTURERS' PRODUCTS COMPARE.

## DATAMAN-48LV

- Plugs straight into parallel port of PC or laptop
- Programs and verifies at 2, 2.7, 3.3 & 5V
- True no-adaptor programming up to 48 pin DIL devices
- Free universal 44 pin PLCC adaptor
- Built-in world standard PSU - for go-anywhere programming
- Package adaptors available for TSOP, PSOP, QFP, SOIC and PLCC
- Optional EPROM emulator

## DATAMAN S4

- Programs 8 and 16 bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 microcontrollers and more
- EPROM emulation as standard
- Rechargeable battery power for total portability
- All-in-one price includes emulation leads, AC charger, PC software, spare library ROM, user-friendly manual
- Supplied fully charged and ready to use

## S4 GAL MODULE

- Programs wide range of 20 and 24 pin logic devices from the major GAL vendors
- Supports JEDEC files from all popular compilers

## SUPPORT

- 3 year parts and labour guarantee
- Windows/DOS software included
- Free technical support for life
- Next day delivery - always in stock
- Dedicated UK supplier, established 1978

**Still as unbeatable as ever.** Beware of cheap imitations. Beware of false promises. Beware of hidden extras. If you want the best, there's still only one choice - Dataman.

Order via credit card hotline - phone today, use tomorrow.

Alternatively, request more detailed information on these and other market-leading programming solutions.

## MONEY-BACK 30 DAY TRIAL

If you do not agree that these truly are the most powerful portable programmers you can buy, simply return your Dataman product within 30 days for a full refund

**hotline**  
01300 320719



Orders received by 4pm will normally be despatched same day.  
Order today, get it tomorrow!

**DATAMAN**

Dataman Programmers Ltd, Station Rd,  
Maiden Newton, Dorchester,  
Dorset, DT2 0AE, UK  
Telephone +44/0 1300 320719  
Fax +44/0 1300 321012  
BBS +44/0 1300 321095 (24hr)  
Modem V.34/V.FCN.32bis  
Home page: <http://www.dataman.com>  
FTP: [ftp.dataman.com](ftp://ftp.dataman.com)  
Email: [sales@dataman.com](mailto:sales@dataman.com)