

THE FINGER THAT NO-ONE FORGETS

Soon your fingerprint will be the key to your identity - and your car

PCs: THE BIOS AND THE HARD DISKS

Setting-up is the hardest part of upgrading your PC

USING PICs WITH THE I²C BUS

More data into fewer pins with the I²C standard

18-CHANNEL INFRA RED REMOTE CONTROLLER

Can be built into other equipment

PLUS

- THE BATH DUCK
- Q METER
- TECHNICAL TIPS



Vol. 27 Issue: 9 14th August 1998 -
10th September 1998 £2.75 U.S.A. \$4.95

Electronics Principles 5.0

'A COMPLETE PC BASED ELECTRONICS COURSE'

If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.

Now includes the PIC16F84 & PIC16C71 hardware and instruction set.

EP5.0 is a significant upgrade of our popular electronics software with even more analogue, digital and microprocessor electronics PLUS over a hundred new engineering maths topics to further your understanding of formulae and calculations. Approved by Microchip, the PIC16F84 microcontroller hardware and instruction set has been introduced and brought to life through colourful interactive graphics where you can study the architecture of this device, changing the data values to simulate all of the registers and the complete instruction set, including direct/indirect addressing, program/data memory and input/output port configuration. In addition the analogue to digital functions of the PIC16C71 device. If you would like to learn more about the principles of these popular microcontrollers then it could be made easier.

Electronics Principles software is currently used in hundreds of UK and overseas schools and colleges to support City & Guilds, GCSE, A-Level, BTEC and university foundation courses.

Telephone for a list of the 560 topics included.

Available separately as individual modules.

1. DC Principles £19.95*
2. AC Principles £19.95*
3. Transistor & Op-Amp Principles £19.95*
4. Engineering Mathematics Principles £19.95*
5. Digital Principles £19.95*
6. Microprocessor Principles £19.95*
7. PIC Principles £19.95*

Complete Electronics Principles 5.0 £99.95*

ACTIVE FILTERS: RC Low Pass Active Filter:

Constructing low frequency passive filters often requires the use of inductors which can have large values and therefore are both expensive and bulky. The same low frequency cut-off points can be determined using active filters, where inductors are rarely used owing to their d.c. resistance. The simple circuit shown has a roll-off of -20dB per decade. To achieve steeper slopes the circuits can be...


OSCILLATORS: Astable Multivibrator.

The formulae to determine the period of C2 will sign gradually red output by red at high imped...

Period T1 = $0.7 \times .000001 \times$

Period T2 = $0.7 \times .00001 \times$

Frequency = $\frac{1}{.007 + .175}$

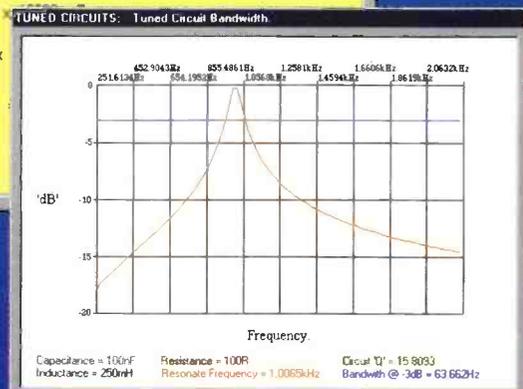

Windows 3.1, 3.11, NT, '95 & '98

EPT Educational Software. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.

Tel/Fax: 01376 514008. sales@eptsoft.demon.co.uk <http://www.eptsoft.demon.co.uk>

*UK and EC countries add £2 per order for post & packing. VAT should be added to the total.

Outside Europe £3.50 for air mail postage by return.

Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date.

Cheques & Postal Orders should be made payable to EPT Educational software.

Contents

Volume 27 No.9

Next Issue
11th September 1998

& Features & Projects




The Fingers That No-One Forgets 10

Fingerprints are a familiar means of identification, but they are not very easy to identify automatically. Neural networking and several new hardware developments are all part of this fast-developing security technology.

Getting MORE out of PICs (Part 4): The I2C Bus 20

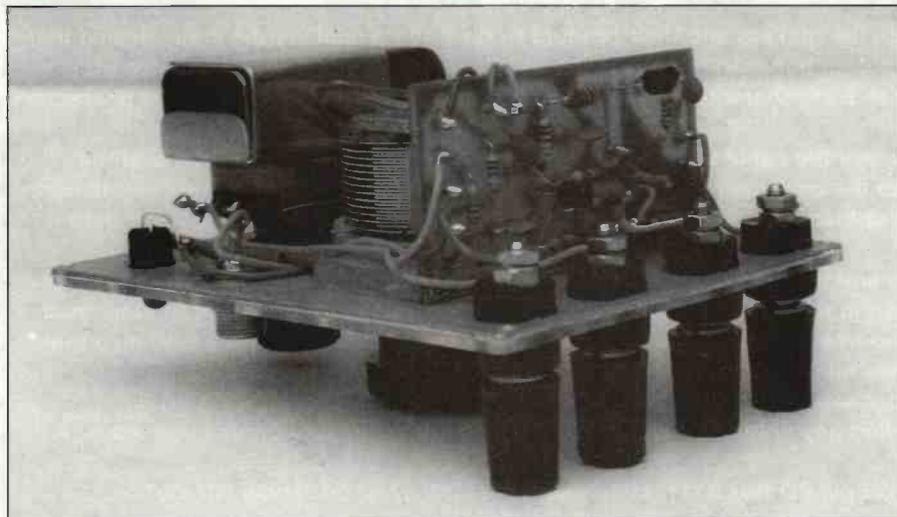The Phillips/Signetics I2C bus standard is now used by around 1,000 ics to send data by clock and data signal rather than via a 16-bit data bus. In the first of two articles, Robin Abbott describes how to drive the I2C bus from a PIC.



DIY PC - Part 3: The BIOS and the Hard Disks 26

The main cause of problems with a newly constructed or upgraded computer is completing the set-up and getting the operating system installed. Robert Penfold looks at some teething problems, and how to cure them without feeling like a dummy.

Recruitment Today, or 'Which Engineer'? 34

ETI visits the Engineering Recruitment Show and finds that employers are still looking for a sound skills base when interviewing

18-Channel Infra-red Remote Controller 38

Pei An describes a general purpose infra-red remote receiver which could be implemented in equipment where remote control is needed. Its partner is a handset transmitter using the BL9148/BL9150 chipset.

A 'Q' Meter Adapter 47

Raymond Haigh's adapter circuit allows the Q factor and inductance of RF coils to be measured with a low-impedance output signal generator and a high-impedance electronic multimeter.

Technical Tips 52

Andrew Armstrong dips into his collection of useful design fragments, including microamp voltage regulation and temperature reduction for solenoids.



Bart's Bath Duck 56

It looks like an ordinary illuminated duck, but Bart Trepak's water safety sensor may save you from a painful scalding (or freezing) on bath night, and provide that colour coded use for a blue LED that you've always wanted to try.

Timing in Electronics (Part 3): The Long and The Short 60

Owen Bishop describes the use of divider chains to produce prolonged timing periods, with two demonstration boards: a divide-by-60 chain and a 15-minute timer are included, with programming examples for the 4018, 4541 and Basic Stamp.

Review: osziFOX Handheld Universal Storage Oscilloscope 67

This 20-MHz scope looks very much like a 'pen'-sized multimeter and has a lot of functionality in a small space

Regulars

News 4,5,6,7 **Practically Speaking** 8

Terry Balbirnie describes how to trim and mount rotary pots and rotary switches correctly.

ETI PCB Service 69

PCB foils 71

Round the Corner 74


SUBSCRIPTIONS
& BACK ISSUES HOTLINES:
01858 435344
ORDERS:
ENQUIRES:
01858 435322
Lines Open 9am - 6.30pm

Subscribe & Save

Phone the hotline and take advantage of our special offer detailed on page 33.



New TTI dual and triple bench power supplies

Feedback Instruments of Crowborough, Sussex are distributing a pair of new dual- and triple- output bench power supplies from UK manufacturer TTI. The dual EX345D and triple EX345T deliver up to 280 and 305 watts respectively.

The power supplies are designed to provide accurate high resolution controls and readouts for exact setting of voltage and current levels, with separate, simultaneous voltage and current metering on each output. Line and load regulation are designed to be consistent and precise, and to provide high grade transient response with low noise.

The EX354D dual power supply has two independent isolated outputs with 0-35V and 0-4A capability. The outputs operate in constant voltage or constant current mode with automatic crossover and mode indication. Where higher voltages or currents are required, the outputs can be wired either in series or in parallel to provide voltages up to 70V or currents up to 8A.

The EX354T has an additional "logic voltage" output with a 5A current capability. This output can be selected to 5V or 3.3V via a front panel switch and delivers an accuracy of +/- 2 percent.

The EX354D retails at around £354 and the EX354T at around £399 list price.

For more information contact Feedback Instruments, Park Road, Crowborough, E. Sussex TN6 2QR, UK. Tel 01892 653322 Fax 01892 663719.

BAEC Offers to Members

The British Amateur Electronics Club is offering its members help with PCB manufacture and components.

The long-standing BAEC always welcomes new members.

For information contact the Secretary, Mr. J F Davies, 70 Ash Road, Cuddington, Northwich, Cheshire SW8 2PB. Email john@fdavies.u-net.com



Micro-Monitor sits quietly in your keyboard cable

Micro-Spy is the name adopted by both the makers and their product to describe a mini cryptic cable device that plugs into Pentium or PC/AT X86 computers between the keyboard and the computer and records keyboard strokes. The Micro-Spy can record up to 2500 characters keyed in and then loops, leaving the last 2500 characters in place when it is read.

To retrieve the information, simply carry the cable with its built-in data collector away to your PC, load the accompanying Windows 95 software to the computer and connect up the Upload unit via one of the comms ports. The data collection unit plugs into the upload unit. Selecting Upload Data will display the contents of the data collector.

Between devices like the Micro Spy and the increasing monitoring of email and Internet use by company employees, this may be the time to bear in mind that the office computer is definitely not the place to store your personal secrets or indulge in frank and free discussions about your colleagues on company time (and also that removing data without authorisation has much the same legal standing as removing any other kind of documentary information without authorisation.

And talk to your data-doctor if you find any unfamiliar-looking lumps and bumps in your connecting leads. A complete kit is available at £195.


For more information, contact Micro-Spy, PO Box 3111, Milton Keynes, MK6 3ZH. Tel. 01908 607-007.

Smallest speech synthesis LSI chip aims to put the sound back in appliances

OKI Semiconductor have developed the MSM9831, one of the industry's smallest single-chip speech synth LSIs, for applications including voice guidance systems, vehicle navigation systems and mechanical sound effects for digital appliances. With the increasing move from mainly mechanical to mainly digital equipment in everyday life, some "response sounds" expected by users are now being replaced by synthesised sounds.

A non-linear 8-bit PCM algorithm allows the MSM9831 to produce equivalent sound quality to a 10-bit straight PCM. The available sampling frequencies range from 4kHz to 16kHz, and voice quality and playback time to suit the application can be chosen by manufacturers. The MSM9831 provides up to 11 seconds playback time at 4kHz with up to 31 playback channels.

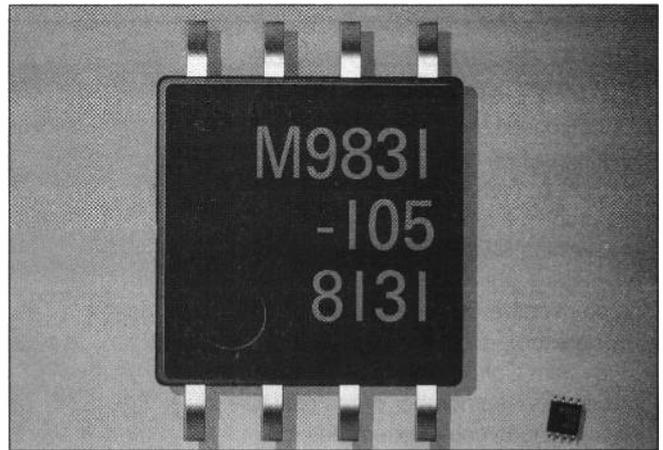By using a special serial interface configuration, the normal number of pins has been halved, so that the device is small enough to fit into many portable appliances such as digital cameras, PDAs and portable CD players. The 8-pin SOP



(small outline package) is 6.8 x 5mm and holds a 10-bit DAC, a low-pass filter and 384 kbits of Mask rom. The power supply ranges from 2 to 5.5 volts, offering different voltage availability for different applications.

For further information contact Roger Bailey, Oki Europe, Shaftsbury Court, 18 Chalvey Park, Slough, Berks SK1 2HT. Tel 01753 516577 Fax 02735 517195.

The three best suggestions for a helpful (or not ?) "response sound" that might to be built into an everyday piece of household or workshop equipment each get a freebie from our Book Box. Suggestions must be printable. Computers don't count - they say quite enough already.

1998 Radio Spectrum Strategy Document released

The Radiocommunications Agency released the 1998 edition of the document Strategy for the future use of the Radio Spectrum in the UK in July.

The document provides the latest update to the consideration of how the radio spectrum between 9kHz and 105GHz will be managed into the 21st century. It currently takes account of the passing of the new Wireless Telegraphy Act 1998, the establishment of the UK Spectrum Strategy Committee and the 1997 World Radio Conference. The document also discussed the outcome from a series of demand studies. Minister for Small Firms Barbara Roche was quoted as saying in the foreword that "Radio contributes 1.8 percent of GDP and is creating 1000 new jobs a week; therefore a coherent and dynamic strategy towards managing the radio spectrum is virtually important." Given time, it could become vitally important. The fourth edition of the document follows on from recent issues facing users



such as the introduction of UMTS, digital broadcasting and spectrum pricing. The document is intended to continue a dialogue with users, so it is vital that radio spectrum users make their needs known to the DTI.

Agency publications including the Strategy document are available from The Information and Library Service, Radiocommunications Agency, New Kings Beam House, 22 Upper Ground, London SE1 9SA, UK. Tel. The Agency's Telephone Enquiry Point Service 0171 211 0211 8.30am to 5.30pm Monday to Friday. Fax 0171 211 0507 Web www.open.gov.uk/radiocom

Cable assemblies reduce EMI/RFI emissions


As CE regulations introduced in 1996 relating to EMI and RFI emissions are becoming more strictly enforced, one of the problems facing designers is maintaining MEI/RFI suppression when cables are attached, as the cable acts as an effective aerial to radiate interference.

System Connections (Cambridge) Ltd. is one of a number of manufacturers specialising in cable assemblies for telecoms and data communications who are combating this problem with fully shielded cable sets.

Their Telco range uses specialised shielded cables, metal or metallised connector hoods and specific assembly techniques to exceed current emission regulations.



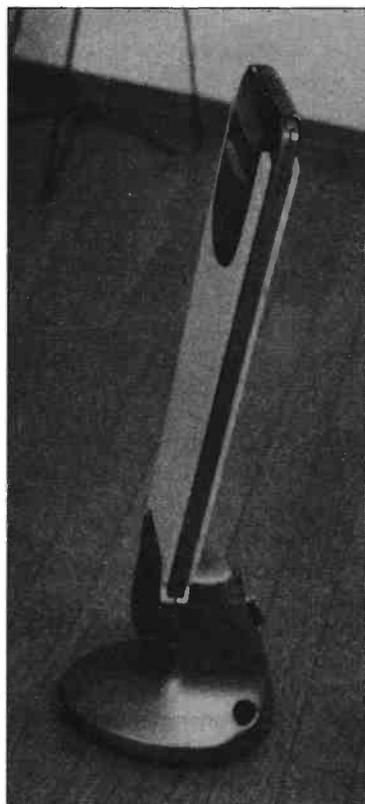For further information contact Stephen Smith at System Connectors (Cambridge) Ltd. Tel 01223 860041 Fax 01223 863625.



NEC announces the world's first application of NXT flat panel technology

The world's first NXT flat panel technology loudspeakers have been launched by NEC Home Electronics in Japan in July.

The Euromint IS-101 'CD audio system' is based on the flat panel speak technology developed by New Transducers (NXT), Cambridge, UK, which allows the entire panel to vibrate and emit sound through 360 degrees around the panel with high clarity and without the need for a conventional speaker enclosure.

The NEC loudspeaker also provides "unprecedented wide 3-D sound" using SRS/Focus technology in combination - another first on the market - to give high specification horizontal and vertical sound reproduction characteristics.

The Euromint configuration is made up of a conventional 8-cm woofer installed in the pedestal combined with an NXT flat-panel mid-range unit and two NXT flat panel tweeters.

The whole unit includes a CD player and FM tuner in the top of the casing, and being a slimline 47 mm at the top and only weighing 4.2kg is easily movable (within the limits of its cable) for personal listening. Listeners who require stereo from the woofers would have to use two units on the line-in function from an outside, but the NXT flat panels in the upper and mid range give "surround" sound and the Euromint is designed to be used alone. Each speaker has an independent amplifier to maximise its performance.

The unit can be operated via a remote control unit and includes a nightlight and sleep/alarm timer function.

The Euromint is currently only available in Japan at a price of 59k Yen (about £300) but NEC hope that it will be available in Europe at the beginning of 1999 at a roughly comparable price.

For more information contact Monica Conway, NEC Europe Ltd. Tel 0171 353 4383 Fax 0171 353 4384 email monica.conway@uk.necEUR.com

OVERSEAS READERS

To call UK telephone numbers, replace the initial 0 with your local overseas access code plus the digits 44.

High functionality system-on-a-chip from Atmel MegaAVR

Atmel has announced its MegaAVRTM family of 8-bit system-on-a-chip microcontroller family for complex embedded control applications. The Atmega103 is the world's first 8-bit microcontroller to offer 1 Mbit (128KB) of in-system programmable Flash memory, 4 KB of in-system programmable eeprom data memory, 4 Kbytes of SRAM, a true 10-bit, 8-channel A/D converter, a full duplex uart, a watchdog timer, a real time clock with separate oscillator and three timer/counter4s with separate prescaler, packaged in a 64-pin TQFP package. The package allows 48 user programmable inputs/outputs.

The MegaAVR is a two-address machine with a two-stage pipeline and 32 8-bit working registers that provides single clock instruction execution for most instructions, which equates to 1 MIPS per megahertz. The MegaAVR's 120 instructions are optimised for every efficient assembly and C-language code density, exceeding that of most other 8-bit and 16-bit microcontrollers.


Devices such as analogue cellular phones, paper currency validators and electronic cameras are making dramatic demands in terms of instruction throughput, low power and a small footprint. These applications used to required a 16-bit microcontroller. With the MegaAVR family they can use an 8-bit processor at lower cost. Another significant advantage for updating in the field is the ability of update the application code simply and easily due to the Flash program memory.

Also out now, the MegalCE is a full featured real-time in-circuit emulator for the MegaAVR family of Flash-based microcontrollers.

MegalCE is optimised to offer real time emulation, supporting Flash memory densities up to 128KB, plus 4K of eeprom and up to 64KB of SRAM. Providing access to all the I/O pins, it emulates any MegaAVR peripheral set including full duplex uarts, timer/counters, real time clocks and the MegaAVR's 10-bit, 9-channel A/D converter. It allows an unlimited number of break points, including breaks triggered by external events such as an oscilloscope or logic analyser. It can also trigger external devices so that events can be captured and analysed. Single-step execution and an extensive trace buffer allow designers to identify the exact instruction or C statement that triggers a particular event.

The emulator is available from any Atmel distributor. AVR Studio is included with MegalCE and is available as freeware from the Atmel website www.atmel.com

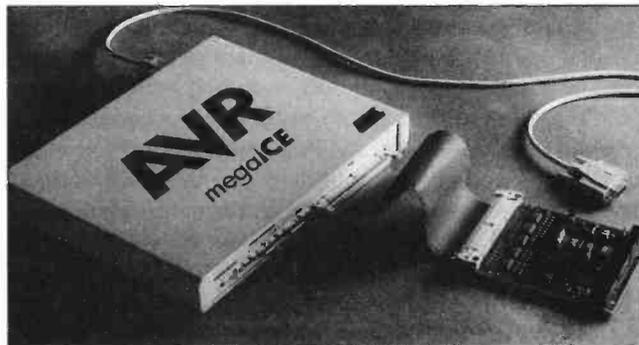For more information please contact Bob Henderson, Atmel UK, Riverside Way, Camberley, Surrey GU15 3YL. Tel 01276 686677 Fax 01276 686697.



Keep track of your Internet travels with a monitor-top timer

An established product with a useful look about it here: if you have ever wondered how much time you (or members of your family) are spending web-browsing each month, Oregon Scientific have produced a neat clock/timer to help keep track. Home use of the Internet is the fastest-expanding area of web use and now accounts for over 25% of all access, most of it, you might think, by your teenage son or daughter.

The Internet Timer is a neat package that fits on top of the PC and uses a flexible set of time memories to allow you to follow either the count-up or count-down running time, and the total elapsed time simultaneously. You can therefore run an accumulating memory for elapsed timer intervals, add time



to the memory for particular sessions, and so on.

The Timer has a large 69 x 19-mm LCD for easy reading and can stand freely on the desk or seated on top of any standard monitor using a "hook and loop" tape supplied.

The Oregon Scientific Internet Timer costs typically from £9.99 to £12.99 from leading electrical stores. It comes with a 1.5V battery, and the readout shows up to 99 hours and 59 minutes. "After which," say the makers tactfully, "even the most dedicated Internet surfer should perhaps consider taking a break." If you use more than that, you can either afford a whole team of timers, or you are likely to be receiving a stiff letter from your Bank manager sooner or later.

For more information, contact Andrew Dickson, Oregon Scientific tel 01628 826688 fax 01628 8236469 email admin@lha-pr.demon.co.uk

PRACTICALLY SPEAKING


TERRY BALBIRNIE

This month we shall look at a few practical points about the use of panel-mounted potentiometers and rotary switches. For these purposes, any of my comments about a potentiometer applies equally well to a switch.

On the panel

When you are mounting a potentiometer, you must first cut the spindle to the right length for your control knob. The bottom of the knob should end up close to the panel. Spindles are always supplied much longer than you need in practice (rather like those jeans you used to get in the 1980s). Take care, however, not to cut off too much, or the grub screw in the knob will have nothing to tighten against and will not be secure. To cut the spindle, grip the end (the spindle, that is, not the potentiometer itself) in a small vice and support the body with one hand. Cut the spindle to the required length using a sharp hacksaw.

When you have drilled the hole in the panel, you may find that the potentiometer body does not locate correctly because there is a small plastic protrusion or metal tag (the "locating lug") on it. Many people simply cut this off, not knowing why it was there in the first place. However, it is much better to drill a small hole for it to pass through (see the photograph). The locating lug will then prevent

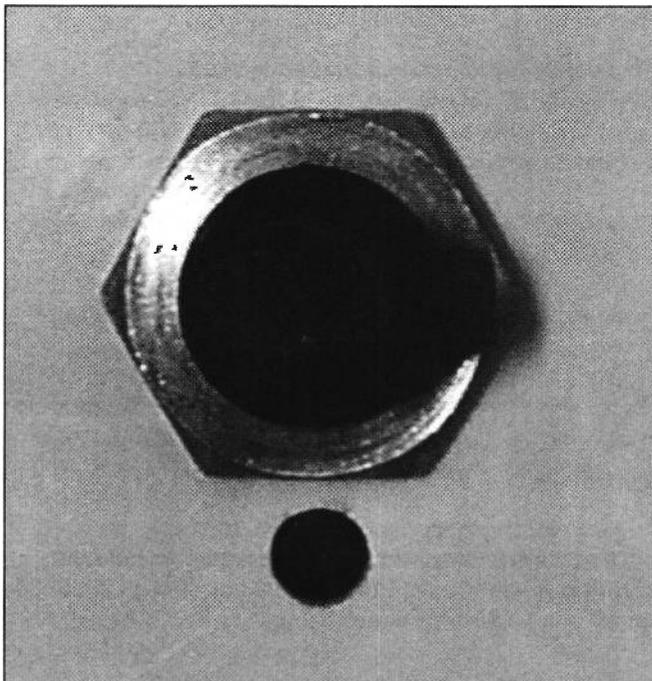

the potentiometer from rotating in use if the fixing nut worked loose and the control knob was turned hard to its limit (as happens all too easily). The whole body would then turn, and this could even result in the connecting wires breaking off. Unsecured pots work loose quite easily, and it really spoils the look and feel of a construction to have a "free floating" pot on the front panel.

Anti-rotation

Potentiometers soldered directly to a PCB and then panel mounted do not need a locating lug because the construction prevents them from rotating. However, PCB-type potentiometers are often used for free panel mounting, and it is then essential to tighten the fixing nut securely and use the serrated washer supplied with it as a precaution against loosening.

Potentiometers are made in a range of spindle diameters. Most types available to the amateur have a 6mm diameter. This is suitable for the vast majority of control knobs. Although most knobs are secured with a grub screw, some up-market ones are held in place with collets. The best type of control knob has a recess on the underside to conceal the fixing nut. However, many of the types used in miniature circuits are too small to have this recess.

Fewer positions

Sometimes a project design specifies a single-pole rotary switch requiring, say, eight positions. When you look in the suppliers' catalogues, you find the switch is shown as having twelve positions. Some people just use it like that so that four of the positions do nothing. However, usually switches of this type can be adjusted to give any number of positions up to the specified maximum and it is obviously better to do this properly.

First, remove the fixing nut to reveal the metal washer. If the spindle end of the body is tapped on the table, the washer will probably fall out. If it is too tight, you will need to lever it out gently with a small blade. The washer has a small tab on the underside. Also, if you look at the place where the washer used to be, you will see a ring of holes. The tab may be placed in any one of them. The holes are usually numbered (although you may need a magnifying glass to see it). By using the appropriate hole, the switch will provide the required number of positions. You must turn the spindle fully anticlockwise before engaging the tab.

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television sets. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full software control via a simple 2 wire link to any IBM type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**

FLOPPY DISK DRIVES 2 1/2" - 14"

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are **BRAND NEW** or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call for over 2000 untested drives for spares or repair.

- 1 1/2" Panasonic JU363/4 720K or equivalent RFE £24.95(B)
- 1 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 1 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 1 1/2" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE £18.95(B)
- 1 1/2" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 1 1/2" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- 1 1/2" Table top case with integral PSU for HH 5 1/4" Flopp or HD £29.95(B)
- 1" Shugart 800/801 B SS refurbished & tested £210.00(E)
- 1" Shugart 810 B SS HH Brand New £195.00(E)
- 1" Shugart 851 B double sided refurbished & tested £260.00(E)
- 1" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 1" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES

- 1 1/2" TOSHIBA (19 mm H) MK2101MAN 2.16 Gb. New £199.00
 - 1 1/2" TOSH. (12.5 mm H) MK1002MAV 1.1 Gb laptop. New £115.00
 - 1 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £12.95
 - 1 1/2" FUJII FK-309-26 20mb MFM I/F RFE £59.95
 - 1 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
 - 1 1/2" CONNER CP3044 40mb IDE I/F (or equiv.) RFE £69.00
 - 1 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn) £69.00
 - 1 1/2" QUANTUM 40S Prodrive 42mb SCSI I/F, New RFE £49.00
 - 1 1/2" WESTERN DIGITAL 850mb IDE I/F New £185.00
 - 1 1/2" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
 - 1 1/2" SEAGATE ST-238R 30 mb RLL I/F Refurb £69.95
 - 1 1/2" CDC 94205-51 40mb HH MFM I/F RFE tested £69.95
 - 1 1/2" HP 97548 850 Mb SCSI RFE tested £99.00
 - 1 1/2" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 1 1/2" NEC D2246 85 Mb SMD interface. New £199.00
 - 1 1/2" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00
 - 1 1/2" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (D)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- ITS FA3445ETKL 14" Industrial spec SVGA monitors kW to 400 kW - 400 Hz 3 phase power sources - ex stock £245
- BM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- BM 53F5501 Token Ring ICS 20 port lobe modules £750
- 3M MAU Token ring distribution panel 8228-23-5050N £95
- UM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- LLGON 8360, 11805-1880 MHz hybrid power combiners £250
- rend DSA 274 Data Analyser with G703(2M) 64 Vc £600
- farconi 8310 Programmable 2 to 22 GHz sweep generator £2650
- farconi 2022 10KHz-1GHz RF signal generator £1550
- farconi 2030 opt 03 10KHz-1.3 GHz signal generator, New £1550
- IP1650B Logic Analyser £3750
- IP3781A Pattern generator & HP3782A Error Detector £POA
- IP621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- IP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- IP54121A DC to 22 GHz four channel test set £POA
- IP130A opt 020 300 MHz pulse generator, GPIB etc £8500
- IP A1, A0 8 pen HPGL high speed drum plotters - from £950
- G+G Brookdeal 95035C Precision lock in amp £650
- low Eng. Mod 1200 computerised inspection system any DMC-3000A High quality CCD colour TV camera £1100
- caltech 590 CV capacitor / voltage analyser £POA
- lithel ICR40 dual 40 channel voice recorder system £3750
- lakers 45KVA 3 ph On Line UPS - New batteries £9500
- 1 R5030UV4 Cleanline ultrasonic cleaning system £9500
- linal Tally MTF64 High speed line printer £2200
- tel SBC 486/133SE Multibus 486 system, 8Mb Ram £945
- lemans K4400 64Kb to 140Mb demux analyser £2950

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL OR SEE OUR WEBSITE

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -

At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCELLENT little used condition.

Tilt & Swivel Base £475
VGA cable for IBM PC included.
Only £119 (E) Order as MITS-SVGA
External cables for other types of computers CALL.

As New - Ex Demo

17" 0.28 Mitsu Mitsubishi Diamond Pro monitors Full multisync etc. Full 90 day guarantee. £325.00 (E)

Just in - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed fan controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 1/2" x 15 1/2" D.
Only £99 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 1 3/4" D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 1 1/2". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PII all solid state colour monitors, complete with composite video & optional sound input. Attractive test style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"£135 22"£155 26"£185 (F)


DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call or see our web site.

LOW COST PC'S

Always over 1000 PC's from stock. 1000's of spares and accessories. Call or see our web site for info.

- Intel SBC 486/125C08 Enhanced Multibus (MSA) NEW £1450
- Zeta 3220-05 A0 4 pen HPGL fast drum plotters £1150
- Nikon HF-X11 (Ephiphot) exposure control unit £1450
- Motorola VME Bus Boards & Components List. SAE / CALL £POA
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM band printer £1950
- Fujitsu M3041D 600 LPM printer with network interface £1250
- Perkin Elmer 299B Infrared spectrophotometer A £500
- Perkin Elmer 597 Infrared spectrophotometer £3500
- VG Electronics 1035 TELETEXT Decoding Margin Meter £3750
- LightBand 60 output high spec 2u rack mount Video VDA's £495
- Sekonik SD 150H 18 channel digital Hybrid card recorder £1995
- Taylor Hobson Talysurf amplifier / recorder £750
- ADC SB200 Carbon dioxide gas detector / monitor £1450
- System Video 1152 PAL waveform monitor £485
- ANRITSU 9854A Optical DC-2.5Gb/b waveform monitor £5,650
- ANRITSU MS9001B1 0.6-1.7 um optical spectrum analyser £POA
- ANRITSU ML93A optical power meter £990
- ANRITSU Fibre optic characteristc test set £POA
- VISION ENGINEERING TS3 Dynascopic microscope £1850
- R&S FTDZ Dual sound modulator £650
- R&S SBUFE-1 Vision modulator £775
- WILLTRON 8630B 12.4 / 20GHz RF sweep generator £5750
- TEK 2445 150 MHz 4 trace oscilloscope £1250
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1955
- TEK 1502 Portador TDR (time domain reflectometer) £600
- PHILIPS PW1730/10 66KV XRAY generator & accessories £POA
- CLAUDE LYONS 12A 240V single phase auto. volt. regs £325
- CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs £2900

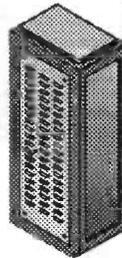

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable fixing side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels. £345.00 (G)
OPT Rack 2 Rack. Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm-1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)
Sold at LESS than a third of makers price !!



A superb buy at only £245.00 (G)
42U version of the above only £345 - CALL

BATTERY SCOOP - 50% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. MB bolt terminals. Fully guaranteed. Current makers price over £70 each!
Our Price £35 each (C) or 4 for £99 (D)

RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive stocks covering types such as - Military, Octal, Cradle, Hermetically Sealed, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting, CALL US WITH YOUR NEEDS. Many obsolete types from stock. Save ££££'s

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.
Order as: XT RAM UG. 256k. £34.95 or 512k £39.95

- SIMM SPECIALS**
- 1 MB x 9 SIMM 9 chip 120ns Only £8.50
 - 1 MB x 9 SIMM 3 chip 80 ns £10.50 or 70ns £11.95
 - 1 MB x 9 SIMM 9 chip 80 ns £10.50 or 70ns £11.75
 - 4 MB 70 ns 72 pin SIMM -with parity- Only £35.00
 - INTEL 486-DX33 CPU £19.95 INTEL 486-DX66 CPU £59.00
- FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR £££
- MOTOROLA 25 Mhz 68040 (XC68040RC25M) CPU'S £59.00 shipping charges for RAM / CPU upgrades is code B

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged.
Special Price ONLY £99.00
Microsoft - Windows for Workgroups 3.11 & DOS 6.22. Supplied on 3 1/2" disks with licence & concise documentation. £39.95
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
shipping charges for software is code B

DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk



ALL MAIL & OFFICES
Open Mon - Fri 9.00 - 5:30
Dept ET, 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9:00 - 5:30
215 Whitehorse Lane
South Norwood
On 88A Bus Route
N. Thornton Heath & Selhurst Park SR Rail Stations

NEW DISTEL
Visit our web site
www.distel.co.uk
email admin@distel.co.uk

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to Total order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change price / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1998. E & O.E. 06/98

The Fingers That No-One Forgets

Fingerprints have long been part of police investigations, but demand for personal and commercial security has spurred a rush of development on fingerprint readers for everyday use in buildings, computers and even portable phones.

Of all "biometric identifiers", fingerprints are still the most famous. Tracing fingerprints has been synonymous with police work since Sir Edward Henry implemented them for criminal identification in India in the late 19th century, and later in the United Kingdom. Every fingerprint is different (the only exception is the fingerprints of identical twins). Fingerprints are fairly difficult to forge, and very rarely forgotten or left behind. They also have legal status as reliable evidence of identity, unlike some personal markers such as digital signatures.

In the last few years fingerprints could be stored as computer data by scanning an existing fingerprint (or the finger itself, known as live scanning) with an optical reader coupled to a digitiser to provide a digital file that pattern-recognition software could analyse and store.

Glass optics limited the extent to which readers could be miniaturised (and installed), but recent advances in semiconductor fabrication and pattern recognition software mean that fingerprints can be read by solid-state imaging ics other than the CCDs already in use. Some of these sensors can be made small enough to build into computer keyboards and other personal possessions such as mobile phones. They are likely to become a widespread means of secure ID in the very near future, particularly in fighting mobile phone fraud.

Capacitance

Since 1995, a team of scientists at the Bell Laboratories, part of US telecommunications giant Lucent Technologies, have been developing the FPS100 and FPS100A imaging chips

with reading surfaces made up of a dense matrix of tiny capacitive plates. The array of sensors measures the capacitance generated between the surface of the chip and the surface of a finger. The ridges of the fingerprint contact the surface directly, but the "valleys" of the pattern remain clear of it. The software monitors the discharge times of the capacitance readings and converts these to a signal. The signal is processed into a greyscale image. This image is then analysed to provide the data which is stored for pattern recognition.

A significant security aspect of the method of analysis normally used is that the fingerprint pattern itself cannot be reconstructed from the data file. The data file holds only certain information, based on a selection of fingerprint features, to be compared with the original enrolment file and verify that the same finger is involved.

The Lucent system marketed by Veridicom of Santa Clara, California, has four main components:


- * a silicon sensor to measure the ridges and valleys of the finger pressed against the chip
- * analysis software that reconstructs the fingerprint in digital form and searches for the unique features (minutiae) that identify an individual fingerprint
- * matching software that uses special algorithms to match the input fingerprint to the "enrolment" sample previously stored for the user
- * data protection software that protects the fingerprint files from unauthorised copying or tampering




When a finger is placed on the chip's surface, the sensor array creates an 8-bit raster-scanned image of the ridges and valleys of the fingerprint.



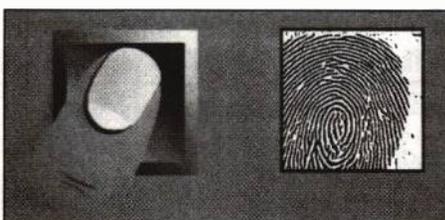During image capture, automatic on-chip adjustments to sensitivity and gain control are made to obtain the best image. Integrated temperature and resistance sensors make it very difficult to fool the sensor



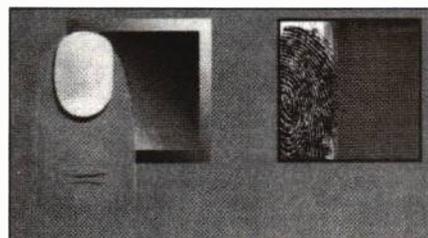
The image presented to the sensor is captured. An on-board 8-bit ADC digitises the array output which is converted to a grayscale image



The quality of the image is analysed. Error codes flag problems like incorrect image position, no finger present or fingers that are too wet or too dry



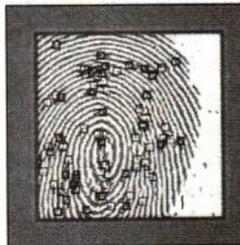The captured greyscale image is enhanced to reduce noise and enhance ridges. Then it is converted to binary form



The minutia (ridge endings and bifurcations) of the fingerprint are identified. A set of minutia unique to that fingerprint is extracted and stored as a minutia template of that individual


Finger plate

Lucent's capacitive imaging chip has around 90,000 (300 x 300) sensor pixels printed as the top metal layer of a CMOS chip with a surface roughly the size of a postage stamp, and covered with a thin layer of dielectric. When a finger touches the top of the chip, each sensor acts as the bottom plate of a capacitor, with the finger as the top plate. The chip has its own earth wires to discharge static carried by users (who are unlikely to remember to ground themselves each time they want to use the ID reader).

The company has also developed a coating for the reading surface combining titanium nitride and silicon nitride. The silicon acts as the dielectric, and the titanium gives the surface its hardness. This coating is many times harder than glass, and protects the chip from the wear and tear of daily use, moisture and airborne chemicals, and contact with acidic skin oils. The surface is highly resistant to scratching and abrasion, and is tough enough for industrial and commercial applications like ATMs.

When touched, the sensor array creates an 8-bit raster-scanned image (500 dpi) of the ridges and valleys of the fingerprint, and in the FPS100 ic an on-board ADC digitises the output. There is an 8-bit interface bus compatible with most microprocessors. There are also resistance and temperature sensors integrated that make it difficult to fool the system with, for instance, artificial fingerprints (see below). The stored file is a 300-byte data file of the fingerprint.

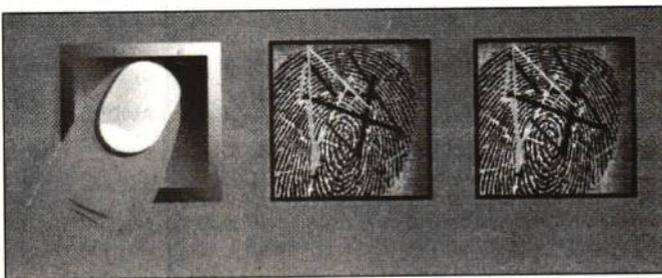The matching software is designed to amplify the signal differences between the ridges and valleys of the print.



A live reading from a finger placed on the sensor is compared to the minutia data template stored for that person. If the data match, the individual's identity is verified. If the data do not match, the attempt is rejected.

Minutiae

Fingerprint features are divided into two types: the patterns, such as whorls, arches and loops, that are formed by the collective paths of the ridges, and the minutiae, which are the ridge bifurcations, endpoints and other localised features. These are the "corners" seen on fingerprint patterns under a magnifying glass among the repetitive ridge patterns. It is the exact positions of these minutiae that provide the most easily analysable and distinctive differences. The pattern analysis software homes in on them.

Using silicon technology also allows extra functions to be added to the chips, such as A/D converters and on-board microprocessors, with little extra cost and no extra size. These chips are not yet crowded: there is a lot more to go on them.


The image processing and analysis software developed at Veridicom must extract the minutiae from the inherently noisy fingerprint image, which can be contaminated by dirt, uneven pressure, cuts and scars, individual skin texture and even the stretching effect of skin plasticity. It enhances the ridge features and reduces the noise to produce a binary image of ridges on a white background. The software examines the ridges to locate the minutiae, and passes that information on to the comparison software. An adaptive filter matches the pattern of ridges all over the print to give a more complete picture. This filter adjusts its passband to take account of the bandwidth of the actual signal, rejecting noise outside that range. It adapts to different signal frequencies - in this case spatial frequencies of minutiae. Many adaptive filters are, in effect, 2-D digital signal processing algorithms with a built in capability to adjust some of parameters according to the input data.

Veridicom's senior scientist Tony Russo worked on the matching code for several years. The software takes the list of minutiae information and plots the geometric relationships between their positions. Each detail, or minutia, is related to the others by distance, angle type and other features. These complex geometric relationships are compared between the input fingerprint and the database fingerprint. A match is accepted if a number of these relationships meet a specified threshold.

The matching is less exhaustive than for forensic work, as the input fingerprint is matched against a known sample - a bank customer or employee - and only the validity of that match needs to be established.

Using the sensor interface is just a matter of "press here", and the fingerprint is read. Printing the capacitive plates during silicon fabrication means that each sensor's pixel element positioning is precise, and each sensor gives identical resolution, without the risk of distortion that can arise from optical light paths. A success rate in accurate matching of greater than 99 percent has been reported.

- Fingerprints have been in use since the 19th Century
- The fingerprint data file does not normally store a whole image, and the fingerprint image cannot be reconstructed from it. As well as reducing file size, this is a useful security feature.
- Lucent's capacitive imaging chip has around 90,000 sensor pixels printed on a CMOS chip roughly the size of a postage stamp
- Each fingerprint detail, or minutia, is related to the others by distance, angle type and other features.

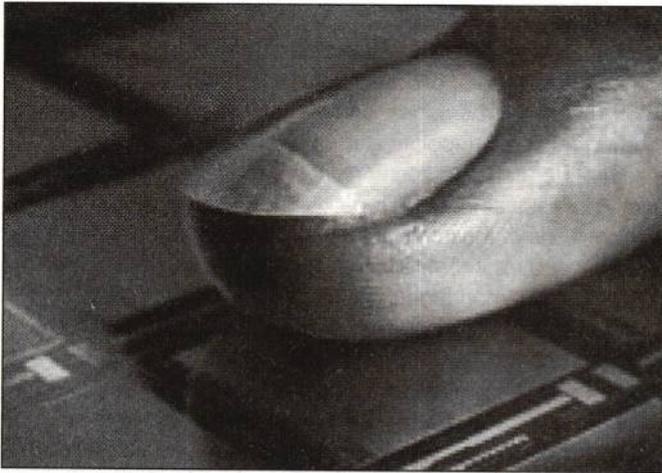

Touching a Seimens capacitive sensor

On the phone

German company Seimens Nixdorf have developed capacitive fingerprint sensor which can be manufactured for less than US\$50 (laser scanners now used in optical scanning cost around \$1000). A small, low cost sensor like this could be integrated in mobile phones or car ignition locks, and a sensor fitted in a mobile phone has already been exhibited.

The 1.7 cm² chip's surface contains over 65,000 capacitive sensor elements with the resolution of 500 dpi. The chip sends the image of the fingertip to the computer, where the minutiae are extracted, and compares 12 - 24 characteristic points with the stored original data.

Currently the software applications for the sensor are running on a Pentium, but in two years' time the company want to implement the image processing in a digital signal processor directly on the chipcard. Today the data already being digitised on the chip itself, making it possibly "the most advanced in the world as far as integration is concerned", according to Seimens.

Another advantage of fitting sensors in mobile phones - apart from user security - is itemised billing among authorised users. Used in a car ignition lock it could feasibly replace ignition keys altogether.

Following hardware applications, the plan is to mount the sensor on a smartcard to replace PIN numbers. Getting the price down "by three to five times what it is now" is one necessary goal for such a mass application.


Seimens' researchers hope to achieve this by means of a membrane sensor in which the sensor surface consists of passive sensor elements.

Thermal imaging


Thomson CSF Semiconductors Specifiques (TCS) have developed another new technique that uses an array of thermal sensors in their FingerChip(tm). The FC15A140 chip is a two dimensional array of 50um-square pyro-electric sensors with multiplex electronics and video output buffering. The array is long and narrow. To build up a complete fingerprint scan the user must draw the finger across the sensor chip while the reader takes a number of separate thermal readings. As it works fast, one pass of the finger can produce about 50 separate images, which are collated by the software into an accurate facsimile of the print.

Again, the thermal sensing is based on the fact that the skin contacts the sensor at the ridges, but not at the valleys, where it is the air (or water, etc.) in the valleys that makes contact. A damp finger couples better with a sensor surface than a dry one, giving a clearer image. At pixel level, it is the difference between the thermal conductivity of skin and air that makes the difference. The valleys do not need to be deep to create a signal.

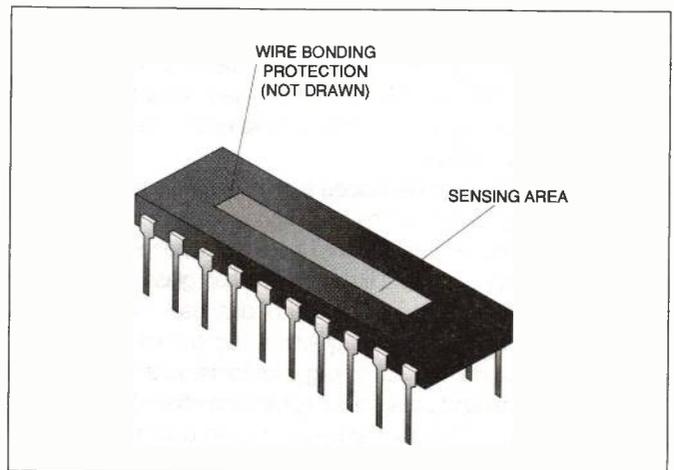
The sensing system can only work if the finger and the chip are at significantly different temperatures, but it does not matter whether the chip or the finger is warmer. If the finger is warmer than the chip,



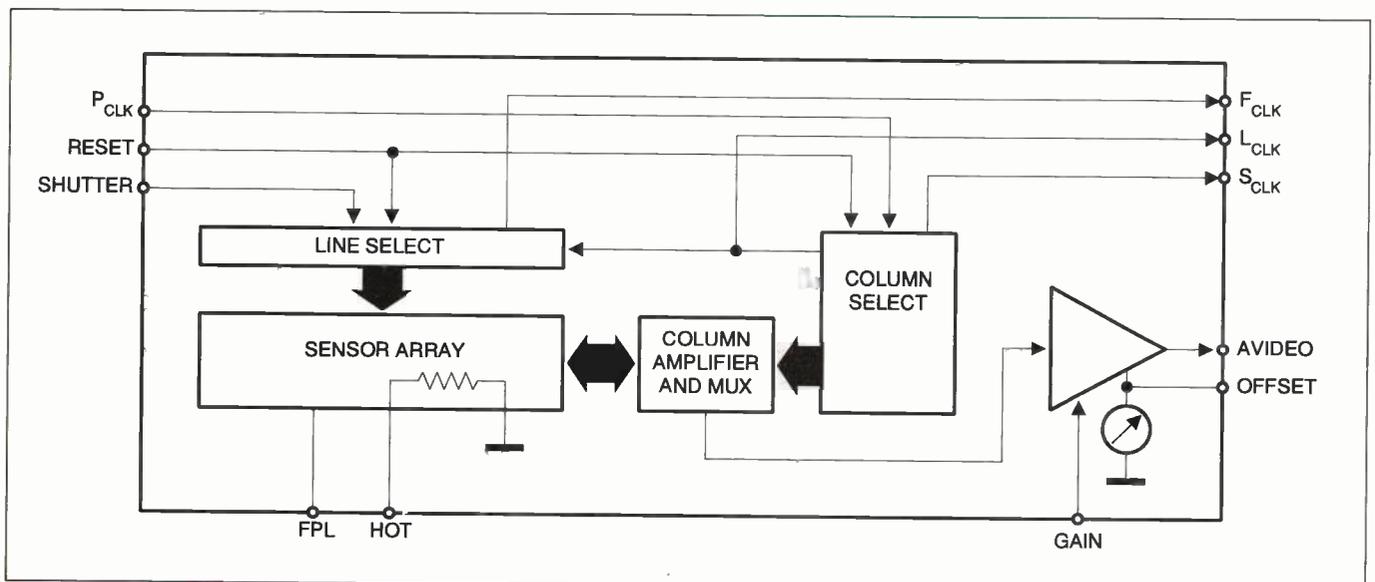The FC15A140 FingerchipTM die chip showing the sensing area



The block diagram of the FC15A140

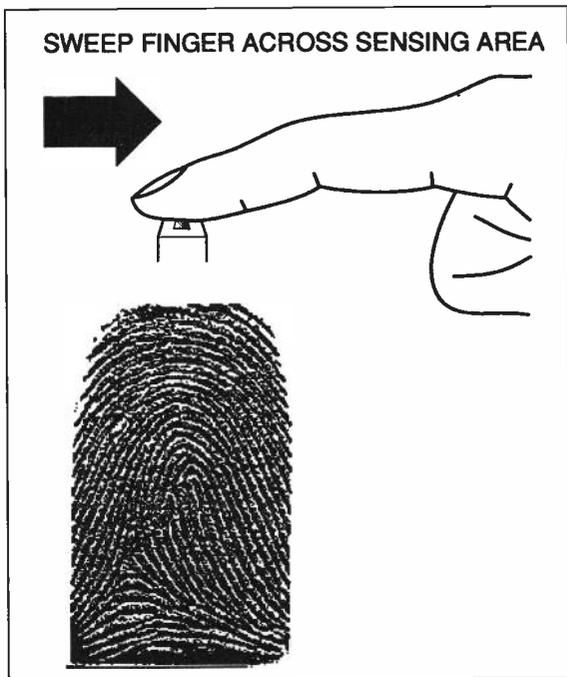

Movement of the finger across the sensing area, and the area of fingerprint imaged

then as the finger is moved over the array, the pyroelectric sensors receive extra heat in proportion to the shape of the fingerprint section over the array. They warm up, and after an integration period, dependent on the clock rate, the temperature difference between the start and end of the period is sampled. Then the current temperature is used as the new reference, and the next change in temperature is read.


Clearly, if the finger and the sensor are at the same temperature there will be no change in temperature, and therefore nothing to measure. To avoid this becoming a problem in practice, a heating element is included in the array. In a cold area this would not be used (unless it is so cold that build up of ice would otherwise occur). In a hot area, extra heat may be needed to warm the pyroelectric sensor array above the temperature of the finger. Then the finger moving across the array cools rather than warms it, so that the image is inverted. This can automatically be corrected by the verification software. The ideal is a good signal to noise ratio, and this depends on the implementation of the chip.

Data is clocked out of the array serially, with 280 rows of 30 pixels. The output signal must be converted to digital form using an analogue to digital converter, and then reconstructed using software.

There is a good reason for the array being of this apparently strange shape. If it were made large enough to cover the entire area of the fingerprint in one scan, then it would use five times as much silicon as the chosen shape uses. This would approximately multiply the cost by five. By using a moving finger, the size and cost of the sensor is kept down, while the repeat image scanning is able to provide a much larger image file than most systems if required, which makes it more suitable for 1-to-many comparisons, which require more detail than 1-to-1. As a heat difference of as little as 0.1 degree C can work under normal conditions, the moving finger also avoids the retention of heat and a build up of thermal equilibrium between the ridges and valleys and the sensor that could occur if the finger was pressed against the surface.

Another advantage of sweeping is that it tends to clear dirt off the sensor face, instead of accumulating it. Bearing in mind the tendency to "noise" in fingerprints, this is significant.

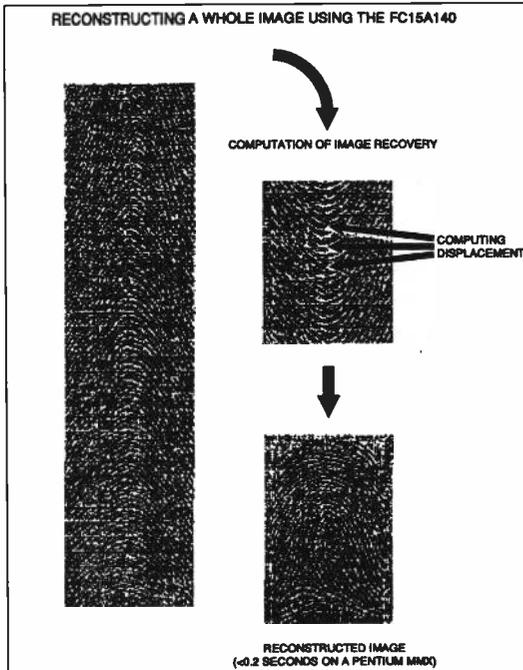On the other hand, using only a single line of pixels would not permit the image to be reconstructed in the normal case where the



Reconstructing a whole image from samples using the FC15A140

This image can then be processed by a suitable fingerprint identification algorithm.

One major advantage of a heat-based sensor is that it should be protection against the use of forged fingerprints (moulded in latex, for example) or any kind of substitute print that was not firmly attached to the owner's body.

Bureau work

Bureau work is different in some ways from individual identification for security purposes. Most fingerprint readers are taking an instant reading from the owner to compare with a single, known data file already stored. Cambridge Neurodynamics participates in fingerprint bureau work (such as that required by police forces) more than many fingerprint security businesses. @B:Neurodynamics' system is designed to provide both image and data files originating with latent prints (prints read from surfaces at the scene of a crime); tenprints (full sets taken on paper by the police or the military for their records and scanned in from the paper source), and damaged and partial prints retrieved in lieu of anything better, as well as single prints from security readers.

Fingerprints are familiar, so it is not always recognised how difficult it is to distinguish one print from another automatically. Pattern recognition is an extremely complex science. The difference between obtaining a graphics file and obtaining a matchable data file resembles the difference between scanning a letter as a graphics image, and subjecting it to optical character recognition so that it can be "read" by a word processor. The graphics file will return an image of a letter A, but cannot recognise it as a letter A, or use it as text in a database, wordprocessor or spellchecker. It is only a pattern of pixels. To utilise it, the pattern must be OCR'd and recognised as an orthographic component, a letter.

To extract the pattern data from a fingerprint so that it can be automatically compared with other fingerprints is much more difficult. First, the image is analysed for one of the five major fingerprint classifications, according to the broad pattern type on the print. This homes in on the central part of the print, where the ridges usually form a "key feature" of a major whorl or loop. A neural network algorithm determines its location on the print, so that it will

speed of the finger moving over the sensor is neither constant nor repeatable. However, rather than capturing a single line of information, a narrow strip is captured. As long as there is some overlap between scans, a complete image can be built up without errors caused by variations in speed. If there is no overlap, then more than one pass may be required to build a complete image. A system can return a reconstructed image from about 50 partial images in under a second on a 133-MHz Pentium.

afterwards only be compared with prints of the same class, greatly reducing the number of comparisons needed.

Following this, the minutiae, as described earlier in this article, are analysed. Once all these characteristics are mapped and stored, making a comparison even through a very large database becomes more straightforward.

Programming each analysis stage is a very major task in artificial intelligence, with two main goals: accuracy is very important, as lives may depend on it; and the database searches involved are far larger than the one-to-one matches needed for security applications. For instance, matching any given suspect against a single print required manipulation of a "tenprint" file, as burglars - unlike employees or banking customers - do not select a particular finger when leaving prints behind. Prints are very often partial or extremely "noisy", and the size of a database search increases exponentially as the size of the database increases.

Unlike security access software, which does not normally store graphics files of fingerprints (for security reasons as well as saving space), security record systems do store "images for humans to look at", as human input is still required in the difficult environment of investigative matching.

Neurodynamics produce a low-cost fingerprint reader using a conventional optical system of a small solid state camera and prism, but their approach, designed to work with a variety of image readers, is a prime example of the ingenuity of software.

The company also produces N.VISAGE facial identification software. Security by facial recognition normally has not always enjoyed high confidence as many systems cannot tell the difference between the owner's face and a photograph of the same face.


Systems that use advanced software to build up three-dimensional images and compensate for variables like a new beard or a change of head rotation give more secure matching

The N.VISAGE system uses infra-red to capture multiple frames from a face approaching the camera, scanning with a single beam, or with two beams set up opposite each other so that the subject walks through a "sheet" of sensing light to build up contours into a 3D image which is then used for pattern matching. As IR is invisible, the scans can be made in darkness or daylight without the subject knowing, and stored for later matching with scans taken from suspects.


Ultrasound

Another method of reading fingerprints developed in recent years uses ultrasound. The system was developed by Ultra-Scan in the USA as a response to pass-rate problems with optical scanners.

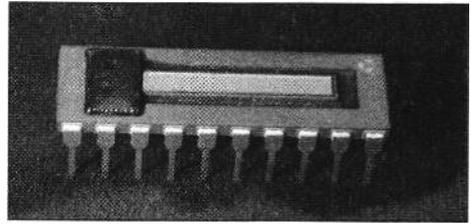
Ultrasound has the advantage over purely optical readers that the reading area does not need a frequently-replaced platen surface, and is not affected by the dirt and natural oil that tends to



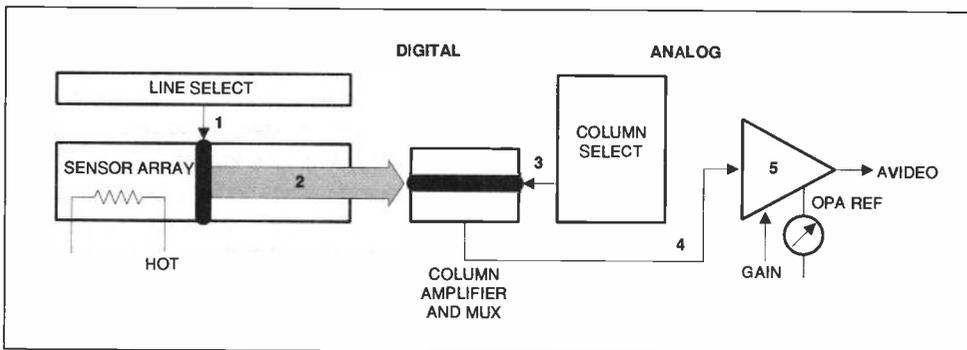
The FC15A140 Fingerchip™ with the sensor in the middle and the connections covered at the left hand end.




A functional diagram of the FC15A140

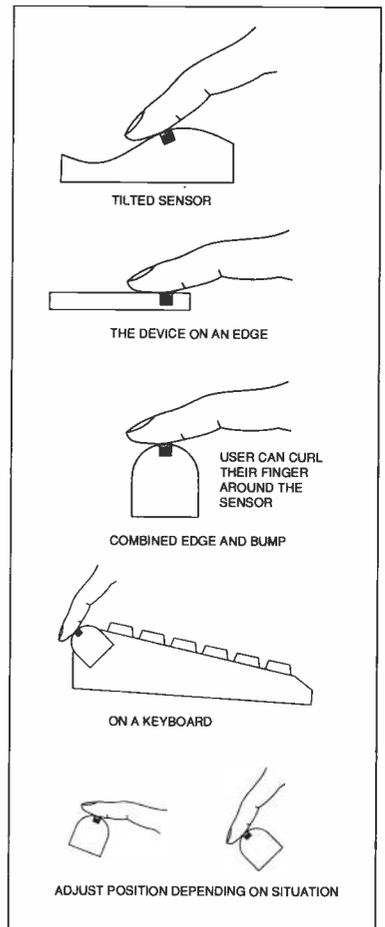

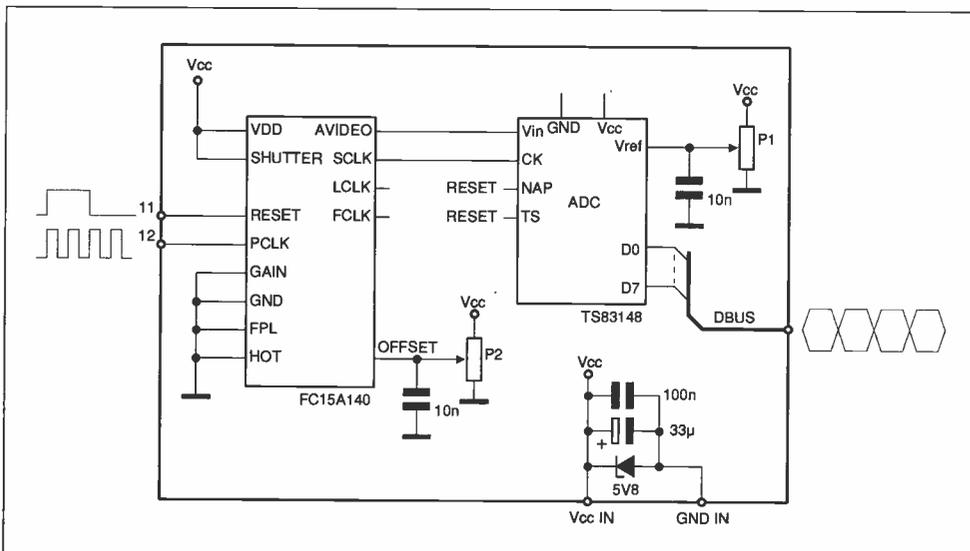Various configurations for mounting the sensor in equipment. The sensor has a very small footprint, but is not ideal for a completely flat surface



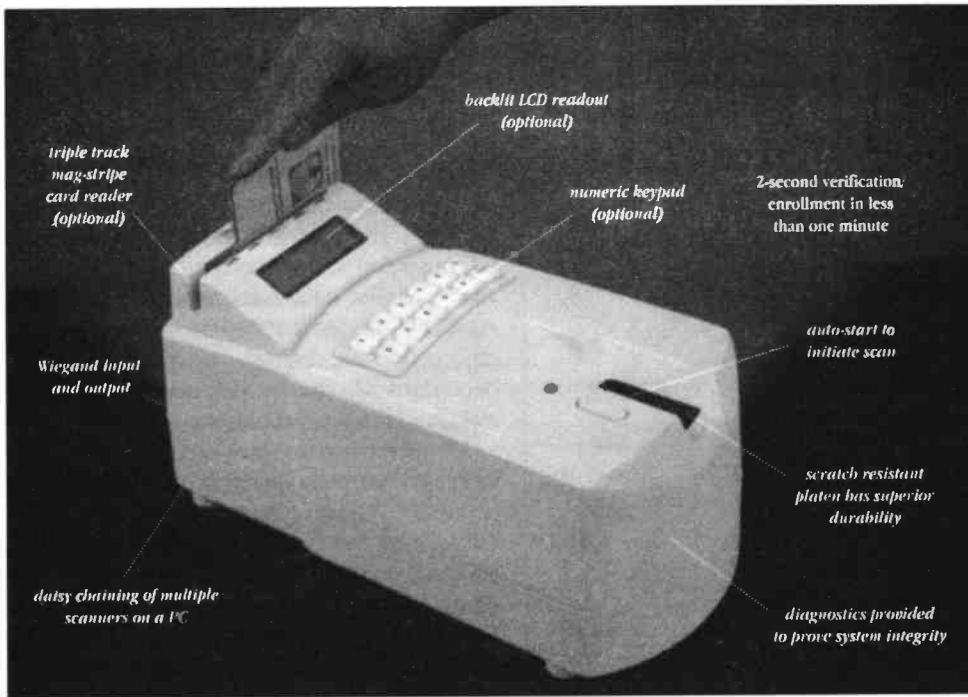A final system implementation of the FC15A140 directly connected with the ADC, and using the rule "one clock stroke, one data". Future versions will integrate to ADC on the chip



Ultra-Scan Series 700 ID Station™ with integrated finger scan, cardswipe and keypad options

accumulate even on fairly clean fingers. As the system does not rely on direct contact with the fingerprint pattern, it can also read an image through the latex gloves that must be worn by many people in Health professions. Many optical scanners use a soft surface on the reader to improve finger contact, whereas ultrasound, like capacitive and heat-sensitive readers, uses a hard-surfaced reader much less susceptible to wear.

Optical scanning also faces problems with, for example, very dry or very oily fingers, low humidity conditions and fingers with an uneven skin surface, along with the usual problems of dirt on the digit or the platen. Acoustic waves can travel through solid objects (like particles of everyday dirt) that are opaque to light.

Poor performance by optical scanners in some large-scale tests demonstrate that imperfect readings cannot simply be "fixed in software". The software may be (as programmers often tell us) the "clever bit" but it cannot entirely compensate for what is not captured accurately in an application where accuracy actually matters.

Ultrasonic acoustic energy passes through or is reflected from materials in its path, so that an image can be formed by reading the relative acoustic impedance between materials, including the solid ridges and hollow valleys of a fingerprint. When an acoustic wave meets an interface between materials of different acoustic impedance, part of the incident energy is reflected, and the rest passes through the interface. The reflections are picked up and read at a predetermined point to provide a signal which is then digitised to give the image data files. The plane surface of the platen would provide a convenient field from which to read reflections.

The fingerprint data is digitised inside the scanner and processed using a digital signal processor built into the scanner module. This means that the fingerprint image can be encrypted at the scanner before it is sent to the host computer, removing the likelihood of the fingerprint data being siphoned off or altered before it is encoded as a data file.

Ultra-Scan's hardware development and choice of software was based on experience gained working with the Identification Division of the FBI, and experiencing the shortfall in live-scanning technology available at the time (and as recently as 1996). Until the recent development of security biometrics, the matching of archived prints

has been the main requirement for fingerprint matching.

Types of scanner

The range of reader modules produced gives some idea of the basic applications in fingerprint reading: the Series 500 is a forensic scanner, providing high resolution images to meet forensic requirement for law enforcement agencies: no distortion, wide greyscale range, high contrast and 500 dpi resolution. The series 600 is a fast, ruggedised scanner for large-scale applications, able to perform identity verification in 1.7 seconds. The Series 700 'Integrated ID Scanner™' includes a card reader, keypad and LCD readout, with Wiegand input/output and RS-232 ports. The Series 700 are recommended for access control and time-and-attendance (clocking in and out). The Series 400 provides two OEM models, the 401 with the


same functions as the Series 500, and the 411 corresponding to the Series 600. An OEM version of the Series 700 is planned for later in 1998.

Two image sizes are used for scanning: the Full Scan (1.2 x 0.8 in) and the Express Scan (0.5 x 0.5 in). The scan sizes are stored in firmware and can be altered in the field for different applications. Full Scans are used chiefly for enrolment, usually with a single scan.

Series 400 scan times with default image sizes

Series 400 500 dpi	Express	Full
Scan	1.7 sec	4.6 sec
Verify or enrol	3 sec	8.1 sec
Series 400 250 dpi	Express	Full
Scan	0.8 sec	2.3 sec
Verify or Enrol	1.7 sec	4 sec

- Live print matching is less exhaustive than for forensic work, as the input fingerprint is matched against a known sample, instead of an entire database.
- Fingerprints are so familiar that it is not always recognised how difficult it is to distinguish one from another automatically.
- Dirt on the finger or the reader is one of the biggest problems for fingerprint readers, particularly optical ones.
- Without a dual images from separate cameras, or separate readings from a single camera, face recognition cameras can be triggered with a photograph.

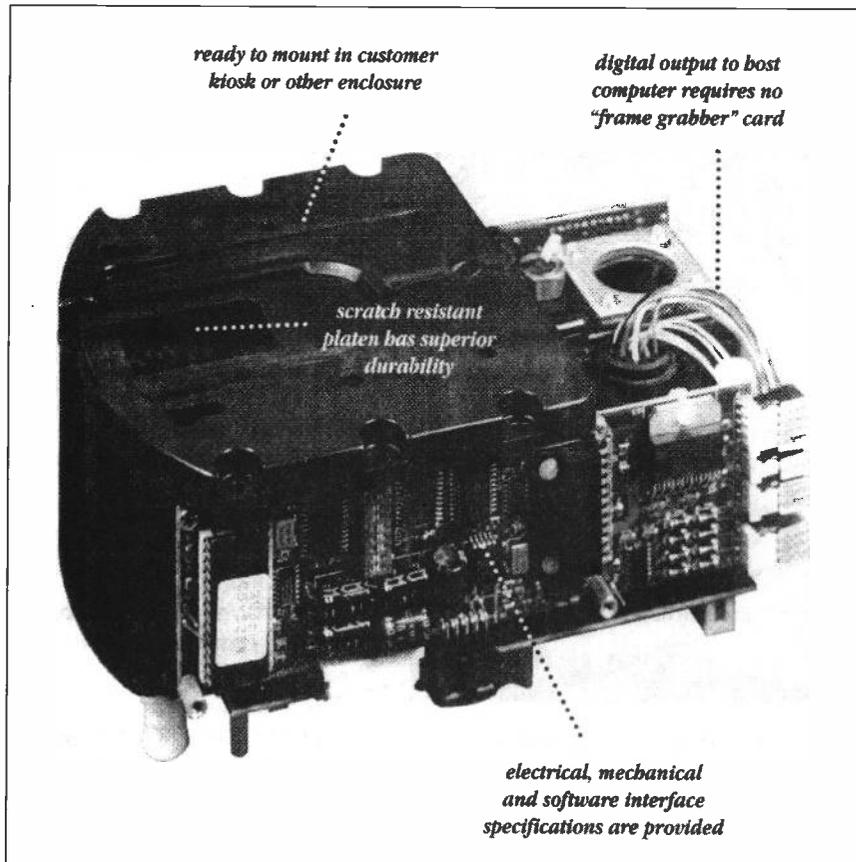

regular replacement (unlike soft coated platens) and virtually no cleaning, the reader is designed for low maintenance and a working life of more than 5 years in heavy use - good for a public interface.

Ultra-Scan do not release construction details of their ultrasound hardware, but extensive literature and support is provided to OEMs and other users on software applications and interfacing. The readers are packaged into a number of ways so that they can be built into other equipment, operate as simple plug-in units or combine with other security devices such as swipecard readers and keypads.

UltraScan have also promoted an industry-wide standard for fingerprint readers in their 1996 document *Fingerprint Reader Specifications for Single Finger Live-Scan Devices (Proposed)*. The company points out that a great many test figures on optical scanners in particular have been produced under ideal conditions - moisturised fingers and assistance with accurate placing of the finger - that do not occur in real-life scanning.

Optical tests

Tests carried out by Network Computing in the USA on six optical fingerprint readers showed that there was more difficulty getting an accurate

Images are stored (normally) as templates, containing the information about the minutiae extracted from the image, which gives a binary data TIF file of between 25 and 451 bytes. The recommended size for most analysis is 100 bytes (giving a file size of 1KB with the template). The larger the file, the more minutiae are extracted and the more rigorous the comparison possible. If the fingerprint image is to be stored, the file will be much larger, in the region of 236 KB for one finger or 470 KB for two. The minimum processor size recommended is still a 486, although faster results will be obtained with a faster processor.

Processing times using a Pentium 200 with 64MB ram

Enrollment	Scan size	Processing	Match time
Series 500/Model 401	Full	3.52 sec	0.9 sec
Series 600/700/Model 411	Full	1.77 sec	0.9 sec
Verification			
Series 500/Model 401	Express	1.29 sec	0.25 sec
Series 600/700/Model 411	Express	0.67 sec	0.25 sec

Three types of "start" settings can be used to initiate a scan: pushbutton (typically, a quick push initiates an Express scan and holding the button down initiates a Full scan); an autostart, which senses a finger placed on the platen and sends an ascii response to the host computer via the RS-232 port, and an ascii command issued via the RS-232 port by the host computer to the scanner. The OEM 400 models can also be operated from an external switch or an Ultra-Scan autostart request switch.

Diagnostics that run each time the scanner is powered up verify that all parts of the scanner are running at specification and that the quality of images does not deteriorate over time. A grey-scale calibration is performed on the scanner, and a code is sent via the serial port if the scanner fails any part of the diagnostics. Coupled with the fact that the reading surface needs no maintenance, no

identification from people with less marked ridge definition - including many women and Asian people. Generally, men's fingerprints, with thicker skin surface, are easier to read than women's. Out of 20 people tested per system, nearly all the scanners rejected one valid user even after five attempts to read.

More entertainingly (but only for computer criminals), the tests found that latent fingerprints on a tabletop, carefully dusted with toner and lifted with adhesive tape, copied onto acetate on a photocopier, damping the ink side of the image and presenting it to contact readers, two of the readers were fooled into validating the print. In the case of silicone rubber copies of the fingertip skin moulded from wax finger imprints, four of the six scanners tested were fooled. Fingerprints may be distinctive, but they are by no means unforgeable.

Compatibility

A large number of companies are working on fingerprint biometrics using several different techniques. Studies have found that fingerprint minutiae may have up to seven distinct characteristics, and the average finger has about 70 minutiae, which would give 490 pieces of data for comparison. However, as many of the minutiae are similar, this is not enough to ensure a completely accurate match; hence the use of geometrical information relating to minutia positions in some algorithms, or comparison of the whole or part of the image in others, or a combination.

There is no general standard either for the template data (the stored information about a single print) or for the data extraction algorithms used, and these are kept confidential by the companies that develop them, for both commercial and security reasons. This can increase security and commercial competitiveness, but it also reduces compatibility between systems.

Faces forward

Earlier in this article we touched on the developing technology of facial recognition. TrueFace is a patented face recognition



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ



Prices Exclude Vat @17.5%. Add £1.25 carriage & vat to all orders. Cheques / Postal orders payable to ESR Electronic Components.

DIL Sockets

6 Pin DIL 0.3"	£0.06
8 Pin DIL 0.3"	£0.06
14 Pin DIL 0.3"	£0.11
16 Pin DIL 0.3"	£0.11
18 Pin DIL 0.3"	£0.12
20 Pin DIL 0.3"	£0.11
24 Pin DIL 0.3"	£0.13
28 Pin DIL 0.3"	£0.13
40 Pin DIL 0.3"	£0.19
Turned Pin	
8 Pin DIL 0.3"	£0.11
14 Pin DIL 0.3"	£0.20
16 Pin DIL 0.3"	£0.23
18 Pin DIL 0.3"	£0.26
20 Pin DIL 0.3"	£0.28
24 Pin DIL 0.3"	£0.35
28 Pin DIL 0.3"	£0.41
40 Pin DIL 0.3"	£0.64
SIL Pin Header Strip	
1 x 36 Way Straight	£0.38
2 x 36 Way 90°	£0.56
1 x 36 Way 90°	£0.54
2 x 36 Way 90°	£0.80
Available in 2,3,4,5 & 10 way. Also female PCB sockets & jumper links.	
20 Way Socket Strip	£0.54

Transistor Sockets

T018-4 Base Socket	£0.24
T05 Base Socket	£0.24

IDC Cable Sockets

10 Way Socket	£0.23
14 Way Socket	£0.34
16 Way Socket	£0.31
20 Way Socket	£0.26
26 Way Socket	£0.35
34 Way Socket	£0.52
40 Way Socket	£0.66
50 Way Socket	£0.75

PCB Box Headers

10 Way Straight	£0.27
14 Way Straight	£0.36
16 Way Straight	£0.36
20 Way Straight	£0.41
26 Way Straight	£0.57
34 Way Straight	£0.57
40 Way Straight	£0.63
50 Way Straight	£0.96
10 Way 90°	£0.33
16 Way 90°	£0.42
20 Way 90°	£0.53
26 Way 90°	£0.70
34 Way 90°	£0.72
40 Way 90°	£0.83
50 Way 90°	£0.95

PCB Latch Headers

10 Way Straight	£0.50
16 Way Straight	£0.70
20 Way Straight	£0.78
26 Way Straight	£0.81
34 Way Straight	£0.86
40 Way Straight	£1.56
50 Way Straight	£1.29
10 Way 90°	£0.58
16 Way 90°	£0.78
20 Way 90°	£0.82
26 Way 90°	£1.06
34 Way 90°	£1.14
40 Way 90°	£1.26
50 Way 90°	£1.74

DIL Headers

14 Way DIL	£0.54
16 Way DIL	£0.59
24 Way DIL	£0.90
40 Way DIL	£1.02

Transition Headers

10 Way Transition	£0.49
14 Way Transition	£0.47
16 Way Transition	£0.47
20 Way Transition	£0.54
26 Way Transition	£0.62
34 Way Transition	£0.67
40 Way Transition	£0.90
50 Way Transition	£1.02

Red Line Plug

2.5mm Jack Plug	£0.21
2.5mm Line Socket	£0.16
2.5mm Chassis Socket	£0.34
3.5mm Mono Plug	£0.24
3.5mm Mono Line Skt	£0.30
3.5mm Mono Chassis	£0.14
3.5mm Stereo Plug	£0.33
3.5mm Stereo Line Skt	£0.37
3.5mm Stereo Chassis	£0.30
1/2 Mono Plug	£0.30
1/2 Mono Line Socket	£0.35
1/2 Mono Chassis Skt	£0.40
1/2 Stereo Plug	£0.40
1/2 Stereo Line Socket	£0.38
1/2 Stereo Chassis Skt	£0.40
1/2 Stereo Speaker Plug	£2.65

DIN Series

2 Pin Line Plug	£0.21
2 Pin Chassis Socket	£0.15
3 Pin Line Plug	£0.27
3 Pin Chassis Socket	£0.28
4 Pin Line Plug	£0.24
4 Pin Chassis Socket	£0.26
5 Pin Line Plug 180°	£0.30
5 Pin Chassis Skt 180°	£0.32
5 Pin Line Plug 240°	£0.24
5 Pin Chassis Skt 240°	£0.32
5 Pin Line Plug 360°	£0.24
5 Pin Chassis Skt 360°	£0.27
6 Pin Line Plug	£0.32
6 Pin Chassis Socket	£0.35
7 Pin Line Plug	£0.37
7 Pin Chassis Socket	£0.44
8 Pin Line Plug	£0.44
8 Pin Chassis Socket	£0.36

Phono Series

Red Line Plug	£0.20
Black Line Plug	£0.20
Yellow Line Plug	£0.20
White Line Plug	£0.20
Red Line Socket	£0.20
Black Line Socket	£0.20
Yellow Line Socket	£0.20
White Line Socket	£0.20
Red Chassis Socket	£0.20
Black Chassis Socket	£0.20
Gold Plated Plug Red	£0.76
Gold Plated Plug Black	£0.76

XLR Series - metal

3 Pin Line Plug	£1.50
3 Pin Line Socket	£1.50
3 Pin Chassis Plug	£1.41
3 Pin Chassis Socket	£1.73
Neutrik Line Plug	£1.73
Neutrik Line Socket	£1.99
Neutrik Chassis Plug	£2.13
Neutrik Chassis Socket	£2.37

D Type Connectors

Solder Bucket

9 Way Male Plug	£0.29
9 Way Female Socket	£0.28
15 Way Male Plug	£0.39
15 Way Female Socket	£0.39
15 Way H.D. Plug	£0.47
15 Way H.D. Socket	£0.78
23 Way Male Plug	£0.49
23 Way Female Socket	£0.49
25 Way Male Plug	£0.46
25 Way Female Plug	£0.41

IDC Ribbon Mounting

9 Way Male Plug	£1.08
9 Way Female Socket	£1.08
25 Way Male Plug	£1.18
25 Way Female Socket	£1.13

Right Angled PCB

Plastic D Covers

9 Way Cover - Grey	£0.30
9 Way Cover - Black	£0.30
15 Way Cover - Grey	£0.33
15 Way Cover - Black	£0.33
23 Way Cover - Grey	£0.36
23 Way Cover - Black	£0.36
25 Way Cover - Grey	£0.36
25 Way Cover - Black	£0.36
9 to 9 Cover / Case	£0.96
25 to 25 Cover / Case	£0.84
9 to 25 Cover / Case	£0.96

Audio Connectors

Sub-Miniature

3A 125V 1A 250V	£0.58
5mm Ø Mounting Hole	£0.58
SPST 5 x 10mm	£0.58
SPST 5 x 10mm	£0.60
SPDT c/off 5 x 10mm	£0.60
DPDT 9.2 x 10mm	£0.66

Miniature

6A 125V 3A 250V	£0.70
6.2mm Ø Mounting Hole	£0.70
SPST 8 x 13mm	£0.60
SPDT 8 x 13mm	£0.60
SPDT c/off 8 x 13mm	£0.60
SPDT c/o Biased 2 way	£1.10
SPDT c/o Biased 1 way	£1.04
DPDT 12 x 13mm	£0.72
DPDT c/off 12 x 13mm	£0.80
DPDT c/o Biased 2 way	£1.28
DPDT c/o Biased 1 way	£1.28

Standard

10A 250V Push on terminals	£1.44
6.2mm Ø Mounting Hole	£1.44
SPST 18 x 30mm	£1.42
SPDT 18 x 30mm	£1.42
SPDT c/off 18 x 30mm	£1.52
DPDT 21 x 30mm	£1.78
DPDT c/off 21 x 30mm	£1.78

Slide Switches

Miniature

300mA 125V	£0.20
7 x 15mm Mounting Hole	£0.20
DPDT 7 x 23mm	£0.20

Standard

1A 125V	£0.20
5.5 x 12mm Mounting Hole	£0.20
DPDT 12 x 35mm	£0.24
DPDT c/o 12 x 35mm	£0.27

Rotary Switches

150mA 250V	£1.50
Make before Break	22mm Ø
9.8mm Ø Mounting Hole	£1.41
1 Pole 12 Way	£0.84
2 Pole 6 Way	£0.84
3 Pole 4 Way	£0.84
4 Pole 3 Way	£0.84

RF Connectors

BNC Plug 50Ω Solder	£0.93
BNC Plug 50Ω Crimp	£0.62
BNC Plug 75Ω Solder	£0.95
BNC Plug 75Ω Crimp	£0.70
BNC Chassis Socket	£0.83
F Plug - Twist	£0.24
F Plug - Crimp	£0.24
TNC Plug 50Ω Solder	£1.24
TNC Plug 50Ω Crimp	£0.85
TNC Plug 75Ω Solder	£1.40
TNC Plug 75Ω Crimp	£1.16
UHF Plug 5mm Cable	£0.63
UHF Plug 11mm Cable	£0.83
UHF Chassis Skt - Sar	£0.50
UHF Chassis Skt - Rnd	£0.73

Extensive range of RF connectors in stock, inc.FME, SMA, Mini UHF & N Type.

Terminals

Colours Red, Black, Green, Blue, White or Yellow	
2mm Solder Plugs	£0.18
2mm Chassis Sockets	£0.26
4mm Solder Plugs	£0.30
4mm Stackable Plugs	£0.40
4mm Chassis Sockets	£0.23
4mm Binding Posts	£0.54
33mm Crocodile Clips	£0.13

Power Connectors

DC Low Voltage

DC Plug 0.71D 2.35OD	£0.46
DC Plug 1.31D 3.4OD	£0.32
DC Plug 1.71D 4.0OD	£0.50
DC Plug 1.71D 4.75OD	£0.46
DC Plug 2.11D 5.0OD	£0.24
DC Plug 2.51D 5.0OD	£0.24
DC Plug 3.11D 6.3OD	£0.46
DC Line Socket 2.1mm	£0.64
DC Line Socket 2.1mm	£0.56
DC Chassis Skt 2.5mm	£0.46
DC Chassis Skt 2.5mm	£0.46

IEC Mains 6A 250Vac

Relays

PCB Mounting	
1A 24Vdc DPDT 5V	£1.44
1A 24Vdc DPDT 12V	£1.60
3A 110V SPDT 6V	£0.58
3A 110V SPDT 12V	£0.58
5A 110V SPDT 6V	£0.72
5A 110V SPDT 12V	£0.72
5A 110V DPDT 6V	£0.93
5A 110V DPDT 12V	£0.93
5A 240V DPDT 6V	£1.76
5A 240V DPDT 12V	£1.76
10A 240V SPDT 6V	£1.44
10A 240V SPDT 12V	£1.44

Computer Accessories

Adapters

9M Gender Changer	£2.18
9F Gender Changer	£2.29
25M Gender Changer	£2.60
25F Gender Changer	£2.80
9 Male - 25 Female	£1.90
9 Male - 25 Male	£1.90
9A - 6 Mini Din Male	£2.40
9F - 6 Mini Din Female	£2.40
5M Din - 6F Mini Din	£2.08
5F Din - 6M Mini Din	£2.08

Testers / Patch Boxes

Mini Tester 7 LEDs	£6.68
Check Tester 18 LEDs	£6.98
Enhanced + Switches	£15.25
25D Jumper Box M-F	£2.90
25D Patch Box M-F	£7.32
Anti-Static Wrist Strap	£4.76
R522 Surge Protector	£5.43
Mains Surge Protector	£11.99
4 Gang Surge Block	£15.50

Leads & Cables

Modem Leads

1.5m Printer Lead	£3.40
5m Printer Lead	£9.38
10m Printer Lead	£8.75
Serial Printer 25M-9F	£4.50
Serial Printer 25M-25F	£4.45

Null Modem Leads

9 Female - 9 Female	£3.45
25 Female - 25 Female	£4.63
9 Female - 25 Female	£2.90
9&25F to 9&25F	£5.54
25Male to 9Female	£4.08
25Male to 25Female	£4.75

PC Link Leads

Interlink 25M to 25M	£4.38
----------------------	-------

Patch Lead

25Male to 25Male	£4.12
36Male to 36Male	£5.90

Internal Leads

Floppy Cable A/B	£2.99
Hard Disk 2xIDE	£1.65
Power 3½-2 x 3½	£1.88
Power 5¼-2 x 5¼	£1.50
Power 5¼-2 x 3½	£2.24
Power 5¼-3½, 5¼	£2.24

Networking

BNC T Piece FFF	£2.40
BNC T Piece F	£1.02
BNC Coupler F	£1.02
BNC Coupler M	£1.65
BNC Ratchet Crimper	£17.44
50Ω BNC Terminator	£1.24
Thinnet Cable per m	£0.39

Push Switches

Miniature Round

250mA 125V 28 x 10mm	£0.24
7mm Ø Mounting Hole	£0.24
Non Latching Push to Make	£0.24
Black PTM	£0.24
Red PTM	£0.24
Yellow PTM	£0.24
Green PTM	£0.24
Blue PTM	£0.24
White PTM	£0.24
Non Latching Push to Break	£0.24
Black PTB	£0.24

Standard Square

1A 250V	£0.60
39 x 15MM	£0.60
12mm Ø Mounting Hole	£0.60
Non Latching Push to Make	£0.60
Black PTM	£0.60
Red PTM	£0.60
Blue PTM	£0.60
White PTM	£0.60
Latching - push On push Off	£0.65
Black	£0.65
Red	£0.65
Blue	£0.65
White	£0.65

Rocker Switches

Miniature

6A 250V Solder Tags	£0.69
SPST 21 x 14 x 16mm	£0.92
DPDT 21 x 24 x 22mm	£1.02
SPST - Red Neon	£1.02
SPST - Green Neon	£1.02
SPST - Amber Neon	£1.02

Standard

15A 250V Push on Tags	£0.62
SPST 30 x 11 x 22mm	£0.62
DPDT 30 x 25 x 22mm	£1.12

Illuminated

15A 250V Push on Tags	£0.84
SPST 30x14mm Red	£1.40
DPST 30x25mm Amber	£1.40
DPST 30x25mm Green	£1.40

Boxes & Cases

Many more sizes available

General Purpose Plastic

75 x 56 x 25mm	£0.93
75 x 51 x 22mm	£0.93
111 x 57 x 22mm	£1.05
79 x 61 x 40mm	£1.59
100 x 74 x 41mm	£1.69
118 x 98 x 45mm	£1.95
150 x 100 x 60mm	£2.65
150 x 80 x 50mm	£2.47

Diecast Aluminium

50 x 50 x 31mm	£2.24
100 x 50 x 25mm	£2.98
112 x 62 x 31mm	£3.55
120 x 65 x 40mm	£4.19
150 x 80 x 50mm	£5.39
121 x 95 x 61mm	£5.99

Two Piece Aluminium

133 x 70 x 37mm	£2.08
102 x 102 x 37mm	£1.94
102 x 70 x 37mm	£1.76
133 x 102 x 37mm	£2.19
102 x 63 x 50mm	£1.86
76 x 51 x 25mm	£1.34
152 x 102 x 50mm	£2.90
178 x 127 x 63mm	£3.62
203 x 152 x 76mm	£4.68
102 x 102 x 63mm	£2.15
133 x 102 x 63mm	£2.57
152 x 102 x 76mm	£3.23

Steel/Aluminium Plastic coated steel top, Aluminium base

152 x 114 x 44mm	£4.19
203 x 127 x 51mm	£4.99
229 x 127 x 63mm	

technology belonging to Miros Inc. of Wellesley, USA. Trueface is designed as the "core technology" for a number of security software packages, including TrueFace PC (secure log-on to desktop PCs), and TrueFace Access, which is used for controlling entries such as doorways, or for clocking workers' time and attendance.

Preventing the system from being fooled with a photograph, as we said above, is essential for serious security. TrueFace can either be used with two camera modules, which effectively provide "stereo vision" that can distinguish between a 3D face and a 2D photograph, or it can be set to input two facial orientations (that is, a small move of the head) to make sure that the image comes from a 3D source.

Combined with a keypad or magnetic card reader, this gives a very flexible means of entrance security.

The TrueFace software uses neural networking to recognise faces, so that the software can learn from a variety of images that may be, for instance, affected by a change of angle or variations in lighting. It also samples features from all over the face, whereas some systems home in on distances and angles only in the eye/nose/mouth area.

The advantage of neural networks over fixed algorithms in pattern recognition, and particularly in facial recognition where the variation in faces is so great within the standard pattern, is that it is very difficult to write algorithms which cover all the relationships between possible inputs and possible actions. Neural networking is adaptable and can give a closer "fit" to the images it actually has to work with as it "learns" the best relationship between inputs and outputs (actions towards a known goal taken by the software on the basis of the inputs).

The TrueFace software can continuously monitor a video signal for new faces appearing in its field of view, or it can be accessed on demand by a key click, for example where the user may need to be matched to one area of a very large database ("Electronics Laboratory", for example!). The software engine in this case is a PC Dynamic Linked Library (DLL) or a Unix library, independent of particular computer peripherals. It can therefore work with virtually any database, smart card reader, video camera, scanner, frame grabber or image capture card, including the low-cost PC video cameras popular with Internet users in the States.

The main criterion is that the minimum height of the face within the image is 80 pixels of 8-bit grey-scale (like all biometric systems, the image is converted to greyscale before processing). Some face recognition systems need higher-specification cameras to deliver a sufficient frame rate to function properly.

Fast enough

The main requirement for a scanner or image capture card is that it should be fast enough to match the software in processing a pair of images to verification in about 1 second. Another new application, TrueFace Isolator, allows an unmanned camera to recognise, isolate, crop and scale a face from any background area. This is being used for "live" automatic recognition of faces, and for producing images for ID cards quickly and without manual setup.

As it is mainly used for access, speed is a real factor. TrueFace can verify a live image in about 1 second on a Pentium PC and produce a best match on a database at 500 faces per second on a Pentium 200 PC. Faster processors can process the faces roughly in proportion to the increase in processing speed.

Having compared a captured face image with a stored file, the software returns a "confidence level" on how good the match is in about a second, and then refers to a user-

definable threshold to decide whether the confidence level indicates that the two faces are the same.

Because face recognition requires little or no special action on the part of the subject, it is convenient for the person seeking entry or logging on, and has the added advantage to the user (if so desired) that faces can be read and analysed for surveillance purposes without the knowledge of the person being scanned. No other automatic biometric can yet do this. Even voice recognition, which is well established, is easier to thwart through changing a normal timbre, or signal distortion, than a visual image.

Identical twin faces can still fool facial systems, but, as Miros says, "What percentage of all fraud is caused by a twin perpetrator?"


The Miros software - in the form of TrueFace CyberWatch Logon95 - is available for individual PCs armed only with a small video camera mounted on the monitor, and can be downloaded from their website for around US\$100. Another application combines it with a Mobile Phone Kit from US company ChatVideo!, which includes a mobile camera, microphone and loudspeaker headset and software that allows the user to talk, hear and see, using the Internet as the phone provider. And we thought that personal stereos were the last word in ignoring other pavement (or sidewalk) users.

The future

In biometrics, the ingenuity of the hardware is necessary to capture image data that can be analysed by the software, often under somewhat difficult conditions. The ingenuity of the software is important, because the better the software is, the more reliable are the comparison results from the signal delivered from the hardware, and the more flexible is the processing that can be obtained from it.

BUT the hardware must be capable of measuring something which is different for different people, substantially constant for the same individual, and only works with a actual living individual, not with a photo or replica. (There speaks a hardware engineer!)

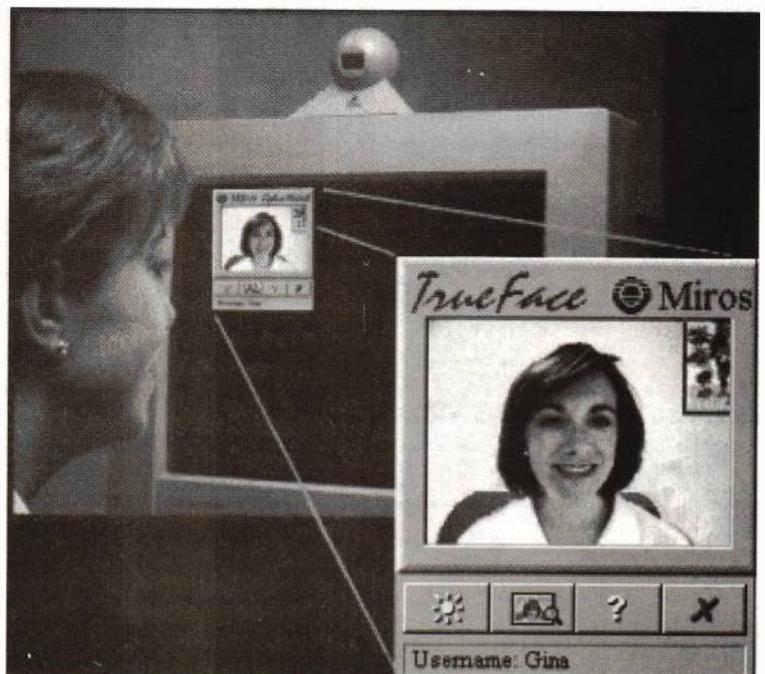
Security will probably come to depend on multiple biometric readings. As we have seen, there already exist security systems that depend on at least two readings, such as finger and face, or finger and swipecard. It may be a while yet before we give up plastic cards in favour of our built-in barcodes.



A monitor-top camera sends the image to Trueface recognition software

Easy-PC

Electronics CAD for Windows 95 and NT

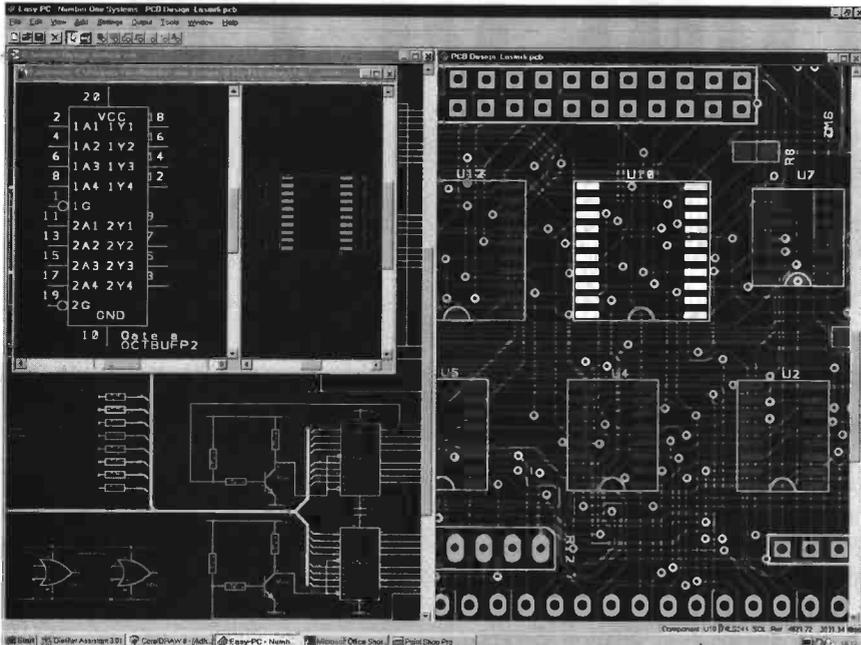

- True Windows graphical user interface
- Multi-sheet Schematics - Projects.
- Full links to our Analogue, Digital and Electromagnetic Simulators.
- Impressive, high speed, gridless, shape-based autorouter options.
- Design rule and connectivity checks.
- Full Windows outputs.
- Gerber, Excellon and DXF outputs.
- Free technical support! No dongles or maintenance contracts.
- Trade up allowance from other products.
- New entry level version available.
- New demo' available - please call!

Number One Systems

Ref: ETI, Harding Way, St.Ives,
Cambridgeshire, PE17 4WR,
United Kingdom

Tel: 01480 461778 Fax: 01480 494042

International: +44 1480 461778/494042

email: sales@numberone.com

http://www.numberone.com

Amiga genlock pcb (uncased) for fitting videos it has a 23pin D lead to plug into the computer and pcb pins for composite video in and out. When no video input is connected the normal computer display is shown on the composite video out when the video input is added the white areas on the screen are replaced by the video image. The pcb is powered from the computer. £19.98

WATCH SLIDES ON TV

"Liesgang diat" automatic slide viewer with built in high quality colour tv camera, composite video output with a BNC plug. In very good condition with few signs of use £108.00

Board cameras all with 512x582 pixels 4.4x3.3mm sensor with composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts and require 10 to 12vdc power supply 47MR size 60x36x27mm with 6 infra red leds (gives the same illumination as a small torch would) £50.00+vat = £58.75

40MP size 39x38x23mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole. £57+vat = £66.98

40MC size 39x38x28mm camera for 'C' mount lens this gives a much clearer picture than with the small lenses £68.79

standard 'C' mount lens F1.6 16mm for 40MC £26.43+vat = £31.06

Waterproof camera with stylish tilt & swivel case
£92.76 + vat = £109.00 or 10+ £89.32 + vat = £104.95

DTA30 Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty. HMA20 hand held MOSFET analyser identifies gate drain and source and if P or N channel. DTA30 & HMA20 £38.34 each DCA50 component analyser with lcd readout identifies transistors mosfets diodes & LEDs lead connections £69.95

Speaker cabinets 2 way speaker systems with motorola tweeters

speaker dia	15"	12"	8"
power rating	250WRMS	175WRMS	100WRMS
impedance	8ohm	8ohm	8ohm
frequency range	40hz-20khz	45hz-20khz	60hz-20khz
sensitivity(1W/1M)	97dB	94dB	92dB
size in mm	500x720x340	450x640x345	315x460x230
weight	21.1kg	16.8kg	7.4kg

price each for black vinyl coating £139.95 £99.99 £54.94
grey felt coating £159.97** £119.97** £64.99
(* = not normally in stock allow 1 week for delivery)
Power amplifiers 19" rack mount with gain controls
STA150 2x160Wrms (40hm load) 14kg £202.11
STA300 2x190Wrms (40hm load) 11kg £339.00
STA900 2x490Wrms (40hm load) 15kg £585.00
LEDs 3mm or 5mm red or green...7p each yellow 11p each
cable ties 1p each £5.95 per 1000 £49.50 per 10,000

Rechargeable Batteries		£0.99
AA(HP7) 500MAH		£1.55
AA 500MAH with solder tag		£1.75
AA 950MAH		£2.20
C(HP11) 1.2AH		£3.60
C 2AH with solder tags		£2.60
D(HP2) 1.2AH		£4.95
D 4AH with solder tags		£4.95
PP3 & 4V 110mA		£1.55
1/2AA with solder tags		

Sub C with solder tags £2.50
AAA (HP16) 180MAH £1.75
1/3 AA with tags (philipsCTV) £1.95
Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100ma and discharged at 250ma or less 1300MAH capacity (lower capacity for high discharge rates) £2.95

Special offers please check for availability
stick of 4 42 x 16mm nicad batteries 171mmx16mm dia with red & black leads 4.8v £5.95
5 button cell 6V 280MAh battery with wires (Varta 5x250DK) £2.45

Orbitel 866 battery pack 12v 1.60AH contains 10 sub C cells with solder tags (the size most commonly used in cordless screwdrivers and drills 22 dia x 42mm tall) its easy to crack open and was manufactured in 1994, £8.77 each or 110.50 per box of 14BCI box 190x106x50mm with slots to house a pcb the lid contains an edge connector (12 way 8mm pitch) and screw terminals to connect in wires and 5 slide in cable blanks. £2.95

7 segment common anode led display 12mm £0.45
Alipax A82903-C large stepping motor 14v 7.5' step 27ohm 68mm dia body 6.3mm shaft £8.95 or £200.00 for a box of 30 Polyester capacitors box type 22.5mm lead pitch 0.9uf 250vdc 18p each 14p 100+ 9p 1000+1uf 250vdc 20p each, 15p 100+, 10p 1000+Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case 75p each 60p 100+Philips 123 series solid aluminium axial leads 33uf 10v & 2.2uf 40v 40p each, 25p 100+ Solid carbon resistors very low inductance ideal for RF circuits 27ohm 2W, 68ohm 2W 25p each 15p each 100+ we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test £9.95 Hand held ultrasonic remote control £3.95

CV2485 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £8.50 per 100 Varta R300NH Streamer tape commonly used on nc machines and printing presses etc. it looks like a normal cassette with a slot cut out of the top £4.95 each (£3.75 100+)

Heatsink compound tube £0.95
HV3-2405-E5 5-24v 50mA regulator ic 18-264vac input 8 pin DIL package £3.49 each (100+ 2.25)

All products advertised are new and unused unless otherwise stated wide range of CMOS TTL 74HC 74F Linear Transistors kits rechargeable batteries capacitors tools etc always in stock

Please add £1.95 towards P&P (orders from the Scottish Highlands, Northern Ireland (incl of Man, Isle of Wight and overseas may be subject to higher P&P for heavy items), vat included in all prices

JPG Electronics 276-278 Chatsworth Road Chesterfield S40 2BH
Mastercard/Visa Orders (01246) 211202 fax 550959

JPG ELECTRONICS

ETI 276-278 Chatsworth Road,
Chesterfield S40 2BH

Access Visa Orders (01246) 211202 fax 550959
Callers Welcome 9.30am-5.30pm Monday-Saturday



DISTANCE LEARNING COURSES in:

Analogue and Digital Electronic
Circuits, Fibres & Opto-Electronics
Programmable Logic Controllers
Mechanics and Mechanisms
GCSE and BTEC Mathematics

- Courses to suit *beginners* and those wishing to *update* their knowledge and practical skills
- Courses are delivered as self-contained kits
- No travelling or college attendance
- Learning is at your own pace
- Courses may have BTEC Certification and Tutoring

For information contact:

NCT Ltd., P.O. Box 11

Wendover, Bucks HP22 6XA

Telephone 01296 624270; Fax 01296 625299

Web: http://www.nct.ltd.uk.

Getting MORE out of PICs

Part 4

Robin Abbott

The first of two parts on using the I²C bus. [part 1 of 2]

There are two main serial buses widely used for integrated circuit control: the I²C bus and the SPI bus. Both buses are designed for relatively low-speed communications for those integrated circuits which rarely require configuration.

The SPI bus is based on a three-wire interface: one wire for the clock, one wire for transmitted data, and one for received data. It is easy to drive, and therefore is not the subject of this series. It has the disadvantage that it is not easy to hang multiple devices on the bus, or to have multiple bus masters.

The I²C bus is a two-wire bus which is more difficult to drive. There are approximately 1,000 types of integrated circuit, mainly in the consumer markets, which use this type of bus. The bus is a proprietary standard designed by Phillips/Signetics. It has a great advantage with devices which have traditionally been multi-pin, and which can now be fitted into much smaller packages. Also, a number of devices can be driven on the single two-wire bus, which reduces the I/O count on the processor circuitry and makes pcb layout easier. This flexibility comes at the expense of increased interface complexity, and of relatively slow transfers.

Among PIC applications, the devices I have used most often which run on the I²C bus are the small 8-pin serial eeproms. These suffer from slow access, but are mainly intended for storing

configuration information or for data logging where speed is not significant. This article will describe how to drive the I²C bus from a PIC, and the following article (in next month's issue) will describe a complete serial eeprom programmer/reader application.

Slave devices

Devices on the I²C interface can be master devices, slave devices or both. There must be at least one master, and there can be any number of slaves (limited by the addressing range of devices).

Figure 1 shows a configuration for two master devices and three slave devices. The wires on the interface are the clock line SCL and the data line SDA. The master device controls the clock line SCL. Normally devices use open-collector drivers on the I²C bus, so the bus usually has a pullup resistor on SCL and SDA. This allows multiple devices to drive the bus simultaneously, so that if two masters attempt to access the bus at the same time there is no excessive current drain. For the purposes of this article, we shall assume only one master device as it is very rare that an I²C bus has dual masters.

In any transfer of data there is always one device which acts as the master and one which acts as the slave. The master supplies the clock for the transfer, and defines which device is to be addressed and whether the transfer is a read or a write

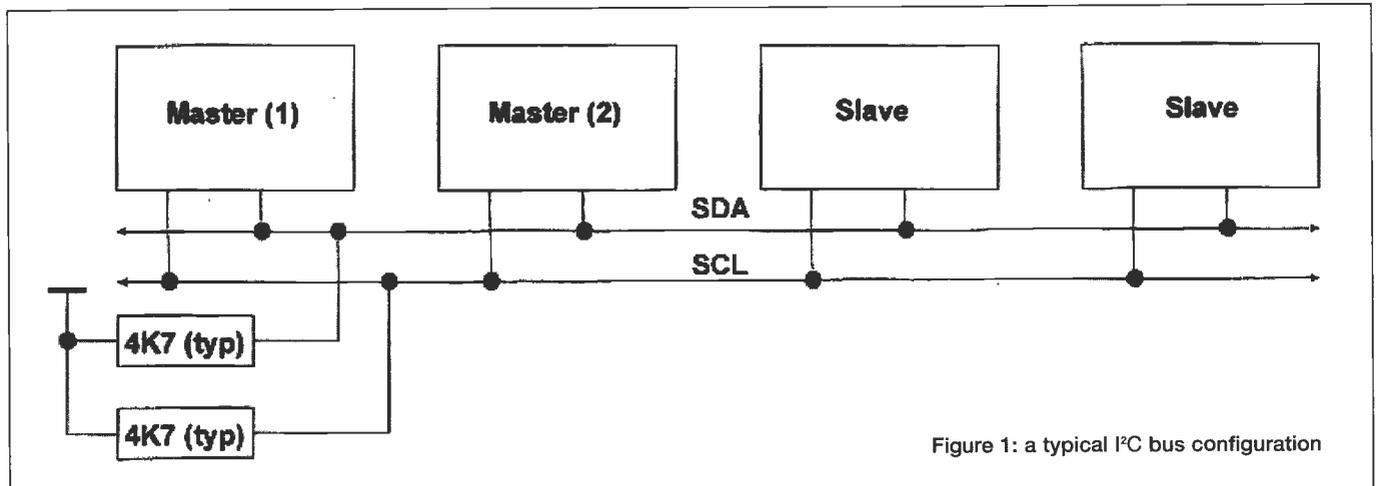


Figure 1: a typical I²C bus configuration

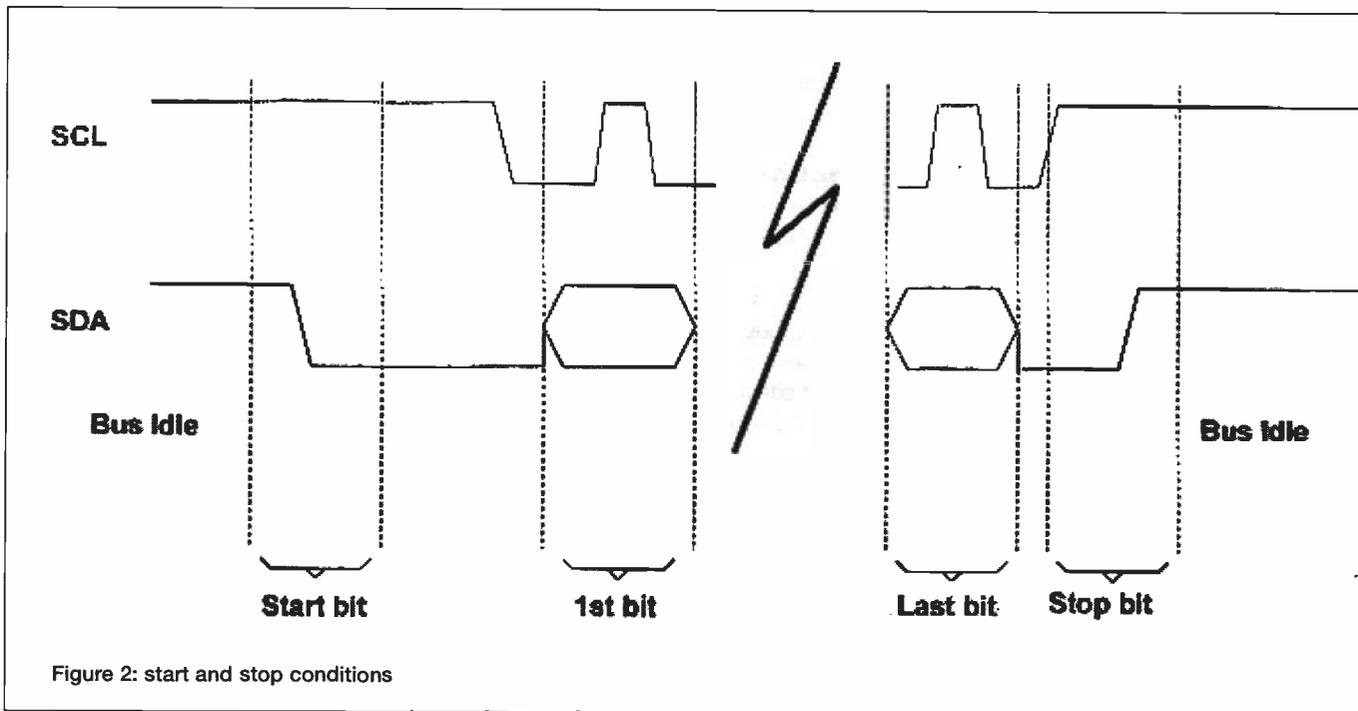


Figure 2: start and stop conditions

access. The slave checks the address, and if it is correct responds as defined by the master. In any transfer there will be eight bits and one acknowledgement bit sent. The acknowledgement bit is always sent by the device which is reading from the bus: if the master is transferring to the slave, the slave device acknowledges; if the slave is transferring to the master, the master acknowledges.

Bus states and data transfer

The idle state of the bus is defined by both the data and clock lines staying high. When the clock line is low, the data line can change without affecting the state of the bus. When the clock is high, the data line can only change to alter the state of the bus. The master bus must issue a start condition to gain control of the bus, and a stop condition when it has finished with the bus. A start condition is defined as the data line falling from high to low when the clock line is high, and a stop condition is defined as the data line rising from low to high when the clock line is high. These state changes are illustrated in **figure 2**.

Once a start condition has been issued, the master device can initiate transfer of one or more bytes to or from the slave device. Data is transferred using the clock. Each clock pulse (defined as a high period of the clock) transfers a single bit. The data can change when the clock is low, but must stay stable while the clock is high. Data is transferred in eight bits with the most significant bit transferred first. Following the eight data bits, the master must issue one final pulse for the acknowledgement. The transfer of a single byte with an acknowledgement is illustrated in **figure 3**.

It is important to note that several bytes may be transferred between the start and stop states: for example, many bytes may be read sequentially from a serial eeprom without issuing start and stop states between bytes. This increases the transfer speed.

Addressing and controlling slave devices

Most I²C slave devices have an address which is sent by the master device immediately after the start bit. The address forms the first seven bits of the first byte. The final bit of the first byte transferred is normally the read/write bit which defines whether a read or write

transfer is to be initiated. This bit is low to write, and high to read.

The address of slave devices usually has a fixed part and a variable part. The fixed part occupies the upper bits of the address, and the variable part allows several devices of the same type to share the same bus. The fixed part is the same for a group. For instance, I²C memory devices such as serial eeproms and serial ram devices have a fixed address part of 1010 (binary).

The lower bits of the address (the variable part) can be selected using pins of the device. Some I²C devices have address pins, normally named A0, A1 and so on. These pins can be connected to Vss or Vdd. Thus, to define the address as 001 on a device with three address pins, A0 would be connected to Vdd, and pins A1 and A2 would be connected to Vss.

Some devices use the variable part of the address for internal decoding. For example, the 24LC16 eeprom device uses the three variable address bits to provide the top three address bits of the eeprom memory. There can only be one 24LC16 device on an I²C bus, and no other devices with the same fixed address part can share that bus or the devices will clash.

For example, a 24LC65 has a fixed address of 1010, and a variable part of 001, giving the overall address 1010001. The sequence to read a byte from a LC65 is as follows:

Start State

- Send the byte 10100011 (Read from address 1010001)
- Receive single bit acknowledgement from the LC65
- Receive byte from LC65
- Send single bit acknowledgement to the LC65
- Send stop bit

The acknowledgement bit sent by the slave is low if the slave device recognises the address and has acted on the command, and high otherwise. The acknowledgement bit sent by the master is low if further bytes are to be received, and high if this is the last byte read.

Once a master device has control of the bus (having sent a start state and an address), then that master, and the addressed slave, can send or receive further bytes until a stop state is sent and the bus returns to the idle state. The further bytes sent depend on the specific device. For example an address and a

write bit sent to the 8570 serial ram is followed by a single eight-bit internal address which is the ram address to be written, followed by one or more bytes to be written to that address and the following addresses sequentially.

Driving the I²C bus from a PIC in practice

The routines shown below provide a completely general-purpose I²C interface. A full serial eeprom programmer/reader using these routines will be in next month's article.

There is one main routine which has two entry points. This main routine provides a complete 8-bit interface to the I²C bus. It may be configured to send a start state before the transfer, to send a stop state after the transfer, to read or write eight bits to the bus, and finally to read or write an acknowledgement bit after the transfer.

Variables

The variables and definitions necessary for the I²C routines are shown in listing 1. This include file is set up to use the 18-pin PIC general-purpose module shown in the first part of this series. The general-purpose module includes a DIL socket suitable for 8-pin eeprom devices.

Not all variables are used in this month's article; some are intended for the eeprom routines. The variables are as follows:

- PROCFREQ** This is the processor frequency in kHz. This frequency must be set correctly for the correct operation of the eeprom, particularly at higher processor frequencies.
- picio** This is the port used for the I²C bus. For the demonstration this is set to PORTA.
- scl** This is the bit on the I²C port which is use for the serial clock, the SCL line to the I²C bus. On the demonstration this is bit 0 of port A.
- sda** This is the bit on the I²C port which is use for the serial data, the SDA line to the I²C bus. On the demonstration this is bit 1 of port A.
- sclv,sdav** These represent the values of the port bit when set. Sclv is 1, and sdav is 2.
- writeval** This is the value to be written to the eeprom. It may be used for other purposes when the eeprom is not being accessed.
- temp-temp4** These are five temporary variables used in the I²C and eeprom routines. They may be freely reused when the eeprom and I²C buses are not being accessed.

Listing 1

```

;
; This is the IIC bus header file
;

#ifndef __PICDE
TRUE EQU 1
FALSE EQU 0
#endif

PROCFREQ EQU .4000 ; Processor frequency in
                    KHz

EES SETUP EQU .100 ; Set up time for IIC in
                    nS
EEHOLD EQU .0 ; Hold time for IIC in
                    nS
EECLOCKWID EQU .600 ; Minimum High clock
                    width for IIC
EECLOCKWIDLO EQU .1400 ; Minimum low clock width
                    for IIC
OPDELAY EQU .1000 ; Output delay from clock
                    for IIC
STOPSETUP EQU .600 ; Stop bit set up time
                    for IIC
FREQNS EQU (.1000000/PROCFREQ)*4 ;
                    Clock Cycle (nS)

picio EQU PORTA ; Port to be used
                    for IIC bus
scl EQU 0 ; Serial clock bit on
                    IIC bus port
sda EQU 1 ; Serial data bit on
                    IIC bus port
sclv EQU 1 ; Value of clock bit
                    if set
sdav EQU 2 ; Value of data bit
                    if set

#define RAMPAGE0 BCF STATUS,RP0 ; RAM page 0
#define RAMPAGE1 BSF STATUS,RP0 ; RAM page 1
#define ROMPAGE0 BCF PCLATH,3 ; ROM page 0
#define ROMPAGE1 BSF PCLATH,3 ; ROM page 1
;
; System variables
;
cblock 20h
writeval ; Holds value to write to IIC bus
temp ; 5 temp registers
temp1 ;
temp2 ; IIC routines
temp3
temp4
endc

```

Write/Read eight bits to the I²C Bus

Listing 2 shows the routines which are used to read and write the I²C bus. The routines are optimised for time not space. The first half of the listing shows the macros which are used to ensure that bus timing is met. Each macro is called with a parameter which is the number of machine cycles between two bus changes, the macro then inserts the necessary number of NOPs to ensure the time is met. A machine cycle is four clocks of the processor's main oscillator.

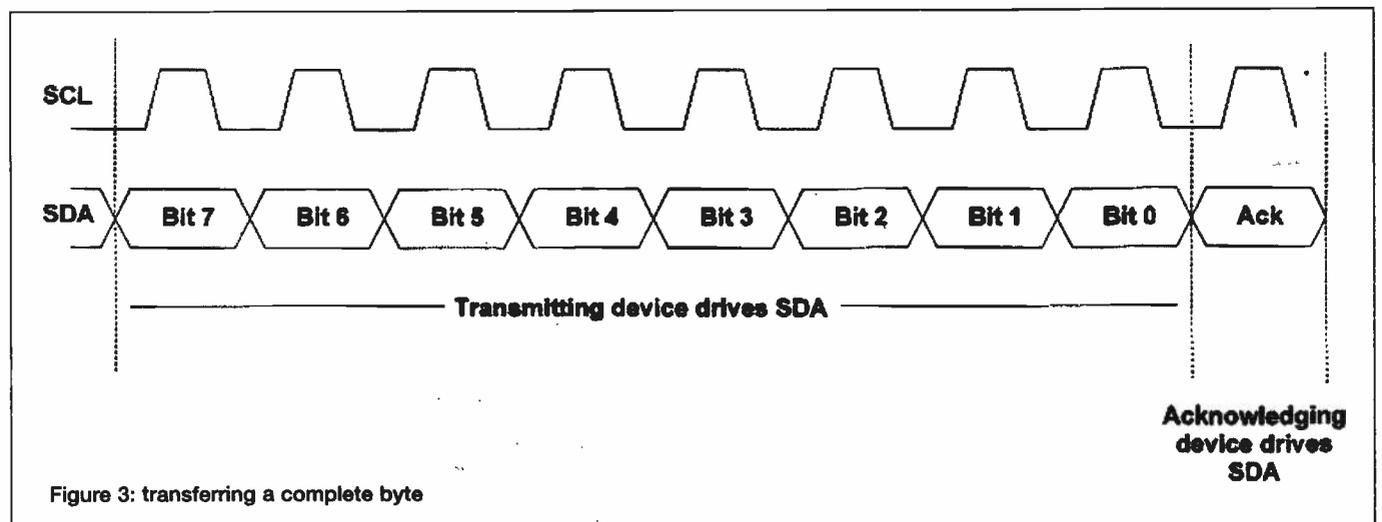


Figure 3: transferring a complete byte

Listing 2 - IIC Routines

```

:XXXXXXXXXXXXXXXXX
;
; IIC read/write
; Uses : temp, temp1,2,3,4
;
;XXXXXXXXXXXXXXXXX
;
; delay macros
;
; These are the number of delay cycles needed between
actions, these vary
; according to processor frequency and are essential at
20MHz clock to meet
; the IIC characteristics
;

SETUPCYC EQU (ESETUP/FREQNS)+(((ESETUP/FREQNS)*FRE
QNS)!=ESETUP)
HOLDCYC EQU (EEHOLD/FREQNS)+(((EEHOLD/FREQNS)*FRE
QNS)!=EEHOLD)
CWCYC EQU (EECLOCKWID/FREQNS)+(((EECLOCKWID/FREQNS)*FR
EQNS)!=EECLOCKWID)
CWCYCLO EQU (EECLOCKWIDLO/FREQNS)+(((EECLOCKWIDLO/FRE
QNS)*FREQNS)!=EECLOCKWIDLO)
WAITOP EQU (OPDELAY/FREQNS)+(((OPDELAY/FREQNS)*FRE
QNS)!=OPDELAY)
STOPCYC EQU (STOPSETUP/FREQNS)+(((STOPSETUP/FREQNS)*FR
EQNS)!=STOPSETUP)

STOP macro exdelay
x=STOPCYC-exdelay
while x>0
NOP
x--1
endw
endm

WAITCLOCK macro exdelay
x=WAITOP-exdelay
while x>0
NOP
x--1
endw
endm

SETUP macro exdelay
x=SETUPCYC-exdelay
while x>0
NOP
x--1
endw
endm

HOLD macro exdelay
x=HOLDCYC-exdelay
while x>0
NOP
x--1
endw
endm

CLOCKWID macro exdelay
x=CWCYC-exdelay
while x>0
NOP
x--1
endw
endm

CLOCKWIDLO macro exdelay
x=CWCYCLO-exdelay
while x>0
NOP
x--1
endw
endm

; Write/read 8 bits to IIC, check ack
; Call WriteIICStart for start bit to the local IIC bus
; Call WriteIICNoStart for no start bit to the local IIC
; Call with scl bit driving
; Call with sda bit set to read for a Read operation, and
driving for Write op.
; temp2 is index, and returns the state of the ACK bit
from the device
; temp3 bit 0 is not used
; temp3 bit 1 indicates to generate a stop after the
transfer
; temp3 bit 2 indicates to generate ack if set (Read ack
if reset)
; temp3 bit 3 indicates to read from device if set
; temp4 reads input byte, or writes output byte
; Ends driving sda & scl

WriteIICStart bcf picio,sda ; Call here for
Start bit - drops
data
WriteIICNoStart movwf temp4 ; Call here for no
start bit


```

```

doiic movlw picio ; Move default bus
to FSR
movwf FSR
movlw 8
movwf temp2
bcf 0,scl ; drop clock
btfsc temp3,3 ; leap forward if
read
goto rdeelop
;
wrteelop bcf 0,sda ; This writes 8 bits
to the IIC
rlf temp4 ; now get correct
port bit
skpnc ;
bsf 0,sda ;
SETUP 1 ; clock now high
bsf 0,scl ; clock low again
CLOCKWID 1
bcf 0,scl ; clock low again
CLOCKWIDLO 7
decfsz temp2 ; and loop
goto wrteelop
;
; rdeelop clrf temp4 ; This reads 8 bits
from the IIC
clrc ;
bsf 0,scl ; clock now high
CLOCKWID 4
btfsc 0,sda ; now read input
setc ;
rlf temp4 ; Read in bit
bcf 0,scl ; clock low again
CLOCKWIDLO 4
decfsz temp2 ; and loop
goto rdee2
;
; This section handles the last bit (acknowledge or read
ack), and handles stop
endthis bcf 0,sda ; Acknowledgement is
low
;
etstop bsf FSR,7 ; either read or
drive SDA
Read from data line
bsf 0,sda;
btfsc temp3,2 ; Now drive data
line if ack
bcf FSR,7
SETUP 2 ; Send the last
clock
bsf 0,scl
;
WAITCLOCK 1
btfsc 0,sda ; Test state of
acknowledgement bit
; and if 1, then
leave in temp 5
incf temp2
;
CLOCKWID 3
bcf 0,scl
;
bsf 0,sda ; Data line high
bsf FSR,7 ; End by driving the
data line
bcf 0,sda
bcf FSR,7
;
btfss temp3,1 ; 1/2
return ; 1 If no stop
;
bit return with scl low
;
dostop bcf 0,sda ; Call here to do a
stop bit
SETUP 1 ; otherwise clock
high
bsf 0,scl
;
STOP 1 ; If stop return
driving high on
scl/sda
bsf 0,sda
return
;
; Generate a quick stop bit on the local IIC bus
; rapidly clock 8 bits and then do no_ack and STOP bit
;
quikstop movlw picio
movwf FSR
movlw 8
movwf temp2
quikclk bsf 0,scl
CLOCKWID 1
bcf 0,scl
CLOCKWIDLO 4
decfsz temp2
goto quikclk
movlw 2
movwf temp3 ; Set for stop bit and
;
read ack goto etstop

```

For example, the value CWCYC is set to the minimum number of machine cycles that the PIC must wait between raising the clock line and dropping it (the clock width). Now when the routine raises the clock it calls the macro CLOCKWID with a parameter of 1 (the number of machine cycles between the instruction to raise the clock, and the instruction to drop it). The macro now inserts NOPs to make up the total required number of clock cycles.

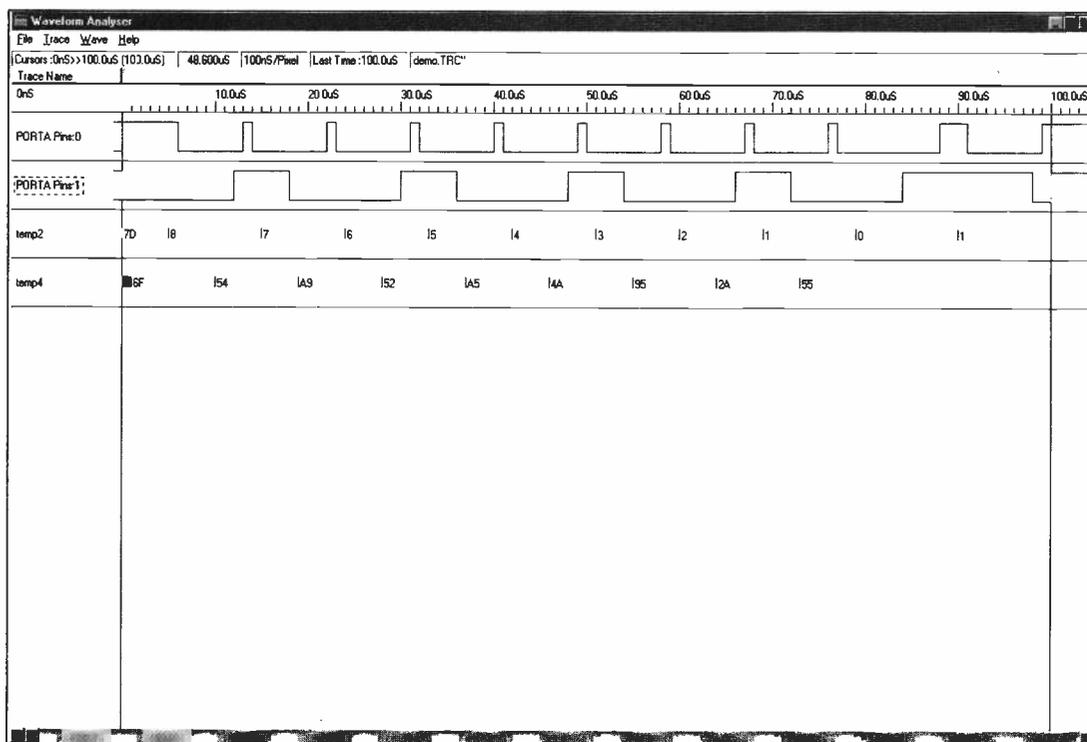

There are two bus read/write call points to be used by user routines:

WriteI2CStart This is the call point which should be used when a start bit is to be generated. Before calling this routine the caller should ensure that the scl bit is high. In a write operation W should hold the value to be written to the bus.

WriteI2CNoStart This is the call point which should be used when no start bit is to be generated. In a write operation W should hold the value to be written to the bus.

The following variables are used by these routines:

- temp2 This variable returns the state of the acknowledgement bit, 0 or 1 after the transfer is complete.
- temp3 This defines the actions to be undertaken on the bus.
- bit 0 Not used
- bit 1 If set, a stop bit is generated after the transfer
- bit 2 If set, an ack is generated by the PIC after the transfer.
- bit 3 If set, a read from the bus is performed, and the read byte is returned in temp4, otherwise the value in W is written
- bit 4 Not used
- bit 5 Not used
- bit 6 Not used
- bit 7 Not used
- W The W register holds the value to be written to the bus when the routine is called.
- temp4 This is the byte which is read from the I²C bus when a read operation is to be performed.

It is the responsibility of the calling routine to ensure that the SDA line is set to read or write depending on the operation to be undertaken. The routine returns with SCL and SDA both set to drive the I²C bus.

quikstop this routine sends a number of clocks and terminates the bus operation with a stop bit. It is used to terminate the bus in the middle of an operation.

Figure 4 shows the waveform generated by the routines when sending the value AA hex to the I²C bus with a start bit and stop bit. This is printed from the PICDESIM logic analyser, and so is an accurate simulation report. The value of the pins of port A, and the variables temp2 and temp4, are also shown as the routine runs. Note that temp2 returns with the value 1, which is read as an acknowledgement bit from the bus.

Note that this routine is running with a PIC clock of 4MHz, and that the total time (measured by the cursors) is approximately 100 microseconds, it can be seen that the I²C bus is not very fast when driven by software! When reading from eeprom, this is as fast as a byte can be read sequentially. Random address reads take up to about 500us.

Initialisation

To initialise the I²C bus the SCL bit must be set to drive, it must also be set to the value 1. As the processor could be reset when the I²C bus is in any state the initialisation routine also writes clocks and a stop bit to the I²C bus. This has no effect normally, but terminates any current I²C operation when the device is reset.

Next Month - Using the routines

Next month we shall look at using these routines to drive 24LC65 devices, to make an EEPROM reader/writer. The LCD module driving article will be held over until the article after that.

Obtaining software

The software listings for this month's articles will be available from the ETI web site after the next article, and will be available on a disk from the author at the end of the series.



Simulation Circuit Capture PCB Autorouting CAD/CAM

Imagine an electronics design system that lets you draw schematics onto the screen and then simulate them at the touch of a button. Now imagine pressing another button and seeing the schematic replaced with a PCB rats-nest. Pressing another button starts the autorouter, and finally you can click on File then Save As to create a complete set of CAD/CAM files.

Too easy? We hope so. Quickroute has always been designed first and foremost to be easy to use. That's why simulation, circuit capture, PCB autorouting and CAD/CAM support are all integrated into **one** package, so that you only have to learn **one** package.


But it doesn't end there. We have included a wide range of features in Quickroute to help you work effectively. For example our Gerber import facility lets you check your CAD/CAM files before sending them to your manufacturer.

We have also introduced a major new PLUGIN module called the SymbolWizard that actually creates custom symbol designs for you. Simply select a template, specify pad and spacing properties and SymbolWizard creates the schematic and PCB symbols for you!

If you would like to find out more about Quickroute, why not call us on FREEphone 0800 731 28 24, or visit our web site on www.quickroute.co.uk. Prices start at under £100 including UK P&P and VAT for a complete system.

**"modern, powerful
and easy to use"**

Elektor Electronics 97

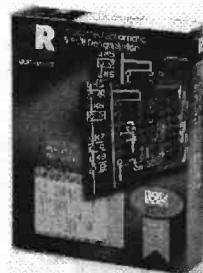

FREEphone

0800 731 28 24


Int +44 161 476 0202 Fax 0161 476 0505

Web www.quickroute.co.uk

30 DAY MONEY BACK GUARANTEE



THE QUICKROUTE

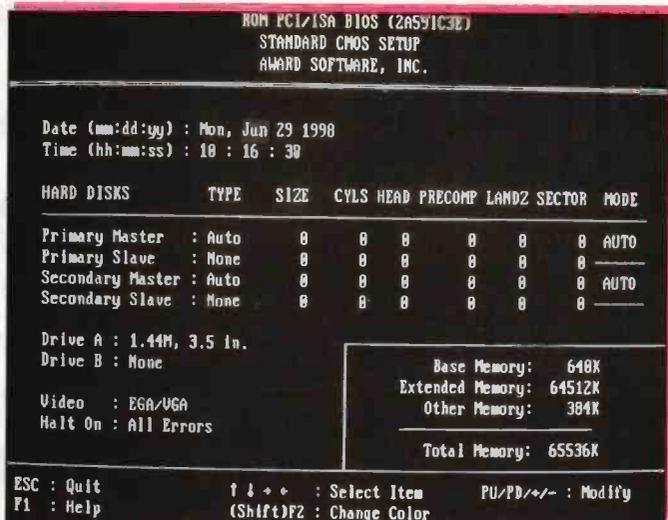

The "Standard CMOS Setup" page of the Award BIOS. This will auto-detect IDE drivers, but you have to set the correct floppy drive type/s.

The microprocessor (under all normal circumstances!) will only fit onto the motherboard the right way round, and the ZIF sockets used on PC motherboards are of a very high quality. If there appears to be a problem with the processor, it is more likely that the motherboard is not configured right. Where appropriate, check that the jumpers or DIP switches have the correct settings for the exact microprocessor you are using. If the computer fails to enter the normal BIOS preliminary routines and just beeps at you, some form of memory failure is the likely culprit. Study the section of the motherboard manual that deals with memory to make sure that you are not trying to use a memory arrangement that the motherboard can not handle. Remember that SIMMs, unlike DIMMs, must normally be used in pairs. If you are using a single one pair of SIMMs they might work properly only if they are fitted in the appropriate pair of sockets (usually the bank 0 sockets). If the motherboard has provision for both SIMMs and DIMMs it will probably not be possible to use both types together, or one bank of SIMMs may have to be left unused.


The most likely cause of memory problems is that one or more of the modules is not fitted into its holder correctly. Even some of the more up-market motherboards have quite crude memory sockets that make it difficult to fit or remove the

modules. Make quite sure that the memory modules are all fitted right down into their holders at both ends. In theory it is not possible to fit any memory modules around the wrong way, but in practice some SIMMs seem to fit either way round into their holders, however, on close inspection a module the wrong way round will be clearly off-centre. Whenever memory problems are suspected, it is probably worthwhile removing all the memory modules and re-fitting them. This often clears the problem.


The BIOS

Many would-be upgraders and PC builders are put off by worries about dealing with the BIOS (basic input/output system). In early PCs the BIOS Setup program was run from a floppy disk, and stored only a few items of information in the battery-powered CMOS ram, such as the time, date, types of disk drive fitted, and the amount of memory. These are still stored in the battery-backed memory of the computer, but so are dozens of other parameters. It is this multitude of settings that is so daunting for first-time users. However, the BIOS defaults should ensure that the PC works reliably and reasonably quickly, and you do not have to deal with things like the memory timing. Nowadays the BIOS often detects the drive types, etc., leaving you nothing to do except enter the correct time and date.

- **Cables can easily become disconnected as you connect up the other cables. Often the connector will not pull completely free, giving no indication that all is not well.**
- **In theory it is not possible to fit any memory modules around the wrong way, but some SIMMs will "fit" incorrectly either way round into their holders**
- **Nowadays the BIOS often detects the drive types, leaving you nothing to do except enter the correct time and date**
- **If you like trying to tweak things for optimum performance you can experiment with the ram and I/O timing settings.**
- **Although the new hard disk will be low-level formatted, it needs high-level formatting and the operating system added before it will boot**
- **Life will be much easier if you set up the disk correctly at the start**
- **Microsoft does not allow Windows 98 to be sold on its own, and it can only be obtained with some kind of hardware**
- **In Windows 98 there is now a conversion utility to make the change from FAT16 to FAT32.**

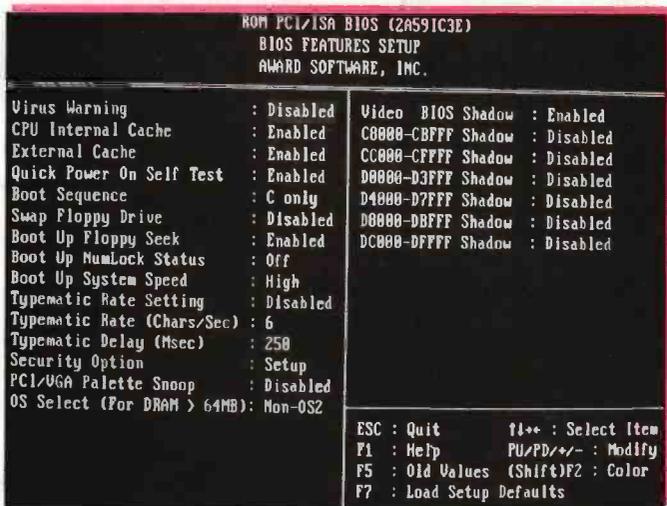

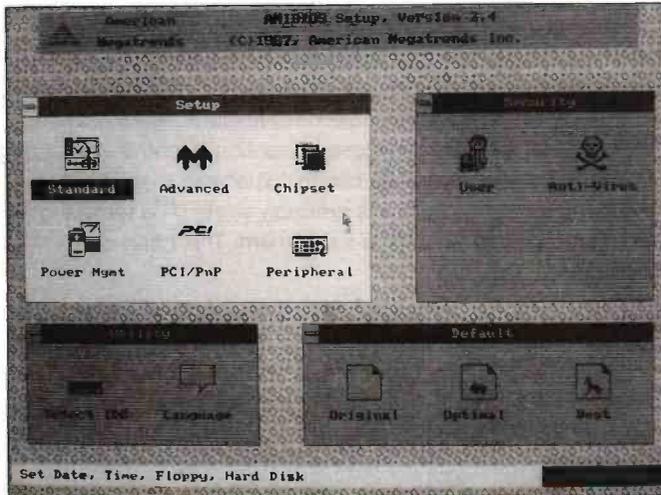The BIOS Features Setup enables you to select the boot drives and search sequence. As with other sections of the BIOS, the default settings should give good results.



The modern AMI Setup programs can be controlled using a mouse. The "Standard" section is the one used to set the time, date, and so on

Now that virtually every motherboard has its own custom BIOS, a custom Setup program is needed to handle it correctly. The Setup is normally in an eeprom on the motherboard, and is activated by pressing the delete key while the BIOS is going through its start-up routine. An on-screen message normally tells you which key to press when this stage of the start-up routine has been reached. BIOS Setup programs vary somewhat depending on the age of the motherboard and the BIOS manufacturer. Most can only be controlled via the keyboard, and some basic on-screen instructions provide details of the key functions. Some recent AMI BIOS Setup programs will detect a mouse. The number of parameters controlled by the BIOS is now so great that the Setup program invariably divides then into several categories.


The most important category is the standard CMOS set-up. This deals with traditional BIOS parameters such as the drive types, time and date. Most of this is perfectly straightforward, and only the IDE devices are likely to give any problems. Various parameters must be entered for the hard disk drive/s, and the manual for each drive should give the appropriate BIOS settings. Any modern BIOS should be able to automatically detect the drive types.

There are two ways of handling this. If you select "auto" as the drive type, the drive will be automatically detected and the appropriate parameters entered into the BIOS each time computer is booted up. The only problem with this method is that it can extend the boot-up time quite significantly with some drives. The alternative is to go into the auto-detection routine, which tests each of the IDE devices and places suitable parameters into the BIOS. This is probably the better option, as it should ensure that there is no boot-up delay.

There may be a BIOS setting specifically for CD-rom drives, but it is often absent. Selecting "auto" is the easy solution to the problem, but with some drives it produces a long boot-up delay, and is not always reliable. Again, the better option is to use the auto-detection routine so that suitable parameters are entered into the BIOS. These settings have no real significance for a CD-rom drive, and the auto-detect facility will probably just enter zero for each parameter.

Other BIOS settings

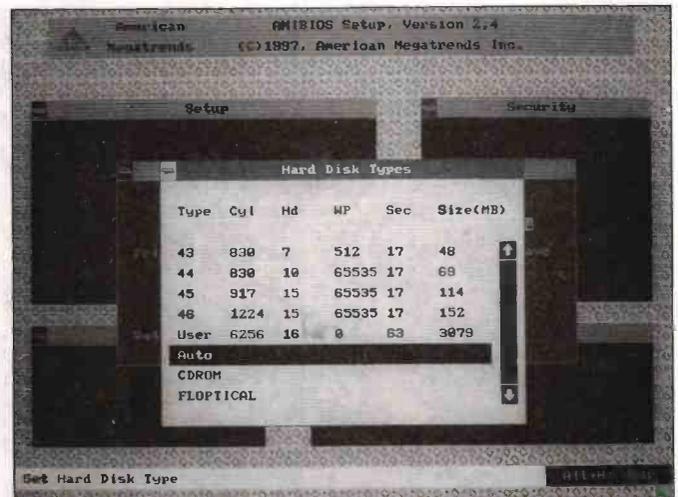The only other section of the BIOS that may need your intervention to get satisfactory results is the one that deals with memory. This will be called something like "Chipset Features", and by default it will probably have an automatic configuration



Selecting the drive type with the AMI Setup program. Forget the 40 or so predefined drive types. Select Auto, or user if you want to enter the correct figures yourself

enabled. On most recent motherboards this will detect the type of memory and set the BIOS parameters accordingly. The BIOS is not able to detect the ram speed, and has to be rather conservative. It will probably set a ram speed of 70 nanoseconds, which is suitable for fast page ram. If you are using the EDO or SDRAM varieties this should be changed to 60ns. It may be necessary to tell the BIOS which type of ram is in use, but with most modern types this is unnecessary. If you like trying to tweak things for optimum performance you can experiment with the ram and I/O timing settings. The usual way of doing this is to try various settings, using a speed test program to check the system performance each time a change is made. Some settings that give fast operation may also give poor reliability. It's a matter of finding settings that give both speed and reliability.

It is worth looking through the various options available via the BIOS Setup program, as some of these allow some customisation. For example, you can normally select whether "Num lock" is on or off after boot-up, as well as which drive/s are used during the boot-up sequence. Many modern motherboards have a sensor that monitors the CPU temperature and sounds an alarm or shuts down the computer if a certain threshold temperature is exceeded. The BIOS Setup program may offer a range of threshold temperatures, and may even tell you the current CPU temperature. Perhaps more usefully, the section dealing with the on-board serial and parallel ports enables you to select the port addresses and interrupt numbers. This can sometimes help avoid conflicts with expansion cards such as an internal modem. In the case of the parallel printer port you can also select its operating mode. This may default to the standard (output only) mode, and will probably have to be changed to EPP or ECP operation in order to work properly with a modern printer or a scanner.

There is usually a BIOS setting that enables or disables support for Plug and Play operating systems. On the face of it, this feature should be enabled if you are using Windows 95 or 98. In practice, there can be the odd problem if this support is enabled, and it is safer to leave it at the default "off" setting.

There will almost certainly be a facility for low-level formatting a hard disk drive. Modern hard disks are supplied with the low-level formatting already completed, and you should not attempt to format them with this program. There will also be an option that enables the BIOS to be returned to its default settings. This is useful if you should tinker a little too much and completely scramble the settings.

Speed reading

There can be problems when dealing with the UDMA33 hard disk interface. This is an improved version of the EIDE interface, which is itself an upgraded version of the original IDE interface. EIDE and IDE drives are fully compatible with the UDMA33 interface, and UDMA33 drives are fully compatible with the earlier interfaces. If you upgrade the motherboard to one that has a UDMA33 interface, but you continue to use your old drive, there will be no improvement in drive performance. Similarly, upgrading to a UDMA33 drive will not bring any major improvement in performance if the motherboard has only one of the earlier hard disk interfaces. To get the higher speed of a UDMA33 drive you require a motherboard and hard drive that both support this interface. Additionally, the BIOS must also support the UDMA33 interface, but if the motherboard supports this feature it would seem reasonable to assume that the BIOS will as well. The only other requirement is that the operating system you are using supports this interface and that it is equipped with a suitable driver. If you do not already have a suitable driver, a Windows 95 driver is apparently available from the Intel website <http://developer.intel.com/design> (look for the file called SETUPEX.EXE). However, a suitable driver should be supplied with the hard drive, or (more probably) with the motherboard.

UDMA33 hard disk drives are normally trouble-free when installed in a new computer, but not always when installed as an upgrade along with a new motherboard. The problem seems to be that Windows 95/98 does not automatically remove old drivers when installing new ones. This can lead to conflicts between the new and old drivers. At boot-up the operating system is likely to play safe, and revert to a basic 16-bit MS-DOS driver that will provide relatively poor performance. In theory, correct operation can be obtained by going into the Control Panel, then System and Device Manager. Select the offending drivers, delete them, and reboot the system. In practice this will not always work, because the new drivers may not have installed properly. If there are still some of the

dreaded exclamation marks against the drivers in Device Manager, then all is certainly not well. Deleting the damaged drivers, rebooting, and then doing any necessary re-installation may put things right. In practice, you may have to delete and reboot repeatedly until everything sorts itself out. (This is known as the "try everything until it works" method, and seems to occur in computer troubleshooting up to very high levels.)

There can sometimes be problems with IDE devices for no apparent reason. This is probably due to obscure compatibility problems between certain makes of hard drive and CD-rom drive. It is most likely to occur when trying to use old and new hard drives together, but it can also occur when using a UDMA33 hard drive and a CD-rom drive on the same IDE interface. The CD-rom may fail to work at all, or can work in an erratic fashion. In either case, simply operating the incompatible drives on separate IDE interfaces will usually clear the problem.

Beating the system

One problem with building a new PC from scratch or undertaking a major upgrade that includes a new hard disk is that the completed PC usually needs some further work before it is fully operational. Although the new hard disk will be low-level formatted, it still requires high-level formatting and the operating system to be added before you can boot from it successfully. Having the disk supplied with the low-level formatting completed saves a fair amount of time, and it also solves that old problem of the computer tending to hang-up at switch-on with a totally blank hard disk connected. The default BIOS settings will cause the computer to attempt to boot from floppy drive A before trying the hard disk, so there should be no problem in booting from a system disk in drive A. If the hard disk drive is supplied with partitioning and formatting software, it is probably best to use that rather than the DOS programs. Follow the instructions supplied with the software and you should soon be able to boot from the hard drive successfully. Otherwise, the MS-DOS/Windows 95/98 FORMAT and FDISK programs should be copied to the boot disk.

Things are unlikely to be much more difficult using the DOS programs. FDISK is run first, and this is used to partition the disk. The menu system makes it easy to create or remove partitions. Newcomers to PC construction sometimes make the mistake of not using FDISK because they only require a single partition. This will not work because the disk cannot be formatted at all until it has been partitioned with FDISK. There must be an active partition for the format program to work on, and you must use FDISK to set the whole disk as a single partition before it can be formatted. Depending on the vintage of the DOS version you are using, the maximum size for a single partition may be 2.1 GB.

Even if it is possible to set a large hard drive as a single partition, this may not be the best way of using your disk drive, and it is worth giving some thought to the way in which the computer will be used before partitioning the disk. There are programs that enable the partitioning to be altered

The image shows a BIOS setup screen with the following text:

```
ROM PCI/ISA BIOS (2A591C3E)
SeeCPU & CHIPSET SETUP
AWARD SOFTWARE, INC.

Auto Configuration      : Enabled
DRAM Timing             : 60ns
DRAM Leadoff Timing     : 18/6/3
DRAM Read Burst (EDO/FP): x222/x333
DRAM Write Burst Timing : x222
Fast EDO Lead Off       : Enabled
Refresh RAS# Assertion : 4 Clks
Fast RAS To CAS Delay   : 3
DRAM Page Idle Timer    : 2 Clks
DRAM Enhanced Paging    : Enabled
Fast MA to RAS# Delay   : 2 Clks
SDRAM(CAS Lat/RAS-to-CAS): 3/3
SDRAM Speculative Read  : Disabled
System BIOS Cacheable  : Disabled
Video BIOS Cacheable   : Disabled
8 Bit I/O Recovery Time : 1
16 Bit I/O Recovery Time : 1
Memory Hole At 15M-16M : Disabled
Specific PCI 2.1 Transfer: Disabled

Spectrum Spread         : Disabled

Flash BIOS Protection  : Disabled
Hardware Reset Protect: Disabled
***** CPU Setup *****
CPU Type                : Intel P55C
User's favorite         : Disabled
CPU Speed               : 280 (66*3) 2.8U

ESC : Quit      F10 : Select Item
F1  : Help     PU/PD/+/- : Modify
F5  : Old Values (Shift)F2 : Color
F7  : Load Setup Defaults
```

By default the DRAM timing will probably be 70ns. Modern ram can use the 60ns setting.

ROM PCI/ISA BIOS (2A59IC3E)
 INTEGRATED PERIPHERALS
 AWARD SOFTWARE, INC.

IDE HDD Block Mode	: Enabled	Onboard Parallel Port	: 378/IRQ7
IDE Primary Master PIO	: Auto	Parallel Port Mode	: ECP+EPP
IDE Primary Slave PIO	: Auto	ECP Mode Use DMA	: 3
IDE Secondary Master PIO	: Auto	USB Keyboard Support	: Disabled
IDE Secondary Slave PIO	: Auto		
IDE Primary Master UDMA	: Auto		
IDE Primary Slave UDMA	: Auto		
IDE Secondary Master UDMA	: Auto		
IDE Secondary Slave UDMA	: Auto		
On-Chip Primary PCI IDE	: Enabled		
On-Chip Secondary PCI IDE	: Enabled		
Onboard FDC Controller	: Enabled		
FDC Write Protect	: Disabled		
PS/2 mouse function	: Enabled		
Onboard Serial Port 1	: 3F8/IRQ4	ESC : Quit	F10++ : Select Item
Onboard Serial Port 2	: 2F8/IRQ3	F1 : Help	PU/PD/+/- : Modify
COM2 Mode	: Standard	F5 : Old Values (Shift)F2	: Color
		F7 : Load Setup Defaults	

The default "Integrated Peripherals" settings should give good results, but you may need to change the printer port mode.

without wiping the disk and starting from scratch, but they are not cheap and do not generally guarantee that there will be no loss of data. Life will be much easier if you set up the disk correctly at the start.

Once the required partitions have been set up on the disk you should format them. The active partition is the one that the computer will boot from, and is normally drive C. This is formatted using the FORMAT C: /s command so that the system files are copied to drive C and it is made bootable. Alternatively, do a straightforward format of drive C and use SYS.COM to transfer the system files to drive C. If there are any other partitions they will be drives D, E, etc., and they must be individually formatted. Of course, you do not need to boot from these partitions and the system files are not copied to them. It should be possible to boot from the hard drive once the formatting has been completed.

These days most PC users run Windows 95 or 98, and putting MS-DOS onto the disk is really just a first step in getting Windows installed. In the unlikely event that you have the floppy disk version of Windows 95/98, you should first install the mouse driver, and then run the Windows Setup program to install Windows onto the hard disk. With the CD-ROM version you must first install the mouse driver and the CD-ROM driver. Some new CD-ROM drives do not make any mention of MS-DOS compatibility on the box, but in most cases suitable drivers are actually included. If the CD-ROM drive does not include MS-DOS drivers it is necessary to resort to a generic driver. No doubt such drivers can be purchased somewhere, but at present I am only aware of one solution to this problem: use another computer to make a Windows 98 recovery disk. This offers the option of CD-ROM support during the boot-up process.

With the mouse and CD-ROM drive operational, you can then run the Setup program on the Windows 95/98 CD-ROM and install the operating system. This is largely automatic, and the user has to do nothing more than answer a few simple

questions and follow a few basic instructions. If you have an upgrade version of Windows 95 or 98, note that you do not have to install the old version first and then upgrade it. The full version of Windows is included on the upgrade CD-ROM or disks, and this can be installed onto a "clean" hard disk. During the installation process you will almost certainly be asked to prove that you have something to upgrade by inserting the disk containing the old Windows Setup program into the appropriate drive. Do not throw away, give away or recycle your old Windows Setup disk!

Buying problems

There is no need to buy an operating system if you are upgrading an old computer,

or scrapping an old machine and building a replacement. It is quite legitimate to use the old operating system on a new or upgraded computer, because you will still be running just a single copy of it. The situation is different if you are building a computer from scratch, and to be legitimate you should buy an operating system for the new PC. Microsoft does not allow Windows 98 to be sold on its own, and it can only be obtained with hardware. There is a "get out clause" here, because "hardware" does not necessarily mean a complete computer system. Therefore, when buying a motherboard and processor, or perhaps just a hard disk drive, you may also be able to obtain the full version of Windows 98. The alternative is to buy Windows 3.11/MS-DOS 6 and an upgrade to Windows 98. In theory this should give a total cost that is about the same as buying the full version of Windows 98, but in practice it could well cost more.

FAT chance

FAT16 is the 16-bit disk filing (File Allocation Table) system used by MS-DOS and Windows up to the original version of Windows 95. This was still the default disk filing system in the later versions of Windows 95, but from OSR2 onwards there was some support for the improved 32-bit FAT32 filing system. This support has been improved in Windows 98, and there is now a conversion utility that makes the change from FAT16 to FAT32. For most users it is well worthwhile doing this. FAT16 can only handle large disk partitions by using a large sector size. Unless a large hard disk is split into lots of small partitions this results in a sector size of 32k. The important factor here is that the filing system only allows one file to be assigned to each sector. This means that something like a 100-byte batch file will occupy some 32k of disk space! In theory an average of about 16k per file will be wasted, but due to the large number of small files used by most Windows programs the real figure seems to be about 20k or so. FAT32 permits a sector size as small as 4k to be used, which greatly reduces the

amount of wasted hard disk space. In fact it seems to give an effective increase in capacity approaching 20 percent. Programs should also load slightly faster.

The conversion utility is accessed via Start, Programs, Accessories, System Tools, and then selecting Drive Converter (FAT32). The conversion process is largely automated and requires little user input. Read the warnings in the Windows 98 manual before going ahead with the conversion. The drawbacks are mainly minor, but users of dual-boot systems that can boot either Windows 98 or their old version of MS-DOS will find that the MS-DOS boot option is no longer available. The "real" versions of MS-DOS are not compatible with FAT32. The Windows 98 version will still be available though, either via the MS-DOS prompt option in the Programs menu, or Start, Shutdown, and Restart Computer in MS-DOS Mode.

Spitting image

You may wish to copy the image of an old disk drive to a new drive so that all your old programs run exactly as they did before, complete with any customisation. Unless you are unlucky it should be easy enough to run the old drive alongside the new one, and copying files from one drive to the other is then quick and easy.

However, simply copying programs and their support files across to the new drive will not give the desired result with Windows. Unless the programs are properly installed, Windows will not know they are there and they will probably not run properly. It is possible to copy an image of the old disk across to the new disk, complete with all the system files. It should then perform just like the old drive, booting-up and running all the programs properly. There are utilities available that give


varying degrees of help with this process. This may seem like the ideal way of getting your new PC up and running, but I would certainly recommend taking the longer route of reinstalling everything "from scratch", and then copying across your data and customisation files.

This will take longer, but it is likely to provide a better installation. One major drawback of Windows is that it tends to get clogged up with obsolete files over a period of time. Making an exact copy of an old hard drive retains all this clutter. Reinstalling everything from the beginning will be time consuming, but it is a good opportunity to get the computer "cleared out" and working efficiently.

USB

Although USB (universal serial bus) ports have had little impact yet, it seems likely that this interface will be central to computing soon. Most modern motherboards have a USB port, but a connector and lead is usually an optional extra. One reason for the lack of use so far is that USB ports tend to give problems with Windows 95. If you go into the System Manager there will probably be an entry for the USB port, but it will almost certainly be accompanied by an exclamation mark and warning notices to the effect that it is not installed properly and is not working. Even when using the last version of Windows 95, getting the USB port to work reliably seems to be problematic. Probably the only practical solution is an upgrade to Windows 98. This operating system will install proper support for the USB port, and the exclamation mark in Device Manager should miraculously disappear (!)

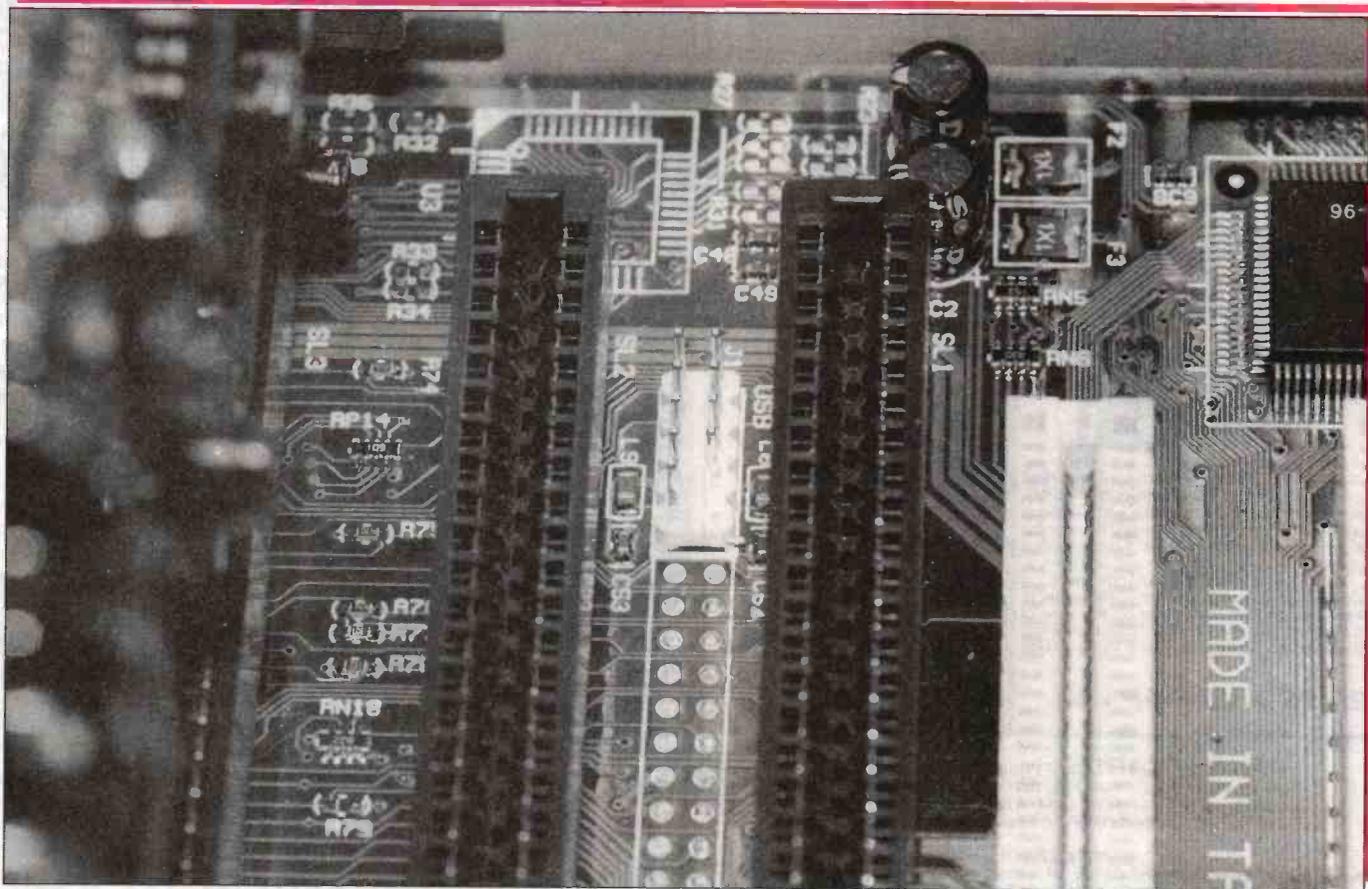Some more details on upgrading a modern PC system will appear in the next issue of ETI.



Most modern motherboards have a USB port, but you may have to delve between expansion slots to find it. You may also need Windows 98 to make it work

CROWNHILL ASSOCIATES LIMITED

The Old Bakery, New Barns Road,
Ely Cambs. CB4 7PW

Tel: +44 (0)1353 666709 Fax: +44 (0) 1353 666710

Low cost professional quality Smart Card Systems

CHIPDRIVE EXTERN

Intelligent programmer for Smart Cards using the International Standard T=0 or T=1 protocols also Memory and Secure Memory using PC, 2-wire & 3-wire interfaces

Supplied with software to read and write to most popular secure smart cards, inc GSM, PAY PHONE and ACCESS CONTROL cards.

T=0 or T=1 @ 3.579MHz
RS232 @ 9600 -11500 bps

£69 + VAT

Internal Supply / Ni-MH

£7.50 P&P

Size: 100x70x80 mm
Weight 660 Gram

Supplied with CardServer API for easy development of SmartCard Applications using Visual Basic, Delphi or C++
Supplied with Sample Memory cards & Secure Smart cards

CE Compliant



Chip Drive Intern

3.5" floppy bay version of the CHIPDRIVE.

Applications are available to provide SmartCard controlled access of data on Hard drives or "PC-LOCK", to control access to the whole PC Fully Compatible with TOOLBOX for systems development. Supplied with cardserver.dll API

£85 + £5 P&P + VAT

CHIPDRIVE extern



NEW CHIPDRIVE - micro

Fully Compatible with TOOLBOX for application development. Featuring the same functionality as Chip Drive Extern but in a small neat low cost package, similar in size to a smart card. Supplied with cardserver.dll API

£65 + £5 P&P
+ VAT



Most popular smart cards are plastic, the size of a credit card, with an embedded microprocessor containing an operating system and erasable non-volatile memory.

Physical protection against unauthorised tampering with the card is provided through the following scheme:

The microprocessor and memory are created as a single chip. This ensures there are no data paths that can be monitored or probed. This chip is connected to a thin circuit board and encapsulated with an epoxy. The "module" is then glued within a well milled into the plastic card. This prohibits physical access to the microprocessor and provides a more durable medium than magnetic stripe cards.

ChipDrive Developer Kit
micro, sample cards and Toolbox
£99.95 + P&P + VAT

<http://www.towitoko.co.uk>

<http://www.crownhill.co.uk>

<http://edsim.cambs.net>

TOOLBOX



Driver and application software is available for the CHIPDRIVE family of terminals including the command set DLL for Windows 3.11/95/NT, easy to use 16 and 32 Bit DLLs with just one function call to the "CardServer", a powerful Background task which relieves the application programmer from device and card administration. Featuring automatic protocol and card type detection. Allowing several applications to access one terminal dependent on the type of card inserted. Supplied on CD ROM containing cardserver.dll, applications and source code examples.

£29.95 + £5 P&P + VAT

The microprocessor operates under control of a "built in" program called an operating system. A serial Interface - which makes it impossible to access the memory directly - is employed to communicate with the card. An ISO (International Standards Organization) protocol is used to exchange commands and data with the card.

Finally, Holograms, signature stripes, photos, etc can be applied to the card for additional security. And the card can be custom printed with your artwork.

Crownhill can supply OPEN ARCHITECTURE cards, that will allow you, the end user to create your own operating system, to control access to the EEprom memory of up to 64Kbits (8Kbytes) in size. Crownhill have off the shelf operating systems for Control access. Electronic purse and Portable Document applications. Others can be written to your specification.

SMARTCARDS Available from Stock:

GemPlus, Atmel, Xicor, Siemens, SGS Crownhill and more.....
SLE4442,4432,4418,4428,4404. AT88SCxx, AT24c01-16.
GPM103,GFM1K,2K,4K,GPM416 Phone Cards, Loyalty Cards

THE SMARTEST SOLUTION

Crownhill can offer a broad range of smart cards from just £1.00. and Smart Card sockets for just £1.45 ea. PIC Microchip based Smart Cards now available at just £4.50 ea.....DEVELOP YOUR OWN SMART CARD!
Crownhill can supply over 150 different types of IC from more than 12 silicon suppliers, which can all be incorporated into smart card format. Some cards are available from stock, most are manufactured to the customers' specification.

ELECTRONICS DIRECT

SUBSCRIBE & SAVE WITH ELECTRONICS DIRECT

Our subscription deals just get better and better - no you can save almost £20 if you subscribe today!

ETI, code: 0215

Electronics Today International - The Project Magazine for all Electronics Constructors.

The single source guide to electronics for today and tomorrow, packed with numerous projects for enthusiasts of all abilities.

The detailed features and up-to-the-minute news items keep all readers fully informed of the latest, exciting developments in this ever changing hobby, whilst the equipment reviews ensure that you always know exactly what to buy.

15 issues for the price of 13

UK: NOW ONLY £35.75 YOU SAVE £5.50

Europe: £43.42, Overseas: £47.84, USA: \$79.00

30 issues for the price of 26

UK: NOW ONLY £71.50 YOU SAVE £13.75

Europe: £86.84, Overseas: £95.68, USA: \$158.00.



ACORN ARCHIMEDES WORLD, code: 0215

In the constantly changing world of IT, it is vital to keep abreast of all the latest trends and developments. Of course, this is easier said than done. However, you CAN keep fully informed by reading Acorn Archimedes World, Britain's most respected computing magazine devoted to all Acorn 32-bit RISC OS systems. The wide ranging editorial brings you in-depth hardware and software reviews, evaluates new products and forecasts what will happen next, and includes a dedicated educational section. Each issue also comes with a free cover-mounted disc, often containing complete, usable programs as well as workable and playable demos.

15 issues for the price of 13

UK: NOW ONLY £51.35 YOU SAVE £7.90

Europe: £60.45 Overseas: £66.56, USA: \$109.00

31 issues for the price of 26

UK: NOW ONLY £102.70 YOU SAVE £19.75

Europe: £120.90, Overseas: £133.12, USA: \$218.00



REMEMBER, it's always cheaper to subscribe - and you avoid future cover price increases!

All savings are based upon buying the same number of issues from your newsagent, UK only.

BINDERS

Keep your favourite magazines in mint condition in one of our sturdy binders.

Each binder will hold up to 13 issues.

Code: bind 02

£7.50 U.K. £8.00 Overseas

BINDERS AVAILBALE

● ETI ● ARCHIMEDES WORLD




'Electronics Direct' is the One Stop Shop for all your computing, electronics and amateur radio needs from Nexus Direct. We are offering some sensational deals on Subscriptions, Books & Reader Offers - all available direct by mail order. Remember, all our prices include postage and packing - so there are no hidden extras to add! You can order by phone, fax or use the coupon.

ELECTRONICS DIRECT

Please order all your goods using the coupon below ensuring you fill in all sections OR simply use our order hotline. Thank you.


SAVINGS ON BOOKS

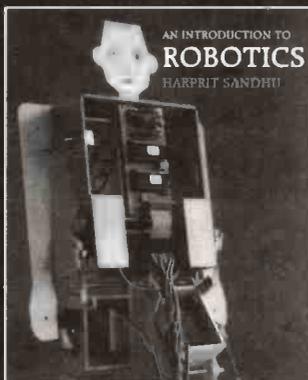

AN INTRODUCTION TO ROBOTICS.

A fascinating and unique book that breaks new ground by exploring the exciting world of robotics in a clear and concise way. Both the theoretical and practical aspects are presented in an uncomplicated fashion using everyday English, which makes this an ideal book for the amateur. Divided into two sections, the first part explains how and why robots work and are controlled, while the second shows you how to make a simple two legged humanoid robot that can be programmed to walk. There are no complicated formulas or equations to grapple with or incomprehensible circuit diagrams to decipher - this robot can be built on your kitchen table and can be run from any personal computer! All you need are model aeroplane servos, a controller, a power supply and some plywood - and all parts are easily available in the UK and the USA. This is a book that will be of interest to modellers and everyone with a fascination for things mechanical and electronic.

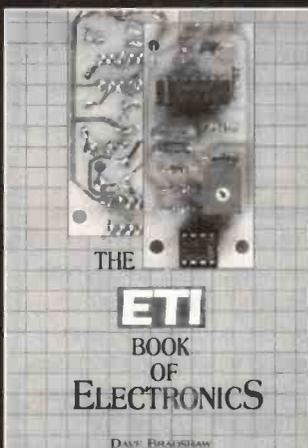
Code: NB299
ONLY £11.95 UK £12.95 Overseas



ETI BOOK OF ELECTRONICS

This is the perfect book for beginners, offering a clear and concise introduction to both the theories and principles of electronics. Each chapter also allows you to put this theory into practice with an easy to follow project to make, including a loudspeaker divider, continuity tester, 'brown-out' alarm, freezing alarm, loudspeaker, mini-amplifier and a burglar alarm.


Code: NB214
ONLY £12.95 UK £13.95 Overseas

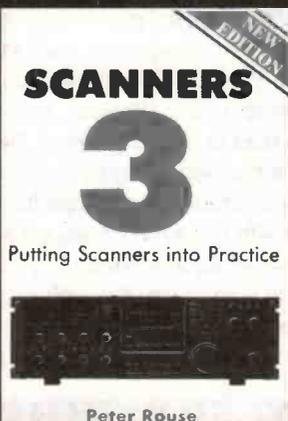

SCANNERS 3 - PUTTING SCANNERS INTO PRACTICE

This is the fourth revised and completely updated edition of Scanners, the complete VHF/UHF radio listeners guide, containing everything you need to know to put your scanner to better use. There is a great deal more information than ever before on frequency listing; in particular, actual frequencies used by coastal stations, airfields and the emergency services. Also included for the first time is a section on the HF (short wave) band as many scanners now cover this range.

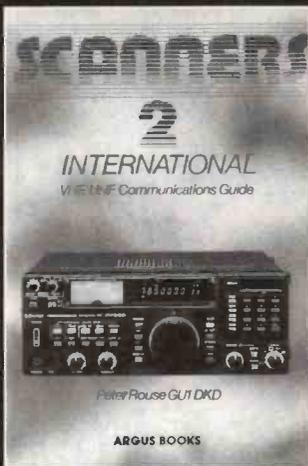Code: NB217
ONLY £11.95 UK £12.95 Overseas



SCANNERS 2 INTERNATIONAL

The companion book to 'Scanners' provides even more information on the use of VHF and UHF communication bands, and gives details on how to construct accessories to improve the performance of scanning equipment. The book is international in its scope and contains frequency allocations for all three ITU regions, including country-by-country variations.

Code: NB216
ONLY £11.95 UK £12.95 Overseas

SUBSCRIPTIONS

Magazine	Code	No. of Issues	Price
.....	£.....
.....	£.....
.....	£.....
Total Subscription Value			£.....

Subscription No. if renewing

READERS OFFERS/BOOKS/BINDERS

Title	Code	Qty	Price
.....	£.....
.....	£.....
.....	£.....
.....	£.....
.....	£.....

Total Order Value £.....

METHOD OF PAYMENT

The total value of my order is £
I enclose a Cheque/P.O. made payable to
Nexus Special Interests Ltd. or please debit my
Mastercard/Visa/AMEX account

Card No. [.....]

Expiry/..... Signature

Your Details

Name: (Mr/Mrs/Miss)
Initial Surname
Address:
.....
Postcode/Zipcode Country
Telephone:

Send to:
Electronics Direct
Nexus House
Azalea Drive
Swanley
Kent
BR8 8HU

Please Note
All prices include P&P where appropriate. All subscriptions start with the first available issue. Every effort will be made to despatch your order within 14 days but please allow up to 28 days for delivery. Individual items may be dispatched separately. These offers are not to be used in conjunction with any other promotion.

Please tick this box if you do not wish to receive direct mail from other companies

ELECTRONICS DIRECT
Express Order Hotline
01322 616300
9am - 5pm Monday - Friday

BOOKS DIRECT

Recruitment Today, Or Which Engineer?

Technical staff shortages there may be, but employers are still looking for a sound skills base when interviewing

Qualified to degree or PhD level in engineering or science..." "significant product development experience ..." "a wide range of technological skills ..." "graduate engineer with 3.5 years' experience ..." "RF engineering" "embedded real-time software ..." "If you are degree qualified OR have relevant experience ..."

Extracts from recruitment adverts in a well-known trade journal around the end of the academic year show that there are any number of large companies falling over themselves to catch the engineering talent now pouring off the educational production lines.

"talented senior development engineer to lead a team ..." *"take our design capability into the next generation ..."* *"pioneering multi-disciplined engineer ..."* *"test, commissioning, support and board layout ..."* *"leading new developments..."* *"Engineers drive our business ..."*

The more elusive creature that employers want to net is the engineer with 3 to 5 years' experience in the specific job slot they need to fill, or a closely related one. That particular trophy is a harder one to find, because engineers with practical qualifications tend to be snapped up the minute they stick their heads out into daylight. For that reason, engineers and technicians with good skills and experience and a flexible attitude may well find adjacent fields open to them - provided the interviewer is convinced that they have what it takes to do the job.


The travelling IEE Engineering Recruitment Show concentrates on experienced engineers and recent graduates. When the show came to Hammersmith, London, we asked a number of the exhibitors what they were looking for, and whether they were finding it.

Up to 10 years

Established in Berkshire in 1998 to manufacture cellular phones under the prestigious **Panasonic** brand name, **Matsushita Communication Industrial UK** is now a thriving part of the Matsushita empire turning over more than £200 million annually, and a major employer in the Berkshire/Oxfordshire area. Their original GSM handheld cellular phone was the first to gain Type Approval in the UK. Having built up their cellular phone line, the company is expanding again and moving into other digital mobile technologies.

Panasonic are looking both for graduates, and engineers with up to 10 years' experience, particularly in RF and software. The company is in an expanding phase, with a high demand for technical people and attracting staff from other large organisations. Salaries, they say, are competitive, and people tend to stay with them. (Retaining well-trained technical staff is a problem faced by nearly all engineering firms in these days of shortages and competition.) They are looking for people with telecommunications expertise - and finding them. Awareness that telecomms is going to be the growth industry for some time to come is high at the moment.

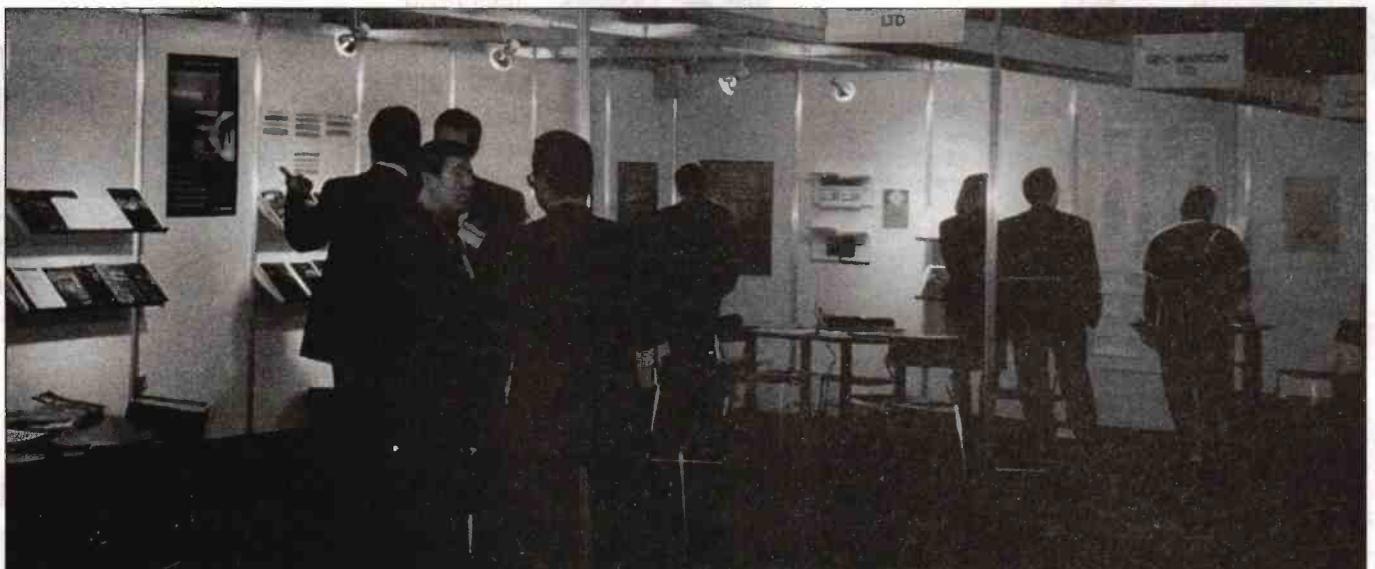How is the company finding the basic skills among recent graduates? The news is good and bad: there is no skills



problem "if you can get the right people". In general, the standards among new graduates is good - but a previous fair produced some very poor applicants, believed to be the unfortunate leftovers from the previous year who had failed to establish themselves in a career in the intervening time. It's a salutary warning that a degree qualification is not an instant passport to success even in these days.

One problem faced by companies recruiting technical staff is that many graduates expect to move quickly into management. Career offices are tending to advise engineers that the management path is likely to be more prestigious and profitable than working at the cutting face. Unfortunately, in the UK this is still true in many cases, but graduates need to know that if they want to work for leading companies, they will progress to management mainly through work on project teams, and then only if they show strong technical competence as well as other qualities.

The Panasonic recruiters always carry out basic tests "because the applicants can't always do them, even though their degree should have covered it." The days when employers could assume that successful students had mastered all the elements of the course passed a long time ago. (A colleague of ours dates it, somewhat bitterly, to the introduction of "new maths" into the school syllabuses and the resulting sidelining of tougher mathematical disciplines in too many cases.) In general, maths is not seen as a major problem, but the weak areas are effectively in the whole educational system, not just in a few applicants. Weakness in essential hard engineering skills like transistor biasing is a problem, "even in First Class Honours" - many students get too focussed on one project and fail to develop a breadth of knowledge and flexibility.

Applicants with very specific experience at top levels are still hard to obtain, and specialised skills tend to be developed in-house.

This is the case in many companies, and there is a problem here for engineers of some years' standing in one project area: they can become overspecialised. It may be better to look for a sideways move every few years to avoid being left behind when demand changes. Panasonic find that the best age range for experienced engineers is between 26 and 35, widely seen as the best compromise between up to date study and experience in the field.

Many companies offer training, but keeping up with changes independently is now an important part engineering at all levels, particularly in the higher salary bands.

Good skills, poor maths

Roke Manor Research were finding a good supply of graduates to interview, but having more difficulty obtaining experienced people in RF and digital signal processing, currently among the most competitive fields. Skills relevant to mobile communications and mobile phones are also much in demand.

Roke have found that graduate applicants are weak in essential maths. A shortage of technical candidates means that candidates are getting onto good courses with two Es at A level, and are failing to deliver in some areas. The recruiters have found that the younger universities and former Polytechnics provide some very good specialised courses at MSc level, but are less reliable at Degree and HNC. Roke tend to concentrate on "traditional good quality universities" which attract higher A level passes and generally provide a good level of skills, but this this is by no means infallible.

The Roke recruiters have no problem with older applicants, and will undertake a certain amount of retraining to get good experienced applicants up to speed in specific skills. They stress that they tend to attract people "in work rather than out of work" - an indication that they are looking for people who are currently active in technical fields, rather than displaced managers and others hoping to join or rejoin a technical career.

The goal of Continuing Professional Development is encouraged but is considered to be a personal matter. Like most large employers, Roke look upon CPD as just one approach to keeping abreast of developments and a useful motivator for the individual, but not as a career qualification. Engineers need to keep up with changes outside their immediate field if they are to compete with more recent trainees, but the skills they can demonstrate are more important to employers than how they acquired them.

The advice at all levels is to "keep flexible" - but not to opt for a broad-based engineering degree. Mixed engineering qualifications spread skills too thinly to produce good results on one of the major engineering fields. Roke would like to see colleges design more

courses in consultation with industry to


create more relevant graduates. There is demand for software skills with direct commercial application, such as embedded systems software. The computer science course at York University was well regarded, as was Manchester UMIST for commercial software.

Biasing matters ...

GEC Marconi were experiencing finding experienced people, particularly in software. The "big shortage area" is in people with 3-5 years' experience. Too many years in one field can be a positive disadvantage: they find that people with more than 10 years' specific experience risk falling behind in other fields and losing their flexibility, so unless their skills are the exact fit to the job requirement they may be less useful than someone with fewer years on the job but more recent training.

Once again, the demand is for "doers, not managers". Embedded software, ADA software, C++, structured design methodologies and digital signal processing are particularly in demand.

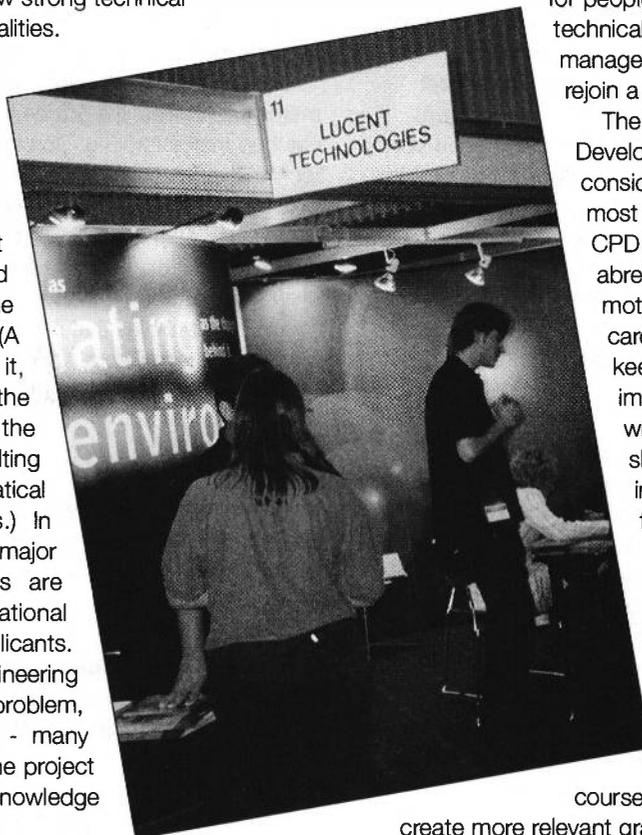GEC says that there is an element of truth about weakness in basic skills. The message is: "biasing a transistor does matter". The engineer must be able to follow calculations even



when using a simulator, and understand the basis of the data generated. The trend towards wide-ranging, mixed media degrees is again judged to be counter-productive. Put bluntly: "We are very rarely interested in them, because they cannot design printed circuit boards." The general degree "dilutes the time spent learning about electronics." People with MBAs and other business qualifications are not required. A good level of management training is available to staff who can do the tech job productively for a number of years.

GEC admits that engineering in the UK still pays less well across the board than some careers because many of the best people are dedicated, but that skills shortages (the Best People are hard to find) are gradually pushing salaries up, particularly in the telecomms field. It is a seller's market for people with good skills.

The **Central Laboratory of the Research Councils (CLRC)** develops very high level instrumentation for test facilities and universities, among others. They are IEE certified for graduate training, and anyone working for them can expect technical training in line with their involvement with high-level research. Unfortunately, one side effect of this enlightened policy is difficulty retaining trained engineers - nearly always a problem for companies that train, even where salaries are good, as younger and more restless employees move on looking for a change of experience and a chance of promotion elsewhere.

However, trainees or no trainees, CLRC still find that technical staff are at their most useful at around 30 - 35 years of age - that desirable time when a combination of training and experience comes into its own.

Software shortage

Lucent Technologies at Swindon are part of one of the largest technology companies in the world and start graduates off at around £18k, with teamwork and product training, and management development for people with aptitude.

@B: Unsurprisingly, with the advantages of a very large, very modern company with a wide spread of interests, they have no trouble attracting good graduates in most disciplines. They are currently looking for electronics, RF and software engineers with telecomms backgrounds. Finding software engineers, "real time and applications", is the biggest problem because the field is expanding faster than the supply of good engineers.

Lucent employ contractors as well as permanent staff, and are keen to convert contractors to permanent if they get on well in the company. They describe their success in persuading good contractors to settle down in one spot as "gradual". The '90s is a buoyant time for contract engineers, especially in software. It remains to be seen how long this remains the case in the 2000s. Lucent uses a recruitment agency, Venus, which determines the company's selection process.

Japanese entertainment electronics giant **Sony** describes its company culture as "easy-going, laid back, but very productive" - rather like the company's legendary Walkman in the '80s. Sony has a very high technical standard, and is looking for graduates in computer science, electronics and micro-electronics. Success in getting the right people is "reasonable - we are not saying it's easy". Finding good experienced people is harder. The company is expanding and there are plenty of vacancies.

Sony's experience with basic skills is "no real problem", but they would like to see people with better grounding in specific technologies. They are definitely looking for graduate skills, particularly C++ and systems engineering at present.

Experienced engineers changing jobs are welcome but the company looks carefully at relevant experience versus salary

expectations. People who have retrained or are moving into a new area should not expect to achieve their previous salary level until they have practical experience in their new field. This advice is almost universal now, but some older engineers still go forth unprepared for the fact that they will have to drop down the salary tree again until they build up a track record in their new field.

In the end ...

A career move more often adopted in the USA than the UK is for engineers to take a year or three out of work in their late thirties or early forties and study for a second degree to update their skills. Americans are used to financing their own education on a shoestring, so this is perhaps not such a shock to them as it is to a Brit suddenly compelled (unless they have an understanding and well-salaried partner) to go back to living on beans and bananas. Nonetheless, the signs are that midlife study will become increasingly important in all professions.

For prospective students who are concerned about their maths capabilities, the advice is: find a college that offers catchup maths tutoring. Don't trade off a college with a good technical reputation for a lesser one with remedial maths, but take the trouble to find out if there is a thorough program of engineering maths at your first choice. It is difficult to top up maths without the help of a tutor, and essential if you hope for even a reasonably high-level career. Nobody who works with figures now believes that it is sufficient to rely on calculating machines or simulators.

Good luck.

Contacts:

Sony: (CVs and covering letter outlining your suitability to) Marc Schonagen, Sony, Jays Close, Viables, Basingstoke, Hants RG22 4SB. Email sony.hr@ccmail.eu.sony.co.jp Web www.topjobs.net

Lucent Technologies: Operations HR Account Manager, Lucent Technologies, Swindon Road, Malmesbury, Wilts SN16 9NA. Tel 01666 832303 Fax 01666 832196 Web www.lucent.co.uk/

or

The Venus Group, Clarence House, The Promenade, Cheltenham GL50 1NW Tel 01242 224333 Fax 01242 224999 Email: Christie@venus-group.co.uk Web www.venus-group.co.uk

CLRC: Application forms and information from: Recruitment Office, Personnel Division, Rugherford Appleton Bavoratory, Chilton, Didcot, Oxfordshire OX11 0QX. Tel 01235 445435 (ansmac) quoting reference VN1647/98. Web www.cclrc.ac.uk Technical queries: Steve Quinton tel 01235 445534 Email s.p.h.quinton@rl.ac.uk

Roke Manor Research: CV to Roke Manor Research Ltd., Roke Manor, Romsey, Hants SO51 0ZN Email chris.prince@roke.co.uk Web www.roke.co.uk

Panasonic: CV to Mark Robinson, Matsuhite Communications Industrial UK Ltd., Daytona Drive, Colthrop, Thatcham, Bers RG19 4ZD. Tel. 01635 871466.

GEC: Many different establishments: check recruitment advertising in trade journals or your college library.

30% discount for ETI readers on 30V 5A and 50V 3A power supplies



305LDD 30V 5A £139 inc vat & delivery
503LDD 50V 3A £139 inc vat & delivery

Features

- Twin 3.5 digit lcd displays
- Coarse & fine voltage control
- Over current alarm
- Floating outputs
- Low noise & ripple
- Rugged steel case
- 12 month guarantee
- Service manual available



Vann Draper Electronics Ltd
The test & measurement specialists
www.vanndraper.co.uk

Vann Draper is offering over 30% discount to readers of Electronics Today International on two of their digital display power supplies.

The 305LDD and 503LDD power supplies normally sell for £186.83 and are available to readers of ETI magazine for just £139 fully inclusive of vat and delivery.

Both power supplies are delivered ready to use complete with mains lead, operating manual and a 12 month guarantee.

To order simply post the coupon to Vann Draper Electronics Ltd at Unit 5, Premier Works, Canal St, South Wigston, Leicester LE18 2PL. Alternatively tel 0116 2771400, or fax 0116 2773945. or E-mail sales@vanndraper.co.uk

Key specifications

- Output rating : 0-30V 5A (305LDD), 0-50V 3A (503LDD)
- Output ripple : Typically 10mV
- Load regulation : Typically 0.2%
- Digital display : 2 x 3.5 digit, accuracy 0.1 decimal digit
- Protection : Continuous short circuit, overload alarm
- Size & weight : 310 x 260 x 120mm, 5.5kg
- Power requirements : 220/240Vac 50/60Hz

Use this coupon for your order

Please supply me :

- 305LDD power supply(s) at £139 inc vat & del
- 503LDD power supply(s) at £139 inc vat & del
- Service manual(s) at £15 inc vat & del

Name :

Address :

Tel no :

Total £.....

Cheques payable to Vann Draper Electronics Ltd
Or debit my visa, master, access or switch card :

Card type :

Card No :

Expiry date :

Switch iss no :

Signature :

Overseas readers can still obtain this discount but carriage charges vary according to country. Please telephone, fax E-mail or write to Vann Draper.

18-Channel Infra-red Remote Controller

By Pei An

This article describes a general purpose infra-red remote receiver which could be implemented in equipment where remote control would be desirable. Its partner is a handset transmitter using the BL9148/BL9150 chipset.

The remote controller consists of a receiver board with 18 remotely controlled digital outputs (figure 1), which responds to a transmitter handset with an 18-key keypad. The handset requires two 1.5-V AA size batteries. The maximum control distance is up to 10 meters. The handset unit or the chips are available from the author.

Today's television sets, VCRs, satellite decoders, hifi, CD players etc. are expected to have remote control facilities. There are also emerging applications such as domestic lights, garage doors, curtains, air conditioners, heating appliances and computers, and so on. It won't be long before we can choose whether or not to walk across the room at all.

With a multi-channel controller like the one described here there are many more complex control opportunities than with a simple one.

Output waveforms

As has been mentioned, there are 18 controlled outputs on the receiver board. They have three output waveforms (figure 2).

Among the 18 outputs, ten of them have a single pulse output form (SP, key 7 to key 16). When one of these buttons on the remote handset is pressed, one infra-red emission cycle is produced by the handset. On the receiver side, a single low-to-high-then-low pulse is produced at the corresponding output.

Two channels have a *latched pulse* output waveform (LP, key 17 and key 18). When a button is pressed, the handset produces one infra-red emission cycle. On the receiver side, the corresponding output changes the logic status from one to the other.

Six channels among have a *continuous high pulse* output waveform (CP, key 1 to key 6). When a button on the handset is pressed continuously, the handset repeatedly produces the infra-red emission cycle. On the receiver side, the corresponding output goes from logic low to logic high state and stays high as long as the button is pressed.

These output forms can be used for different applications. Some suggestions are given lower down this article.

How It works

Figure 3 illustrates the principle of the remote control system. The handset consists of an 18-key keypad, a key encoder IC (BL9148), an infra-red light emitter and its driver (figure 3a). The key encoder detects which key is pressed, then outputs a stream of digital

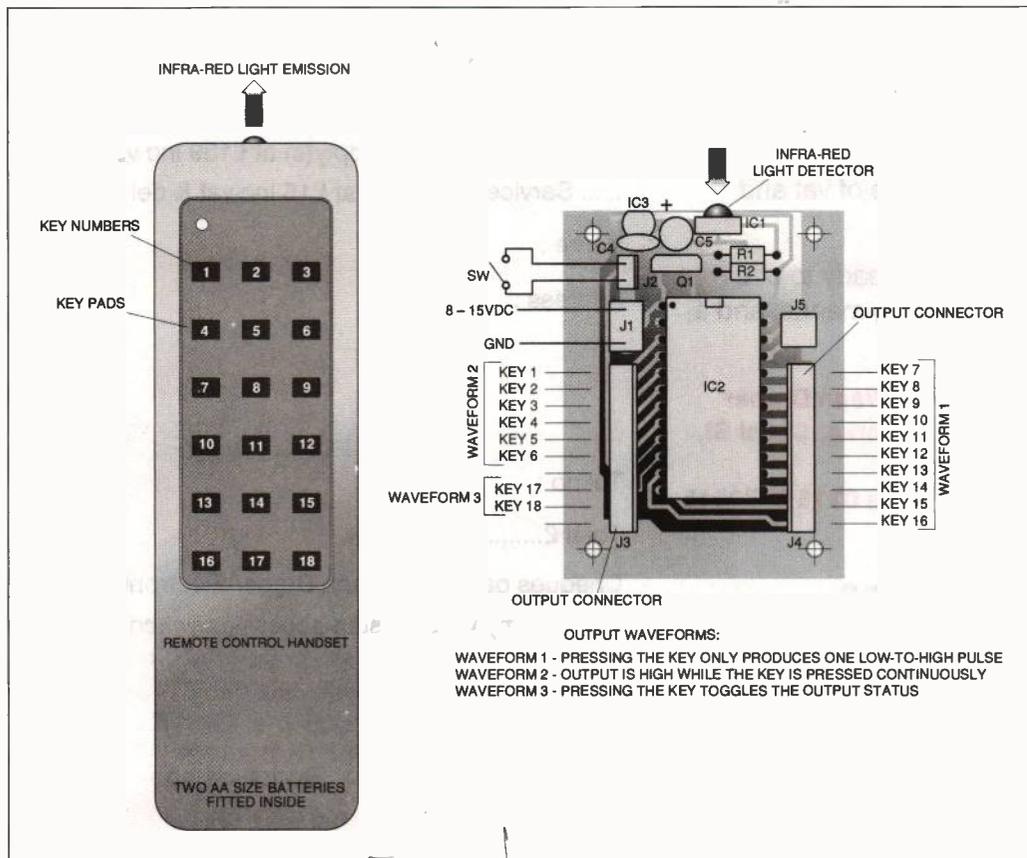


Figure 1: the 18-channel infra-red remote control system

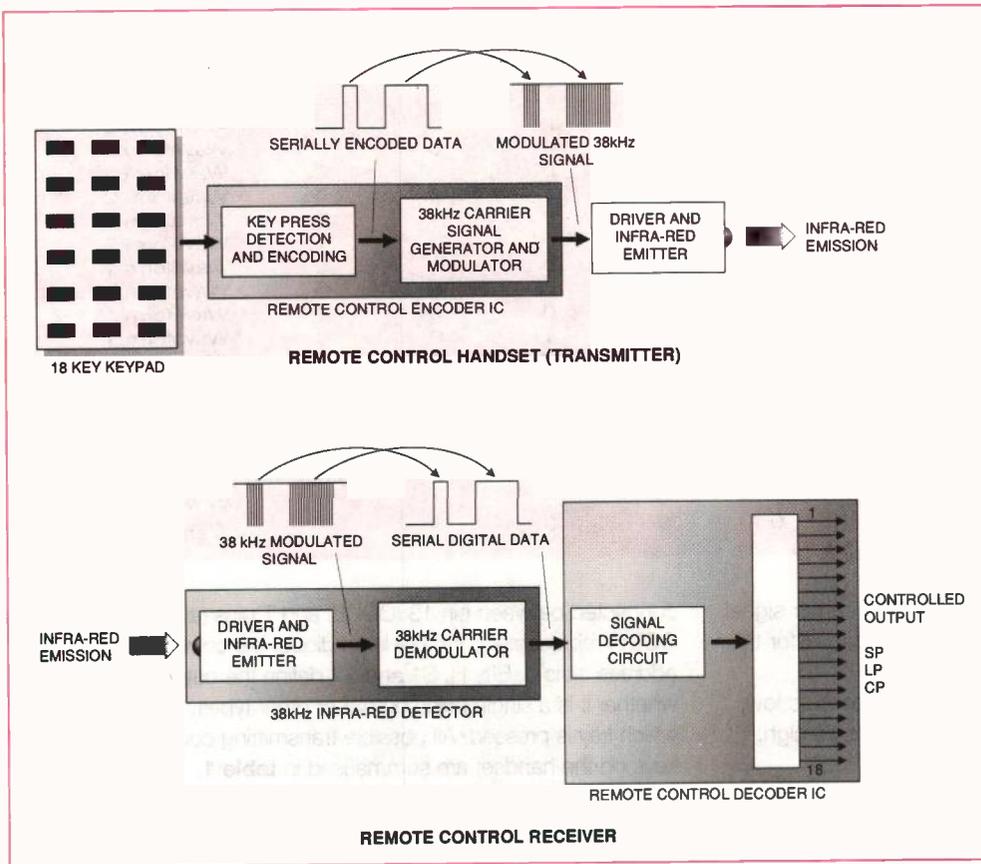


Figure 3: the principle of a typical remote control system

data (a stream of "0" and "1") which is unique to the pressed key. This data modulates a 38-kHz carrier signal. When the data is 0, no carrier signal is produced. When it is 1, the 38-kHz carrier signal is produced. The signal is amplified by the infra-red LED driver and is transmitted by the LED emitter.

The receiver board consists of an infra-red detector which is tuned to receive only the 38-kHz signal (figure 3b). When it detects a 38-kHz carrier, the output goes high; when it does not receive the carrier signal, it goes low. The output from the detector is fed into a decoder ic (BL9150) which is in pair with the encoder. The received data is decoded first, and then causes the corresponding output change status.

The reason why the 38-kHz carrier signal is used to transmit the code is because that there is always interference in the environment. This however interferes in a random manner. Using a specific frequency signal for the data to be transferred could eliminate this interference to some extent.

The second reason is that using an oscillating carrier signal reduces electrical power consumption required for transmitting the data, as the transmitted signal consists only of pulses. To reduce power consumption even further, the carrier signal has a duty cycle of 1/3. This means that the switch-on period of the infra-red emitter is shortened still further.

The format of the codes generated by the encoder is unique to a certain encoder/decoder pair. This means that different remote control systems can be operated in the same area. The code for the present encoder/decoder will be explained later.

The handset

The circuit of the remote control handset is given in figure 4. It consists of a BL9148 encoder, a 3 x 6 key matrix, a 455-kHz ceramic resonator, one infra-red emitting LED and two transistors which drive the LED.

The encoder ic, BL9148, is a CMOS device and requires a voltage supply 2.2V to 5.5V. The ic automatically detects which is key pressed. When no key is pressed, the ic is in the standby mode. Once a key press is detected, the ic is activated and outputs an encoded data stream. In the standby mode the quiescent current is less than 10 uA and in the active mode, the

current consumption is around 1 mA. This chip is ideal for battery-powered applications.

From figure 4 we see that pin 16 and pin 1 of the ic are connected to the positive and negative rails of a power supply. Pin 4 to pin 9 (K1 to K6) and pin 10 to pin 12 (T1 to T3) form a 6 x 3 scanning key matrix. Pin 13 (CODE) is used to set a user address of the handset. Pin 15 (TX) is the data output which is a stream of burst of the 38-kHz carrier signal. When no key is pressed, the TX line is always at logic high state. The 455-kHz

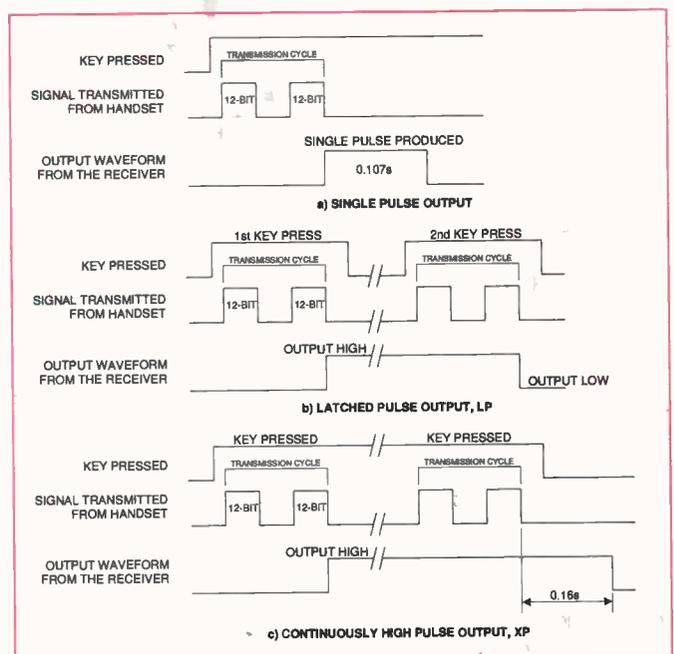


Figure 2: waveforms of the controlled outputs on the receiver board

- Ten channels with single pulse operation
- Two channels with latched pulse operation
- Six channels with continuous high pulse operation
- No adjustment needed on the receiver board.

Table 1: encoded data format for keys

Key	H	S1	S2	D1	D2	D3	D4	D5	D6	Output waveform
1	1	0	0	1	0	0	0	0	0	Waveform 2
2	1	0	0	0	1	0	0	0	0	Waveform 2
3	1	0	0	0	0	1	0	0	0	Waveform 2
4	1	0	0	0	0	0	1	0	0	Waveform 2
5	1	0	0	0	0	0	0	1	0	Waveform 2
6	1	0	0	0	0	0	0	0	1	Waveform 2
7	0	1	0	1	0	0	0	0	0	Waveform 1
8	0	1	0	0	1	0	0	0	0	Waveform 1
9	0	1	0	0	0	1	0	0	0	Waveform 1
10	0	1	0	0	0	0	1	0	0	Waveform 1
11	0	1	0	0	0	0	0	1	0	Waveform 1
12	0	1	0	0	0	0	0	0	1	Waveform 1
13	0	0	1	1	0	0	0	0	0	Waveform 1
14	0	0	1	0	1	0	0	0	0	Waveform 1
15	0	0	1	0	0	1	0	0	0	Waveform 1
16	0	0	1	0	0	0	1	0	0	Waveform 1
17	0	0	1	0	0	0	0	1	0	Waveform 3
18	0	0	1	0	0	0	0	0	1	Waveform 3

ceramic resonator is used to produce the 38-kHz carrier signal. It is connected between pins 2 and 3. The driver circuit for the LED consists of two transistors (T1 and T2, BC557 and ZTX300) and has an inverting action. When TX is at logic low, the LED is turned on, and goes off when TX is at logic high.

connected between pin 13 (CODE) and T pins (anode connected CODE) represents 1. If there is no diode, the corresponding address bit is 0. Bits H, S1 and S2 define the output waveform—whether it is a single pulse output or other types. D1-D6 specify which key is pressed. All possible transmitting codes for the 18 keys on the handset are summarised in **table 1**.

Encoded signals

Once a key press is detected, at least two identical 12-bit serial digital data are generated inside the encoder ic (the two transmissions are termed as a *transmission cycle*, see **figure 5a**). The signal is not the one output from pin 15 (TX). Pin 15 is the 38-kHz carrier signal which is modulated by the signal. The actual signal at pin 15 has a waveform which is shown in **figure 5c**. It can be seen that pin 15 (TX) is always at logic high state if no key is pressed. The 38-kHz carrier signal has a 1/3 duty cycle. The logic low period is 8.8 us and the period is 26.3 us (see **figure 5c**).

The bit functions of the 12 serial data bits from bit 0 to bit 11 in sequence are:

C1, C2, C3, H, S1, S2, D1, D2, D3, D4, D5, D6

C1, C2, C3 are user defined address bits. Possible combinations are 011, 101 and 111 (001 is not used). The address must be the same as that on the decoder ic. This allows up to three remote control systems to work in the same vicinity without interfering each other. Bits C1, C2 and C3 are determined by the connection of T1, T2 and T3 pins. A diode

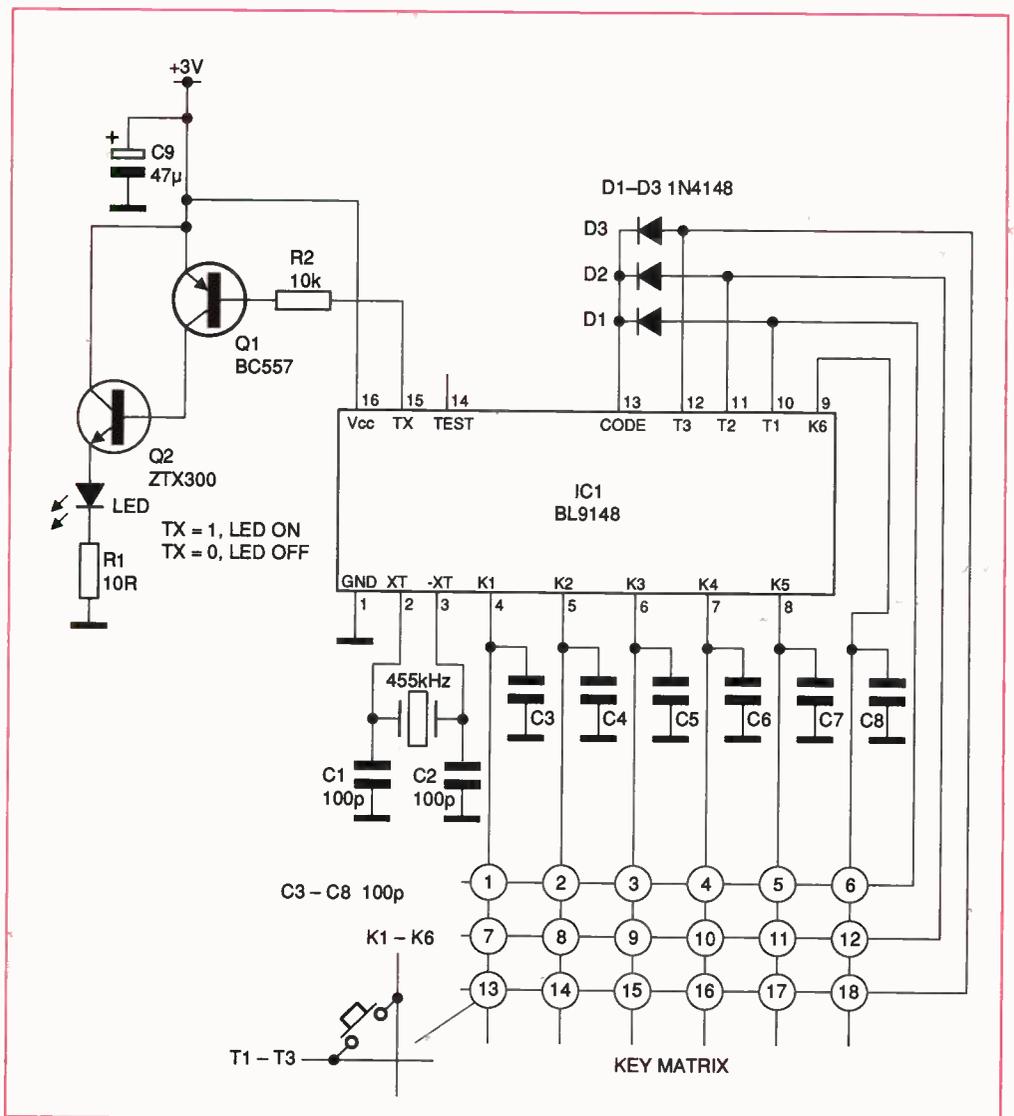


Figure 4: the circuit diagram of the remote control transmitter

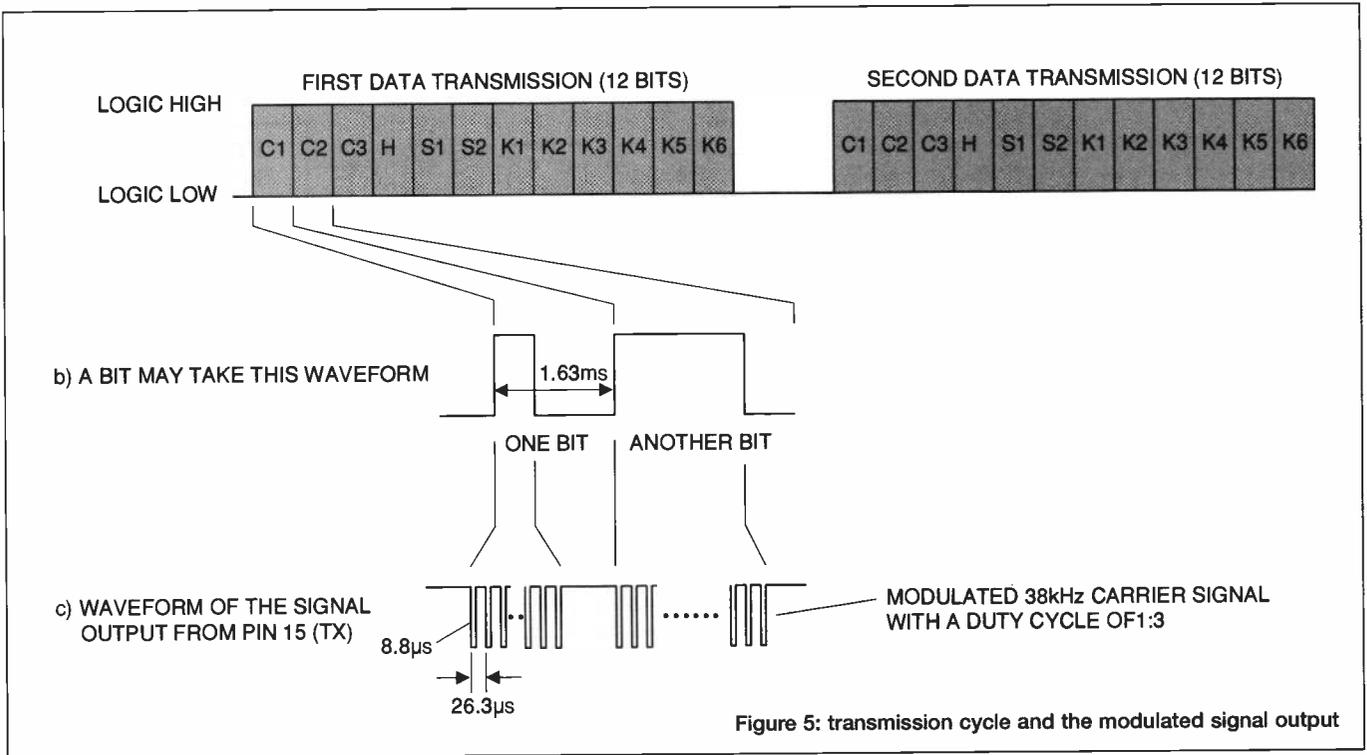


Figure 5: transmission cycle and the modulated signal output

If the external resonator is 455 kHz, the period for one bit is 1.62 millisecond ($a = 405$ micro second). A serial data 0 and 1 are represented by different duty cycles. 0 has a 1/4 duty cycle and 1 has a 3/4 duty cycle (figure 6a). As an example, if an encoded data 010100100100 is to be transmitted, the serial

data has the waveform as shown figure 6b. If a single pulse key is pressed (keys 7 to 18), only one transmission cycle is generated (figure 6c). If a continuous high pulse key is pressed (keys 1 to 6), The cycle is transmitted repeatedly (see figure 6d).

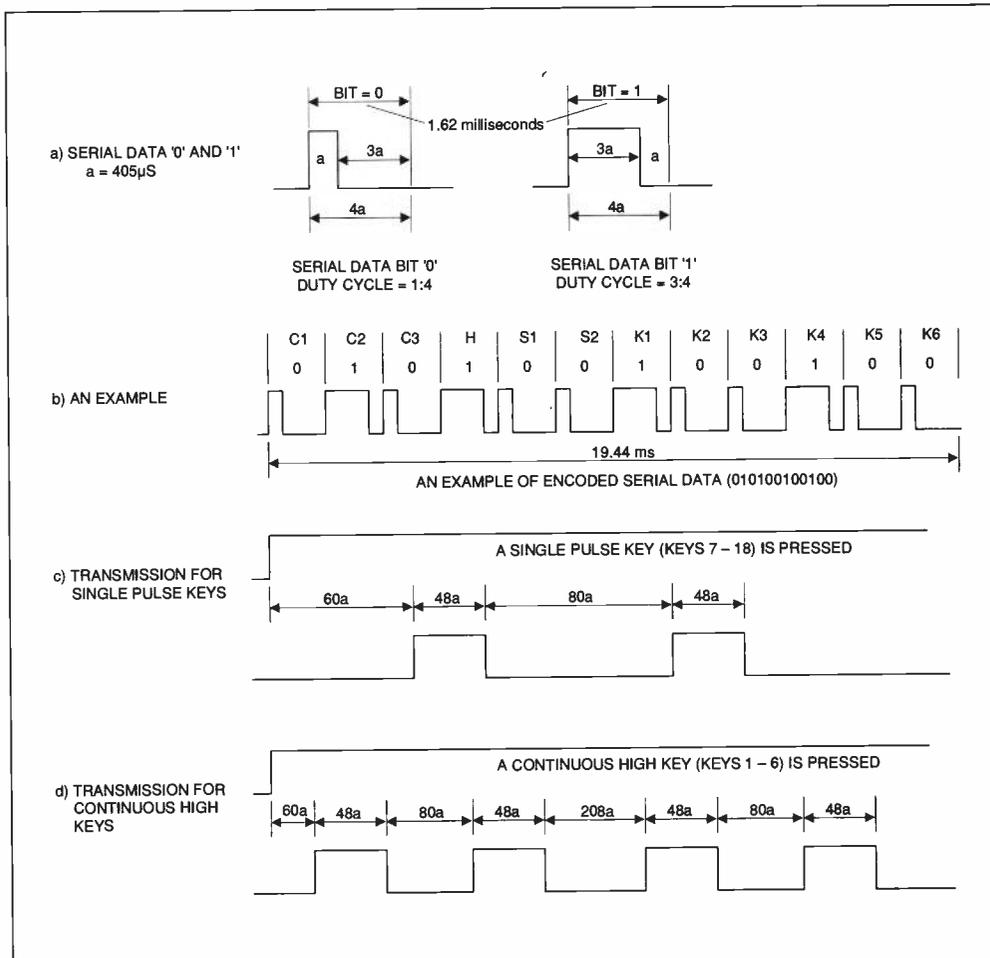


Figure 6: the format of the encoded serial data

The receiver board

The circuit of the receiver board is given in figure 7. It consists of a 38-kHz infra-red detector (IS1U60), a decoder (BL9150, which is in pair with the encoder) and a 7805 voltage regulator.

The infra-red detector is the IS1U60. It is housed in a 3-pin plastic package and incorporates a circuit capable of receiving a modulated 38-kHz infra-red signal and converting it to a digital pulse train at the output. The pin-out and the internal block diagram of the IC are shown in figure 8. The voltage supply is +5V and the current consumption is typically 3 mA. It will receive infra-red emission coming in a 30-degree angle (see figure 7). When it receives a 38-kHz infra-red light, the output goes high. The signal output from the IS1U60 is inverted by T1 before it is fed into the decoder.

The decoder, BL9150, only requires a 5 percent tolerance capacitor and a 5 percent


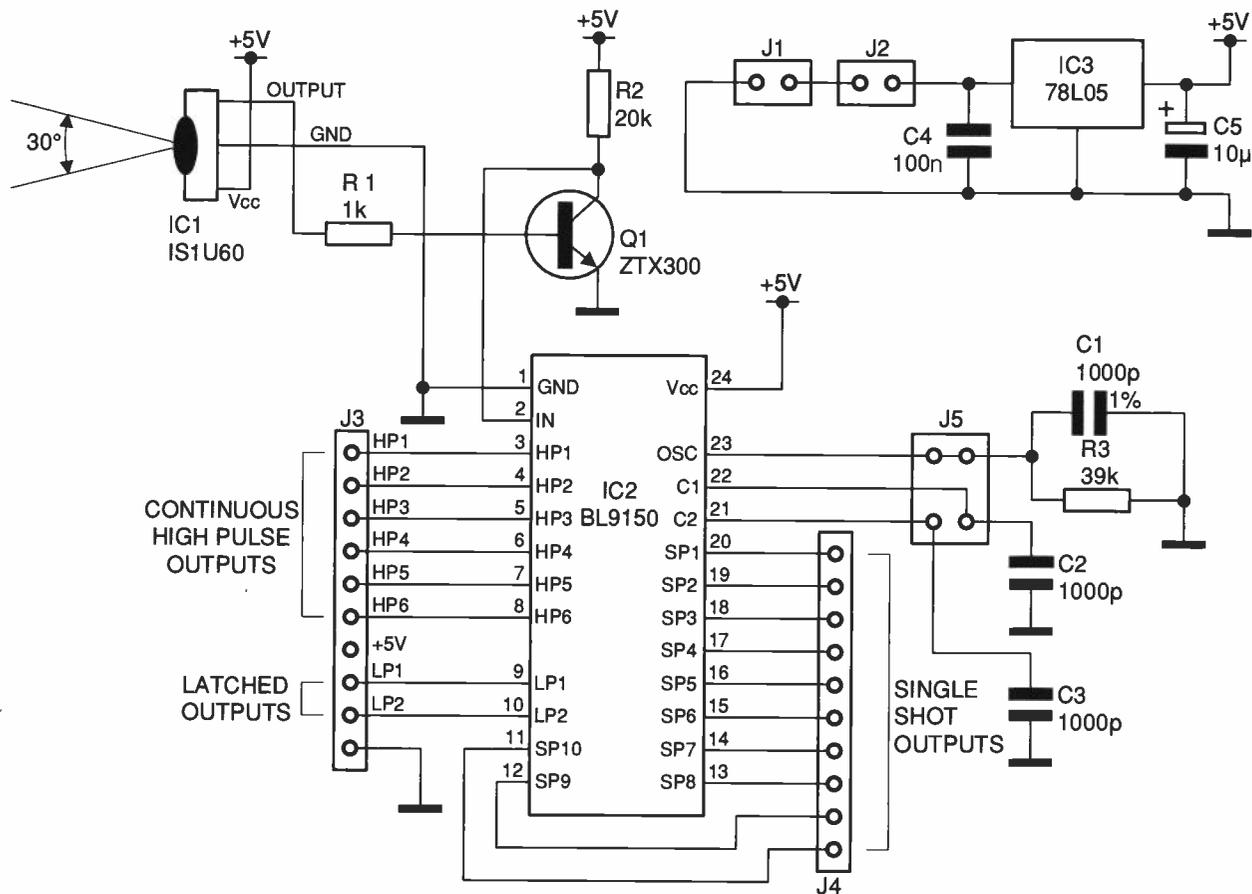


Figure 7: the circuit of the remote control receiver

tolerance resistor to make it to work. The 18 controlled outputs are from pins 3 to 20. As was explained earlier (see figure 2), the waveforms of the outputs are different. HP1 to HP6 (pins 3 to 8) are continuous high pulse output. LP1 and LP2 (pins 10 and 9) are latched outputs. SP1 to SP10 (pins 20 down to 11) are single pulse outputs. They are available from connectors J3 and J4. C1 (pin 22) and C2 (pin 21) set the address of the decoder. Pins 21 and 22 are pulled to Vcc internally. Capacitors C1 and C2 are used to generate a reset signal when the decoder is firstly power on. The BL9150 is a CMOS device. The quiescent current is typically 1 mA.

The decoder operates by receiving the first serial data of the transmission cycle and storing it in a register. The decoder then receives the second data. If the second data is identical to the first, the transmission is valid. Next, the decoder checks if the address of the serial data received is the same as the address selected by C1 and C2 pins. If it is, the received data will be latched to the output and the output goes high. If the addresses are different, the received data will not be latched to the output. If the two received data are different, the decoder resets itself and is ready to receive the next data.

Figure 8: the pin-out and internal diagram of the IS1U60

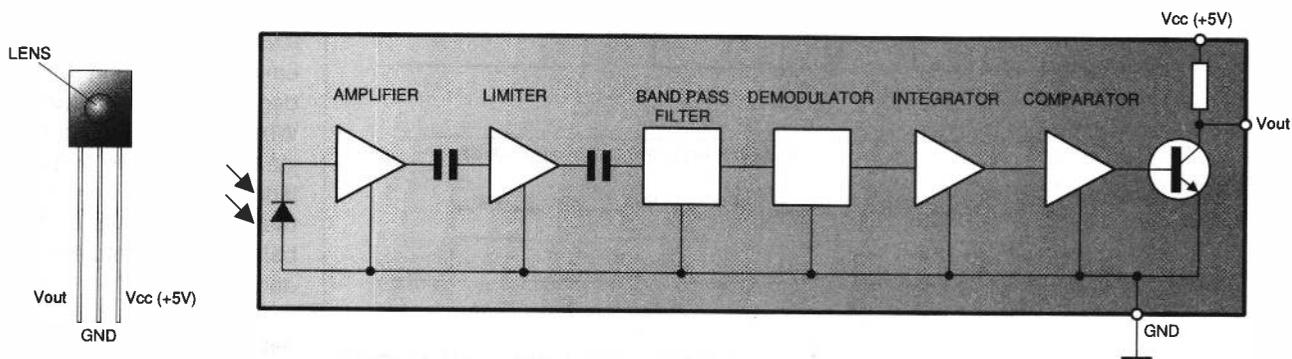



**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683**

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Beckman 9102 - 20MHz - Dual Channel.....	£150
Cossor 3020 - 60MHz Dual Channel.....	£250
Gould OS 245A/250/255/300/3000/3351/4000.....	from £125
Hewlett Packard 180A/180C/181A/182C.....	from £200
Hewlett Packard 1740A, 1741A, 1744A, 100MHz dual ch.....	from £350
Hewlett Packard 54100D - 1GHz Digitizing.....	£295
Hewlett Packard 54200A - 50MHz Digitizing.....	£150
Hewlett Packard 54201A - 300MHz Digitizing.....	£150
Hitachi V650F - 60MHz Dual Channel.....	£350
Hitachi V152F/V302B/V302F/V353F/V550B/V650F.....	from £125
Intron 2020 - 20MHz Digital Storage (NEW).....	£650
Iwatsu SS 5710/SS 5702 - 20MHz.....	from £125
Kikusui COS 6100 - 100MHz, 5 Channel, 12 Trace.....	£475
Kikusui 5100 - 100MHz - Dual Channel.....	£350
Meguro - MSO 1270A - 20MHz Digital Storage (NEW).....	£650
Nicolet 310 - L.F. D.S.O. with twin Disc Drive.....	£550
Nicolet 3091 - L.F. D.S.O.....	£900
Philips PM 3211/PM 3212/PM 3214/PM 3217/PM 3234/PM 3240/PM 3243/PM 3244/PM 3261/PM 3262/PM 3263/PM 3540.....	from £125
Philips PM 3295A - 400MHz Dual Channel.....	£1750
Philips PM 3335 - 50 MHz/20Ms/s D.S.O. 2 ch.....	£1500
Philips PM 3055 - 50 MHz DUAL Timebase.....	£450
Tektronix 434 - 25MHz - 2 Channel Analogue Storage.....	£250
Tektronix 454 - 150MHz - 2 Channel.....	£400
Tektronix 468 - 100MHz D.S.O.....	£750
Tektronix 2213 - 60MHz Dual Channel.....	£425
Tektronix 2221 - 60MHz Digital Storage 2 Channel.....	£1500
Tektronix 2215 - 60MHz Dual trace.....	£450
Tektronix 2235 - 100MHz Dual trace.....	£450
Tektronix 2335 - Dual trace 100MHz (portable).....	£800
Tektronix 2225 - 50MHz dual ch.....	£750
Tektronix 2440 - 300 MHz/500 Ms/s D.S.O. 2 Ch.....	£3750
Tektronix 455 - 50MHz Dual Channel.....	£350
Tektronix 464/466 - 100MHz An storage.....	from £350
Tektronix 465/465B - 100MHz dual ch.....	from £350
Tektronix 475/475A - 200MHz/250MHz Dual Channel.....	from £475
Tektronix 485 - 350MHz - 2 channel.....	£900
Tektronix 5403 - 60MHz - 2 or 4 Channel.....	from £250
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch.....	from £300
Tektronix 7704 - 250MHz 4 ch.....	from £650
Tektronix 790 - 500MHz.....	from £850
Trio CS-1022 - 20MHz - Dual Channel.....	£125

Other scopes available too

SPECIAL OFFER

HITACHI V212 - 20MHz DUAL TRACE.....	£180
HITACHI V222 - 20 MHz DUAL TRACE + ALTERNATE MAGNIFY.....	£200

SPECTRUM ANALYSERS

Advantest 4133B - 10KHz - 20GHz (60GHz with external mixers) + Ext. Keyboard.....	£7250
Advantest 4131B - 10KHz - 3.5GHz.....	£4950
Ando AC8211 - Spectrum Analyser 1.7GHz.....	£2950
Anritsu MS610B - 10KHz - 2GHz - (Mini).....	£4750
Anritsu MS341A + MS3401B - (10Hz - 30MHz.....	£3995 + £4995
Anritsu MS62B - 10KHz - 1700MHz.....	£2500
Avcom PSA65 S - 1000MHz - portable.....	£1500
Hewlett Packard 3580A - 5Hz-50KHz.....	£995
Hewlett Packard 182T with 8559A (10MHz - 21GHz).....	£3750
Hewlett Packard 35601A - Spectrum Analyser Interface.....	£1000
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser.....	£7500
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser.....	£7500
Hewlett Packard 852A + 8558B - 0.1 to 1500MHz.....	£3250
Hewlett Packard 182T + 8558B - 0.1 to 1500MHz.....	£2750
Hewlett Packard 8754A - Network Analyser 4-1300MHz.....	£2000
Hewlett Packard 8591A - 9KHz - 1.8GHz.....	£4995
Hewlett Packard 8594E - 9KHz - 2.9GHz.....	£7000
Hewlett Packard 3582A - 0.02Hz - 25.6KHz (dual ch.).....	£2000
Hewlett Packard 3585A - 20Hz - 40MHz.....	£4995
Hewlett Packard 8754A (opt. H26) - 4MHz - 2.6GHz.....	£2950
IFR 7750 10KHz - 1GHz.....	£3250
Marconi 2370 - 110MHz.....	£995
Marconi 2371 - 30KHz - 2000MHz.....	£1250
Meguro MSA 4901 - 1-300GHz (AS NEW).....	£1500
Meguro MSA 4902 - 1-1GHz (AS NEW).....	£1995
Poirdar 641-1 - 10MHz - 18GHz.....	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz.....	£1800
Takeda Riken 4132 - 1.0GHz Spectrum Analyser.....	£2000
Tektronix 7L18 with mainframe (1.5-60GHz with external mixers).....	£2000
Tektronix 495P - 100Hz - 1.8GHz programmable.....	£4950

MISCELLANEOUS

Adret 740A - 100KHz - 1120MHz Synthesised Signal Generator.....	£800
ANRITSU ME 462B DF/3 Transmission Analyser.....	£3000
Danbridge JP30A - 30KV Insulation Tester.....	£1500
Anritsu MG642A Pulse Pattern Generator.....	£1500
Dranetz 626 - AC/DC - Multifunction Analyser.....	£850
EIP 331 - Frequency counter 18GHz.....	£700
EIP 345 - Frequency counter 18GHz.....	£1500
EIP 545A - Frequency counter 18GHz.....	£1500
EIP 575 - Frequency counter 18GHz.....	£250
Farnell AP70-30 Power Supply (0.70v/30A) Auto Ranging.....	£750
Farnell TSV-70 MKII Power Supply (70V - 5A or 35V - 10A).....	£250
Farnell DSG-1 Synthesised Signal Generator.....	£125
Farnell ESG-1000 Synthesised Signal Generator 1GHz (as new).....	£1650
Flure 5100A - Calibrator.....	£2500
Gullidine 9152 - T12 Battery Standard Cell.....	£550
Hewlett Packard 331A - Distortion Analyser.....	£300
Hewlett Packard 3336C - Synthesised Signal Generator (10Hz - 21MHz).....	£1000
Hewlett Packard 3437A System voltmeter.....	£350
Hewlett Packard 3456A Digital voltmeter.....	£200
Hewlett Packard 3438A Digital multimeter.....	£200
Hewlett Packard 3488A - Switch/Control Unit.....	£650
Hewlett Packard 35600A Dual Ch. Dynamic Signal Analyser.....	£3750
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser.....	£2250
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen.....	£1500
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available).....	£650
Hewlett Packard 3455A 6 1/2 Digit M/Meter (Autocal).....	£750
Hewlett Packard 3478A - Multimeter (5 1/2 Digit) + HP - 1B.....	£550
Hewlett Packard 356A - Selective Level Meter.....	£1000
Hewlett Packard 3776A - PCM Terminal Test Set.....	£1500
Hewlett Packard 3779A/3779C - Primary Mux Analyser.....	from £990
Hewlett Packard 3784A - Digital Transmission Analyser.....	£4995
Hewlett Packard 37900D - Signalling Test Set (No 7 and ISDN).....	£6000
Hewlett Packard 4262A - Digital LCR Meter.....	£1350
Hewlett Packard 4275A - LCR Meter (Multi-Frequency).....	£3950
Hewlett Packard 4338A - Millionmeter (As New).....	£2000
Hewlett Packard 4342A 'Q' Meter.....	£995

Hewlett Packard 435A or B Power Meter (with 8481A/8484A).....	from £750
Hewlett Packard 4279A - 1MHz C-V Meter.....	£4500
Hewlett Packard 4348A - (TIMS) Transmission Impairment M/Set.....	£1500
Hewlett Packard 4872A - Lan Protocol Analyser.....	£1750
Hewlett Packard 5420A Digital Signal Analyser.....	£350
Hewlett Packard 5335A - 200MHz High Performance Systems Counter.....	£600
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter.....	£250
Hewlett Packard 5316A - Universal Counter (IEEE).....	£500
Hewlett Packard 5183 - Waveform Recorder.....	£1750
Hewlett Packard 5238A Frequency Counter 100MHz.....	£250
Hewlett Packard 5370A - 100MHz Universal Timer/Counter.....	£450
Hewlett Packard 5384A - 225 MHz Frequency Counter.....	£650
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005.....	£995
Hewlett Packard 6253A Power Supply 20V - 3A Twin.....	£200
Hewlett Packard 6255A Power supply 40V - 1.5A Twin.....	£200
Hewlett Packard 6266B Power Supply 40V - 5A.....	£220
Hewlett Packard 6271B Power supply 60V - 3A.....	£225
Hewlett Packard 6622A - Power Supply, Dual O/P.....	£1650
Hewlett Packard 6623A - Power Supply, Triple O/P.....	£1650
Hewlett Packard 6652A - Power Supply (0 - 20V, 0 - 25A).....	£1250
Hewlett Packard 6264B - Power Supply (0 - 20V, 0 - 25A).....	£400
Hewlett Packard 7475A - 6 Pen Plotter.....	£250
Hewlett Packard 7550A - 8 Pen Plotter A3/A4.....	£450

HEWLETT PACKARD 6261B Power Supply 20V-50A £450 Discount for Quantities

Hewlett Packard 83555A - Millimeter - Wave source Module 33-50GHz.....	£4250
Hewlett Packard 8015A - 50MHz Pulse Generator.....	£750
Hewlett Packard 8405A - Vector Voltmeter.....	£350
Hewlett Packard 8165A - 50MHz Programmable Signal Source.....	£1650
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various Plug-Ins available) extra.....	£1250
Hewlett Packard 8152A - Optical Average Power Meter.....	£250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011).....	£1100
Hewlett Packard 8180A - Data Generator.....	£1500
Hewlett Packard 8182A - Data Analyser.....	£1500
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various plug-in options available).....	£2500
Hewlett Packard 83554A - Wave Source Module 26.5 to 40GHz.....	£3500
Hewlett Packard 8620C Sweep oscillator mainframe.....	from £250
Hewlett Packard 8656A - Synthesised Signal Generator (990MHz).....	£2000
Hewlett Packard 8658B - Synthesised Signal Generator.....	£2950
Hewlett Packard 8750A Storage normaliser.....	£375
Hewlett Packard 8756A - Scalar Network Analyser.....	£1500
Hewlett Packard 8757A - Scalar Network Analyser.....	£2250
Hewlett Packard 8903A - Audio Analyser (20Hz - 100KHz).....	£2600
Hewlett Packard 8903E - Distortion Analyser (Mint).....	£2000
Hewlett Packard 8958A - Cellular Radio Interface.....	£2000
Hewlett Packard 8901A - Modulation Analyser.....	£3400
Hewlett Packard 8920A - R/F Comms Test Set.....	£6000
Hewlett Packard 8922b - GSM Radio Comms Test Set.....	£9995
Hewlett Packard P382A Variable Attenuator.....	£250
Hewlett Packard 1630D - Logic Analyser (43 Channels).....	£650
Hewlett Packard 1650A - Filled with 16510A/16515A/16530A/16531A - Logic Analyser.....	£4000
Hewlett Packard 11729B - Carrier Noise Test Set.....	£2000
Krohn-Hite 2200 Lin/Log Sweep Generator.....	£995
Krohn-Hite 4024A Oscillator.....	£350
Krohn-Hite 5200 Sweep, Function Generator.....	£350
Krohn-Hite 5500 Phase Meter.....	£250
Leader 3216 - Signal Generator (100KHz - 140KHZ) AM/FM/CW with built-in FM stereo modulator (mint).....	£995
Marconi 2019 - 80KHz - 1040MHz Synthesised Sig. Gen.....	£1450
Marconi 2019A - 80KHz - 1040MHz - Synthesised Signal Generator.....	£1600
Marconi 2022A - 10KHz - 1GHz AM/FM Signal Generator.....	£2000
Marconi 2041 - (10KHz - 2.7GHz) Low Noise.....	£7500
Marconi 2205 - Modulation Meter.....	£1995
Marconi 2610 - True RMS Voltmeter.....	£850
Marconi 2871 Data Comms Analyser.....	£1000
Marconi 2955 - Radio Comms Test Set.....	£3000
Marconi 6960 - Power Meter & Sensor.....	from £350
Philips PM 5167MHz function gen.....	£400
Philips 5190 L.F. Synthesiser (G.P.I.B.).....	£800
Philips 5193 Synthesised Function Generator.....	£1500
Philips 5518 Synthesised Function Generator.....	£1500
Philips PM5519 - TV Pattern Generator.....	£350
Philips PM5716 - 50MHz Pulse Generator.....	£525
Philips PM6652 - 1.5GHz Programmable High Resolution Timer/Counter.....	£900
Phirma 4000 - 6 1/2 Digit Multimeter (NEW).....	£430
Racal 1992 - 6 1/2 GHz Frequency Counter.....	£450
Racal Dana 9081/9082 Synth. sig. gen. 520MHz.....	£800
Racal Dana 9084 Synth. sig. gen. 104MHz.....	from £500
Racal Dana 9303 R/F Level Meter & Head.....	£650
Racal Dana 9917 UHF frequency meter 560MHz.....	£175
Racal Dana 9302A R/F multivoltmeter (new version).....	£375
Racal Dana 9082 Synthesised am/fm sig gen (520MHz).....	£500
Racal 9301A - True RMS R/F Multivoltmeter.....	£300
Racal 6111/6151 - GSM Radio Comms Test Set.....	£POA
Rohde & Schwarz LFM2 - 60MHz Group Delay Sweep Gen.....	£1600
Rohde & Schwarz Scud Radio Code Test Set.....	£300
Rohde & Schwarz CMS 54 Radio Comms Monitor.....	£6250
Rohde & Schwarz CMTA 94 GSM Radio Comms Analyser.....	£7500
Schaffner NSG 203A Line Voltage Variation Simulator.....	£950
Schaffner NSG 222A Interference Simulator.....	£850
Schaffner NSG 223 Interference Generator.....	£850
Schaffner WSG 431 Electrostatic Discharge Simulator.....	£1250
Schlumberger 4031 - 1GHz Radio Comms Test Set.....	£4995
Schlumberger 2720 1250MHz Frequency Counter.....	£500
Schlumberger 7060/7065/7075 Millimeters.....	from £350
Schlumberger Stablock 4040 Radio Comms Test Set.....	£3500
Solartron 1250 - Freq. Response Analyser.....	£2500
Stanford Research DS 340 - 15MHz Synthesised Function (NEW) and arbitrary waveform generator.....	£1200
Syston Donner 6030 - Microwave Frequency Counter (26.5GHz).....	£2500
Tequipment CT71 Curve Tracer.....	£250
Tektronix TM5003 + AFG 5101 Arbitrary Function Gen.....	£2500
Tektronix 1240 Logic Analyser.....	£500
Tektronix DAS9100 - Series Logic Analyser.....	£500
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PG508, FG504, FG503, TG501, TR503 + many more.....	£POA
Tektronix AM503 + TM501 + P6302 - Current Probe Amplifier.....	£995
Tektronix PG506 + TG501 + SG503 + TM503 - Oscilloscope Calibrator.....	£1995
Tektronix AA5001 + TM5006 M/F - Programmable Distortion Analyser.....	£1995
Tektronix 577 - Curve Tracer.....	£1150
Time 9811 Programmable Resistance.....	£400
Time 9814 Voltage Calibrator.....	£550
Toellner 7720 - Programmable 10MHz Function Gen (AS NEW).....	£700
Valhalla Scientific - 272A Programmable Resistance Standard.....	£POA
Wandel & Goltermann PFJ-8 - Error/Jitter Test Set.....	£12500
Wandel & Goltermann PCM4.....	£11000
Wandel & Goltermann PCM4 (+ options).....	£9950
Wayne Kerr 4225 - LCR Bridge.....	£600
Wayne Kerr 6425 - Precision Component Analyser.....	£275
Wayne Kerr 8905 - Precision LCR Meter.....	£850
Wavetek 171 - Synthesised Function Generator.....	£250
Wavetek 178 Programmable Sig Source (0.0001Hz - 13MHz).....	£POA
Wavetek 184 - Sweep Generator - 5MHz.....	£250
Wavetek 3010 - 1-1GHz Signal Generator.....	£1250
Willron 6409 - RF Analyser (1MHz - 2GHz).....	£POA
Wiltron 6620S - Programmable Sweep Generator (3.6 - 6.5GMHz).....	£650

**MANY MORE ITEMS AVAILABLE -
SEND LARGE S.A.E. FOR LIST OF EQUIPMENT
ALL EQUIPMENT IS USED -
WITH 30 DAYS GUARANTEE.
PLEASE CHECK FOR AVAILABILITY BEFORE
ORDERING - CARRIAGE & VAT TO BE ADDED
TO ALL GOODS**

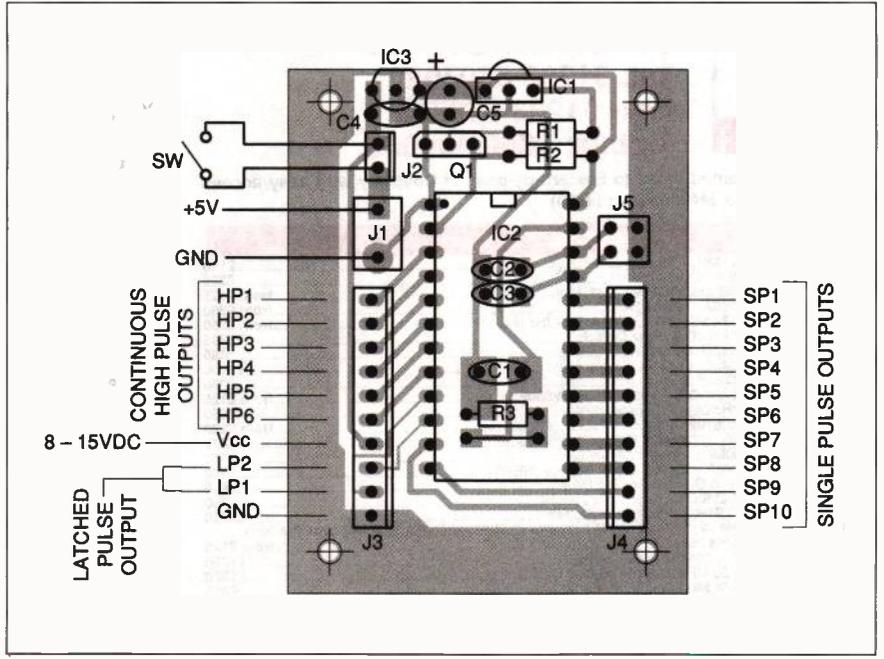
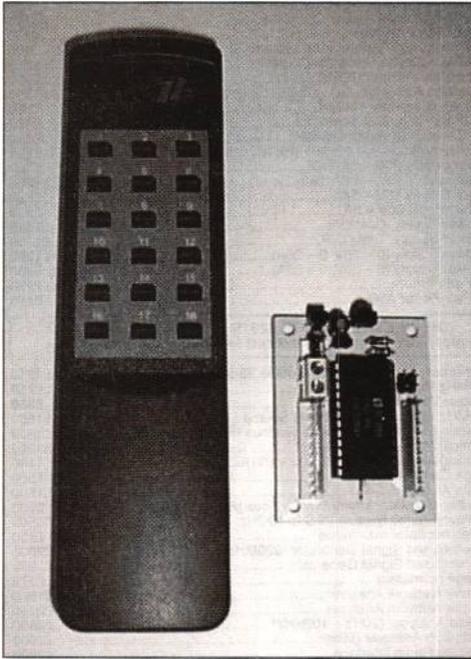


Figure 9: the handset unit with the Receiver PCB Figure 10: the component layout of the remote control receiver board

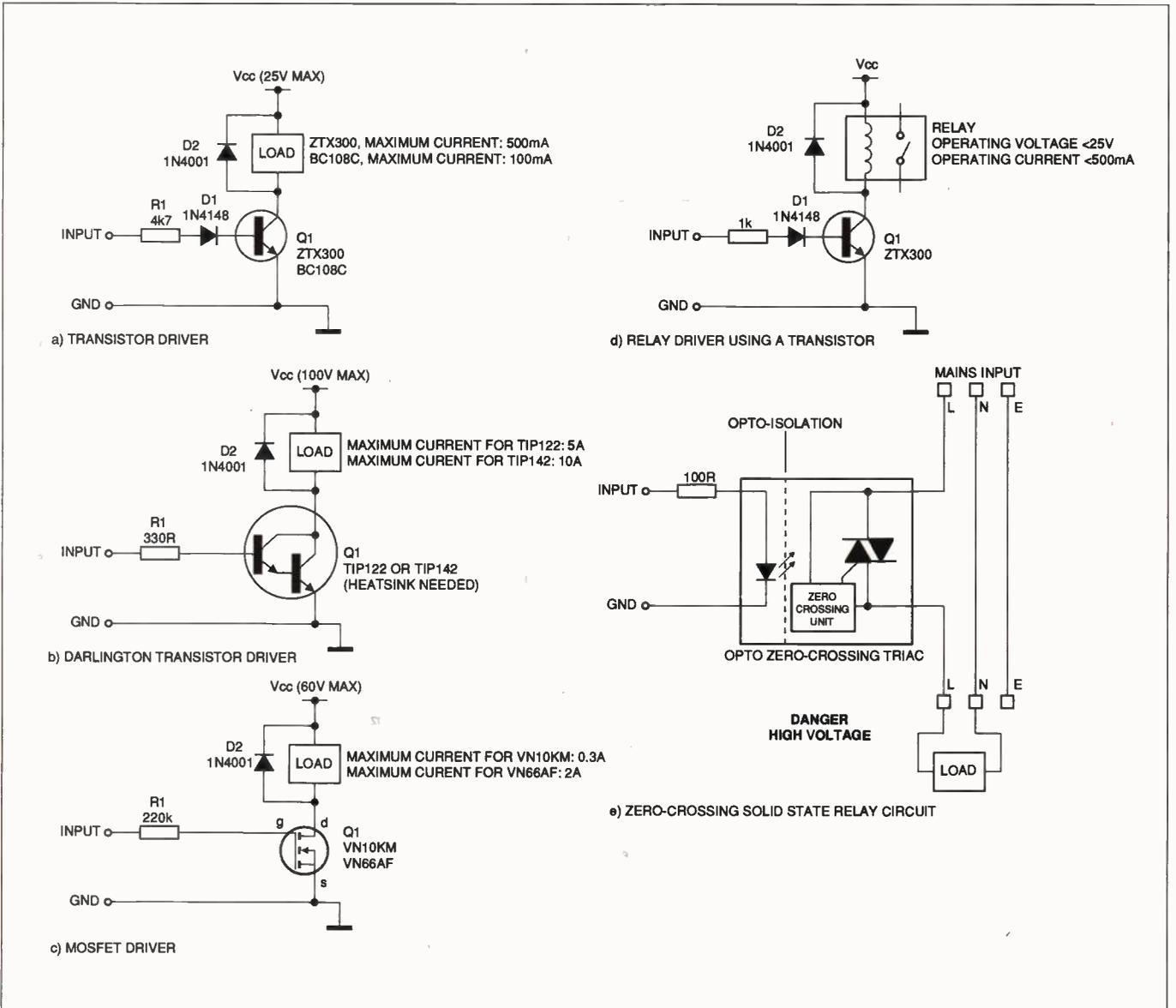


Figure 12: various power drivers

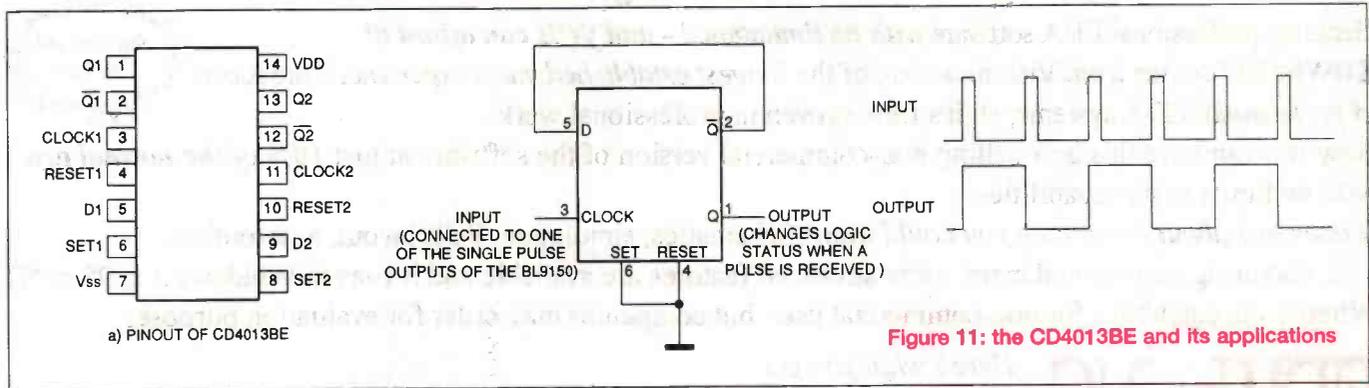


Figure 11: the CD4013BE and its applications

Construction and testing

The receiver is constructed on a single-sided PCB. The component layout is given in **figure 10**. The board is easy to put together. Use an ic socket for the decoder ic. There is no adjustment required on the board. Once the components are mounted correctly, the system should work straight away. During testing, you could connect some LEDs to the outputs and point the handset at the receiver board.

The transmitter is available as a single unit, but the circuit is given and the transmitter can be built on a piece of stripboard for experiments. A keypad (Maplin JM09K) can be used to operate it.

Application notes

Latched outputs (2 outputs) can be used for controlling lights. If a key is pressed, the corresponding light is switched on and stays switched on. If the key is pressed again, the light goes off. This can also be used for controlling other electrical appliances.

The single shot (10 outputs) outputs are useful in light dimmer applications. A single pulse will cause the lighting control circuit to increase the power output light bulb by one step. The outputs can also have a latch action using an external CD4013 (see the circuit in **figure 11**).

The continuous high outputs (6 outputs) can be used for controlling curtains. When a key is pressed, the curtains open (or close). If the key is released, the curtains stop! So the actual position can be controlled.

To control electrical devices operating at a higher voltage and current, transistor, mosfet transistor and relay drivers can be used. For mains controls, optically-isolated solid state relays can be used. Some of the driver circuit types are shown in **figure 12**.

Parts and kit

The project is available as a whole kit, which includes an assembled handset and an unassembled receiver board with decoder ics and other components. The price is £39.00 sterling including P&P. The handset unit alone is priced £21.00. Handset parts are not available separately. The receiver IC BL9150 and PCB are £8.00 and £6.00 respectively. Please add £3.00 post and packing to each order. If you require information or other receiver components, please make your enquiry to **Dr. Pei An, 11 Sandpiper Drive, Stockport, Cheshire, SK3 8UL UK. Tel/Fax 0161 477 9583. Email: pan@fs1.eng.man.ac.uk.**

PARTS LIST for the 18-channel Remote Controller

Receiver board

Resistors

(1 percent metal film 0.25W)

R1	1k
R2	20k
R3	39k

Capacitors

C1-C3	1000 pF ceramic disc 5 percent
C4	100 nF ceramic disc
C5	10 uF electrolytic

Semiconductors

IC1	IS1U60 infra-red detector
IC2	BL9150 18 key decoder ic
IC3	78L05 +5V voltage regulator
T1	ZTX300 npn transistor

Others

J1	2-way screw terminals
J2	2-way PCB connector
J3,J4	10-way PCB connector
J5	2 x 2 PCB pins
PCB and PCB pillars	

Components used in the handset

Resistors

(1 percent metal film 0.25W)

R1	10R
R2	10k

Capacitors

C1-C8	100 pF ceramic disc capacitors
C9	47 uF electrolytic capacitors
TX	455 kHz

Semiconductors

D1-D3	1N4148
IC1	BL9148 18 key encoder ic
T1	BC557 pnp transistor
T2	ZTX300 npn transistor
LED	Infra-red emitting diode, maximum forward current: 100 mA

Others

PCB, key board, handset housing

Most components are available from Maplin. The encoder and decoder ics (BL9148 and BL9150), the receiver PCB and the handset unit are only available from the author (see text).

Professional Electronics Design - **90% Discount!**

- Genuine, professional EDA software *with no limitations!* - *and YOU can afford it!*
- **EDWin NC** comes from Visionics: one of the *longest established, most experienced* producers of professional EDA systems, so it's fully proven in professional work.
- Now you can have this best-selling non-commercial version of the software at just **10% of the normal price**, with no limits in its capabilities.
- *It does just about everything you could want!* Schematics, simulation, PCB layout, autorouting, manufacturing outputs and many more advanced features are available and it runs in Windows 3.x, 95 or NT.
- Where's the catch? It's for non-commercial use - but companies may order for evaluation purposes



EDWin NC

Electronics Design
for Windows

We aim to dispatch
immediately we receive payment,
but please allow 14 days.
Postage £5 UK; Overseas £10
Prices inc. VAT.

**Don't forget -
Phone Today for Your
90% Discount!**


Here's what you get:

- **EDWin NC BASIC:** Schematics, PCB Layout Basic Autorouter, manufacture outputs, Max. 100 component database, 500 device Library **£49.00**
- **EDWin NC De Luxe 1:** BASIC + Professional Libraries and unlimited database **£79.00**
- **EDWin NC De Luxe 2:** BASIC + Professional Libraries and Mix-mode simulation **£79.00**
- **EDWin NC De Luxe 3:** BASIC + Professional Libraries, unlimited database, Mix-mode Simulation and Arizona Autorouter **£115.00**
- **EDWin NC De Luxe 4:** De Luxe 3 + Thermal Analyser, EDSpice Simulation, EDCoMX Spice model kit **£199.00**
- **EDWin NC De Luxe 5:** De Luxe 4 + ED-EMA (EMC Analyser) **ALL FOR ONLY £235.00**



Order hotline: 01992 570006 Fax 01992 570220 E-mail: visionics.eu@dial.pipex.com

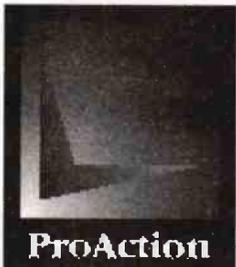Swift Eurotech Ltd., Twankhams Alley, 160 High Street, Epping, Essex, CM16 9AQ



Serious Stuff Games Roundup

If you have, or know someone who has, an Acorn computer then you could do worse than looking at our roundup; a complete guide to ProAction's titles. The best bit - it's FREE, and if you quote ETI when ordering we'll send a demo disc!

ProAction's software is distributed by R-Comp & R-Comp Interactive
R-Comp Interactive, 22 Robert Moffat, High Legh, Knutsford, Cheshire WA16 6PS
Tel: +44 (0)1925 755043 Fax: +44 (0)1925 757377 Email: proaction@rcomp.co.uk

Ref. DB: 16th July 1998



A'Q'METER ADAPTER

This simple adapter by Raymond Haigh enables the Q factor and inductance of RF coils to be measured with a signal generator and multimeter.

Anyone involved in radio construction will, from time to time, wish to measure the inductance of RF coils and transformers, and to compare their performance by determining the Q factor. Most serious experimenters will have a multimeter and signal generator in their workshops, and the unit described here enables these items to be used for Q metering purposes.

The Q factor

The Q factor of a tuned circuit defines its ability to magnify a signal at its resonant frequency, and to reject signals at frequencies off resonance; that is, its selectivity. An inductor with a Q of 100 arranged in an L/C tuned circuit will magnify a 1mV signal to 100mV. If the Q factor is reduced to 20, the voltage developed across the inductor will then be only 20mV. This is an important aspect of signal amplification; one without recourse to valves or transistors and the added noise these devices introduce.

Turning to the question of selectivity: for a a medium-wave coil tuned by a capacitor to resonate at 1MHz with a Q factor of 100 the bandwidth at the 3dB down (half power) points is 10kHz. If its Q is reduced to 20, the bandwidth widens to 50kHz and selectivity is seriously impaired.

The benefits of a high Q factor, under most circumstances, are very clear. Indeed, the standards of performance achieved by early valve receivers can be attributed, in no small measure, to the quality of their RF and IF coils and transformers. The quest for miniaturisation and the ability to maintain sensitivity by means of high-gain, low-cost semiconductor devices, has sometimes led to the Q factor being traded off for reductions in size. Home constructors are not always preoccupied with extreme miniaturisation, and space can often be found, especially with simple or single band receivers, for larger, and possibly more lightly coupled, inductors, in order to secure the advantages of their higher Q factors. Even when small size is important, it is still desirable to select inductors with the highest possible Q.

Methods of measurement

Q factor can be measured by determining either the magnification or the selectivity of a resonant circuit formed by an inductor and a capacitor. The Q of a good quality air-spaced variable capacitor can, for all normal purposes, be regarded as infinite, and any resistive or dielectric losses which reduce the Q of the tuned circuit can be attributed solely to the inductor. Q measuring instruments which rely on the phenomenon of signal magnification place the coil under test in series with a variable capacitor. The capacitor tunes the coil to resonate with a signal injected into the circuit, and the magnified voltage developed across either the inductor or the capacitor (the voltages across the two components are identical) is compared with the applied signal voltage.

A diagram showing the basic arrangement is given in **figure 1**.

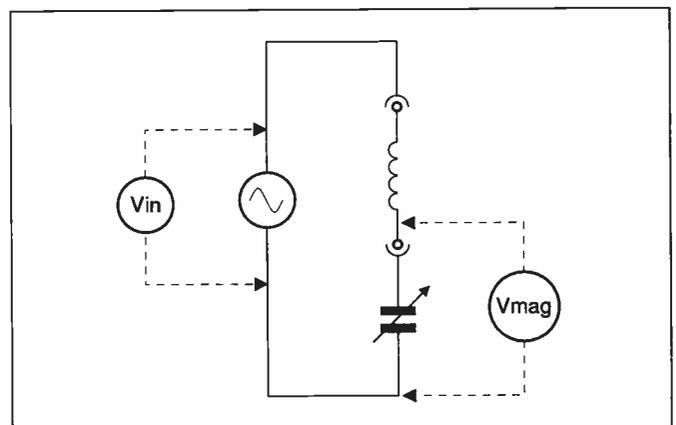
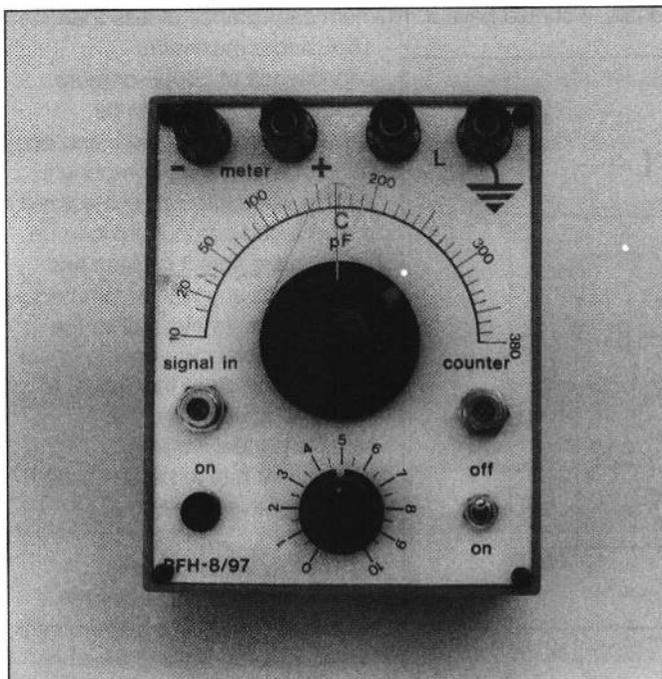


Figure 1: method of deriving the Q factor from the selectivity of a tune circuit: $Q = \text{resonant frequency}/\text{bandwidth at } 0.707 \text{ of } V \text{ at resonance}$

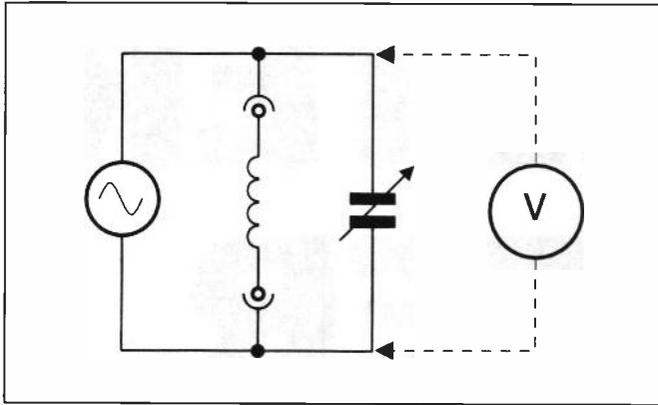


Figure 2: method of deriving the Q factor from the magnification effect of a tune circuit: $Q = V_{mag}/V_{in}$

The meter used for the measurements must be a high-impedance electronic instrument, and the signal generator must have a very low output impedance, or the accuracy of the measurements will suffer. Such a circuit cannot normally be used to measure the Q of coils wired into equipment.

Measuring instruments which exploit the relationship between selectivity and Q test the inductor in a parallel tuned circuit. A simplified diagram is given in **figure 2**. Signal source and voltmeter must both have a high impedance in order to avoid damping the tuned circuit.

The adapter unit described here provides the necessary low-to-high impedance buffers between the signal generator, the voltmeter, and the inductor under test, so that selectivity can be measured, and the Q factor determined, with reasonable accuracy. With this arrangement, the Q factors of coils wired into equipment can usually be checked and, if the variable capacitor is calibrated, inductor values can be measured also.

The circuit of the adapter unit

The circuit of the adapter is given in **figure 3**, where Q1 acts as a low-to-high impedance buffer for the signal generator, and Q2 as a high-to-low impedance buffer for the testmeter. Blocking capacitor C1 avoids the possibility of the output circuitry of the signal generator disturbing the operation of Q1. This transistor is configured in the grounded gate mode, and input impedance at the source is accordingly low and output

impedance at the drain high. The signal from the generator is applied across the source bias resistor R1, and the output voltage is developed across L1, an RF choke which acts as the drain load. Coupling to the inductor under test is by means of the low-value capacitor C2.

The inductor to be checked is connected in a parallel resonant circuit with variable capacitor C4. The Q of RF coils is best measured at the mid-point of their tuning range, and C4 can be set to simulate this.

The high impedance at the gate of Q2 minimises damping on the tuned circuit. The gate is grounded by R3 to avoid the possibility of damage to the device when there is no coil connected, and this resistor has been given a high value in order to maintain the input impedance of the stage.

Output to the moving coil meter is developed across source resistor R5. As there is a DC potential at the source, a blocking capacitor C6 has to be provided, and a signal rectifier, D1, shunt connected. R6 and R7, wired in series with the meter, set the sensitivity of the voltage measuring circuit, and R7 is adjustable so that the pointer can be set to a convenient scale reading.

R2 eliminates a tendency for Q2 to become unstable when very high Q coils are being tested. Bypass capacitor C3, connected across the supply rails, also ensures the stability of the circuit.

A frequency counter makes the unit much easier to use and improves the accuracy of the measurements, especially when the signal generator is not finely calibrated. An output for a counter is taken from the drain of Q2 via blocking capacitor C5. Further guidance on connecting a counter is given later.

An instrument of this kind can be inadvertently left switched on when it is not in use. Low current LED D2, with its dropping resistor R8, acts as a visual reminder that current is being drawn from the battery.

Components

All the components are widely available and constructors should experience no difficulty in obtaining them. No doubt many spares boxes will already contain the necessary parts.

A good quality air-spaced variable capacitor must be used for C4. (Polythene dielectric variables reduce Q measurements by around 10 percent). Its precise value is not critical but, ideally, it should have a minimum capacitance of less than

15pF and a maximum capacitance of 350pF or more. Suitable units can often be salvaged from old radios, and one gang of a two gang component can be wired into circuit if desired. If a salvaged component is to be fitted, make sure it is clean and dry, remove any built-in trimmers, and use a testmeter, set to the highest resistance range, to check for any shorting of the vanes. A single-gang Jackson type 0 variable is ideal if a new component has to be purchased. Maplin list this item in their catalogue.

The low-value coupling capacitor C2 can be a ceramic type. In the prototype instrument it was formed by twisting together,

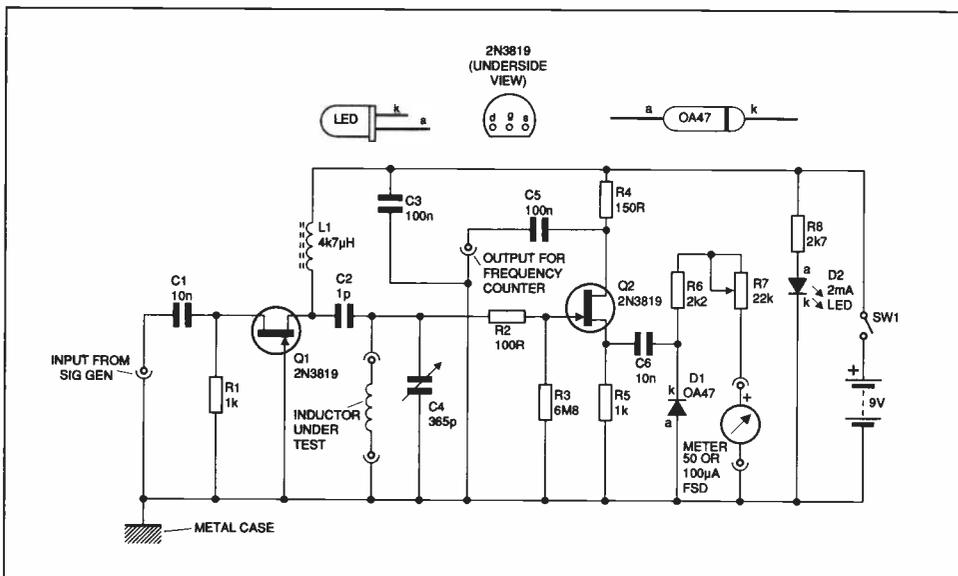


Figure 3: the circuit of the Q meter adapter

fairly tightly, lengths of plastic insulated, solid core, hook-up wire. The length of the twisted section should be about 6mm.

An OA47 is listed as the meter rectifier D1, but most germanium signal diodes should work well. Do not substitute a silicon diode. A slight improvement in accuracy was perceived when a Schottky diode was used in this position, and constructors may wish to try this. An inexpensive general purpose device should prove satisfactory.

Any test meter or moving coil meter with a full-scale deflection of 50 or 100uA will be suitable. It should have a 0-100 graduation, and a meter with a large scale will, of course, be easier to read accurately.

Provided lead lengths are not excessive, there is no need to screen the connections between the adapter, signal generator, multimeter and, if used, the frequency counter. If preferred, therefore, terminals can be fitted instead of the coaxial connectors quoted in the parts list. The output from some simple signal generators can be low, especially as they are tuned into the upper HF region. If low readings are encountered even when R7 is set for maximum sensitivity, fitting a J310 FET in the Q1 position will give more gain and boost the output. The use of this 'hotter' device will not affect the stability of the adapter unit, but its lead-out arrangement is different from that of the 2N3819, and **a length of insulated sleeving should be placed on its centre (source) lead to prevent shorting.**

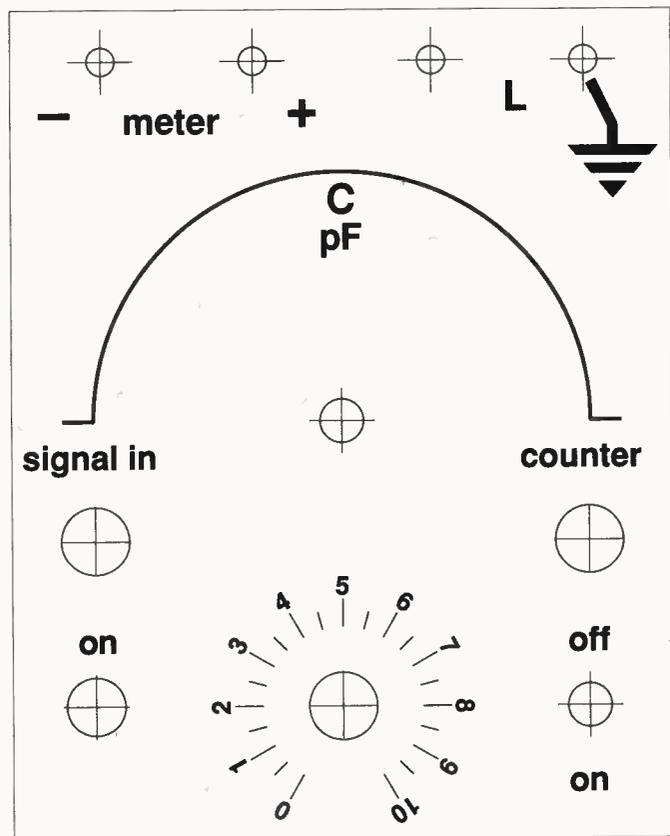


Figure 4: the component layout

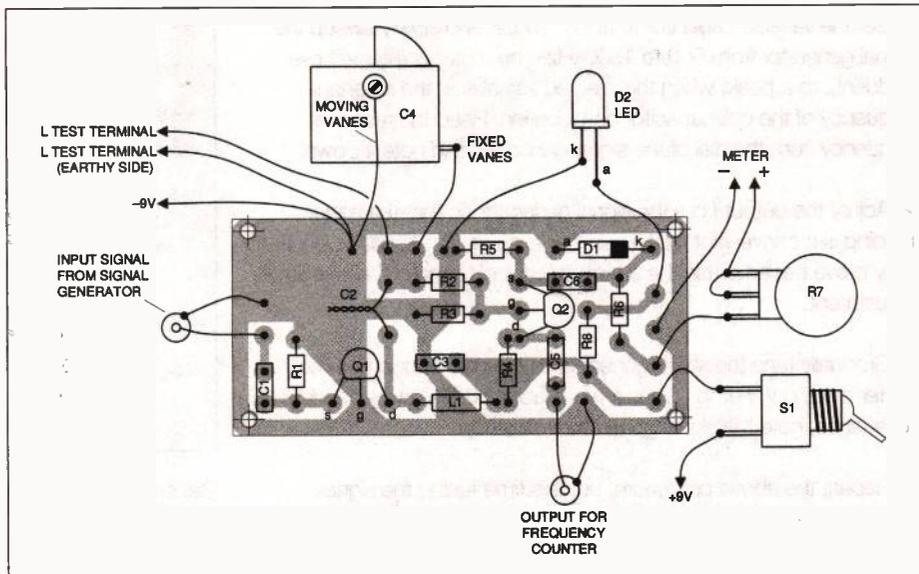


Figure 5: the front panel layout used in the prototype, approximately real size

Construction

Most of the small parts are mounted on a printed circuit board. The component layout is given in **figure 4**. Vero pins, inserted at the lead-out points, make the task of off-board wiring easier.

The PCB, together with the remaining components, is mounted on the lid of a small box, and the arrangement adopted for the prototype is shown in the photographs. The PCB is secured by means of small Perspex brackets Supaglued to the underside of the lid. The retaining clip for the PP3 battery is likewise Supaglued to the potentiometer case. It is a good idea to check the PCB for poorly soldered joints, bridged tracks or wrongly placed components before mounting it. The moving vanes of the variable capacitor are connected to the negative supply rail. If a metal case is used (this is recommended), it should be connected to the negative supply rail also.

The front panel layout is shown in **figure 5**. The panel was marked out on thin card and annotated with rub-down letters and numerals. A piece of 2mm acetate sheet, drilled jointly with the box lid, protects the card panel. Capacitor calibrations have been omitted so that constructors who wish to adopt this arrangement can mark up a copy of the panel layout to suit their own component. The 'earthy' inductor terminal is indicated on the panel so that an appropriate connection can be made when testing coils wired into equipment.

When the off-board wiring has been completed and checked, connect a fresh 9V battery. Current consumption, including that of the LED indicator, should be in the region of 7mA.

Measuring Q values

The input from the signal generator should be kept as low as possible consistent with meter readings of around 75 percent of full-scale. Too high an input **may cause** clipping of the signal and the accuracy of the measurements will be impaired (the results will err on the low side).

If a 100uA meter, or a test meter **switched** to this range, is used, the sensitivity control, R7, will have to be set towards maximum, that is, to a low resistance. If a 50uA meter is connected, R7 can be turned closer to the half-way position.

A medium wave coil is useful for getting the feel of the unit. Connect an inductor of this kind across the test terminals and proceed as follows:

1: Set the variable capacitor to about 150pF and slowly sweep the signal generator from 500 to 1500kHz. The meter pointer will rise, suddenly, to a peak, when the injected signal is at the resonant frequency of the coil/capacitor combination. Read the resonant frequency from the dial of the signal generator and note it down.

2: Adjust the output from the signal generator so that the meter reading is a convenient round number such as 60, 70, 80 or 90. It may prove easier to use the sensitivity control to make the final small adjustment.

3: Gradually tune the signal generator to a higher frequency. The meter reading will drop. When it has reached 0.707 of the reading at resonance, note the signal generator frequency.

4: Repeat the above procedure, but this time tuning the signal generator below the resonant frequency. Again, note the frequency when the meter pointer has dropped to the 0.707 position.

5: The Q of the coil can now be calculated from the following formula:



$$Q = \frac{\text{frequency at resonance}}{\text{higher 0.707 frequency} - \text{lower 0.707 frequency}}$$

The use of a round number for the meter reading at resonance just makes the arithmetic easier. 70 is a good scale marker to choose for the peak. The 0.707 point is then, near enough, 49.5, and the readings are being taken over a segment of the pointer swing where the meter is likely to be at its most linear.

An actual example should help to make the process clear. The inductor is a Toko medium wave RF coil with a quoted Q value of 70 and a nominal inductance of 330uH. The variable capacitor in the adapter is set to 150pF and a meter with a FSD of 100uA is connected.

Generator frequency for peak response (meter pointer set to read 70) = 720.48 kHz

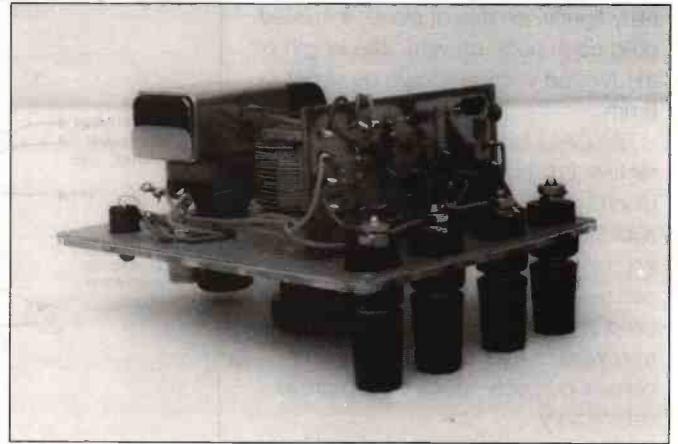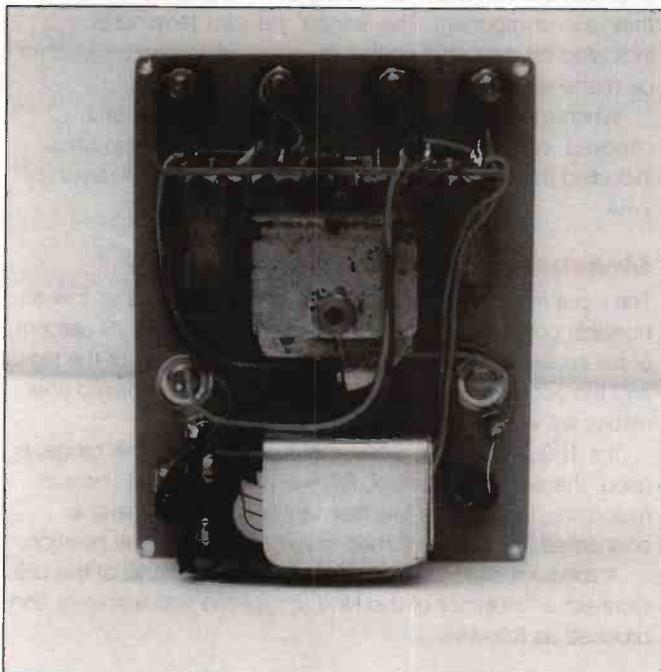Generator frequency above resonance to give meter reading of 49.5 = 726.50 kHz



Generator frequency below resonance to give meter reading of 49.5 = 716.15 kHz

$$Q = \frac{720.48}{726.50 - 716.15} = 69.61$$

The procedure takes longer to describe than it does to execute. In this instance the correlation between the manufacturer's quoted figure and the Q measurement is close. However, core setting has a significant effect on Q, especially with modern miniature coils, and the measurements can produce results which differ by up to 20 percent from the figures quoted by manufacturers.

When measuring the Q of commercial or home-made coils, it is a good idea to set any cores at roughly the mid-way position, and to set the variable capacitor to simulate the mid-point of the proposed tuning range. Intermediate frequency transformers already have the necessary tuning capacitors wired inside the screening can, and the variable capacitor in the unit should be set to its minimum value. When measuring the Q of IFTs, always adjust the cores to give a peak reading at the intended operating frequency, for example, 455 or 470 kHz.

Measuring the inductance value of coils

The variable capacitor in the unit will have to be calibrated if inductance values are to be measured. Connecting a capacitance meter and marking off the dial at appropriate round-number settings is the easiest and quickest method of doing this. Constructors who do not have access to meter of this kind can, however, use inexpensive, close-tolerance ceramic capacitors as a means of calibration. Obtain ten 10pF and three 100pF capacitors, and proceed as follows:

1: Disconnect the variable capacitor, connect up the signal generator and meter, and wire a suitable coil to the test terminals (a medium wave coil is ideal).

2: Connect one of the 100pF capacitors across the coil and adjust the signal generator to peak the meter reading.

3: Remove the 100pF fixed capacitor, reconnect the unit's variable capacitor, and adjust it to restore the peak. Mark the scale accordingly.

4: Repeat this procedure with different series and parallel combinations of the fixed capacitors until the scale is marked out. The 10pF components will, of course, facilitate the sub-division of the scale.

When the capacitor has been calibrated, the relationship between

inductance, capacitance and frequency, in a tuned circuit at resonance, can be used to determine the unknown value of the inductor. For radio frequency work, the following variant of the standard formula is a convenient one:

$$f = \sqrt{\frac{25330.3}{L \times C}}$$

where f is in MHz; L is in uH and C is in pF.

Transposing the formula to give the value of the inductor:

$$L = \frac{25330.3}{f^2 \times C}$$

Using the same Toko medium wave coil as an example, set the variable capacitor to 100pF (a convenient round number) and slowly sweep the signal generator up from 500kHz. With this particular inductor, the meter peaked at 871kHz, (or 0.871MHz). Inserting this value in the formula:

$$L = \frac{25330.3}{0.871^2 \times 100} = 333.89\mu\text{H}$$

The manufacturers quote a nominal value of 330uH, but this will vary over fairly wide limits depending on the setting of the cup core.

Harmonics

Resonant circuits are responsive to harmonics of their fundamental frequency, and the swing of the variable capacitor will usually cover at least the second, even on the lower frequency ranges. Fortunately, the instrument is far less sensitive to harmonics, and provided the input from the signal generator is kept reasonably low, it will be very obvious when the fundamental is being injected. This is, of course, more of a problem when coils of unknown inductance are being checked and it is not possible to estimate the appropriate capacitor setting and the likely resonant frequency. In these cases, the generator must be slowly swept over its ranges until the dramatic peaking of the meter occurs at the fundamental frequency.

In-situ measurements

The adapter can be used to check coils wired into equipment. Disconnect the equipment from its power supply before making any tests, and keep the leads to the coil as short as possible.

If the inductor is at 'earth' potential as far as DC is concerned,

and if there are no signals present (other than the test signal from the generator), its Q can be measured while it is operating. The adapter imposes a minimal loading on the coil under test, and it is possible to observe the rise in Q with increasing amounts of positive feedback in regenerative circuits.

Unloaded Q factors, whether measured or quoted by manufacturers, can seldom be realised in practice. The damping effects of transistor input and output impedances, and other circuit elements, inevitably reduce the operating Q level. This is particularly evident with miniature coils which usually have tightly coupled impedance matching windings.

Using a frequency counter

Unless the signal generator is of a very high quality, a frequency counter will considerably improve the accuracy of the readings, particularly in the case of HF coils with a high Q factor. (With inductors of this kind, comparatively narrow 0.707 bandwidths have to be measured on signal generator ranges where the calibration is often in fairly broad increments.) Accordingly, provision is made for connecting a unit of this kind to the adapter. @B:Do not attempt to overcome any lack of sensitivity in the frequency counter by increasing the input from the signal generator beyond that suggested earlier. If counter-triggering becomes erratic, perhaps when the generator is tuned to the '0.707 position', connect the counter directly to the unattenuated output of the signal generator.

PARTS LIST

for the Q Meter Adapter

Resistors

All 0.25W, 5 percent tolerance

R1, R5	1k
R2	100R
R3	6M8
R4	150R
R6	2K2
R7	22k linear potentiometer
R8	2k7

Capacitors

C1,C6	10nF ceramic
C2	1p5 ceramic, or twist insulated wires together (See text)
C3, C5	100nF ceramic
C4	365pF air-spaced variable capacitor (See text)

If the variable capacitor is to be calibrated by the substitution method, ten 10pF and three 100pF close-tolerance ceramic capacitors will also be required.

Inductors


L1	4700uH miniature RF choke.
----	----------------------------

Semiconductors.

Q1	2N3819 (See text)
Q2	2N3819
D1	0A47 (See text)
D2	low current (2mA) LED

Miscellaneous

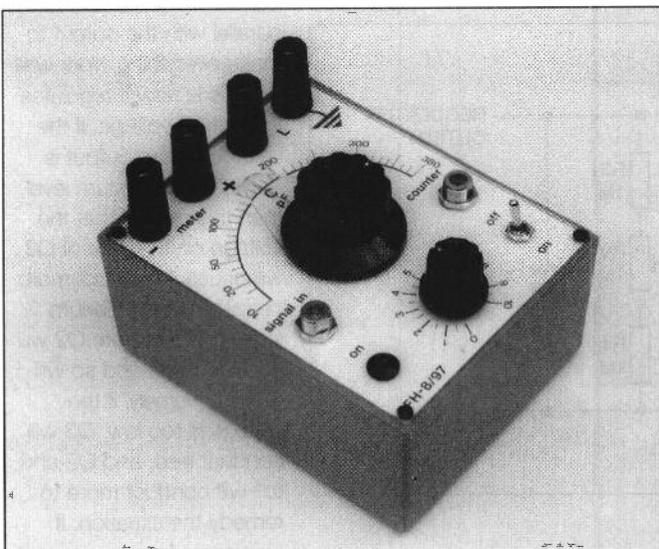PCB making materials, Vero pins and hook-up wire. Four terminals and two co-axial sockets. Miniature toggle switch, LED holder, PP3 battery and connector. Metal or plastic case, front panel making materials and two control knobs.



TECH TIPS

Different ways of doing things

Andrew Armstrong

Many people who work in the field of electronics develop their own collection of design fragments which can add up to a useful part of a larger design. This is the first of an occasional series of circuit techniques and design hints.

The origins of most of these circuits stretch back into the depths of time, to past design projects and problems that needed solving - not necessarily by the circuits here, but on a path that passed through them along the way. Other people will have independently encountered and solved the same problem, or similar ones. If, as this series progresses, I find the odd useful one which does not fit well into the magazine, I will try to find time to put it on to the website.

If you are looking for something specific, email me at eti@aaelectron.co.uk or drop me a line c/o Nexus House (see page 76) and I will include anything I can find which is relevant in a subsequent part.

Microamp voltage regulation

The range of single-chip voltage regulators is excellent, and for most applications there is a suitable one available at a reasonable price. The use of discrete regulator circuitry has rightly declined almost to zero. Occasionally, however, there is a requirement which cannot be met by an available chip, and then discrete circuitry is necessary.

One such requirement involved a battery operated device, which had to operate for a minimum of one year from a PP3 battery. The circuit needed between 4.5V and 5V, so regulation was definitely needed. The specification required a very low drop-out voltage, so that the equipment would continue to function until the PP3 battery was down almost to the regulator output voltage, and that it should consume as little current as possible to operate itself.

These two characteristics were not, at the time, included in any easily available regulator. One or two came near, but in addition to having a slightly higher power consumption than was desirable, available re-entrant regulators also increase their power consumption dramatically as the input voltage gets very close to the output voltage. This is because they employ a pnp transistor with its emitter to the input positive supply, and its collector supplying the positive regulated output. When the transistor has to be switched on to the point of saturation, the base current must rise considerably. In addition, when the transistor is fully saturated, it is difficult to limit the base current to only that which is actually required.

At the time I could find no re-entrant regulator chips using mosfets and possessing the required characteristics. I did see one fairly recently - it was only available in surface mount and cost too much, but otherwise it was a possible candidate.

The circuit shown in **figure 1** does what is required, although it has its limitations. It uses a p-channel mosfet as the series pass element, so that the voltage drop across the regulator can be arbitrarily small if a device with a suitably low on resistance is chosen, and if the input voltage is sufficient to bias it fully into conduction. Because the gate requires no actual current for it to remain switched on, the only requirement for drive current is that the mosfet must be capable of switching off, so there must be a resistor which discharges the gate bias voltage. The current through this resistor may be very small, but the smaller it is, the slower will be the switch-off, and therefore the less will the regulator will be able to respond to rapid reductions of load current.

In extreme cases the delay could be sufficient to cause oscillation, in less severe cases there may be an unacceptable level of overshoot if the load current suddenly reduces.

Therefore, it may be necessary to add a large value capacitor, 100uF or even more, in parallel with the output to make everything work well.

This is how it regulates the output voltage: if the voltage on the output is above its equilibrium level, then this means that the voltage on the gate of Q3 will cause it to conduct more heavily than equilibrium level, and therefore Q2 will conduct less, and so will Q1. Conversely, if the voltage is too low, Q3 will conduct less, and Q2 and Q1 will conduct more to remedy the situation. If

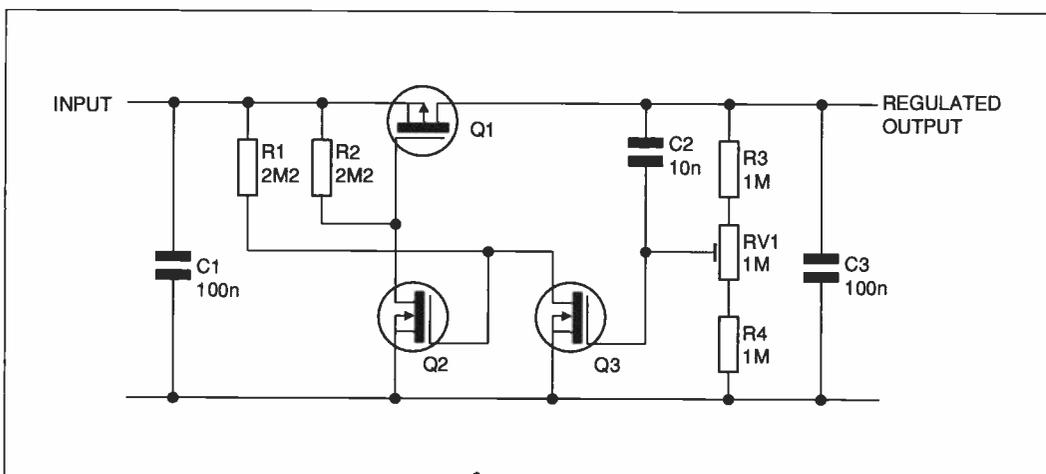


Figure 1: a very low power mosfet voltage regulator

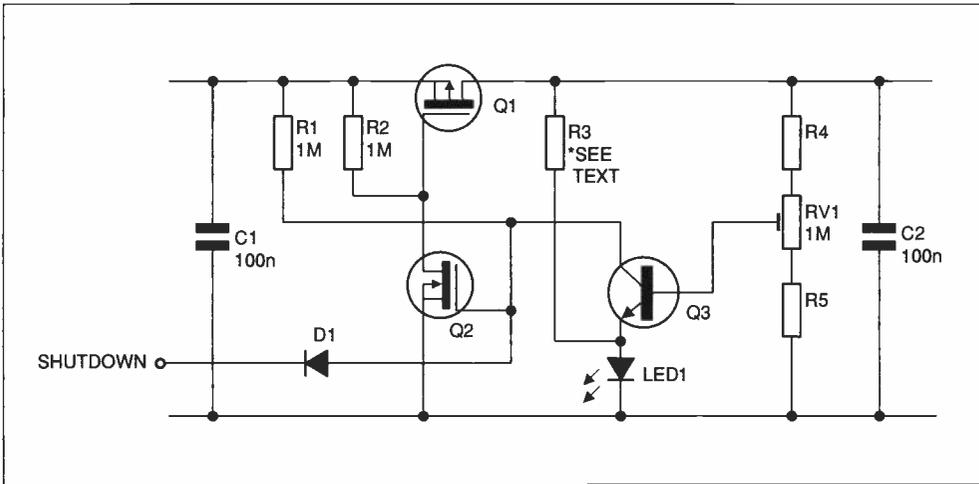


Figure 2: a low power voltage regulator with improved stability

there is insufficient input voltage to meet the set output voltage, then Q3 will be switched off, Q2 and Q1 will be switched fully on, and the output voltage will be very close to the input voltage. Inspection of the circuit reveals that the current drawn to operate the regulator does not rise particularly in this mode.

Tempco

There is no actual voltage reference in the circuit. For its voltage reference it relies on the turn-on voltage of Q3. This has four main consequences. First of all, the cost is minimised, because a voltage reference is not needed. Secondly, the current consumption is minimised for the same reason. Then, it is unavoidable to have an adjustment in the circuit because of the tolerance of mosfet turn-on voltage, even for fets from the same batch. Finally, and perhaps most seriously, the turn-on voltage of a mosfet is temperature sensitive, so that if a precise regulated output is needed then it will not be good enough.

This last problem is addressed in the circuit of figure 2, which is not much more expensive in terms of parts cost. This

employs the little-known property of a light-emitting diode that it can act as a reasonable low current voltage reference. If approximately 50 uA is fed through a red LED, the voltage across it will be about 1.8V, and this will not be nearly so temperature dependent as the turn-on voltage of a mosfet.

The current to drive the LED is drawn from the regulated output of the circuit, so that the current will remain constant and hence voltage variations will be minimised. Variation of regulated voltage with temperature is not eliminated because of the

variation is base/emitter voltage of Q3. If necessary, an approximate compensation could be made by adding a diode in series with R5, or a carefully chosen thermistor in parallel with it. However, if a very precise regulated output is required, then it may be better to use a low-current voltage reference and a low-current op-amp to control the output. This circuit is better used when low-cost and a reasonable degree of regulation are the main criteria.

The circuit in figure 2 also illustrated the possibility of shutting the circuit down by the use of an external logic signal. If the cathode of D1 is taken to logic 0, then the circuit will switch off, making it suitable for use in cases where the load need only be energised occasionally.

The value of R3 should be chosen to pass approximately 50uA through the light emitting diode. This figure may be chosen differently, according to the size of LED used, but 50uA is a reasonable average.

The shut-down capability illustrated in figure 2 could also be used with the circuit in figure 1 but has not been shown there, in the interests of simplicity.

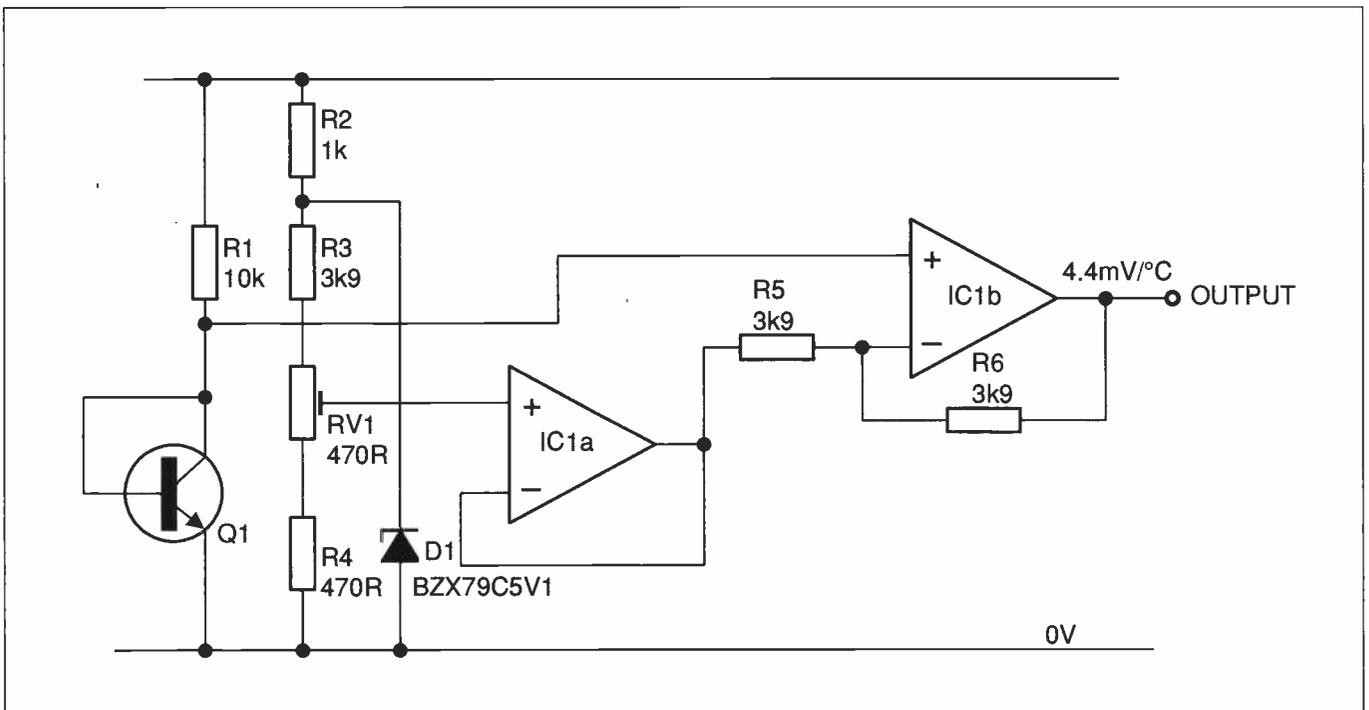


Figure 3: using a transistor as a good, low-cost temperature sensor

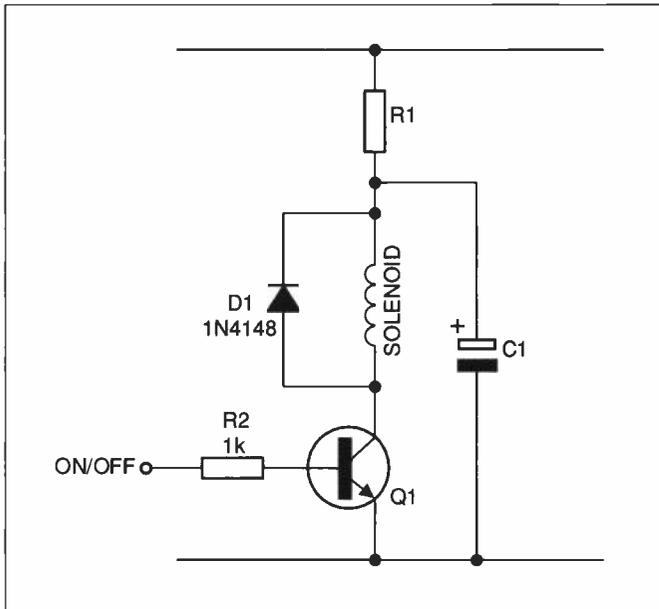


Figure 4: a simple way to reduce the power dissipated in a solenoid

Temperature measurement

There are occasions when the variations of base/emitted voltage in a transistor with temperature can be a benefit rather than a nuisance. It might be considered a benefit when a transistor is used as an amplified diode to temperature-compensate the output stage of a class A/B amplifier. Closer consideration reveals that if the output stage were not temperature sensitive, then the temperature sensitivity of the amplified diode would no longer be necessary.

However, it is possible to use this temperature variation to measure the actual temperature. If a constant current is fed through a silicon P-N junction, then the voltage across it changes the rate of 2.2 mV per degree Centigrade. One snag associated with this is that the voltage drop at a given temperature is not necessarily the same for different

samples of the same type of diode or transistor run at the same current. It is only the change which is predictable, so that if a diode or transistor is to be used for accurate temperature measurement, then a calibration adjustment is required.

There is a way to avoid the need for a calibration adjustment, by using the fact that, whatever the precise voltage drop of the device at a given temperature, the amount by which it changes when the current is varied does remain constant. Therefore, if the current through a diode is varied over a range of 10 to 1, and the voltage at the lower current subtracted from the voltage at the higher current, the result will be a voltage relating to the actual temperature with no calibration required. However, this approach required significant circuit complexity, and would only be suitable for use if a large number of temperature measurement channels were used. In this case, the cost and delay associated with calibrating them would be considerable, while the extra circuit complexity would not grow linearly with the number of channels.

For most projects likely to be encountered in ETI, only one or two measurement channels are likely to be needed, so that the use of a calibration control will result in the simplest solution. The circuit of **figure 3** illustrates a way in which this property may be used to provide a temperature measurement. It uses more components than would be used with a precision temperature measuring device such as the AD590, but the temperature sensing device is very much cheaper than the overall cost of the circuit is very competitive.

Further, if IC1B were wired as a comparator, then with no extra complexity this circuit would form a thermostat. This type of thermostat would be good enough to control the temperature of a room, or for example of a PCB etching tank, although it may not be suitable for precise laboratory applications. It could certainly be used to provide a cheap substitute for the now-obsolete **LM3911**. The temperature setting would use a potentiometer

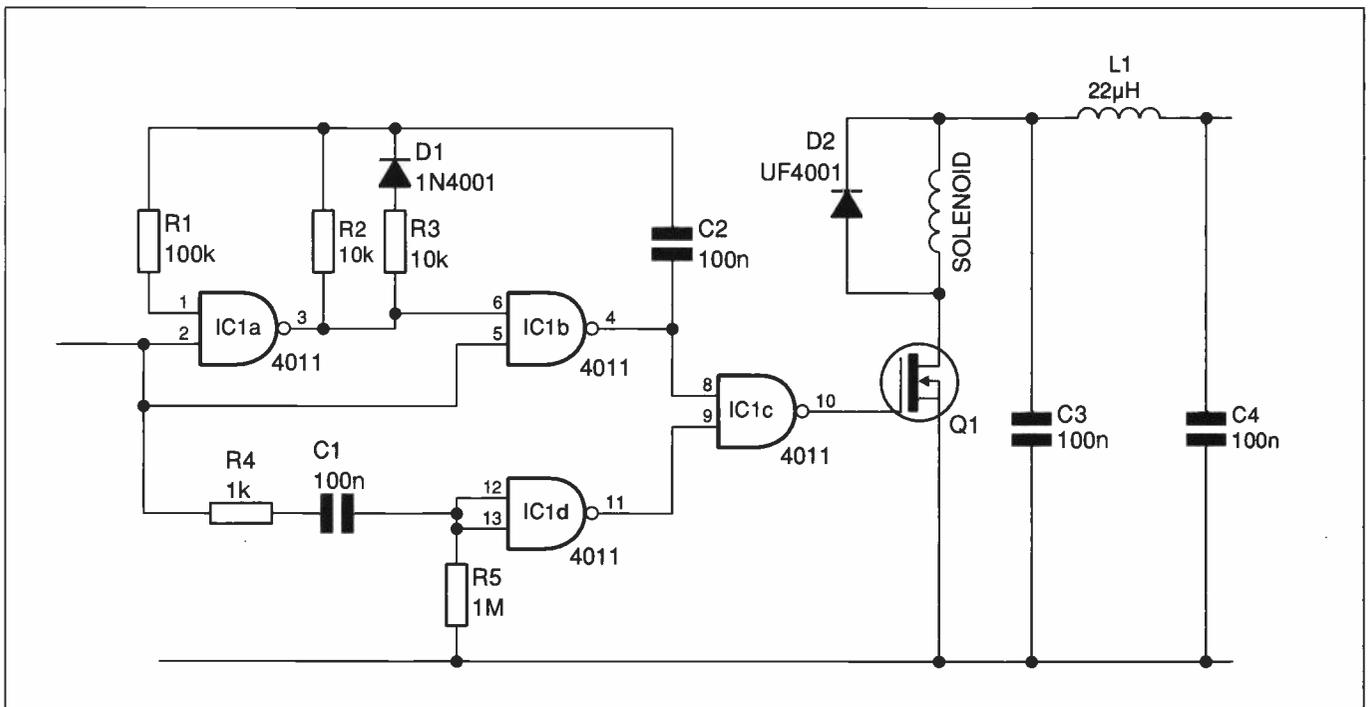


Figure 5: a way to minimise the power drawn by a solenoid where power consumption is critical

instead of a preset in the calibration position, and actual calibration would be carried out by positioning the knob to match the actual temperature to the scale.

Temperature reduction

If used in the ON position for a long time, solenoids get hot. The first time I encountered this problem was when I build a comprehensive charging and control system for the secondary battery supply in a large camper van. What I wanted to do was to connect the subsidiary battery to the main battery with the lowest possible

resistance path when the following two conditions were satisfied: the vehicle was running and charging its main battery, and the voltage difference between the two batteries was not so great that a dangerous current would flow. The purpose of this was to permit the subsidiary battery to be charged as fully as possible as rapidly as possible while the vehicle was actually running, without any risk of compromising the capability of the vehicle to start even if use of the interior lights etc. had completely flattened the secondary supply.

To this end the secondary battery was charged via two separate paths. The first was via a diode with a series current-limiting resistor from the switched side of the ignition, and via a starter solenoid directly from the main battery. The solenoid was only switched on in the above specified conditions.

This worked very well, with the secondary battery rapidly being recharged to a high-enough voltage for it to be safe to switch on the starter solenoid, and the charging thereafter proceeding rapidly.

The problem which became apparent was that the starter solenoid draws a lot of current to operate its coil, and becomes dangerously hot if left switched on for a protracted period. The solution I employed at the time was to use a spare cmos gate as a delay timer to switch a large wire-wound resistor in series with the coil after it had time to pull in properly. The circuit shown in **figure 4** achieved this end more simply. The value of C1 is chosen so that it has enough charge to guarantee to energise the solenoid fully, while the value of R1 is chosen so that the required holding current, but not much more, will flow.

Two interesting points about this circuit are that, although the overall dissipation is much reduced, unnecessary heat is still generated by R1. The second point to note is that, although the current flowing in the solenoid may be substantial, a 1N4148 diode would normally be sufficient to pass the current flowing in the coil when Q1 is switched off, thus protecting Q1 from destruction by voltage spike. Normally, diodes can pass a brief peak current of 10 or more times their continuous rating without any damage, so long as the duration is within the limits specified for that type of diode, and the device is allowed to reach thermal equilibrium before another such pulse is applied.

It is not only vehicle starter solenoids which can become excessively hot if energised continuously. Even if the heat is within reasonable limits, a lot of power is wasted if a solenoid is energised at full power

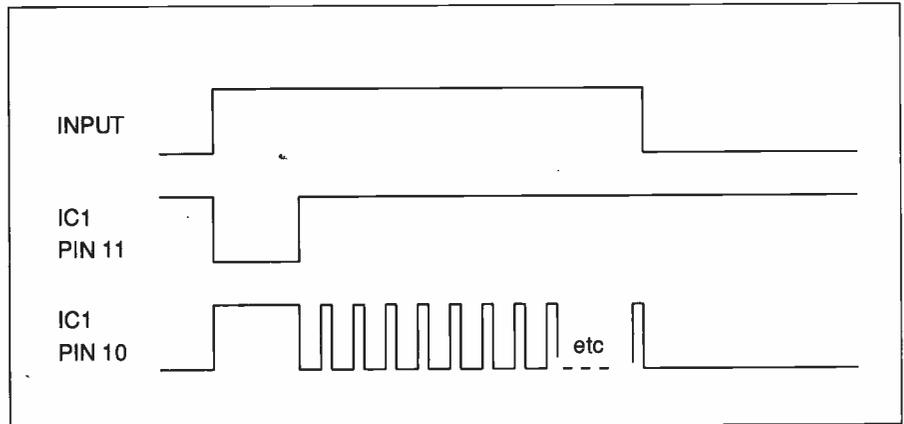


Figure 6: timing diagram given by the circuit of figure 5

continuously, because the holding current is normally much less than the pull-in current.

Another way to reduce the power consumption, by as much as possible if this is the main requirement, is shown in **figure 5**. What this does is to switch the solenoid on continuously for a short period, then subsequently to mark:space ratio modulate the current to provide an adequate holding current. This is like a switched mode power supply, with the solenoid acting as both load and magnetic energy storage element.

If the input is at logic 0, then IC1 pin 4 is forced to logic 1, and IC1 pin 11 remains at logic 1 in its normal state, so that the output remains off. When there is a 0 to 1 transition on the input, IC1 pin 11 switches from 1 to 0 for a time period determined by the values of R5 and C1. This period is chosen to be sufficient to pull in the solenoid. The function of R4 is to limit the current which will flow when the input returns to logic 0, when the right hand pin of C1 has discharged to 0V via R5. The current to restore this point close to 0V instead of the -5V it would have been, flows in the input protection diodes of IC1d - and limiting this current is good for long term reliability.

After this period, which is about 150ms with the values shown, the output of IC1 pin 11 reverts to its normal logic 1 state, and the output is now controlled by the oscillator. This is illustrated by the timing diagram in **figure 6**.

The oscillator is of a conventional type, but has its mark:space ratio modified by the addition of R3 and D1. The values chosen should make the on time of the output about half the off time. The resistor value may be altered to set the current to the level actually required to hold the solenoid in reliably.

The oscillation frequency has been chosen to be a reasonable compromise between the need to minimise the ripple on the current flowing in the solenoid, and the need to minimise losses due to circulating currents in the core, which is not laminated or arranged in any way to reduce circulating currents in a dc solenoid. The frequency may be altered to suit specific solenoids being driven.

When the input returns to logic 0, the oscillator is immediately disabled, and the output switches off.

The catch diode for this circuit is of a higher rating than that for **figure 4** because it has to conduct for two thirds of the time that the solenoid is ON, rather than one pulse occasionally.

Finally, L1 and C4 prevent switching noise from leaving the confines of the circuit and radiating from the power supply connections.

Bart's BATH DUCK

Bart Trepak's scalded foot gave him the idea for a bathwater warning device mounted in the most appropriate fashion, and using a blue LED for instant temperature identification.

I guess that I have always been a sucker when it comes to electronic gadgets - show me a corkscrew with a built-in digital wine thermometer or a can opener with a built-in calculator and I am hooked. Of course, some gadgets are more useful than others, so my fascination is usually limited to "I wonder how they managed to fit that in there?" I stop short of actually buying unless I can see a clear need for it or can adapt it for some purpose useful to me. Naturally, my fascination extends to electronic components but there I am far more easygoing because of the relatively low cost. The very fact that a new component has become available is usually enough to persuade me to send off for one first and think up a use for it later.

LEDs are a particularly good example. I suppose it is the magic of seeing a piece of plastic glow red or green when a current is fed into it. Seeing a new, blue one listed in a catalogue was something I could not resist. Having obtained a few, the question then became "what I could do with them?" that I could not do with a cheaper red or green one. I was idly pondering this question the day I stepped into a scalding hot bath . . .

"Eureka" I shouted (it was actually "You *****", but it sounded enough like the exclamation reserved for great discoveries to pass unnoticed by other members of the household) as the solution dawned on me - faster, incidentally, than it did on Archimedes. Luckily, I retained enough presence of mind not to run down the street in my birthday suit, but then my discovery was not quite as earth shattering (or as profitable) as that of the great man. I realised that what I needed to do, apart from put my foot under the cold water tap, was to build a device that would display the temperature of the water before I got in and my toe found out the hard way.

A full blown thermometer was obviously an overkill, but a simple device which would show if the water was too hot for comfort would be most welcome. Since a freezing cold bath is only marginally less unpleasant than a scalding hot one, a three-LED display would be ideal. What better than a "cold" colour like blue to show TOO COLD, a "hot" red to show TOO HOT and a green LED to show when the temperature was just right.

Sensor

The first requirement is a sensor. We are spoilt for choice nowadays, with temperature sensing devices from the humble silicon diode to fancy integrated circuits with matching prices which provide an output voltage or current proportional to temperature.

The best sensor to use for this project, however, is a thermistor. Not only does this produce a relatively large output change for a given temperature, so that the signal does not need further amplification, but it is also relatively cheap. The only disadvantage is that it is non-linear but, since we are not displaying the actual temperature but merely determining if it is too high or too low, this is not important.

A thermistor is basically a device whose resistance varies with temperature. Devices with positive or negative temperature coefficients (PTC or NTC) are produced, although the latter seem to be more generally available, so I have used this type for this circuit. With these, the resistance changes inversely with temperature, so that, as

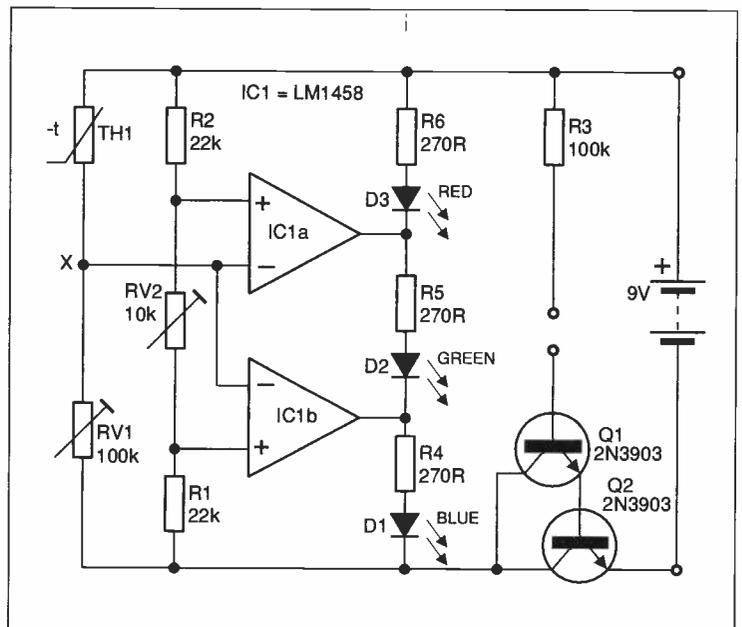


Figure 1: the Duck circuit

the temperature increases, the resistance falls. The value is normally specified at 25 degrees C, and devices are available with resistance values of a few hundred to tens of thousands of ohms which fall to a few ohms (or a few hundred ohms) at a high temperature. The precise value at any particular temperature is not too important in this application as virtually any NTC thermistor could be accommodated simply by changing the value of resistor RV1. Since the unit must be battery operated (mains electricity and bathrooms should, famously, be kept well apart) the current consumption of the circuit should be kept low. Therefore, a higher value of thermistor resistance is preferable.

The complete circuit of the bath temperature indicator is shown in **figure 1** and it can be seen that the thermistor is connected in series with a resistor RV1 across the 9V battery supply, assuming that Q2 is switched on. The voltage at the junction of the two resistors (marked X) will therefore depend on the relative values of the resistors so that, if they both have the same value, the voltage will be one half of the supply, or 4.5 volts. If the temperature rises, the thermistor resistance will fall and the voltage at point X will rise above 4.5 volts. If the temperature falls, this voltage will fall. Incidentally, if a PTC thermistor were to be used, the relative positions of RV1 and TH1 would need to be altered, with the thermistor placed in the lower arm (connected to the negative rail).

“cleanly” between the two states, especially if the input voltage changes slowly. But this is not necessary in this circuit.

Because everybody’s idea of what is too hot or too cold varies, the two voltages representing these conditions must be made variable and since the voltage representing TOO HOT will always be higher than that representing TOO COLD, these can be obtained by a single potential divider chain consisting of R1, RV2 and R2. If RV2 is adjusted to minimum (zero) resistance, then the voltage at the non-inverting inputs of both comparators will be the same and since R1 and R2 have equal values this will be the mid-supply voltage. As RV2 is increased in value, the voltage across it will increase so that the voltage at the non-inverting inputs of both comparators will vary symmetrically about the mid-supply voltage. R1 and RV2 therefore sets the lower trip level and R2 and RV2 the upper one with RV2 effectively defining the range of temperatures which is considered to be not too hot or not too cold.

To see how this circuit works, suppose that the temperature is very low so that the voltage at point X is below the value set at the junction of R1 and RV2. The inverting inputs of both comparators will therefore be below their non-inverting inputs so both comparator outputs will be high at + 9 volts. In this condition, only LED D1 (the blue LED) will have a voltage across it and will therefore light with R4 limiting the current to a safe value.

As the temperature increases, the voltage at point X will rise until it becomes higher than that set by R1/RV2 but lower than that due to R2/RV2 and the output of the lower comparator IC1b will therefore switch to 0 volts causing LED1 to go out. The output of IC1a will however remain high so that LED D2, the green LED, will now light to signal that the temperature is alright. Should the temperature continue to rise, the voltage at X will eventually also exceed that set by R2/RV2 so that the output of comparator IC1a will also go low, causing LED D2 to extinguish and LED D3 to light, indicating that the temperature is too hot.

In a real circuit, things would not normally work so smoothly, because the outputs of most op-amps do not switch between the full supply rails and it would not be unusual for the output to swing only to within 2 volts of the negative line. This would normally mean that when the

temperature was at the safe value and output of IC1a was high, the output of IC1b would be low but would only fall to around 2 volts. This could still be enough to light an LED which has a forward volt drop of 1.5 - 2 volts. In this situation, both the lower LEDs D1 and D2 would come on - which is not what is required. The answer is either to use a more expensive CMOS op-amp for IC1, so that the outputs swing much closer to the supply rails, or to insert a low voltage zener diode (2.7V or 3.3V) or a few forward biased silicon diodes between R4 and D1 to increase the effective forward voltage drop of the LED. Luckily, blue LEDs, which are manufactured from silicon carbide and not gallium arsenide as is the case with red, green and yellow ones,

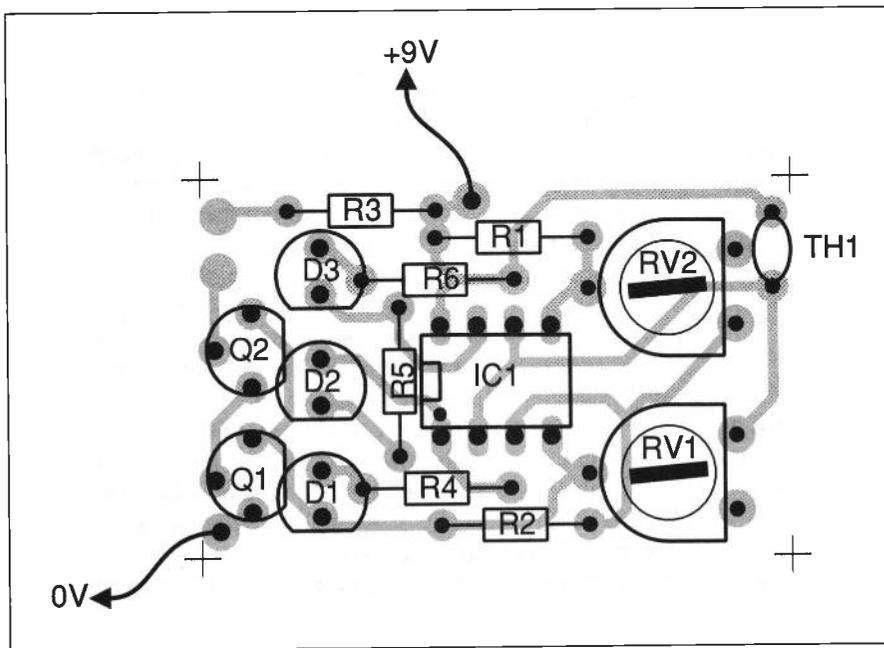


Figure 2: the component layout

Comparators

To determine the category into which the water temperature falls and which LED should be lit, the voltage at point X needs to be compared with a voltage which represents the “TOO HOT” state and another which represents the “TOO COLD” state. This is done by means of two comparators. These are basically op-amps with no feedback, so that the gain is very high and any small imbalance in the voltage at the two inputs will result in the output limiting at the positive or negative supply rail, depending on which input has the higher voltage. Sometimes a little positive feedback is added by connecting a high-value resistor from the output to the non-inverting input to cause the output to switch

exhibit a higher forward voltage drop of around 2.5 - 3 volts. In this case, the LED will either not light or it will glow only very faintly and no other components should be required. This is a point to bear in mind should you want to build the circuit using a cheaper yellow or amber LED for D1.

Switch

It was envisaged that the circuit together with the battery would be fitted into a waterproof box of some kind and simply allowed to float in the water with the thermistor either on the outside or in contact with the wall of the container where it would monitor the temperature of the bath water. However, a battery-powered circuit of this sort which draws a current of 10 mA or so has to be fitted with an on/off switch if the battery is to last any reasonable length of time, but most small switches such as sliders or toggles are not waterproof, so a different method of on and off switching had to be found.

Water is a pretty good conductor of electricity so the solution adopted here is to use a simple touch switch circuit consisting of two transistors connected in Darlington configuration, which produces a transistor with a very high gain, together with two contacts mounted on the surface of the "box", plus a series resistor. The contacts should be arranged so that when the box is placed in the water, they are bridged, causing a small base current to flow into the first transistor Q1 resulting in the second transistor Q2 conducting heavily and effectively switching on the supply for the rest of the circuit. When the box is removed from the water, the contacts will no longer be bridged, so the transistors will switch off, saving the battery. The contacts can easily be sealed to prevent water from entering the box and should be positioned sufficiently far apart to prevent them being bridged accidentally by drops of water and surface tension remaining on the box when it is removed from the water.

Construction

A suitable printed circuit board layout is given in **figure 2** which is small enough to allow the device to be fitted into almost any sized box which will accommodate the PP3 battery and construction should not present any problems even to a beginner. The thermistor will probably need to be connected to the circuit board with flying leads to allow more flexibility in positioning, as will the sensor pads, so that a few centimetres of insulated wire should be soldered to the appropriate points on the circuit board to connect these components.

Once construction of the board is complete, the two preset resistors should be adjusted with RV2 initially set to minimum resistance and RV1 to maximum. With a 9-volt PP3 battery connected and the thermistor placed in water which you consider to be at the correct temperature for a bath, RV1 should be adjusted to give a voltage of around half the supply across it. Next, place the circuit in water that is just about bearable and adjust RV2 until the RED LED goes out and the GREEN LED lights. Placing the thermistor in cold water will automatically ensure that the BLUE LED lights. To ensure that the circuit remains switched on while these adjustments are made, the sensor pads may be bridged by touching them with wet fingers or

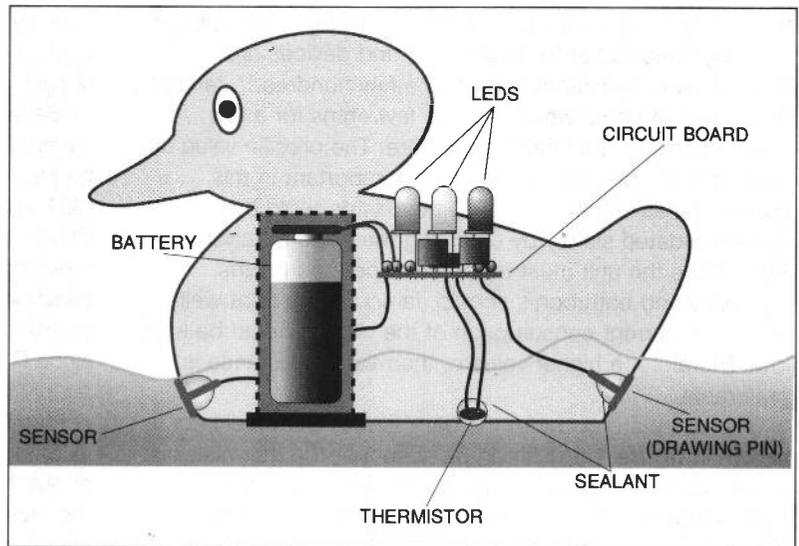


Figure 3: a suitable internal arrangement in a duck

by temporarily soldering the two leads together. The conductivity of the water may also upset the adjustment, especially if a high resistance unencapsulated thermistor is used so that it is important that water is not allowed to bridge the thermistor leads. The thermistor may be placed in a thin polythene bag when it is dipped in the water while the circuit is set up.

Once the circuit is working satisfactorily, it should be fitted into its "box". The thermistor should be mounted adjacent to the wall of the box which will be in contact with the water and in good thermal contact with it which may be difficult to achieve. Better still, a small hole may be drilled in the box to allow the thermistor to protrude into the water. If this is done, the circuit will respond better to changes in the water temperature but the hole for the leads will need to be sealed with Araldite or a silicone sealer (available in most DIY shops for sealing gaps around sinks and baths) to prevent water from entering the box. A thin smear of adhesive should also coat the component itself to prevent it being "short circuited" by the water if the thermistor is an unencapsulated type.

The sensor pads may be made by drilling two small holes in the box and pushing drawing pins into them. If possible, use ones that have been plated which will prevent them from rusting and arrange them on the box so that the water will drain from them when it is removed from the bath. If possible, do not place them on one face as this could result in the circuit being switched on if left on a wet surface or one which became wet of which there are many in a bathroom. The distance between them is immaterial, but should be at least a centimetre or two and they should be connected to the appropriate points on the printed circuit board by flying leads.

It is important that the circuit is housed in a waterproof box which can of course be any shape as long as it floats in an upright position with the thermistor and sensor contacts submerged and the LEDs showing. For this, perhaps, the most appropriate shape is a duck or a toy boat (which can always double as a toy if you are into playing with such things in the bath!). The most important requirement is that it has a tightly fitting cap which covers an opening large enough to enable the PP3 battery to be inserted and changed. A look along the shelves in a supermarket will reveal many suitable plastic containers

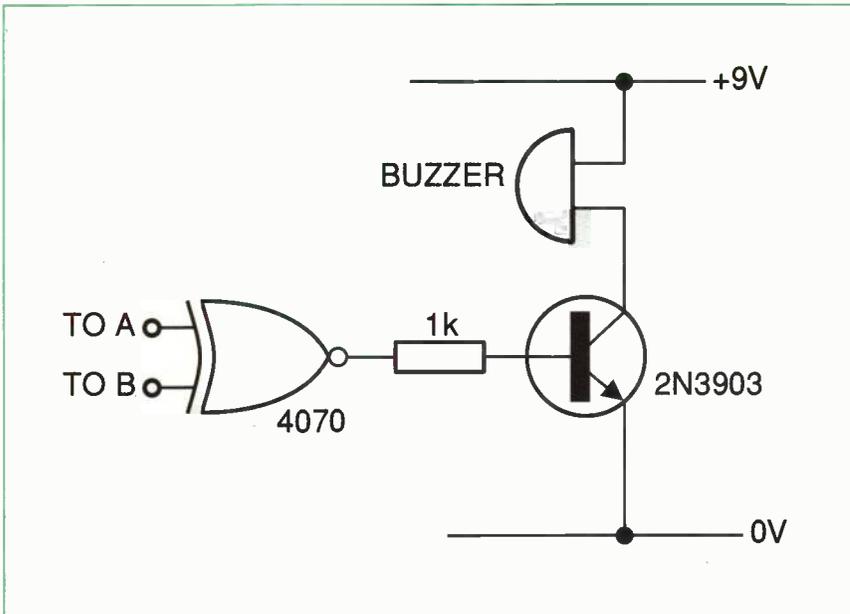


Figure 4: adding an over/under temperature alarm

such as shampoo bottles, etc. If the chosen one is round and could therefore float in any position, it can be suitably weighted down to ensure that it floats in the correct position with the thermistor and the contacts always submerged. The battery itself will probably act as a suitable weight especially if it is secured so that it cannot move about inside the box. The exact details will depend on the size and shape of the box and are therefore left to the ingenuity of the constructor, but figure 3 shows the general idea.

The prototype was built into a hollow polythene duck into which the circuit was fitted. The "battery compartment" was made from a film container which is just large enough to fit a PP3 battery and connector and has a tight fitting cap. This was inserted into the base of the duck by cutting a suitable diameter hole and sealing any gaps around the container with sealant. Note that the circuit had to be calibrated **before** it was fitted into the duck to avoid the necessity of making further holes in it to gain access to the pre-sets.

Other applications

The circuit is not limited to showing the temperature of a bath and may also be used for displaying the temperature of the water in a hot water tank or the air in a room or freezer but for this application RV1 may need to be re-adjusted. It may also be possible to mount it on a mixer bath (or kitchen) tap instead and in these cases, it is not too important to have a waterproof case. Because the sensor pads will not now be immersed in water, a more conventional on/off switch such as a push button will need to be fitted in place of the two transistors.

Providing the circuit is not used in damp or wet conditions, a mains adapter could be used enabling the unit to be powered continuously. The circuit could then be used as the basis of a dry-condition over/under temperature alarm by the addition of a buzzer. Since the outputs of the comparators are both high or both low when the temperature is outside the set limits, and only assume different levels when the temperature is correct, an exclusive or gate connected to these points will give an


output high only at this time. Connecting a buzzer so that it switches off in this condition as shown in figure 4 will therefore sound the alarm when the temperature drifts outside the set limits. It should be remembered that the output of most op-amps does not drop to zero when the output is low so that a further potential divider may be required between points A and B and the logic gate to provide recognisable low logic levels to the gate.

As well as providing over/under temperature monitoring or warning, it is also possible to replace the thermistor with, say, a light dependant resistor (LDR), in which case the circuit would indicate if the light level at a particular location was suitable for (for example) photography or environmental monitoring. In general the value of any parameter such as temperature, light level, pressure, weight etc. could be displayed provided a suitable

sensor which converts the parameter in question to resistance can be devised.

Editor's note: an LED-scale sensor circuit built into a tobacco tin and detecting hot water level in the domestic tank has been the means of avoiding bathtime conflicts around the editorial household for many years. It beats us why they don't come fitted as standard. Now: who is going to send us a design for an indicator that warns you when the shower is about to run freezing cold - before it does it?

PARTS LIST for the Bath Duck	
Resistors	
R1	22k
R2	22k
R3	100k
R4	270R
R5	270R
R6	270R
RV1	100k
RV2	10k
Semiconductors	
IC1	LM1458
Q1, Q22	N3903 npn
D1	Blue LED
D2	Green LED
D3	Red LED
Miscellaneous	
TH1	Thermistor (see text)
Printed circuit board, 8-pin dill ic socket, battery connector, etc.	

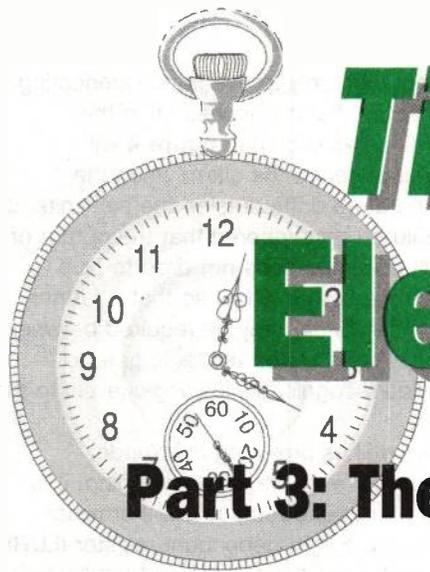

Timing in Electronics

Part 3: The long and the short of it

Owen Bishop

Divider chains can be used to prolong timing periods. Two demonstration boards - a divide-by-60 chain and a 15-minute timer are included, with programming examples for the 4018, 4541 and Basic Stamp.

On the previous part of this series in issue 7, I described a practical crystal clock running at 1Hz. The crystal naturally vibrates at high frequency, and we use a binary dividing chain to slow down the oscillations to more useful frequencies. With a 32.768 kHz crystal we use a 15-stage binary dividing chain to produce the 1-Hz output. You can also use 4.194304 MHz crystals and a 22-stage binary chain to produce 1Hz. In both examples, the crystal frequencies are predetermined to produce a convenient 1-Hz signal after repeated binary division.

The 555 timer described in the first article in issue 6 also runs at 1Hz and needs no dividing chain. This is a reasonably stable timer because we can use a polycarbonate capacitor for frequencies around 1Hz. Polycarbonate capacitors are stable, have low tempco and are made with 1 percent precision. In any case we can include a trimmer resistor in the circuit for final adjustment to exactly 1Hz or whatever other frequency is required.

Unfortunately those ancients of Babylon who pioneered our units of time were not 'binary-minded'. They worked in sixties, so when we move from seconds to minutes and hours, we have to leave binary behind. It would be possible to cut a crystal that, divided by a suitable number of binary stages,

would give a 1-minute frequency, but this does not seem to have been done. We need a divide-by-sixty chain.

The 555 timer is an excellent and precise device with many applications. The difficulty with using it for long-period timing is that it depends on the precision of the capacitor, and large-value capacitors such as electrolytic and tantalum capacitors are not precise. They are also unstable. The best way to obtain long period timing is to build a short-period timer (such as the 1-Hz 555 timer) and feed its output to a divide-by-sixty chain.


Divide-by-sixty chain

Figure 1 shows a practical divide-by-sixty chain. Given a 1-Hz input from the crystal clock or 555 timer, as shown in the figure, the output has a frequency of 0.1667 Hz, or 1 cycle per minute. No single divide-by-60 ic is available, so we are tackling the division in two stages. First we use a 4018 to divide by 6, and then we take the output from this and feed it to a 4017 for division by 10. The two dividers (or we can also think of them as counters) are rather different in their action, so we shall look more closely at each one in turn.

The 4018 is usually known as a divide-by-n counter because it can be set to divide by any number from 2 to 10. This is a useful feature because we can use this ic to build

dividing chains for other values. To divide by 6 we take the 03-bar output from pin 6, and use this as the output of the ic but at the same time feed it back to the IN input at pin 1 (see table 1). There are also five inputs that allow the counter to be pre-loaded with a starting value. We do not use this facility here so these inputs (pins 2, 3, 7, 9 and 12) must be connected to the 0V rail, as must the LOAD input at pin 10. The RESET input at pin 15 is held low by a resistor R1. A push-button wired as in **figure 1** allows the counter to be reset. Instead, the reset input could be connected to a logical output to reset the counter digitally.

Figure 1: a divide-by-60 chain

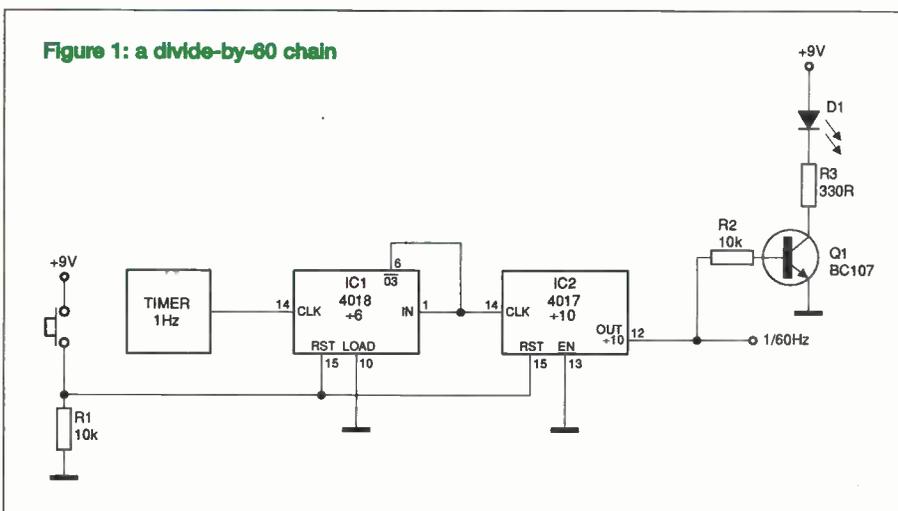

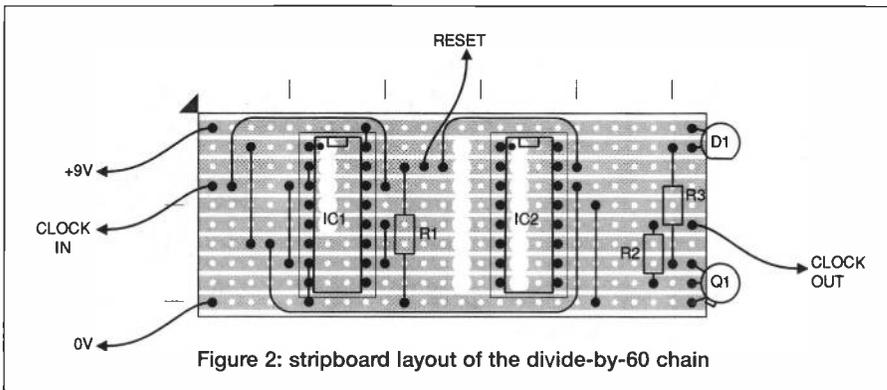


Figure 2: stripboard layout of the divide-by-60 chain

Table 1: Programming the 4018

Take the output listed, or AND the two listed outputs together, to obtain the division required, then feed back the output to IN (pin 1).

Divide by	Output from pin no.
2	5
3	4 AND 5
4	4
5	4 AND 6
6	6
7	6 AND 11
8	11
9	11 AND 13
10	13

The 4017 is unusual in that its 10 outputs are normally at logic low but on each count one of these goes high. This feature has some interesting applications but we use the special divide-by-10 output at pin 12, which goes high on counts 0 to 4 and low on counts 5 to 9. In other words, it has a frequency one-tenth that of the input.

This practical project (figure 2) includes a transistor-switched LED to indicate the state of the output. It is best to build and test the circuit in two stages. First assemble IC1, complete with the pull-down resistor R1. Note that a solder blob connects pins 2 and 3. Pins 7 and 8 are also connected in this way and to the 0V strip. Strips H and J are not cut beneath IC1. Connect either one of the 1Hz timers to pin 14 and use a testmeter to monitor the output of IC1 at pin 1. The output is low for three 1Hz flashes on the timer's LED, then high for three flashes, repeating. If this does not operate correctly, check that all the relevant pins are connected to 0V and that the reset pin (pin 15) is also at 0V.

Next assemble IC2 and the LED circuit (R2, R3, Q1 and D1). The only connections to 0V are the ENABLE (pin 13) and the 0V-supply terminal (pin 8). The RESET (pin 15) shares resistor R1 with IC1, so that both counters may be reset at the same instant. Switch on and count the flashes on the 1-Hz clock. The LED is on for counts 1 to 30 and off for counts 31 to 60, repeating. The circuit is a precise minute-timer.

Longer periods

The chain may be extended to increase the time period. Just adding another 4018 to the output of figure 1 allows you to increase the time to any whole number of minutes between 2 and 10 minutes (see table 1). It is possible to design a switching system so that the circuit can be switched to provide

several different output frequencies. However, if you want to divide by 10 only, use a 4017 instead of a 4018 as the wiring is easier. You could use other divide-by-ten (decade) dividers such as the 4029 (decade/binary, up/down), 4518 (dual decade, up/down) and the 74HC390. The latter contains two dividers, to divide by 2 and by 5, which can be used individually. If you need division by 10, divide by 5 first, and then divide by 2. If you connect the counters the other way round, you get an asymmetrical output.

Adding another complete divide-by-sixty chain to figure 1 increases the period to 1 hour. This can be increased to 2 to 10 hours by following with a 4018. A period of 24 hours could be obtained from 1 hour by using two 4018s to divide by 6 and then divide by 4. The use of dividing chains gives very precise periods, with the same precision as the initial timing circuit. A crystal clock with an inexpensive crystal has a precision of 15 ppm and a zero or very low tempco. This is equivalent to 1.3 seconds in 24 hours.

The circuits we have described so far are intended to provide a timed period, at the end of which something happens (or something stops happening). So far we have been content merely to switch an LED off at the end of the period. But we can design circuits to produce all kinds of actions and these will be the subjects of a future installment. Another way in which these circuits can be used is to measure the time elapsed since the circuit was set to run. This is another topic that will appear in future issues. For the moment we will look at a few more methods for generating the fundamental timed periods.

Ready-made chains

The technique of coupling a fast clock to a long dividing chain works so well that a number of integrated circuits are available which have the circuitry for the clock and the chain on a single chip. Of course, building up a chain to your own specification allows you to plan it to produce a number of different timing periods at various points along a single chain. But if you want a single long period with the minimum of wiring and using the minimum of board-space, then the dedicated timing ic is the answer.

One well-established example of this is the 4541 timer ic (figure 3) which, in spite of what we said just now about single long periods, does have the facility for producing four periods of different lengths. The clock is

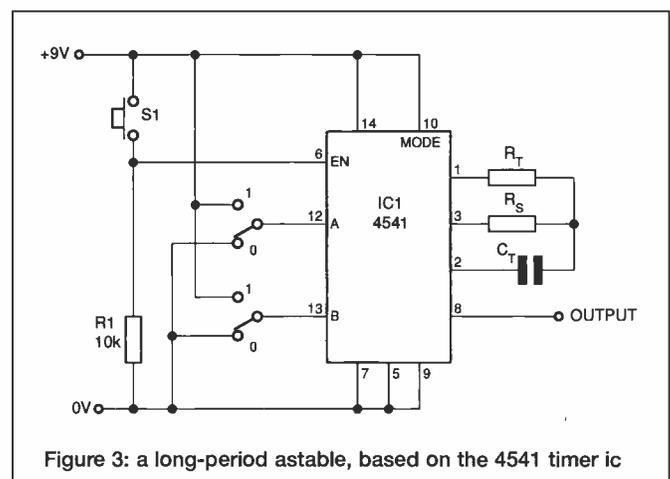


Figure 3: a long-period astable, based on the 4541 timer ic

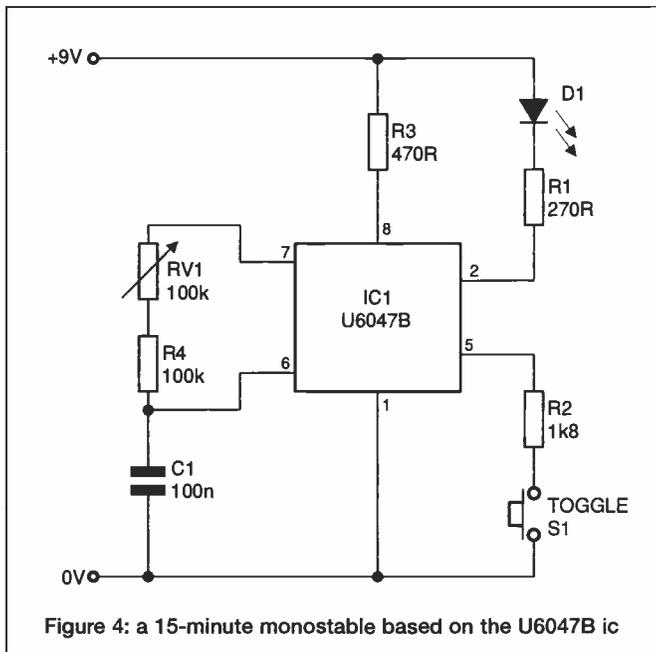


Figure 4: a 15-minute monostable based on the U6047B ic

based on charging a capacitor. The timing capacitor CT can have a value between 100pF and 100nF, so we can use polycarbonate or multilayer ceramic capacitors for maximum precision. The timing resistor RT can be between 5k and 1M. The basic frequency is $f = 1/(2.3RTCT)$. This gives a wide range of possible basic frequencies, from 4.35Hz to 870kHz. But the basic frequency is divided by one of four amounts, depending on the division control inputs, as in **table 2**.

Input A	Input B	Divides by
0	0	8192
0	1	1024
1	0	256
1	1	65536

This provides output ranging from 66.4uHz (period about 4.2 hours) to 3.4kHz (period 300 us). Division amounts can be switched by the use of two single-pole double-throw switches as shown in **figure 3** or under logical control. Pressing S1 resets the counter, after which the ic counts continuously as a low-frequency astable. If pin 10 (MODE) is wired to the 0V rail instead of to the positive rail, counting stops after 1 period.

A more recent ic operating on similar principles (though without the facility for switching ranges) is the U647B. This is intended for automotive use. With filtering on the power line provided by R1 and C1, it is relatively immune to the spikes and surges commonly encountered in car power supplies. The ic has many applications outside the automotive field as our second practical project for this month shows (**figure 4**). Basic timing is provided by RT and CT. RT may have any value between 59 k and 650 k, and CT may range from 1nF to 4.7uF. These values give a timing period from 3.7s to 1229 min (just over 20 hours).

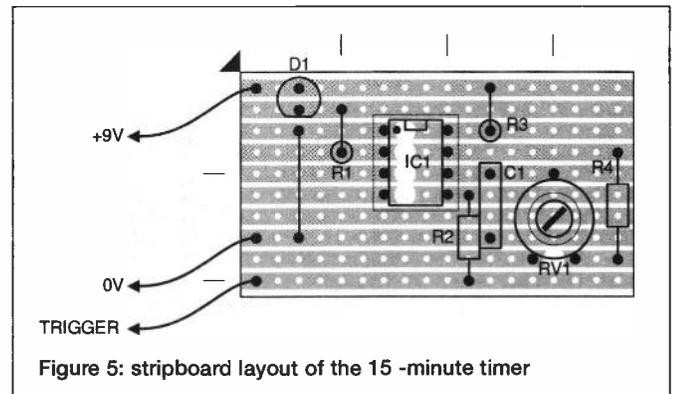


Figure 5: stripboard layout of the 15 -minute timer

One-hour timer

This design (**figure 5**) may be adapted for any period within the range of the U647B. It is just a matter of changing the values of RT and CT within the limits specified in the previous section. This design does not include the decoupling capacitor which is necessary to filter out spikes, but, if you are intending to use the device in a car or other 'noisy' environment, wire a 47 nF capacitor between the supply rails. Once again we are using only an LED to indicate the state of the timer, but it should be mentioned that the output of this ic is capable of driving much heavier loads. The output stage at pin 2 consists of an open-collector Darlington transistor able to switch up to 300 mA. So this ic can be used for switching on various devices for precisely timed periods. The output can switch a relay and is protected by a diode to prevent damage due to induction.

Starting and stopping errors

The usual way to use a counting chain is to have the clock running continuously and to reset the counter(s) when timing has to start. Counting starts on the next rising or falling edge of the clock's output. The 4060 used as the first counter in the crystal clock advances one count on the falling edge. The 4018 used in the divide-by-60 chain counts on the rising edge. Whichever kind of edge is used, there is an indeterminate delay of up to one clock cycle before the first active edge arrives and counting begins. Thus the timing period may be up to one clock period late in starting. In the case of the crystal clock, the period of oscillation of the 32.768 kHz crystal is about 30us, so the average delay is only 15us. This is insignificant when measuring periods of a second or more.

If we are using the output to indicate when the timing period ends, there is no further error. If we are using the clock to measure the time interval between, say, a 'start' pulse and a 'stop' pulse, we do this by counting the number of clock pulses between 'start' and 'stop'. There is a similar error at the end. Again, with high clock frequency and a relatively long

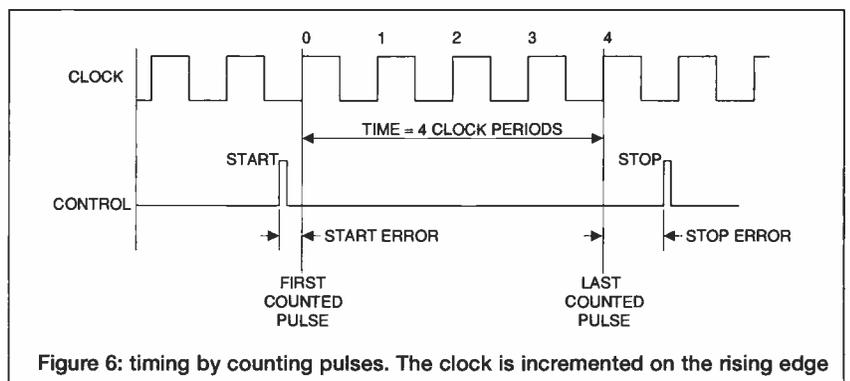


Figure 6: timing by counting pulses. The clock is incremented on the rising edge

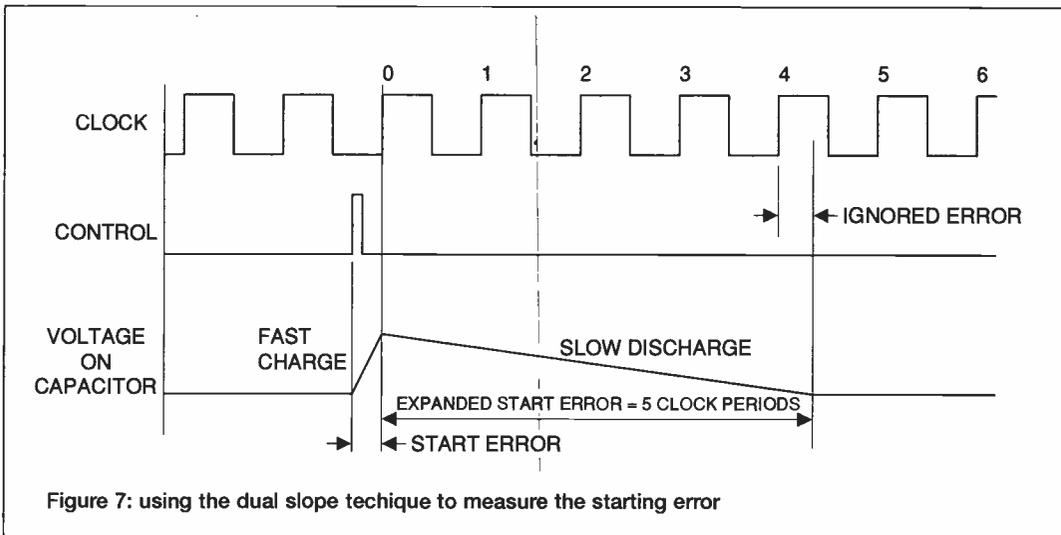


Figure 7: using the dual slope technique to measure the starting error

timing period the error can be ignored. The general aim for high precision timing is to make the clock period as short as possible and use a long counting chain.

A problem arises when we are timing periods that are only a few clock periods long. We might want to time the length of the flash of a camera flash-gun using a photo-sensor to detect the flash with logic to produce the 'stop' and 'start' pulses. There is a limit on how fast the clock can go. As well as a circuit to count the clock pulses we need to measure the time interval between the 'start' pulse and the first clock edge, and between the last clock edge and the 'stop' pulse (figure 5). The circuitry to do this is fairly complicated and we have to take into account the various delays inherent in the system, but the principle of one such technique is easily understood.

The idea of a dual slope integrator is known from its application in analogue-to-digital conversion. In measuring the short time interval between the 'start' pulse and the first clock pulse, we start charging the capacitor at the 'start' pulse and continue charging until the first clock edge occurs (figure 6). We charge it from a constant-current circuit, so that the voltage built up on the capacitor is proportional to the length of the start-up period. The capacitor is then discharged through another constant current circuit which restricts the current to, say, 1/1000 of the charging current. The capacitor takes 1000 times longer to discharge than it took to charge. We can not show this to scale in the figure. There the start error has been expanded by only about 25 times. The time taken to discharge the capacitor can be measured against the clock. In effect we have expanded this short period by 1000. There is still a 'stop' error in measuring the length of this period but this is on 1/1000 the scale and can be ignored. A similar charge-discharge technique is used to measure the period between the last clock edge and the 'stop' pulse.

Time stamp

In these days when we come across a microprocessor inside even a humdrum appliance such as a cheap fan heater, it is not surprising to find that it is simpler and less expensive to tackle complex measuring tasks by using software in place of hardware. The dual slope integration technique described above is certainly one in which

the pulse counting, and the calculation of errors and the final result is better done by a computer. This is not to say that we need a whole PC to perform the task. A humble micro-controller will do the job adequately.

One such device is the Basic Stamp, and we shall use this to illustrate how a microcontrollers can be used in time measurement or in the production of timed

output pulses. The Basic Stamp is so called because it can be programmed in its own version of Basic. This includes commands specially designed to make it easy to do things that the Stamp is likely to be used for. This includes timekeeping.

The command of special interest for time-keeping is PULSIN, which measures the length of an input pulse and returns the pulse length in units of 10us. The maximum length measurable is 65535 units of 10us. This comes to 0.65535 seconds, so the Stamp is obviously a candidate for measuring short time periods. The units are based on the period of the Stamp's clock, which is a ceramic resonator, accurate to +/-1 percent.

Figure 7 shows a circuit suitable for measuring the length of a photoflash, or some other short-lived phenomenon involving light. Photodiodes have a rapid response time, often only 250ns. Some have even shorter times, such as the BPX65 with a response time of 0.5ns. VR1 is set so that the voltage at the (0) terminal of IC1 is higher than that at the (+) terminal and the output of IC1 is 0V. IC1 is wired as a comparator. It has a reasonably high slew rate, which suits it for this application, and can operate on a supply of +/-2.5 V. During the flash there is an increase in the leakage current through the photodiode. This causes an increase in the voltage across R1. The voltage at the (+) terminal of IC1 rises above that at the (0) terminal. The output of the circuit rises close to 5 V, the equivalent of a logical high input. In summary, we get a positive pulse lasting as long as the flash.

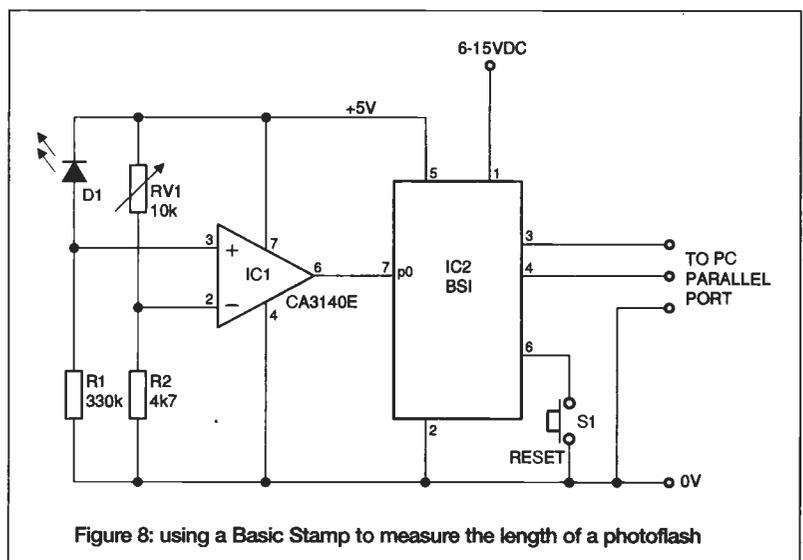


Figure 8: using a Basic Stamp to measure the length of a photoflash

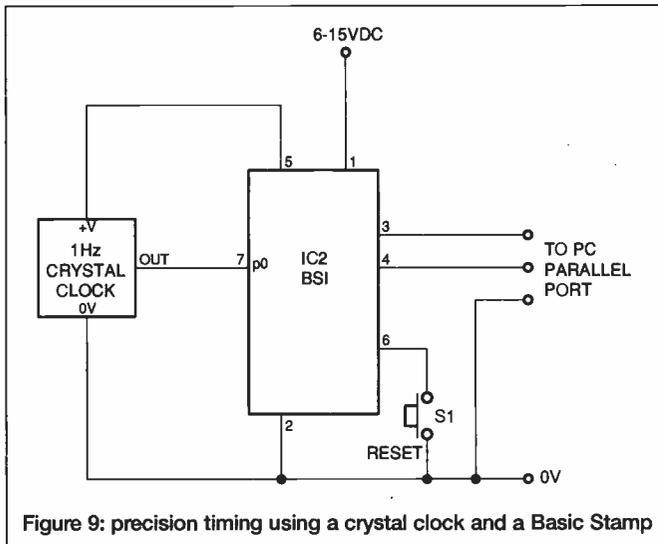


Figure 9: precision timing using a crystal clock and a Basic Stamp

We use PULSIN to measure the length of the flash by measuring the length of the pulse received at pin p0 (table 3). This is a very basic Basic program with plenty of scope for expansion. To use this program the Stamp must be connected to a PC, using the special lead provided in the Stamp kit. The syntax of PULSIN is:

pulsin pin, condition, byte or word

The condition is 0 for a low pulse, or 1 for a high pulse. In the program we are waiting for a high pulse at pin p0, and the time is to be stored in word 1. The easiest way to read the result is to use DEBUG to send the contents of w1 to the PC. Eventually the Stamp might be programmed to send the result to a LCD numeric display.

Table 3: Programming the STAMP

```
' Program to measure a flash
pulsin 0, 1, w1
debug w1
```

Run the program by pressing the reset button. Then operate the flash. If the flash is operated within 0.65 seconds, its duration in units of 10us then appears on the computer screen.

Another application of the circuit is to measure the length of time for which the photodiode detects a shadow. A light source and a photodiode are set up to that an object (for example, a model racing car) comes between them. There is a low output each time the car passes by. Knowing the length of the car, we could then calculate its velocity. The program has '0' as the second parameter of PULSIN. It could include a routine to calculate and display the velocity. There are numerous other ways in which physical events can be made to generate pulses and Stamp or similar microcontrollers (such as the PIC family) can be programmed to measure them.

Measuring long periods

The Stamp's built-in ceramic resonator is a convenient way of timing short periods but its precision is insufficient for timing long periods. For longer periods we employ a precise pulse-generator, such as the crystal clock unit, and use the Stamp to count the pulses and then flash an LED, sound an alarm, or take other appropriate action when a particular count is reached.

Figure 8 shows how the crystal clock is interfaced to a Stamp. The clock needs only 300 uA, plus about 15 mA for the LED. This can easily be powered from the Stamp's 5V regulated output. If you want to power other things from the same source, omit the transistor and LED from the clock. The figure shows the Stamp connected to the PC for programming and for reading results by using DEBUG during the development stages. Later it could be freestanding with outputs controlling LEDs, relays and anything else that needs time control. We plan to include a working project of this kind in a future part of this series.


A program for using the Stamp with an external clock appears in the Application Notes in the Programming Manual, so we shall not repeat it here. Our version is using a 1-Hz clock instead of their 2-Hz clock, so the second line of subroutine 'tick' must read:

```
if b0<2 then MAin
```


As it says in the Manual, this timer can measure periods up to 18 hours or, if modified to count minutes instead of seconds, up to 45 days. Quite a lot of counter ics would be needed to do the same thing in software.

Supplier

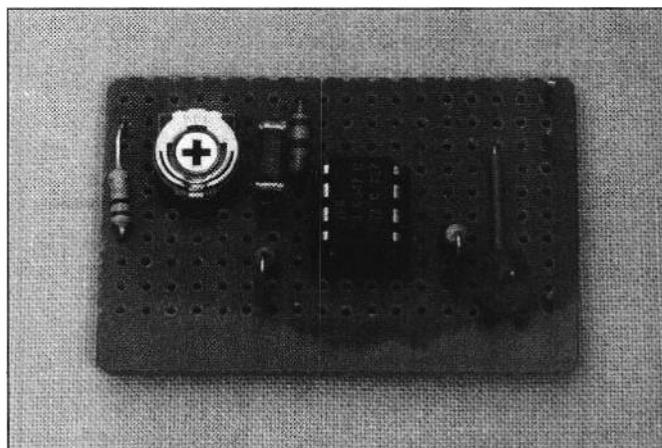The Basic Stamp is available from Milford Instruments, 120 High Street, South Milford, Leeds, LS25 5AQ, UK. Tel 01977 683 665 Fax 01977 681465.



The divide-by-60 chain board (see figure 2)

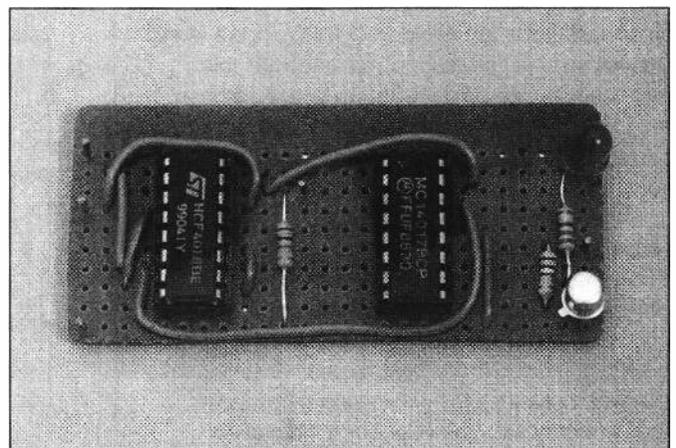

The 15-minute monostable board (see figure 4)

1



Technical productsyours for under £4

The Electromail CD-ROM Catalogue provides a virtual technical superstore, product encyclopaedia, and a help line with round-the-clock service - the moment you slip it into your computer!

It's quite amazing just how much you can get out of it. Products from batteries to bearings, fuses to fans, semi-conductors to computers, hand to power tools. On-line advice, and access to a full library of data sheets, providing detailed information on almost every product in our range.

But the best thing about Electromail, is that it's open just when you want to go shopping. 24 hours a day. 365 days a year.

And in most cases your order will be despatched on the very

ELECTROMAIL

a more professional choice

same day you order (failing that, the next working day).

The Electromail CD-ROM Catalogue offers you more products and services than any of the alternatives. Send for your copy and get a head

start in your business, your home or hobby ... and at just £3.99 with free delivery, it's not worth struggling on without it!

HOW TO ORDER



Tel 01536 204555 or Fax 01536 405555

When ordering by fax or phone quote stock no. 313-6988 and have your credit card details handy. Alternatively, you can open your own Electromail account - please ask for details.


Electromail, P.O. Box 33, Corby, Northants, NN17 9EL. Tel: 01536 204555 Fax: 01536 405555



CHELMER VALVE COMPANY

If you need Valves/Tubes or RF Power Transistors etc. ...then try us!

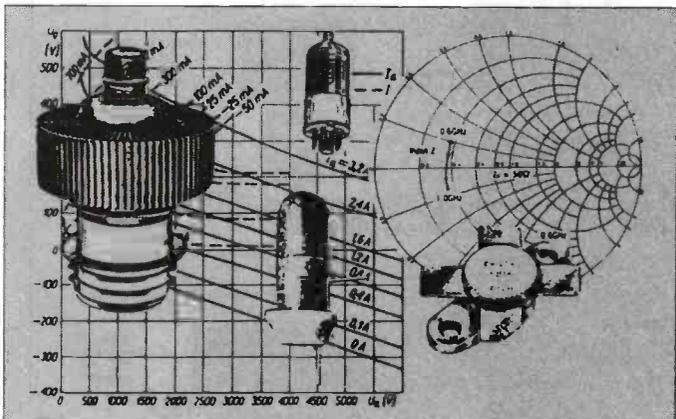We have vast stocks, widespread sources and 35 years specialist experience in meeting our customers requirements.



Tuned to the needs of the Radio Amateur

Chelmer Valve Company, 130 New London Road, Chelmsford, Essex CM2 0RG, England.

Tel: 44-01245-355296/265865

Fax: 44-01245-490064

Suppliers of Quality Electronic Things at Very Friendly Prices

Nuts Limited



Laser Pointers £15

- B/W Board Camera £40
- B/W Cased Camera £50
- Colour Board Camera £95
- Colour Cased Camera £125
- Date & Time Module £45
- 4 Channel Switcher £50

CCD Cameras From £40

Post & Packing £2.50

Nonuts Limited

2 Chase Cottages, New Road, Aldham, Essex CO6 3QT

Tel. 01206 213322 Fax 01376 561373

All Money, Cheques, Postal Orders, Visa & Access Accepted

Surplus Electronic Goodies Purchased

Microcontroller Development from Forest...

We've changed our ownership, and reduced our prices!

PIC & AVR Microcontroller Programmers

PIC Serial - Handles newer PIC devices in a 40 pin multi-width ZIF socket. 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, PIC 14000 etc. Also In-Circuit programming. Price: £40/kit, or £45 built & tested.

PIC Introductory - Programs 8 & 18 pin devices: 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508, and 12C509 etc. Price £20/kit.

AVR - Programs all current DIP devices in a 40 pin ZIF. Price: £35/kit £40 built & tested.

Note: All our programmers operate on a PC, using a standard RS232 serial interface (COM1, 2, 3, or 4). No hard to handle parallel cable swapping! All programmers are supplied with instructions, Windows 3.1/95/98/NT and programming software for the AVR or PIC.

AVR, PIC, & HC11 Windows Based Development:

Simulator allows assembly and simulation of your AVR, PIC or HC11 projects in **one Windows program**. Incorporate multiple files, view help file information directly from the code, edit within project, build and track errors directly in the source, then simulate. Simulator allows 3 breakpoint types, follow code in the source window, set breakpoints directly in code. Run programs, or single step, or step over subroutines. **Logic Analyser Display!** Track variable values and trace for display on the Trace Analyser. Input stimuli include clocks, direct values and asynchronous serial data. Profile your program - examine frequently called routines which are timed and use the information to optimise out bottle necks. PIC Version Simulates up to 50 times faster than MPSIM!

Cost £20.00. Please specify Windows 3.1, or Windows '95 (32 bit) and either AVR, PIC, or HC11 version



Forest Electronic Developments

60 Walkford Road, Christchurch, Dorset, BH23 5QG.
http://dSPACE.dial.pipex.com/robin.abbott/FED
01425-274068 (Voice/Fax)

PIC BASIC

FED's PIC BASIC products - straightforward, capable, powerful, rapid development. Operating in a Windows Development Environment our modules need no assembler or UV eraser to program your PIC's, and operate from a serial link to your PC. The 16C74 module features - 8k EEPROM, up to 2000 lines of BASIC, 27 lines of programmable I/O, 8 A/D inputs, Interrupt driven serial RS232 interface, Peripheral I²C bus interface, LCD display driver routines, up to 178 bytes for variables and stack, extendible with optional external RAM and all the standard 16C74 features. 16C57 version still available - ask for details.

COMPILER HALF PREVIOUS PRICE! - The FED PIC BASIC compiler for the 16C74. It produces hex code to program your 16C74 directly with no need for external EEPROM. Compatible with the EEPROM versions of PIC 16C74 BASIC modules - develop on an EEPROM based module then compile and program your PIC chips directly.

16C74 Module Kit (8k EEPROM, 4MHz) £35.00, Pre-built £42.00
16C74 Module Kit (8k EEPROM, 20MHz) £40.00, Pre-built £46.00
Compiler - £30.00

Coming Soon....

PIC BASIC - surface mount modules and updated development system, watch for details!

AVR & PIC devices

PIC16C74/JW Erasable 20MHz	£18.00	PIC16C558	£5.00
PIC16C74A-04P	4MHz £8.00	PIC16C74A-20P 20MHz	£10.00
PIC16F84-04P	4MHz £6.00	PIC12C508-04P 4MHz	£1.80
AVR	Ring for details		

Prices are inclusive, Add £3.00 for P&P and handling to each order. Cheques/POs payable to Forest Electronic Developments, or phone with credit card details.



HOW DOES YOUR EQUIPMENT MEASURE UP? AT STEWART OF READING THERE'S ALWAYS 'SCOPE' FOR IMPROVEMENT!

CAN YOU BELIEVE IT 4 TRACE TEXTRONIX 7704A FOR ONLY £350



2x200MHz, 2x75MHz Sweep Delay Graphics etc. OTHER COMBINATIONS AVAILABLE

TEKTRONIX 2215 - DUAL TRACE 60MHZ



Sweep Delay, includes 2 probes ONLY £400



PHILIPS PM3217 - Dual Trace 80MHz Delay
This really is a very good oscilloscope including 2 Probes, Pouch & Front Cover ONLY £400

TEKTRONIX 400 SERIES



468 Digital Storage Dual Trace 100MHz Delay £650
465 Analogue Storage Dual Trace 100MHz Delay £395
465 Dual Trace 350MHz Delay Sweep £750
475 Dual Trace 200MHz Delay Sweep £500
465 Dual Trace 100MHz Delay Sweep £400



HC 3502
Dual Trace 20MHz, 5mV/20V/div, 0.2u secs-0.5 Sec/div, X-Y: X5 Magnifier, TV Sync etc
Hardly Used £150 Un-Used £200

PHILIPS PM3296A Dual Trace 400MHz Dual TB Delay Cursors IEEE £2250
FLUKE PM3022 2x2Ch 100MHz Delay TB Cursors £999
TEKTRONIX 2465 4 Ch 300MHz Delay Sweep Cursors etc £2000
TEKTRONIX 2445/2445A 4 Ch 150MHz Delay Sweep from Cursors etc £1000
TEKTRONIX TAS465 Dual Trace 100MHz Delay Cursors £900
TEKTRONIX 2235 Dual Trace 100MHz Delay Sweep £750
WATSU SS5711 4 Ch 100MHz Delay Sweep £350
PHILIPS 3055 2+1 Ch 50MHz Delay Dual TB £475
GOULD OS100 Dual Trace 30MHz £200
GOULD OS300 Dual Trace 20MHz £200

MARCONI 2019 Syn AM/FM Signal Gen 60KHz-100MHz £1400
MARCONI 2017 Phased Lock AM/FM Signal Gen 10KHz-1024MHz £1750

CAN YOU BELIEVE IT - A 1GHZ GENERATOR FOR ONLY £450

H.P. 8640A AM/FM Signal Gen 500KHz-1024MHz - Audio Option £225
FARNELL SS6520 Syn AM/FM Signal Gen 10-520MHz £450
FARNELL PS6520 Syn AM/FM Sig Gen 10-520MHz Portable £4500
MARCONI 6311 Programmable Sweep Gen 10MHz-200GHz £1500
H.P. 8656A Syn Signal Gen 0.1 - 990MHz £1500
PHILIPS PM5189 Programmable Syn Func Gen 0.1MHz-500MHz £1500
PHILIPS PM5192 Programmable Syn Func Gen 0.1MHz-20MHz £1000
H.P. 3325A Syn Function Gen 21MHz £1250
PHILIPS PM5134 Sweep Func Gen 0.001Hz-20MHz £400
PHILIPS PM5132 Sweep Func Gen 0.1Hz-2MHz £250

CLASSIC AVO METER
A Digital AVO DAI16 3 1/2 digit Complete with Batteries and Leads Only £30

METROHM
9A - 500V Battery Megger (a useful back-up for a 2 lead Megger)
Complete with Batteries and Leads £33

SOLARTRON 7045
4 1/2 digit Bench Multimeter with leads £80

SOLARTRON 7151 DMM 6 1/2 digit IEEE £450
SOLARTRON 7150 DMM 6 1/2 digit IEEE £300
True RMS

LOOK!! BRAND NEW OSCILLOSCOPES - NEVER USED LIMITED STOCK



DMS 3850A DIGITAL STORAGE/DMM
Handheld LCD Display 2 Channel 50MS/S. Auto range. 4 digit DMM/Capacitance/Frequency Counter. Battery Operation or external 7.5-9VDC i.e. AC Adaptor (Not supplied). RS232 Comes in Black Carrying Pouch complete with 2 scope probes, DMM leads. Manual FOR ONLY £400




OTS 40 DIGITAL STORAGE
Dual Trace 40MHz 20MS/S Storage. Cursors + On Screen Readout. Sweep Delay. Interface etc. etc. Supplied Un-used in original box complete with 2 Probes & Manual




DTA 20 Dual Trace 20MHz AH Mag. TV Trng. etc.
Used & boxed supplied with 2 probes & Manual £225



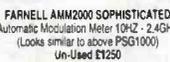FARNELL PS61000 10KHz - 1GHz
Am/Fm Synthesised Signal Generator Portable Un-Used £1500 Used £995



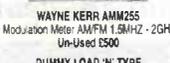FARNELL AMM2000 SOPHISTICATED
Automatic Modulation Meter 10Hz - 2.4GHz (Looks similar to above PS61000) Un-Used £1250



WAYNE KERR AMM255
Automatic Modulation Meter AM/FM 1.5MHz - 2GHz 3 1/2 Digit Un-Used £500



DUMMY LOAD IN TYPE
50ohm 75 Watts Un-Used £30

NEW & HARDLY USED

PANASONIC VP8177A FM/AM SIGNAL GENERATOR
100KHz-100MHz, FM 0-100KHz, Output -10dB-96dB AM 0-60%; 32 Preset Memory, Digital Display Frequency & Output. Un-Used £750 Used £450

KENWOOD FL180A WOV/FLUTTER METER
0.003% - 16%; Freq. 30KHz/0.15KHz RMS/AVERAGE/PEAK. Weighted Filters; Digital Display or rpm. 4 digit Freq Counter (0.01KHz-9.999KHz/0.01KHz-55KHz) Used £400 Un-Used £500

POWER SUPPLY MOEEL HSP9010
0-30 Volts, 0-10 Amps Current Limiting, 2 Meters Used £160 Un-Used £200

GOODWILL GVT427 DUAL CHANNEL AC MILLIVOLT METER
10uV 300V in 12 Ranges Frequency 10Hz - 1MHz Used £100 Un-Used £125

GOODWILL GFC 80100 FREQUENCY COUNTER
Range 1Hz - 120MHz 8 Digit Display 15mV RMS Sensitivity Un-Used £75

ANALOGUE MULTIMETER Model HC260TR AC/DC Volts;
DC Current 10Amps; 17 Ranges; Continuity Buzzer; Transistor Tester Un-Used £15

STEREO AUDIO BALANCE to UNBALANCED CONVERTOR
for Car Radio Servicing Un-Used £10

FARNELL LFI
Sine / Sq Oscillator 10Hz - 1MHz Un-Used £75

POWER SUPPLIES
FARNELL AP100/30 0-100Volts, 0-30Amps Auto Ranging £1000
FARNELL H6025 0-80Volts, 0-25Amps £400
FARNELL TS770MHz 70Volts, 5Amps/35Volts 10Amps £200
FARNELL L12-10C 0-12Volts, 0-10Amps £175
FARNELL L130-2 0-30Volts, 0-2Amps Twice £130
FARNELL L130-1 0-30Volts, 0-2Amps Twice £130
THURLEY/HANDAR TSX1420 Precision PSU 18Volts, 20Amps £275
THURLEY/HANDAR TSX2222 Programmable Source, 2Amps Twice GPB Digital £450
THURLEY PL320 0-30Volts, 0-2Amps GPB Digital £150
THURLEY PL310 0-30Volts, 0-1Amps Digital £110

MANY MORE POWER SUPPLIES AVAILABLE



STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL
Telephone: (0118) 9268041. Fax: (0118) 9351696
Callers Welcome 9 am - 5.30 pm Monday to Friday (other times by arrangement)



Used Equipment - GUARANTEED. Manuals supplied

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

REVIEW

osziFOX universal storage oscilloscope

A handheld 'scope with promise in the field

NoNuts Ltd.
2 Chase Cottages
New Road
Aldham
Essex CO6 3QT
Tel/fax 01206 213322

When I first saw this I didn't believe it. It's about the same size as any normal self contained pen-type digital multimeter, but it is a 20-MHz oscilloscope as well as a meter. It does need an external power source, which is hardly surprising. It is still impressive to fit all so much functionality into so small a package.

With this pocket scope, a gas-powered soldering iron, and perhaps half a dozen small hand tools, you have the basic equipment to fault find and repair a wide range of equipment. You can also use it with a PC to capture waveforms via the serial port.

Essential



EQT LTD STEVENAGE
Professional Sub-Contract Manufacturing & Suppliers to the Electronics Industry

Do you have a requirement for any of the following services:


PCB Assembly (Conventional and Surface Mount)	Product Design/Consultation
Wave & Hand Soldering	Full Procurement Service
Complete Equipment Manufacture	PCB Test & "Burn in" Facilities
Device Programming from hand written sheets or PC 3 1/2" disc	Enclosure Design & Manufacture
Cable Harness Assembly/loom Manufacture	PCB Artwork Manufacture
Card Cage and Module Wiring	Circuits Drawn Professionally
Full Inspection	Kit Procurement & Supply
	Component Sales
	Refurbishment a speciality
	Top Quality Work at Reasonable Rates

Phone Steve on (01438) 360406 or fax details of your requirements to us on (01438) 352742
EQT LTD, UNIT 5, First Floor, Caxton Point, Bessemer Drive, Stevenage HERTS SG1 2XT

information

As a standalone instrument it is minimalist in operation. Menu and select buttons are used to select the different functions, while input range selection (1V, 10V, 100V and AC, DC, GND input coupling) is carried out by two three-way slide switches. Compared with a desktop instrument, the setting of timebase and trigger levels is fiddly, but if you are debugging audio or logic it is likely that one setting will do for most measurements, while the instrument is not suitable for use in the kind of development laboratory environment where very accurate waveform measurements are needed.

The printout of the hardware Help (figure 1) gives a fair view of the controls and their functions. The scope comes into its own in situations where you would not otherwise have an oscilloscope available, and it can help you to trace at which stage in an amplifier distortion is introduced, or which half of a waveform is being clipped. This sort of information is usually all you need to identify the necessary repair.

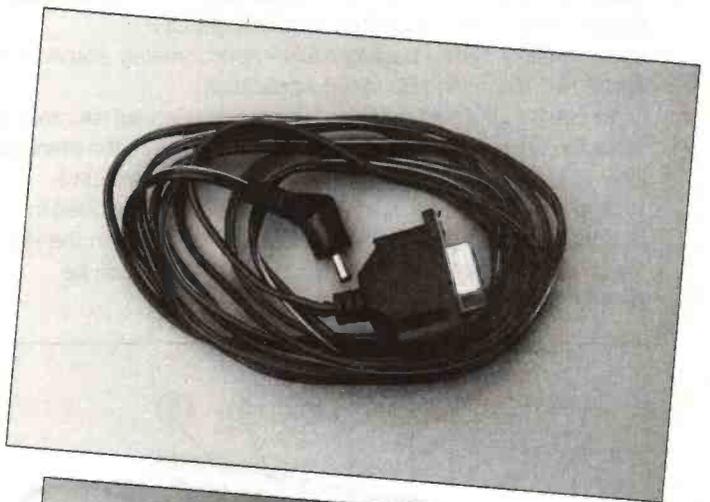

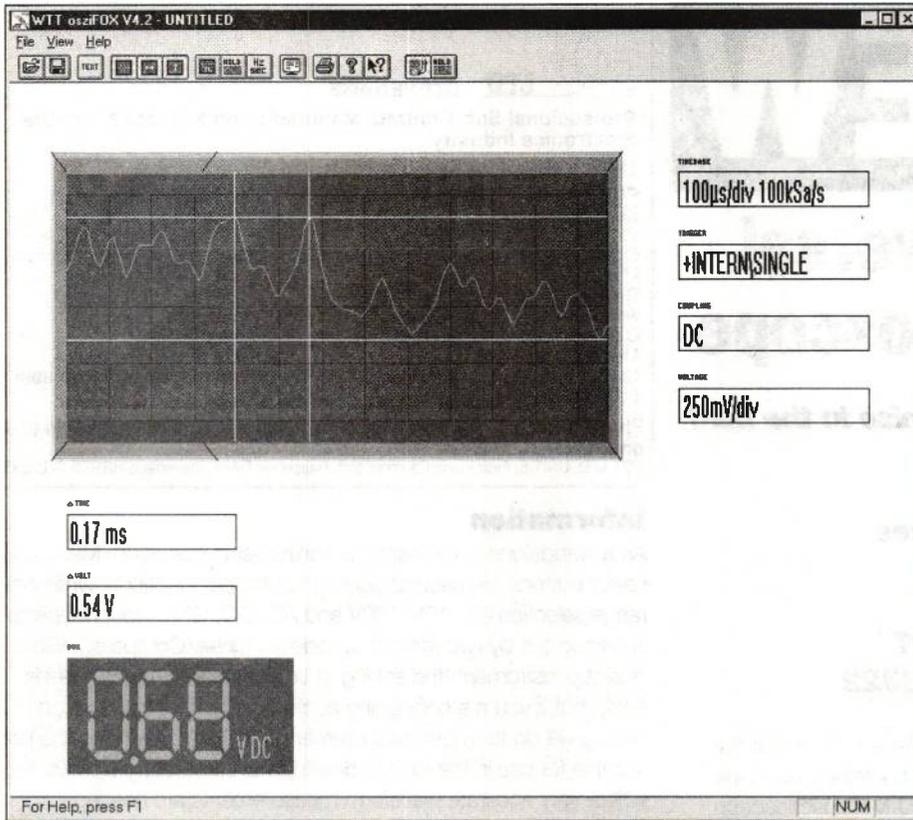


Figure 1: the hardware Help screen

The bandwidth is specified as 5MHz, with sample periods of 50ns, 100ns, 0.5µs, 1µs, 5µs, 10µs, 50µs, 0.1ms, 0.5ms, and 1ms. The resolution is 6 bits, and there is 128 bytes of ram. The display on the side of the instrument is a 16 x 32-dot liquid crystal, green-backlit.

Power is from a 9V to 13V source. In practice I found a small 12V sealed lead acid battery convenient for the function. Power consumption is quoted as: backlight OFF - approximately 12mA; backlight ON - approximately 85mA. A 1-Ah battery has a long life in this application.

In use, I found that the auto trigger function was reluctant to allow the applied signal to trigger the scope, while the standard internal trigger and single shot modes were very effective.

The croc-clip power lead and a data lead are included in the pack. Instructions and other documentation are in the Help file on the software disk that is included, and this can be printed out or read on-screen.

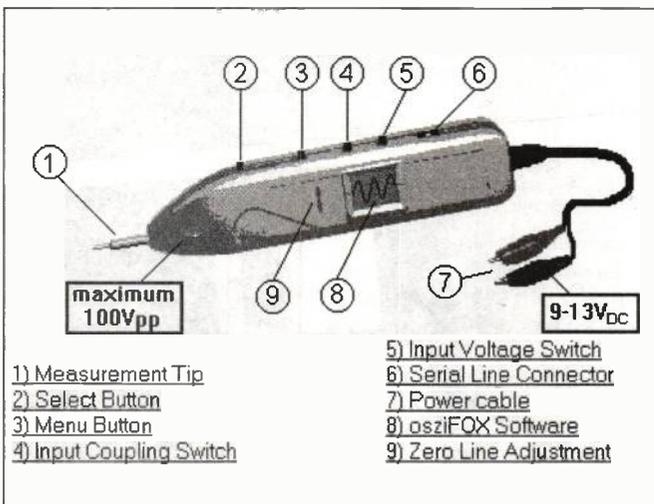


Figure 2: a PC screen showing waveform and DVM readings

Software

You may be wondering why the oscilloscope has more memory than is reflected by the LCD screen fitted. This is to provide for its other function, which is to display captured waveforms on the screen of a PC. Interface software to run under Windows is provided, and this captures waveforms and DVM readings as shown on the screen printout (figure 2). The resolution and length of trace on the PC screen is much better than that on the LCD screen, so the usefulness of the instrument for more complex measurements is enhanced.

The screen captured also shows the use of cursors to measure voltage and time. On the toolbar is a button to switch from time display to frequency, and it is possible to hold one waveform to compare with a current one.

The PC is not used to control the oscilloscope, but functions merely to indicate the current settings. The timebase, trigger level and so on

must be set using the menu and select buttons.

Software to run under DOS is also provided, but it did not prove possible to verify the complete operation of this. It would load, and it displayed the last waveform which had been shown when the Windows software was running. However, it claimed that the oscilloscope was connected to Com 1, to which in my case the modem is actually connected. When I manually configured it to Com 3 it would still not display current waveforms under DOS.

No doubt this is due to some sort of clash with the Win95 drivers, and it may reasonably be expected to work correctly on a basic DOS machine which does not have Windows installed. This does raise the possibility of using an otherwise obsolete PC with the osziFOX 'scope. Still, if you have Windows installed, the Windows interface is more convenient for the purpose, and works well.

On the other hand, if you have a laptop PC for other reasons, this can form a useful adjunct to the portable oscilloscope. We could be seeing this kind of thing in the armoury of PC or network support staff in some contexts.

In conclusion

At a price of around £75 this handheld oscilloscope is remarkably good value for anyone who can make good use of its functionality, and a nice present for anyone who likes to keep their pocket-collection up to date.

For more information contact NoNuts Ltd. (see head of this article).

All the documentation is in a Help file on the software disk

ETI can supply printed circuit boards for most of our current projects - see the list below for boards available. For recent boards not listed, check the constructional article for an alternative supplier.

Please use this order form or a copy of it. Check that all relevant information is filled in, including the Unit Order Code, and that you have signed the form if sending a credit card number. Overseas customers please add postage appropriate to the

number of units you are ordering. Make cheques/POs/money orders, in £ sterling only, payable to Nexus Special Interest Limited. Please allow 28 days for delivery. Access/Visa orders may be made on 01442 266551 (ask for Readers Services).

Only boards listed here are available from our PCB Service. For past issues of magazines, or binders, please see page 74 or contact Readers Services for information.

Name and issue of project Unit code Price

ETI PCB Service Issue 9 1998

Ricky Sound (Music Lovers)	E/998/1	£5.09
Q Meter	E/998/2	£5.09
Bath Duck	E/998/3	£5.09

ETI PCB Service Issue 8 1998

PIC Electronics Security Switch	E/898/1	£5.09
PIC Multiplexed LED Display	E/898/2	£5.09
PIC Non-multiplexed LED Display	E/898/3	£5.09
Easy Parker	E/898/4	£6.77
Tiny Traffic Lights	E/898/5	£5.09
Q Meter	E/898/6	£5.09
Bath Duck	E/898/7	£5.50

ETI Issue 7 1998

PIC 16C74 Development Board	E/798/1	£5.09
Surface Mount Diagnostic Interface	E/798/2	£5.09
Surface Mount Logic Probe	E/798/3	£5.09
Mains Monitor	E/798/4	£12.33
Aquaprobe	E/798/5	£5.50

ETI Issue 6 1998

PIC Development Board	E/698/1	£5.50
Signal Generator	E/698/2	£8.99
Headlight Delay Unit	E/698/3	£5.50
6-Interval Games Timer	E/698/4	£5.09

ETI Issue 5 1998

UHF Transmitter (DS)	E/598/1	£5.07
UHF Transmitter Encoder	E/598/2	£5.09
UHF Receiver Front End (DS)	E/598/3	£5.07
UHF Receiver IF stage (DS)	E/598/4	£5.07
Fridge Thermometer	E/598/5	£5.50
AVR Controller	E/598/6	£5.50
27C16 Eprom Programmer	E/598/7	£7.87
Guardian Light	E/598/9	£6.22

ETI Issue 4 1998

LED Voltmeter	E/498/1	£5.64
BB Ranger Control Board	E/498/2	£6.22
BB Ranger Score Board	E/498/3	£22.89
Line-Up Oscillator with Glitch	E/498/4	£8.99
Tic Tac Toe	E/498/5	£8.44

ETI Issue 3 1998

Medium Wave Loop	E/398/1	£5.64
AA Cell Eliminator	E/398/2	£7.32
PIC Based Double Bass Tuner	E/398/3	£5.64
5 Range Capacitor Meter	E/398/4	£6.77
MIDI Drum Pads	E/398/5	£5.64

ETI Issue 2 1998

Smartcam main board	E/298/1	£5.09
Smartcam opto-sensor board	E/298/2	£5.09
Both smartcam boards	E/298/1&2	£7.00
Switched Mode Internal Power Supply	E/298/5	£7.87
Auto Cupboard Light	E/298/3	£5.64

ETI Issue 1 1998

Control Centre Desk-Top Unit	E/0198/1	£8.99
Control Centre Main Section	E/0198/2	£7.87

ETI Issue 13 1987

4-Go Rocket Launcher - main board	E/1397/1	£5.64
4-Go Rocket Launcher - relay board	E/1397/2	£6.22
Mighty Midget	E/1397/3	£9.54

Please supply:

Quantity Project Unit Order Code Price Total price

.....
-------	-------	-------	-------	-------	-------

Prices are inclusive of post and packing in the UK. Overseas Post and Packing (if applicable): Add £1 per unit

Name

.....

Address

.....
.....

I enclose payment of £ (cheque/PO/money order in £ Sterling only) to:

PCB Service, READERS SERVICES DEPARTMENT, Nexus Special Interests Ltd., Nexus House, Azalea Drive, Swanley, Kent BR8 8HU

□ □ □ □ □ □ □ □ □ □ □ □ □ □ □ □

Signature:

Card expiry date:

ETI Issue 12 1997

PC Phonecard Reader: ITT Cannon only	E/1297/1	£6.22
Minute Minder	E/1297/2	£13.98
Medium Wave Receiver - RF board	E/1297/3	£11.76
Medium Wave Receiver - Tuning board	E/1297/4	£5.09
Medium Wave Receiver - Audio board	E/1297/5	£5.09
Medium Wave Receiver - PSU board	E/1297/6	£6.77

ETI Issue 11 1997

Total Harmonic Distortion Meter	E/1197/1	£13.43
Alphanumeric Morse Touchkey	E/1197/2	£5.09

ETI Issue 10 1997

The IQ Tester	E/1097/1	£5.64
Fake Flasher	E/1097/2	£5.09
DC Motors (Part 2)	E/1097/3	£6.77
Valve Tester - Main Board	E/1097/4	£21.22
Valve Tester - Socket Board	E/1097/5	£5.09
Valve Tester - Heater Regulator	E/1097/6	£5.09
All three Valve Tester boards	E/1097/4/5/6	£30.30
The IQ Tester (previously E/897/2)	E/1097/7	£5.64

ETI Issue 9 1997

Eprom Emulator	E/997/1	£16.49
The Power Supply	E/997/2	£5.09
Electronic Door Chimes	E/997/3	£5.09
Digital Power Supply	E/997/4	£10.11

ETI Issue 8 1997

The Brake Light Tester	E/897/1	£5.09
DC Motors (3 experimental boards)		
DC Motors: The first Control Unit	E/897/3	£5.09
DC Motors: The 4046 Circuit	E/897/4	£5.09
DC Motors: The Crystal Drive Circuit	E/897/5	£5.09
All three DC Motors boards	E/897/3/4/5	£11.50

ETI Issue 7 1997

Eprommer: main board (double sided)	E797/1	£13.32
Eprommer: PSU board	E797/2	£5.64
Eprommer: personality modules (double sided):	E797/3	
Any ONE module board: £5.09; two modules: £7.90; three modules: £11.85; four modules: £15.80; five modules: £19.75; All six modules: £23.70		

Please specify which Eprom modules you require. Modules are for 2716, 2732, 2764, 27128, 27256 or 27512. One order code/overseas postal charge applies whether a selection or all six personality module boards are ordered.

Are Your Lights On?	E/797/4	£5.09
Peak Reading VU Meter	E/797/5	£5.09

Terms of trade

Terms strictly payment with order. We cannot supply credit orders, but will supply a proforma invoice if requested. Proforma orders will not be processed until payment is received. All boards are manufactured from the foils that appear in the ETI Foils Pages for the appropriate issue. Please check that our foils are suitable for the component packages you intend to use before ordering as we cannot supply modified boards or replace boards that have been modified or soldered. Boards are only supplied in the listed units. Sorry, we cannot break units. Prices and stock may be altered without prior notice. Prices and stock listed in this issue supersede prices and stock appearing in any previous issue. ETI, Nexus Special Interests and their representatives shall not be liable for any loss or damage suffered howsoever arising out of or in connection with the supply of printed circuit boards or other goods or services by ETI, Nexus Special Interests or their representatives other than to supply goods or services offered or refund the purchaser any money paid in respect of goods not supplied.

ADVERTISERS INDEX

Agar.....72	NCT.....19
Ambyr Ltd.....72	No. One Systems.....19
Broadcast Warehouse.....72	No Nuts.....73
Chelmer Valves.....65	Plancentre Publications.....72
Crown Hill Associates.....32	Proaction.....46
Display Electronics.....9	Quick Route Systems.....25
EPT Educational Software.....IFC	Scientific Wire Co.....72
EQT.....67	Stewarts of Reading.....66
Equinox.....IBC	Swift Eurotech.....46
ESR Electronic Components.....17	Telnet.....43
Forest Electronics.....66	Variable Voltage Technology Ltd.....72
JPG.....19	
Labcenter Electronics.....OBC	Van Draper.....37
Milford Instruments.....70	

CONTROL & ROBOTICS from Milford Instruments


BASIC Stamps-

- Re-Programmable
- BASIC language
- RS232 Serial ports
- 8 or 16 I/O lines
- SPI/DTMF
- Fast development



Scenix

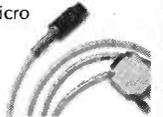- Fastest 8-bit micro
- 50MIPS
- Flash Eprom
- 18/28 pins
- PIC16C5x pin replacement




Serial LCDs

- RS232 Serial interface
- 2x16 to 4x40
- Simple 3-pin connection
- Integral Keypad option
- Large Numerics option
- Driver chips available for OEM use



Robotics

- Humanoid
- 5-Axis Arm
- Walking Insect

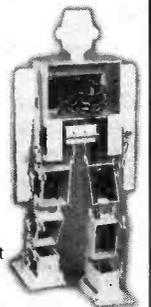

3-Axis Machine

- Stamp 2 based
- Drills PCBs
- 3-Axis movement
- Stepper drive
- 4 thou resolution
- Win 3.1 software



Servo Controller

- Control up to 8 servos
- RS232 Commands




IR Decoder


- Uses any remote
- 7 digital outputs
- Toggle/momentary
- Re-Programmable

Milford Instruments 01977 683665 www.milinst.demon.co.uk


FOILS FOR THIS ISSUE

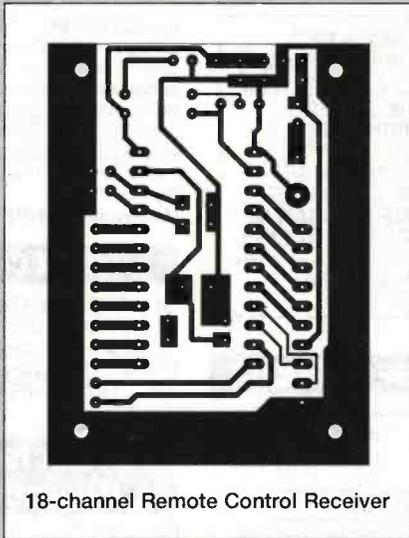


18-channel Remote Control Receiver

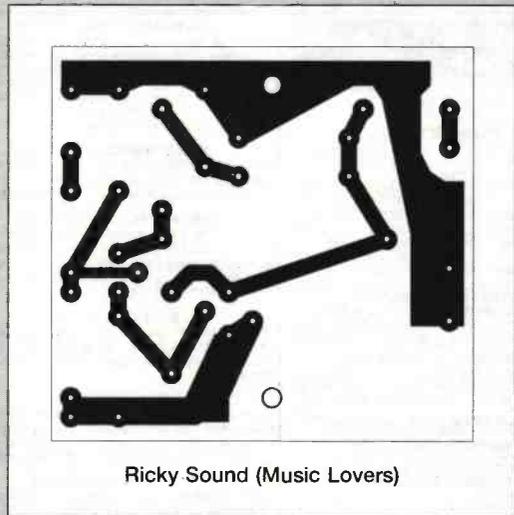

Ricky Sound (Music Lovers)

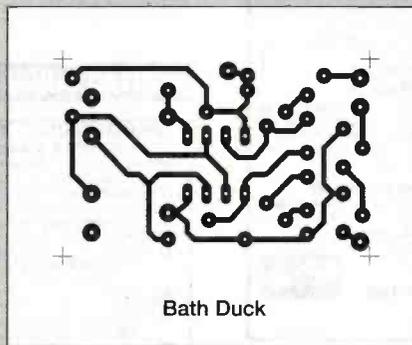

Bath Duck

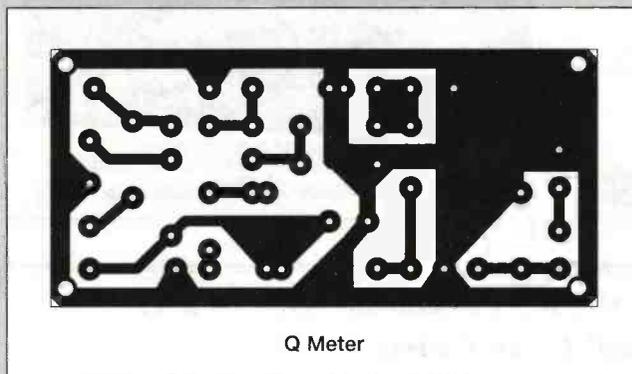

Q Meter



Classified



Mark Colyer 01322 660070

Send your requirements to:
ETI Classified Department, Nexus, Nexus House,
Azalea Drive, Swanley, Kent BR8 8HY
Lineage: 85p per word (+VAT) (minimum 20 words)
Semi display: (minimum 3cms)
£12.50 + VAT per single column centimetre



Ring for information on series bookings/discounts.
All advertisements in this section must be pre-paid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60

OUTPUT 0-260V

Price P&P

0.5KVA 2.5 amp max £33.00 ~~£5.00~~ (£45.83 inc VAT)

1KVA 5 amp max £45.25 ~~£7.00~~ (£61.39 inc VAT)

PANEL MOUNTING

0.5KVA 2.5 amp max £34.00 ~~£5.00~~ (£47.00 inc VAT)

1KVA 5 amp max £46.25 ~~£7.00~~ (£62.57 inc VAT)

2KVA 10 amp max £65.00 ~~£8.50~~ (£96.36 inc VAT)

3KVA 15 amp max £86.50 ~~£11.50~~ (£111.83 inc VAT)

5KVA 25 amp max £150.00 Plus Carriage & VAT

10KVA 45 amp max £300.00 Plus Carriage & VAT

6KVA 3 PHASE Star £205.00 Plus Carriage & VAT

Buy direct from the Importers. Keenest prices in the country

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO

(110-240V Auto transfer either cased with American socket and mains lead of open frame type. Available for immediate delivery

500VA ISOLATION TRANSFORMER

New manuf. surplus C Over insulates with top plate and solder connections. 0.240V AC Prim. 5-0-100-110-120V & Screen Sec. Wt 10.5K

Size: H195 x W155 x D135mm. Price £25.00. Carr. £7.00 (£49.94 ind.)

RANGE OF XENON FLASHTUBES

Write/Phone your enquiries

ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft 40 watt £14.00 (callers only) (£16.45 inc VAT)

2ft 20 watt £9.00 (callers only) (£10.58 inc VAT)

12in 8 watt £4.80 + 75p p&p (£5.52 inc VAT)

9in 5 watt £3.96 + 50p p&p (£4.46 inc VAT)

6in 4 watt £3.96 + 50p p&p (£4.46 inc VAT)

230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £6.05 + £1.40 p&p (£8.75 inc VAT)

The above Tubes are 3500/4000 angst. (350-400nm) ideal for detecting security markings, effects lighting & Chemical applications.

Other Wave Lengths of U.V. TUBE available for Germicidal & Photo. Sensitive applications.

Please telephone your enquiries.

400 WATT BLACK LIGHT BLUE UV LAMP

GES Mercury Vapour lamp suitable for use with a 400W P.F. Ballast

£39.95 INCL. P&P & VAT

12V D.C. BILGE PUMPS

500 GPH 15ft head 3 amp £19.98

1750 GPH 15ft head 8 amp £34.55

Also now available 24V D.C. 1750 GPH 15ft head 5 amp £35.55.

All designed to be used submerged. PRICES INCLUDE P&P & VAT

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical uses etc. Approx 16 joules. Adjustable speed £50.00 + £3.00 p&p (£52.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)

SAE for further details including Hy-Light and industrial Strobe Kits.

5KVA ISOLATION TRANSFORMER

As New Ex-equipment fully shrouded Line Noise Suppression, Ultra Isolation Transformer with terminal covers and Knock-out cable entries. Primary 120/240V Secondary 120/240V 50/60 Hz. .005 pF Capacitance Size L.37 x W.19 x H.16cm Weight 42 Kilos. PRICE

£120.00 +VAT

ex-warehouse. Carriage on request.

24V DC SIEMENS CONTACTOR

Type 3TH9022 DB 2 x NO and 2 x NC 230V AC 10A contacts Screw or Din Rail fixing. Size H 120 x W 45 x 0.75mm. Brand New Price £7.63 incl. P&P and VAT.

240V AC WESTOOL SOLENOIDS

TT2 Mod 1 flat. 1 MAx stroke 1/4 in. Base mounting 1/2in. stroke 5lbs pull approx. TT8 Mod 1 Flat. 2 Max stroke 1/8 in. Front mounting 1/2in. Front mounting 1/2 in. stroke 15lbs pull approx. Price incl. p&p & VAT. TT2 £5.88, TT8 £8.81. SERIES 400 £7.64.

AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan. Price £7.29 incl. P&P and VAT. Other voltages and sizes available from stock. Please telephone your enquiries.

INSTRUMENT CASE

Brand new Manuf. by Imhof L31 x H18 x 19cm deep. Removable front and rear panel for easy assembly of components. Grey finish complete with case feet. PRICE £16.45 INCL. P&P & VAT 2 off £28.20 Inclusive.

DIE CAST ALUMINIUM BOX

with internal PCB guides. Internal size 265 x 165 x 50mm deep. Price £9.93 incl p&p & VAT. 2 off £17.80 incl.

230V AC SYNCHRONOUS GEARED MOTORS

Brand new Ovoid Gearbox Crouzet type motors H 65mm x W 55mm x D 35mm 4mm die shaft x 10mm long. 6 RPM anti cw £9.99 incl p&p & VAT. 20 RPM anti cw Depth 40mm £11.16 incl p&p & VAT.

SOLID STATE EHT UNIT

Input 230/240V AC, Output approx 15KV. Producing 0mm spark. Built-in 10 sec timer. Easily modified for 20sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case

£8.50 + £2.40 p&p (£12.81 inc VAT) NMS

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Argon Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

WASHING MACHINE WATER PUMP

Brand new 240V AC. fan cooled. Can be used for a variety of purposes. Inlet 1 1/2in. outlet 1 in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

SWC SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE

TINNED WIRE SILVER

PLATED COPPER WIRE

SOLDER EUREKA WIRE

NICKEL CHROME WIRE

BRASS WIRE LI TZ WIRE

BIFILAR WIRE MANGANIN

WIRE TEFFEL WIRE NICKEL

SAE BRINGS LIST 18 RAVEN

RD LONDON E18 1HW

FAX 0181 559 1114

TRANSFORMERS

Variable Voltage Technology Ltd

TRANSFORMERS

For valve and transistor circuits

HT Filament chokes high & low voltage

Standard and custom design

large and small quantities

Unit 24E, Samuel Whites Estate, Medina

Road, Cowes, Isle of Wight PO31 7LP

Tel 01983 280592 Fax 01983 280593

PRINTED CIRCUIT BOARDS

PRINTED CIRCUIT BOARDS

DESIGNED & MANUFACTURED

• PROTOTYPE OR PRODUCTION QUANTITIES

• FAST TURNROUND AVAILABLE

• PCBs DESIGNED FROM CIRCUIT DIAGRAMS

• ALMOST ALL COMPUTER FILES ACCEPTED

EasyPC / Aries / VUTrax / CadStar

Gerber / HPGL / IDraw and many others.

• ASSEMBLY & TEST AVAILABLE

TELEPHONE 01232 738897

INTERNATIONAL +44 1232 738897

agar FAX - 01232 738897

Circuits Email - agar @ argonet.co.uk

Unit 5, East Belfast Enterprise Park

308 Albertbridge Road, Belfast, BT5 4GX

PLANS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and com-puter graphics tablet. 150 projects. For catalogue, SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

QUARTZ CRYSTALS

QUARTZ CRYSTALS 100 KHz - 100 MHZ at low cost. Full list available and technical advice. Q-Electronic Design Associates. Tel: 0181-391-0545. Fax: 0181-391-5258.

ELECTRONIC MANUFACTURING

Professional Sub-Contract Manufacturing and Suppliers to the Electronics Industry.

Phone Steve on (01438) 360406 or fax details of your requirements to us on (01438) 352742.

EQT LTD., UNIT 5, First Floor, Caxton Point, Bessemer Drive, Stevenage HERTS SG1 2XT

SOFTWARE

PIC Principles software

Now available as a separate module of Electronics Principles 5.0.

Provides a thorough introduction and understanding of the PIC devices and contains a huge amount of additional information.

See inside front cover for details.

CLASSIFIEDS

GET

RESULTS

FAST

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

TEL 0181-995 1560 FAX 0181-995 0549

ACCOUNT CUSTOMERS MIN. ORDER £10



Ample Parking Space

Broadcast Warehouse

FM TRANSMITTERS & ACCESSORIES

FM radio kits, Prebuilt kits, Custom built and Professional FM broadcast equipment. In use by broadcasters worldwide. We also ship worldwide and accept major credit cards. Equipment hire and R.S.L. consultation service available. All equipment is fully guaranteed for 12 months.



call for your free brochure.


PHONE / FAX: 0181 2880192



TRANSMITTERS, AMPLIFIERS, STEREO, R.D.S., ANTENNA'S & MUCH MORE

1 WATT L.C.D. P.L.L. TRANSMITTER

ONLY £84.99 (KIT FORM)

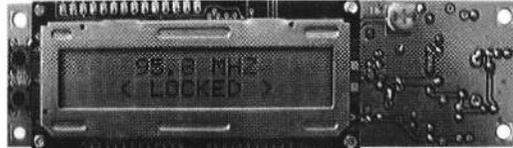

check out our products online
www.broadcast-warehouse.com

HOBBY, COLLEGE, HOSPITAL AND PROFESSIONAL RADIO

To Advertise in the next available issue of ETI

call Mark Colyer

01322 660070

Remember classified get results fast

NEW FROM NEXUS!

An Introduction to Robotics

A fascinating and unique book that breaks new ground by exploring the exciting world of robotics in a clear and concise way. Both the theoretical and practical aspects are presented in an uncomplicated fashion using everyday English, which makes this an ideal book for the amateur. Divided into two sections, the first part explains how and why robots work and are controlled, while the

second shows you how to make a simple two legged humanoid robot that can be programmed to walk. There are no complicated formulas or equations to grapple with or incomprehensible circuit diagrams to decipher, - this robot can be built on your kitchen table and can be run from any personal computer! All you need are model aeroplane servos, a controller, a power supply and some

plywood - and all parts are easily available in the UK and the USA. This is a book that will be of interest to modellers and everyone with a fascination for things mechanical and electronic. This is the way of the future, stay one step ahead and order your copy today! Only £11.50 UK & £12.50 Overseas (Includes Postage & Packing).

Telephone orders: 01322 616300 and ask for Nexus Direct

Please send me..... copies of NB299 @.....

I enclose my cheque/PO for £..... made payable to Nexus Special Interests OR please debit my Access/ Visa.

□	□	□	□	□	□	□	□	□	□	□	□	□	□	□	□
---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---


Expiry date..... Signature..... Name.....

Address.....

Post code..... Telephone No.....

Complete details and return coupon to: Nexus Direct, Nexus House, Azalea Drive, Swanley, Kent BR8 8HU.

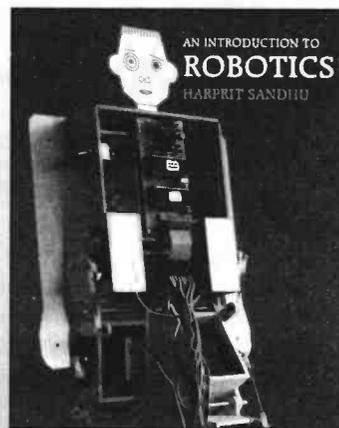If you do not wish to receive mailing from other companies, please tick box.



All adverts must be prepaid.
Cheques payable to:
Nexus Media Ltd.

ETI

Name

Address

Daytime Tel: No:

Signature

Date

PLEASE DEBIT MY ACCESS/BARCLAY CARD No.

□	□	□	□	□	□	□	□	□	□	□	□	□	□	□	□	□	□	□	□
---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---

EXPIRY DATE

FOR SALE COMPONENTS PLANS OTHER—PLEASE STATE

Please ring the required heading.

20 words lineage
£19.97
inc vat

3 x 1
£44.06
inc vat

ELECTRONIC TODAY INTERNATIONAL
CLASSIFIED ADVERTISEMENT DEPARTMENT,
NEXUS HOUSE, AZALEA DRIVE, SWANLEY, KENT BR8 8HU

Round the Corner

Limits to growth
In the light of the increasing complexity of semiconductors, it is exciting to hear from Ball Semiconductor that they have successfully transferred the metalisation pattern of an integrated circuit on to the surface of a sphere. The surface area of a sphere is proportional to the cube of its radius, so increasing the radius by 26 percent approximately doubles the area on which circuitry can be fabricated.

Ball's long term plan is to build a semiconductor fab in a sealed tube, and to make larger designs by joining ball integrated circuits using contact bumps on their surface. That's another way to increase the number of semiconductors in a small space. Early in the next century something more powerful than today's most powerful PCs will be small enough to lose in your pocket (always assuming you can get the heat out).

This could be useful, if plans to shut down analogue radio broadcasting early in the next century come to pass. Current DAB receivers are more

expensive than many people want to pay, and a reduction in the cost of processing would be welcome.

First, manufacturers will aim to sell the biggest systems they can for the real buffs. Later the tiny systems will appear. For constructors and designers the big systems are likely to hold more possibilities for add-ons and ideas than the small ones to begin with, but the size of construction is coming down too. Invest in a good bench magnifier rather than assuming that miniature construction is not practical.

The face of electronics is changing. Among other steps forward, we would like to hear from readers what projects and features they would like to see in future issues of the magazine, even if they seem impractical to start with.

There are many new components appearing, and advanced versions of older ones. If you are interested and have internet access, email us on eti@aaelectron.co.uk, and don't forget the website on <http://www.aaelectron.co.uk/eti/> But ordinary pieces of paper in non-virtual envelopes are very welcome, as always.

Next Month

Volume 27 No 9 of Electronics Today International will be in your newsagents on 14th August 1998. Mike Bedford will be reporting on the progress with Digital Audio Broadcasting. Robert Coward starts a construction project on a pro-standard large-scale moving display which can be built into a flight case. John Howden describes how to exploit plain spreadsheet programs to do circuit simulation. We are working on a major software review. See you in August.

Contents are in preparation but are subject to space and availability.

Make sure of your copy of **ELECTRONICS TODAY INTERNATIONAL**

Complete this coupon and hand it to your newsagent

Please order me a copy of *ETI* every month

Reserve me a copy Deliver it to my home

Name: _____

Address: _____

Postcode _____

ETI is distributed to newsagents wholesalers by Cornag Magazines Marketing, Tavistock Road, West Drayton, Middlesex, UB7 7QE.

Tel: 01895 444055 Fax: 01895 433602.

ETI
ELECTRONICS
TODAY INTERNATIONAL

Published by

Nexus Special Interests Limited
Nexus House, Azalea Drive,
Swanley, Kent BR8 8HU

Tel: 01322 660070 Fax: 01322 615636

Sorry, we cannot answer queries about projects or other technical queries on the phone. Our administration assistant Jenny can often help with other queries about this issue

Our web is <http://www.aaelectron.co.uk/eti/>
Email address: eti@aaelectron.co.uk.

Please note! This is currently only an editorial web site. Please send enquiries about subscriptions, advertising etc. to Nexus Special Interests' postal address above.

EDITORIAL

Editor

Helen Armstrong

Administration Assistant

Jenny Etheridge

Consultant

Andrew Armstrong

PRODUCTION

Designer

Paul Forster

Technical Illustrator

John Puczynski

Production Executive

Marie Quilter

Printed By

Wiltshire Ltd., Bristol

Origination by

Atelier, St. Austell

SALES

Midland and Southern Area Sales

Mark Colyer

01322 660070

Northern Area Sales

Denise Barrow

0161 776 4460

Newstrade Sales Manager

David Pagendam

MANAGEMENT

Group Managing Director

Tony DeBell

Divisional Managing Editor

Dawn Frosdick-Hopley

Divisional Sales Manager

Roy Kemp

Circulation Manager

William Pearson

Group Marketing Manager

Aileen O'Connor

SUBSCRIPTIONS


UK: Orders 01858 435344

Enquiries 01858 435322

USA: Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505-4509, USA. For VISA/Mastercard orders phone: (310) 375 6258. Fax: (310) 375 0548. Pacific Time 9am - 9pm weekdays 10am - 6pm weekends. Visa/MC/Discover accepted.

READERS SERVICES

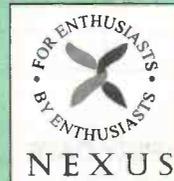Back issues (last 12 months) £3.20 per issue if available. Bins for *ETI* £7.50 each including UK post and packing. Overseas please add £1.50. Cheques to Nexus Special Interest at Nexus House, or phone VISA/Mastercard orders to Readers Service Department 01322 660070



© Nexus Special Interests Limited 1998
All rights reserved
ISSN 0142-7229

The Publisher's written consent must be obtained before any part of this publication may be reproduced in any form whatsoever, including photocopies, and information retrieval systems. All reasonable care is taken in preparation of magazine contents, but the publishers, editors and their agents cannot be held legally responsible for loss howsoever arising from errors or other published material.

The Affordable Solution for 8051 & AVR™ Microcontroller Support Tools

DISTRIBUTORS FOR



IAR Microcontroller Development Tools

C-Compilers, Assemblers, Simulators

8051, Atmel AVR, Hitachi H8



MICRO-PRO DEVICE PROGRAMMER

The complete programming solution!

Supports:

MICROCONTROLLERS

Atmel 89C, 89S, 90S(AVR),
Generic 87C, Dallas 87C520

FLASH MEMORY

Atmel 29C, 49F

SERIAL/PARALLEL EEPROM

Atmel 24C, 25C, 59C, 93C, 28C

CONFIGURATORS

Atmel 17C, Xilinx XC17

Not all devices may be supported within each family.



NOW SUPPLIED WITH LIBRARIES FOR...
29C, 49F, 24C, 25C, 59C, 93C
28C, 17C, XC17

Only... **£124.95**

Order Code: **MPW-PLUS**

PROFESSIONAL AVR™ MICROCONTROLLER STARTER SYSTEM

System Contents

- Combined Serial & Parallel Device Programmer
- Evaluation module for 8, 20 & 40-pin DIL devices
- In-System Programming (ISP) Cable
- Integrated Windows™ Development Environment
- AVR™ Basic LITE (1k bytes code) Compiler
- AVR™ Assembler
- Mains Power Supply Adaptor
- PC Serial Cable (Connects to PC COM Port)
- Atmel CD-ROM Datbook
- One AT90S1200 DIL Microcontroller



Figure 1

Order Code: **AVR2-ST**

Only... **£99.95**

WRITE IN BASIC RUN IN A FLASH

AVR™ BASIC

- Compiled BASIC generates tight AVR™ machine code
- Not a Run-Time Interpreter; NO code overhead!
- Target speeds comparable with assembler
- Breaks the cost barrier for small projects
- Ideal for educational, hobbyist and professional use

NEW PRODUCT!
Order Codes:
AVR-BAS-LITE
AVR-BAS-8K
Only... **£24.95**
and **£149.95**

FLASH 8051 Professional Starter System

System Contents

- Combined Serial & Parallel Device Programmer
- Evaluation module for 20 & 40-pin DIL devices
- In-System Programming (ISP) Cable
- Keil PK51-2K Integrated Windows™ Development Environment (2K code limit). Includes C-Compiler, Macro Assembler, Linker, Hex Creator, Editor & Simulator
- Mains Power Supply Adaptor
- PC Serial Cable
- Atmel CD-ROM Datbook
- One AT89S8252 40-pin DIL Microcontroller

System layout shown in Fig 1 above

Order Code: **EQ-8051-ST1**

Only... **£124.95**

Micro-ISP Series III


Serial Programming System for the Atmel AVR™ & 89S microcontroller families



NEW PRODUCT!

Typical In-System Programming (ISP) Scenario shown below:

Supports: Atmel 89S, 89LS, 90S(AVR)

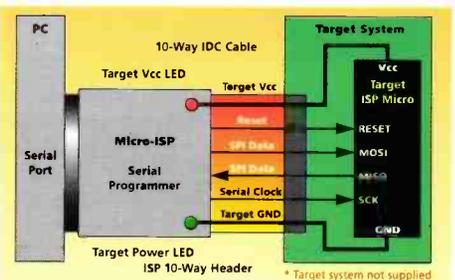


Order Code: **UISP-S3-SYS**

Only... **£39.95**



THE ULTIMATE 8051 TOOL SET

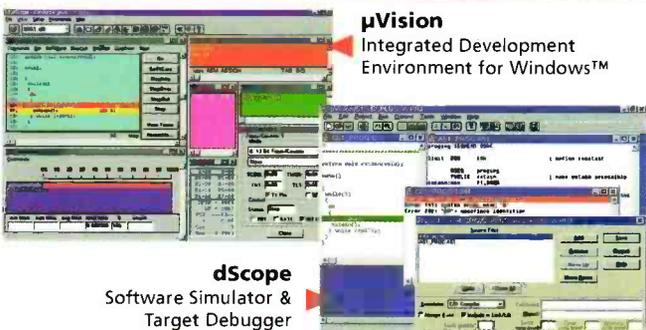

- Optimising Ansi-C Compiler
- Macro Assembler
- Linker
- Software Simulator
- Integrated Editor
- Hex Creator

Starter Systems supplied with 2K Toolset & Development Systems supplied with 8K Toolset are available for Atmel, Dallas, Siemens, Temic 8051 microcontroller derivatives



The Embedded Solutions Company

3 Atlas House St Georges Square Bolton BL1 2HB England



For sales tel: +44 (0) 1204 529000, fax: +44 (0) 1204 535555, e-mail: sales@equinox-tech.com, Web Site: www.equinox-tech.com


EQUINOX DISTRIBUTORS: AUSTRALIA Farnell +61 2 9645 8888 AUSTRIA Farnell +43 0660 87 75 BELGIUM Alcom Electronics NwSa +32 3 227 36 47 BRAZIL HasteC +55 11 522 1799 Anacom +55 11 453 5588 DENMARK Farnell +45 44 53 66 44 EIRE Farnell +353 1 8309277 FINLAND Farnell +358 9 3455 400 FRANCE Farnell +33 474 65 94 66 Newtek +33 1 4687 2200 GERMANY Elektronik Laden +49 52 32 81 71 Farnell +49 89 61 39 39 39 Ineltek GmbH +49 7321 93850, MSC Vertriebs GmbH +49 08 9945532 12 GREECE Microtec +30 1 5395042 4 HONG KONG Farnell 800 968 280 (HK Direct Toll Free) ITALY Farnell +44 113 231 1311 Grifo Italian Technology +39 51 89 20 52, Newtek Italia +39 2 33 10 53 08 MALAYSIA Farnell +60 3 773 8000 NETHERLANDS Alcom Electronics BV +31 10 4519533 Antratek +31 10 450 4949 Farnell +31 30 241 2323 NEW ZEALAND Farnell +64 9 357 0646 NORWAY ACTE NC +47 63898900 Jakob Hatteland Electronic AS +47 53763000 PORTUGAL Anatronc +35 119 371 834 Farnell +44 113 289 0040 SINGAPORE Farnell +65 788 0200 SPAIN Anatronc SA +34 1 366 01 59 Farnell +44 113 231 0447 SWEDEN ACTE NC +46 8 445 28 70 Farnell +46 8 730 50 00 SWITZERLAND Anatec Ag +41 41 748 32 41 Farnell +41 1 204 64 64 UNITED KINGDOM Abacus Polar +44 1925 626626, Farnell +44 113 263 6311 Rapid Electronics +44 1206 751166 Quarndon Electronics +44 1332 332651 USA Hitools Inc +1 408 298 9077 Newark Electronics +1 800 718 1997, Peachtree Technology +1 770 888 4002 Pioneer Standard +1 888 832 3976

Equinox reserves the right to change prices & specifications of any of the above products without prior notice. E&OE. All prices are exclusive of VAT & carriage. AVR™ is a trademark of the Atmel Corporation

PROTEUS


Schematic Capture

NEW Version IV

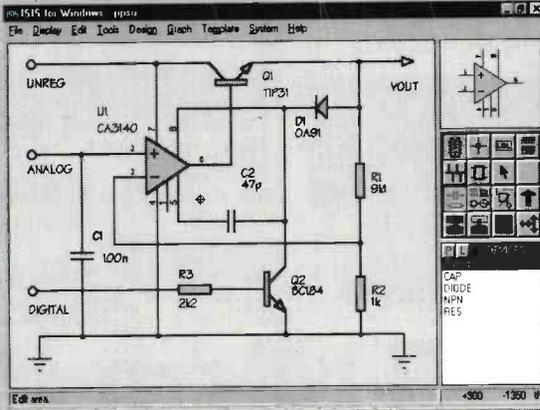

- Produces attractive schematics like you see in the magazines.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Full support for buses including bus pins.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.

Simulation

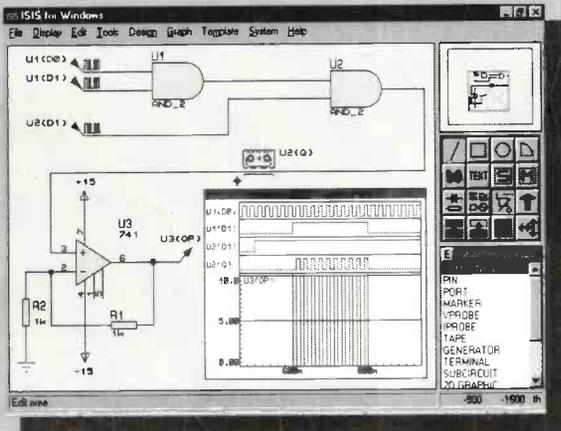

- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.

FREE
SOFTWARE
ISIS & ARES Lite
Schematic & PCB
Design

**SHAREWARE VERSIONS
AVAILABLE TO DOWNLOAD
FROM OUR WEBSITE**

<http://www.labcenter.co.uk>

labcenter
Electronics

The IVth Generation


New Features

- Component Auto-Placer
- Pinswap/Gateswap Optimizer
- Background Regeneration of Power Planes
- Enhanced Autorouting with Tidy Pass
- Full Control of Schematic Appearance
- Extensive New Component Libraries

Available in 5 levels - prices from £295 to £1625 + VAT.
Call now for further information & upgrade prices.

PCB Design

NEW Version IV

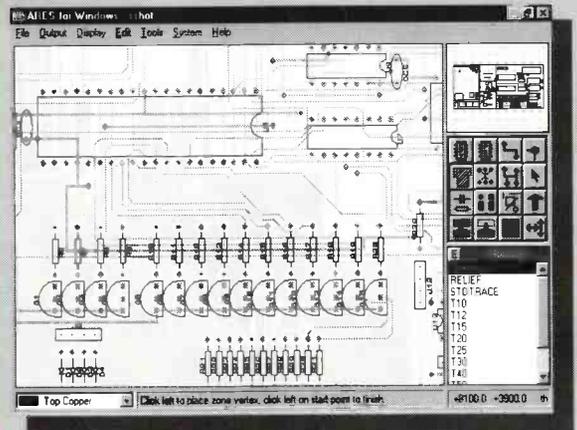

- Automatic Component Placement.
- Rip-Up & Retry Autorouter with tidy pass.
- Pinswap/Gateswap Optimizer & Backannotation.
- 32 bit high resolution database.
- Full DRC and Connectivity Checking.
- Shape based gridless power planes.
- Gerber and DXF Import capability.

**"PROTEUS
is particularly good**

with its rip-up-and-retry

EWV January 1997

autorouter"

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857. EMAIL: info@labcenter.co.uk
53-55 Main St, Grassington. BD23 5AA. WWW: <http://www.labcenter.co.uk>

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.