

ELECTRONICS *in* ACTION


May 1994 £2.25

PC Sound Sampler

Digital Echo Unit

Stereo Infra Red Headphones

Active Loudspeakers

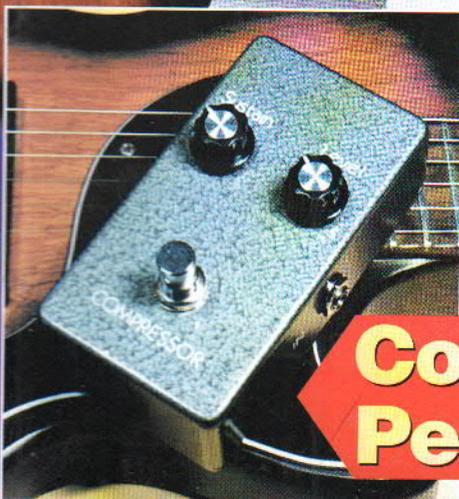

Compressor Pedal Give yourself a bit more OOMPH!




ISSN 0969-3564
9 770969 356005

Design and Verify Circuits. Fast.

DOS, Windows
versions available


Electronics Workbench®

NEW Version 3

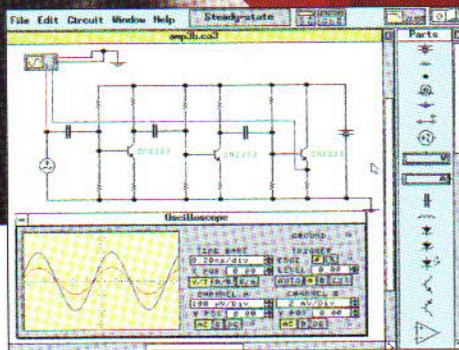

Analog Module includes:

- complete control over all component values
- ideal *and* real-world models for active components
- resistors, capacitors, inductors, transformers, relays, diodes, Zener diodes, LEDs, BJTs, opamps, bulbs, fuses, JFETs, and MOSFETs
- manual, time-delay, voltage-controlled and current-controlled switches
- independent, voltage-controlled and current-controlled sources
- multimeter
- function generator (1 Hz to 1 GHz)
- dual-trace oscilloscope (1 Hz to 1 GHz)
- Bode plotter (1 mHz to 10 GHz)
- SPICE simulation of transient and steady-state response

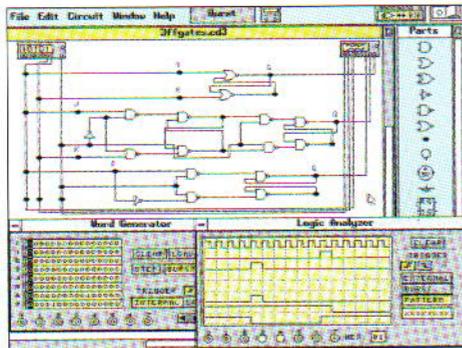

Digital Module includes:

- fast simulation of ideal components
- AND, OR, XOR, NOT, NAND and NOR gates
- RS, JK and D flip-flops
- LED probes, half-adders, switches and seven-segment displays
- word generator (16 eight-bit words)
- logic analyzer (eight-channel)
- logic converter (converts among gates, truth table and Boolean representations)




Complement Your Test Bench

Here's why Electronics Workbench belongs on *your* test bench: Wires route themselves. Connections are always perfect. And the simulated components and test instruments work just like the real thing. The instruments are indestructible and the parts bin holds an unlimited supply of each component. The result: thousands of electronics professionals and hobbyists save precious time and money. **Over 90% would recommend it to their friends and colleagues.** Electronics Workbench: the ideal, affordable tool to design and verify your analog and digital circuits before you breadboard.

And now the best is even better - Electronics Workbench Version 3.0 is here. It simulates more and bigger circuits, and sets the standard for ease of use. Guaranteed!

NEW Features in Version 3

- new components include JFETs, MOSFETs, voltage-controlled and current-controlled sources and manual, time-delay, voltage-controlled and current-controlled switches
- real-world models for opamps, BJTs, JFETs, MOSFETs and diodes - over 100 models available
- MS-DOS version now supports up to 16 MB of RAM for simulation of bigger circuits
- new Microsoft® Windows™ version available
- technical support now also available on CompuServe®

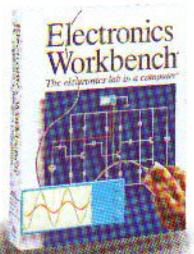

Just £199!

Electronics Workbench®

The electronics lab in a computer™

Call: (0203) 233216 

ROBINSON MARSHALL (EUROPE) LTD.

Nadella Building, Progress Close, Leofric Business Park,
Coventry CV3 2TF TEL: (0203) 233216 FAX: (0203) 233210

*30-day money-back guarantee.

Shipping charges - UK £4.99. All prices are plus VAT.
All trademarks are the property of their respective owners.



ELECTRONICS *in* **ACTION**

ISSUE 8 VOLUME 1

EDITOR

Paul Freeman-Sear

NEWS EDITOR

Geoff Martin

**DESIGN
and TECHNICAL
ILLUSTRATION**

Iain Houston

CONTRIBUTORS

Andrew Armstrong

Dr. Pei An

Daniel Coggins

John Linsley-Hood

Alan McKeon

Mike Meechan

Brian Padgett

Peter Roberts

Paul Stenning

ADVERTISING SALES

Gilly Martin

☎ 0442 842069

4 Here is the news...

What's going on in the technology world
A news view from all points of the compass.

8 Research World

Technical advances from around the globe.

9 Subscriptions

Cut out the middle man get your copy direct from us.

10 the Centronic Sound Machine

Sample the better things in life with Dr. Pei An's PC compatible sound sampler.

20 Signal to Noise

Another batch of correspondence from the post bag.

24 An Act for the Cabaret

Peter Roberts dons hat and cane and explains the theory behind his 'Cabaret' active loudspeaker design.

30 The Evolution of Audio Amplifier Design Part 4

John Linsley Hood wonders - 'True Hi-fi at last?'

36 Under Pressure

What's compact, easy to build and flattens you before giving you a boost? Daniel Coggins audio compressor.

42 Cordless Audio

Andrew Armstrong helps us keep our neighbours friendly with his Infra Red stereo audio transmitter.

46 The Alchemist

Mike Meechan now gets to grips with this Hi-Fi pre-amp.

52 Echo Base

Echo Echo Echo. Paul Stenning's Digital echo unit will ensure you have astounding repeat performances, again and again.

60 Ideas Forum

Where innovative ideas turn into inventions.

61 At Your Service

The one stop shop for PCBs past and present.

62 Technoshop

More offers and exchanges in our monthly team-up with The Technology Exchange.

64 Future View

Alan McKeon, International Vice President of Iterated Systems, considers still and moving images and how the human eye sees them, how computers handle them and how they will be delivered across the information super-highway.



Page 10



PO BOX 600, BERKHAMSTED
HERTS. HP4 1NL
TELEPHONE 0442 842069
FAX 0442 842279

The musical sound of technology

Thank you for your comments regarding the magazine. I know you have been telling friends about us and what a refreshing change our mag is. Do let us know if there any newsagents where we cannot be found.

There continues to be a growing interest in Electronic Music Technology as those colleges and universities already running courses will verify. You will see amongst these pages another college offering such a course. It is good to see that this branch of electronics education is quickly expanding. The means to explore musical creativity using electronic instruments and computers has never been greater and is within easy reach financially to many people. It is right therefore that the best way to get maximum benefit from such highly complex technology is to use the facilities and guidance of a college course. Keep an eye out in future editions of this mag for the college that might be able to help you.

Finally we hope this special audio edition will help those at home, at college or university to enjoy the fruits of audio electronics and music.

Paul Freeman-Sear

Every care is taken when compiling the magazine. However, the publishers cannot be held legally responsible for errors in the magazine or from loss arising from those errors. Any errors discovered will be published in the next available edition of the magazine.

Electronics in Action is published on the third Thursday of the month preceding the cover date. The magazine contents remain the copyright of Quantum House Publications Ltd. Any reproduction requires written consent of Quantum House Publications Ltd. All prices contained in the magazine are correct at time of going to press. The publishers or the advertisers cannot be held responsible for any variations in price or availability after the magazine has gone to press.

Published by **Quantum House Publications Ltd.**, PO Box 600, Berkhamsted, Herts. HP4 1NL. Newstrade distribution by Seymour, Windsor House, 1270 London Rd., Norbury, London SW16 4DH Tel: 081 679 1899. Reproduction by Island Graphics, Chesham, Bucks. Tel: 0494 773082. Printed by Wiltshire (Bristol) Ltd., Philip St., Bedminster, Bristol BS3 4DS. Tel: 0272 760076

NEWS

This years Awards were presented by His Royal Highness The Duke of York at a special dinner for finalists at the Science Museum at the end of March.


This is the ninth annual occasion that the Awards have been made for young minds with a talent for electronic design. The scheme was set up to help bridge the gap between the two different worlds of science and commerce where very often few clever inventions ever leave the laboratory bench owing to poor marketing and packaging.

The Young Electronic Designer Awards scheme is open to students in secondary schools, colleges and universities between the ages of 12 and 25, and challenges young designers to invent and produce an electronic device that meets an everyday need.

The event is organised by the YEDA Trust, a registered charity, and sponsored by Texas Instruments Ltd. and Mercury Communications Ltd.

For further information on how to enter for next year contact:

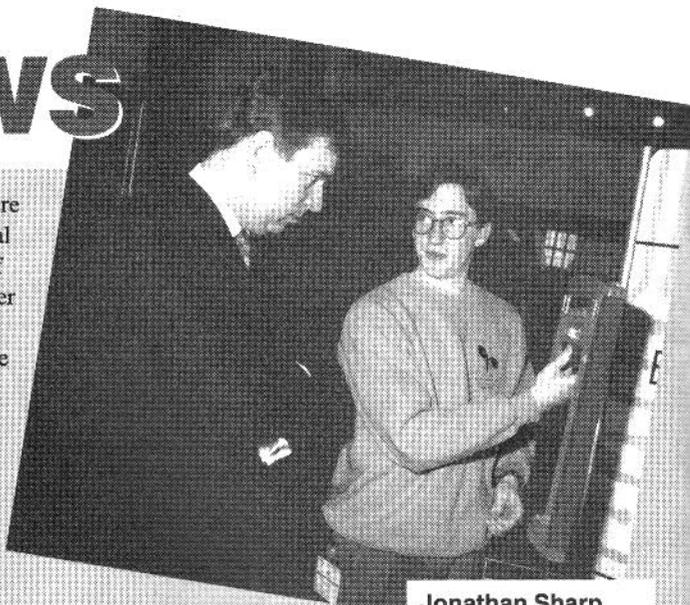The YEDA Trust, 24 London Road, Horsham, West Sussex, RH12 1AY Tel: (0403) 211048 Fax: (0403) 210770



Jonathan Sharp demonstrates his award winning project to the Duke of York

Young Electronic Designer Awards

The following is a list of this years finalists and the winners together with their ideas.

SENIOR CATEGORY

Jonathan Sharp (23) 1st Prize Winner
Brunel University, Egham, Surrey
A rechargeable electronic foot measuring device for use in shoe shops.

Samantha Haines (19)
Cheltenham College, Cheltenham, Glos.
A physiotherapy aid indicating weight distribution between the feet of stroke patients and others with sporting injuries.

Richard Mead (18)
Cheltenham College, Cheltenham, Glos.
A built-in device to discourage the theft of electrical appliances.

New PCMCIA card in Europe

IBM has extended its family of PCMCIA (Personal Computer Memory Card Interface Association) cards to the European market. These include Infrared Wireless Adapters, an audio adapter, a Data/Fax Modem card and an RS232 Adapter based on the PCMCIA standard. A PCMCIA card makes a PC more flexible. Originally designed for the mobile computing market where low power consumption and small size are critical, these credit card-sized cards can

make it easier to change the configuration of any type of PC and use it as a communications, I/O, storage and multimedia device.

IBM offers three infrared wireless adapters, for PCMCIA and each card includes a transceiver giving mobile users the benefits of a wireless Local Area Network (LAN).

The adapters transfer data at 1Megabit/sec and can be used with new or existing wired LANs such as Ethernet or LANs running Novell's Open Data Link Interface.

It is a non-line of sight adapter, which means that transceivers do not have to be aimed at each other or at a fixed position and will have full communication in a 30' x 30' room.

Kevin Noakes (22)

The Royal Naval Engineering College, Plymouth
Medical Monitor which automatically records and displays patient data such as temperature and respiration rates.

Caroline Turner (20)

Southampton University, Southampton, Hampshire
A low cost Time Interval Analyser for measuring the quality of recording/replay systems in conjunction with oscilloscopes.

Andrew Sime (18)

Hampton School, Hampton, Middlesex
A microprocessor based digital aquarium controller.

INTERMEDIATE CATEGORY

Gareth Sylvester-Bradley (17)

Bryanston School, Blandford, Dorset
A hand-held digital anemometer.

Nichola Hirschmann (18)

Woldingham School, Woldingham, Surrey
A project to develop a hardware solution to sequential computing to facilitate faster data processing speeds.

Graham Reith (17)

Merchiston Castle School, Edinburgh
The Intelligent Drawer, a system for cashiers at check-out tills enabling the correct change to be dispensed involving the fewest number of coins.

Neil Gray (16) & Roberto Tyley (15)

Blyth Ridley County High School, Blyth, Northumberland
A hazard detection and indication system to help with the safe evacuation of a building in the event of fire or other emergency.

Stephen Sinfield, Angela Assorto, Alasair Mitchell & Avi Bhattacharyya (All 17)

1st Prize Winners

St Albans School, St Albans, Hertfordshire
'Centralan' - an electronic corrosion tester for central heating systems.

Anthony Powell (15)

Chigwell School, Chigwell, Essex
An electronic timer mechanism to open/close doors at pre-set intervals.

JUNIOR CATEGORY

Oliver Webster & Fraser Prudhoe (both 13)

Amble Middle School, Amble, Northumberland
An in-car alarm which is activated when a motorist exceeds a pre-set speed limit in fog.

Jonathan Moodie & Jeremy Brettell (both 14)

1st Prize Winners

Cheltenham College, Cheltenham, Glos.
'Hypofill', a device which recharges hyperdermic syringes with the required dose of insulin for diabetics with impaired vision.

Claire Athey (14)

Bancroft's School, Woodford Green, Essex
An electronic learning device involving visual association.

Louise Valentine & Helen Berry (both 14)


Cardinal Newman School, Luton, Bedfordshire
A pocket-sized carbon monoxide warning device for cyclists and other road users.

Alistair Phipps (15)

Merchiston Castle School, Edinburgh
JIVE (Junior Interactive Visual Educator) a computer based system to develop key learning skills in pre and primary school children.

Rebecca Salmen & Alys Patterson (both 14)

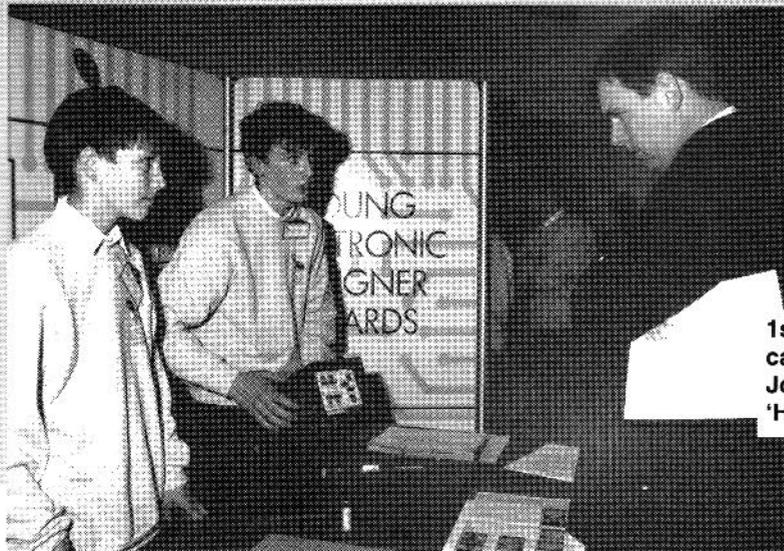King Edward VII School, Sheffield
'Number Spin', a device which randomly selects and displays numbers for children with impaired vision.



1st prize winners in the junior category, Jeremy Brettell and Jonathan Moodie show their 'Hypofill' to the Duke of York

An infrared wireless LAN allows users to share resources such as printers, ad hoc networks and disk drives by infrared-enabled mobile computer networks. For those wanting to take electronic mail and files away from their offices, wireless LANs provide a convenient way of uploading and downloading files from the desktop or even LAN-attached servers. They also allow multiple mobile users to share the same desktop printers and LAN access point.

The IBM Infrared Wireless Adapter is priced at around US\$150.

The Audio Adapter Card expands multimedia opportunities for portable

computing by adding high-definition 16-bit stereo sound to many software applications.

The audio adapter consists of a PCMCIA Type II card connected to a small, detachable, tethered Audio Interface Module. The module has a built-in mono microphone, stereo line-internal stereo microphone in-jack and stereo-out/headphone jack. The audio adapter features a high quality 16-bit stereo CODEC to record and play back audio signals. The card can record and play back upto a sampling frequency of 48KHz, using 8 or 16bit resolution in stereo or mono form.

The audio adapter will be shipped

with drivers for DOS and OS/2 operating systems that are compliant with PCMCIA Standard Version 2. A driver for Windows 3.1 that consists of a point enabler for Intel 82365SL chipsets is available with the initial release of the product. IBM software is packaged with the adapter to add a full range of audio functions, including text to speech translation, internal MIDI synthesis capabilities and .WAV recording and playback.

In DOS, OS/2 and Windows environments, the audio adapter card allows a full range of programs to be run, including: IBM's Linkway Live V1.0 and StoryBoard Live V2.0 for DOS; Microsoft Video for Windows; Lotus Freelance Graphics for Windows

2.0 and WordPerfect Presentation for Windows 2.0 in the Windows environment.

The 14.4/14.4 Data/Fax Modem allows users to communicate at data rates up to 57.6Kbps (with V.42bis data compression) and fax rates upto 14.4Kbps. It also supports AT and Fax Group 3, Class 1 and 2 commands used by most third party fax and data software. A lowerspeed, lower-cost 2.4/9.6Kbps data/fax modem will be available in the second quarter of the year.

BT Brings Information Superhighways closer


BT has taken another step forward in bringing the information superhighway nearer to reality. They have produced a device at its Martlesham Heath Laboratories, which will increase the capacity of current optical fibre links from around 1,900 simultaneous phone conversations to a high of 78,000. The technology also has the potential to handle 150,000 calls over 150km of continuous fibre optic cable.

The new product is expected to play a major part in tomorrow's information superhighways in allowing existing 1.3 micron fibre optics - of which there are more than three million kilometres in BT's UK network - to achieve far greater data rates over much longer transmission distances.

The superhighways could carry a mixture of analogue and both compressed and uncompressed digital signals to make it technically possible to deliver such services as three-dimensional television, interactive multimedia services (sometimes referred to as video on demand), high quality audio and computer data to the office or home.

Previously, BT researchers have been involved in the development of 1.5 micron amplifiers, which led to improvements in capacities in the longer wavelength 'window'. The current breakthrough increases the signal strength by 1,000 times at 1.3 microns in the region of the spectrum where pulse distortion is about 10 times lower.

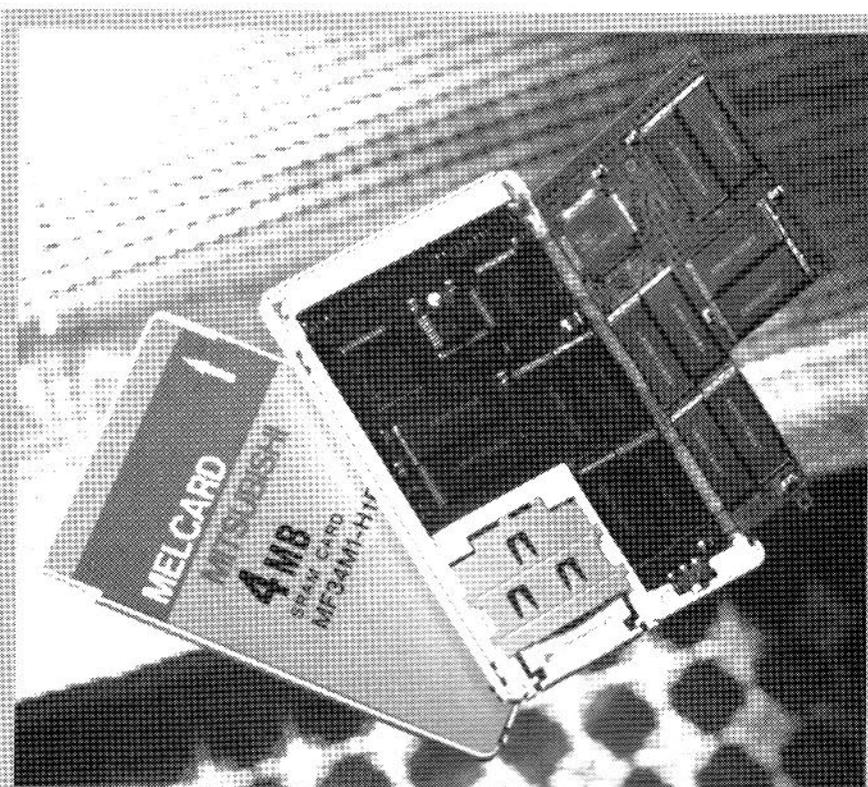The new optical amplifier is compatible with the existing optical fibre infrastructure and will allow the full bandwidth of BT's existing fibre optic investment to be used.



World's Thinnest IC Packaging Technology

The world's thinnest IC packaging technology is now in mass production. Dual Tape Carrier Packaging or DTP as it is known, is only 0.5mm thick and has been designed to make memory cards just 3.3mm thick with capacities greater than hard disk drives.

Mitsubishi has created DTP by making a variety of improvements particularly in moulding. The first memory cards produced incorporating the new process were the company's 4Mbyte SRAM cards called MelCards.

Hard disk drives that are currently being built into the latest notebook PCs

in Japan have memory capacities up to 40Mbytes. DTP based memory cards, however can more than double that capacity and measure just 3.3 x 54 x 85.6mm. Furthermore, through the use of ICs, access times are considerably faster than can be achieved by magnetic media.

The benefits of solid state memory cards over conventional rotating media such as hard disk drives is that they provide long term reliability and have the major advantage of having no internal moving parts, and therefore nothing to wear out.

The full 20 bit treatment

Independent classical recording company, Modus Music has acquired two Nagra D recorders to further the company's commitment to 20 bit recording.

The company which produces recordings for labels as diverse as EMI, Chandos, Conifer, ASV, BMG and even Sony in Japan, has been able to offer a 20 bit recording and editing capability since November last year. With the purchase of the two Nagras, equipped with on-board 20 bit A to D converters,

the company now has five 20 bit capable recorders in the field.

"The engineering quality is first class," confirms producer Tryggvi Tryggvason. "We often use two machines simultaneously for security, along with at least one time coded DAT so everything is in triplicate."

"Usually we record in stereo but having the facility for multitracking is very useful on a few occasions, where we have an organ that we require to overdub for instance. We have already used the four track facility in order to keep voices separate and not commit them to the mix until later. We can of course synchronize the two machines to provide us with an eight track system".


Modus operates four editing suites at its Hayes headquarters, with a choice of hard disk editing systems for 20 bit mastering. The label also maintains an almost permanent presence at All Saints Parish Church in Petersham, making extensive use of "one of the very best acoustics, anywhere".

Tryggvason sees the time when demand will dictate that all of Modus's work be in the 20 bit domain, as being in the near rather than the distant future. That of course will be good news for the CD listening public and good news for the Nagra D.

Control Network Research

The Cybernetics Department of the University of Reading has launched a three year S.E.R.C. (Science and Engineering Research Council) funded project to demonstrate the benefits of applying Echelon's LONWORKS control network architecture to process control applications.

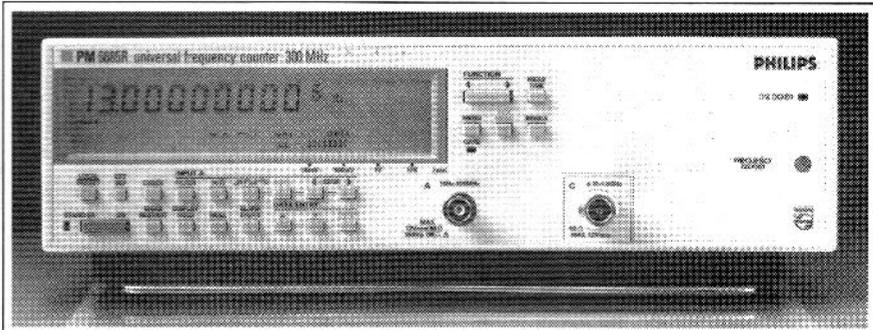The project has been set up in collaboration with Quad Europe who manufacture soldering machines, Toshiba who make the Neuron chip for Echelon, PAA Ltd, an independent consultancy and Echelon, developers of the LONWORKS architecture for



Atomic Accuracy

Fluke has increased the accuracy of its portable frequency counter/calibrators with the introduction of the PM6685 Rubidium. The built-in rubidium atomic clock gives a 10-digit display and an accuracy of 2.5×10^{-10} relative measuring resolution in a second, making this gadget the most accurate counter on the market.

The rubidium reference provides very high stability, even under severe operating conditions. The rubidium atomic resonance principle is intrinsically 100 times more stable than conventional electromechanical crystal resonators, which makes the use of a rubidium reference the right choice for field measurements and calibrations demanding accuracies better than one part in 10^8 , or where frequent calibration of the counter is not possible.

Warm-up time is within 6 minutes for a 1×10^{-9} accuracy.

Frequency options up to 4.5GHz.

linking Neuron-based control systems.

"The aim of the project is to show how distributed process control can bring benefits to a real life application," remarked Kevin Warwick, Head of Cybernetics at the University of Reading. "By distributing intelligence, wiring costs are decimated, the network stays up and running when one component fails and time-saving parallel processing becomes a reality," he said.

In three years, the University aims to develop a process control system suitable for commercial development.

Devices can be connected using any type of cable - twisted pair, power mains, optical fibre or RF. A mixture of these can be supported through routers.

The network centre is controlled by the Neuron chip, containing three microprocessors, on-board memory and a complete seven-layer open systems protocol. It is fully programmable and can be used in intrinsically safe applications by altering clock speed and power consumption. Neuron chips cost around \$10 today and should be \$5 within the year.

Musical Instrument Technology

Have you ever considered a career which combines both your interest in electronics and music? If you have then maybe you should be studying for a BTEC National Diploma in Musical Instrument Technology at Newark and Sherwood College, in Nottinghamshire. The College has for a number of years been one of the leading institutions in this specialized field and is able to offer one of only three such Courses in the country.

This exciting course was developed by course tutor Colin Boothman in conjunction with industry and BTEC. It lasts for two years and is designed for anyone who wishes to follow a career in sound production or reproduction. Much of the course material is practically based and students get the opportunity to carry out projects such as the

construction and testing of amplifiers, effects units and midi keyboards. Time is also spent looking at

electronics theory, the study of acoustics, microelectronics, musicianship and recording techniques. Although the course is mainly concerned with musical instrument electronics, music

theory and keyboard tuition are also included and the college's 16 track recording studio is available for use. The Programme of study is unit based and because the course leads to a nationally recognised qualification which is equivalent to 'A' levels it's equally appropriate for those wishing to go straight into employment and those who wish to carry on their studies at degree level. Past students have progressed to BEng, and BSc, degree courses in electronics and music electronics.

To gain a place on the course Students are normally required to have 3-4 GCSEs (including maths and science) and a genuine interest in music. Mature students with relevant experience will also be welcomed.

Newark and Sherwood College is based in the historic town of Newark-on-Trent and has gained an international reputation for its music based courses, attracting students of all ages from all over the world. As well as the National Diploma in Musical Instrument Technology the College also runs courses in subjects as diverse as Music Industry Studies, Piano Tuning and Violin Making.

Applications for the 1994/95 intake of students are currently being considered and if you would like further information about this course please telephone 0636 701411 for a brochure.

Research World

Technical Advances from around the Globe

Making the transition from electron beam X-rays lithography

A US company, Lockheed Corp., expects to be producing 0.15-micron microwave monolithic ICs by 1996 using X-ray lithography. It has already demonstrated 0.25-micron fabrication of MMIC amplifiers as it gears up for volume production of F-22 avionics modules.

Paul Hoff, director of MMIC circuit and module development at the defence contractor's Lockheed Sanders unit said Lockheed is making the transition from electron-beam to X-ray lithography as it moves toward affordable production of 0.25-micron MMICs for next-generation fighter aircraft.

Lockheed opened an automated module fabrication facility at the end of 1993 as the first step in the transition from e-beam to X-ray lithography. Hoff said the contractor expects to demonstrate production of 0.25-micron MMICs in a year.

The high cost of producing MMICs has been a major hurdle to broader military and commercial applications. Hoff said Lockheed's goal is to reduce the cost of high-performance MMICs for the F-22 from \$10 to \$2 per device.

Lockheed is the U.S. Air Force's prime contractor for the F-22 fighter and is also a member of the Texas Instrument Inc./Raytheon team for the second hardware-development phase of the Pentagon's Microwave/Millimeter-Wave Monolithic Integrated Circuits (Mimic) programme. That effort focuses on reducing MMIC production costs, conducting MMIC systems demonstrations and foundry support.

Using e-beam lithography, Lockheed has demonstrated MMIC technology by reducing the size of such equipment as a custom-made phase shifter to 200 equivalent phase-shifter chips in a 3-in wafer. While e-beam equipment is competitive with X-ray lithography in terms of definable feature size, it writes features directly, rather than patterning

an area in a single exposure. The increased time involved makes the process unsuitable for mass production.

Since each F-22 avionics module will contain about 20 MMICs at 0.25-micron feature size, Lockheed has begun the transition to X-ray lithography to produce the high-performance parts affordably. Lockheed Sanders produced its first X-ray-defined MMIC last year and is under contract with the Advanced Research projects Agency (Arpa) for a MMIC manufacturing demonstration using X-ray lithography.

Lockheed currently uses an X-ray stepper developed by Hampshire Instruments, a start-up that has gone out of business since the purchase.

Along with the X-ray source, Lockheed's MMIC foundry includes gear for attaching components using epoxy and solder with 0.5-mil placement accuracy, a robotic wire bonder and a carrier prober. The equipment permits direct attachment of MMICs and ceramic substrates to module housings of aluminium and silicon carbide.

The line has the capacity to assemble similarly to the wideband receive module being developed by Lockheed Sanders for the F-22 electronic countermeasure suite.

"To realize the full potential of MMICs, the cost must drop," Hoff said during a technology briefing recently. "X-ray lithography can realize a 10-20 times throughput advantage over e-beam lithography, with an associated reduction in chip cost."

If the market takes off, high-volume MMIC production could provide a badly needed technology driver for X-ray lithography. The physics of Gallium Arsenide, a semi-insulating material that naturally isolates devices from one another, makes it easy to define small-geometry devices. For example, a metal semiconductor field-effect transistor (MESFET) can be defined entirely with a metal pattern over a doped epitaxial layer. That makes it easy to push gallium arsenide designs below 0.25 micron.

"Gallium arsenide reduces many of the processing steps required in silicon, cutting back on alignment problems," Heaton said. Another advantage is the confinement of the really fine detail to small areas of the circuit. Those considerations apply to the broadband power amplifiers the company plans to produce in volume.

Making photovoltaics more economical

A potentially low-cost solar energy technology which uses solar concentrators and a photovoltaic cell is currently generating 1KW at Georgia Power's Shenandoah Environment and Education Centre in Newman.

The system, which has a measured, stabilized efficiency for converting sunlight in electricity without degradation of 15.5%, has been certified for participation in the Photovoltaics for Utility Scale Applications (PVUSA) project.

Called an integrated high-concentration photovoltaic (IRCPV) array, it consolidates structural, electrical, thermal and optical components into simple building blocks.

The integrated array is intended to eliminate unnecessary components so construction is simplified, to reduce capital and labour costs.

Central to the IRCPV system is a high-concentration solar cell developed at Stanford University. Sunlight-concentration solar cell systems use smaller area silicon cells than systems without concentrators.

According to EPRI, system efficiency can be raised to 20% by the end of 1994.

Amonix recently demonstrated a stable individual cell efficiency of 24%. Current plans are to build a 20KW unit in 1994.


The company believes that by the end of the decade it will be able to deliver systems based on this technology for \$2000/KW or provide power at 5 cents/KWh with a production run of 100MW.

At that price it should become competitive for a wide range of applications including utility scale generation in high sunlight areas.



WHO KNOWS WHERE TECHNOLOGY WILL TAKE US?

Every month Electronics in Action attempts to find out by presenting you with top quality construction projects, excellent features on the latest technology, and a peek at the future by some of the finest scientists and industrialists the world has to offer. A 12 month subscription will ensure that you stay fully informed about, and be a part of future developments. All this for £27 (post free)* if you live in the UK or £42 if you are overseas. Which just leaves us wondering - How long before we have personal rocket packs on the beach?

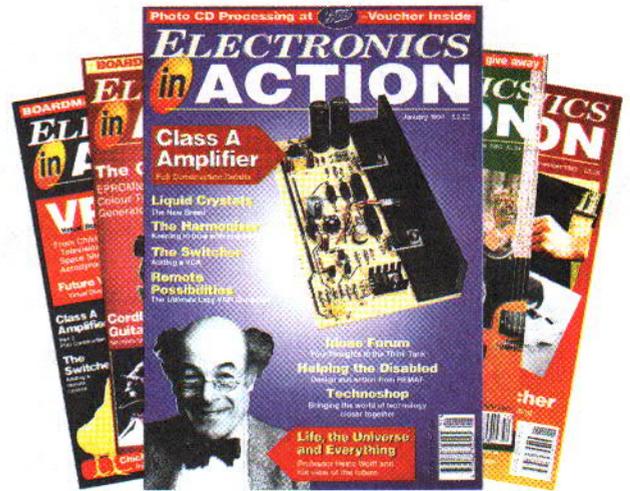

MAKE SURE YOU'RE NOT MISSING OUT

SUBSCRIPTIONS

Please start my 12 month subscription to **Electronics in Action** from the issue

Please print your name and address in **BLOCK CAPITALS**

Name

Address

..... Postcode

I enclose a cheque/postal order (payable to Electronics in Action) for £

Please send this form to: **Electronics in Action, PO Box 600, Berkhamsted, Herts. HP4 1NL**

ELECTRONICS
in ACTION

*In the UK only

the Centronic Sound Machine



Sample the better things in life with Dr. Pei An's PC compatible digital sound sampler

Computer technology has developed rapidly in recent years. Nowadays modern computers work at much greater speed than their old generations. Most of them

are equipped with VGA (Video Graphic Array) cards and high-resolution colour monitors which allow the computers to produce impressive graphics on screen display. Some computers are installed with sophisticated sound cards which enable the computer to generate complicated

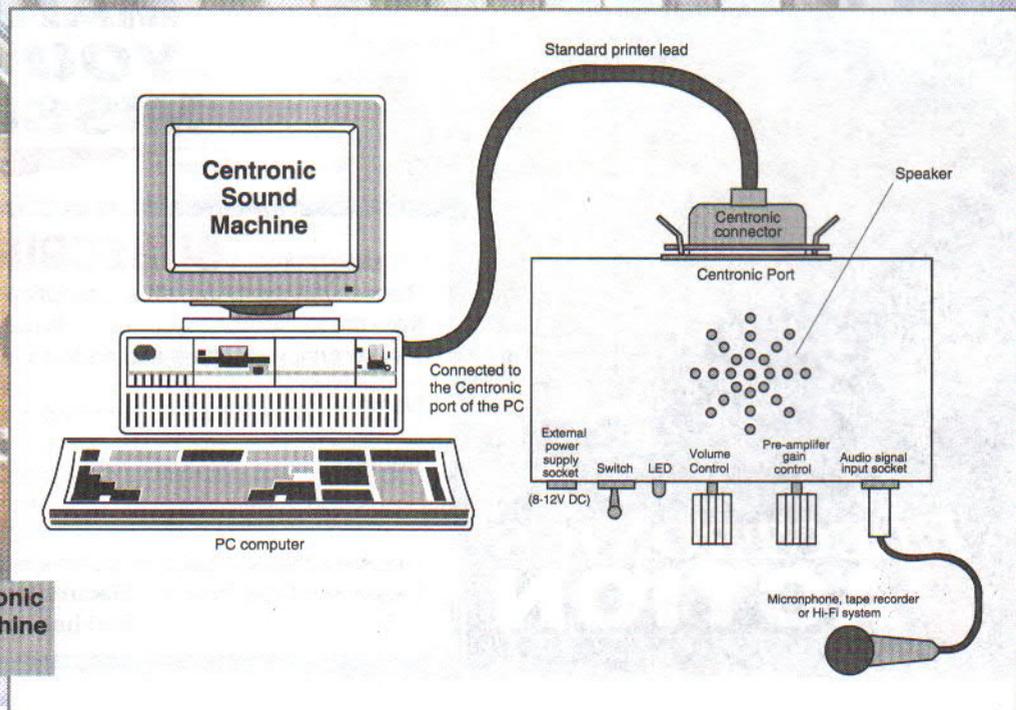


Fig.1 Centronic Sound machine system

sounds such as music and speech.

This is a computer project and is called, for want of a better term, 'the Centronic Sound Machine'. Briefly it is a sound sampling and playing-back device. It allows a computer to digitize sound samples into digital form and to convert the digitized data back to sound. Sounds to be digitized may come from a microphone, a tape recorder or a hi-fi system. This device is supported by several pieces of public domain musical software and is capable of producing high quality musical sounds. It is plugged directly into the PC's printer port and costs less than £30 to build. Figure 1 shows the simple arrangement of the Centronic Sound Machine system.

Computer Sound

The simplest form of sound wave is the sine wave. The amplitude (A) and frequency (f) are two parameters determining the characteristics of the sine wave (see Figure 2a). The amplitude represents the loudness of the sound and the frequency determines the pitch. Sounds from the real world, however, are far from sine waves. They are complicated and consist of a number of sine waves (Figure 2b). For example, when a piano playing a note of a basic frequency of 440Hz, it emits the basic sound wave of 440Hz. Meanwhile, it also emits other sounds, also termed as overtones, that occur as multiples of the sound's basic frequency e.g. 880Hz, 1320Hz, 1760Hz and other multiples of 440Hz with each having different amplitudes. The combination of overtones is unique for a particular musical instrument and determines the characteristic of the instrument.

Synthesising natural sounds digitally, mainly uses two methods. The first one is the Frequency Modulation (FM) method and the other one is the Wavetable method. The principle of the FM method is that a sine wave of a basic frequency is modulated by an envelope of a particular shape. The frequency of the sine wave determines the frequency of the sound and the envelope determines the progression of the sound's loudness. In

most cases, the envelope is described by four parameters characterising the Attack, Decay, Sustain and the Release (Figure 3a). Sounds from various musical instruments can be synthesized by varying these parameters. The wavetable method is a new technique and has almost replaced the FM synthesis in the professional music industry. It uses actual digitized sound samples to reproduce sound of musical instruments and results in a very lifelike sound effect. The working of this Centronic Sound Machine is based on this method.

Sound digitizing and reproducing

Digitizing, also termed as sampling, is a process in which an analogue sound signal is converted into digital data. This is performed by a device known as the Analogue to Digital Converter (A/D converter). The sound is sampled at regular intervals (Figure 3b) determined by the sampling rate (or sampling fre-

For example, a sampling rate of 4000Hz will generate 4000 digital values per second. With a sampling rate of 44100Hz, 44100 bytes of data are generated. This is obvious that the data will occupy a huge amount of memory space. Therefore, a compromise has to be made between the sampling rate and sample quality. To choose an optimum sampling rate, Shannon's formula is used. According to the formula, to retain all the information of a sound signal to be digitized, the minimum sampling rate should be equal to a frequency which doubles the highest frequency of the sound. Since the highest frequency that our ears can hear is around 20000Hz, a sampling frequency of at least 40000Hz is needed. This is why most audio CD systems utilize a sampling rate of 44100Hz.

Playing-back is a process in which digital sound data is used to reproduce the sound. Digital to Analogue converters are used in this case (Figure 3b). When a digitized sound is played back at the same rate as its sampling rate, it sounds the same as the original. If the playing back rate is lowered, the reproduced sound is slower and lower. On the contrary, if the sample is played back at a higher rate, the sound is faster and higher. This technique is used to create various sound effects. For example, if we sample a sound from a musical instrument playing Concert A (440Hz) with a sampling rate of 10KHz, and then we play back the sample at a rate of 20KHz, the sound of the sample will still have similar characteristics of that instrument but is one octave above the original.

The Works

The centronic sound machine consists of 6 units: the pre-amplification unit, A/D conversion unit, Centronic interfacing unit, D/A conversion unit, audio amplification unit and power supply unit. When digitizing sound, the sound signal from the microphone or

from other sources, is amplified by the pre-amp unit. This amplified signal is fed into the A/D converter unit where it is converted into digital data. The data is then read into the computer via the Centronic interfacing unit. To play back digital sounds, the Centronic port sends data to the D/A conversion unit, where sound is reproduced by an audio ampli-

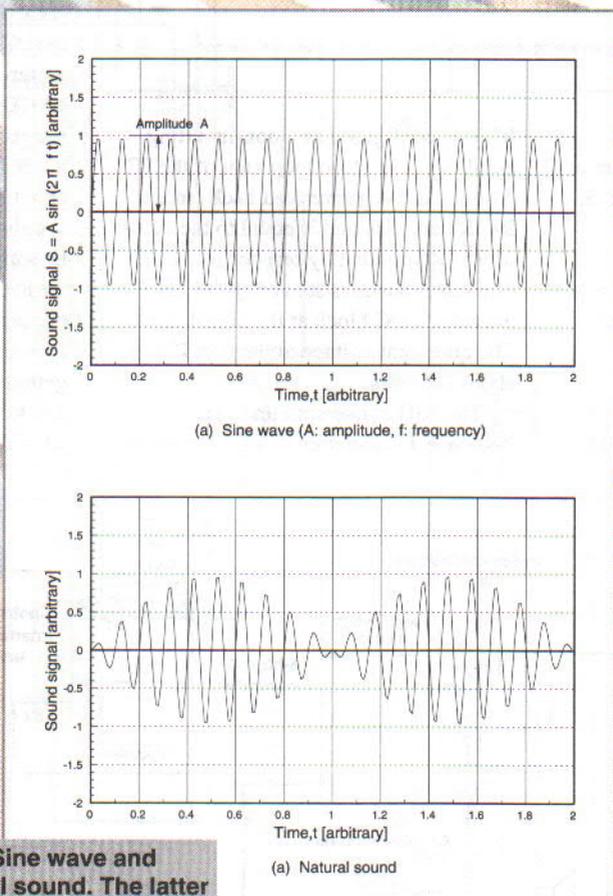


Fig.2 Sine wave and natural sound. The latter is composed of sound waves.

quency). The sampling rate is measured as the number of A/D conversions per second and has a unit of Hz. The quality of the digitized sound increases with the sampling rate. A high sampling rate will result in a digital sample which is truer to the original. However, a high sampling rate also generates massive data.

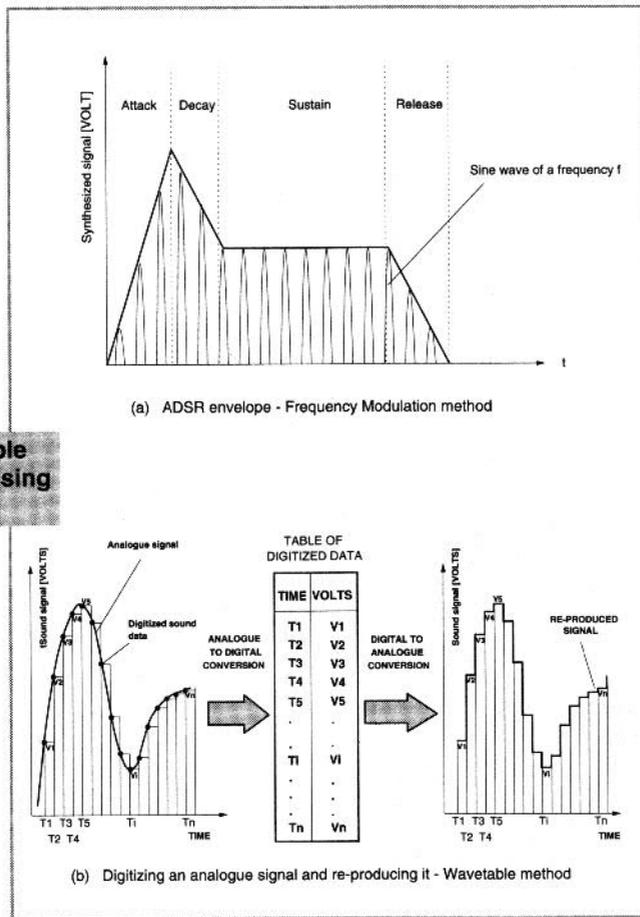


Fig.3 FM and wavetable methods for synthesising natural sounds

fier and then fed to the speaker. The block diagram and the circuit diagram of the device are given in Figures 4 and 5, respectively.

A detailed description of the Centronic port and the way it is controlled has been discussed in detail in the article "Mission Control" in April's issue of the Electronics in Action.

The pre-amplification unit is based on a popular operational amplifier 741

IC. It is configured as a non-inverting amplifier. The close loop gain of the IC is set by the negative feedback circuit R4, R5 and R6, and is equal to the value of R5+R6 divided by resistor R4. The input impedance is set at 27K by R3. C1 provides a DC block at the signal input. The quiescent voltage at pin 6 of IC1 is about 1.2 volts.

The A/D conversion unit uses a ZN448 A/D converter IC (IC2), which is

an 8-bit successive approximation analogue to digital converter with a guaranteed accuracy of 0.5 LSB and minimum conversion time of 9 μ s. A clock generator and a bandgap voltage reference are included on the chip. When the -CONVERT input (pin 4) receives a low-going signal, the A/D converter is triggered to start A/D conversion and the -BUSY output (pin 1) becomes low. The -BUSY output will go high at the end of the conversion indicating that the conversion is completed. The -RD input (pin 2) is the data enable line which is taken low to enable the data on the output lines (pins 18 to 11) which otherwise are in impedance state. Refer to the circuit diagram (Figure 5), the -CONVERT output (pin 4) is connected to one of the control group lines of the Centronic port. To start a conversion, the computer will send a high-to-low-then-high signal to the -CONVERT line, then the computer reads the -BUSY output line and check whether it goes to high. When the high state is detected, the PC reads data from the A/D converter. A clock capacitor (C4) of a value of 100p is connected across pin 3 and the ground (pin 10) which enables the on-board clock generator to operate at about 800 KHz. A negative power supply ranging from -3V to -30V should be supplied to pin 5 (-V) via a tail resistor R8, the value of which has to be chosen according to the voltages. In the present circuit, the negative voltage is generated by a diode pump circuit, RT1, D1, C5 and R10, driven from the -BUSY output. Pin 8 of the IC is the

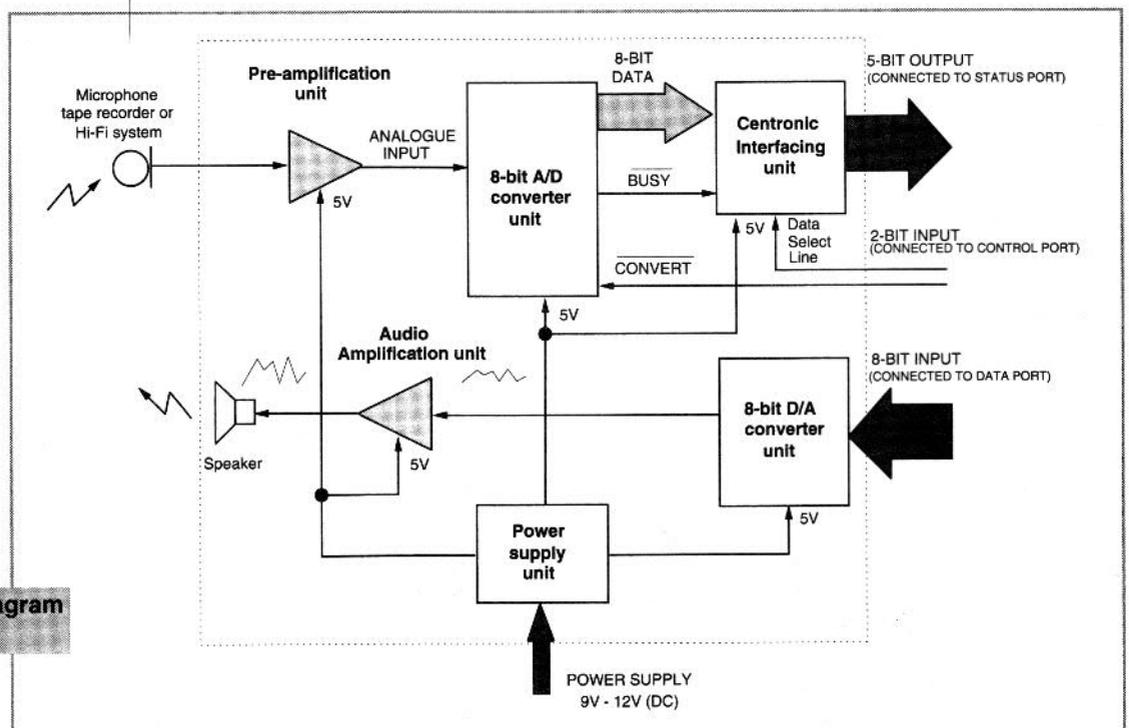


Fig.4 Block diagram of the system

output of the 2.55V on-board reference $V_{ref,out}$. To use this reference, a resistor R7 and a decoupling capacitor C3 are required and $V_{ref,out}$ (pin 8) is connected to $V_{ref,in}$ (pin 7). The sound signal from the pre-amp is fed to V_{in} (pin 6). The digitized value for an input voltage is determined using the following equation:

$$\text{Decimal value} = \frac{\text{Input voltage}}{2.55} \times 255$$

The interfacing unit consists of a 74LS241 IC (IC3). Since the Centronic port only has 5 input lines and one of them has already been used for monitoring the -BUSY output of ZN448, only four lines are left for reading the data. To read an 8-bit byte, 74LS241 IC, the 3 state octal buffer, is used. When pin 1 (the 1st enable input) is taken low, the four left hand side buffers work (ie. the outputs will follow the status of the inputs). When pin 19 (the 2nd enable input) goes high the 4 right hand side buffers will work. If pin 1 and pin 19 are connected together to form the Data Selection Line (DSL), by putting the line low and then high, we can read 4 bits connected to the left hand buffers and the other 4 bits connected to the right hand buffers in turns. Operating in such a manner, the 8-bit data from the A/D converter can be read into the computer.

The digital to analogue unit consists of an 8-bit D/A converter ZN426E (IC4) which consumes a typical supply current of 5 milliamps and has a setting time of typically 9 μ s. It is contained in a standard 14 pin DIL encapsulation. The device has an on-board 2.55V voltage reference with its output at pin 6 ($V_{ref,out}$). To use this reference, an external load resistor R11 (390 ohm) and a decoupling capacitor C6 (4.7 μ F) are used. The voltage reference output is directly connected to the reference voltage input at pin 5 ($V_{ref,in}$). The analogue output voltage is taken from pin 4 (V_{out}) and is in the range 0 to 2.55 volts. The relationship between the output voltage and the value of the input data is shown below:

$$\text{Output Voltage} = \frac{\text{Input data}}{255} \times 2.55[V]$$

This signal is fed into the audio amplification unit which is based on the TBA820 IC (IC5). This IC requires a power supply from 3 volts to 12 volts and is able to provide an output power of up to 2 watts RMS using an 8 ohm

speaker. Pin 2 on IC5 is the inverting input and there is an internal 6K resistor between the input and output of the IC. This allows the voltage gain of the amplified to be adjusted by an external resistor (R15) and the voltage gain is approximately equal to the value of the internal resistor divided by resistor R15. R15 is recommended to be in the range from 22 to 220R, C8 and C9 provides DC blocking. C10 decouples the supply to the pre-amplified stages of IC5, which helps to give the circuit good ripple rejection. C11, C12 and R17 are components to prevent high frequency instability. R16 and C13 are boot-strapping components which give the circuit good efficiency. C15 is the power supply decoupling capacitors and C14 is the output coupling capacitor. The input sound signal from the D/A converter is attenuated by a variable resistor R13.

The power supply unit uses a 7805 5V regulator (IC6) and requires an 8-12V DC power supply. The current required is below 500mA.

Testing

After soldering, a careful inspection must be conducted to check all the joints and connectors to make sure there are **no shorts**. After this, power can be connected to the device. An oscilloscope can be used to check the waveform at pin 3 (CLOCK) of ZN448. It should be a 800KHz square wave. Plug a microphone into the audio signal input socket, the waveform of the sounds picked up by the microphone can be seen at pin 6 of 741 IC. **Unplug ZN426 IC from the socket** and connect pin 6 of 741 IC to pin 4 (V_{out}) of ZN426, if the audio system is OK, sound received by the microphone can be heard from the speaker. At this stage, the device can be connected to the computer. First of all, switch off the computer and the sound machine, then plug the device to the printer port using the printer lead. Next switch on the sound machine and the computer. If the computer does not boot up properly turn off the computer, unplug the device and check the board again. If everything

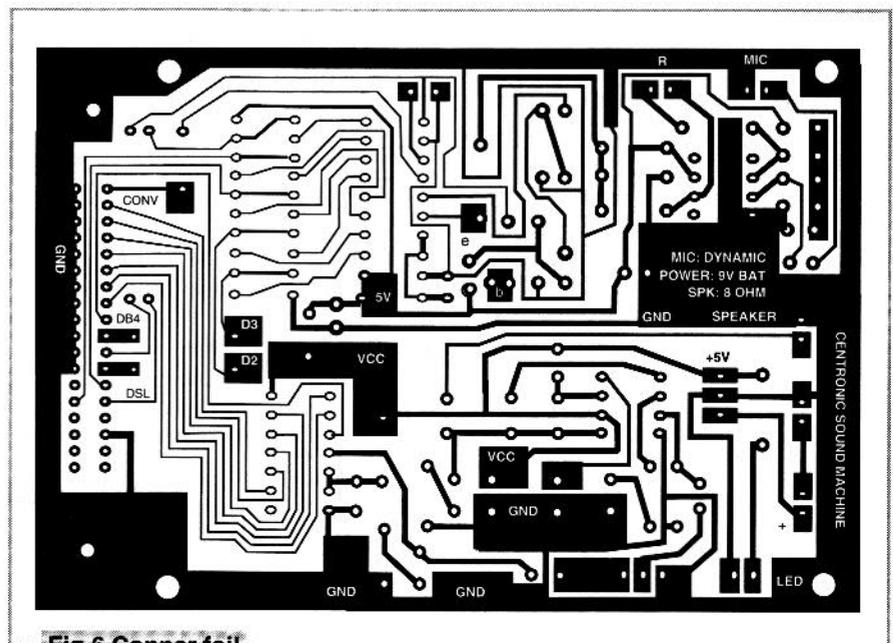


Fig.6 Copper foil

Construction

The Centronic sound machine is constructed on a single-sided print circuit board. The full size copper foil pattern and component layout are shown in Figures 6 and 7. The printed circuit board is available from the EIA PCB service (see page 61).

Components may be mounted in the following order: links, resistors, diodes, DIL IC sockets, capacitors, electrolytic capacitors, PCB connectors, the voltage regulator, Centronic connector and finally the ICs. It is suggested that IC sockets are used for all ICs.


is OK, you can now run programs. Firstly, use a musical software (such as the one introduced later) to check the D/A circuit, then use the control program provided to check the whole circuit. Please follow the instructions given by the software and adjust the volume control and pre-amplification gain to achieve the best result.

Programming

1 Control program

A program for controlling the sound sampling and play back has been written in TURBO PASCAL 6 and is listed below. The flow chart of the program is

Fig.7 Component layout of the centronic sound machine

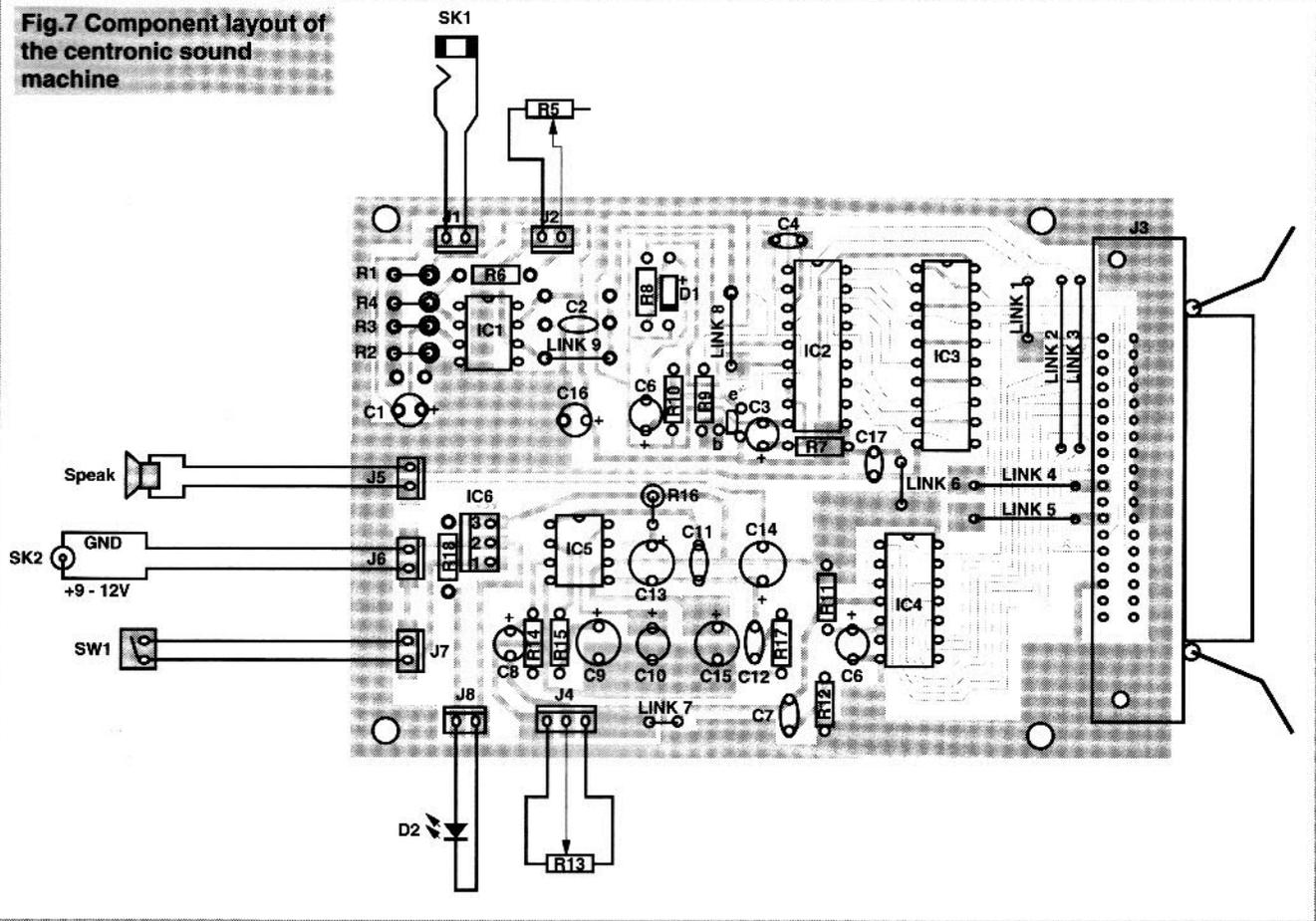

shown in Figure 8. This program is written as a demo to show how to use the device to sample sound and play. The program will sample the sound for about 10 seconds, then play the sample back over and over again. Readers are encouraged to develop their own software to include more functions and achieve various sound effects.

To start the sound sampling, a short high-to-low-then-high pulse is sent to the convert input. After this the computer starts to check the BUSY outline continuously until it becomes high. Then the computer sets the data selection line high and reads the 4-high bits from the converter. Next the data selection line is taken low and the computer reads the 4 low bits. The two readings are rearranged and combined to form a signal 8-bit data. To play back the digitized sound, the computer sends data to the D/A converter and the sound is produced by the D/A converter.

The complete program list is given at the end of this article. Readers can either type the program into the computer or contact the EIA office (details are at the end of this article) for the software on floppy disks. Messages in {} are the explanations and can be omitted when inputting the program into the computer. It is noted that the variable DELAY

NUMBER in the program has to be experimented by the readers to find the best value, since different computers may run at different speeds and the time delay must be changed accordingly.

Public domain software

There are several public domain software packages available from various PD software libraries which support the D/A converter module connected to the printer port. One of them is **ModEdit** which allows users to create sound files (MOD files). This program combines a memory-resident program **ModRes** which is able to play back the music created from within the editor environment. It is easy to compose with ModEdit, which is pull-down menu driven. You just enter the notes one by one into the computer under the edit environment. To hear the music you have entered, you select the correct option from the menu.

Applications

The idea of converting an analogue sound into a digital form, processing it and converting it back to the analogue form is very useful for the purpose of producing various sound effects and studying characteristics of the sound. The following is a brief introduction of what we can do with this device.

1 Simple Effects

The simplest way of experimenting digital sound effects is that you store a long sequence of sampled sound data, such as your speech, in the memory. Then you program the computer to play them back in different ways. If the playback rate is higher than the sampling rate, you will be surprised to find that you sound like a little baby. If it is lower, you sound like an old man. Another sound effect is to send the sampled sound data in the reverse order. What a sound that will be!

2 Delay effect

This effect will delay a sound sample (played in the same order as it was received). The effect of delay can be achieved using the following procedures. The computer samples the sound and stores the digitized data in the memory. In between each sample, the computer sends a previously stored value to the D/A converter, to produce a delay effect.

3 Echo and reverberation

Samples are taken and stored in the memory. Each sample is sent out to the D/A converter. It is immediately followed by sending data which are a fraction of an earlier sample stored in

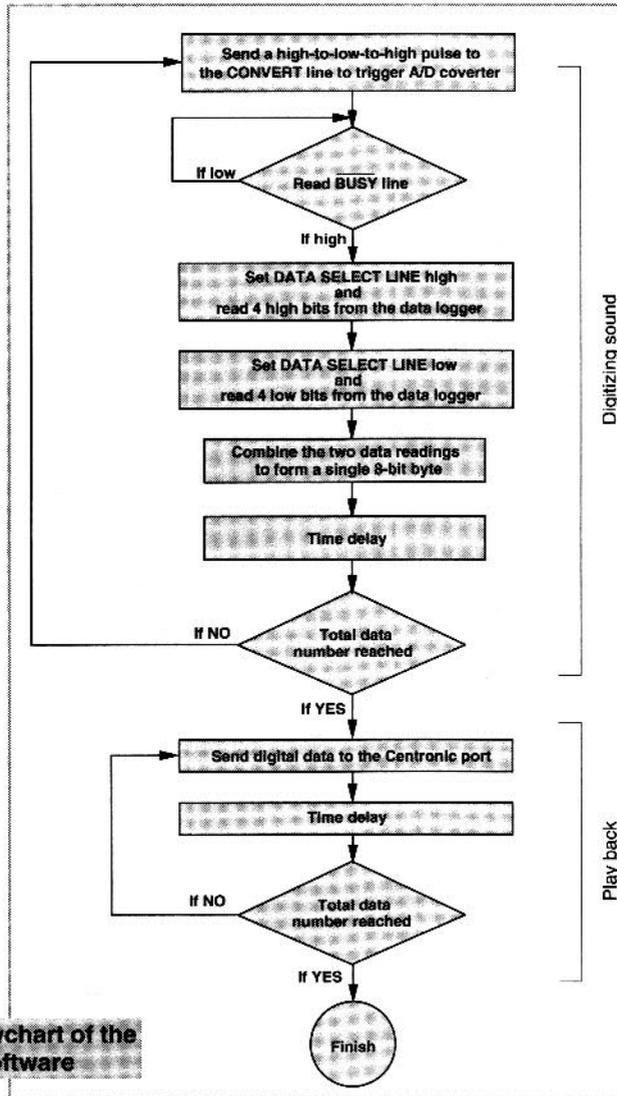


Fig.8 Flowchart of the control software

the memory. We therefore hear the sound plus a faint echo of the sound already heard earlier. Processing in this way gives just a signal echo. The computer can be also programmed to play the echo many times with its amplitude gradually decreased. We thus get a repeated echo, gradually dying away.

Previous data (X)	Current data (Y)	Weighted data $aX + bY$ ($a=b=0.5$)
100	120	110
110	130	120
120	140	130
130	120	125
...

4 Filtering

Filtering is achieved by summing a fraction of the current sample with a fraction of the previous sample. The summed value is sent to the D/A converter. An example is shown above. At each sample, the resulting value sent out becomes the previous sample for the next stage. The fraction weights for the two values, a and b , can be changed as

long as the sum of the two is equal to 1 (e.g. $1/4X + 3/4Y$, or $1/20X + 19/20Y$). Processing in this way, rapid changes in the signal do not have a significant effect on the output signal, since they are averaged out with the previous values. Only low frequency changes are effectively in changing the output value. As a result, the program acts as a low-pass filter.

(0.25W, Metal film 1%)	C1	3.3 μ F/10V electrolytic	
R1,R2	4K7	C2,12	220nF Mylar film
R3	27K	C3,6	4.7 μ F/10V electrolytics
R4	2K2	C4	100pF Ceramic disc
R5	100K potentiometer	C5	1 μ F/10V electrolytic
R6	150K	C7	100nF ceramic disc
R7,11,18	390R	C8	22 μ F/10V electrolytic
R8,R9	47K	C9,13	100 μ F/10V electrolytics
R10	1K0	C10	47 μ F/10V electrolytic
R12,17	1R	C11	220pF ceramic disc
R13	47K potentiometer	C14,15	220 μ F electrolytics
R14	10K	C16	10 μ F electrolytic
R15	100R	C17	100nF ceramic disc
R16	56R		

If the sign of the previous value is reversed before adding a small fraction of it to a large fraction of the current signal, the reversed effect is produced (i.e. $aY - bX$, $a+b=1$ and $a>b$). The resulting signal is composed mainly of the most recent sample and the influence of earlier samples is removed by subtraction. Low-frequency trends die out quickly and high frequency changes are retained. We therefore have a high-pass filter. To combine the low-pass and high pass filter, we obtain a band-pass filter. Different filter combinations can be achieved to create various sound effects.

5 Fourier analysis

The Fourier analysis, also known as Fourier Transformation named after the mathematician J.B. Fourier, is a process which divides a sound into a finite number of different sine waves. This analysis will tell you how a sound is composed and what are the dominant frequencies. Numerical procedures of Fourier transformation are available from various software libraries and textbooks. You can develop a program to record the sounds of birds, musical instruments and voices of your friends, carry out the Fourier Analysis and find out the characteristics of these sounds. This information can be used as a data base to recognise birds, musical instruments and you friends by analysing their sounds.

6 A BIG Program

Combining these ideas and others together, you can write a BIG program that not only plays the preprogrammed music and speech but also composes music itself and understands what you say.

List of the control program

```
program Centronic_Sound_Machine;
{Program written by Pei An for controlling the CENTRONIC SOUND MACHINE}
{Program is written for 12MHz 80286 machine and LPT1 Centronic port}
uses
  crt;
var
  byte1,byte2,truebyte:byte;
  i,j,delaynumber:integer;
  ii:longint;
  soundbyte:array [1..63000] of byte; {Total number of digitized data is 63000}

procedure delaytime;
{Delay a short while}
begin
  for i:=1 to delaynumber do j:=10;
end;

Procedure sample;
{To digitize sounds}
begin
  for ii:=1 to 63000 do begin
    begin
      port[890]:=1;           {CONVERT=0, DSL=1}
      port[890]:=0;         {CONVERT=1, DSL=1}
      {To start A/D converter}
    repeat
      byte1:=port[889];      {To check the BUZY line and read byte1, byte1=xxxxhxx}
    until byte1<128;
      port[890]:=2; {DSL=0}
      byte2:=port[889];      {To read byte2, byte2=xxx1111x}
      byte1:=byte1 and 120;   {byte1 and 00011110 = 000hxxx0}
      byte1:=byte1 shl 1;    {shift 1 bit left, byte1=0000hxxx}
      byte2:=byte2 and 120;   {byte2 and 00011110 = 00011110}
      byte2:=byte2 shr 3;    {shift 3 bits right, byte2=11110000}
      truebyte:=byte1 or byte2; {byte1 or byte2 =11110000 or 0000hxxx = 1111hxxx}
      port[888]:=truebyte;   {To send data to D/A converter}
      soundbyte[ii]:=truebyte;
      delaynumber:=15;      {To set delaynumber=25. This number is for 12MHz 286}
      {For other machines, this number needs to be changed}
      delaytime;           {To delay a short time}
    end;
  end;
end;

Procedure playsound;
{To play back the sound via D/A converter}
begin
  repeat
    delaynumber:=40;       {Delaynumber for play back the sound}
    for ii:=1 to 63000 do begin{Loop to play back the sound}
      delaytime;           {Time delay}
      port[888]:=soundbyte[ii]; {Sent data to D/A converter from port[888]}
    end;
    delay(1000)
  until ii<0
end;

{-----main program-----}
begin
  clrscr;
  writeln('Connect the microphone to the device');
  writeln('Use pre-amplification gain and volume control to obtain the best sound quality');
  writeln('Start sampling. Press RETURN to start sampling');
  writeln('At the end of the sampling, a beep will sound'); readln;
  sample;
  sound(440); delay(500); nosound;
  writeln('Finished sampling. Press RETURN to start replaying');
  writeln('The digitized sound will be played back over and over again');
  readln;
  playsound;
end.
```

Anyone who would like a copy of this program on a 3.5" disk should send a cheque for £3.50 made payable to Dr. P. An to the EIA office along with your name and address

Semiconductors

- IC1 741 (MC1741) Op-Amp IC
- IC2 ZN448E A/D converter IC
- IC3 74LS241 octal buffer IC
- IC4 ZN426E-8 D/A converter IC
- IC5 TBA820M audio amplifier IC
- IC6 7805 (M78M05CV) 5V voltage regulator IC
- TR1 ZTX108C
- D1 1N914 or 1N4148
- D2 Red 5mm LED

Additional items

- PCB See page 61
- IC sockets 8-pin (2 off), 18-pin (1 off) and 20-pin (1 off)
- J1,J2,J5,J6,J7 2 way PCB connector
- J4 3 way PCB connector
- J3 36 pin female Centronix-type connector
- SK1 1/4 in Mono moulded jack socket
- SK2 2.5mm power socket
- SW1 Toggle switch
- Knobs Knobs for R5 and R13 POTs
- LINK1-LINK9 0.6mm copper core wire
- Microphone Unidirectional dynamic dual impedance (600 ohm and 50 Kohm) microphone
- Speaker 8 ohm impedance
- Spacers 6BA spacers (4 off) for PCB mounting
- Screws 6BA screws for mounting the PCB

Parts

VIEWDATA RETURNS Made by Tandata, includes 1200.75 modern, k/bd, RGB and comp o/p, printer port. No PSU. £6 MAG6P7
IBM PC CASE AND PSU Ideal base for building your own PC. Ex equipment but OK. £14.00 each REF: MAG14P2

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8

SOLID STATE RELAYS Will switch 25A mains. Input 3.5-26v DC 57x43x21mm with terminal screws £3.99 REF: MAG4P10

300DPI A4 DTP MONITOR Brand new, TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £24.99. REF: MAG25P1

ULTRAMINI BUG MIC 6mmx3.5mm made by AKG, 5-12v electret condenser. Cost £12 ea, Our's four for £9.99 REF: MAG10P2

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back anodised metal case. £99 each REF: MAG99P1

GX4000 GAMES MACHINES returns so ok for spares or repair £9 each (no games). REF: MAG9P1

C64 COMPUTERS Returns, so ok for spares etc £9 ref: MAG9P2

FUSELAGE LIGHTS 3 foot by 4" panel 1/8" thick with 3 panels that glow green when a voltage is applied. Good for night lights, front panels, signs, disco etc. 50-100v per strip. £25 ref: MAG25P2

ANSWER PHONES Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF: MAG18P1, BT Response 400's £25 ea REF: MAG25P3 Suitable power supply £5 REF: MAG5P12

SWITCHED MODE PSU ex equip, 60w +5v @ 5A, -5v @ 5A, +12v @ 2A, -12v @ 5A 120W220v cased 245x88x55mm IEC input socket £6.99 REF: MAG7P1

PLUG IN PSU 9V 200mA DC £2.99 each REF: MAG3P9

PLUG IN ACORN PSU 19v AC 14w, £2.99 REF: MAG3P10

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref: MAG6P9

ACORN ARCHIMEDES PSU +5v @ 4.4A, on/off sw uncased, selectable mains input, 145x100x45mm £7 REF: MAG7P2

GEIGER COUNTER KIT Low cost professional twin tube, complete with PCB and components. £29 REF: MAG29P1

SINCLAIR C6 13" wheels complete with tube, tyre and cycle style bearing £6 ea REF: MAG6P10

AA NICAD PACK encapsulated pack of 8 AA nicad batteries (tagged) ex equip, 55x32x32mm. £3 a pack. REF: MAG3P11

13.8V 1.9A psu cased with leads. Just £9.99 REF: MAG10P3

360K 5.25 brand new half height floppy drives IBM compatible industry standard. Just £6.99 REF: MAG7P3

PPC MODEM CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

TOWERS INTERNATIONAL TRANSISTOR GUIDE. A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: MAG20P1

SINCLAIR C6 MOTORS We have a few left without gearboxes. These are 12v DC 3,300 rpm 6"x4", 1/4" OP shaft. £25 REF: MAG25

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the above motor but suitable for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG8P1 2 x PP3 req'd.

***MINIATURE RADIO TRANSCENDERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x52x155mm. Complete with cases and earpieces. 2xPP3 req'd. £30.00 pair REF: MAG30.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

LQ3600 PRINTER ASSEMBLIES Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc in fact everything bar the case and electronics, a good stripper! £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

SPEAKER WIRE Brown 2 core 100 foot hank £2 REF: MAG2P1

LED PACK of 100 standard red 5m leds £5 REF: MAG5P4

JUG KETTLE ELEMENT good general purpose heating element (about 2kw) ideal for heating projects. 2 for £3 REF: MAG3

UNIVERSAL PC POWER SUPPLY complete with flyleads, switch, fan etc. Two types available 150w at £15 REF: MAG15P2 (23x23x23mm) and 200w at £20 REF: MAG20P3 (23x23x23mm)

***FM TRANSMITTER** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever why pay £700? or price is £26 REF: MAG26 Transmits to any FM radio.

***FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd. £5 REF: MAG5P5

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units have the looks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just £3 REF: MAG3P1

100 WATT MOSFET PAIR Same specs as 2SK343 and 2SJ413 (8A, 140v, 100w) 1 N channel, 1 P channel, £3 a pair REF: MAG3P2

VELCRO 1 metre length of each side 20mm wide (quick way of fixing for temporary jobs etc) £2 REF: MAG2P3

MAGNETIC AGITATORS Consisting of a cased mains motor with lead. The motor has two magnets fixed to a rotor that spin round inside. There are also 2 plastic covered magnets supplied. Made for remotely stringing liquids! you may have a use? £3 each REF: MAG3P3

BULL'S BULLETIN BOARD

100MHZ DUAL TRACE OSCILLOSCOPES JUST £259 RING FOR DETAILS

MASSIVE WAREHOUSE CLEARANCE FANTASTIC £20.00 REDUCTION REFURBISHED PC BASE UNITS COMPLETE WITH KEYBOARD

FROM ONLY £29.00 AMSTRAD 1512 BASE UNITS GUARANTEED PERFECT WORKING ORDER.

A LOW COST INTRODUCTION TO THE HOME COMPUTER MARKET.

AMSTRAD 1512SD

1512 BASE UNIT, 5.25" FLOPPY DRIVE AND KEYBOARD. ALL YOU NEED IS A MONITOR AND POWER SUPPLY. WAS £49.00 NOW ONLY £29.00 REF: MAG29

AMSTRAD 1512DD

1512 BASE UNIT AND KEYBOARD AND TWO 5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR AND POWER SUPPLY. WAS £59.00 NOW ONLY £39.00 REF: MAG39

SOLAR POWER PANELS

3FT X 1FT 10WATT GLASS PANELS 14.5v/700mA NOW AVAILABLE BY MAIL ORDER £33.95

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE APPLICATIONS, SOME OF WHICH MAY BE CAR BATTERY CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANYWHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

FREE SOFTWARE!

Brand new, UNUSED top quality Famous brand licensed software discs. Available in 5.25" D5DD or 5.25" HD only. You buy the disk and it comes with free BRAND NEW UNUSED SOFTWARE. We are actually selling you the floppy disc for your own 'MEGA CHEAP' storage facilities, if you happen to get software that you want/need/like as well..... you get a 'MEGA BARGAIN' too!

D5DD PKT10 £2.99 REF: MAG37 PKT100 £16.00 REF: MAG16

*****WE BUY SURPLUS STOCK*****

TURN YOUR SURPLUS STOCK INTO CASH. IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE.

1994 CATALOGUE.

PLEASE SEND 45P, A4 SIZED SAE FOR YOUR FREE COPY. MINIMUM GOODS ORDER £5.00. TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES, & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILLINGLY GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX BN3 5QT

MAIL ORDER TERMS: CASH PO OR CHEQUE WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY TELEPHONE ORDERS WELCOME

TEL: 0273 203500 FAX: 0273 323077

TOP QUALITY SPEAKERS Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality general purpose speaker. £2 each REF: MAG2P4 or 4 for £6 REF: MAG6P2

TWEETERS 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

AT KEYBOARDS Made by Apricot these quality keyboards need just a small modification to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: MAG6P3

XT KEYBOARDS Mixed types, some returns, some good, some foreign etc but all good for spares! Price is £2 each REF: MAG2P6 or 4 for £6 REF: MAG6P4

PC CASES Again mixed types so you take a chance next one off the pile £12 REF: MAG12 or two the same for £20 REF: MAG20P4

COMMODORE MICRODRIVE SYSTEM mini storage device for C64's 4 times faster than disc drives, 10 times faster than tapes. Complete unit just £12 REF: MAG12P1

SCHOOL STRIPPERS We have quite a few of the above units which are 'returns' as they are quite comprehensive units they could be used for other projects etc. Let us know how many you need at just 50p a unit (minimum 10).

HEADPHONES 16P These are ex Virgin Atlantic. You can have 8 pairs for £2 REF: MAG2P8

PROXIMITY SENSORS These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with fly leads. Pack of 5 £3 REF: MAG3P5 or 20 for £8 REF: MAG8P4

SNOOPERS EAR? Original made to clip over the earpiece of telephone to amplify the sound-it also works quite well on the cable running along the wall! Price is £5 REF: MAG5P7

DOS PACKS Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: MAG5P8 Worth it just for the very comprehensive manual! 5.25" only.

DOS PACK Microsoft version 5 Original software but no manuals hence only £3 REF: MAG3P6 5.25" only.

FOREIGN DOS 3.3 German, French, Italian etc £2 a pack with manual. 5.25" only. REF: MAG2P9

CTM644 COLOUR MONITOR. Made to work with the CPC464 home computer. Standard RGB input so will work with other machines. Refurbished £59.00 REF: MAG59

PIR DETECTOR Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) £8 REF: MAG8P5

WINDUP SOLAR POWERED RADIO AM/FM radio complete with hand charger and solar panel! £14 REF: MAG14P1

COMMODORE 64 TAPE DRIVES Customer returns at £4 REF: MAG4P9 Fully tested and working units are £12 REF: MAG12P5

COMPUTER TERMINALS complete with screen, keyboard and RS232 input/output. Ex equipment. Price is £27 REF: MAG27

MAINS CABLES These are 2 core standard black 2 metre mains cables fitted with a 13A plug on one end, cable the other. Ideal for projects, low cost manufacturing etc. Pack of 10 for £3 REF: MAG3P8 Pack of 100 £20 REF: MAG20P5

SURFACE MOUNT STRIPPER Originally made as some form of high frequency amplifier (main chip is a TSA5511T 1.3GHz synthesiser) but good stripper value, an excellent way to play with surface mount components £1.00 REF: MAG1P1

MICROWAVE TIMER Electronic timer with relay output suitable to make enlarger timer etc £4 REF: MAG4P4

MOBILE CAR PHONE £5.99 Well almost! complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6

ALARM BEACONS Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: MAG5P11

FIRE ALARM CONTROL PANEL High quality metal cased alarm panel 350x165x80mm. With key. Comes with electronics but no information. sale price 7.99 REF: MAG8P6

SUPER SIZE HEATSINK Superb quality aluminium heatsink. 365 x 183 x 61mm, 15 fins enable high heat dissipation. No holes! sale price £5.99 REF: MAG6P11

REMOTE CONTROL PCB These are receiver boards for garage door opening systems. You may have another use? £4 ea REF: MAG4P5

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF: MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref: MAG5P13 ideal for experiments! 30m for £12.99 ref: MAG13P1

LOPTX Line output transformers believed to be for hi res colour monitors but useful for getting high voltages from low ones! £2 each REF: MAG2P12 bumper pack of 10 for £12 REF: MAG12P3.

SHOP OPEN 9-5.30 SIX DAYS A WEEK

PORTABLE RADIATION DETECTOR

£49.99

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook.

REF: MAG50

EUROPEAN COMPUTER MARKETING (U.K.)

ROWAN HOUSE, WOODLANDS ROAD, RILLINGTON, MALTON, YO17 8LD, N YORKSHIRE

SALES AND INFORMATION HOTLINE

All prices are exclusive of V.A.T @ 17.5% and UK mainland delivery. Export orders are welcome. Please call for carriage to country of destination. Payment by cheque, bankers draft, cash or postal orders.

Subject to availability despatch is normally effected within 2 days from receipt of cleared payment. Please allow 7 working days for cheque clearance. All orders will be fulfilled within 28 days unless otherwise notified.

0944 - 758989

FAX: 0944 - 758989

E & O.E All prices subject to change without notice. Please call before ordering. Goods are not supplied on a trial basis.

TOP QUALITY DEALS!!

		120MB HDD	170MD HDD	210MB HDD
386 SX-40MHZ	MONO VGA	:£620.00	:£635.00	:£650.00
	COLOUR SVGA	:£696.00	:£711.00	:£726.00
386DX-40MHZ	MONO VGA	:£635.00	:£650.00	:£665.00
	COLOUR SVGA	:£717.00	:£726.00	:£745.00
486SX-25MHZ	MONO VGA	:£695.00	:£710.00	:£725.00
	COLOUR SVGA	:£775.00	:£786.00	:£805.00
486DX-33MHZ	MONO VGA	:£832.00	:£847.00	:£862.00
	COLOUR SVGA	:£912.00	:£923.00	:£942.00
486DX-50MHZ	MONO VGA	:£934.00	:£949.00	:£964.00
	COLOUR SVGA	:£1014.00	:£1024.00	:£1044.00
486DLC-40MHZ	MONO VGA	:£734.00	:£749.99	:£764.00
	COLOUR SVGA	:£814.00	:£824.00	:£844.00



STANDARD FEATURES INCLUDE: MINI TOWER OR DESK TOP CASE WITH DIGITAL SPEED DISPLAY, 3.5" FLOPPY DRIVE (1.44MB), 5.25" (1.2MB) FLOPPY DISK DRIVE, 2 SERIAL/21 PARALLEL/GAMES PORT, 102 KEY UK KEYBOARD, MICROSOFT COMP MOUSE, * 3 YEAR WARRANTY, MS DOS 5, MS WINDOWS 3.1. ALL SYSTEMS ARE SOAK TESTED FOR 48 HRS.

MOTHERBOARDS

ECM100 386SX-40MHZ	£62.00
ECM101 386DX40MHZ128K CACHE	£92.00
ECM102 486SX25MHZ VLB 256K CACHE	£147.00
ECM103 486SX33MHZ VLB 256K CACHE	£160.00
ECM104 486DX33MHZ VLB 256K CACHE	£278.00
ECM105 486DX40MHZ VLB 256K CACHE	£290.00
ECM106 486DX50MHZ VLB 256K CACHE	£379.00
ECM107 486DLC40MHZ VLB & CO-PRO	£162.00

HARD DISK DRIVES

ECM108 120MB IDE CONNER	£153.00
ECM109 170MB IDE CONNER	£169.00
ECM110 210MB IDE CONNER	£173.00
ECM111 250MB IDE CONNER	£178.00
ECM112 330MB IDE CONNER	£210.00
ECM113 1GB FAST SCSI-2 FUJITSU	£640.00

MEMORY

ECM114 256K SIMMS MODULE	£CALL
ECM115 1MB SIMMS MODULE 70NS	£CALL
ECM116 4MB SIMMS MODULE 80NS	£CALL

LATEST DESIGN CASES

ECM117 DELUXE DESKTOP	£45.00
ECM118 DELUXE SLIMLINE CASE	£52.00
ECM119 DELUXE MINITOWER	£48.00
ECM120 DELUXE FULLTOWER	£80.00
ECM121 DELUXE MULTIMEDIA	£87.00

KEYBOARDS

ECM122 102 KEY UK KEYBOARD	£14.00
ECM123 HIGH QUALITY (CORPORATE) KEYBOARD	£23.00
ECM124 CHERRY KEYBOARD	£26.00

ADD-ON CARDS

ECM131 I/O CARD 2S/1P/1G	£11.00
ECM132 IDE CARD 2HD/2FD WITH CABLES	£11.00
ECM133 IDE & I/O CARD 2HD/2FD/2S/1P/1G WITH CABLES	£14.00
ECM134 IDE CACHE CONTROLLER 2HD/2FD	£62.00
ECM135 ADEPTIC 1542C SCSI HIGH PERFORMANCE KIT	£192.00

COMMS PRODUCTS

ECM136 FAX/MODEM 9600/4800 WITH BITFAX FOR DOS	£49.00
ECM137 FAX/MODEM 9600/2400 WITH BITFAX FOR DOS/WINDOWS	£57.00
ECM138 POCKET FAX/MODEM 9600/2400	£57.00

MONITORS

ECM154 MONO VGA 14" MONITOR	£85.00
ECM155 COLOUR SVGA 14" MONITOR	£169.00
ECM156 COLOUR SVGA 14" NON INTERLACED	£182.00
ECM157 COLOUR SVGA 15" NON INTERLACED	£CALL
ECM158 COLOUR SVGA 17" NON INTERLACED	£560.00

SOFTWARE

ECM163 MS DOS V5.0	£25.00
ECM164 MS DOS V6.0	£37.00
ECM165 MS WINDOWS V3.1	£33.00
ECM175 MS DOS V3.3 (FOREIGN) GERMAN 5.25" ONLY	£22.00
ECM176 MS DOS V3.3 (FOREIGN) FRENCH 5.25" ONLY	£22.00
ECM177 MS DOS V3.3 (FOREIGN) ITALIAN 5.25" ONLY	£22.00

CD TITLES

ECM150 WORLD ATLAS CD	£25.00
ECM151 GUINNESS DISC OF RECORDS 1993 CD	£25.00
ECM152 WORLD VIEW WITH VIDEO FOR WINDOWS	£25.00
ECM153 KODAK PHOTO CD ACCESS SOFTWARE	£20.00
ECM166 AA HOTELS & RESTAURANTS	£20.00
ECM167 SHAREWARE OVERLOAD	£15.00
ECM168 PUBLISHERS DREAMS	£35.00
ECM169 WIN PLATINUM	£25.00
ECM170 WORLD FACT BOOK '93	£25.00
ECM171 WINDOWS MASTER	£22.00
ECM172 BUSINESS MASTER 2ND EDITION	£22.00
ECM173 VIDEO MOVIE GUIDE '93	£35.00
ECM174 TOOLWORKS REFERENCE LIBRARY	£25.00

DISPLAY CARDS

ECM139 MONO CARD WITH PRINTER PORT	£16.00
ECM140 VGA CARD 256K	£36.00
ECM141 16 BIT SVGA CARD 512K	£39.00
ECM142 TRIDENT 8900CL 16 BIT SVGA 1MB	£52.00
ECM143 TSENG LAB ET4000 1MB 16.7MB COLOURS	£64.00

PRINTERS

ECM125 HP DESKJET 510	£239.00
ECM126 HP DESKJET 550	£419.00
ECM127 HP LASERJET 4L	£492.00
ECM128 PANASONIC KXP1123 24 PIN DOT MATRIX	£139.00
ECM129 CANON BJ10SX BUBBLE JET	£184.00
ECM130 PARALLEL PRINTER CABLE	£2.90

MULTI MEDIA

ECM144 MITSUMI CD ROM & INTERFACE CARD	£125.00
ECM145 PANASONIC S62 DUAL SPEED CD ROM COMPLETE KIT	£159.00
ECM146 SOUNDBLASTER V2 COMPATIBLE WITH SPEAKERS	£45.00
ECM147 SOUNDBLASTER PRO WITH CD INTERFACE	£82.00
ECM148 AMPLIFIED POWER SPEAKERS	£24.00
ECM149 VIDEO CAPTURE CARD AND VIDEO FOR WINDOWS	£215.00
ECM178 MICROSOFT COMPATIBLE MOUSE	£14.00
ECM179 ANALOG JOYSTICK (REQUIRES GAMES PORT)	£22.00

FLOPPY DRIVES

ECM160 3.5" 1.44MB FLOPPY DISK DRIVE	£32.00
ECM161 5.25" 1.2MB FLOPPY DISK DRIVE	£40.00
ECM162 FLOPPY DRIVE MOUNTING KIT	£7.00

TELECOM PRODUCTS

UNFORTUNATELY WE ARE UNABLE TO LIST OUR FULL LINE OF TELECOM PRODUCTS AS IT IS SO LARGE. BELOW IS A LISTING OF CATEGORIES. FULL LISTS ARE AVAILABLE BY TELEPHONE/FAX.

STANDARD AND FEATURE PHONES
SPECIAL APPLICATION PHONES
OPERATOR HEADSETS
SPECIAL ENVIRONMENT TELEPHONES
NOVELTY & CLOCK RADIO TELEPHONES
DECORATIVE TELEPHONES
ANSWERING MACHINES
ANSWERING MACHINE TAPES & ACCESSORIES
CORDLESS TELEPHONES
CORDLESS ACCESSORIES BATTERIES & AERIALS
CT2 DIGITAL CORDLESS TELEPHONES
FULL RANGE OF CELLULAR TELEPHONES
RADIO PAGING SYSTEMS (WIDE AREA)
RADIO PAGING SYSTEMS (LOCAL AREA)
PAYPHONES
PAYPHONE ACCESSORIES
FACSIMILE MACHINES
FAX SWITCHES & MODEMS
BUSINESS TELEPHONE SYSTEMS
CALL BARRING DEVICES
AUDIO & VISUAL INDICATORS
VOICE MAIL SYSTEMS
FAX-ON-DEMAND SYSTEMS
FULL LINE OF OFFICE PRODUCTS (COPIERS ETC)
SECURITY PRODUCTS

COMING SOON
VIDEOCONFERENCING SYSTEM
CALL METERING DEVICE (TELEMETA)
CALLER IDENTIFICATION (SUBJECT TO APPROVAL)

EUROPEAN COMPUTER MARKETING OFFERS
YOUR ULTIMATE LINE OF SUPPLY!!!
THE ULTIMATE SERVICE!!!
VERY COMPETITIVE PRICES!!!
AND THE HIGHEST QUALITY PRODUCTS !!!

SALES & INFORMATION HOTLINE 24 Hrs
ALSO PRODUCT DETAILS & LATEST PRICES
AVAILABLE BY FAX-ON-DEMAND CALL FROM
A FAX MACHINE AND PRESS START WHEN
REQUESTED 0944 - 758989

TRADE & CORPORATE ENQUIRIES WELCOME

Signal to NOISE

A Selection of your views and comments raided from the post bag


Evolving Evolution

Your new magazine continues to find interesting topics to beguile the reader. Long may it continue at this standard.

I regret that there is a bit of a snarl up in the correlation between the text/illustrations of the 'Evolution of Audio Amps' Part 3, in relation to Figure 3. The correct drawing is shown here. I don't think anyone would wish to build this circuit, but please print the correction to keep the record straight, with my apologies.

I apologise to your readers for the errors which occurred in this figure of the April 1994 article, in which TR2 and TR3 had unfortunately got their numbering crossed, and C3 had become interposed between TR1 collector and TR2 base, instead of being connected between TR2 base and collector.

John Linsley-Hood
Taunton
Somerset

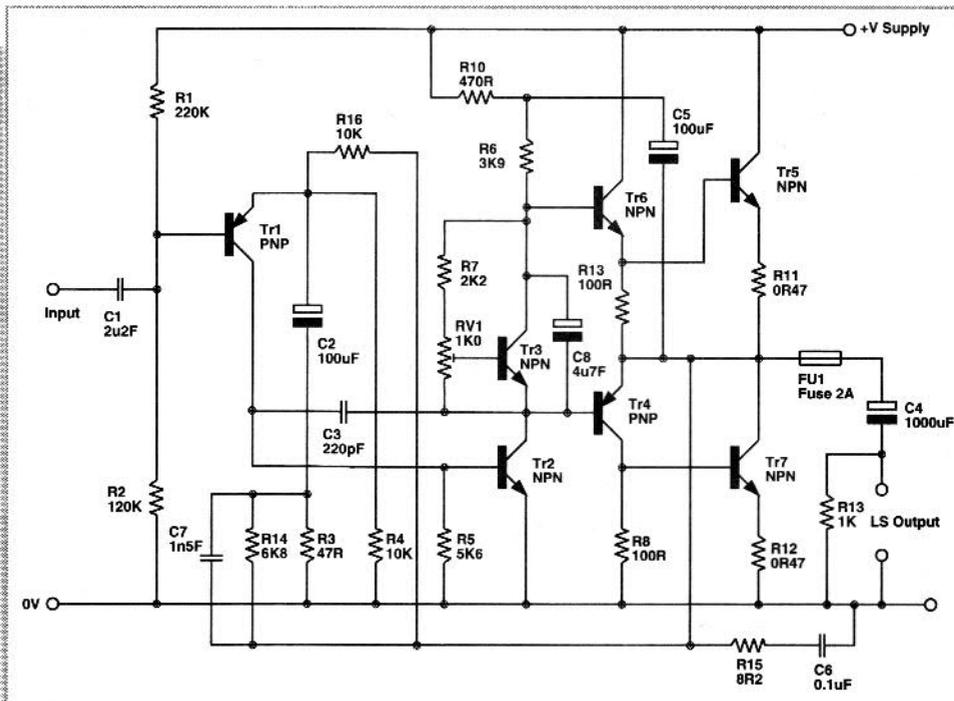

at the face. However when immersed in a liquid of reasonable refractive index the light is no longer reflected. This could be detected by a LED/photodetector combination at the end of the rod. The length of the rod determines the detection level.

However my main reason for writing was to comment on the general standard of the construction projects in EIA. After a good start, with some innovative and well thought out designs, the level seems to be falling back to that of other hobby magazines.

The A-B guitar switching box that appeared in the April issue is a good example of what I mean. The author does not fully understand the operation of the 4066 analogue switch. After raising the DC level of the signal to half the supply by means of IC1 he then removes the DC component before passing the signal through the 4066. The signal is therefore referenced to the 4066 negative supply and will be prone to unnecessary distortion. In addition only one 4066 is in fact required. SW1 could quite easily switch the LEDs directly and the use of the other half of two sections of IC2 in parallel makes no significant improvement in performance.

Similar middle-headed design was evident in the circuit for an egg incubator which appeared in the February issue. Temperature control is a simple matter that nowadays can be achieved with one IC as even the author admits! If he insists on safety then why not isolate or insulate the probe instead of the whole circuit? Even more thoughtless is to generate a relatively stable reference voltage using IC5c to feed the setpoint control and then to have a separate reference, D1, to produce the zero offset current.

Perhaps I could make three suggestions that I believe would maintain or even improve on the early high standard of EIA.

Firstly as many readers are primarily interested in the design aspect of the circuits, why not extend this part of project articles at the expense of construction details. These are usually the same anyway and could even be repeated every month in a separate section at the back of the magazine with only special points included in the project description. The article could then concentrate in far more detail on why the author had chosen a particular design and, more importantly, what other options he had considered. Generating and

Ideas, Criticisms and back to Ideas

In the Ideas Forum of the April issue of Electronics in Action you asked for a simple solution to the problem of detecting the level of a non-ionic fluid. There are in fact a great many simple solutions. Off the top of my head I could suggest the following all of which have been used commercially:

- 1 A float containing a magnet that operates a reed switch sealed in a tube.
- 2 Detection of the reduction in temperature of a self-heated probe such as a thermistor when it is immersed in the liquid. National Semiconductor produced (and may still do) an IC, the LM903, which utilised this principle.
- 3 Use of a transparent rod with the bottom face angled so that light is normally totally internally reflected

evaluating ideas is fundamental to the innovative process, something EIA is supposed to be nurturing.

Alternatively why not actively encourage criticism of published designs and seek suggestions for improvements. Having a practical starting point might tempt readers to think and experiment more than maybe Ideas Forum is doing. I noticed you did take a small step in this direction in publishing a letter commenting on Mike Meechan's mixer project.

The final point concerns information about the range of ICs now available. Much inelegant design is due to either being unaware of an IC which will perform a function simply and effectively or of then using it incorrectly due to lack of understanding or inability to read a data sheet. Although catalogues do contain information on a range of ICs, this is not comprehensive or up-to-date. I remember a regular column in the old Practical Electronics called Semiconductor Update which each month featured details and applications for a handful of new ICs which could be relevant to the hobbyist. It used to be one of the first pages I turned to! How about something similar for EIA? I'm

certain it would be of more value to innovative readers than rehashing tired old circuits. I'll even volunteer to write it for you!

**Andrew Chadwick
Hull**

Thank you for your comments and valued criticism. I have to say that one of the main objectives of the magazine is to get people to look at the circuits we publish and to update or improve them if needs be or to use them for a different application. We have to remember these are all working prototypes and not well established designs. Yes I agree, part of the emphasis should be on why the author chose an idea or design and is in our brief to potential authors. Regarding the latest news on ICs, we already have a couple of articles prepared. However, I will take you up on your suggested designs, please forward them for possible publication.

Finally - No doubt Daniel Coggins and David Silvester, the authors of the projects you mention, will provide suitable return comments. - Ed.

Stereo Image

I find the projects by Mike Meechan most interesting as I am in the music business myself and into electronics as a hobby.

I have a problem which may or may not be able to help me with. I came across an article dated back about 1980 on a Stereo imager which used a VCA chip namely a 1537A. At the time it was available from a company called Aphex audio systems in London. However they no longer exist. Can you give me any idea of where I might find such a chip?

**M Coutts
Aberdeen**

PS An idea for a project - A stereo imager/panner for studio use.

Any suggestions from any music people out there? - Ed.

If you have any views, comments, criticism or ideas please address them to:
Signal to Noise
The Editor
Electronics in Action
PO Box 600
Berkhamsted
Herts. HP4 1NL

PHOTOCOPY SERVICE

As our January issue was so popular and is now sold out, we have introduced a new service to enable you to obtain any articles that you may be missing. Each article copy costs £2.00 (including P&P).

PHOTOCOPIES

Please Photocopy me the following articles:

Month	Title of article	
.....	@ £2.00
.....	@ £2.00
.....	@ £2.00
.....	@ £2.00

Please print your name and address in **BLOCK CAPITALS**


Name

Address

..... Postcode

I enclose a cheque/postal order (payable to Electronics in Action) for £

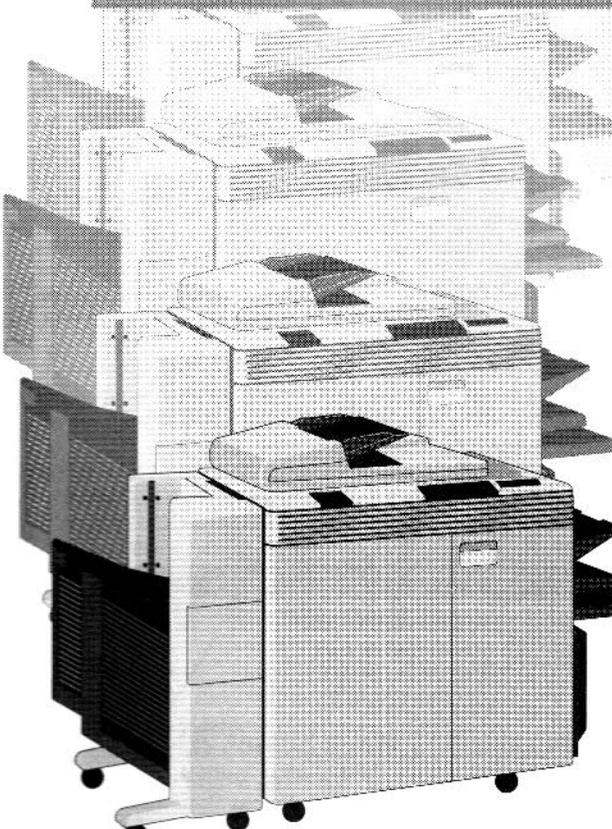Please send this form to: **Electronics in Action, PO Box 600,
Berkhamsted, Herts. HP4 1NL**



EXPRESS COMPONENTS

MAINS IONIZER KIT. Very useful kit that increases the flow of negative ions, helps clear cigarette smoke, dust, pollen etc. Helps reduce stress and respiratory problems. £15. kit, £20 built.

COMBINATION LOCK. Electronic 9 key combination lock suitable for alarms, cars, houses etc, easily programmable. Includes mains 2A relay o/p. 9v operation. £10 kit, £14 built.

VARIABLE POWER SUPPLY. Stabilized, short circuit protected. Gives 3-30v DC at 2.5A, ideal for workshop or laboratory. £14 kit, £18 built. 24VAC required.

LEAD ACID CHARGER. Two automatic charging rates (fast and slow), visual indication of battery state. Ideal for alarm systems, emergency lighting, battery projects etc. £12 kit, £16 built.

PHONE LINE RECORDER. Device that connects to the 'phone line and activates a cassette recorder when the handset is lifted. Ideal for recording 'phone conversations etc! £8 kit, £12 built.

ROBOT VOICE. Turns your voice into a robot voice! answer the phone with a different voice! £9 kit, £13 built.

PHONE BUG DETECTOR. This device will warn you if somebody is eavesdropping on your 'phone line. £6 kit £9 built.

PHONE BUG. Small bug powered by the telephone line. Only transmits when the phone is used. Popular surveillance product. £8 kit, £12 built.

STROBE LIGHT. Bright strobe light with an adjustable frequency of 1-60hz. (a lot faster than conventional strobes!) £16 kit, £20 built.

4W FM TRANSMITTER. 3 RF stages, audio preamp. 12-18vDC. Medium powered bug £20 kit, £28 built.

3 CHANNEL LIGHT CHASER. 3x 800w output, speed and direction controls, can be used with 12 led's (supplied) or TRIACS for mains lights (also supplied). 9-15v DC. £17 kit, £23 built.

25W FM TRANSMITTER. 4 stage, a preamp will be required. (Our preamp below is suitable) £79 built. (no kits).

SOUND EFFECTS GENERATOR. Produces any thing from bird chips to sirens! add sounds to all sorts of things £9 kit £13 built.

FM/AM SCANNER. Well not quite, you have to turn the knob yourself but you will hear things on this radio (even TV) that you would not hear on an ordinary radio! A receiver that covers 50-160MHZ both AM and FM. Built in 5w amplifier. £15 kit, £20 built.

CAR ALARM SYSTEM. Works on vibration and/or voltage drop from door etc being opened. Entry and exit delays plus adjustable alarm duration. Low cost protection! £12 kit, £16 built.

15W FM TRANSMITTER. 4 stage, high power bug. You will need a preamp for this (see our preamp below which is ok) £69 built. (no kits).

1W FM TRANSMITTER. 2 stage including preamp and mic. Good general purpose bug. 8-30VDC. £12 kit, £16 built.

50 I/C's for £1.50
Nice mix of chips at a bargain price!

CERAMIC CAPACITOR PACK
Good mixed pack of 100 capacitors for just £1.00

ELECTROLYTIC PACK 1
100 small mixed electrolytic capacitors just £1.00

ELECTROLYTIC PACK 2
50 larger electrolytic mixed capacitors

RESISTOR PACK NO 1
250 low wattage resistors, ideal for most projects etc. Just £1.00

RESISTOR PACK NO 2
Hi wattage pack, good selection of mixed wattages and values 50 in all, bargain price just £1.00

PRESET PACK
Nice selection of 25 mixed preset pots for just another £1!

RELAY PACK NO 1
6 mixed relays for £1, that's just 17p each.

CONNECTOR PACK
10 different connectors, again for £1

FUSE PACK NO 1
40 mixed 20mm fuses, ideal for repairs etc, or just to stock up the spares box! Just £1.00

FUSE PACK NO 2
30 mixed 1.25" fuses again ideal for spares etc. Just £1.00

WIRE PACK
25 Metres of insulated wire for just £1.00, good for projects etc.

SLEEVING PACK
100 assorted pieces of sleeving for connectors etc. Yours for just £1.00

DIODE PACK
100 assorted diodes for just £1.00

LED PACK
20 light emitting diodes for £1.00

TRANSISTOR PACK
50 mixed transistors, another bargain at £1.00

BUZZER PACK
10 things that make a noise for just £1.00!

POT PACK
10 pots for £1, (5 different types) a snip at £1.00

DISPLAYS
10 seven segment displays for £1.00

ORDER 10 PACKS OR MORE AND CHOOSE ONE FREE PACK!!

FREE COMPONENT CATALOGUE WITH EVERY ORDER!!

BULK PACKS

99p
Post

KITS 'N MODULES

PREAMP MIXER. 3 channel input, independent level and tone controls. Ideal for use with the hi power FM transmitters. £15 kit, £19 built.

TREMBLER ALARM. Designed for bikes etc, adjustable sensitivity, preset alarm time, auto reset. Could be adapted for all sorts of "borrowable" things £12 kit, £16 built.

ULTRASONIC RADAR. A project that can be used as a movement detector in an enclosed space. Range about 10 metres, 12vDC. Good basis for car, shed, caravan alarm etc. £14 kit, £19 built.

PHONE CALL RELAY. Very useful kit that incorporates a relay that operates when the phone rings. Can be used to operate more bells, signalling lights etc. Good for noisy environments or if you have your headphones on! £10 kit, £14 built.

PORTABLE ALARM SYSTEM. Small 9v alarm system based on a mercury switch. The alarm continues to sound until disabled by the owner. Buzzer included. £11 kit £15 built.

800W MUSIC TO LIGHT EFFECT. Add rhythm to your music with this simple sound to light kit. £8 kit, £12 built.

MOSQUITO REPELLER. Modern way to keep the midges away! Runs for

about a month on one 1.5v battery. Frequency is set to drive away mosquitos etc. £7 kit, £11 built.

3 CHANNEL SOUND TO LIGHT. Can be used anywhere as no connection is made to hi fi. Separate sensitivity controls for each channel, 1,200W power handling. Microphone included. £14 kit, £19 built.

MINI METAL DETECTOR. Detects pipes, wires etc up to 20cm deep. Useful before you drill those holes! £8 kit, £12 built.

0-5 MINUTE TIMER. Simple time switch adjustable from 0-5 mins, will switch 2A mains load. 12v op. Ideal for laboratory, photographic projects etc. £7 kit, £11 built.

7 WATT HI FI AMPLIFIER. Useful, powerful amplifier 20hz-15hz, 12-18vdc. Good for intercoms, audio systems, car etc. £7 kit £11 built.

INCAR SOUND TO LIGHT. Put some atmosphere in your car with this kit. Each channel has 6 led's that create a beautiful lighting effect! £10 kit, £14 built.

VOX SWITCH. This is a sound activated switch, ideal for use on transmitters, CB's, tape recorders etc. Adjustable sensitivity, built in delay. Mic input. £7 kit, £11 built.

LIQUID LEVEL DETECTOR. Useful item, can be used to detect fluid levels in watertanks, baths, ponds, fish tanks etc. Could also be used as rain alarm with an easily constructed sensor. £5 kit, £9 built.

FM TRANSMITTER. Mini FM transmitter 2 transistor, comes with FET miniature mic and is tuneable from 63 to 130MHZ. £7 kit, £11 built.

FUNCTION GENERATOR. Generates sinusoidal, saw tooth and square waveforms from 20hz up to 20khz. Separate level controls for each waveform. 24vac. £15 kit, £20 built.

5 WATT SIREN. Powerful siren kit with an impressive 5 watts output. Ideal for alarms etc. £6 kit £10 built.

TELEPHONE AMPLIFIER. Very sensitive amplifier which using a 'phone pickup coil (supplied) will let you fol-

low a telephone conversation without holding the handset to your ear! £11 kit £15 built.

SWITCH PACK
10 switches for just £1.00

12v FLOURESCENT. A useful kit that will enable you to light large flourescent tubes from your car battery etc. 9v mains transformer required. £8 kit, £12 built.

KNOB PACK
10 knobs for just £1.00

REMEMBER! YOUR FREE COPY OF OUR CUT PRICE COMPONENTS CATALOGUE SENT WITH EVERY ORDER!!!

How to place your order.....

By phone.....0273 771156


By FAX.....0273 206875

By Post...PO box 517 Hove Sussex BN3 5QZ


Payment by ACCESS, VISA, CHEQUE OR POSTAL ORDER.

Cheques and postal orders should be payable to Express Components.

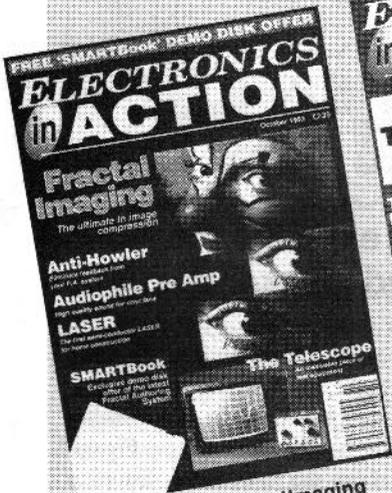
ALL PRICES ARE SUBJECT TO 99p POST AND VAT. Some of our products may be unlicensable for use in the UK (particularly the FM transmitters.)



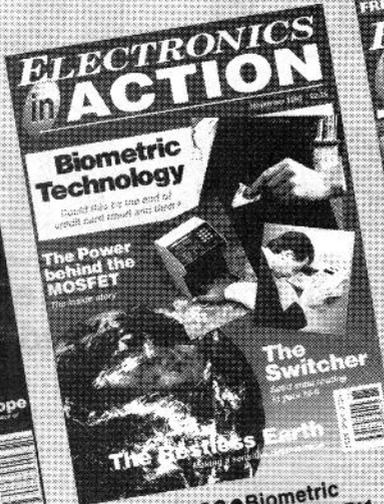
October 93 • Fractal Imaging
• The Telescope Pt1 • Anti-Howler • Audiophile Pre-amp
• Sine wave generator



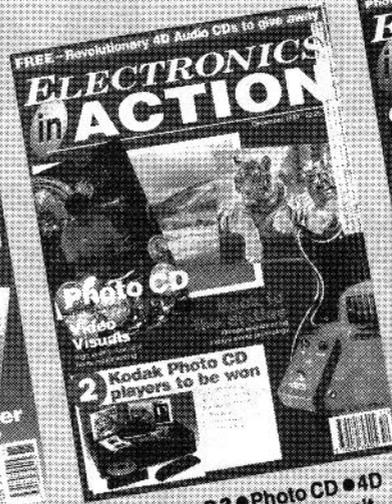
November 93 • Biometric Technology • The Switcher Pt1
• Seismometer Project • The Telescope Pt2



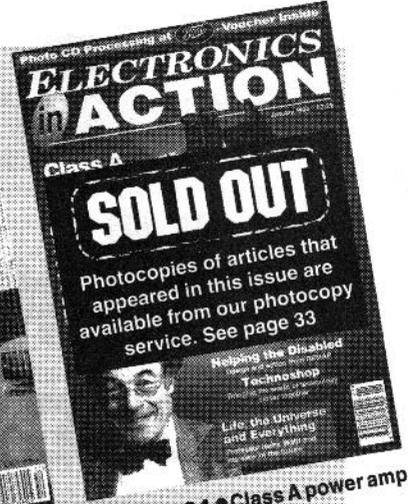December 93 • Photo CD • 4D Recording • Video editing unit
• Stereo tremolo unit
• The Switcher Pt2



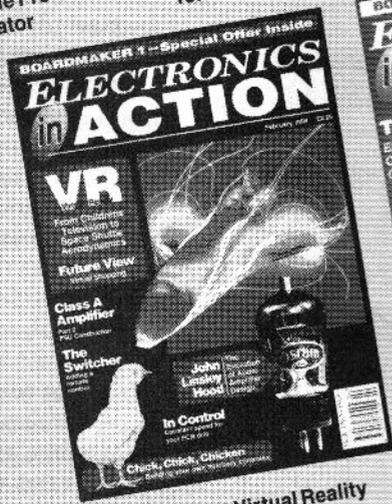
January 94 • Class A power amp
• The Harmoniser
• Remote control extender
• The Switcher Pt3



February 94 • Virtual Reality
• Class A amp Pt2 • Hatchery Controller • The Switcher Pt4



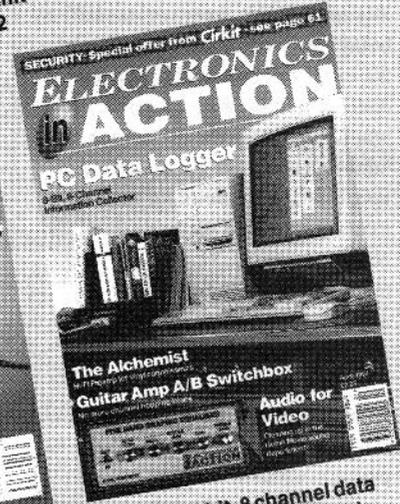March 94 • Colour test pattern generator • Cordless guitar project • Plug-in mains wiring tester • Intelligent Communication Networks • The Switcher Pt5



April 94 • 8 bit, 8 channel data logger for PC • 5 band graphic equaliser • The Alchemist - HiFi preamp • A/B Switchbox for guitar amp • Water level detector

HAVE YOU MISSED A FEW?

Fear not, our Back Numbers Dept. should be able to furnish you with almost any issue (our January issue was simply too popular). Fill in the coupon (or a photocopy of it) and post it to us with a cheque or postal order for the correct amount.

BACKNUMBERS

Print your name in **BLOCK CAPITALS**

Name

Address

..... Postcode

Please send me issue(s) of the October '93 edition

Please send me issue(s) of the November '93 edition

Please send me issue(s) of the December '93 edition

Please send me issue(s) of the February '94 edition

Please send me issue(s) of the March '94 edition

Please send me issue(s) of the April '94 edition

Each copy (including postage & packing) costs £2.50

I enclose a cheque/postal order for

Please send to: **Electronics in Action, PO Box 600 Berkhamsted, Herts. HP4 1NL**



An Act for the Cabaret

Part 1 Peter Roberts dons hat and cane and explains the theory behind his 'Cabaret' active loudspeaker design.

Ever looked at the distortion versus frequency curve of a loudspeaker? It gets incredibly high at low frequencies, 10% being fairly common. Fortunately the ear is tolerant of low frequency distortion. Note I said tolerant, you would recognise the difference between 10% and 1% distortion if you heard it. Reasons for this tolerance include the brains' ability to synthesise missing frequencies using harmonics as cues. Noticeable, acceptable and tolerable distortion levels vary with frequency, level and programme material and are the realms of psycho-acoustics.

There is a way to reduce low frequency distortion (dating back to 1950) which I came across by accident when I was designing an earlier active speaker.

The distortion is caused by the increased cone movement necessary at low frequencies. The lower the frequency the more cone excursion required. There will be non linearity in the cone suspension and the magnetic circuit, over the distance travelled, and this will cause distortion. There is usually a fair amount of non linearity especially at the extremes of travel.

The very simplified equivalent circuit of a drive unit is shown in Figure 1. The coil represents the mechanical compliance (opposite of stiffness) of the cone surround. The capacitor represents the moving mass of the cone and coil. The L-C resonant circuit so formed gives the resonant frequency of the speaker.

If you are having trouble visualising it, consider this. The mechanical load of an electric motor is reflected as a change

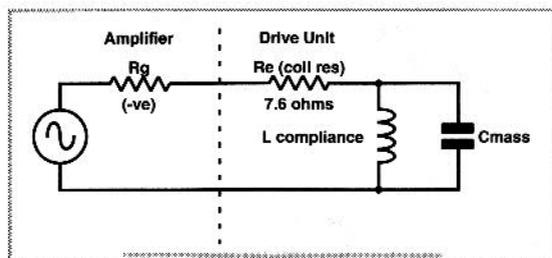


Fig.1 Simplified equivalent circuit of amplifier

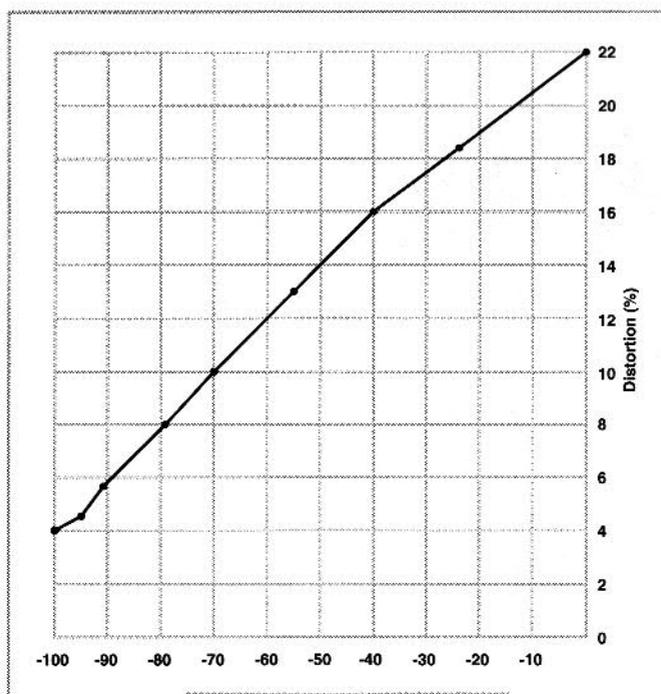


Fig.2 Negative resistance as % of voice coil

in electrical load on its supply. Similarly, the mechanical properties of the speaker have been reflected into the electrical circuit. This is a time honoured way of electrically modelling speaker performance. If we could short the coil and capacitor in the LC resonant circuit, we could damp the tuned circuit and damp out the speaker resonance. Unfortunately the voice coil resistance stops us directly shorting the tuned circuit. What we can do through is generate a negative resistance in the drive amplifier. This lowers the net resistance in

circuit and damps the speaker. Since we are also shorting the compliance we are also reducing the non-linear distortion. Figure 2 shows the reduction in distortion of an actual speaker as the negative resistance is increased, while Figure 3 shows the improvement in damping for a negative resistance of 85% of the voice coil resistance.

This technique was first described in 1950 by an American, by the name of Warner Clements. It was taken further in 1981 by Karl Erik Stahl of Sweden who designed an amplifier which could independently control the output inductance, capacitance and negative resistance, and thus electronically tweak the compliance, moving mass and damping of the drive unit connected to it. I should point out that there is a patent on this particular technique.


Funnily enough, the lower distortion etc. is a beneficial side effect of the main reason for using negative resistance. This is to tune the Qts of the drive unit to a suitable value

for a particular cabinet size. If the Qts is too high you get an underdamped response, with a muddy boomy bass (see Figure 4) and conversely if the Qts is too low you get an overdamped response with a loss of bass. Changing the Qts is a different, more precise way of saying we are changing the damping. The only drawback is that the amplifier driving the speaker has been matched to it and will not operate correctly with other speakers.

The Wizard of Oz

The full equivalent circuit of a closed box bass system is a second order high

Fig.3 Response to step function

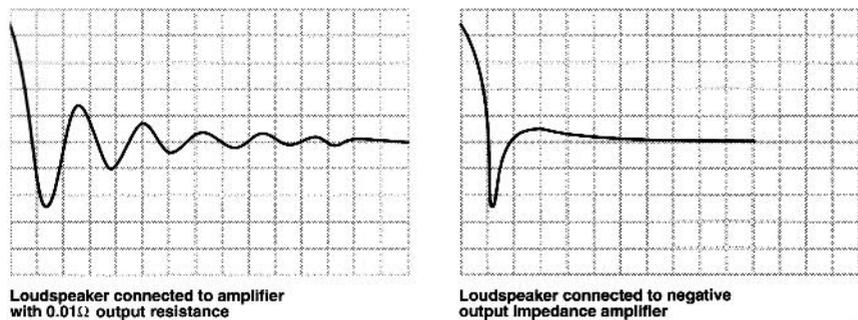

quency. This gives you the box tuning frequency.
 To determine the length of the port, use the nomogram in Figure 8, which is due to Small of Thiele/Small fame. Locate the box volume you require on the V_b column, for the example given, 2 cubic ft. Also find the box tuning frequency,

pass filter. The port in a bass reflex design introduces another second order filter. It was understanding these filters that led an Australian TV design engineer, Thiele, to formulate a method of designing bass reflex systems, back in 1961. He also showed that one can put in an extra second order filter, making a sixth order design.

This extra filter not only removes any rumble, it also reduces the cone excursion. A sixth order bass reflex gives a cone excursion one quarter the size of a closed box for the same output and -3dB bass down point (see Figure 5).

A bass response to down under

There are only three drive unit parameters needed to design a bass reflex speaker, the Q_s , the volume equivalent of compliance (V_{as}) and the resonant frequency. Even these are not always given (in some catalogues, all three values are not presented) However given some test gear they can be measured fairly easily, this is described later. Using graphs or tables one can then design an enclosure. Some authorities say you need a computer and a speaker design program, but these are not really necessary. It is when you stray off the beaten track of the classic alignments, that you need a computer. Indeed working with graphs often gives you more feel about the design. See Figure 6, which shows the Q_t versus volume

multiplier for a standard bass reflex speaker. Look along the bottom axis and find the Q_t of the drive unit, extend the point vertically upwards until it intersects the curve. Then project horizontally across to find the volume multiplier. This is the factor by which you

example 40Hz, on the F_b column. With a ruler linking the two points extend the line to the L_v/S_v column. From here project a horizontal line across until it intersects one of the curves. In this case it intersects two curves. If the larger diameter one is a reasonable length (ie.

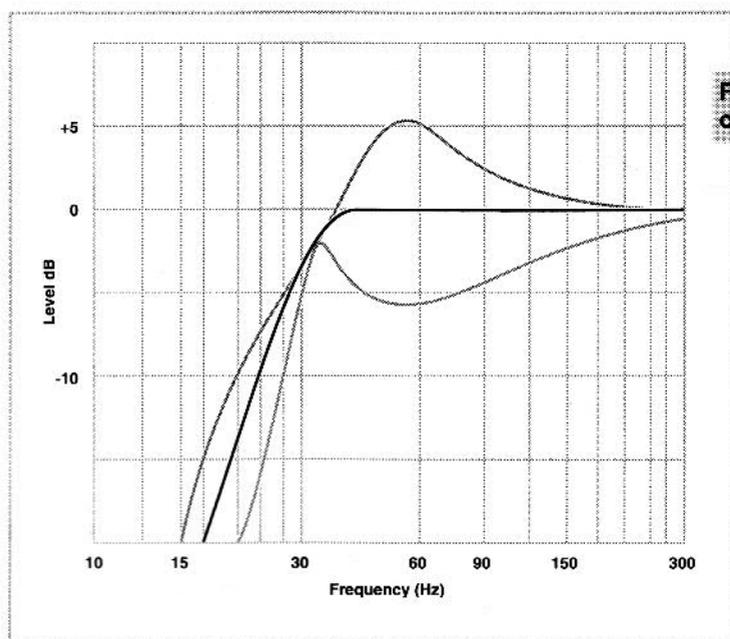


Fig.4 The effect of varying Qts

multiply the V_{as} , to give the enclosure volume.


Similarly, to find the port tuning frequency see Figure 7. Multiply the tuning frequency factor by the drive unit resonant fre-

less than 25 cm) it is best to go for that. Extend the intersect point vertically upwards to give the port length. The larger diameter port will give a lower port air velocity.

My Kef B200A has a Q_t of 0.6, a resonant frequency of 29Hz and a V_{as} of 100 litres. Multiplying the V_{as} by the 3.5 factor given in Figure 6, corresponding to the Q_t of 0.6, gives a box size of 350 litres or 12 cubic feet, which might impress one's fellow hi-fi addicts but would make you unpopular with anyone else. This also shows that a low compliance woofer is required for a bass reflex design, to achieve a small cabinet size. For a closed box design a high compliance driver is needed so that the air in the box can be the dominant compliance.

As can be seen from Figure 6 low Q_t values will give a small enclosure size.

Fig.5 Cone excursion against frequency for different designs (Cabinet, drive unit and cut-off frequencies identical)

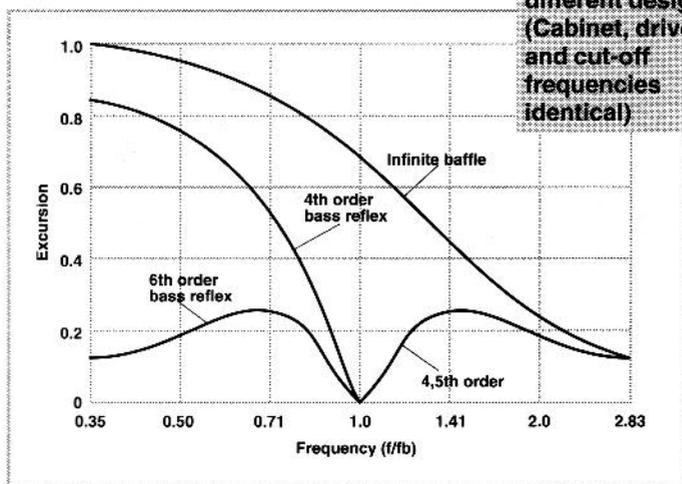

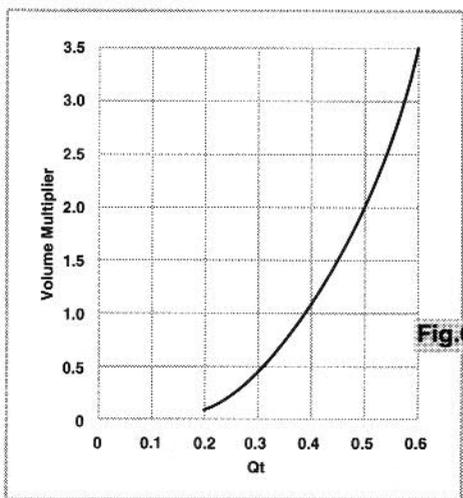


Fig. 6

Since the Q_t is inversely related to magnet size, a large speaker magnet is needed to give a low Q_t and large magnets are expensive. An alternative way to vary the Q_t is with a negative or positive output resistance from the amplifier driving the speaker. It is then possible to vary the Q_t at will, so that a given speaker can be matched to a given enclosure. Given the Kef B200A above, using negative resistance, one could easily modify the Q_t to 0.3, giving a volume multiplier of 0.47, hence a much more suitable cabinet size of 47 litres. The distortion and damping will have improved as well.

Figure 6 is a plot of the function


$$\frac{V_b}{V_{as}} = Q_t^{2.87} \times 15$$

where V_b is the box volume and V_{as} is the volume equivalent of compliance.

Figure 7 is a plot of

$$\frac{F_b}{F_s} = Q_t^{-0.9} \times 0.42$$

Fig. 8 Nomogram and chart for design of ducted vents

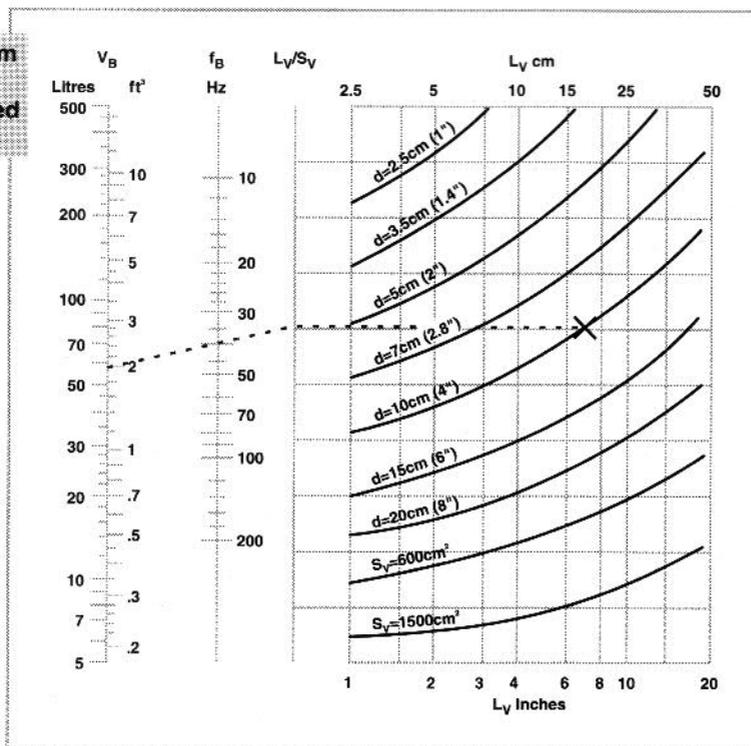

where F_b is the box resonant frequency and F_s is the drive unit resonant frequency.

The cutoff frequency can be computed from

$$F_{co} = Q_t^{-1.4} \times 0.26 \times F_s$$

For the B200A example, the -3dB point would thus be 40.7Hz.

I use the sixth order designs for which you also need to know the Q and the frequency cut-off of the extra electronic filter. Note that you cannot "bolt-on" the electronic filter to a standard reflex design, the system has to be treated as an integrated whole. Thus the sixth order box size and port tuning will be different to a standard fourth order design. The sixth order alignments can give a considerable bass extension for a given box size than the standard reflex design. For the B200A example the sixth order cut-off would be 29Hz for the same cabinet size as the standard fourth order reflex.

The sixth order parameters are presented in tabular form in Bywater and Weibulls paper, Alignment of filter assisted vented box loudspeaker systems with enclosure losses. JAES May 1982. Another paper from the considerable body of work by Australian speaker engineers, presumably prompted by Thieles work. Some of the worlds leading speaker engineers have Australian connections. Once you have heard a speaker designed according to their principles, you wouldn't give a XXXX for anything else.

Measuring the manifold

To measure the drive unit parameters firstly, if the speaker is brand new, you need to run it in. Believe me, the resonant frequency and especially the compliance can change significantly as the suspension loosens up. I run units in for 8 hours minimum at 20Hz and 10watts. Measure the resistance of the voice coil,

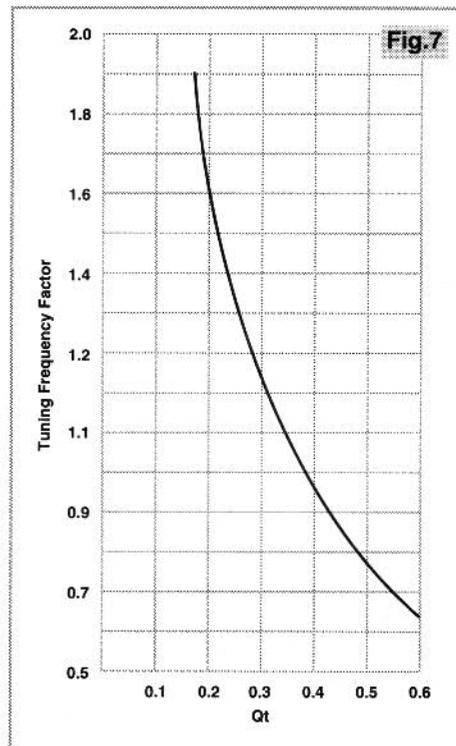


Fig. 7

Re. Then create the set-up shown in Figure 9. You need a audio signal generator with a high output or an amplifier to boost the output of a low output unit. The 680 ohm resistor simulates a constant current source. The frequency counter and AC voltmeter are optional to improve accuracy.

With the oscillator frequency set to about 100Hz, Set the oscillator output level so that 100mV RMS (or 100mV peak to peak if using the oscilloscope) is developed across the 10ohm resistor. Then each 10mV represents 1 ohm, so that if you read 76mV the resistance is 7.6 ohm. Switch the output to the speaker, lying face up on the bench. Adjust the frequency until the output is a peak as observed on the 'scope. Note this frequency and the voltage. You now have the resonant frequency F_r and the resistance at resonance, R_s . Divide R_s by the Dc resistance R_e to give r_o . Compute $r_o * R_e$. You then need to find the two frequencies f_1 and f_2 either side of resonance which have this resistance.

$$\text{Then } Q_{ts} = f_r \left(\frac{R_e}{R_s} \right) / (f_2 - f_1)$$

$$Q_m = f_r \frac{ro}{f2-f1}$$

$$Q_e = \frac{Q_m}{ro-1}$$

The total Q_t is made up of the Q_m , mechanical Q and the Q_e , the electrical Q . We can modify the electrical Q with the negative resistance technique to lower the Q_t to that required for one's design then

$$\frac{1}{Q_{t(\text{required})}} = \frac{1}{Q_m} + \frac{1}{Q_e} \left(\frac{1}{1+Rg/Re} \right)$$

where Rg is the negative resistance.

To measure the compliance, V_{as} , put the drive unit in a ported unstuffed cabinet with a known volume V_b litres. In the cabinet, the speaker will have 2 resonant frequencies f_b and f_1 . Use the test set-up in Figure 8 to find these frequencies. Now tape some stiff card

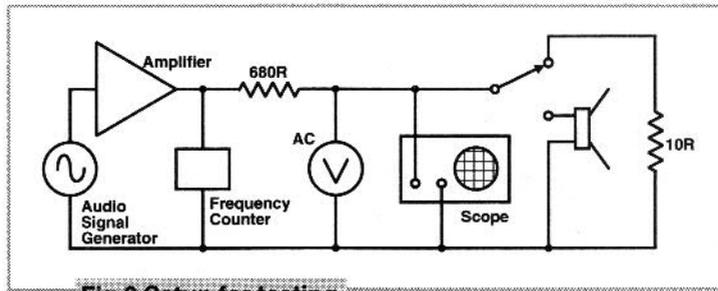


Fig.9 Setup for testing loudspeakers

more air the cone has to move. This means large cone excursions for the bass driver. For instance to generate 1 acoustic watt at 50Hz, the closed box cone excursion of an 200mm diameter driver would be 45mm, a 300mm driver would have 20mm and a 375mm unit 13mm. The 45mm throw is extremely difficult to accomplish. Exceptional designs like ATC's can achieve about 38mm. If those distances look large, it is because 1 acoustic watt/m is a sound level of

Design choices


The question is how much acoustic power does one need? Surprisingly little if you listen at normal domestic listening levels. However, if you trying to reproduce orchestral levels in your living room or you are merely a head-banger, then to achieve bass transients like the cannons in the 1812 overture with adequate dynamic range you need something better than your average 165-200mm bass driver.

Bigger is better

So for low frequency bass the bigger the driver the better. However usually the bigger the driver the greater the compliance so to achieve a reasonable box size, a compromise has been set with a 250mm driver.

This size also will be less troubled by the break-up modes of the cone, which are problematical with large cones at high frequencies. Further it allows a 2 way design, which is easier to integrate than a 3 way. The more is better approach does not work here, a good 2 way design is far superior to a 3 way design costing the same price.

The Cabaret is a tower of power, namely a tower type active speaker design. Despite being 60 litres capacity, its footprint area is small and it does not need stands. It's 3dB down point is 30Hz. To achieve substantial outputs the amplifiers used are 40 watts. A Morel drive unit is used which has a different magnet topology to a standard speaker, see Figure 10. The massive coil assembly gives a low resistance change with a loud programme and optimises the negative resistance operation.

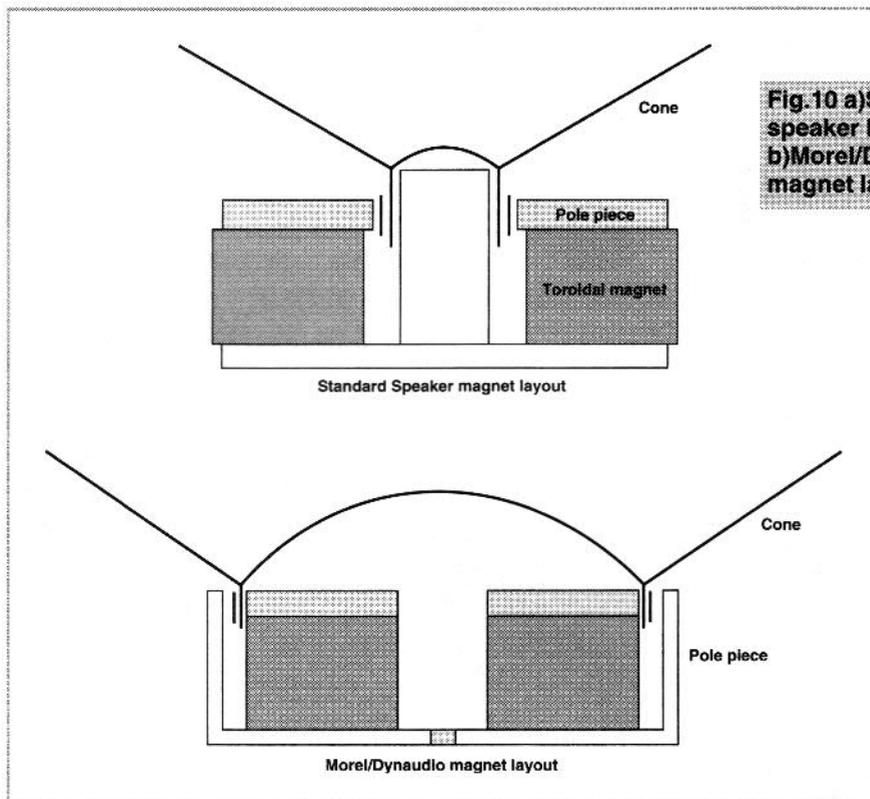

**Fig.10 a) Standard speaker layout
b) Morel/Dynaudio magnet layout**

over the port hole to make a closed box. Measure the one resonant frequency, f_b

$$\text{Then } \frac{V_{as}}{V_b} = \frac{(f_n^2 - f_b^2)(f_b^2 - f_1^2)}{f_n^2 f_1^2}$$

This is also a useful test to run on the completed speaker.

Come on down

To generate high levels of low frequency sound the speaker cone has to move air. The lower the frequency the

120dB which is the threshold of pain.

There are 4 rules about bass frequencies here, for a given output level;

- 1** If the cone area is doubled, the cone excursion is halved and vice versa.
- 2** If the frequency is halved, say 50 to 25Hz, the cone excursion is increased by a factor of four.
- 3** If the cone excursion is halved the acoustic power is halved.
- 4** If the cone area is doubled, for the same excursion the acoustic power increases by 4 times.

NEXT MONTH


Peter Roberts begins building the 'Cabaret' Loudspeaker

POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

★ PRICES INCLUDE V.A.T. ★ PROMPT DELIVERIES ★ FRIENDLY SERVICE ★ LARGE (A4) S.A.E., 60p STAMPED FOR CATALOGUE ★

OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK

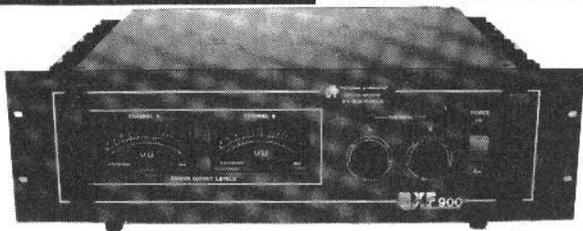THOUSANDS PURCHASED BY PROFESSIONAL USERS




THE RENOWNED MXF SERIES OF POWER AMPLIFIERS
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)
ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19"xH3 1/4" (2U)xD11"
MXF400 W19"xH5 1/4" (3U)xD12"
MXF600 W19"xH5 1/4" (3U)xD13"
MXF900 W19"xH6 1/4" (3U)xD14 1/2"

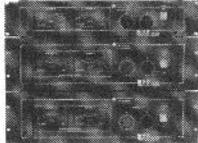PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH



OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DCL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.




Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA


Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series. **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized HI-FI speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for HI-FI monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

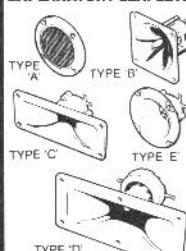

ibf FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

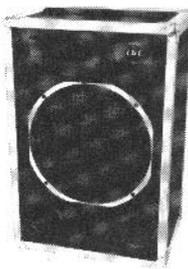

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET
FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

ibf FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
ibf FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair

IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS

Features:
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and HI-FI etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 - £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE- INSTRUMENTS, P.A., DISCO, ETC

ALL EMINENCE UNITS 8 OHMS IMPEDANCE
8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £39.74 + £2.50 P&P
RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P
RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P
RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. PRICE £36.67 + £3.50 P&P
RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB.
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P
RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB.
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.
10" 50WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/4" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB.
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz. VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 - £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz. VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 48mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P

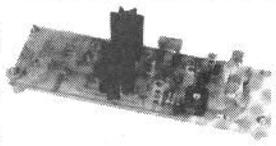


PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR.

Tel.: 0702 - 527572 Fax.: 0702 - 420243



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



HART

HART AUDIO KITS – YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HART KITS give you the opportunity to build the very best engineered hifi equipment there is, designed by the leaders in their field, using the best components that are available.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

In short HART is your 'friend in the trade' giving you, as a knowledgeable constructor, access to better equipment at lower prices than the man in the street.

You can buy the reprints and construction manual for any kit to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

Our list will give you fuller details of all our Audio Kits, components and special offers.

AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hifi system. This kit is your way to get £K performance for a few tenths of the cost! Featured on the front cover of 'Electronics Today International' this complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic:- "The external view is that of a thoroughly professional piece of audio gear, neat elegant and functional. This impression is greatly reinforced by the internal appearance, which is redolent of quality, both in components and in layout." Options include a stereo LED power meter and a versatile passive front end giving switched inputs using ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility so that for use with tuners, tape and CD players, or indeed any other 'flat' inputs the power amplifier may be used on its own, without the need for any external signal handling stages. 'Slave' and 'monobloc' versions without the passive input stage and power meter are also available. All versions fit within our standard 420 x 260 x 75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised, and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/heat-sink fitted with IEC mains input and output sockets. All the circuitry is on professional grade printed circuit boards with roller tinned finish and green solder resist on the component ident side, the power amplifiers feature an advanced double sided layout for maximum performance. All wiring in this kit is pre-terminated, ready for instant use!

RLH11 Reprints of latest articles.....£1.80
K1100CM HART Construction Manual.....£5.50

LINSLEY HOOD 1400 SERIES ULTRA HIGH-QUALITY PREAMP

Joining our magnificent 80 Watt power amplifier now is the most advanced preamplifier ever offered on the kit, or indeed made-up marketplace. Facilities include separate tape signal selection to enable you to listen to one programme while recording another, up to 7 inputs, cross recording facilities, class A headphone amplifier, cancellable 3-level tone controls and many other useful functions, all selected by high quality relays. For full details see our list.

Send or phone for your copy of our List (50p) of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write or telephone your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows:-INLAND Orders up to £20 - £1.50,
Orders over £20 - £3.50. Express Courier, next working day £10.

OVERSEAS - Please see the ordering information with our lists.

LINSLEY HOOD 'SHUNT FEEDBACK' R.I.A.A. MOVING COIL & MOVING MAGNET PICKUP PREAMPLIFIERS



Modern, ultimate sound systems are evolving towards built-in preamplifiers within or near the turntable unit. This keeps noise pickup and treble loss to a minimum. We now offer two units, both having the sonically preferred shunt feedback configuration to give an accurate and musical sound, and both having the ability to use both moving magnet and moving coil cartridges.

Kit K1500 uses modern integrated circuits to achieve outstanding sound quality at minimal cost. The very low power requirements enable this unit to be operated from dry batteries and the kit comes with very detailed instructions making it ideal for the beginner. K1500 Complete kit with all components, printed circuit board, full instructions and fully finished case.....£67.99
Instructions only.....£2.80

Kit K1450 is a fully discrete component implementation of the shunt feedback concept and used with the right cartridge offers the discerning user the ultimate in sound quality from vinyl disks. Can be fitted inside our 1400 Preamp, used externally or as a standalone unit. It has a higher power requirement and needs to be powered from our 1400 Series preamplifier or its own dedicated power supply. K1450 Complete Discrete Component RIAA Phono Preamp.....£109.58
Factory Assembled and Tested.....£159.58
K1565 Matching Audio Grade Power Supply with potted toroidal transformer and limited shift earthing system.....£79.42
Factory Assembled and Tested.....£118.42
U1115 Power Interconnect Cable.....£7.29

SPECIAL OFFER PRECISION Triple Purpose TEST CASSETTE TC1DD.

Are you sure your tape recorder is set up to give its best? Our latest triple purpose test cassette checks the three most important tape parameters without test equipment. Ideal when fitting new heads.

A professional quality, digitally mastered test tape at a price anyone can afford.

Test Cassette TC1DD.....Our price only £10.99.

DISK-COUNT Classical CDs.

Top Quality, Full Digital (DDD) Compact Disks of the great classical favourites.

Like everyone else we didn't like the idea of paying silly prices for CDs. After a long search we have now located a source of top quality classical recordings at prices that make you suspect the quality - until you try them! Send for our list of titles.

CD ROMs

Like music CDs these have overpriced for some time but with low prices of CD ROM drives the multimedia revolution is with us now. Send for our list of titles. Most popular up to now have been "Too Many Typefonts" with 514 TrueType fonts along with 393 ATM and lots of others. "Shareware Overload" with over 6100 programs extending to 550MB and "Kodak Photo CD Access". The first two are only £12.95, the Kodak only £24.

TECHNICAL BOOKSHELF

Modern Books. Selected to represent the state of the art today.

"THE ART OF LINEAR ELECTRONICS."

J.L. Linsley Hood.

Just Out! Hot off the Press, the definitive electronics and audio book by the renowned John Linsley Hood.

This 300+ page book will give you an unparalleled insight into the workings of all the types of audio circuits. Learn how to read circuit diagrams and understand amplifiers and how they are designed to give the best sound. The virtues and vices of passive and active components are examined and there are separate sections covering power supplies and the sources of noise and hum. As one would expect from this writer the history and derivation of audio amplifier circuitry have an entire chapter, as does test and measurement equipment.

Copiously illustrated this book is incredible value for the amount of information it contains on the much neglected field of linear, as opposed to digital, electronics. Indeed it must be destined to become the standard reference for all who work, or are interested in this field.

SPECIAL OFFER.

With each book purchased you may request a FREE extended index, written by the author, exclusively from HART. 0-7806-0868-4.....£16.95

Don't forget most of our Kits have reprints of articles by John Linsley Hood that you can purchase separately.

"THE ART OF SOLDERING"

R Brewster.

Absolutely essential reading for anyone who ever picks up a soldering iron. Written from knowledge gained in a lifetime in the field, this is the first book ever solely devoted to this essential and neglected skill for all electronic enthusiasts. Covers everything from the correct choice of soldering iron and solder to the correct procedures to follow with many illustrations and practical exercises.

0-85935-324-3.....£3.95

"AUDIO" F.A. Wilson.

320 pages. 178 x 111. Publ. 1985

BP111 "AUDIO" by F.A. Wilson.....£3.95

"AN INTRODUCTION TO LOUDSPEAKERS & ENCLOSURE DESIGN" V Capel.

160 pages. 178 x 111. Publ. 1988

BP256.....£2.95

"LOUDSPEAKERS FOR MUSICIANS" V Capel.

176 pages. 178 x 111. Publ. 1991.

BP297.....£3.95

"HOW TO USE OSCILLOSCOPES & OTHER TEST EQUIPMENT" R. A. Penfold.

112 pages. 178 x 111. Publ. 1989

BP267.....£3.50

Classics from the "Golden Age"

"THE WILLIAMSON AMPLIFIER."

D.T.N. Williamson.

In April 1947, Williamson's power amplifier, using excellent quality push-pull output valves, a special output transformer, and a highly filtered power supply, became an overnight success. The author takes the reader deep into his design considerations, offering practical advice on how to build the units plus concise instructions on setting up the new amp. A cult classic.

1947, Reprinted 1990. 40 pages.

0-9624-1918-4.....£4.95

LOUDSPEAKERS; THE WHY AND HOW OF GOOD REPRODUCTION.

G.A. Briggs

This easy-to-read classic, last revised in 1949, introduces the reader to concepts such as impedance, phons and decibels, frequency response, response curves, volume and watts, resonance and vibration, cabinets and baffles, horns, room acoustics, transients, crossovers, negative feedback, Doppler and phase effects, and much more. A provocative survey of the right questions about sound reproduction.

1949 reprinted 1990. 88 Pages. 215 x 140

0-9624-1913-3.....£6.95

COMPUTER TITLES.

"A CONCISE ADVANCED USERS GUIDE TO MS DOS"

N. Kantaris.

144 pages. 198 x 130. Publ. 1992

BP264.....£3.95

"A CONCISE USERS GUIDE TO MS DOS 5"

N. Kantaris.

144 pages. 198 x 130. Publ. 1992.

BP318.....£4.95

"MAKING MS DOS WORK FOR YOU"

N. Kantaris & P.R.M. Oliver

160 pages. 198 x 130. Publ. 1993.

BP325.....£4.95

"A CONCISE USERS GUIDE TO WINDOWS 3.1"

N. Kantaris.

160 pages. 198 x 130. Publ. 1992.

BP325.....£4.95



QUALITY AUDIO KITS

24 hr. SALES LINE (0691) 652894

ALL PRICES INCLUDE UK/EC VAT

HART

HART ELECTRONIC KITS LTD
3 PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

The Evolution of Audio Amplifier Design

Part 4 True Hi-Fi at last?

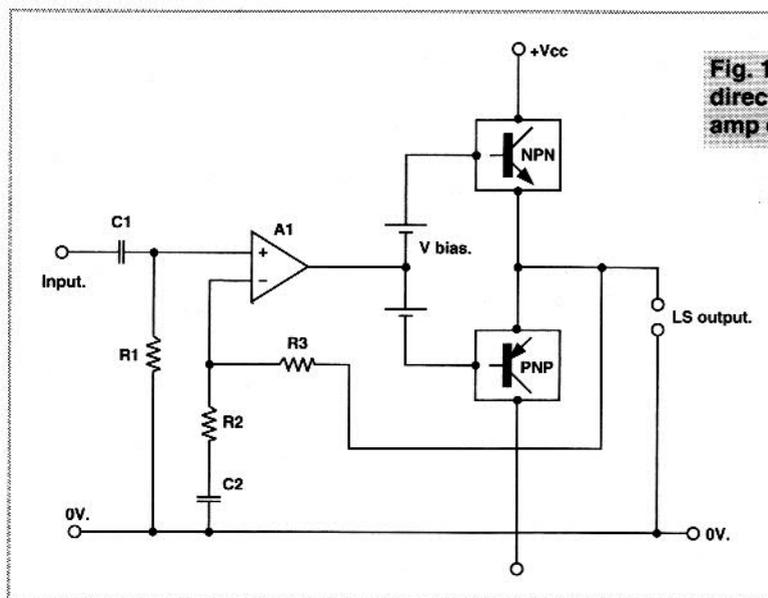


Fig. 1 Basic direct coupled amp circuit

In the last part of this article I looked at the developments in audio amplifier circuitry up to the early 1970s, and I think that this was about the time when transistor operated power amps. began to meet the standards of quality achieved by valve designs some 15-20 or more years before. There were, of course, residual advantages and relative disadvantages in both of these systems, and, in general, these remain to this day.

Valves vs. Transistors

On the side of the valve amps., they used old and trusted technology, they were overload and output short-circuit proof, though they did **not** like operating into an open circuit load, which could cause the output valves to spark

over from anode to grids inside the glass envelope. They normally only needed to, or indeed could, use a moderate degree of negative feedback, usually about 26dB (20x) or so, and this usually allowed a good loop stability margin and a thoroughly house-trained approach to awkward LS load characteristics, and, provided that they had a decently designed output transformer, they would have a frequency response which covered from a few Hz, to say, 100KHz.

On behalf of the transistor systems, one could claim that, by about 1975, almost all of the amplifiers from the better manufacturers had thoroughly respectable harmonic and intermodulation distortion figures -

which did not worsen greatly at very low power levels - an adequate degree of load stability, and a reasonable reactive load transient response. (I know

that I tend to be a bit unenthusiastic about the average solid state amp. transient response, but then, if judged by the same standards, valve amps. were usually a whole lot worse. For excellence in this quality at that time one needed to turn to the better DIY designs.)

What transistor operated power amps. *did* offer that none of the valve amps. could match, was freedom from the need to use an output transformer. In particular, where the amp. was powered from a pair of +ve and -ve supply lines, its output could be coupled directly to the LS load; a layout which I have shown in schematic form in Figure 1.

Although it is 'direct coupled', the amplifier will not work at full gain right down to DC since it is usually necessary to include a capacitor, C2, in the negative feedback loop (R3,R2,C2) in order to stop long-term DC level drifts in the voltage amplifier (A1) causing unwanted DC offsets at the LS output terminals, and that capacitor sets a lower limit to the LF response of the amplifier - given by the formula $f_l = 1/(2\pi C2R2)$. For an extended bass response a large capacitor (usually electrolytic) was needed for C2, and this led to further problems.

The other enormous advantage of solid-state amp. designs was the amount of power they could provide. When this

advantage was first realised, LS system designers - who mostly had tunnel vision where their own speciality was concerned - began to design speaker units whose improved sound quality was gained at the cost of very low acoustic efficiency. After all, why worry? A few hundred watts is easy enough to obtain. Well, so it is, but not with valve designs, which operate, almost always, in class 'A', at a maximum efficiency which will not exceed 25%.

So, for a stereo pair of 100 watt valve amplifiers, one is going to use and dissipate somewhere in the region of 0.8 - 1KW of power. This kind of kit is very expensive to buy, hot in use and too large to tuck away out of sight on a bookshelf. A further advantage of the solid-state approach is that if it is designed competently, and treated with reasonable care, it will have an exceedingly long service life - unlike the hot-glass devices, which will deteriorate continuously in use, and whose valves will need replacing after five years, and the electrolytics after ten to fifteen, if one wishes to retain the original performance of the system.

But there are snags

Aluminium electrolytic capacitors, of the kind generally available in the 1960s, did not work well if they were operated (as in Figure 1) with zero voltage between their terminals. Under this condition they could, in due course,

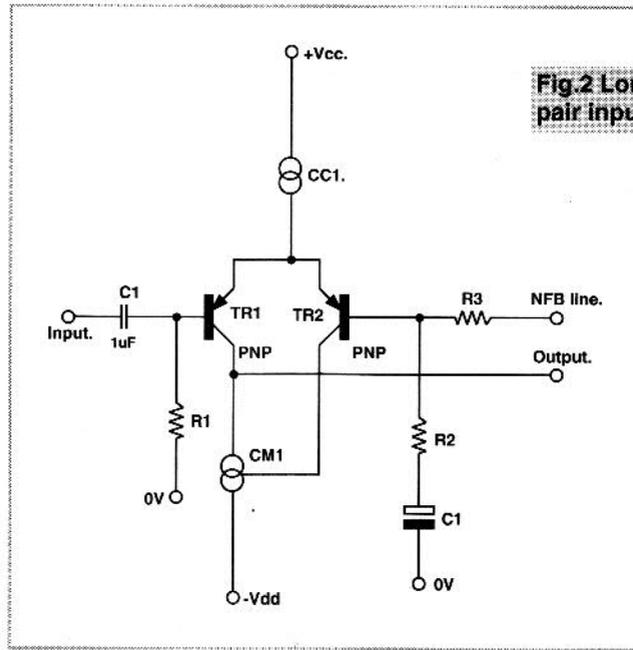


Fig.2 Long tailed pair input stage

would be about the size of a pea, and cost in those days about 10p.

[However, a point which must be remembered here is that the components used in the feedback circuit (R3,R2,C2) are critical in determining the amplifier performance, and C2, in particular, must have the highest practicable electrical performance. Some ultra-Fi systems put up with the operating problems which arise from this decision, and delete C2 altogether.]

Another problem which cropped up, immediately the direct-coupled layout was adopted, (in which the large capac-

Since the mechanical contacts in the fuse holder or relay sockets may well become tarnished or corroded with time, better practice is to have some purely electronic current limiting circuitry to prevent possible LS damage, but even this is not always a good idea, since it can cause peak-clipping of the output signal - which is unpleasant to the listener. It is because such overload-protected solid state amps. will hard-clip on any over-voltage swing - however brief - which makes the average valve amp., with its gentle overload characteristics, seem, in use, to be more powerful than the theoretically more beefy transistor design.

Still, this is a quality which will mostly appeal to the 'heavy metal' and 'hard rock' brigade - especially if they like their music loud. Since they don't make very comfortable neighbours, it is lucky that there aren't too many of them.

Circuit design techniques

There are, I suppose, four main objectives for the audio amplifier designer - reliability, pleasing sound quality, good technical specification and simplicity of design. Luckily these requirements are not incompatible, provided one doesn't go 'over the top' on specifications. The evolution of circuit design over the years has given the amplifier designer a wide range of circuit layouts from which to choose, which help improve circuit performance in various ways.

Long-tailed pair input stages

In general, small-signal (preamp. type) circuitry encounters few problems and is easy to design. Since the circuit layouts used in this, where discrete components

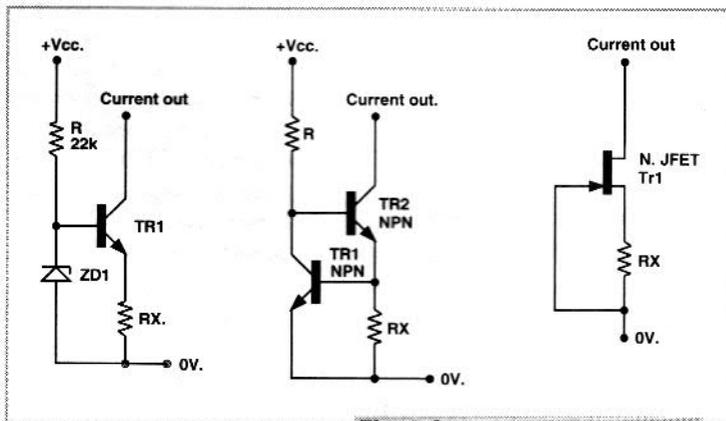


Fig. 3 Current source circuits

become both leaky and noisy. Also, they would go short-circuit if reverse biased. Tantalum capacitors were much better in this respect, and could tolerate both long duration zero voltage operation, in addition to occasional small (up to, say, 1V) reverse voltages, without breakdown, but they were expensive. So, what really gave the boost to the 'direct coupled' scheme was the development of the (then quite cheap) epoxy resin encapsulated Tantalum 'bead' capacitors, in which form a 100µF/3V device

ity output coupling capacitor was no longer used), was that of LS protection. Good quality LS units are expensive, and if one of the output transistors went 'short-circuit' the whole output of one or other of the power supply rails would pour through the LS speech coil, causing a loud noise followed by some expensive smoke. The simple answer usually adopted is to use a 'slow blow' fuse, or a DC offset-level sensitive relay 'cut-out' in the LS output circuit.

rather than ICs are used, are very similar to those used in power amps. we can consider these together. As a rule, all modern designs, both for pre. and power amps, now use split rail (+/-V) power supplies, with both the input and output signals referred to a '0V' line, and this is most easily arranged by the use of an input 'long-tailed pair circuit' of the kind I have sketched in Figure 2. This layout has a much lower THD than a single transistor amplifier stage, and is balanced about the '0V' line - a feature needed in a direct coupled system. I have shown Tr1 and Tr2 as PNP transistors in this circuit, but it could equally well be turned upside down and built with NPN ones.

Constant-current sources and 'Current Mirrors'

The use of a high dynamic impedance 'constant-current source' (CC1) as the 'tail' is a good idea because it improves the integrity of signal transfer from Tr2 to Tr1, and it also helps to reject distortion, noise and 'hum' signals from the +ve line. The use of a 'current-mirror' as its output load combines the outputs from Tr1 and Tr2, doubles the circuit gain, and also helps exclude unwanted rubbish from the -ve line.

I have used conventional 'short-hand' symbols for the current source and current mirror parts of the circuit. These will usually be circuit arrangements of the kind shown in Figure 3 and 4. The circuit used in Fig. 3a is often used in commercial systems, but for a high dynamic impedance Rx must be moderately large, and this requires that ZD1 should be a zener diode, and zeners are noisy. The layout of Figure 3b is better,

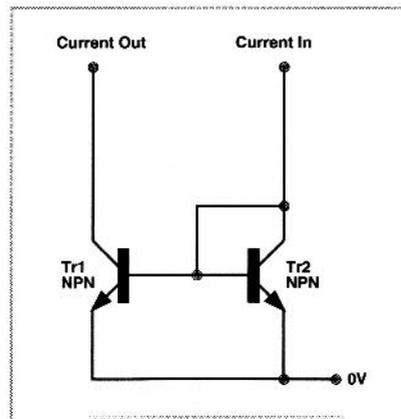
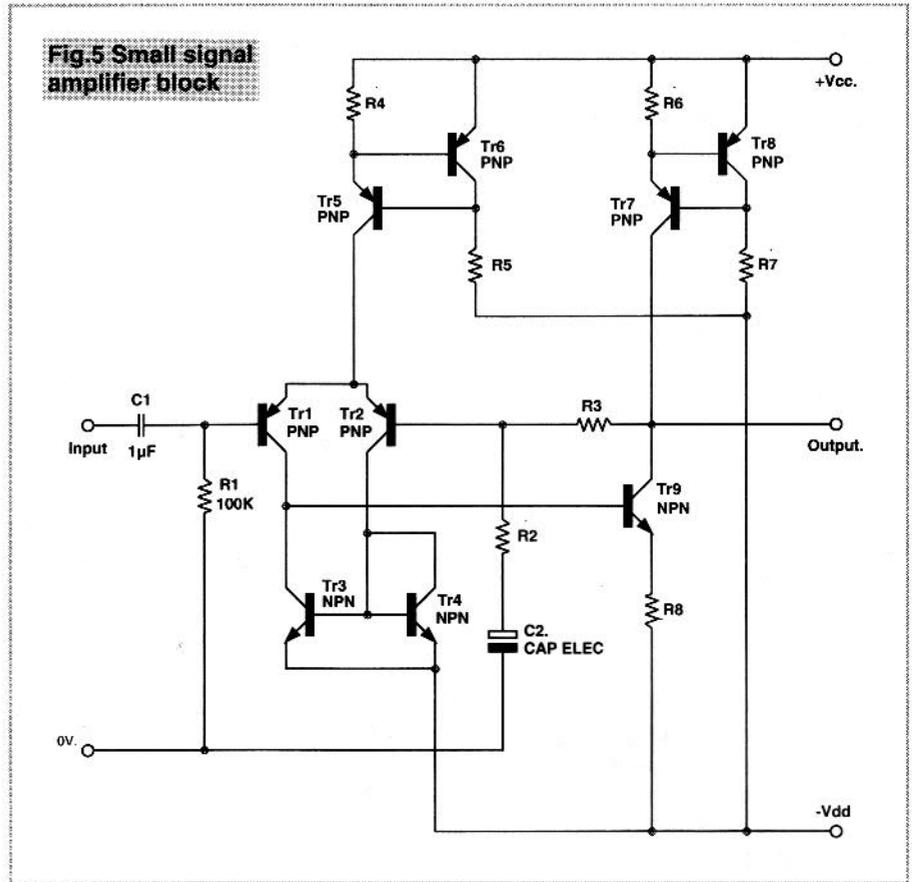


Fig. 4 Simple current-mirror layout

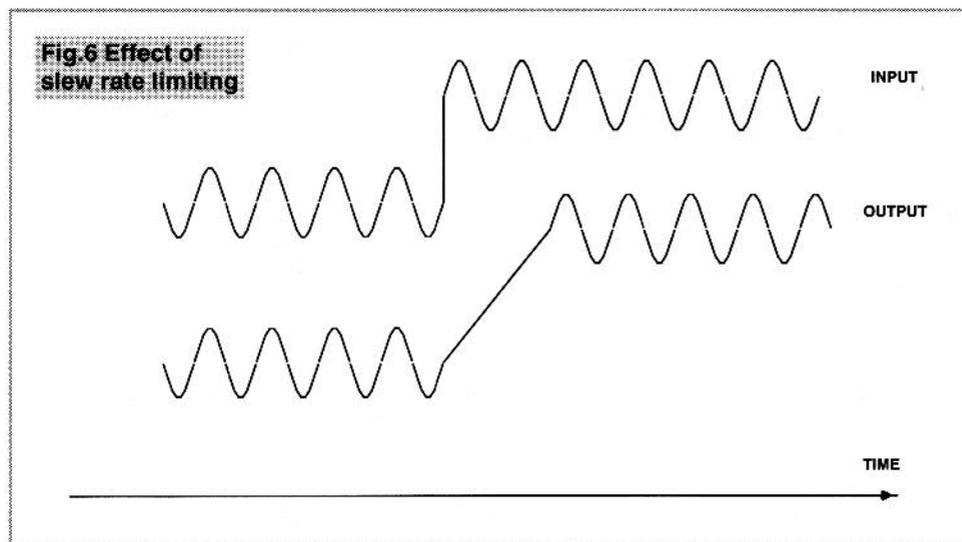


Fig. 6 Effect of slew rate limiting

and is my own preference for this job. The junction FET circuit of Figure 3c, has an excellent performance, within the voltage limits imposed by the FET breakdown characteristics - usually 20-30V.

The circuits of both 3a and 3b can be turned upside down, using PNP transistors, to operate towards a -ve voltage line. The circuit of 3c, since it is a two-terminal layout, works happily in either direction, provided the polarities are observed. In all these circuits, Rx determines the output current. Two-terminal constant current diodes, for fixed output currents, using similar internal circuitry to that of Figure 3c, are commercially available, with working voltages up to 100V, and with dynamic impedances of up to 10M or more, but they are dear.

The other useful circuit block is the 'current mirror', for which I have shown a simple circuit layout in Figure 4: an arrangement which acts to 'mirror' the input current at its output. Once again this circuit is available as a commercial device, offering various input:output 'mirror' ratios. This circuit makes a high dynamic impedance and

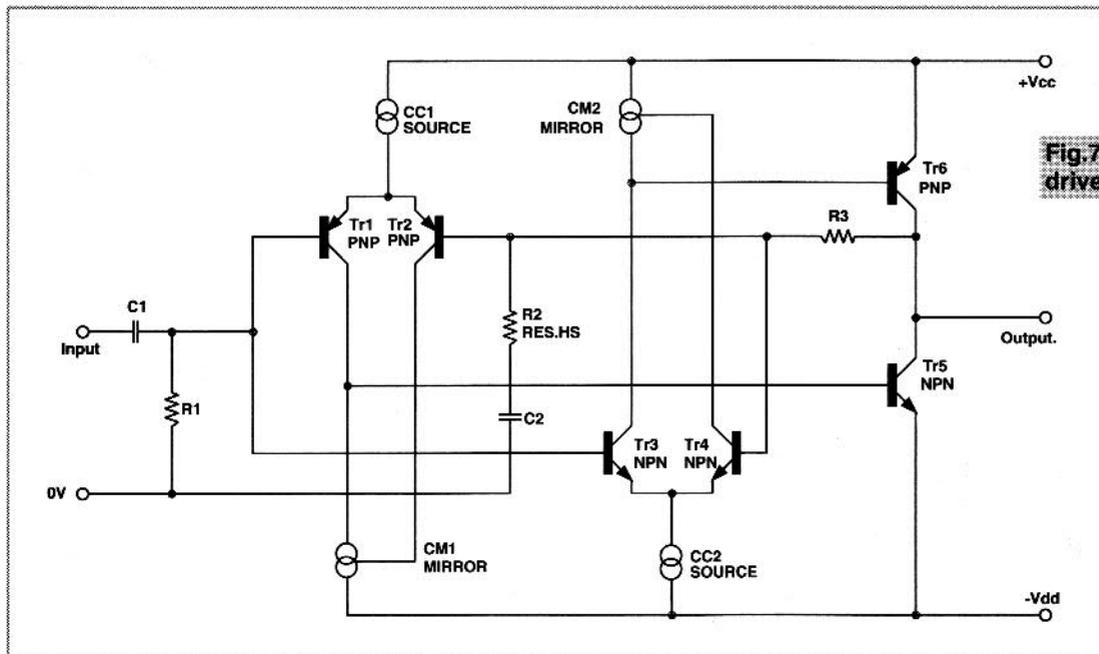


Fig. 7 Symmetrical drive circuit

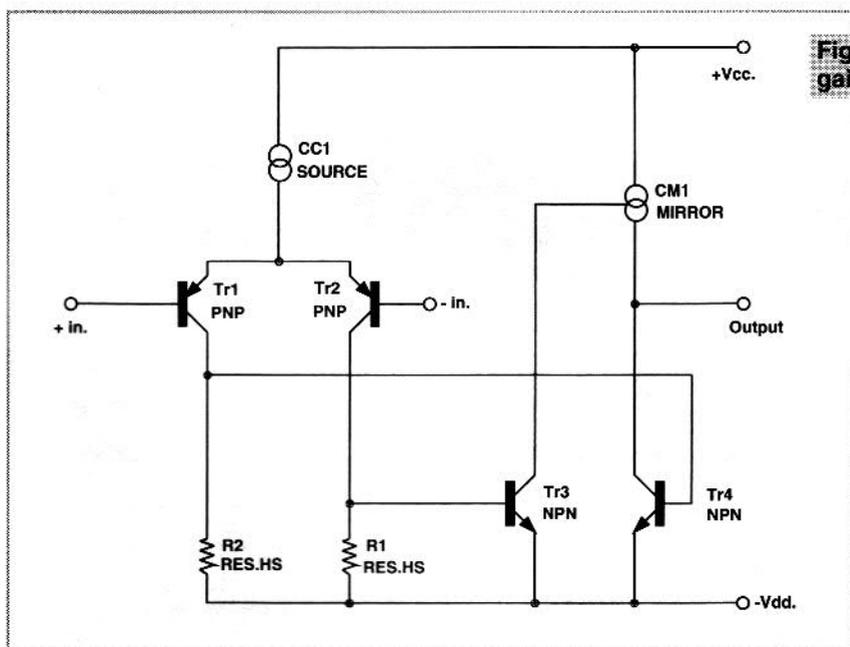


Fig. 8 NS/Hitachi gain block circuit

high gain 'active' load, particularly effective in improving the performance of a long-tailed pair, leading to the kind of circuit I have shown in Figure 5. I have elaborated this by the addition of Tr9, and a further constant current load, to make a complete high performance gain block, with an open-loop (i.e., before negative feedback is applied) gain of some 100,000x or more, and a very low distortion.

Once again, this whole circuit can be turned upside down with N instead of P devices, and vice versa. Anyone needing a high performance small-signal amplifier stage and not wishing to use an IC, (perhaps because the output voltage swing is too large for a normal IC to handle), could use this circuit without reservations.

Symmetry

A potential problem with all amplifier systems is that of 'slew rate limiting' - or Transient Intermodulation Distortion' as it is more romantically called - in which a large input signal can drive the amplifier into a condition, shown in Figure 6, when any smaller signal applied to the amplifier at the same time could be blotted out.

This defect could occur with any unsymmetrical circuit, such as, for example, the circuit of Figure 5 if there was a significant amount of capacitance connected across its output, since although this could be discharged rapidly when Tr9 was turned hard 'on', it could take a longer time to charge up again through its constant current load (Tr7/Tr8). In this case, the most straightforward

answer would be to simply double-up the circuit with its mirror image, shown

schematically in Figure 7, which is as fast to respond in the +ve going direction as in the -ve one.


This layout has been used in some very good preamplifier systems, as well as in some excellent audio power amplifiers, with circuits developed by engineers, mainly working in the USA, such as Hafler, Borbeley and Bongiorno. However, the same symmetrical drive capability can be obtained more simply by the layout shown in Figure 8, first shown by National Semiconductors as an IC design, but used commercially by Hitachi in an audio power amplifier,

'Cascode' circuits

The other circuit tool available to the amplifier designer to increase bandwidth, reduce distortion, and isolate input from output, is the 'cascode' connection, shown for various bipolar transistor and FET combinations in Figure 9, and, once again, they can be inverted to use P-type devices if more convenient for the circuit. All these arrangements have the common advantage that the amplifier transistor (Tr1) operates into a low impedance, fixed voltage load, so there is virtually no feedback through the transistor. Also, since the cascode transistor (Tr2) is just a current amplifier, and feedback free, the stage will give a very high voltage gain, and a very low distortion if used with a high impedance load.

All the circuit layouts shown above are used by circuit designers, in various combinations, to produce very high

Fig.9 Various N-type cascodes

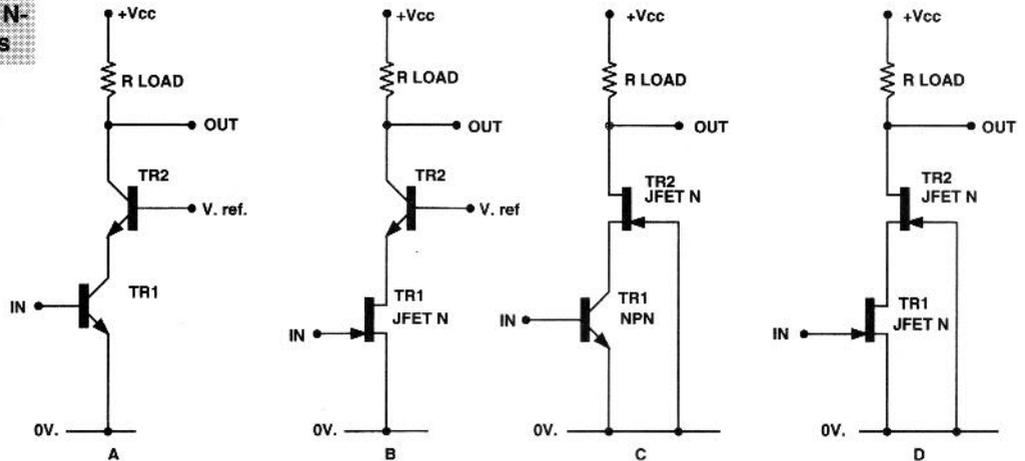


gain, low distortion gain blocks, and these have been used (in the position of 'A1' in Figure 1), as the basis for power amplifier designs, with some kind of impedance converting stage between the amplifier block and the LS output. Much patience is required to get these parts to live together.

Power amplifier design

As I have suggested above, the design of pre-amplifier stages, which are mainly just voltage amplifiers operating into resistive loads, is a pretty easy task, and a power amplifier - according to Figure 1 - is just a voltage amplifier with a pair of push-pull emitter follow-

ers hung on the end to reduce the output impedance to a low enough level for the system to be able to drive a loudspeaker adequately loudly. Unfortunately, this is where the real problems begin, and I'll look at these next month.

NEXT MONTH PROBLEMS, PROBLEMS, PROBLEMS.

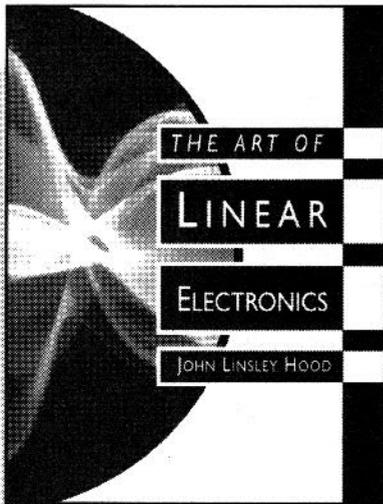

Drawing on the considerable expertise of the author, this practical handbook gives a complete working knowledge of the basics and technology of linear electronics.

- applications in audio, radio, instrumentation and television
- from thermionic valves to MOSFET transistors, quartz crystal oscillators to silver oxide button cells
- Information on material properties or conventions used

June 1993 400pp PAPERBACK
0 7506 0868 4 £16.95

A BEST SELLER FROM

BUTTERWORTH
HEINEMANN

QTY	Title	ISBN	Price
<input type="checkbox"/>	The Art of Linear Electronics	0 7506 0868 4	£16.95

Add £2.50 postage and packing

£2.50

Add VAT at local (see below)

TOTAL _____

VAT RATES:

6% Belgium; 25% Denmark; 5.5% France; 7% Germany; 1.2% Italy; 6% Netherlands;
5% Portugal; 3% Spain; 0% UK and Eire

FOR COMPANIES REGISTERED FOR VAT, PLEASE SUPPLY YOUR REGISTRATION NUMBER BELOW (Customers outside the EEC should leave this blank).

VAT Number:

I enclose a cheque made payable to Reed Book Services Ltd for £

Please debit my credit card - tick appropriate box:

Access/Mastercard Visa AMEX Diners Club

Card Number:

Expiry Date: /

If your credit card is registered at an address different from the one below please supply:

Name:

Address:


Signature Date:

T401ELXAO1

You may order by returning the form to:

Sam Hill, Butterworth-Heinemann, Linacre House, Oxford OX2 8DP
OR Tel: (0933) 410511 and quote ref: T401ELXAO1.

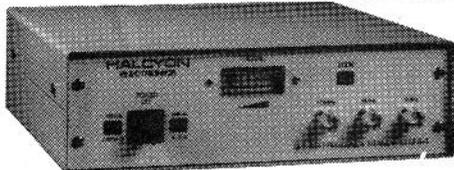THE DEFINITIVE 'OFF-AIR' FREQUENCY STANDARD



Still only
£195.+VAT
carriage extra

- * Provides 10MHz, 5MHz & 1MHz
- * Use it for calibrating equipment that relies on quartz crystals, TCXOs, VCXOs, oven crystals
- * Phase locks to DROTWICH (rubidium controlled and traceable to NPL)
- * For ADDED VALUE also phase locks to ALLOUIS (caesium controlled and traceable to OP - French equivalent to NPL)
- * British designed and British manufactured
- * Sine wave option of 10, 5 and 1MHz. Nominal 1V into 50 ohm
- * 13MHz option for G.S.M.

Output frequencies:
10MHz, 5MHz, 1MHz
Short term stability: better than 1×10^{-8} (1sec)
Typical: $= 4 \times 10^{-8}$ (1sec)
Long term: Tends to 2×10^{-8} (1000sec)

IDEAL BEGINNERS SCOPE, SCOPEX 4S6/AQUILASCOPE 6MHz SINGLE TRACE, INT/EXT TRIG, TRACE LOCATE, BRIGHT LINE AUTO, 10mV SENSITIVITY, 1µS-mS/cm, etc. £95

PHILIPS PM3085 10MHz DUAL TRACE & T/B	£750	LEADER LCG396 NTSC COL. PATT. GEN.	£395
LEADER L80-9C ALIGNMENT SCOPE	£195	UDI2026 SONAR SCANNER, SURFACE UNIT	£975
AVO 8's Mk.2.5.6.	FROM £55	TEK 834 PROG. DATA COMMS. TESTER	£295
PHILIPS PM3232 10MHz DUAL TRACE	£185	7SEG 12" x 9" DISPLAYS DIGITEX/SIGNALEX	£15 & £10
TELEQUIPMENT D67 25MHz DUAL TRACE DEL T/B	£195	RADIOMETER BKF6 DIST. METER 20Hz-20KHz	£95
GOULD DS255 15MHz DUAL TRACE	£195	CITOH C6800 6PEN 44 PLOTTER, CENTRIS/32	£135
TELEQUIPMENT D61A 10MHz DUAL TRACE	FROM £90	GENERAL RADIO 1531A XENON STROBOTAC	£79
IWATSU SS5116 DUAL TRACE 10MHz	£175	BACHARACH MV2 MERCURY SNIFFERS	£69
TELEQUIPMENT D1011 10MHz DUAL TRACE	£165	FISONS FI-MONITORS LIQ LEVEL SENSORS	£85
TEKTRONIX 2215 60MHz DUAL TRACE DEL T/B	£450	JAQUET TIMER 1110secs RES'N 0.01s	£59
TEKTRONIX 453A 50MHz DUAL TRACE DEL T/B	£249	COMMODORE PETS. D/DRIVES, PRINTERS	£29 ea
H.P. 8405A VECTOR V/METER 1GHz	£385	COMARC 2305 MV SOURCES, DUAL RANGE	£49
PLESSEY TCT10 SIG GEN/ANAL. 30-300 BDS	£95	INTRON IF6422 FUNC GEN 0.1Hz-2MHz	£125
TELEQUIPMENT D67A 25MHz 2T DEL T/B	£215	GOULD 2400 APEN CHART RECORDER	£149
HITACHI VC 6015 10MHz DIGITAL STORAGE	£295	X-Y RECORDERS A3 & A4	FROM £35 TO £139
HP1340A X-Y DISPLAYS	£149	PHILIPS PM6456 FM STEREO GENERATOR	£195
DEPTLING V20 SINGLE PAN BAL 0.1mg/200g	£69	MARCONI TF2300 FM/AM MODULATION METER	£195
ANALYTICAL BALANCES WITH WEIGHTS 250g	£99	MCKENZIE 7DAY TEMP/HUMIDITY RECORDER	£95
VACUUM PUMPS 1.5 & 2.8m ³ /hr	£125 & £149	FEEDBACK SOS603 1MHz SINE/SQUARE OSC	£125
KINGSHILL NS1540 15V 40A PSUs CASED, AS NEW	£195	FARNELL E350 0-350V 100mA, 2 x 6.3V	£59 TO £69
ACRON 402P SYNC PULSE GENERATOR & 60SP ENCODER	£375EA £695/pr	COMMUNICATIONS RECEIVERS, HF,LF,VHF	POA
MARCONI TF2304 AM/FM MOD METER PORTABLE	£249	LCR BRIDGE WAYNE KERR CT492	£79
MARCONI TF2330 WAVE ANALYSER 20Hz-50KHz	£149	LCR O BRIDGE AVO B151	£195
H.P.5316A 1GHz/CTR, OPTS 1,2 & 3	£595	LCR BRIDGE MARCONI TF2700	£195
LEVELL TM6B MICRO V-METER 450MHz	£95	LCR BRIDGE MARCONI TF 2701	£125
LEVELL TM3B MICRO V-METER 3MHz	£85	LCR MARCONI TF1313 0.25%	£95
		LCR COMPONENT COMPARATOR AVO CZ457/S	£95

LIST AVAILABLE BUT 1000'S OF UNLISTED BARGAINS FOR CALLERS. ALL PRICES EXC. OF P & P AND VAT
QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED




HALCYON ELECTRONICS



423, KINGSTON ROAD, WIMBLDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383. FAX 081-542 0340

READY NOW

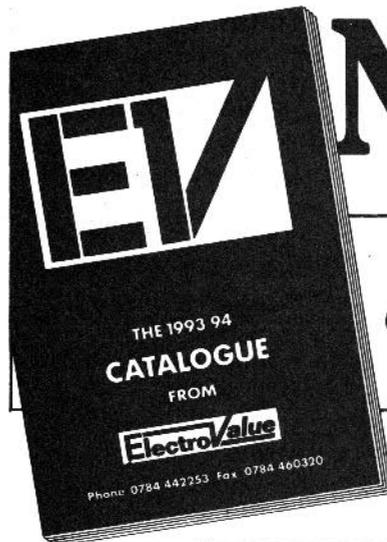

Every keen constructor needs it

THE 1993-94

ElectroValue CATALOGUE

Profusely illustrated, this 140+ page A4 size catalogue packs a wealth of information on items from the highly sophisticated to modest but essential screws, washers and wire, etc. With 28 years in personal mail Order service we know how much you rely on quality of goods above everything plus back-up service from the supplier i.e. Electrovalue. We've got the catalogue you want *and we deliver the goods*

To get your Catalogue

Send cheque or posts / order for £1.50 to address on coupon or phone your Credit Card No. & its expiry date. Catalogue comes with two £1 vouchers, each for spending with orders value £10 or more.

*Shops at

Egham, Surrey
28 St. Jude's Road, Englefield Green.
Tel: 0784 434757.

Burnage, Manchester
680 Burnage Lane
Tel. 061 4324945.

*PERSONAL SHOPPERS, NOT MAIL ORDER

DISTRIBUTORS FOR

SIEMENS

PROFESSIONAL
ELECTRONIC
PRODUCTS

●
SEMICONDUCTORS
OPTO-ELECTRONICS
FERRITES
CONNECTORS
SWITCHES
CAPACITORS
INDUCTORS
etc.

ELECTROVALUE LTD., UNIT 3, CENTRAL TRADING ESTATE,
STAINES, MIDDX. TW18 4UX

Tel: 0784 442253 Fax: 0784 460320

Your 1993/94 Catalogue please, to

Name

Address

Block letters please, and POST CODE

I enclose a cheque/postal order for £

AE1

If not using this coupon please quote this journal when writing



DELCLIA

THE TRANSMITTER PEOPLE

4 WATT PPO FM BROADCAST (Built)

TRANSMITTER: with Low Pass Filter

Modulation 75KHz Wide Band

Range up to 4-2 miles

Supply 10-16 Volts AC/DC

Current 250mA

Audio Input 100mV (ADJ)

Frequency range 88-108MHz FM

Stability ± 20KHz

Size W. 70mm, D. 90mm, H. 50mm.

MANY USER CONTROLS Price: £23.50

7 WATT PPO FM BROADCAST

(Built) TRANSMITTER: Higher Watt

Version of above Transmitter

(Range 7 miles) **Price: £52.50**

KIT: 3 WATT TRANSMITTER 80-108MHz

Coil Tank Controlled up to 3 miles range.

Supply 12V dc at 0.5 amps **Price: £12.50**

ALL PRICES INCLUDE VAT
PLEASE ADD £1 P&P PAYMENT WITH
ORDERS TO:

DELCLIA ELECTRONICS,
14 ST. MERYL PARK, GLEN ROAD,

BELFAST, BT11 8FY. Tel: (0232) 611995

Please send two 1st class stamps for our catalogue.



Under Pressure

What's compact, easy to build and flattens you before giving you a boost?
An Audio compressor
by Daniel Coggins

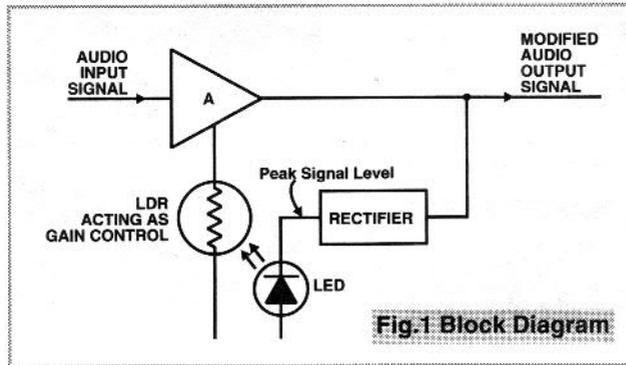


Fig.1 Block Diagram

It is also partly responsible for giving disc jockey's their 'magic' voices! The disadvantage of this is to reduce the 'light and shade' of the sound to the extent that one could argue that it becomes 'flat' and synthetic.

However, in broadcasting it is usually necessary to employ compression to protect transmitters from large signal peaks, though BBC Radio 3 uses much less compression than say, Radio One or Capital radio. When recording, compression can be used to get 'optimum' recording levels (as on some cassette players) or to 'tighten up' the sound of percussive or stringed instruments.

Design Considerations

This design was a result of some experimentation to produce a compressor with a suitable response that could be used with stringed amplified instruments in

Most readers with an interest in audio or electronic music will already be familiar with compressors. Basically a compressor (or 'sustain' unit as it sometimes gets called in the context of musical instruments) is used to flatten out signal peaks, as well as boosting the amplitude of low level signals. This effectively reduces the

signals' dynamic range and gives the effect of making the signal sound subjectively louder, due to its higher average level.

This effect is frequently used in broadcasting for making advertisements 'stand out' and also as general signal conditioning to make certain daytime radio stations appear louder than others.

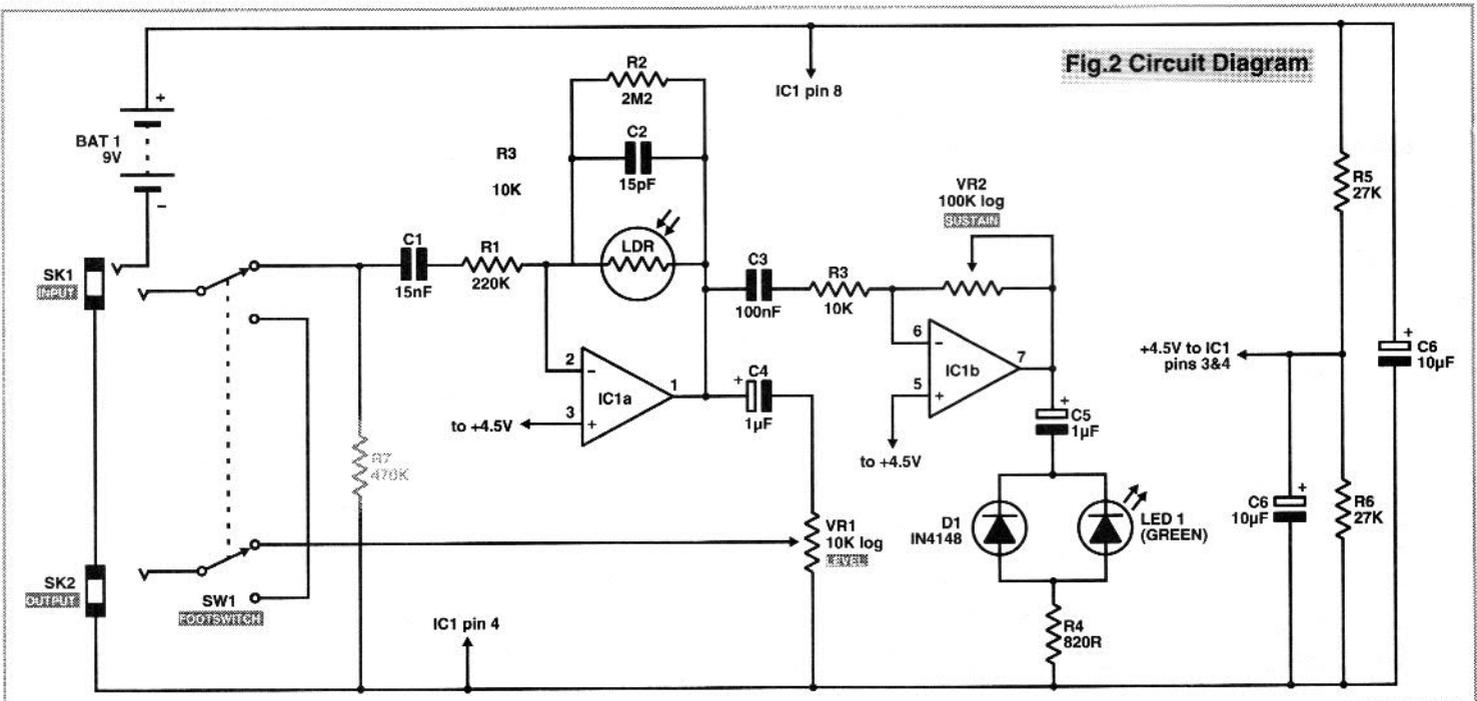


Fig.2 Circuit Diagram

The Works

Let us first look at what a compressor basically does, electronically speaking.

An audio signal (see Figure 1) is fed into an amplifier and the output of this amplifier is fed to a 'side chain' where the average peak level is detected (rectified) and used to control the gain of the aforementioned amplifier.

The final signal is then taken from this amplifiers' output. Various methods of controlling the amplifier exist: by using isolating transformers, or FET's as voltage controlled resistors - or by using an optical coupler, a nice solution which is used in this design. The great advantage of it is the minimal noise due to isolating the DC control voltage from the audio path.

So, if we feed a low level signal into the amplifier, the average peak level will be very low so the LED will not shed much light onto the LDR (light dependent resistor). Consequently, the amplifier will have high gain and will boost the low level to a much higher one, that is, until the peak level is sufficient to light the LED and effectively reduce the amplifiers gain, and so maintain a constant output level. The opposite process takes place for very loud signals.

It is possible to adjust the threshold at which these changes occur, simply by adjusting the amount of voltage to the LED. Because there is plenty of available gain, a level control/attenuator at the output is provided to enable the effect to be set to a wide range of levels. The attack and decay times

are somewhat a function of the threshold in this circuit, and so it is best to call the control a 'sustain' control.

'Sustain' is often associated with the compression of notes from musical instruments, because with a guitar for instance, the note reaches a peak amplitude very quickly and then rapidly dies away to a much lower level. Using a compressor can make the note have a constant amplitude by inherently compensating for this. However, the note does die out eventually, as the compressor will only sustain a signal as long as it is there - and a guitar string does not provide a signal when it has ceased to vibrate. If infinite sustain is what you want - then use acoustic feedback in conjunction with a compressor.

order to 'thicken up' the sound and still retain the natural attack of the notes. Of equal importance was the release time which was tailored to be near-instantaneous in order to facilitate fast passages of notes or quick rhythms.

Other applications of this simple but effective design will be considered later, but as it stands it is intended for use with electric guitars, or electric basses - where it works very well. Using just one dual op-amp with an optical link and a few other parts, this has to be one of the simplest designs ever, but the noise spec. is quite reasonable, as is the current consumption.

Circuit Description

SK1 is a stereo 1/4" socket configured to switch the 9V battery into the circuit when a jack is inserted. The supply goes to IC1 - a dual JFET low noise op-amp - and is decoupled by C7. This 9V rail is potential divided to 4.5V by equal value resistors R5 and R6, decoupled by C6 and provides an operating point for both op-amps non-inverting terminals.

The footswitch SW1 is used to bypass the circuit if so desired and does so by either connecting both 'in' and 'out' sockets together or by routing the signals through the circuit.

C1 couples the input signal via R1 to IC1a. This gives the circuit an input impedance of 220K - fine for the majority of guitar pickups. R2 assigns a maximum gain of 10 (20db) to this inverting amplifier stage. LDR1 is a miniature light dependant resistor whose resistance is extremely high in dark conditions

(several megohms), and this resistance will decrease linearly as light levels increase (see Figure 3b). This varying resistance modifies the overall gain of the amplifier stage formed by IC1 - by connecting it in parallel with feedback resistor R2. C2 is used here to prevent RF breakthrough at high gain (which prevents the circuit from functioning properly - it is also very annoying!), and the chosen value gives high frequency roll-off progressively with increasing gain. This is an important consideration, as the noise level obviously increases as the gain of IC1a increases for low input

levels (and zero level) and is predominantly heard as hiss, which is largely eradicated by this capacitors' inclusion.

The output of this stage is coupled to the footswitch via C4 and VR1 - the level control - and also through C3 and R3 to IC1b - another inverting amplifier with a variable gain of up to 20dB. However, the purpose of this stage is to raise the signal to a large enough level to drive the LED. C5 couples the audio signal to LED1 but (most importantly) is half-wave rectified by D1. Current limiting is provided by R4. The LED glows with proportion to the average

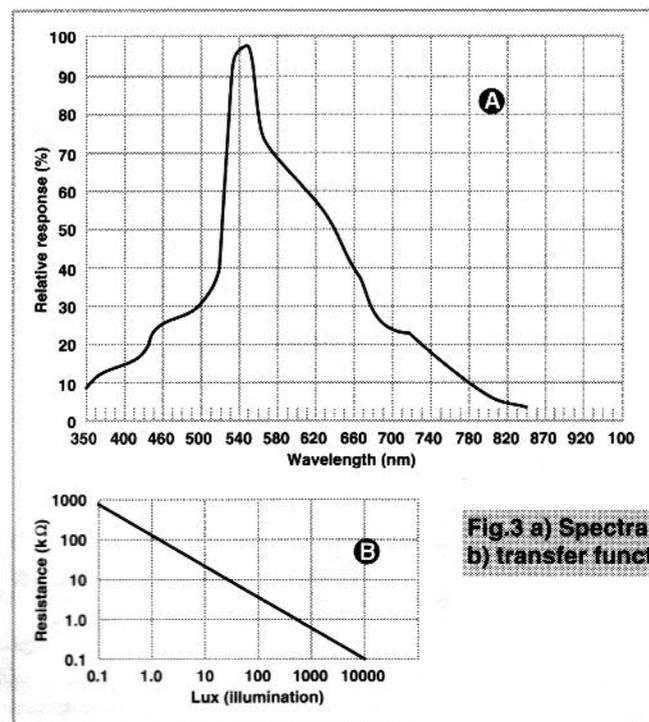
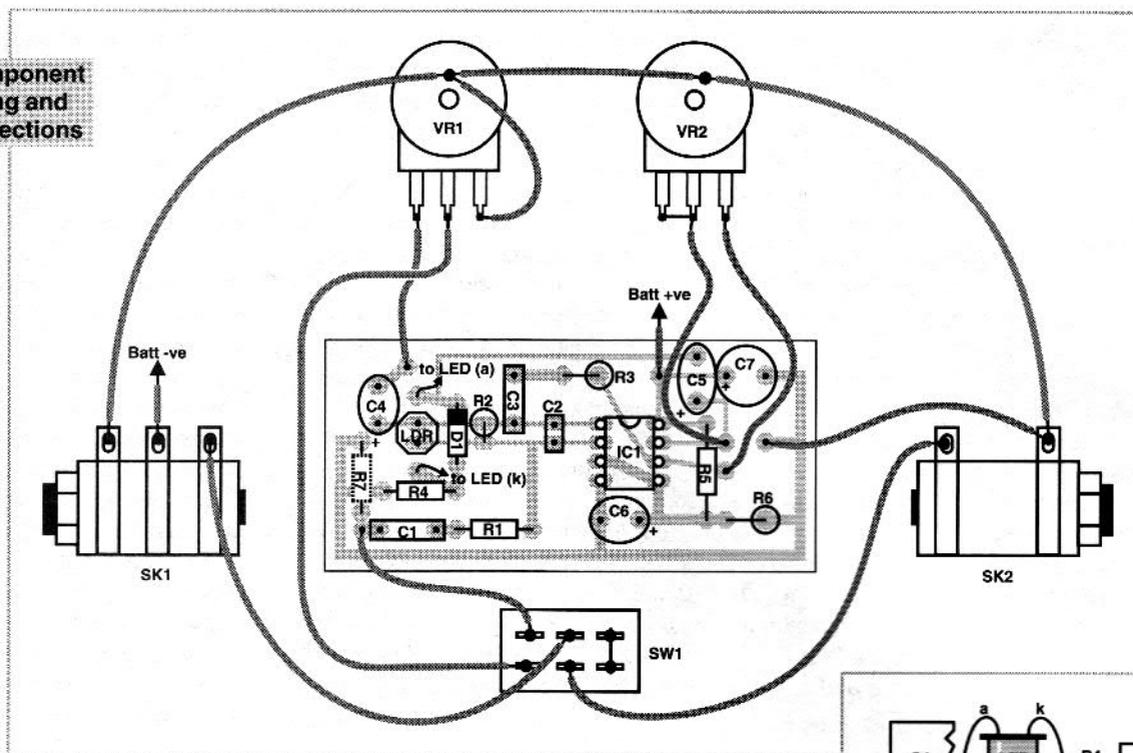


Fig.3 a) Spectral response
b) transfer function of LDR

Fig.4 Component positioning and interconnections

peak signal level fed to it, and just how much of this level is determined by the setting of VR2.

By placing the LED so that its lens is illuminating the LDR's active face, the circuit will now operate as a compressor.

Why a GREEN LED? Because if we look at Figure 3a, we will see that the best spectral response for this particular LDR is about 550nm - which is approximately the wavelength of green light. Which goes some way to suggesting that red and yellow LED's will not give suitable results here, as their wavelengths are far outside of the LDR's peak spectral response. If only I'd known this when I threw away all those 'faulty' ORP 12's when I couldn't get them to work with red LED's!

Construction Details

Using the PCB available from EIA, check that it fits into the guide slots in the specified case. Then, in accordance with Figure 7a solder all the resistors and capacitors and D1 onto it, being careful to check polarities. Solder in IC1 and then the LDR - take great care not to overheat this sensitive component.

Figure 7b shows how the LED is mounted upside down so that it looks directly at the LDR. Take care when bending the leads, leaving about 5mm clearance from the LED case. Again, be sure to get the LED polarity correct!


Once satisfied that the PCB is complete, connect it to the remaining com-

ponents as shown in Figure 4 - use some screened cable for connection 6 and connect one end of the screen to the case, to keep the noise down.

Drill out the case as shown in Figure 5 and use rub-down letters to label the controls/switch/sockets.

Several coats of clear lacquer will ensure that these words remain visible after rough handling - this is a foot-operated device!

Assemble the finished unit by putting the 'guts' into the case (neatly, of course!) and furnishing it with a fresh PP3 and a little foam rubber to prevent

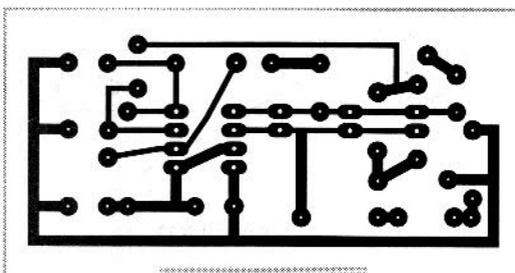
**Fig.5 Foil Pattern**

any internal movement in use.

Testing and Use

Connect an ammeter between battery negative and case - it should read around 4-5mA. Gross deviations from this figure suggest that you should go back and check for any mistakes....

It might be worth pointing out that as this unit features a light dependant component that a light - proof case is essential for proper operation, but before you put on the lid plug your instrument into the input socket, turn up VR2 fully, dim the lights and make a few sounds -

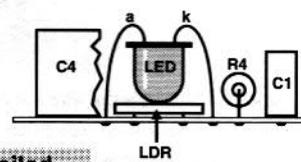**Fig.4b Detailed positioning of the LED and LDR**

you should see the LED glow in harmony with you! If not, then press SW1 or check the LED's polarity again. Make sure it is at 90 degrees to the PCB. Assuming all is well, fasten the lid to the case, connect up to your amplifier and pluck a single note. It should be possible to hear the compression effect, but bear in mind that on low settings it will be quite subtle - and if SW1 is in the wrong position the thing will sound as normal, because it is!

Try playing soft and loud alternately - and slowly and quickly to appreciate the effects of compression. Higher settings of the 'sustain' control will give more dramatic compression and will require a corresponding high setting of the 'level' control. Low settings of sustain (up to around mid-way) will give a limiting effect, 'squashing' signal peaks, but not affecting the quieter signals as much. The 'squashed' sound can be quite expressive, especially as the LDR responds sluggishly at low signal levels and quite quickly at higher light levels. This is how it preserves the attack of the notes. This non-linearity gives the unit a sound not dissimilar to the old valve compressor/limiters of the 60s, and as such is quite subjectively pleasing.

As with any effect that can produce

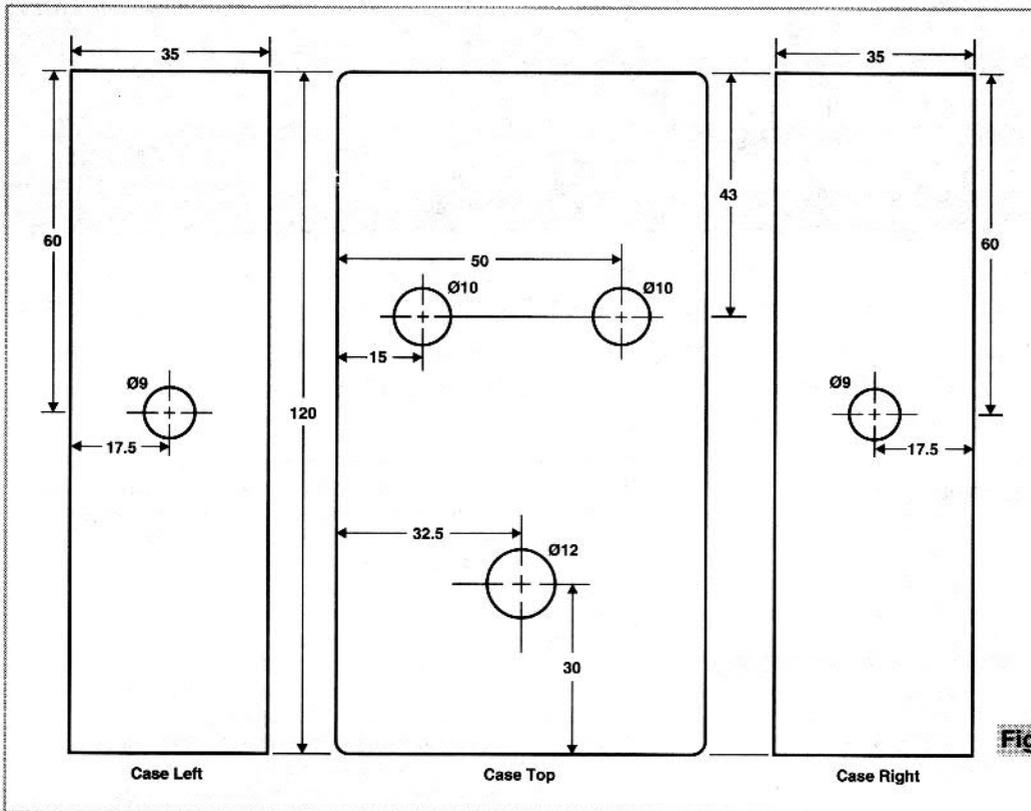


Fig. 6 Drilling Details

high gain levels it is best to put it as close to the beginning of the signal chain as possible (i.e. the guitar), in order to avoid excessive noise. Remember that a compressor always seeks to amplify low level signals and will interpret noise as a signal, too.

Afterthoughts

It may be of interest to note that this design was largely the result of trial and error and the component values were chosen as a result of subjective listening tests. For instance, the value of C3 in conjunction with R3 gives significant bass roll-off as far as the side chain is concerned, resulting in greater compression at mid to high frequencies. The net

result of this, particularly with a bass guitar is to reinforce the strength of lower notes, with slightly greater dynamics than for higher notes or harmonics. If you wish to try different values here or, for instance C5 / R4 / R2 / C2 / R1 / C1, feel free to do so - it is in this way that you can make the sound work for YOU. Audio *is* subjective and of course so is music, but technology and all the rules and equations that it carries with it must only be a means to an end. Avoid 'paralysis by analysis' and experiment!

In a simple circuit such as this, there is a lot going on interactively, which can lead to more complex and interesting results. Should the footswitch in this

design produce any 'clicks' or 'thumps', connect a 470K resistor (R7) shown as dotted on the overlay, between C1 (switch side) and ground - this should minimise it.

By combining this design with that of last months' A-B BOX you can make a compressor with greater reliability, quieter and with LED status indicators.

You may wish to modify the side-chain by simply connecting a large capacitor across LED1 to modify the release time for putting say, speech or music through this unit - but that is somewhat crude and would best be expanded upon..... over to you!

Reference

RS data sheet F14188

Resistors

(all 1/4W 5% carbon)

R1	220K
R2	2M2
R3	10K
R4	820R
R5,6	27K
R7	470K optional
VR1	10K log potentiometer
VR2	100K log potentiometer

Capacitors

C1	15n mylar/polyester
C2	15p ceramic plate
C3	100n mylar/polyester
C4,5	1µ/16V radial electrolytic
C6	10µ/16V radial electrolytic
C7	47µ/16V radial electrolytic

Semiconductors

IC1	TL072 Dual J/FET OP AMP
D1	1N4148 silicon diode
LED1	Green Low Current 5mm LED
LDR1	Light Dependent Resistor type NSL 19 - M51 (RS stock No.596 - 141)

Additional Components

B1	PP3 9V battery and clip
SK1	stereo 1/4" skeleton jack socket
SK2	mono 1/4" skeleton jack socket
SW1	heavy-duty DPDT footswitch
Die cast box - 120 x 65 x 40 mm (bimbox type 5004)	
PCB (see page 61)	
Solder/wire/screened cable	
rub-down letters/spray lacquer	
Knobs to suit VR1	
Foam rubber anti-slip base	


Parts

Buying Tips

The LDR can be obtained from ELECTROMAIL (RADIO SPARES mail order subsidiary - Tel. 0536 204555. The footswitch and diecast case can be obtained from Maplin (order codes FH93 and LH71 respectively)

POWERFUL SCHEMATIC CAPTURE, PCB DESIGN AND AUTOROUTING ALL FOR JUST £395...

PROPAK AR provides all the features you need to create complex PCB designs quickly and easily. Draw the circuit diagram using the powerful facilities of ISIS DESIGNER+ and then netlist into ARES AUTOROUTE for placement, autorouting and tidy up. Advanced real time design rule checks guarantee that the final PCB will correspond exactly with the schematic thus saving you from costly layout errors and time consuming debugging.

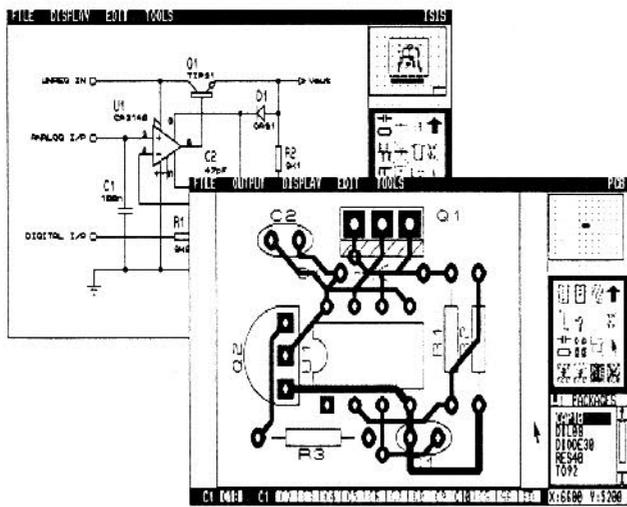

- Attractive, easy to use graphical interface.
- Object oriented schematic editor with automatic wire routing, dot placement and mouse driven place/edit/move/delete.
- Netlist generation for most popular CAD software.
- Bill of Materials and Electrical Rules Check reports.
- Two schemes for hierarchical design.
- Automatic component annotation and packaging.
- Comprehensive device libraries and package libraries including both through hole and SMT parts.
- User definable snap grids (imperial and metric) and Real Time Snap to deal with tricky SMT spacings.
- Manual route editing features include Auto Track Necking, Topological editing and Curved tracks.
- Autorouting for single, double and multi-layer boards.
- Non autorouting PROPAK is available for just £250 if you do not need or want the router.
- Full connectivity and design rule checking.
- Power plane generator with thermal relief necking.
- Graphics support to 800x600 Super VGA.
- Output to dot matrix and laser printers, HP and Houston plotters, Postscript devices, Gerber and Excellon NC machines plus DXF and other DTP file formats.

CADPAK Two Programs for the Price of One

ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

**Only
£79**


Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.

PCB II

High performance yet easy to use manual PCB layout package. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

Alan Chadwick writing in ETI (January 94) concluded... "At £79 I thought this was an excellent buy."

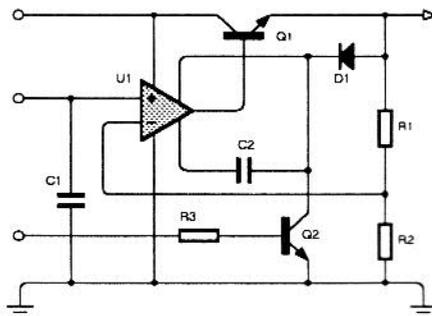ISIS ILLUSTRATOR Schematic Drawing for Windows



**From
£99**

Running under Windows 3.1, ISIS ILLUSTRATOR lets you create presentation quality schematic drawings like you see in the magazines. Furthermore, when the drawing is done, transferring it to another document is just a matter of pasting it through the Clipboard.

Now used by a number of prominent technical authors to illustrate their latest books and magazine articles.

Labcenter
Electronics



Call us today on 0274 542868 or fax 0274 481078 for a demo pack - state DOS or Windows. Multi-copy and educational discounts available.

Prices exclude p&p (£5 for U.K.) and VAT. All manufacturers' trademarks acknowledged.

14 Murriner's Drive, Bradford, BD9 4JT.

Inverter toroidal transformers 225VA
 10.5-0-10.5 primary 0-260-285 secondary £ 29.95
LEDs 3mm or 5mm red or green 6p each
 yellow 11p each
 High intensity red, green or yellow 5mm 30p each
 cable ties 1p each £5.95 per 1000 £49.50 per 10,000
High quality photo resist copper clad epoxy glass boards
 Dimensions single sided double sided
 3x4 inches £1.09 £1.55
 4x8 inches £2.75 £2.99
 6x12 inches £6.20
 12x12 inches £12.25

Rechargeable Batteries
 AA (HP7) 500mAh £0.99
 AA 500mAh with solder tags £1.55
 AA 700mAh £1.75
 C (HP11) 1.8AH £2.20
 C 2AH with solder tags £2.60
 D (HP2) 1.2AH £2.60
 D 4AH with solder tags £4.95
 PP3 8.4V 110mAh £4.95
 1/2AA with solder tags £1.55
 Sub C with solder tags £2.50
 AAA (HP16) 180mAh £1.75
 1/3 AA with tags (philipsCTV) £1.95
Standard charger charges 4 AA cells in 5 hours or
 4Cs or Ds in 12-14 hours + 1xPP3 (1,2,3or4 cells may
 be charged at a time) £5.95
High power charger as above but charges the Cs
 and Ds in 5 hours AAAs Cs and Ds must be charged in
 2s or 4s £10.95
Nickel Metal Hydride AA cells high capacity with no memory.
 1000mAh £3.85
 1200mAh £4.40
Special offers please check for availability
 F cells 42x 16mm dia 1.2v £1.45
 Stick of 4 171mmx16mm dia £5.95
 with red & black leads 4.8v £5.95
Computer grade capacitors with screw terminals
 38000uf 20v £2.50 87000uf 10v £1.95
 68000uf 15v £2.95 10000uf 16v £1.50
 58000uf 60v £4.95
 7segment common anode led display 12mm £0.45
 LM2931ATS 0 low drop out 5v regulator £0.85
 TO220 package £0.85
 7812 and 7912 12v 1A regulators £26.00 per 100
 LM337k TO3 case variable regulator £1.95
 GaAs FET low leakage current S8873 £12.95 each
 £9.95 10+ 7.95 100+
 BS250 P channel mosfet £0.45
 BC559 transistor £3.95 per 100
 74LS05 hex inverter £10.00 per 100
 used 8748 Microcontroller £3.50
 SL952 UHF Limiting amplifier LC 16 surface
 mounting package with data sheet £1.95
 AM27502 1.25 each 90p 100+
 CD4007UB 10p 100+ 8p 1000+
 Sinclair light gun terminated with a jack plug and PP3
 clip gives a signal when pointed at 50hz flickering
 light with output wave form chart £ 3.95
DC-DC converter Reliability model V12PS 12v in 5v
 200mA out 300v input to output isolation with data
 £4.95 each or pack of 10 £39.50

Hour counter used 7 digit 240v ac 50 Hz £1.45
QWERTY keyboard 58 key good quality switches new £5.00
 Airpax A82903-C large stepping motor 14v 7.5' step
 27ohm 68mm dia body 6.3mm shaft £8.95
 or £200.00 for a box of 30
Polyester capacitors box type 22.5mm lead pitch
 0.9uf 250vdc 18p each 14p 100+ 9p 1000+
 1uf 250vdc 20p each 15p 100+ 10p 1000+
 2.2uf 250vdc (27.5mm pitch) 30p each 20p 100+ 15p 1000+
 3.3uf 100vdc 30p each 20p 100+ 15p 1000+
 1uf 50v bipolar electrolytic axial leads 15p each
 7.5p 1000+
 0.22uf 250v polyester axial leads 15p each 7.5p 100+
 Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch
 32x29x17mm case 75p each 60p 100+
Philips 123 series solid aluminium axial leads
 33uf 10v & 2.2uf 40v 40p each 25p 100+
Philips 108 series 22uf 63v axial 30p each 15p 1000+
 Multilayer AVX ceramic capacitors all 5mm pitch 100v
 100pf, 150pf, 220pf, 10,000pf (10n) 10p each 5p 100+
 3.5p 1000+ 500pf compression trimmer 60p
 40 of 370vdc motor start capacitor (dielectric type
 containing no pcbis) £5.95 or £49.50 for 10
Welwyn W23 9W 120ohm 35p each 20p 100+
 680 ohm 2W metal film resistor 4p 100+ 2p 1000+
 Solid carbon resistors very low inductance ideal for RF
 circuits 270hm 2W, 680hm 2W 25p each 15p each
 100+ we have a range of 0.25w 0.5w 1w and 2w solid
 carbon resistors please send SAE for list
P.C. 400W PSU (Intel part 201035-001) with standard
 motherboard and 5 disk drive connectors fan and
 mains inlet/outlet connectors on back and switch on
 the side (top for tower case) dims 212x149x149mm
 excluding switch £26.00 each £138.00 for 6
MX180 Digital multimeter 17 ranges 1000vdc 750vac
 2Mohm 200mA transistor Hfe 9v and 1.5v
 battery test £12.95
 AMD 27256-3 Eproms £2.00 each 1,25 100+
 DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each
 40p 100+
 Disk drive boxes for 5.25 disk drive with room for a
 power supply light grey plastic 67x268x247mm £7.95
 or £49.50 for 10
 Hand held ultrasonic remote control £3.95
 CV2486 gas relay 30 x 10mm dia with 3 wire
 terminals will also work as a neon light 20p each
 or £7.50 per 100
 A23 12v battery for car alarms or lighters 75p each
 100+ £50.00 per 100
 All products advertised are new and unused unless
 otherwise stated. Wide range of CMOS TTL 74HC 74F
 Linear Transistors kits. Rechargeable batteries
 capacitors tools etc always in stock.
 Please add £1.95 towards P&P
 VAT included in all prices
 Callers welcome

JPG ELECTRONICS
276-278 Chatsworth Road
Chesterfield S40 2BH
Access/Visa Orders
(0246) 211202

Chelmer Valve Company
for
High Grade Audio Valves

Major Brands e.g Mullard, Brimar, Philips, GE (UK), GE(USA), etc.

A2900 GEC.....£12.00	GZ34 Mullard.....£10.00
E80F Philips.....£10.00	GZ37 Mullard.....£7.00
ECC81/CV4024 Mullard.....£6.00	6CA7/EL34 GE.....£9.50
ECC82/CV4003 Mullard.....£6.00	6L6GA Sylvania.....£7.00
ECC88 Mullard.....£6.00	6SN7GT Brimar.....£4.50
E88CC Mullard.....£8.50	6V6GT Brimar.....£4.00
EF86/CV4085 Mullard/GEC.....£8.50	12AT7WC Sylvania.....£6.00
EL84 Mullard.....£6.00	6146B GE.....£15.00
EL84 GE (USA).....£5.00	6350A GE.....£17.50
GZ32 Mullard.....£8.00	7581 GE.....£12.00
GZ33 Mullard.....£8.00	

PRE-AMP VALVES

ECC81/12AT7.....£5.00	ECC82/12AU7.....£4.00
ECC83/12AX7.....£5.00	ECC85.....£4.00
ECC88.....£5.00	EF86.....£4.00
E81CC (GOLD PIN).....£6.00	E82CC (GOLD PIN).....£6.00
E83CC (GOLD PIN).....£6.00	E88CC (GOLD PIN).....£7.00
E80F.....£9.00	E83F.....£5.50
6SL7GT.....£4.00	6SN7GT.....£4.20

POWER VALVES

2A3 (OCTAL) or (4pin).....£14.00	211.....£22.00
300B.....£50.50	811A.....£9.50
845.....£29.90	EL34/6CA7.....£7.50
EL84/6BQ5.....£4.00	

POWER VALVES - contd.

E84L/7189A.....£15.00	KT66.....£9.20
KT88.....£12.50	KT88 (GOLD Q).....£18.50
6L6GC.....£6.50	6L6WGC/5881.....£8.00
6V6GT.....£5.00	6146B.....£10.20
6336A.....£40.00	6550A.....£11.00

RECTIFIERS

GZ33.....£4.50	GZ34/5AR4.....£5.00
SU4G.....£5.00	5Y3GT.....£3.20
SZ4GT.....£3.50	SOCKETS
B9A (PCB).....£1.60	B9A (CHASSIS).....£1.60
OCTAL (CHASSIS).....£1.75	4PIN (UX4).....£3.00
4PIN (for 211 & 845).....£11.00	

PREMIUM: Our own BRAND from selected worldwide sources, processed in our special facility to provide low noise/hum/microphony Pre-Amp valves and Power Valves burnt-in for improved stability and reliability.

Add £1.00 per valve for matching if required.
 Plus Post & Packing £3.00 + VAT at 17.5% for UK/Europe.
 Send Fax order with cheque or credit card details to:
 Chelmer Valve Co., 130 New London Rd, Chelmsford, Essex CM2 0RG
 Tel: (0245) 265865 Fax: (0245) 490064

HERE TO STAY

SpiceAge for Windows, Level 1, £100 + VAT

We are offering a special version of SpiceAge for Windows to students and serious hobbyists. The version will analyse medium sizes of circuits and may be upgraded to the professional version for the price difference.

SpiceAge is the program used by professional circuit designers that lets you "breadboard" even before you plug in your soldering iron. It gives you quiescent DC voltages, frequency response curves and 'scope-like traces of your circuit ideas. Imagine how easy it is

to test new components and values without the risk of smoke! SpiceAge has a friendly editor that lets you tell it what components to put in your circuit and how to connect them. SpiceAge has a "lab" full of "test equipment" to let you inject signals and "probe" for voltages, currents, dissipations, dB gains, phase angle, group delay and power consumption.

Requires Windows 3.1 or higher. S.A.E. please for information pack or £5 for demonstration kit. ACCESS/VISA or cheque with order. Please state disk size. Those Engineers Ltd, Dept EA4 31 Birkbeck Road, London NW7 4BP. Tel 081-906 0155, Fax 081-906 0969.


Those Engineers Ltd

The screenshot shows the SpiceAge software interface with several analysis windows open:

- Output waveform:** Displays waveforms for 'Output waveform' and 'Input waveform'. A note says: "See what happens when you overdrive a common-emitter amplifier. Power taken from supply." It shows a peak-to-peak voltage of 2.34V and a frequency of 1.25K.
- Fourier:** Shows a frequency spectrum plot. A note says: "Fourier analysis shows the harmonics produced by overdriving the amplifier." It shows a fundamental frequency of 1.25K.
- Transient:** Shows a time-domain plot. A note says: "SpiceAge can simulate non-linear and linear circuits. This is a 555 wired as an oscillator." It shows a peak-to-peak voltage of 1.00V and a frequency of 3.14K.
- Digitizing cursor readout:** Shows a plot with a cursor indicating a value of 1.00V.

Cordless Audio

Part 1

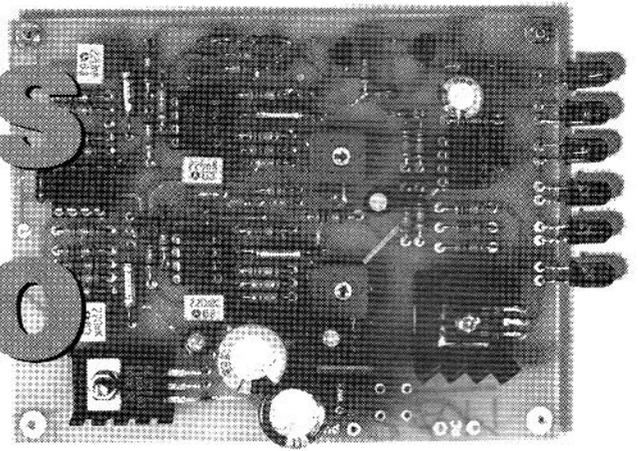

Andrew Armstrong helps us keep our neighbours friendly with his Infra red stereo audio transmitter

As Britain becomes more crowded, and newer housing is more cramped, the sound of heavy metal played through loudspeakers at high volume becomes less acceptable. Listening on headphones is a good answer, but the cable tends to get snagged and people trip over.

The answer is to use an infra red headphone link. Unfortunately the ones I have seen on sale are only mono, and intended for use with a television, so I have designed a stereo transmitter to use

with a hi-fi system. Obviously a direct cable connection will offer better sound, but the design here is intended to provide a good quality link for use when a cable is impractical.

Modulation

There are several ways to send sound information via infra red. The simplest is to modulate the brightness of the led directly with the sound signal. The most obvious disadvantages of this approach are that LEDs are not perfectly linear, that infra red in the environment will interfere directly with the signal, and that this method makes it difficult to provide stereo modulation.

The linearity problem can be solved by using pulse width modulation, but a much better answer is to learn from radio transmission standards and to

frequency modulate a high frequency carrier. This can be reasonably linear, and it avoids most interference problems. One example is infra red from a light source. It will contain 100Hz and near harmonics thereof which are far below any reasonable carrier frequency.

Stereo

A number of years ago I read that there was a Standard for infra-red stereo headphones which used 95KHz for one channel, and 250KHz for the other. I do not know if there are any infra-red headphones to this standard manufactured now, but in case there are I will use these frequencies in order to be compatible.

The frequency modulated carriers are provided by two voltage controlled oscillators. The LM566 is a reasonably

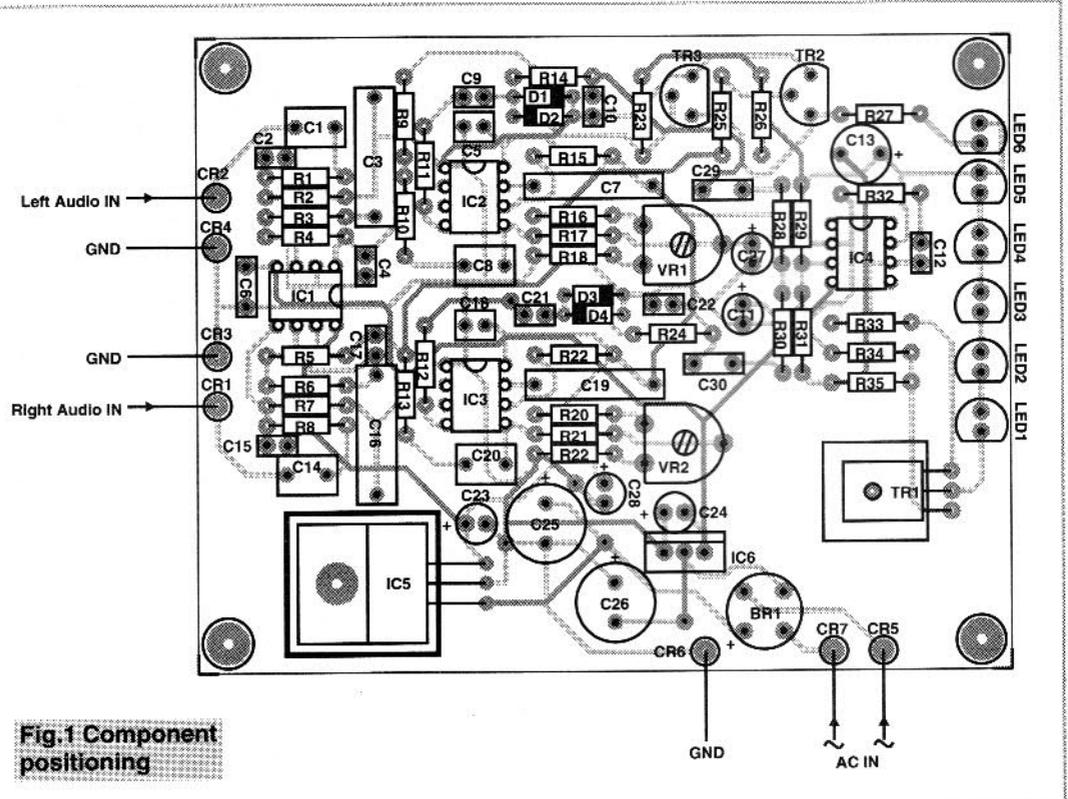


Fig.1 Component positioning

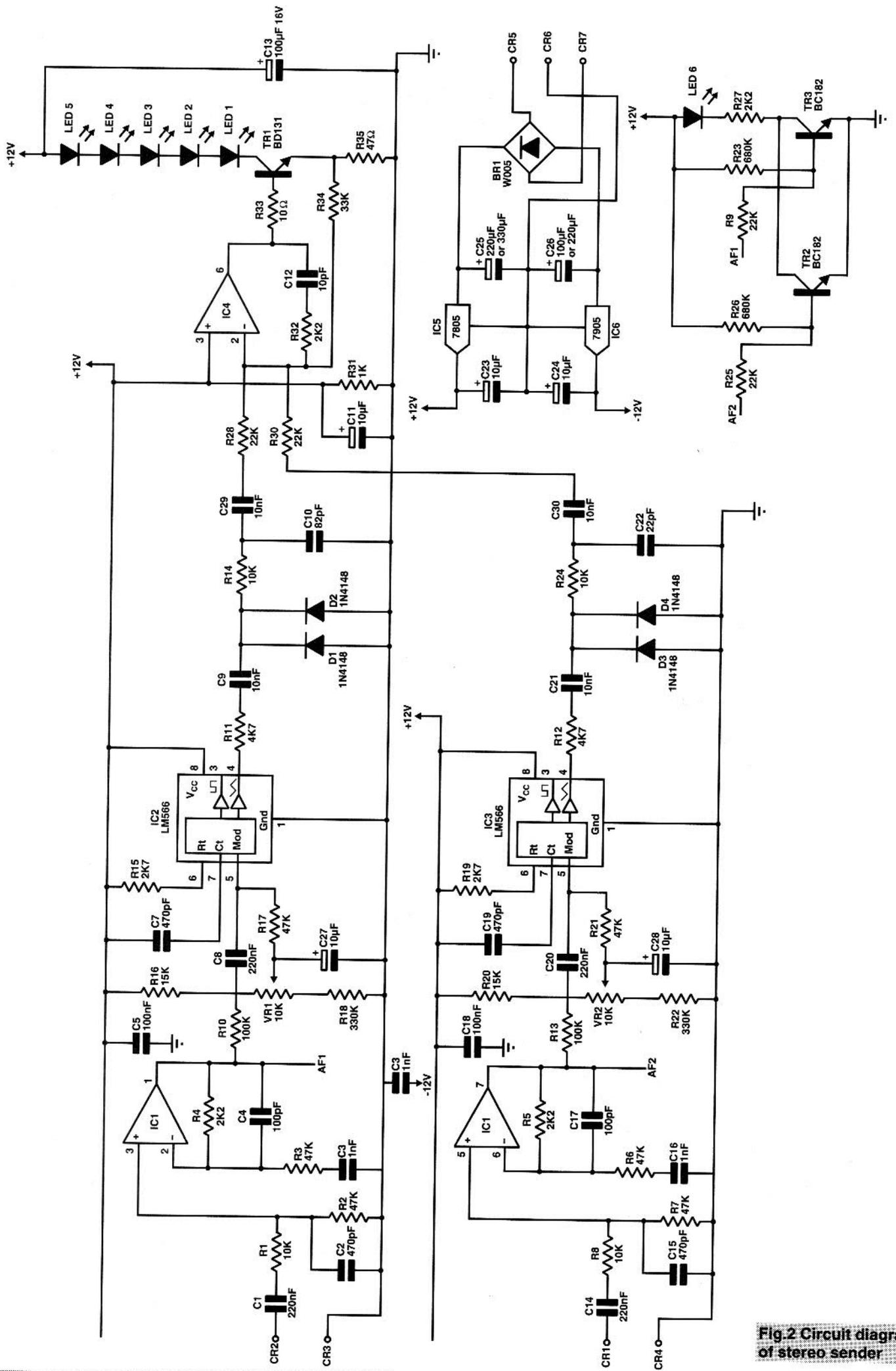


Fig.2 Circuit diagram of stereo sender

priced VCO which covers the required frequency range, and is available from Cirkit, so I chose that for this project.

One way to transmit the left and right signals would be to use two separate strings of LEDs, but economy and elegance suggested that a single string should be used. Simple square wave modulation was then ruled out because, if one modulating signal is on and the other off, should the LEDs be on or off? Linear addition of the squarewave drives might work, but experience has taught me that in a potentially non-linear system, in any situation where beats between frequencies or harmonics can occur, they probably will, and in so doing will spoil the performance of the system. Accordingly, I decided to generate sine-wave drive signals if it could be done without too much complexity.

The Signal Path

Starting at the input, for the left-hand channel, the audio signal is filtered to remove any RF which may be present, and fed to a low-noise op-amp which buffers the signal. The op-amp circuit also provides pre-emphasis to bring the high frequency content of the modulation more in line with the middle frequency content. De-emphasis can then be applied at the receiver, resulting in a lowering of the noise level.

This buffered output is fed to the modulation input of the VCO, via an attenuating network comprising R10 and R17. Because the left-hand side of R17 is decoupled to ground, it works as a potential divider with R10 at audio frequencies. The buffered signal is AC coupled rather than DC coupled to the

modulation input of the VCO, because the bias voltage on the modulation input is used to set the exact VCO frequency.

The triangle wave output from the VCO is fed via R11 and C9 to a pair of back-to-back diodes. The resistor value is chosen so that the diodes will gently round off the peaks of the triangle wave, and it is AC-coupled to make this work symmetrically. Some of the remaining harmonics are removed by the RC filter comprising R14 and C10. The resultant signal when displayed on an oscilloscope appears to be a good sine wave.

Signals from the two channels are added in the high frequency op-amp which drives the output transistor. The function of this stage is to vary the current through the light-emitting diodes linearly with the input signals, and tests show that it does this effectively. The



op-amp chosen for the job is unity-gain stable, but it cannot be guaranteed to be stable if its output is fed through a further active device before feedback is applied. Any instability will only manifest itself at frequencies of several megahertz, so the gain of the op-amp stage itself is reduced at frequencies well outside the operating range of the circuit by C12 and R32. As a further precaution to keep the circuit stable, a 10 ohm resistor is placed in series with the base of Tr1, to prevent oscillation caused by the strange and complex impedances which transistors can sometimes exhibit on their terminals.

This stage draws a significant current, so in order to avoid unnecessary disruption of the power supply voltage to the rest of the unit, local decoupling is provided by C13. The ground connection of C13 is directly routed to R35 on the PCB layout to avoid coupling output signals into an earlier part of the circuit via common ground resistance.

Ancillary Bits

On-board voltage regulators are provided in order to guarantee a clean power supply. Since the regulators are there anyway, the rectifier and smoothing capacitors are also fitted to the board, so the only extra component required is a mains transformer.

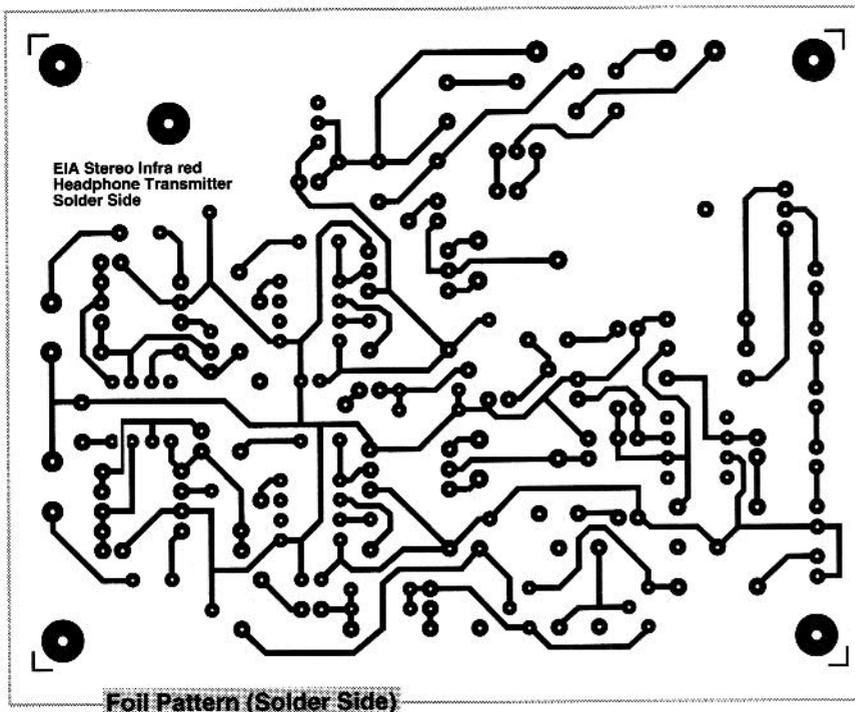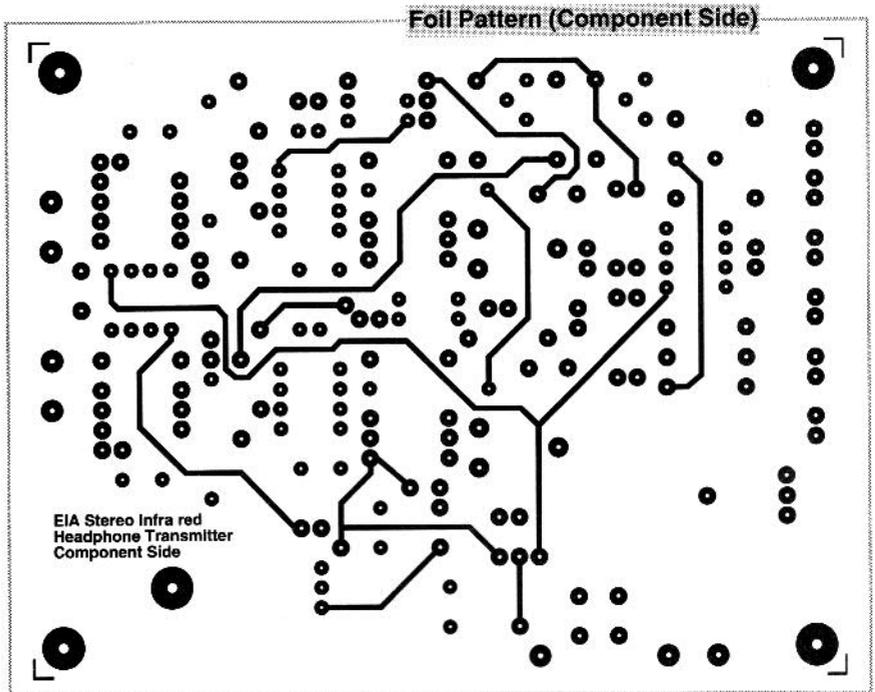An indication of the correct signal level for a reasonable modulation index is provided by the circuitry comprising Tr2 and Tr3. This circuit flashes the LED if either of the buffer amplifier outputs swings positive enough to bias the transistor On. Considering the left hand channel, Tr3 has some bias provided already by R23, so that a 200 millivolt positive excursion on IC1 pin 1




will serve to light the LED. Initial tests showed that this level of signal gave a reasonable amount of modulation, but should the indicator need to be changed, the value of R23 can be changed.

Assembly and Testing

The PCB for this project is double sided, and the first thing to do is to insert and solder the links between top and bottom of the PCB. Track pins are ideal, but bits of clipped component lead will do. Separate pin throughs are provided for components which obscure their top connections, but ones whose top connections are accessible should be top soldered.

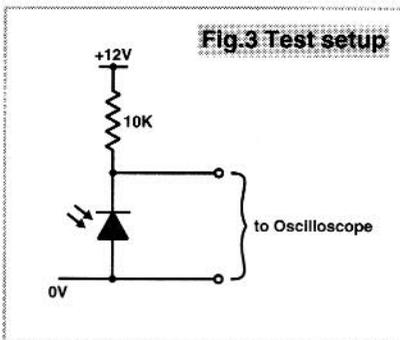Several IC connections are top soldered, which is not clear on the photograph of the prototype because I used sockets in developing this design. IC sockets are not easy to top solder, so I used the Multicore Copperset through hole plating system to make these connections.



If all the top soldered connections are made, the infra red LEDs are the only other item needing special attention. Their polarity is not obvious, and their illumination or otherwise cannot be seen. My solution to the problem was to set the lab power supply to 4V, and connect the infra red LED to the supply via a 1K resistor. Measuring the voltage across the LED indicates polarity, as the LED conducts at about 1.1V, but is capable of blocking 4V with no trouble.

When assembly is complete, test the power supply first, initially using a current limited lab power supply to feed +/-15V into the reservoir capacitors in case all is not well. Assuming that you measure +/- 12V on IC1, the next step is to set the frequency of the voltage controlled oscillators. Connect a frequency meter to pin 3 of IC2 and adjust RV1 to set the frequency to 95KHz. Then measure on pin 3 of IC3 and adjust VR2 for a frequency of 250KHz.

Without a receiver, further testing is limited. If you purchase the infra red diode which the receiver will use, then

Parts

R1,8,14,24	10K	
R2,4,5,7,17,21	47K	
R3,6,27,32	2K2	
R9,25,28,29,30	22K	
R10,13	100K	
R11,12	4K7	
R15,19	2K7	
R16,20	15K	
R18	390K	
R22	150K	
R23,26	680K	
R31	1K	
R33	10R	
R34	33K	
R35	47R	
VR1,2	10K preset	
VR3	10K log stereo potentiometer	
Capacitors		
C1,4,8,14,20	220n polyester	
C2,15	470p ceramic	
C3,16	1n polystyrene	
C4,17	100p ceramic	
C5,6,18	100n ceramic or polyester	
C7,19	470p polystyrene 2%	
C9,21,29,30	10n ceramic or polyester	
C10	82p ceramic	
C11,23,24	10µ radial electrolytic	
C12	10p ceramic	
C13	100µ 16V low esr electrolytic (eg Electromail part 105-903)	
C22	22p ceramic	
C25	220µ or 330µ 25V radial electrolytic	
C26	100µ or 220µ 25V radial electrolytic	
Semiconductor Devices		
D1,2,3,4	1N4148	
BR1	W005	
LED1,2,3,4,5	Infra red LEDs eg Electromail 635-296	
LED6	red LED	
TR1	BD131	
TR2, 3	BC182 or BC108 or similar	
IC1	NE5532	
IC2, 3	LM566 (available from CirKit)	
IC4	LM318	
IC5	7812	
IC6	7912	

Additional Items
 Heatsinks for TR1 and IC5
 M3 nuts and bolts for same
 Receiver diode for testing (and later use in the receiver) Electromail 195-574

you can test that the transmitter is transmitting by using the circuit of Figure 2 to detect the modulated waveform. This will only work close to the transmitting LEDs - the signal from the receiving diode will need a lot of amplification to work in the receiver.

Finally, if you connect the oscilloscope across R35, and apply a signal to each input in turn, you should be able to see the frequency of the waveform change. Then you will have got as far as is possible until the receiver is built.

The Receiver

As it stands, this is no use without a receiver. The receiver design will be published in Part Two. Currently I am torn between using a pair of phased-locked loops to demodulate the signals, or using a conventional FM detector, possibly using an IC intended for an FM radio. It may take more than a month to choose and design a good-enough system, and if the receiver design does miss the next issue, I apologise to those who have to wait for the following month.

the Alchemist

Part 2

Mike Meechan now gets to grips with this hi-fi pre-amp project

Last month, we looked at the mechanics involved in getting sound off the vinyl disc via the moving coil-type cartridge. This month, before unravelling the secret of The Alchemist, let us look at an enemy which is ever-present in all audio systems, that of noise.

Noise

Since any RIAA equalisation is done post-front end, as far as moving coil signal conditioning is concerned, it is a matter simply of straight amplification. Or is it...? Let us look closely at what is involved.

In any electrical system, and before we even think about man-made noise or interference, naturally-occurring noise lurks in there somewhere, even if it's below audible levels or above the audible upper frequency ceiling. We must appreciate a basic understanding of noise before any efforts can be made to minimise effects which it might have on an electronic system intended to amplify, with a great deal of integrity, a low-level signal which may indeed originate from a vinyl record groove. Many forms of noise are naturally-occurring, whilst others are man-made. Good design techniques, with judicious input filtering, shielding of sensitive areas of the circuit etc. can just about eliminate the effects of man-made noise. Naturally occurring noise, however, is another matter.

Where very low level signals, high amplification factors, and specific working impedances for optimum performance are required, the problems caused by noise worsen by a large order of magnitude. We're now going to look at the mechanics of noise, and what can be done about it before we put the theories into practise.

The Physics of Noise

Noise Figure and EIN

It can be illustrated using statistical mechanics and the laws of thermodynamics that resistors will contribute noise because of thermal activity. It is a naturally-occurring phenomena, and is generated irrespective of how perfect the

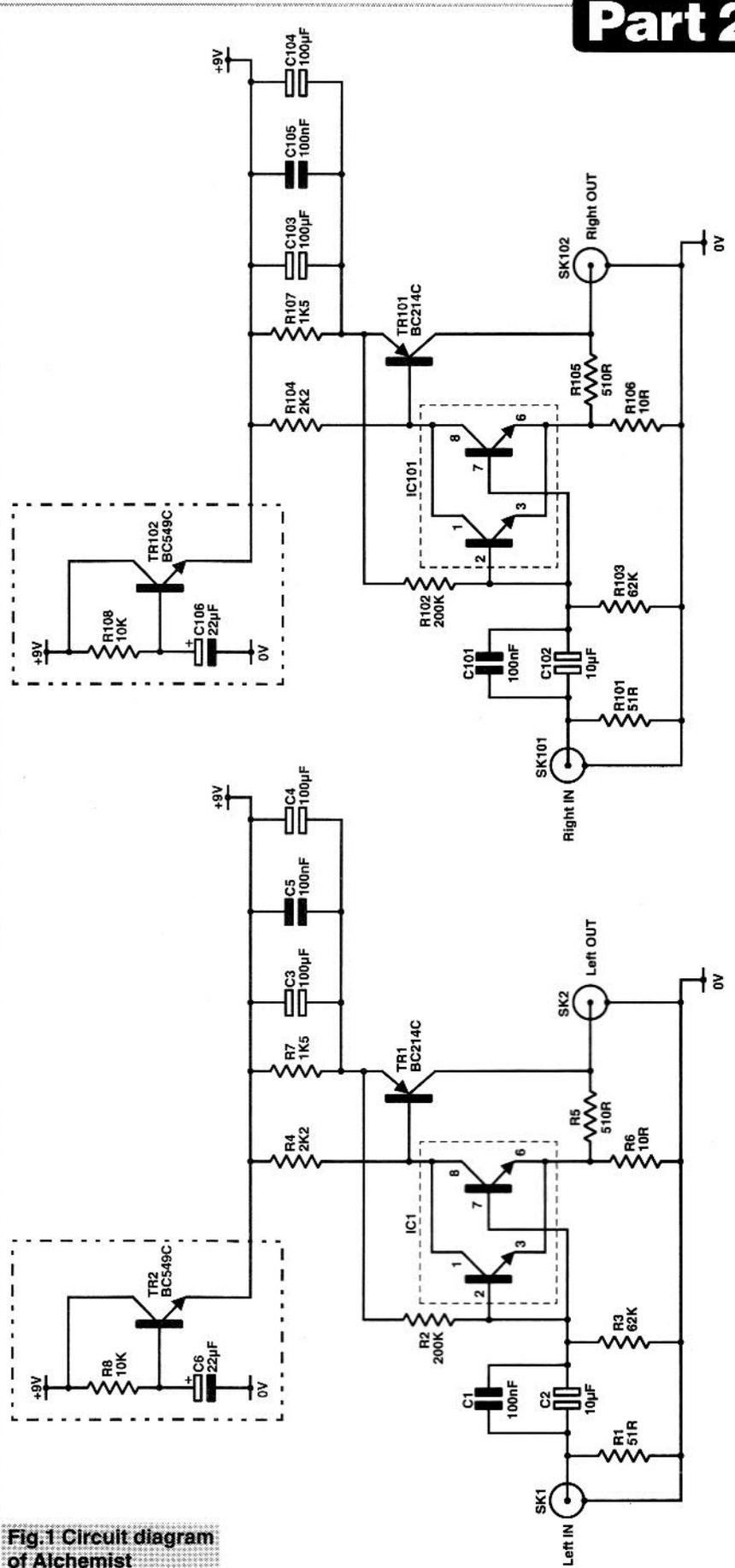


Fig.1 Circuit diagram of Alchemist

resistor is. Noise must be added to any signal dropped across a resistor, irrespective of the quality of the resistor. Since they are an integral part of amplifier design and application, it is as well to understand, from the onset, what physical limitations they place upon the absolute lowest value of noise which can be achieved from a given circuit.

Noise from resistance in series with the amplifier input is generated according to the following equation;

$$e_n = \sqrt{4KTBR}$$

where

K is Boltzmann's constant ($1.38 \times 10^{23} \text{ J/K}^{-1}$)

T is the absolute temperature in **K**, and is typically quoted at room temp (290K)

B is the noise bandwidth in Hertz

e_n is the amplifier noise voltage V/√Hz

R is the resistance in ohms

The coil resistance of a moving magnet cartridge is around 500R, (although it can be as much as 2K) while the moving coil's is around a tenth of that, although some have resistances as low as 5R. The noise voltage is normally quoted in nV/√Hz. The value of a 50R resistor is calculated as shown below;

$$E_n = \sqrt{4KTBR}$$

$$= 4 \times 1.38 \times 10^{-23} \times 298 \times 50 \times 20 \times 10^{23} \\ = 128 \text{ nV}$$

This figure is known as the thermal noise or so-called Johnson Noise, named after J.B. Johnson who first explained it in 1928 when he presented his paper, 'Thermal Agitation of Electricity in Conductors'. The significance of Johnson noise is that it sets a lower limit on the noise voltage on any signal source or amplifier having resistance.

Another naturally-occurring, irreducible form of noise is 'shot noise', which is caused by statistical fluctuations in the current. When referred to the standard reference level of 0.775V (0dBu), noise from a 500R resistor (moving magnet cartridge) is as follows;

$$20 \log \frac{0.775}{128 \times 10^{-23}} \\ = -135.6 \text{ dBu}$$

Unfortunately, when the input signal is amplified, so is the noise, and if the ratio of signal power to noise power is the same at the output of the amplifier as at the input, it is said to be 'noiseless'. With a typical output of around 0.5mV from the MC cartridge and a gain of around 64dB from the amplifier, signal-to-noise is typically 72dB, dropping to about 52dB with very low output cartridges (50μV). This is the best which can be achieved, and assumes an amplifier which adds no noise of its own, which is a practical impossibility. Real amplifiers degrade this ratio by injecting noise of their own, and this is in addition to any present on generated by the load resistor at the amplifier input.

The degree of this noise impairment is known as the noise figure of the amplifier and is expressed as a ratio in the form;

$$NF = \text{SIG}_{\text{out}} \times N / \text{SIG}_e \times N$$

and $NF \text{ dB} = 10 \log (NF \text{ of the power ratio})$

These other noise sources are caused by 'additional' noise sources such as 1/f or 'flicker noise', which we'll discuss later. In an MC preamplifier application, keeping the noise figure as near the theoretical minimum is of paramount importance, since the noise figure is the amount by which the Equivalent Input Noise (EIN) is higher than the thermal noise of a resistor of specified value - or the cartridge - which would normally be connected to the amplifier input. Noise

The Works

It has been designed for source impedances below 250R so the collector current for the SSM2210 should be around (or higher than) the 2.5mA mark. Regrettably, as we've already shown, r_{bb}, even at 28R, is the limiting factor on noise at current levels such as these. In order to achieve better performance in this respect, the two halves of the SSM2210 are paralleled to reduce r_{bb} by a factor of 2 to around 14R.

Total input voltage noise for this design can be calculated as follows:

$$e_n = \sqrt{4KT(r_{bb} + R3) + e_{n2}}$$

Numerically, this equates to:

$$0.623 \text{ nV}/\sqrt{\text{Hz}}$$

The current noise is 5pA/√Hz which flows through a son (typical) cartridge

source resistance and causes an additional 0.25nV/√Hz. Since the Johnson noise of a 50R resistor is 0.9nV/√Hz, the noise figure is:

$$NF = 1.9 \text{ dB} \\ 0.9 \text{ nV}$$

The circuit has only one internal capacitor, C1. This functions as an AC bypass for both stages. There is also no input stage load resistor bypassing, yet there is 56dB or better of supply rejection referred to the input. In spite of this, the constructor can add the optional supply filter of C3 and R7 (shown inside the dashed section of the circuit diagram) which improves matters in this respect by 50dB. Noise injected from power supply lines is an often-overlooked aspect of low noise designs,

probably due to the inherent high rejection qualities of operational amplifiers in this respect (attributed, in the main, to good PSRR and differential inputs), and their widespread use in this field.

The single-ended nature of many low-noise designs means that they do not enjoy the inherent supply rejection of differential designs. Where the load resistor is tied directly to the power supply, noise from this supply must be no higher than $(R_L I_c V_{cc}) / (3KT/q)$ or the overall noise performance of the system will suffer.

Normally, AC coupling of the 10R feedback resistor is a problem. It is eliminated here because a DC biasing scheme is used. This biases both stages simultaneously without relying on feedback from the output.

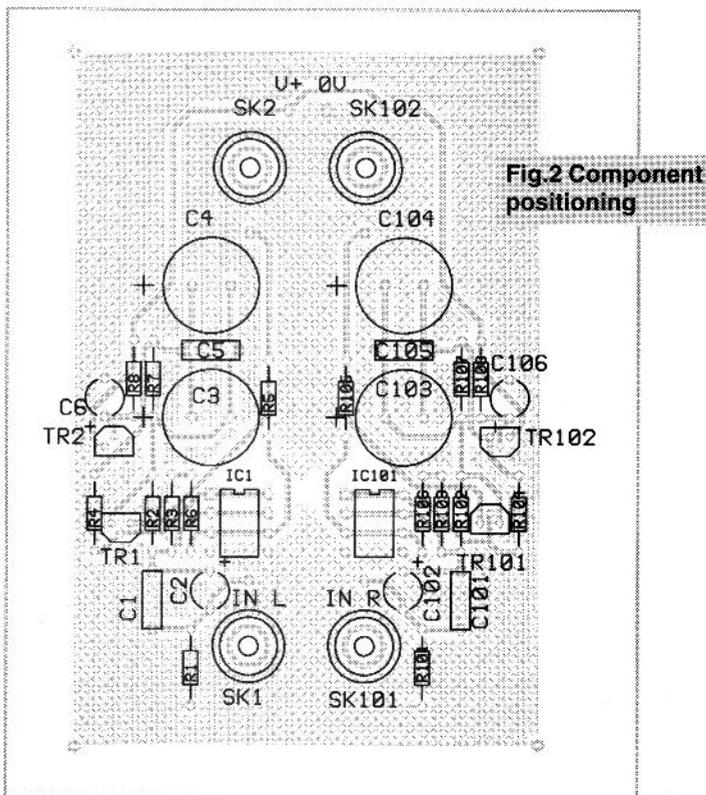


Fig.2 Component positioning

figures of 3dB or less can be assumed to be good, and those of 1dB or less, excellent. EIN can also be specified as the noise measured at the amplifier output plus the amplifier gain when the input is terminated with a resistor of the nominal value of cartridge impedance.

The Use of Transformers in Low Noise Design


Obviously, cartridges have an impedance which can't be altered. While the impedance of the moving magnet type is high enough that, with the right choice of op-amp, it can be amplified directly, with little or no noise degradation, the MC-type cannot. Consequently, noise takes on special significance in the design of MC preamplifiers, since the much lower impedance of the MC type means that the direct op-amp approach can't be taken if adequate signal-to-noise ratio is to be maintained. This is because we can't adequately match the higher optimum source impedance or noise resistance of most op-amps - more of this later - to the much lower source resistance of the cartridge. There are three accepted solutions to the problem. With the first, and earliest method employed, optimum performance may be obtained by using a transformer with a turns ratio selected to transform the actual source impedance of the cartridge to the noise resistance of the amplifier. However, the transformer has several shortcomings which include cost, distortion at low frequencies, (caused by magnetic nonlinearities in the core which cause saturation), and the inability to handle transients because of leakage inductance and stray capacitance, which also affects performance at HF. There are further losses from the magnetic properties of the core, and from winding resistance, the latter worsening noise performance because it is, in itself, a source of Johnson noise. Also, the very low level signals present both on the primary and secondary windings of the transformer

mean that hum pick up can be a problem, and special, purpose-designed shielding, manufactured from materials such as mumetal, is sometimes used so that noise performance isn't impaired. In spite of these shortcomings, transformer coupling is used extensively in many high quality moving-coil preamplifier designs. These match the very low impedance of the MC cartridge to the much higher impedance needed to load the op-amp optimally for noise, and also produce the necessary 20-30dB of gain. Ortofon, one of the companies who pioneered the manufacture of moving coil type cartridges, use the transformer approach extensively in their head amp designs. To summarise, the transformer must match the source resistance to the characteristic noise resistance of the op-amp or transistor so that the best noise performance is attained (when $R_s = R_w$), match the impedance of the cartridge (non-critical), and provide some degree of voltage gain for the cartridge input signal.

Transistor Preamp Stage

The need for a very low value of circuit input impedance, in order to minimise thermal noise effects, can be met because of the much lower characteristic OSI (Optimum Source Impedance or noise resistance) of the transistor, so that it can be used directly to amplify the signal. With transistors, noise voltages and noise currents alter in magnitude and in ratio to one another. Lower collector current gives rise to lower noise current - not inconceivably, since the current noise is due to minor random discontinuities in the device currents (i.e. shot noise) which adds to the fluctuations caused by noise. The ratio between the two - noise impedance - can therefore be altered.

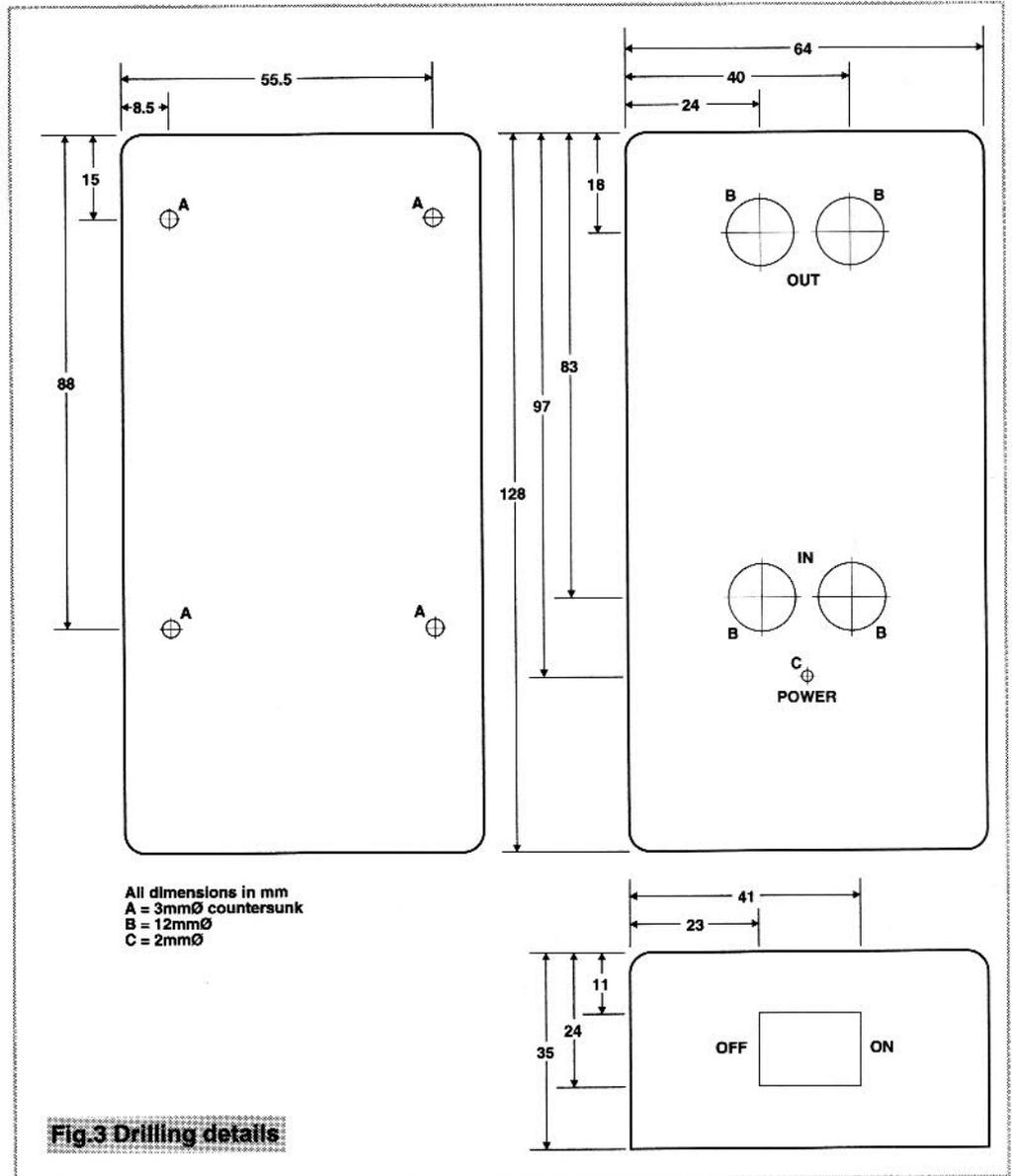The resistance value at which the device is optimally quiet for audio purposes is also the value which coincides with that required for optimum device transfer characteristics. In other words, there is good frequency versus



phase linearity response, and so the device will be stable at high frequency, and in high feedback-low gain configurations.

With bipolar transistors, the theoretical value for emitter-base voltage noise is a function only of absolute temperature and collector current

$$e_n = kT \sqrt{\frac{2}{qI_c}}$$


This formula indicates that a reduction in voltage noise, e_n , can be made low in value by increasing collector current. This is borne out in practise as I_c is increased until a level is reached where parasitic transistor noise limits any further reduction. This noise floor is usually created by and modelled as an equivalent resistor (r_{bb}) - the so-called 'base-spreading resistance' - in series with the base of the transistor. This is, in fact, the real part of h_{ie} . Low parasitic transistor noise is therefore an important factor in ultra-low noise applications. For finite source impedance, current noise must be considered as a quadrature addition to voltage noise. Shot noise is white noise - equal energies at all frequencies - which worsens with increasing emitter current. Base spreading resistance decreases with increasing emitter current, so thermal noise because of this parasitic resistance decreases also. This gives rise to something of a conflict of interest - low emitter current lessens shot noise but increases thermal noise because increases, while higher current lessens the thermal noise effect but worsens shot noise.

To find the collector current which yields the minimum overall equivalent input noise with a given R_s , i.e. a compromise between thermal noise and shot noise, the total noise formula can be differentiated with respect to I_c and set to zero for finding a minimum. For very low R_s - as in the case of a moving coil cartridge - the r_{bb} of the transistor must be added to R_s in the calculation.

Even a noiseless source has an irreducible source of Johnson noise from the value of its source resistance and, in any case, the amplifier adds its own noise. We've already shown that the amplifier's noise voltage is added to the input signal while its noise current generates a noise voltage across the source impedance. With a low source resistance - 50R cartridge - a low e_n is more important, so in practise we run

the transistor at a much higher value of collector current. This also has the benefit of widening the bandwidth of the system.

We can bring the OSI down by reducing the ratio of inherent noise voltages and currents. Lower OSI can be achieved by paralleling identical, low noise, input devices. This maintains the same noise voltage but alters the noise current. The noise impedance changes proportionately because the base spreading resistance of the transistor - which, as far as noise is concerned, adds itself to the source resistance of the cartridge - is reduced by a factor dependent upon

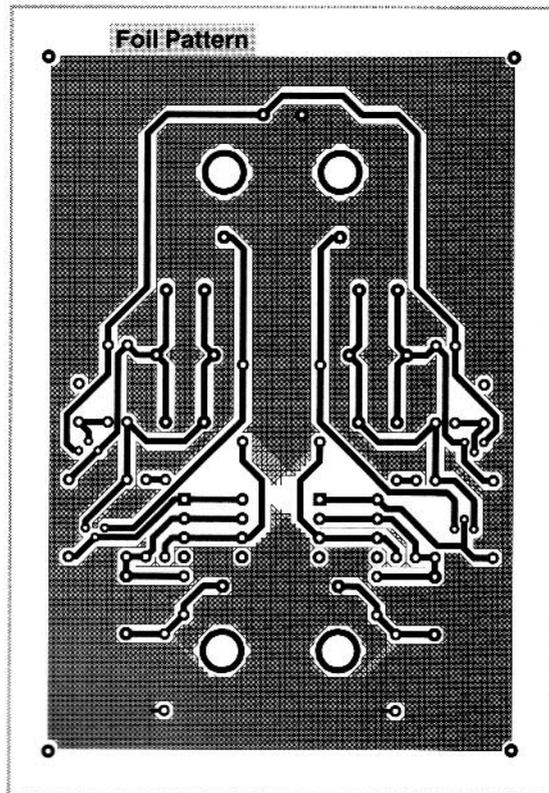

the number of devices placed in parallel. In the Alchemist design, noise is reduced by the square root of this paralleling factor. Shot noise (or Schottky noise) contribution can be reduced by maintaining a high collector current (which reduces dynamic emitter resistance), while voltage noise is inversely proportional to the square root of stage current. Conversely, current noise increases proportionally to the square root of stage current. Fortunately, high current

noise is of less importance when dealing with low impedance sources such as MC cartridges, and optimisation of impedances is not necessary. Designs of this type are marketed by companies such as Braithwaite, Linn/Naim and Ortofon.

From a commercial viewpoint, care-

ful selection and matching of components is a time-consuming - and therefore costly - process. To even out the spread in characteristics of electrically unmatched, but ostensibly identical devices, where there may be differences in the base-emitter turn-on voltage, for example, resistors are sometimes used to create a biasing network. Regrettably, resistors in the collector arm of the circuit mean a loss of some usable signal. Conversely, circuit topologies based around a common base connection between all transistors use individual emitter resistors. This swamps any differences in device characteristics, at the expense of a small but finite addition to the base-spreading resistance of the transistor in question which, in turn, worsens noise performance.

Supermatched Pairs

An ideal way to avoid using either a transformer, or having to closely match several discrete transistors in a head amp design is to make use of what is known as a supermatched pair. This exploits the low-noise-at-low-source-impedance characteristics of the discrete transistor, but without the attendant selection/matching problem, or the introduction of superfluous and performance-damaging passive component arrays.

Monolithic transistor arrays have been around for a long time, but ultimate performance was being compromised by statistical fluctuations in the material itself, and in the processing environment. The so-called 'super-

matched' transistor differs in that many individual transistors are physically located in a way which tends to average out any residual process or material gradients. This yields a pair which offers order-of-magnitude improvements both in matching properties, and in parasitic base and emitter resistance specifications, since the paralleling of many devices reduces overall r_{bb} and r_{ee} , which are around 20R and 0.4R respectively for packages such as the SSM2220 and the LM394. Such values are considerably smaller than for other small signal transistors. Typical h_{FE} mismatch is 2%, and is valued at 500 minimum when I_c is equal to 1mA. Broadband noise is very low, and the devices have no excess noise at lower current levels, although the large geometry transistor design, used to minimise base-spreading resistance, results in

relatively higher collector-to-base capacitance (C_{OB}) than ordinary transistors. The Miller effect from these can limit voltage-gain bandwidth, especially for high gain applications.

Construction

The circuit is simple but effective. There are no lineup procedures, no presets to trim, and no matching of components. For this reason, all of the components there are can be considered to be critical to the well-being of the design, and tolerances and types specified in the parts list should be strictly adhered to if noise and distortion performance is not to be compromised or impaired. The first job which must be carried out is a drilling operation. The four mounting holes must be opened out to 3mm, while the phono socket mounting holes (if intended for use with those specified in the Parts List) should be drilled using a 8mm drill. Use new, sharp drills and speeds around the 3000rpm mark or higher. The PCB must also be trimmed slightly if it is to fit in the box specified. This amounts to about 1.5-2mm on each side.

Since the ground plane was extended around to the far side of the board using PCB material which has just been removed, a wire link must be soldered to the underside of the board to join both halves of the ground plane together. This should be done on the central part of the board. Note also that whilst R3 and R5, R103, R105 are shown earthed in the circuit diagram, various gremlins in the PCB design seem to have thwarted this. The node connecting these two resistors (adjacent to and just in front of pin 1 IC1, pin 8 of IC101, should be joined to the ground plane with a wire link/ large blob of solder. C4, C104 optional supply decoupling capacitors seemed to have suffered in this respect too, with the earth connection to the - pin missed. Bridge across from this to the ground plane. Once this is complete, the IC sockets should be soldered in first, followed by resistors and small capacitors. R1,101 should be chosen, in accordance with the cartridge manufacturer's specifications, to be a proper impedance match for the device concerned. Transistors come next, then Veropins and the larger non-polarised electrolytics, before finishing with the two gold-plated phono sockets. These are optional but make for a tidy and uncluttered interior. They also eliminate the possibility of any infiltration of the signal by hum or other stray pick-up. Should off-board connectors be more

attractive for whatever reason, ensure that the connecting leads are adequately shielded and screened and that good earthing arrangements are strictly adhered to. The sockets are mounted on the reverse (foil) side of the PCB. Use the washers supplied and tighten the nuts securely. The earthing tag can be soldered to the surrounding earthed trackwork while the centre, signal pin is joined to its associated Veropin using a short length of wire. The connections to the centre pins should be shrouded. Throughout construction be aware of solder bridges across tracks.

Rather than have one set of 'IN' and one set of 'OUT' sockets, the output of the circuit can, instead, be terminated in a phono plug/screened lead combination. In this way, one set of potentially-unreliable, potentially hum-inducing connections are eliminated. It goes without saying, of course, that both the screened lead and the phono plugs should be of a quality commensurate with the performance expected of the unit.

The last connections to be made are the output phono leads/plugs (if you've omitted the output sockets SK2 and SK102), power connections to and from the on/off switch and finally, the battery clip connection. The diecast box is drilled with reference to the diagrams shown in Figure 3. The PCB is mounted inside the box using M3 tapped spacers or PCB standoffs. Spacers are bolted to the lid part of the box. Where metal spacers are used, all but one of the screws should be insulated using plastic washers. This avoids the PCB being earthed in four different places and the hum loops it might cause. Deviate from these at your peril - when I was measuring noise and distortion performance, non optimised ground paths in the input and output leads used to connect the measuring apparatus caused performance to be worsened in both respects by at least two orders of magnitude.

Current consumption is low enough (about 10mA) that the unit can be powered from a 9V PP3 battery. This eliminates the possibility of hum induction from the power supply, but a mains PSU could be used, as long as it's adequately screened (ideally in a separate box) and well-regulated. The preamp should, in any case, be housed in its own metal box - the diecast example specified in the parts list is ideal. The battery can be wrapped in some foam and sealed inside this box and changed once a year or thereabouts. The mounting position for the switch has to satisfy two, somewhat

conflicting, criteria. It must be positioned where it is easily accessible but not able to be inadvertently knocked on or off. A DPDT rocker switch from RS was used in the prototype and seemed ideal. A worthwhile addition is the LED across the switched supply. I used a high efficiency type fed through an 8K2 resistor.

When interfacing between turntable and preamp, The Alchemist should be sited as near to the turntable as possible, connected to the cartridge with short, high quality screened lead. Connections between it and the preamp should also be as short as practical. We've mentioned already that the moving-coil cartridge, because of its low impedance/ low inductance nature, is able to drive long and or capacitive cables. However, longer cables are more prone to hum pick-up and other forms of interference injection and so should be avoided where possible. All that now remains is to connect the battery, turntable, amplifier, select a favourite track, turn on The Alchemist, and listen to it work its magic on vinyl.

(all 1/4 watt 1% metal film)

R1,101	51R (or in accordance with cartridge manufacturer's specifications)
R2,102	200K
R3,103	62K
R4,104	2K2
R5,105	510R
R6,106	10R
R7,107	510R (see text)
R8,108	10K (optional supply smoothing)

C1,101	10µF non-polarised radial electrolytic
C2,102	100µF non-polarised radial electrolytic
C3,103	} 25µF/16V radial electrolytic
C4,104	

Semiconductors

IC1,101	SSM2210
Tr1,101	BC214C
Tr2,102	BC549C (optional supply smoothing)

Additional items

PCB, Veropins, PCB mounting gold-plated phono sockets (Maplin JZ05F, JZ05G), 8 pin DIL IC sockets, type M5004 diecast box (Maplin LH71N), on/off switch, PP3 battery clip and battery (both optional), screened lead, phono plugs, LED

Parts

SHAREWARE REFERENCE GUIDE

Find out what really is available in PD & shareware - games business, scientific, education etc. You'll find them all here.

Thousands of the best PD & shareware programs for DOS & Windows described in detail with hardware requirements for each. Find what you need and take the guesswork out of choosing PD & shareware programs.

The most complete and up-to-date shareware reference book available today. For your copy send £2.50 by cheque, PO, cash or pay by Acces/Visa to:


**PDSL, Winscombe House, Beacon Rd,
Crowborough, East Sussex, TN6 1UL.
Tel 0892 663298 Fax 0892 667473**

PROMOTE YOURSELF


If your company has not placed an advert within Electronics in Action then you are missing the golden opportunity of getting through to scores of electronics engineers, technicians, scientists and electronic hobbyists. Telephone **Gilly Martin** on **0442 842069** for an immediate booking

GET YOURSELF KNOWN

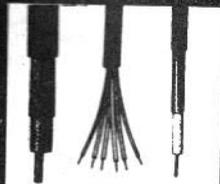Call us now! We have the widest range of components available - At competitive prices!




CABLES

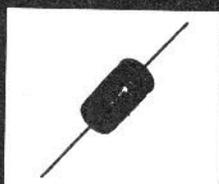


CAPACITORS



VIDEO HEADS

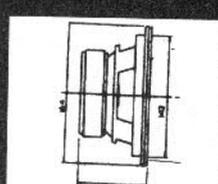

SPEAKERS

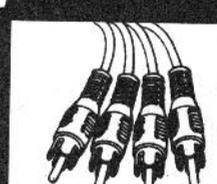

CONNECTORS



ESPECIALLY
JAPANESE
SEMICONDUCTORS

CRICKLEWOOD

ELECTRONICS

Cricklewood Electronics Ltd. 40 Cricklewood Broadway, London NW2 3ET
Telephone: 081 452 0161

Faxsimile: 081 208 1441

All Major Credit Cards Accepted



WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES
Dual Trace plug-in with TB from £200
Many plug-in options available. 4Traces;
Differential etc. PLUG-INS SOLD SEPARATELY

TEKTRONIX 2235 Dual Trace 100MHz Delay Sweep.....	£800
PHILIPS 3065 2-1 channels 100MHz Dual TB Delay Sweep.....	£700
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep.....	£550
HP 1715A Dual Trace 200MHz Delay Sweep.....	£400
HP 1740A Dual Trace 100MHz Delay Sweep.....	£400
TEKTRONIX 2215A Dual Trace 60MHz Delay Sweep.....	£500
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep.....	£400
HITACHI V422 Dual Trace 50MHz Delay Sweep.....	£325
TELEQUINTE D83 Dual Trace 50MHz Delay Sweep.....	£200
GOULD OS3000A Dual Trace 40MHz Delay Sweep.....	£200
KIKUSUI 5530 Dual Trace 35MHz.....	£180
GOULD OS1100 Dual Trace 30MHz.....	£160
HITACHI V223 Dual Trace 20MHz CRT Delay Sweep.....	£300
GOULD OS300 Dual Trace 20MHz.....	£200
GOULD OS250B Dual Trace 15MHz.....	£125
TEKTRONIX 466 Dual Trace 100MHz Storage.....	£450

THIS IS JUST A SAMPLE. MANY OTHERS AVAILABLE

PHILIPS PM 5139 Programmable synthesizer/Function Generator 0.1MHz-50MHz IEEE-488 as new.....	£1500
MARCONI 2019 Synthesised AM/FM Sig/Gen 80KHz-1040MHz.....	£2000
MARCONI 2018 Synthesised AM/FM Sig/Gen 80KHz-520MHz.....	£950
EIP/DANA 3510Microwave Frequency counter 20Hz-18GHz.....	£350
RACAL 9921 Frequency Counter 30Hz.....	£300
RACAL/DANA 1991 Nanosecond Universal counter.....	£800
RACAL 9301A RF Millivoltmeter True RMS 10KHz-1.5GHz.....	£450
RACAL 9301A RF Millivoltmeter True RMS 10KHz-1.5GHz.....	£250
PHILIPS 9009 Auto Mod. Meter 10MHz-1.5GHz Wide deviation.....	£250
LYONS PG73N Pulse Gen. PRF 1Hz-20MHz.....	£150
GOULD Bicomation K5000D Logic Analyser.....	£500
FARNELL PS0520H Synthesised Sig Gen AM/FM 100KHz-520MHz.....	£500
LEADER LSG216 AM/FM Sig/Gen 0.1-30MHz & 75-115MHz.....	£400

BRUEL & KJAER Vibration Exciter System
Consisting of Exciter Control 1047; Power amp 2708 in exciter
body 4832. (up to 1750N - 4001bf)
Other B & K equipment available

SPECTRUM ANALYSERS

HP 141T with 855A & IF Plug-in 10MHz-18GHz.....	£2000
HP 141T with 854B & 8552B 500KHz-1250MHz.....	£1000
HP 140T with 8554L & 8552A 500KHz-1250MHz.....	£1000
HP 141T with 8556A & 8552B 20Hz-300KHz.....	£1000
HP 140T with 8553L & 8552A 1KHz-110MHz.....	£1000
MARCONI TF2370 30Hz-110MHz.....	£1500
HP 1820 with 8558B 100KHz-1500MHz.....	£1500
HP 3562A 0.02Hz-25.5KHz.....	£2000

DATRON 1061A - 6 1/2 digit true RMS AC/Current.....	£1250
DATRON 1065 Multimeter 5 1/2 digit AC/DC/Ohms IEEE.....	£900
HAYLETT PACKARD 3490A Bench Multimeter 5 1/2 digit AC/DC/Ohms.....	£200
PHILIPS PM2534 Multifunction DMM 6 1/2 digit GP/B IEEE.....	£450
BLACK STAR Jupitor 500 Sine/Sq/Tri 0.1Hz - 80MHz.....	£125
MARCONI Digital Frequency Meter 2430A 10Hz - 200MHz.....	£150
MARCONI Universal Counter Timer 2437 DC - 200MHz.....	£175
MARCONI Universal Counter Timer 2438 DC - 200MHz.....	£225
HP 3311A Function Generator 0.1Hz - 1MHz Sine/Square/Triangle.....	£125
BLACK STAR Jupitor 500 Sine/Sq/Tri 0.1Hz - 80MHz.....	£70
FEEDBACK FG600 Sine/Sq/Tri 0.1Hz - 100KHz.....	£60
MULTIMETERS Hand-Held M2365-32 ranges AC. DC 10A Diode/ Transistor Tester, Freq counter.....	£32.50

FARNELL ELECTRONIC LOAD RB1030-35 1KW 30A 35V.....

HP 8690 Sweep Osc with 86974 Plug-in 26.5-40GHz.....	£300
RACAL/DANA RF Power Meter 9104.....	£400
RACAL/DANA 9341 Databridge, Automatic LCR & Q.....	£350
WAYNE KERR 8605 Automatic Precision bridge 0.05%.....	£900
WAYNE KERR 8605 Automatic Component bridge 0.1%.....	£925
WAYNE KERR 8424 Digital Component Meter L.C.R.....	£125
FARNELL PSU TV570MK2 70V 5A/30V/10A.....	£300
FARNELL PSU H6025 0-50V 0-25A Metered.....	£400
FARNELL PSU 302 0-30V 0-30A Metered.....	£30
FARNELL B3020 0-30V 20A.....	£250
FARNELL B3010 0-30V 10A.....	£200
HP 8208B 0-320V DC 1A Metered.....	£125
MARCONI TF2700 Universal LCR Bridge. Battery from.....	£150
AVO Characteristic Meter VCM163.....	£300
FARNELL LA520 RF Power Amp. 1.5-520MHz 300mW.....	£175
RACAL 9100 Absorption Wattmeter 1MHz-1GHz 3W.....	£100

FARNELL Isolating Transformers
GU500, 240V 500VA, unused.....

£50

NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay timebase.....	£847
HAMEG OSCILLOSCOPE HM804 Dual Trace 60MHz Delay Sweep.....	£653
HAMEG OSCILLOSCOPE HM205.3 Dual Trace 20MHz Component Tester.....	£553
All other modes available - all oscilloscopes supplied with two probes	
BLACK STAR EQUIPMENT (P&P all units £5)	
APOLLO 10 - 100MHz Counter timer Ratio/Period/Time interval etc.....	£222
APOLLO 100 - 100MHz (As above with more functions).....	£325
METEOR 100 FREQUENCY COUNTER 100MHz.....	£119
METEOR 500 FREQUENCY COUNTER 600MHz.....	£145
METEOR 1000 FREQUENCY COUNTER 10GHz.....	£189
JUPITOR 300 FUNCTION GEN 0.1Hz - 500KHz Sine/Square/Tri.....	£119
ORION COLOUR BAR GENERATOR PAL/NTSC.....	£225
All other Black Star Equipment Available	
OSCILLOSCOPE PROBES Switchable x1 x10/PAP £3.....	£12

Used Equipment - GUARANTEED. Manuals supplied if possible

This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering.
CARRIAGE all units £16. VAT to be added to total of Goods and Carriage

STEWART of READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
TELEPHONE (0734)268041 Fax: (0734)351696

Callers Welcome 9am-5.30pm Monday to Friday (until 6pm Thursday)



OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX - 031 667 2611

The supplier to use if you're looking for:


- A WIDE RANGE OF COMPONENTS AIMED AT THE HOBBYIST
- COMPETITIVE VAT INCLUSIVE PRICES
- MAIL ORDER - generally by RETURN OF POST
- FRIENDLY SERVICE



Open: Monday - Thursday 9.15 - 6.00
Friday 9.15 - 5.00 Saturday 9.30 - 5.00



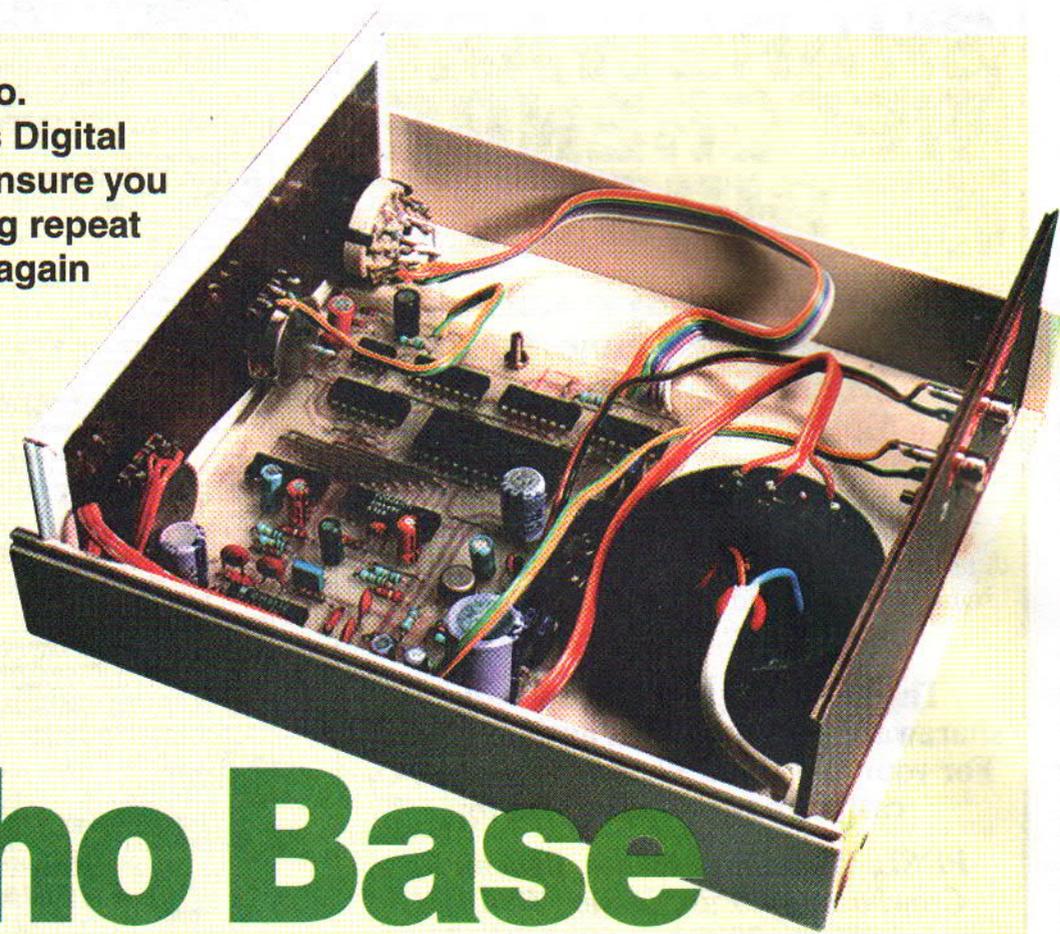Echo Echo Echo.
Paul Stenning's Digital
echo unit will ensure you
have astounding repeat
performances, again
and again.



Echo Base

This digital echo unit resulted from a discussion with a friend who is a member of a local amateur dramatic group. Until now they had been producing echo sound manually by tape recording the same sound several times at lower recording levels - I ad-

mire their patience! Although this method worked OK for longer echoes on single sounds, it could not be used to add a short reverberation on speech.

An exact specification was not offered, they felt that almost anything would be better than the existing system.

We decided that about half a second between echoes would be more than adequate for a maximum delay range. The shortest delay is so fast that sounds resembling microphone feedback can be obtained. Metallic alien reverberations similar to those on the "Smash" instant

The Works

The complete circuit diagram appears in Figures 1, 2 and 3.

Starting with the digital section. IC1 is the clock generator, which runs at four times the sampling frequency. The frequency is adjustable over a limited range by VR1, the Delay Fine control. This slightly unusual configuration gives an output with an approximately equal mark-space ratio.

The A-D convertor

IC7, requires a negative bias on pin five. Since the current required is minimal, this negative voltage is obtained by rectifying the clock signal from IC1, giving approximately -4V.

IC2 produces the four timing pulses required, three of which are inverted by gates in IC3. When Q1 goes high, the A-D convertor IC7 starts a conversion. When Q2 is high, the data in the RAM is sent to the D-A convertor IC8, which produces the appropriate voltage.

When Q3 is high, the

data from the A-D is stored in RAM. Finally when Q4 pulses high, the address counters IC4 and IC5 are incremented.

SW2 (Delay Coarse) sets the count reached by the address counters before they are reset. This sets the amount of the RAM chip to be used.

Ideally I would have had just one continuously variable delay pot, on the 555 clock circuit. However, it was not possible to achieve the required range with a respectable frequency response due to the A-D conversion time.

The ZN448E (IC7) is an 8 bit successive approximation A-D convertor. Nine clock cycles are required for each conversion. The eight data lines are tri-state, and controlled by the OE- pin.

The device contains a built in clock circuit, the frequency of which is set by C13. The data sheet gives the maximum clock frequency as 1MHz, and a graph shows that a capacitor value of 100pF will give this. However tests with several devices showed that 100pF gave a



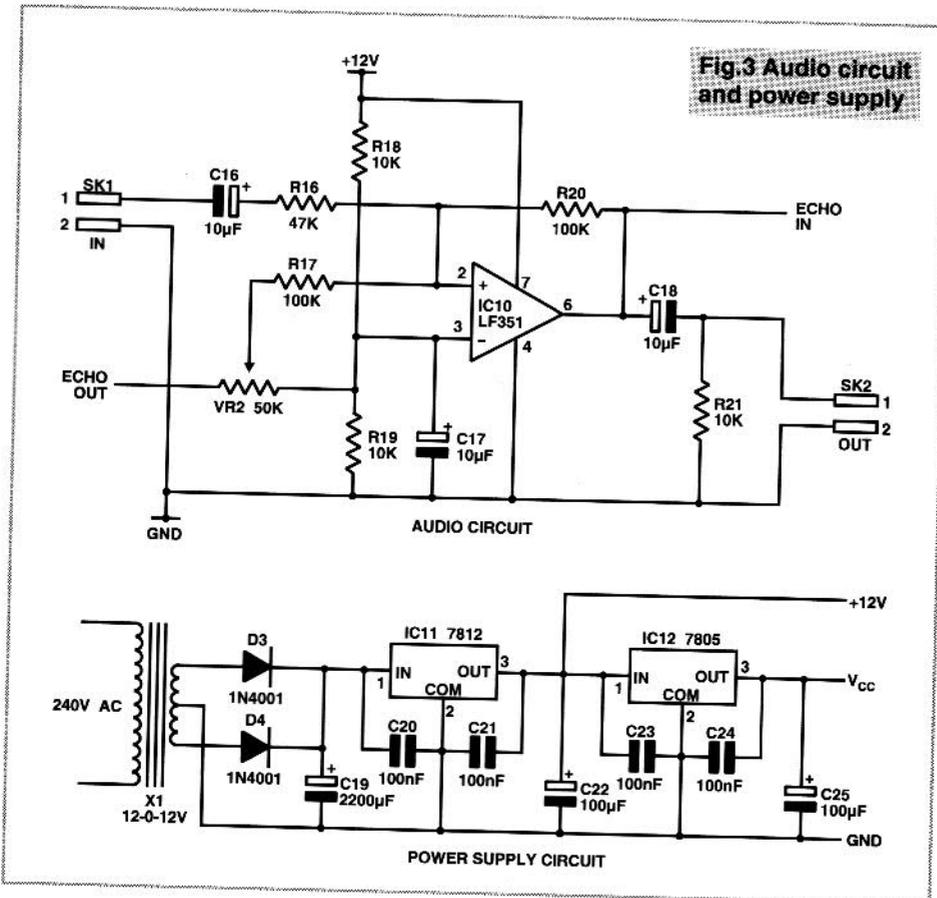


Fig.3 Audio circuit and power supply

panel, and then position the PCB and transformer in the base of the case. The PCB should be mounted with three M3 screws, with extra nuts to act as spacers. The transformer is also mounted with M3 hardware, which should ideally be nylon to insulate the mounting frame from the outside world. A 10VA toroidal transformer was used in the prototype because it was to hand, however a 250mA conventional type is suitable.

The rear panel needs to be drilled for the audio input and output sockets, and the mains flex. The hole for the latter should be fitted with a cable gland or grommet, and the cable must be secured to prevent it being pulled out.

The interwiring is shown in figure 5, the pots are shown viewed from the rear. Audio coax may be used for the connections to the rear panel sockets if desired, although the prototype worked fine with ribbon cable. The remaining connections may be made with ribbon cable or whatever is available.

The mains flex should be connected to the flying leads on the recommended transformer with a chock-block type connector. No mains switch or fuse were fitted on the prototype for simplicity. A 3A (or lower) fuse must be fitted in the mains plug.

Testing and Using.

Ensure that the internal mains connections are adequately insulated. Connect the unit to the mains and switch on. If a

Construction.

The circuit is constructed on a single sided PCB, which is available from Electronics in Action (see page 61). The track layout and component positioning are shown in Figure 5.

There are 30 links that should be made first, using thin (approx. 26SWG) tinned copper wire. The resistors, diodes and capacitors can then be fitted in size order. Sockets may be used for the IC's if required - since all the devices are static sensitive this may be a good idea. Do not insert the IC's into the sockets until the remainder of the PCB construction is complete.

IC11 and IC12 will become warm in operation and should be mounted on a small heatsink. The mounting tabs of both devices are connected to the 0V rail so no insulation washers are required. A small amount of silicone grease or heat transfer paste should be placed between the devices and the heatsink.

Terminal pins may be fitted in the holes for the off-board wiring, so that the connections can be made after the PCB is fitted into the case.

The prototype was constructed in a plastic case,

190mm x 165mm x 68mm, see parts list for details. A suitable overlay for the front panel is shown in Figure 5. Two photocopies may be taken (enlarge to 162mm * 64mm), one can then be used as a drilling template while the other may be fixed to the front panel with clear self-adhesive vinyl. No actual values are shown for the delay controls, since they might confuse a nontechnical user.

Set the stop on SW1 to position six. Fit the pots and switches to the front

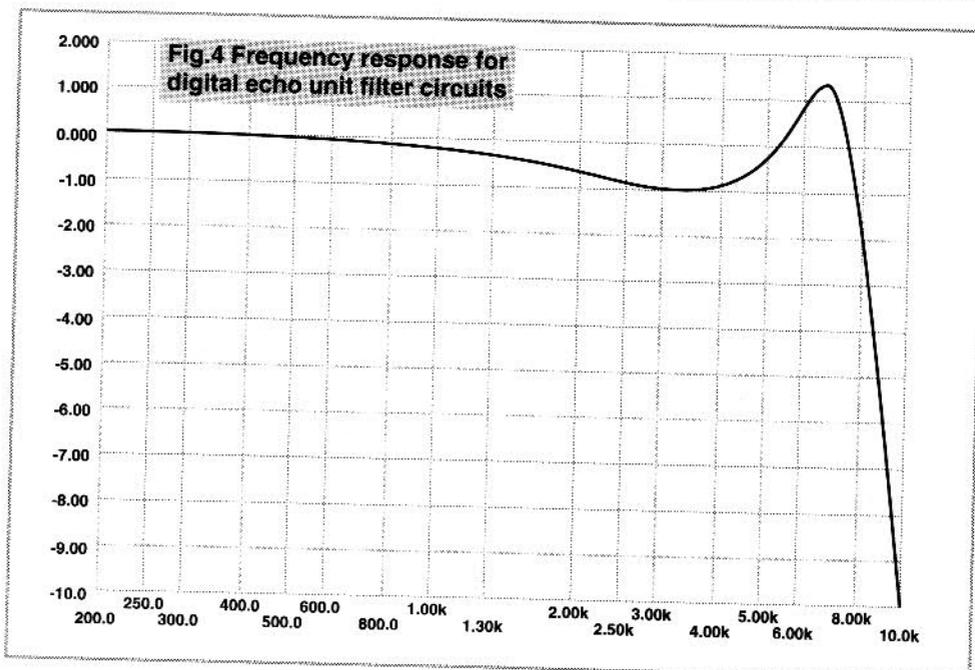


Fig.4 Frequency response for digital echo unit filter circuits

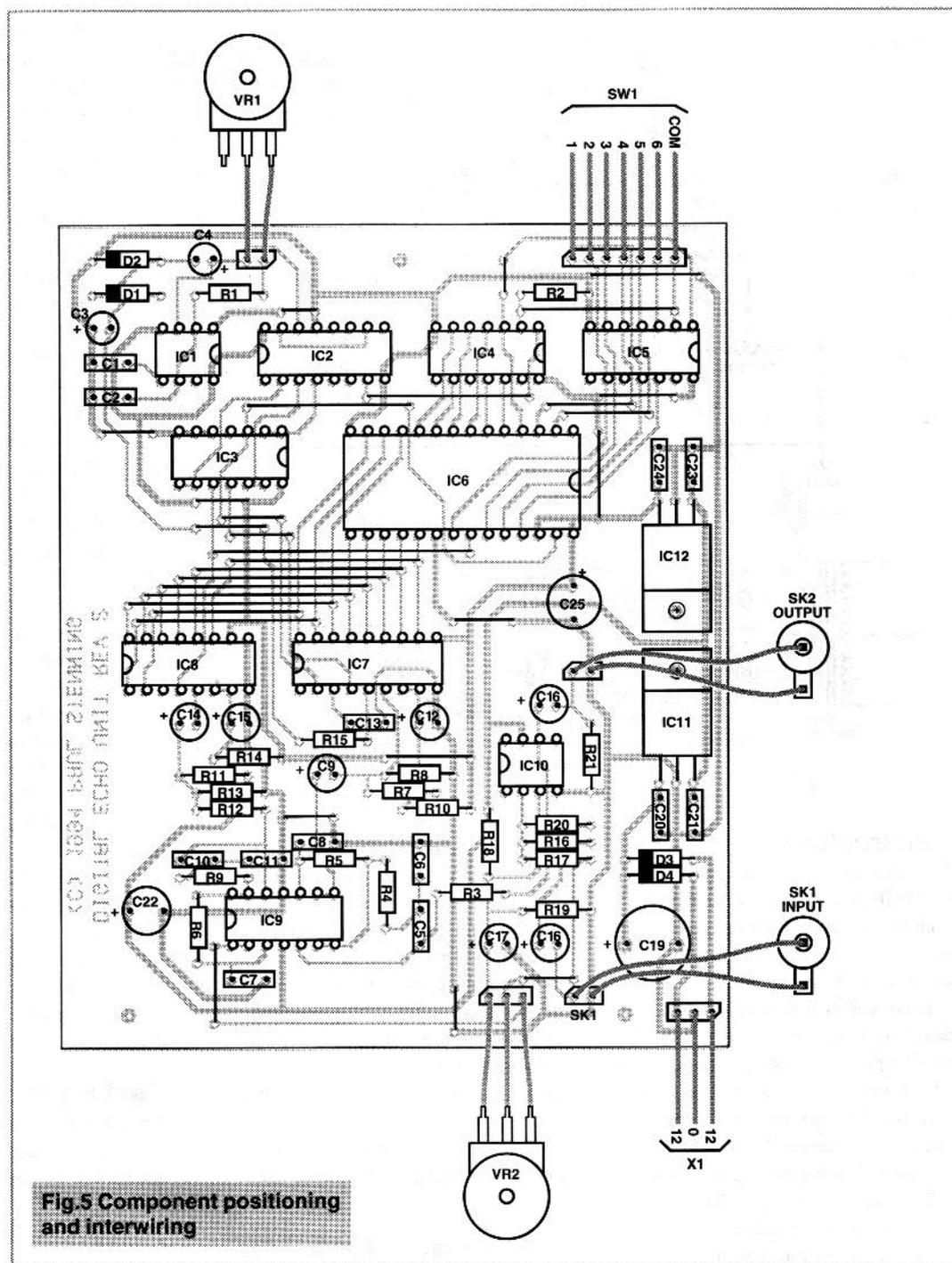


Fig. 5 Component positioning and interwiring

test meter is available, check the voltage outputs from IC11 and IC12 on the appropriate pins. The voltages required should be 12V +/-0.5V and 5V +/-0.25V.

Unless an audio pulse generator and oscilloscope are available, the remainder of the unit is probably best tested by connecting it to suitable audio equipment and trying it. The effects can be heard readily on male speech.

The audio input signal should be between 0.5 and 1V RMS for optimum performance. Lower levels will give greatly increased distortion on the echo signals due to the lower number of sampling points available. Larger signals (over 2.5V pk-pk) will be distorted

due to clipping at the A-D converter. If the signal level is likely to vary significantly, this unit should be preceded by an automatic level control or compressor circuit.

Initially set both delay controls fully clockwise. As the repeat control is advanced, the echo should be heard more times. You may notice that if a sound is repeated several times it becomes a little more distorted each time. With a more normal decay, the distortion will tend to occur as the sounds are getting quieter, and will generally pass unnoticed. When the control is at maximum, all the signal is recycled which can cause some awful sounds!

By operating the delay controls, the

period between each echo can be altered. You may notice an apparent pitch shift as the Fine Delay control is operated, this is due to sounds being replayed at a different rate to the one they were recorded at. Momentary bursts of noise may also be heard as the Coarse Delay control is set to longer periods, this is due to old data stored in the RAM being replayed. Neither of these effects is relevant in practice, since the controls would not be altered when the unit is being used.

The best way to understand the unit's capabilities is to play with it for a while. Have fun . . . fun . . . fun!

Resistors

(0.25W 5% or better)

R1,2,7,8	10K
R18,19,21	22K
R3,5,6,12	2K2
R4,9	390R
R10,14	100K
R11,13,17,20	68K
R15	47K
R16	20K or 22K Lin Pot
VR1	47K or 50K Log Pot

Capacitors

C1	10nF
C2	220pF
C3,4,9,14	10µF
C16,17,18	
C5,6,10,11	4n7
C7,8	2n2
C12,15	1µ0
C13	47pF
C19	2200µF/25V
C20,21,23,24	100nF
C22,25	100µF/16V

Semiconductors

IC1	7555
IC2	4017
IC3	4001
IC4,5	4024
IC6	6264
IC7	ZN448E
IC8	ZN428E
IC9	LF347
IC10	LF351
IC11	7812
IC12	7805
D1,2	1N4148
D3,4	1N4001

Additional Items

SK1,2 Phono Socket
SW1 1 Pole 12 Way Rotary
X1 12-0-12V 250mA
 PCB, Knobs, Case, Wire
 2 Core Mains Flex.
 13A Plug with 3A Fuse, IC Sockets
 M3 Screws and Nuts.
 The plastic case used for the prototype is made by Bafbox, and is available from RS/Electromail, stock no 506-788.

ELECTRONICS in ACTION

Digital Echo

COARSE

DELAY

FINE


REPEAT



Fig.6 Front panel template

Baylin Publications

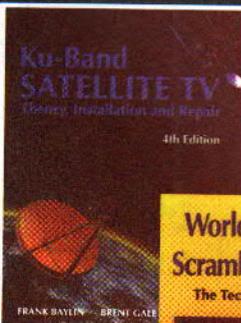ALL ITEMS EX-STOCK.
Ku Band Satellite TV, Theory, Installation & Repair
 4th Edition.
 Footprints, dish theory, cables, site survey, polar mount adjustment.
£25.



24 River Gardens,
 Purley, Reading.
 RG8 8BX, England.
 Tel/Fax 0734-414468
 Mobile 0836-582785
 Pay by: UK£ cheque,
 Access, Mastercard,
 Visa,
 C.O.D.

World Satellite TV and Scrambling Methods
 The Technicians' Handbook

European Scrambling Systems, Circuits, Tactics & Techniques. By John McCormac, digital sound, smart cards, pirate decoders, for hackers. **£32.**

World Satellite TV & Scrambling Methods. 2nd Edition, by Baylin, Madox & McCormac for the service engineer. **£29.**

Home Satellite TV Installation Videotape. Forty minutes VHS Pal. See how 3 metre dishes are installed. **£27.**

Satellite Installation Guide. 3rd Edition. By John Breeds. **£13.**

The Satellite Book. 2nd Edition. A complete guide to satellite TV. Theory and practice by John Breeds. **£31.**

World Satellite Almanac. 3rd Edition by Mark Long. 300 Footprints, Frequencies, Transponder Loading, Orbital Assignments. **£69.**

World Satellite Annual. Update by Mark Long. **£39.**

TVRO System Analysis and Aiming Software. 5.25 or 3.5 disk, (DOS 3.2). Calculates dish size and lists coordinates of all satellites in view. **£39.**


Satellite Toolbox Software. for IBM Comp. Hard Disk-5.25 or 3.5. **£59.**

Wireless, Cable & SMATV. Microwave broadcasting & cable TV. **£35.**

World Satellite Yearly by Dr. Baylin, Loading and 200 Footprints. **£38.**

PRICES INCLUDE P. & P. UK. Airmail Europe add 10%. Outside Europe +20%.

SYSTEM 200 DEVICE PROGRAMMER

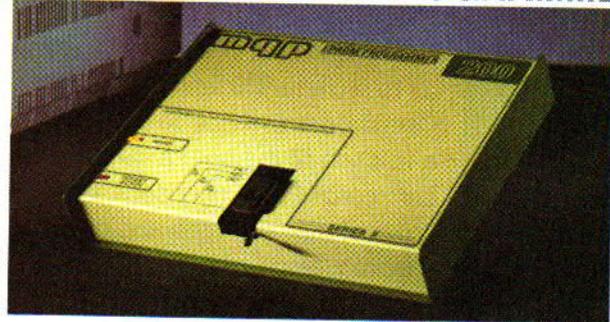

SYSTEM: Programs 24,28,32 pin EPROMs, EEPROMs, FLASH Memories and EPROM Emulators as standard, quickly, reliably and at low cost
 Expandable to cover virtually any programmable part including serial EEPROMs, PALs, GALs, EPLDs and microcontrollers, in many different packages.

DESIGN: Not a plug-in card but connecting to the PC serial or parallel port; it comes complete with powerful yet easy to use software, cable and manual.

SUPPORT: UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.

mqp



ASK FOR FREE INFORMATION PACK

MQP ELECTRONICS Ltd
 Park Road Centre
 Malmesbury, Wiltshire SN16 0BX. UK
 Tel: 0666 825146 Fax: 0666 825141

GERMANY 089/4602071
 NORWAY 0702-17890
 SWEDEN 8 590 754 04
 ITALY 02 92 10 35 54
 FRANCE 1 69 30 13 79
 Also from VEROSPEED UK

Next Month in ELECTRONICS in ACTION

We'll supply the...

SURROUND SOUND DECODER

You supply the popcorn and movie!



On Sale May 19th

Available from leading newsagents

ELECTRONICS in ACTION

58

MAY 1994

Printed Circuit Boards

HIGH QUALITY PRINTED CIRCUIT BOARDS BY MAIL ORDER!

Our unique Mail Order system allows us to provide you with High Quality Circuit Boards made to BS Spec. at a fraction of the cost available commercially. Simply send your order stating the type and quantity required, along with either Artwork or Gerber Cad Data.

Spec: 1.6mm fibreglass, 1 oz Copper, Non plated holes, Roller-Tinned finish.

REMEMBER TO ADD:

PHOTOPLOTTING	£10.00
POST & PACKING	£5.00

Send a Cheque or Postal Order along with your order to:

MAIL ORDER CIRCUITS,
Meridian Centre, King Street,
Oldham, OL8 1EZ
Fax: 061 624 2389

QUANTITY 1-8		
Sq In	2 Sides	1 Side
0-20	£8.00 ea	£5.00 ea
21-40	£10.00 ea	£7.00 ea
40-90	£15.00 ea	£11.00 ea

QUANTITY 9-20		
Sq In	2 Sides	1 Side
0-20	£5.00 ea	£3.00 ea
21-40	£7.00 ea	£4.00 ea
40-90	£9.00 ea	£6.00 ea

Please allow 21 days for delivery.

Due to the nature of our system, only Prototyping work can be carried out. For information on other commercial orders, please contact AO Electronics, Coventry.

MAIL ORDER

COURSES

Musical Instrument Technology

BTEC National Diploma

If you're interested in electronics and music why not combine the two and study for a BTEC National Diploma in Musical Instrument Technology. This practically based course leads to a nationally recognised qualification and covers the following subject areas:

- Practical Electronics - Acoustics
- Electronics Theory - Recording Techniques
- Music Systems - Information Technology
- Musicianship - Microelectronics
- Electrical & Electronics Principles

For further details telephone 0636 701411 or write to



NEWARK & SHERWOOD COLLEGE

Friary Road, Newark, Notts, NG24 1PB

MAY

The Sniff continues

That ultra sensitive nose on a chip announced by IBM might well detect certain chemical reactions at molecular level and could provide remote electronic signals say from the upper atmosphere. One wonders whether it is beyond the bounds of possibility to generate smells (chemicals) from electrical signals?

Car Security

Change the simple system of a mechanical key to unlock the door and start the engine by an electronic key. This would not only open the door but it could start the engine through unlocking an encrypted code for the electronic ignition system. This way no thief could get the car moving as the spark plugs would not fire. This makes you think how primitive the system is. The under-bonnet electronics could be potted in black epoxy resin with a minimum of wires and information externally. This would give added security. The encrypted code for this vehicle, apart from being unique, could also be the registration number and if in the event the car does somehow move without the electronic key it would automatically trigger off an alert beacon.


Car Parking

Proximity detector on front and rear of car for parking in small spaces giving alert of distances with a change of audible pitch.

Mains Failure

Audible warning for failure of deep freeze units.

Ideas Forum

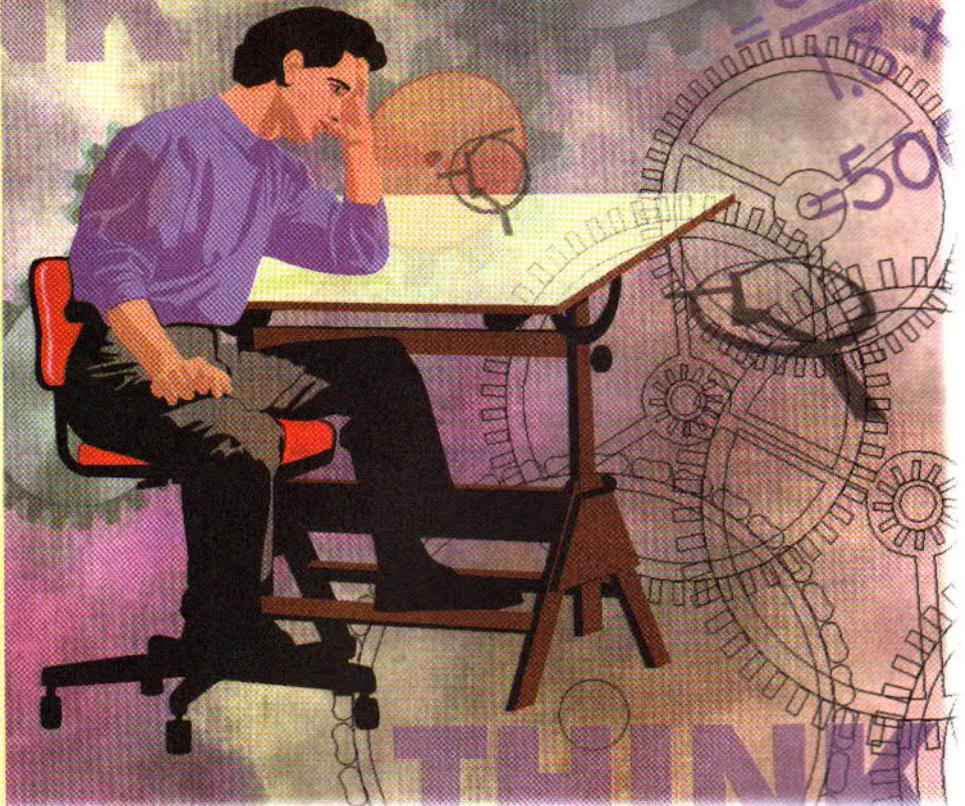

Work those brains, exercise, exercise, exercise!

Ideas never come easy do they? Some say that talking to a like minded person will bring out the best in you. The more you talk, the greater the chance that an idea will come out in conversation. Also to some it depends on what the weather is like or how much sleep you have had the previous night.

All great inventions start as little notions that get scribbled down and expanded upon, and that's what the Electronics in Action Ideas Forum is all about. Now you are the inventors.

Even though great inventions come to mind, the tragedy is you may dismiss the

idea as worthless. So if you think of a good idea discuss it with a friend to see if they agree with you that what you have to tell the world is brilliant. Then ask yourself, do lots of other people want to hear about it and would you like them to benefit from your idea? Is there a market for it? If there is, who will mass manufacture it? These are some of the questions that have to be thought about.

If you have any suggestions or have developed any of the ideas that have been appearing in this column we would love to hear from you, feel free to drop us a line. It could be the first step along the road to fame.

Electronics in Action, PO Box 600, Berkhamsted Herts. HP4 1NL

At Your Service

So you don't fancy messing up your best measuring jug with Ferric Chloride, but you still want to make some of our projects properly - with a PCB? This is where we step in. At Electronics in Action we can offer, at very reasonable prices, PCBs for all of our featured projects.

Just select which PCBs you require, fill in the coupon and post it to us with a cheque or postal order (for the full amount) made payable to **Electronics in Action**.

The coupon lists all the projects featured in the last four issues and anything older than that is listed below. We have left some blank spaces on the coupon should you wish to order an older PCB.

January Issue

QH0194-1
The Harmoniser (2 boards) £10.00
QH0194-2
Power Amplifier (double sided) £7.00
QH0194-3
Remote Control Extender £5.00

December issue

QH1293-1
Guitar Tremolo £5.00
QH1293-2
Switcher main board £10.00
QH1293-3
Switcher Front panel £6.00
QH1293-4
Video Editing Unit £8.00

November Issue

QH1193-1
Power Supply (double sided) ... £6.00
QH1193-2
Telescope Input board £5.50
QH1193-3
Drainpipe Seismometer £5.50

October Issue

QH1093-1
Telescope Main Board £12.00
QH1093-2
Hi-fi Preamp £4.50
QH1093-3
Laser Zone £5.00
QH1093-4
Anti-howler (double sided) £5.50
QH1093-5
Sig Gen board £4.50
QH1093-6
Crossover unit £3.00

Please print your name and address in **BLOCK CAPITALS**

Name

Address

Postcode

Send the completed coupon (include 80p for postage and packing) to:

At Your Service, Electronics in Action
PO Box 600, Berkhamsted, Herts. HP4 1NL

Please enter amount required in appropriate box

<input type="checkbox"/>	QH0594-1	PC Sound sampler	£6.00
<input type="checkbox"/>	QH0594-2	Audio Compressor for guitar	£3.50
<input type="checkbox"/>	QH0594-3	The Alchemist Hi-Fi Preamp	£4.50
<input type="checkbox"/>	QH0594-4	Digital Echo unit	£6.50

April Issue

<input type="checkbox"/>	QH0494-1	5-Band Graphic Equaliser	£5.00
<input type="checkbox"/>	QH0494-2	8-channel PC Data logger	£7.50
<input type="checkbox"/>	QH0494-3	Guitar A/B switchbox	£5.00
<input type="checkbox"/>	QH0494-4	Deionised water level detector	£5.00
<input type="checkbox"/>	QH0494-5	Simple Intercom	£5.00

March Issue

<input type="checkbox"/>	QH0394-1	Testcard Generator	£7.00
<input type="checkbox"/>	QH0394-2	Guitar Transmitter (double sided)	£8.00
<input type="checkbox"/>	QH0394-3	Mains Checker	£5.00

February Issue

<input type="checkbox"/>	QH0294-1	Hatchery Controller	£8.00
<input type="checkbox"/>	QH0294-2	12V drill speed controller	£5.00
<input type="checkbox"/>	QH0294-3	The Switcher IR transmitter	£5.50
<input type="checkbox"/>	QH0294-4	The Switcher IR receiver	£3.50
<input type="checkbox"/>	QH0294-5	The Switcher VCA board	£7.50

Total remittance including P&P

£

Allow 28 days for delivery

BK Electronics	28	Hart Electronics	29
Baylin Publications	57	Mail Order Circuits	58
Butterworth Heineman	34	JPG Electronics	41
J & N Bull	18	Labcenter Electronics	40
Chelmer Valve Company	41	MQP Electronics Ltd.	57
Cirkit Distribution Ltd.	OBC	Newark & Sherwood College	58
Cricklewood Electronics Ltd.	51	Omni Electronics	51
Delcia	35	Public Domain & Shareware Library ..	51
Electrovalue	35	Stewart of Reading	51
European Computer Marketing (UK) .	19	Robinson & Marshall	IFC
Express Components	22	Those Engineers Ltd.	41
Halcyon Electronics	35	Tsien (UK) Ltd	IBC

ADVERTISERS' INDEX

Technoshop

Bringing the world closer together

Electronics in Action in co-operation with The Technology Exchange Ltd., the international technology matchmaking service based in the UK, brings you each month a selection of technology partnership opportunities to which you are invited to respond.

The Technology Exchange, which was formed in 1985 as a not-for-profit technology sourcing service to industry, holds a biannual 'Technoshop' Technology Transfer Fair at Heathrow Airport and several 'Techmart' Fairs overseas for the United Nations (UNIDO).

For this issue of Electronics in Action, we are presenting a series of offers of licence, joint venture and patents rights for sale from organisations in 34 countries.

If you would like to have an introduction to any of the sources of the offers describes in these profiles, please write to The Technology Exchange quoting the reference number at the head of the entry and giving full contact details for the contact person in your own organisation and your requirements for a new product or process development.

The only cost associated with this process is a simple £10 plus VAT introduction fee for each entry to which you respond. For this we will send you full contact details for the source of the offer and invite them to send you more detailed information about their offer.

The code letters at the head of each offer indicate the stage of development, type of offer and the type of organisation making the offer as indicated in the table

Each entry is preceded by a reference number and letters indicating STATUS, OFFER and SOURCE.

Please respond directly to:

The Technology Exchange Ltd.
Wrest Park
Silsoe
Bedford
MK45 4HS
or Fax: 0525 860664
Phone: 0525 860333

The payment of £10 plus VAT (£11.75) per item should be sent with your requests.

KEY

Example S P O S J
Status Offer Source

Status: Indicates the stage of development.		
P Patent of design only	M Laboratory model	W Working prototype
U Pre-production units available	F In current production	C Commercialised
Offer: Indicates the type of agreement sought.		
L Manufacture under licence	S Design and/or patent for sale	J Joint venture offer
Source: Indicates the type of organisation making the offer.		
C Limited Company	E Educational Institution	R Independent Research Organisation
G Government Research	P Private Individual	

408737 **TAPA-CHIP-CARRIER ARRAY AND MANUFACTURING PROCESS**

Continuous roll by roll production. Use of HT films and of high vacuum processes. Application in all fields of electronic equipment technology.

108733 **KNOW-HOW FOR COMPOSITION RESISTOR PRODUCTION**

Vacuum technology for film deposition on ceramic carrier by way of plasmatron sputtering.

708750 **SWITCH TECHNOLOGY**

Production technology and process for automated series production of crossbar switches, solenoids and welded precious metal contact components.

507434 **CLGY-1 SEMICONDUCTOR SOS PRESSURE SENSOR**

New type SOS (silicon on sapphire) pressure sensors, using good dielectric strength sapphire to replace P-N junction isolation, have higher working temperature, high radiation resistant property, high accuracy, sensitivity and frequency response. It can be used in many areas such as aerospace, nuclear engineering, energy, oil and chemical engineering etc. Main specifications: pressure range 0-50.0kg f/sq cm; operating temperature: -40 degrees C to +200 degrees C; fall output: 100mV; Accuracy: 0.2%, 0.3%, 0.5%, 1.0% of full scale.

507443 **THE EQUIPMENT AND TECHNOLOGY FOR MANUFACTURE OF CERAMIC TRIMMING CAPACITOR**

The main application of Phi 7 ceramic trimmer is for frequency adjusting in the circuits of small sized radio receivers, walk-talkers, receive-recorders and color TV. The ceramic trimmers have advantages of small volume, easy frequency modulation and excellent electrical properties. The production line has mostly realised automisation for the equipment, and jigs have also been automised.

207431 **LONG WAVELENGTH INGAAS PHOTODIODES**

Long wavelength InGaAs photodiodes are key devices for optical communication and new products of high technology. The structures include PIN photodiode and avalanche photodiode (APD). The dark current for PIN photodiodes is less than 1nA, responsibility > 0.7 mA/mW. The multiplity factor for APD is larger than 30, responsibility > 0.5 mA/mW.

607452 **MULTI-FUNCTIONAL CONTROLLER FOR BACKDROP LIGHT**

This equipment is used to control and adjust backdrop light. It features large in unit capacity and output, small size, full-standard elements and devices, full-electronic circuits, easy maintenance etc. It is capable of adjust in the light either

manually or automatically with program control or audio control, and matrix control for all the light is also available.

707442 **ASSEMBLING AND MANUFACTURING TECHNIQUE FOR HIGH-FREQUENCY LOW-NOISE TRANSISTORS**

The transfer of the exclusive techniques includes: Product research development, manufacturing method and formulation, quality control used to fabricate cased TO-92 B37 (Model M), R246 (3P cross and 4P cross), SOT-23 (3Pmini) and SOT-143 (4Pmini), as well as high-frequency, low-noise transistors for black/white TV tuners and color TV tuners.

307430 **RESISTANCE-OXIDE-SEMICONDUCTOR FIELD-EFFECT TRANSISTOR (ROST)**

The present invention (ROST) relates to an IGFET in which two gate terminals are set up. The device provides speciality of its transfer curve with non-cut-off, remote cut-off and sharp cut-off characteristics. When necessary, the values of cut-off voltage are obtained by means of gate bars.

307444 **THE FABRICATION TECHNIQUE FOR LC FILTER**

The transfer of the exclusive techniques includes: product research development, manufacturing method and formulation, as well as quality control used to fabricate high-pass LC filter for TV tuner, band-pass LC filter for FM receiver. LC filter for CATV system and isolator.

307435 **PTC CERAMIC THERMAL SENSOR**

The PTC sensor is a kind of semiconducting thermal sensor with a main composition of Barium Titanate. It is a good semiconductor below Curie temperature while its resistivity increases rapidly by 3-5 orders of magnitude within a narrow range of temperature above Curie point. Because of this characteristic, PTC sensors have wide applications in electrical utensil, electronic industry and medical treatment, such as the electrical heater with constant temperature, motor starter, over current protector etc.

208217 C L/J G **BATTERY SEPARATOR**

Glass fibre paper type of battery separator has features of quick electrolyte absorption, high electrolyte retention,

acid resistance, low internal resistance, fine pore size, no gas generation other than O₂ and H₂ etc. The separator paper is used for sealed lead acid battery.

908210 C L/J G **ELECTRIC FAN PRODUCTION**

MAJRO series of electric fans of our factory or of advanced design. They have high air flow, small power consumption, low temperature rise, and negligible noise. We would export items of electric fan technology as follows: 1) fan assembly (involving equipment, training, inspection testing and repairing); 2) technology for manufacturing fan parts; 3) technology for manufacturing motor and complete set of equipment.

108118 C L/J G **PLATED TYPE CYLINDRICAL NICKEL CADMIUM STORAGE BATTERY**

Plant and technologies for producing plated nickel cadmium storage batteries with the annual production capacity of 300,000 cells. By additional improvements the plated type of cylindrical nickel cadmium storage batteries to other specification can be produced.

108117 C L/J G **SINTERED TYPE PRISMATIC NICKEL CADMIUM STORAGE BATTERY**

Plant and technologies for producing sintered prismatic nickel cadmium storage batteries with the production capacity of 100,000 cells (20 Ah each) per year. Batteries to other specifications can also be produced.

108218 F L/J G **ELECTRONIC ENERGY-SAVING LAMP**

This electronic energy-saving lamp is produced by means of the latest patented technology. The product has the unique temperature and voltage protective device. Its circuit design can raise lighting efficiency. So it has solved the problem of service life of the energy-saving lamp.

7445 **24 SERIES VIGURESE, CHINESE, ENGLISH AND RUSSIAN PRINTER**

The new product is based on the STONE-2401 electric printer while its software and hardware are redesigned. It can be used as a Vigurese printer, a Chinese printer, an English printer and a Russian printer. There are three subtypes: Vigurese-Chinese-English printer, Russian-Chinese-English printer and Russian-English printer. This product can be utilised in countries and

regions where Vigurese, Chinese, English, Russian are used.

108116 C L/J G **SINTERED PLATE CYLINDRICAL SEALED NICKEL CADMIUM STORAGE BATTERY**

The product is in accordance with the IEC standards using all sintered electrodes. The battery capacities of 0.5, 1.5, 3.5 Ah, can be discharged at high, medium or low rates. The products are characterised by good performance at low temperature, long service life, shock and vibration tolerance, easy maintenance.

907400 **TECHNOLOGY AND EQUIPMENT FOR PRODUCTION OF CIVIL POLYCRYSTALLINE SILICON SOLAR BATTERY**

The technology and special equipment for producing civil polycrystalline silicon solar cells include: The process of casting polycrystalline silicon ingots. The process of producing polycrystalline silicon solar cells adopts the world advanced technique, such as screen printing, plasma etching, antireflection spray film coating etc. The process of sealing and packing modules uses some special equipment.

107399 **SILICON SOLAR CELL MANUFACTURE TECHNIQUE**

AMI 5, 25 degrees C, conversion efficiency of single solar cell is 12-13% AMO 25 degrees C, TJDG BSR, BSE conversion efficiency is 13-13.5%. It was awarded the silver medal in 1980. Using for the terrestrial solar array and satellite solar array.

8115 C L/J G **METALLISED FILM CAPACITOR**

can be used in single phase electric machines such as refrigerator, air conditioner, washing machine, electric fan, ventilator and water pump. It is also applicable in power factor correction eg in fluorescent light.

**MORE
TECHNOSHOP
NEXT MONTH**

Future View

Alan McKeon, International Vice President of Iterated Systems, considers still and moving images: how the human eye sees them, how computers handle them and how they will be delivered across the digital information super-highway.

The human eye sees the world as a set of attractive pictures, continuous images whose elements flow one into the other and are understood as a whole - basically in analogue form. When we take pictures into the world of computers, on the other hand, they are approximated into a digital format, sampled at a given resolution - rather like looking through a mesh - and then encoded and stored digitally as a series of ones and zeros. These closed sets of information are then used to reproduce the image on screen or in print. The challenge to computer hardware and software designers has always been to encode images in the same natural way that the eye sees them - and reproduce them in the same way that the brain decodes them.

During the seventies and eighties, mathematical researchers investigated this challenge, exploring Chaos Theory and Fractals. Fractal images were first identified by the Swedish mathematician Helge Von Koch in the early 1900s, although it was only in 1978 that Benoit Mandelbrot first used the term fractal to mean 'a broken structure possessing similar looking forms at many different sizes'. Mandelbrot's research in pure mathematics enabled him to prove that natural structures and forms could be described and imitated using recursive algorithms (sets of mathematical instructions). He demonstrated that apparently disparate collections can be thought of as single geometric structures, and pictures of them created.

Mathematically, it is the infinite complexity of fractals combined with low information content that makes them fascinating. Most people are now familiar with fractally-produced 'paisley' patterns and computer 'landscape generators' which can create entire terrains from small sets of data. Using



fractals to create psychedelic patterns or imaginary landscapes is, however, of fairly limited use. It was British-born Dr Michael Barnsley and his research team at Georgia Tech who first began seriously to examine how the process might be reversed, and a practical and valuable tool created.

Rather than 'growing' an image from a small amount of data they set out to discover ways in which real-world images could be described in terms of fractal mathematics. Barnsley's Collage Theorem proposed that all images could be reduced, using fractal analysis, and defined by simple formulae. A highly complex and information-rich picture could therefore be described in very brief terms.

The process of identifying the fractal codes was extremely time consuming until 1988, when Barnsley discovered the Fractal Transform process. This automated the identification of fractal codes within real-world images so that computers could take over the task. Very quickly Barnsley and his team

were using this discovery to provide a completely automatic compression/decompression process.

Fractal images share many of the same qualities of images in nature; unlike other digitised pictures they are scalable, stretchable and can be zoomed or enhanced at will. The iterative nature of the mathematics simply creates 'new' detail.

Asymmetric processing

So what does this mean to the delivery of services on the digital information super-highway? Look at the parallels in standard publishing delivery - printing a magazine is time and cost intensive, but buying a magazine is easy and cheap. Fractal compression is similarly 'asymmetrical' - whilst the compression

process is intensive, decompression is low cost and very fast. File sizes are small (important for bandwidth), and because information is stored in a descriptive rather than representative language (rather like Postscript) decompressed images can be reproduced at resolutions and bit-depths independent of the original input.

Resolution independence, as this aspect of the technology is known, is one of the key components and advantages of fractal image handling. Without a fixed resolution, for instance, one compressed image can serve as both thumbnail portrait and full screen picture. More traditional image compression techniques have their qualities defined at the time of compression, which can make them more than a little inflexible if at some later date one needs to use them in a way not foreseen at the time.

Using fractals, images can also be zoomed to reveal details without the pixellation and blockiness associated with the techniques available to date.

The data is simply 'reiterated' to fill in the gaps. Fractally compressed images are in any case easier for the eye to read, since they mimic the natural process. Even at extremely high compression ratios, or at high zoom levels, where the image might be expected to deteriorate beyond recognition, fractal images tend to appear as slightly blurry images rather than as a mass of barely indistinguishable pixels.

In terms of where we are now, the vision of the super-highway is in many ways just that, a future horizon, and the idea of fully 'wired' areas, a thousand channels of interactive TV, video on demand and home shopping have yet to hit the mainstream. However, given the upgrading of current linking technologies that carry voice and data, of bulletin board services and gateways into and out of the all consuming InterNet, we can foresee sporadic growth in an unregulated way - with the InterNet as the backbone of the first incarnation of the digital super-highway.

Most immediately, the implementation of Graphical User Interfaces (GUIs) (and the way in which fractal image compression will make it easier to include images as well as text) will make these services more and more usable and

tive and much more visual than they are at present. Teleshoppers will be able to see and stroll around a store; video previews and reviews will be instantly available and Video On Demand services will enable you to browse through listings, look at a clip and then download the video of your choice. And even if you are going out you will probably be able first to call on pictures of the theatre or restaurant or museum you want to visit, as well as book your tickets.


Hold on - We are connecting you

It has to be said in passing that this is a marketing person's dream - to be able to target, precisely and according to demographic

In essence the vast installed base of PCs will drive down component costs and drive technological advances very much faster than static technologies such as CD-I and 3DO on their own, and software advances will make 'surfing the net' immensely simpler.



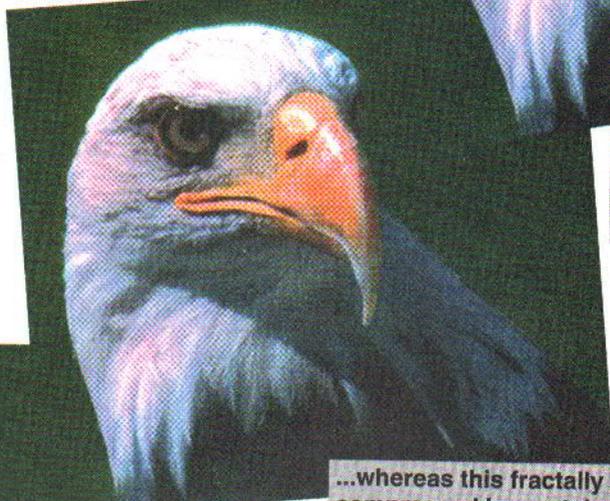...Reduced even further to 20KB, fractal images can show insignificant loss of detail. (Despite a transfer to print, virtually no difference can be seen even in the original photograph)



...whereas this fractally compressed image takes up only 40KB...

profile and a host of other criteria, the customers you want without requiring them to step outside of their doors.

As time goes by the 'front end' of all these on-line services will continue to be the personal computer, at least in some form. They

will form the basis of all interactive multimedia systems, while other devices and systems gradually migrate and become 'pluggable' to PCs. Both CD-I and 3DO have already announced plans to do just that. With the various communications technologies we have today gradually converging it is possible, even likely, that in the future some hybrid machine combining the qualities of television, videophone and general purpose computer will offer access to the super-highway via one control unit.

More Power to the PC

The GUI, however, is only the first of the massive computational requirements needed to mask the complexity of the underlying technology so that we are able to extract value from

the information super-highway. As the data itself becomes more visual even greater processing power will be needed to analyze and recognize images intelligently. The 'agents' that will process data intelligently for you, so that you only receive information on the subjects you want to learn about, will not develop on non-PC platforms; other technologies - the multimedia games machines, for instance - whilst they are maturing towards compatibility with the PC, do not have the competitive pressures of the PC platform. They cannot double in power and halve in price every eighteen months.

Today's PCs offer a vast installed base and a broad spectrum of niche markets (therefore providing low barriers to entry for software developers). This in turn leads to a proliferation of titles and applications, and still greater demand for PCs and power.



Image files take up huge amounts of disk space. This original uncompressed bitmap represents 1,181KB of storage...

accessible, and much more likely to become a part of every day life.

The services available on the InterNet now and accessible to an ever growing pool of users will inevitably be reflected in the services delivered on the full highway. On-line education, for instance, is available now, as is teleshopping. On an InterNet super-highway these services will be interac-

Seeing is believing

The key principle of all these developments, and the factor which links them all, is of course their dependency on the use of images. Where advanced compression techniques such as the Fractal Transform fit into the scheme of things is obvious - even with the fastest modem speeds and/or ISDN lines, raw images/visuals will always take up enormous space - with moving images the problem is simply exacerbated.


The fractal approach is a key enabling technology NOW and will continue to develop as the super-highway itself does. From still and moving image compression to intelligent image recognition the fractal architecture of images will, as we move into the late 1990s and the next millennium, be as important to the development of the digital super-highway as Euclidean geometry was to the development of CAD/CAM in the 70s and 80s. It may be unseen and (as yet) unknown to many but the developments in the fractal world will be key to the delivery, use, extension and development of the super-highway.

Biography

Alan McKeon, now International vice president of Iterated Systems, set up Iterated Systems Ltd. in 1991 as the UK subsidiary of Iterated Systems Inc. The UK was the first country to host an overseas office. Prior to joining Iterated Systems, Alan worked for Microsoft UK Ltd. where he was responsible for setting up a new sales channel via OEMs. He joined Microsoft from Dun & Bradstreet subsidiary Nielsen Marketing Research, where he established a pan-European specialist software division offering high value information analysis tools on the PC platform to leading FMCG retailers and manufacturers.

Alan has a BSc in Mathematics and Management Science from Manchester University.

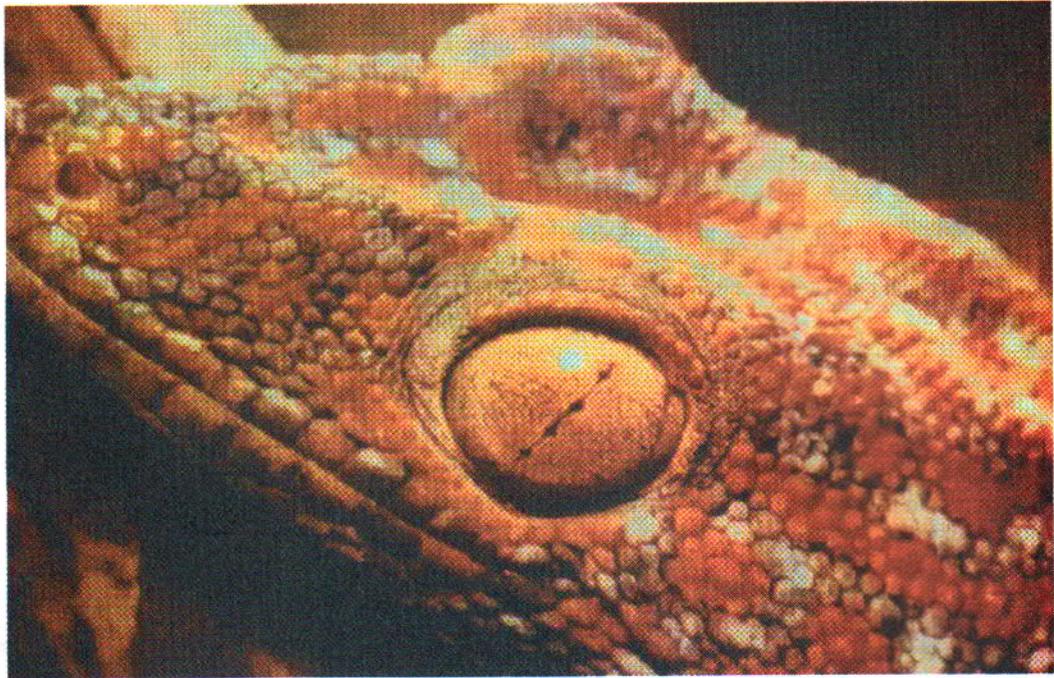Iterated Systems has grown since its inception to supply a range of products across a broad international base, offering ultra-high compression ratios to very small file sizes, fast decompression times and resolution independence.



The Fractal Transform's resolution independence enables pictures to be zoomed without blockiness. The first zoom (B) using traditional techniques, reveals the individual pixels that comprise the image. The second, fractal image (C), although zoomed to an even higher degree, shows only a slight blurriness and is much easier for the human eye to 'read'.


At last, a fully functional upgradeable PCB CAD system to suit any budget. Substantial trade-in discounts are available against other "professional" PCB design packages ...

... call now for details.

Board Capture

Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

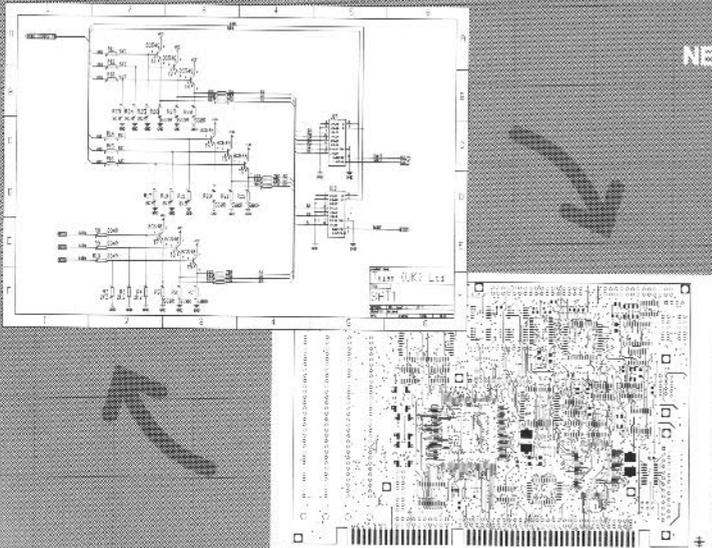

BoardMaker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

BoardMaker2 - Advanced level

- All the features of BoardMaker1 +
- Full netlist support - BoardCapture, OrCad, Schema, Tango, CadStar and others
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

NEW

Board Router

Gridless re-entrant autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing


Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)

Call, write or fax for more information or a full evaluation kit

Tsien (UK) Limited
Aylesby House
Wenny Road, Chatteris
Cambridge
PE16 6UT

Tel (0354) 695959
Fax (0354) 695957

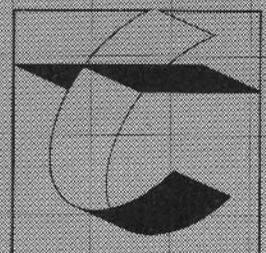

tsien

CIRKIT ELECTRONIC CONSTRUCTORS CATALOGUE

- ◆ 240 Pages
- ◆ 26 Sections
- ◆ Over 4000 lines
- ◆ Send for your copy today!

£1.90
+30p p+p



Cirkit

Cirkit Distribution Ltd

Park Lane • Broxbourne • Hertfordshire • EN10 7NQ • Tel: Sales (0992) 448899 • Fax (0992) 471314

