


# everyday electronics

FEB. 72


15p

**A NEW MAGAZINE  
BRINGING A FASCINATING  
HOBBY TO EVERYONE**

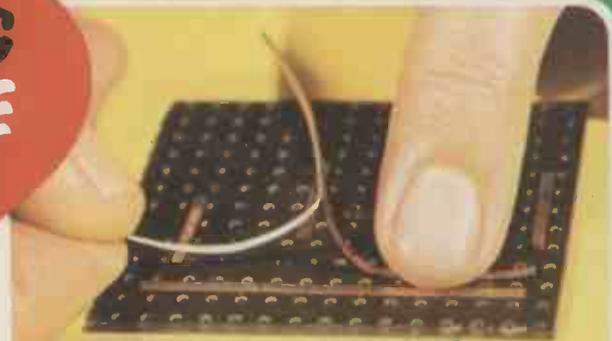**PROJECTS EASY TO CONSTRUCT  
THEORY SIMPLY EXPLAINED**



**STICK DOWN WIRING**

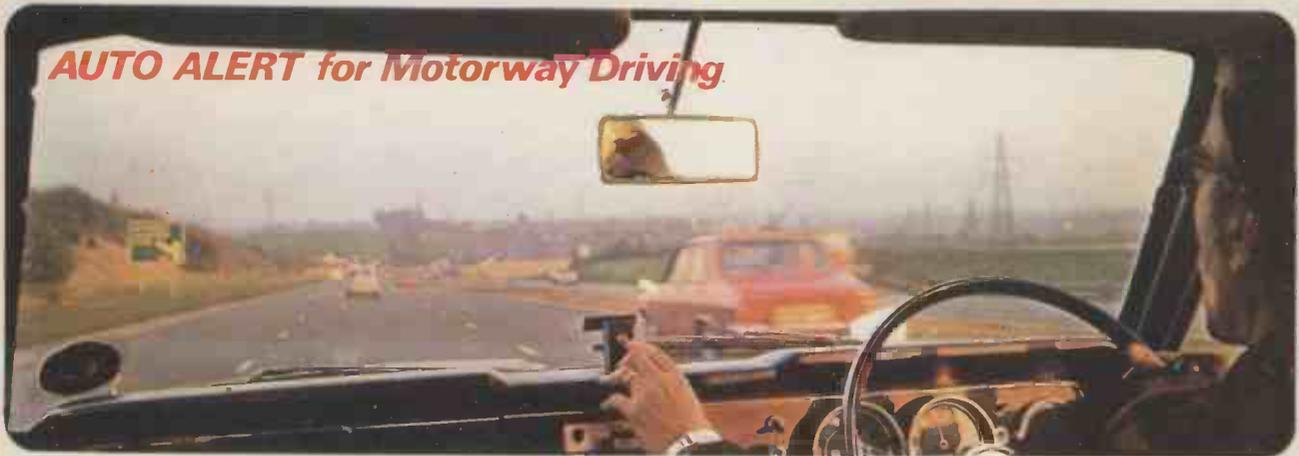

**AUTO ALERT for Motorway Driving**



**WAA WAA PEDAL**

**RAIN WARNING ALARM**



# ADCOLA Soldering Instruments add to your efficiency

## THE NEW 'INVADER'

### ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

\*Additional Stock Bits (illustrated) available

#### COPPER

B 38  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14  $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 24  $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

B 12  $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58  $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

#### LONG LIFE

B 42 LL  $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 38 LL  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL  $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 44 LL  $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

PRICE  
£1.85



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



**ADCOLA PRODUCTS LTD.,**  
(Dept. Y), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

\* Write for price list and catalogue

# SAFELOC

## of robust construction


Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

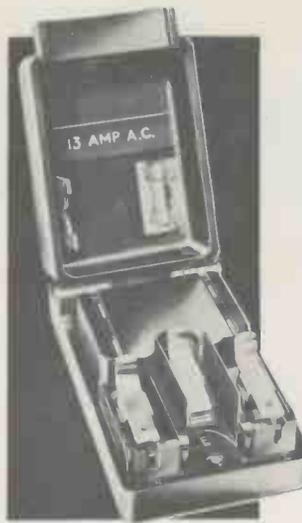Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.



If ordering by post, send cash with order.

PRICE £2.60+10p P.&P. EACH

Special bulk order wholesale and industrial rates on application



# RENDAR®


Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex. Tel. Burgess Hill 2642

### FELSTEAD (EE4) ELECTRONICS

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE

Selection from our list, sent free for stamped addressed envelope. (Free overseas). Cash with Order only—No COD or Caller service. Charges (Min. 6p.) in brackets after all items apply to G.B. & Eire only. Regret Orders under 25p. plus charges unacceptable. SAE please, for enquiries or cannot be replied to. Overseas Orders welcomed.

**RECORDING TAPE:** Finest quality/value British Mylar available: STANDARD 5" 600ft 36p; 5" 900ft 50p; 7" 1200ft 56p; LONG PLAY 5" 900ft 50p; 5" 1200ft 56p; 7" 1800ft 80p. (7p on 5" and 5" 9p on 7"). Other sizes. Cassettes and accessories in list. **WARTHERIGES:** All with standard fittings and stylus. Mono GP67 85p; Stereo-compatible Mono GP91/8C £1.10; STEREO GP93 £1.40; Stereo Ceramic GP94 £1.95. (6p) Comparatives shown in list with more types incl. Sonotone 9TACH Goldring &c. at lowest prices **DIAMOND STYLUS:** Single tip types: Acos GP37, GP59, GP65/67, GP71, BSR TC8/LP/ST; COLLARO O. P and DC284; GARRARD GC2, GC8, GC12, GC810; BONETTE BF40, O. P and T; PHILIPS 3301 (3060, 3066, 3302, 3304) 3010 (12, 13, 16); SONOTONE 197/207. ALL AT 40p each (6p). Double-try turn-over types (78 sap. on other side). For Acos GP73, GP91 (for cartridges GP93, GP94 &c.) GP918C (for stereo-compat. types) GP104, BSR BT4 (BT3, BT5), ST9 (BT8), ST12/14/15, SONOTONE 2TA, 2TA, 9TACH, PHILIPS 3306 (3310, 3224, 3228/22, GP280) GARRARD GCM21, 22, GC823, GK825 and 26, GCM21T and 22T, GK24T, GC8231, GK825T & 26T GCM31, GC836, GC835, GC838, KS40A, KB41B, etc. ALL AT 75p (6p). **DOUBLE DIAMOND STYLUS:** (Same dia. tip each side: no 78) for all types £1.50 (6p). **PICK-UP WIRE:** Super thin twin flex screened, sheathed, 6p per yard. (Up to 6 yds, 6p. over charges paid.) All sapphires in list. **MICROPHONES:** CRYSTAL: LAPEL 1", clip/hand, lead 3.5mm jack plug 32p (6p). CM20 Cream Plastic hand 52p; CM21 Grey Plastic Hand/Desk 62p; both have 3.5mm jack plug and lead (9p either). "STICK" 60 EL-02; CM70 "PLANET" Metal, tapered, with neck cord, adaptor for stands 11 47p; "MIG 91" hand/desk 81p; "MIG 96" Curved metal hand grip £1.00. All with leads (all 5p). **MICROPHONE INSERTS:** Diam. 1.75 or 0.9 either size 27p (Up to 6 for 6p). **DYNAMIC:** 200 Cardioid Ball, 60K/600 Ω, built-in volume control, on/off switch, special 20t lead, the best value anywhere 28-30; UD130, uni-dir. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4.30; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug 83-87 (27p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1.87 (27p) — or pair for stereo 54-25 changes paid. **SMALL 2 1/2" 3 Ω or 8 Ω, state which 37p (6p). More speakers in list. HEADPHONES:** High resistance 2000 Ω adjustable 92p (7p). **EARPIECES:** with lead and min. 2.5mm or 3.5mm (state which) jack plug, MAGNETIC 9p. **CRYSTAL (3.5mm plug only) 24p (up to 3 for 6p. any type). SOLDERING IRON:** Slim, modern, British high speed, 81", all parts replaceable, highest quality fully guaranteed £1.17 (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OUTPUT (3 Ω for OC73, &c.) £1.19. **DRIVER:** 15A81 12p, 12 for 6p). **CONNECTING WIRE:** Packs of 5 colla, each coil 5 dia., asstd. colla **SOLD CORE 14p. FLEXIBLE or SUPER THIN** for transistor wiring &c. either 18p. (Any pack 6p). **RETRACTABLE FLEXIBLE LEADS. (CURLIES):** With phono plug ca. end 6ft 23p, 12ft 38p. With phono plug/phono socket other end 6ft 25p, 12ft 42p (6p lead any type). **VIBRATORS:** 12V 4-pin non-synch 12HD4, 2 1/2" ex. pins 27p. SAME but 3 1/2" ex. pins. **USA, 20p. 12V 7-pin, synch. (12BR7) 2 1/2" ex. pins 62p (6p any type). TRANSISTORS:** AC128 12p, AF115 20p, AF116 16p, AF117 20p, OA 130p, OR 10p, OS 81 12p, OC44 14p, OC45, OC71, OC72, OC75, OC810, OC820, all at 12p each, OC81 18p, OC170 20p, OC171 12p, BY100/800piv 14p. Many more incl. power tubes, thyristors, &c., in list. **MAINS NEONS:** fly leads 10p. **NEON SCREWDRIVER (pocket tester) 17p (6p either).** **MAINS BATTERY ELIMINATOR:** Input 240V AC, Output 3, 6, 7.4 and 9V DC by switch selector, On/off switch, pilot lamp, leads, plug, adaptor to suit most transistor sets and cassette recorders. Suitable for model use: £3.15 (24p). **OUR CURRENT LIST** (see heading) includes more details of all above plus many other items, replacement parts, many unrepresented Special Offers, and cable, croc. clips, Volume controls, Din plugs, Co-Ax, standard, miniature, phono plugs, sockets and adaptors, Tape Recording and Record Player accessories, panel and Test meters and equipment, Multimeters, term. motors, test prods, switches—rotary, toggle, slide cabinet, lamp &c.—electrolytics, minis, Veroboard, valve holders, extending aerials for cars and portable sets, ind. lamps and bulbs, dials, mikes, telephone amplifiers and pick-ups, drive cord, inter-coms, capacitance and resistance testing boxes stereo headphones etc., etc.

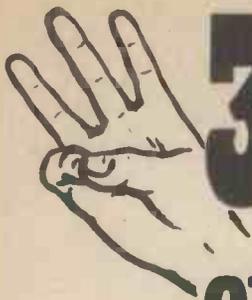

# 3 WAYS

## of obtaining components quickly & easily

HOME RADIO (Components) LTD.  
Dept. EE, 234-240 London Rd.,  
Mitcham, CR4 3HD. 01-648 8422

# 1

**CALL AT No. 240  
London Rd., Mitcham**

If you live within easy reach of Mitcham or are in the area at any time do call on us. We are almost opposite Mitcham Baths. We open 9 a.m. every weekday. On Wednesdays we close 1 p.m. and all other days, including Saturdays, 5.30 p.m. On Saturdays we have extra staff to deal with queries. We carry a vast stock of components, and 999 times out of a 1,000 we can immediately lay our hands on the particular item required.

# 2

**JOIN OUR CREDIT  
ACCOUNT SERVICE**

We began our Credit Account Service about 18 months ago and it has proved extremely popular. Little wonder! Our customers find it a very simple and convenient way of purchasing all their radio and electronic needs. We supply pre-paid envelopes and order forms and no matter how many orders you send us you make only one payment per month. There are several other advantages with our Credit Account Service. Please write or phone for details.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

# 3

**and  
ORDER BY MAIL  
OR TELEPHONE**

Although we are kept busy selling "over the counter" we supply even more by Mail Order. You can telephone any time of day or night, Sundays included. If you ring out of office hours a recording machine takes your message for us to deal with as soon as we open shop again. Our number is 01-648 8422. If you wish to order by post our address is in the panel at the top of the page. We deal with all orders promptly.



**WHICHEVER WAY YOU  
CHOOSE** you need the Home Radio Catalogue

In its 315 pages are listed over 8,000 components, over 1,500 of them illustrated. Each copy contains 10 Vouchers, each worth 5p when used as instructed. Free Supplements are supplied regularly to keep you up-to-date. The Catalogue costs 50p over the counter, or 70p including postage and packing.

*Post this Coupon with  
Cheque or PO for 70p*

*Please write Name and Address in block capitals.*

Name .....

Address .....



**HOME RADIO (Components) LTD.**  
Dept. EE, 234-240 London Rd., Mitcham, CR4 3HD



**DRILL CONTROLLER NEW IWK MODEL**  
Electronically change speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available. £2.25 plus 13p post and p.

**MAINS OPERATED CONTACTOR**

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 1/2 in. £1 each.



**NEED A SPECIAL SWITCH**

**Double Leaf Contact.** Very slight pressure closes both contacts. 5p each, 60p doz. Plastic push-rod suitable for operating 5p each, 45p doz.



**AUTO-ELECTRIC CAR AERIAL**

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v. positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £6 plus 25p post and ins.



**TOGGLE SWITCH**

3 amp. 250v. with fixing ring 7p each, 75p doz.

**MICRO SWITCH**

5 amp. changeover contacts. 9p each, £1 doz. 15 amp. Model 10p each or £1.05 doz.



**MINIATURE WAFER SWITCHES**

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 18p each, £1.80 dozen, your assortment.



**WATERPROOF HEATING ELEMENT**

26 yards length 70W. Self-regulating temperature control. 50p post free.

**BLANK SWITCH**

Double pole with neon let into side so luminous in dark. Ideal for dark room light or for use with waterproof element, new plastic case 30p each. 3 heat model 40p.



**CAR ELECTRIC PLUG**

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 38p each or 10 for £3.42.



**TREASURE TRACER**

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. £2.95 plus 20p post and insurance.



**QUICK CUPPA**

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12v. car model also available same price. Jug heater £1.50 plus p. & p. 14p.



**SNAP ACTION SLIDE SWITCH**

Rated 5v. 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuums, etc. 5p each, 10 for 45p.



**NUMICATOR TUBES**

For digital instruments, counters, timers, clocks, etc. Hi-vac XN. 3 Type £1.45 each, 10 for £13.



**12 WAY SUB-MINIATURE MULTI-CORE CABLE**

7-0078 copper cores, each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 20p per yard.



**LIGHT CELL**

Almost zero resistant in sunlight increases to 10 K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1in. dia. by 1/2in. thick. Rated at 500 MW, wire ended. 43p with circuit.

**0-8 AMMETER**

3in. square full vision for flush mounting. Moving iron instrument. Ideal for charger. Price 43p each 10 for £3.90.



**THE FULL-FI STEREO SIX**

The amplifier

sensation of the year you will be amazed at the fullness of reproduction and as the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled in simulated teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains/on/off switch. UNREPEATABLE PRICE is £9 plus 38p post and insurance.

**DISTRIBUTION PANELS**

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2 less plug £2.25 with fitted 13 amp plug; £2.40 with fitted 15 amp plug, plus 23p P. & I.



**THIS MONTHS SNIP**

Smiths 24 hour 2on/2off Time switch this is the popular model, as used in the Autocut and Morphy Richards time switches. Only needs a case and an output socket. 230v 50 cycles. Contacts switch up to 13 amps. Price £2.75p.



**TANGENTIAL HEATER UNITS**

This heater unit is the very latest type, most efficient, and quiet running. It is fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £3.50. 2kW Model as above except 2 kilowatts. £2.50. Don't miss this. Control 8 switch 25p. P. & P. 40p.



**POCKET CIRCUIT TESTER**

Test continuity of any low resistance circuit, house wiring, car electronics. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied). 30p or 2 for 50p post paid.



**COMPUTER TAPE**

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video audio sound. 1in. wide £1.00 plus 33p post and insurance, with cassette. 1/2 in. wide £1.00 plus 30p post and insurance with cassette. 1/4 in. wide 75p plus 25p post and insurance with cassette. Spare spools and cassettes—1in 75p. 1/4 in. 75p each plus 20p post and insurance.




**1 HOUR MINUTE TIMER**

Made by famous Smiths company, these have a large clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch £1-15.



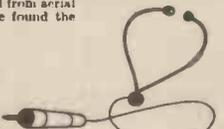**RADIO STETHOSCOPE**

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transducers and all parts including probe tube and crystal earpiece. £2—twin stethoscope instead of earpiece 75p extra post and ins. 20p.



**70 THINGS YOU CAN MAKE**  
Send S.A.E. today for list of 70 constructor projects—Instruments—alarms—counters—locks—radios, etc., etc.


**SOLDER GUN**

A must for every busy man, gives almost instant heat also illuminates job. Dual heat 100/140 watt £3.75 plus post and insurance 20p. BIG JOE 250 watt model £4.75 plus post and ins. 40p.



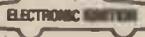**CAPACITOR DISCHARGE CAR IGNITION**

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We now supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price £4.95 plus 20p post. When ordering please state whether for positive or negative systems. Also available, ready made ignition systems for 6v. vehicles. £5.25 plus 20p.



**TYPE 25 RELAYS**

These are miniature relays. Size approx. 1 1/2 inch high x 1 1/2 inch wide x 1 1/2 inch deep. 4 change over silver/gold contacts. Contact rating lamp 100v D.C. Fitted with a plastic cover. Coil operates approx. 250 Mw D.C. available with the following coils: 28 ohm for 4v—7.5v 45 ohm for 1v—2.5v 52 ohm for 4.9v—6v 90 ohm for 5.5v—11.5v 130 ohm for 10v—15v 530 ohm for 17v—36v 1250 ohm for 27v—44v 2500 ohm for 31v—65v 5900 ohm for 27v—44v 75p each, 10 for £8.75p. Also one with 16,500 ohm coil but this has only 2 heavy duty change over gold contacts. Price £1.45.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

**DRIVER ALERT WAA-WAA PEDAL RAIN SENSOR**

and other features

To receive these kits promptly send approximate quoted price and we will refund any change.

Veroboard. We are now stocking this in various sizes. Prices as follows:

0-1	0-15	
2 1/2 x 3 1/2	22p	16p
2 1/2 x 5	24p	24p
3 1/2 x 5 1/2	24p	14p
3 1/2 x 5	27p	27p
2 1/2 x 3 1/2 (plastic)	75p	57p
17 x 3 1/2	100p	75p
17 x 5 (plain)	—	75p
17 x 3 1/2 (plain)	—	52p
17 x 2 1/2 (plastic)	—	37p
2 1/2 x 5 (plastic)	—	17p
2 1/2 x 3 1/2 (plastic)	—	15p
Pin intersection tool	47p	47p
Spot face cutter	37p	37p
Pkt. 50 pins	20p	20p

**FLOURESCENT CONTROL KITS**

Each kit comprises seven items—Choke, 2 tube ends, starter, holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-alien, mostly resin filled. Kit A—10-20 w. £1. Kit B—30-40 w. £1. Kit C—80 w. £1.20. Kit E—65 w. £1.90. Kit F for 8 1/2, 125 w. tube £1.75. Kit MF1 is for 6in., 9in. and 12in. miniature tubes £1. Kit MF2 for 21in., 13 w. miniature tube £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23 p on first kit then 18p on each two kits ordered. Kit F 33p then 23p for each kit ordered. Kit MF1 18p on first kit then 15p on each two kits ordered. Box Sign for Window Display, at home, office or shop, 2ft. wide x 14in. high x 5in. deep. This is an illuminated box sign made from sheet metal hammer finish enamel with a clear plastic window. You simply have your message printed or written on poster board or thick card. (Or use stick down letters available at most stationers). You will then have a box sign normally costing anything between £10-£15. Illumination is by a 2ft. fluorescent tube with control gear enclosed. Message card can be changed quite easily from hinged top back. Price £3 each, plus 65p post, etc. Enclosed Illuminated Box Sign. As previous item but with geared motor moving the message making it change eight times a minute. Very attention arresting. To use this for your own messages you would have to have each sign written on card then cut this up in strips which could be glued to the one supplied with the box sign. Price £4.50, plus 65p post and service. Geared Motor with take off socket. The gear train is driven by normal type induction motor and gives a final speed of 6 r.p.m. The motor is mounted behind a chrome plate through which the take off drive protrudes and was originally intended to drive a spit for cooking, is also ideal for driving models or for driving a colour changing disc for the local dance hall, discotheque, etc. Really well made assembly, Price £1.75 plus 25p post etc.

**2 1/2 KW FAN HEATER**

Three position switching to suit changes in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/2 kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control at safety cut-out. Complete kit £3.95. Post and ins. 38p.

**KITS FOR PREVIOUS PROJECTS**

- Kits of parts available as follows:—
- HOME SENTINEL INTRUDER ALARM** Electronics Components with case £3.75
- SNAP INDICATOR** All components but not case or battery 75p.
- WINDSCREEN WIPER CONTROL** All components including metal for chassis £2.00.
- RECORD PLAYER** All components, but not case, loudspeaker, record deck or pick-up £5.50
- DEMO DECK** All Components as listed £8.75
- ASTRON RADIO** Electronics parts less case £3
- REMOTE TEMPERATURE COMPARATOR** All electronic parts less case £4-25
- ELECTRO LAUGH** Parts, less case £2
- TRANSISTOR MICROPHONE** all parts £1.70

**J. BULL (ELECTRICAL) LTD.**

(Dept. E.E.) 7 Park Street, Croydon CRO 1YD  
Callers to 100/3 Tamworth Road, CROYDON

Everyday Electronics, February 1972

## STEREO AMPLIFIER SYSTEM FOR £21



Stereo amplifier with double wound mains transformer (200-250v. a.c.); 2 x ECL82 valves giving 2 x 2½W; printed circuit (10" x 3½") mounted on metal chassis. Ganged tone controls, sep. vol. controls; on-off switch; excellent channel separation. Output trans. for 3-ohm speakers. For crystal, ceramic cartridges or radio tuner. Only £6.25 (post 40p).

Beautifully finished teak or walnut wooden cabinets 10½" x 5½" x 7" deep, fitted 6" x 4" speakers, 3-ohm. £8 per pair (post 35p). Cabinets only £6 pair (post 25p).

**PACKAGE DEAL.** B.S.R. autochanger C129 fitted stereo cart., two speakers in cabs. (above), amplifier (above). All for £21 (carr. £1.50) All necessary audio plugs and leads supplied

## GLADSTONE RADIO

66 Elms Road, Aldershot, Hants.  
Telephone: 22240.

## Hi-Fi KITS



- \* INDUCTION OR SYNCHRONOUS MOTOR
  - \* FULL SIZE TURNTABLE WHEEL
  - \* EXCELLENT PERFORMANCE
  - \* RIGID BASE
- ILLUSTRATED THE V-300 THREE SPEED MODEL

FROM  
**£14.75**

OTHER MODELS AVAILABLE

- V-100 SINGLE SPEED
- RB101 SINGLE SPEED BELT DRIVEN
- P105 PICKUP ARM

POST COUPON OR WRITE FOR BROCHURE

## VALEK LTD

LARK STREET, DARWEN, LANCs. Tel. 71881

NAME .....

ADDRESS .....

## RUSSIA HERALDS THE DAWN OF A NEW ERA IN RADIO TECHNOLOGY!

ADVANCE 1972 model SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING SOME LOOKOUT OF DATE IN 1984!

THE FABULOUS **ASTRAD VEF 17** PORTABLE RADIO & COMMUNICATIONS RECEIVER

THE OFFER ONLY PROMISE!

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!

**28 TRANSISTORS AND DIODES!**  
**WAVEBANDS:**  
STANDARD LONG and MEDIUM  
Plus 5 SHORT WAVEBANDS  
Plus ULTRA SHORT WAVES  
(V.H.F. AM, FM, MW, LW, USW.)



BATTERY MODEL **£19.75** BOX POST ETC. 50p  
MAINS/BATTERY ELIMINATOR **£1.38** extra

WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!!

\*COMPARE ITS PERFORMANCE with **£75** RADIOS!

Just think of the year 1984 and the "perfect radio" that might be produced then with all the advanced qualities it could possibly have—now place the fantastic ASTRAD (VEF) 17 in front of you and switch on, and you'll see for yourself that the incredible Russians have done it all HERE AND NOW! It's the radio perfectionist's dream come true! THIS ONE SUPERSEDES ALL EARLIER MODELS! Complete with optional battery eliminator for both battery and mains use. We're almost giving them away at only £19.75—a fraction of today's Russian miracle price! We challenge you to compare performance and value with that of £75 radios. \* You can't lose, refund if not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto, for absolute "pin-point" station selection. Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! The Russians have really surpassed themselves this time, proving once again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space communications. YES, EVERY WAVEBAND instantly at your fingertips, including Standard Long, Medium Short and Ultra Short Waves to cover the four corners of the earth 24 hours a day, including all normal transmissions VHF, AM, FM, MW, LW, USW, plus local & new stations not yet operational, and messages from all over the world. Unique side control waveband selection unit gives incredible ease of station tuning! Superb, sweet tone—controlled from a whisper to a roar that will fill a hall! Genuine push-pull output ON/OFF volume and separate Treble and Bass tone controls for perfection of reproduction and tone! Press-button dial illumination! Runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 33in. approx. It's also a fabulous CAR RADIO. Elegant Black and Chrome case. SIZE 12in. x 9in. x 4in. overall approx. Designed to give years of perfect service (UK service facilities and spares available for years to come if ever necessary!). With WRITTEN GUARANTEE. Simple instructions and circuit diagram. ONLY £19.75 (with mains battery eliminator £1.38 extra. POST, ETC., 50p. Standard "longlife" batteries plus extra sensitive earphone for personal listening 25p extra if required. Can also be used through extension amplifier, tape recorder or public address system. (Sorry—we cannot change these new radios for any earlier models already purchased.) Refund if not delighted.

BRAND NEW! SAVE **£13.98** NOW! FIRST CLASS MAKER'S OF LUXE MODEL!

Cassette TAPE RECORDER and PLAYER



RECOMMENDED LIST PRICE **£26.97**  
OUR PRICE **£12.99**  
POST ETC 30p

WITH REMOTE CONTROL MICROPHONE

MAKE NO MISTAKE—this is the EXPENSIVE model with "PIANO KEYBOARD" CONTROL PANEL and SPECIAL RECORDING LEVEL! SAVE £13.98! Due to price we cannot mention famous maker's name—but rest assured you're getting one of the BEST! Our latest cassette model—no fiddling with awkward tape and reels. Just "slap in" a cassette and off you go! (takes 30-, 60- and 90-minute standard Philips Cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Separate volume control! Rapid Rewind! Beautiful tone from a whisper to a roar! Completely self-contained—record everywhere. Separate jacks for remote control microphone, etc. Size 9" x 4½" x 2½" overall approx. Case design can vary slightly. With carry handle. With WRITTEN G'TEE and instructions. Only £12.99, post 30p. ALSO AVAILABLE: SPECIAL BATTERY/MAINS AC/DC MODEL, ready to plug in. £3.50 extra if required. Refund g'tee. BONUS one per customer: Cassette tape, set of Standard batteries and microphone stand all for 51p extra if required.

## SHOPERTUNITIES LTD.

Dept. EE/F/4, 164 UXBRIDGE ROAD (facing Shepherd's Bush Green), LONDON W12 8AQ. (Thurs. 1. Fri. 7). Also 37/39 HIGH HOLBORN (opposite Chancery Lane) LONDON, W.C.1. (Thursday 7 p.m.). BOTH STORES OPEN.

## FIND BURIED TREASURE! Transistorised Treasure Locator

This fully portable transistorised metal locator detects and tracks down buried metal objects—It signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES, ETC.** Etc. Extremely sensitive, will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. **ONLY £2-37**

**ONLY £2-37**  
built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2-37 + 25p p. & p.** (Sectional handle as illustrated. 75p extra). Parts available separately. Made up looks worth £15!

## Eavesdrop on the exciting world of Aircraft Communications.

### V.H.F. AIRCRAFT BAND CONVERTOR

**ONLY £2-37**  
Listen in to AIR-LINES, PRIVATE PLANES, JET PLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower, Hear for yourself the disciplined voices hiding tenseness on talk down. Be with them as they take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, KINGSTON, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do to extend rod aerial, place close to any ordinary medium wave radio (even tiny portables). **NO CONNECTIONS WEAR-NEVER NEEDED.** **SEND ONLY £2-37 + 25p p. & p.** for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

## SHORTWAVE TRANSISTOR RADIO



only  
**£2-25**

Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2". Only £2-25 + 17p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

## INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY  
**£2-75**



**CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT?** Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. **No soldering necessary.** Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. **SEND £2-75 + 25p p. & p.** (parts available separately).

## ELECTRONIC ORGAN



ONLY **£2-75**

Don't confuse with ordinary electronic organs that simply blow air over mouth-organ type reeds etc. Fully transistorised. **SELF CONTAINED LOUDSPEAKER.** Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering necessary, Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated step-by-step, simple instructions. **ONLY £2-75 + 25p p. & p.** for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

## Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY **£4-95**



**FULLY TESTED & INSTALLED PRIG-TORISED BUILT CIRCUIT METAL DETECTOR MODULE.** Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and **YOU HAVE A PORTABLE TREASURE LOCATOR EARLY WORTH ABOUT £20!** Extremely sensitive—penetrates through earth, sand, rock, water, etc.—**EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC.** Signals exact location by "beep" pitch increasing as you near buried metallic objects. **So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIL!** £4-95 + 30p carr. etc. (High quality Danco Stethoscope headphones £2-75 extra if required.) **EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.**

## BUILD 5 RADIO AND ELECTRONIC PROJECTS

only **£1-97**



Amazing Radio Construction set! Become a radio expert for £1-97. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 37p extra as illus. (if required) (parts available separately) no soldering necessary. **Send £1-97 + 25p p. & p.**

## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

**CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES!** Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. **IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron.** Once used you will never want to be without it—**TAKE IT ANYWHERE.** Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). **CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE** using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones. Components, nuts, screws, wire, etc. no soldering. **£2-25 + 25p p. & p.** Parts available separately.



Only **£2-25**

**CONCORD ELECTRONICS LTD. (EE 4) 8 Westbourne Grove, London, W.2. Callers welcome 9 a.m.-6 p.m. inc. Saturday**

## G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

**SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE ! ! ! !**

<b>RESISTORS, 1/4 watt</b>		<b>TRANSISTORS</b>	
assorted	100 50p	P.N.P. Untested but mainly O.K.	50 50p
Wire-wound 1 to 3 watt	20 50p	N.P.N. Untested but mainly O.K.	50 50p
5 to 7 watt	15 50p	OC71 equivalent	5 50p
10 watts	10 50p	Light-sensitive Diodes	10 50p
	12 50p	(These produce up to 1 ma from light)	
<b>MULTI-TAPPED PAPER CONDENSERS</b>		OC44 Mullard 1st grade	4 50p
TV types	50 50p	OC45 Mullard Boxed	5 50p
Miniature	15 50p	2G378 Output, Marked	5 50p
<b>ELECTROLYTIC CONDENSERS</b>		2G371 Driver, Marked	5 50p
Suitable for Mains		AS5 22, Marked	5 50p
Radio/TV	10 50p	BY 127 Rectifiers	4 50p
Transistor types	20 50p	AM407 Rectifiers	4 50p
Mixed (both types)	15 50p	(1200V)	
<b>POLYSTYRENE CONDENSERS</b>		STC 3/4 Rectifiers	6 50p
MULLARD POLYESTER COND.	50 50p	DIODES (OA 81 & OA 91)	40 50p
SILVER MICA	100 50p	<b>WIRE</b>	
<b>WIRE-WOUND 3-Watt SLIDERS</b>		Solid Core, Insul. 100yds.	50p
Assorted	15 50p	Stranded ditto 50yds.	50p
<b>NUTS AND BOLTS. Mixed length/type</b>		<b>SOLAR CELLS</b>	
8 B.A.	100 50p	Large Selenium	2 50p
6 B.A.	100 50p	Small	3 50p
4 B.A.	100 50p	(6 cells will power a Micro-matic radio)	
2 B.A.	100 50p	<b>CO-AXIAL CABLE</b>	
<b>METAL SPEAKER GRILLES</b>		Semi Air-spaced 15yds.	50p
7 1/2in. x 3 1/2in.	6 50p	<b>CRYSTAL TAPE RECORDER MIKES</b>	
<b>EARPIECES, MAGNETIC</b>		CYRSTAL EARPIECES	1 50p
No Plug	6 50p	3-5mm Plug	2 50p
2-5mm Plug	4 50p	TRANSISTORISED Signal Kit	1 50p
3-5mm Plug	4 50p	TRANSISTORISED Signal Tracer Kit	1 50p
<b>500 MICRO-AMP LEVEL METERS</b>		TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 ma. meter as indicator)	1 50p
<b>VEROBOARD, TRIAL PACK 5 BOARDS + CUTTER</b>	50p		

**STOCKTAKING CLEARANCE! IMPOSSIBLE TO REPEAT!** We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.

Gross weight 2 lb. ... .. £1 (postage 20p)  
Gross weight 5 lb. ... .. £2 (postage 30p)

**Unrepeatable Offer ! ! ! !**  
**Surplus VEROBOARDS, 3 1/2" x 2 1/2" x .15"**  
**Only 10p each or £1-00 per dozen**

## TANTALUM CAPACITORS. COMPARE THE PRICE—ONLY 10p EACH ! ! ! !

Sub-miniature types	Miniature types	5-6 µF	35 volts
0.047µF 50 volts	0.022µF 20 volts	8.2 µF	10 volts
0.056µF 50 volts	0.033µF 20 volts	8.2 µF	35 volts
0.07 µF 20 volts	0.047µF 20 volts	15 µF	35 volts
0.1 µF 20 volts	0.068µF 35 volts	18 µF	35 volts
0.1 µF 50 volts	0.12 µF 35 volts	22 µF	15 volts
0.18 µF 20 volts	0.15 µF 35 volts	27 µF	120 volts
0.33 µF 35 volts	0.22 µF 50 volts	56 µF	15 volts
0.47 µF 35 volts	0.47 µF 50 volts	56 µF	20 volts
0.68 µF 20 volts	0.68 µF 35 volts	150 µF	6 volts
1.0 µF 15 volts	0.68 µF 50 volts	Standard	
2.2 µF 3 volts	1.0 µF 75 volts	6.8 µF	50 volts
2.7 µF 35 volts	1.8 µF 20 volts	7.5 µF	20 volts
3.0 µF 12 volts	2.2 µF 20 volts	8.2 µF	150 volts
10.0 µF 1.5 volts	2.7 µF 50 volts	12 µF	35 volts
	3 µF 12 volts	12 µF	50 volts
	3.3 µF 15 volts	39 µF	20 volts
	4.7 µF 35 volts	10 µF	25 volts
	5.6 µF 6 volts	35 µF	050 µF 15 volts
		6 volts	270 µF 6 volts

## NEW ! NEW ! NEW ! NEW !

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light-sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner. Light sensitive aerosol spray ... .. £1  
Developer spray ... .. 50p

**G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.**

# BUDGET HIGH-FIDELITY STEREO SYSTEMS



**ONLY**  
**£40-95**  
carr. £1.75

**PREMIER STEREO SYSTEM "ONE"** Consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loud-speaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Mono/Stereo switch. Stereo Headphone socket. Black leatherette cabinet with aluminium front panel. Size: 12½" x 6½" x 2½". (Amplifier available separately if required £16.25. Carr. 40p).

**ONLY**  
**£57-75**  
carr. £1.75

**PREMIER STEREO SYSTEM "THREE"**. This consists of KLINGBE K6003 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pick-up, tuner, tape in and out. Stereo earphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone STAHGD diamond stereo cartridge. A pair of HMF Speakers size 16½" x 10½" x 9" fitted EMI units complete the matching system. **ONLY £57-75.** Carr. £1.75.

**PREMIER STEREO SYSTEM "TWO"**, as above but with Garrard SP25 MK III and magnetic cartridge. **ONLY £48.** Carr. £1.75.

**FREE**

**STEREO HEADPHONES**  
and all leads and plugs supplied with all systems.

## PREMIER HI-FI OFFERS

- Philips 580 Stereo Amplifier (List £29-00) **£21-00**
- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52-50) **£39-50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49-00**
- Metrosound ST20E Stereo Amplifier in teak case (List £28-50) **£28-50**
- Golding GL75 less cartridge (List £41-61) **£29-00**
- Garrard SP25 III with Goldring G800 cartridge (List £28-35) **£15-50**
- Garrard AP76 less cartridge **£19-50**

Garrard 3500 with Sonotone 9TA stereo cartridge (List £15-50) **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£14-00**

Carriage and Insurance 50p extra any item.

## SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID PERSEPX COVER. Total list price over £34.

PREMIER PRICE

**£18-90**

P. & P. 50p.



## HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.

**£2-47**

P. & P.

STEREO STETHOSCOPE SET Low Imp. £1.25

P. & P. 10p

MONO STETHOSCOPE SET Low Imp. 52p. P. & P. 10p.



## E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2½in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.

**£3-47**

P. & P. 40p

## NEW LOW COST PREMIER 800 STEREO AMPLIFIER



A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 6½" x 2½".

**ONLY £16-25** Carr. 40p.



## WELLER "EXPERT" SOLDER GUN.

Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 P & P watt. 240 volt A.C. **£4-25** 30p

"Markeman" Soldering Iron. Lightweight ¼" pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. £1-50 P & P 15p



## TAPE CASSETTES

- C60 (60 min.) 37p 3 for £1.05
- C90 (90 min.) 62p 3 for £1.80
- C120 (120 min.) 87p 3 for £2.55

P. & P. 5p.

**FREE CASSETTE HEAD CLEANER** with every 10 cassettes purchased.

All cassettes can be supplied with library cases at 3p. extra each

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

- |                                    |                               |
|------------------------------------|-------------------------------|
| LP3 3' 250' P.V.C. 28p             | LP6 6½' 1800' P.V.C. 75p      |
| TT3 3½' 450' POLYESTER 37p         | DT6 6½' 1800' POLYESTER £1-12 |
| DT3 3½' 600' POLYESTER 57p         | TT6 6½' 2400' POLYESTER £1-87 |
| SP5 5' 600' P.V.C. 42p             | ET7 7' 1200' P.V.C. 62p       |
| LP5 5' 900' P.V.C. 50p             | LP7 7' 1800' P.V.C. 75p       |
| DT5 5' 1200' POLYESTER 75p         | DT7 7' 2400' POLYESTER £1-25  |
| TAPE SPOOLS 3" 5p, 5", 5½", 7" 9p, | TT7 7' 3600' POLYESTER £2-50  |
- Post and Packing 3" 5p, 5", 5½", 7" 10p. (3 reels and over Post Free).



# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451

OXFORD ST

TOTTENHAM COURT RD

DOMINION

# Sinclair Q16/Micromatic

## Q16 High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies without loss.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

## Specifications:

**Construction:** Special sealed seamless sound or pressure chamber with internal baffle.

**Loading:** up to 14 watts RMS.


**Input Impedance:** 8 ohms.

**Frequency response:** From 60 to 16,000 Hz. confirmed by independently plotted B and K curve.

**Driver unit:** Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension for excellent transient response.

**Size and styling:** 9½ in. square on face x 4½ in. deep with neat pedestal base. Black all over cellular foam front with natural solid teak surround.

**Price £8.98.**

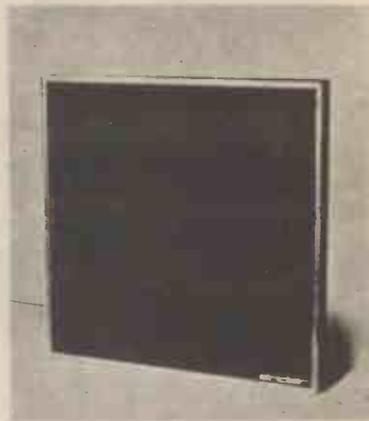

## Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided, matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

## Specifications:

**Size:** 36 x 33 x 13 mm (1.8 x 1.3 x 0.5 in.)

**Weight:** including batteries, 28.4 gm (1 oz.)

**Case:** Black plastic with anodised aluminium front panel and spun aluminium dial.

**Tuning:** medium wave band with bandspread at higher frequencies (550 to 1,600 KHz).

**Earpiece:** Magnetic type.

**On/off switching:** By inserting and withdrawing earpiece plug.

Kit in pack with earpiece, case, instructions and solder **£2.48.**

Ready built, tested and guaranteed, with earpiece **£2.98.**

*Two Mallory Mercury batteries type RM675 required from radio shops, chemists, etc.*



To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address


for which I enclose cash/cheque/money order

E.E. 4A

Sinclair Radionics Ltd., London Rd, St. Ives  
Huntingdonshire PE17 4HJ.  
Telephone St. Ives (048 06) 4311

**sinclair**
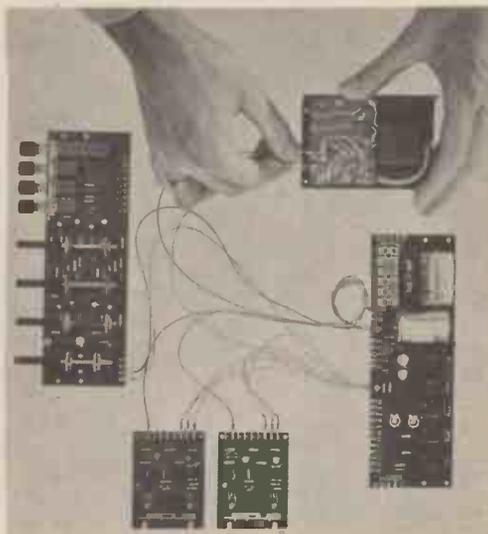
# Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same – there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative – Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one – Masterlink – which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together – the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

**Guarantee** If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

**sinclair**

Sinclair Radionics Ltd., London Road,  
St. Ives, Huntingdonshire PE17 4JH.  
Telephone: St. Ives (04806) 4311

## Specifications

Output – 30 watts music power (10 watts per channel R.M.S. into 3 Ω).

Inputs – Mag. P.U. – 3mV correct to R.I.A.A. curve 20–25,000 Hz ± 1dB. Ceramic pick-up – 50mV. Radio – 50 to 150mV. Aux. adjustable between 3mV. and 3V.

Signal to noise ratio – Better than 70dB.

Distortion – better than 0.2% under all conditions.

Controls – Press buttons for on-off, P.U., radio and aux. Treble +15 to –15 dB at 10 kHz. Bass +15 to –15 dB at 100 Hz. Volume, Stereo Balance.

Channel matching within 1dB.

Front panel – brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

**£29.95**

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE17 4JH

Please send Project 605 post free  Details and list of stockists

Name .....

Address .....

for which I enclose £29.95 cheque/money order/cash. E.E. 4B

### BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 50 cycle, 0.38 amp (Type 2) 28 r.p.m. Torque 20lb inch. Reversible. 1/80th h.p. 50 cycle, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. Input. Price, either type £3.15 plus 27p P. & P. or less transformer £2.13 plus 27p P. & P.

### 12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of approx. 125 RPM. Size 4 1/2" x 2 1/2" dia. Price 95p incl. post.

### 230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox. 1 R.P.M. cw 1 R.P.H. A/cw 10 R.P.H. A/cw 30 R.P.M. cw 2 R.P.H. cw 15 R.P.H. A/cw 60 R.P.M. cw 3 R.P.H. A/cw 20 R.P.H. cw 6 R.P.H. cw 30 R.P.H. cw  
cw = Clockwise. A/cw = Anti-clockwise rotation. Fraction of makers' price. All at 75p incl. P. & P.

### G.E.C. 12 WAY 15 AMP. CONNECTORS

NEW in maker's carton. BAKELITE £1-25 per doz. FLEXIBLE £1-50 per doz. Post paid (Minimum 1 doz.)

### PROGRAMME TIMERS

(Mfr. by 'Magnetic Devices Ltd.'). 240V A.C. 5 r.p.m. 'Crouzet' motor. Drives 15 cams, each operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW PRICE: £5-75. P. & P. 25p.

### 230V AC SOLENOID

Extremely powerful with approx. 14lb pull, 1" travel. Fitted with mounting feet. Size: 4" long, 2 1/2" wide, 3" high. £2-00 incl. P. & P.

### 230-250 VOLT A.C. SOLENOID

(Similar to above illustration). Approx. 1 1/2 lb. pull. Size of feet 1 1/2" x 1". Price 85p incl. P. & P. Manufactured by Westool Ltd.

### 18-24 VOLT D.C. SOLENOID

Size o.a.l. 3 1/2" x 1 1/2" x 1". Maximum push 1" at approx. 1 lb. PRICE: 75p incl. P. & P.

### MINIATURE RELAYS

9-12 volt D.C. operation. 2 c/o. 500 M.A. contacts. Size only 1 in. x 1/2 in. x 1 in. PRICE: 58p. Post paid.

30-36 volt D.C. operation. 2 c/o 500 M.A. contacts. 3,200 ohm coil. Size only 1 in. x 1 in. x 1 in. PRICE: 45p. Post paid.

### YENNER Electric Time Switch

200/250V Ex. G.P.O. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2-75, 15A £3-25, 20A £3-75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.

### MICRO SWITCH

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 incl. post. (Min. order 20)

### "HONEYWELL" LEVER OPERATED MICRO SWITCH

15 amps. 250 volt A.C. c/o contacts. NEW in maker's carton. Price: 10p for £1-90 incl. P. & P.

### VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/140V a.c. 50/60 OUTPUT

VARIABLE 0.260V

All Types (and Spares)

from 1 to 50 amp from stock.

SHROUDED TYPE

1 amp, £7-00 2.5 amp, £8-05

5 amp, £11-75

10 amp, £22-50 20 amp, £49-00

15 amp, £25-00 25 amp, £58-00

37.5 amp, £82-00 50 amp, £98-00

All plus £1-00 carr. where not specified.

OPEN TYPE (Panel Mounting) 1 amp, £4-75.

1 amp, £7-00 2 1/2 amp, £8-05. Carr. 40p on open type.

### Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 200 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 140 mA. Diameter 3/4 in. Shaft length 2 in, dia. 1/8 in. All at £1-50 each. P. & P. 5p.

50 WATT. 1/5/10/25/50/100/250/500/1/1/1/2-5/5kΩ. All at £1-12 each. P. & P. 11p.

25 WATT. 10/25/50/100/250/500/1/1/1/2-5/3-5/5kΩ. All at 78p each. P. & P. 15p.

### STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and trigger circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT Speed adjustable 1 to 36 Flash per sec. All electronic components included. Veroboard S.C.R. Uniunction Xenon Tube and instructions £6-30, plus 25p P. & P.

NEW INDUSTRIAL KIT Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10-50. P. & P. 50p.

HY-LIGHT STROBE KIT This strobe has been designed and produced for use in large rooms, halls and the photographic field and utilises a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12-00. P. & P. 50p.

SPECIALLY DESIGNED, FULLY VENTILATED METAL CASE, including reflector. £40.00 P. & P. 45p. Post paid with kit.

### THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe. Incorporating:

- Heavy duty power supply.
- Variable speed from 1-23 flash per sec.
- Reactor control circuit producing an intense white light.

The brilliant light output of the "SUPER" HY-LIGHT gives fabulous effects with colour filter. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.

ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Light Kit including reflector £70.00 P. & P. 45p. 7-inch POLISHED REFLECTOR. Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.

### RELAYS

New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

1	2	3	4	1	2	3	4
45	6-9	2 HD M	50p	700	15-35	2 c/o HD	73p*
185	12-18	4 c/o	73p	700	16-24	6M	65p*
230	9-12	4 c/o	78p*	1,250	24-36	4 c/o	63p*
280	9-12	2 c/o	73p*	2,500	36-45	6M	63p*
600	18-32	4 c/o	78p*	2,400	30-48	4 c/o	50p*
700	16-24	4M 2B	63p*	5,800	40-70	4 c/o	63p*
700	16-24	2 c/o	78p*	9,000	40-70	2 c/o	50p*
700	12-24	2 c/o	63p*	15k	85-110	6M	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty, All Post Paid. \*Including Base.

### 12 VOLT D.C. RELAY

Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)

### 'DIAMOND H' 230 VOLT A.C. RELAYS (UNUSED)

Three sets c/o contacts rated at 5 amps. Price: 50p P. & P. 10p. (100 lots £40-00 incl. P. & P.)

### 'KEY SWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. BOXED. Price: 40p. P. & P. 5p. (100 lots £32-00 incl. P. & P.)

### 230 VOLT A.C. SOLENOID OPERATED FLUID CONTROL VALVE

Adjustable flow control, all metal construction. Will handle hot or cold liquids, water, oil, paraffin, etc. Available with 1/2 in. inlet/outlet, or 3/8 in. inlet/outlet. Either type £1-50 P. & P. 20p

## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt —£3-20. Kit Form £2-70

300 Watt —£2-70. Kit Form £2-20

All plus 10p post and packing.


Please send C.W.O. to:—

## DEXTER & COMPANY

5 UELSTER HOUSE, 19, KING STREET, CHESTER CH1 2AH Tel: 0244-25883, As supplied to H.M. Government Departments.

## VEROSTRIP

LENGTH 8'5"

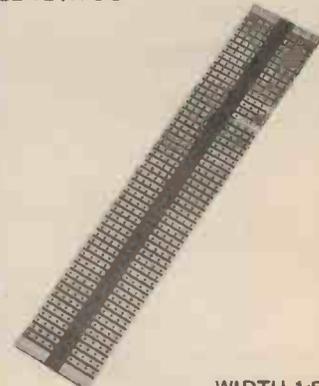

WIDTH 1'5"

Available from your Local Retailer

0.1 and 0.15 pitch Vero Strip is suitable for all applications where Tag Boards can be used.



VERO ELECTRONICS LTD. INDUSTRIAL ESTATE CHANDLERS FORD HANTS.


# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
Dept. E.E. 57 BRIDGMAN ROAD, LONDON, W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.  
9 LITTLE NEWPORT ST.  
LONDON WC2H 7JJ 01-437 0579



# your soldering appliance specialists.

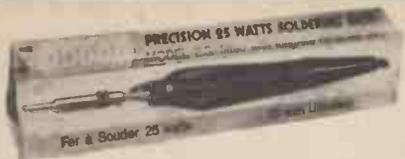

**E.240** 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price **£1.80**.

**ES.240** 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit and packed in a transparent display box. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price **£1.83**



**CN.240/2** Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price **£1.70**

**CN.240** Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price **£1.70**

**G.240** Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price **£1.83**.



**CCN.240** New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety: fitted with 3/32" iron coated bit. Spare bits 1/8", 3/16" and 1/4" available. Can also be supplied for 220 volts. Price **£1.80**


**CCN.240/7** The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price **£1.95**



## SK. 2 SOLDERING KIT


This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price **£2.40**.

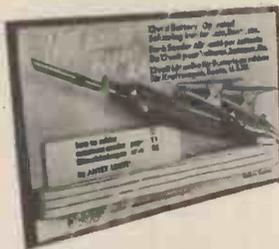
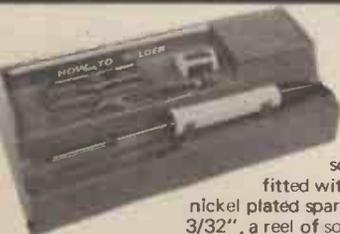
## MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price **£1.95**.




## SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price **£2.75**
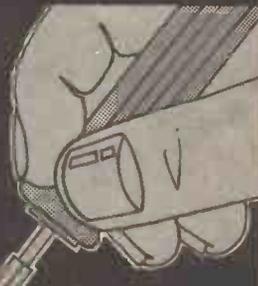
# sign here to answer all your soldering problems.



from electrical, radio or car accessory shops or from **Antex Ltd., Freeport** (no stamp required) **Plymouth**  
**PL1 1BR Telephone 0752 67377/8**

Please send the Antex colour catalogue.

Please send the following:

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I enclose cheque/P.O./Cash (Giro No. 2581000)

Name \_\_\_\_\_

Address \_\_\_\_\_

EE.4

**BROAD BAND NEW GUARANTEED**

**SEMICONDUCTORS & COMPONENTS**  
SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

**RETURN OF POST SERVICE**

**TRANSISTORS**

20301 20p	2N3404 32p	40310 45p	BC212L 13p	B8X28 32p	NKT281 27p
20302 20p	2N3405 45p	40311 35p	BCY30 27p	B8X90 32p	NKT401 27p
20303 20p	2N3414 27p	40312 45p	BCY31 30p	B8X91 32p	NKT402 27p
20306 42p	2N3415 27p	40314 37p	BCY32 50p	B8X76 22p	NKT403 75p
20308 30p	2N3416 37p	40320 47p	BCY33 25p	B8X77 27p	NKT404 62p
20309 30p	2N3417 37p	40323 32p	BCY34 30p	B8X78 27p	NKT405 75p
20371 15p	2N3570 21.25	40324 47p	BCY38 40p	B8Y10 27p	NKT406 62p
20374 20p	2N3572 97p	40326 37p	BCY39 60p	B8Y11 27p	NKT431 62p
20381 22p	2N3605 27p	40329 30p	BCY40 50p	B8Y14 15p	NKT453 62p
20404 22p	2N3606 27p	40330 47p	BCY42 15p	B8Y25 17p	NKT459 62p
2N696 20p	2N3607 27p	40347 87p	BCY43 15p	B8Y26 17p	NKT603F82p
2N697 17p	2N3702 11p	40348 42p	BCY54 32p	B8Y27 17p	NKT613F 32p
2N698 25p	2N3703 10p	40360 52p	BCY58 22p	B8Y28 17p	NKT674F 30p
2N705 12p	2N3704 11p	40361 47p	BCY59 22p	B8Y29 17p	NKT677F 30p
2N706 12p	2N3705 10p	40362 57p	BCY60 97p	B8Y32 25p	NKT713 25p
2N709 62p	2N3707 11p	40406 57p	BCY71 25p	B8Y37 25p	NKT10419 30p
2N718 25p	2N3708 07p	40407 40p	BCY72 17p	B8Y38 22p	NKT10439 37p
2N724 30p	2N3709 09p	40408 52p	BCZ10 27p	B8Y39 22p	NKT10519 37p
2N727 30p	2N3710 09p	40410 52p	BCZ11 42p	B8Y40 22p	NKT10519 37p
2N914 17p	2N3711 15p	40467A 57p	BD116 1.25	B8Y61 32p	NKT2039 32p
2N916 17p	2N3715 1.25	4060A 35p	BD121 60p	B8Y52 32p	NKT2039 32p
2N918 20p	2N3716 1.30	4060B 57p	BD122 82p	B8Y53 37p	NKT2039 32p
2N920 22p	2N3791 22.06	AC107 30p	BD124 60p	B8Y54 40p	NKT2039 37p
2N930 27p	2N3819 35p	AC126 20p	BD131 75p	B8Y56 90p	NKT80111 37p
2N1090 22p	2N3823 97p	AC127 25p	BD132 85p	B8Y78 47p	NKT80111 77p
2N1091 22p	2N3854 27p	AC128 20p	BDY10 1.25	B8Y78 45p	NKT80112 77p
2N1131 25p	2N3854A 27p	AC154 22p	BDY11 1.62	B8Y82 52p	NKT80112 77p
2N1132 25p	2N3855 27p	AC156 25p	BDY17 41.50	B8Y90 57p	NKT80112 77p
2N1302 17p	2N3855A 27p	AC187 62p	BDY18 1.62	B8Y95A 12p	NKT80113 77p
2N1303 17p	2N3856 30p	AC188 37p	BDY19 1.97	B8W41 42p	NKT80211 11.12
2N1304 22p	2N3856A 30p	ACY17 27p	BDY20 1.12	B8W70 42p	NKT80211 11.12
2N1305 22p	2N3858 25p	ACY18 25p	BDY38 97p	C111 75p	NKT80212 92p
2N1306 25p	2N3858A 30p	ACY19 25p	BDY60 1.25	C424 27p	NKT80212 92p
2N1307 25p	2N3859 27p	ACY20 25p	BDY61 1.25	C425 55p	NKT80213 92p
2N1308 30p	2N3859A 30p	ACY21 25p	BDY75 1.00	C426 40p	NKT80213 92p
2N1309 30p	2N3860 30p	ACY22 20p	BF115 25p	C428 37p	NKT80214 92p
2N1307 17p	2N3866 11.50	ACY28 20p	BF117 47p	C744 30p	NKT80214 92p
2N1313 25p	2N3877 40p	ACY40 20p	BF163 37p	D16P1 37p	NKT80214 92p
2N1314 35p	2N3877A 40p	ACY41 25p	BF167 18p	D16P2 37p	NKT80214 92p
2N1322 80p	2N3900 37p	ACY44 40p	BF173 15p	D16P3 37p	NKT80214 92p
2N1333 25p	2N3900A 30p	AD107 30p	BF177 30p	D16P4 30p	NKT80214 92p
2N1439 27p	2N3901 87p	AD149 87p	BF178 30p	GET102 30p	NKT80214 92p
2N1471B 1.00	2N3903 35p	AD150 62p	BF179 30p	GET113 20p	OC20 75p
2N1711 25p	2N3904 35p	AD161 37p	BF180 30p	GET114 20p	OC22 50p
2N1889 82p	2N3905 37p	AD182 37p	BF181 32p	GET118 20p	OC23 60p
2N1893 87p	2N3906 37p	AF106 42p	BF184 25p	GET119 20p	OC24 60p
2N1927 87p	2N4056 37p	AF110 42p	BF185 25p	GET120 50p	OC25 60p
2N1944 87p	2N4059 17p	AF115 25p	BF194 17p	GET875 12p	OC26 27p
2N2160 87p	2N4060 12p	AF116 25p	BF195 15p	GET880 30p	OC28 62p
2N2193 40p	2N4061 12p	AF117 25p	BF196 42p	GET887 20p	OC29 62p
2N2193A 62p	2N4062 12p	AF118 62p	BF197 42p	GET889 22p	OC35 50p
2N2194A 30p	2N4244 47p	AF119 30p	BF198 42p	GET890 22p	OC36 62p
2N2217 27p	2N4285 17p	AF124 22p	BF200 52p	GET896 22p	OC41 22p
2N2218 25p	2N4286 17p	AF125 20p	BF224 14p	GET897 22p	OC42 25p
2N2219 25p	2N4287 17p	AF126 20p	BF225 10p	GET898 22p	OC44 20p
2N2220 25p	2N4288 17p	AF127 17p	BF237 23p	MJ400 1.07	OC45 12p
2N2221 25p	2N4289 17p	AF129 37p	BF238 23p	MJ420 1.12	OC46 15p
2N2222 30p	2N4290 17p	AF178 42p	BF244 23p	MJ421 1.12	OC70 15p
2N2270 47p	2N4291 17p	AF179 72p	BFW61 47p	MJ430 1.02	OC71 12p
2N2287 80p	2N4292 12p	AF181 42p	BFX12 52p	MJ442 1.24	OC72 12p
2N2388 17p	2N4303 47p	AF181 42p	BFX13 22p	MJ480 87p	OC74 32p
2N2369 17p	2N6027 62p	AF239 42p	BFX29 30p	MJ481 1.25	OC75 32p
2N2369A 17p	2N6028 57p	AF278 47p	BFX30 30p	MJ490 1.00	OC78 22p
2N2410 42p	2N6029 47p	AF280 62p	BFX42 37p	MJ491 1.37	OC77 30p
2N2438 27p	2N6030 42p	AF271 32p	BFX44 37p	MJ1800 12.17	OC81 20p
2N2474 32p	2N6031 42p	AF276 25p	BFX45 27p	MJ1801 12.17	OC82 20p
2N2489 22p	2N6174 52p	AS72 37p	BFX84 25p	MJ520 60p	OC83 25p
2N2540 22p	2N6175 52p	AS72X 27p	BFX85 32p	MJ521 73p	OC84 25p
2N2513 35p	2N6176 45p	AS79 27p	BFX86 25p	MJF102 42p	OC139 32p
2N2514 30p	2N6232A 30p	AS79 38p	BFX87 27p	MJF103 37p	OC140 32p
2N2546 62p	2N6245 45p	AS79 25p	BFX88 25p	MJF104 37p	OC170 30p
2N2596 82p	2N6246 45p	AS79 32p	BFX89 62p	MJF105 37p	OC171 30p
2N2711 25p	2N6249 87p	AS79 54p	BFX98A 70p	MJF8633 32p	OC200 40p
2N2712 25p	2N6285 23.25	AS79 86 32p	BFY10 30p	MKT0013 47p	OC201 60p
2N2713 27p	2N6286 22.75	AU103 1.25	BFY11 42p	NKT124 42p	OC202 75p
2N2714 30p	2N6297 22.62	AS221 42p	BFY17 22p	NKT126 27p	OC203 42p
2N2805 62p	2N6300 47p	BF127 47p	BFY28 32p	NKT128 27p	OC204 42p
2N2904 30p	2N5306 40p	BC108 10p	BFY19 32p	NKT128 27p	OC205 90p
2N2904A 32p	2N5307 37p	BC109 10p	BFY20 30p	NKT135 27p	OC207 75p
2N2905 87p	2N5308 37p	BC113 15p	BFY21 42p	NKT137 32p	OCPT1 42p
2N2905A 40p	2N5309 62p	BC115 15p	BFY24 45p	NKT210 30p	ORP12 50p
2N2906 25p	2N5310 49p	BC116A 15p	BFY25 25p	NKT211 30p	ORP61 50p
2N2906A 27p	2N5312 47p	BC118 10p	BFY26 20p	NKT212 30p	PA6A 22p
2N2907 30p	2N5355 27p	BC121 20p	BFY29 50p	NKT213 30p	TI834 62p
2N2923 15p	2N5356 32p	BC122 20p	BFY30 50p	NKT214 22p	TI843 27p
2N2924 15p	2N5395 87p	BC125 20p	BFY41 50p	NKT215 22p	TI844 10p
2N2925 15p	2N5396 32p	BC126 20p	BFY43 62p	NKT216 37p	TI845 10p
2N2926 25p	2N5397 87p	BC140 37p	BFY90 23p	NKT217 42p	TI846 11p
Green 14p	2N5467 37p	BC147 10p	BFY51 20p	NKT219 30p	TI847 11p
Yellow 12p	2N6005 27p	BC149 10p	BFY52 10p	NKT222 27p	TI848 12p
Orange 12p	2N6020 22.00	BC149 10p	BFY53 17p	NKT224 25p	TI849 12p
2N3011 30p	2N6102 50p	BC152 17p	BFY56A 57p	NKT225 22p	TI850 12p
2N3014 32p	2N6103 25p	BC157 20p	BFY75 30p	NKT229 30p	TI851 12p
2N3035 18p	2N6104 25p	BC158 11p	BFY76 42p	NKT237 35p	TI852 12p
2N3064 40p	2N6105 32p	BC159 12p	BFY77 57p	NKT238 25p	TI853 22p
2N3065 62p	2N6106 35p	BC160 18p	BFY90 62p	NKT240 27p	TI860 22p
2N3133 30p	2N6503 27p	BC167 11p	BFW68 27p	NKT241 27p	TI861 25p
2N3134 30p	3N83 40p	BC168B 10p	BFW69 25p	NKT242 20p	TI862 27p
2N3135 25p	3N128 70p	BC168C 11p	BFW60 25p	NKT243 62p	TIP29A 60p
2N3136 25p	3N140 77p	BC169B 11p	BPX25 1.85	NKT244 17p	TIP30A 50p
2N3390 20p	3N141 78p	BC169C 12p	BPX29 1.40	NKT246 20p	TIP31A 62p
2N3391 20p	3N142 55p	BC170 12p	BPY10 1.45	NKT261 20p	TIP32A 62p
2N3391A 30p	3N143 67p	BC171 15p	BRV39 47p	NKT262 30p	TIP33A 75p
2N3392 17p	3N152 87p	BC172 15p	BSX19 17p	NKT264 20p	— 1.02p
2N3393 15p	R.C.A. 52p	BC175 22p	BSX20 17p	NKT271 20p	TIP34A 22.05
2N3394 15p	40650 55p	BC182 10p	BSX21 37p	NKT272 20p	TIP35A 22.90
2N3402 22p	40251 32p	BC183 09p	B8X26 45p	NKT274 20p	TIP36A 23.68
2N3403 22p	40309 32p	BC184 11p	B8X27 47p	NKT275 20p	—

**TTL. LOGIC I.C. NEW PRICES**

1-11 12-24	1-11 12-24	1-11 12-24
SN7400 0.20 0.18	SN7433 0.80 0.75	SN7479 0.32 0.30
SN7401 0.20 0.18	SN7437 0.84 0.78	SN7473 0.43 0.41
SN7402 0.20 0.18	SN7438 0.84 0.60	SN7474 0.43 0.41
SN7403 0.20 0.18	SN7440 0.83 0.21	SN7475 0.46 0.44
SN7405 0.20 0.18	SN7441AN 0.87 0.83	SN7476 0.45 0.44
SN7406 0.80 0.75	SN7442 0.85 0.81	SN7480 0.70 0.65
SN7407 0.80 0.76	SN7443 2.88 2.70	SN7481 1.40 1.38
SN7408 0.20 0.18	SN7444 2.88 2.70	SN7482 0.87 0.84
SN7409 0.20 0.18	SN7445 2.50 2.40	SN7483 0.87 0.82
SN7410 0.20 0.18	SN7446 1.00 0.95	SN7484 2.00 1.85
SN7411 0.23 0.21	SN7447 1.00 0.95	SN7485 3.82 3.40
SN7412 0.48 0.46	SN7448 1.00 0.95	SN7486 0.33 0.30
SN7413 0.40 0.38	SN7449 1.00 0.95	SN7490 0.87 0.84
SN7420 0.20 0.18	SN7450 0.20 0.18	SN7491AN 1.87 1.80
SN7423 0.51 0.47	SN7451 0.20 0.18	SN7492 0.87 0.84
SN7427 0.48 0.45	SN7453 0.20 0.18	SN7493 0.21 0.14
SN7428 0.80 0.75	SN7454 0.20 0.18	SN7494 0.87 0.84
SN7430 0.23 0.15	SN7460 0.20 0.18	SN7495 0.87 0.84
SN7432 0.48 0.42	SN7470 0.40 0.38	SN7496 0.87 0.84

**MULLARD SUB-MIN ELECTROLYTIC**

C425 range axial lead  
Values: (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 8/40; 8/40; 10/16; 10/16; 12.5/25; 16/40; 20/16; 20/64; 25/64; 25/64; 32/10; 32/10; 32/40; 32/40; 50/40; 50/40; 64/10; 64/10; 80/16; 80/16; 100/64; 125/10; 125/16; 200/64; 200/10;

# YOURS FREE FOR 7 DAYS



## The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

**TO TRY IT, IS TO PROVE IT**

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

### WHAT READERS SAY

#### "T.V. ENGINEER"

"So in two years I have come from a labourer on a building site to a T.V. Engineer, with the help of your books."  
*C.G., Sheppey.*

#### "OUT OF DATE"

"These books make all other publications out of date with their simplicity and interest."  
*J.W.R. Newbury.*

#### "ADD MY BLESSINGS"

"You can add my blessings to your already long list of praises about your Basic publications."  
*P.J.J. Rustington.*

**POST NOW FOR THIS OFFER!!**

A TECH-PRESS PUBLICATION

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY** £4.50 Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. **BASIC ELECTRONICS** £5.40 Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

**BASIC ELECTRICITY**  **BASIC ELECTRONICS**   
Prices include Postage and Packing.

Signature \_\_\_\_\_  
(If under 21 signature required of parent or guardian)

NAME \_\_\_\_\_  
BLOCK LETTERS

FULL POSTAL ADDRESS \_\_\_\_\_

## NOW BUILD ON! — WITH LST

FEATURING SOME OF THE MANY COMPONENTS FROM THE FREE LST CAT. HAVE YOU SENT FOR YOURS YET???

### TRANSISTORS

We stock all popular types but how about our **INTRODUCTION KIT £1**—consisting of: OC71, OC44, OC45, AC128, BC107, 2N2926, OC72 incl. data and connection chart.  
ORDER AS PACK NO: EE1

### DIODES INTRODUCTION KIT 50p

2 x OA81, 2 x OA200 4 x 1N4001 (All recently used in EE projects)  
ORDER AS PACK NO: EE2

### VEROBOARD

36 square inches total area (approx) consisting of .1 and .15 matrix  
ORDER AS PACK V10:

### ZENER DIODES

Consisting of a 1 Watt and a 400 milliwatt Zener (or regulator) diode plus FREE 24 page circuit book.  
ORDER AS PACK EE3

### CAPACITOR PACK

10 popular values of capacitor including polyester and electrolytic good starting stock! Normal Cat. price over 65p  
ORDER AS PACK EE4

### PHOTORESISTOR ORP12

Price includes data sheet. (German LDR03 type)  
ORDER AS PART NO: LDR03

### NEON PACK

Consisting of 10 miniature neon indicator bulbs 65Vac 90 Vdc. Use 270k resistor for mains use.  
ORDER AS PACK: EE5

### BOOKS ETC:

Designers Guide to British Transistors: Data on 1000's of common types £1.40  
110 Semiconductor Projects.  
Marvellous book for the enthusiast: £1.35

### HOW TO ORDER:

Cut out whole advert.  
Tick boxes for packs required.  
Fill out name and address enclose payment.  
ALL ITEMS THIS AD. POST FREE.

PLEASE NOTE: Our "Experimenters Bargain Pack £2."—(Last months ad.) now withdrawn. All orders despatched day of receipt. Spares for all packs in our FREE catalogue.

**LST ELECTRONIC COMPONENTS LTD.,**  
DEPT. E.E.,  
7 COPTFOLD ROAD,  
BRENTWOOD,  
ESSEX.

STOCKISTS-DISTRIBUTORS OF: IR, WELLP, MULLARD, NEWMARKET, SIEMENS, RCA, ISKRA VEROBOARD, S-DECS, TEXAS, G.E.

FROM:—

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

ENCLOSED/CASH/CHEQUE/PO. £ : p

PLEASE PRINT CLEARLY TICK BOX → FOR CAT. ONLY



# everyday electronics

PROJECTS.  
THEORY....

## THEORY AND PRACTICE

Many an enthusiastic and impatient beginner has no doubt pondered about the importance of theoretical knowledge to the would-be constructor: just how deeply need one go into the seemingly abstruse subject of circuit theory before starting to build electronic projects?

Well, the honest answer is that if one confines oneself to building simple designs, such as described in this magazine, then there is no reason at all why one should not do just this, straight away. The detailed diagrams we provide certainly leave little if anything to doubt; the position of every component is indicated and all wiring connections are clearly shown. The accompanying components list gives in each case all the information necessary when asking for or writing for these items. Yes, it should be possible for most beginners to tackle our projects without delay, even though the technical explanations of the circuit operation may not be comprehensible at this stage.

Provided that proper components have been used and wiring connections made exactly as depicted in the diagrams, correct results should be obtained first time. (The value of checking and rechecking the wiring before connecting the power supply cannot be over emphasised.)

## PRACTICAL VALUE


All the above is quite true, yet it must not be interpreted as encouragement to turn a blind eye to theory, to ignore fundamental principles entirely.

There is a perfectly sound and strictly practical reason for acquiring a knowledge of at least the basic principles of electronics as soon as possible. If something does go awry with a project due to a faulty component, even an elementary knowledge of the circuit operation will assist in tracking down the defective part. The remedy, likely as not, will then be simple to effect. But without that certain amount of basic knowledge one is of course confronted with an enigma that defies solution.
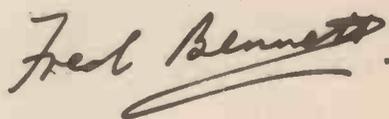
## A BIGGER VIEW

Apart from facilitating fault-finding, an appreciation of the manner in which the circuit operates adds greatly to the general enjoyment one can derive from this hobby. The more advanced one's knowledge, the more attractive electronics becomes. An ever extending vista of interesting and tempting applications is seen as understanding of electronic fundamentals grows.

So, beginners, by all means have a go with the project of your choice. But do also take advantage of our tutorial series *Teach-In*. Then in a short while those circuit descriptions will become less mysterious and each circuit diagram will have its own interesting story to tell.



Our March Issue will be published on Friday, February 18

EDITOR F. E. BENNETT ● M. KENWARD ● B. W. TERRELL B.Sc.  
ART EDITOR J. D. POUNTNEY ● P. A. LOATES ● S. W. R. LLOYD  
ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Subscription Rates including postage for one year, to any part of the world, £2.35.

Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



# ..EASY TO CONSTRUCT ..SIMPLY EXPLAINED

VOL. 1 NO. 4


FEBRUARY 1972

## CONSTRUCTIONAL PROJECTS

<b>AUTO ALERT</b> <i>The motorist's "dead man's handle"</i> by David C. Dick	190
<b>RADIO CONTROL MONITOR</b> <i>For testing transmitter function</i> by F. G. Rayer	195
<b>RAIN WARNING ALARM</b> <i>Protect the washing</i> by Frank Brown	208
<b>WAA-WAA PEDAL</b> <i>Musical effect for guitars and organs</i> by P. J. Tyrrell	214

## GENERAL FEATURES

<b>EDITORIAL</b>	188
<b>RUMINATIONS</b> by Sensor	194
<b>DIGITAL COMPUTERS</b> by C. N. Seal and A. Smith	198
<b>TEACH-IN</b> Part 4: Power by Mike Hughes	203
<b>USING STICK DOWN WIRING</b>	212
<b>ACTION!</b> <i>An evening class visited</i>	218
<b>MEMORY STORE</b> <i>Retrieval</i> by Dick Railton	221
<b>ABBREVIATIONS</b>	221
<b>SHOP TALK</b> <i>Component buying</i> by Mike Kenward	222
<b>READERS' LETTERS</b>	225

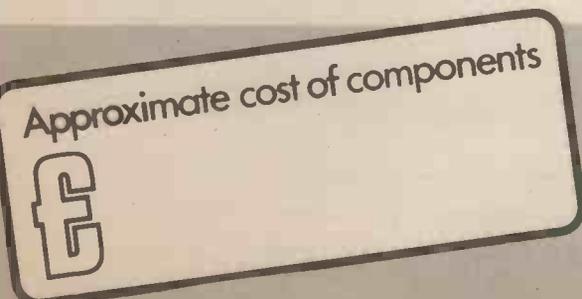

The approximate cost of components given, for constructional articles, in the box shown opposite is an estimated cost compiled from suppliers current catalogue and advertised prices. Parts for some projects may work out more expensive while others may be cheaper than our quoted price, depending on where the components are purchased.

We would like to point out that we, as publishers, cannot supply kits of parts or individual items for any of the published designs.

# AUTO ALERT

FOR MOTORWAY  
DRIVING

By David C. Dick

Approximate cost of components



2.50 inclusive

**Keep a check on your awareness. The Auto Alert provides added safety for all long distance drivers.**

**W**ITH the ever-increasing growth of new dual carriageway roads and motorways, the average car driver is tempted to travel longer distances than he would previously have tackled.

The urge to "do the whole journey in one go" or to "cover the distance at night while the roads are quiet" has involved many a motorist in a nasty and often lethal accident. The tedium of a long unbroken motorway journey, the monotony of night driving, the hypnotic swishing of windscreen wipers and the blow of warm air from the heater are all possible causes of that lack of concentration (or even nodding off!) which at motorway speeds can be the cause of an extremely dangerous situation.

## **"DEAD MANS HANDLE"**

The "dead man's handle" is the name given to a particular kind of footswitch which is fitted in the driver's cab of modern locomotives. The switch has a middle off position and the driver has to keep it in the middle position in normal driving. If the driver should faint or take ill his foot will either press the pedal fully down or his foot will lift off the pedal. Either way a contact is made and a warning klaxon sounds in the driver's cab. After a certain delay, if the pedal is not reset, the train's braking system will come on automatically.

A footswitch of this kind cannot be fitted in a car as the driver's left foot will be needed from time to time to press the clutch for gear changes and to operate the headlamp dip switch. However, the principle of the switch is a good one and can be adapted for use in a car.

## **CAR SYSTEM**

The Auto Alert consists of a timing unit and two relays that are used to turn on a warning light and to sound the car horn. The Alert is turned on and a push-button or footswitch (whichever is preferred) is depressed to set the circuit. After a predetermined time interval the

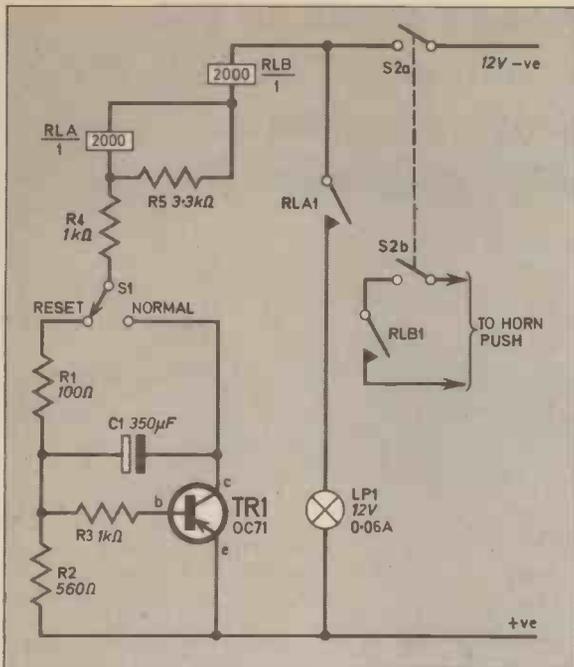


Fig. 1. Complete circuit diagram of the Auto Alert. S1 is the push button or footswitch that resets the unit.

## Components....

### Resistors

- R1 100Ω
  - R2 560Ω
  - R3 1kΩ
  - R4 1kΩ
  - R5 3.3kΩ
- All ½ Watt ±10% carbon

### Capacitor

- C1 350 μF elect, 15V

### Transistor

- OC71 Germanium pnp

### Switches

- S1 Single pole double throw micro-switch or push button (see text)
- S2 Double pole single throw car type toggle

### Relays

- RLA G.P.O. 3000 type, 2,000 ohm coil with single pole normally closed contacts
- RLB G.P.O. 3000 type, 2,000 ohm coil with heavy duty single pole normally closed contacts

### Miscellaneous

- LP1 12V bulb and holder
- Car switch panel—two hole type (see text)
- Metal brackets (2 off see text)
- 10 way connecting strip, hardboard, connecting wire and 4BA fixings
- Materials for foot switch if used (see text and Fig. 5)

Shop Talk Refers

light on the Alert will come on and the driver should press the switch to reset the Alert. If, due to lack of concentration, the driver fails to notice the light and does not press the switch then, after a further short interval, the car horn will sound to warn the driver.

Thus a regular check is kept on the concentration of the driver and any tendency to lose concentration will be noticed before it gets to the eyelid drooping or daydream driving stage.

It is important that the unit is not regarded as an automatic "waker-upper". The first time that the horn operates the driver must take the warning, pull off the road and not drive again until he is sure that he is sufficiently alert.

## CIRCUIT OPERATION

Assume the circuit (Fig. 1) to be in the "normal" condition with C1 fully discharged. When voltage is applied TR1 will be passing current due to the voltage at its base being the same as at the collector. As C1 gradually charges up TR1 will slowly turn off and the current passing through the relays will diminish. As resistor R5 is fitted across the coil of RLA the current flowing through RLA at any time will be less than that flowing through RLB; thus RLA will drop out before RLB.


When RLA contacts close lamp LP1 will light and, unless this is noticed within approximately 20 seconds, RLB contacts will also close and sound the car horn. If, however, the light is noticed and the reset button pressed, the circuit will return to the "normal" position (C1 fully discharged) by the following method.

With S1 in the reset position C1, which is now charged up, provides the collector voltage. To discharge C1, TR1 must conduct and it does so because R1 and R2 form a potential divider across the supply so that a negative voltage is applied to the base. Capacitor C1 then discharges through TR1 and R2. During the "reset" time current passing through R1 and R2 will keep both relays energised, so preventing the horn from sounding and extinguishing the warning lamp LP1.

Variation of the value of C1 will alter the time interval—increase C1 to increase the time and decrease C1 to decrease the time.
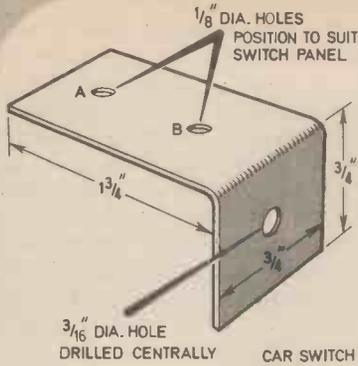
## CONSTRUCTION

The design of the unit was drawn up to enable it to be constructed with only a minimum of skills. First, take a two-hole car switch panel; this is available from any car accessories shop and already has two holes drilled in the outer face with two smaller holes drilled in the top lip. The two larger holes in the face will be used for mounting the switch S2 (see Fig. 3) and the lampholder for lamp LP1. The next components to be fitted are the two metal brackets. The brackets used in the prototype were bought



# AUTO ALERT

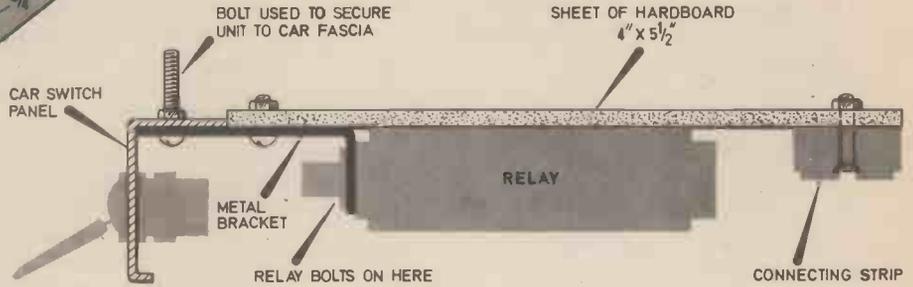


Fig. 2. (top left) Mounting bracket for relays RLA and RLB.

Fig. 3. (above) Showing how the mechanical parts fit together.



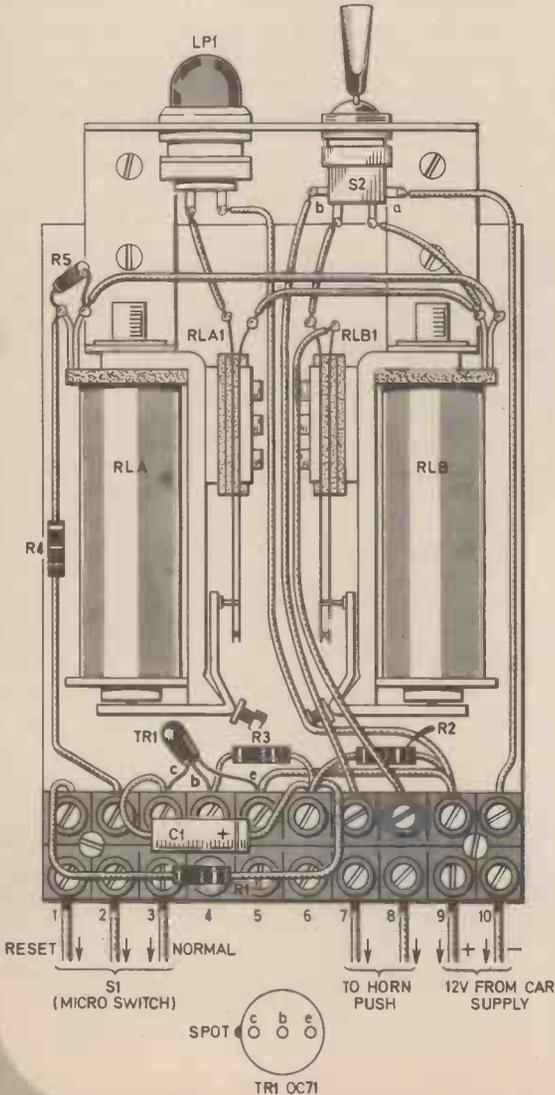


Fig. 4. (left) Layout and wiring of all components except SI. The wire from position 2 on the connecting strip goes to the centre contact of SI.

Fig. 5. (below) Construction of the foot switch.

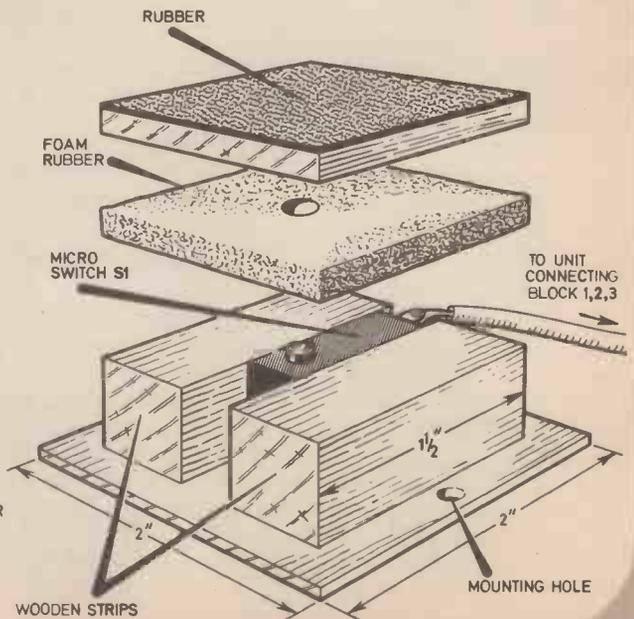

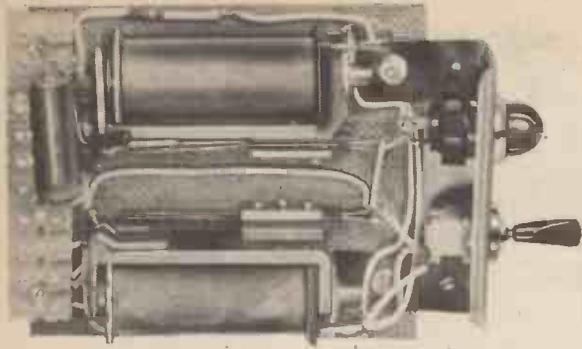

**Prototype Auto Alert. Switch S1 and some of the wiring has been slightly modified.**

ready drilled from Woolworths for a few pence each. If these are not available they can be made from the measurements given in Fig. 2.

Using two 1 inch long bolts, bolt together the switch panel and the two brackets. The longest legs of the brackets are placed under the top lip of the switch panel (see Fig. 3) and the bolts are placed up through holes "a" in the brackets. The excess length of these bolts will be used later to secure the entire completed unit to the underside of the car dashboard.

A sheet of hardboard measuring 4 inches by 5½ inches is next bolted to the brackets using the remaining small holes "b" in the brackets (see Fig. 3). The hardboard will act as a baseboard for the circuitry and as a dust cover for the relay contacts and other components. A ten-way screw connecting strip is bolted across the bottom of the baseboard as in Fig. 4. This connecting strip is used to mount the components in preference to a conventional tag strip as this makes for easier fitting of the complete unit into the car. If constructors have facilities for soldering in the car (a 12 volt soldering iron or an extension mains lead, for example) then they may prefer to use a normal tag strip and solder all the connections.

We are now ready to mount the components. The lampholder and switch S2 should be mounted on the switch panel, and the two relays are fixed to the brackets.

## RELAYS

At the end of the relay next to the coils and spring set tags, there is a square of paxolin with three holes drilled in it. Through the two outer holes are screws which are normally used for the mounting of the relay. These two screws and the paxolin square can be removed as they will not be used. This leaves a circular nut which is used to hold the coil core to the relay frame. This nut should be undone and the bolt from the relay coil passed through the remaining hole in the bracket. The nut should then be screwed back on using a washer. Both relays are thus held

securely to the unit. See Figs. 3 and 4.

The relays purchased for the prototype were fitted with further contacts; in this case the unwanted layers of spring contacts should be removed otherwise the relay will not operate at the low current necessary. Relay RLB is used to switch the horn and as the horn takes a substantial current it is considered necessary to fit heavy-duty relay contacts to handle the current. It should be remembered, however, that the relay should hardly ever be used to switch on the horn and therefore heavy-duty contacts are not essential.


## WIRING

The wiring should be carried out as in Fig. 4. Where more than one wire goes into one hole of the connecting strip it is a good idea to solder the wires together before screwing down. This will improve future fault liability.

Remember to connect the electrolytic capacitor in the correct polarity. Also it is important to connect the transistor in the manner given in the diagram. The red spot of the transistor body is at the side next to the collector lead and the base connection is the middle lead. If the leads are reversed the unit will not work and it is probable that the transistor will be destroyed. If you construct the unit using a tag strip or solder the connections affix the transistor after completing the wiring and hold each lead in a small pair of pliers while soldering to prevent overheating and thus damaging the transistor.
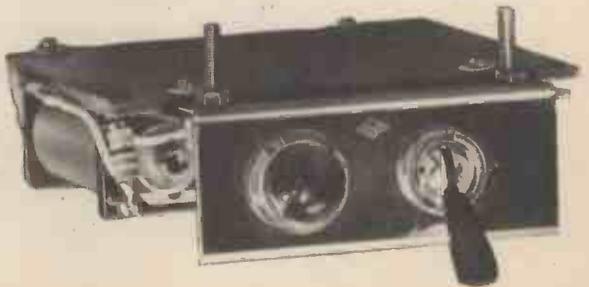
## RESET SWITCH

Either a footswitch or a dashswitch can be used for S1. The cover illustration depicts a dash-mounted push-button and lamp. If such an arrangement is required the on/off switch and the unit can be placed in the car dash panel and the lamp and push-button can be mounted remotely in a convenient position or with the on/off switch in the panel. A micro-switch is probably best used with the footswitch design given and a normal change-over push-button (momentary contact type) used for a dash-mounted button.



## THE FOOTSWITCH

The construction of the footswitch is shown in Fig. 5. The micro-switch is held between two strips of wood, each strip being approximately 1½ inches long and of the same height as the micro-switch body. This means that the operating plunger of the micro-switch will protrude above the level of the wood strips. It was found sufficient to glue the pieces together with Evo-Stik, and this gave a permanent joint. The completed piece can then be glued to the base section. The base section is 2 inches square and can be constructed from any kind of material; in the prototype a piece of hardboard was used. The base should have two holes drilled in it as in Fig. 5, these holes will be used later for fixing the switch to the car floor.

Next, a piece of foam rubber, ½ inch thick and 1½ inches square, should be glued across the wood strips, a hole being cut in the foam around the micro-switch plunger. On top of the foam rubber another piece of hardboard 1½ inches square is glued, this piece of hardboard is covered with rubber to prevent slipping. The footswitch is now complete and can be screwed to the car floor with self-tapping screws.

## FITTING

Before fitting carefully check the wiring for any mistakes. Two holes should be drilled in the underside of the car dashboard and the two bolts from the unit pushed through the holes and secured with nuts, preferably using spring or serrated washers. The wiring from the footswitch should now be brought up to the unit and screwed into the connecting strip at the appropriate points. To make the wiring inconspicuous, it can be taken up under carpets, where this is convenient. Wires can now be taken from the unit to the horn wiring and to the supply.

The two leads from the unit to the horn push are connected across the push, the polarity does not matter (one side of the push may be connected to earth). Supply wiring will depend on the earth polarity of the car and this should be checked before connecting the unit. The live supply can be taken from the ignition switch.

Once the wiring to the car is complete the unit is ready for use, press the reset button and hold it pressed until the unit is turned on, then release and check the function of the unit. Remember do not keep your foot on the reset button all the time and do not use the Alert to keep you awake. □

## Ruminations By Sensor

### An Act of Charity

I thumped the television set on the top right hand corner. That was two months ago and since then it has behaved itself. There was a shift in the tuning position of the three programmes, but the set has remained stable. I did not strike it in anger, although in the circumstances one might have been forgiven for doing so, for it had developed an intermittent fault that caused it to go out of tune, losing sound and vision, usually during the news or when Bamber Gascoigne was giving the answer to one of the "University Challenge" questions. The trouble never occurred during the advertisements. Such behaviour could not be allowed to continue, I had to act.

The set is on rental. I ought to have sent for the service engineer, but I know from my own experience that intermittent

faults are the most time consuming and frustrating aspects of a serviceman's life, or indeed, of anyone concerned with the reliability and maintenance of electronic equipment. Such faults often fail to appear when the engineer is called but can be depended upon to show up when his van has turned the corner.

Even if the fault does appear in the presence of the serviceman the slight disturbance created by the action of removing the back of the set or of connecting a test meter will often cause it to disappear again. Many of these intermittent faults are caused by "dry" joints (badly soldered connections which develop into high resistance joints after a period of time) and although there are techniques that can aid the serviceman, the diagnostic procedure is largely a matter of poking, prodding, tapping and on occasion, "thumping" various parts of the set, coupled with a keen visual inspection of the soldered joints.

This last is far from easy when the set has been in use for some time and has accumulated a thick layer of grime over the component boards. The idea

behind the tapping and thumping business is to cause the fault to appear so that it can be diagnosed by conventional methods; this is why I thumped my television—to present the serviceman with an easier job! However, I achieved a temporary "cure" instead. How long it will last is anyone's guess.

### An Uplifting Experience

Low insulation resistance can cause strange and sometimes dangerous faults to develop. An acquaintance of mine who worked for the electricity board was sent to investigate a complaint made by the trustees of an old chapel. It was alleged that ladies using the chapel toilet had received electric shocks.

My acquaintance, rather daringly, poured a bucket of water down the toilet and was rewarded for his boldness by a mild but stimulating electric shock. It was discovered that the insulation of some nearby cable had deteriorated and an earth leak had developed via the concrete floor. Users of the toilet thus formed a parallel path for the leakage current, with disconcerting but fortunately not disastrous results.

# RADIO CONTROL MONITOR

Provides a quick check on radio control transmitter function. Pocket size and self powered for ease of operation "in the field."

By F. G. Rayer, A.I.E.R.E.

THE 27MHz radio frequency (r.f.) band used for the control of models by radio, extends from 26.96MHz to 27.28MHz; transmissions for this purpose may consist of an unmodulated carrier wave, or a carrier wave which is modulated by one or more audio frequency tones. Signals which are radiated by the transmitter can be checked with a monitor.

The simple monitor described here is self powered and of compact size, so it can readily be carried out of doors, with the transmitter, model and other equipment. It allows a quick check of normal carrier-wave power and frequency, and of any audio modulation tones which may be used.



## CIRCUIT

The complete circuit is shown in Fig. 1. A coil consisting of three windings, L1, L2 and L3 forms the basis of the circuit. L1 is the tuned winding, and the operating frequency is set to that of the transmitter by means of the trimmer C1. With the coil and trimmer described, the whole of the model control band is easily covered. When the transmitter and the tuned circuit (L1 and C1) are set to the same frequency, and the monitor is held in a position where it picks up sufficient r.f. (radio frequency) energy, L1 absorbs some of the power from the transmitter. The monitor has two indicating devices, operated by the power absorbed.

Winding L2 is inductively coupled to L1 and when L1 absorbs r.f. power this is induced in L2 and provides current for the small lamp LP1. Resonance between the transmitter and monitor frequencies is shown by maximum brightness of this lamp. The brightness of the lamp also shows that the transmitter is producing its normal r.f. power.

Winding L3, with the diode D1 and earpiece TL1, give audible monitoring of the tones produced by the transmitter. So the control and tone-producing circuits of the transmitter can be immediately checked, by listening with the earpiece. The diode acts as a detector to extract the audio signal from the amplitude modulated r.f. signal that the transmitter provides.

Some changes in components will not unduly affect the circuit. The earpiece TL1 can be between 35 and 250 ohms impedance, of the kind used with transistor radio receivers. It would also be quite possible to use a different wire gauge or tube size for the coil, although some experiment with the number of turns would then be necessary.

The lamp must be a low-consumption type; a 6 volt 0.04 amp bulb, as used for cycle dynamo rear lamps, is most suitable, but a 6V 0.06A could be used. Bulbs which take the smallest current will give the more sensitive indication.

## CONSTRUCTIONAL DETAILS

The monitor is constructed to the details shown in Fig. 2, then inserted in a 3½ inch long by 1¼ inch diameter paxolin tube.

A piece is 1/16 inch thick paxolin 3½ inches long is cut to such a width that it is a tight fit inside the 1¼ inch tube. For part of its length the paxolin is further reduced in width, so that it fits tightly inside a 1 inch diameter paxolin tube. The paxolin sheet is best cut slightly oversize, and then filed to fit.

The 1 inch diameter tube that is the coil former is 1 inch long. All windings are of 24 s.w.g. enamelled copper wire, wound side by side. Drill six 1/16 inch holes in the tube as shown in Fig. 2, thread the wire through hole A, smear part of the tube with Bostik 1, or similar adhesive or cement, and wind on nine turns to form L1,

# R.C. MONITOR



Approximate cost of components

£ 1.30 inclusive

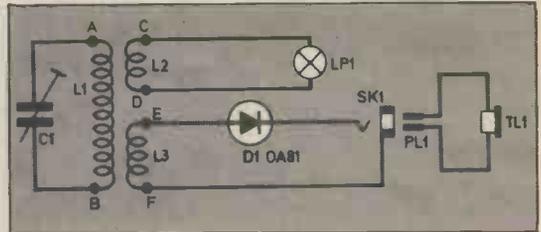


Fig. 1. Complete circuit diagram of the Radio Control Monitor.

## Components....

### Capacitor

C1 6—25pF ceramic trimmer

### Diode

D1 OA81 **Shop Talk refers**

### Lamp

LP1 6V 0.04A screw in bulb (see text)

### Earpiece

TL1 35Ω to 250Ω earpiece with miniature jack plug (PL1)

### Socket

SK1 Miniature jack socket to suit earpiece plug

### Miscellaneous

24 s.w.g. enamelled copper wire  
P.V.C. covered connecting wire  
 $\frac{1}{16}$  inch s.r.b.p. or paxolin board  $3\frac{1}{2}$  in. x  $1\frac{1}{2}$  in.

Thin paxolin  $1\frac{1}{4}$  in. square for end pieces (2 off)

Paxolin tube 1 in. x 1 in. diameter and  $3\frac{1}{2}$  in. x  $1\frac{1}{4}$  in. diameter

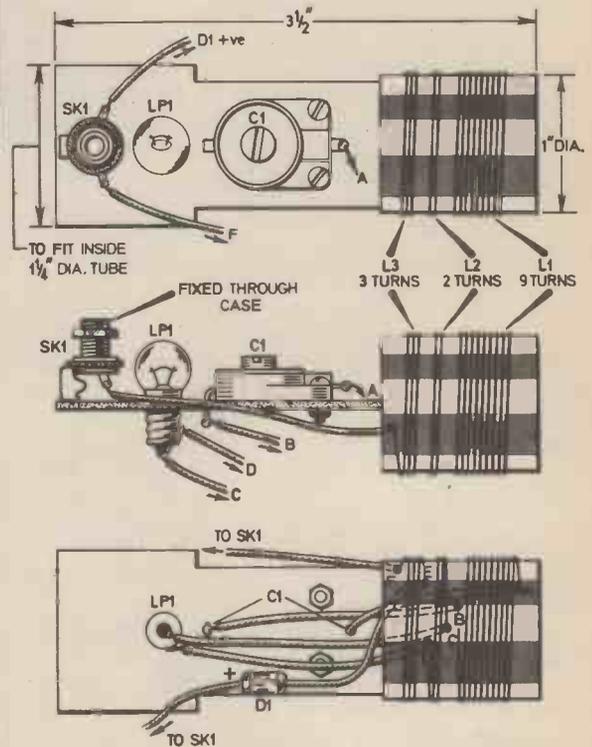


Fig. 2. Constructional details showing the complete unit without the case. The three views show the top, side and underside of the unit. SK1 is mounted through the outer case.

finishing by pulling the end through hole B. Make L2 (two turns) and L3 (three turns) the same way.

The tube is then cemented in place on the panel, with the wire ends running back (as shown in Fig. 2) identified with coloured 1mm p.v.c. sleeving. The lamp LP1, is a screw fit in a hole drilled through the panel. Leads C and D are soldered to its side and end pip. Since, with careful use, the bulb should never need replacing, this method of fixing is suitable. Two 8BA bolts hold the trimmer, and the miniature jack socket is fitted through a hole in the outer tube.

### TESTING

To test the monitor, set the trimmer about half open, using a non-inductive trimming tool, and bring the monitor coil into the field of the transmitter aerial (tank) coil. Rotate the trimmer with the trimming tool to tune L1 to resonance with the transmitter; this is shown by maximum brilliance of the lamp. At the same time move the monitor away from the transmitter coil, as required, so that the bulb only glows dimly.

If the transmitter is of a type producing audio tones, plug in the earpiece, operate the transmitter, and listen for the audio signals.

Slight re-adjustment of the trimmer is necessary after the monitor has been fitted in its protective case. The tubular case has a  $\frac{1}{4}$  inch hole for the jack socket, a similar hole through which to see the lamp filament, and a third smaller hole allowing the trimmer to be adjusted with a trimming tool. Both ends of the tube are closed with paxolin discs cemented on. The tubular case must not be made of metal of any type.


### METHOD OF USE

The monitor is held by the jack end, and its coil brought near the power amplifier or tank coil of the model control transmitter. The trimmer is adjusted with a non-inductive trimming tool, and tuning should be quite sharp. Move the monitor slightly away from the transmitter, so that LP1 filament only just glows at the correct tuning point. This gives the sharpest resonance indication, and avoids blowing the filament.

If the transmitter is totally enclosed in such a way that the tank coil cannot be approached, a loop consisting of one or two turns of insulated wire can be placed in the aerial connection, and the monitor approached to this.

If the transmitter has variable frequency tuning, as with self-energised oscillators, a check on transmitter frequency can be made by noting that its tuning agrees with maximum brilliance of the lamp, keeping coupling loose.

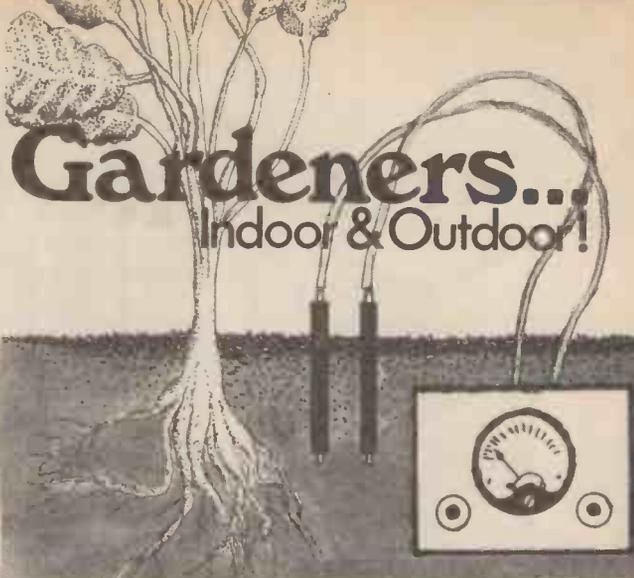Where the transmitter has tuning adjustments which govern the output power, note that these are set so that the lamp lights with its usual brightness. For tone transmitters, plug in the earpiece and listen in turn for each normal tone. Lack of any indication at all will show that the transmitter has failed. □



## Soil Moisture Meter

Don't kill your plants by over-watering—plants of different species have their own requirements. This meter measures soil moisture at root depth.

## Darkroom Timer

Do your own printing? Then this timer is for you; it has switched positions to cover the range of times normally used for exposures in the darkroom.

## Signal Injector





For fault finding in radio's and amplifiers.

## ALL FEATURED IN THE March ISSUE OF

On sale

Friday February 18.

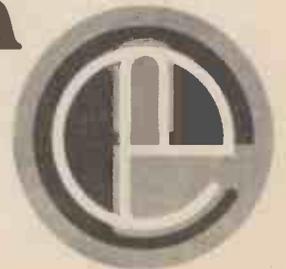

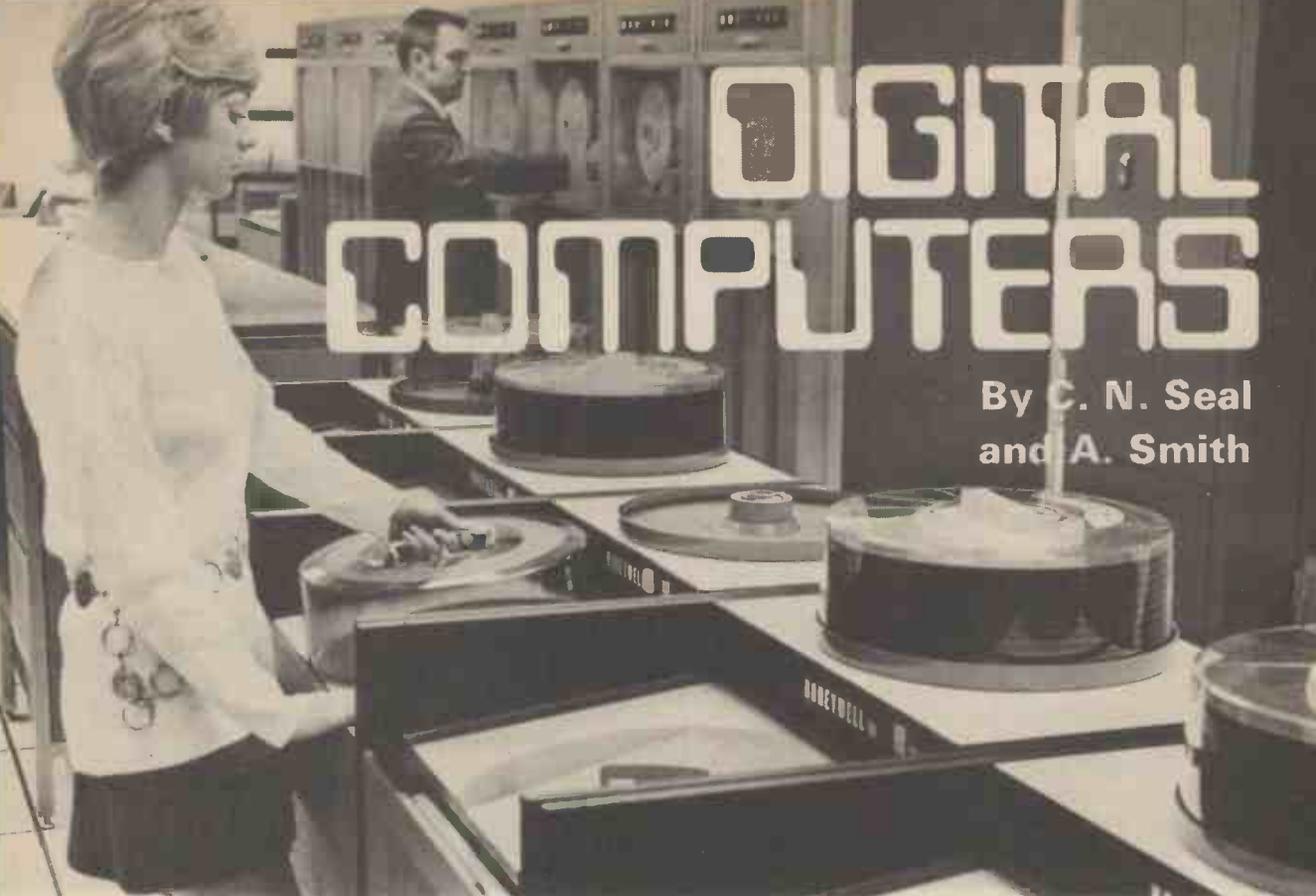

# DIGITAL COMPUTERS

By C. N. Seal  
and A. Smith

**M**ANY aspects of modern life use a computer; more and more of us find that computers have become part of our everyday lives. We feel their effect most in the management of our financial affairs. Our cheques are processed by computers which read magnetic ink patterns printed on the cheques; internal banking transactions, such as transfers from one account to another, are performed by computer. Our salaries, with bonus, overtime, and other remunerations, are calculated by computers which also deduct tax, National Insurance contributions, and so on. Details are then printed onto our payslips and salary cheques.

Invoices are processed and printed by computers which also calculate and subtract discounts, and prepare all necessary bills. Large scale industrial control can be performed continuously by computers in places such as oil refineries, steel mills, breweries, car manufacturing plants, and so on.

Any of you that have travelled by air would probably have had all details of your booking stored in a computer. At each booking point there would be a computer terminal—a link between the booking clerk and the computer—which indicates details of any flight, and in particular, whether there are any spare seats available.

Computer terminals are not confined to airline booking offices. Many small companies with a

need for computer aid, but without the necessary funds to own their own computer system, utilise a time-sharing process. These users each have a remote terminal linked to the central computer system via the Post Office telephone lines.

The computers used for these systems are capable of processing several different user's programmes, apparently simultaneously. This is called multiprogramming. The link between the terminal and the computer is made after the operator has dialled the correct number on a conventional telephone. The time taken for processing the customer's programme is recorded, and is consequently used to determine the cost.

## DEFINITION

A computer may be defined as a device capable of automatically accepting data, applying a sequence of processes to the data, and supplying the results of these processes to its user. There are basically two types of electronic computer; analogue and digital.

**Heading photograph.** Magnetic discs and tapes can store massive amounts of information. Each of the disc drives in the foreground can store 18.4 million characters of data, enough to store the entire contents of the Bible twice. The tape drives at the rear can store 14 million characters. (Honeywell Information Systems Ltd.)

An analogue computer is a machine in which the value of a signal is proportional to the value which it represents. Such a signal is continuously variable, and may take any one of a large number of possible values. For instance, a car engine tachometer reading reflects the changes in the engine rotational rate. The indication is analogous to engine speed.

In contrast to the analogue signal, the digital signal has a discrete numerical value. It either exists and has one value, or it does not exist and has another value. This gives us the two "states" we require for use in the digital computer. A positive signal can represent the figure one, and no signal can represent zero.

## DIGITAL COMPUTER


For the purposes of this article we shall only consider the digital computer. To understand digital computer functioning we must first appreciate the number system used for making the calculations.

The earliest system resulted from man's desire to know "how many." To answer this he used the tally system; for each item counted he made a mark, or tally. Whilst providing some means of measuring, this system proved very limited and unwieldy for even comparatively small numbers.

For convenience we now use the decimal system which runs through a cycle of ten symbols before any are repeated. It is said to have a base of ten. Any decimal number can be broken down into a number of tens, a number of tens of tens (hundreds), and so on.

Although the decimal system is logical and consistent, it requires the use of ten digits which makes it unsuitable for electronic representa-

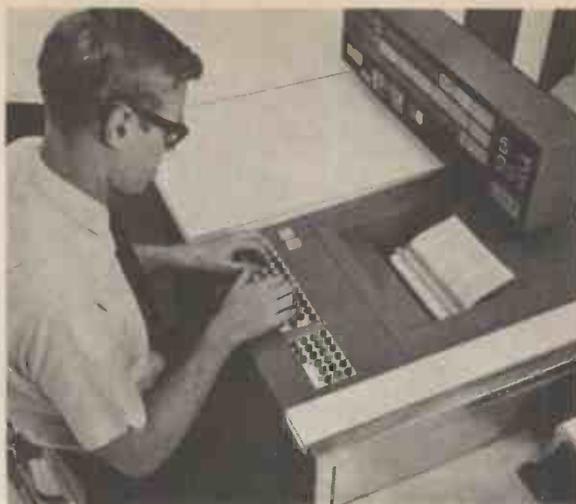**The cleanliness of the modern computer room can be seen here. The girl operator is using the keyboard to enter information into the computer memory. (International Computers Ltd.)**



**An operator uses a console to write instructions directly into the main or control memory areas of the computer. (Honeywell Information Systems Ltd.)**

tion. We must, therefore, study an alternative system which we call binary.

In the binary system the base number is two, and each binary digit, or bit, can only have one of two possible values, zero or one. The rules for the construction of this system are similar to those for decimal, as also are the rules for addition and subtraction; we just carry when the count becomes greater than one, or borrow two instead of ten.

As the numerical value increases, the number of bits required to represent it also increases. In the computer we must restrict the number of bits per character or per word to keep the calculations manageable. Usually computers confine the length of a character or a word to between six and forty bits.

## SOFTWARE

Software is a term describing the programme of instructions, usually supplied by the computer manufacturer, to enable communication with the computer and control of its operation. So great is the importance of software that investment in its production represents a high percentage of funds allocated for design, development, and marketing of computer systems. Indeed, computer sales can depend on the availability and versatility of the software, and not on the hardware—the mechanical and electronic parts of a computer.

Software includes all manner of operating procedures and programmes, such as assemblers or compilers—programmes which convert programmes written in symbolic languages such as FORTRAN and COBOL into the machine code required by the computer.

Other types of programmes include Executives—programmes which control the operation



A pair of visual display units are shown here against a background of magnetic tape drives. Information is shown on the face of a cathode ray tube, as in a television set. (Burroughs Machines Ltd.)

of other programmes; Subroutines—programmes designed to perform routine calculations; and Diagnostic Routines—programmes used by the service engineer to facilitate fault finding, and to indicate whether the system is functioning correctly.

Assemblers, Executives, and Subroutines form part of a processing package—a software package enabling the user to fulfil his data processing requirements. This package is normally called an Applications Package, and is software written especially to the users own requirements.

As previously mentioned, hardware comprises the physical units in a computer system—the mechanical and electronic assemblies.

## HARDWARE

Computer system hardware consists of two main areas. The first is the Central Processor, more commonly called the C.P. which performs all the major calculative and control functions. We shall consider C.P. operation later in this article. The second area embraces the peripherals commonly called input/output devices.

## PERIPHERALS

To place a programme and the associated data into the C.P., we must have some form of reading, or input device. The commonest input device is the operators keyboard, or console, which enables direct manual communication with the C.P. It is generally used to instruct the C.P. to read data from an input source, or to input parameters and additional data during programme runs.

The information typed into the keyboard, or console, may be printed on paper, or displayed on a television monitor type unit which presents

the information on the screen of a cathode ray tube.

There are basically four methods of supplying new data to the computer. The most common method is probably the punched card.

## PUNCHED CARD

This is a card containing rows and columns punched with holes in the required code. Punched card readers can have either optical or mechanical reading arrangements.

Optical readers contain lamps and photocells arranged so that the card passing between them causes a pulse of light for each hole detected.

In the mechanical systems, the card passes between a set of contacts and metal fingers which press lightly against the card. When a hole passes a contact the finger is allowed to press against the contact and complete the circuit.

Speeds of card readers vary between 400 and 1,000 cards per minute, with about 800 cards per minute being typical. The cards are relatively cheap, easy to sort, and in some cases the data contained on the card is printed along the top edge allowing the card to be read visually. However, they are bulky, making them difficult to store. They are affected by atmospheric conditions, particularly humidity, and are easily damaged.

## PUNCHED TAPE

Punched paper-tape is another common input medium. The tape is normally a one inch wide strip of paper-tape on a spool. The data is contained in rows, or frames, punched in a computer readable code. Tape is often produced by other devices, such as a typewriter or cash register. Tape readers are normally optical devices, operating similarly to the optical card reader.


Tape readers can operate at speeds of between 300 and 2,000 frames per second, with around 1,000 frames per second being typical. Paper tape is inexpensive, but because the data is punched serially it cannot easily be amended.

## MAGNETIC INK READERS

Magnetic ink character readers enable cheques and similar documents to be read. Each cheque contains a series of numbers printed in magnetic ink. The reader senses the shape of the magnetic field emitted by each character. Cheque readers can process up to 1,600 cheques per minute.
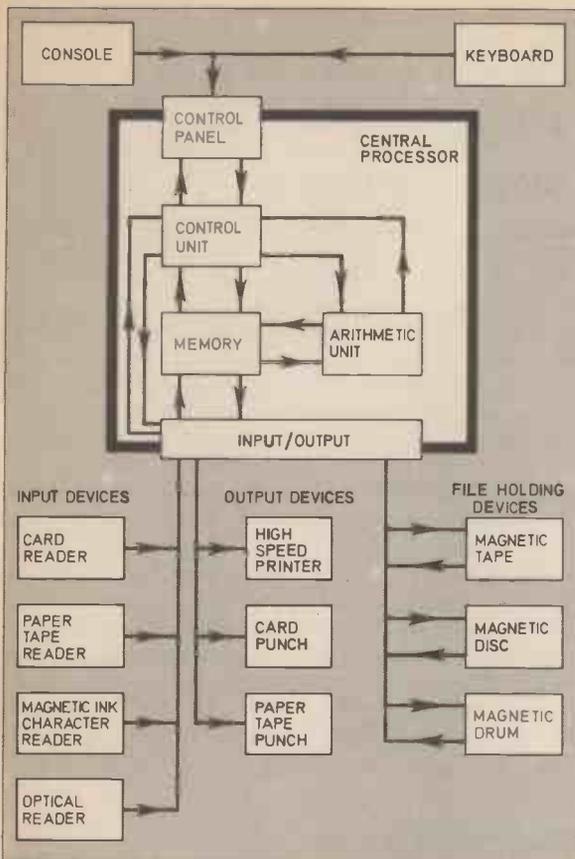
## OPTICAL READERS

Optical character readers have not yet been fully developed as a method of reading handwriting, such as signatures, but most in use are able to read standard shaped letters of the alphabet, using a photoelectric cell to scan characters



This illustrates the general organisation of a typical computer system. Major data and control paths are indicated. A system may use some, or all of the input and output devices, and in the case of the file holding devices, the system may utilise a number of each type.

printed in ordinary black ink.

The devices mentioned so far have been input devices, supplying data to the computer. Punched cards and paper tape can also be used to take data from the computer. Card and tape punches are, however, rather slower than the readers.

## OUTPUT

The commonest output device is the high speed line-printer. This is a machine which types the data onto paper in complete lines, instead of a character at a time. Speeds vary from 300 lines per minute to around 1,500 lines per minute, with 650 lines per minute being typical. A line can be up to 132 characters wide.

These high printing speeds are extremely useful where large quantities of information are required. A line-printer is considered essential for all commercial computer applications, for presentation of report and analysis details, and financial statements.



A finance company uses this large computer installation for the maintenance of the accounts for customers and dealers. The system uses a variety of peripheral devices, including a high speed printer, magnetic tape drives, magnetic disc drives and a paper tape reader. (*The National Cash Register Company Ltd.*)

## STORAGE

The third group of peripherals are known as storage, or file holding devices, and are input and output devices. These peripherals operate on similar principles to the domestic tape recorder, by placing a pattern of magnetic fields on a ferrous oxide surface.

Magnetic recording tape is similar to domestic recording tape, but has a finer grade of oxide coating enabling a higher density of data to be held. It is also wider than domestic tape,  $\frac{1}{2}$  inch being a standard.

The data is recorded in serial form, and consequently, if some data near the end of the tape is required, some time is taken to reach it—this is called the “data access” time. This is ideal for storing information used in a serial form, such as programmes.

Magnetic discs, another storage device and much faster access time than any other type, look similar to a stack of records on an auto-changer spindle. Both side of each disc are coated with oxide. Read/write heads project into the gaps between pairs of discs and can read from, or write to, both discs.

The magnetic discs revolve at a very high set speed, and by synchronising the head position, information can be read, or written. This type of device is called a direct access device because any item of data can be found easily and quickly.

Magnetic drums are cylinders coated with ferrous oxide on the outside. Read/write heads are spread along the length of the drum, and as the drum rotates at a set speed, data is transferred to, or from the required area of the drum.



An engineer uses a light pen to amend an engineering diagram. This system is used in the development of printed and integrated circuits. (Digital Equipment Company Ltd.)

## CENTRAL PROCESSOR

The central processor unit, or C.P. is the nerve centre of a computer operation. It is here that all calculative and control functions are performed. To do this the C.P. must contain four essential circuit areas. These are; memory, control, arithmetic, and input/output.

When we make any sort of calculation we must have some means of retaining the facts required to arrive at the solution. We use our brain when doing this manually, or perhaps a pencil and paper for the more complex operations. The combination of these could be called our memory unit. The computer memory performs this type of function. It is simply an area in which it can store the data, the programme to process the data, and the results obtained.

## MEMORY

The computer memory is like a large electronic filing system. It contains hundreds of "memory locations", each with an exclusive address, and each capable of containing one data statement, or a programme command.

Each location consists of a number of magnetic cores, which are minute ferrous oxide impregnated rings. Each binary bit is stored in one of these cores, and can be read in less than one microsecond.

The programmer arranges his programme so that the instructions occupy a sequential block of memory locations. When the programme is run the address of the first location is entered into a programme counter. As each instruction is executed the counter is incremented, and therefore contains the address of the next instruction. Consequently the machine can complete all the required calculations automatically.

An instruction to the computer does not contain the data that is to be processed, but the address of the location in the memory.

When executing the instruction, the computer

control takes the data from memory, and moves it to the arithmetic area for modification as prescribed by the instruction.

## ARITHMETIC UNIT

The arithmetic unit of the C.P. is the work-horse area in which all calculations are carried out. It consists basically of an accumulator, or a number of accumulators, and an adding network.

To add two numbers together the machine takes the first number from memory and places it in the accumulator. The second number is then removed from memory, added to the accumulator and the sum of the two is retained in the accumulator. The result may then be stored in a new memory location to leave the arithmetic unit free to continue other processes.

## CONTROL UNIT

All the data movements and manipulations must be correctly sequenced and routed. This is the task of the control unit which acts as switching device. As each programmed instruction is extracted from the memory it is translated into a series of actions which direct the memory and arithmetic units to supply and process the appropriate data. The control unit also directs the input/output unit when an instruction requires action on the part of a peripheral device.

## THE FUTURE

Future developments look towards the building of smaller computers. Increased use of integrated circuits has already caused the central processor to become one of the physically smaller units of a system.

It appears that the domestic computer may soon become a reality. Industry and commerce will be able to draw data from central banks via a world-wide computer network, using satellite communication systems. □

**Computer usage is not restricted to office and factory. Here, a small computer is mounted on an experimental potato picking machine. The use of this computer is to control and evaluate the performance of the machinery. (Digital Equipment Company Ltd.)**



Everyday Electronics, February 1972



# TEACH-IN

## ... FOR BEGINNERS

By Mike Hughes M.A.


### 4

## POWER

**L**AST month when we connected the 10 kilohm resistor in series with a 1mA meter, the reading in milliamps had the same numerical value as the voltage that was driving the current. Go back to using the single 10 kilohm in series with the meter and change the voltage of the battery to 4.5 volts. The current will be 0.45mA. Thus by changing the scale of the meter, we have a simple voltmeter which can measure up to 10 volts full scale. By putting two 10 kilohm resistors in series we have a voltmeter with a full scale reading of 20 volts. A two range voltmeter is shown in Fig. 1.

Make yourself a simple voltmeter using these principles. Initially it can be made up on the Demo Deck but if desired a separate meter could be bought and a separate instrument made.

A voltmeter of this type will usefully measure voltages in many electronic circuits but it suffers from a problem. This problem is that it has a resistance that in itself can "shunt" the circuit which is providing the voltage to be measured.

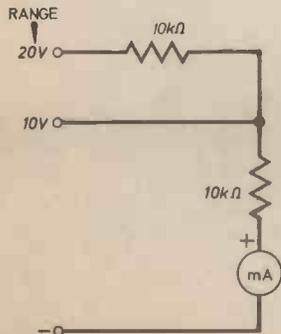

**Fig. 1. A two range voltmeter. The numerical value of the current (in milliamps) gives the voltage value being measured.**

This upsets the balance within the circuit and an erroneous voltage will be measured which will always read lower than actual. This means that the meter lacks sensitivity.

### SENSITIVITY

The sensitivity of a meter is rated as the number of ohms the meter presents for every volt it measures. The unit we have just made is 1,000 ohms per volt and is fairly poor; more typically one requires a meter having a sensitivity of at least 10,000 ohms per volt. To make this we would have to use a basic movement having a sensitivity of 100 microamps (a microamp is one millionth of an ampere) and all our resistors would have to be scaled up in value by a factor of 10.

Test the effect of poor voltmeter sensitivity by connecting two 22 kilohm resistors in series across a 9V battery, and then use our 1,000 ohms per volt meter to measure the voltage between one end of the resistors and the common junction of the two (Fig. 2), then do the same with two 1 kilohm resistors. The reading should be 4.5V.

Justify in your own minds exactly what is happening and why the actual reading is less. The reason for this is that the 10 kilohm resistance of the meter has more shunting effect on the circuit using 22 kilohm resistors than with that using 1 kilohm resistors.

### POTENTIAL DIVIDERS

The circuit of Fig. 2 is sometimes called a potential divider because the midpoint of two resistors has a potential which is based on the

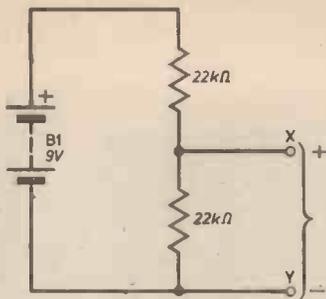


Fig. 2. Circuit for demonstrating voltmeter sensitivity.

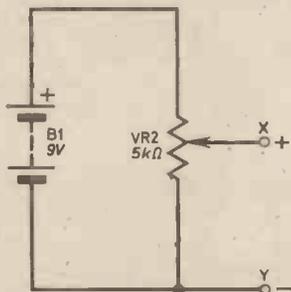


Fig. 3. The circuit diagram to be wired up on the Demo Deck to illustrate the function of a "potential divider."

potential difference across both resistors and the ratio of their values.

Substitute VR2 for the two resistors and use the wiper as the midpoint which can be varied in position to alter the ratio of the resistances either side of the wiper (Fig. 3). Measure the voltage between one end and the wiper as the knob is turned. You should get a smooth change from zero to 9V. Now try the same experiment with VR3 and VR4.

There is a great deal one can say about the principles of resistor networks, but in this beginners guide we have covered just sufficient to be of use later.

## POWER

We are all familiar with the term POWER when applied to electricity. In any context it is the ability to do work whether it be manpower, horsepower or electrical power. In the latter case it is usually associated with the ability to heat something, light something or move something—the cone of a loudspeaker for example.

Driving voltage itself is not sufficient to do work—we must have current flow as well. Power is a function of both voltage and current and is measured in units of or fractions of a "watt".

Power measured in watts,  $P = V \times I$

where  $V$  is the potential difference in volts and  $I$  is current flow in amperes. We can use this expression to calculate any one of the terms if the other two are known.

The current drawn by an electric fire of power 1.5 kilowatt (1.5kW) running from 250V mains

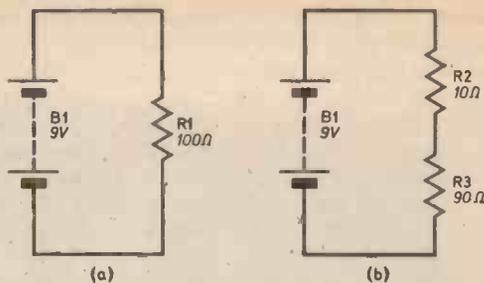


Fig. 4. The power dissipated in R1 is greater than in each of R2 and R3, but the total power dissipated in each circuit is identical.

will be given by

$$I = \frac{P}{V} = \frac{1500}{250} = 6 \text{ amperes}$$

Most frequently we are concerned with calculating the amount of power required by or dissipated in a circuit. The power dissipated in a resistor shows itself as heat, and is calculated from the current flowing through the resistance and the potential difference across it. The "potential drop" is equal to the value of the resistor multiplied by the current flowing through it (Ohm's Law)— $V = I \times R$ . We can substitute  $I \times R$  for  $V$  in the expression for power and obtain

$$P = I \times I \times R \text{ this is usually written } P = I^2 \times R$$

This means that we can calculate the power dissipated in any resistor purely from knowing the current flowing in the resistor and the ohmic value of the resistor.

Look at Fig. 4a. We have a 100 ohm resistor connected across a 9V battery. What is the power dissipation in it? First of all calculate the current:


$$I = \frac{V}{R} = \frac{9}{100} = 0.09 \text{ ampere}$$

The power dissipated is therefore,

$$0.09 \times 0.09 \times 100 = 0.81 \text{ watt.}$$

Resistor R1 would have to be capable of dis-

Fig. 5. The ORP12, a typical photo conductive cell, shown in diagrammatic form together with the circuit symbol and designation, PCC, for these devices.

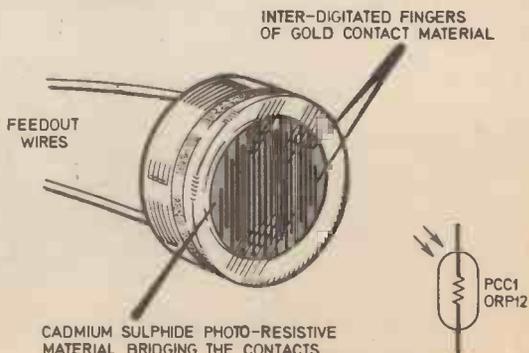

sipating this amount of heat without undue rise in its temperature and the nearest commercially available type is a one watt device.

Fig. 4b shows two resistors in series across a 9 volt battery. Try calculating the dissipation in each resistor. First of all calculate the current flowing through the circuit as a whole then use this value of current in conjunction with the ohmic value of each of the resistors in turn. The answers are 0.08W for R2 and 0.73W for R3. Note that, although they are in the same circuit there is considerable difference in their respective dissipation. To prevent overheating the nearest commercial grades that we would use are  $\frac{1}{8}$  and 1 watt devices respectively.

## LIGHT DEPENDENT RESISTOR

Some electronic components have their maximum rating specified in terms of power as opposed to current. This is usual when overheating is likely to cause irreparable damage to the component. A typical example of this is the photo conductive cell or light dependent resistor. This is a very interesting and useful component because it enables us to make a whole range of simple but fascinating circuits that are actuated by light.

As its name implies it is a resistor whose ohmic value varies as light falls on it. The one we shall be talking about is readily available

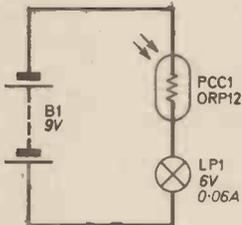


Fig. 6. (above) The circuit to demonstrate the action of a photocell. When bright light is incident on the cell, the lamp LP1 will light. (below) The wiring of this circuit on the Demo Deck.

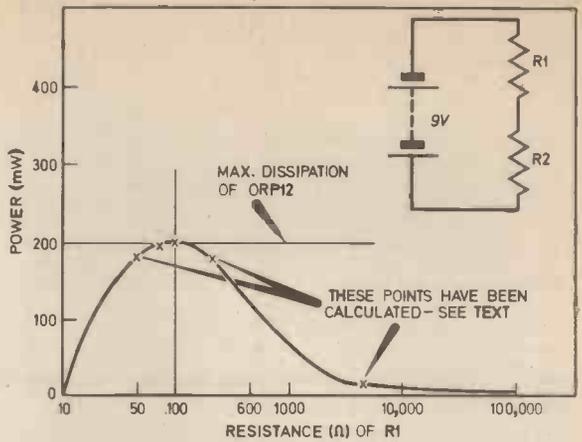
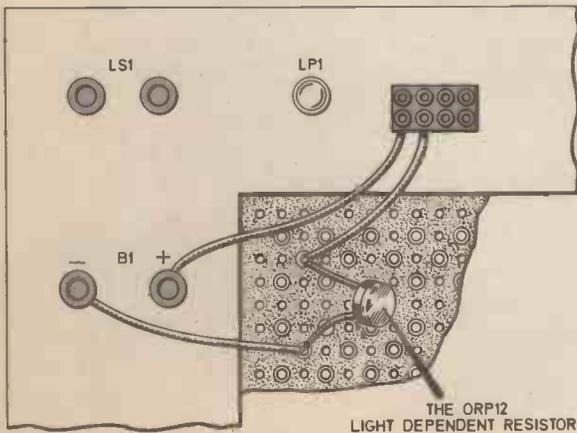


Fig. 7. Graph showing the power dissipation in R1 for various values of resistance with R2 held constant at 100 ohms. This is a maximum when  $R1 = R2$ .

and comparatively cheap—the ORP12. The appearance of the device is shown together with its symbol in Fig. 5; you can see that, like a resistor, there are two leads from it and the polarity of connection is not important.

There are several different types of this device (the ORP12 is perhaps the most common) but they can all be recognised by the distinctive interlocking fingers making contact with the photosensitive material—cadmium sulphide (CdS). Photographers will no doubt be familiar with the device because it is used as the sensor in CdS exposure meters.

The manufacturer of the ORP12 states that the resistance will typically vary from 10 Meg ohm in absolute dark conditions to approximately 75 ohm in conditions of extreme brightness. They also state that at no time may one dissipate more than 200mW in the device nor may one operate it with a potential difference greater than 110V across it.

## EXPERIMENT

Use the Demo Deck to wire up the simple circuit of Fig. 6. Under normal room lighting conditions the resistance of the cell will be in excess of 500 ohm and this will prevent sufficient current to light the lamp. If you shine a very bright torch at the cell from close range you can make its resistance fall to approximately 75 ohm and the lamp will light up. You will probably be aware that the sensitivity of this circuit is poor because all the control is effected with extreme levels of light. This is because we are requiring the cell to pass quite a high current (60mA) to light the lamp and it is rather difficult to make its resistance fall sufficiently to do this.

Try working out the power dissipation in the photo cell for various light levels and see if we are exceeding the manufacturer's rating. The resistance of the photo cell varies typically from 5 kilohm down to 75 ohm for the range of lighting we are considering. Because the current

**Table 1: REFERENCE DATA AND CHARACTERISTICS OF THE ORP12**

Maximum power dissipation (ambient temp 25 degrees centigrade)	200mW
Absolute maximum cell voltage	110V
Cell resistance at 50 lux	2.4 kilohm
Sensitive area	0.6 cm <sup>2</sup>
<hr/>	
Typical resistance at 1000 lux with lamp colour temperature 2700 degrees Kelvin	75-300 ohm
Ultimate dark resistance at 110V	10 Megohm
Nominal rise time of resistance	75mS
Nominal fall time of resistance	350mS

through the cell will change as its resistance changes we cannot say that the power dissipation will be the same for every condition, in fact it is quite definitely *not* the same.

Try calculating the power dissipation in the photo cell when it has the following resistance values: 5 kilohm, 200 ohm, 100 ohm, 75 ohm and 50 ohm. To help you, assume that the bulb is simply a 100 ohm resistor.

You should find that when the photo cell resistance is 100 ohm the power dissipated is 202mW and at either side of this resistance value the dissipation is less. This is very important to appreciate because it tells us that the power dissipated is a maximum when the resistance of the cell equals the resistance of the load (the bulb). Strictly speaking, we are overstretching the capabilities of the photo cell by about 1 per cent when its resistance is exactly 100 ohm. In practice, however, this condition is unlikely to be maintained for any considerable period of time and besides, the dissipation limitation has a safety factor on its side and a momentary stress in excess of the rating can be permitted.


## SPECIFICATIONS

Sooner or later one will need to refer to the manufacturer's specifications regarding components. Through this series we shall give you the most important specifications of the components we are using. The ORP12 is quite easily specified—see Table 1.


The parameter "Lux" is a measurement of light intensity; 50 lux is that equivalent to a dimly lit room while 1,000 lux is an exceptionally bright light—the intensity to be obtained a few inches away from a 100 watt bulb. The only parameter which you might not understand at this stage is the rise and fall time. These indicate that it takes a period of time for the cell to respond to changes in light level—the times shown for the ORP12 are quite long by electronic standards and are due to the fact that the reaction within the cell is almost a photochemical effect. Some other types of photoelectric devices can respond to millions of changes of light per second!


## EXPOSURE METER EXPERIMENT

We have already said that the light dependent resistor is used in cadmium sulphide exposure

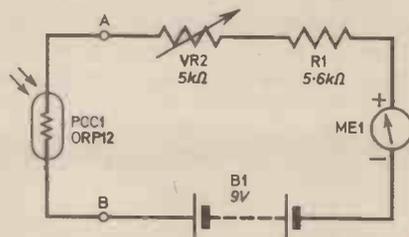

**Fig. 8. (above right) The circuit diagram for a simple ohm meter which can be calibrated for use as an exposure meter. (right) This circuit wired up on the Demo Deck.**

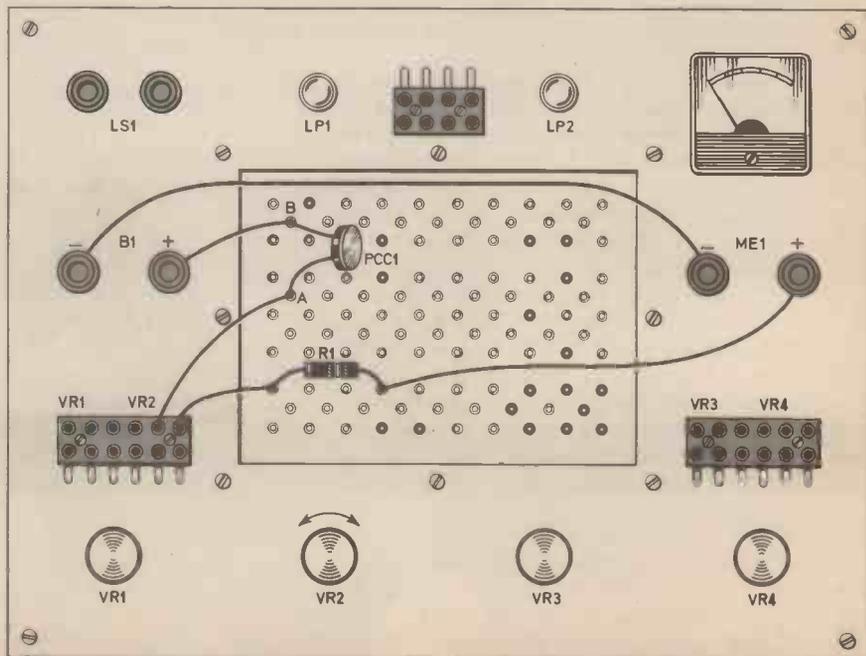

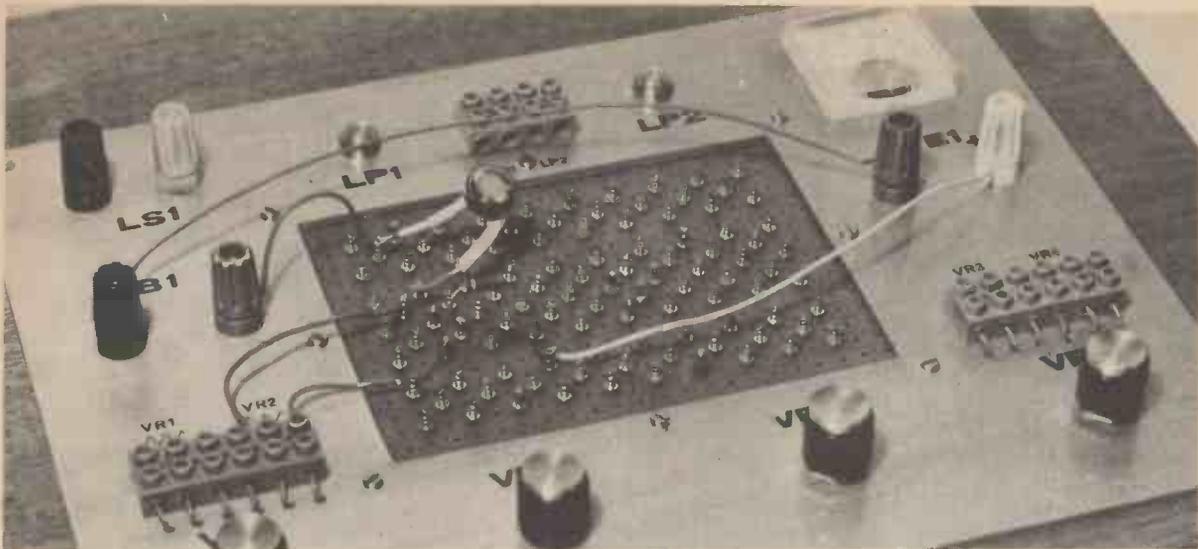

meters so now we will use the Demo Deck to make a simple version of this. Fig. 8 shows the circuit. It is a simple ohm meter where the ORP12 is a resistor whose ohmic value we shall be constantly observing.

It is usual with ohm meters to have zero ohm reading full scale on the meter. We are using a 1 mA (f.s.d.) meter, so must arrange that when we short circuit the input to the meter (across points A and B) exactly 1 mA is permitted to flow. As we are using a 9 volt battery we must incorporate a limiting resistor.

This is calculated using Ohm's Law,

$$\text{i.e. } R = \frac{V}{I} = \frac{9 \text{ ohm}}{0.001} \\ = 9 \text{ kilohm}$$

Because the battery voltage will vary a little with time we must make this resistor variable so that we can always set a zero ohm reading of full scale.


We could use a 10 kilohm potentiometer to do this but there is a danger that while adjusting it one might inadvertently reduce the resistance value to zero and pass excessive current through the sensitive meter. To prevent this happening we shall use a fixed resistor of 5.6 kilohm in series with VR2 (5 kilohm) on the Demo Deck. The combined effect of these two resistors will give us a variable range from 5.6 to 10.6 kilohm—ample to allow for battery variations but at the same time it will be impossible to pass more than about 2 mA through the meter (this would not cause any serious damage to the meter). With new batteries we should get our full scale zero ohms reading with VR2 set to almost maximum resistance.

#### METHOD

When set for zero ohm at full scale, disconnect the short circuit between points A and B and allow the ORP12 to come into circuit. We are now introducing extra resistance, thus the

current through the meter will fall. If a lot of light is falling on the cell its resistance will be low (say 100 ohm) and this will have very little effect on the total circuit resistance, hence the meter will still read fairly high up the scale. If you prevent light falling on the cell, its resistance increases rapidly and the current displayed on the meter falls dramatically. Different levels of light between these extremes will give graded readings on the meter. For a given film speed one could carry out some trial exposures and experimentally produce a scale (or graph) which will convert the meter current reading into photographic light value numbers.

Next month : Capacitors

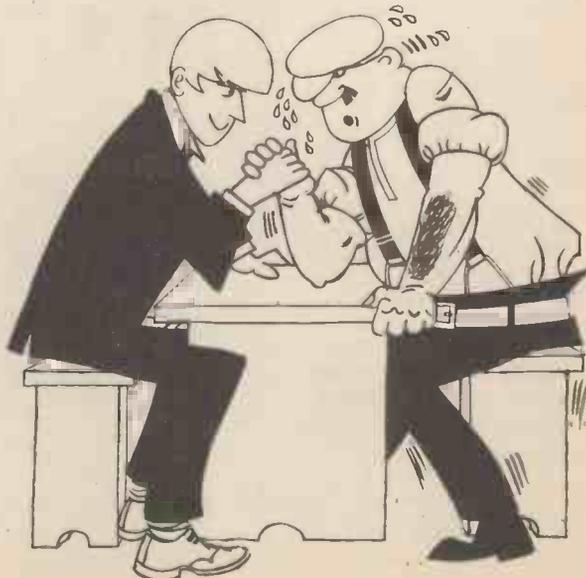

# rain warning ALARM

By  
Frank Brown

Protect the washing from rain, snow and damp with this simple device.

**T**HE device to be described will provide an alert when rain or snow is falling or when the atmosphere is saturated as when steam or mist is forming. It can serve as a water level alarm with no modifications to the sensor input and, as it is sufficiently sensitive to detect a human breath at a foot range, it could find use as a novelty item at parties.

Two alarm circuits are offered; an audio tone generator pitched at 2.5kHz and a lamp flasher. While a tone is to be preferred for remote hailing a flashing lamp would be preferable to a person hard of hearing or if the device is used in a party role.

## COMPOUND PAIR

The transistors TR1 and TR2 in Fig. 1. are so arranged to very much magnify any small current that might appear at the base/emitter junction of TR1. This compound pair configuration is a cheap way of making up what is, in effect, a very high gain transistor with an amplification factor that approximates to the product of the individual transistor gains.

The small current to be amplified is produced whenever snow, rain or moisture bridges the copper strips of a 0.1 in. matrix veroboard sensor which appears in the input circuit.

These strips are so connected (Fig. 2.) as to make the whole board area moisture sensitive.

The load of the compound pair is the alarm circuit comprising TR3 and TR4. Since the smallest of input currents to TR1 is capable of switching TR2 hard on, this means that nearly

all of the line volts will appear at the junction of the collectors of the compound pair.

## AUDIO ALARM

The audio alarm circuit consists of a *pnp/npn* free running multivibrator designed to produce a penetrating tone without recourse to a transformer.

The Fletcher-Munson curves of equal loudness show that the human ear is most sensitive to sounds between 2kHz and 4kHz. Using the components specified, the alarm will produce a note of approximately 2.5kHz and, although the power output from the alarm is relatively small the note produced is quite piercing.

With moisture completing the input circuit and TR2 switched on, C1 charges by way of R2, R3 and LS1 until the voltage it acquires is sufficient to switch on TR3 which, in turn, switches on TR4. The collector of TR4 is thus taken to a negative potential. The switching process is hastened by feedback through C1 so that TR4 is very rapidly bottomed.

This change cannot immediately be followed

Approximate cost of components

£

1.80 excluding case

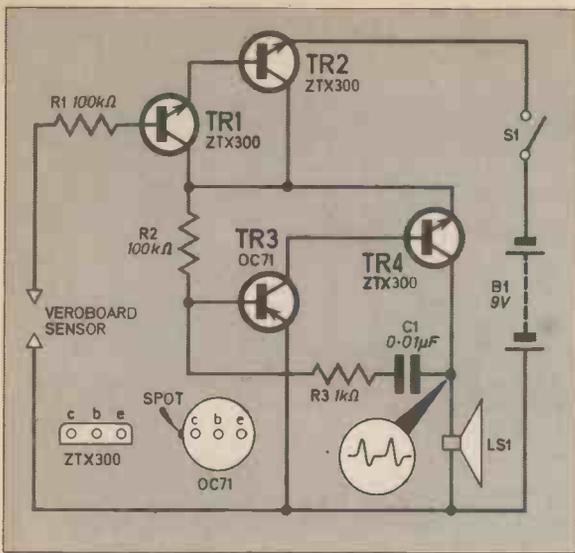


Fig. 1. Circuit diagram of the rain warning alarm.

by C1 which discharges via R3 and TR3 base/emitter. Having R3 in circuit increases the discharge time constant and therefore, the mean d.c. level to the loudspeaker which, of course, means a greater sound output.

With the discharge of C1 both TR3 and TR4 are cut off and the oscillator recycles. The frequency at which the transistors are turned on and off and therefore the frequency of the tone generated depends on the value of C1 and the resistance of its charge path; an increase in either means a decrease in frequency and vice-versa. The output waveform appearing across LS1 is shown in Fig. 1.

If at any time after the unit is built greater sound output is required a 0.47μF capacitor connected across the loudspeaker will prove a simple expedient rather than experimenting with different values for R3. It must be realised that any increase in output will mean a heavier current drain. With the components given, consumption with the oscillator functioning worked out at around 15mA.

## LAMP FLASHER

Since this type of multivibrator circuit provides periodic short bursts of power (see output waveform) to a load it is ideal for flashing a lamp.

To change the alarm circuit of Fig. 1. for lamp operation means the change of only three components. A 6V 0.06A lamp replaces LS1, and R2 and C1 are changed to 470 kilohms, and 2.2μF respectively. If an electrolytic is used for C1, the positive side must be connected to the collector of TR4.

For the timing components given above the flash rate is about two flashes every second.

Since the flash interval is very brief battery power taken is small compared to the audio alarm.

## CONSTRUCTION

The majority of components are mounted on a 2½ inch x 1 inch, 0.15 inch matrix piece of

## Components....

### Resistors

R1 100kΩ (or 500kΩ lin. potentiometer—see text)

R2 100kΩ

R3 1kΩ

All ½ watt ±10% carbon

### Capacitor

C1 0.01μF

### Transistors

TR1, TR2, TR4 ZTX 300 silicon npn (3 off)

TR3 OC71 germanium pnp

### Loudspeaker

LS1 8Ω 2in diameter (or similar small speaker—see text)

### Switch


S1 Single pole on/off toggle

### Miscellaneous

B1 PP9 battery, 5in x 4in x 2½in aluminium chassis, Veroboard 16 holes x 7 strips 0.15 matrix (see text), 4in x 3in x 0.1in matrix (for sensor), wire, 4 BA fixings.

Shop Talk refers
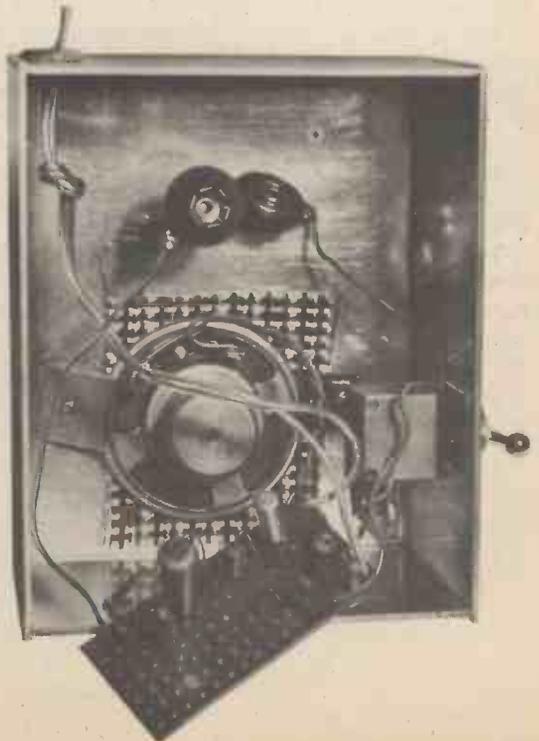
## Prototype construction of the Rain Warning Alarm.



# rain warning

# ALARM



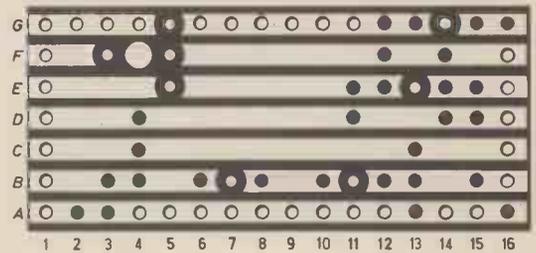
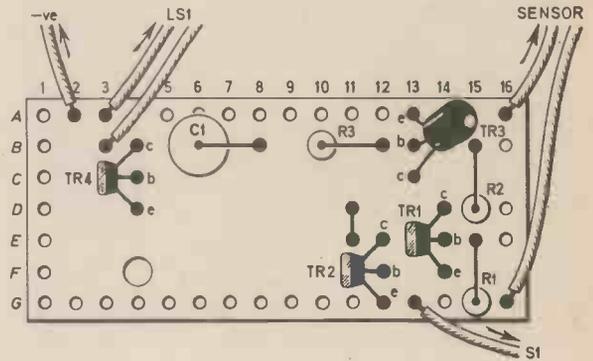
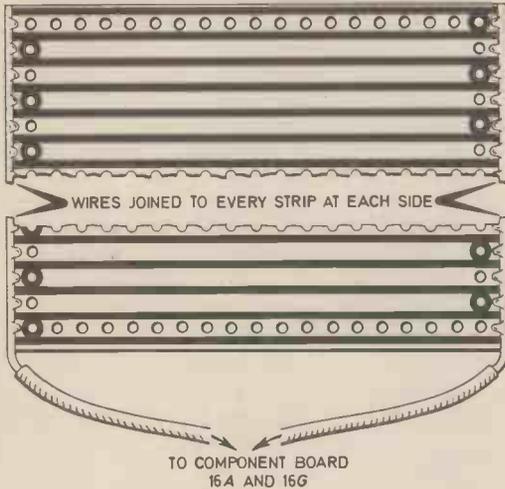


Fig. 2. (above) Wiring of the Veroboard strips to form the sensor.

Fig. 3. (right) Layout and wiring of the components mounted on the Veroboard.

Fig. 4. (below) Layout and wiring of all parts mounted in the case.

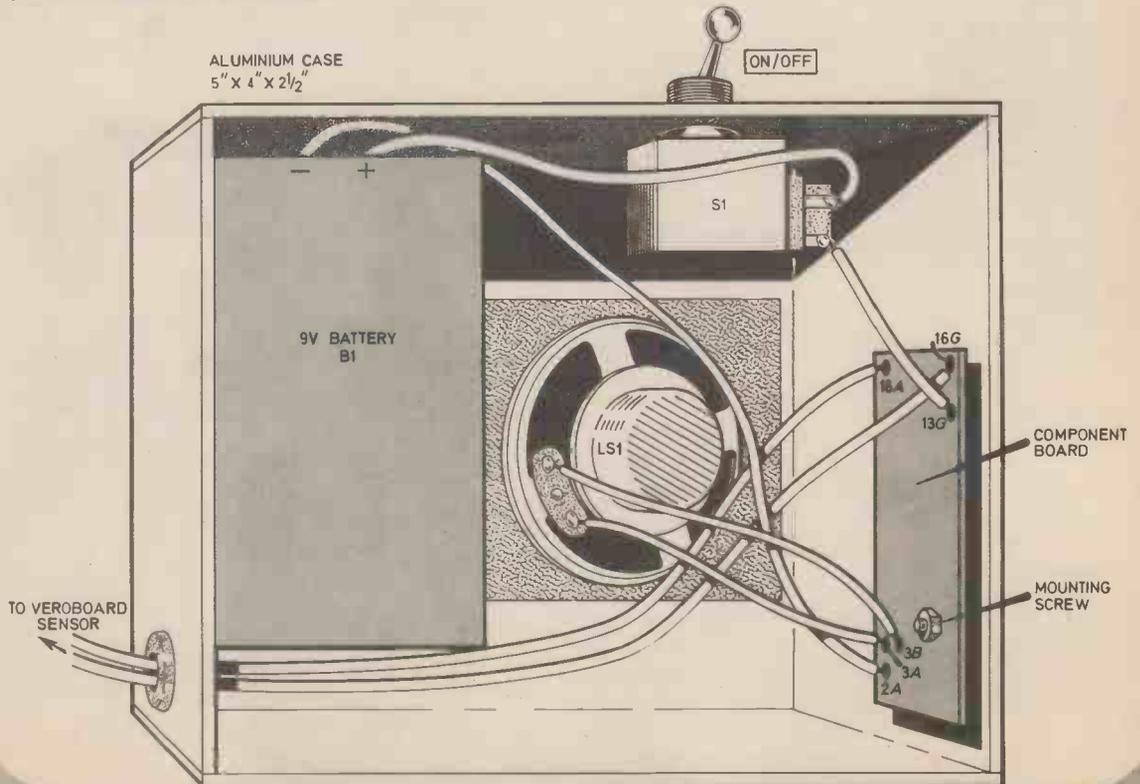

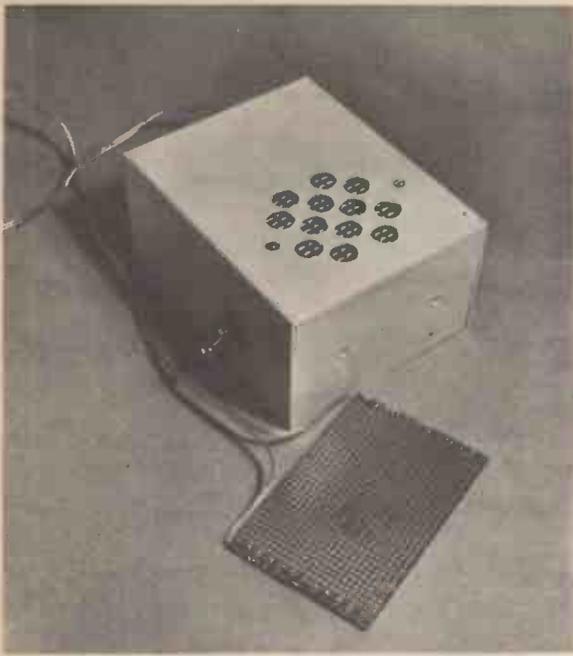

The completed unit with the sensor

Veroboard (the same size as that given away with the first issue), with the speaker and switch arranged on a small aluminium case.

The circuit performance will not suffer from alternative forms of layout so tag-strip or Cir-kit can be used.

The Veroboard layout and wiring diagram is shown in Fig. 3. The size of the piece of board used could be reduced slightly if a very compact unit is required, however since the battery used should be fairly large for a long life, reduction in size of the Veroboard was not considered advantageous. Construct the board as shown in Fig. 3 taking care when soldering the transistors not to overheat them. This particularly applies to the OC71 which is a germanium device and which should be soldered in, using a heat shunt, after all other components and leads have been attached.

After checking the board for mistakes, mount it in the case and connect up S1, LS1 B1 and the sensor (Fig. 4). Finally check the circuit and the battery polarity and switch on. A quick operational check can be made by touching the copper strips on the sensor with one finger, the unit should immediately give the warning signal. Test the sensitivity of the alarm by blowing on the sensor.

If required a small two-way socket may be included in the lead to the sensor (which is not polarity conscious) so that the sensor could be disconnected from the unit for installation.

When making up the Veroboard sensor simply solder on two lengths of wire at either end of a 4 inch x 3 inch piece of 0.1 inch matrix Vero-

board so that the wire bridges all the copper tracks. Then, with a spot-face cutter or twist drill, make breaks on either side to alternate tracks as in Fig. 2. If high sensitivity is not required the size of the piece of Veroboard used may be reduced. The 0.1 inch matrix board is however most suitable.

If other values of loudspeaker are to hand, such as 3 or 15 ohm types, these can be used but it will mean experimenting with the value of C1 since substitution will produce frequency change.

## APPLICATIONS

When siting the sensor the only requirement is that it should be placed on a flat surface. The length of lead to the sensor will not affect circuit performance.

If a 500 kilohm potentiometer is substituted for R1 the input sensitivity can be made variable. Since the base/emitter breakdown voltage of the ZTX 300 is 5V there is no danger of transistor destruction for the condition of maximum sensitivity with little resistance in the input line.

For use as a water level alarm the sensor should be arranged vertically with the lower two tracks at the required height. Obviously, rising water bridging these tracks will trigger the alarm.

As a novelty item the Veroboard could be attached to the top of the aluminium chassis. For this the lamp flasher circuit is used so that anyone breathing or blowing on the sensor literally blows the lamp on. ■



# USING STICK DOWN WIRING

The Waa Waa Pedal featured in this issue utilises stick down wiring; this article describes how to use it.

THE series of photographs below show how to use stick down wiring; photographs (a) to (e) show the *Waa Waa Pedal* being built.





Stick down wiring or Cir-kit, to use its trade name, is available in two sizes  $\frac{1}{16}$  and  $\frac{1}{8}$  inch width, and can be used with either plain or perforated, mounting panels. The *Waa Waa Pedal* unit described in this issue utilises  $\frac{1}{16}$  inch width Cir-kit with a perforated s.r.b.p. panel. The Cir-kit forms the connections in the same way that the copper on Veroboard or a printed circuit form connections for the components.

## LAYING THE CIRCUIT

To use stick down wiring first design a component layout or use that provided in the article (Fig. 3 in *Waa Waa Pedal*), cut the circuit board to size using a hacksaw, drill any mounting holes

and de-burr the board. The *Waa Waa Pedal* design utilises Veroboard pins for the connection of flying leads and this practice is to be recommended when using Cir-kit. The pins provide firm anchorage points for the leads and hence no strain is put on the copper strips. The pins should be inserted by supporting the board under the pin and tapping the pin in gently until it is half-way through the board (a). Mark the position of each copper strip on the board using a felt tip pen. Once all the pins have been inserted and checked the Cir-kit can be laid.

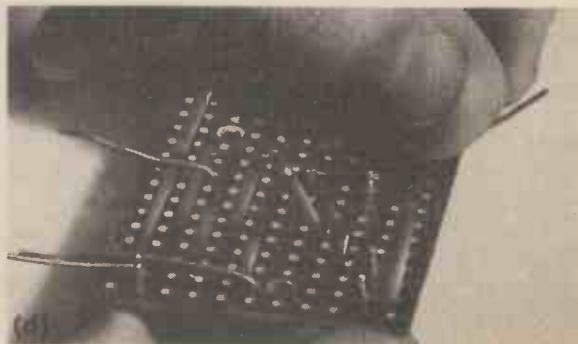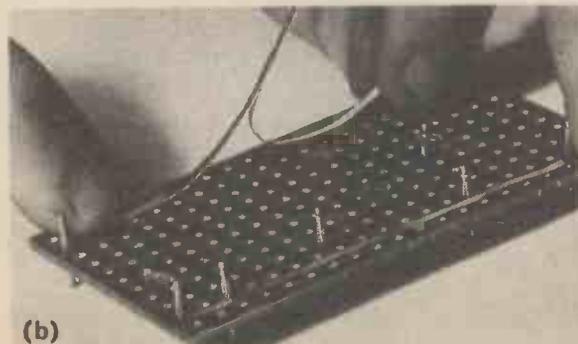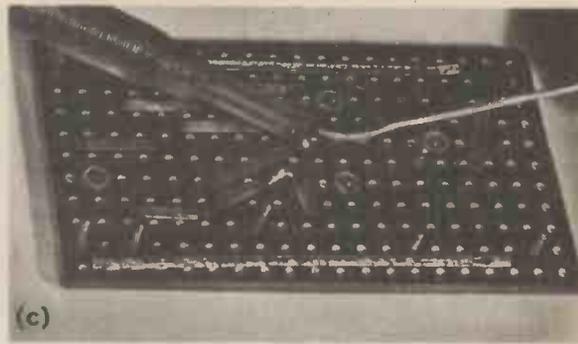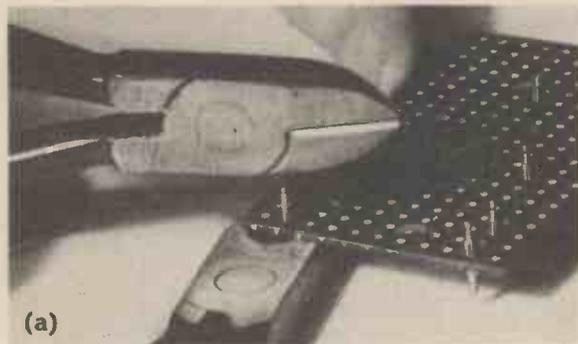Lay the copper strip along the first section marked and cut the strip to the required length for this section. Check the length and position and carefully peel off part of the white backing strip, taking care not to touch the self adhesive back. Position the strip, peel off the remaining



backing and lay the strip in place pressing the ends firmly down (b). Continue to lay each strip until all are in place, check the layout and firmly press all strips down; this can be done using the side of a pencil or a finger nail, run along each strip. If a strip is found to be incorrectly positioned it can be carefully removed, before pressing firmly down, and replaced.

Where there are bends in the strip cut the copper in sections so that each straight section can be laid with an overlap on the next straight section. Next go over the strips and bridge each corner with solder so that each strip forms a continuous electric circuit (c).

## MOUNTING COMPONENTS

Mount all the components (except any diodes and transistors) drilling all holes in the appropriate positions first, if using plain s.r.b.p. board, holding the components in place by their leads bent over onto the copper strip (d). Check that all components are mounted in right positions and that any polarities are correct, e.g., on electrolytic capacitors. Cut off the excess wire so that only a small part is bent over the copper strip to hold the component and solder this part to the copper. Next cut some lengths of p.v.c. covered stranded connecting wire and, after stripping about  $\frac{3}{16}$  inch of the covering off, twist the strands together and tin the end, connect these wires to the pins by wrapping them around the pin and soldering (e). Check the positions of the components and leads and each soldered

joint before continuing.

## SOLDERING SEMICONDUCTORS

Finally, the transistors and diodes can be mounted and the board checked carefully. When mounting germanium transistors and diodes you must always use a heat shunt to protect them from the heat of the soldering iron and it is wise to carry out this practice when mounting silicon devices also.

The heat shunt, which can be a pair of long nosed pliers or a proper shunt sold for the purpose, is held between the component and the joint to be soldered, on the lead to which the soldering is being carried out. Keep the shunt on the wire until the joint has cooled down before transferring it to the next lead.



Transistors and diodes are mounted on the board and soldered in the same way as other components—checking position and polarity before cutting the leads and checking joints after soldering.

Once all the components and flying leads are mounted it is advisable to check the whole board against the circuit diagram, checking each joint of every component and making sure that no components link with any components or wires that they are not meant to.
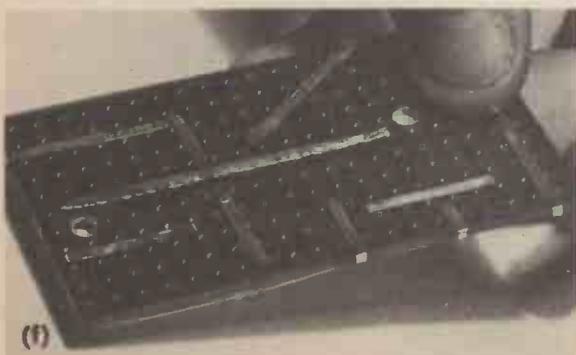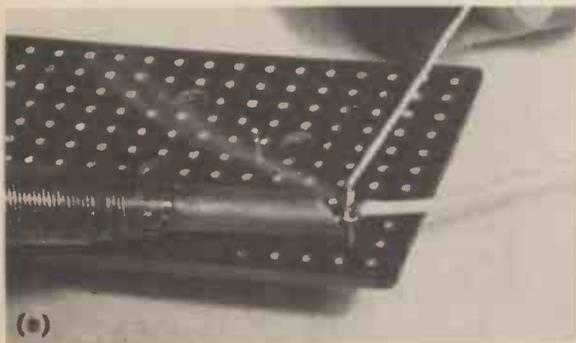
## ADVANTAGES

Stick down wiring has some advantages that are not apparent from the *Waa Waa* board design. The first of these advantages is that cross-overs of the strip can be made easily by making a "bridge" over one strip using insulation tape and laying the second copper strip over this (f). The copper strip may also be taken around the edge of the component board so that the circuit pattern can be continued on both sides of the board should this be required (f).

Finally a word of warning, when soldering to Cir-kit it is best to be as quick as possible as excess heat will affect the adhesive and eventually lift the copper away from the board. This point should be noted when fitting the components as any desoldering of those mounted incorrectly will hasten the peeling off of the strips. If this does happen another strip will have to be laid to replace the damaged one. □



Photographs showing how to use stick down wiring.

- (a) Inserting pins for flying leads.
- (b) Laying the copper strip.
- (c) Joining the corners with solder.
- (d) Mounting components—all except semi-conductors.
- (e) Fixing the flying leads.
- (f) A cross-over and continuation of the strip on the other side of the board.

# WAA-WAA PEDAL

by P.J. Tyrrell

Add this exciting sound to your world of music

THE waa waa effect so often heard in "pop" music nowadays, is produced by passing the audio signal from a musical instrument such as an electric guitar or electronic organ through a filter network. Varying the characteristics of the filter generates the waa waa sound.

## FILTER CIRCUIT

The filter employed in this circuit is comprised of components C2, C4 and L1 (Fig. 2).

If we plotted a graph of the output voltage level against the frequency of the input signal we would obtain the curve (a) shown in Fig. 1.

By varying any of the three filter components, it is possible to shift this curve along the frequency axis as shown by curves (b) and (c) thus varying the characteristics of the filter. By doing this smoothly and continuously the desired waa waa sound is produced.

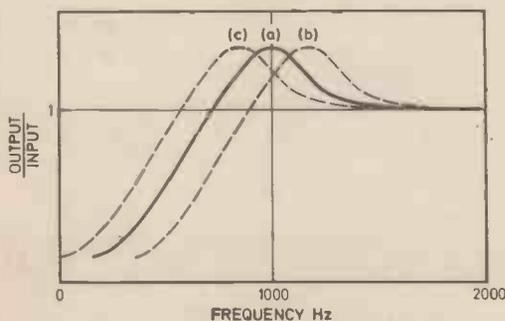


Fig. 1. Filter characteristics.

## COMPLETE CIRCUIT

The complete circuit diagram is shown in Fig. 2. The first stage containing transistor TR1 is a standard circuit configuration called an "emitter follower". This is merely a matching device which presents a very high input impedance, such as required by an electric guitar, with

a low output impedance suitable for inputting to the waa waa generator.

The waa waa generator itself is made up of transistors TR2 and TR3 which are both connected in the "emitter follower" mode on either side of the filter network.

Feedback from the output of TR3 is through R7 and VR1 to the input of TR2. This is known as a "positive feedback loop".

The function of capacitors C3 and C5 is to prevent the passage of any d.c., only allowing the a.c. signal to pass unhindered.

The input signal to TR1 emerges at the emitter and is passed via capacitor C2 to the base of TR3 and at the same time applies a voltage to the B side of the inductor L1. The signal out of TR3 is fed back to the base of TR2 via the potentiometer VR1 (which is linked to the pedal) and a signal is caused to pass through the emitter circuit of TR2 applying a voltage to the A side of L1, the magnitude of this voltage being governed by the setting of VR1.

Thus, so far we have deduced that an input signal causes a potential difference to be set up across the inductor L1, and the magnitude of this potential difference is proportional to the amount of signal fed back to side B of L1 via VR1.

Thus by varying VR1, using the foot pedal, the potential difference across L1 can be varied. This variation of potential difference across L1 causes the effective inductance of L1 to vary and hence alter the filter characteristic, producing the waa waa sound at the output.

Approximate cost of components



2.90 excluding case

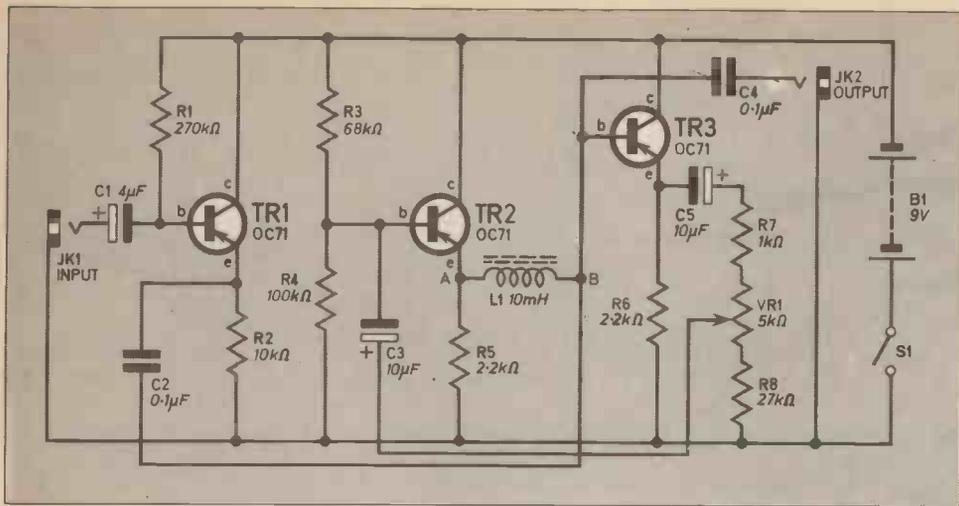


Fig. 2. The complete circuit diagram of the waa unit.

## Components....

### Resistors

- R1 270k $\Omega$
- R2 10k $\Omega$
- R3 68k $\Omega$
- R4 100k $\Omega$
- R5 2.2k $\Omega$
- R6 2.2k $\Omega$
- R7 1k $\Omega$
- R8 27k $\Omega$

All  $\frac{1}{2}$  watt carbon  $\pm 10\%$

### Potentiometer

- VR1 5k $\Omega$  linear

### Capacitors

- C1 4 $\mu$ F elect. 12V
- C2 0.1 $\mu$ F
- C3 10 $\mu$ F elect. 12V
- C4 0.1 $\mu$ F
- C5 10 $\mu$ F elect. 12V

### Transistors

- TR1, TR2, TR3 OC71 Germanium *pnp* (3 off)

### Inductor

- L1 10mH (approx) 520 turns of 40 s.w.g. enamelled copper wire wound on a ferroxcube pot core type LA1 or any other coil with an inductance of approximately 10mH

### Miscellaneous

- S1 On/off switch
- JK1, JK2 standard Jack sockets (2 off)
- B1 9V battery and clip (PP9)
- 0.15 inch matrix plain Veroboard (12 x 20 holes), Veropins,  $\frac{1}{16}$  inch Cir-kit stick-down wiring, 20 s.w.g. aluminium sheet, case and pedal materials: ribbed rubber sheeting, 2 $\frac{1}{2}$  inch door hinge, foam rubber, knob, small wood screws (10 off), 2 x 6BA bolts for inductor fixing, Meccano parts: 3 $\frac{1}{2}$  in. perforated strip, 2in. perforated strip with boss at one end, 57-tooth gear, 19-tooth gear, 1 $\frac{1}{2}$  in. perforated wheel, 1in. rod to suit perforated wheel.

Shop Talk  
refers

## FIXING TO THE BOARD

The main circuitry is built on a piece of 0.15 inch matrix plain Veroboard (12 x 20 holes) using Cir-kit stick-on wiring and Veropins. A full description of how to use this material is given on page 212.


The component and Cir-kit wiring layout and drilling details are shown in Fig. 3 (a) and (b). The layout is not critical and can be rearranged if desired to suit individual requirements. Veropins are used for flying lead connections. They are indicated in Fig. 3 (b) by a circle around the black dot.


## THE INDUCTANCE

The inductor is quite easily made by winding 520 turns of 40 s.w.g. enamelled copper wire on an LA1 ferroxcube pot core to give an inductance of 10 millihenries (mH).


If you do not like the idea of winding your own inductor there are some available on the market with values near to 10mH.

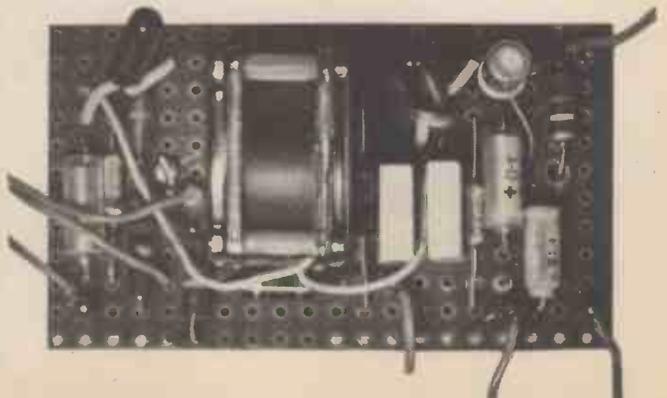This inductor is attached firmly to the board by means of two 6BA bolts through locations E12 and I12 from below before fitting the other components.



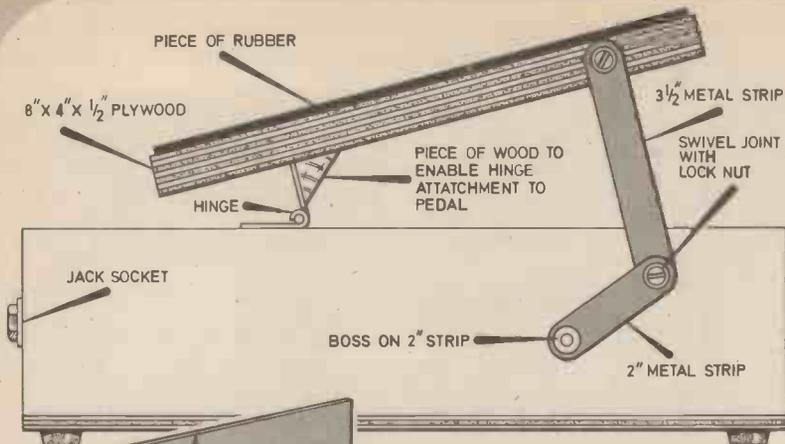


# Waa-Waa Pedal

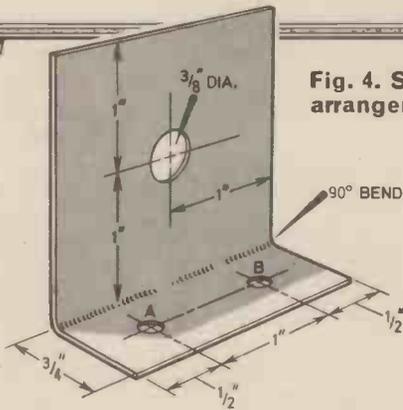

**Fig. 4. Side view showing pedal arrangements.**

**Fig. 5. The underside of the waa waa pedal showing positions of all components.**

**Fig. 6. The bracket dimensions for mounting VR1.**

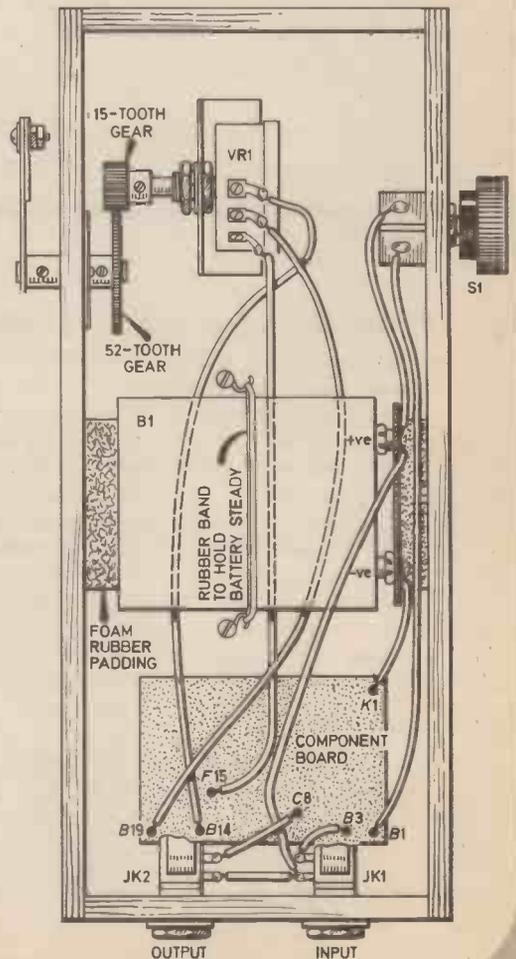

**Fig. 7. Case dimensions.**

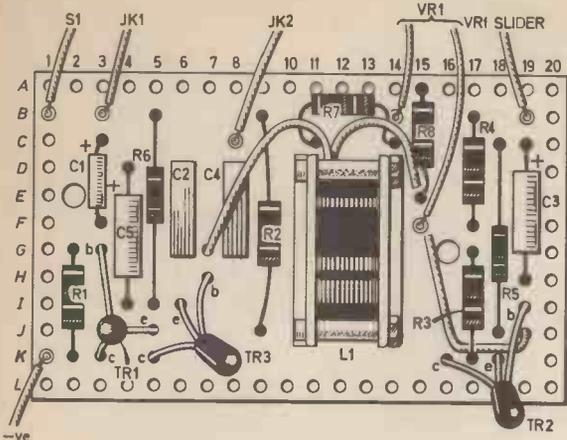


Fig. 3(a). Component layout on top side of board.

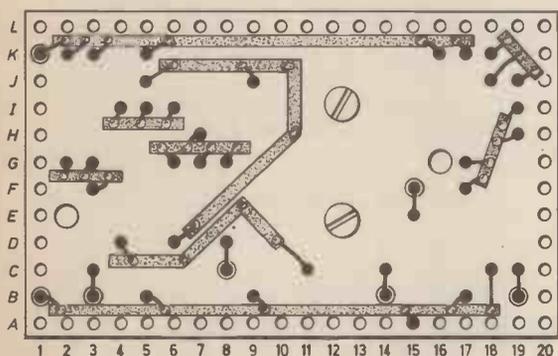


Fig. 3(b). Positioning of Cir-kit wiring on under-side of board.

## PEDAL POTENTIOMETER LINKAGE

In the prototype the pedal was linked to the potentiometer by means of some Meccano parts as shown in Figs. 4 and 5. A 19-tooth gear was drilled out and fitted on the shaft of the potentiometer, VR1, and a 57-tooth gear was mounted through the case (using a 1 inch length of rod, diameter  $\frac{5}{32}$  inch) using a perforated wheel screwed to the inside of the case which acts as a bearing.

Two perforated strips, dimensions in Fig. 4, complete the linkage mechanism.

It is not essential to use the above Meccano parts as brass strips, for example, will do equally well in place of the perforated Meccano strips. Also, the gears need not be as used in the prototype; any set of gears may be used so long as the up and down movement of the pedal moves the slider of VR1 over the majority of its track.

## CASE AND PEDAL

The case is shown in Fig. 7 together with its dimensions. The material used in the prototype was  $\frac{1}{4}$  inch plywood. All joints were nailed and

glued and the completed case was covered in a self-adhesive plastic material with a wood grain finish to give a neat appearance.

The pedal itself was made from a piece of  $\frac{1}{2}$  inch thick plywood and attached to the top of the case by means of an ordinary door hinge and a piece of wood as shown in Fig. 4. A piece of ribbed rubber sheet was glued to the top of the pedal to prevent slipping when in use.

## ASSEMBLY


Begin by screwing the pedal to the case top and attach the linkages, bearing and large gear to the case.

Secure VR1 to its mounting bracket, shown in Fig. 6, and screw in position. Turn VR1 fully clockwise, and with the pedal pulled up as far as possible, slide on the small gear and tighten in this position. Depressing the pedal will turn VR1 anti-clockwise.

The input and output sockets, JK1 and JK2, and switch S1 can now be fixed firmly in position. Screw the component board in position and connect up all the flying leads, Fig. 5.

Pieces of foam rubber should now be glued to the sides of the case where the battery will fit, and the battery placed in position. It can be held securely in this position by means of a strong rubber band across the battery fixed by wire clips as shown in Fig. 5.

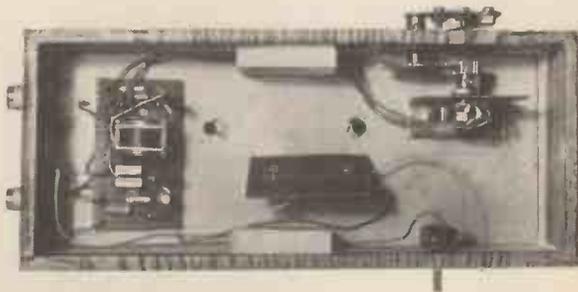Screw on the base and the unit is complete and ready for use. If desired four small rubber legs may be attached to the base to prevent slipping when in use.



Photograph of the prototype pedal. Coaxial sockets were originally used for the input and output socket.

## USING THE UNIT

This unit was designed for use with an electric guitar but can be used with almost any device since its input impedance is high. It should be interposed between the guitar and the amplifier and the waa waa effect is obtained by moving the pedal up and down whilst playing.

Different rates of pedal movement alters the waa waa effect produced.

If it is to be used with an electronic organ, the first stage of the circuit can be deleted, thus inputting directly to capacitor C2. □

# ACTION!

**O**N the borders of the Kent countryside our *Teach-In* author Mike Hughes conducts two evening classes in electronics at the Orpington and District Adult Education Centre. We went along one Wednesday evening to the "advanced" beginners class—Mondays for beginners who, at the time, were all busy building Demo Decks!

The advanced class, eleven of them, come from varied spheres—everything from a quantity surveyor to a printing firm director—and when we took the photographs they were all busy building test equipment. Most of the students took up electronics just over a year ago when Mike first started a beginners class at the centre, they have been aided in their quest for knowledge by a cash allowance from the college to purchase test gear kits.

Reasons for joining Mike's first class varied from general interest in building a specific item to requiring more knowledge of the electronics now being used at work (paint chemist). All the students are keen to learn and some have already built ambitious projects of their own.



The "advanced" beginners class, they are (from left to right, back row first) M. J. Algeo, J. B. Leach, H. A. Fussell, G. E. Gill, R. Hierons, B. B. Cox, Mike Hughes (standing) and P. J. Acock. Between them they are building a range of test instruments for their own use and for demonstration to the beginners class; the class already has an oscilloscope built by Mike Hughes.



# BI-PRE-PAK



**TELEPHONE DIALS**  
Standard Post Office type.  
Guaranteed in working order.

**ONLY 50p**

**8 RELAYS FOR £1**  
Various Contacts and Coil Resistances. No individual selection, Post & Packing 25p

### NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V. 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1,000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes. brand new stock clearance	50p
H18	10	OC71/75 uncodded black glass type PNP Germ.	50p
H19	10	OC81/81D uncodded white glass type PNP Germ.	50p
H28	20	OC200/11/213 PNP Silicon uncodded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

### NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/11 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mV. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

### MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



### OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.

### FULLY TESTED AND MARKED SEMICONDUCTORS

£p		£p	
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
AC177	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC107	0-13	2N1308-9	0-35
BC108	0-13	2N3819FET	0-45
BC109	0-14		
BF194		<b>Power Transistors</b>	
BF274	0-15	OC20	0-50
BFY50	0-20	OC23	0-30
BSY25	0-57	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-15	AD149	0-30
OC41	0-13	AU110	1-25
OC44	0-13	25034	0-25
OC45	0-13	2N3055	0-63
OC71	0-13		
OC72	0-13	<b>Diodes</b>	
OC81	0-13	AA42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN914	0-07

### F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 In a plastic encapsulation, coded as 3823E; it is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+20p each.



### BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC35 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

#### 1 amp Miniature Plastic Diodes

IN4001, 500+ at 4p each, 1,000+ at 3p each.  
IN4004, 500+ at 5p each, 1,000+ at 5p each.  
IN4006, 500+ at 6p each, 1,000+ at 5p each.  
IN4007, 500+ at 8p each, 1,000+ at 7p each.

### FREE CATALOGUE AND LISTS FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS & SUBSTITUTION CHARTS



### CLEARANCE LINES

#### COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

**NOW ONLY 50p each**  
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully-Tested Unmarked	5p	5p	4p
Matched Sets, 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p,	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rect's 25-volt	25p	22p	20p

#### INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	50p	40p	35p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
PA234 1-watt Audio Amp.	1-00	90p	80p
UL914 Dual 2 1/2 Gate	40p	35p	30p

#### LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each  
16 pin type at 16p each.

#### BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines:  
**B.P.I. Transistor Equivalents and Substitutes;** 40p  
This includes many thousands of British U.S.A., European and C.V. equivalents.  
**The Hi-Fi Radio Valve & Transistor Data Book 9th Edition;** 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.  
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....  
ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

# BI-PRE-PAK LTD

DEPT. E, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF  
TELEPHONE: SOUTHEND (0702) 46344

## BSR C.109 SUPERSLIM


### STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL

£7.75 Post 25p.

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves EOL152, E230/81. Response 50-12,000 cps. Sensitivity 200mV. Post 25p.

## R.C.S. PORTABLE PLAYER CABINET

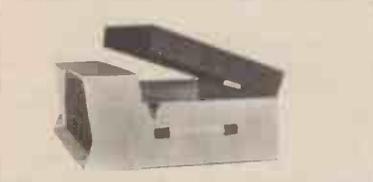

Really smart appearance with space for R.C.S. Amplifier and most modern autochangers. Size 18 x 16 x 8 in. Metal fittings. Carrying handle. Two-tone lacquer finish. Popular colours. £4 Post 25p.

GARRARD SINGLE PLAY TA MK II Ideal Discoboth or Hi-Fi. Stereo/Mono £10

GARRARD PLAYERS with Sonotone STA Cartridges Stereo Diamond and Mono Sapphire. SP25 MK III £16. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

R.C.S. TEAKWOOD BASE. Ready cut out for mounting (State player make and model) £2-75

R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. £2-25

EMI PICK-UP ARM with mono xtal and stylus £1-25. HI-FI PICK-UP CARTRIDGES. Diamond Stereo/Mono. STA £2-50; GP84 £2-50; GP93 £2-00; Mono GP91 £1-50; GC8 £1-25; ACOS LP. only 50p.

## E.M.I. WOOFER AND E.M.I. TWEETER KIT

£5-75 Post 25p

Comprising a fine example of a Woofer 10 1/2 x 8 1/2 in. with a massive Ceramic Magnet, 40oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines.

Impedance Standard 8 ohms  
Maximum Power 12 watts  
Useful Response 35 to 18,000 cps  
Base Resistance 45 cps

## WEYRAD P50-TRANSISTOR COILS

RAFV Ferrite Aerial... Spare Cores 3p  
OC P50/LAC... Driver Trans. LFDT4 50p  
L.F. P50/2CC 470 kc/s... Printed Circuit, PCAL 50p  
I.R.F. P50/3CC... J.B. Tuning Gang... 65p  
PS1/L or PS1/2... Weyrad Booklet... 10p  
PS3/W... OPT... 55p  
Mullard Ferrite Rod 8 x 1/2 in. 20p, 8 x 1/2 in. 25p

## VOLUME CONTROLS

Long spindles, Midget Size 8 K. ohms to 2 Meg. LOG or LIN. LFS 15p, D.F. 25p. STEREO L/S 50p, D.F. 75p. EDGE 6K, S.P. Transistor 25p. Ideal 625 and colour. £10p yd.

WIRE-WOUND 3-WATT POTS. 10 OHMS to 100 K. 40p

VEROBOARD 0-15 MATRIX 2 1/2 x 5 in. 26p, 2 1/2 x 3 1/2 in. 17p, 3 1/2 x 3 1/2 in. 26p, 3 1/2 x 5 in. 30p.

EDGE CONNECTORS 16 way 25p; 24 way 35p. PINS 38 per packet 21p. FACE CUTTERS 35p.

S.B.P. Board 0-15 MATRIX 2 1/2 in. wide 8p per 1 in., 8 1/2 in. wide 4p per 1 in.; 5 in. wide 5p per 1 in. (up to 17 in.).

S.B.P. undrilled 1/4 in. Board 10 x 8 in. 15p.

BLANK ALUMINIUM CHASSIS 18 s.w.g. 2 in. sides, 7 x 4 in. 45p; 9 x 7 in. 80p; 11 x 7 in. 70p; 13 x 7 in. 90p; 14 x 11 in. 95p; 15 x 14 in. 95p; 11 x 3 in. 50p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 6p; 8 x 6 in. 15p; 14 x 8 in. 15p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 28p; 16 x 8 in. 28p; 14 x 9 in. 34p; 12 x 12 in. 40p.

1 1/2 in. DIAMETER WAVE-CHANGE SWITCHES 25p.

2 p. 2-way, or 2 p. 6-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.

1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 60p, 2 water 90p. Extra wafers up to six 80p each.

TOGGLE SWITCHES. sp. 14p; dp. 18p; dp. dt. 23p.

"THE INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER 900/250V. A.C. £2-35 Post 25p. Leadst. S.A.E.

HI-FI STOCKISTS. RETURN OF POST. DESPATCH. MINIMUM POST AND PACKING 15p

## RADIO COMPONENT SPECIALISTS

List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.)

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240V. AC Output voltage available at 6 or 9 or 12 or 15 or 18 or 20V. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST FREE Details S.A.E.

## GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12V or H.T. line 200-300V D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2. Response 25 cps. to 25 Kc/s. 25db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. Guaranteed. Details S.A.E. 90p Post 10p

NEW TUBULAR ELECTROLYTICS CAN TYPES  
2/350V .14p 250/25V .14p 18+16/500V .55p  
4/350V .14p 500/25V .20p 50+50/250V .35p  
8/450V .14p 1000/25V .35p 60+100/350V .58p  
16/450V 1bp 1000/50V .47p 32+32/250V .18p  
32/450V 20p 8+8/450V 18p 32+32/450V .33p  
50/25V 10p 8+8/450V 20p 350+50/325V .80p  
50/50V 10p 16+16/450V 25p 32+32+32/350V 43p  
100/25V 10p 32+32/350V 25p 100+50+50/350V 48p  
SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 16V 10p; 500, 1000mF 12V 18p; 2000mF 25V 42p.  
CERAMIC 1pF to 0.01 mF. 4p. Silver Mica 2 to 5000pF, 4p.  
PAPER 350V-0.1 4p, 0-5 13p; 1mF 15p; 2mF 150V 15p.  
500V-0-001 to 0-05 4p; 0-1 5p; 0-25 8p; 0-47 25p.  
SILVER MICA. Close tolerance. 1, 2, 2-2, 5-001 5p; 500-2-200 pF 10p; 2-200-5-800pF 20p; 6-800pF-0-01, mid 30p; each.  
TWIN GANG. "0-0" 208pF +176pF, 85p. Slow motion drive 365+365 with 25+25pF, 80p 500pF slow motion, standard 45p; small 3-gang 500pF £1.60.

SHORT WAVE, SINGLE. 10pF 30p; 25pF 50p; 50pF 55p.  
CHROMIUM TELESCOPE RESISTORS. 250 Ohm base, 25p, 20p.  
TUNING SOLID dielectric. 100pF 500pF, 35p each.  
TRIMMERS. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 8p; 250pF, 10p; 600pF, 10p; 750pF 10p; 1250pF 10p.  
SILICON REC. 40-LUCAS 2DS500 Bridge 70V 5 amp £1.

RECTIFIERS CONTACT COOLED 1/2 wave 60mA 38p; 65mA 45p. SILICON BY213 30p; BY203 30p; BY127 30p.  
EX-OVERHEAT RESISTORS. 100mA 200mA 20p.  
NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p.

RESISTORS. 1 w., 1/2 w., 20% 1p; 2 w. 5p 10 ohms to 10 meg HIGH STABILITY. 1/2 w. 2% 10 ohms to 1 meg., 10p.  
Ditto 5% Preferred values 10 ohms to 10 meg., 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 8-2 ohms 10p

## SCOOP! METAL PLINTH AND PLASTIC COVER

Cut out ready for Garrard or E.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 1/2 x 14 1/2 in. High including cover. £5-50 Post 25p

## MAINS TRANSFORMERS ALL TOP 25p each

250-0-250 80 mA. 6-3 v. 4 amp. £1-40  
250-0-250 80 mA. 6-3 v. 3-5 a. 6-3 v. 1 a. or 5 v. 2 a. £2-00  
300-0-300 80 mA. 6-3 v. 3-5 a. 6-3 v. 1 a. or 5 v. 2 a. £2-50  
300-0-300 v. 120 mA. 6-3 v. 4 a. G.T. 6-3 v. 2 a. £2-00  
MINIATURE 200 v. 20 mA. 6-3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA. 6-3 v. 2 a. 2 1/2 x 2 1/2 in. 90p  
P.E. AURORA TRANS. 12 + 12v. 500mA £1-50  
MINI-MAINS 200, 100mA. 1 1/2 x 1 1/2 in. 50p  
HEATER TRANS. 6-3v. 3 a. 50p  
Ditto tapped sec. 1-4 v., 2-3, 4, 5, 6-3 v., 11 amp. 80p  
GENERAL PURPOSE 12V. Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2-00  
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2-00  
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3-00  
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. Input/Output. 150w. £2-00 500w. £5. 1000w. £12.  
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 15v. 1 1/2 amp. £1-20; 2 amp. £1-50; 4 amp. £2-00.  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p. All transformers Postage 25p extra.

## E.M.I. 13 1/2 x 8 in. LOUDSPEAKERS

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As Illustrated) Post 15p  
With flared tweeter cone and ceramic magnet, 10 watts. £4  
GENERAL PURPOSE. 12V. Tapped Outputs. Flux 10,000 gauss. £2-25  
State 3 or 8 or 15 ohm. Post 15p  
Recommended Teak Cabinet Size 16 x 10 x 9 in. Post 25p £5

## LOW MINI-MODULE £3-25 LOUSPEAKER KIT

Post 25p  
Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter re-creates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 x 10 x 9 in. Modern design with fluted wood front. Highly recommended. £5 Post 25p

## ALL MODELS "BAKER SPEAKERS" IN STOCK

## BAKER 12in. MAJOR £9



80-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free

Module kit, 80-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

BAKER "BIG-SOUND" SPEAKERS  
'Group 25' 12 inch £7 25 watt 3 or 8 or 15 ohm  
'Group 35' 12 inch £9 35 watt 3 or 8 or 15 ohm  
'Group 50' 15 inch £19 50 watt 8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. dia. speaker 20 x 13 x 9 in. £9. Post 25p For 13 x 8in. speaker 16 x 10 x 9 in. £5. Post 25p For 10 x 6in. speaker 16 x 10 x 6 in. £4. Post 25p LOUSPEAKER CABINET WADDING 18in. wide, 16p ft.

## GOODMANS 6 1/2 ins. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Gamba cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. HI-FI Enclosures Systems, etc. £4

## ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 2 1/2 in. deep. Rating 10 watts, 8 ohm or 15 ohm models. £1-90 Post 10p

Horn Tweeters 2-18ks/s. 10W 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-18 Kc/s. 15W, 8 ohm 43p. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm, 2 1/2 in. dia.; 35 ohm, 2 in.; 8 in 25 ohm, 2 1/2 in. dia.; 3 in. dia.; 8 x 4 in.; 8 x 5 in. £1 EACH 15 ohm, 3 1/2 in. dia.; 7 x 4 in.; 8 x 5 in. TYPE 8 ohm, 6 x 4 in. 3 ohm, 2 1/2 in. 3 in. 5 in. 5 x 3 in. 7 x 4 in. LOUSPEAKERS P.M. 3 OHMS. 6 in. £1, 10 in. £1, 21 in. £2; 8 x 4 in. 90p. £1, 17 1/2 in. x 6 in. £1, 90.

Sin. WOOFER 8 watts max. 20-10,000 cps, 8 or 15 ohm £1-80. ELAC 10in. 10W. De Luxe Ceramic, 8 ohm. £4. RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 8 watt 3 or 8 or 15 ohm models £1.95 each Post 15p.

OUTLET TRANS. EL34 etc. 25p. 6W TRANS. 50d 12-25p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. GOODMANS' OUTPUT TRANSFORMER 5 watt push-pull for valves EL84 etc., 3, 8 and 15 ohms 85p, Post 20p.

BAKER 100 WATT ALL PURPOSE POWER AMPLIFIER. 4 inputs speech and music. £39 POST FREE  
Mixing facilities. Response 10-30,000 cps. Max. output 100 WATT. Tapped Outputs all loudspeakers. A.G. 200/250V. Separate Treble and Bass controls. Guaranteed Details S.A.E.

## ALL EAGLE PRODUCTS

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4  
BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add high fidelity, high level and effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4-25.  
BARGAIN FM TUNER 89-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £10  
BARGAIN FM TUNER as above less cabinet £7-50  
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3-50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p.  
BALANCED TWIN FEEDER 15p. 50 ohm or 300 ohms.  
JACK SOCKET Std. open-circuit-14p. closed circuit 23p; Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p.  
JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p.  
VALVE HOLDERS, 6p; CERAMIC 8p; GANS 5p.

E.M.I. TAPE MOTORS Post 15p. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 185mA. Spindle 0.187 x 0.75 in. £1-25  
Size 3 1/2 x 2 1/2 in. (Illustrated).  
BALFOUR GRAM MOTORS 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1/4 x 3/20. Size 2 1/2 x 2 1/2 in. Post 15p 85p

CUSTOMERS FREE CAR PARK. CALLERS WELCOME  
337 WHITEHORSE ROAD, CROYDON  
Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-3 p.m.)  
Buses 50, 68, 159 pass door. Rail Selhurst Tel. 01-684-1665

# MEMORY STORE

Retrieval By

Dick Railton

**E**LECTRONICS today offers reward in so many different areas of our lives that it is difficult to remember clearly those times when it hardly existed at all, and then only in the form of the mysterious "wireless". Perhaps it became my hobby because of the thrill experienced the first time I heard an identifiable voice in a pair of uncomfortable headphones attached to my very own "crystal set".

The greatest single item then in favour of wireless was that a boy, with the aid of normal workshop tools, a lump of the magic crystal, tuning condenser (now called a capacitor) and headphones, could achieve results equal to the best minds of the century—almost

anyway. Thus the sense of power which could grow from this may well be the key, though I think not.

To me, my hobby went hand-in-hand with Wells, Huxley and Willy Von Braun, long before Peenmunde, Flash Gordon and the slowly growing ranks of Science Fiction writers. Our faith in journeys through space to conquer the Universe could only be supportive of and by our hobby. It may be easy to say, but hindsight has shown the dreams of youth to be true. After all, it is not a question now of "Is there life elsewhere in the Universe?", it is more a case of where and how much.

The war itself gave tremendous impetus to the growing electronics industry and, via the Government surplus stores, the hobby benefited accordingly. Here, in fact, electronics began to emerge as something applicable outside mere wireless. Slowly it produced applications in medi-

cine, industry, the cinema, the theatre and the home. Examples abound.

The most successful valve amplifier ever is undoubtedly the Williamson, designed by the man of the same name—an amateur/professional. The equipment was largely amateur-proved before commercial adoption. The same can be said of the Dinsdale solid-state equipment and the Lindsay-Hood class A equipment. All these are audio equipments and represent only a tiny part of electronics as a hobby. You can't ask much more of any hobby than that it allows you to be amongst the first to do something and that at the same time you enjoy the doing.


The person coming to electronics for the first time nowadays has far more scope in real terms than was available years ago. Thus it seems difficult to me to see how anyone cannot be interested.

## ABBREVIATIONS

The following is a list of abbreviations used in the text of articles and in components lists. Only the direct meaning of the abbreviations is given, no attempt has been made to describe the meaning of the words in full. For further information and full descriptions readers should follow the Teach-In series.

a.c.	alternating current
a.f.	audio frequency
a.f.c.	automatic frequency control
a.g.c.	automatic gain control
a.m.	amplitude modulation
BA	British Association (nut and bolt sizes)
cm	centimetre
d.c.	direct current
d.p.d.t.	double-pole double-throw
elect.	electrolytic
e.h.t.	extra high tension
e.m.f.	electromotive force
f.e.t.	field effect transistor
f.s.d.	full scale deflection
f.m.	frequency modulation
ft.	feet
g.	gram
h.t.	high tension
i.c.	integrated circuit
in.	inch
l.d.r.	light dependent resistor
lin.	linear
log.	logarithmic

l.t.	low tension
m	metre (measurement of length)
mm	millimetre
m.w.	medium wave
npn	transistor structure (two types)
pnp	
oz	ounces (avoirdupois)
p.i.v.	peak inverse voltage
p.v.c.	polyvinyl chloride
r.f.	radio frequency
r.m.s.	root mean square
s.p.s.t.	single-pole single-throw
s.r.b.p.	synthetic resin bonded paper
s.w.g.	standard wire gauge
t.r.f.	tuned radio frequency
u.h.f.	ultra high frequency
u.j.t.	unijunction transistor
v.h.f.	very high frequency
%	per cent
A	ampere (amp)
dB	decibel
F	Farad
H	Henry
Hz	Hertz (cycles per second)
$\Omega$	ohm
V	volt
W	watt
p	pico ( $\div 1,000,000,000,000$ )
$\mu$	micro ( $\div 1,000,000$ )
m	milli ( $\div 1,000$ )
k	kilo ( $\times 1,000$ )
M	Mega ( $\times 1,000,000$ )

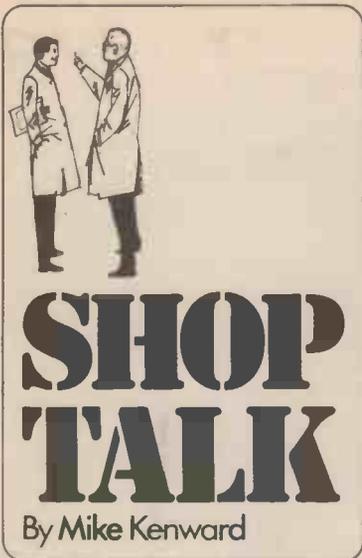

ONE or two readers have made enquiries as to substitute components that can be used in our circuits. There are some points concerning substitutes that will probably be useful: first resistors. In general we use  $\pm 10$  per cent,  $\frac{1}{4}$  watt carbon types;  $\pm 10$  per cent is now a more common tolerance than  $\pm 20$  per cent and this is often the reason for quoting the lower figure. If you wish to use  $\pm 5$  per cent (or better) types by all means do so. A similar point can be made with wattages,  $\frac{1}{4}$  watt types are common but you can use  $\frac{1}{2}$  watt, 1 watt or even larger types provided they will fit on the component board. Never use a lower wattage type than that specified.

### Capacitors

Capacitors are more difficult to lay down rules about, electrolytic types often have tolerances of  $-10$  per cent to  $+100$  per cent or  $-10$  per cent to  $+50$  per cent so you can see that substitution by a similar value to that which we quote should not unduly affect the circuit e.g. for a  $25\mu\text{F}$  capacitor having a  $-10$  per cent to  $+50$  per cent tolerance its value could be anything between  $22.5\mu\text{F}$  and  $37.5\mu\text{F}$  so you could probably use values between  $20\mu\text{F}$  and  $40\mu\text{F}$  without seriously affecting operation of the circuit. Voltage of electrolytics is more important and you should not use types having a lower voltage rating than that given—higher ratings may be used but it is a good idea to stay within four

times the specified voltage e.g. for a 12V electrolytic you could use capacitors having working voltages from 12V to about 50V.

With most other types of capacitor we do not state a tolerance or working voltage and often no specific type. In these cases the general rule is buy the cheapest available and do not worry about working voltage unless we state it. Incidentally condenser is the old term for capacitor—motor mechanics and some “behind the times” firms still use condenser, don’t be put off by it.

### Auto Alert

The G.P.O. type relays used in the *Auto Alert* may be expensive if new ones are purchased, there are plenty of shops selling second hand ones in good condition for about 50p and this could save as much as £2 when buying both. It is important that each relay only has one set of normally closed contacts, if the one you buy has more, undo the mounting screws and remove the unwanted contacts. You must make sure that the coils on the relays are 2000 ohms, there are other values.

If a dash mounted push button is used remember that it must be a push to changeover and release to restore type; there are various types available from the larger suppliers. The micro-switch used with the foot pedal is of a similar operational type—this is standard for most micro-switches so buy a cheap one, the current rating is not important.

### Radio Control Monitor

“Powerless”, pocketable and very useful, the *Radio Control Monitor* is also easy to build. Variable capacitors may vary slightly (sorry about that) but most types will be satisfactory. Any trouble with the tube can be overcome by a good look at all the catalogues you bought.

It is possible to make up the tube with paper and varnish, wrapped around suitable formers but it may be a bit messy.

### Rain Warning Alarm

The loudspeaker used in the *Rain Warning Alarm* is not critical either in size or impedance. The 8 ohm impedance, 2 inch diameter speaker specified could be slightly increased in size and still fit inside the case described. However,

as stated in the text, any small 3 to 15 ohm speaker could be used if these are more easy to obtain. The power rating of this speaker should be between 50mW and 1W.

As stated in the text the Veroboard sensor should be made from 0.1 inch matrix. If you have some 0.15 inch matrix board to hand, this could be used but the sensitivity of the alarm will suffer.

### Waa Waa Pedal

The inductor will probably be the most difficult part to obtain for the *Waa Waa Pedal*. The Ferro-cube pot core is available from some of the larger suppliers and may also be in local shops. If you buy this you will have to take it apart (quite a simple process) and wind the 500 odd turns on the bobbin inside. Although this takes some time it is a simple process. However, we have seen some inductors of about 10 millihenries (8-12 mH will suffice) advertised in the catalogues. These are wound on ferro cores similar to that specified and they are probably cheaper than buying the cube and the wire and winding your own.

Meccano parts for the gears and pedal linkage are available from most toy and model shops.

Cir-Kit, the stick down wiring, that is used on the *Waa Waa* component board is available from most of the component shops. The  $\frac{1}{16}$  inch wide type should be used as this fits between the holes on the perforated board.

### New Products

Very little new products information has found its way into the office this month, in fact the only worthwhile new product for amateurs is a 12V 35W soldering iron shown below with its bayonet fitting metal transit cover.



The iron is fitted with 12ft of lead and 25 amp battery clips to enable easy connection to a car battery. Just the job for soldering in the car projects that we give designs for, such as the *Auto Alert* in this issue. The heat shroud enables the iron to be packed away immediately after use. Manufactured by Solderstat Limited the “Motorist Pack” costs £2.87.

# 28watts, r.m.s. 40Hz to 40kHz $\pm$ 3dB



## Viscount III Audio Suite complete **£49**

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic and ceramic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

### PRICES SYSTEM 1

Viscount III R101 amplifier	£22.00+90p p&p
2 x Duo Type II speakers,	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG.	
cart ridge plinth and cover	£23.00+£1.50
	p&p

Total £59.00

Available complete for only **£52.00+£3.50**  
p&p

### SYSTEM 2

Viscount R101 amplifier	£22.00+90p p&p
2 x Duo Type III speakers	£32.00+£3 p&p
Garrard SP25 Mk. III with MAG.	
cartridge, plinth and cover	£23.00+£1.50
	p&p

Total £77.00

Available complete for **£69+£4** p&p

### SYSTEM 3

Viscount III Amplifier R100	£17.00+90p p&p
2 x Duo Type II speakers, pair	£14.00+£2 p&p
Garrard SP25 Mk. III with CER. diamond	
cartridge, plinth and cover	£21.00+£1.50
	p&p

Total £52.00

Available complete for only **£49.00+£3.50**  
p&p

### SPEAKERS Duo Type II

Size approx 17" x 10 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ ". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts. 3 ohms. Simulated Teak cabinet. £14 pair+£2 p&p.

Duo Type III Size approx 23 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ ". Drive unit 13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair+£3 p&p.

### SPECIFICATION R101

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within  $\pm$  1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities; headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio—65dB. P.U.2. —58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

# R+TV

Radio and TV Components (Acton) Ltd. 21E High Street, Acton, London W3 6NG  
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.  
Goods not despatched outside U.K.

# TECHNICAL TRAINING

## *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns. Certs.
  - Radio Amateurs' Examination
  - General Radiocommunications Certificate.
  - C. & G. Radio Servicing Theory.
  - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics

#### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. CA26, Intertext House, Stewarts Road, London, SW8 4UJ

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).....

NAME..... AGE.....  
(Block Capitals Please)

ADDRESS .....

2/72

Member of the ABCC

Accredited by the CACC

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

# DISCOUNTS UP TO 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG · THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

### SPECIAL OFFER £18

Garrard 5P25 Mk. III  
Goldring G800H  
Teak plinth and tinted cover.  
Ready wired for immediate use.  
Please add £1.25 for post and packing.

Sinclair 2000 Mk. II ... £22.50  
Sinclair 3000 ... £32.50  
Sinclair PRO 60/2+Z30 PZ5 £15.00  
Sinclair PRO 60/2+Z30 PZ6 £17.75  
Sinclair PRO 60/2+Z50 PZ8/Trans. ... £22.95  
Sinclair AFU ... £4.70  
Sinclair 605 (New Product) £20.50  
Goodmans Max. Amp. ... £37.95  
Teleton SAQ206B (New Prod) £17.95  
Wharfedale ... £49.75

### TURNTABLES

Please add 75p for P. & P.  
Garrard 5P25 Mk. III ... £10.25  
Garrard Zero 100—Auto (New Product) ... £40.95  
Garrard Zero 100—Single Play (New Product) ... £37.95  
Garrard 2025TC with Sonotone 9TAMC ... £8.95  
Garrard SL65B ... £13.50  
Garrard AP76 ... £19.95  
Garrard 401 ... £27.00  
BSR MP60 ... £10.00  
Pioneer PL12AC ... £36.00  
Thorens TD125 ... £62.50  
Thorens 150AB11 ... £42.50  
Goldring GL69/2 ... £20.00  
Goldring GL69/P2 ... £26.95  
Goldring GL75 ... £27.95  
Goldring GL75P ... £35.95

Sinclair IC12 integrated circuit amplifier ... £1.85  
Eagle TSA149 7wRMS ... £24.95  
Eagle TSA151 15w RMS ... £34.50

### CARTRIDGES

Please add 10p for P. & P.  
Goldring G850 ... £3.75  
Goldring G800 ... £6.50  
Goldring G800E ... £10.50  
Goldring G800SE ... £15.50  
Sonotone 9TAMC Diamond £1.75  
Shure M3DM ... £4.50  
Shure M445/7/C ... £7.00  
Shure M55E ... £8.75  
Shure M75E ... £12.75  
Shure V15 Type 2 ... £27.75  
Shure M44E ... £7.00  
Shure M31E ... £8.50  
Shure M32E ... £8.00  
Audio Technica AT35 ... £12.95  
Audio-Technica AT66 ... £4.95

### AMPLIFIERS

Please add 50p for P. & P.  
Alpha Highgate FA212 ... £27.50  
Alpha Highgate FA300 ... £29.00  
Alpha Highgate FA400 ... £30.00  
Armstrong 521 (cased) ... £44.95  
Amstrad 8000 Mk. II ... £16.95  
Amstrad IC2000 ... £34.00  
Dulci 207 ... £15.95  
Dulci 207m ... £21.00  
Leak 30 Delta Range (New Product) ... £51.00  
Leak 70 Delta Range (New Product) ... £61.00  
Metrosound ST20E ... £26.00  
Philips R580 ... £18.00  
Pioneer SA500 ... £36.00  
Pioneer SA700 ... £65.00  
Pioneer SA900 ... £92.00  
Rogers R/brook Chassis ... £35.50  
Rogers R/brook Cased ... £39.50  
Rogers R/bourne Chassis ... £44.00  
Rogers R/bourne Cased ... £48.50  
Sansui AU101 ... £32.00  
Sansui 555A ... £59.95  
Sansui AU666 ... £75.00  
Rotel RA301 ... £32.75  
Rotel RA601 ... £49.80

### PLINTHS & COVERS



£3.20

(As illustrated) Plus 35p post and packing. Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard 5P25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for BSR, McDonald MP60 and others.

For AP76; AP75; SL72B; SL75; SL95B. £4 plus 35p P. & P. Also finished in walnut to match Japanese equipment—at no extra charge.

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. E.E.4 174 Pentonville Road, London, N1. Telephone 01-278 1769  
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.  
**MAIL ORDERS:** Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).  
2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

REMEMBER  
TO USE THE  
POSTCODE



# Readers Letters

## Reversed Sentinel

May I take this opportunity to tell you that I look like being an ardent fan of EVERYDAY ELECTRONICS, for a long time to come. Having had, for a long time, the urge to "have a go" at something in the electronics field, but always being beaten due to the lack of knowledge on the subject, I was delighted when your magazine came out. It looked at last as if even I was going to be able to tackle something with some hope of success, and after the clear concise way you are presenting the projects, I had every confidence this would be the case.

But alas, no. I have just completed the *Home Sentinel* and let me say right away—but the wrong way round.

With light falling on the cell face the relay is pulled in, when the light is interrupted, the relay clicks out. Following the instructions in the article, with light on the cell face, I backed off the variable resistor until the relay clicked out, but when the light is cut off to the cell, the relay will not pull in, and no amount of adjustment will make it function as it was intended to. I must say, even in its present state, I am highly delighted to think I have been able to make it, and to have it function at all.

Could you please suggest what could have gone wrong with it. I am afraid that if it will involve the use of test equipment, I will have to be content with it.

A suggestion I would like to make, that I am sure a lot of other readers in the same position as myself will endorse, would be the inclusion in the magazine of a readers "Questions and Answers" section. In this way, someone always asks the question that has been bugging everyone else, and then they all have the answer.

Another suggestion is that once a month is too long to wait for the next issue, please let us have an issue once a week, or at worst, once a fortnight.

If you could spare the time to answer my query, I would be extremely grateful.

D. Hill  
Leeds.

The contacts on your relay are obviously normally open types—the use of normally closed contacts would solve the problem. If the relay you have does not have normally closed contacts then reverse the positions of PCC1 and R1 and all will be well.

Once a month may well be too long for some readers but we often find it too short a period in the editorial offices—one reason why some readers are still waiting for replies to their letters.

## Projects

Congratulations (if not too late) on your new magazine EVERYDAY ELECTRONICS. I never thought this magazine would interest the "whole family" and now we look forward to the next edition to arrive.

My reason for writing is to ask if you intend to print in future editions any projects like intercoms? My three children are always asking me to install an intercom unit in their three bedrooms. Will this be a future project? If not would you be so kind as to advise me where to obtain the necessary diagrams etc.

Peter Pleydell  
Coventry.

I am writing to you on behalf of my colleagues and myself to ask if you have any circuit diagrams concerning high power amplifiers suitable for electric guitars. I would be most grateful if you could send me a circuit diagram for an amplifier of about 100 watts. I have made the *Fuzz Box* you described in issue 2 of EVERYDAY ELECTRONICS. I found it most enjoyable and interesting to make and results were very pleasing.

I think that many people would enjoy making a treasure locator and I suggest that this would be a very interesting constructional project for a future edition.

Philip Crossland,  
Derek White  
Yorkshire.

Unfortunately we cannot supply circuit diagrams or designs other than those published. The 100 watt amplifier is rather too complicated to form an E.E. project. However the other suggestions—the intercom and treasure locator will almost certainly be dealt with in future issues.

## Binders

May I make a suggestion? Offer self binders indexed volume by volume attractively produced and gold titled to grace a modern library shelf to hold your issues as they appear and keep them in good clean reference order.

Price today? Haven't a clue; perhaps £1.25 to £1.50 each, the cheaper the selling price that can be maintained, the better.

L. F. Tearry  
Kent.

*We have already thought of making binders available and when we know what they will look like and how much they will cost, we will publish a notice giving full details—so watch the next few issues.*

## Clear Fuzz

First, congratulations to you and your staff on a first class magazine. I am so pleased with it that I shall soon be placing a subscription order to ensure that I don't miss an issue.

Secondly, with reference to your *Fuzz Box* project; I am a keen follower of any electronic music developments so I decided to build this project for experimentation purposes. I have never used Veroboard before, but I have managed to get the entire circuit onto the piece provided in the No. 1 edition. An even bigger surprise was the fact that it worked first time. In fact this is the first time this has ever happened to a project I have built.

The unit is now in use by a professional pop group, one of who is a friend of mine, and has proved exceptionally reliable even under overload. As suggested I included the bypass footswitch to switch the effect in and out.

I, however, take none of the credit for this as it is due to you for a well laid out, easy-to-understand way of going about the various projects.

C. A. Bradberry  
West Dulwich.

Although you are well satisfied with your *Fuzz Box* some readers have had problems. With the circuit as published there is a danger of damaging transistor TR2. To avoid this a 10 kilohm resistor should be placed between the potentiometer VR1 and the positive line. Also, if a footswitch is fitted, the unit should be made to turn off when the input and output are shorted together.

# YATES ELECTRONICS

(FLITWICK) LTD.

## RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction.  
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4W  
Eric wire wound. 1/4W 2% Electrofil TR5.

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7Ω-2.2MΩ	E24	1-99 100+
1/4	10%	3.3MΩ-10MΩ	E12	1-0p 0-8p
1/4	2%	1Ω-1M	E12	1-0p 0-8p
1/4	5%	4.7Ω-1MΩ	E12	1-0p 0-8p
1/4	10%	1Ω-10Ω	E12	6p 5-5p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/4W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0-1 matrix).  
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 6p each.

## SEMICONDUCTORS

AC126	12p	BFY52	22p	OC81	12p	2N3055	72p
AC127	12p	BSY56	30p	OC82	12p	2N3702	15p
AC128	12p	BSX21	25p	ORP12	48p	2N3703	14p
AD140	40p	BY124	73p	IN4001	73p	2N3704	17p
AF115	20p	BYZ10	20p	IN4002	10p	2N3705	15p
AF117	20p	BYZ13	20p	IN4003	11p	2N3706	12p
BC107	10p	OA85	7p	IN4004	12p	2N3707	18p
BC108	10p	OA91	5p	IN4005	13p	2N3708	10p
BC109	10p	OA202	7p	IN4006	13p	2N3709	11p
BFY50	22p	OC71	12p	IN4007	13p	2N3710	12p
BFY51	22p	OC72	12p	2N2926	11p	2N3711	14p

## ZENER DIODES

400mW 5% 3.3V to 30V, 15p.

## LINEAR IC's (D.I.L.)

709a	50p	741	50p
710a	50p	748	50p

## BRUSHED ALUMINIUM PANELS

12in x 6in=25p; 12in x 2 1/2in=10p; 9in x 2in=7p.

## DEPT. E.E.

ELSTOW STORAGE DEPOT,  
KEMPSTON HARDWICK,  
BEDFORD.

## C.W.O. PLEASE. POST AND PACKING.

PLEASE ADD 10p TO ORDERS UNDER £2.  
Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
5p stamp appreciated.  
10% DISCOUNT TO ALL CALLERS ON SATURDAYS

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0-001μF, 0-0015μF, 0-0022μF, 0-0033μF, 0-0047μF, 2 1/2p, 0-0068μF, 0-01μF, 0-015μF, 0-022μF, 0-033μF, 3p, 0-047μF, 0-068μF, 0-1μF, 4p, 0-15μF, 6p, 0-22μF, 7 1/2p, 0-33μF, 11p, 0-47μF, 13p.  
160V: 0-01μF, 0-015μF, 0-022μF, 0-033μF, 0-047μF, 0-068μF, 3p, 0-1μF 3 1/2p, 0-15μF, 4 1/2p, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 7 1/2p, 0-68μF, 11p, 1-0μF, 13p.  
MULLARD POLYESTER CAPACITORS C260 SERIES  
250V P.C. mounting: 0-01μF, 0-015μF, 0-022μF, 3p, 0-033μF, 0-047μF, 0-068μF, 3 1/2p, 0-1μF, 4p, 0-15μF, 0-22μF, 5p, 0-33μF, 6 1/2p, 0-47μF, 8 1/2p, 0-68μF, 11p, 1-0μF, 13p, 1-5μF, 20p, 2-2μF, 24p.

## MYLAR FILM CAPACITORS 100V

0-001μF, 0-002μF, 0-005μF, 0-01μF, 0-02μF  
2 1/2p, 0-04μF, 0-05μF, 0-068μF, 0-1μF, 3 1/2p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

6p each  
(μF/V) 10/2-5, 40/2-5, 80/2-5, 160/2-5, 320/2-5, 500/2-5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6-4/6-4, 25/6-4, 50/6-4, 100/6-4, 200/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2-5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1-6/25, 6-4/25, 12-5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64, 20/64, 32/64.

## MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6-4, 800/4, 1000/2-5, 9p, 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1600/2-5, 12p, 160/64, 250/40, 400/2-5, 640/16, 2000/4, 1000/10, 1600/6-4, 2500/2-5, 15p, 250/64, 400/40, 640/25, 3200/4, 1000/16, 1600/10, 2500/6-4, 4000/2-5, 18p.

## ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

## VEROBOARD

0-1	0-15
2 1/2 x 3 1/2	22p
2 1/2 x 5	24p
3 1/2 x 3 1/2	24p
3 1/2 x 5	28p
17 x 2 1/2	75p
17 x 3 1/2	100p
17 x 5 (plain)	82p
17 x 3 1/2 (plain)	60p
17 x 2 1/2 (plain)	42p
2 1/2 x 5 (plain)	12p
2 1/2 x 3 1/2 (plain)	11p
Pin insertion tool	52p
Spot face cutter	42p
Pkt. 50 pins	20p

## JACK PLUGS AND SOCKETS

Standard screened	18p	2-5mm insulated	8p
Standard insulated	12p	3-5mm insulated	8p
Stereo screened	35p	3-5mm screened	13p
Standard socket	15p	2-5mm socket	8p
Stereo socket	18p	3-5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable 15p/metre

## BATTERY ELIMINATOR

£1-50  
9V mains power supply. Same size as PP9 battery.

# SPECIAL January Sale Offer

Save £1.00 on the unique

## RADIONIC X30 KIT

if ordered  
before  
Feb 12th  
subject to  
availability



## NO SOLDERING

with the printed circuit board  
Radionic x 30 Kit. The Components  
special in and work straight away.  
Build 33 fascinating experiments:  
Transistor Radios, Burglar Alarm,  
Morse Code Buzzer etc.  
Radionic Kits are safe — they're  
battery operated. Fully illustrated  
110 page Instruction Manual.

Recommended retail price £7.97  
Special Price £6.97  
Plus 20p post & pack

ORDER NOW FROM

# Irwin & Partners Ltd.

294 Purley Way, Croydon CR9 4QL.

## WILSIC SOUND EFFECTS KITS WAH-WAH PEDAL KIT (Illustrated)



Kit comprises a SELECTIVE AMPLIFIER  
MODULE KIT to convert the FOOT  
VOLUME CONTROL PEDAL (as photo)  
to Wah-Wah operation. Amplifier  
module £1-75, pedal unit £5-13, COM-  
PLETE KIT £6-50 add 38p for assembly of  
module, but please note we cannot  
supply kits fully built.

REVERBERATION UNIT KIT. For dimension effect. Connects between  
sound source, mic., etc., and amplifier. Battery powered. COMPLETE  
KIT £9-20 (excluding case £7-50). Assembled in slimline cabinet £12-50.

VIBRATO UNIT KIT. Foot pedal unit with variable speed and depth  
controls. COMPLETE KIT £5-25.

SEND 15p for the WILSIC PLANS BOOK, with full details of these  
kits; circuits, drawings and price lists.

LATEST CATALOGUE 5p (stamps)

WILSIC ELECTRONICS LTD.

6 COPLEY ROAD, DONCASTER, YORKS.

## AMAZING MINI-DRILL



## FOR PRECISION MODEL WORK



Indispensable for precision  
drilling, grinding, polishing,  
etching, gouging, shaping.  
Precision power for the  
enthusiast. Shockproof.  
Completely portable power  
from 4 1/2 volt external battery.  
So much more scope with  
MINI-DRILL. Super Kit (extra  
power, interchangeable  
chuck) £4-50 p.p. 13p.  
De Luxe Professional Kit  
with 17 tools £7 p.p. 23p.

ONLY  
£2  
P & P 10p

+ 6 TOOLS  
Money  
refund  
guarantee

MERLIN SUPPLY CO.

Dept. EE2D, Nailsea, Bristol BS19 2LP

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS

**TYPE SW.100**  
100 x 80 mm.

50μA	20V. D.C.	23-10
50-0-50μA	50V. D.C.	23-10
100μA	300V. D.C.	23-10
100-0-100μA	1 amp. D.C.	23-10
500μA	5 amp. D.C.	23-10
1mA	300V. A.C.	23-10
	VU Meter	23-75

**BAKELITE PANEL METERS**  
TYPE S-80  
80 mm. square fronts

50μA	20V. D.C.	22-60
50-0-50μA	50V. D.C.	22-60
100μA	300V. D.C.	22-60
100-0-100μA	1 amp. D.C.	22-60
500μA	5 amp. D.C.	22-60
1mA	300V. A.C.	22-60
	VU Meter	23-37

## "SEW" CLEAR PLASTIC METERS

**Type MR.85P. 4 1/4 in. x 4 1/4 in. fronts.**

50μA	20V. D.C.	22-80
100μA	50V. D.C.	22-80
500μA	300V. D.C.	22-80
1 amp.	5 amp.	22-80
15 amp.	30 amp.	22-80
20V. D.C.	50V. D.C.	22-80
150V. D.C.	300V. D.C.	22-80
15V. A.C.	300V. A.C.	22-80
300V. A.C.	3 Meter 1mA	22-87
500μA	VU Meter	23-30
500-0-500μA	1 amp. A.C.*	22-80
1mA	5 amp. A.C.*	22-80
1-0-1mA	10 amp. A.C.*	22-80
5mA	20 amp. A.C.*	22-80
10mA	30 amp. A.C.*	22-80

**Type MR.38P. 1 21/32 in. square fronts.**

200μA	20V. D.C.	21-60
300μA	50V. D.C.	21-60
500μA	300V. D.C.	21-60
750μA	1 amp.	21-60
1 amp.	2 amp.	21-60
2 amp.	5 amp.	21-60
10 amp.	3V. D.C.	21-60
10V. D.C.	15V. D.C.	21-60
15V. D.C.	20V. D.C.	21-60
100V. D.C.	100V. D.C.	21-60
150V. D.C.	300V. D.C.	21-60
300V. D.C.	500V. D.C.	21-60
750V. D.C.	15V. A.C.	21-60
15V. A.C.	50V. A.C.	21-60
50V. A.C.	150V. A.C.	21-60
300V. A.C.	500V. A.C.	21-60
500V. A.C.	5 Meter 1mA	21-70
15mA	VU Meter	22-10

**Type MR.52P. 2 1/2 in. square fronts.**

50μA	10V. D.C.	22-00
50-0-50μA	20V. D.C.	22-00
100μA	50V. D.C.	22-00
100-0-100μA	300V. D.C.	22-00
500μA	15V. A.C.	22-10
1mA	300V. A.C.	22-10
5mA	3 Meter 1mA	22-10
10mA	VU Meter	23-20
50mA	1 amp. A.C.*	22-00
100mA	5 amp. A.C.*	22-00
500mA	10 amp. A.C.*	22-00
1 amp.	20 amp. A.C.*	22-00
5 amp.	30 amp. A.C.*	22-00

**Type MR.45P. 2 in. square fronts.**

50μA	5 amp.	21-70
50-0-50μA	10V. D.C.	21-60
100μA	20V. D.C.	21-60
100-0-100μA	50V. D.C.	21-60
200μA	300V. D.C.	21-60
300μA	15V. A.C.	21-80
500-0-500μA	300V. A.C.	21-80
1mA	5 Meter 1mA	21-85
5mA	VU Meter	22-25
10mA	1 amp. A.C.*	21-70
50mA	5 amp. A.C.*	21-70
100mA	10 amp. A.C.*	21-70
500mA	20 amp. A.C.*	21-70
1 amp.	30 amp. A.C.*	21-70

## "SEW" BAKELITE PANEL METERS

**Type MR.65P. 3 1/4 in. x 3 1/4 in. fronts.**

50μA	10V. D.C.	22-20
50-0-50μA	20V. D.C.	22-20
100μA	50V. D.C.	22-20
100-0-100μA	300V. D.C.	22-20
200μA	15V. A.C.	22-30
500μA	300V. A.C.	22-30
500-0-500μA	3 Meter 1mA	22-37
1mA	VU Meter	23-37
5mA	50mA A.C.*	22-20
1 amp.	100mA A.C.*	22-20
5 amp.	200mA A.C.*	22-20
10 amp.	1 amp. A.C.*	22-20
15 amp.	1 amp. A.C.*	22-20
20 amp.	5 amp. A.C.*	22-20
30 amp.	10 amp. A.C.*	22-20
50 amp.	20 amp. A.C.*	22-20
5V. D.C.	30 amp. A.C.*	22-20

**Type MR.65. 3 1/4 in. square fronts.**

500μA	25μA	23-50
1 amp.	50μA	22-75
5 amp.	50-0-50μA	22-35
15 amp.	100μA	22-35
30 amp.	100-0-100μA	22-25
50 amp.	500μA	22-20
5V. D.C.	1mA	21-90
10V. D.C.	1-0-1mA	21-90
20V. D.C.	5mA	21-90
50V. D.C.	10mA	21-90
150V. D.C.	50mA	21-90
300V. D.C.	100mA	21-90
30V. A.C.*		21-95
50V. A.C.*		21-95
150V. A.C.*		21-95
300V. A.C.*		21-95
500mA A.C.*		21-95
1 amp. A.C.*		21-95
5 amp. A.C.*		21-95
10 amp. A.C.*		21-95
20 amp. A.C.*		21-95
30 amp. A.C.*		21-95
50 amp. A.C.*		21-95
VU Meter		23-10

**\*MOVING IRON— ALL OTHERS MOVING COIL**  
Please add postage

## SEW EDUCATIONAL METERS

**Type ED.107. Size overall 100mm x 90mm x 108mm.**  
A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to demonstrate internal working. Available in the following ranges:

50μA	20V. D.C.	24-40
100μA	50V. d.c.	24-40
1mA	300V. d.c.	24-40
50-0-50μA		24-45
1-0-1mA	Dual range	24-40
1A d.c.	500mA/5A d.c.	24-65
15A d.c.	5V/50V d.c.	24-65
10V d.c.		24-40

**EDGWISE METERS**  
Type PE.70. 3 17/32 in x 1 15/32 in. x 2 1/4 in. deep

50μA	20V. D.C.	23-10
50-0-50μA	50V. D.C.	23-00
100μA	300V. D.C.	23-00
100-0-100μA	1 amp. D.C.	22-90
500μA	5 amp. D.C.	22-75
1mA	300V. A.C.	22-45
5mA	20 amp. A.C.	22-45
10mA	30 amp. A.C.	22-45
50mA	50 amp. A.C.	22-45
100mA	VU Meter	23-40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

# MULTIMETERS for EVERY purpose!

## ROUND SCALE TYPE PENCIL TESTER MODEL TS-68

Completely portable, simple to use pocket sized tester. Ranges: 0/3/30/300V AC and DC at 2,000 ohms. Resistance 0-20K ohms. ONLY £1-97 P. & P. 13p.

**MODEL TE-90** 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 v. D.C. 0/3/30/120/300/1,200 v. A.C. 0/3/6/30/60/300MA. D.C. 16K/160K/1.6/16 MEGΩ. -20 to +63 db. £7-60. P. & P. 15p.

**SKYWOOD SW-500** 50KΩ/Volt. Mirror scale. DC Volts 0/3/12/30/300/600. DC Current 20uA/6/600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +57 db. £7-50. P. & P. 15p.

**270 WTR MULTI-METER**  
Features A.C. current ranges. 20,000 o.p.v. 0/3/2-5/10/50/250/500 1000 V D.C. 0/2-5/10/50/250/500/1000 V AC. 0/50uA/1/10/100MA/1/10 1000 V AC. 0/100MA/1/10 100 Amp AC 0/5K/50K/500K/5MEGΩ. 50MEGΩ. -20 + 62 db. £15, P. & P. 25p.

**FTC-401 TRANSISTOR TESTER**  
Full capabilities for measuring A, B and ICs. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £8-97. P. & P. 15p.

**AG75 AUDIO GENERATOR**  
Portable, mains operated. Sine wave 20 to 200,000 Hz. Square wave 20 to 30,000 Hz. Output voltage Sine 17V P/P. Square 21V P/P. Distortion less than 1%. £17-50, P. & P. 37p.

**TE-200 RF SIGNAL GENERATOR**  
Accurate wide range signal generator covering 120 Kcs-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 37p. Size 140 x 215 x 170 mm.

**BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR**  
New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price £27-50. Carr. 25p.

**240° Wide Angle 1mA Meters**  
MW1-6 60mm square £3-97  
MW1-8 80mm square £4-97  
P. & P. extra

**TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE**

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. L. 1 μH to 111 μH. C. 10 pF to 110 nF. 6 Ranges ±2%. TURN'S RATIO 1:1/1000. 1:11000. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100uA. Meter indication. Attractive 2 tone metal case. Size 7 1/4" x 5" x 2 1/2". £20. P. & P. 35p

**UM.049 MULTIMETER**  
20,000 O.P.V. overload protection. 0/3/30/60/300/600/3000 V DC. 0/6/30/120/600/1200 V AC. 0/60uA/12/300 MA. D.C. 0/60K/6MEGΩ. -20 + 63 db. £4-50, P. & P. 15p.

**Model S-100TR MULTI-METER TRANSISTOR TESTER** 100,000 o.p.v. MIRROR SCALE OVERLOAD PROTECTION 0/12-1-8/3/12/30/120/600 V DC. 0/6/30/120/600 V AC. 0/12/600uA/12/300MA/12 Amp. DC. 0/10K/1 MEG/100 MEG. -20 to + 50 db. 0-01 - 2 mid. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £13-50, P. & P. 25p.

**TMK MODEL TW-50K 46** ranges, mirror scale, 50KΩ/Volt. D.C. 5K Volt A.C. D.C.: Volts 125, 25, 12, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50uA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEGΩ, 10 MEGΩ. Decibels -20 to +81.5 dB. £8-50. P. & P. 17p.

**HT100B4 MULTI-METER**  
Features A.C. current ranges. 100,000 o.p.v. Mirror scale. Overload protection. 0/3/2-5/10/50/250/500/1000 V DC. 0/2-5/10/50/250/1000 V AC. 0/10/250uA/2-5/25/250 MA/10 Amp DC. 0/100 Amp AC. 0/20K/200K/2MEG/20 MEGΩ. -20 + 62 db. £12-50, P. & P. 25p.

**RUSSIAN 22 RANGE MULTIMETER**  
Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 0/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V AC. DC Current 10 uA/1/10/100mA/1A. Resistance 500 ohms/3/30/300K/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £6-97 P. & P. 25p.

**TO-3 PORTABLE OSCILLOSCOPE**  
3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 megΩ 25pF. X amp. sensitivity 0.9v p-p/CM. Bandwidth 1.5 cps-800KHz. Input Imp. 2 megΩ 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lbs. 220/240V. A.C. Supplied brand new with handbook. £37-50. Carr. 50p

**HONEYWELL DIGITAL VOLTMETER VT.100**  
Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100v. D.C. Input: Fully floating (3 poles). Input power: 10-230v. A.C. 50/60 cycles. Overall size: 5 1/2 in. x 2 1/3 1/16 in. x 8 3/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. £49-97. Carr. 50p.

**G. W. SMITH & CO (RADIO) LTD.**  
Also see next two pages

# SEMICONDUCTOR VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	2N4548	35P	BC114	15P	BFW90	22P	NKT219	30P
2N3415	22P	2N4548	35P	BC114	15P	BFW90	22P	NKT219	30P
2N3416	27P	2N4549	40P	BC115	15P	BFW91	22P	NKT223	27P
2N3417	37P	2N4550	50P	BC116	15P	BFW92	22P	NKT224	27P
2N3418	130P	2N4551	25P	BC117	15P	BFW93	22P	NKT225	27P
2N3419	87P	2N4552	25P	BC118	15P	BFW94	22P	NKT226	27P
2N3420	17P	2N4553	25P	BC119	30P	BFX20	25P	NKT227	30P
2N3421	17P	2N4554	25P	BC120	30P	BFX21	25P	NKT228	30P
2N3422	17P	2N4555	25P	BC121	30P	BFX22	25P	NKT229	30P
2N3499	17P	2N4632	25P	BC198	30P	BFX99	25P	NKT306	30P
2N3500	17P	2N4633	25P	BC199	30P	BFX00	25P	NKT307	30P

Integrated Circuits	FH111	25P	SN7430	20P	VALVES	0A2	88P	2574	30P	EL95	85P
CA3000	180P	FH111	25P	SN7430	20P	0A2	88P	2574	30P	EL95	85P
CA3001	177P	FH111	25P	SN7440	20P	0B2	45P	2525	40P	EM90	45P
CA3002	262P	FH111	25P	SN7441A	20P	0C4	30P	2526	65P	EM81	60P
CA3011	75P	FH111	25P	SN7442	75P	0L4	20P	30C18	80P	EM84	35P
CA3012	88P	FH111	25P	SN7443	135P	1B5	40P	30C17	90P	EM86	11.00P
CA3013	105P	FH111	25P	SN7444	135P	1C4	80P	30C18	80P	EM87	70P
CA3018	84P	FH111	25P	SN7445	20P	1T4	25P	30P19	85P	EM88	40P
CA3018A	110P	FH111	25P	SN7446	20P	1U5	80P	30P12	120P	EM89	40P
CA3020	184P	FH111	25P	SN7447	20P	2D21	35P	30P14	95P	EZ40	65P
CA3020A	160P	FH111	25P	SN7448	20P	3Q4	60P	30L15	85P	EZ41	60P
CA3021	156P	FH111	25P	SN7449	20P	3R4	35P	30L17	80P	EZ20	27P
CA3022	130P	FH111	25P	SN7450	20P	3V4	48P	30P12	80P	EZ21	27P
CA3023	126P	FH111	25P	SN7451	20P	4A4	75P	30P19	85P	GZ31	45P
CA3028	105P	FH111	25P	SN7452	20P	5U4	35P	30P17	75P	GZ34	40P
CA3029	87P	FH111	25P	SN7453	20P	5V4	45P	30P13	93P	KT66	22.00P
CA3029A	102P	FH111	25P	SN7454	20P	6Y3	40P	30P14	90P	KT78	22.00P
CA3030	187P	L904	40P	SN7455	20P	6Z4G	40P	35L6	50P	MU14	75P
CA3036	78P	MC724P	60P	SN7456	20P	6AQ5	38P	807	50P	PC38	80P
CA3039	82P	MC780P	247P	SN7457	20P	6AT6	35P	8763	70P	PC189	85P
CA3041	109P	MC788P	146P	SN7458	20P	6AU6	25P	9146	180P	PCF80	80P
CA3042	109P	MC790P	124P	SN7459	20P	6AV6	30P	AZ31	55P	PCF82	84P
CA3043	137P	MC792P	88P	SN7460	20P	6BA6	25P	CV31	35P	PCF84	60P
CA3044	120P	MC795P	88P	SN7461	20P	6BE6	30P	D4P91	30P	PCF86	80P
CA3045</											

# HI-FI EQUIPMENT

SAVE UP TO  
**33 1/3% OR MORE**  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!



## RECORD DECKS

- B.S.R.**  
Mini Mono† £4.97  
CL29† £8.70  
MP60 £10.75  
610 £14.65  
611 £13.65  
612 £9.85  
613 £13.45  
614 £14.45  
615 £13.45  
616 £14.45  
617 £13.45  
618 £14.45  
619 £13.45  
620 £14.45  
621 £13.45  
622 £14.45  
623 £13.45  
624 £14.45  
625 £13.45  
626 £14.45  
627 £13.45  
628 £14.45  
629 £13.45  
630 £14.45  
631 £13.45  
632 £14.45  
633 £13.45  
634 £14.45  
635 £13.45  
636 £14.45  
637 £13.45  
638 £14.45  
639 £13.45  
640 £14.45  
641 £13.45  
642 £14.45  
643 £13.45  
644 £14.45  
645 £13.45  
646 £14.45  
647 £13.45  
648 £14.45  
649 £13.45  
650 £14.45



- GARRARD**  
2025 T/C\* £25.50  
3600\* £9.75  
SP25 III £10.50  
SL63 £13.45  
AP76 £18.90  
SL72B £22.95  
SL75B £22.50  
SL90B £32.95  
401 £27.45  
ZERO 100A £44.97  
ZERO 100S £41.97  
GOLDRING  
GL69/2 £18.97  
GL72 £23.25  
GL75 £23.25  
GL76 £29.97  
GL79 £38.50  
LID 72 £23.75  
LID 75 £3.95  
G99 £19.95  
PIONEER  
PL12AC £36.50

- THORENS**  
TD125 £59.65  
TD125AB £94.25  
TX25 £6.70  
TD150AII £34.50  
TD150ABII £40.25  
TX11 £3.77

† Mono \* Stereo Cartridge  
All other models less Cartridge  
Carriage 50p extra any model.

## RECORD DECK PACKAGES

- Decks supplied ready wired in plinth and cover fitted with cartridge.  
Garrard  
2025 T/C with Sonotone 9TAHCD £13.95  
Garrard SP25 Sonotone 9TAHCD £15.95  
Garrard SP25III Goldring G800 £18.95  
Garrard AP76 Goldring G800 £29.95  
Garrard SP25III/Shure M75-6 £19.95  
Garrard AP76/Shure M75-6 £30.95  
BBS MP60 Audio Technica AT35 £21.50  
Goldring GL69/2 Goldring G800 £37.50  
Goldring GL75 Goldring G800 £42.50  
Goldring GL75 Goldring G800E £46.55  
Carriage 50p extra any model.



## ★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER 812E ONLY 6" x 4" x 2 1/2" 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 85-108Mc/s. Ready built ready for use. Fantastic value for money. £6.37. P. & P. 124p. Stereo multiplex adaptors £4.97.

## SINCLAIR EQUIPMENT

Project 60. Package offers.  
  
2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. £16.75 Carr. 37p. Or with PZ6 power supply £18.85 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. £20.25 Carr. 37p.  
Transformer for PZ8. £2.97 extra.  
Add to any of the above £4.87 for active filter unit and £13.90 for pair of Q16 speakers.  
Project 60 FM Tuner £20.25 Carr. 37p. All other Sinclair products in stock  
3000 Amp £23.75 Carr. 37p. 3000 Amp £31.50 Carr. 37p. Neoteric Amp £43.95 Carr. 37p. IC10/IC12 £2.50  
NEW PROJECT 605 - £20.97 Carr. 37p.

## LATEST CATALOGUE

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS

VALUE 50p  
272 pages, fully illustrated and detailing thousands of bargains.

SEND NOW  
**ONLY 37 1/2 p**  
P & P  
10p

## TELETON SAQ-206 STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag, xtal, aux tape. Volume, bass, treble, sliding bandpass, scratch filter and loudness controls. List £22.50 OUR PRICE £18.50 Carr. 37p.



**GRIT AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR OF SPEAKER SYSTEMS.** Output 4 watts per channel. Excellent reception. AFC, built-in MPX. Car/XTAL Input. Total List £50.25. OUR PRICE £22.75. Carr. 62p.  
Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired £38.50. Carr. £1.00.

## LAFAYETTE LA. 324 STEREO AMPLIFIER

12.5 + 12.5 watt B.M.S. Mag/Car/Tuner/Tape Inputs. Excellent performance. Compares with amplifiers up to £40.  
OUR PRICE £24. Carr. 37p.

## TAPE CASSETTES

Top quality in plastic library boxes.  
C90 60 min 37p. 3 for £1.05  
C60 90 min 50p. 3 for £1.65  
C120 120 min 67p. 3 for £1.80  
Cassette Head Cleaner 55p. Post Extra

## TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 01/003/1/3/1/3/10/30/100/300V. B.M.S. 4cpa.-1.2 Mc/s. Decibels -40 to +40dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.50. Carr. 25p.

## TMK MODEL 117 P.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 26 ranges with leads. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3 - 1200V. AC VOLTS 3 - 300V RMS. 8 - 900V P.P. DC CURRENT 10 - 125mA.  
Resistance up to 2000M ohms. Decibels -20 to +61 db Complete with leads/instructions. £17.50, P. & P. 20p.

## 230 VOLT A.C. 50 CYCLES RELAYS

Brand new, 3 sets of changeover contacts 44 5 amp rating. 50p each. P. & P. 10p (100 lots £40). Quantities available.

## PRS-2 PHOTO ELECTRIC RELAY SYSTEM

Inexpensive warning or counting system consisting of an inverter and relay unit. Relay unit has variable sensitivity control and switch for intermittent alarm operation. Exciter unit has removable infra red filter and A.C. outlet socket to operate bells, counters, etc. 240V A.C. Complete with cables and instructions. £9.97 P. & P. 25p.

## HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.  
2 Station £2.97, P. & P. 15p.  
3 Station £5.25, P. & P. 15p.  
4 Station £8.62, P. & P. 17p.

## EMT LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7.50 each. P. & P. 37p.  
Model 450. 13" x 8" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3.50 each. P. & P. 25p.

## TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive, soft 240V AC. Operates on adjustable headband. Magnetic, impedance 2,600 ohms.  
£1.97, P. & P. 15p.

## MP7 MIXER PREAMPLIFIER

5 microphone inputs, 13" x 5" with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Input Mics: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.  
£5.97, P. & P. 20p.

## HOSIDEN DH-025 STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY £2.97. P. & P. 124p.

## 1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphones switching. 2 gain headphones sockets. 6" x 4" x 2 1/2". P. & P. 15p.

## SH628 STEREO HEADSET

Outstanding value. Soft earpads adjustable headband. 8-16 ohms. 20-20,000Hz. Complete with cable and stereo jack plug. £1.87. P. & P. 15p.

## U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/3/1.5/7.5/30/60/150/300/600/900 VDC and 75mV. 0/3/1.5/7.5/30/60/150/300/600/900VAC. 0/800uA/1.5/6/80/60/150/600MA/1.5/6 AMP. D.C. 0/1.5/6/15/60/150/600MA/1.5/6 AMP. A.C. 0/200 Ω/3K/30K Ω. Accuracy DC 1%, AC 1-5%. Knife, edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9.50 plus P. & P. 25p.

## RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage. Input 220/240V A.C. Size 185 x 85 x 105mm. £8.97. P. & P. 25p.



## UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s-30mc/s. FET. 8 Meter, Variable BFO for SSB, Built-in Speaker, Bandspread, Sensitivity Control. 220/240V. A.C. or 12V. D.C. 128" x 48" x 7". Brand new with instructions. £25. Carr. 37p.

## LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8. Meter, Bandspread, B.F. Gain. 18" x 9 1/2" x 8 1/2". 220/240V. A.C. or 12V. D.C. Brand new with instructions. £45. Carr. 50p.

## TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for every day use. 7 amp. Bandwidth 2CF8-1 MHz. Input imp. 2 meg Ω 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. £22.50. Carr. 50p.



## TE-16A Transistorised Signal Generator

4000Hz-30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800Hz modulation. 5 1/2" x 5 1/2" x 3 1/2". Complete with instructions and leads. £7.97. P. & P. 20p.

## RUSSIAN Q1-16 DOUBLE BEAM OSCILLOSCOPE

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 3 sec to 100 mill sec/cm. Complete with accessories and instructions £27. Carr. paid.

# POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. 1/2 in. dia. shafts. Bulk quantities available.  
25 WATT 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 72p. P. & P. 7p.  
50 WATT 10/15/25/50/100/250/500/1000/2500 or 5000 ohms. 21.05 P. & P. 7p.  
100 WATT 1/6/15/25/50/100/250/500/1000 or 2500 ohms. £1.37 P. & P. 7p.

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality . Low price . Immediate delivery  
8-280 General Purpose Bench Mounting  
1 Amp £7.00  
2.5 Amp £7.95  
5 Amp £11.75  
8 Amp £15.90  
10 Amp £22.50  
12 Amp £23.80  
20 Amp £49.00  
8-280B Panel Mounting  
1 Amp £7.00  
2.5 Amp £8.05  
Please add postage  
ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS.  
Special discounts for quantity

# G.W. SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0377  
OPEN 9-6 MONDAY TO SATURDAY

# Everyday Electronics Classified Advertisements

RATES: 7p per word (minimum 12 words). Box No. 7p. extra. Semi-display—£4.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

## RECEIVERS and COMPONENTS

### NEW GUARANTEED DEVICES ORDER WITH CONFIDENCE

#### MICROCIRCUITS:

SN76013 (like IC12) £1.50; 709 35p; 741 36p; PA230 90p; PA234 84p; PA237 £1.50; SL702C 40p.

#### TRANSISTORS:

2N2926 Grn 8p; 2N3055 50p; BC107B 9p; BC108C 9p; BC109C 9p; BFX86 15p;

#### 1 AMP RECTIFIERS:

50V 5p; 100V 4p 200V 5p; 400V 6p.

BRIDGES: 50V 30p; 100V 31p; 400V 35p.

#### PRINTED CIRCUIT RESIST PEN: 80p.

Discounts begin at 10 off.

#### JEF ELECTRONICS (E.E.2)

York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ. Mail order only. C.W.O. P & P 2p per order. Overseas 65p.

Money back if not satisfied.  
List free on application.

#### DO-IT-YOURSELF ... we stock a large range

of audio and electronic components at very competitive prices, e.g.: Chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale & Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for FREE list. (2 x 3p stamps for fabric samples.) Mail-order ONLY. No callers please.

### AUDIOSCAN

Dept. EE272

4, PRINCES SQUARE,  
HARROGATE, YORKS.

**POLYSTYRENE CAPACITORS** 125v Values from 160pf to 0.015 (No 4700pf) 16p dozen, post 5p. IC's ON PANELS 7400 Series at least 10—75p, post 10p with details. **COMPUTER PANELS**, 5-BC108, DIODES 15p, post 9p, 4—80p, post 10p. **AMERICAN PANELS** total at least 30 transistors, first grade components, details provided 3—55p, post 10p. **PANELS** with 10 x B8X26, 500 Meg Silicon PNP 35p, post 5p. **MIXED PANELS** 8 for £1, post 15p, no midge panels, plenty of components, at least 60 transistors. **FERRITE ROD** 7 x 1/2 12p, post 8p each, 27p for 6. **LAZ POT CORES** ex equipment, 20p post paid. **ORP12** on panel ex equip. 35p post paid. **COPPER CLAD PAXOLIN** single sided 13 x 1 1/4, 30p, post 8p each. **COMPUTER RELAYS** DEDT 700 ohm coil, weigh 1/2 oz. also weigh 1 oz, carry 2 amp and 5000 ohm coil weigh 1 1/2oz carry 2 amp. 55p post paid. **Large relay** 7000hm weighs 1 1/2 oz. 35p post paid. **SMALL SYNCHRONOUS MOTOR** with gear train 200-250v 30p post paid. **ELECTROLYTICS** 5,000mf 25v 40p post paid.

**ASSORTED PANELS WITH RES. CAPS, DIODES, INDUCTORS.**

3 lb. 76p post paid.

### J.W.B. RADIO

75 HATFIELD ROAD, SALFORD 6, LANCs.

MAIL ORDER ONLY

## SERVICE SHEETS

**SERVICE SHEETS (1925-1971)** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

## HOLIDAYS

**HOLIDAY FOR BOYS**, 14/16 years, Summer 1972. Tuition and practical work in electronics (and tape recording), engineering (Karting), photography, 11 days in Norfolk—£16. Write for free brochure: Inter-School Christian Fellowship, c/o 1 Hubbard Road, London SE27 9PJ.

## PRINTED CIRCUITS

**MAKE YOUR OWN** printed circuits. Industry use etched printed-circuits boards because they are the cheapest and most flexible method of mounting components. Now you can make your own. Send £1.20 for your kit today (FREE two circuit diagrams for experimenting) to **SPECIALIST ELECTRONICS**, P.O. Box 39, 2 Woodland Avenue, Brentwood, Essex.

## EDUCATIONAL

**TECHNICAL TRAINING** in Radio, TV & Electronics through world-famous ICS. For details of proven home-study courses write: ICS (Dept. 566), Intertext House, London, SW8 4UJ. Accredited by the CACC.

**ENGINEERS**—get a technical certificate. Exam and Certificate Postal Courses in all branches of Engineering, Electronics, Radio & TV, Computers, Draughts., Building, etc. Write for helpful **FREE BOOK: B.I.E.T.** (Dept. H.23), Aldermaston Court, Reading RG7 4PF.

## MISCELLANEOUS

**UNIMIXER 4S** mono/stereo mixing unit £45. Recent reviews, specs, from manufacturers; Soundex Ltd., 18 Blenheim Road, London, W4 1ES.

**RECORD TV SOUND** using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p + 10p P&P. **CROWBOROUGH ELECTRONICS (E.E.)**, Eridge Road, Crowborough, Sussex.

## 12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other lights or 12V Equipment.

Unbeatable at **£3-30** post paid

or in kit form **£2-90**

Easy to construct

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire Large S.A.E. for lists

## CHROMASONIC electronics

### 1972 CATALOGUE

10p post free

56 FORTIS GREEN ROAD, LONDON N10 3HN

**FASCIA PANELS, DIALS, NAME-PLATES** etc. (single or multiples) in etched aluminium to individual specification. Hardware supplies for constructors, s.a.e. details and list.

R. A. Marsh,  
29 Shelbourne Road,  
Stratford on Avon, Warwks.

## FREE Nippiboard type 1A

when you buy **SL403D** I.C. amp still only £1-99 plus 9p post & packing  
TWO SL403D £3-90 (p&P 10p) and 3free ICAs.  
IC used in **EE Record Player**

## use nippiboard

PRINTED WIRING BOARD  
for transistor circuits in E.E., P.E. and P.W. eg  
E.E. Home Sentinel-srbp type 1A 15p  
E.E. Windscreen Wiper Control-fibreglass type1B 16p  
E.E. Fuzz Box - srbp type 1A 15p  
E.E. ASTRON medium wave receiver-srbp1A 15p

## NIP ELECTRONICS

Dept. NB/EE, P.O. Box 11, St Albans, Herts.

## PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

**MAKE YOUR OWN PANELS** IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN. **TRIAL KIT** (36 sq. in.) ... £1-28 carr. pd.  
No. 1. KIT (54 sq. in.) ... £1-88 carr. pd.  
No. 2. KIT (72 sq. in.) ... £2-39 carr. pd.  
MPE Ltd., Dpt. D.E. Bridge St. Clay Cross, Derby

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually **SECRET** since they won't be heard by conventional means. Actually it's **TWO KITS IN ONE** because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project **REALLY FUN-TO-BUILD** with the **EASY-TO-FOLLOW** instructions. An extremely flexible design with quite an **AMAZING RANGE**—has obvious applications for **SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS**, etc.

GET YOURS! SEND £5-20 NOW

TO: **BOFFIN PROJECTS'**  
DEPT. KEE.

4 CUNLIFF ROAD,  
STONELEIGH, EWELL, SURREY

## JOHN SAYS...

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable FI/F2 rejection. Module £7. Unit £8-90. **WAA-WAA** Pedal kit of all parts, incl. all mechanics & instr. Only £2-95. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrot etc. costs £18-00 in modules. **SYNTHESIZER MODULES** and other miracles. Send 15p for illust. list.  
D.E.W. Ltd., 254 Ringwood Road, Farndon, Dorset.

**INDISPENSABLE GUIDE** for Hi-Fi equipment; buy Audio Supply's new 100 page photographically illustrated catalogue (60p). Fair cash terms and service. Our associates' manufacture records from customers' tapes. Specify requirements to Sound News, 18 Blenheim Road, London, W4 1ES.

The components you want for EE designs plus good service, prompt delivery & attractive discounts

# ELECTROVALUE

## Electronic Component Specialists


### THIS MONTH'S SELECTION OF POPULAR ITEMS FROM THE ELECTROVALUE CATALOGUE

#### TRANSISTORS

No.	Type	Purpose	Price
2N697	sil. NPN	General	18p
2N1304	Ger. NPN	"	28p
2N1305	PNP	"	28p
2N2646	sil. UJT	Oscillator, SCR driver	47p
2N2924	NPN	Small sig. amp	11p
2N3055	NPN	High power	60p
2N3702	PNP	Low power	15p
2N3704	NPN	Low power	18p
AC126	Ger. PNP	Small sig./driver	20p
AC128	PNP	Low power	20p
AD148	PNP	High power	58p
AD176	NPN	Low power	16p
AD181	NPN	Med. power	35p
AD182	PNP	Med. power	38p
BC108	sil. NPN	Small signal	11p
BC109	NPN	Low noise	12p
BC168	NPN	Small signal	10p
BC169	NPN	Low noise	11p
BF194	NPN	RF amp.	14p
BFY51	NPN	Med. current	20p
OA90	Ger. diode	RF detector	6p
OA91	"	General	5p
SD1	"	Silicon Rectifier 1 amp	10p
W02	"	Silicon bridge 1 amp	40p

(Sil.=Silicon. Ger.=Germanium)

#### CAPACITORS

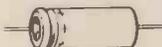Non-polarised		Electrolytic	
			
Polystyrene		1nF 40V	6p
		5mF 64V	6p
		10mF 64V	6p
		20mF 64V	6p
		25mF 25V	6p
10pF	3p	50mF 25V	6p
22pF	3p	80mF 25V	6p
100pF	3p	100mF 25V	7p
220pF	3p	220mF 25V	10p
470pF	3p	470mF 25V	12p
1000pF	3p	1000mF 25V	20p
2200pF	3p	2000mF 25V	30p
4700pF	4p	5000mF 25V	82p
Polyester M K T		Many other higher and lower ratings will be found in the catalogue.	
0-01mF	5p	Close tolerance and high stability types also.	
0-02mF	5p		
0-047mF	6p		
0-1mF	8p		
0-22mF	6p		
0-47mF	10p		
1mF	14p		

#### RESISTORS

½ watt and ¼ watt, all at 1p each in the following values (in ohms): —  
10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and all values in this series up to 10 Megohms.

#### Power Resistors

3 watts—7p each: 7 watts—9p each.

Values as for ½ watt series, but up to 10 Kohms only.

Many other types and values available. Full details in catalogue.

#### VEROBOARD

The universal circuit building board

Unclad, 0-1" matrix

2" x 3-75" 10p

2-5" x 3-75" 15p

5" x 3-75" 25p



Copperclad Veroboard also in stock in all standard sizes and matrices; also edge connectors, pins, etc.

#### PEAK SOUND ENGLEFIELD 840

Brilliantly designed hi-fi amplifier with facility to take add-in stereo FM tuner. Super performance. 20+20 watts RMS into 8 ohm speakers. As advertised £49-50. Brand new, and guaranteed in maker's carton

£33-50

(+75p carr in U.K.)

#### VOLUME CONTROLS, ETC.

Very wide ranges carried including the following popular types: —

4-7Kohms, 10Kohms, 22 Kohms, 47, 100, 220, 470 Kohms; 1 Megohm, 2-2 Megohms.



Log or linear tracking

MONO 12p each; STEREO (matched tracks) 42p

Any type with double pole mains switch—12p extra

STEREO BALANCE CONTROLS  
Log/Antilog, 10K, 47K, 1M  
Dual antilog 10K only.

#### MAIN LINE AMPLIFIERS

70 watt power amplifier in module form ready to build into any system. With full instructions.

Amplifier module ... net £12-60

Power supply kit ... net £6-00

Matching pre-amplifier kit (for magnetic or ceramic pick-up) ... net £3-30

Note—All the above prices are for mono.

FOR STEREO for building into your own cabinet. Two amplifier modules and pre-amp kits are required with matched controls plus one power supply kit, net price £38-40

#### MISCELLANEOUS ITEMS

##### INDICATOR LAMPS

NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C 24p. Neon, square red type LSSC/P, 18p; amber type LSSC/A, 18p; clear type LSSC/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0-04A square red type LSSC/R-6V, 30p, 6V 0-04A amber type LSSC/A-6V, 30p; 6V 0-04A clear type LSSC/C-6V, 30p; 6V 0-04A green type LSSC/G-6V, 30p; 12V 0-04A LSSC/R-12V, 34p; 34V 0-04A LSSC/R-28V, 45p.

CÖLVERN 3 watt Wire-wound Potentiometers. 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1K, 1-5K, 2-5K, 5K, 10K, 15K, 20K, 50K, 32p each

##### DIN CONNECTORS

	plug	socket
Loudspeaker	2-pole	12p 10p
Audio	3-pole	13p 10p
Audio	4-pole	14p 12p
Audio	5-pole 180 deg	15p 12p
Audio	5-pole 240 deg	15p 12p
Audio	6-pole	15p 13p

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES, 40p. (Postage 3p if ordered alone).

KNOBs—NUTS, SCREWS, WASHERS—TERMINALS—LOUDSPEAKERS—TRANSFORMERS AND MANY OTHER ESSENTIAL ITEMS — see Catalogue

#### OVERSEAS CUSTOMERS WELCOME

#### COMPONENTS DISCOUNTS

allowed on all items other than those at net prices.

10% on orders for £5 or more

15% on orders for £15 or more

POSTAGE & PACKING FREE on orders for £2-00 or more. Please add 10p if under.

Overseas orders welcomed. Prices subject to alteration without prior notice.

To ELECTROVALUE, ENGLEFIELD GREEN, EGHAM, SURREY  
Please send a Goods to value of £..... as detailed on sheet attached, plus FREE copy of catalogue.

b Copy of catalogue.  
(strike out item which does not apply)

NAME .....

ADDRESS .....

Enclosed please find £.....cash/cheque/money order.

EE. 3

10p CATALOGUE FREE WITH ORDERS FOR £1-00 OR MORE

The Electrovalue catalogue (64 pages and cover, 8½ x 5½ins) is crammed with money saving items, and illustrated technical information. FREE with orders for £1-00 or more. Sent separately it costs you 10p post free. Write your order on a sheet of paper with coupon attached

# ELECTROVALUE

28 ST. JUDES ROAD, ENGLEFIELD GREEN.  
EGHAM, SURREY,

Telephone: Egham 5533 & 4757 (STD 0784-3) Telex: 2644475

Hours 9-5.30 : Sat. 1.0 p.m.

# CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER  
DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL

## COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY  
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY  
(WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N-9 803 1685

**MIDGET FLEX CONNECTOR**  
Approx. 2 amp rating.  
Two-pin non-reversible  
midget flex connector.  
Approx. size:  
2in. x 1/2in. Ideal for loudspeaker  
connections, etc. 8p plus 2p P. & P.

**MAINS TRANSFORMER**  
Fused Primary 240V. Secondary  
220V @ 1A. This transformer  
is made to a very high  
standard and is a  
small size: 2in. x 2 1/2in.  
x 2 1/2in. 63p plus 15p  
P. & P.

2N3055  
**POPULAR POWER  
TRANSISTOR**  
Now at our Low Price  
60p each  
Please include 5p P. & P.


**BARGAIN S.C.R.**  
**TESTED THYRISTOR**  
400 volt. 3 amp.  
45p each 5 for £2.00  
Please include 5p P. & P.

### BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator, 2 1/2in x 2 1/2in x 3 1/2in approx.  
6V £1.50, 9V £1.50, 7 1/2V complete with cable and plug for Philips Cassette. £2 plus 6p P. & P. each.



### D.P.D.T. SLIDE SWITCH

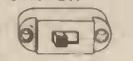

SIZE  
1 1/2ins long x wide  
each  
13p  
3p Postage

### WAFER SWITCHES

1 pole 12 way  
2 pole 2 way  
2 pole 3 way  
2 pole 4 way  
2 pole 6 way  
3 pole 4 way  
4 pole 3 way  
25p each. Please inc.  
5p P. & P. Up to 3  
switches.



### ALUMINIUM CHASSIS

Made from 18 gauge aluminium 4 sided  
chassis with corner brackets. All are 2 1/2"  
depth.  
8 x 3-41p 12 x 3-53p 14 x 9-94p  
6 x 4-45p 12 x 5-61p 16 x 6-86p  
8 x 6-53p 12 x 8-83p 16 x 10-108p  
10 x 7-83p 14 x 8-60p  
Please send 10p per chassis P. & P.



### POTENTIOMETERS

All types 1" and less diameter.  
**SINGLES DUAL**  
5K Log or 5K  
10K Lin Less 10K  
25K Switch 25K Less  
50K 50K Switch 50K  
100K 17p ea, 100K  
250K Double 250K 45p.  
500K Pole 500K each  
1M Switch 1M  
2M Switch 2M  
25p ea,  
Up to 3 Pots. Please add  
5p. P. & P.

**COMPONENT BARGAIN**  
1 32 + 16 mFd 275V Capacitor; 1 Speaker Output  
Transformer; 2 B9A Valve Holders; 1 4,700 pF  
Capacitor; 1 175 ohm W/W Resistor; 1 330 ohm, 1W  
Resistor; 1 12 kΩ 1/2W Resistor. All mounted on a  
small Amplifier Panel. Only 38p. P. & P. free.

**STEREO HEADSET**  
8 ohm impedance, complete with plug and 5ft  
lead. A very comfortable phone set. Listen to  
stereo without noise interrupting the pleasure.  
Wonderful value. £2.50 plus 10p P. & P.

**SINGLE EARPIECES**  
Crystal or magnetic  
plus lead and 3/8 m/m  
or 2/3 m/m plug. Please  
state which one required.  
18p plus 3p. P. & P.

**BARGAIN BOARDS**  
Components galore for the  
experimenter.  
Ex computer boards with:  
Resistors,  
Capacitors and  
useful Transistors — at least 4  
transistors per board.  
BARGAIN PRICE 30p per board.  
5 BOARDS £1.20. P. & P. Free  
on this item.

**TOGGLE SWITCHES**  
S.P.S.T. . . . . 10p each  
D.P.D.T. . . . . 15p each  
Please include 3p P. & P.

**LOUDSPEAKER BARGAINS**  
E.M.I. 460 set 3, 8, 15 ohm  
£3.50 plus 38p. P. & P.  
E.M.I. 350 set 8 ohm.  
£7.50 plus 38p. P. & P.

**MINI LOUDSPEAKERS**  
2 1/2" 8 ohm 38p 2 1/2" 40 ohm 38p  
3" 8 ohm 40p 2 1/2" 75 ohm 38p  
Plus 3p. P. & P. on each Mini  
Speaker.

### CAPACITORS

Mini Electrolytics all values up  
to 1000MFD @ 15V-7p each.  
Small PP Capacitors only in  
packs of 10 but you can mix  
values—25p for 10.  
250MFD @ 25V-15p  
500MFD @ 25V-21p  
1000MFD @ 25V-27p  
2000MFD @ 25V-34p  
3000MFD @ 25V-45p  
5000MFD @ 25V-58p  
Please inc. 10p. P. & P. with  
orders under £2 value.

### PRINTED CIRCUIT KIT

Everything for  
producing your  
own printed  
circuits.  
£1.40 plus  
10p. P. & P.

### PRINTED CIRCUIT BOARD

8 x 6-10p 10 x 5-15p  
9 x 5-10p 12 x 12-30p  
Please inc. 3p. per board P. & P.

### EA1000 3 WATT AUDIO AMPLIFIER MODULE

An Audio Amplifier designed around the  
TAA621 Linear I.C.—  
Supply Voltage . . . . . 9-24V  
Speaker Imp. . . . . 8-16 ohm  
Frequency . . . . . 50Hz-20kHz  
Overall Size . . . . . 2in x 3in x 1/2in  
Ideal Amplifier for radios, record players,  
stereo units, etc.  
Full technical data and diagrams with each  
module. All guaranteed and a bargain at



£2.63 + 5p P. & P.

**EX COMPUTER PRINTED CIRCUIT PANELS**  
2in. 4in. packed with semi-conductors and top  
quality resistors, capacitors, diodes, etc. Our  
price 10 boards 50p. P. & P. 7p. With a guaranteed  
minimum of 35 transistors. Data on  
transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1,  
P. & P. 18p. With a guaranteed minimum of 85  
transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to  
OC22 on each board. components 2 boards (4  
OC22) 50p. P. & P. 8p.

9 OA5, 3 OA10, 3 Pin Diode, 25 Resistors, 14  
Capacitors, 3 IFT 872, 3 IFT 872L, 1 IFT 875.  
All being traded on panels 1 1/2in x 4in. 4 for £1,  
P. & P. 25p.

**709C OPERATIONAL AMPLIFIER TO5**  
8 lead 1.1. 100 off 50p. 50 off 35p.  
100 off 20p.

**250 MIXED RESISTORS** 62p  
1/2 & 1 watt.

**150 MIXED HI STABS** 62p  
1/2, 1 & 1 watt 5/8" x better.

**QUARTZ HALOGEN BULBS**  
With long leads. 12V 55W for car spot lights,  
projectors, etc. 50p each. P. & P. 5p.

**GPO EXTENSION TELEPHONES**  
with dial but without bell. 85p each. P. & P. 30p.  
£1.75 for 2. P. & P. 30p.

**BARGAIN RELAY OFFER**  
Single pole change over silver contacts 25V to  
50V. 2.5k Ω coil. \* for 50p. P. & P. 5p.

**KEYTRONICS** mail order only  
44 EARLS COURT ROAD  
LONDON, W.8 01-478 8499

## The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for  
those tricky jobs

ASSEMBLY—SOLDERING—  
GLUING—WIRING—DRILLING  
ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

**TWIN VICE: £5.90 (24p P & P)**  
ALSO AVAILABLE  
**SINGLE VICE: £3.37 (20p P & P)**  
**COVENTRY MOVEMENT CO LTD.**  
Dept. E.3  
BURNSALL ROAD, COVENTRY  
CV5 6BJ STD 0203-74363

## INSTRUMENTAL AUDIO EFFECTS

**SUPER "FUZZ" UNIT KIT.** CONNECTS  
BETWEEN GUITAR & AMPLIFIER. OPER-  
ATES FROM 9v BATTERY (not supplied).  
ALL COMPONENTS AND PRINTED CIRCUIT  
BOARD WITH FULL INSTRUCTIONS. KIT  
PRICE: £2.60 post paid.

CREATE "PHASE" EFFECT ON YOUR  
RECORDS, TAPES ETC., UNIQUE CIRCUITRY  
ENABLES YOU TO CREATE PHASE  
EFFECT AT THE TURN OF A KNOB. OPER-  
ATES FROM 9v BATTERY (not supplied)  
COMPLETE KIT OF COMPONENTS WITH  
PRINTED CIRCUIT BOARD & FULL INSTRU-  
CTIONS. KIT PRICE: £2.60 post paid.

MAIL ORDER ONLY.  
S.A.E. ALL ENQUIRIES.

## DABAR ELECTRONIC PRODUCTS

98A, LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ

# Build yourself a TRANSISTOR RADIO



## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Ear-piece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 5" heavy duty Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost


**£8-50**

P. P. & Ins. 50p

(Overseas P. & P. £1)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

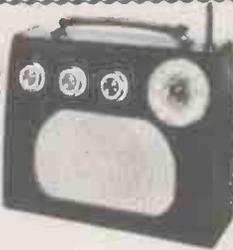

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 7in. x 4in. Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)

## Exclusive to readers of "EVERYDAY ELECTRONICS" "EVERYDAY SEVEN"




MEDIUM and LONG WAVE PORTABLE. Specially designed circuit for easy construction incorporating 7 transistors and 2 diodes, air spaced tuning capacitor, push pull output using 600 mw transistors, heavy duty loud-speaker for quality sound and

room filling volume, internal Ferrite Rod aerial, Volume/on/off control, tuning control and wave change switch. Handsome, strongly made wooden case, size 11½" x 7½" x 3½" with carrying handle and black knobs with spun silver inserts. The ideal radio for those who are comparatively inexperienced in electronic construction. Easy build plans are supplied free with parts or available, separately for 25p.

Total building costs **£4-98** P. P. & Ins. 41p. (Overseas Post £1)

## ROAMER SIX

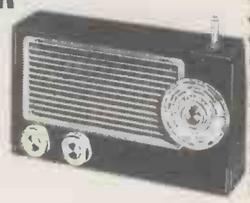


6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy B.P. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3-98** P. P. & Ins. 26p. (Overseas P. & P. £1)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

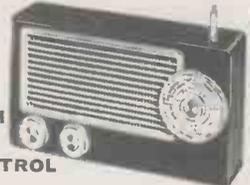

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 5" heavy duty Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)

## POCKET FIVE



3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 6½ x 1½ x 3½in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 21p. (Overseas P. & P. 63p)

## TRANSONA FIVE



NOW WITH 3in SPEAKER

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone 3in. moving coil speaker. Attractive case with red speaker grille. Size 8½ x 4½ x 1½in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 26p. (Overseas P. & P. 63p)

## NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT

### COMPONENTS INCLUDE:

Tuning Condenser; 2 Volume Controls; 2 Slider Switches; 4"x2½" Speaker; Terminal Strip; Ferrite Rod Aerial; 3 Plugs and Sockets; Battery Clips; 4 Tag Boards; Balanced Armature Unit; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three ½" Knobs.

Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction

All parts including **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)

## FULL AFTER SALES SERVICE

- Callers slide entrance Barratts Shoe Shop
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- |               |                          |                |                          |
|---------------|--------------------------|----------------|--------------------------|
| ROAMER TEN    | <input type="checkbox"/> | EVERYDAY SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT  | <input type="checkbox"/> | TRANS EIGHT    | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX     | <input type="checkbox"/> |
| POCKET FIVE   | <input type="checkbox"/> | EDU-KIT        | <input type="checkbox"/> |

Parts price list and plans for .....

Name .....

Address .....

(Dept. E.E.4.)


# HENRY'S RADIO LIMITED

## ENGLAND'S LEADING ELECTRONIC CENTRES



HI-FI · ELECTRONIC COMPONENTS · TEST · P.A. · DISCOTHEQUE · LIGHTING · MAIL ORDER

### 10th EDITION CATALOGUE

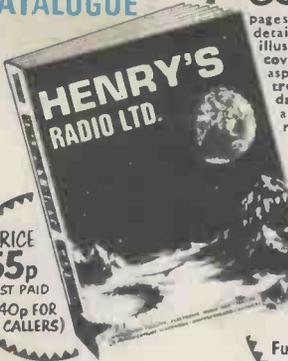

**350**

pages fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

**PRICE 55p**  
POST PAID  
(40p FOR CALLERS)

**10,000**

Stock lines at Special Low Prices and Fully Guaranteed

### PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. PW), 3 Albemarle Way, London, E.C.1.—for catalogue by post only.

All other mail and callers to "303", see below  
**A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!**

### HOME EQUIPMENT

- AF105 50kV multimeter (illus.). Price £8-50, p.p. 20p. Leather case £1-42. 200H 20kV/V. Price £3-87, p.p. 20p. Case 62p. 500 30kV/V multimeter. Price £8-87, p.p. 20p. Leather case £1-50 THL33 2kV/V. Price £4-12, p.p. 15p. Leather case £1-15.
  - TE65 Valve voltmeter. Price £17-50, p.p. 40p.
  - SE250B Pocket pencil signal injector. Price £1-75, p.p. 15p.
  - SE500 Pocket pencil signal tracer. Price £1-50, p.p. 15p.
  - TE20D RF generator. Price £15, p.p. 40p.
  - TE22D Matching audio generator. Price £17, p.p. 40p.
  - TE15 Grid dip meter. Price £12-50, p.p. 40p.
  - TO3 Scope 3 in. tube. Price £37-50, p.p. 50p.
  - TE22 Audio Generator. Price £17, p.p. 40p.
  - CI-5 Pulse Scope. £39-00, p.p. 50p.
  - U4341 AC/DC Multitester and transistor tester. AC & DC Current. In steel case. Price £10-50, p.p. 15p.
  - TMK 500 30kV/V Multitester. Price £8-87, p.p. 13p. Leather case £1-98.
- LARGEST RANGE of Panel Meters, Edge Meters and Test Equipment of every sort. Full details in latest catalogue—see above.**

### LOW COST HI-FI SPEAKERS

- E.M.I. Size 1 3/4" x 8 1/4". Large Ceramic Magnet. TYPE 150 6 watt, 3, 8 or 15 ohms £3-20. Post 22p.
  - TYPE 150TC Twin cone version £2-75. Post 22p.
  - TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3-85. Post 25p.
  - TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7-70. Post 28p.
- POLISHED CABINETS For 150, 150TC and 450 £4-50. Post 30p.**

### SPEAKER KITS

- WHARFEDALE 4-8 ohms. PEERLESS 8 ohm Systems.
- Unit 3, 8" 15W £10-20. 20-2 8" 30W £11-25.
- Unit 4, 12" 25W £13-50. 20-3 8" 40W £16-75.
- Unit 5, 12" 35W. £19-50. 4-30 12" 40W £22-75.
- GOODMANS DIN 20 KIT 20W 4ohm £10-75
- Carriage etc. 50p each or 75p per pair for Kits.

- ### STEREO HEADPHONES
- With stereo jack. Post 15p.
- Dulci SH650D £2-25
  - Rotel RH600 £4-67
  - Akai ASE95 £3-50
  - Eagle SE30 £5-97
  - Koss K711 £7-97
  - Pioneer SE30 £9-45
  - Koss PRO4A £15-50

### HI-FI TO SUIT EVERY POCKET



**SAVE 40% ON LIST UP TO 40% PRICES PLUS FREE 'BIB' Groov-Kleen Record Cleaner. Value £1-99**

ROTA 1500, 5 + 5 watts Garrard 2025TC with 9TAHC diamond ceramic. Plinth/Cover. Type 60 Compact Speakers. Size 16 x 9 1/4 x 6 1/2" SAVE £44-90 Carr. £29

TELETON '206', Garrard SP25 Mk. III, Goldring G800 Series Carr., Plinth/Cover. New 15 watt Quality SDL1 Bookshelf Speaker Systems, all leads etc. SAVE £54-95 Carr. £30-00

TELETON F2000, Med. Wave, Stereo FM Tuner Amplifier, Garrard 2025TC, 9TAHC Diam., Plinth/Cover. Type 60 Speaker Systems as above, all leads, etc. SAVE £56-95 Carr. £36

or with 2 x SA125 Speakers £48-95 Carr. £2

ROTA 2200 10 + 10 Watt. Garrard SP25 III/G800H. Plinth/Cover. New 15 watt SDL2 Twin Speaker Systems, all leads, etc. SAVE £62-50 Carr. £32

**LOW PRICES PLUS 12 MONTHS GUARANTEE & DEMONSTRATIONS**

**FREE LATEST SPECIAL PRICE STOCK LIST & STEREO SYSTEMS Ref. 16/17**

**FREE BROCHURES**

- P.A., DISCO and LIGHTING No. 18
- TRANSISTORS, I.C.'s No. 36

**20 WATT I.C. AMPLIFIER**

Toshiba 20 watt Power Amplifier. £4-57.

Toshiba Pre-Amplifier I.C., £1-50.

Data and suggested circuits No. 42, 10p.

SL403D 3 watt I.C. with 8 page data and circuits £1-50.

IC12 6 watt I.C. £2-50.

**TEXAS PRE-AMPLIFIERS & I-100W AMPLIFIERS**

Circuits, layouts and data £1-25 post paid.

**NIXIE TUBES** (post 15p per order)

XN3 or XN13 0-9 side view with data sheet, 85p each.

GN4 end view 0-9 with socket and data, £1-75. All I.C.'s for Digital Clocks in stock. HENRY'S CLOCK CIRCUIT No. 29/2 15p.

### BUILD THIS VHF FM TUNER


5 MULLARD TRANSISTORS 300 kc/s BAND-WIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO.

A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.

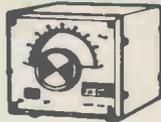**TOTAL £6-97, p.p. 20p. Cabinet 100p. Decoder Kit £3-97. Tuning meter £1-75**

Mains unit (optional) Model PS900 £2-47.

Mains unit for Tuner and Decoder PS1200 £2-62.



### HIGH QUALITY SILICON AMPLIFIERS AND PRE-AMPLIFIERS

Self powered Silicon—FET Pre Amplifiers. Push button selectors, tape record/play, adjustable levels, drive up to 4 x PA25 or 2 x PA50

FET 9/4 Mono or single channel. All facilities plus microphone. Mixing.

### SPECIAL OFFER £10-50

**SILICON POWER AMPLIFIERS RMS OUTPUT**

PA 25 25 watts into 8 ohms £7-50.

PA 50 50 watts into 4 ohms £9-50.

MU442 Power Supply for 1 or 2 PA25's or 1 only PA50, £6-00. Post 20p

**FREE BROCHURE No. 25 ON REQUEST. NO SOLDERING—ALL UNITS INTERCONNECTING. ON DEMONSTRATION AT "356".**

### TERRIFIC SAVINGS!

- | GARRARD - BSR - THORENS GOLDRING PLINION CONNOISSEUR | CHASSIS (P) (less cartridge) | ASSEMBLED (P) (less cartridge, with cover) | ASSEMBLED (with cart. P & C) |
|--|------------------------------|--|------------------------------|
| *SP25 Mk III £11-30                                  | *MP60 £19-97                 | MP60(TDIP) £17-75                          | 2025TC/9TAHCD £14-95         |
| †AP76 £11-30   | MP60 £11-30                  | HT70 PC £23-50                             | SP25/3-G800H £19-95          |
| *MP160 £15-15  | PL12AC £36-50                | GL72 PC £30-95                             | AP76-G800 £29-95             |
| *HT70 £16-60   | GL72 PC £30-95               | GL75 PC £43-75                             | HT70PC/G800 £29-95           |
| GL72 £22-95  | TD150AB/ £45-50              | GL75 £28-97                                |                              |
| GL75 £28-97  | TX11 £45-50                  | Dual12/15 £39-00                           | BD2 £32-25                   |

**CHASSIS WITH CARTRIDGE**

- \*2025TC/9TAHCD £9-50
- \*3300/9TAHCD £9-98
- TEAK \*P11/T1 Std. £3-25
- PLINTH \*BN1 Deluxe £8-50
- WITH †P4/T4 Std. £4-75
- COVER †BN4 Deluxe £8-50
- (State \*P6/T6 Std. £3-25)
- deck) †BSR Deluxe £6-25

Post etc.—Chassis 50p, with plinth/cover 70p, Plinth/Cover 30p Carr. 15p.

**300mW TRANSISTOR AMPLIFIER MODEL 4-300**

Fully assembled 4TR Amplifier. Size 5 1/4 x 1 1/2 x 8 in. 1-10mV adjustable sensitivity. Output 3-8 ohms. Fitted Vol. control. 9 volt operated. Thousands of uses plus low cost.

Price £1-75, p.p. 15p (or 2 for £3-25, p.p. 15p).

### SIN-LAIVE PROJECT 60 PACKAGE DEALS —SAVE POUNDS!

2 x Z30 amplifier, stereo amp supply, PZ5 power supply, £16-75, Carr. 40p. Or with PZ6 power supply £18-25. Carr. 40p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply £20-25, Carr. 40p. Transformer for PZ8 £2-45 extra. NEW! Project '60S' stereo system £20-97. Any of the above with Active Filter unit add £4-75 or with pair Q16 speakers add £16. Also new FM Tuner £20-25, 2000 Amplifier £23-75, p.p. 50p. 3000 Amplifier £31-50. Also IC12 £2-50.

### "BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.

**TOTAL COST TO BUILD £7-98**

p.p. 32p (Battery 22p). All parts sold separately—Leaflet No. 2.

7" PORTABLE (as previously advertised) £6-98, p.p. 35p from stock—Leaflet No. 1.

### MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

Electronic Components, Audio and Test Gear Centre  
**356 EDGWARE ROAD, LONDON, W.2.**  
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre  
**354 EDGWARE ROAD, LONDON, W.2.**  
Tel: 01-402 5854

P.A., Disco & Lighting Centre  
**309 EDGWARE ROAD, LONDON, W.2.**  
Tel: 01-723 6963

Mail Orders. Special Bargain Shop, Industrial Sales  
**303 EDGWARE ROAD, LONDON, W.2.**  
Tel: 01-723 1008/9

"309", "354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY