
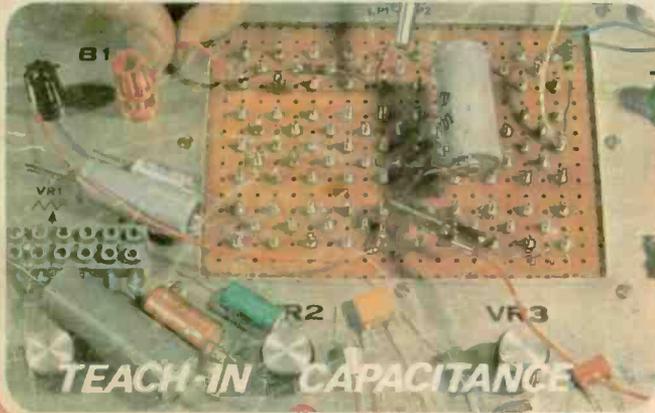
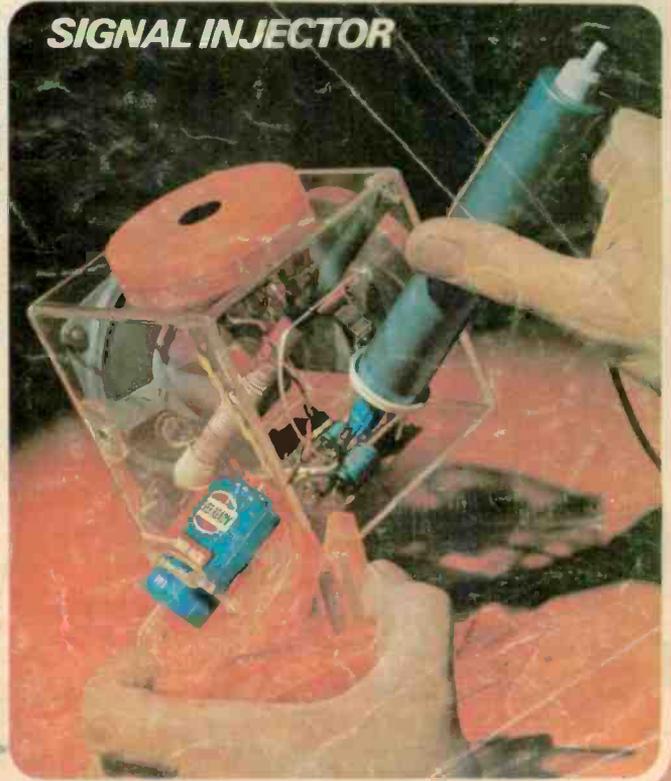


An exciting **STUART PLARGE** & **everyone**

# everyday electronics

MAR.72  
15p

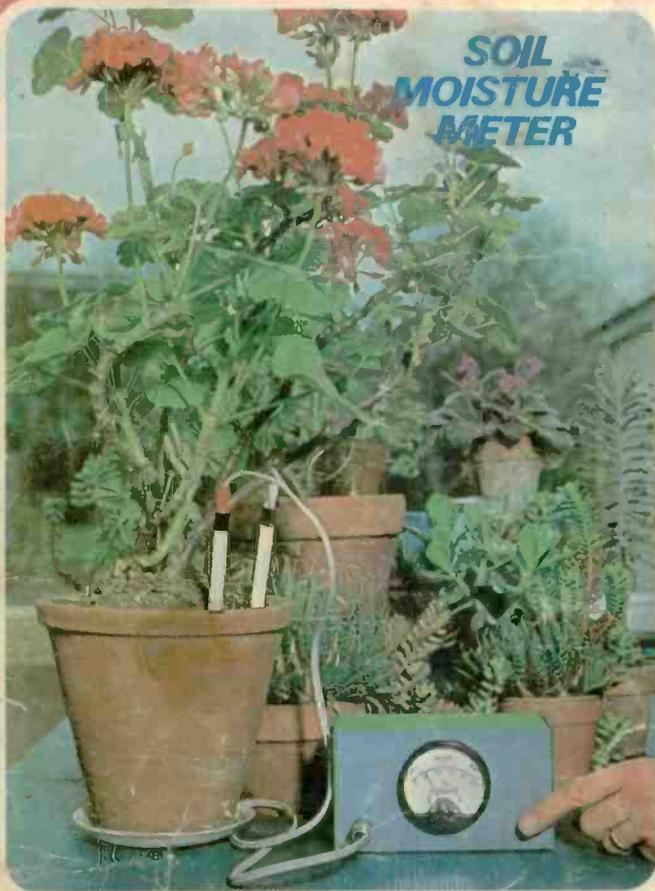

# ADCOLA Soldering Instruments add to your efficiency

## THE NEW 'INVADER'

### ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

\*Additional Stock Bits (illustrated) available

#### COPPER

- B 38  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
- B 14  $\frac{1}{8}$ " — 2.4 mm CHISEL FACE
- B 24  $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE
- B 12  $\frac{1}{4}$ " — 4.75 mm LEVEL BIT
- B 58  $\frac{1}{2}$ " — 6.35 mm CHISEL FACE

#### LONG LIFE

- B 42 LL  $\frac{1}{4}$ " — 4.75 mm CHISEL FACE
- B 38 LL  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
- B 14 LL  $\frac{1}{8}$ " — 2.4 mm CHISEL FACE
- B 44 LL  $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

PRICE  
£1.85



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

\* Write for price list and catalogue



**ADCOLA PRODUCTS LTD.,**  
(Dept. Y), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

### MW/LW TRANSISTOR RADIO



Complete set of parts for this MW/LW Transistor Radio. Originally sold by world-famous company as a set for more than £17. Coverage 192-555m+1070-1870m. 9 volt 6 transistor superhet using 3 AF17 in RF and IF stages powered by a two stage AF amplifier using OC81D, 2 x OC81. Output approx. 500mW. Transistors 3 x AF17, OC81D + 2 OC81. Also works off car-serial. Full instruction book 12pp free with parts. Red only, ply case, rexine covered. Requires PPT battery, price £23½ extra. 3½in high-quality speaker. Price £26 plus 40p P. & P.

### STEREO AMPLIFIER Type SHV—2 x 3 Watts

Fully built. Separate vol., base and treble controls each channel; 12 x 4½ x 6in high. EZ80 and 2 x ECL82 valves. O.P. trans. for 3-ohm speakers. Double wound mains trans. Suitable for crystal magn. cartridge, tuner, etc. with mono-stereo switch. 200-250V a.c. mains. £7-25, 50p P. & P.



### 1½W MAINS GRAMOPHONE AMPLIFIER

EZ80, ECL82, O.P. Transformer (3 ohm). Vol./On-off and Tone Control. Double wound mains transformer. 2½ x 2½ x 2½in separate but wired to chassis, 4 x 2½ x 4½in over valves. £3-37½ including 5in speaker (£2-75 less speaker). (Post paid.) (Two less 10%.)

### MAINS TRANSFORMERS (240-250V input)

Postage in brackets  
6-3V at 2½A, 40p (15p).  
250V at 50mA and 6-3V at 1½A, 50p (20p).  
220V at 1A, 6-3V at 2A and 250V at 50mA, 75p (25p).  
90V at 20mA and 1-4V at 250mA, 50p (15p).  
Deduct 10 per cent from total bill for more than one transformer.

Complete set of parts with wiring diagram for battery eliminator to give 90V. H.T. at 20-30mA and 1-4V at 125 or 250mA (adjustable). With un-drilled aluminium box approx. 8 x 3 x 3in, trans., choke, two rectifiers, condensers.  
Price £2-75 plus 25p P. & P.

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants

(2 mins. from Station and Buses), FULL GUARANTEE. Aldershot 22240  
(CLOSED WEDNESDAY. S.A.E. for enquiries please.)

### FELSTEAD (EES) ELECTRONICS

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE

Selection from our list, sent free for stamped addressed envelope. (Free overseas) Cash with Order only—No CCD or Caller service. Charges (Min. 6p.) in brackets after all items apply to G.B. & Eire only. Regret Orders under 25p. plus charges unacceptable. SAE please, for enquiries or cannot be replied to. Overseas Orders welcomed.

**RECORDING TAPE:** Finest quality/value British Mylar available: STANDARD 5" 600ft 36p; 6" 900ft 60p; 7" 1200ft 56p; LONG PLAY 5" 900ft 50p; 5" 1200ft 56p; 7" 1800ft 81p.


**ARTICLES:** (7½p on 5" and 5½", 9p on 7"). Other sizes. Cassettes and accessories in list. ARTICLES: £1-10; STEREO GP93 £1-40; Stereo Ceramic GP94 £1-95. (6p) Comparatives shown in list with more types incl. Sonotone 9TAHC Goldring &c. at lowest prices. **DIAMOND STYLUS:** Single tip types: Acco GP37, GP59, GP65/67, GP71. BSR TCS/LP/ST; COLLARO O. P. and DC284; GARRARD GC2, GC8, GC12, GC810; ROSETTE BF40, O. P. and T; PHILIPS 3301 (3060, 3066, 3302, 3304) 3010 (12, 13, 10); SONOTONE 197/207. ALL AT 40p each (6p). Double-tips, turn-over types (78 &c.) on other side). For Acco GP73, GP91 (for cartridges GP93, GP94 &c.) GP918C (for stereo-compat. types) GP104, RSR 874 (ST3, ST5), ST9 (ST8), ST11/14/15, SONOTONE STA, 9TA, 9TAHC, PHILIPS 3306 (3310, 3224, 3228/22, GP280) GARRARD GCM21, 22, GC823, GK825 and 26, GCM21T and 22T, GKM24T, GC8231, GKN25T & 26T, GCM31, GCR36, GC835, GC838, K840A, K841B, etc. ALL AT 75p (6p). **DOUBLE DIAMOND STYLUS:** (Same dia. 1½p each side: no 78) for all types £1 50 (6p). **PICK-UP WIRE:** Super thin twin flex screened, 6p per yard. (Up to 6 yds. 9p, over charges paid.) All sapphires in list. **MICROPHONE:** CRYSTAL: LAPEL 1½", clip/hand, lead 3-5mm jack plug 32½p (4p). CM20 Cream Plastic hand 52½p; CM21 Grey Plastic Hand/Desk 82½p; both have 3-5mm jack plug and lead (9p either). "NITICK" 60 21 02; CM70 "PLANET" Metal, tapered, with neck cord, adaptor for stands £1-47½; "MIC 81" hand/Desk 81p; "MIC 45" (curved metal hand grip £1.00. All with leads (all 9p). **MICROPHONE INSERTS:** Diam. 1.75 or 0.9 either size 27½p (1p to 6 for 6p). **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM160, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3-87½ (27½p each). **SPEAKERS:** Still very popular 12" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1-87½ (27½p)—or pair for stereo £4 25 charges paid. **SMALL 2½"** 3 Ω or 8 Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000 Ω adjustable 92½p (7½p). **EARPIECES:** with lead and min. 2-5mm or 3-5mm (state which) jack plug, MAJOR 9p. **CRYSTAL (3-5mm plug only) 24p** (up to 3 for 6p, any type). **SOLDERING IRON:** Slin, modern, British high speed, 4½", all parts replaceable, highest quality fully guaranteed £1-17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OT TPT1 (3 Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds., ass't. col. FOLIO CORE 14p. **FLEXIBLE or STPEP THIN:** for transistor wiring &c. either 15p. (ANY 12" 12p). **RETRACTABLE FLEXIBLE LEADS:** (CURLIES): With phono plug ex. end 6ft 25p, 12ft 38p. **DYNAMIC MICROPHONE:** 500 Ohm, 50K/600 Ω, full-in volume control, 200 Ω switch, special 20ft lead, the best value anywhere £5-30; 1"130, um-in. mesh ball 50K/600 Ω jack plug, cable, adaptor, £4-90; DM



*Call 'em what  
you will ...*

*... the best place  
to get them is*

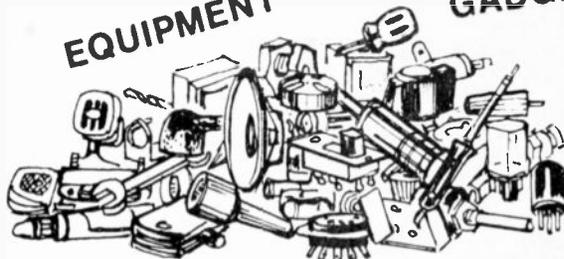ITEMS COMPONENTS  
BITS & PIECES PARTS  
EQUIPMENT GADGETS



# HOME RADIO (COMPONENTS) LIMITED

240 London Road, Mitcham. CR4 3HD

Phone: 01-648 8422



Until you've tried the service provided by Home Radio (Components) Limited you've no idea how simple it can be tracking down and obtaining components. It becomes a pleasure instead of a bind! But first you need the Home Radio Catalogue, listing over 8,000 components, more than 1,500 of them illustrated. At 70 pence, including p & p, it's a gift—especially as every copy contains 10 vouchers each worth 5 pence.

Send coupon today.

**POST THIS COUPON** with your  
cheque or postal order for 70p



Please write your Name and Address in block capitals

NAME Stuart Pearce

ADDRESS .....



HOME RADIO (COMPONENTS) LTD., Dept. EE  
234-240 London Road, Mitcham, Surrey CR4 3HD.

● 24-hour Phone Service  
Ring 01-648 8422

Ask for details of our  
Credit Account Service

The price of 70p applies only to catalogues purchased  
by customers in the U.K. and to BFPO addresses.

**THIS FANTASTIC OFFER ONLY FROM US!**

**SAVE £20.25 NOW!**

**NEW SOLID STATE BATTERY/MAINS AC**

**Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**

**OUR PRICE £23.75** CARR. ETC. 35p

**RECOMMENDED RETAIL PRICE £44**

**Latest sensation in the world of sound!** First-class makers. Fabulous V.H.F. AM/FM Radio AND Cassette Tape Recorder and Player combined, AND runs off standard batteries or mains (plug in the 220/240v. AC line cord). Record, play back anything, anywhere! Even tape direct from Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44, WE OFFER AT ALMOST HALF PRICE!** Wonderful features: \* Press button Keyboard Control panel! \* New "pop up" Cassette ejection system! \* "MAGIC EYE" Visual Battery check/recording level indicator or built in automatic leveller. \* Separate ON/OFF, HI-LO volume controls! \* Heavy duty built-in speaker! \* Earphone (for personal listening or "monitoring") and extension speaker sockets! \* Remote control microphone! \* Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case, size 11 1/2in. x 9 1/2in. 3 1/2in. overall approx., with carry handle. Designs vary slightly. Takes standard 30, 60, 90 or 120-minute Philips Cassette Tapes obtainable everywhere. The amazing built-in full circuit V.H.F. AM/FM Radio gives you superb clarity of tone, incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus BBC, National V.H.F. Picks up dozens of foreign stations. Also fabulous in car! You could pay ££££'s more for a Car Radio or Car Cassette player ALONE! £23.75, CARR. 35p. Simple instructions, remote control microphone with on/off switch and microphone stand. **BONUS—Standard Batteries and Cassette Tape 25p extra.**

**COMMERCIAL TRAVELLERS** Please note: Merchandising office at our Holborn Store. (PERSONAL SHOPPERS WELCOME AT BOTH STORES).

**SHOPERTUNITIES LTD. S/L**

**ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!**

**BRAND NEW RUSSIAN WORLD BEATER!**

**6 WAVEBAND WORLD WIDE RECEPTION** **10 TRANSISTOR PLUS 3 DIODES PORTABLE RADIO**

**£9.97** BOX POST ETC. 43p

**NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!**

**THE VERY LATEST MODEL, SUPERSEDING ALL PREVIOUS MODELS:—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION.** Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! \*Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection! Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. **YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE!** Yes, 6 separate wavebands including Standard Long, Medium and Short Waves to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even messages from all over the world. Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2in. length. It's also a fabulous **CAR RADIO—any speed requires no additional aerial. UNIQUE!** Elegant Black, White and Chrome finished case. SIZE 10 1/2in. x 8in x 3 1/2in. overall approx. Magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST, ETC., 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

**\*COMPARE ITS PERFORMANCE with £34 RADIOS!**

Dept. EE/4, 164 UXBRIDGE ROAD, LONDON W12 8AQ (facing Shepherd's Bush Green) (THURSDAY 11, FRIDAY 7). Also at 37/39 High Holborn, LONDON, W.C.1 (Thurs. 7). Both stores open MON.—SAT. 9 a.m.—6 p.m.

**INSTRUMENTAL AUDIO EFFECTS**

**SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied) ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.**

**CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.**

**MAIL ORDER ONLY.**

**S.A.E. ALL ENQUIRIES.**

**DABAR ELECTRONIC PRODUCTS**

98a, LICHFIELD STREET, WALSAIL, STAFFS. WS1 1UZ

**VEROBOARD**

**VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK**

0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER.

\*TRADE DISTRIBUTOR N. Rose (Electrical) Ltd., London, W.C.1.

**vero**

VERO ELECTRONICS LTD.  
Industrial Estate, Chandler's Ford, SO2 3JL. Tel: Chandler's Ford 2821

**Vary the strength of your lighting with a DIMMASWITCH**

The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt £3.20. Kit Form £2.70  
300 Watt—£2.70. Kit Form £2.20

All plus 10p post and packing.  
Please send C.W.O. to:—

**DEXTER & COMPANY**  
5 ULVER HOUSE, 19, KING STREET, CHESTER CH1 2AH Tel: 0244-25883, As supplied to H.M. Government Departments.



# The Specification sounds fine the System sounds great

## Viscount III Audio Suite complete £49

**14W + 14W per channel. 40Hz to 40kHz ± 3dB Total distortion at 10 watts at 1kHz-0.1%**

This is real value for money! We have designed 3 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. It is available in 2 versions—R100 for ceramic cartridges, and R101 for magnetic and ceramic. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For all systems we have chosen the famous Garrard SP25 Mk. III deck which comes complete with simulated teak plinth and dust cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

**PRICES SYSTEM 1**

Viscount III R101 amplifier	£22.00 + 90p p&p
2 x Duo Type II speakers	£14.00 + £2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
<b>Total</b>	<b>£59.00</b>

Available complete for only **£52 + £3.50 p&p**

**SYSTEM 2**

Viscount R101 amplifier	£22.00 + 90p p&p
2 x Duo Type III speakers	£32.00 + £3 p&p
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23.00 + £1.50 p&p
<b>Total</b>	<b>£77.00</b>

Available complete for **£69 + £4 p&p**

**SYSTEM 3**

Viscount III Amplifier R100	£17.00 + 90p p&p
2 x Duo Type II speakers, pair	£14.00 + £2 p&p
Garrard SP25 Mk. III with CER. diamond cartridge, plinth and cover	£21.00 + £1.50 p&p
<b>Total</b>	<b>£52.00</b>

Available complete for only **£49 + £3.50 p&p**


**SPEAKERS**

**Duo Type II** Size approx 17" x 10 1/2" x 6 1/2". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Simulated Teak cabinet. **£14 pair + £2 p&p.**

**Duo Type III** Size approx 23 1/2" x 11 1/2" x 9 1/2". Drive unit 13 1/2" x 8 1/2" with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. **£32 pair + £3 p&p.**

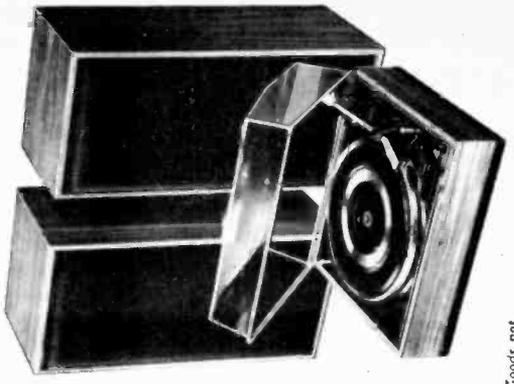**SPECIFICATION R101**

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within ± 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: head- phone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. (all controls at max) R101—P.U.1 and radio—65dB. P.U.2 -58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx 13 1/2" x 9" x 3 1/2".



Goods not despatched outside U.K. Send S.A.E. for fully illustrated leaflet



Radio and TV Components (Acton) Ltd. 21E High Street, Acton, London W3 6NG 323 Edgware Road, London, W2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.

# YATES ELECTRONICS (FLITWICK) LTD.

DEPT. E.E.  
ELSTOW STORAGE DEPOT,  
KEMPSTON HARDWICK,  
BEDFORD.

C.W.O. PLEASE. POST AND PACKING,  
PLEASE ADD 10p TO ORDERS UNDER £1.  
Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
5p stamp appreciated.  
10% DISCOUNT TO ALL CALLERS ON SATURDAYS

## RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.  
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4W  
Eric wire wound. 1W 2% ElectroSil TRS.

Power watts	Tolerance	Range	Values available	Price
1	5%	4.7Ω-2.2MΩ	E24	1-99 100+
1	10%	3.3MΩ-10MΩ	E12	1-0p 0-8p
1	2%	10Ω-1M	E12	1-0p 0-8p
1	10%	10Ω-3.9Ω	E12	1-0p 0-8p
1	5%	4.7Ω-1MΩ	E12	1-0p 0-8p
4	10%	1Ω-10Ω	E12	6p 5-3p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1W, lin 1/2W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELTON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0.1 matrix).  
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

## SEMICONDUCTORS

AC107	15p	BC108	10p	BFY52	22p	OC71	12p	IN4006	12p
AC126	12p	BC109	10p	BY127	12p	OC72	12p	IN4007	12p
AC127	12p	BC147	13p	BZY10	20p	OC81	12p	2N2926R	9p
AC128	12p	BC148	13p	BZY13	20p	OC82	12p	2N29260	9p
AC131	12p	BC149	13p	OA85	7p	OC82D	12p	2N2926Y	9p
AD140	50p	BC157	14p	OA90	5p	ORP12	50p	2N2926G	10p
AF114	20p	BC158	14p	OA91	5p	IN4001	6p	2N3055	60p
AF115	20p	BC159	14p	OA202	7p	IN4002	10p	2N3702	13p
AF116	20p	BF179	32p	OC26	45p	IN4003	10p	2N3703	11p
AF117	20p	BFY50	22p	OC44	12p	IN4004	10p	2N3707	13p
BC107	10p	BFY51	22p	OC45	12p	IN4005	12p	2N3711	10p

## ZENER DIODES

400mW 5% 3.3V to 30V, 15p.

## LINEAR IC's (D.I.L.)

709a	50p	741	50p
710a	50p	748	50p

## BRUSHED ALUMINIUM PANELS

12in x 6in=25p; 12in x 2in=10p; 9in x 2in=7p.

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2μF, 0.0068μF, 0.01μF,  
0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 0.1μF, 0.15μF, 0.22μF, 7μF,  
0.33μF, 11p, 0.47μF, 13p.  
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3p, 0.15μF,  
0.22μF, 7p, 0.33μF, 6p, 0.47μF, 7p, 0.68μF, 11p, 1.0μF, 13p.  
MULLARD POLYESTER CAPACITORS C280 SERIES  
250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF,  
3p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF, 13p,  
1.5μF, 20p, 2.2μF, 24p.

## MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF,  
2p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

6p each  
(μF/V): 10/2.5, 40/2.5, 80/2.5, 160/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4,  
400/4, 6.4/6.4, 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 4/10, 16/10, 32/10, 64/10,  
125/10, 200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1.6/25, 6.4/25, 12.5/25,  
25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.64/64, 2.5/64, 5/64, 10/64,  
20/64, 32/64.

## MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6.4, 800/4, 1000/2.5, 9p, 100/64, 160/40, 250/25,  
400/16, 640/10, 1250/4, 1000/6.4, 1600/2.5, 12p, 160/64, 250/40, 400/2.5, 640/16,  
2000/4, 1000/10, 1600/6.4, 2500/2.5, 15p, 250/64, 400/40, 640/25, 3200/4, 1000/16,  
1600/10, 2500/6.4, 4000/2.5, 18p.

## ELECTROLYTIC CAPACITORS Miniature P.C. mounting

6p each  
(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

## VEROBOARD

0.1	0.15
24 x 3 1/2	22p
24 x 5	24p
34 x 3 1/2	24p
34 x 5	28p
17 x 2 1/2	75p
17 x 3 1/2	100p
17 x 5 (plain)	82p
17 x 3 1/2 (plain)	60p
17 x 2 1/2 (plain)	42p
24 x 5 (plain)	11p
34 x 3 1/2 (plain)	11p
Pin insertion tool	52p
Spot face cutter	42p
Pkt. 50 pins	20p

## JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable 15p/metre

## BATTERY ELIMINATOR

£1.50  
9V mains power supply. Same size as PP9 battery.


# YOURS FREE FOR 7 DAYS

## The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 vols.) BASIC ELECTRONICS (6 vols.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

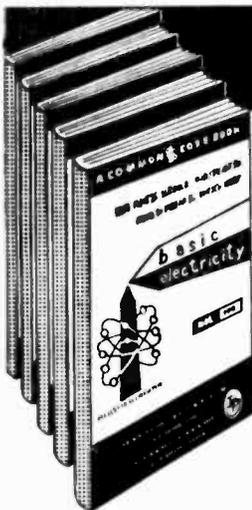

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

### WHAT READERS SAY

- ... CAREFULLY WRITTEN ...  
... I am very satisfied with these carefully written and well expressed manuals ... A.W., Shanklin.
- ... VALUABLE ASSISTANCE ...  
... Your valuable assistance has enabled me to find a good position as a Radio and TV Engineer ... D.S., Bristol.
- ... THEY ARE INVALUABLE ...  
... I find that as a base for a course in Electronics they are invaluable and I have yet to find anything even to approach the same standard ... H.N., Rotherham.

- To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP
- Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50 Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. BASIC ELECTRONICS £5.40 Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.
- Tick Set required (Only one set allowed on free trial)
- BASIC ELECTRICITY  BASIC ELECTRONICS
- Prices include Postage and Packing.
- Signature \_\_\_\_\_  
(If under 21 signature required of parent or guardian)
- NAME \_\_\_\_\_  
BLOCK LETTERS
- FULL POSTAL ADDRESS \_\_\_\_\_

**POST NOW FOR THIS OFFER !!**

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS!

### CLEAR PLASTIC METERS

**TYPES W.100**  
100 x 80 mm.

50μA	23-60	20V D.C.	23-10
50-0-50μA	23-45	50V D.C.	23-10
100μA	23-20	300V D.C.	23-10
100-0-100μA	23-45	1 amp. D.C.	23-10
500μA	23-35	5 amp. D.C.	23-10
1mA	23-10	300V A.C.	23-10
		VU Meter	23-75

### BAKELITE PANEL METERS

**TYPE S-80**  
80 mm.

square fronts

50μA	23-20	50μA	23-20
50-0-50μA	23-10	50V D.C.	22-80
100μA	22-75	300V D.C.	22-80
100-0-100μA	22-80	1 amp. D.C.	22-80
500μA	23-00	5 amp. D.C.	22-80
1mA	22-80	300V A.C.	22-80
		VU Meter	23-37

## "SEW" CLEAR PLASTIC METERS

### TYPE MR.56P. 4 1/2" x 4 1/2" fronts.

50μA	23-60	10V D.C.	22-80
50-0-50μA	23-10	20V D.C.	22-80
100μA	23-10	50V D.C.	22-80
100-0-100μA	23-00	300V D.C.	22-80
200μA	23-00	15V A.C.	22-80
500μA	22-90	300V A.C.	22-80
500-0-500μA	22-90	8 Meter 1mA	22-87
1mA	22-80	VU Meter	22-80
1-0-1mA	22-80	1 amp. A.C.	22-80
5mA	22-80	5 amp. A.C.	22-80
10mA	22-80	10 amp. A.C.	22-80
		20 amp. A.C.	22-80
		30 amp. A.C.	22-80

### TYPE MR.58P. 1 21/32" square fronts.

50μA	22-10	50μA	22-10
50-0-50μA	21-90	100-0-100μA	21-75
100μA	21-75	200μA	21-75
100-0-100μA	21-90	500μA	21-65
200μA	21-75	500-0-500μA	21-60
500μA	21-60	1mA	21-60
1-0-1mA	21-60	2mA	21-60
2mA	21-60	5mA	21-60
5mA	21-60	10mA	21-60
10mA	21-60	20mA	21-60
20mA	21-60	50mA	21-60
50mA	21-60	100mA	21-60
100mA	21-60	150mA	21-60

### TYPE MR.45P. 2 1/2" square fronts.

50μA	22-25	5 amp. A.C.	21-70
50-0-50μA	22-10	10V D.C.	21-50
100μA	22-10	20V D.C.	21-50
100-0-100μA	22-10	50V D.C.	21-50
200μA	21-87	300V D.C.	21-50
500μA	21-75	15V A.C.	21-80
500-0-500μA	21-70	300V A.C.	21-80
1mA	21-70	8 Meter 1mA	21-85
5mA	21-70	VU Meter	22-25
10mA	21-70	1 amp. A.C.	21-70
50mA	21-70	5 amp. A.C.	21-70
100mA	21-70	10 amp. A.C.	21-70
500mA	21-70	20 amp. A.C.	21-70
1 amp.	21-70	30 amp. A.C.	21-70

### TYPE MR.52P. 2 1/2" square fronts.

50μA	23-10	10V D.C.	22-00
50-0-50μA	22-80	20V D.C.	22-00
100μA	22-80	50V D.C.	22-00
100-0-100μA	22-80	300V D.C.	22-00
500μA	22-30	15V A.C.	22-10
1mA	22-00	300V A.C.	22-10
5mA	22-00	8 Meter 1mA	22-10
10mA	22-00	VU Meter	23-20
50mA	22-00	1 amp. A.C.	22-00
100mA	22-00	5 amp. A.C.	22-00
500mA	22-00	10 amp. A.C.	22-00
1 amp.	22-00	20 amp. A.C.	22-00
5 amp.	22-00	30 amp. A.C.	22-00

### TYPE MR.52P. 2 1/2" square fronts.

50μA	23-10	10V D.C.	22-00
50-0-50μA	22-80	20V D.C.	22-00
100μA	22-80	50V D.C.	22-00
100-0-100μA	22-80	300V D.C.	22-00
500μA	22-30	15V A.C.	22-10
1mA	22-00	300V A.C.	22-10
5mA	22-00	8 Meter 1mA	22-10
10mA	22-00	VU Meter	23-20
50mA	22-00	1 amp. A.C.	22-00
100mA	22-00	5 amp. A.C.	22-00
500mA	22-00	10 amp. A.C.	22-00
1 amp.	22-00	20 amp. A.C.	22-00
5 amp.	22-00	30 amp. A.C.	22-00

### TYPE MR.45P. 2 1/2" square fronts.

50μA	22-25	5 amp. A.C.	21-70
50-0-50μA	22-10	10V D.C.	21-50
100μA	22-10	20V D.C.	21-50
100-0-100μA	22-10	50V D.C.	21-50
200μA	21-87	300V D.C.	21-50
500μA	21-75	15V A.C.	21-80
500-0-500μA	21-70	300V A.C.	21-80
1mA	21-70	8 Meter 1mA	21-85
5mA	21-70	VU Meter	22-25
10mA	21-70	1 amp. A.C.	21-70
50mA	21-70	5 amp. A.C.	21-70
100mA	21-70	10 amp. A.C.	21-70
500mA	21-70	20 amp. A.C.	21-70
1 amp.	21-70	30 amp. A.C.	21-70

## "SEW" BAKELITE PANEL METERS

### TYPE MR.65. 3 1/2" square fronts.

50μA	23-00	300mA	21-90
50-0-50μA	22-75	1 amp.	21-90
100μA	22-75	5 amp.	21-90
100-0-100μA	22-65	15 amp.	21-90
200μA	22-65	30 amp.	21-90
500μA	22-40	50 amp.	21-90
500-0-500μA	22-20	5V D.C.	21-90
1mA	22-20	10V D.C.	21-90
5mA	22-20	150V D.C.	21-90
10mA	22-20	300V D.C.	21-90
50mA	22-20	30V A.C.	21-90
100mA	22-20	50V A.C.	21-90
500mA	22-20	300V A.C.	21-90
1 amp.	22-20	500mA A.C.	21-95
5 amp.	22-20	1 amp. A.C.	21-95
10 amp.	22-20	5 amp. A.C.	21-95
20 amp.	22-20	10 amp. A.C.	21-95
50 amp.	22-20	20 amp. A.C.	21-95
5V D.C.	22-20	30 amp. A.C.	21-95
		50 amp. A.C.	21-95
		VC Meter	23-10

**\*MOVING IRON—ALLOTHERS MOVING COIL**  
Please add postage

## SEW EDUCATIONAL METERS

meter movement is demonstrate internal in the following ranges:

50μA	25-00	20V d.c.	24-40
100μA	24-65	50V d.c.	24-40
1mA	24-40	300V d.c.	24-40
50-0-50μA	24-35		
100-0-100μA	24-40	Dual range	
1A d.c.	24-40	500mA/5A d.c.	24-65
5A d.c.	24-40	5V/50V d.c.	24-65
10V d.c.	24-40		

## EDGWISE METERS

TYPE PE.70. 3 1/2" x 1 15/32" x 1 15/32" deep.

50μA	23-10	500μA	22-75
50-0-50μA	23-00	1mA	22-45
100μA	23-00	300V A.C.	22-45
100-0-100μA	23-00	300V A.C.	22-45
200μA	22-90	VU Meter	23-40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

# MULTIMETERS for EVERY purpose!

### MODEL TE-200. 30,000 O.P.V. Mirror scale, overload protection 0/5/3/15/80/300/1,200V. D.C. 0/5/30/120/600/1,200V. A.C. 0/300μA/5mA/50mA/300mA/600mA. 0/5K/80K/800K/8 meg. ohm -20 to +63 db. \$2-97. P. & P. 15p.

### MODEL PL434 20kΩ/Volt D.C. 8kΩ/Volt A.C. Mirror scale. 5/3/12/30/120/600V D.C. 3/30/120/600V A.C. 50/600mA/80/600 mA. 10/100K/1 Meg/10 MegΩ. -20 to +46db. \$6-97. P. & P. 12p.

### MODEL 5025 57 Ranges, Giant 5 1/2" Meter, Polarity Reverse Switch. Sensitivity: 50K/Volt D.C. 5K/Volt A.C. D.C. Volt 125, 25, 12.5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volt: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 501A, 2-5, 5, 25, 50, 250 500mA. 5, 10 amp. Resistance: 2K 10K 100K 1MEG. 10 MEG. Decibels: -20 to +85 db. \$12-50. P. & P. 17p.

### TKM MODEL TW-202CH FEATURES RESETTABLE OVERLOAD BUTTON. Sensitivity 20KΩ/Volt D.C. 5KΩ/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts 0.5, 2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K. 50K db. \$11.50. P. & P. 17p.

### ROUND SCALE TYPE PENCIL TESTER MODEL TS.68

Completely portable, simple to use pocket sized tester. Resistance: 0/5/30/300V A.C. and DC at 2,000 ohms p.v. Resistance 0-20K ohms. ONLY \$1-97 P. & P. 13p

### TKM MODEL 117 F.E.T. ELECTRONIC VOLT METER

Battery operated. 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2" DC VOLTS 0 3-1200V. AC VOLTS 3-300V RMS. 0-900V P.F. DC CURRENT RENT 12-12MA. Resistance up to 2000Ω ohm. Decibels -20 to +51 db Complete with leads/instructions. \$17.50. P. & P. 20p.

### TE-65 VALVE VOLT METER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. \$17-50. P. & P. 30p. Additional probes available: R.F. \$2-12; H.V. \$2-50.

### TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20cps to 200 kc/s on 4 bands Square: 20cps to 30 kc/s. Output impedance 5,000 ohms, 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. \$17-50. Carr. 37p.

### TE-20RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-250 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V A.C. Brand new with instruction manual. \$17-50 P. & P. 37p. S.A.E. for details.

### TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-111 megΩ 6 Ranges ±1% L. 1μH-111 HENRY'S 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:1/100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2" x 5" x 2 1/2". \$20. P. & P. 25p.

### MODEL LT.101 1000 O.P.V. 0/10/50/250/1000 V. D.C. 0/10/50/250/1000 V. A.C. 0/1/100 M.A. 0/1/10 K ohms. \$1-97. P. & P. 15p.

### MODEL TE-200 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V. D.C. 0/10/50/250/1,000V. A.C. 0/50 mA/250 mA. 0/80K/6 megΩ. P. & P. 15p.

### TKM MODEL MD.120 Mirror scale. 20kΩ/Volt D.C. 10kΩ/Volt A.C. 30/60/300/600/3,000 V. D.C. 6/120/1,200 V. A.C. Current 0-60μA/0-120/300mA. 0-60K/0-5 MegΩ. -20 to +53 db. \$4-22. P. & P. 15p.

### MODEL 500 30,000 O.P.V. with overload protection mirror scale 0/5/2.5/10/25 100/250/500/1,000V. D.C. 0/2.5/10/25/100/250/500/1,000V. A.C. 0/50mA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg. 60 MegΩ. \$2-87. Post paid.

### TKM LAB TESTER. 100,000 O.P.V. 6 1/2" Scale Buzzer Shunt Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5KΩ/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 3, 10, 50, 250, 500, 1,000V. D.C. Current: 10, 100μA, 2.5, 10, 100, 500mA. 2.5, 10, 100, 100K, 10MEG, 100 MEGΩ. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size 7 1/2" x 6 1/2" x 3 1/2". \$18-90. P. & P. 25p.

### U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. \$67 o.p.v. 0/3/15/7.5/30/60/150/300/600/900 VDC and 75mV. 0/3/15/7.5/30/60/150/300/600/900VAC. 0/300μA/1.5/6/50/60/150/300/600mA/1.5/6 AMP. D.C. 0/1.5/6/15/60/150/600V.D.C. 1.5/6 AMP. AC. 0/200Ω/5K/30KΩ. Accuracy DC 1%, AC 1.5%. Knife, edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. \$2-50 plus P. & P. 25p.

### RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V D.C. 2.5/10/50/250/500/1000V A.C. DC Current 100 mA/1/10/100mA/1A. Resistance 300 ohm/3/30/300K/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$2-97 P. & P. 25p.

### HONEYWELL DIGITAL VOLT METER VT.100

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2, 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2" x 2 1/2" x 1 1/2". AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. \$49-97. Carr. 50p.

G. W. SMITH & CO (RADIO) LTD.  
Also see next two pages

# SEMI-CONDUCTORS / VALVES

## ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	22P	2N4848	35P	BC114	15P	BFW90	22P	NKT129	80P	
2N3416	22P	2N4849	35P	BC115	15P	BFW91	22P	NKT223	80P		
2G301	20P	2N3417	27P	2B102	25P	BC116	15P	BFX12	22P	NKT224	22P
2G302	20P	2N3439	180P	2B103	25P	BC118	15P	BFX13	22P	NKT225	22P
2G303	20P	2N3440	27P	2B104	25P	BC119	15P	BFX29	25P	NKT229	80P
2G306	20P	2N3564	17P	2B105	25P	BC120	15P	BFX30	25P	NKT237	85P
2G308	20P	2N3565	17P	2B106	25P	BC122	15P	BFX32	25P	NKT238	85P
2G309	20P	2N3566	22P	2B303	60P	BC125	15P	BFX44	87P	NKT240	27P
2G371	15P	2N3568	25P	2B304	70P	BC126	15P	BFX68	87P	NKT241	27P
2G374	20P	2N3569	25P	2B601	32P	BC134	12P	BFX84	25P	NKT242	20P
2G381	22P	2N3570	125P	2B602	35P	BC135	12P	BFX85	30P	NKT243	20P
2N388A	49P	2N3872	97P	2B603	27P	BC138	15P	BFX86	25P	NKT244	17P
2N404	20P	2N3875	27P	2B604	40P	BC137	15P	BFX87	25P	NKT245	20P
2N694	15P	2N3876	27P	2N128	70P	BC138	20P	BFX88	25P	NKT246	17P
2N697	15P	2N3877	22P	2N140	72P	BC140	35P	BFX89	62P	NKT262	30P
2N698	25P	2N3878	18P	2N141	77P	BC141	35P	BFX93A	70P	NKT264	20P
2N699	30P	2N3879	20P	2N142	55P	BC147	10P	BFY11	42P	NKT271	20P
2N706	10P	2N3641	18P	2N143	67P	BC148	10P	BFY18	25P	NKT282	20P
2N708A	12P	2N3642	18P	2N152	37P	BC149	12P	BFY19	25P	NKT274	20P
2N709	12P	2N3643	20P	40323	55P	BC152	17P	BFY21	42P	NKT275	20P
2N709	45P	2N3644	25P	40320	50P	BC153	20P	BFY24	45P	NKT278	25P
2N718	25P	2N3645	25P	40321	32P	BC164	20P	BFY29	40P	NKT281	27P
2N718A	30P	2N3691	15P	40309	32P	BC157	15P	BFY30	40P	NKT401	87P
2N726	25P	2N3692	18P	40310	45P	BC158	11P	BFY41	62P	NKT402	90P
2N727	25P	2N3693	18P	40311	35P	BC159	11P	BFY43	62P	NKT403	78P
2N814	17P	2N3704	18P	40314	47P	BC160	12P	BFY45	62P	NKT404	65P
2N815	17P	2N3705	18P	40314	47P	BC161	12P	BFY47	62P	NKT405	65P
2N816	17P	2N3706	18P	40314	47P	BC162	12P	BFY49	62P	NKT406	62P
2N818	25P	2N3703	10P	40315	37P	BC168B	12P	BFY82	20P	NKT406	62P
2N829	22P	2N3704	12P	40314	47P	BC168C	14P	BFY63	15P	NKT451	62P
2N830	20P	2N3705	10P	40317	37P	BC169B	14P	BFY66A	17P	NKT452	62P
2N837	62P	2N3706	10P	40319	55P	BC169C	16P	BFY76	42P	NKT453	47P
2N1690	22P	2N3707	12P	40320	47P	BC170	12P	BFY77	42P	NKT718	20P
2N1091	22P	2N3708	10P	40323	52P	BC171	15P	BFY90	65P	NKT774	42P
2N1131	25P	2N3709	10P	40324	47P	BC172	15P	BX119	17P	NKT734	27P
2N1132	25P	2N3710	10P	40326	37P	BC175	22P	BX120	15P	NKT735	27P
2N1302	17P	2N3711	10P	40329	30P	BC177	20P	BX121	20P	NKT773	25P
2N1303	17P	2N3713	187P	40344	27P	BC178	20P	BX126	45P	NKT781	30P
2N1304	22P	2N3714	200P	40347	67P	BC179	20P	BX127	47P	OC18	60P
2N1305	22P	2N3715	200P	40348	67P	BC180	20P	BX128	32P	OC19	32P
2N1306	25P	2N3718	255P	40360	40P	BC182L	10P	BX160	60P	OC20	85P
2N1307	25P	2N3773	240P	40361	40P	BC183	9P	BX161	62P	OC22	60P
2N1308	25P	2N3791	275P	40362	60P	BC183L	9P	BX176	16P	OC23	60P
2N1309	25P	2N3819	240P	40370	30P	BC184	11P	BX177	20P	OC24	60P
2N1507	17P	2N3820	55P	40409	67P	BC184L	11P	BX178	25P	OC29	60P
2N1613	20P	2N3823	50P	40407	67P	BC186	25P	BX184	15P	OC38	85P
2N1631	25P	2N3854	27P	40408	62P	BC187	27P	BX187	15P	OC39	85P
2N1632	30P	2N3854A	27P	40409	62P	BC212L	12P	BX126	17P	OC29	60P
2N1637	30P	2N3855	27P	40410	62P	BC213L	12P	BX127	15P	OC35	60P
2N1638	27P	2N3855A	30P	40412	60P	BC214L	15P	BX128	17P	OC36	60P
2N1639	27P	2N3856	30P	40474A	57P	BCY10	27P	BX129	17P	OC41	22P
2N1701	16P	2N3856A	35P	40484A	55P	BCY30	30P	BX132	25P	OC42	22P
2N1711	24P	2N3858	25P	40488	72P	BCY31	30P	BX133	25P	OC44	25P
2N1869	35P	2N3868A	30P	40600	57P	BCY32	30P	BX137	25P	OC45	15P
2N1893	37P	2N3859	27P	40603	60P	BCY33	30P	BX138	20P	OC46	15P
2N2147	72P	2N3859A	32P	AC107	30P	BCY34	35P	BX139	22P	OC70	15P
2N2180	97P	2N3860	30P	AC126	30P	BCY38	45P	BX143	60P	OC71	18P
2N2193	40P	2N3866	100P	AC137	24P	BCY39	60P	BX161	32P	OC72	13P
2N2193A	45P	2N3866A	100P	AC138	24P	BCY40	60P	BX162	32P	OC73	13P
2N2194	40P	2N3877A	40P	AC151	18P	BCY41	15P	BX153	37P	OC74	13P
2N2194A	40P	2N3900	37P	AC152	22P	BCY42	15P	BX154	40P	OC75	25P
2N2217	25P	2N3900A	40P	AC154	22P	BCY43	15P	BX156	90P	OC76	25P
2N2218	20P	2N3901	97P	AC176	20P	BCY54	82P	BX179	45P	OC77	40P
2N2219	20P	2N3903	20P	AC187	25P	BCY58	22P	BX190	67P	OC78	20P
2N2220	25P	2N3904	25P	AC188	25P	BCY59	22P	BX193A	18P	OC81	20P
2N2221	25P	2N3905	40P	AC177	25P	BCY60	25P	C420	15P	OC82	25P
2N2222	30P	2N3906	25P	ACY18	24P	BCY70	15P	CA50	15P	OC82	25P
2N2222A	25P	2N4058	12P	ACY19	24P	BCY71	20P	GET102	55P	OC82D	25P
2N2297	30P	2N4059	10P	ACY20	20P	BCY72	16P	GET113	25P	OC83	25P
2N2368	15P	2N4060	12P	ACY21	20P	BCY78	30P	GET114	30P	OC84	25P
2N2369	15P	2N4061	12P	ACY22	20P	BCY79	30P	GET118	30P	OC139	25P
2N2369A	15P	2N4062	12P	ACY23	20P	BCY80	30P	GET120	30P	OC140	25P
2N2410	42P	2N4244	47P	ACY39	47P	BCZ11	40P	GET873	18P	OC170	25P
2N2483	27P	2N4245	15P	ACY40	14P	BD112	50P	GET880	45P	OC171	30P
2N2484	32P	2N4249	15P	ACY41	15P	BD116	112P	GET887	15P	OC200	40P
2N2539	32P	2N4250	15P	ACY44	25P	BD121	65P	GET889	22P	OC201	78P
2N2540	32P	2N4254	42P	AD140	47P	BD123	80P	GET890	22P	OC202	80P
2N2613	35P	2N4255	42P	AD146	47P	BD124	75P	GET892	22P	OC203	40P
2N2614	35P	2N4257	42P	AD150	62P	BD131	75P	GET897	22P	OC204	20P
2N2646	47P	2N4285	17P	AD161	35P	BD132	80P	GET898	22P	OC205	75P
2N2711	25P	2N4286	17P	AD162	35P	BDY10	125P	MAT100	25P	OC206	95P
2N2712	25P	2N4287	17P	AF109	45P	BDY20	105P	MAT101	25P	OC207	78P
2N2713	27P	2N4288	16P	AF114	25P	BDY61	125P	MAT120	25P	OCPT1	42P
2N2714	30P	2N4289	12P	AF115	25P	BDY92	125P	MAT121	25P	ORP12	50P
2N2904	25P	2N4291	15P	AF117	20P	BF117	47P	MJ420	80P	ORF61	42P
2N2905	25P	2N4292	15P	AF118	44P	BF162	28P	MJ421	80P	P346A	22P
2N2905A	20P	2N4294	17P	AF121	30P	BF164	20P	MJ430	102P	BT140	15P
2N2906	20P	2N4303	47P	AF124	22P	BF168	15P	MJ440	95P	BT144	15P
2N2906A	25P	2N4994	15P	AF125	18P	BF169	35P	MJ450	97P	BT183	62P
2N2907	25P	2N4995	15P	AF126	18P	BF170	35P	MJ460	102P	BT184	62P
2N2923	15P	2N5027	52P	AF127	18P	BF171	35P	MJ491	137P	BT185	12P
2N2924	15P	2N5028	52P	AF139	28P	BF170	35P	MJ491	137P	BT185	12P
2N2925	15P	2N5029	47P	AF178	42P	BF173	30P	MJ530	60P	BT186	12P
2N2926	12P	2N5030	42P	AF179	45P	BF177	30P	MJ530	60P	BT187	12P
2N2926B	12P	2N5172	12P	AF180	60P	BF178	25P	MJ537	70P	BT188	12P
2N2927	15P	2N5174	62P	AF181	40P	BF179	25P	MJ537	70P	BT188	12P
2N3011	20P	2N5175	62P	AF186	39P	BF180	35P	MJ552	70P	BT189	12P
2N3014	25P	2N5176	45P	AF239	30P	BF181	35P	MJ552	70P	BT189	12P
2N3063	20P										

# HI-FI EQUIPMENT

SAVE UP TO  
**33 1/2% OR MORE**  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!



## RECORD DECKS

B.S.R. Mini Mono† £4-97	BL65D £13-45
CI29† £6-70	AP76 £18-90
MP60 £10-75	BL72B £23-95
610 £14-05	BL75B £26-50
110 £11-85	BL90B £28-95
310 £9-85	ZERO 100A £45-95
810 £24-47	ZERO 100S £42-95
MP60 TFD1 £17-65	GOLDRING
MP60 TFD2 £15-85	GL69/2 £18-97
610 T.P.D.1 £20-97	GL69P £25-95
610 T.P.D.2 £18-75	GL72 £22-95
210 Package* £9-85	GL72P £25-95
H.T.70 £16-56	GL75 £23-95
H.T.70 Pack. £22-90	GL75P £25-95
<b>TEORENS</b>	LID 72 £3-75
TD125 £29-65	LID 75 £3-95
TD125AB £24-25	GL85 £47-95
TX25 £6-70	GL85P £55-95
TD150A11 £24-50	LID 85 £4-85
TD150AB11 £40-25	GI01 £22-60
TX11 £3-77	G99 £21-95
<b>GARRARD</b>	<b>PIIONEER</b>
2025 T/C* £3-50	PL12AC £36-50
3500* £9-50	
SP26 1H1 £10-75	

† Mono • Stereo Cartridge  
All other models less Carriage  
Carriage 50p extra any model.

## RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge. (Garrard)	
2025 T/C with Sonotone 9TAHCD	£13-95
Garrard SP25 Sonotone 9TAHCD	£16-95
Garrard SP25H Goldring G800	£18-95
Garrard AP76 Goldring G800	£29-95
Garrard SP25H11/Shure M75-6	£19-95
Garrard AP76/Shure M75-6	£30-95
B8R MP60 Audio Technica AT.35	£21-00
Goldring GL72 Goldring G800	£37-50
Goldring GL75 Goldring G800	£42-50
Goldring GL75 Goldring G800B	£46-95

Carriage 50p extra any model.

## SDM 8V HI-FI PHONES

Input 8-16 Ω Frequency 20-18,000 Hz stereo or mono switch, separate volume controls each earpiece, padded head-band. £3-97, p/p 20p



## SINCLAIR EQUIPMENT

Project 60. Package offers.

2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. £16-75 Carr. 37p. Or with PZ6 power supply £18-85 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. £20-55 Carr. 37p.

Transformer for PZ5. £2-97† extra. Add above to the above £4-87† for active filter unit and £18-90 for pair of Q16 speakers. Project 60 FM Tuner £19-95. Carr. 37p. All other Sinclair products in stock.

2000 Amp £23-75 Carr. 37p. 3000 Amp £31-50 Carr. 37p. Neoteric Amp £43-95. Carr. 37p. IC10/IC12 £2-60.

NEW PROJECT 605 - £20-97, Carr. 37p.

## LATEST CATALOGUE

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS

VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

SEND NOW

ONLY  
**37 1/2 p**  
P & P  
10p



## TELETON SAQ-206B STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal, aux tape. Volume, bass, treble, sibilant balance, scratch filter and loudness controls. List £32-50. OUR PRICE £19-95 Carr. 37p.

## TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/ Amp and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/Cer phono inputs. AFC/Built-in MPX. List £51. OUR PRICE £29-75. Carr. 50p.

★ SUGGESTED SYSTEM ●  
F.2000, (Garrard) 2025T/C Changer fitted stereo cartridge, with plinth and cover and pair of Q.W.S. 3 way Speakers. Total Rec. Price £97-73. OUR PRICE £54-65. Carr. £1.

## ★ TRANSISTORISED FM TUNER



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 V battery. Coverage 88-108 Mc/s. Ready built kit ready for use. Factory price £16-95. OUR PRICE £12-95. Carr. 37p. Stereo multiplex adaptors £4-97.

## HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5MΩ/100MΩ. Output 60MW. £5-97. P. & P. 15p.

## NS-1600W STEREO AMPLIFIER



Except for a 1000W 6x4x2 1/2in. amplifier. All silicon transistor. Handsome Walnutcase. Switched input selector.


separate balance, volume, treble, bass controls. Output 2x 6W RMS. Inputs Mag, Tape, Xtal, Tuner, Tape Out. £14-75. Carr. 37p.

## EA.41 REVERBERATION AMPLIFIER



Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc. and output into your amplifier. Volume control, depth of reverb control. Beautiful walnut cabinet. 7 1/2 x 3 x 4 1/2in. £5-97. P. & P. 15p.

## BH.001 HEAD-SET AND BOOM MICROPHONE

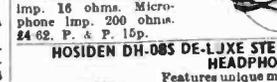

Moving coil. Ideal for language teaching, communications. Headphone Imp. 16 ohms. Microphone Imp. 200 ohms. £4-62. P. & P. 15p.

## HOSIDEN DH-085 DE-LUXE STEREO HEADPHONES



Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack plug. £7-97. P. & P. 12p.

Model 8-100TR MULTI-METER/TRANSISTOR TESTER 100,000 o.p.v. MIRROR SCALE/OVERLOAD PROTECTION 0/12-8/3/12/30/120/600 V D.C. 0/8/30/120/600 V. A.C. 0/12/600mA/12/3000mA/12 Amp. D.C. 0/10K/1 MEG/100 MEG. -20 to +50 db. 0.01 - 2 mfd. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £13-50. P/P 25p.



## MCA. 220 AUTOMATIC VOLTAGE STABILISER

Input 88-125 VAC or 176-250VAC. Output 120VAC or 240VAC. 230VA rating. £11-97. Carr. 30p.



## BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000 Hz; Square 18-50,000 Hz Output max. 10 dB (10 K ohms) Operation internal batteries Attractive 2-tone case 7 1/2 x 5 x 2 1/2 in. Price £17-50. Carr. 17p.



TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. £7-97. P. & P. 20p.




## TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CFS-1 MHz. Input Imp. 2 meg Ω 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 V a.s. Supplied brand new with handbook. £22-50. Carr. 50p.


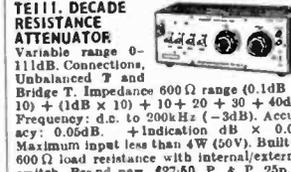
## TE111. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.05dB. + Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new. £27-50. P. & P. 25p.



## 230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40) Quantities available.



## POWER RHEOSTATS


High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. In. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 72p. P. & P. 7p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1-05 P. & P. 7p. 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £1-37 P. & P. 7p.

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

5-260 General Purpose Bench Mounting	8-280B Panel Mounting
1 Amp £7-00	1 Amp £7-00
2.5 Amp £8-05	2.5 Amp £8-05
5 Amp £11-75	
8 Amp £15-90	
10 Amp £22-50	
12 Amp £23-80	
20 Amp £49-00	

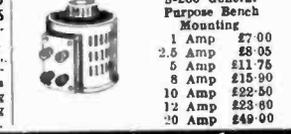Please add postage ALL MODELS INPUT 230 VOLTS. 50/60 CYCLES. OUTPUT VARIABLE 0-260 VOLTS. Special discounts for quantity



RP214 REGULATED POWER SUPPLY Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 230/240V AC. Size 185 x 85 x 100mm. £8-97 P. & P. 25p.

PS.1000B REGULATED POWER SUPPLY Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 230/240V AC. Size 4" x 3 1/2" x 6 1/2". £11-97. P. & P. 25p.



## UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s-30mc/s. FET. 8 Meter, Variable BFO for SSB. Built-in Speaker, Bandsread, Sensitivity Control. 220/240V. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.




## LAFAYETTE HA-800 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, 8. Meter, Bandsread, RF Gain, 15" x 9" x 8 1/2". 18 lbs. 220/240V. A.C. or 12v. D.C. Brand new with instructions. £45. Carr. 50p.



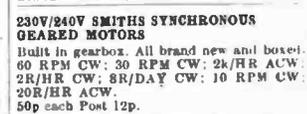
## 230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new units boxed. 60 RPM CW: 30 RPM ACW: 2k/HR ACW: 2R/HR CW: 8R/DAY CW: 10 RPM CW: 20R/HR ACW. 50p each Post 12p.



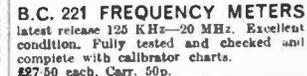
## B.C. 221 FREQUENCY METERS

Latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27-50 each. Carr. 50p.


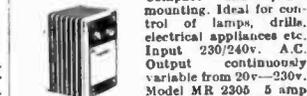
## SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS


Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20V-230V. Model MR 2310 5 amp 86 x 46 x 38mm £8-37. Model MR 2310 10 amp 90 x 46 x 60mm £11-97. Postage 12p.



## AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

150 W	£2-37	P. & P. 17p
300 W	£3-25	P. & P. 22p
500 W	£4-97	P. & P. 32p
1000 W	£7-25	P. & P. 37p
1500 W	£8-97	P. & P. 42p
5000 W	£36-00	P. & P. £1

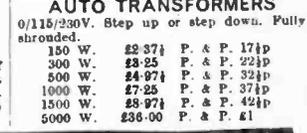

# G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-6 MONDAY TO SATURDAY

# CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER  
DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL

## COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)  
13 SOUTH MALL, EDMONTON, N-9 803 1685

**MIDGET FLEX CONNECTOR**  
Approx. 2 amp rating. Two-pin non-reversible midget flex connector. Approx. size: 2 1/2" x 1/4". Ideal for loudspeaker connections, etc. 8p plus 2p P. & P.

### MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 50M/A. 6-3V. @ 1A. This transformer is made to a very high standard and is a small size: 2 1/2" x 2 1/2" x 2 1/2". 83p plus 15p P. & P.

2N3055  
**POPULAR POWER TRANSISTOR**  
Now at our Low Price 50p each  
Please include 5p P. & P.



### BARGAIN S.C.R.

**TESTED THYRISTOR**  
400 volt. 3 amp.  
45p each 5 for £2.00  
Please include 5p P. & P.



### COMPONENT BARGAIN

1 32 + 16 mFd 275V Capacitor; 1 Speaker Output Transformer; 2 B9A Valve Holders; 1 4,700 pF Capacitor; 1 175 ohm W/W Resistor; 1 330 ohm, 1W Resistor; 1 12 k Ohm Resistor. All mounted on a small Amplifier Panel. Only 38p. P. & P. free.

### STEREO HEADSET

8 ohm Impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. £2.50 plus 10p P. & P.

### SINGLE EARPIECES

Crystal or magnetic plus lead and 3 1/2 m/m or 2-5 m/m plug. Please state which one required. 19p plus 3p P. & P.

### BARGAIN BOARDS

Components galore for the experimenter. Ex computer boards with: Resistors, Capacitors and useful Transistors — at least 4 transistors per board.



### TOGGLE SWITCHES

S.P.S.T. 10p each  
D.P.D.T. 15p each  
Please include 3p P. & P.

### LOUDSPEAKER BARGAINS

E.M.I. 450 set 3, 8, 15 ohm  
£3.25 plus 38p. P. & P.  
E.M.I. 350 set 8 ohm.  
£7.00 plus 38p. P. & P.

### MINI LOUDSPEAKERS

2 1/2" 8 ohm 38p 2 1/2" 40 ohm 38p  
3" 8 ohm 40p 2 1/2" 75 ohm 38p  
Plus 3p. P. & P. on each Mini Speaker.

### BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc. into the a.c. mains through this compact eliminator, 2 1/2" x 2 1/2" x 3 1/2" approx. 6V @ 150, 9V @ 150, 7 1/2V complete with cable and plug for Philips Cassette. £2 plus 5p P. & P. each.



### D.P.D.T. SLIDE SWITCH

SIZE 1 1/4" long & wide  
13p each  
3p Postage

### WAFER SWITCHES

1 pole 12 way  
2 pole 2 way  
2 pole 3 way  
2 pole 4 way  
3 pole 4 way  
4 pole 3 way  
22p each. Please inc. 5p P. & P. Up to 3 switches.



### ALUMINIUM CHASSIS

Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.

6 x 3—41p 12 x 3—53p 14 x 9—94p  
6 x 4—48p 12 x 5—61p 16 x 8—86p  
8 x 6—58p 12 x 8—83p 16 x 10—109p  
10 x 7—68p 14 x 3—60p

Please send 10p per chassis P. & P.



### CAPACITORS

Mini Electrolytic all values up to 100MFD @ 15V—7p each. Small PP Capacitors only in packs of 10 but you can mix values—25p for 10.

250MFD @ 25V—15p  
500MFD @ 25V—21p  
1000MFD @ 25V—27p  
2000MFD @ 25V—34p  
3000MFD @ 25V—45p  
5000MFD @ 25V—58p  
Please inc. 10p. P. & P. with orders under £2 value.

### PRINTED CIRCUIT KIT



Everything for producing your own printed circuits.  
£1.40 plus 10p. P. & P.

### PRINTED CIRCUIT BOARD

8 x 6—16p 10 x 8—18p  
9 x 5—16p 12 x 12—30p  
Please inc. 3p. per board P. & P.

### EA1000 3 WATT AUDIO AMPLIFIER MODULE

An Audio Amplifier designed around the TAA621 Linear I.C.—  
Supply Voltage . . . . . 9-24V  
Speaker Imp. . . . . 8-16 ohm  
Frequency . . . . . 50Hz-20kHz  
Overall Size . . . . . 2 1/2" x 3 1/2" x 1 1/2"  
Ideal Amplifier for radios, record players, stereo units, etc.  
Full technical data and diagrams with each module. All guaranteed and a bargain at



### POTENTIOMETERS

All types 1" and less diameter.  
BUNGLES DUAL  
5K Log or 5K  
10K Lin Less 10K  
25K Switch 25K Less  
50K 50K Switch  
100K 17p ea, 100K 45p-  
250K Double 250K  
500K Pole 500K each  
1M Switch 1M  
2M 25p ea, 2M

Up to 3 Pots. Please add 5p. P. & P.

### RESISTORS

We stock all recognised values of resistors all at 10% or closer tolerance. We regret we can only mail them in lots of ten. You can send for mixed values. All Midget types.  
1 watt lots of 10—13p  
1/2 watt lots of 10—13p  
1 watt lots of 10—25p  
Please include 3p P. & P. for each 10 resistors.

£2.63 + 5p P. & P.



## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 75p  
Size 12



### THIN GAUGE SOLDER, ESSENTIAL FOR soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 75p Size 10



### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

19A 60/40 18 18p\*  
Size 5 (Ultra-  
ted) Savbit 18 18p\*  
15 60/40 22 22p\*

\*Recommended Price



### INVALUABLE FOR STRIPPING FLEX. THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 50p



# SAFEbloc

## of robust construction

Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.

If ordering by post, send cash with order.

PRICE £2.60+10p P.&P. EACH


Special bulk order wholesale and industrial rates on application



# RENDAR®

Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex. Tel. Burgess Hill 2642
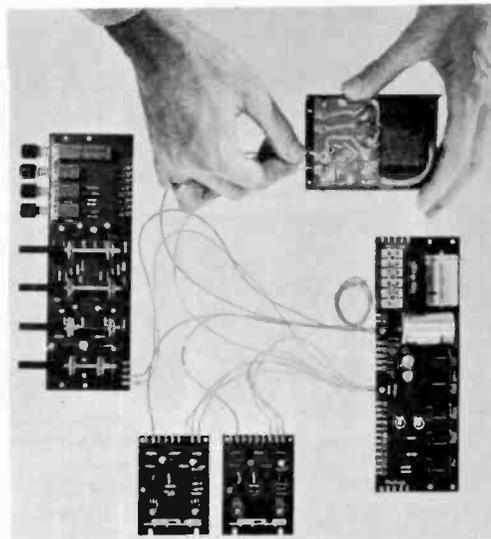
# Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same – there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative – Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one – Masterlink – which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together – the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

#### Guarantee

If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

## sinclair

Sinclair Radionics Ltd., London Road.,  
St. Ives, Huntingdonshire PE17 4HJ.  
Telephone: St. Ives (04806) 4311

Everyday Electronics, March 1972

#### Specifications

Output – 30 watts music power (10 watts per channel R.M.S. into  $3\Omega$ )

Inputs – Mag. P.U. – 3mV correct to R.I.A.A. curve 20–25,000 Hz  $\pm$  1dB. Ceramic pick-up – 50mV. Radio – 50 to 150mV. Aux. adjustable between 3mV. and 3V.

Signal to noise ratio – Better than 70dB.

Distortion – better than 0.2% under all conditions.

Controls – Press buttons for on-off, P.U., radio and aux. Treble +15 to –15 dB at 10 kHz. Bass +15 to –15 dB at 100 Hz. Volume. Stereo Balance.

Channel matching with 1dB.

Front panel – brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

## £29.95

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ

Please send Project 605 post free  Details and list of stockists

Name .....

Address .....

for which I enclose £29.95 cheque/money order/cash.

E.E. 4B

# NOW BUILD ON! — WITH LST

FEATURING SOME OF THE MANY COMPONENTS FROM THE FREE LST CAT. HAVE YOU SENT FOR YOURS YET???

## TRANSISTORS

We stock all popular types but how about our **INTRODUCTION KIT £1**—consisting of: OC71, OC44, OC45, AC128, BC107, 2N2926, OC72 incl. data and connection chart.  
ORDER AS PACK NO: EE1

## DIODES INTRODUCTION KIT 50p

2 x OA81, 2 x OA200 4 x 1N4001 (All recently used in EE projects)  
ORDER AS PACK NO: EE2.

## VEROBOARD

36 square inches total area (approx) consisting of .1 and .15 matrix  
ORDER AS PACK V10:

## ZENER DIODES

Consisting of a 1 Watt and a 400 milliwatt Zener (or regulator) diode plus FREE 24 page circuit book.  
ORDER AS PACK EE3:

PACK 50p

## CAPACITOR PACK

10 popular values of capacitor including polyester and electrolytic good starting stock! Normal Cat. price over 65p  
ORDER AS PACK EE4

50p

## NEON PACK

Consisting of 10 miniature neon indicator bulbs 65Vac 90 Vdc. Use 270k resistor for mains use.  
ORDER AS PACK: EE5

50p

## BOOKS ETC:

Designers Guide to British Transistors: Data on 1000's of common types £1:40  
110 Semiconductor Projects.  
Marvelous book for the enthusiast: £1:35

## HOW TO ORDER:

Cut out whole advert.  
Tick boxes for packs required.  
Fill out name and address enclose payment.  
ALL ITEMS THIS AD. POST FREE.

PLEASE NOTE: Our "Experimenters Bargain Pack £2."—(Last months ad.) now withdrawn. All orders despatched day of receipt. Spares for all packs in our FREE catalogue.

**LST ELECTRONIC COMPONENTS LTD.,**  
DEPT. E.E.,  
7 COPTFOLD ROAD,  
BRENTWOOD,  
ESSEX.

STOCKISTS-DISTRIBUTORS OF: IR. WELLEN, MULLARD, NEWMARKET, SIEMENS, RCA, ISKRA VEROBOARD, S-DECS, TEXAS, G.E.

FROM:—

NAME .....

ADDRESS .....

ENCLOSED/CASH/CHEQUE/PO. £ : p

PLEASE PRINT CLEARLY TICK BOX → FOR CAT. ONLY



## FIND BURIED TREASURE!

Transistorised Treasure Locator

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phone used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC.** Extremely sensitive, will signal presence of certain objects buried of several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY £2:37 + 27p p. & p. (Sectional handle as illustrated 70p extra). Parts available separately. Made up looks worth £10!

ONLY £2:37

**Eavesdrop on the exciting world of Aircraft Communications**

## V.H.F. AIRCRAFT BAND CONVERTOR

ONLY £2:37  
Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, air-traffic tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency bands including **HEATHROW, GATWICK, LUTON, KINGSWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL.** This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portables). **NO CONNECTIONS WHATSOEVER NEEDED.** SEND ONLY £2:37 + 25p p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

**CONCORD ELECTRONICS LTD. (EE 4) 8 Westbourne Grove, London, W.2. Callers welcome 9 a.m.—6 p.m. inc. Saturday**

## SHORTWAVE

## TRANSISTOR RADIO



only £2:25

Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2". Only £2:25 + 17p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

## INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY £2:75



CAN'T SLEEP? NO NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. SEND £2:75 + 25p p. & p. (parts available separately).

## ELECTRONIC ORGAN

ONLY £2:75

Don't confuse with ordinary electronic organs that simply blow air over mouth-organ type reeds etc. Fully transistorised. **SELF CONTAINED LOUDSPEAKER.** Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering necessary. Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated step-by-step, simple instructions. ONLY £2:75 + 25p p. & p. for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (part available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

## Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY £4:95

FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! £4:95 + 30p cart. etc. (High quality Danish Stethoscope headphones £2:75 extra if required). **EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.**

## BUILD 5 RADIO AND ELECTRONIC PROJECTS

only £1:97

Amazing Radio Construction set! Become a radio expert for £1:97. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 37p extra as illus. (if required) (parts available separately) no soldering necessary. SEND £1:97 + 25p p. & p.

## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHE YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops!—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones. Components, nuts, screws, wire, etc. etc. no soldering. £2:25 + 25p p. & p. Parts available separately



Only £2:25



# everyday electronics

PROJECTS...  
THEORY.....

## BROADMINDED

A word of caution to newcomers. You'll have to be broadminded to read and enjoy this magazine.

Once upon a time the predominant reason for taking up "electronics" as a hobby was an interest in building radio receivers. But, as is now generally appreciated, radio is merely one special application or branch of this all-embracing technology.

The great expansion in uses of electronic circuits over the last two decades has been of untold benefit to the ordinary person. No longer is an interest in one particular specific application the requisite for involvement in the most exciting technology of the age. Electronics is wide open to *all* who want to use it.

## AN ALL-PURPOSE TOOL

This is no exaggeration. The projects for the private constructor already published in these pages should have made this clear. And new readers can be assured that future designs will demonstrate even further how versatile and how useful is the electronic circuit—even in its simplest form.

Electronics is the all-purpose tool everyone can use to add to comfort or convenience at home, or to assist in the greater enjoyment of

other spare time pursuits. Its practical applications know no bounds, and as a mind broadener, we reckon a lively interest in electronics has no equal.

## COMMON GROUND

So it's not surprising that our pages have become a meeting place for a great variety of individuals, including, for example, photographers, motorists, gardeners, and pop musicians; not to mention those legions of handymen whose interests are less specific but who are always ready and eager to seize upon a likely project for use in or around the home. Where else are such diverse interests likely to find common ground?

So if you consider yourself to be broadminded, EVERYDAY ELECTRONICS should suit you. Join the growing band of electronics constructors who have fun building our designs and enjoy the benefits that electronic aids can provide.



Our April issue will be published on Friday, March 17

EDITOR F. E. BENNETT • M. KENWARD • B. W. TERRELL B.Sc.  
ART EDITOR J. D. POUNTNEY • P. A. LOATES • S. W. R. LLOYD  
ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Subscription Rates including postage for one year, to any part of the world, £2.35.  
Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



.....EASY TO CONSTRUCT  
.....SIMPLY EXPLAINED

VOL. 1 NO. 5

MARCH 1972

## CONSTRUCTIONAL PROJECTS

<b>DARKROOM TIMER</b> <i>Get the exposure right</i> by Robert A. Shakleford	246
<b>SIGNAL INJECTOR</b> <i>For testing radios and audio equipment</i> by Alan Jardine	265
<b>SOIL MOISTURE METER</b> <i>Ensures correct watering</i> by D. Bollen	270

## GENERAL FEATURES

<b>EDITORIAL</b>	244
<b>CASES FROM CHASSIS</b> <i>An easy way to make cases</i> by V. S. Evans	251
<b>ELECTRONICS AT SEA</b> <i>Electronics used in ocean going vessels</i> by W. Maconachie	254
<b>TEACH-IN</b> <i>Part 5—Capacitance</i> by Mike Hughes	259
<b>RUMINATIONS</b> by Sensor	264
<b>MEMORY STORE</b> <i>Retrieval</i> by Derek Burn	274
<b>SHOP TALK</b> <i>Construction problems</i> by Mike Kenward	277
<b>READERS LETTERS</b>	278, 281

Approximate cost of components



The approximate cost of components given, for constructional articles, in the box shown opposite is an estimated cost compiled from suppliers current catalogue and advertised prices. Parts for some projects may work out more expensive while others may be cheaper than our quoted price, depending on where the components are purchased.

We would like to point out that we, as publishers, cannot supply kits of parts or individual items for any of the published designs.

**T**HE circuit diagram of a timer which can be used in conjunction with an enlarger to provide stable exposure control is shown in Fig. 1. Stability is achieved by using a tantalum capacitor in the timing circuit and high stability resistors of the metal oxide type could also be used in the timer where extended range coupled with good stability is desired.

### CIRCUIT DESCRIPTION

The delay is achieved by charging the tantalum capacitor C1 through resistor R1. When the voltage across the capacitor exceeds the trigger voltage of the unijunction transistor TR1 the unijunction turns on and C1 discharges rapidly through R3 producing a short pulse of current. This pulse is amplified by TR2 and turns on the silicon controlled rectifier CSR1.

In the off state almost the total d.c. supply voltage is dropped across the relay coil and the

relay is energized. Current may then flow through the load via relay contacts RLA2 while at the same time the other relay contact RLA1 latches the circuit d.c. supply. When CSR1 turns on it short circuits the relay which is de-energized and its contacts return to the normally open state switching off the load supply and also the timer supply.


A timing cycle is initiated by pressing the two-pole push-on/release-of switch. This allows the relay to latch its contacts, switching on the lamp, while at the same time the capacitor has any residual charge on it removed by shorting it to the ground line. When switch S2 is released the capacitor begins to charge and the timing cycle begins. Obviously variations of R1 will vary the rate at which C1 charges and hence vary the delay before the load is turned off.

Switch S3 is provided to allow manual override of the timer to allow focusing and exposure measurement to be carried out.

# DARKROOM TIMER

A variable range timer designed for photographic work but suitable for any application needing a timed range from 0 to 4½ minutes

By Robert A. Shackelford.

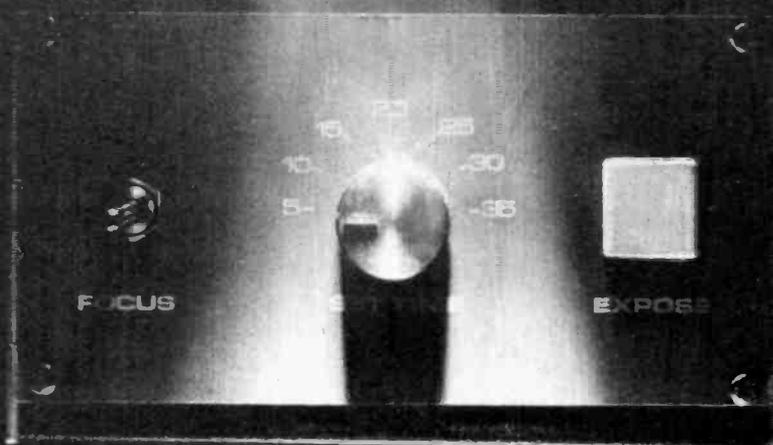




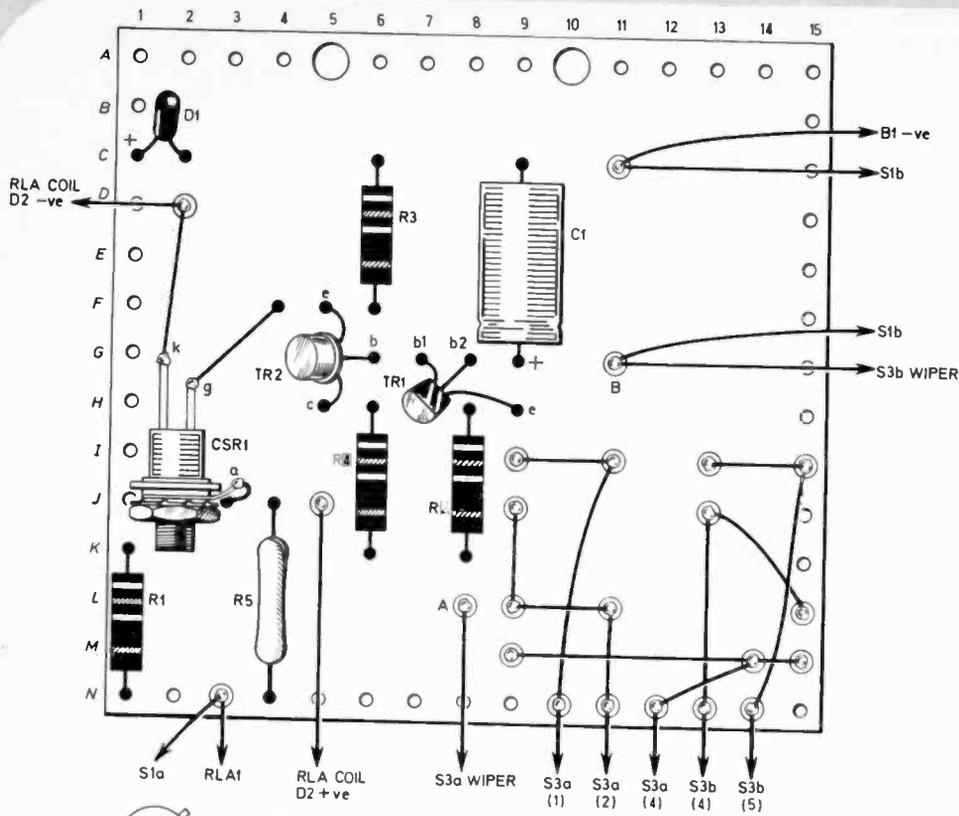


Fig. 3. Layout and wiring of the components mounted on the board. The preset potentiometers are mounted on the underside of the board (shown below) so that they can easily be adjusted.

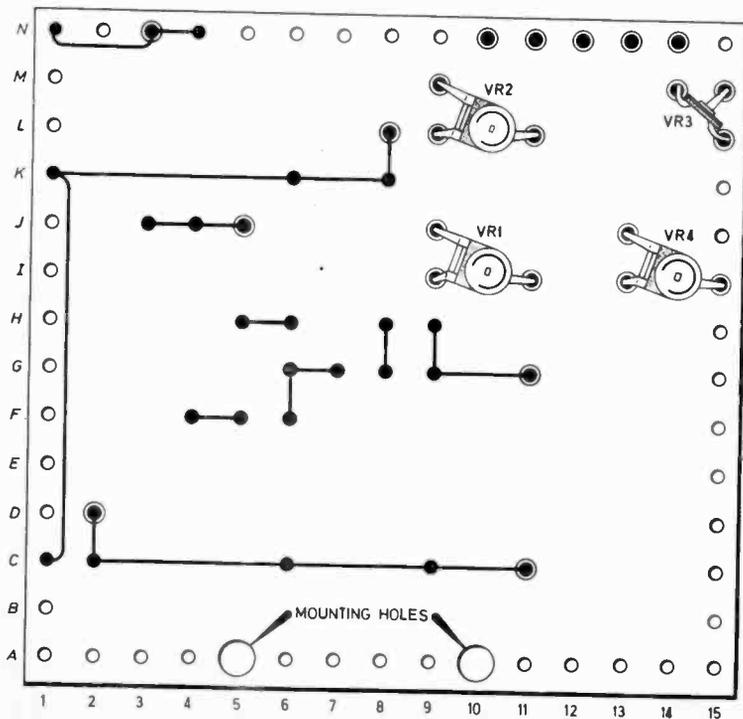

# DARKROOM TIMER



Inside view of the prototype timer.

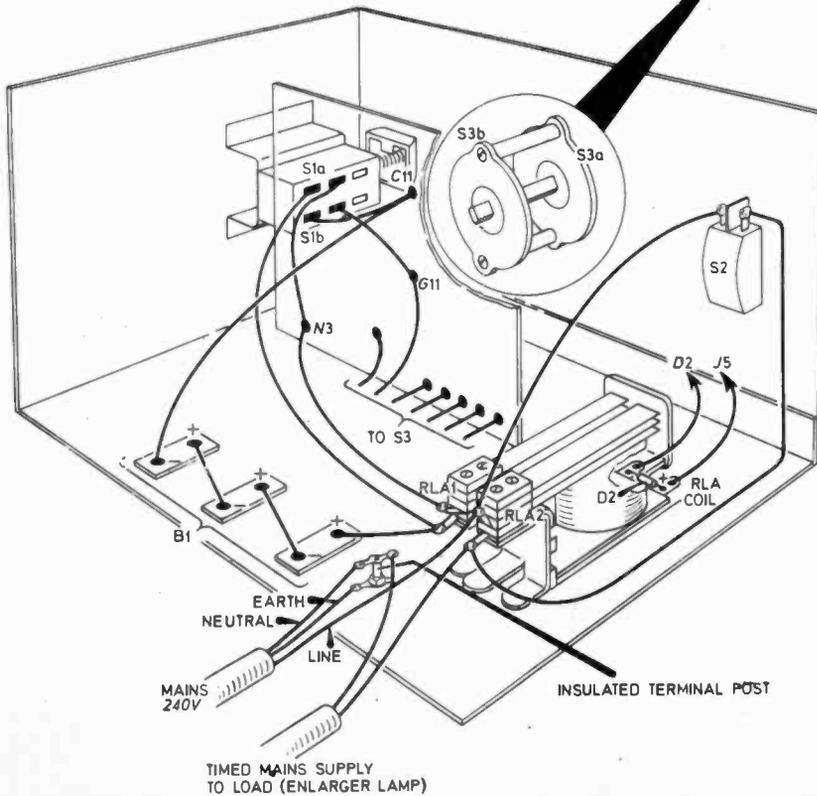
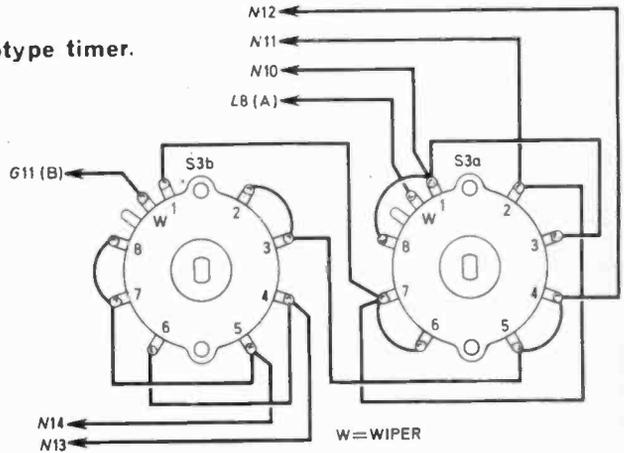
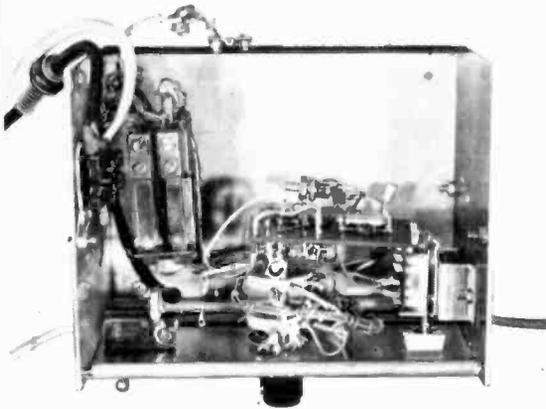


Fig. 4. Layout and wiring of the components mounted in the case; the board has been cut away to show S3 and S1. The board is held by a bracket fixed to S1. Switch S3 has also been shown separately, as it would appear when dismantled, for clarity. The batteries are not shown but their clips are wired up in the approximate positions of the batteries.

# Components....

SEE  
**SHOP  
TALK**

## Resistors

- R1 820 $\Omega$
- R2 220 $\Omega$
- R3 33 $\Omega$
- R4 3.3k $\Omega$
- R5 22 $\Omega$  5 watt wirewound
- All  $\pm 5\%$   $\frac{1}{2}$  watt carbon except where stated.

## Capacitors

- C1 100 $\mu$ F tantalum 12V

## Variable Resistors

- VR1 25k $\Omega$  skeleton preset
  - VR2 50k $\Omega$  skeleton preset
  - VR3 100k $\Omega$  skeleton preset
  - VR4 25k $\Omega$  skeleton preset
- }  $R_t$

## Semiconductors

- D1 ZC12 or similar 12V, 250mW, Zener diode
- TR1 TIS43 unijunction, silicon *npn*
- TR2 C762 or 2N697 silicon *npn*
- CSR1 CRS 3/05 or similar 50V, 3 amp controlled silicon rectifier (thyristor)
- D2 IN914 (or any similar small diode)

## Switches

- S1 2 pole push-on, release-off pushbutton
- S2 single pole single throw toggle
- S3 2 pole 9 way wafer switch

## Miscellaneous

- RLA1 12V 150 $\Omega$  relay having 2 normally open contacts (Keyswitch MK2 or similar)
- B1 PP6 9V batteries—3 off wired in series.
- Aluminium case 6 $\frac{1}{2}$  in x 4 in x 4 in, plain perforated Veroboard 3.2 in x 3 in x 0.2 in matrix, Vero pins to suit board, battery connectors (3 off), insulated terminal post, earth tag, connecting wire, mains lead and plug, knob, 4BA fixings.

of different shapes and sizes and methods of fixing may vary. The only critical parameters are that it should have two normally open contacts and if the unit is to be used for controlling enlarger exposures, the contacts should be suitably rated to carry the lamp current.

Start construction by cutting the board to size and inserting the mounting pins in the positions shown. Connect the pins in the required manner using tinned copper wire and insulating sleeve where required (Fig. 3). Next mount all the components checking the polarity of the capacitors and diodes and the connections to CSR1 and transistors, which should be mounted after the other components and flying leads have been soldered in.

The tantalum capacitor C1 may be either the polarised or non-polarised type and may not be the same shape as that shown in Fig. 3. The correct polarity for polarised types is shown on C1 in Fig. 3.

Once the board is complete and has been checked for wiring errors and dry joints it may be mounted in the chassis, together with the remaining components, and connected up as shown in Fig. 4. Wires to components mounted on the front panel must be left long enough to facilitate removal of the panel for setting up.

Take particular care when wiring the mains to the relay, S2, and the load and make sure that an earthing tag is fitted to the case and connected to the mains earth. The output to the load can be connected directly to the enlarger lamp or terminated in a suitable two-way mains line socket.

## SETTING UP

To set the timer up it is only necessary to remove the front panel to gain access to the preset potentiometer. If a multimeter set to its ohms range is connected across one set of relay contacts (**without the unit connected to the mains supply**) or used on a d.c. volts range to monitor the voltage across the relay coil, then circuit operation will be easily visible, alternatively the unit may be connected to the mains supply and a mains lamp bulb used as the load.

The potentiometers should be set half-way around their tracks and with switch S3 set to the desired time, the circuit triggered by briefly pressing switch S2. The duration of the time delay may then be measured by measuring the time for which the meter pointer is deflected from its initial condition or the lamp is on. The potentiometers may then be adjusted as required and the process repeated until all the desired times are set up.

The front panel can then be designated with the time positions. Once this is complete the unit is ready for use and can be connected to the enlarger lamp and mains supply as required.

□

and provide a mount for S1. Switch S1 is also used to mount the circuit board and thus it determines the layout to a certain extent. The layout given need not be followed exactly and the bracket used to mount the switch and board may be modified to suit the parts used.

The circuitry itself is assembled on plain 0.2 inch matrix Veroboard, using Vero terminal pins and the switches and relay are mounted on the front panel and floor of the case respectively. The case is earthed to the main supply through a 3 core mains lead and plug.

Battery B1 is made of three PP6 9V types wired in series; the type and quantity of batteries are determined exclusively by the relay voltage and current requirements.

Mounting of the relay has been left to the individual, as there are so many on the market

# CASES

## from CHASSIS

by V.S. Evans

### An inexpensive case for your projects, using aluminium chassis

**H**AVING decided to build an electronic project—perhaps to your own design, or maybe partly so, early consideration should be given to the form of its eventual housing.


This may well be an important factor in deciding the size of the circuit board, control panel, or even method of construction and assembly.

#### HOME BUILT AND READY MADE CASES

Making a neat and presentable cabinet in wood or metal can be quite a problem, and usually requires the use of special tools and skills and takes some time and patience. The alternative is to use or adapt something already made up to the approximate size required.

Instrument cases and die cast boxes can of course be purchased, although a bit expensive, but are excellent for high class permanent projects.

**Fig. 1.** Front panel is attached to the chassis by means of four self-tapping screws through the flanges

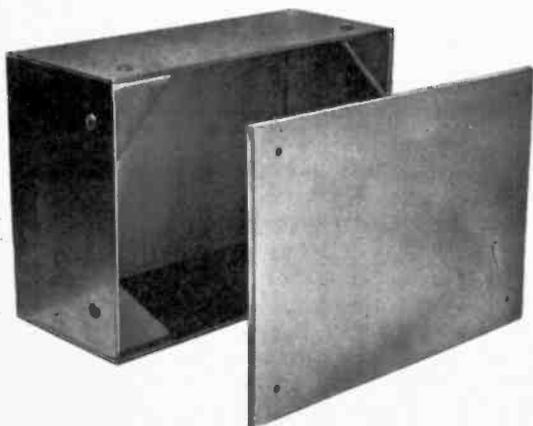

#### ALUMINIUM CHASSIS


For less exacting or experimental projects use can be made of the considerably cheaper aluminium chassis available by fitting a panel of Paxolin, Formica or Perspex to the open side and using this as the front and control panel.

This panel is made to fit the aluminium chassis such that it rests on the corner flanges of the chassis, Fig. 1 which are slightly recessed, so that quite a neat job results. Small self-tapping metal screws are used to fix the panel to the flanges.

#### RE-USABLE

If the project is one of a temporary nature, or maybe a prototype which may well be dismantled and re-built, it is as well that the metal case itself (the chassis), is left untouched, i.e. no holes or metal cut-outs are made. This way your case will serve again and again and need

**Fig. 2.** The Circuit board is fixed to the front panel by four bolts and spacer nuts.

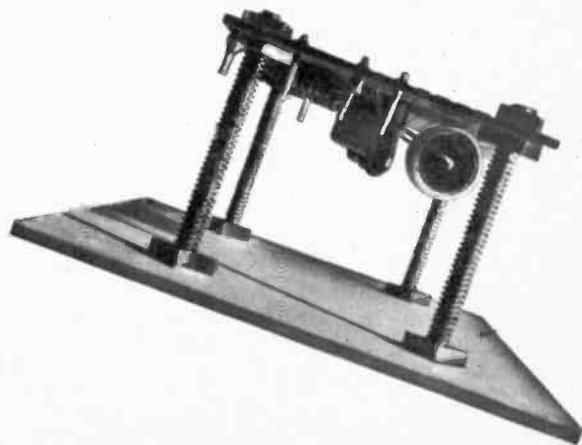

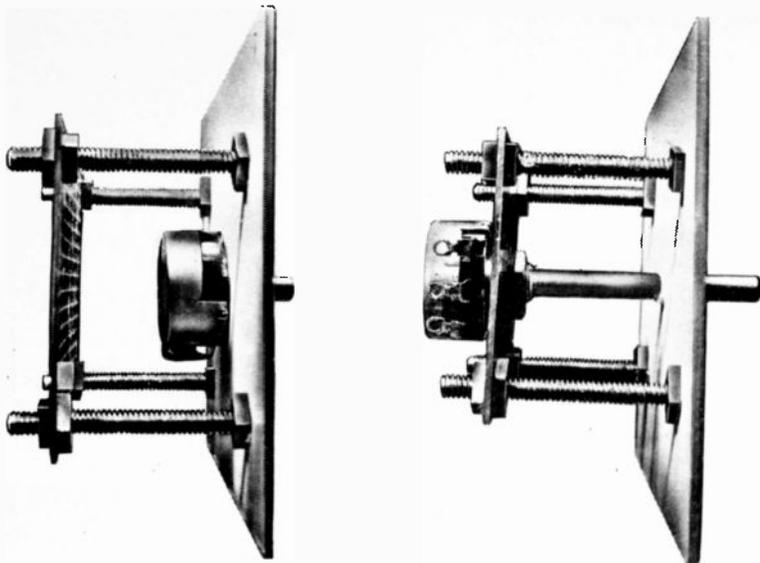


Fig. 3 (a) (left) Fixing the potentiometer to the front panel if there is not enough space on the component board.

Fig. 3 (b) (right). Alternative method for potentiometer fixing.

never be discarded as being full of unwanted holes.

### COMPONENTS ATTACHED TO PANEL

To avoid "mutilating" the case, all controls and the component board etc. are mounted on, or attached to, the front panel. This leaves considerable scope for the constructors ingenuity. Fig. 2, shows how the circuit board can be attached to the back of the panel with 4 bolts of suitable length. Spacing sleeves or nuts being used to hold the board at a "distance." Remember to make allowance for corner flanges of the chassis when designing the dimensions of component board.

Controls such as variable potentiometers and variable capacitors can be mounted on the cir-

cuit board with their spindles protruding through holes drilled in the panel or they can be mounted directly onto the front panel as in Figs. 3(a) and (b).

### USING BRACKETS

An alternative method can be employed where the circuit board is attached vertically or horizontally to the panel with small angle brackets. This method would be used where the panel is carrying something bulky such as a meter or multiple wafer switch. Angle brackets may also be used to attach a metal heat sink carrying a power transistor, or, say a horizontal deck to support a mains transformer Fig. 4. If a small loudspeaker is involved this can also be mounted on the panel—the fret being simply a symmetrical pattern of holes drilled in the panel opposite the loudspeaker cone, Fig. 5.

By using a combination of these various ways to attach everything to the front panel, the case can be left virtually "untouched". Panels made from Formica offcuts are cheap, easily cut with a scribe and metal straight-edge, and can be regarded as expendable.

### HOLES AND SLOTS

Although it is still necessary to cut holes and slots in the panel for mounting such things as meters, slide switches, etc., it is considerably easier with formica because in most instances the hole or slot can usually be deeply scribed with a scribe and then pushed out. It may then be necessary to "clean up" the hole with a small file. Small holes should be drilled in the usual way.

With Paxolin and Perspex it is slightly more difficult. The usual method for making a large circular hole is to drill around the circumference

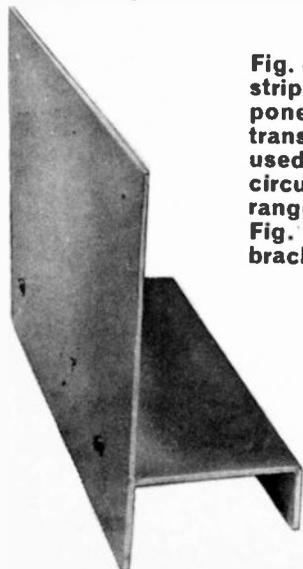


Fig. 4. Using a metal angle strip to support heavy components such as mains transformers. This can be used in conjunction with circuit board fixing arrangement as shown in Fig. 2. or with angle brackets.

of the hole to be removed and then clean up with a file, this takes some time. There are special tools on the market for this—a tank cutter and a disc cutting saw. Both of these fit into drills but they tend to be costly.

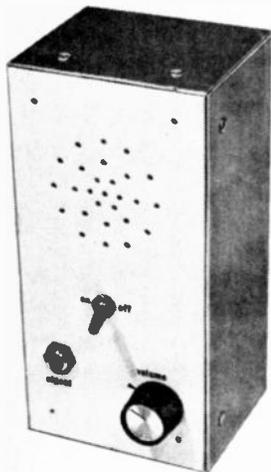


Fig. 5. A completed case of a small amplifier showing holes drilled for loudspeaker

### FINISHING AND LETTERING



With Formica and Perspex panels there is no finishing required as these are available in a variety of colours with excellent finishes.

With Paxolin, however, its finish is smooth but it is only available in a brown colour which looks ugly. This can be sprayed to the colour of choice using any of the aerosol sprays on the market or even painting with a paintbrush will do. It is best to try the paint on an offcut first to make sure that the Paxolin is not affected by the paint.

As far as labelling the control panel, Letraset is by far the best method, adding a touch of professionalism. All three of the panel materials mentioned above readily accept Letraset.

To prevent the labels from being scratched off it is necessary to cover them with varnish, Letracote Gloss is ideal for this job as it protects the lettering and gives the panel a gloss finish. The whole panel can be sprayed or just the regions of lettering as preferred. □

Fig. 6. Various sizes and shapes of available chassis.

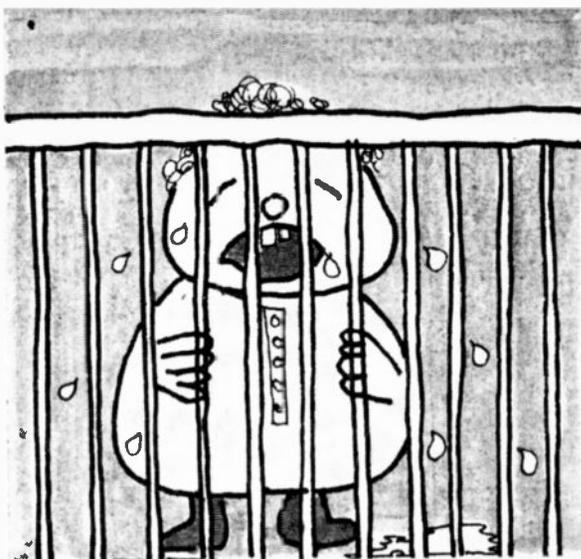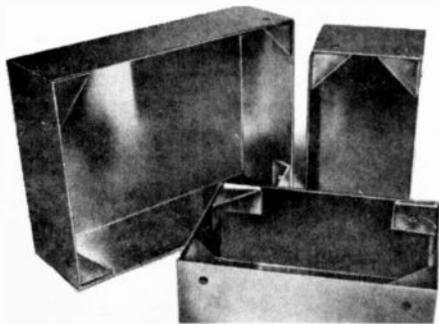

## Baby Alarm


Keep a check on the kids while you watch T.V. Simple to construct and easy to install, this device gives you peace of mind



## Simple Calculator

Teaching aid for multiplication or can be used for quick calculations

## Power Supply Unit

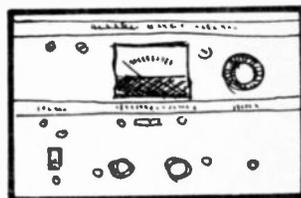

Just right for testing low voltage circuits

## All in the April issue of



on sale  
Friday,  
March 17

**W**HEN the young Marconi demonstrated his wireless apparatus by sending a transmission over a distance of less than two miles on Salisbury Plain in 1896, there were many eminent scientists of the day who dismissed the novelty as a toy; and many who firmly believed that wireless waves would be diverted or distorted by hills. As for the possibility of transmitting across water—why, the very suggestion was ridiculous in the extreme. Everyone knew that the wireless waves needed a return path through the earth. Besides, water would absorb the wireless energy like blotting paper.

### **NO LIMIT**

Marconi confounded these opinions on 11th May, 1897, when he carried out a successful transmission from Lavernock Point, near Penarth, to the island of Flat Holm in the Bristol Channel—a distance of three and a half miles. Though some doubters still stuck to their guns, this was hailed as a tremendous scientific achievement, and when a week later he succeeded in sending a message over a distance of nine miles across water, right across the Bristol Channel to Brean Down in Somerset, scientific enthusiasm was such that there were those who claimed that there was no limit to what could now be achieved with sufficiently high-power apparatus.

No limit, indeed. Within four years Marconi had sent his transmissions across the Atlantic from Poldhu in Cornwall to Signal Hill in Newfoundland; and to-day, no more than a lifespan since the time when the young man first arrived in England, ships at sea can communicate daily

by Morse or speech with stations right across the world, and even modest 75-watt radiotelephone sets such as those used by Sir Francis Chichester, Robin Knox-Johnson, and Chay Blyth can carry their words across 5,000 miles of ocean. Moreover, during that lifespan, like strong branches from the main trunk of pure communication, have sprung electronic aids to navigation and safety in the shape of direction-finding, echo sounding and radar.

Electronics now contribute to efficient commercial ship operation as intercommunication systems, hyperbolic position-fixing systems, closed-circuit television, automatic steering equipment, data loggers, and automatic systems using intricate computer techniques. One must, in fact, have the thought in mind that between the time that this article is written and the date of its appearance in print some new technique or application may be evolved and announced. Such is the rate of acceleration in the marine electronics industry.

### **RADIO AND ELECTRONICS**

Except for the periods immediately after the two world wars, it is during the past few years that this expansion of the use of electronics at sea has been most marked. This is pointed by the fact that in April, 1968, the title of the Radio Officers Union was officially changed to the Radio and Electronic Officers Union, while a number of companies now give extended training to their radio officers to bring them up to the rank of electronics officers. Indeed, even before the last war the responsibilities of the Merchant Navy radio officer—the traditional

# **Electronics**

## **Ocean-Going Vessels**

"sparks"—usually went well beyond the operation and maintenance of his communication station and included the maintenance—and sometimes the operation into the bargain—of echo sounders and direction-finders. Of course, in more recent times he has also become responsible for the maintenance of radar, intercommunication and sound distribution networks, closed-circuit TV for navigation or entertainment purposes, data logging equipment, communal aerial systems, etc.

With the increasing use of automation at sea, and its dependence on electronics for much of its primary control and transmission of data and instructions, a ship's electronics installations are becoming much more complex from day to day and there is even talk—although it is still only talk—of the possibility of sending ships to sea without a crew at all. One wonders—is there indeed no limit?

But that is still in the future. At this moment the use of electronics on board ship is sufficiently considerable to be interesting. Ships' electronic installations naturally differ according to their needs which, of course, are dictated in part by international regulation and also by

**The Lavernock and Brean Down experiments, May 1897, showing the method by which an increase in distance from three miles to eight miles was obtained. For these experiments kites covered with tin foil were used as aerials.**

**The control room and studio of the comprehensive television installation on board a cruise liner which distributes a choice of four programmes to more than 400 receivers in the ship's cabins and public rooms.**

**Navigational CCTV on a container ship in the Manchester Ship Canal clearly shows the forward tug which would otherwise be completely invisible to the officers on the bridge.**

# at Sea

**By W. Machonachie**

*Everyday Electronics, March 1972*



the type of service in which they are engaged. There is thus no "typical" merchant ship installation although regulations lay down the minimum equipment to be carried by four classes of merchant ship and also by fishing vessels.

## SHIP CLASSIFICATION

The classification of ships as set out in the Merchant Shipping (Radio) Rules is, as might be expected in an official document, a little on the wordy side, but briefly summarised, Class I ships are those carrying more than 250 passengers on voyages of more than 16 hours duration. Class II covers passenger ships not in Class I and all cargo ships of 1600 tons or more. Cargo ships of 500 tons upwards but less than 1600 tons are Class III, and those of 300 tons and more but less than 500 tons constitute Class IV. The rules are not applied to sailing ships, pleasure yachts, or ships smaller than 300 tons, while fishing vessels have their own regulations.

Although there is therefore no typical merchant ship installation it is possible to define fairly accurately a typical installation for a type or class of ship. One of the most common ocean-going ships is the cargo liner, carrying general cargo on a regular service run—say from Southampton to Cape Town. She may carry up to twelve passengers, but is not classified as a passenger ship, and so far as her electronic equipment is concerned she can in broad terms be equated with the refrigerated meat or fruit carrier, or with the container ship, oil tanker, or bulk cargo carrier. All these ships run on international voyages and their electronics must cater primarily for the communication needs of their crews and owners and for the safe, economical and efficient running of the ships and their cargoes.

## STATUTORY REQUIREMENTS

This type of ship—general cargo, tanker, bulk carrier, etc.—whether she be 1600 tons or 300,000 tons, must be equipped to a minimum standard before she is allowed to leave port. The mandatory requirement is for a wireless telegraphy installation capable of both main and emergency operation; an automatic alarm receiver, unless she carries enough radio officers to maintain a continuous human watch; a direction-finder; a portable transmitter/receiver for emergency use in a lifeboat. All this equipment must be of an officially approved nature, and her crew must include at least one qualified radio officer. Her wireless telegraphy installation has to comprise a main transmitter and separate receiver, both powered from ship's

The electronics officer of a cargo liner with the data logger which monitors 350 performance points in the main and auxiliary machinery, the refrigeration plant, and in the cold cargo space.

mains, as well as an emergency or reserve transmitter and a reserve receiver which derive their power from batteries so that they can be operative in the event of a failure of the mains supply.


The installation must also include a watch-keeping receiver, fitted with a loudspeaker, and capable of reception in the 500kHz band, and an automatic keying device which can be made to operate either the main or the reserve transmitter in case of emergency and cause them to transmit the auto-alarm signal.

This the statutory minimum for Class II ships, which includes some of the largest vessels afloat today, may not seem to comprise a very sophisticated installation. There is, for instance, no compulsion to carry radar—at the present moment. In practice, however, only a very few ships nowadays carry no more than will satisfy the law.
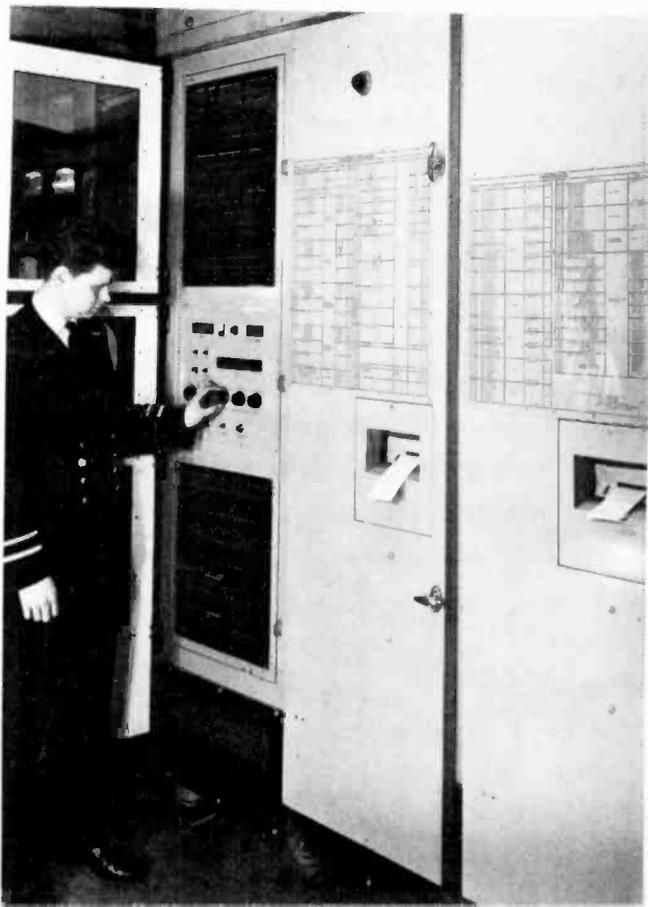
## NORMAL INSTALLATION

Walk aboard an ocean-going ship and you will almost certainly find at least one radar set on the bridge. Indeed, many now fit two radars, with interswitching arrangements so that units are in effect interchangeable if either set should suffer a breakdown.

In the wheelhouse you will also see an echosounder, or perhaps two—one recording and the other of the visual indicating type. Her direction-finder will probably be fully automatic, and both this and the radar will be coupled to the gyro-



compass. Moreover, the direction-finder may now be linked with the auto-alarm receiver so that if an auto-alarm signal, preceding the distress call, is received while the radio officer is not on watch, the direction-finder will automatically take a bearing on the distress position.

Our Class II ship will almost certainly have a v.h.f. radiotelephone for short-range speech communication with port facilities such as pilots, tugs, and harbourmasters, and this may have remote control extension units in both wings of the bridge and also in the radio office. The wheel-house will contain the master control panel of a crew-call and talk-back system providing internal two-way communication with working areas on and below decks and with loudhailing facilities as well, while an internal telephone network will also be provided.

Loudspeakers in crew quarters will be accessible to the crew-call system and will also be linked to a broadcast receiver and amplifier installation to enable personnel to listen to news and entertainment during their off-duty times. Outlet points from a communal aerial system will be fitted in crew's cabins so that they can use their own personal broadcast receivers if they wish. Broadcast radio entertainment is not all that ships' crews can enjoy at sea—television programmes, too, can be watched through the provision of multi-standard receivers which more and more ships are fitting as permanent installations in crew's and officer's mess-rooms.

## **CCTV AND ELECTRONIC MONITORING**

On many large passenger liners today television is a "must" and an installation can be a very comprehensive one indeed, with hundreds of receivers or monitors in public rooms and cabins, offering a choice of four programmes or more. Such a system will be a combination of closed-circuit and off-air TV, taking the latter when within range of suitable shore transmissions and also generating its own on-board programmes with telecine, videotape, and from the ship's own studio and cameras.

Closed-circuit television has another marine application. If the ship is a large oil-tanker, bulk carrier or container vessel with the bridge aft and perhaps as much as 1,000 feet distant from the bows, she may well have a CCTV installation for navigational purposes. In such an installation the TV camera is mounted in the bows or up on the foremast and a monitor is fitted in the wheel-house to give her officers a close-up view of objects immediately ahead which would otherwise be obscured from human-eye observation. Provided with a remote-controlled steerable camera and facilities for measuring the range and bearing of buoys, tugs, or other comparatively small objects close ahead of the ship, such a system can be invaluable when a very large vessel has to manoeuvre in restricted or busy waterways or has to negotiate canal locks and dock entrances.

Again, CCTV cameras are sometimes used to observe machinery operation in the engine room, where a different kind of electronic watchkeeper in the form of a data logger is often used to monitor hundreds of points of main engine and auxiliaries performance, such as oil pressures, fuel flow, temperatures of bearings and fluids, as well as temperatures and humidity levels in cargo holds and cold stores—in fact, any data which have to be checked regularly.

Data loggers or alarm monitoring systems of this kind are capable of producing a complete check on 400 parameters, with comparisons and off-limits alarm warnings, every three minutes, and will produce an instant readout on demand. The same round of tasks laboriously performed by human agency would keep several men fully occupied for a complete day's work.

## **SATELLITE AND HYPERBOLIC NAVIGATION SYSTEM**

So far in use on only a very few ships is a system of navigation, or more properly position-finding, which derives information from four United States Navy satellites in polar orbit. These circle the earth every 108 minutes at an altitude of 600 miles, passing over the North and

**The electronics officer of a transatlantic cargo liner using the facsimile weather chart receiver and recorder on the bridge.**



South Poles, and broadcasting signals which announce their position every two minutes. The special shipborne observation equipment comprises a receiver, a data handler and a teleprinter. The system operates by measuring the Doppler effect variations in the broadcast frequency received from each satellite as it passes, but the shipboard installation is costly and cumbersome and the system is at present in use on only one or two high-prestige ships.

In much more common use are the Decca and Loran hyperbolic position-fixing systems which require only relatively simple and inexpensive receiving and metering equipment on board ships that wish to use them. Decca is very accurate but is relatively short-range and global coverage would therefore require a considerable number of shore station "chains." Loran, perhaps less accurate, will operate over greater distances from the shore transmitters, but so far serves only about one-fifth of the globe with more than 100 shore stations. The system of this type which appears to hold most promise is Omega, the v.l.f. hyperbolic system first developed for United States military use and since made available to commercial ships and aircraft. With four shore stations now in operation, transmitting on 10.2 kHz and 13.6kHz. Omega will later give complete global coverage with a total of eight shore stations.

## WEATHER CHARTS

It goes without saying that knowledge of the weather conditions that lie ahead of a ship is of the greatest value, not only from the point of view of safety, but also because any delay in a voyage is nowadays a very expensive business. Weather forecasts and ice warnings have been a regular feature of international and maritime radio communications for many years—indeed, the *Titanic* received a number of warnings of ice before she struck the fatal berg.

Until a few years ago ships at sea had to rely on the reception of very lengthy coded morse

**A typical communications console in the radio room of a modern passenger vessel. The two s.s.b. main transmitters are not visible in this picture.**



broadcasts for their advance weather information. On board ship this involved the time-consuming and laborious task of decoding each transmission after the radio officer had copied it down, and then transferring the verbal information into symbols and figures on a chart, always with the possibility of error. Today some thirty weather facsimile transmitting stations have been established throughout the world by the World Meteorological Organisation, and these broadcast synoptic charts at regular scheduled times. These charts, compiled by the meteorologists and complete with all isobars and symbols, may be received in full facsimile by any suitably equipped ship, free of charge.

The suitable equipment consists only of a special receiver covering 51 spot frequencies and combined with a facsimile chart recorder which produces a permanent image of the chart printed in black or brown on white paper.

## MANDATORY—THE MINIMUM

It will be seen that in the majority of well-run ships the mandatory requirement is regarded as the minimum, and any or all of the additional aids we have discussed may also be found in use on board ships for which they are suited.

Large passenger vessels may be expected to carry a wider range of equipment, sometimes with duplicated communications installations, while in such ships high-frequency long-range radiotelephony, nowadays using single-sideband, is the rule rather than the exception. Indeed, many cargo ships also make considerable use of high frequency radio telephone, and some passenger ships and tankers are now fitted with high-speed automatic transmission and reception with automatic error-correcting facilities and teleprinters linked into the shore Telex system.

So far this article has dealt only with the electronics usage of ocean-going ships. Electronics are just as useful to smaller vessels and fishing trawlers, and the types of equipment they employ and the ways in which they use them will be reviewed in a later article. □

### Acknowledgement

Photographs kindly provided by The Marconi International Marine Co., Ltd.





ELECTRONIC CIRCUITS -  
..... IN THEORY and PRACTICE

# TEACH-IN

## ... FOR BEGINNERS

By Mike Hughes M.A.

### 5 CAPACITANCE

**T**HIS month we are going to introduce another very important electronic component, the "capacitor", but first of all let's look at the principle behind it. To do this we will revert to our simple water analogy.

#### CAPACITY AND CHARGE

There is no need to have a complete circuit to ensure water flow—we could, for example, have used a hose pipe connected to a source of pressure to fill a bucket. Taking this a little bit further if we used a pump that was only capable of producing a pressure equivalent to 30ft of water and we started to pump water into the bottom of a 40ft reservoir tank the initial rate of flow would be large and limited only by the resistance of the hose pipe. As the tank filled, the "back pressure" would cause the flow rate to fall and would stop altogether when the level of water in the tank reached 30ft.


By closing the tap at the inlet of the tank we could take away the pump and hold the water in the tank as "stored energy". By opening the tap the water would flow out at a rate governed only by the resistance of the pipe and the water level in the tank. As the level falls the flow rate reduces until the tank is empty.

We have already defined the electronic analogues of pressure, resistance and flow rate, but we must now introduce a fourth parameter—the quantity of water stored in the tank. In electronic terms we call this the "charge". The water tank is equivalent to the capacitor which has the capacity to hold a given charge.

#### THE CAPACITOR

In its simplest form a capacitor is two plates of metal separated by a very small distance, see Fig. 1. Connecting a battery in series with a resistor across these plates will cause electrons to be pulled away from the plate connected to the positive terminal and "push"

Fig. 1. Schematic diagram of capacitor being charged.

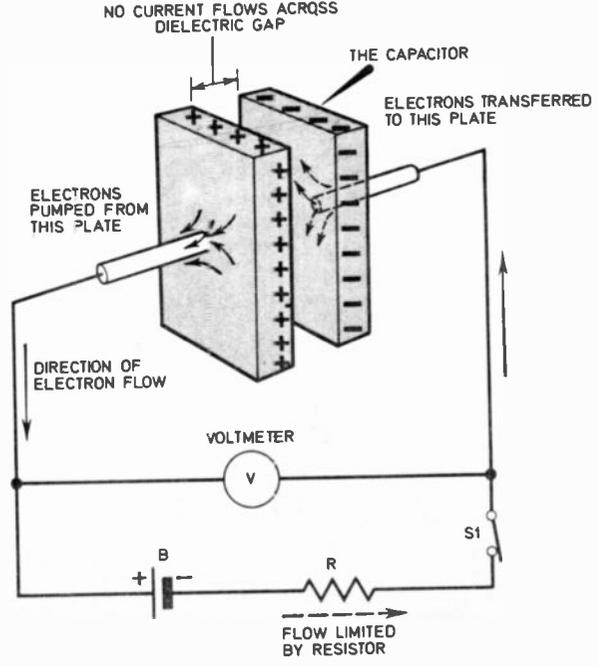

them through the resistor to the other plate.

Initially the rate of flow will be limited only by the resistor but as the electrons leave one plate so it will start to show a positive potential with respect to the other. This potential difference will build up as time progresses and slow down the flow rate—just like the pump, hosepipe and tank. Eventually the potential across the capacitor will equal that of the battery and flow will stop.

By observing a voltmeter connected across the capacitor you could see this happening; this will be shown experimentally later. Opening the switch in Fig. 1 is just like turning off the tap and removing the pump. The charge of electrons will stay on the right hand plate and the potential difference will be maintained as shown on the meter. When we do this in practice you will see that the charge leaks away through the resistance of the voltmeter.

By connecting a resistor across the capacitor as in Fig. 2 we can deliberately make the electrons regain their original equilibrium. Initially the flow rate will be high but will get less and less until the capacitor is discharged and the current stops flowing. In principle that is all a capacitor does in any circuit.

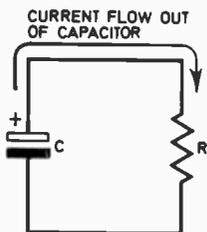


Fig. 2. Capacitor discharging through a resistor.

## DEFINITIONS AND UNITS

Electronic charge is measured in units called coulombs. One coulomb is defined as the number of electrons that flow past a given point in a wire when a current of one ampere flows for one second.

Capacitance is measured in Farads. A capacitor has a capacitance of one Farad when, if it has been charged with one coulomb of electricity, produces a potential difference of one volt across the plates of the capacitor.

This can be represented mathematically by

$$C = \frac{Q}{V}$$

where  $C$  is the capacitance measured in Farads

$Q$  is the charge on the plates

and  $V$  is the potential difference across the plates produced by the existence of  $Q$ .

To obtain a charge of one coulomb we would have to have a current of one ampere flowing for one second. This is a very high current in electronic terms and we only experience it in very high power circuits. Thus it should seem fairly logical that values of capacitance we

encounter should be very much less than one Farad.

Usually we deal with millionths of Farads—microfarads ( $\mu\text{F}$ ), thousandths of millionths—nanofarads ( $\text{nF}$ ) and billionths—picofarads ( $\text{pF}$ ).

## CAPACITOR TYPES

Unlike resistors there is a much wider choice of differing styles of capacitor of both the fixed and variable type. Their circuit symbols are given in Fig. 3.

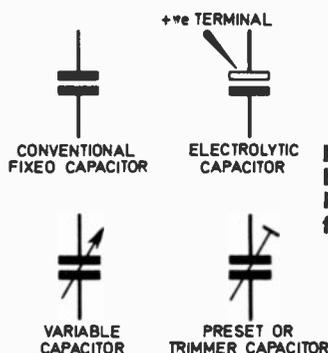


Fig. 3. Circuit symbols used for different kinds of capacitors fixed and variable.

It has always been a battle to obtain large values of capacitance in a small physical size because the phenomena that causes it is purely geometric—the area and separation of the two plates. If the distance between the plates is decreased, the capacitance increases, but by bringing the plates closer together (in most cases less than a thousandth of an inch) we have to introduce a spacer material—the “dielectric”.

The dielectric itself can help increase capacitance but we immediately encounter another problem (except for very expensive dielectric materials), that these materials that enhance capacitance, very often exhibit poor insulation properties. If we used a very poor insulator as a dielectric any charge stored would leak away within the capacitor itself. We would say the capacitor was “leaky”.

Some dielectrics will not withstand high voltages across them particularly when they are very thin.

## ELECTROLYTIC

Some very effective dielectrics are in the form of a paste where the initial flow of current through the initially “leaky” capacitor produces an electro-chemical reaction that actually forms an insulator. Capacitors which use this form of dielectric are called “electrolytic”, and they exhibit polarity properties (i.e. the capacitor can only be connected into circuit one way round). We usually turn to this type of capacitor when very high values of capacitance are required. They come in all shapes, sizes and working voltages.

Different types of capacitor are usually described by the type of dielectric and Fig. 4 shows some of the more important ones.

### SILVER MICA AND POLYSTYRENE

Provided they are obtained from a respectable source, leakage is not usually a problem—this is well taken care of in manufacture. Nevertheless, the best type to use when this is the controlling parameter is the silver mica type. These are limited to low values of capacitance from 1pF up to 10,000pF; the higher values in the range tend to be rather expensive. They can operate up to about 300V but individual manufacturers types might differ widely.

Polystyrene capacitors have a similar range of capacity and are usually available at different voltage workings—typically from 30V to 500V. While they are not as effective as silver mica types in all applications, they are nevertheless very good insulation wise, and are a little cheaper.

### CERAMIC AND POLYESTER

Ceramic dielectric devices also have a similar range of values and working voltages but sometimes are available with wider tolerances (this makes them cheaper) and some types are very sensitive to changes of temperature—this can be a useful or bad thing depending on the application.

Perhaps the most used by the amateur today is the polyester device. These start in value at about 0.01 $\mu$ F (10,000pF) and go up to 1 $\mu$ F with voltage ranges of from 50 to 300V. Overlapping this range and going up to about 5 $\mu$ F are polycarbonate types that are a little more expensive than polyester.

### TANTALUM

For miniaturisation and high capacitance one can turn to solid Tantalum types. These are fairly new on the amateur scene and are inexpensive. These types have a very low leak-

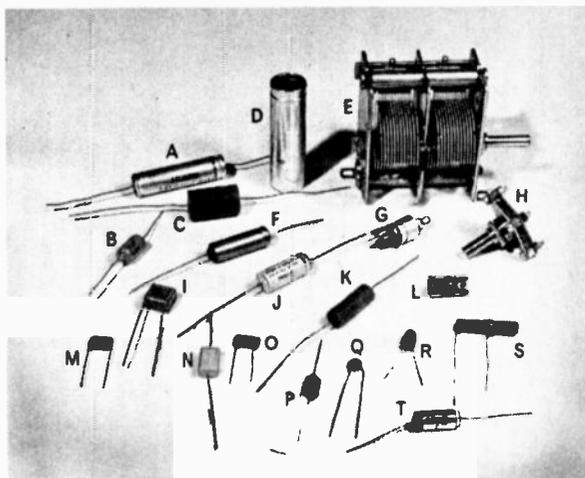


Fig. 4. Shown above is a variety of common capacitor types: A paper; B polyester; C tubular metallised polyester; D electrolytic can-type; E ganged variable; F electrolytic; G beehive trimmer (concentric); H variable; I metallised polyester; J paper dielectric; K tubular mixed dielectric; L trimmer (compression); M and N metallised polyester; O silver mica (printed circuit type), P silver mica; Q disc ceramic; R tantalum; S high voltage (pulse) ceramic; T polystyrene.

### TOLERANCE

A word about tolerance values. Like all components, capacitors have tolerances which usually vary from one type to another. Generally, silver mica types are within  $\pm 1$  per cent and have their values printed on them. Polystyrene can range from  $\pm 2$  to  $\pm 10$  per cent and also have printed values; likewise with ceramics but the tolerance can be as high as  $\pm 20$  per cent. Polyester types are usually  $\pm 20$  per cent but values are frequently put on them in colour code form. The code is exactly the same as for resistors except that the values are in units of picofarads (pF), see Fig. 5. Polycarbonate types are similar but values are usually printed.

Electrolytics are usually used where tolerancing is not very important and one requires "at least" a certain value. They generally have tolerances of +100 to -25 per cent. Invariably they have values printed on them.

### VARIABLE CAPACITORS

Variable capacitors are limited to comparatively low values—typically up to 500pF. Their most usual application is for tuning radios and this range of values is ideal. The most frequent type encountered uses an air dielectric and has a number of interleaved plates (to increase the total surface area). One set of plates is attached to a spindle and they can be moved relative to a fixed set. The shape of the vanes is designed so that in the radio tuning application the fre-

Table 1: COMPARISON OF DIFFERENT CAPACITOR TYPES

Type	Capacitance Range	Working Voltage	Tolerance
Silver Mica	1—10,000pF	Typically 300V	$\pm 1, \pm 2\%$
Polystyrene	10—10,000pF	30—500V	$\pm 2, \pm 10\%$
Ceramic	50—10,000pF	30—500V	$\pm 20\%$
Polyester	0.01—1 $\mu$ F	50—300V	$\pm 20\%$
Polycarbonate	0.01—5 $\mu$ F	50—600V	$\pm 20\%$
Solid			
tantalum	0.02—270 $\mu$ F	6—100V	$\pm 20\%$
Electrolytic	1—20,000 $\mu$ F	10—600V	-25 to +100%

age current—typically 0.02 microamp per microfarad volt. Available values range from 0.022 $\mu$ F to 270 $\mu$ F with working voltages generally from 100 to 60V respectively.

See Table 1 for a comparison of types.

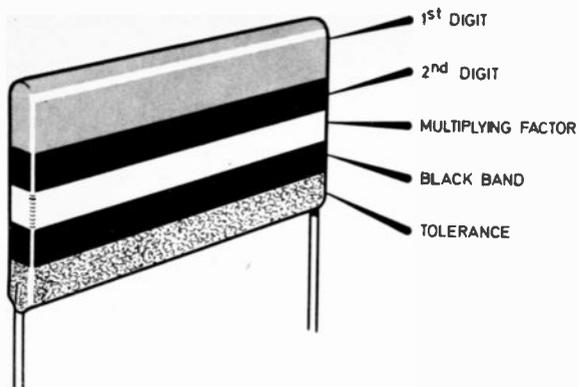


Fig. 5. An example of the capacitor colour code.

quency of the tuned signal varies in direct proportion to the degree of rotation.

As with resistors it is sometimes impossible to rely on manufacturing tolerances and preset trimmer types are required. These can be of the compressional type where the gap between two plates is adjusted with a screw, or the concentric type where one cylinder is made to slide over another thus varying the effective surface area of overlap. Values of trimmers are very low and rarely exceed 150pF.

### EXPERIMENT 1

We shall now demonstrate the function of capacitors on the Demo Deck. For this we shall use one that will come in handy later. Ideally we specify an electrolytic with a high value, 500 $\mu$ F at 25V. Provided you have one in the range 250 to 1,000 $\mu$ F and its working voltage is in excess of 12V it will do.

The circuit diagram and layout on the Demo Deck for this experiment is shown in Figs. 6(a) and (b).

First make a 10V range voltmeter by using a 10 kilohm resistor in series with the 1mA meter. Make two flying leads that have crocodile clips on their ends and attach the ends without clips to your voltmeter—make sure you know which one is going to the positive terminal. Now solder the capacitor across any pair of turret tags—identify the terminal of the capacitor (identified with a + sign or a red spot at this end). Solder a 10 kilohm resistor to the positive end of the capacitor and attach its free end to another tag. Now connect a flying lead to the negative end of the capacitor and take it to the negative terminal of the 9V battery.

Similarly connect a flying lead to the free end of the resistor but leave the other end of the lead free for the time being. Now use the crocodile clips to connect the voltmeter across the capacitor—positive lead to the positive end.

### OBSERVATIONS

Initially nothing should show on the meter. Now connect the free wire from the resistor to the positive terminal of the battery. This connection acts as S1 in the circuit diagram. The

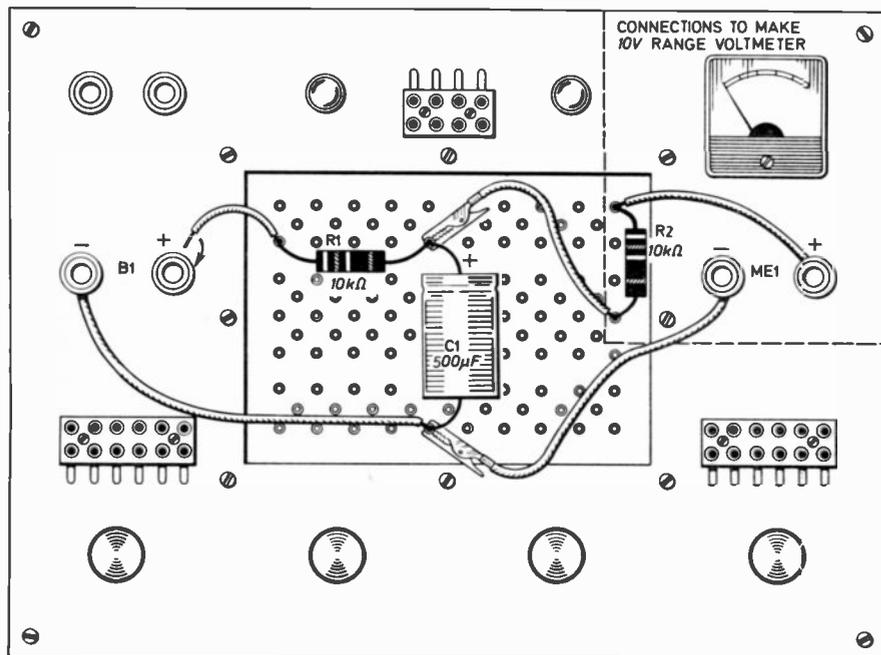
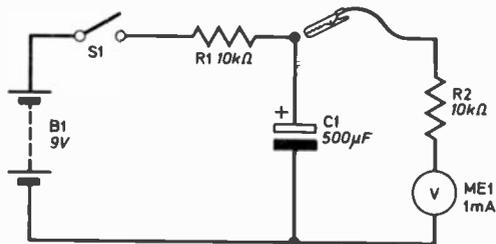


Fig. 6(a) (above). The circuit diagram for experiment 1.

Fig. 6(b) (left). The circuit wired up on the Demo Deck.

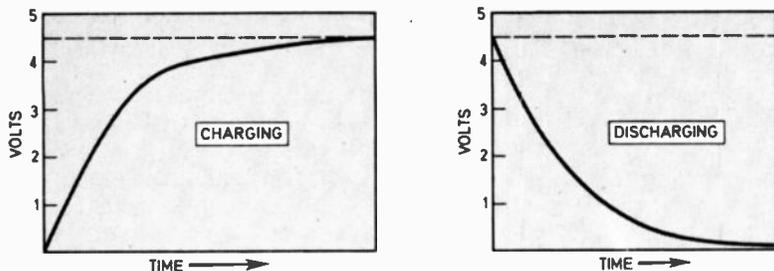


Fig. 7. Typical charge and discharge curves for a capacitor. Similar curves should be obtained from the results of experiment 1.

voltage across the capacitor will start to rise—fast at first, due to the high current flow—but the rate of rise will get less and less until the meter reads about 4.5V (0.45mA on the scale). The reason why the voltage does not rise above 4.5V is that the resistance of the meter (approximately 10 kilohm) forms a potential divider with the supply resistor. Now disconnect the lead from the positive battery terminal.

The voltage across the capacitor will fall caused by current flowing through the meter circuit—again fast at first and then the rate will tail off until no charge is left. Although it is difficult, try plotting a graph of voltage charged to (reading on meter), against time and then do the same for discharge. You should get curves rather like those shown in Fig. 7.

Although it requires buying another identical capacitor, you could do the same experiment with two 500 $\mu$ F capacitors in parallel. You will then notice an appreciable increase in the time of both charging and discharging.

## SERIES AND PARALLEL COMBINATIONS

Putting capacitors in parallel increases the

total capacitance

$$C_{\text{total}} = C_1 + C_2 + C_3 + \text{etc}$$

If you put the two capacitors in series you would find a decrease in the rate thus when series connected capacitance is reduced and is always less than either individual value—rather like resistors in parallel. The rule for capacitors in series is

$$\frac{1}{C_{\text{total}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \text{etc}$$

## EXPERIMENT 2

Use the Demo Deck to wire up the circuit of Fig. 8 but do not connect the positive terminal of the battery yet. We are going to charge the capacitor to 9V through a 10k ohm resistor and

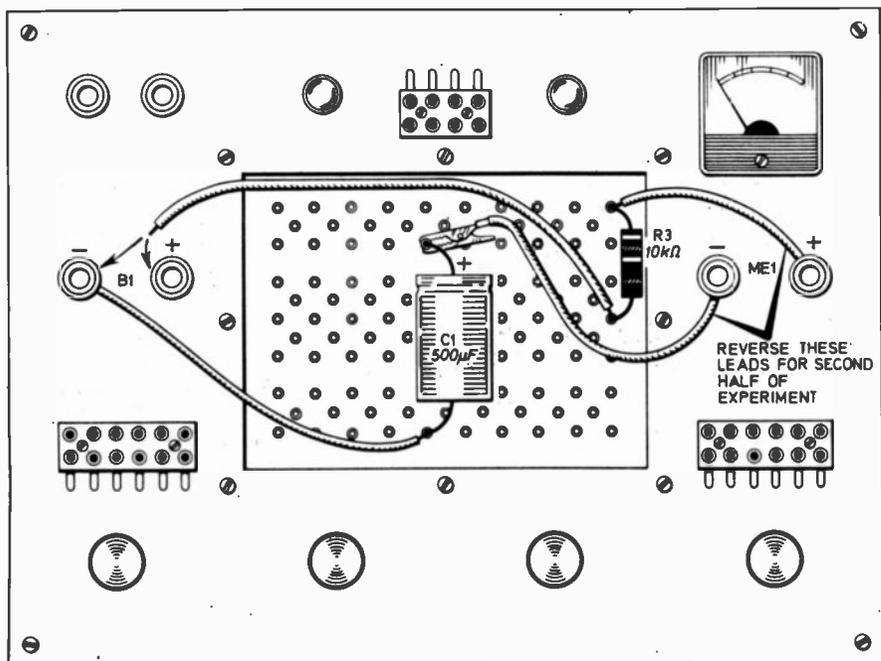
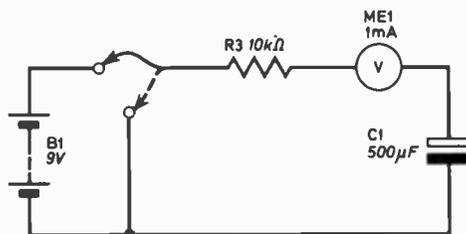


Fig. 8(a) (above). The circuit diagram for experiment 2.

Fig. 8(b) (left). The circuit wired up on the Demo Deck.

monitor the current on the 1mA meter in series.

Now connect the battery and watch the meter. Initially the charge current will be 0.9mA but this will gradually fall until full charge has been reached, i.e., the current becomes zero.

Now disconnect the positive lead from the battery and hold it on the negative terminal. Note that the meter tries to read backwards. Repeat the whole experiment, but when you get to the second half, reverse the connections to the meter. The negative current you saw can now be read from the meter scale. This is caused by the capacitor discharging back through the resistor.

Because the immediate "start" current was 0.9mA you can see that the only thing that limited the current in the first instance was the resistor. You could say that when the resistor is short circuited to the battery negative terminal, you were applying zero volts to the capacitor.

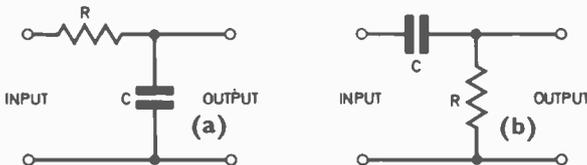


Fig. 9 (a) Integrator and (b) differentiator circuits.

The two experiments carried out demonstrate a pair of very important basic circuits which are

usually seen in the form of Fig. 9. They are respectively called integrator and differentiator circuits.



Next month: Semiconductors and experiments with diodes.

## Ruminations By Sensor

### Take a Card

A friend, who has just returned from the U.S.A., told me that the electronic construction hobby is highly organised over there. Apart from a large number of retailers specializing in the supply of components to the hobby market over the counter or by mail order, there have appeared, in drug stores, supermarkets and other unlikely places, complete kits of parts with full instructions for building electronic projects. The parts are mounted on a card covered by plastic; even the resin cored solder is supplied.

Where integrated circuits are used, the reductions in physical size and in the number of individual components required for a project have made it possible to supply everything required on a card no larger than E.E.

The advantages to the construc-

tor are obvious and apply equally to other complete kits; all the parts are of the correct type and can be expected to work together without difficulty. There are no delivery problems and no frustrations due to unavailability of any component, it would seem to make things almost too easy. But what about all those components one already has? Are these doomed to lie on the workshop shelf until they become obsolete? And what of the pleasure one can gain by searching the advertisements in EVERYDAY ELECTRONICS looking for bargain price components? Personally, I would rather buy components as and when I need them and the phrase "any component sold separately" in a kit advertisement, gladdens my heart.

### Take Another Card

I tend to lump together all "things sold on cards" as belonging to that class of cheap and nasty products that were once found in the cheaper stores, particularly at Christmas time. I think especially of one called, if memory serves me right, "The Young Carpenter", which con-

tained a "tin" saw, a wooden hammer, trisquare and few other useless "tools". The saw buckled at the first attempt to cut anything, the wooden hammer head broke from its shaft, and the glasspaper disintegrated at the first rub. How much damage to a young child's confidence could be wrought by a toy like this? The young fingers, not very skilful to begin with, the eager desire to make something, inexorably doomed to failure from the outset. It's enough to make anyone neurotic! I found my father's hacksaw and looked for something to saw; my mother's shopping basket lay near to hand and I carefully cut through the handle. There was no malice in the deed, I just wanted to saw something! It was very satisfying—but the aftermath was uncomfortable.

I am waiting for some manufacturer to bring out a range of educational toys and I suggest one might start with "The Young Roadmender". This would contain a pneumatic drill—realistic noise—really works—keeps children quiet for hours. For other people's children, of course.



**A**LTHOUGH only a simple instrument in the field of radio servicing, the pocket signal injector is a most valuable and handy tool for both the amateur and professional.

Because no mains power supply is required for its operation, and due to its small, compact size, this signal injector can be used almost anywhere—in the car, for example, where fault diagnosis can be carried out on the car radio which would normally be removed from the car necessitating, usually, in the car battery and speaker being removed also.

The signal injector is not, in general, able to pinpoint a malfunctioning component, but enables the stage containing the faulty component to be isolated enabling tests appropriate to this stage to be carried out.

### **CIRCUIT DESCRIPTION**

The circuit diagram for the complete signal injector is shown in Fig. 1.

It can be seen that the collector of TR1 is capacitively coupled to the base of TR2 by capacitor C1, and TR2 collector is capacitively

Approximate cost of components

£

0:80 excluding case

A useful pocket instrument for fault location on transistor radio receivers and audio equipment

# **SIGNAL INJECTOR**

BY ALAN JARDINE

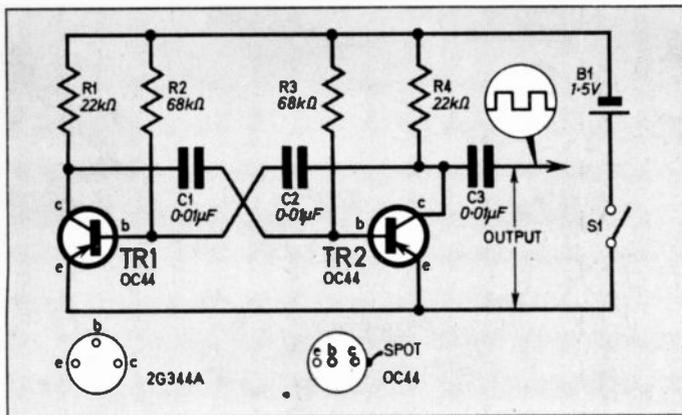


Fig. 1. The complete circuit diagram of the signal injector. Output is taken from the collector of TR2, and is a "square" wave of basic frequency 11kHz.

## Components....

### Resistors

- R1 22kΩ
- R2 68kΩ
- R3 68kΩ
- R4 22kΩ
- All ½ watt ± 10%

SEE  
**SHOP  
TALK**

### Capacitors

- C1 0.01μF
- C2 0.01μF
- C3 0.01μF high voltage type (see text)

### Transistors

- TR1, TR2 OC44 or 2G344A germanium pnp (2 off)

### Switch

- S1 on/off push button

### Miscellaneous

- B1 1.5V battery type HP7
- SK1 3 mm insulated socket
- PL1 3 mm miniature plug
- Veroboard, 4 x 25 holes 0.15 inch matrix
- 1 inch diameter tube about 5½ in long (it is advisable to obtain one with a clip-on lid);
- 1 crocodile clip; 1 in nail; rubber grommet.

coupled to the base of TR1 by capacitor C2.

This cross-coupling produces what is in effect an oscillator, due to the feedback action of the capacitors. This type of oscillator is called an astable (free-running) multivibrator.

Basically the multivibrator has two states, TR1 "on" (conducting)—TR2 "off" (non-conducting), and TR2 "on"—TR1 "off." The transistor states are activated by the capacitors C1 and C2; the length of time each is "on" and "off" is dependent on the values of C1, C2 and R2, R3.

## OUTPUT WAVEFORM

The output voltage seen at the collector of TR2 is a square wave formed by the periods of TR2 being "on" and "off" as shown in Fig. 2.

The ratio of the time one transistor is "on" to the other is known as the mark/space ratio. In this case C1=C2 and R3=R2, each transistor is on for the same length of time and so it is 1.

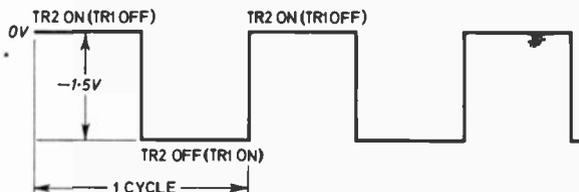


Fig. 2. The waveshape obtained at the output. This is made up from periods of TR2 conducting and non-conducting, the resultant effect being a square wave. A similar wave form is available at the collector of TR1.

The frequency (in Hz) of the square wave at TR2 is given by:  $f = 1 \div (1.4C \times R)$  where C is in Farads, R in ohms. For the circuit of Fig. 1 the frequency is 1kHz.

This signal can be regarded as a sine wave of frequency 1kHz with harmonics up to 10MHz. Thus the signal can be injected into any stage of a radio set and will produce a continuous note if the set is in working order.

The capacitor C3, in the output stage, has no influence on the signal produced by the multivibrator—its function is to prevent any current flowing into the injector from the radio under test.

It must be stressed at this point that this signal injector is primarily designed for use on transistor radio sets. If it is going to be used on mains sets, capacitor C3 should be a high voltage type, at least 350 volts working and

# SIGNAL INJECTOR




The photograph on the left shows the completed signal injector being used to test the Astron receiver. Complete test procedure for the Astron is given in the text of this article. The injector can also be used with other radios and audio equipment.

The signal injector completely wired up except for S1 and the earth lead. The probe is secured to the case cap.



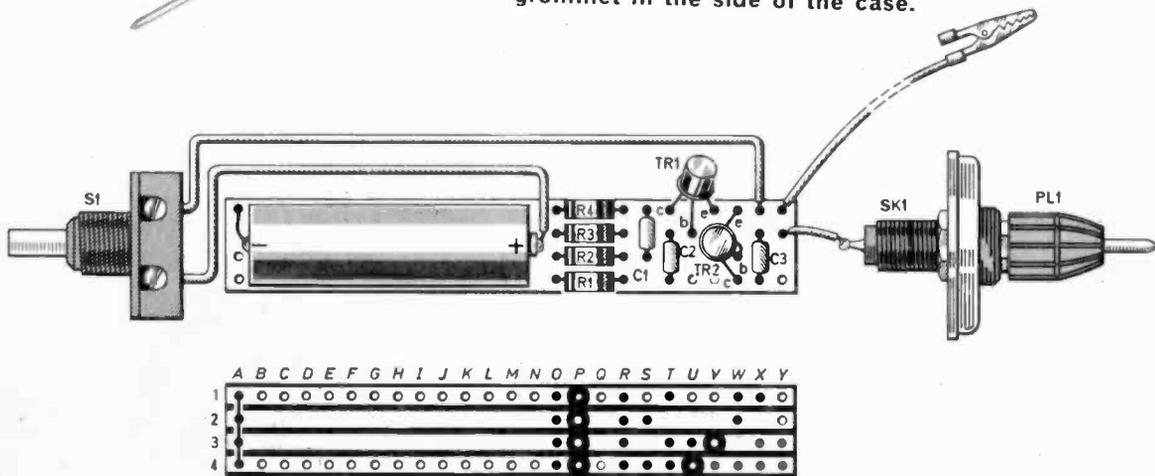Layout and wiring diagram of the complete signal injector. The lead to the crocodile clip passes through a grommet in the side of the case.



the metal case housing the unit must be adequately insulated. Several layers of insulating tape wrapped around the metal case should and must be used.

## **VEROBOARD LAYOUT**

The resistors, capacitors and transistors are all mounted with the battery on a piece of 0.15 inch matrix Veroboard of dimensions  $3\frac{3}{4}$ in.  $\times$   $\frac{5}{8}$ in. (4  $\times$  25 holes). The layout of the components is shown in Fig. 3(a).

The Veroboard length was chosen so that the battery can be attached to give a rigid, secure structure.

The underside of the board should be cut as shown in Fig. 3(b). Note the wiring across the copper strips at A1 to A4.

## **MOUNTING THE COMPONENTS**

Once the Veroboard is cut we can mount the components, starting with the resistors R1, R2, R3 and R4 followed by the capacitors C1, C2 and C3.

A piece of tinned wire should now be soldered across the 4 strips of copper at A1 to A4 with one end protruding through the top of A4 for later connection to the battery.

Solder a 3 inch piece of insulated wire to the positive terminal of the battery and place the battery on the Veroboard in position shown. Secure in this position by wrapping some insulating tape around the battery and board.

Solder the bare lead from A4 to the battery base (negative terminal).

Next the flying leads to locations X4 and Y4 should be soldered. X4 lead should be about 5 inches long and Y4 should be about 2ft.

The probe flying lead should now be soldered in position indicated, Y2. This should be about 2 inches long and be of seven strand insulated wire.

All that remains to be done on the board now is to solder the transistors in position. Remember when soldering transistors, to use a heat shunt on the leads being soldered. A small pair of snipe nose pliers held across the lead being soldered will act as an efficient heat shunt. If no heat shunt is used permanent damage to the transistors may result.

Now take the leads from X4, Y4 and the positive battery terminal to the end of the board as shown. These may be held in position by means of a piece of insulating tape on the side of the battery.

Connect the push-button switch S1, as shown and ensure it is in the off position.

## **CASE**

The case used in the prototype was an empty "Steradent" tube which is an aluminium tube with a plastic clip-on cap. A plastic clip-on cap

should be used since it affords insulation of the probe from the case and no lead twisting results from the clip-on action.

A small hole is drilled in the centre of the cap to suit a 3mm insulated socket (which forms part of the probe), and a nut and washer hold it securely in position.

Another hole is drilled in the opposite end of the tube to suit the switch S1.

The switch used, and obtainable from Woolworths, was found to be a little large to fit into the tube. It is necessary to file a little off each corner of the switch to enable an easy fit.

At the rear, and on the side of the tube, drill a small hole about  $\frac{3}{16}$  inch diameter for the fly lead from Y4. A rubber grommet should be used in the hole for protection of this wire.

## **PROBE**

The probe is very easily constructed. It consists of a 1 inch nail with its end filed to a smooth point and its head soldered to the inside of the 3mm plug. A length of insulated sleeving is then pushed over the stem of the nail, leaving about  $\frac{1}{4}$  inch of tip exposed, and the plug cap screwed on. Push the plug into the socket on the lid of the tube—the probe is now complete and the fly lead from location Y2 on the Veroboard can now be soldered to the tag on the socket.

## **ASSEMBLY**

First of all, check that the correct transistor lead connections have been made and that the battery is connected the right way round.

Thread the lead Y4 through the hole on the side of the case. Now lay a thin piece of foam rubber along the bottom of the Veroboard and lap it around the battery end (this may be held in position by a dab of glue and prevents possible shorting against the case) and slide the whole unit, switch end first, into the tube.

Screw the plastic fixing nut on the switch and clip on the lid. The grommet should now be placed in position and a crocodile clip attached to the end of the exterior lead.

The unit is ready for use.

## **TESTING**

Testing the unit is a simple matter. Apply the probe to the aerial socket or aerial connection of a radio set that is known to be in working order, and attach the crocodile clip to the earth line in the radio and switch on.

With the volume knob turned up, a high pitched tone should be heard whatever the setting of the tuner dial.

If there is no sound, recheck the circuit and investigate for breaks in the circuit, short circuiting and dry joints.

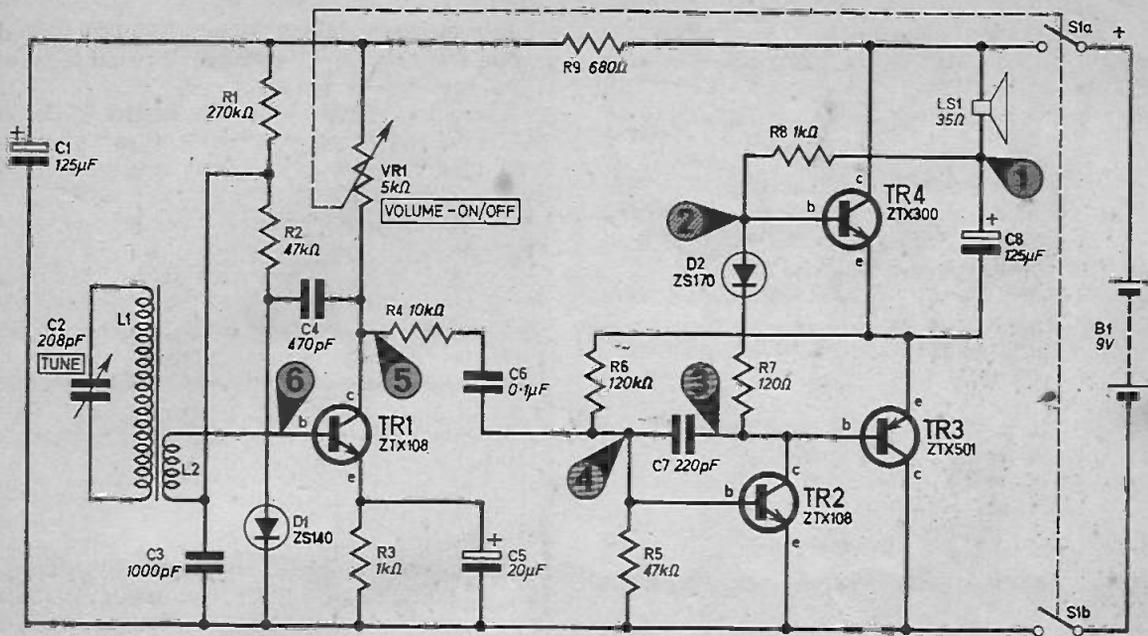


Fig. 4 The circuit diagram of the Astron receiver with the test points indicated for fault location and checks.

## FAULT LOCATION

The completed signal injector may prove a very useful instrument for the constructors of the *Astron* receiver featured in the January edition of *EVERYDAY ELECTRONICS* as well as constructors of other projects or for use in fault locating on commercial transistor receivers.

The *Astron* circuit will be used to illustrate the use of this instrument, but it will be seen that the testing procedure can be adopted for use on other types of receivers, amplifiers, etc.

Basically what happens is that we work backwards through the circuitry from the loudspeaker listening to the volume and tone of the signal emerging from the loudspeaker.

When a point is reached which produces "no sound", then the fault lies between this point and the previous one. The absence of any sound indicates such things as a faulty component, dry joint, circuit break or wrong connection. When such a "noiseless" stage is reached, this region should be checked in detail.

For the *Astron*, signal injection should be at points 1 to 6 as indicated in Fig. 4.

Assuming that the radio is in perfect working order, the testing procedure should give results as listed below.

## PROCEDURE

Turn the volume control full on and adjust the tuner so that no station is tuned—this results in a hiss from the loudspeaker. Attach the crocodile clip to the negative side of capacitor C1 and apply the probe to the points 1 to 6 in numerical order.

**Point 1** A high-pitched sound of low volume will be heard over the loudspeaker. This indicates that the loudspeaker is functioning.

**Point 2** A louder sound of the same pitch will result, indicating that the TR4 side of the output stage is functioning.

**Point 3** The probe of this point produces higher pitched sound but with a reduction in volume as compared with test point 2. This indicates the functioning of the other half of the output stage—that containing TR3.


**Point 4** This point is to test the driver stage containing TR2. A very loud sound is heard that has a lower pitch than point 3.

**Point 5** A higher pitch sound than previous test point with the same volume level. Satisfactory signal indicates R4 and C6 free from fault.

**Point 6** This position tests the performance of TR1. The sound produced by probing this point is very loud, with a lower pitch than previous test point.

It is important to test in the way described above, i.e., working back from the loudspeaker. Only if the stage previous to the one on test gives a satisfactory result can any conclusions be drawn about the one on test.

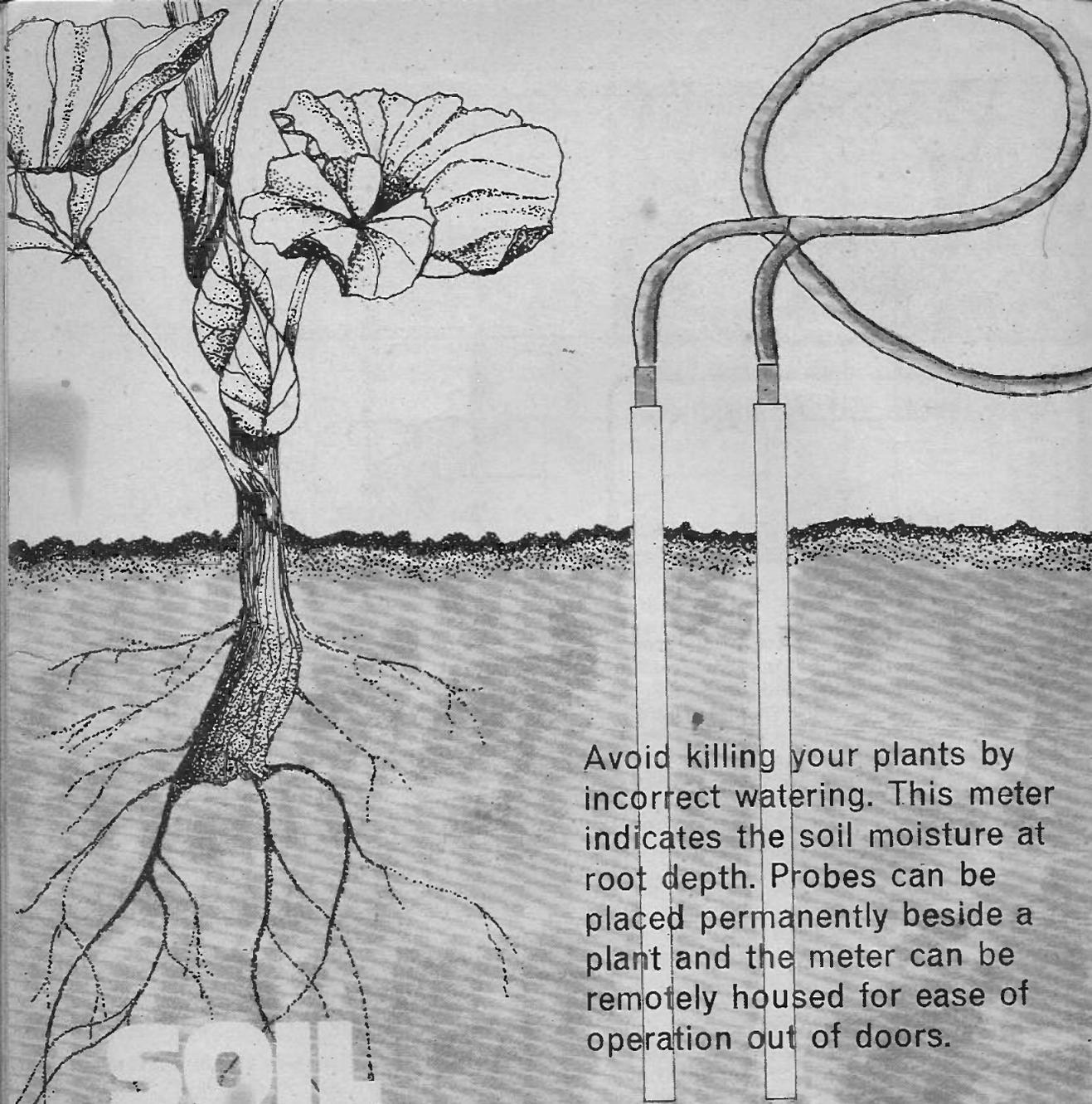When a faulty stage is located, it should be examined in detail—it may be necessary to use other test equipment for this purpose. When rectified the above test procedure should be carried out again starting from test point 1. □



Avoid killing your plants by incorrect watering. This meter indicates the soil moisture at root depth. Probes can be placed permanently beside a plant and the meter can be remotely housed for ease of operation out of doors.

# SOIL MOISTURE METER

**By D. Bollen**



Approximate cost of components



3.00 excluding case

ON the face of it, watering the garden would seem to be a simple pastime, but it often does more harm than good. A light sprinkling during dry weather will, for example, merely attract rootlets to the surface and cause excessive transpiration, while water applied to apparently dry soil could percolate down to where roots are actually lying in sodden earth. Even more critical is the watering of plants in pots and seed boxes, because there is no large volume of earth to act as a moisture buffer.

Obviously, plants of different species have their own individual water requirements, and the only reliable way of ensuring that they are catered for is to measure soil moisture content at root depth.

## MOISTURE MEASUREMENT

The electrical conductivity of a soil is approximately proportional to its moisture content, and the principle adopted here is to measure the a.c. current flowing between a pair of copper electrodes inserted in the ground. This gives a meter reading linearly calibrated in terms of percentage saturation which can be readily adapted to suit soils of widely differing porosity. It might be thought simpler to use d.c. current between the electrodes, but this would only result in electrode corrosion and errors due to polarisation of the electrodes.

The basic arrangement of the moisture meter is shown in Fig. 1, with an oscillator supplying current to the electrodes via an a.c. microammeter and a series resistor. Insulated sleeving is fitted over the electrodes in such a way that only the ends are exposed to the soil, thus the depth at which readings are taken will depend on how far the electrodes are inserted.

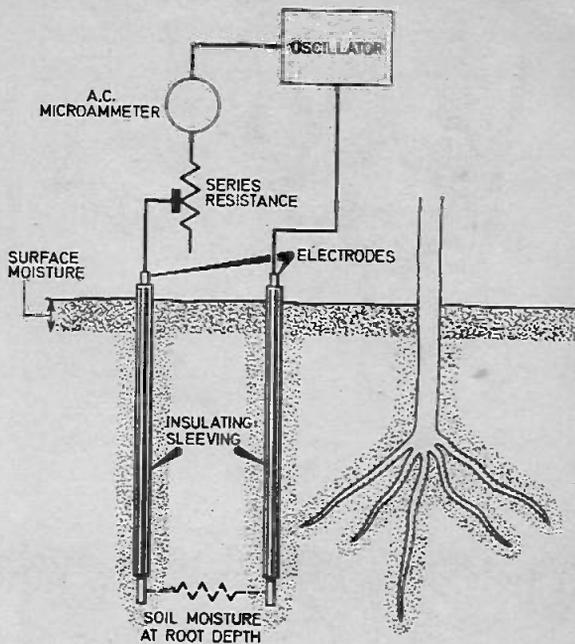


Fig. 1. Basic arrangement of the moisture meter.

## Components . . . .

SEE  
**SHOP  
TALK**

### Resistors

- R1 4.7k $\Omega$
- R2 68k $\Omega$
- R3 68k $\Omega$
- R4 4.7k $\Omega$
- All  $\pm 10\%$   $\frac{1}{2}$  watt carbon

### Capacitors

- C1 1 $\mu$ F polyester (250V d.c.)
- C2 0.1 $\mu$ F polyester (250V d.c.)
- C3 0.1 $\mu$ F polyester (250V d.c.)

### Semiconductors

- D1-D4 OA 200 (4 off)
- TR1 BC 108 Silicon npn
- TR2 BC 108 Silicon npn

### Switch

- S1 Single pole push to make

### Meter

- ME1 500  $\mu$ A f.s.d. moving coil meter (100 $\mu$ A may be used—see text)

### Miscellaneous

- VR1 10k $\Omega$  vertical skeleton preset potentiometer
- B1 PP3 9V battery
- JK1 3.5 mm mono jack socket
- PL1 3.5 mm mono jack plug
- 2 $\frac{1}{2}$  in x 2 $\frac{1}{2}$  in x 0.25 in matrix plain perforated circuit board, insulated sleeving, mounting pins to suit board, battery connectors, 24 in x  $\frac{1}{8}$  in outside diameter copper tubing, case (approximately 4 in x 3 in x 3 in), connecting wire and probe leads.

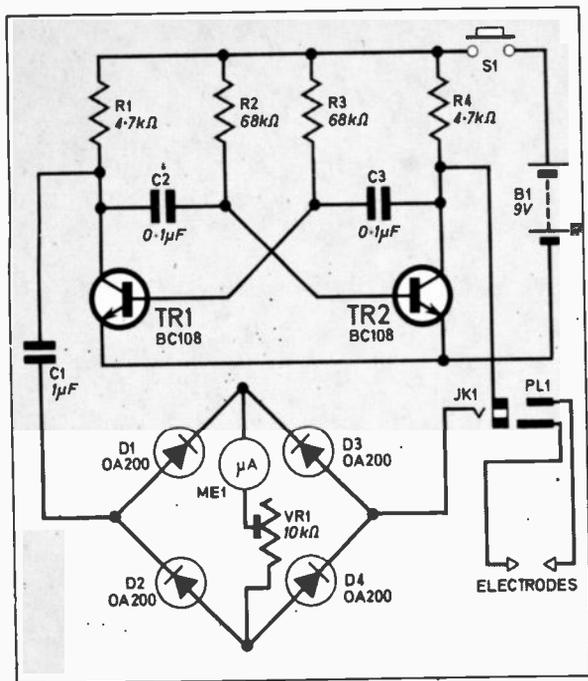


Fig. 2. Complete circuit diagram of the soil moisture meter.

## CIRCUIT

The complete circuit of the moisture meter is given in Fig. 2. Transistors TR1 and TR2 are cross-coupled by capacitors C2 and C3 to form a multivibrator oscillator which provides a square-wave output of 8V amplitude at a frequency of about 100Hz. The output is taken through capacitor C1 which serves to prevent a flow of d.c. between the electrodes.

The multivibrator functions by the alternate switching of TR1 and TR2 actioned, at the selected frequency, by the charging of C2 and C3 through R2 and R3. Variation of these components will alter the frequency of the multivibrator.

The output is taken from across the collectors of the two transistors so that current is flowing through the probe circuit at all times. If the output was taken across one transistor only, then no current would flow when that transistor was fully conducting.

The a.c. microammeter in Fig. 2 consists of diodes D1 to D4, which form a bridge rectifier and meter ME1. The preset potentiometer VR1 functions as a series meter resistor and is also used for calibration. A.C. current passes from the collector of TR1, via C1, through the a.c. microammeter, and then by way of JK1 and PL1 to the electrodes, through the soil, and returns to the collector of TR2.

Switch S1 in Fig. 2 is a push button switch which energises the circuit only when a reading is being taken. The meter ME1 has a 500μA

movement, but 100μA and 50μA movements may be used if their terminals are shunted by a resistor of 270 ohm or 120 ohm respectively. A convenient meter scale calibration would be 0-100, or 0-10, representing 0 to 100 per cent saturated—a method of altering the meter marking is given later in the article.

## CONSTRUCTION

The moisture meter components can be housed in a small plastics food container or any other suitable small case, with ME1, S1, and SK1 fixed to the front. The remaining components are assembled on a piece of 0.25 inch matrix plain, perforated circuit board which is bolted to the meter terminals, see Fig. 3.

The photograph used in the heading of this article shows the meter face as marked in the prototype. To designate the meter as shown the movement must be taken from the case and the metal scale carefully removed from the movement. Unwanted markings already on the face can then be carefully removed using an abrasive cleaner or metal polish. Once this has been done new markings can be inked in and the meter reassembled, once again taking care not to damage the movement.

Commence construction by cutting the circuit board to size, and drill two holes to take the meter terminals. Insert all turret tags in the locations shown and then solder on link wires, resistors, VR1, capacitors, and leads, using insulated sleeving where necessary. When the circuit board has cooled, solder the diodes and transistors to the turret tags, using a heat shunt if you are not proficient at soldering the leads quickly.

If the meter polarity is not the same as in Fig. 3, the connections to the solder tags should be reversed. Also, where a 100μA or 50μA meter movement is employed, the appropriate value of shunt resistor should be soldered across the meter tags, as mentioned earlier.

Having mounted the meter, push button switch and socket on the front panel, attach the circuit board to the meter and connect up the leads as shown in Fig 4. The battery can be taped to the inside of the box, or a special clip made to hold it in place.

To check that the circuit is functioning correctly, temporarily solder a 4.7 kilohm resistor across SK1, connect up the battery and press S1. Now adjust VR1 for a full-scale meter reading. If the meter does not respond at all when S1 is pressed, the circuit should be checked for wiring errors. Check the polarity of the diodes and the transistor connections in particular.

## ELECTRODES

Take two pieces of  $\frac{3}{16}$  inch outside diameter copper tubing about 12 inches long (or longer if desired) and flatten one end of each with a


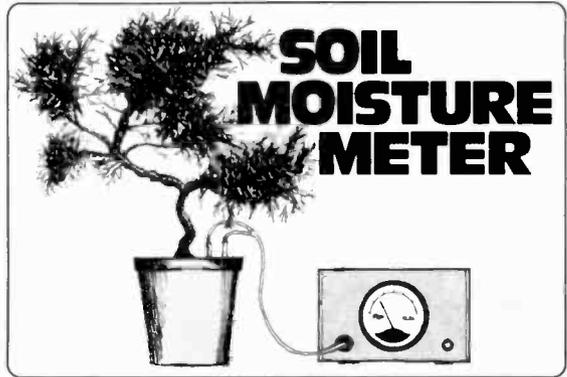
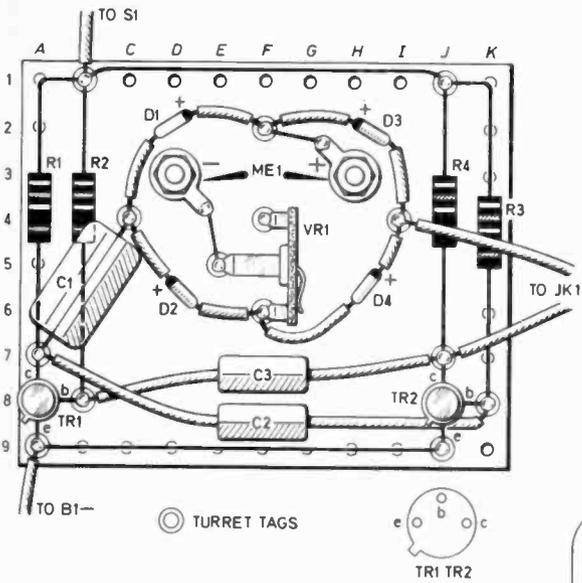
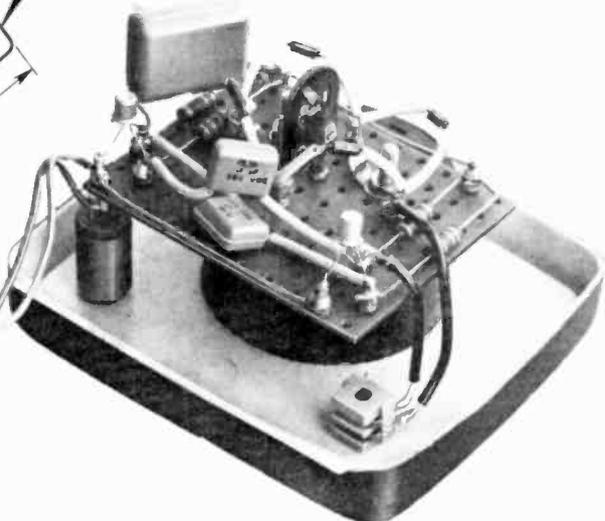
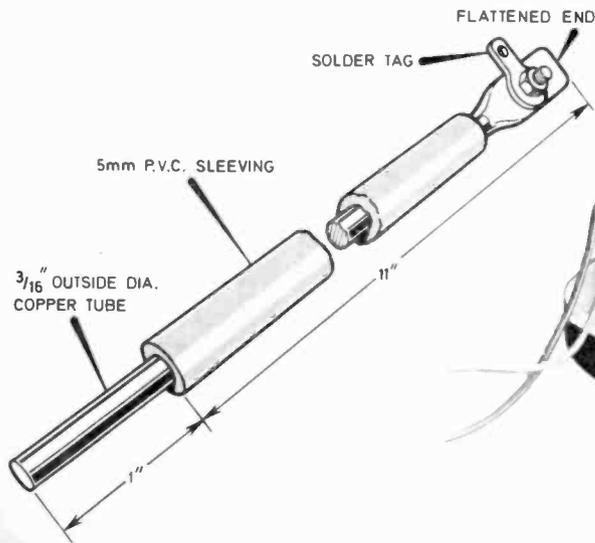


Fig. 3 (above). The layout and wiring of the complete circuit board. This board is mounted by the meter terminals.

Fig. 4 (right). Connections of the flying leads from the circuit board to the remaining components.

Fig. 5 (below). Construction of the moisture probe—two are required. These are connected by two core wire to JK1 via PL1.

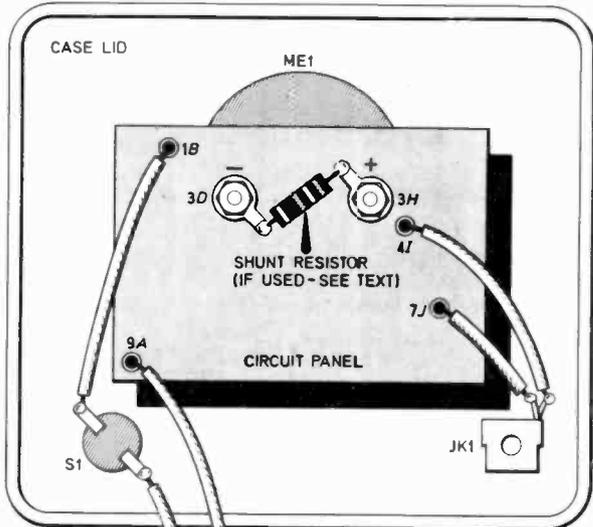

hammer, see Fig. 5. Drill the flattened ends to take 6 B.A. screws. Push insulated sleeving over the electrodes leaving about 1 inch of the unflattened ends bare.

The moisture probes may be permanently installed or used at various locations with the meter. Having decided on the location of the electrodes, and the length of cable necessary (this should not exceed 20 yards) solder the ends of the cable to the electrode tags and fit PL1.

## SETTING UP AND CALIBRATION

It is advisable to check that the probe cable does not introduce too much capacitance into circuit, especially when a long run is used. Support the electrodes off the ground on a piece of dry wood, connect PL1 to the meter and press S1. If there is a slight movement of the meter pointer away from zero this can be compensated for by adjustment of the meter zeroing screw.

Push the electrodes into the ground, about 3 inches apart, to the required depth, and then pour about two gallons of water onto the soil around the electrodes and leave for an hour or two, until the soil is saturated at root depth,

then press S1 and adjust VR1 for a full scale (100 per cent) reading. If, after calibration, there is a prolonged dry spell, the meter reading will slowly decline and may eventually reach zero.

## USING THE MOISTURE METER

Some plants will thrive best if their moisture level is maintained within limits, for example, house leeks 10-30 per cent, roses 30-70 per cent, and marrows 70-95 per cent. Cacti, on the other hand, will demand a seasonal watering programme varying from, say, 60-80 per cent in summer down to 5-10 per cent in winter.

There are many books available on gardening and the various moisture requirements of plants can be found from these books. If you require the probes to be permanently installed for monitoring of one plant a second set of probes could be constructed and used with the meter to check other plants both indoors and outdoors. A set of smaller probes may be useful when checking small pot plants.

Meter calibration can be checked from time to time when the soil becomes saturated after a heavy rainfall. □

---

## MEMORY STORE

### Retrieval By

Derek Burn

I SUPPOSE that it is true to say that I became involved in electronics by the back door. My only formal training had been a wireless mechanic's course in the RAF, and that was a very long time ago and almost forgotten. Then one day a new neighbour passed the house carrying under one arm a very large and impressive model boat and under the other an equally impressive box covered with an incredible array of knobs and dials. This fascinating sight could not be allowed to pass unremarked and I just had to find out more. I think perhaps a dormant interest had been aroused, for the immediate result of a most interesting conversation was that I gained a new friend and a new hobby.

The magnificent boat was of course radio-controlled, and it turned out that it was not working very well. Hoping that at least a part of my RAF course had stuck, I rashly offered to try to put things right. Fortunately it wasn't too difficult for these were the early days of radio control when

valves and very simple circuits were the only hope for success.

We soon reached that triumphant stage when the gear would work correctly on about half of our visits to the local pond—and that was quite a fair performance in those days!

About this time, commercial equipment was beginning to appear featuring that new-fangled gadget, the transistor. Naturally we could not afford such luxuries, but at least we could try to learn something about the device and attempt to build our own gear. This was a very exciting period for radio control.

The transistor made it possible to devise very much more sophisticated circuitry which was small and light, and yet more reliable than the valve equipment that it replaced. Our visits to the pond became more frequent and much more successful.

As I learnt more about these transistors, I became fascinated by their possibilities, and my interests widened to cover any aspect of electronics that took my fancy. The main reason for this active interest was curiously my inherent laziness.

I had always been put off by the enormous amount of tin-bashing which seemed to be such an

essential feature of the electronics of the valve era. The transistor changed all that. The chassis was now just a piece of printed circuit board, and I felt that I could now get stuck in!

Probably because I was never very successful with r.f. circuits (oscillators would never oscillate and amplifiers invariably did), the ham scene did not appeal to me. However, I discovered an unexpected talent for making multi-vibrators that worked, and so I was led inevitably into the field of digital circuits. As it happened, model radio control also moved in this direction with the introduction of the so-called digital proportional system, and so my interest in that aspect of electronics was maintained.

The scope of this type of circuitry is almost limitless, bounded only by one's imagination. Well, almost only, another factor being patience. After all, there is a limit to the number of bistables one is prepared to wire up!

Happily, just at this time, integrated circuits burst upon the amateur scene, and really complex circuits such as digital clocks became a reality. I can see no end to this type of electronics for many years to come, and I am happy that it should be so.

# ANTEX

## your soldering appliance specialists.



**E.240** 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price £1.80.

**ES.240** 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit and packed in a transparent display box. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price £1.83



**CN.240/2** Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price £1.70

**CN.240** Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price £1.70

**G.240** Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price £1.83.



**CCN.240** New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety; fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. Price £1.80

**CCN.240/7** The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price £1.95



### SK. 2 SOLDERING KIT


This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price £2.40.


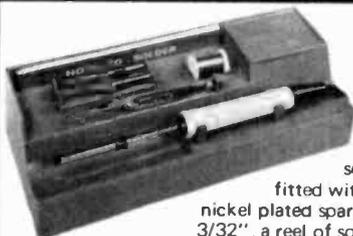
### MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price £1.95.




### SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price £2.75
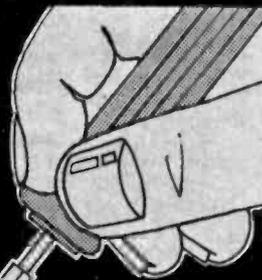
## sign here to answer all your soldering problems.



# ANTEX

from electrical, radio or car accessory shops or from Antex Ltd., Freeport (no stamp required) Plymouth

PL1 1BR Telephone 0752 67377/8

Please send the Antex colour catalogue.

Please send the following:

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I enclose cheque/P.O./Cash (Giro No. 2581000)

Name \_\_\_\_\_  
Address \_\_\_\_\_

E.E.3

So many of the components you want for EE designs are in the Electrovalue catalogue. Good service, delivery and discounts

# ELECTROVALUE

## Electronic Component Specialists

### THIS MONTH'S SELECTION OF POPULAR ITEMS FROM THE ELECTROVALUE CATALOGUE

#### TRANSISTORS

(Sil. = Silicon. Ger. = Germanium)


No.	Type	Purpose	Price
2N697	Sil. NPN	General	18p
2N1304	Ger. NPN	"	28p
2N1305	PNP	"	26p
2N2646	Sil. UJT	Oscillator, SCR driver	47p
2N2824	NPN	Small sig. amp	11p
2N3055	NPN	High power	60p
2N3702	PNP	Low power	13p
2N3704	NPN	Low power	13p
AC126	Ger. PNP	Small sig./driver	20p
AC128	PNP	Low power	20p
AD149	PNP	High power	55p
AC176	NPN	Low power	15p
*AD161	NPN	Med. power	33p
*AD162	PNP	Med. power	30p
BC108	Sil. NPN	Small signal	11p
BC109	NPN	Low noise	12p
BC168	NPN	Small signal	10p
BC189	NPN	Low noise	11p
BF194	NPN	RF amp.	14p
BFY51	NPN	Med. current	20p
OA80	Ger. diode	RF detector	6p
OA91	"	General	6p
SD1	"	Silicon Rectifier 1 amp	10p
W02	"	Silicon bridge 1 amp	40p

\*Matched pair AD161/AD162 60p

#### CAPACITORS

Non-polarised

Electrolytic

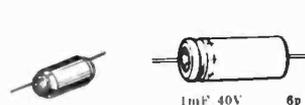

Polystyrene

10pF	3p	1mF 40V	6p
22pF	3p	5mF 64V	6p
100pF	3p	10mF 64V	6p
220pF	3p	20mF 64V	6p
470pF	3p	25mF 25V	6p
1000pF	3p	50mF 25V	6p
2200pF	3p	80mF 25V	6p
4700pF	4p	220mF 25V	7p
		470mF 25V	12p
		1000mF 25V	20p
		2000mF 25V	30p
		5000mF 25V	62p

Polyester M K T

0.01mF	5p
0.02mF	5p
0.047mF	6p
0.1mF	6p
0.22mF	6p
0.47mF	10p
1mF	14p

Many other higher and lower ratings will be found in the catalogue. Close tolerance and high stability types also.

#### VOLUME CONTROLS, ETC.

Very wide ranges carried including the following popular types:—

4.7Kohms, 10Kohms, 22 Kohms, 47, 100, 220, 470 Kohms; 1 Megohm, 2.2 Megohms.



Log or linear tracking

MONO 12p each; STEREO (matched tracks) 42p

Any type with double pole mains switch—12p extra

DUAL CONCENTRIC

In any combination of above values 60p, with switch 72p

STEREO BALANCE CONTROLS

Log/Antilog, 10K, 47K, 1M  
Dual antilog 10K only.

#### MAIN LINE AMPLIFIERS

70 watt power amplifier in module form ready to build into any system. With full instructions.

Amplifier module kit	net £12.60
Power supply kit	net £6.00
Matching pre-amplifier kit (for magnetic or ceramic pick-up) less panel, knobs and chassis	net £3.30

Note—All the above prices are for mono.

FOR STEREO for building into your own cabinet. Two amplifier modules and pre-amp kits are required with matched controls plus one power supply kit, net price £38.40

10p CATALOGUE FREE WITH ORDERS FOR £1.00 OR MORE

The Electrovalue catalogue (64 pages and cover, 8½ x 5½ins) is crammed with money saving items, and illustrated technical information. FREE with orders for £1.00 or more. Sent separately it costs you 10p post free. Write your order on a sheet of paper with coupon attached

# ELECTROVALUE

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 OHB

Hours 9-5.30 : Sat. 1.0 p.m.

Telephone: Egham 5533 & 4757 (STD 0784-3)

Telex: 264475

ELECTROVALUE — an independent company from its establishment in 1965

#### RESISTORS

½ watt and ¼ watt, all at 1p each in the following values (in ohms):—

10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and all values in this series up to 10 Megohms.

Power Resistors

3 watts—7p each; 7 watts—9p each.

Values as for ½ watt series, but up to 10 Kohms only.

Many other types and values available. Full details in catalogue.

#### VEROBOARD

The universal circuit building board

Unclad, 0.1" matrix

2" x 3.75" 10p

2.5" x 3.75" 15p

5" x 3.75" 25p



Copperclad Veroboard also in stock in most standard sizes and matrices; also edge connectors, pins, etc.

Simple to Build, Astoundingly Good 10W/15Ω BAXENDALL SPEAKER

As originally designed by P. J. Baxendall and described in Wireless World. 10 watt/15 ohm loudspeaker with equaliser network speaker unit and specially designed cabinet in kit form. Size when built approx. 18" x 12" x 10". Price, inc. carriage paid in U.K. Nett £13.90

#### MISCELLANEOUS ITEMS

INDICATOR LAMPS

NEON chrome bezel, round red NR/R 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C 24p. Neon, square red type L55C/P, 18p; amber type L55C/A, 18p; clear type L55C/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type L55C/R-6V, 30p; 6V 0.04A amber type L55C/A-6V, 30p; 6V 0.04A clear type L55C/C-6V, 30p; 6V 0.04A green type L55C/G-6V, 30p; 12V 0.04A L55C/R-12V, 34p; 34V 0.04A L55C/R-28V, 45p.

KNOS—NUTS, SCREWS, WASHERS — TERMINALS AND MANY OTHER ESSENTIAL ITEMS — see Catalogue

COLVERN 3 watt Wire-wound Potentiometers, 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1K, 1.5K, 2.5K, 5K, 10K, 15K, 25K, 50K, 32p each

DIN CONNECTORS

	plug	socket
Loudspeaker	2-pole	12p 10p
Audio	3-pole	13p 10p
Audio	4-pole	14p 12p
Audio	5-pole 180 deg	15p 12p
Audio	5-pole 240 deg.	15p 12p
Audio	6-pole	15p 13p

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES, 40p.

HANDBOOK OF TESTED TRANSISTOR CIRCUITS, 40p.  
COLOUR CODE WALL CHART, 15p. (Add 3p for P/P if any of above three items are ordered separately.)

OVERSEAS CUSTOMERS WELCOME

#### COMPONENTS DISCOUNTS

allowed on all items other than those at net prices.

10% on orders for £5 or more

15% on orders for £15 or more

POSTAGE & PACKING FREE on orders for £2.00 or more. Please add 10p if under.

Overseas orders welcomed. Prices subject to alteration without prior notice. Terms of business — C.W.O. as in catalogue

To ELECTROVALUE, ENGLEFIELD GREEN, EGHAM, SURREY  
Please send a Goods to value of £..... as detailed on sheet attached, plus FREE copy of catalogue.

b Copy of catalogue.  
(strike out item which does not apply)

NAME .....

ADDRESS .....

Enclosed please find £..... cash/cheque/money order.

EE. 5

We will try and clear up a few points that have come to light during the last month. First it would appear that in January issue two components were missed out of components lists. In the *Astron* R9 680ohms was left out ( $1/4W \pm 10\%$  carbon) and in *Electro Laugh* D1 1N914, diode was left out.

When constructing the *Electro Laugh* please note the link between P7 and Q7 is not very clear on Fig. 3 as C6 has printed rather darker than it should have.

In the *Astron* we have also managed to show two C5's on Fig. 3—the one on the left should be C6—and we have transposed the battery leads on Fig. 4. We have also made the same mistake with the battery leads in the *Rain Alarm*, February issue Fig. 4, sorry about these points.

Whilst talking about these projects there are some other points worth mentioning. The speaker used in the *Astron* is the same as that specified for the *Demo Deck*. Due to demand created by these articles the speaker is at present unobtainable, however, some firms have similar size speakers in stock and one of these could be used, provided that its impedance is not less than about 20 ohms. Speakers with much higher impedance than the 35 ohms specified will not provide such a high output power.

Some readers have enquired about the earpiece used in the *Electro Laugh*, it is a magnetic device and is generally available for around 60p. After some experimenting the unit was also found to work well into a small 75 ohm speaker and this makes a good alternative to the earpiece.



### Component Wiring

Apparently new constructors are having difficulty in following our Veroboard layout and wiring diagrams. The main problem seems to be that readers are unsure about what is copper and what is board. In all our diagrams the black strips are the board and the white the copper. The small black dots are connections of the wires to the strips and the large black circular areas with white holes are the areas where the copper has been cut away with a drill or spot face cutter.

Another point that is worrying some constructors is the type of wire we use for making links on the board. In general the wire is 22 s.w.g. tinned copper wire but

in some cases—where bare wire could touch other wires or components—single strand covered wire should be used.

We hope that has solved a few problems from previous months—now let us look at this month.

### Moisture Meter

The 0.25 inch matrix perforated circuit board used in the *Moisture Meter* is the same as that used in the *Demo Deck*. To state the position about supply once again, it is made by R. S. Components but not available to readers from them. The board must be purchased through one of the normal components retail firms and a number of them either stock it or will get it for you; the same applies to the mounting pins used.

When it comes to covering the probes with insulating sleeving Home Radio sell some heat shrinkable sleeving which is easy to use and is eminently suitable for the job. The tubing is called Polyshrink and is available in a range of sizes to suit various diameters to be covered from  $1/8$  inch to  $3/4$  inches.



### Darkroom Timer

The list of semiconductors used in the *Darkroom Timer* is varied but the Zener diode, silicon controlled rectifier and diode are all items that are readily available in a variety of type numbers. Indeed many suppliers no longer quote the type numbers but list such things as Zener diodes by the voltage and power rating as we have given in the components list. It is not necessary with this type of device to search for the correct type number provided the ratings we quote are the same.

The wafer switch used is a 2 pole 9 way type and we have shown this as having two wafers, however, it is available in a number of types—all suitable—and some may only have one wafer or possibly two with 12 ways on each, it is only necessary to use 8 of the tags and a wiper.
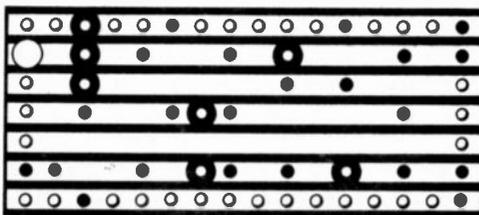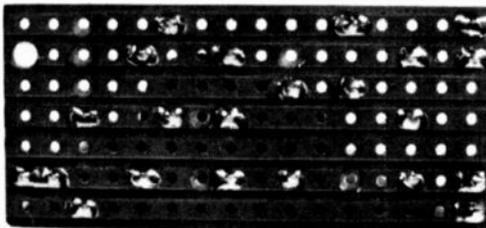
### Signal Injector

As far as we can see there are no buying problems concerning the *Signal Injector*—provided you take note of the advice given in the article concerning the tube used as a case.



Compare the photograph with the drawing and identify the strips of copper, soldered connections and breaks in the strips.

REMEMBER  
TO USE THE  
POSTCODE



# Readers Letters

## Mystery!

Why is the subject of electronics surrounded by such an air of mysteriousness? I am new to electronics and have learned a lot from the first three issues of your magazine. If I want to develop a film there is no mystery. All I need is a developing tank, a bottle of developer and bottle of fixer. It's as easy as making a cup of tea. Your magazine is helping to destroy the mystique that has shrouded the subject for far too long. Carry on the good work.

Russ West  
London.

## Letraset

Thank you for your latest publication, EVERYDAY ELECTRONICS, a great alternative to P.E. which I have been taking for a number of years. I have just completed the record player featured on your first edition, with a few alterations in layout, to suit the plinth I made and I am delighted with results. I have one request to make, could you please inform me where I can purchase Letraset so often prescribed by your authors for projects but never a source of supply mentioned. I would be grateful if you would also let me know which sheet I would require for audio and if possible, price.

G. H. James  
Scotland.

*Letraset is available in a vast range of type faces from most large stationers. Each sheet contains a range of letters and numbers and hence any designation can be made up; the prices of the sheets vary.*

## Projects

Having just read my first copy of your magazine, EVERYDAY ELECTRONICS. I find this magazine most interesting as it deals with the practical aspects of electronics which are often complicated by theory in other periodicals.

I wonder if you have considered the use of electronics as used on small boats as most professionally manufactured electronic aids are very expensive. It would seem

that there is a demand for practical advice as to the construction of instruments which would be of use to small boat owners.

B. L. Strang  
Edinburgh.

*The boat owner will not be overlooked in future issues.*

It was quite by chance that I picked up a copy of the January 1972 issue of EVERYDAY ELECTRONICS and was so pleased that I have now ordered the first two copies and have placed a firm future order.

I am writing, because I expect that you are feeling your way as regards to the contents and level of your articles. There must be many like myself who reached a fair knowledge in the use of the valve and due to circumstances had to chop the hobby only to find now that there have been so many changes that it is most difficult to take up the hobby again.

Your *Teach-In* article is just right for us as is the m.w. reflex receiver. I am looking forward to making a start on the *Windscreen Wiper Control*, when I get the copy.

G. V. Pride  
Dorset.

## Device Function

May I offer the following comments concerning your new magazine, for which I have placed a regular order, in the hope that they may be of some assistance to you.

You appear to be aiming at simplicity and this is most important, but being specialists, I fear you may drift into the complication and jargon which so limits the field of other electronics magazines. You see I am sure there are a great number of do-it-yourself practical people who would like to widen their hobby scope, without having to do a great deal of research and study. They are the type of people who want to use the equipment in some useful way. After all, many people use motors, relays, solenoids etc., in gadgets and models, without knowing much about equipment designs—flux densities—back e.m.f., etc.

In a good deal of reading I have not come across a clear statement of what transistors and S.C.R.s do, without a long and difficult explanation of how (which incidentally seems to vary). Maybe as specialists you do not appreciate that the practical person is not interested in the how, he accepts a transistor as a "little thimble with three or more wires sticking out of it." What he wants to know is which wire to connect to what in order to make a timer work, a flash gun to flash, a bell to ring etc. In this respect, please keep printing a drawing of the base of the various transistors you use in your projects.

F. R. Holmes  
Darlington.

*We will keep printing those base drawings and, if you follow Teach-In you will be able to learn, fairly simply, what the various devices actually do.*

## Preferred

I am a beginner in electronics and therefore E.E. is of great interest to me. My only criticism is that in projects such as the *Electro Laugh* (which I shall make in the near future), which are built on Veroboard, you only show the holes round the edge. Construction would be greatly simplified if all the holes were shown, mistakes are hard to avoid as it is. I hope you can put this right soon.

In Mr. Sproston's article *Component Buying & Supplying* he mentioned the notorious F. J. Camm who did not use preferred values for resistors and capacitors. Why have these? Why not have multiples of 1, 2, 3, 4, etc., instead of the E12 series, with the addition of multiples of 1.5, 2.5, 3.5, 4.5, etc., instead of E24 series? This does happen to some extent with electrolytic capacitors. Where do the preferred values derive from originally?


Colin Walls  
Southend-on-Sea.

*We have found from past experience that in most cases when all the holes—or a large number of them—are shown on Veroboard layouts that this tends to make them harder rather than easier to follow. It is a simple matter when constructing a unit to place a transparent ruler along each set of holes to make it easier to follow.*

*Preferred value resistors are necessary because manufacturers would turn out almost any value otherwise. We have the various series of values because they have been calculated so that any specified value can be made up from the fewest possible number of individual preferred values.*

*Everyday Electronics, March 1972*

# BUDGET HIGH-FIDELITY STEREO SYSTEMS

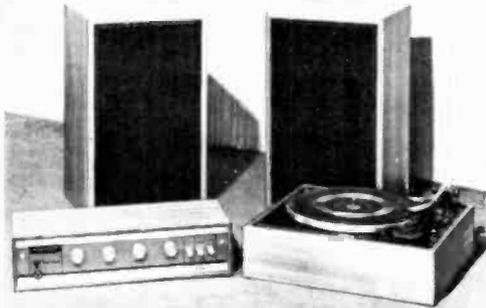

**PREMIER STEREO SYSTEM "ONE"** Consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Mono/Stereo switch, Stereo Headphone socket. Black leatherette cabinet with aluminium front panel. Size: 12½" x 6½" x 2½". (Amplifier available separately if required £16.25. Carr. 40p).

**ONLY £40-95**  
carr. £1.75

**PREMIER STEREO SYSTEM "TWO"**, as above but with Garrard BP25 MK III and magnetic cartridge. **ONLY £48. Carr. £1.75.**

**ONLY £57-75**  
carr. £1.75

**PREMIER STEREO SYSTEM "THREE"**. This consists of KLINGER KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pick-up, tuner, tape in and out. Stereo earphone socket. Garrard BP25 MK. III in teak finish plinth with cover and fitted Sonotone 9TAHC diamond stereo cartridge. A pair of HMF Speakers size 16½" x 10½" x 9" fitted EMI units complete the matching system. **CNLY £57.75. Carr. £1.75.**

**FREE**  
ALL LEADS AND PLUGS SUPPLIED FREE WITH ALL SYSTEMS

## PREMIER HI-FI OFFERS

- Philips 580 Stereo Amplifier (List £29.00) **£21.00**
  - Rogers Ravensbrook II Stereo Amplifier in teak case (List £52.50) **£39.50**
  - Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49.00**
  - Metrosound ST20E Stereo Amplifier in teak case (List £39.50) **£28.50**
  - Golding GL75 less cartridge (List £41.61) **£29.00**
  - Garrard SP25 III with Goldring G800 cartridge (List £28.35) **£15.50**
  - Garrard AP76 less cartridge **£19.50**
  - Garrard 401 Transcription Unit (List £40.15) **£29.00**
  - Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£9.97**
  - Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£12.45**
- Carriage and Insurance 50p extra any item.

## SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.  
Total list price over £34.

**PREMIER PRICE £18.90**  
P. & P. 50p.



### HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.

**£2.47 P. & P.**

STEREO STETHOSCOPE SET Low Imp. £1.25 P. & P. 10p  
MONO STETHOSCOPE SET Low Imp. 52p. P. & P. 10p.




### E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2½in tweeters and crossover network. Impedance 8 or 16 ohm. Handling capacity 10W. Brand new.

**£3.47 P. & P. 40p**
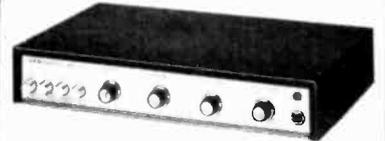
## NEW LOW COST PREMIER 800 STEREO AMPLIFIER



A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1% Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 180mV. Din sockets for inputs and outputs. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 6½" x 2½".

**ONLY £16.25 Carr. 40p.**



**WELLER "EXPERT" SOLDER GUN.** Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. **£4.25 P & P 30p**



"Marksmen" Soldering Iron. Lightweight ¼" pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. £1.50 P & P 15p



### TAPE CASSETTES

C60 (60 min.)	37p	3 for £1.06
C90 (90 min.)	62p	3 for £1.80
C120 (120 min.)	87p	3 for £2.55

P. & P. 5p.

**FREE CASSETTE HEAD CLEANER** with every 10 cassettes purchased.

All cassettes can be supplied with library cases at 3p. extra each

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP5 3" 250' P.V.C.	25p	LP6 6½" 1800' P.V.C.	75p
TT3 3" 450' POLYESTER	37p	DT6 6½" 1800' POLYESTER	£1.12
DT3 6½" 600' POLYESTER	57p	TT6 6½" 2400' POLYESTER	£1.27
BP5 5" 600' P.V.C.	48p	SP7 7" 1800' P.V.C.	55p
LP6 5" 900' P.V.C.	50p	LP7 7" 1800' P.V.C.	75p
DT5 5" 1800' POLYESTER	75p	DT7 7" 2400' POLYESTER	£1.25
		TT7 7" 3600' POLYESTER	£2.50

TAPE SPOOLS 3" 5p, 5", 6½", 7" 9p, Post and Packing 3" 5p, 5", 6½", 7" 10p. (2 reels and over Post Free).



# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



# TECHNICAL TRAINING

## *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns. Certs.
  - Radio Amateurs' Examination
  - General Radiocommunications Certificate.
  - C. & G. Radio Servicing Theory.
  - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics



### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. FA 26, Intertext House, Stewarts Road, London, SW8 4UJ

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).....

NAME..... AGE.....  
(Block Capitals Please)

ADDRESS .....

2/72

Member of the ABCC

Accredited by the CACC

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

# DISCOUNTS UP TO

## 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons GUARANTEED 12 MONTHS.

AKAI · LEAK · SINCLAIR · TELETON · ARMSTRONG · ROTEL  
THORENS · PHILIPS · GOLDRING · ROGERS · PIONEER

### SPECIAL OFFER £18

Garrard SP25 Mk. III  
Goldring G800H  
Teak plinth and tinted cover.  
Ready wired for immediate use.  
Please add £1.25 for post and packing.

Sinclair 2000 Mk. II	£21.50
Sinclair 3000	£29.75
Sinclair PRO 60/2+Z30 PZ5	£15.75
Sinclair PRO 60/2+Z30 PZ6	£17.75
Sinclair PRO 60/2+Z50 PZ8/Trans.	£22.95
Sinclair AFU	£4.70
Sinclair 605 (New Product)	£20.50
Goodmans' Max. Amp.	£37.95
Teleton SAQ206B (New Prod)	£17.95
Wharfedale	£42.25
Sinclair IC12 Integrated circuit amplifier	£1.85
Eagle TSA149 7wRMS	£24.95
Eagle TSA151 15w RMS	£34.50

### TURNTABLES

Please add 50p for P. & P.  
\*Garrard 1025T with Cart-ridge ... £5.97  
Garrard SP25 Mk. III ... £10.95  
Garrard Zero 100—Auto (New Product) ... £41.25  
Garrard Zero 100—Single Play (New Product) ... £38.25  
Garrard 2025TC with Sonotone 9TAHC ... £9.20  
Garrard SL65B ... £13.95  
Garrard AP76 ... £20.25  
Garrard 401 ... £27.95  
BSR MP60 ... £10.00  
Pioneer PL12AC ... £36.00  
Thorens TD125 ... £62.50  
Thorens 150AB11 ... £42.50  
Goldring GL72/2 ... £21.75  
Goldring GL72/P2 ... £27.20  
Goldring GL75 ... £27.95  
Goldring GL75P ... £35.95

### CARTRIDGES

Please add 10p for P. & P.

Goldring G850	£3.65
Goldring G800	£6.25
Goldring G800E	£10.50
Goldring G800SE	£15.50
Sonotone 9TAHC Diamond	£1.45
Shure M3DM	£4.50
Shure M445/7 C	£7.00
Shure M55E	£8.75
Shure M75E	£12.45
Shure V15 Type 2	£27.75
Shure M44E	£7.25
Shure M31E	£8.50
Shure M32E	£8.00
Audio-Technica AT35	£6.95
*GCS 36	£4.95
	95p

### AMPLIFIERS

Please add 50p for P. & P.

Alpha Highgate FA400	£33.00
Armstrong 521 (cased)	£44.50
Amstrad 8000 Mk. II	£16.95
Leak IC2000	£29.95
Leak 30 Delta Range (New Product)	£51.00
Leak 70 Delta Range (New Product)	£61.00
Metrosound ST20E	£26.00
Philips R580	£18.00
Pioneer SA600 (New Prod)	£65.00
Pioneer SA700	£92.00
Pioneer SA900	£92.00
Rogers R/brook Chassis	£35.50
Rogers R/brook Cased	£39.50
Rogers R/bourne Chassis	£44.00
Rogers R/bourne Cased	£48.50
Sansui AU101	£32.00
Rotel RA301	£32.75
Rotel RA601	£49.80
Tripletone 800 amp Series 3	£28.50
Europhon 10+10	£16.95
Goldring Lenco 15 watts	£32.95

### PLINTHS & COVERS



£3.20\*

(As illustrated)  
Plus 35p post and packing  
Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard SP25, 2025TC, 3000, AT60, 2000, 2500, 3500, 5100, 1025, SL65B. Also for BSR, McDonald MP60 and others.

For AP76, AP75, SL72B, SL75, SL95B. \*£4.20 plus 55p P. & P. Also finished in walnut to match Japanese equipment—at no extra charge.

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. E.E.5 174 Pantonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS. Please note that cheques can only be accepted together with cheque cards (not Barclay Card)

2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

REMEMBER  
TO USE THE  
POSTCODE



# Readers Letters

## The Bug

I don't know whether I should express my thanks for your new publication, or whether I would be perhaps better advised by my inner self to make this a letter of condemnation of you and your colleagues!

The reason for this indecision on my part, as you may have already guessed, is that I have been well and truly bitten by "the bug." Since I first picked up *E.E.* in my local newsgent just before Christmas my diet has been one entirely made up of resistors, capacitors, and other mysterious ingredients, some more indigestible than others! I have now devoured two issues of *E.E.* and two of big brother *P.E.* but my appetite shows no sign of abating.

Since cutting my teeth on Meccano many years ago I have always been a dabbler, and have run the whole gambit of the more "fiddling" pastimes—model-making, marquetry, fretwork, paper-folding, printing, in fact any hobby that can be enjoyed in a reasonably small space. But until now the radio/electronics world had remained totally incomprehensible, then along comes *E.E.* and suddenly I begin to get a glimmer of light through the haze and glimpse a whole new area of pleasant and useful activity. Or to come back to earth and use my wife's expression "I see we have a new collection of gadgets cluttering up the kitchen!"

Anyhow, for better or worse, the die has been cast and I am anxious to try out my new soldering iron, and actually construct something. Trouble is, for a couple of reasons, progress is not what I had hoped it might be, and I have yet to hear the first cries of my first-born electronic creation, and am still being denied the heart-warming patter of tiny oscillators!

You see, first of all as a complete absolute beginner, there are many things not covered by "first-step" *Teach-In* type articles. What is needed is a couple of really basic articles which assume no pre-knowledge at all. For example, what sort of wire do I use for connecting components;

How does one *actually* mount components on to various types of perforated board; what is used for connecting links (in illustrations e.g. January cover—Laugh Simulator—it looks like bare wire of paper clip proportions). It is the same with books borrowed from library—components are explained in great detail, but the ordinary bricks and mortar are largely ignored.

J. G. Richards  
Sale.

*The bare wire used for connecting components on a circuit board is normally 22 s.w.g. tinned copper wire—as used for the soldering exercises in Teach-In part 1. Where necessary single strand covered wire may also be used. The Using Printed Wiring Board article in our first issue deals with the component mounting question and Shop Talk this month refers to Veroboard.*

## Laugh

I am a very keen reader of your magazine and although electronics in today's form is fairly new to me I have tried several of your projects (with great success) and find them very well explained and easy to construct. I must however tell you about one of them in the January edition, the *Electro Laugh*. I set to work and constructed this project only to find that it would not work. After checking my wiring several times I was about to give up when I discovered (by referring to the circuit diagram) that you have made a mistake. I refer to Fig. 4. This shows the copper strip on the Veroboard as being cut at point Q24 when in fact it should not be cut at all. After soldering a piece of wire across this cut I found that the laugh simulator worked quite well.

Brian Wadsworth  
Staffs.

*This point may help some readers who are having similar troubles. There is actually no mistake in the Electro Laugh wiring, this difficulty has arisen because a link shown under C6 in Fig. 3 has become obscured. Reference is made to this project in Shop Talk this month.*

## Connections

I am writing to you, concerning the *Astron M.W. Receiver*. I followed the instructions very carefully not forgetting to solder the transistors as requested, on completion I switched on expectingly, but alas, there was no sound apart from the faintest crackling when I switched on. Determined not to be dismayed I checked and rechecked the circuit, till it came to my notice that D1 and D2 in Fig. 1 did not show the same polarities as in Fig. 3. Where upon I reversed the polarities of D1 and D2 to correspond with Fig. 1 but still the result was the same, next I noticed that TR1 and TR2 in Fig. 3 were facing in opposite directions yet they are both *n.p.n.* and have the same value, could you please advise.

M. Torpey  
Wood Green.

*The diode connections are correct in both Figs. 1 and 3, the positive sign on the diodes corresponds to the arrow head in the circuit symbol.*

*It would seem that you have been misled by the perspective view of the transistors in Fig. 3. Both TR1 and TR2 face the same way, the leads have been shown bent in different directions for clarity. When wiring in transistors refer to the base diagram (shown between the two parts of Fig. 3 in this case) and the lead markings on the wiring diagram.*

*Some points concerning construction of the Astron\* are also given in Shop Talk this month.*

## Further Control

I have experienced a similar difficulty with the *Windscreen Wiper Control* as mentioned by Mr. Bacon in your January issue, the maximum delay being seven seconds.

I adjusted R2 to the point of cut-off, disconnected the negative end and found the sum of R2 plus R3 was 200 kilohms. As no adjustment of values at this point could be helpful, I reconnected R2, disconnected C2 and found the control operated normally.

As C2, on test, was satisfactory, I reconnected it with a 125 ohm resistor in series and this achieved the desired result, the delay being variable from five to thirty seconds with R2 operational over the full range.

J. Roscoe  
Cheshire.

*From this letter it would seem that the problem can be caused by leakage through C2. Readers can either fit a resistor in series or try another capacitor for C2.*

# G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

## NEW LINES I.I.I.I.I

E.M.I. Speakers with twin tweeters ...	£3.75
8 watt amplifiers complete ...	£2.80
Cassette Tapes: C60, 57p; C90, 75p; C120, 90p	
<b>GOLDRING MAGNETIC CARTRIDGES (G850)</b>	
Cardioid Ball type Mikes (usually £6-60)	£4.75
Intercom with Battery & Lead	£3.75
Neons, with resistor and 2 ft lead	£2.50
Speakers, 8 ohm, 2 1/2 in	5p
MULLARD DATA BOOK FOR 1972	30p

## TRANSISTOR EQUIVALENT BOOK, LATEST EDITION

Mikes, Low impedance, dynamic stick type with on/off switch	£1.00
.. Crystal, hand	50p
.. Crystal, Inserts with bracket	20p
Lockable car aerials	20p
Dee-Gee 25 watts pencil bit soldering irons	£1.25
Speakers, 2 1/2 in, 8 ohms	98p
Insulating Tape, 1/4 in wide, 10 yard rolls	30p
Miniature Output Transformers	5p
Rotary Switches, 4 pole 3 way or 2 pole 6 way	15p
Switch cleaner, aerosol cans	50p

## Electrolytic Capacitors

2,000 µf 25 volt Rev. ....	25p	Miniature type. Both wires same end.	
1,000 µf 70 volt	35p	5 µf 10 volt	} 3p each
10,000 µf 35 volt	35p	10 µf 10 volt	
10,000 µf 25 volt	35p	30 µf 10 volt	
2,000 µf 18 volt	20p	50 µf 10 volt	
60 µf ... 200 µf 300 volt	30p	<b>Axial leads</b>	
400 µf 275 volt	25p	250 µf 25 volt	10p
10 µf 6 volt	2p	500 µf 25 volt	15p
10 µf 25 volt	4p	1,000 µf 25 volt	25p
16 µf 250 volt	8p	2,000 µf 25 volt	25p
32 µf 275 volt	8p	400 µf 40 volt	20p

## STOCKTAKING CLEARANCE! IMPOSSIBLE TO REPEAT!

We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sell only by weight.

Gross weight 2 lb	£1 (postage 20p)
Gross weight 5 lb	£2 (postage 30p)

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.

## UNBEATABLE PRICE ! ! ! !

LINEAR INTEGRATED CIRCUITS. Direct from manufacturer, all 100% to specification.

709C	35p	100 up	24p
741C	50p	100 up	35p

## VEROBOARD

2 1/2 in x 1 in x 0.15 in 6p	5 in x 3 1/2 in x 0.15 in 28p	3 1/2 in x 3 1/2 in x 0.1 in 24p
3 1/2 in x 2 1/2 in x 0.15 in 16p	17 in x 2 1/2 in x 0.15 in 55p	5 in x 2 1/2 in x 0.1 in 23p
3 1/2 in x 3 1/2 in x 0.15 in 20p	17 in x 3 1/2 in x 0.15 in 74p	5 in x 2 1/2 in x 0.1 in 28p
5 in x 2 1/2 in x 0.15 in 20p	3 1/2 in x 2 1/2 in x 0.1 in 21p	
Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0-1 or 0-15) 36 for 18p.		
Special Offer Pack consisting of 5 2 1/2 in x 1 in boards and a Spot Face Cutter—50p.		

**RECORD PLAYER CARTRIDGES.** Well below normal prices!  
 G90 Magnetic Stereo Cartridges, Diamond Needle, 6mV output, £2.75. ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible, Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1.25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1.63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1.50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1.88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1.25.

**TRANSISTORISED FLUORESCENT LIGHTS,** 12 volt. All with reverse polarity protection. 8 watt type with reflector, suitable for tents, etc., £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch, 22 in x 2 in x 1 in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.

## MULLARD POLYESTER CONDENSERS

1,000pF, 1,200pF, 1,500pF, 1,800pF, 2,200pF, 15p per dozen (all 400V working). 0.15µf, 0.22µf, 0.27µf, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

## RESISTORS

1/2 and 1 watt. Most values in stock, 75p per 100. 10p per dozen of any one value. WIRE WOUND MAINS DROPPERS. Hundreds of values from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered 'assorted' at 50p per dozen.

# NEW B.V.A. VALVES

Full list. Return Post Service. Cash with order. Stamped addressed envelope. Post Free over £3.00 order.

DY86/7	40p	U25	75p	OC41	13p
EB91	25p	U26	75p	OC44	13p
ECC82	42p	U37	75p	OC83	45
ECC80	40p	U191	72p	71	13p
EF80	40p	U193	41p	72	13p
EF85	41p	U251	87p	73	13p
EF183/4	56p	6/30L2	77p	81	17p
EH90	51p	6AT6	49p	OC81D	13p
EY51	37p	6BW7	69p	OC83	20p
PC86	51p	6CD6	140p	OC170	23p
PC97	41p	6F23	77p	OC171	23p
PC900	51p	20L1	97p	OC200	25p
PCC84	46p	20P4	100p	OC201	25p
PCC89	61p	30C15	69p	2N3819FET	45p
PCF80	51p	30C17	79p		
PCF86	61p	30F5	82p	<b>POWER TRANSISTORS</b>	
PCF80 1/2	61p	30FL1	64p	OC26	25p
PCF805	65p	33FL2	64p	28	30p
PCF808	67p	30L15	76p	35	25p
PCL82	52p	30L17	72p	AD149	30p
PCL83	61p			2N3055	63p
PCL84	51p	<b>TRANSISTORS</b>		D2008B	100p
PCL805	57p	AC107	15p		
PCL86	51p	126	13p	<b>DIODES</b>	
PL36	75p	127	17p	BY127	20p
PL81	57p	128	13p	BY133	20p
PL83	51p	176	25p	30P12	77p
PL84	60p	ACY17	15p	30PL1	64p
PL500	85p	AF239	37p	30P4MR	100p
PL504	85p	AF186	50p	30P19	75p
PY81	45p	AF139	37p	30PL13	92p
PY82	35p	BC108	13p	30PL14	92p
PY800/1	45p	107	13p	30PL15	92p
R19	65p	BF194	15p		

## R. J. BENNISON

WHOLESALE SUPPLIES

1 WHARFE DALE PLACE, HARROGATE

## The most accurate pocket size CALCULATOR in the world

The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send £4.50 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

**CARBIC LTD.** (Dept. EE2)  
 54 Dundonald Road, London, SW19 3PH.



**FREE**  
 BOOKLET ON REQUEST

## WILSIC SOUND EFFECTS KITS WAH-WAH PEDAL KIT (Illustrated)



Kit comprises a SELECTIVE AMPLIFIER MODULE KIT to convert the FOOT VOLUME CONTROL PEDAL (as photo) to Wah-Wah operation. Amplifier module £1.75, pedal unit £5.13. COMPLETE KIT £6.50 add 38p for assembly of module, but please note we cannot supply kits fully built.

**REVERBERATION UNIT KIT.** For dimension effect. Connects between sound source, mic., etc., and amplifier. Battery powered. COMPLETE KIT £9.20 (excluding case £7.50). Assembled in slimline cabinet £12.50. **VIBRATO UNIT KIT.** Foot pedal unit with variable speed and depth controls. COMPLETE KIT £5.25. SEND 15p for the WILSIC PLANS BOOK, with full details of these kits; circuits, drawings and price lists.

LATEST CATALOGUE 5p (stamps)  
**WILSIC ELECTRONICS LTD.**  
 6 COPLEY ROAD, DONCASTER, YORKS.

# BI-PRE-PAK



**TELEPHONE DIALS**  
Standard Post Office type.  
Guaranteed in working order.  
**ONLY 50p**

**8 RELAYS FOR £1**  
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

### NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries, 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors, Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors, Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs, 1000 PIV, 1 amp, plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoiled black glass type PNP Germ.	50p
H19	10	OC81/81D uncoiled white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoiled TO-5 can	50p
H29	20	OA47 gold bonded diodes coded HC52	50p

### NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, B5Y95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW, Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

### MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



### OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulat. on.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.

### FULLY TESTED AND MARKED SEMICONDUCTORS

AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC107	0-13	2N1308-9	0-35
BC108	0-13	2N3819FET	0-45
BC109	0-14		
BF194	0-15	<b>Power Transistors</b>	
BF274	0-15	OC20	0-50
BFY50	0-20	OC23	0-30
BSY25	0-57	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-15	AD149	0-30
OC41	0-13	AU710	1-25
OC44	0-13	25034	0-25
OC45	0-13	2N3055	0-50
OC71	0-13		
OC72	0-13	<b>Diodes</b>	
OC81	0-13	AAV42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9144	0-07

### F.E.T. PRICE BREAKTHROUGH !!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3B23E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each



### BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706, 6A/B, B5Y26-29, B5Y95A, ECY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to B-113/4, BC153/4, BF153/160, etc. £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3B23E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

#### 1 amp Miniature Plastic Diodes:

IN4001, 500+ at 4p each; 1,000+ at 3p each.  
IN4004, 500+ at 5p each; 1,000+ at 3p each.  
IN4006, 500+ at 6p each; 1,000+ at 5p each.  
IN4007, 500+ at 8p each; 1,000+ at 7p each.

### FREE CATALOGUE AND LISTS FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS & SUBSTITUTION CHARTS



### CLEARANCE LINES

#### COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

**NOW ONLY 50p each**  
post and packing 25p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested			
Unmarked	5p	5p	4p
Matchec Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matchec Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7.5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8.2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

#### INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	50p	40p	35p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
PA234 1-watt Audio Amp.	1-00	90p	80p
UL914 Cui-2 1/P Gate	40p	35p	30p

#### LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each  
16 pin type at 16p each.

#### BOOKS

We have a large selection of Reference and Technica Books in stock.

These are just two of our popular lines:  
**B.P.I Transistor Equivalents and Substitutes;** 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.  
**The Hi-Fi Radio Valve & Transistor Data Book 9th Edition;** 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.  
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

**BI-PRE-PAK LTD**

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0782) 46344

**TRANSISTORS**


A SELECTION FROM OUR LIST

AAV30	10p	BD115	75p	OC16	50p	2N1303	18p
AAV42	15p	BD123	85p	OC20	50p	2N1304	22p
AAZ13	10p	BD124	80p	OC22	50p	2N1305	22p
AAZ15	10p	BD131	75p	OC23	60p	2N1306	22p
AAZ17	10p	BD132	80p	OC24	60p	2N1307	25p
AC107	35p	BDY11	10p	OC25	40p	2N1308	25p
AC126	30p	BDY17	10p	OC26	25p	2N1309	25p
AC127	25p	BDY17	10p	OC28	60p	2N1613	20p
AC127Z	50p	BF139	25p	OC71	25p	2N2147	75p
AC128	20p	BDY38	65p	OC35	50p	2N2160	60p
AC176	20p	BDY60	10p	OC36	60p	2N2217	25p
AC187	25p	BF154	20p	OC42	40p	2N2218	20p
AC188	25p	BF155	15p	OC43	50p	2N2218A	20p
ACY17	10p	BF156	20p	OC45	12p	2N2219	20p
ACY18	25p	BF158	15p	OC70	12p	2N2219A	20p
ACY20	20p	BF159	25p	OC71	12p	2N2220	20p
ACY21	20p	BF180	85p	OC72	20p	2N2221	20p
ACY22	10p	BF194	15p	OC75	25p	2N2221A	20p
ACY39	55p	BF195	15p	OC76	25p	2N2222	20p
ACY40	20p	BF196	15p	OC77	40p	2N2222A	20p
ACY44	25p	BF197	15p	OC81	20p	2N2222B	20p
AD140	50p	BF198	15p	OC81D	20p	2N2222C	20p
AD149	50p	BF200	20p	OC82	25p	2N2222D	20p
AD161	35p	BF201	20p	OC83	25p	2N2222E	20p
AD162	35p	BF202	20p	OC84	25p	2N2222F	20p
AF114	25p	BF203	20p	OC139	35p	2N2369A	15p
AF115	25p	BF204	20p	OC140	40p	2N2369B	15p
AF116	25p	BF205	20p	OC141	60p	2N2369C	15p
AF117	20p	BF206	20p	OC170	25p	2N2369D	15p
AF118	60p	BF207	20p	OC171	25p	2N2369E	15p
AF124	25p	BF208	20p	OC201	75p	2N2905A	25p
AF125	20p	BF209	20p	OC202	80p	2N2905B	25p
AF126	20p	BF210	20p	OC203	80p	2N2905C	25p
AF127	20p	BF211	20p	OC204	80p	2N2905D	25p
AF130	20p	BF212	20p	OC205	80p	2N2905E	25p
AF180	50p	BF213	20p	OC206	80p	2N2905F	25p
AF181	45p	BF214	20p	OC207	80p	2N2905G	25p
AF182	45p	BF215	20p	OC208	80p	2N2905H	25p
AF183	45p	BF216	20p	OC209	80p	2N2905I	25p
AF184	45p	BF217	20p	OC210	80p	2N2905J	25p
AF185	45p	BF218	20p	OC211	80p	2N2905K	25p
AF186	40p	BF219	20p	OC212	80p	2N2905L	25p
AF239	40p	BF220	20p	OC213	80p	2N2905M	25p
ASV26	20p	BF221	20p	OC214	80p	2N2905N	25p
ASV27	20p	BF222	20p	OC215	80p	2N2905O	25p
ASV28	20p	BF223	20p	OC216	80p	2N2905P	25p
ASV29	20p	BF224	20p	OC217	80p	2N2905Q	25p
ASV30	20p	BF225	20p	OC218	80p	2N2905R	25p
ASV31	20p	BF226	20p	OC219	80p	2N2905S	25p
ASV32	20p	BF227	20p	OC220	80p	2N2905T	25p
ASV33	20p	BF228	20p	OC221	80p	2N2905U	25p
ASV34	20p	BF229	20p	OC222	80p	2N2905V	25p
ASV35	20p	BF230	20p	OC223	80p	2N2905W	25p
ASV36	20p	BF231	20p	OC224	80p	2N2905X	25p
ASV37	20p	BF232	20p	OC225	80p	2N2905Y	25p
ASV38	20p	BF233	20p	OC226	80p	2N2905Z	25p
ASV39	20p	BF234	20p	OC227	80p	2N2906A	25p
ASV40	20p	BF235	20p	OC228	80p	2N2906B	25p
ASV41	20p	BF236	20p	OC229	80p	2N2906C	25p
ASV42	20p	BF237	20p	OC230	80p	2N2906D	25p
ASV43	20p	BF238	20p	OC231	80p	2N2906E	25p
ASV44	20p	BF239	20p	OC232	80p	2N2906F	25p
ASV45	20p	BF240	20p	OC233	80p	2N2906G	25p
ASV46	20p	BF241	20p	OC234	80p	2N2906H	25p
ASV47	20p	BF242	20p	OC235	80p	2N2906I	25p
ASV48	20p	BF243	20p	OC236	80p	2N2906J	25p
ASV49	20p	BF244	20p	OC237	80p	2N2906K	25p
ASV50	20p	BF245	20p	OC238	80p	2N2906L	25p
ASV51	20p	BF246	20p	OC239	80p	2N2906M	25p
ASV52	20p	BF247	20p	OC240	80p	2N2906N	25p
ASV53	20p	BF248	20p	OC241	80p	2N2906O	25p
ASV54	20p	BF249	20p	OC242	80p	2N2906P	25p
ASV55	20p	BF250	20p	OC243	80p	2N2906Q	25p
ASV56	20p	BF251	20p	OC244	80p	2N2906R	25p
ASV57	20p	BF252	20p	OC245	80p	2N2906S	25p
ASV58	20p	BF253	20p	OC246	80p	2N2906T	25p
ASV59	20p	BF254	20p	OC247	80p	2N2906U	25p
ASV60	20p	BF255	20p	OC248	80p	2N2906V	25p
ASV61	20p	BF256	20p	OC249	80p	2N2906W	25p
ASV62	20p	BF257	20p	OC250	80p	2N2906X	25p
ASV63	20p	BF258	20p	OC251	80p	2N2906Y	25p
ASV64	20p	BF259	20p	OC252	80p	2N2906Z	25p
ASV65	20p	BF260	20p	OC253	80p	2N2907A	25p
ASV66	20p	BF261	20p	OC254	80p	2N2907B	25p
ASV67	20p	BF262	20p	OC255	80p	2N2907C	25p
ASV68	20p	BF263	20p	OC256	80p	2N2907D	25p
ASV69	20p	BF264	20p	OC257	80p	2N2907E	25p
ASV70	20p	BF265	20p	OC258	80p	2N2907F	25p
ASV71	20p	BF266	20p	OC259	80p	2N2907G	25p
ASV72	20p	BF267	20p	OC260	80p	2N2907H	25p
ASV73	20p	BF268	20p	OC261	80p	2N2907I	25p
ASV74	20p	BF269	20p	OC262	80p	2N2907J	25p
ASV75	20p	BF270	20p	OC263	80p	2N2907K	25p
ASV76	20p	BF271	20p	OC264	80p	2N2907L	25p
ASV77	20p	BF272	20p	OC265	80p	2N2907M	25p
ASV78	20p	BF273	20p	OC266	80p	2N2907N	25p
ASV79	20p	BF274	20p	OC267	80p	2N2907O	25p
ASV80	20p	BF275	20p	OC268	80p	2N2907P	25p
ASV81	20p	BF276	20p	OC269	80p	2N2907Q	25p
ASV82	20p	BF277	20p	OC270	80p	2N2907R	25p
ASV83	20p	BF278	20p	OC271	80p	2N2907S	25p
ASV84	20p	BF279	20p	OC272	80p	2N2907T	25p
ASV85	20p	BF280	20p	OC273	80p	2N2907U	25p
ASV86	20p	BF281	20p	OC274	80p	2N2907V	25p
ASV87	20p	BF282	20p	OC275	80p	2N2907W	25p
ASV88	20p	BF283	20p	OC276	80p	2N2907X	25p
ASV89	20p	BF284	20p	OC277	80p	2N2907Y	25p
ASV90	20p	BF285	20p	OC278	80p	2N2907Z	25p
ASV91	20p	BF286	20p	OC279	80p	2N2908A	25p
ASV92	20p	BF287	20p	OC280	80p	2N2908B	25p
ASV93	20p	BF288	20p	OC281	80p	2N2908C	25p
ASV94	20p	BF289	20p	OC282	80p	2N2908D	25p
ASV95	20p	BF290	20p	OC283	80p	2N2908E	25p
ASV96	20p	BF291	20p	OC284	80p	2N2908F	25p
ASV97	20p	BF292	20p	OC285	80p	2N2908G	25p
ASV98	20p	BF293	20p	OC286	80p	2N2908H	25p
ASV99	20p	BF294	20p	OC287	80p	2N2908I	25p
ASV100	20p	BF295	20p	OC288	80p	2N2908J	25p
ASV101	20p	BF296	20p	OC289	80p	2N2908K	25p
ASV102	20p	BF297	20p	OC290	80p	2N2908L	25p
ASV103	20p	BF298	20p	OC291	80p	2N2908M	25p
ASV104	20p	BF299	20p	OC292	80p	2N2908N	25p
ASV105	20p	BF300	20p	OC293	80p	2N2908O	25p
ASV106	20p	BF301	20p	OC294	80p	2N2908P	25p
ASV107	20p	BF302	20p	OC295	80p	2N2908Q	25p
ASV108	20p	BF303	20p	OC296	80p	2N2908R	25p
ASV109	20p	BF304	20p	OC297	80p	2N2908S	25p
ASV110	20p	BF305	20p	OC298	80p	2N2908T	25p
ASV111	20p	BF306	20p	OC299	80p	2N2908U	25p
ASV112	20p	BF307	20p	OC300	80p	2N2908V	25p
ASV113	20p	BF308	20p	OC301	80p	2N2908W	25p
ASV114	20p	BF309	20p	OC302	80p	2N2908X	25p
ASV115	20p	BF310	20p	OC303	80p	2N2908Y	25p
ASV116	20p	BF311	20p	OC304	80p	2N2908Z	25p
ASV117	20p	BF312	20p	OC305	80p	2N2909A	25p
ASV118	20p	BF313	20p	OC306	80p	2N2909B	25p
ASV119	20p	BF314	20p	OC307	80p	2N2909C	25p
ASV120	20p	BF315	20p	OC308	80p	2N2909D	25p
ASV121	20p	BF316	20p	OC309	80p	2N2909E	25p
ASV122	20p	BF317	20p	OC310	80p	2N2909F	25p
ASV123	20p	BF318	20p	OC311	80p	2N2909G	25p
ASV124	20p	BF319	20p	OC312	80p	2N2909H	25p
ASV125	20p	BF320	20p	OC313	80p	2N2909I	25p
ASV126	20p	BF321	20p	OC314	80p	2N2909J	25p
ASV127	20p	BF322	20p	OC315	80p	2N2909K	25p
ASV128	20p	BF323	20p	OC316	80p	2N2909L	25p
ASV129	20p	BF324	20p	OC317	80p	2N2909M	25p
ASV130	20p	BF325	20p	OC318	80p	2N2909N	25p
ASV131	20p	BF326	20p	OC319	80p	2N2909O	25p
ASV132	20p	BF327	20p	OC320	80p	2N2909P	25p
ASV133	20p	BF328	20p	OC321	80p	2N2909Q	25p
ASV134	20p	BF329	20p	OC322	80p	2N2909R	25p
ASV135	20p	BF330	20p	OC323	80p	2N2909S	25p
ASV136	20p	BF331	20p	OC324	80p	2N2909T	25p
ASV137	20p	BF332	20p	OC325	80p	2N2909U	25p
ASV138	20p	BF333	20p	OC326	80p	2N2909V	25p
ASV139	20p	BF334	20p	OC327	80p	2N2909W	25p
ASV140	20p	BF335	20p	OC328	80p	2N2909X	25p
ASV141	20p	BF336	20p	OC329	80p	2N2909Y	25p
ASV142	20p	BF337	20p	OC330			
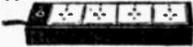
## DISTRIBUTION PANELS

Just what you need for work bench or lab.

4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work. \$3 less plug. \$3-96 with fitted 13 amp plug; \$3-60 with fitted 15 amp plug, plus 29p P. & I.



## RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself! When next one blows. Then reckoning your time at \$1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only \$1 each or \$11 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.



## EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. \$3 plus 30p post and ins.



## MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. 5amp at 50p. Postage 15p for first one then 5p for each one ordered.

## TELEPHONE DIAL

Ex-G.P.O. Perfect working order. 50p each.



## TELEPHONE HAND SET

Ex-G.P.O. Perfect order. 50p each + 20p p. & p.

## SELECTOR SWITCHES

Ex-G.P.O. All in good working order.  
3 pole \$1-25 5 pole \$1-75  
4 pole \$1-50 plus 20p p. & p. 6 pole \$2-00

## KITS FOR PREVIOUS PROJECTS

Kit of parts available as follows—

**HOME SENTINEL INTRUDER ALARM**

Electronic Components with case \$3-75

**SNAP INDICATOR**

All components but not case or battery 75p.

**WINDSCREEN WIPER CONTROL**

Components including metal for chassis \$2.

**RECORD PLAYER**

All components, but not case, loudspeaker, record deck or pick-up \$5-50

**DEMO DECK**

Components as list \$6-75 POST PAID

**FUZZ BOX**

Electronic parts including box \$1-85.

**PHOTOGRAPHIC COLOUR TEMPERATURE METER**

Electronic components less case \$2-65.

**ASTRON RADIO**

All electronic parts less case \$3

**REMOTE TEMPERATURE COMPARATOR**

All electronic parts less case \$4-25.

**ELECTRO LAUGH**

Parts less case \$2

**TRANSISTOR MICROPHONE**

All parts \$1-70

**AUTO ALERT**

All electronic parts and metal bracket \$3-50.

**RAIN WARNING ALARM**

All electronic parts and chassis \$1-30

**WA-WA PEDAL**

All electronic parts \$2-90.

## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 5v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP3, PP4, PP5, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 50p, plus 15p postage.

## MICRO SWITCH

5 amp changeover 5p each. \$1 doz. 15 amp Model 10p each or \$1-00 doz.



## CAPACITOR DISCHARGE CAR IGNITION


### ELECTRONIC IGNITION



This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for improved and even more efficient version (P.W. June), price \$4-95. When ordering please state whether for positive or negative systems. Plus 30p post.
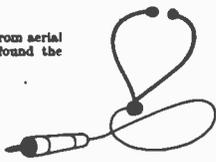
## RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. \$2-45w in stethoscope instead of earpiece 75p extra post and ins. 30p.



## STANDARD WAFER SWITCHES

Standard size 1 1/2" water—silver-plated 5-amp contact. standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	40p							
3 poles	40p	40p							
4 poles	40p	40p							
5 poles	40p	40p							
6 poles	40p	40p							
7 poles	70p	70p							
8 poles	70p	70p							
9 poles	70p	70p							
10 poles	70p	70p							
11 poles	70p	70p							
12 poles	70p	70p							

## TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. \$2-50, 3kW Model as above except 2 kilowatt \$2-80. Don't miss this. Control switch 55p. P. & P. 40p.



## THIS MONTH'S SNIP

### MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into 8 ohms speakers. Input suitable for crystal mic. or pick-up. 9 volt battery operated. Size 2" long x 1 1/2" wide x 1" high. SPECIAL SNIP PRICE 60p each. 10 for \$5.

## POCKET CIRCUIT TESTER

Test continuity for any low resistance circuit house wiring, car electric. Test polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied), 30p or 2 for 50p. Post paid.



# SOIL MOISTURE METER DARKROOM TIMER SIGNAL INJECTOR

and other featured projects. To receive these kits quickly send quoted approx. price and any change due will be refunded.

## INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip OP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over \$5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 50p upwards with circuits and technical data of each. Complete parcel only \$1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.




## BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 5 1/2" x 2" with leads and prods. Price \$1-75 plus 30p postage.

Where postage is not stated then orders over \$5 are post free. Below \$5 add 30p. Semi-conductors add 5p post. Over \$1 post free. S.A.S. with enquiries please.
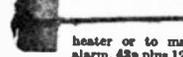
## THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for potter knobs. Quickly adjustable from 30-90°F. 40p. Calibrated dial 50p extra. Suitable box for wall mounting 25p.  
Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-500°F. Internal screw alters the setting to this could be adjustable over 30° to 1000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flame-stat or fire alarm. 45p plus 15p post and insurance.  
Type "D" We call this the 100-stat as it cuts in and out at around freezing point, 3/3 amp. Has many uses one of which would be to keep the loft pipes from freezing. If a length of our blanket wire (16 yd 50p) is wound round the pipes, 40p.  
Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature, 50p.  
Type "F". Glass enclosed for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50° to 150°F. Price 80p.



Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. \$2-95 plus 20p post and insurance.



## TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. \$2-95 plus 20p post and insurance.

## DRILL CONTROLLER NEW I/K/W MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. \$1-50 plus 13p post and insurance. Made up model also available. \$2-95 plus 13p post and p.



## HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermostat as probe. Designer claims temperature control to within 1/10th of a degree. Complete kit with power pack \$5-50.

## AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v. positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. \$5-75 plus 25p post and ins.



## AUTO-LITE

as circuit in Practical Wireless Kit of parts \$1-20 post paid.

## TOGGLE SWITCH

3 amp, 250v. with fixing ring 7 1/2p each, 75p doz.

## CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 25p each or 10 for \$2-42.

## ROCKER SWITCH

15 amp self-fixing into an oblong hole. size approximately 1" x 1 1/2" 6p each. 10 for 54p.

## MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Ex-unused equipment. Size approx. 1 1/2" x 1". Open construction.

Single pole 25p each 10 for \$2-25  
Treble pole 35p each 10 for \$3-15

## BALANCED ARMATURE UNIT

500 ohm, operates speaker or microphone, so useful in intercom or similar circuits. 33p each, \$3-50 doz.

## 2kW FAN HEATER

Three position switching to switch changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit \$3-75. Post and ins. 35p.



**J. BULL (ELECTRICAL) LTD.**  
(Dept. E.E.) 7 Park Street, Croydon CRO 1YD  
Callers to: 162/3 Tamworth Road, CROYDON

# Everyday Electronics Classified Advertisements

RATES: 7p per word (minimum 12 words). Box No. 7p. extra. Semi-display—£4.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

## SERVICE SHEETS

### ★ Service Sheets and Manuals ★

COVERING RADIOS, TELEVISIONS, TAPE RECORDERS, RECORD PLAYERS, ETC. FROM 1933 UP-TO-DATE FROM 40p. EACH - 1971 SERVICE SHEET INDEX LIST 20p. - S.A.E. WITH ENQUIRIES PLEASE

#### 4 NEW BOOKS & PUBLICATIONS

	Price	Post
43. UNDERSTANDING THE SEMICONDUCTOR by C.N. Matthews. 128 pages . . . . .	£1.00	10p
44. TRANSISTOR AMPLIFIERS FOR AUDIO FREQUENCIES by T.Roddam. 264 pages . . . . .	£2.50	20p
45. PHOTO-ELECTRONIC DEVICES by J.B.Danca. 165 pages . . . . .	£2.10	20p
46. AUDIO AMPLIFIERS by Date Publications Ltd. 128 pages . . . . .	£0.55	10p
47. RAPID SERVICING OF TRANSISTOR EQUIPMENT by G.J. King. 160 pages . . . . .	£1.50	15p
48. BEGINNER'S GUIDE TO ELECTRICITY by Clement Brown. Assoc.Brit.I.R.E. . . . .	£1.00	10p
49. BEGINNER'S GUIDE TO ELECTRONICS by Tarance L. Squires. AMIERE . . . . .	£1.00	10p
50. BEGINNER'S GUIDE TO TRANSISTORS by J.W. Reddihough . . . . .	£1.00	10p
51. PRINCIPLES OF SEMICONDUCTORS by M.G. Scroggie. B.Sc.Eng.F.I.E.E. 156 pages . . . . .	£1.50	15p
52. THE PRACTICAL AERIAL HANDBOOK by G.J. King. 232 pages . . . . .	£2.70	20p
53. AERIALS by D.J.W. Sjobbana. Practical Work. 110 pages . . . . .	£0.65	10p
54. ELECTROACOUSTICS: MICROPHONES, EARPHONES AND LOUDSPEAKERS. 300 pages . . . . .	£4.50	30p

Send S.A.E. for 'FREE' List of Practical and Technical Books on Radio & Television now available to -

## BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorkshire. Telephone 0423-86844

## RECEIVERS and COMPONENTS

### JEF ELECTRONICS

#### WE SUPPLY

NEW - BRANDED - GUARANTEED Microcircuits, Transistors, Rectifiers, etc. at highly competitive prices. SN76013N (like super IC12!)-£1.50; 741-36p; 2N3055-50p; 1N4002-4p.

SPECIAL OFFER! 2W AUDIO AMPLIFIER AND PRE-AMPLIFIER COMBINED MICROCIRCUIT-£1.00 only including full instructions and postage and packing.

(E.E.3) York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ.

Mail Order Only. C.W.O. P&P 7p per order. Overseas 50p. Money back if not satisfied.

LIST FREE ON APPLICATION

**DO-IT-YOURSELF**... we stock a large range of audio and electronic components at very competitive prices. e.g.: Chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale & Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for FREE list. (2 x 3p stamps for fabric samples.) Mail-order ONLY. No callers please.

**AUDIOSCAN** Dept. EE372  
4, PRINCES SQUARE, HARROGATE, YORKS.

COMPUTER PANELS 5-BC105, DIODES 15p. post 5p, 4-50p. Post 10p. AMERICAN PANELS TOTAL AT LEAST 50 TRANSISTORS, FIRST GRADE COMPONENTS. 4-55p. Post 10p. ASSORTED PANELS 6-75p. Post 15p. UNIT WITH 4 LAS POT CORES Plus 11 2% CAPACITORS 50p. Post 12p. BINGLES 20p c.p. ORPIL ON PANEL EX EQUIP. 35p c.p. FEBRITE ROD 7 x 1 1/2p. Post 8p each. Post for 5 27p. 10x 7400 SERIES ON PANELS 10-75p. Post 10p. 'FALL OUTS' 5-10p. Post 3p. COPPER CLAD FAXOLIN SINGLE SIDED 8 x 5. 10p. Post 5p each, 13 x 1 1/2. 30p. Post 8p each. SMALL SYNCHRONOUS MOTOR WITH GEAR TRAIN 200-250V. 30p c.p. ELECTROLYTICS 5,000 MFD. 25V. 40p c.p. 25 POSITION SLEEPING SWITCH AC MAINS OPERATED, WITH MAINS RESET. 50p. Post 12p. BANK 10 WIRE WOUND NEONS 30p. Post 7p. ASSORTED TRIMMERS, PRESETS AND MIN. POTS 15-50p c.p. ASSORTED POTS 1/2 SPINDLES SINGLE AND GANGED 15-50p c.p. TRANSFORMER IN DIE CAST BOX MAINS PRIM. SEC 250-0-25 AT 0.65 AMP OR 2 x 15V. 41. Post 25p. SEND LARGE S.A.E. FOR LIST OF PANELS, ETC.

316 ASSORTED PANELS 75p c.p. CONTAIN RES, CAPS, DIODES INDUCTORS, ETC.

### J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCs  
MAIL ORDER ONLY

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

## PRINTED CIRCUITS

MAKE YOUR OWN printed circuits. Industry use etched printed circuits boards because they are the cheapest and most flexible method of mounting components. Now you can make your own. Send £1.20 for your kit today (FREE two circuit diagrams for experimenting) to SPECIALIST ELECTRONICS, P.O. Box 39, 2 Woodland Avenue, Brentwood, Essex.

## EDUCATIONAL

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, T.V., Computers, Draughtsmanship, Building, etc. FREE book from: BIET (Dept. H.23) Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

TECHNICAL TRAINING in Radio, TV & Electronics through world-famous ICS. For details of proven home-study courses write: ICS (Dept. 566), Inter-text House, London, SW8 4UJ. Accredited by the CACC.

## MISCELLANEOUS

RECORD TV SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. CROWBOROUGH ELECTRONICS (E.E.), Eridge Road, Crowborough, Sussex.

## CHROMASONIC electronics

### 1972 CATALOGUE

20p. post free

56 FORTIS GREEN ROAD, LONDON N10 3HN

INDISPENSABLE GUIDE for Hi-Fi equipment; buy Audio Supply's new 100 page photographically illustrated catalogue (60p). Fair cash terms and service. Our associates manufacture records from customers' tapes. Specify requirements to Sound News, 18 Blenheim Road, London, W4 1ES.

UNIMIXER 4S mono/stereo mixing unit £45. Recent reviews, specs. from manufacturers; Soundex Ltd., 18 Blenheim Road, London, W4 1ES.

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW  
S.A.E. for details

TO: BOFFIN PROJECTS'  
DEPT. KEE.  
4 CUNLIFEE ROAD,  
STONELEIGH, EWELL, SURREY

## PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN. TRIAL KIT (36 sq. in.) . . . £1.28 carr. pd. No. 1. KIT (54 sq. in.) . . . £1.88 carr. pd. No. 2. KIT (72 sq. in.) . . . £2.39 carr. pd. MPE Ltd., Dpt D.E. Bridge St. Clay Cross, Derbys

## Build your EE circuit on a

# NIPPBOARD

Printed wiring board for transistor circuits

EE Windscreen Wiper Control	—Type 1B
EE Fuzz Box	—Type 1A
EE Astron Medium Wave Receiver	—Type 1A
EE Remote Temperature Comparator	—Type 1A
EE Transistor Microphone	—Type 1A
EE Electro Laugh	—Type 2A
EE Waa-Waa Pedal	—Type 2A
EE Rain Sensor	—Type 1A

Also suitable for other E.E., P.E., P.W. projects  
S.R.B.P. FIBREGLASS

1A	15p	2AS	28p	1B	18p	2BS	34p
2A	28p	4AS	44p	2B	34p	4BS	52p
3A	36p	6AS	60p	3B	43p	6BS	72p
5A	52p	10AS	90p	5B	62p	10BS	£1.10

## NIP Electronics

DEPT. NB/EE, P.O. BOX 11, ST ALBANS, HERTS.

## 12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3.30** post paid  
or in kit form **£2.90**

Easy to construct  
SALOP ELECTRONICS Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire Large S.A.E. for lists

### JOHN SAYS...

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable FI/F2 rejection. Module £7. Unit £8-90. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. Only £2-95. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrok etc. costs £18-00 in modules. **SYNTHESIZER MODULES** and other miracles. Send 15p for illust. list. D.E.W. Ltd., 254 Ringwood Road, Farndon, Dorset.

# A CATALOGUE

Is the first step to a successful electronic building project. Beginners and experts alike can select their needs from a catalogue which shows the wealth of Professional components distributed by R.S. Components Ltd. (formerly Radiospares). Every Radiospares item specified in constructional features can be supplied, just as quickly as the postman can get to your home.

ALL LISTED COMPONENTS ARE POST PAID TO YOUR HOME IN THE U.K. STRICTLY MAIL ORDER ONLY.

SEND ONLY 25p FOR YOUR COPY OF THIS INVALUABLE 96-PAGE CATALOGUE TO:-

## CELECTRON-E

MAIL ORDER ELECTRONIC COMPONENTS  
P.O. Box No. 1,

Llantwit Major, Glamorgan CF6 9YN

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 36 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4-OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 20 Resistors, 14 Capacitors, 3 GET #72, 3 GET #72B, 1 GET #75. All long leaded on panels 13in x 4in. 4 for £1. P. & P. 25p.

**709C OPERATIONAL AMPLIFIER T05**  
8 lead I.C. 1 off 50p. 50 off 35p.  
100 off 20p.

**250 MIXED RESISTORS** 62p  
½ & 1 watt.

**150 MIXED HI STABS** 62p  
½ & 1 watt 5% & better.

### QUARTZ HALOGEN BULBS

With long leads, 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

### QPO EXTENSION TELEPHONES

with dial but without bell. 95p each. P. & P. 30p. £1-75 for 2. P. & P. 50p.

### BARGAIN RELAY OFFER

Single pole change over silver contacts 26V to 60V. 2-5kΩ coil. 8 for 50p. P. & P. 5p.

**KEYTRONICS** mail order only  
44 EARLS COURT ROAD  
LONDON, W.8 01-478 8499

### BOOINE TYPE N.C.I. GEARED MOTOR



(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 50 cycle. 0-38 amp (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, 0-28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3-15 plus 3p P. & P. or less transformer £2-13 plus 27p P. & P.

### 12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3750 RPM complete with external gear train (removable) giving final speed of approx. 125 RPM. Size 4½" x 2½" dia. Price 95p incl. post.

### 230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox.

1 R.P.M. cw 1 R.P.H. A/cw 10 R.P.H. A/cw  
2 R.P.H. cw 15 R.P.H. A/cw  
60 R.P.M. cw 3 R.P.H. A/cw 20 R.P.H. cw  
6 R.P.H. cw 30 R.P.H. cw

cw = Clockwise. A/cw = Anti-clockwise rotation.

Fraction of makers' price. All at 75p incl. P. & P.

### G.E.C. 12 WAY 15 AMP. CONNECTORS

NEW in maker's carton. BAKELITE £1-25 per doz.

FLEXIBLE £1-50 per doz. Post paid (Minimum 1 doz.).

### PROGRAMME TIMERS

(Mfr. by 'Magnetic Devices Ltd.')

240v A.C. 5 r.p.m. 'Crouzet' motor. Drives 15 cams, each operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW PRICE: £5-75. P. & P. 25p.

### ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octave (less one and flat). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3-00. P. & P. 22p.

### 50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering. No special tools required. The kit includes: Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7-75. P. & P. 30p.

### CRYSTAL RADIO KIT

Complete set of parts, including Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering. Easy to build, full step by step instruction. £1-75 incl. post.

### VENNER Electric Time Switch

200/250V Exc. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2-75, 15A £3-25, 20A £3-75. P. & P. 20p. Also available with solar dial ON dusk. OFF dawn. Price as above.

### MICRO SWITCH

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 incl. post. (Min. order 20)

### "HONEYWELL" LEVER OPERATED MICRO SWITCH

15 amps. 250 volt A.C. c/o contacts. NEW in maker's Carton. Price: 10 for £1-90 incl. P. & P.

### VARIABLE VOLTAGE TRANSFORMERS

INPUT 230,140V a.c. 50,60 OUTPUT

VARIABLE 0.260V

All Types (and Spares)

from ½ to 50 amp from stock.

### SHROUDED TYPE

1 amp, £7-00 2-5 amp, £8-05  
5 amp, £11-75  
10 amp, £22-50 20 amp, £49-00  
15 amp, £25-00 25 amp, £58-00  
37-5 amp, £82-00 50 amp, £98-00

All plus £1-00 cart. where not specified.

OPEN TYPE (Paned Mounting) ½ amp, £4-75.  
1 amp, £7-00 2½ amp, £8-05. Carr. 40p on open type.




### Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A. 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2-5 kΩ, 140 mA. Diameter 3in Shaft length 7in, dia. 1½in. All at £1-50 each. P. & P. 5p.

50 WATT. 1/5/10/25/50/100/250/500/111/1-5/2-5/5kΩ. All at £1-12 each. P. & P. 11p.

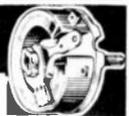25 WATT. 10/25/50/100/250/500/111-1-5/2-5/3-5/5kΩ. All at 78p each. P. & P. 15p



### STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R., Unijunction Xenon tube and instructions £6-30, plus 25p P. & P.

**NEW INDUSTRIAL KIT**

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10-50. P. & P. 50p.

**HY-LYGT STROBE MK III**

This strobe has been designed and produced for use in large rooms, halls and the photographic field and utilises a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12-00. P. & P. 50p. **SPECIALLY DESIGNED. FULLY VENTILATED METAL CASE.** Including reflector. £4-00 P. & P. 45p Post paid with kit.

### THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Light strobe. Incorporating:

- Heavy duty power supply.
  - Variable speed from 1-23 flash per sec.
  - Reactor control circuit producing an intense white light.
- The brilliant light output of the "SUPER" HY-LYGT gives fabulous effects with colour filter.  
Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P. **ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE** specially designed for the Super Hy-Light Kit including reflector £7-00 P. & P. 45p. 7-inch **POLISHED REFLECTOR** Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.

### RELAYS New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

1	2	3	4	1	2	3	4
45	6-9	2 HD M	50p	700	15-35	2 c/o HD	73p*
185	12-18	4 c/o	73p	700	16-24	6M	63p*
280	9-12	2 c/o	73p*	1,250	24-36	4 c/o	63p*
600	18-32	4 c/o	78p*	2,500	36-45	6M	63p*
700	16-24	4M 2B	63p*	2,400	30-48	4 c/o	50p*
700	16-24	4 c/o	78p*	9,000	40-70	2 c/o	50p*
700	12-24	2 c/o	63p*	15k	85-110	6M	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. \*Including Base.

### 12 VOLT D.C. RELAY

Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)

### "DIAMOND H" 230 VOLT A.C. RELAYS (UNUSED)

Three sets c/o contacts rated at 5 amps. Price: 50p P. & P. 10p. (100 lots £40-00 incl. P. & P.)

### "KEY SWITCH" 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. BOXED. Price: 40p. P. & P. 5p. (100 lots £32-00 incl. P. & P.)

### 230 VOLT A.C. SOLENOID OPERATED L.P. VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1½ b.s.p. inlet/outlet. Precision made, British mfg. Price £1-75. P. & P. 20p. Special quotation for quantity.



# SERVICE TRADING CO

All Mail Orders—Also Callers—A ample Parking Space  
Dept. E.E. 57 BRIDGMAN ROAD, LONDON, W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.  
9 LITTLE NEWPORT ST.  
LONDON WC2H 7JJ 01-437 0579

**BRAND NEW GUARANTEED**

**SEMICONDUCTORS & COMPONENTS**  
SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

**RETURN OF POST SERVICE**

**TRANSISTORS**

20301	20p	2N3404	32p	40310	45p	BC212L	18p	B8X28	32p	NKT281	27p
20302	20p	2N3405	45p	40311	55p	BCY30	27p	B8X30	27p	NKT401	87p
20303	20p	2N3412	25p	40312	55p	BCY31	27p	B8X61	25p	NKT402	90p
20304	20p	2N3413	25p	40313	47p	BCY32	50p	B8X76	25p	NKT403	75p
20308	30p	2N3416	37p	40320	27p	BCY33	25p	B8X77	27p	NKT404	62p
20309	30p	2N3417	37p	40323	32p	BCY34	30p	B8X78	27p	NKT405	75p
20371	15p	2N3570	11.25	40324	47p	BCY38	40p	B8Y10	27p	NKT406	62p
20374	20p	2N3572	97p	40326	37p	BCY39	60p	B8Y11	27p	NKT451	68p
20381	22p	2N3605	27p	40329	30p	BCY40	50p	B8Y24	15p	NKT452	62p
2N404	22p	2N3606	27p	40344	27p	BCY42	15p	B8Y25	15p	NKT453	47p
2N495	20p	2N3607	27p	40347	57p	BCY43	15p	B8Y26	17p	NKT603F	32p
2N697	17p	2N3702	11p	40348	52p	BCY44	22p	B8Y27	17p	NKT613F	32p
2N698	25p	2N3703	10p	40360	42p	BCY58	22p	B8Y28	17p	NKT674F	30p
2N706	12p	2N3704	11p	40361	47p	BCY59	22p	B8Y29	17p	NKT677F	30p
2N705A	12p	2N3705	10p	40362	57p	BCY67	97p	B8Y32	25p	NKT713	25p
2N708	15p	2N3706	09p	40379	32p	BCY70	20p	B8Y36	25p	NKT781	30p
2N709	22p	2N3707	11p	40406	57p	BCY71	25p	B8Y37	25p	NKT10419	30p
2N718	25p	2N3708	07p	40407	40p	BCY72	17p	B8Y38	22p	NKT10439	30p
2N725	30p	2N3709	09p	40408	52p	BCY20	27p	B8Y39	22p		37p
2N727	30p	2N3710	09p	40410	52p	BCZ11	42p	B8Y40	22p	NKT10619	37p
2N914	17p	2N3711	12p	40487A	57p	BD118	11.18	B8Y51	32p		32p
2N916	17p	2N3715	11.25	40488A	57p	BD121	65p	B8Y52	32p	NKT20329	47p
2N918	30p	2N3716	11.30	40490	57p	BD123	82p	B8Y53	37p		
2N929	22p	2N3722	42.06	AC107	80p	BD124	60p	B8Y54	40p	NKT20339	37p
2N930	27p	2N3819	35p	AC126	80p	BD131	75p	B8Y56	90p		
2N1090	22p	2N3823	97p	AC127	25p	BD132	85p	B8Y78	47p	NKT80111	77p
2N1091	22p	2N3854	27p	AC128	20p	BDY10	11.87	B8Y79	45p	NKT80112	97p
2N1131	25p	2N3854A	27p	AC134	22p	BDY11	11.85	B8Y82	52p	NKT80113	97p
2N1132	25p	2N3855	27p	AC136	22p	BDY19	11.85	B8Y83	52p	NKT80113	97p
2N1092	17p	2N3706	09p	CG187	62p	BDY18	11.78	B8Y98A	12p		
2N1303	17p	2N3856	80p	AC188	37p	BDY19	11.97	B8W41	42p		11.12
2N1304	22p	2N3856A	35p	ACY17	27p	BDY20	11.12	B8W70	27p	NKT80211	92p
2N1305	22p	2N3858	25p	ACY18	25p	BDY38	97p	C111	75p		
2N1306	25p	2N3858A	80p	ACY19	25p	BDY60	11.25	C424	26p	NKT80212	92p
2N1307	25p	2N3859	27p	ACY20	25p	BDY61	11.25	C425	26p	NKT80213	92p
2N1308	30p	2N3859A	32p	ACY21	25p	BDY62	11.25	C428	40p		
2N1309	30p	2N3860	80p	ACY22	20p	BF115	85p	C268	37p	NKT80214	92p
2N1507	17p	2N3866	11.50	ACY28	20p	BF117	47p	C744	30p		
2N1613	25p	2N3877	40p	ACY40	80p	BF163	37p	DI6P1	37p	NKT80216	92p
2N1631	35p	2N3877A	40p	ACY44	25p	BF167	18p	DI6P2	40p		
2N1632	30p	2N3900	37p	ACY46	40p	DI1P3	19p	DI6P3	37p	NKT80216	92p
2N1638	27p	2N3900A	37p	ACY48	40p	BF177	30p	DI6P4	40p	NKT80216	92p
2N1639	27p	2N3901	97p	AD149	57p	BF178	30p	GET102	30p		92p
2N1671B	11.00	2N3903	85p	AD150	62p	BF179	30p	GET113	20p	OC20	75p
2N1711	25p	2N3904	35p	AD161	37p	BF180	35p	GET114	20p	OC22	60p
2N1889	32p	2N3905	37p	AD162	37p	BF181	32p	GET118	20p	OC23	60p
2N1893	37p	2N3906	37p	AF108	42p	BF184	25p	GET119	20p	OC26	60p
2N2147	32p	2N4058	17p	AF114	25p	BF185	42p	GET120	52p	OC26	60p
2N2148	37p	2N4059	10p	AF115	25p	BF194	17p	GET123	18p	OC26	27p
2N2160	57p	2N4060	12p	AF116	25p	BF196	15p	GET180	30p	OC29	62p
2N2193	40p	2N4061	12p	AF117	25p	BF198	42p	GET187	20p	OC29	62p
2N2193A	42p	2N4062	12p	AF118	62p	BF197	42p	GET189	22p	OC35	60p
2N2194A	30p	2N4244	47p	AF119	20p	BF198	42p	GET189	22p	OC36	62p
2N2217	27p	2N4285	17p	AF124	22p	BF200	32p	GET189	22p	OC41	22p
2N2218	25p	2N4287	17p	AF126	80p	BF224	14p	GET189	22p	OC42	25p
2N2219	25p	2N4287	17p	AF128	80p	BF228	19p	GET189	22p	OC44	25p
2N2220	25p	2N4288	17p	AF127	17p	BF237	23p	MJ400	11.07	OC45	12p
2N2221	25p	2N4289	17p	AF139	37p	BF238	23p	MJ420	11.18	OC46	15p
2N2222	30p	2N4290	17p	AF178	42p	BF244	22p	MJ421	11.12	OC70	15p
2N2270	47p	2N4291	17p	AF179	42p	BF245	22p	MJ430	11.12	OC71	12p
2N2297	30p	2N4292	17p	AF180	52p	BFX12	22p	MJ440	95p	OC72	12p
2N2366	17p	2N4303	47p	AF181	42p	BFX13	22p	MJ480	97p	OC74	32p
2N2369	17p	2N4307	52p	AF239	42p	BFX29	30p	MJ481	11.25	OC75	22p
2N2369A	17p	2N4308	57p	AF279	47p	BFX30	30p	MJ490	11.00	OC76	22p
2N2410	42p	2N4309	47p	AF280	62p	BFX42	37p	MJ491	11.87	OC77	30p
2N2483	37p	2N5030	42p	AF140	32p	BFX44	37p	MF1800	22.37	OC81	21p
2N2484	32p	2N5031	42p	AFY26	25p	BFX68	67p	MJE520	62p	OC81D	21p
2N2539	25p	2N5174	52p	AFY27	37p	BFX84	25p	MJE520	60p	OC83	25p
2N2540	22p	2N5175	52p	AFY28	27p	BFX85	32p	MJE521	73p	OC84	25p
2N2613	35p	2N5176	45p	AFY29	27p	BFX86	25p	MPP102	42p	OC139	32p
2N2614	30p	2N5232A	40p	AFY36	25p	BFX87	27p	MPP103	37p	OC140	32p
2N2646	52p	2N5245	30p	AFY60	25p	BFX88	25p	MPP104	37p	OC140	32p
2N2696	32p	2N5246	40p	AFY68	25p	BFX89	62p	MPP105	37p	OC171	80p
2N2711	25p	2N5249	47p	AFY54	22p	BFX93A	70p	MPB3638	32p	OC200	40p
2N2712	25p	2N5265	23.25	AFY86	32p	BFY10	32p	NKT0013	47p	OC201	60p
2N2713	27p	2N5266	22.75	AU203	41.25	BFY11	42p	NKT124	42p	OC202	75p
2N2714	30p	2N5267	22.62	AU211	42.25	BFY17	32p	NKT126	42p	OC203	42p
2N2845	62p	2N5305	37p	BC107	10p	BFY18	32p	NKT126	27p	OC204	42p
2N2904	30p	2N5306	37p	BC108	10p	BFY19	10p	NKT128	27p	OC205	90p
2N2904A	32p	2N5307	37p	BC109	10p	BFY20	10p	NKT135	27p	OC207	75p
2N2905	37p	2N5308	37p	BC113	15p	BFY21	42p	NKT137	32p	OCPT1	42p
2N2905A	40p	2N5309	62p	BC115	15p	BFY24	45p	NKT210	30p	ORP12	60p
2N2906	25p	2N5310	49p	BC116A	15p	BFY25	25p	NKT211	30p	ORP61	60p
2N2906A	27p	2N5354	27p	BC118	10p	BFY26	20p	NKT212	30p	PR46A	22p
2N2907	30p	2N5355	27p	BC121	20p	BFY29	50p	NKT213	30p	TR184	62p
2N2923	15p	2N5356	22p	BC122	80p	BFY30	50p	NKT214	22p	TR1843	27p
2N2924	15p	2N5365	47p	BC125	20p	BFY41	50p	NKT215	22p	TR1844	10p
2N2925	15p	2N5366	32p	BC126	80p	BFY43	62p	NKT216	37p	TR1845	10p
2N2926	22p	2N5367	37p	BC140	37p	BFY60	23p	NKT217	42p	TR1846	11p
Green	14p	2N5457	37p	BC147	10p	BFY70	29p	NKT219	29p	TR1847	11p
Yellow	12p	28005	75p	BC149	10p	BFY83	22p	NKT224	27p	TR1848	12p
Orange	18p	28020	29p	BC149	12p	BFY83	17p	NKT224	25p	TR1849	12p
2N3011	30p	28102	50p	BC152	17p	BFY56A	57p	NKT225	22p	TR1850	17p
2N3014	32p	28103	25p	BC157	80p	BFY75	30p	NKT229	30p	TR1851	12p
2N3053	18p	28104	25p	BC158	11p	BFY76	42p	NKT237	35p	TR1852	12p
2N3064	40p	28501	22p	BC159	12p	BFY77	57p	NKT238	25p	TR1853	22p
2N3065	62p	28502	35p	BC160	62p	BFY90	67p	NKT240	27p	TR1850	22p
2N3134	30p	28503	29p	BC167	11p	BFW68	27p	NKT241	27p	TR1861	25p
2N3135	28p	28504	30p	BC168B	10p	BFW69	25p	NKT242	30p	TR1862	27p
2N3136	28p	28505	30p	BC168C	11p	BFW60	25p	NKT243	62p	TIP320A	60p
2N3137	28p	28506	30p	BC169B	11p	BPX25	11.85	NKT244	17p	TIP330A	60p
2N3390	25p	28507	30p	BC170	10p	BPX29	11.80	NKT245	50p	TIP31A	62p
2N3391	20p	28508	25p	BC171	15p	BPY10	11.45	NKT261	30p	TIP32A	62p
2N3392	30p	28509	30p	BC172	15p	BPY39	11.80	NKT262	30p	TIP33A	62p
2N3393	17p	R.C.A.	52p	BC175	18p	B8X19	17p	NKT264	20p		11.02
2N3394	17p	R.C.A.	52p	BC178	22p	B8X20	17p	NKT271	20p	TIP34A	22.05p
2N3394	17p	R.C.A.	52p	BC182	10p	B8X21					

# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

**10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND**


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 8" x 2 1/2" Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

**£8-50**


P. P. & Ins. 50p

(Overseas P. & P. £1)

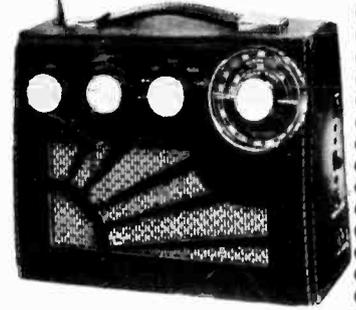

## ROAMER EIGHT Mk I

**NOW WITH VARIABLE TONE CONTROL**

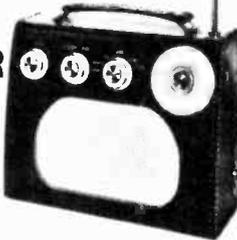

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 8" x 2 1/2" Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)

## Exclusive to readers of "EVERYDAY ELECTRONICS" "EVERYDAY SEVEN"




**MEDIUM and LONG WAVE PORTABLE.**

Specially designed circuit for easy construction incorporating 7 transistors and 2 diodes, air spaced tuning capacitor, push pull output using 600 mw transistors, heavy duty loud-speaker for quality sound and room filling volume, internal Ferrite Rod aerial, Volume/on/off control, tuning control and wave change switch. Handsome, strongly made wooden case, size 11 1/2" x 7 1/2" x 3 1/2" with carrying handle and black knobs with spun silver inserts. The ideal radio for those who are comparatively inexperienced in electronic construction. Easy build plans are supplied free with parts or available separately for 25p.

Total building costs **£4-98** P. P. & Ins. 41p. (Overseas Post £1)


## ROAMER SIX

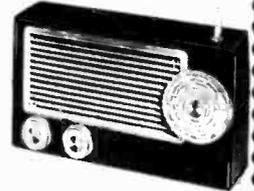

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 3 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3-98** P. P. & Ins. 26p. (Overseas P. & P. £1)

## POCKET FIVE

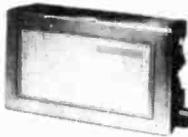

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 31p. (Overseas P. & P. 63p)

## TRANSONA FIVE




**5 TRANSISTORS AND 2 DIODES**

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 22p. (Overseas P. & P. 63p)

## TRANS EIGHT

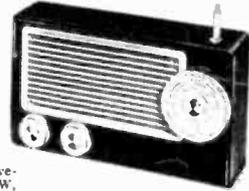

**8 TRANSISTORS and 3 DIODES**

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 6 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P. P. & Ins. 31p. (Overseas P. & P. £1)

## NEW! "EDU-KIT"



**BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.**

**COMPONENTS INCLUDE:**  
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4"x2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 3 Diodes: Resistors: Capacitors: Three 1" Knobs.

Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)

**FULL AFTER SALES SERVICE**

• Callers side entrance Barratts Shoe Shop  
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- |               |                          |                |                          |
|---------------|--------------------------|----------------|--------------------------|
| ROAMER TEN    | <input type="checkbox"/> | EVERYDAY SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT  | <input type="checkbox"/> | TRANS EIGHT    | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX     | <input type="checkbox"/> |
| POCKET FIVE   | <input type="checkbox"/> | EDU-KIT        | <input type="checkbox"/> |

Parts price list and plans for .....

Name .....

Address .....

(Dept. E.E.5.)

# HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI ELECTRONIC COMPONENTS TEST PA DISCOTHEQUE LIGHTING MAIL ORDER

## 10th EDITION CATALOGUE



350

pages fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

PRICE 55p POST PAID (40p FOR CALLERS)

10,000

Stock lines at Special Low Prices and Fully Guaranteed.

## PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. EE), 3 Albemarle Way, London, E.C.1.—for catalogue by post only.

All other mail and callers to "303"—see below HENRY'S CATALOGUE IS A MUST FOR ELECTRONIC COMPONENTS OF ALL TYPES



### F2000 SYSTEM

Teleton F2000 Med/Stereo FM Tuner Amplifier, Garrard 2025TC/9TAHCD Auto with plinth and cover, Pair matching speakers K60. Size 16 x 9 1/2 x 6 1/2 in. All leads etc. List £54.65 Carr. £2.93 or with MP60/SC5MD Single Player £57.50, Carr. £2.



### 206B SYSTEM

Teleton SAQ206BB + 8 watts Stereo Amplifier, Garrard SP25J3, Goldring G800H, plinth and cover, Pair of speakers SDL1 (or K80). Size 15 x 10 1/2 x 7 1/2 in. All leads etc. List £55.95 Carr. £2.90 or with 2025TC/9TAHCD and K60 Speakers 16 x 9 1/2 x 6 1/2 in. £49.95, Carr. £2.



### Z200 SYSTEM

Rota 10 + 10 watts Stereo Amplifier, Garrard SP25J3, Goldring G800H, plinth and cover, pair of speakers SDL2 (or KN800) Size 18 x 10 1/2 x 7 1/2 in. All leads etc. List £65.50 Carr. £2.94



### PHILIPS SYSTEM

RH701 10 + 10 watts Med/Long/Short/Stereo FM Tuner Amplifier, pair RH111 Speaker Systems 10 1/2 x 7 1/2 x 7 1/2 in. McDonald MP60/Plinth/Cover/SC5MD cart. All leads etc. List £89.95 Carr. £2.50 £120

FREE Latest Hi Fi & Tape Recorder 12 page Stock Discount List plus over 100 Stereo Systems. Ref. 16/17.

## PUBLIC ADDRESS, LIGHTING & DISCOTHEQUE EQUIPMENT

DJ1055 30 watt rms Amplifier, 4 inputs, master tone and volume controls etc. 8 ohm output. Cased portable. £33.50, Post 40p.  
DJ105 70 watt rms version. Cased portable. £53.00, Post 40p.  
DISCOAMP 100 watt rms to 8 ohms. 4 inputs, separate bass and treble controls, PFL, etc. Cased for cabinet or rack mounting £76.50, Post 40p.  
McDONALD MP60 fitted to plinth with cover, SC5MD cartridge to match above amplifiers. £17.50, Post 70p.  
DJ3011 3 channel light control unit for above amplifiers. 3 x 1 K Watt. Treble, Bass and Mid range. £33.50, Post 35p.  
EFFECTS PROJECTORS—Coloured rotating light patterns.  
BABY IMP 250 watt Tungsten £23.30  
LIQ1 50—50 watt Q.I. £32.50  
LIQ1 150—150 watt Q.I. £50.00

FULL RANGE OF LIGHTING IN STOCK

### TEST EQUIPMENT

Huge range in stock—too much to list here. It's all in the latest catalogue—prices—specifications etc. Also Panel Meters and Edge Meters.



GARRARD McDONALD GOLDRING TURNABLES

CHASSIS (Post 50p)  
SP25J3 £11.30 HT70 £16.60  
MP60 £11.30 MP610 £13.15  
AP76 £20.50 Zero 1005 £41.97

With PLINTH/COVER (Post 70p)  
MP60 PC £17.65  
HL75 PC £37.35  
HT70 PC £23.50  
GL72P £32.95  
CART/PLINTH/COVER (Post 70p)  
GL72PC/G800 £35.95  
(HL)AP76/G800 £29.95  
HT70 PC/G800 £29.95  
MP60 PC/G800 £17.50  
(HL)SP25J3/G800H £19.95  
(HL)2025TC/9TAHCD £14.95

### ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.  
PRICE PAIR £5.90 Post 10p

### POWER INTEGRATED CIRCUITS

SL403D—3 watt with 8 page data, layouts & circuits £1.50  
P.C. Board 60p; Heat Sink 14p  
IC12—6 watt with data and circuits £2.50  
TOSHIBA—20 watt Power Amp Module £4.57  
TOSHIBA—IC Pre-amplifier £1.50  
TOSHIBA—Data / Circuits Book No. 42 10p


### TEXAS PUBLICATIONS

1-100 watt Amplifiers and PreAmp. Layouts and data £1.25 Price list No. 98A FREE  
700 page IC Data Book (No. 2) 60p  
420 page Transistor Data (No. 3) 60p  
340 page Transistor Data (No. 4) 60p  
(Post etc. 15p each, 20p per 2 or 3 books)
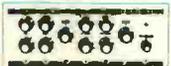
### NIXIE TUBES

(Post 15p per 1 to 6)  
XN3, XN13, GN6 0-9. Side view with data 85p.  
GNP-7, GNP-8 0-9. Side view with decimal points and data 95p  
GN4 0-9 End view with socket and data £1.65

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST



SPECIAL II Anti-Feedback Microphone designed and made for Henry's for all PA/Disco Equipment.  
LIGHT GUIDE 64 fibres sheathed £1 per yd.  
Mono (0-001") £1.50 per 25 metre reel.  
COMPLETE RANGE OF DISCO/PA AND LIGHTING ON DISPLAY AT "309"  
Call, write or phone for details and lists.

### LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.  
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20, Post 22p.  
TYPE 150 TC Twin cone version £2.75, Post 22p.  
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85, Post 25p.  
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70, Post 28p.



POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

### HIGH POWER AMPLIFIER MODULES

MPA12 Quality transformerless low noise amplifiers suitable for all Audio, PA and Hi-Fi use. Modern compact designs. PA25 and PA50 supplied with plug harness for use with MU442 Power Supply.



MPA12/3 18v, 0-8A, 12W, 3-4 ohm, £4.50  
MPA12/15 30v, 0-5A, 12W, 12-16 ohm, £5.25  
MU24/40 Mains unit for 1 or 2 MPA12/3 or 15, £4.50  
PA25 22-0-22v, 1A, 25W, 8 ohm, £7.50  
PA50 22-0-22v, 2A, 50W, 3-4 ohm, £9.50  
MU442 Mains unit for 1 or 2 PA25 or 1 only PA50, £6.00  
Post 20p per unit

### ALL SILICON-FET PREAMPLIFIER AND MIXER SELF POWERED



All inputs. Adjustable input and output. DIN sockets. Tape in and out. Microphone mixing. Suitable up to 4-PA25 or 2-PA50.  
PRICE £10.50 Post 30p

### 300mW TRANSISTOR AMPLIFIER MODEL 4-300

Fully assembled STR Amplifier. Size 5 1/2 x 1 1/2 x 3 1/2 in. 1-10mV adjustable sensitivity. Output 3-8 ohms. Filtered Vol. control. 9 volt operated. Thousands of uses plus low cost.  
Price £1.75, p.p. 15p (or 2 for £1.25, p.p. 15p)



### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO  
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.  
TOTAL £6.97, p.p. 20p. Cabinet 100p. Decoder Kit £5.97.  
Tuning meter unit £1.75  
Mains unit (optional) Model PS900 £2.47, Post 20p  
Mains unit for Tuner and Decoder PS1200 £2.62, Post 20p



### SINCLAIR PROJECT 60 MODULES—SAVE POUNDS!

Z30 £3.60 Z50 £4.38  
STEREO PZ5 £3.98  
60 £7.98 PZ8 £5.97  
PZ6 £6.38




Transformer for PZ8 £2.95  
Active Filter Unit £4.75  
Stereo FM Tuner £20.25  
IC12 £2.50; Q16's £8 ea.  
Post etc. 20p per item

PACKAGE DEALS  
2 x Z30, Stereo 60, PZ5 £16.75  
2 x Z30, Stereo 60, PZ6 £18.25  
2 x Z50, Stereo 60, PZ8 £20.25  
Post 25p extra on above items  
Transformer for PZ8 £2.95  
Post 20p

ALSO IN STOCK  
2000 £23.75; 3000 £31.50  
Post 50p each

NEW PROJECT 605 KIT £20.95  
Post 25p

### "BANDSPREAD" PORTABLE TO BUILD

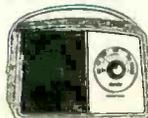

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.  
TOTAL COST TO BUILD £7.98, p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2.

77" MEDIUM AND LONG WAVE PORTABLE (as previously advertised) £6.98, p.p. 35p from stock—Leaflet No. 1.

SLIDER CONTROLS. Top quality 60mm singles and gangs complete with knobs. (Post 1-5 15p; 6 or more 20p)  
5K, 10K, 25K, 50K, 100K, 500K, 1 Meg. Log and Lin 45p each  
10K, 25K, 50K, 100K, Log and Lin ganged. 75p each

## MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S

Electronic Components, Audio and Test Gear Centre  
356 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre  
354 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 5854

P.A., Disco & Lighting Centre  
309 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 6900

Mail Orders, Special Bargain Show, Industrial Sales  
303 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 1003/9

"309", "354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY