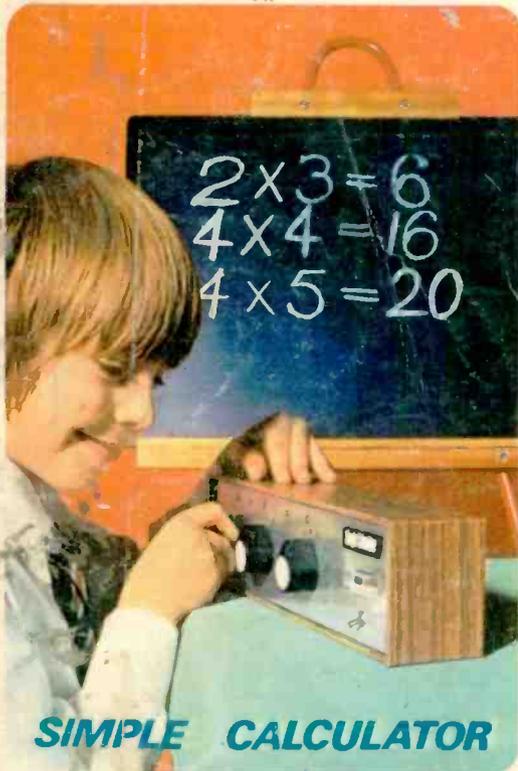


An exciting **BOOK 4** .. for everyone


everyday electronics

APRIL 72


15p



SIMPLE CALCULATOR

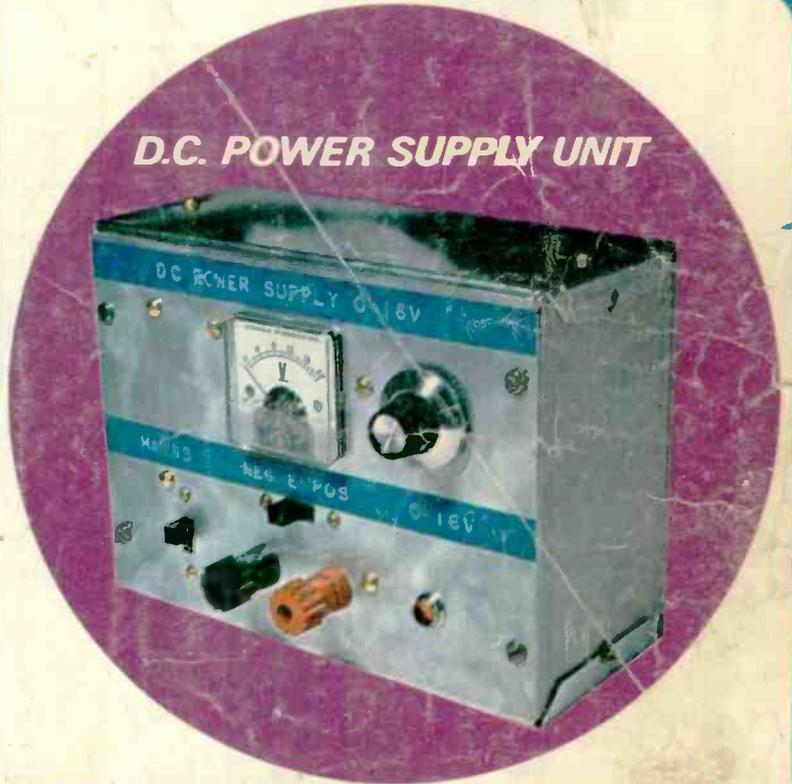

D.C. POWER SUPPLY UNIT

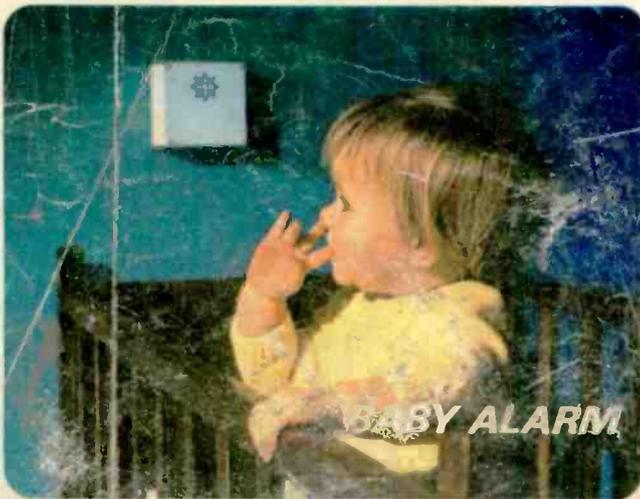

BABY ALARM



WITH REMOTE AUDIO MONITOR

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits

(illustrated) available

COPPER

B 38 $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

PRICE
£1.85



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



ADCOLA PRODUCTS LTD.,
(Dept. Y), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint Loncon Telex • Telex: Adcola London 21851

* Write for price list and catalogue

COMPLETE AMPLIFIER SYSTEM FOR £25



Stereo amplifier with double wound mains transformer (200-250v. a.c.); 2 x ECL82 valves giving 2 x 2½W; printed circuit (10" x 3½") mounted on metal chassis. Ganged tone controls, sep. vol. controls; on-off switch; excellent channel separation. Output trans. for 3-ohm speakers. For crystal, ceramic cartridges or radio tuner. Only £6.25 (post 40p).

Beautifully finished teak or walnut wooden cabinets 10½" x 5½" x 7" deep for 6" x 4" speakers. £5 pair (post 30p). Separate speakers to fit £2.30 pair (post 20p). B.S.R. autochanger C129 fitted stereo cartridge £9 carr. pd.

PACKAGE DEAL—above autochanger, 2 cabinets, 2 separate speakers, plinth & perspex cover, above amplifier. All for £25 (carr. £1.50). All necessary audio leads & plugs supplied. 12 months' guarantee (valves 3 mths).

GLADSTONE RADIO

66 Elms Road, Aldershot, Hants.
Telephone: 22240.

FELSTEAD (EE6) ELECTRONICS LONLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE

Selection from our list, sent free for stamped addressed envelope. (Free overseas). Cash with Order only—No C.O.D. or Caller service. Charges (Min. 6p.) in brackets after all items apply to G.B. & Eire only. Regret Orders under 25p. plus charges unacceptable. H.A.E. please, for enquiries or cannot be replied to. Overseas Orders welcomed.


RECORDING TAPE: Finest quality/value British Mylar available: STANDARD 5" 600ft 36p; 5" 900ft 50p; 7" 1200ft 58p; LONG PLAY 5" 900ft 50p; 5" 1200ft 56p; 7" 1800ft 80p. (7½p on 5" and 5½", 9p on 7"). Other sizes, Cassettes and accessories in list. **CARTRIDGES.** All with standard fittings and styli. Mono GP97 85p; Stereo-compatible Mono GP91/8C £1.10; STEREO GP93 £1.40; Stereo Ceramic GP94 £1.95. (6p) Comparatives shown in list with more types incl. Sonitone 9TAC Golding &c. at lowest prices. **DIAMOND STYLII:** Single tip types: Acos GP37, GP59, GP85/87, GP71, BBR TCS/LP/ST; COLLARO O. P and DC284; GARRARD GC2, GC8, GC12, GC810; RONETTE BF40, G. P and T; PHILIP8 3301 (3060, 3066, 3302, 3304) 3010 (12, 13, 16); MONOTONE 19T/20T. ALL AT 40p each (6p). Double-tip turn-over types (78 sap. on other side). For Acos GP73, GP91 (for cartridges GP93, GP94 &c.) GP918C (for stereo-compat. types) GP104, BBR 8T4 (8T3, 8T5), 8T9 (8T6), ST12/14/15, SONOTONE 9TA, 9TA, 9TALC; PHILIPS 3306 (3310, 3224, 3228/22, GP800) GARRARD GCM21, 22, GC823, GK825 and 26, GCM21T and 22T, GK824T, GC8231, GK825T & 26T, GCM31, GC836, GC835, GC838, KN40A, KN41B, etc. ALL AT 75p (6p). **DOUBLE DIAMOND STYLII:** (Same dia. tip each side; no 78) for all types £1.60 (6p). **PICK-UP WIRE:** Super thin twin flex screened, sheathed, 6p per pair. (1½p to 6 yds, 6p, over charges paid.) All sapphires in list. **MICROPHONES:** CRYSTAL: LAPEL 1½", clip/hand, lead 3.5mm jack plug 32½p (6p). CM20 Cream Plastic hand 62½p; CM21 Grey Plastic Hand/Desk 62½p; both have 3.5mm jack plug and lead (5p either). "STICK" 60 £1.02; CM70 "PLANET" Metal, tapered, with neck cord, adaptor for stands £1.47½; "MIC 91" hand/desk 81p; "MIC 45" Curved metal hand grip £1.00. All with leads (all 9p). **MICROPHONE INSERTS** Diam. 1.75 or 0.9 - other size 27½p (1½p to 8 for 6p). **DYNAMIC:** 209 Cardiod Rail, 50K/600Ω, built-in volume control, on/off switch, special 20ft lead, the best value anywhere £6.30; "D130, uni-dir. mesh ball 50K/600Ω jack plug, cable, adaptor, £4.80; DMI60, omni-dir. ball mesh, 50K, cable, adaptor, jack plug £3.87½ (27p each). **SPEAKERS:** Still very popular 1½" ROUND, fitted tweeter, 3 or 15 ohms (state which) £1.87½ (27½p)—or pair for stereo £4.25 charges paid. **SMALL 2"** 3Ω or 8Ω, state which 37½p (6p). More speakers in list. **HEADPHONES:** High resistance 2000Ω adjustable 92½p (7½p). **EARBIPPES** with lead and min. 2.5mm or 3.5mm (state which) jack plug, MAGNETIC 5p. **CRYSTAL** (3.5mm plug only) 24p (up to 3 for 6p, any type). **SOLDERING IRON:** Slim, modern, British high spec-1, 3½", all parts replaceable, highest quality fully guaranteed £1.17½ (10p). **TRANSFORMERS:** Sub-min 11x11x12mm, OUTPUT (3Ω for OC72, &c.) 14p, or DRIVER 15p (up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5 yds, asstd. cols. **SOLID CORE** 14p. **FLEXIBLE or FUPER THIN** for transistor wiring &c. either 18p. (Any pack 6p). **RETRACTABLE FLEXIBLE LEADS.** (CURLIES): With phono plug ea. end 6ft 52p, 12ft 30p. With phono plug phono socket other end 6ft 25p, 12ft 42½p (6p lead any type). **WIBBATORS:** 12V 4-pin non-synch 12114, 2½" ex. pins 27½p, 3AM2 but 3½" 31p, USA, 20p, 12V 7-pin, synch. 128R7) 2½" ex pins 62½p (6p any type). **TRANSISTORS** &c. AC1126 12p, AF115 20p, AF116 15p, AF117 20p, OA5 10p, OA10 10p, OA81 10p, OC44 14p, OC45, OC71, OC72, OC75, OC810, OC820, all at 12½p each, OC81 18p, OC170 20p, OC171 12½p, BY100/800piv 1-p. Many more incl. power types, thyristors, &c. in list. **MAINS WIGGERS,** by leads 10p. **NEON SCREWDRIVER** (pocket tester) 17½p (6p either). **MAINS BATTERY ELIMINATOR:** Input 240V AC, Output 3, 6, 7½ and 9V DC by voltage selector, On/off switch, pilot lamp, leads, plug, adaptor to suit most transistor sets and cassette recorders. Suitable for model use: £3.15 (24). **OUR CURRENT LIST** (see heading) includes more details of all above plus cartridge replacement table, many unrepeatable Special Offers, and cable, croc. clips, Volume controls, Din plugs, Co-Ax, standard, miniature, phono plugs, sockets and adaptors, Tape Recording and Record Player accessories, panel and Test meters and equipment, Multimeters, min. meters, test probes, switches—rotary, toggle, slide cabinet, lat up &c.—electrolytics, terminals, veroboard, valve holders, extending aerials for cars and portable sets, ind. lamps and bulbs, dials, mikes, telephone amplifiers and pick-ups, drive cord, inter-coms, capacitance and resistance testing boxes stereo headphones etc., etc.



*Call 'em what
you will ...*

*... the best place
to get them is*

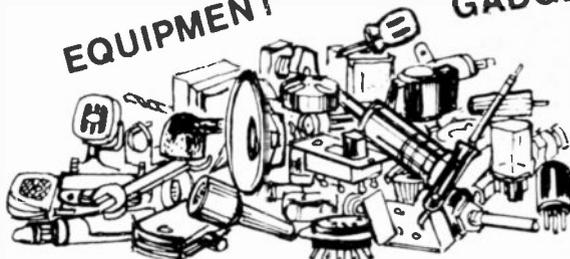ITEMS COMPONENTS
BITS & PIECES PARTS
EQUIPMENT GADGETS



HOME RADIO (COMPONENTS) LIMITED

240 London Road, Mitcham. CR4 3HD
Phone: 01-648 8422



Until you've tried the service provided by Home Radio (Components) Limited you've no idea how simple it can be tracking down and obtaining components. It becomes a pleasure instead of a bind! But first you need the Home Radio Catalogue, listing over 8,000 components, more than 1,500 of them illustrated. At 70 pence, including p & p, it's a gift—especially as every copy contains 10 vouchers each worth 5 pence.

Send coupon today.

**POST THIS COUPON with your
cheque or postal order for 70p**



Please write your Name and Address in block capitals

NAME.....

ADDRESS



HOME RADIO (COMPONENTS) LTD., Dept. EE
234-240 London Road, Mitcham, Surrey CR4 3HD.

●24-hour Phone Service
Ring 01-648 8422

Ask for details of our
Credit Account Service

The price of 70p applies only to catalogues purchased
by customers in the U.K. and to BFPO addresses.

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N-9 803 1685

MIDGET FLEX CONNECTOR
Approx. 2 amp rating.
Two-pin non-reversible midget flex connector. Approx. size: 2in. x 1/4in. Ideal for loudspeaker connections, etc. 8p plus 2p P. & P.

MAINS TRANSFORMER
Fused Primary 240V. Secondary 220V @ 50M/A. 6-3V.
@ 1A. This transformer is made to a very high standard and in a small size: 2in. x 2 1/4in. x 2 1/4in. 63p plus 15p P. & P.

EN3055
POPULAR POWER TRANSISTOR
Now at our Low Price 50p each
Please include 5p P. & P.

BARGAIN S.C.R.
TESTED THYRISTOR
400 volt. 3 amp.
45p each 5 for £2.00
Please include 5p P. & P.

BATTERY ELIMINATOR
Plug your Transistor Radio, Amplifier, Cassette, etc. into the a.c. mains through this compact eliminator. 2 1/2in x 2 1/2in x 3 1/2in approx.
6V £1.50, 9V £1.80, 7 1/2V complete with cable and plug for Philips Cassette. £2 plus 8p P. & P. each.

BULGIN OCTAL PLUG
Ideal for all those multi-way connections. This plug couples with a standard 8-pin valve holder. Plug 12p Socket 6p
Please include 4p p. & p.

WAFER SWITCHES
1 pole 12 way
2 pole 2 way
2 pole 3 way
2 pole 4 way
2 pole 6 way
3 pole 4 way
4 pole 3 way
22p each. Please inc. 5p P. & P. Up to 3 switches.

COMPONENT BARGAIN
1 32 + 16 mFd 275V Capacitor. 1 Speaker Output Transformer. 2 B9A Valve Holders. 1 4,700 pF Capacitor. 1 175 ohm W/W Resistor. 1 330 ohm, 1W Resistor. 1 12 kΩ 1/4W Resistor. All mounted on a small Amplifier Panel. Only 38p. P. & P. free.

HIGH QUALITY IMPORTED HEADPHONES
1,000 Ω per phone 80p
2,000 Ω per phone 88p
Plus 10p P. & P. per pair.

COMPONENT CORNER each
Veroboard Octacs 2in. 3 1/4" x 5 1/4" 17p
Plain Veroboard 1in. 3" x 3" 9p
Standard Toggle Switch DPDT 18p
D.P.D.T. Slide Switch 13p
Experimental Transistor Holders, 3-pin and 4-pin 7p
I.C. Holders for 14 or 16 pin 20p
Please include 3p p. & p. per 3 items

SINGLE EARPIECES
Crystal or Magnetic 3-5mm or 2-5mm (please state which type you require. Complete with lead. 20p plus 3p p. & p.

LOUDSPEAKER BARGAINS
E.M.I. 450 set 3. 8. 15 ohm 23-25 plus 35p. P. & P.
E.M.I. 350 set 8 ohm. 47-00 plus 35p. P. & P.

MINI LOUDSPEAKERS
2 1/2" 8 ohm 38p 2 1/4" 40 ohm 38p
3" 8 ohm 40p 2 1/2" 25 ohm 38p
Plus 3p P. & P. on each Mini Speaker.

ALUMINIUM CHASSIS
Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.
6 x 3 - 41p 12 x 3 - 53p 14 x 9 - 94p
6 x 4 - 45p 12 x 6 - 61p 16 x 6 - 86p
8 x 6 - 58p 12 x 8 - 83p 16 x 10 - 108p
10 x 7 - 63p 14 x 3 - 60p
Please send 10p per chassis P. & P.

CAPACITORS
Mini Electrolytics all values up to 100mFd @ 15V-7p each. Small PP Capacitors only in packs of 10 but you can mix values - 25p for 10.
250mFd @ 25V - 15p
500mFd @ 25V - 21p
1000mFd @ 25V - 27p
2000mFd @ 25V - 34p
3000mFd @ 25V - 45p
5000mFd @ 25V - 58p
Please inc. 10p. P. & P. with orders under £2 value.

PRINTED CIRCUIT KIT
Everything for producing your own printed circuits. £1.40p plus 10p. P. & P.

PRINTED CIRCUIT BOARD
8 x 6 - 10p 10 x 8 - 15p
9 x 5 - 10p 12 x 12 - 30p
Please inc. 3p. per board P. & P.

EA1000 3 WATT AUDIO AMPLIFIER MODULE
An Audio Amplifier designed around the TAA621 Linear I.C.:-
Supply Voltage 9-24V
Speaker Imp. 8-16 ohm
Frequency 50Hz-20kHz
Overall Size 2in x 3in x 1 1/2in
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at

POTENTIOMETERS
All types 1" and less diameter. SINGLES DUAL
5K Log or 5K
10K Lin Less 10K
25K Switch 25K Less Switch
50K 17p ea, 50K 45p.
100K
250K 250K
500K Double 500K each
1M Pole Switch 1M
2M Switch 2M
25p ea.
Up to 3 Pots. Please add 5p. P. & P.

RESISTORS
We stock all recognised values of resistors all at 10% or closer tolerance. We regret we can only mail them in lots of ten. You can send for mixed values. All Midget types.
1 watt lots of 10 - 13p
1 watt lots of 10 - 15p
1 watt lots of 10 - 25p
Please include 3p P. & P. for each 10 resistors.
£2.63 + 5p P. & P.

SAFEBLOC

of robust construction

Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

Ask for Safebloc at your local stockist - or you can order it direct from the manufacturer.

If ordering by post, send cash with order.

PRICE £2.60+10p P.&P. EACH

Special bulk order wholesale and industrial rates on application




RENDAR

Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex. Tel. Burgess Hill 2642

PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS

With Bevelled Former Bars

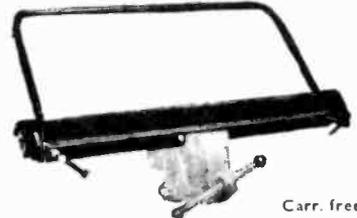

Carr. free

- No. 1. Capacity 18 gauge mild steel x 36in. wide ... £15-00
 - No. 2. Capacity 18 gauge mild steel x 24in. wide ... £12-00
 - No. 3. Capacity 16 gauge mild steel x 18in. wide ... £12-00
- Also new bench models. Capacities 36in. x 18 gauge £35-00 24 in. x 16 gauge £32-00. Carriage free.

End folding attachments for radio chassis. Tray and Box making for 36in. model, 27p per ft. Other models 17p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.
A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

The most accurate pocket size CALCULATOR in the world

The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send £4.50 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

CARBIC LTD. (Dept. EE3)
54 Dundonald Road, London, SW19 3PH.



FREE BOOKLET ON REQUEST

BI-PRE-PAK



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 50p

COMPLETE TELEPHONES
EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY £1 EACH

POST & PACKING. 35p EACH

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V. 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1/2N706A, BS795A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1/2 watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS


TYPE "A": FNP Silicon alloy, TO-5 can.
TYPE "B": PNP Silicon, plastic encapsulation.
TYPE "E": PNP Germanium AF or RF.
TYPE "F": NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		6p	
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC107	0-13	2N1308-9	0-35
BC108	0-13	2N3819FET	0-45
BC109	0-14		
BF194	0-15	Power Transistors	
BF274	0-15	OC20	0-50
BFY50	0-20	OC23	0-30
BSY25	0-57	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-10
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-15	AD149	0-30
OC41	0-13	AUY10	1-25
OC44	0-13	25034	0-25
OC45	0-13	2N3055	0-50
OC71	0-13		
OC72	0-13	Diodes	
OC81	0-13	AA42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9114	0-07

F.E.T. PRICE BREAKTHROUGH!!

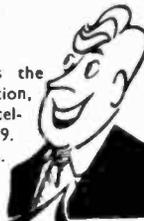This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BS726-29, BS795A, 3CY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BA931-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc. £4-25 per 500; £8 per 1,000.

OC44, OC35 Transistors fully marked and tested. 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested. 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case. 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:

IN4001, 500+ at 4p each; 1,000+ at 3p each.
IN4004, 500+ at 5p each; 1,000+ at 4p each.
IN4006, 500+ at 6p each; 1,000+ at 5p each.
IN4007, 500+ at 8p each; 1,000+ at 7p each.

FREE CATALOGUE AND LISTS FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS & SUBSTITUTION CHARTS

CLEARANCE LINES

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PLS09 and P1500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 cr 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	25p	20p	15p
Gates, factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
SN7490 Decade Counter	50p	45p	40p
UL914 Dual 2 I/P Gate	40p	35p	30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes;

This includes many thousands of British U.S.A., European and C.V. equivalents. The **Hi-Fi Radio Valve & Transistor Data Book 9th Edition;**

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.
Send for lists of these English publications.


NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

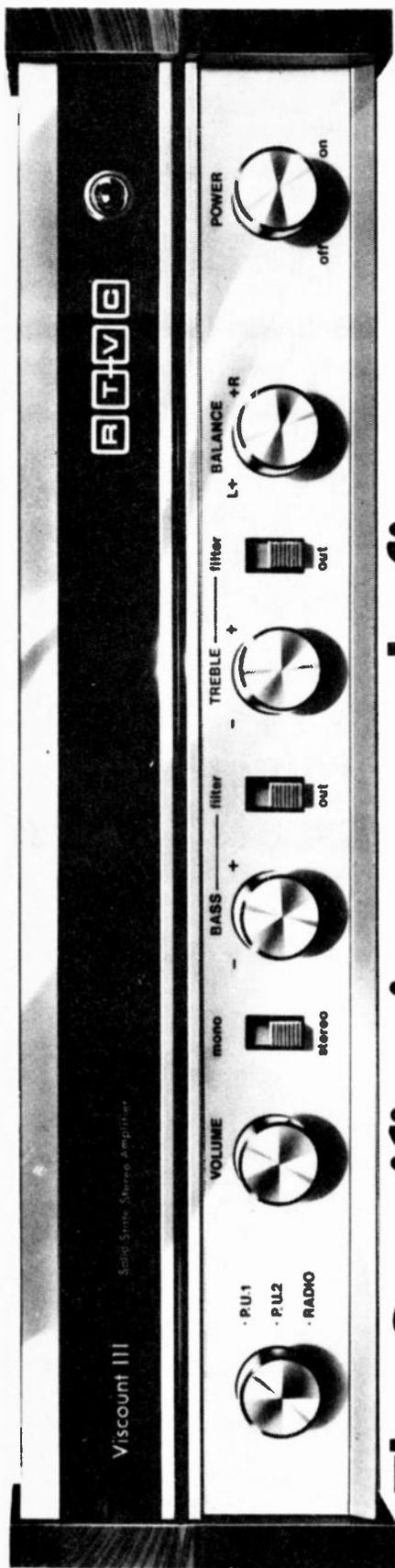DEPT. E 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344



The Specification sounds fine the System sounds great

Viscount III Audio Suite complete £49

14 + 14W per channel 40Hz to 40kHz \pm 3dB Total distortion at 10 watts at 1kHz —0.1%.

This is real value for money! We have designed 3 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. It is available in 2 versions — R100 for ceramic cartridges, and R101 for magnetic and ceramic. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For all systems we have chosen the famous Garrard SP25 Mk. III deck which comes complete with teak finished plinth and perspex cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PRICES

SYSTEM I
Viscount III R101 amplifier £22.00 + 90p p&p
2 x Duo Type II speakers £14.00 + £2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover £23.00 + £1.50 p&p
Total £59.00

Available complete for only £52 + £3.50 p&p

SYSTEM 2
Viscount R101 amplifier £22.00 + 90p p&p
2 x Duo Type III speakers £32.00 + £3 p&p
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover £23.00 + £1.50 p&p
Total £77.00

Available complete for only £69 + £4 p&p

SYSTEM 3
Viscount III Amplifier R100 £17.00 + 90p p&p
2 x Duo Type II speakers, pair £14.00 + £2 p&p
Garrard SP25 Mk. III with CER. diamond cartridge, plinth and cover £21.00 + £1.50 p&p
Total £52.00

Available complete for only £49 + £3.50 p&p


SPEAKERS Duo Type II

Size approx. 17" x 10 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ ". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Simulated Teak cabinet. £14 pair + £2 p&p.

Duo Type III. Size approx. 23 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ ". Drive unit 13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

SPECIFICATION R101

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within \pm 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivity given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max.) R101—P.U.1 and radio—55dB. P.U.2—58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

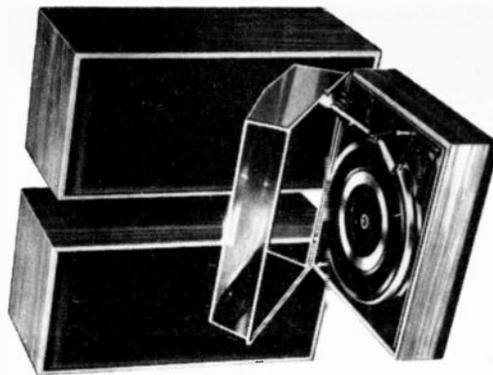

Goods not despatched outside U.K.

RTVOC

Radio and TV Components (Acton) Ltd.,
21c High Street, Acton, London W3 6NG,
323 Edgware Road, London, W2. Mail orders
to Acton. Terms C.W.O. All enquiries S.A.E.



CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price £1.70

CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price £1.70

G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price £1.83.



CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect Insulation (4,000 v A.C.). Will solder live transistors in perfect safety: fitted with 3/32" Iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. Price £1.80

CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price £1.95



E.240 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price £1.80.

ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price £1.83



SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price £2.75



SK.2 SOLDERING KIT

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price £2.40.



MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price £1.95.

sign here
to answer all your soldering problems

I enclose cheque/P.O./Cash (Giro No. 2581000)

Name _____
Address _____
E.E.4

Please send the Antex colour catalogue.

Please send the following:



from electrical, radio or car accessory shops or from **Antex Ltd., Freepost** (no stamp required) **Plymouth** PL1 1BR Telephone 0752 67377/8

DISCOUNTS UP TO

60% ON BRANDED GOODS

ALL BRAND NEW
in manufacturer's sealed cartons
GUARANTEED 12 MONTHS

SPECIAL OFFER
Garrard SP25 Mk. III
Goldring G800H
Teak plinth and tinted cover.
Ready wired for immediate use.
Please add £1.25 for P. & P.

£18

TUNER / AMPLIFIERS

Please add 75p P. & P.
Armstrong 525 (Teak cased) *£68.50
Armstrong 526 AM/FM (Teak cased) ... *£78.50
Leak Delta 75 ... *£130.95
Goodmans Mod 80 ... *£67.95
Rotel FAX 660A ... *£85.60
Philips RH781 ... *£50.00
Philips RH882 (with cas. hd.) *£72.00
Philips RH702 ... *£82.50
Teleton 2100 ... *£29.95
Goodmans One Ten ... *£105.00
Rogers R'brook (Teak cas.) *£80.00
Rogers R'brook (Chassis) *£74.50
Scaneltra 1515 AM/FM ... *£102.50
Scaneltra 3030 FMG ... *£110.50
Scaneltra 1515 FM ... *£74.50

TURNTABLES

Please add 50p P. & P.
Garrard SP25 Mk. III ... *£10.50
Garrard AP76 ... *£19.95
Garrard SL65B ... *£13.25
Garrard 1025T + cart. ... *£5.97
Garrard 401 ... *£39.95
Garrard Zero 100 (Auto) ... *£17.25
Garrard Zero 100 (Single) ... *£10.00
BSR MP60 ... *£22.50
Goldring GL72 ... *£29.25
Goldring GL72/P ... *£27.30
Goldring GL75/P ... *£35.50
Pioneer PL12AC (P. & C.) ... *£34.95
Leak Delta ... *£55.00
Wharfedale Linton + cart. ... *£27.75
Thorens TD125 ... *£57.75
Thorens TD125AB ... *£90.00
Thorens TD150 Mk. II ... *£28.00
Thorens TD150A Mk. II ... *£33.75

AMPLIFIERS

Please add 50p P. & P.
Amstrad 8000 Mk. II ... *£16.95
Amstrad IC2000 ... *£27.90
Armstrong 521 (Teak cased) ... *£43.95
Leak Delta 30 ... *£48.00
Leak Delta 70 ... *£56.00
Metrosound ST20E ... *£24.75
Metrosound ST60 ... *£47.25
Rogers R'brook (Chassis) ... *£35.00
Rogers R'brook (Cased) ... *£37.00
Rogers R'bourne (Chassis) ... *£41.50
Rogers R'bourne (Cased) ... *£46.50
Rotel RA210 ... *£34.50
Rotel RA310 ... *£32.00
Rotel RA610 ... *£48.80
Scaneltra HT58 ... *£29.75
Sinclair PRO60 2 x Z30/PZ5 ... *£15.25
Sinclair PRO60 2 x Z30/PZ6 ... *£17.50
Sinclair PRO60 2 x Z50/PZ8/Trans ... *£21.75
Sinclair AFU (Filter Unit) ... *£4.40
Sinclair 605 ... *£18.75
Sinclair 2000 Mk. II ... *£21.75
Sinclair 3000 Mk. II ... *£29.75
Wharfedale Linton ... *£39.95

TUNERS

Please add 50p P. & P.
Armstrong 523 ... *£39.50
Armstrong 524 ... *£31.00
Rogers R'brook FET4 (Chas.) *£31.00
Rogers R'brook FET4 (Cas.) *£35.00
Rogers R'bourne FET4 (Chas.) *£43.00
Rogers R'bourne FET4 (Cas.) *£48.00
Sinclair PRO60 (Module) ... *£18.50
Sinclair Cased Tuner ... *£34.00
Philips RH690 ... *£33.00
Leak Delta FM (Cased) ... *£55.50
Leak Delta AM/FM (Cased) *£66.50

SPEAKERS

Please add £1.25 P. & P. Price per pair
Amstrad 138 ... *£20.00
Wharfedale Denton 2 ... *£29.00
Wharfedale Linton 2 ... *£37.00
Wharfedale Melton 2 ... *£47.95
Wharfedale Dovedale 3 ... *£61.50
Celestion Ditton 120 ... *£39.00
Celestion Ditton 15 ... *£55.00
Celestion Ditton 25 ... *£89.00
Goodmans Double Maxim ... *£48.50
Goodmans Mezzo 3 ... *£45.75
Goodmans Magister ... *£78.25
Sinclair Q16 ... *£12.50

CARTRIDGES

Please add 10p P. & P.
Garrard GC536* ... 95p
Goldring G850 ... *£3.65
Goldring G800 ... *£6.25
Goldring G800E ... *£10.35
Goldring G800 Super E ... *£15.75
Shure M3D ... *£4.50
Shure M447 ... *£6.80
Shure M44C ... *£6.25
Shure M44E ... *£6.75
Shure M756 ... *£8.50
Shure M75E Type 2 ... *£12.35
Shure M75E Type 2 (Improved) *£27.95
Sonotone 9TAHC ... *£1.65
Audio-Technica AT66 ... *£4.40

PLINTHS & COVERS

£3.20*



Plus 35p post and packing
Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for BSR, McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B. £4.20 plus 35p P. & P. Also finished in walnut to match Japanese equipment—at no extra charge.

All prices correct at time of going to press.



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. E.E.7 174 Pentonville Road, London, N1. Telephone 01-278 1789
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

ERSIN



5 CORE SOLDER

for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 75p
Size 12



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 75p
Size 10



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

19A 60/40 18 18p*
Size 5
(III-ustra-Savbit 18 18p* ted)

15 60/40 22 22p*

*Recommended Price

INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily


adjustable for all standard diameters. Plastic covered handles, can also be used as wire cutter. Recommended retail price 50p



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

RADIO CONSTRUCTOR

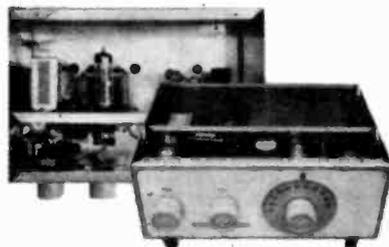MARCH ISSUE FEATURES 'EASY' 2" METRE RECEIVER



By F. G. Rayer, Assoc.I.E.R.E. G30GR.

An excellent project for the newcomer to 2 metre reception — employs a super-regenerative detector, this 3 valve receiver offers no alignment problems.

MORE CONSTRUCTIONAL PROJECTS ON SALE NOW PRICE 20p

Copies may also be obtained direct from the Publishers, 24p. including postage. Published by Data Publications Ltd. 57 Maida Vale, London W.9

BSR LATEST SUPERSLIM

STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR guarantee with 12 months* reliability. AC 200/250v. Size 181 x 111in.



Above motor board 3 1/2in. below motor board 2 1/2in. with STEREO and MONO XTAL £8.75 Post 25p.
MONO-8-COMPATIBLE £7.75 Post 25p.

WCS DE-LUXE 3 WATT AMPLIFIER Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer. Kobs. With high performance Loudspeaker. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £4

R.C.S. PORTABLE PLAYER CABINET

£4 Post 25p.



Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18 x 15 x 8in. Metal fittings. Carrying handle. Popular colours. Two-tone resin cover.

GARRARD SINGLE PLAY TA MK II Ideal Discatheque or Hi-Fi. Stereo/Mono £10

GARRARD PLAYERS with Sonotone 9TA Cartridges Stereo Diamond and Mono Sapphire. SP25 Mk III £16. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

BSR JUNIOR SINGLE PLAYER £4.50 Turntable, 4-speed motor and separate pick-up

EMI PICK-UP ARM with mono stylus and stylus £1.25. **HI-FI PICK-UP CARTRIDGES**, Diamond LP Stereo, Stereo/Mono 9TA £2.50; GP94 £2.50; GP93 £2.00; Mono Sapphire GP91 £1.50; ACOS LP Sapphire £0.50.

E.M.I. WOOFER AND TWEETER KIT

£5.75 Post 25p

Comprising a fine example of a Woofer 10 1/2 x 6 1/2in. with a massive Ceramic Magnet, 4oz. Gauss, 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2in. square has a special lightweight paper cone and magnet flux 10,000 lines. Impedance Standard 8 ohms. Maximum Power 12 watts. Useful Response 35 to 18,000 cps. Base Resistance 45 cps.



WEYRAD P50-TRANSISTOR COILS

RA2P Ferrite Aerial 65p	Spare Cores 3p
OC P50/L1AC 30p	Driver Trans. LFDT4 50p
I.F. P50/2CC 470 kc/s. 33p	Printed Circuit, PCA1 50p
8rd I.F. P50/3CC 33p	J.B. Tuning Gang 85p
P51/1 or P51/2 35p	Weyrad Booklet 10p
P50/3V 35p	OPT 55p

VOLUME CONTROLS 800hm Coax 4p. yd. Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or L/R. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge BK. S.P. Transistor 25p.

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 Ω to 25 K. £2.5p
WIRE-WOUND 3-WATT STANDARD SIZE POTS. LONG SPINDLE 10 OHMS to 100 K 40p

VEROBOARD 015 MATRIX 2 1/2 x 6in. 26p. 2 1/2 x 3 1/2in. 17p. 3 1/2 x 3 1/2in. 26p. 3 1/2 x 5in. 30p. **EDGE CONNECTORS** 16 way 25p; 24 way 38p. **PINS** 36 per packet 2 1/2p. **FACE CUTTERS** 38p. **S.E.B.P. Board 015 MATRIX** 2 1/2in. wide 3p per lin., 3 1/2in. wide 4p per 1 in.; 5in. side 5p per lin. (up to 17in.). **S.E.B.P.** undrilled 1/2in. Board 10 x 8in. 15p.

BLANK ALUMINIUM CHASSIS 18 s.w.g. 2in. sides, 7 x 4in. 40p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 95p; 15 x 14in. 99p; 1 1/2 x 3in. 50p. **ALUMINIUM PANELS** 18 s.w.g. 6 x 4in. 9p; 8 x 6in. 15p; 14 x 5in. 15p; 10 x 7in. 19p; 12 x 5in. 20p; 12 x 6in. 25p; 16 x 5in. 25p; 14 x 9in. 34p; 12 x 12in. 40p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2p. 2-way, or 2p. 6-way or 3p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p. **SILICON REC. 40** LUCAS 200/500 Bridge 70V 5 amp 11. **RECTIFIERS CONTACT COOLED** 1/2in. wide 60mA 35p; 85mA 48p. **SILICON BYZ13 30p**; BY100 30p; BY127 30p. **TOGGLE SWITCHES** 1/2in. 4p; 1/4in. 3p; 1/8in. 2p.

"THE INSTANT" BULK TAP ERASER & HEAO DEMAGNETISER 200/250v. A.C. £2.35 Post 25p. Leadoff S.A.E. 15p



HI-FI STOCKISTS RETURN OF POST DESPATCH

RADIO COMPONENT SPECIALISTS

List 3p. Written guarantee with every purchase.

Everyday Electronics, April 1972

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240v. A.C. Output voltages available 6 or 9 or 12 or 15 or 18 or 20v. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST FREE
Details S.A.E. Size 3 1/2 x 1 1/2in.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 x 1/2". Response 25 cps. to 25 Kcps. 26db gain. For use with valve or transistor equipment. £9p Post 10p
Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V . . . 14p	250/25V . . . 14p	50+50/350V . . . 35p	
4/350V . . . 14p	500/25V . . . 20p	60+100/350V . . . 58p	
8/450V . . . 14p	1000/25V . . . 35p	32+32/250V . . . 18p	
16/450V . . . 18p	1000/50V . . . 35p	32+32/450V . . . 35p	
32/450V . . . 20p	8+16/450V . . . 18p	50+50/325V . . . 60p	
25/25V . . . 10p	8+16/450V . . . 20p	32+32+32/350V . . . 43p	
50/50V . . . 10p	16+16/450V . . . 25p	100+50+50/350V . . . 48p	
100/25V . . . 10p	32+32/350V . . . 25p		

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 12V. 15p; 25V. 20p; 50V. 30p.
1000mF. 12V. 17p; 25V. 35p; 50V. 47p; 100V. 70p.
2000mF. 6V. 25p; 25V. 42p; 50V. 57p.
2500mF. 50V. 82p; 3000mF. 25V. 47p; 50V. 65p.
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 95p.

CERAMIC 1pF to 0.01 mF. 4p. Silver Mica 2 to 5000pF. 4p. **PAPER 350V-0.1 4p.** 0-5 13p; 1mF 15p; 2mF 150V 15p. **500V-0.001 to 0.05 4p.** 0-1 5p; 0.25 8p; 0.47 25p. **SILVER MICA.** Close tolerance 1%; 2-500pF 8p; 500-2-200 pF 10p; 2.700-5.600pF 20p; 6.800pF-0.01, mid 30p; each. **TWIN GANG.** "0-0" 208pF-175pF. 65p; Slow motion drive 365+365 with 25+25pF. 60p 500pF slow motion, standard 45p; small 3-gang 500pF £1.60.

SHORT WAVE, SINGLE. 10pF 30p; 25pF 55p; 50pF 55p. **NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p.** **RESISTORS.** 1/w. 1 w., 20% 1p; 2 w. 5p 10 ohms to 10 meg HIGH STABILITY. 1 w. 2% 10 ohms to 1 meg., 10p. Ditto 5% Preferred values 10 ohms to 10 meg., 4p. **WIRE-WOUND RESISTORS** 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 8-2 ohms 10p.

SCOOP! METAL PLINTH AND PLASTIC COVER

Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 1/2 x 4 1/2 x 7 1/2in. Post 25p
£5.50
ALSO AVAILABLE IN SOLID MAHOGANY NATURAL POLISHED FINISH AT SAME PRICE

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp. £1.50
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.00
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £3.00
300-0-300 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. £3.25
MINIATURE 200v. 20mA. 6.3 v. 1 a. 2 1/2 x 2 1/2in. 75p
MIDGET 225 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2in. 90p
MINI-MAINE 20v. 100mA. 1 1/2 x 1 1/2in. 50p
HEATER TRANS. 6.3v. 3 a. 5.6 v. 1 1/2 amp. 60p
Ditto tapped sec. 4 v. 2.3 a. 5.6 v. 1 1/2 amp. 60p
GENERAL PURPOSE VOLTAGE Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2.25
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2.25
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.25
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.75
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 10v. £2.25; 50v. £2.25; 7.5v. £1.0; 100v. £1.4.
CHARGER TRANSFORMERS. Input 200/250v. for 6 or 15v. 1 1/2 amp. £1.50; 2 amp £1.50; 4 amp. £2.50. FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs, 1 1/2 amp. 4p; 2 amp. £1.80; 4 amp. £2.25 All transformers Postage 25p extra.

E.M.I. 13 1/2 x 8in. LOUDSPEAKERS

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. £4.55 Post 15p
(As illustrated)

With flared tweeter cone and ceramic base rate, 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 15p £2.75

10W MINI-MODULE £3.25 LOUDSPEAKER KIT

Post 25p
Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. x 8 in. Separate Bass, Middle and Treble Loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 8 ohm matching. TEAK VENEER BOOKSHELF ENCLOSURE. 16 x 10 x 9in. Modern design with slatted wood front. Highly recommended. £5 Post 25p

Teak Cabinet Size 18 x 10 x 9in. Post 25p £5

MINIMUM POST AND PACKING 15p

(Export: Remit cash and extra postage.)

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in. MAJOR £9

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch £7	12 inch £9	15 inch £19
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. or 10in. dia. speaker 20 x 12 x 9in. £9. Post 25p For 13 x 8in. or 8in. speaker 16 x 10 x 9in. £5. Post 25p For 10 x 6in. or 6in. speaker 18 x 8 x 6in. £4. Post 25p LOUDSPEAKER CABINET WADDING 18in. wide, 15p 1/2.

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns, Hi-Fi Enclosures Systems, etc. £4

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1.90 Post 10p.

Horn Tweeters 2-16kcs, 10W 8 ohm or 15 ohm £1.50. De Luxe Horn Tweeters 2-18 Kcs, 15W, 15 ohm 25p.

TWO-WAY 3000cps CROSSOVERS 8 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm, 2 1/2in.; 2 1/2in.; 85 ohm, 2in.; 3in 25 ohm, 2 1/2in. dia.; 3in. dia.; 8 x 3in.; 8 x 6in. £1 EACH 15 ohm, 3 1/2in. dia.; 7 x 4in.; 8 x 5in. 3 ohm, 2 1/2in. dia.; 5 x 3in. 5 x 3in. 7 x 4in. LOUDSPEAKERS P.M. 3 OHMS, 6 1/2in. £1.50; 8 x 6in. £1.60; 8in. £1.75; 10 x 6in. £1.90. ELAC 10in. 10W. De Luxe Ceramic, 8 ohm. £4.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £2.00 each. Post 15p. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50p 25p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. GOODMAN'S OUTPUT TRANSFORMER 8 WATT MULTI-RATIO EL84 etc., 3, 8 and 15 ohms 80p. Post 25p.

BAKER 100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. AC 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £39 Post Free

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.50

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and output with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4.50. £3.50

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4inch £12.50

BARGAIN FM TUNER as above less cabinet £8.85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTPUT BOXES, SURFACE OR FLUSH 25p.

BALANCED TWIN FEEDERS 5p. 80 ohms or 300 ohms. JACK SOCKET 8td. open-circuit 14p. closed circuit 28p; Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS 8td. Chrome 15p; 3 5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 8-pin 18p; 8-pin 25p. DIN PLUGS 3-pin 15p; 6-pin 25p. VALVE HOLDERS. 5p; CERAMIC 6p; CA95 5p.

E.M.I. TAPE MOTORS Post 15p.

120v. or 240v. AC. 1.200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. Size 3 1/2 x 2 1/2 in. (Illustrated) £1.25

BALFOUR GRAM MOTORS

120v. or 240v. AC. 1.200 r.p.m. 4 pole 50mA. Spindle 1/2 x 3/20. Size 2 1/2 x 2 1/2 in. Post 15p 85p

CUSTOMERS FREE CAR PARK CALLERS WELCOME
337 WHITEHORSE ROAD, CROYDON
Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)
Buses 50, 68, 159 pass door. Rail Selhurst Tel. 01-684-1665

ELECTRONIC ORGAN



ONLY £2.75

Don't confuse with ordinary electronic organs that simply blow air over mouth-organ type reeds etc. Fully transistorised. SELF CONTAINED LOUDSPEAKER. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play Silent Night, play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED. No soldering necessary, Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions. ONLY £2.75 + 23p p. & p. for kit, including case, nuts, screws, simple instructions etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY £4.95

FULLY TRANSAISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Handy built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and you HAVE A PORTABLE TREASURE LOCATOR EARLY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN £4.95 + 30p carr. etc. (High quality Danish Stethoscope headphones £2.75 extra if required.) EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.



BUILD 5 RADIO AND ELECTRONIC PROJECTS

only £1.97



Amazing Radio Construction set! Become a radio expert for £1.97. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 37p extra as illus. (if required) (parts available separately) no soldering necessary. Send £1.97 + 23p p. & p.

SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENDED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost self-life). CAN BE EARLY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones. Components, nuts, screws, wire, etc. no soldering. £2.25 + 25p p. & p. Parts available separately.



Only £2.25

FIND BURIED TREASURE! Transistorised Treasure Locator



ONLY £2.37

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC. Extremely sensitive, will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY £2.37 + 27p p. & p. (Sectional handle as illustrated 75p extra). Parts available separately. Made up looks worth £15.

Eavesdrop on the exciting world of Aircraft Communications

V.H.F. AIRCRAFT BAND CONVERTOR ONLY £2.37

Listen in to ALL LINES, PRIVATE PLANES, JETPLANES Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower, Hear for yourself the disciplined voices hiding tenderness on talk down. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portables). NO CONNECTIONS WHAT-EVER NEEDED. SEND ONLY £2.37 + 25p p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

SHORT WAVE TRANSISTOR RADIO

only £2.25



Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2" Only £2.25 + 17p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY £2.75



CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. SEND £2.75 + 25p p. & p. (parts available separately).

CONCORD ELECTRONICS LTD. (EE4X) 8 Westbourne Grove, London, W.2. Callers welcome 9 a.m.—6 p.m. inc. Saturday

The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (24p P & P)

ALSO AVAILABLE

SINGLE VICE: £3.37 1/2 (20p P & P)


COVENTRY MOVEMENT CO LTD.

Dept. E.4

BURNSALL ROAD, COVENTRY CV5 6BJ

STD 0203-74363

VEROBOARD

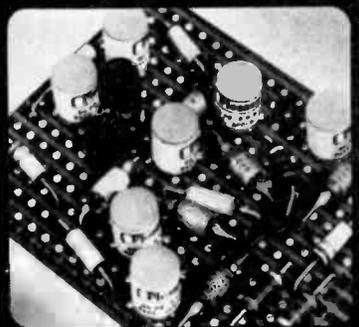

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper

clad universal circuit boards.


AVAILABLE FROM YOUR LOCAL RETAILER

TRADE DISTRIBUTOR N. Rose (Electrical) Ltd., London W.C.1



VERO ELECTRONICS LTD.
Industrial Estate, Cranborne Road,
SOS 22A Tel. Cranborne 3491 2921

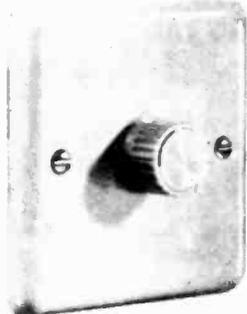Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression: 600 Watt £3.20. Kit Form £2.70 300 Watt—£2.70. Kit Form £2.20

All plus 10p post and packing.

Please send C.V.O. to:—

DEXTER & COMPANY
5 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH Tel: 0244-25883,
As supplied to H.M. Government Departments.

Everyday Electronics, April 1972



DRILL CONTROLLER NEW 1KW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-60 plus 13p post and insurance. Made up model also available. £2-25 plus 13p post and p.

MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 1/2 in. £1 each.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 5p each, 50p doz. Plastic pushrod suitable for operating. 5p each, 45p doz.



AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v. positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5-75 plus 25p post and ins.



TOGGLE SWITCH

3 amp. 250v. with fixing ring 7 1/2 each, 75p doz.

MICRO SWITCH

5 amp changeover contacts, 5p each, £1 doz. 15 amp Model 10p each or £1-00 doz.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 20p each, £1-80 for ten, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

BLANKET SWITCH

Double pole with neon let into side so luminous in dark. Ideal for dark room light or for use with waterproof element, new plastic case 80p each, 3 heat model 40p.




CAR ELECTRIC PLUG

Plugs in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 85p each or 10 for £3-45.



TREASURE TRACER

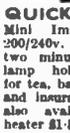Complete Kit (except wooden battery) to make the metal detector as the circuit in Practical Wireless August issue. £3-95 plus 20p post and insurance.



QUICK CUPPA

Mini Immersion Heater, 350w, 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1-25, post and insurance 14p. 12v. car model also available same price. Jug heater £1-50 plus p. & p. 14p.



SNAP ACTION SLIDE SWITCH

Rated 5a, 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuums, etc. 5p each, 10 for 45p.



NUMERICATOR TUBES

For digital instruments, counters, timers, clocks, etc. HI-VAC KN. 3, Price £1-45 each, 10 for £12.



12 WAY SUB-MINIATURE MULTI-CORE CABLE

7-0076 copper cores each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 90p per yard.



LIGHT CELL

Almost zero resistance in sunlight increases to 10 K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1in. dia. by 1/2in. thick. Rated at 500 MW, wire ended, 45p with circuit. Also ORP 12 light cell 45p.



THE FULL-FI STEREO SIX



The amplifier sensation of the year You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal chassis ready for mounting on plinth, this amplifier uses an integrated solid state circuit with an output power of 6 watt R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners. It has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. UNREPEATABLE PRICE is £25 50 plus 20p post and insurance. Stimulated teak cabinet £1-95 (post free when ordered with chassis).

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2-25 plus 25p P. & I



Smiths 24 hour 2 on/3 off Time Switch. This is the popular model, as used in the Autostat and Morphy Richards time switches. Only needs a case and an output socket. 230v 50 cycle. Contacts switch up to 13 amps. Price £3-75.

TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1. 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £2-50. 2kW. Model as above except 2 kilowatts £2-80. Don't miss this. Control 2 switch 55p. P. & P. 40p.



POCKET CIRCUIT TESTER

Test continuity for any low resistance circuit, house wiring, car electronics. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied). 30p or 2 for 50p post paid.



COMPUTER TAPE

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in. wide £1-00 plus 33p post and insurance, with cassette. 1/2 in wide £1-90 plus 30p post and insurance with cassette. 1/4 in wide 80p plus 25p post and insurance with cassette. Spare spools and cassettes—1in 75p, 1/2 in 75p each plus 20p post and insurance.




THIS MONTHS SNIP

MULLARD I.F. AMPLIFIER

3 transistors, 10 tuned circuits, Mullard Ref. No. LP L43289. Frequency not known but believed to be around 465. Mounted on printed circuit board size approx. 3" x 1 1/2". Enclosed and sealed in a metal case with tin copper connecting leads. 75p each. 10 for £6-75. 100 for £22-80.

RADIO STETHOSCOPE

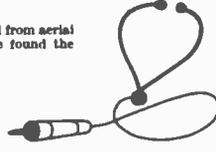Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2-15 in electro-set instead of carpiece 75p extra post and ins. 20p.



CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for an improved and even more efficient version (Practical for positive or negative systems. Also available, ready made ignition systems for 6v. vehicles. £5-25 plus 20p.

TYPE 25 RELAYS

These are miniature relays. Size approx. 1 1/4 inch high x 1 1/4 wide x 1 1/2 deep. 4 change over silver/gold contacts. Contact rating lamp 100v D.C. Fitted with a plastic cover. Coil operates approx. 250 Mv D.C. available with the following coils: 28 ohm for 1v-2.5v 45 ohm for 4v-7.5v 90 ohm for 5.5v-11.5v 130 ohm for 10v-15v 1250 ohm for 27v-44v 2500 ohm for 31v-65v 8900 ohm for 27v-44v 75p each. 10 for £4-75. Also one with 16,500 ohm coil but this has only 2 heavy duty change over gold contacts. Price £1-45.



MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into ohms speakers. Input suitable for crystal mic. or pick-up. 9 volt battery operated. Size 2" long x 1 1/2 wide x 1 1/2 high. SPECIAL SNIP PRICE 60p each. 10 for 55p.

0-8 AMMETER

2in. square full vision for flush mounting. Moving iron instrument. Ideal for charger. Price 45p each. 10 for £2-90.



BABY ALARM SIMPLE CALCULATOR POWER SUPPLY UNIT

To receive these and other featured kits promptly send approximate quoted price and we will refund any change.

Veroboard. We are now stocking this in various sizes. Prices as follows:

2 1/2 x 3 1/2	0-1	0-15
2 1/2 x 5	22p	18p
3 1/2 x 5	34p	34p
3 1/2 x 5 1/2	34p	34p
3 1/2 x 5	37p	37p
17 x 2 1/2	75p	87 1/2p
17 x 3 1/2	100p	75p
17 x 3 1/2 (plain)	—	75p
17 x 2 1/2 (plain)	—	87 1/2p
2 1/2 x 5 (plain)	—	17 1/2p
2 1/2 x 3 1/2 (plain)	—	15p
Pin intersection tool	47 1/2p	47 1/2p
Spot face cutter	37 1/2p	37 1/2p
Pkt. 50 pins	30p	30p

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types: Miniature, 1" long x approximately 1/4" diameter. Will make and break up to 1/2 A up to 300V. Price 18p each, £1-90 dozen. Standard, 2" long x 1/4" diameter. This will break currents of up to 1A, voltage up to 250V. Price 10p each, 80p per dozen. Flat. Flat type, 2" long, just over 1/4" thick, flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1A 200V. Price 80p each, £2 per dozen. Small ceramic magnets to operate these reed switches 6p each, 50p dozen. Dry Reed Relays. Solenoids on moulded bobbins within magnetic shields—printed circuit or panel mounting.

Ref. No.	Coil Resistance	Reed Switches	Price
71005	2 K	1 normally open	85p
81916	6 K	1 normally open	—
		1 normally closed	75p
05003	4 K	1 normally open	85p
62040	1500 & 500 ohms	1 normally open	85p

Multiple Reed Relay, Ref. 48001. Contains 13 normally open reeds within a solenoid. Operates on 600 mW. Coil resistance 92K ohms. Price £1-95 each. Multiple Reed Relay, Ref. 031. 2 normally open 1 normally closed coil resistance 30 ohms. Price 75p. Faostat. This is a thermostat with Sensor on the end of a long capillary tube. The temperature range is 50-120°C approx. The setting is by spindle for pointer knob (knob not supplied). The Sensor can be immersed in the liquid or can be fixed to the container or as when used on a heating cooker, this can be fitted in the centre of a heating element. Price 65p each, £5-85 for ten. Many other thermostats available please request list.

KITS FOR PREVIOUS PROJECTS

Unless otherwise stated, kits contain electronic parts only. The case and special items can be obtained locally. Also batteries are not included. Kits may be returned for refund if construction has not been started. We reserve the right to substitute components should deliveries be protracted so as to avoid undue delay.

HOME SENTINEL INTRUDER ALARM	Electronic Components with case	£3-75
SNAP INDICATOR		75p
WINDSCREEN WIPER CONTROL	Components including metal for chassis	£2
RECORD PLAYER	All components, but not case, loudspeaker, record deck or pick-up	£5-65
DEMO DECK		£6-75 POST PAID
FUZZ BOX		£1-85
PHOTOGRAPHIC COLOUR TEMPERATURE METER		£2-65
ASTRON RADIO		£3
REMOTE TEMPERATURE COMPARATOR		£4-25
ELECTRO LAUGH		£2
TRANSISTOR MICROPHONE		£1-70
AUTO ALERT	All electronic parts and metal bracket	£2-80
RAIN WARNING ALARM	All electronic parts and chassis	£1-80
WA-WA PEDAL		£2-90
DARKROOM TIMER		£4-50
SIGNAL INJECTOR		80p
SOIL MOISTURE METER		£3-00

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

J. BULL (ELECTRICAL) LTD.

(Dept. E.E.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

THIS FANTASTIC OFFER ONLY FROM US!

SAVE £20.25 NOW!

NEW SOLID STATE BATTERY/MAINS AC/DC

Combined V.H.F AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE

Latest sensation in the world of sound! First-class makers. Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder and Player combined. AND runs off standard batteries or mains (plus in the 220/240V. AC line cord). Record, play back anything, anywhere! Even tape direct from radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44. WE OFFER AT ALMOST HALF PRICE!** Wonderful features: * Press button Keyboard Control panel! * New "pop up" Cassette ejection system! * "MAGIC EYE" Visual Battery check/recording level indicator or built in automatic leveller. * Separate ON/OFF, HI-LO volume control! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and external speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case, size 11½in. x 9½in. 3½in. overall approx., with carry handle. Designs vary slightly. Takes standard 30, 60, 90 or 120-minute Philips Cassette Tapes obtainable everywhere. The amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus BBC, National VHF. Picks up dozens of foreign stations. Also fabulous in car! You could pay ££££'s more for a Car Radio or Car Cassette player ALONE! **£23.75, CARA. 35p.** Simple instructions, remote control microphone with on/off switch and microphone stand. **BONUS—Standard Batteries and Cassette Tape 25p extra if required.**

OUR PRICE £23.75 CARR. ETC. 35p

RECOMMENDED RETAIL PRICE £44

COMMERCIAL TRAVELLERS Please note: Merchandising office at our Holborn Store. (PERSONAL SHOPPERS WELCOME AT BOTH STORES).

SHOPERTUNITIES LTD. S|L

ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!

BRAND NEW RUSSIAN WORLD BEATER!

6 WAVEBAND 10 TRANSISTOR PLUS 3 DIODES PORTABLE RADIO

WORLD WIDE RECEPTION **£9.97**

THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

THE VERY LATEST MODEL, SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection! Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. **YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE!** Yes, 6 separate wavebands including Standard Long, Medium and Short Waves to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even messages from all over the world. Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33½in length. It's also a fabulous CAR RADIO—any speaker requires no additional aerial. **UNIQUE!** Elegant Black, White and Chrome finished case. SIZE 10½in. x 8in x 3½in, overall approx. Magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST, ETC., 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

***COMPARE ITS PERFORMANCE with £34 RADIOS!**

Dept. EE/4, 164 UXBRIDGE ROAD, LONDON W12 8AQ (facing Shepherd's Bush Green) (THURSDAY 1, FRIDAY 7). Also at 37/39 High Holborn, LONDON, W.C.1 (Thurs. 7). Both stores open from MONDAY-SATURDAY 9 a.m.-6 p.m.

NOW BUILD ON! — WITH LST

FEATURING SOME OF THE MANY COMPONENTS FROM THE FREE LST CAT. HAVE YOU SENT FOR YOURS YET???

<p>TRANSISTORS We stock all popular types but how about our INTRODUCTION KIT £1—consisting of: OC71, OC44, OC45, AC128, BC107, 2N2926, OC72 incl. data and connection chart. ORDER AS PACK NO: EE1 <input type="checkbox"/></p>	<p>IC AMPLIFIER PLESSEY 5L403D WITH DATA AND CIRCUIT INSTRUCTIONS £1.50 <input type="checkbox"/> ORDER AS 5L403D</p>	<p>NEON PACK 50p Consisting of 10 miniature neon indicator bulbs 65Vac 90 Vdc. Use 270k resistor for mains use. ORDER AS PACK: EE5 <input type="checkbox"/></p>
<p>DIODES INTRODUCTION KIT 50p 2 x OA81, 2 x OA200 4 x 1N4001 (All recently used in EE projects) ORDER AS PACK NO: EE2. <input type="checkbox"/></p>	<p>CAPACITOR PACK 50p 10 popular values of capacitor including polyester and electrolytic good starting stock! Normal Cat. price over 65p ORDER AS PACK EE4 <input type="checkbox"/></p>	<p>BOOKS ETC: Designers Guide to British Transistors: Data on 1000's of common types £1.40 110 Semiconductor Projects. Marvellous book for the enthusiast: £1.35 <input type="checkbox"/></p>
<p>VEROBOARD PACK 50p 36 square inches total area (approx) consisting of .1 and .15 matrix ORDER AS PACK V10: <input type="checkbox"/></p>	<p>PHOTORESISTOR ORP12 50p Price includes data sheet. (German LDR03 type) ORDER AS PART NO: LDR03 <input type="checkbox"/></p>	<p>HOW TO ORDER: Cut out whole advert. Tick boxes for packs required. Fill out name and address enclose payment. ALL ITEMS THIS AD. POST FREE.</p>

PLEASE NOTE: Offer applies UK only—Overseas send extra postage. We will refund any overpayment All orders despatched day of receipt. Spares for all packs in our FREE catalogue.

LST ELECTRONIC COMPONENTS LTD.,
DEPT. E.E.,
7 COPTFOLD ROAD,
BRENTWOOD,
ESSEX.

FROM:—
NAME
ADDRESS
ENCLOSED/CASH/CHEQUE/PO. £ : p
PLEASE PRINT CLEARLY TICK BOX → FOR CAT. ONLY

LST ELECTRONIC COMPONENTS LTD
7 COPTFOLD ROAD
BRENTWOOD ESSEX
Brentwood Z26470

BUDGET HIGH-FIDELITY STEREO SYSTEMS



ONLY
£40-95
carr. £1 75

FREE
LEADS
AND PLUGS
SUPPLIED
WITH ALL
SYSTEMS

PREMIER STEREO SYSTEM "ONE" Consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Power/on/off. Mono/Stereo switch. Stereo Headphone socket. Black leatherette cabinet with aluminium front panel. Size: 12½" x 6½" x 2½". (Amplifier available separately if required £16.25. Carr. 40p).

PREMIER STEREO SYSTEM "TWO", as above but with Garrard 8P25 MK III and magnetic cartridge. **ONLY £48.** Carr. £1.75.

METER BARGAINS



MODEL GT-800 MULTIMETER
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 10, 50, 250, 1,000V (1,000 opV). AC Voltage: 10, 50, 250, 1,000V (1,000opV). DC Current: 1mA, 100mA. Resistance: 0-150K ohms. Decibel: -10 +22dB (at AC 10V range) £2.47. P. & P. 17p.



MULTIMETER 20,000 O.P.V.
Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size 4½" x 2½" x 1". RANGES D.C. Voltages 0-5-25-50-250-500-2500V. A.C. Voltages 0-15-50-100-500-1000V. D.C. Current: 0-50µA 0-5mA-250mA. Resistance: 0-6000 ohms 0-6 megohms (300 ohms and 30 Kohms, at centre scale). Capacity: 10µF to 0.01µF, 0.01µF to 1µF. Decibels -20 to +22dB. £4.90. P. & P. 17p.



MODEL CT-62 MULTITESTER
RANGES—DC Voltages: 0, 5, 25, 100, 500/1,000V (20,000 ohms/V). AC Voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). DC Current: 0, 50µA, 0, 5, 50, 500mA. Resistance: 0, 5k, 600k, 6M, 60M ohms. Decibels: -20 db to +62 db in 5 ranges. £5.62. P. & P. 17p.



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 W. P. & P. watt. 240 volt A.C. £3.95 30p

"Markam" Soldering Iron. Lightweight ½" pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. £1.50 P. & P. 15p

VERITAS V-313 TAPE HEAD DEFLUXER
A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds. **£1.72** P. & P. 10p.

"VERITONE" RECORDING TAPE
SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped-attractively boxed.

LP8 3" 250' P.V.C.	28p	LP6 5½" 1200' P.V.C.	75p
TT3 3" 450' POLYESTER	37p	DT6 5½" 1800' POLYESTER	£1.12
DT3 3½" 600' POLYESTER	57p	TT6 5½" 2400' POLYESTER	£1.87
8P5 5" 600' P.V.C.	42p	SF7 7" 1200' P.V.C.	82p
LP5 5" 900' P.V.C.	55p	LP7 7" 1800' P.V.C.	75p
DT5 5" 1200' POLYESTER	75p	DT7 7" 2400' POLYESTER	£1.25
TAPE SPOOLS 3" 5p, 5", 5½", 7" 9p.		TT7 7" 3600' POLYESTER	£2.50

Post and Packing 3" 5p, 5", 5½", 8p, 7" 10p (3 reels and over Post Free).

PREMIER HI-FI OFFERS

- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52.50) **£38.50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49.00**
- MetroSound ST20E Stereo Amplifier in teak case (List £39.50) **£28.50**
- Golding GL75 less cartridge (List £41.61) **£29.00**
- Garrard SP25 III with Goldring G800 cartridge (List £28.35) **£15.50**

SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE COMPLETE IN TEAK PLINTH WITH COVER.
Total list price over £34.

- PREMIER PRICE **£18.90** P. & P. 80p.
- Garrard AP76 less cartridge **£19.50**
- Garrard AP76 with G800, ready wired to 5 pin Din in plinth with cover **£29.95**

Garrard 401 Transcription Unit List £40.15) **£28.00**

- Garrard 2025 T/C with Stereo Ceramic Cartridge **£9.97**
 - Garrard 2025 T/C with Stereo Ceramic Cartridge ready wired in teak plinth with cover **£12.45**
- Carriage and Insurance 50p extra any item.

PREMIER 800 STEREO AMPLIFIER




(As used in SYSTEM "ONE" above)
A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz -2 db. Distortion: 1%. Output Impedance 8 ohms non. Inputs equalised to R.T.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 6½" x 2½".

ONLY £16.25 Carr. 40p.



HI-FI STEREO HEADPHONES
Designed to the highest possible standard. Fitted 2½in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug. **£2.47** P. & P. 25p.

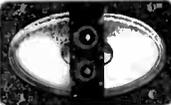STEREO STETHOSCOPE SET Low Imp. £1.25 P. & P. 10p
MONO STETHOSCOPE SET Low Imp. 62p. P. & P. 10p



E.M.I. 13x8in. HI-FI SPEAKERS
Fitted two 2½in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new. **£3.47** P. & P. 40p

VERITAS V-149 MIXER
Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 db. Standard jack plug socket inputs, phonoplugs output. Attractive teak wood grain finish case. **£3.47** P. & P. 12p

TAPE CASSETTES

CGO (60 min.)	37p	3 for	£1.05
C90 (90 min.)	62p	3 for	£1.90
C120 (120 min.)	87p	3 for	£2.55

P. & P. 5p.

FREE Cassette Head Cleaner with every 10 cassettes. All cassettes can be supplied with library cases at 3p. extra each



PREMIER RADIO
23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451

everyday electronics

PROJECTS....
THEORY.....

SELF SERVICE

The enthusiast who has more than a passing or casual interest in electronics will require a few items of test and measuring equipment. These will aid him when building projects, carrying out experiments, and fault finding. Such requirements are not lavish, and can be limited to about four or five items. Furthermore these can be reasonably simple in design, and can be built by the constructor himself, with real saving to his pocket.

EVERYDAY ELECTRONICS will be publishing designs for such items of equipment, from time to time. And this month we make a start by including full details of a mains operated power supply unit.

ON TAP

As we have already declared, many useful electronic devices and gadgets can be battery operated and if proof of this is required, look over the projects we have published to date.

Dry batteries have obvious advantages, but if a fair amount of practical work is intended, it will be found very convenient to have permanently on hand a d.c. supply that can be easily varied to give any output between zero and 16 volts. In other words, a "stand-in" for any of the commonly used batteries. So we recommend this power unit as an important acquisition for every constructor's workshop.

PLUNGE IN

We hope some of the enthusiasm shown by our *Memory Store* writers has been infectious and that many others have, as a result, been encouraged to take the plunge for the first time.

The wife of one reminiscing scribe has indeed taken the plunge—with pen, not soldering iron though—and her cautionary tale is published for the benefit of other wives!

WOMEN'S LIB

But in this enlightened age—equality of the sexes and all that—why should we assume electronics to be an exclusively male hobby?

In industry, the fair sex plays a prominent part in the manufacture of minute devices like transistors and other components; also in the wiring up and assembly of complete electronic equipments. Feminine touch and dexterity (and patience!) are assets in such operations.

There seems no logical reason why these attributes should not be channelled into a recreational activity as well. So perhaps the wife could be recruited as an assistant—or does the thought provoke cries of horror from hubby!

Seriously, there must be quite a number of women who are interested in electronics and who actively participate in this hobby of their own accord. We would like to hear from you, ladies.



Our May issue will be published on Friday, April 21

EDITOR F. E. BENNETT • M. KENWARD • B. W. TERRELL B.Sc.
ART EDITOR J. D. POUNTNEY • P. A. LOATES • S. W. R. LLOYD
ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Subscription Rates including postage for one year, to any part of the world, £2.35.
Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



.....EASY TO CONSTRUCT
.....SIMPLY EXPLAINED

VOL. 1 NO. 6

APRIL 1972

CONSTRUCTIONAL PROJECTS

SIMPLE CALCULATOR <i>An interesting educational project</i> by Mike Hughes	302
D.C. POWER SUPPLY UNIT <i>For testing constructed gadgets</i> by F. C. Judd	320
BABY ALARM <i>Remote audio monitor</i> by A. Lester-Rands	326

GENERAL FEATURES

EDITORIAL	300
RUMINATIONS by Sensor	306
SHOP TALK <i>Equipment and component buying</i> by Mike Kenward	307
THE TAPE RECORDER <i>How it works</i> by John Howcroft	308
WIFELY WOES <i>A constructor's wife advises others</i> by June Burn	313
TEACH-IN Part 6—Semiconductors: Diodes by Mike Hughes	314
FIFTY YEARS OF BRITISH BROADCASTING <i>How it all began</i>	330
IN-STORE WATCH-DOG <i>Electronic food protection</i>	330
TEACH-IN HALF TERM TEST <i>See what you really know</i>	333
READERS LETTERS <i>Comment and criticism from you</i>	334, 337


**SOMETHING
SPECIAL**

**Bound
to suit
your pocket**

The Everyday Electronics Constructors Companion booklet we are giving away next month is aimed at all constructors and will, we are sure, be of value to all our readers. This booklet can only be obtained by buying next month's issue so make sure you do not miss out. For more details on the Constructors Companion and next month's issue see page 325

Simple CALCULATOR

By
**MIKE
HUGHES**

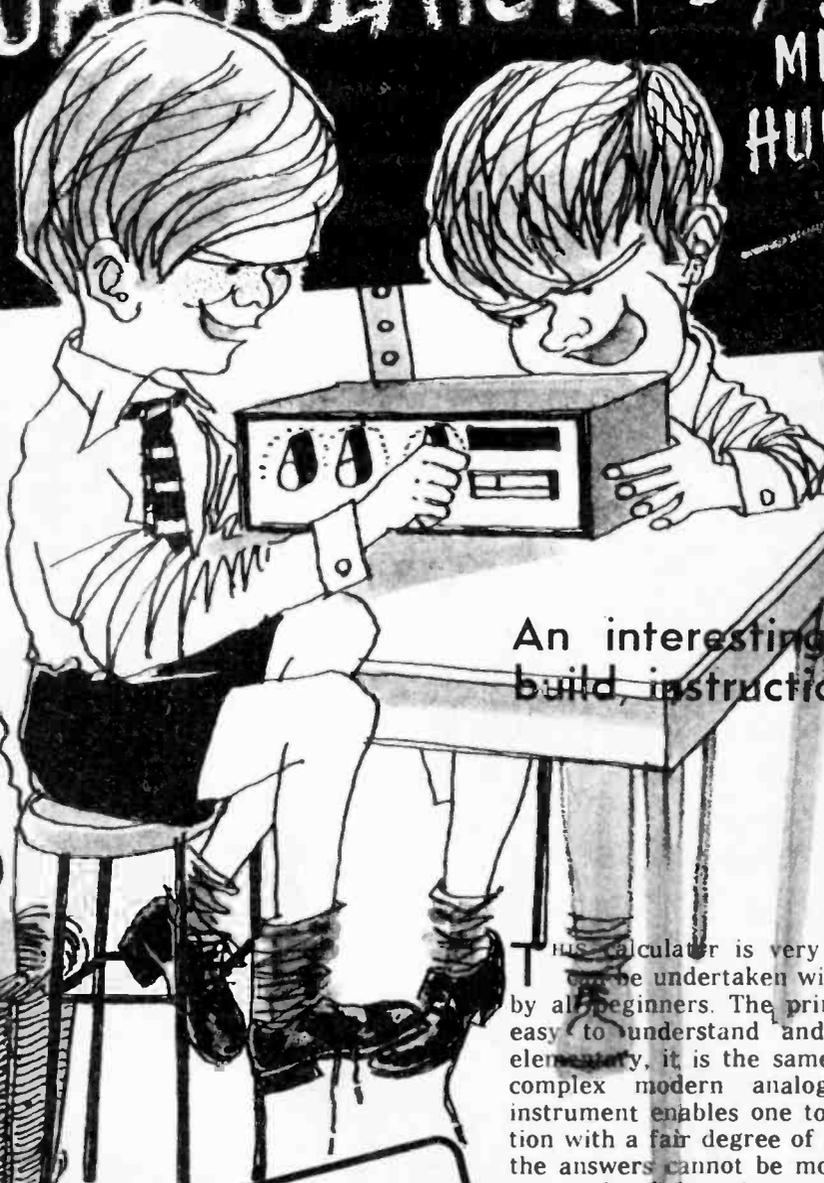

An interesting, simple to
build, instructional aid.

This calculator is very simple to make and can be undertaken without too much worry by all beginners. The principle of operation is easy to understand and, although it seems elementary, it is the same principle as used in complex modern analogue computers. The instrument enables one to carry out multiplication with a fair degree of accuracy—regrettably the answers cannot be more accurate than one can read a dial, so do not embark on the project if you want something that is going to be as good as, or better than, your slide rule. The best way of viewing it is as an interesting instructional aid.

There is very little wiring in the unit and most work will be found to be in the preparation of the knob dials—these control the ultimate accuracy. Before explaining the constructional details let us see how it works.

Approximate
cost of
components...
£ 1.20 plus case

Components....

Resistor

R1 1.2k Ω \pm 10%, $\frac{1}{4}$ W carbon

Variable Resistors

VR1 300 Ω

VR2 5k Ω

VR3 5k Ω

All linear wirewound

SEE
**SHOP
TALK**

Diodes

D1-4 OA81 or equivalent germanium diode

D5 IN4148 or equivalent silicon diode

Miscellaneous

ME1 100 μ A to 1mA edgewise level meter (see text)

S1 single pole single throw toggle switch

B1 9V Battery, PP3 type

Small Terry clip to hold battery, battery connector, pointer knobs, materials for case, connecting wire.

CIRCUIT THEORY

The complete circuit diagram is shown in Fig. 1. Potentiometers VR1, 2 and 3 are all working in their true mode—as potential dividers. Let us assume that we will be running off a 10 volt supply line (in actual fact it does not matter what this voltage is in the final unit). The potential at the wiper of VR1 can be set between zero and 10 volts the value being in direct proportion to the degree of rotation of the wiper. By calibrating the knob of this potentiometer with numbers from 0 to 10 we were able to accurately set a voltage to represent the number in question (we call this voltage the "analogue" of the number).

Potentiometer VR2 takes the potential at the wiper of VR1 and in turn we can tap off any proportion of this potential depending on how far we turn the control of VR2. If we connected a voltmeter between the wiper of VR2 and the common rail (Fig. 2) we could read the voltage

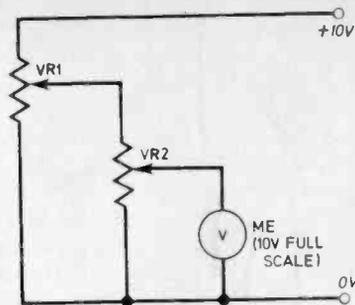


Fig. 2. Theoretical circuit to show the basic operation of the Simple Calculator.

that was left. Let us also calibrate the scale of VR2 with numbers 0 to 1.0 in 0.1 divisions. Set VR1 to five (the potential at its wiper would be 5 volts). Now set VR2 to 0.5 (i.e. half way)—the potential read on the meter would be 2.5 volts. The circuit is actually multiplying 5 by 0.5 to give an answer 2.5 but of course the answer is shown as an analogue voltage. You could work out a similar state of affairs by setting the number 8 on VR1 with 0.4 on VR2; the answer would be shown as 3.2V.

FINAL DESIGN

Obviously for the system to be accurate the battery voltage must be stable and also at first sight it would appear that the supply voltage ought to be 10V. The latter point is not necessarily true because we could make a voltmeter which was arbitrarily calibrated in "numbers" as opposed to real voltage levels. In practice however we need not worry about the battery voltage at all if we use a potentiometer (VR3 Fig. 1) to convert from the analogue voltage back to a number. This is done by having VR3 as a potential divider across the supply voltage. It is possible to set the wiper so that the potential produced by it exactly equals the potential at the wiper of VR2 and the answer is read off on the dial of VR3.

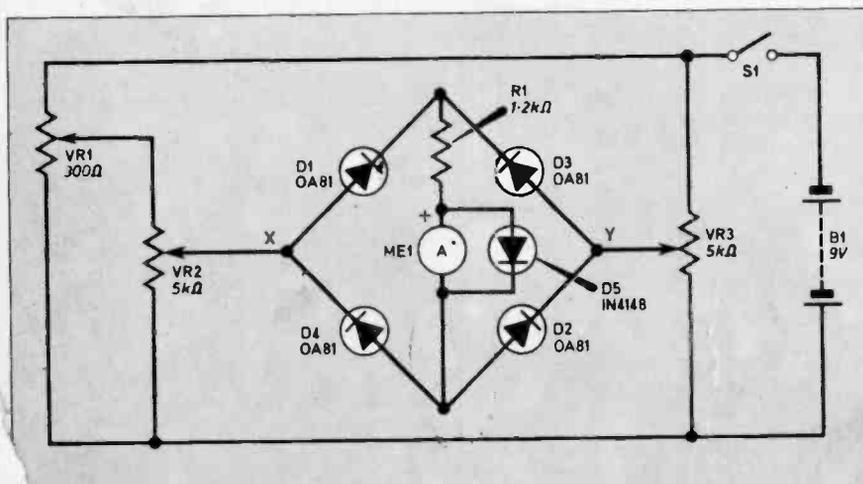


Fig. 1. Complete circuit diagram of the Simple Calculator.

We detect that the potentials at the two wipers are the same by detecting current flow. When there is no potential difference (i.e. potentials at X and Y are the same) no current will flow through the meter and diode circuitry. If that at VR2 is more positive then current will flow through D1, into the positive terminal of the meter and out through D2 (R1 is only there to protect the diodes from excessive current and D5 protects the meter movement). On the other hand if the wiper of VR3 was the more positive, current would flow the other way through D3 again into the positive terminal of the meter but out through D4.

Note that the meter will always read a positive current irrespective of the direction of current flow by virtue of the diode bridge. To find the answer to a multiplication all we have to do is adjust VR2 until the meter shows zero current flow and then read the proportion of rotation of VR3 off its dial.

OPERATION

As with a slide rule you can use the instrument to multiply any magnitude of numbers but you must decide for yourself where the decimal place will occur in the answer. In practice you should always attempt to set the number whose first digit is closest to 10 on VR1, otherwise you might find that the potential of the answer may be less than one unit of calibration and hence difficult to read on the dial.

Because of the independence of the meter to direction of current flow the polarity of the supply is unimportant and because everything is measured in terms of degree of shaft rotation of potentiometers and VR3 is run off exactly the same voltage as VR1 the actual value of the supply is unimportant. In practice it ought to be at least 4.5 volts to ensure sufficient current through the meter to enable one to identify an obvious zero, hence 9 volts will do. The prototype used a small PP3 type battery. Current drain is very small and if an on/off switch is provided the life of the battery ought not to be much less than its shelf life.

CONSTRUCTION

The potentiometers should be wirewound types and **must be linear law**. Note that VR1 has a value of resistance very much less than VR2 or VR3 although the actual values do not have to be the same as the prototype you should keep this ratio of values about the same or greater i.e., VR1 can be anything in the range 100 to 300 ohms while VR2 and VR3 can be 2 kilohms to 5 kilohms.

Diodes D1, 2, 3 and 4 **must be germanium** types to avoid a wide "dead band" on the meter and D5 **must be a silicon** type because it must not pass forward current until 500mV is placed across it. Most edgewise level meters may be used for the meter; the sensitivity should be

between 100 μ A and 1mA; actual sensitivity controls the ease of detecting small variations from zero current. Resistor R1 can be in the range 500 ohm to 1.5 kilohm.

The layout and wiring of the unit is shown in Fig. 3. All wiring is self supporting and layout is not important; the only important things to watch for are the polarities of the diodes and the meter, and to which ends of the potentiometers wires are connected—this is vital otherwise calibration will be reversed! As previously stated the battery polarity is not important in this circuit.


SCALE MARKING

Different types of potentiometer have different overall degrees of rotation and this must be determined for the types you have. Remember that there may be a dead portion of a few degrees at either end of the track. Use an ohm meter to determine the active degree of rotation you have and measure this using a pointer knob moving over a protractor. Once you have found this value (it should be between 260 degrees and 300 degrees, depending on the type of manufacture) divide it by 10 and then use a protractor to exactly mark off ten equal divisions round each potentiometer fixing (Fig. 4). These can be drawn in as radial lines over which a large pointer knob can move.

It cannot be over emphasised that this is the most critical part of the job if the instrument is to be at all accurate. Further subdivisions can be placed inbetween the major divisions if required.

The prototype used a piece of 14 gauge aluminium for the front panel (Fig. 5). Careful scrubbing with dry wire wool in a horizontal direction will produce a satin finish which can be

Fig. 4. Potentiometer control marking. This should be carried out as accurately as possible.

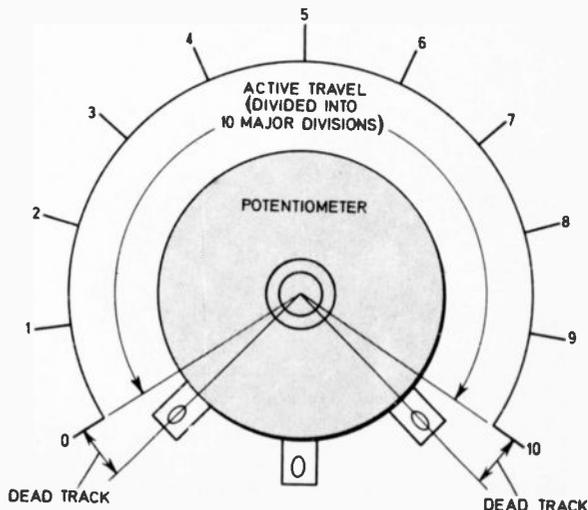

Simple Calculator

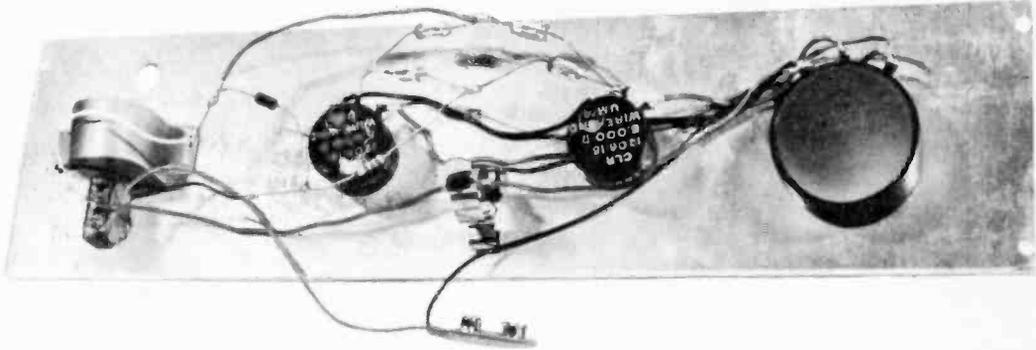


Fig. 3. Layout and wiring of the Simple Calculator. Battery B1 is mounted in a Terry clip fixed to the front panel.



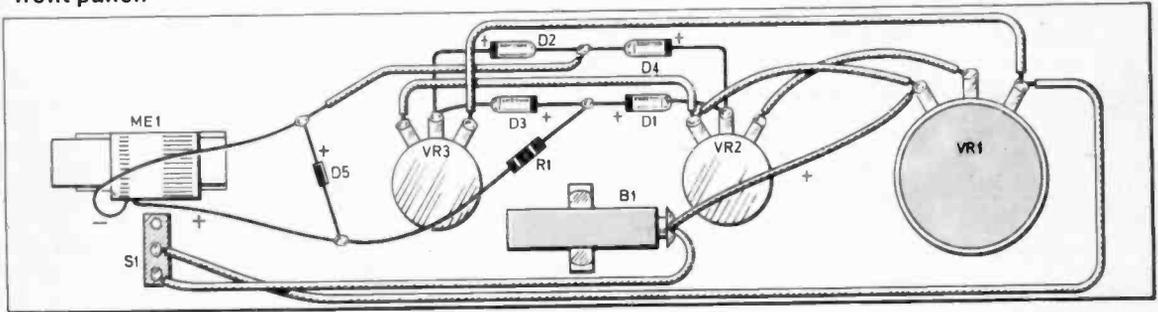


Fig. 5. Front panel drilling details and case dimensions.

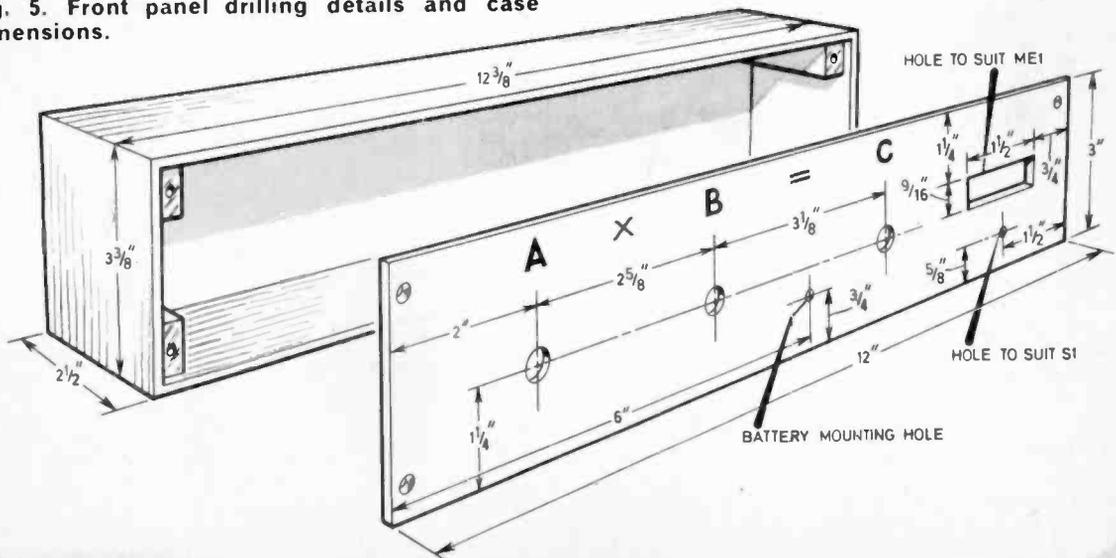

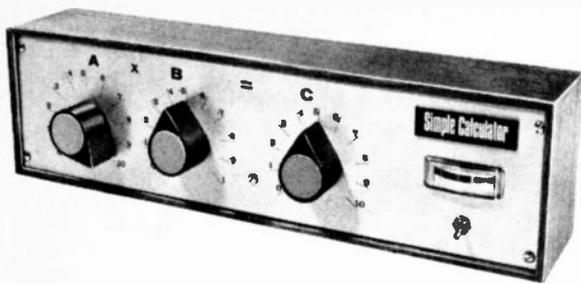

View of the completed Simple Calculator showing the designations affixed to the front panel using Letraset.

immediately lacquered with aerosol polyurethane varnish. This provides a good finished surface which can be marked using Letraset. The surface can then be given a final coat of varnish to protect the lettering. A practical tip to ensure reasonable accuracy is to adjust the zero set of the meter (in simple level meters this may be inside the case) so that the needle is some way up the scale in its neutral position; this makes it easier to determine a zero current position.

A simple wooden case can be made to house the completed unit as shown in Fig. 5. The hole for the meter may differ according to the type of meter used.

APPLICATION

The knobs of the prototype were labelled A, B and C as shown in Fig. 5. This way it is easy to give instructions on how to use the calculator. Set the two numbers to be multiplied together on A and B and then turn C until minimum current is seen to flow through the meter; the answer can be read off dial C.

Reciprocals can be found by setting C at 1, next set the number whose reciprocal is required on B and turn A for zero current—the answer is shown on dial A. An extension of this enables one to carry out divisions where the answer must always be a decimal fraction less than unity. For example 2 divided by 3. Set 2 on C and 3 on B and turn A for zero current. The number displayed on A will be approximately 6.6 this means that the answer is 0.66.

If you wish you may subdivide the main divisions of the scale into ten finer units thus enabling better accuracy with two digit numbers. Obviously the larger the diameter of the scales the easier it is to work accurately, but there is a limit to the ultimate accuracy of the calculator. This is due to the linearity of the potentiometers and the ability of the meter to detect very small current near zero—the latter could be improved by using a more expensive 50µA meter. □

Cover picture: Blackboard and easel kindly loaned by A. W. Gamage Ltd., Holborn

Ruminations

By Sensor

Time to Stare

So restrictions on TV broadcasting hours are to be removed. I'm all for freedom and removal of restrictions but I am very suspicious of this move. There is, already, much more than enough TV for me, I don't want to pay for any more, and if programme time is increased someone has to pay. We all know who foots the bill, like it or not, in the end. As I see it, commercial television companies will seize the opportunity to sell more advertising time and will need to make programmes to fill in the slots between the advertisements. Inevitably, many of these new programmes must be in the "popular appeal" i.e. lowest common denominator class in order to capture the largest audience for the advertisements. So we are

unlikely to see anything different on our screens—just the mixture as before—but more of it.

The B.B.C. will want to compete with the commercial companies for the mass audience and must, therefore, increase its output of "popular" programmes; consequently, there will be a call for an increase in the licence fee. The cost of additional advertising on I.T.V. will be passed on to the consumer, by way of higher prices, resulting in a further increase in the cost of living. What will the viewer get out of it, more mush for morons?

Unnatural Breaks

The other evening I felt in need of some relaxation and I tuned in to I.T.V. to watch *Appointment with Fear*. The Hammer Films spine-chiller looked quite promising but didn't stand a chance; three breaks for advertisements made sure that any feelings of terror that might have been aroused were quickly dispelled. Rhapsodies about beans, margarine and pet food are unlikely to chill the marrow—at

least, not in their currently presented form, and but for the advertisements I could have been in bed ten minutes earlier.

I can switch off, I can choose my programmes but I cannot choose the advertisements that will interrupt my viewing and, perhaps, spoil my carefully selected entertainment. The B.B.C. has recently stepped up the advertising of its own programmes. The programmes have not been interrupted, as yet, for the advertisements but I find them irritating, nevertheless.

What does it all add up to? In my opinion, the entertainment value of television viewing is declining. I may be getting old and crotchety and a bit neurotic, but I look back with nostalgia to the days when full length plays and documentary films were regular features of evening viewing. We complained, from time to time when old films were shown too frequently, but those were surely the great days of television. Somewhere along the way, standards have slipped; it seems such a shame—electronics deserves better than this.

A NUMBER of readers have written to us asking for advice when buying a test meter. Firstly let us say that we will be publishing a design for such a meter at some time—it will be a simple device, easy to construct and providing ranges that would be used most for testing our designs. For those who still want to buy a meter the following advice may be of some assistance.

Firstly most meters are only as good as the price tag, by this we mean that it is probably best to buy the best you can afford. A good meter properly used and carefully treated will last a lifetime and if you buy a good one to start with you will never regret it. How do you know the good ones from the bad? The ranges available and the ohms per volt are the best way to tell (20,000 ohms per volt or more is good).


You can ignore the dB range and the capacitance range, unless you really know what you are doing these are useless so do not buy a meter just because it has these two extra ranges. We would not advise anyone to buy a meter costing less than about £3—you could probably make one as good for less.

If you can find a 20,000 ohms per volt (on d.c. ranges) meter with the following ranges it will satisfy most requirements for transistorised equipment testing and servicing:

- D.C. Volts 0-500 volts in about 4 ranges
- A.C. Volts 0-500 volts in about 3 ranges
- D.C. Current 0-500mA in about 3 ranges
- Resistance 0-5MΩ in 2 or 3 ranges

You may find it difficult to obtain a 500mA d.c. range on the less expensive meters, you could settle for a maximum of 250 mA.

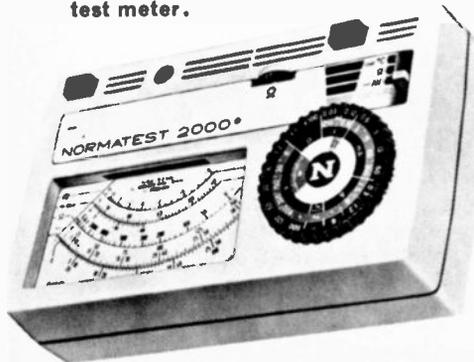The Normatest 2000 multi-range test meter.



Everyday Electronics, April 1972



If you want something really professional for £17.50 the Normatest 2000 multi-range test meter, that has recently been announced in this country, has 41 ranges, is 20,000 ohms per volt d.c. and 4,000 ohms per volt a.c. It covers the range 0-6A d.c., 0-600V d.c., 0-6A a.c., 0-600V a.c., 0-5MΩ in 6 ranges and has a maximum error of ± 2.5 per cent for the d.c. ranges. The meter can also be used to measure temperature (with the addition of a separate thermocouple) and gain -20 to +46dB. The price includes a carrying case and test leads.

We hope this information will be of some assistance, now let's look at possible problems arising from this issue.

Simple Calculator

You can hardly go wrong with the *Simple Calculator* construction, it will even work with the battery reversed! One point to watch is that you use germanium diodes for the bridge and a silicon diode for meter protection. The reasons for this are stated in the text. Almost any small meter will do and there are a number of 1mA range ones available from many suppliers.

Incidentally a centre zero meter could have been used without the bridge but this could have added to the cost. Also the article explains the bridge principle so you can learn something from it, we try to be educational as well as practical!

The wirewound potentiometers can be any rating—you will see

from the photo's that one used in the prototype was much larger than the other two—this does not matter. Incidentally you will find it difficult to buy log wirewound pots as they are not available, so the ones you do buy may not be marked linear, if you see what we mean.

The knobs used on the prototype are home made and are not available, however there are plenty of fairly large pointer knobs that are available.

Baby Alarm

The Newmarket PC2 amplifier module for the *Baby Alarm* is available from Home Radio and LST Components Ltd., incidentally L.S.T. are the distributors; prices may vary slightly its best to check first. Other than the module there should be very few buying problems.

As stated in the text the case used for the microphone does not have to be as large as it is and any small crystal microphone could be used. There are some available from suppliers for 60p or less—both the miniature types and the plastic encased types; this is probably cheaper than buying an insert and a case. If you do buy a complete microphone you will need a line socket to connect the microphone lead to the screened lead that feeds the amplifier.

Power Supply

The transformer used in the *Power Supply Unit* should be of reasonable size to fit the case design and a suitable 13.5V secondary type is available from Henry's Radio Ltd. The meter used in the prototype is a 1mA meter that has been calibrated 0-20V by the author. This meter can be replaced by a 20V f.s.d. meter that is available from G. W. Smith Ltd. Three things to note if you use the 20V meter; it costs the same as the 1mA meter, the two multiplier resistors R4 and R5 (10kΩ each) are replaced by a wire link and, the only point against, the meter is not so versatile if you want to use it in any other equipment at a later date.

Almost any 50 p.i.v. (or greater) bridge rectifier that can pass about 200mA will be suitable for the power supply or, as stated in the text it can be replaced by four individual rectifiers wired up in a bridge; this may be cheaper.



How it Works:

The Tape Recorder

By John Howcroft

ONE of the most important developments in modern communications is the magnetic tape recorder. Now capable of recording, preserving and reproducing high fidelity sound. Besides being a valuable instrument in many scientific projects and daily communication media, tape recorders have become part of the everyday domestic sound system. Modern developments, such as cassettes and more compact battery powered recorders have made taped material very simple to handle, use and store.

HISTORY

The "magnetic sound recorder," as it was originally known was first expounded in theory by Oberlin Smith in 1888. Smith devised a machine which would apply metallic dust to a cotton cord on which sound could then be recorded by a magnetic induction process. The machine did not, however see the light of day.

It was not until 1898 that the first practical magnetic recorder was built, it used a steel wire as the recording media. This "wire" recorder was produced by a Dane named Valdemar Poulsen. The recorder used a mechanical/electrical means of recording and reproducing sound since, at that time, no electronic means were available; the valve had not been invented.

Sound was recorded through a carbon micro-

phone connected into an electric circuit powered by a large dry battery. To replay the recorded sound a set of headphones was substituted for the carbon microphone.

Little more was heard about tape or magnetic recorders until the 1930s when Dr. Karl Stille developed an electronic magnetic recorder. Dr. Stille used steel tape in his machine and similar machines were developed and used for a number of years by the British Broadcasting Corporation.

During the second World War the Allies made use of steel wire recorders while the Germans developed a plastic-based, metallic oxide coated tape; this was the forerunner of today's magnetic tapes. The steel wire medium is now virtually extinct, but was used until quite recently in dictating machines.

MAGNETIC TAPES

The modern recording tape consists of a special plastic base normally acetate or polyester with a coating of ferrous oxide or similar metallic oxide. The particles of metallic oxide can be induced by a magnetic field so that they possess a similar magnetic field. The magnetic impression in these particles can represent a certain sound and, until the tape is disturbed by additional magnetic forces the recorded magnetic impression will remain on the tape.

To apply the necessary force to magnetise the

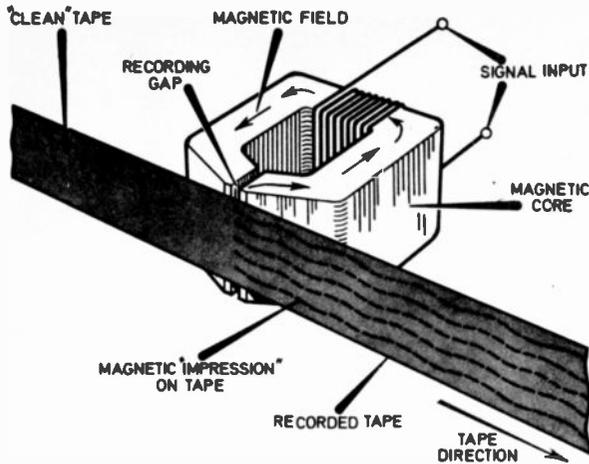


Fig. 1. The basic method of creating a magnetic field on a recording tape.

oxide particles on the tape so that these represent a piece of music or speech we apply the theory of electromagnetism. Magnetism can be created by passing an electric current through a coil of wire, preferably wound around a soft iron core. In the case of a recording head for a tape recorder this core usually consists of a number of soft iron laminates. The amount of magnetism can be varied by the amount of current flowing through the coil. To change the sound waves into an electric current a microphone and an amplifier are used. Sound waves acting upon a microphone mechanism produce a very small electric current. The amplifier magnifies the current produced by the microphone and, in turn, passes it on to the recording head of the tape recorder. The recording head transforms the electric current into a magnetic force. As the sound source varies in frequency and volume so also does the current and the strength and frequency of the magnetic signal at the recording head, and hence on the tape (Fig. 1).

RECORDING HEAD

The metal core of the recording head forms almost a complete circle, with the exception of a very small gap at the point where the tape will pass by it. The space created by the gap is closed by the ferrous oxide coating on the tape resting against the recording head, making a complete 360 degree magnetic field.

Thus the particles on the tape will acquire a magnetic impression or field similar to the signal being created by the current flowing through the coil. As the current varies, so does the magnetic field and, in turn, so does the magnetic impression on the ferrous oxide particles on the tape. During a recording the tape is passing the recording head at a constant speed. The impression of the magnetic particles on the tape is, therefore, a constant process.

BIAS

Unfortunately although the above description is true, in transforming sound waves into magnetic patterns on a tape, a problem which is fundamental to magnetic recording was encountered. This problem had to be solved before magnetic recording could be considered really satisfactory.

It was found that, when a magnetising force is applied to ferrous material the degree of magnetisation produced and retained is not proportional to the applied magnetising force. Beginning from zero, the amount of magnetisation first tends to rise very slowly, then rises more rapidly, then tapers off again as the ferrous material becomes magnetically saturated.


This occurs for magnetisation in either direction, so that the overall curve of induced magnetic flux plotted against magnetising force is as shown in Fig. 2 (curve (a)). The diagram also illustrates what happens to a sine wave signal which is passed through such a recording system.

For clarity, the input is shown as a pure sine wave (curve (b)). When transformed into a magnetic pattern, then recovered for subsequent amplification, the kink in the centre of the magnetisation curve is found to have produced a kink in the signal waveform (curve (c)). The end result is very severe distortion in the reproduced sound.

To overcome this effect, it is necessary to apply a magnetic "bias" to the tape so that the signal does not, as it were, centre on the kinked part of the magnetism curve.

The earliest system of magnetic bias involves placing a magnet near the recording gap, or passing a direct current through the recording head, together with the signal to be recorded, which causes the signal to centre on one of the straight portions of the curve.

Fig. 2. Illustrating the distortion produced by recording without bias.

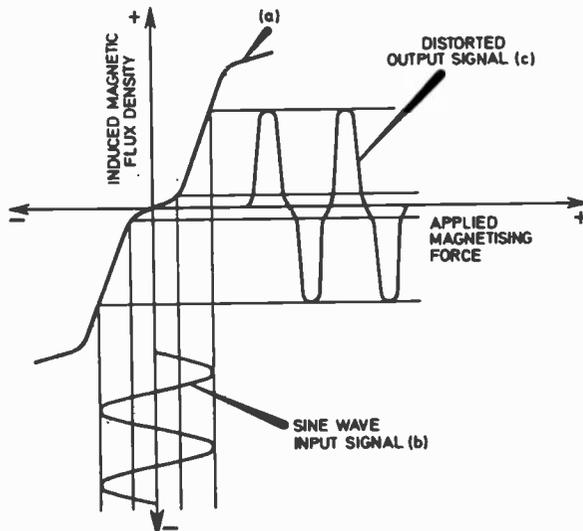

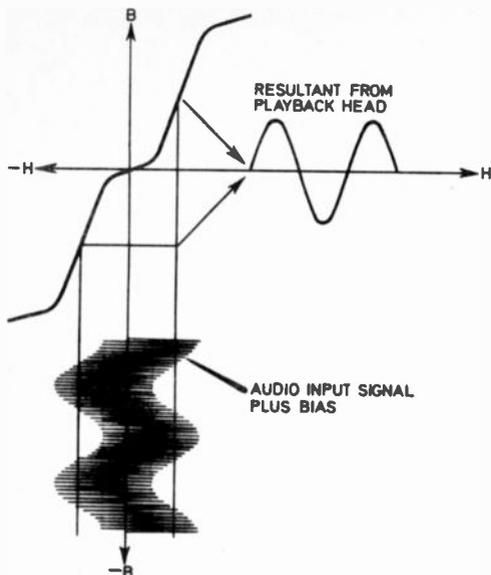


Fig. 3. High frequency bias recording system.

While a relatively simple method "d.c." or "permanent magnet" bias (as this system is called) tends to produce a recording with undue background noise. This is due largely to the fact that each discrete particle on the tape is magnetised in the same direction, so that the tiny pulses they produced are all additive and are heard as noise on playback.

HIGH FREQUENCY BIAS

Nowadays, all but the most elementary recorder's use a system of high frequency bias. A special oscillator in the recorder produces a high frequency signal well above the limit of hearing. During recording, this high frequency bias signal is fed into the recording head, along with the input signal.

Because the bias signal is at a very much higher frequency than the sound signal, the head is responding to a powerful magnetising force, even during instants when the sound signal waveform is passing through zero. This modifies fundamentally the way in which the particles on the tape respond to the sound signal.

In fact, as far as the recording head is concerned, the input signal is a composite waveform as illustrated in Fig. 3. As the tape passes across the gap in the record head, each particle is subject to one or more complete cycles of high frequency energy and is displaced bodily somewhere along its magnetising curve by the simultaneous presence of the audio waveform.

What each particle retains in the way of remanent flux would take far more space to explain than is available here. The end result, when the tape is played back, is an output waveform which is substantially free from non linear distortion, as in Fig. 3.

Because the particles are not all uniformly

magnetised in one direction as with d.c. bias, they do not tend to generate additive noise pulses as they pass across the replay head. The background noise with high frequency bias is therefore much lower than with d.c. bias.

ERASE SYSTEM

In most tape recorders, the high frequency oscillator incorporated to provide the bias is actually made to serve double duty. In a normal tape recorder the threading is arranged so that the tape passes over an "erase" head just before it reaches the record/play head. During replay the erase head is not in use. When a recording is being made, however, a strong signal from the high frequency oscillator is fed into the erase head, creating an intense high frequency magnetic field across the gap in its exposed surface.

The amplitude of this erase signal is made such that it magnetically saturates the particles on the tape in both directions as they pass across the erase gap. As they move out of the gap the magnetic cycling diminishes to zero and the particles are left with zero magnetisation. In other words erasure eliminates any previous recording so that the tape passes to the record head magnetically "clean".

REPLAY

To reproduce sound from a recorded tape is basically a reversal of the procedure and techniques used in recording it without the need for the bias. Where a current flowing through a coil can create a magnetic field, so too can a magnetic field passed through a coil create a current.

The tape is played back by passing it across the playback head in the same direction and at the same speed as when the recording process took place. (It might be noted that many tape recorders use a single head for both recording and playback functions.)

As the tape passes the gap in the playback head the magnetic impression carried by the ferrous oxide particles is induced into the play-

A modern stereo tape recorder.



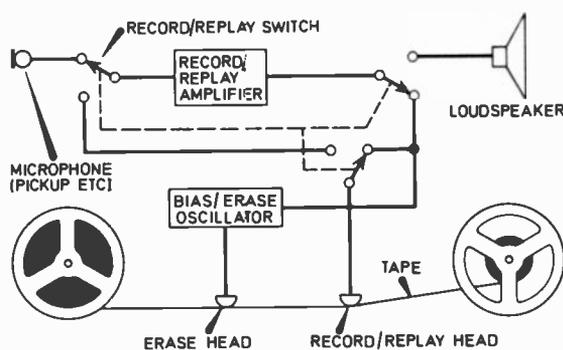
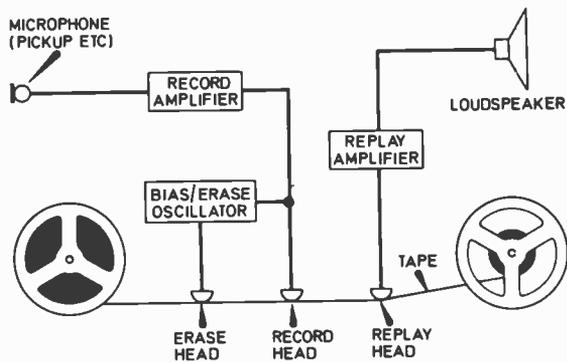


Fig. 4. Block diagrams of two basic tape recorder systems. Left—the system using separate record and replay heads. Right—the system using a single record/replay head.

back head. This magnetic field creates a current within the head and this current is fed into an amplifier and then to a loudspeaker.

The amplifier normally has a special frequency response to compensate for any changes in amplitude of the audio signal due to the record and replay process. Just as one head can be used for record and playback function. Block diagrams of two basic systems are shown in Fig. 4.

TAPE TRANSPORT

The transport mechanism used in a tape recorder is an interesting and essential device. It moves the tape across the recording, playback and erase heads.

On very cheap machines tape movement is achieved merely by motorising the take-up spool, simple though this method may be, it is not very effective. The actual speed of the tape across the heads will vary according to the amount of the tape on the take-up reel. For this reason any tape recorded on a machine of this nature must be played back on the same machine. On another machine the sound would be distorted because of variation in the original tape speed across the heads.

The more usual method of transporting tape, is to have a driving shaft or capstan close to the heads. The tape is held in contact with the capstan by a pressurised idler (or pinch) wheel. The capstan is directly connected to a flywheel (to ensure a constant speed) which is usually belt driven from a central motor.

This motor, through the use of additional belts, also keeps the take-up spool functioning so tape does not spill once it leaves the driving capstan. There is normally a slipping clutch arrangement on the take-up spool. This allows the speed of the spool to vary according to the amount of tape on it so that it keeps pace with the capstan and does not apply too much tension to the tape as it leaves the capstan (Fig 5).

The supply spool is usually more or less free-


wheeling with just a little pressure on it to prevent it from unspooling tape when the driving capstan and take-up spool are stopped. Some tape recorders have two driving capstans—one at each end of the erase and record/playback heads. This ensures a very high degree of accuracy in tape speed, which means more faithful reproduction of material recorded and played back.

Many modern tape recorders use three motors, one drives the capstan and is usually a synchronous motor which maintains a true speed constant to the mains frequency. The other two motors drive the take-up and supply reels. The operation of these two motors is governed by electro-magnetic switchgear to ensure the proper amount of tension on the reels so tape mishandling is eliminated.

FAST WIND

Almost all modern tape recorders are able to wind on and rewind the tape at a fast speed. In either of these modes the tape transport is concerned with but one purpose—that of getting tape onto one reel or the other as quickly as possible. The tape is not required to perform any electronic duty and is therefore lifted free and clear of the heads and released from the driving capstan mechanism. This allows the un-

Fig. 5. Basic mechanical arrangement of a modern tape recorder.

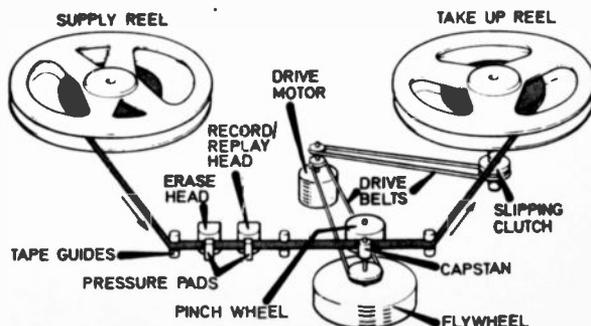

hindered passage of tape in either direction at fast speed. The mechanism lifting the tape clear of the heads also serves to protect the heads. The rate of wear under rewind conditions would soon render the heads useless.

In the fast forward mode, power is applied to the take-up reel. In the rewind mode the supply reel is powered. There is usually a slight braking effect on the opposite reel to prevent tape spillage should the operator decide to stop the tape.

Additional to the transport mechanism are tape guides which ensure proper alignment of the tape as it passes across the heads. Pressure pads are used to make sure the tape is held against the heads during recording and playback so there is no air gap between them. Both of these items help to ensure good reproduction of sound.

MULTI TRACK

Alignment of the tape across the heads is quite important particularly with the multi-track machines (two and four track). Originally tape recorders used just a single track, recorded across the full width of the tape. After playing such a tape it had to be rewound before it could be played again. The single track (which is confined to monaural recording) is used today for high fidelity requirements in professional and broadcast work.


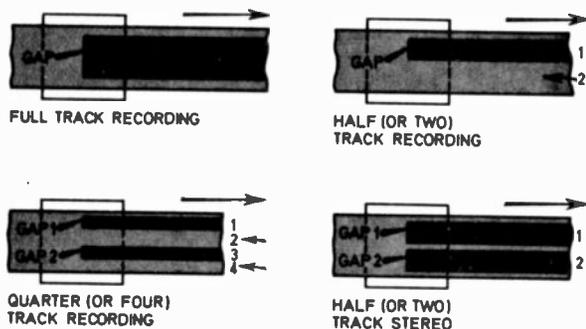


Fig. 6. Various track arrangements. In the four track system gap 1 records tracks 1 and 4, and gap 2 records tracks 2 and 3.

The next advance was the half or two-track system. This means the recording and playback heads are only as wide as half the width of the tape (actually slightly less than half to allow for separation of the two tracks).

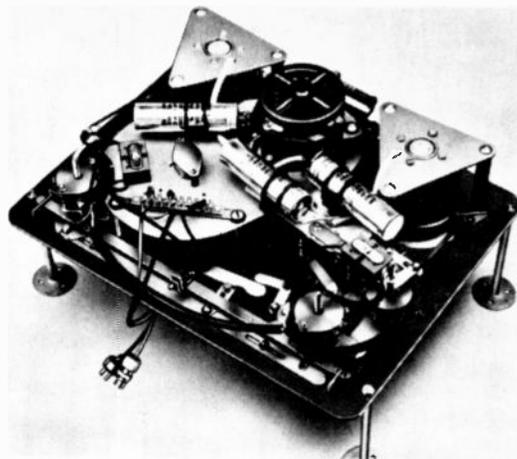With the two-track system a tape could be played through one way, then turned over and played through again using the material on the second track. The two-track machine also opened the way for stereo tape recording using one track for each channel but only (as in the one-track monaural system) capable of being played in one direction.



The underside view of a Brenell tape deck. This deck used three separate motors, one synchronous type for the capstan and the other two to drive each spool.

The four-track system solved the matter of letting one run a tape back and forth using stereo material. It also allows one to put a considerable amount of monaural material on a single reel of tape. This is done by ignoring the stereo mode completely and recording different monaural material on each of the four tracks (Fig. 6).

TAPE SPEED

The amount of material which can be recorded on a given length of tape can also be varied by the speed of the tape past the heads. Standard speeds in common use today are $7\frac{1}{2}$, $3\frac{3}{4}$, and $1\frac{7}{8}$ inches per second (in/sec). Other speeds are also used, such as 15 and 30 in/sec for sound studios and broadcast use. The faster speed is used where the utmost in fidelity of sound is required. The slower speed is only practical for voice reproduction and is used on some dictation machines or for recording lectures where fidelity is less important than extended playing time.

However, more advanced electronics and higher precision heads—at greater cost, of course—can offset the loss of fidelity at low tape speeds. Most modern domestic tape recorders offer high fidelity at $7\frac{1}{2}$ in/sec however, and this means reasonable tape costs for those building up their own libraries.

It should be realised, however, that the quality of the recorded material will not always match the quality of the original when taping from discs. And, of course, there is a variation in the ability of different tape recorders to duplicate the original fidelity of the sound.

As can be seen the modern recorder is a long way from the Poulson machine of the 1890s and with the introduction of electronic noise reduction systems and advances in the mechanical and tape aspects the tape recorder will go on advancing for some time. □



... but it most certainly is *NOT* decorative.

SINCE the main purpose of this magazine is to encourage and instruct our men-folk in a new hobby, I have prevailed upon the Editor to allow me a little space to present the other side of the coin—a wife's-eye-view of amateur electronics.

As the wife of a keen electronics man myself, it seems only fair to pass on to other wives a few hints and tips picked up over the years. His new hobby does cause some slight (?) disruption of the domestic scene. Of course, some of the lads may have workshops, or rooms set aside for their hobby. This is fine, girls, but do persuade him to fix up an intercom, otherwise you'll never speak to him.

My husband works on the dining-room table in our all-purpose living-room. This way, we do occasionally manage to exchange the odd word, but this



... I have yet to solve the problem of getting it off the wallpaper

Everyday Electronics, April 1972

Wifely Woes

arrangement can lead to domestic friction. Electronic equipment may be functional but it most certainly is *not* decorative, and all those trailing wires do have a nasty habit of getting entangled with the cleaner!

If he is messy with the soldering-iron, try to get some newspaper between the carpet and the flying solder—it's hell trying to get blobs of the stuff out of the Axminster/Wilton. I have yet to solve the problem of getting it off of the wallpaper, although this can usefully provide an excuse for demanding a change of decor.

Of course, your husband's new hobby will have its fringe benefits. As he becomes more proficient, he will be able to make all sorts of useful gadgets for the home and car—or so I am told! Let's face it though, these marvels of science seldom seem to materi-



... don't use his soldering iron as a tin opener

A few hints and tips for constructors' wives, passed on by the wife of last month's Memory Store author

By JUNE BURN

alise. In my experience, electronic test equipment breeds only more electronic test equipment. Still, I don't really want an electrically heated loo seat, do you?

This can be an irritating hobby, but bear with it. Ask him what he's making (even if you don't understand one word of the answer), sympathise when it doesn't work (it never does at first), don't use his soldering iron as a tin opener, and your marriage will probably survive this new interest. After all, while he's immersed in his transistors and integrated circuits, he's not got his mind on other birds, neither is he in the local with the boys. Mind you, there have been times when I would have liked to get my hands on that chap with the boat (see last month). Well, how would you like solder all over your cooker?



... he's not got his mind on other birds

ELECTRONIC CIRCUITS—
..... IN THEORY and PRACTICE



TEACH-IN

... FOR BEGINNERS

By Mike Hughes M.A.

6 SEMICONDUCTORS: Diodes

THIS month we introduce a very important family of components called “semiconductors.” Much has been written describing these devices and many people might wince if they looked at the background theory in detail. Nevertheless, in the practical sense they are fairly easy to understand and once you get the hang of their basic functions they are not so formidable.

In this series we shall limit ourselves to two types of semiconductor—the “diode” already mentioned in *Teach-In* Part 2, and the “transistor.”


N- AND P-TYPE DOPING

First of all a few words about semiconductors in general; if you have difficulty understanding the reasons why they work, do not worry—it is useful if you can, but not disastrous if you cannot.

They are usually made from the metals, germanium or silicon, which have the unusual property (for metals) of having very poor electrical conductivity in their pure states at room temperature. This is because the atoms are bonded together in a very precise manner and there are no “spare” electrons “floating about” as is the case of copper for example.

If we heat up the pure material we can “dislodge” a number of electrons and it will start to conduct electricity in the usual way. Alternatively, if we introduce an impurity into the metal (e.g., arsenic or phosphorus) we can distort the precise equilibrium so that an extra electron is available for conduction for every

Fig. 1. Schematic diagrams of a p-n junction (a) no voltage applied—not biased (b) reverse biased (c) forward biased.

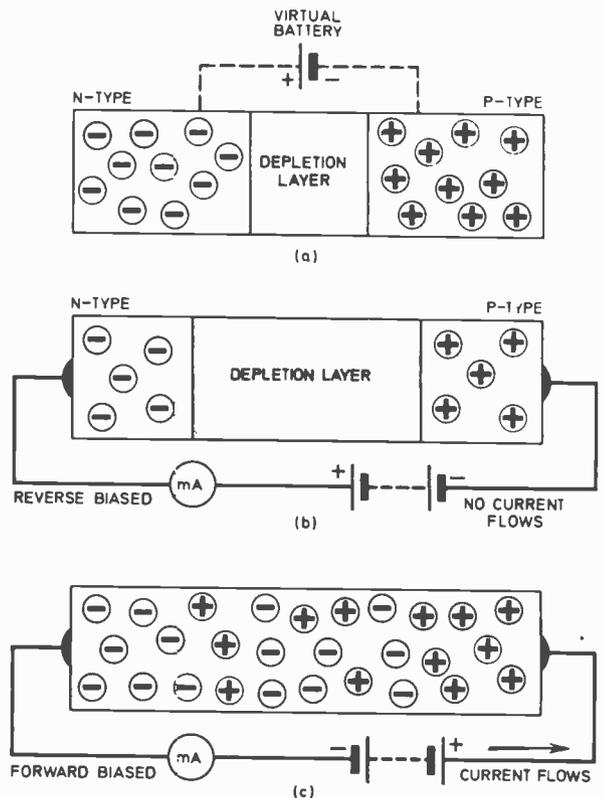

impurity atom added—this is known as “doping.” These extra electrons will be free to move about thus increasing the electrical conductivity. By “adding” electrons in this manner we say we are introducing “negative carriers” (of current) and the resultant material is called an “n-type” semiconductor.

We could have “doped” the material with boron which has the effect of absorbing an electron for every atom added. This leaves a “hole” where the electron should have been. As this also upsets the equilibrium an electric current can be made to pass, only this time because the holes move (from positive to negative). A material doped in this way is called “p type”; the p standing for “positive carriers.”

In practice the level of doping is very low and typically is only a few parts per million.

Because we can artificially control the conductivity in this way the metals germanium and silicon are called semiconductors.

P-N JUNCTION

Using modern techniques it is possible to bring together n- and p-type materials so that they are in perfect contact. At the interface between the two, the spare electrons in the n-type will cancel out the spare holes in the p-type, and a band is built up that is devoid of either positive or negative carriers.

At first you might think that this cancellation process would go on until all possible opposite pairs of carriers had cancelled out—but this is not so.


As the electrons move from the n-type material they leave it with a small positive charge. Likewise the holes moving from the p-type material will leave behind a slight negative charge. Eventually the negative charge in the p-type will start to repel any more electrons attempting to move across the interface and the cancellation process will stop at this point. The band of cancelled carriers is normally called the “depletion layer.”

THE DIODE

The semiconductor diode is simply a p-n junction. Let's see why it will only allow current to flow in one direction. The potential across the junction caused by the cancellation process is as if we had connected a battery between the p- and n-type materials with its negative terminal going to the p-type Fig. 1(a).

If we now connect a battery across the two materials (positive terminal to the n-type and negative terminal to the p-type), we will allow more cancellation to take place at the junction thus increasing its width Fig. 1(b); but because there are no free carriers in the depletion layer no current can flow across it.

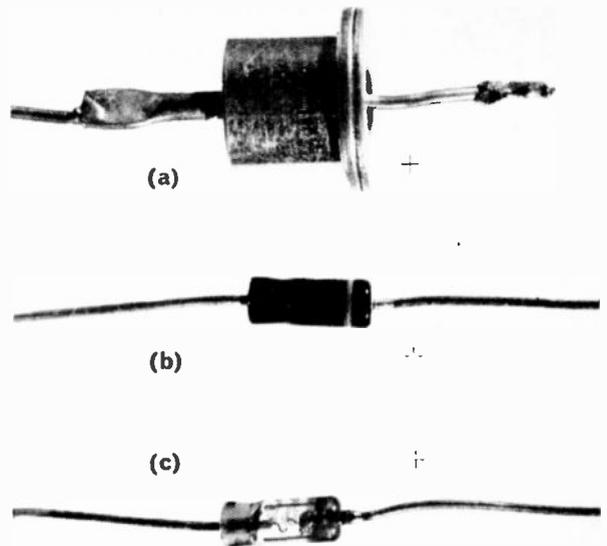In practice there are always a few carriers present (generated by other impurities or heat) and so there will be a minute current detectable



Three common diodes: (a) medium power rectifier, BY100 silicon (b) signal diode IN4148 silicon (c) signal diode OA91, glass encapsulated point-contact germanium (Magnified x 2½).

—this we call “leakage current.” If this leakage current is too great the junction becomes valueless. If, on the other hand, we had connected the battery in the opposite sense Fig. 1(c), the depletion layer would be destroyed when the voltage exceeded that of the “virtual” battery.

In the absence of the depletion layer (which was acting like an insulating barrier) current can flow virtually unlimited. When the battery was connected so no current flowed, the junction is said to be “reverse biased,” but when current flows it is said to be “forward biased.”

The voltage level of the virtual battery is rather important because it is quite noticeable in electronic circuits. For germanium it can be from 50 to 300mV and 300 to 600mV for silicon; variations are caused by changes of temperature.

BREAKDOWN AND POWER DISSIPATION

If we reverse bias the junction and apply larger and larger voltages, eventually we reach a level when the depletion layer breaks down and conduction suddenly occurs. This level is called the “reverse breakdown voltage” and can destroy the junction. This can vary from one or two volts to thousands of volts depending on the way the junction was made. Usually this sets the limit which we must never exceed but in some cases (Zener diodes) practical use is made of this parameter.

When conducting in a forward direction the material shows a degree of electrical resistance (even though it is usually small) and consequently some power is dissipated; this generates

heat and a rise in temperature degrades the junction performance. We always have to set a maximum forward current to prevent this happening.

All diodes work on the same principle and the only variations are in the magnitudes of reverse voltage and forward current limits, while the quality is defined by the reverse leakage current.

Like all semiconductors, diodes are sensitive to heat and although they are reasonably tolerant you should avoid overheating them when soldering (see *Teach-In Part 1*). With glass encapsulations you should not bend the lead out wires too close to the seal otherwise you might crack the glass!

DIODE TYPES

Diodes are identified by type numbers which are usually printed on the case. Regrettably one cannot identify any particular characteristic from this number and the only way to become familiar with these is to look them up in manufacturers' data sheets.

As there are thousands of different types of diodes made it is impossible to cover all possibilities in this series but by and large you will find that you can deal with most eventualities with either one of the following or similar types. OA91—a low voltage current germanium diode encapsulated in glass; 1N4148—this is very similar to the OA91 except that it is made from silicon; 1N4004—a reasonably high voltage (400V) medium current (1A) device made from silicon.

Because they are low voltage and current devices the OA91 and 1N4148 are sometimes

referred to as "signal diodes" while high voltage and medium to high current devices—such as the 1N4004 are called "rectifiers." The most important characteristics of these devices are given in Table 1.

POLARITY AND TEST

The two terminations of the diode have names. If you refer to Fig. 2, the end to which the arrow



Fig. 2. The circuit symbol used for the diode showing the polarities. Current flow is out of the cathode.

head of its symbol is pointing is called the cathode and this is usually marked on the actual device with a band, spot, or a + sign. The other (unmarked) end is called the anode. If you

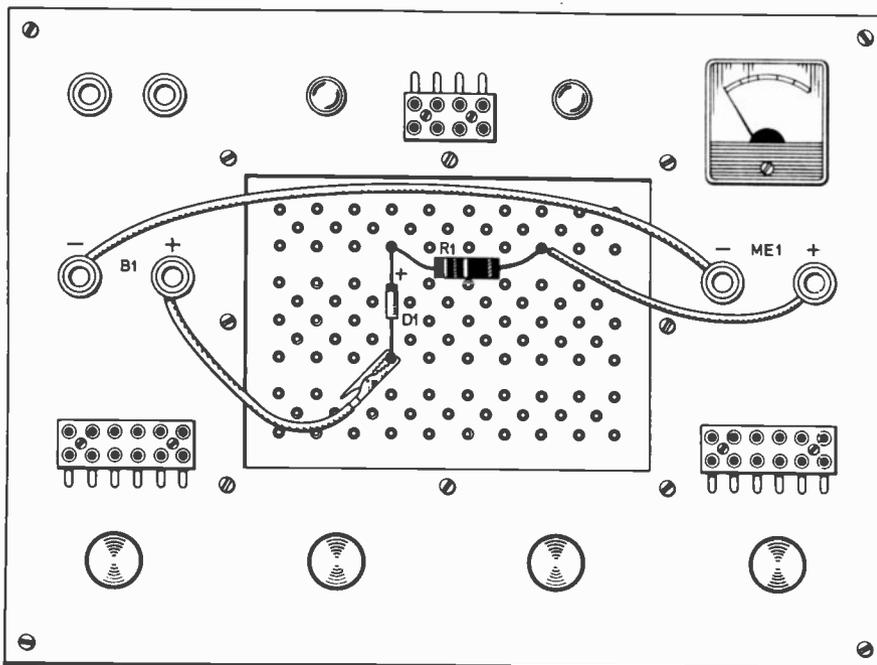
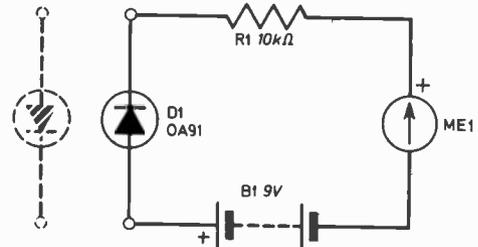


Fig. 3(a) (above). The circuit diagram for polarity test and demonstrating current flow in one direction only.

Fig. 3(b) (left). The circuit of Fig. 3(a) wired up on the Demo Deck.

Table 1: PARAMETERS OF SOME COMMON DIODES

Type No.	Description	Max. reverse voltage (V)	Max. leakage current (μ A)	Max. forward current
OA91	Germanium point contact signal diode	115	275 at 100V	50mA
1N4148	Silicon planar diffused signal diode	75	0.025 at 20V	225mA
1N914	Silicon planar diffused signal diode	75	0.025 at 20V	110mA
AA143	Germanium gold bonded signal diode	30	20 at 20V	60mA
OA200	Silicon alloy diffused signal diode	50	0.1 at 50V	160mA
ZS10A	Silicon alloy diffused signal diode	60	0.05 at 60V	100mA
1N4004	Silicon planar diffused rectifier	400	5 at 400V	1A

make the anode positive with respect to the cathode the diode is forward biased and will conduct. Try this for yourself using the Demo Deck (see Fig. 3), then reverse the diode to see that no current flows when it is reverse biased.

Use each of the three diodes to see that by and large they all exhibit the same effect. This is a simple test that can be used to see if a diode is working correctly.

CHARACTERISTICS—FORWARD BIASED

We will now try and plot what is called the

diode "characteristic" curve. This is simply a curve or graph that shows the amount of current flowing through it for different applied voltages.

To prevent passing too much current through the diode we shall limit it with an external resistor R3 in series with the diode, see Fig. 3(a).

Use VR1 on the Demo Deck to make a potential divider to use as a variable voltage source, and a 10 kilohm resistor in series with the 1mA meter to make a 10V full-scale voltmeter.

Connect the diode D1 (OA91) as indicated in Figs. 4(a) and (b).

Prepare a table for recording the voltages at points A and B— V_A and V_B respectively.

Starting at zero volts and working up in small increments, measure V_A (crocodile clip at point A) and then V_B (clip at point B) for each increment. Repeat the experiment with the silicon diode, 1N4148.

It can be seen that the voltage across the diode is equal to $(V_A - V_B)$ —multiply by 1000 to convert to mV.

Now the current flowing through the diode at each measurement is determined indirectly using the voltage seen across R3 and applying Ohm's law. In this case $I = V_B \div R3$. Since the

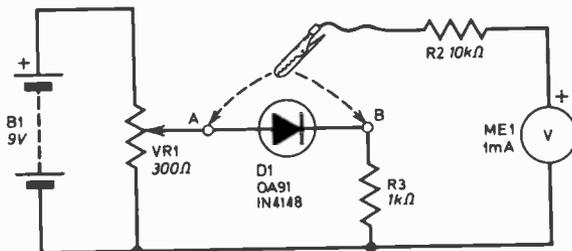


Fig. 4(a) (above). The circuit diagram for measuring the diode characteristics.

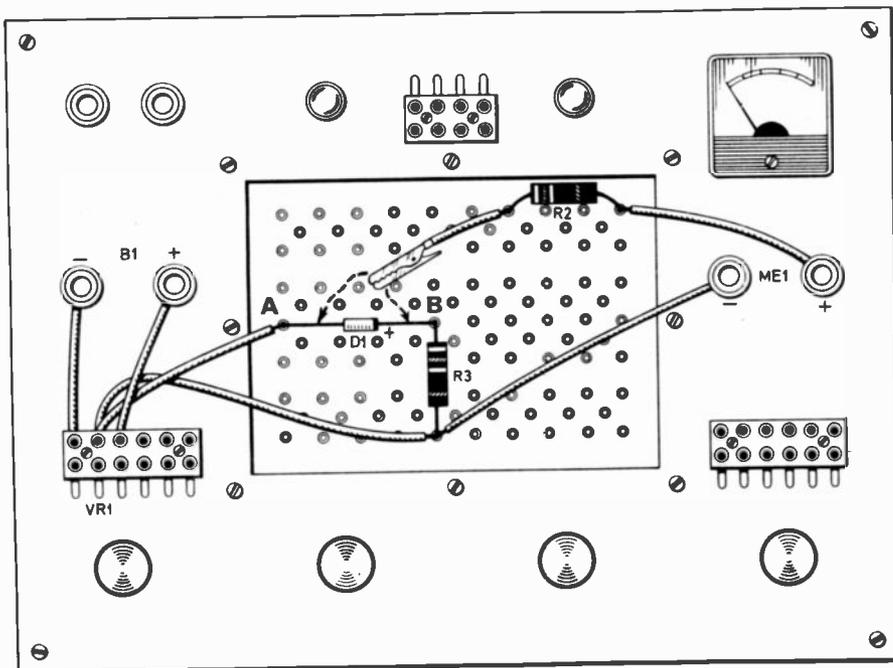


Fig. 4(b) (left). The circuit of Fig. 4(a) wired up on the Demo Deck.

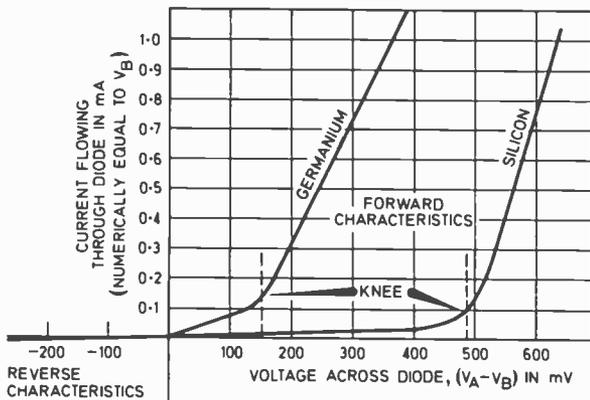


Fig. 5. Forward and reverse characteristics for the OA91 (germanium) and IN4148 (silicon) diodes obtained using circuit of Fig. 4(a). The two curves would eventually become parallel straight lines if we were able to plot the characteristics to a higher voltage.

value of R_5 is 1 kilohm, the numerical value of V_B (in volts) gives the current flowing, in mA.

Plotting graphs of current flowing against the applied voltage will give curves similar to those in Fig. 5.

It can be seen that for the germanium diode, OA91, there is a sudden change from passing little current to complete forward biasing at about 150mV. For the silicon diode, IN4148, this change occurs at a much higher voltage, 500mV.

This abrupt change or "knee" of the graph occurs when the voltage we are applying just exceeds the virtual battery across the junction of the diode.

—REVERSE BIASED

Although we do not have a high enough voltage available to cause reverse breakdown you can start to plot the reverse characteristics of these two diodes by reversing them in the circuit, i.e., cathode to the wiper of VR1 and measuring current for different voltages exactly as before. Of course you should read zero current at all voltages. Leakage current will be present but will not show up because our measuring system is not sufficiently sensitive.

TACHOMETER EXPERIMENT

We can demonstrate a very simple application of where two diodes can be used in a circuit. It is a very crude form of tachometer that will record on a meter the rate at which a contact is made to open and close. The circuit is shown in Fig. 6(a) and should be wired up on Demo Deck as shown in Fig. 6(b). You will only need one extra component—a $16\mu\text{F}$ capacitor with a minimum working voltage of 12V. D1 is the OA91 and D2 the IN4148 (another OA91 would work equally as well for the latter).


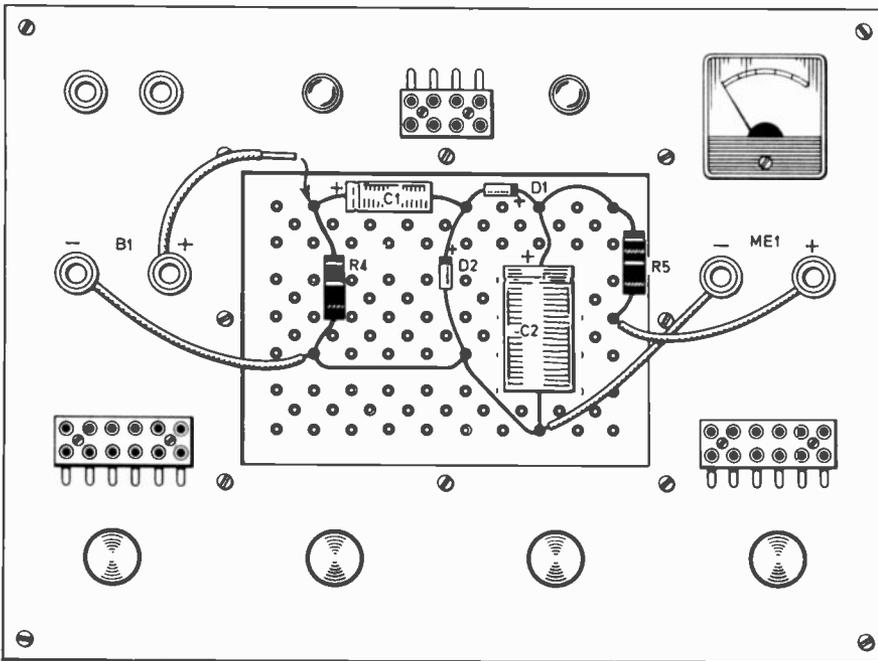
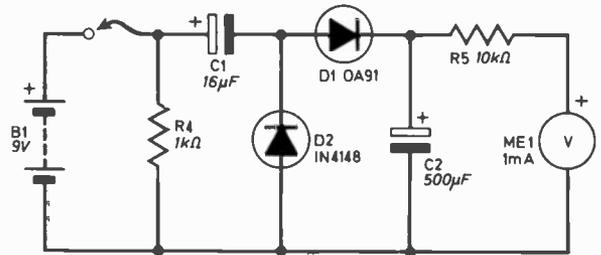


Fig. 6(a) (above). The circuit diagram for the Tachometer experiment.

Fig. 6(b) (left). The circuit of Fig. 6(a) wired up on the Demo Deck.

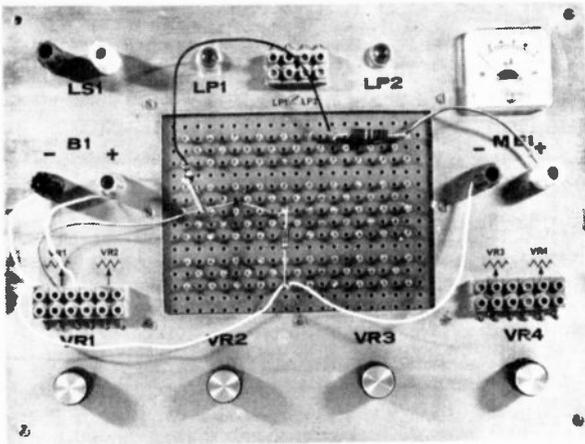

Photograph of the Demo Deck in use for measuring the characteristics of the IN4148 (silicon) diode.

METHOD

To operate the circuit, momentarily connect the positive end of C1 to the +9V supply and watch the meter, it will kick up a small amount and then slowly settle back towards zero. Now "dab" the wire on the +9V terminal at a regular rate—say once a second—and notice that the meter starts to read higher and although there is a slight waver in the reading you can see an average current level. Now speed up the rate of making the contacts—the meter reads higher. Note that this circuit will only work for rates up to a few a second.

THEORY

The circuit we are using is called a "diode pump" and works as follows: initially there is no charge on C2 so the meter reads zero. When you apply the positive lead to C1 a momentary charge current will flow through C1, D1 and C2 which are all in series.

Because C1 has a small capacitance, it will charge up quickly—C2 only attaining a small charge—and the charge current stops (even though the wire is still connected to the battery).

Capacitor C2 does, however, charge up by a small finite amount and this causes the "kick" you see on the meter, but C2 will then start to discharge slowly through the 10 kilohm resistance of the meter circuit.

When you disconnect the battery, C1 will discharge through R5 and D2.

During the charging part of the cycle, D2 was reverse biased because the potential at its cathode was predominantly more positive than the anode, but now the positive charge at the positive end of C1 is applied, through R5, to the anode and so it conducts this charge away at a rate limited by the value of R5.

The potential at the cathode of D2 thus falls to zero. Because C2 has a slight positive charge on it D1 now becomes reverse biased and pre-

vents C2 discharging back through the circuit. If you re-apply the +9V to C1 the charge part of the cycle starts again and the potential at C2 will either rise back to its previous level or go higher, depending on time between pulses.

The circuit gets its name "pump" because the two diodes work rather like the leather flap valve of an old-fashioned water pump that is pumping squirts of water into a bucket with a hole in the bottom.

The circuit given here is purely for demonstration purposes and cannot be used for many practical applications due to its inability to work at pulse rates greater than about three per sec (i.e., frequency of about 3Hz) but the principle is used very frequently particularly in equipment such as electronic car rev-counters.

Next month we shall deal with the principles of the transistor and armed with that information we shall be able to move on to make some simple circuits. □

Now try the Test on page 333.

TEACH-IN PART 5—ERRATA

We apologise for a technical error with regards to the capacitor colour coding system given in last month's *Teach-In*.

There are numerous capacitor colour coding systems in use and the one given last month refers to the very popular Mullard C280 series and should be amended as follows: the first three bands are correctly labelled, i.e., 1st and 2nd digits and the multiplier. The fourth band gives the tolerance and is either black or white indicating ± 20 and ± 10 per cent respectively.

The fifth band indicates the working voltage, red 250V, yellow 400V.

Next Month's: Transistors



THOSE who contemplate carrying out much experimental and constructional work with transistorised electronics will find that the use of batteries as a power supply can prove rather expensive.

A simple variable voltage power supply of the kind illustrated in this article will more than pay for itself in quite a short time and unlike batteries it doesn't run down. It will supply any voltage up to 16V at a nominal maximum current of 100mA and is fully protected against overload even to the extent of a direct short circuit across the output.

At very low current drain i.e. in the region of 10 to 20mA, the maximum voltage is about 17V which is suitable for many *npn* silicon transistor audio pre-amplifiers for example, requiring between 16 and 18V for operation.

POSITIVE OR NEGATIVE EARTH

Either the positive or negative rails can be "earthed" according to the requirements of the circuit being supplied. It is only necessary to move switch S2 to the appropriate position.

The meter always indicates the voltage at the output terminals i.e. the operating voltage being used. The a.c. ripple at any operating voltage and up to maximum nominal current drain is less than 0.5mV.

At any steady continuous current drain the voltage variation at any setting is negligible.

CIRCUIT DESCRIPTION

The complete circuit diagram is shown in Fig. 1 and is a fairly simple arrangement employing a small power transistor, TR1, to control the output voltage.

The transformer T1 steps down the mains voltage to 14V a.c. (r.m.s.) and applies this to points X and Y on the "diode bridge" network. This arrangement of the diodes gives full-wave rectification across points A and B.

The reservoir capacitor C1 connected across the bridge "smoothes" the pulsating d.c. from the bridge producing a mean d.c. level of about 20V with a small amount of "ripple" voltage. This is applied to the series combination of R1 and the Zener diode, D5. Capacitor C2 across

D.C. POWER SUPPLY



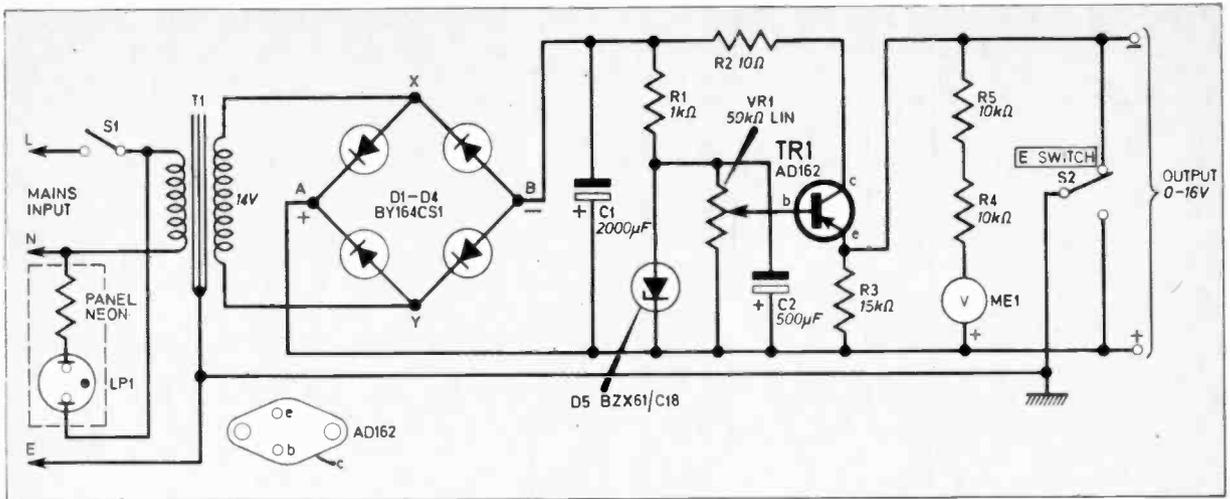


Fig. 1. The complete circuit diagram of the D.C. Power Supply Unit.

D5 helps to eliminate ripple voltage that may be present.

The Zener diode has the property of being able to supply a constant voltage over a wide range of current flow through it.

A small amount of voltage is dropped across R1 (Zener current limiting resistor) while D5 supplies a constant voltage of 18V to the potentiometer VR1 which controls the voltage applied to the base of TR1.

The inclusion of TR1 in the circuit affords stabilisation since without it, loads drawing large current would cause the voltage across the Zener to vary.

The voltage output from TR1 is a function of the potential drop across the transistor and also a function of the base-emitter voltage and affords stabilisation as follows.

UNIT



A simple stabilised supply providing 0 - 16 volts d.c. continuously variable output.

by F. C. Judd

Components

Resistors

- R1 1k Ω \pm 1% $\frac{1}{4}$ W hi-stab.
- R2 10 Ω 10W wirewound
- R3 15k Ω \pm 10% $\frac{1}{4}$ W carbon
- R4 10k Ω \pm 1% $\frac{1}{4}$ W hi-stab.
- R5 10k Ω \pm 1% $\frac{1}{4}$ W hi-stab.

SEE
**SHOP
TALK**

Capacitors

- C1 2000 μ F 25V elect.
- C2 500 μ F 25V elect.

Diodes

- D1-D4 BY164CS1 Bridge type rectifier (1 off) or if desired 1N4002 (4 off)
- D5 BZX61/C18 18V 1W Zener or any 18V 400mW Zener

Transistors

- TR1 AD162 germanium pnp

Potentiometers

- VR1 50k Ω linear carbon

Miscellaneous

- T1 240V primary 12 to 14V 200mA secondary transformer.
- ME1 0-1mA 75 Ω internal resistance meter
- S1 Mains switch slide type, D.P.S.T.
- S2 Slide type switch, D.P.D.T.
- LP1 Mains panel neon with built in resistor 2 insulated terminals (1 red, 1 black); 0.15in matrix perforated s.r.b.p. size 3 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in.; 16 s.w.g. aluminium 3 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in. for heatsink; control knob to suit VR1; aluminium angle $\frac{1}{2}$ x $\frac{1}{2}$ in.; various B.A. nuts and bolts for fixing of panel components; aluminium for building housing case or Universal chassis parts—CU168 (7 x 5in.) 2 off, CU147 (7 x 3in.) 2 off, CU145 (5 x 3in.) 2 off.

The base-emitter voltage is the difference between the output voltage and the voltage supplied to the base of TR1 via VR1 from the Zener diode (which is constant for any setting of VR1).

If the output voltage decreases (due to heavy load for example) so the base-emitter voltage increases, causing the output voltage to increase and in doing so causes the base-emitter voltage to decrease thereby decreasing the output voltage. Thus the circuit is self-compensating and the output voltage remains substantially constant for a wide range of output loads.

The supply rails can only be earthed by the switch S2 which connects either the positive or negative rail to common earth.

No part of the circuit, except the frame and core of the mains transformer, is directly connected to the panel and case, which is earthed.

CONSTRUCTION

The prototype was constructed in a box made from Universal chassis parts with everything mounted on the front panel, but any size case

will do. The layout is not critical and may be modified to suit individual requirements. However it is essential that a heatsink be used to mount TR1 otherwise damage will occur to TR1.

Most of the components are mounted on a piece of 0.15in matrix perforated s.r.b.p. size 4 x 2 $\frac{1}{4}$ in. The layout of these components on the board is shown in Fig. 2.

Begin by wiring up the board as indicated, attaching all the flying leads and remembering to use a heat shunt when soldering the Zener diode, D5, in position.

The next thing to do is to make the mounting bracket for the component board and the heat-sink, and cut and drill the front panel to the sizes given in Figs. 3 and 4.

When this is done, attach the remaining components including the transformer T1, to the front panel in the positions indicated.

It is best next to attach TR1 to its heatsink making sure that TR1 is completely insulated from the heatsink by using the appropriate size mica washer and insulating bushes. Connection to the collector (which is the body of the transistor) is made via a solder tag under one of the securing bolts.

Now connect the transistor to the component board via the flying leads and then attach it to the front panel in the positions indicated.

Connect all the flying leads from the component board and the transformer to the panel mounted components and wire an R3, R4 and R5 as shown in Fig. 5. Connect a suitable length of mains lead to S1 as shown.

THE METER

The resistors R4 and R5 are hi-stability types, and in series with the 1mA full scale deflection meter convert it to a 20V voltmeter.

Although the prototype was built with this kind of meter arrangement, it may be better to use one of the readily available 20V voltmeters which costs the same as the 1mA meter and need no calibration. The 20V meter would



D.C. POWER SUPPLY UNIT


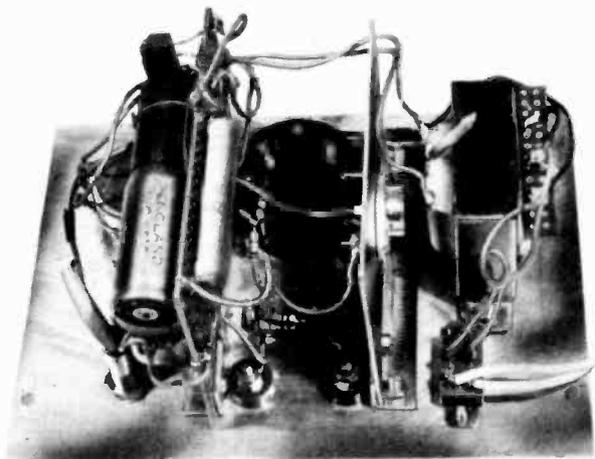


Fig. 5. Shows the positioning of all the components in the aluminium case and the flying lead connections to the component board. Ensure that TR1 is fully insulated from the heatsink by using a mica washer and plastic bushes.

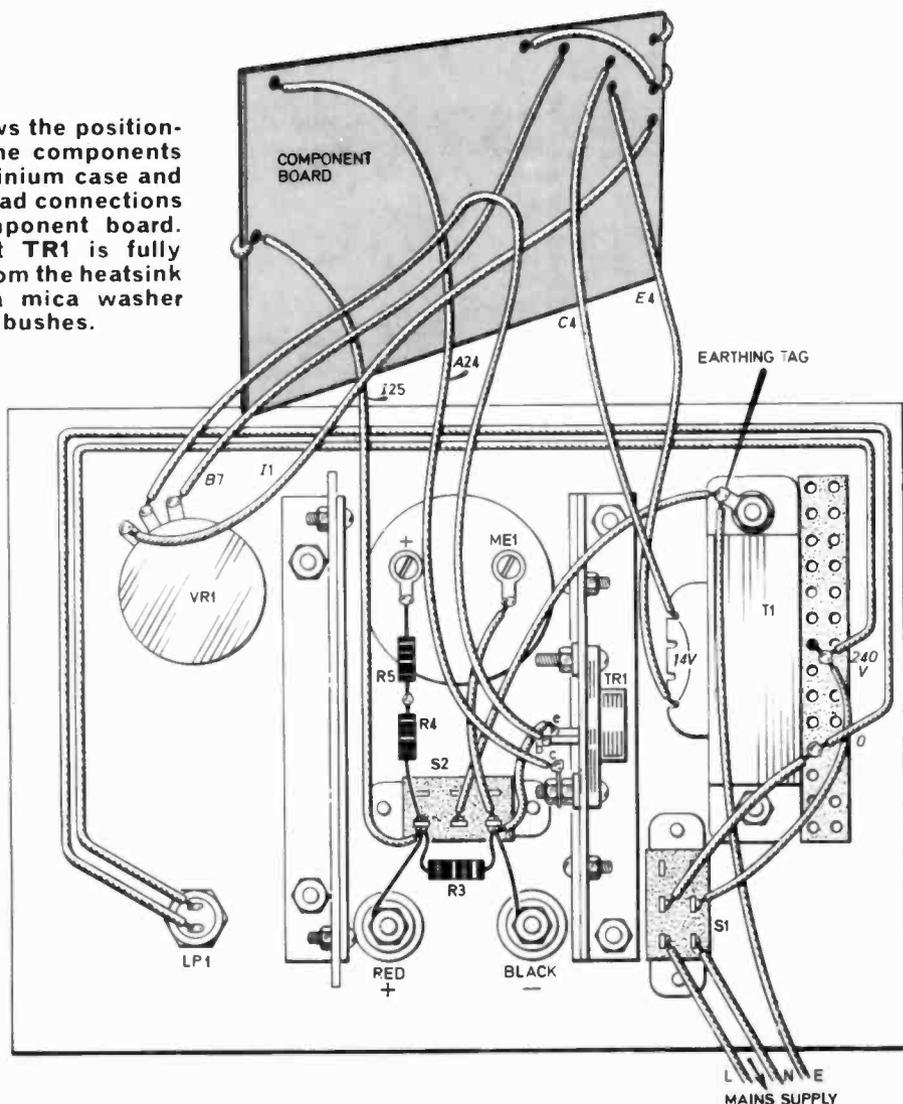

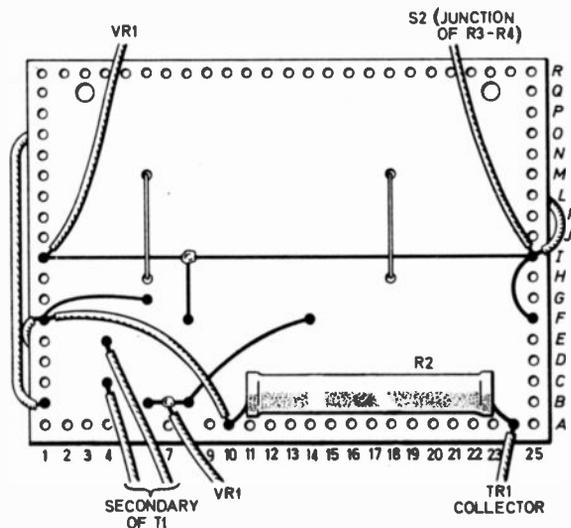
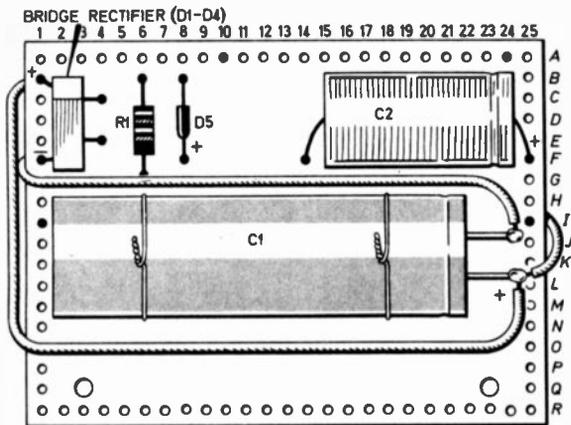


Fig. 2. The layout of the components on both sides of the board.

replace the 1mA meter and the series resistors R4 and R5.

If however, a 1mA f.s.d. meter is used as the voltmeter, it will be necessary to remove the meter scale and recalibrate it to read 0 to 20 volts.

This is done as follows: take off the meter cover and remove the meter scale by undoing the two retaining screws; gently slide the scale away from the meter. The original figures can be erased and new figures 0-20 inscribed.

USING THE UNIT

It is a simple matter setting up the power supply unit for a specific job and should be carried out as follows: attach the battery leads from the test project to the negative and positive insulated terminals on the unit panel, decide which lead is the earth lead and switch S2 (marked E on front panel) to the correct position.

Turn VR1 fully anticlockwise (zero volts) and then plug in to the mains and turn on switch S1. Rotate VR1 to give desired voltage level—this is indicated on the meter.

The completed power supply unit is protected against temporary short circuits by the inclusion of the high wattage resistor R2 which will dissipate any power due to overload. However do not leave the unit running with a short circuited output, but switch it off until the overload is removed.

A direct short circuit will instantly reduce the output volts to zero and this will be shown on the meter. The unit will comfortably supply up to 100mA continuous at any voltage below 16V and between 150 and 200mA intermittent at 16V.

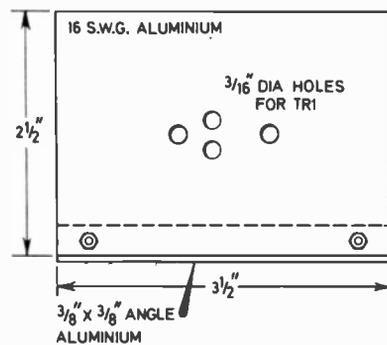
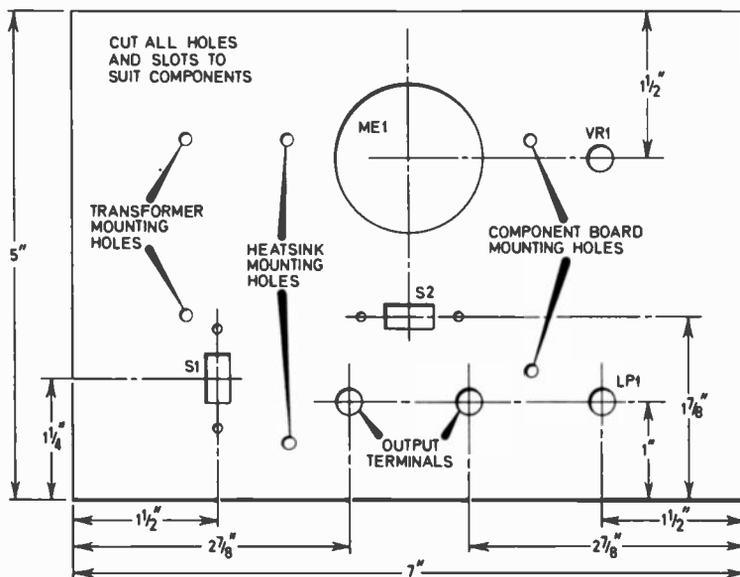


Fig. 3. (above) The dimensions of the heatsink for TR1.

Fig. 4. (left) The dimensions of the front panel showing positions of holes and cut-outs for mounting the components.

Order Now!

FREE

Presented free
with the
May 1972 issue of
Everyday Electronics



**CONSTRUCTORS
COMPANION**

inside every copy of the MAY issue of Everyday Electronics

This is a booklet you will not want to be without. It provides a useful reference on many aspects of electronics. A list of transistors with types, base connections and brief data is provided together with information on transistor circuit configurations. Resistor and capacitor types and colour codes; data on other circuit components. Features on various constructional methods and the art of soldering will interest all new constructors.

Metal Locator

Designed for construction simplicity and ease of operation this single transistor metal locator provides a meter indication when buried metal is located. Just right for beachcombing or searching your back garden.


Electronic Sound and Music

Our feature article next month describes how to make your own electronic music using an ordinary tape recorder and an audio tone generator that will also be described in this same issue.

There is bound to be a heavy demand for this special May issue. Make certain of your copy by placing an order with your usual supplier.


ON SALE FRIDAY APRIL 21.

Bee Counter

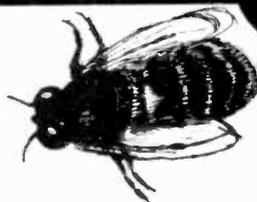

May is the time when the bee-keeper has new colonies. This electronic Bee Counter is just the thing for recording the growth of a colony.

Baby Alarm

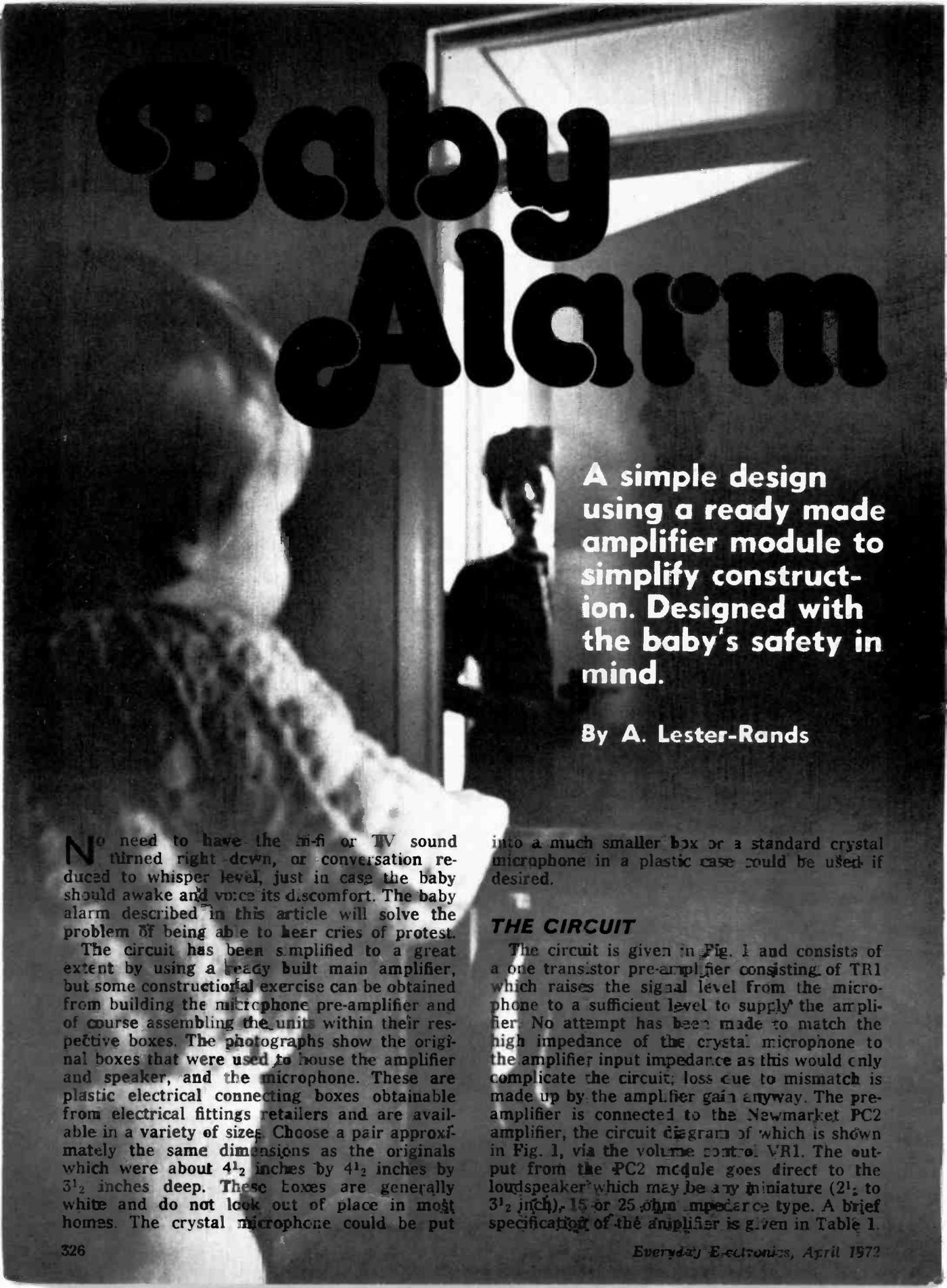

A simple design using a ready made amplifier module to simplify construction. Designed with the baby's safety in mind.

By A. Lester-Rands

No need to have the hi-fi or TV sound turned right down, or conversation reduced to whisper level, just in case the baby should awake and voice its discomfort. The baby alarm described in this article will solve the problem of being able to hear cries of protest.

The circuit has been simplified to a great extent by using a ready built main amplifier, but some constructional exercise can be obtained from building the microphone pre-amplifier and of course assembling the units within their respective boxes. The photographs show the original boxes that were used to house the amplifier and speaker, and the microphone. These are plastic electrical connecting boxes obtainable from electrical fittings retailers and are available in a variety of sizes. Choose a pair approximately the same dimensions as the originals which were about 4½ inches by 4½ inches by 3½ inches deep. These boxes are generally white and do not look out of place in most homes. The crystal microphone could be put

into a much smaller box or a standard crystal microphone in a plastic case could be used if desired.

THE CIRCUIT

The circuit is given in Fig. 1 and consists of a one transistor pre-amplifier consisting of TR1 which raises the signal level from the microphone to a sufficient level to supply the amplifier. No attempt has been made to match the high impedance of the crystal microphone to the amplifier input impedance as this would only complicate the circuit; loss due to mismatch is made up by the amplifier gain anyway. The pre-amplifier is connected to the Newmarket PC2 amplifier, the circuit diagram of which is shown in Fig. 1, via the volume control VR1. The output from the PC2 module goes direct to the loudspeaker which may be any miniature (2½ to 3½ inch), 15 or 25 ohm impedance type. A brief specification of the amplifier is given in Table 1.



Approximate
cost of
components...
£4.00 plus case

CONSTRUCTION

The pre-amplifier is constructed on a small piece of plain circuit board as shown in Fig. 2 and this and the PC2 amplifier are bolted on one side of the amplifier case. The capacitors used in the prototype are printed circuit types with both wires at one end. This simplifies construction and provides a neater finished job, however, this type of capacitor does not have to be used. If the capacitors available are larger than those specified this will not matter as there is plenty of room for larger types on the component board. The finished board is a similar size to the PC2 amplifier and the two units are mounted together on one side of the case.


Table 1: NEWMARKET PC2 AMPLIFIER CHARACTERISTICS

Operating voltage	9V
Output	up to 400mW into 15Ω load
Input resistance	1kΩ
Input sensitivity	1mV for 50mW output
Quiescent (no signal) current	10mA

With a box the same size as the original, or larger, there should be ample space for a PP9 battery as well as the loudspeaker. The layout of the components on the front panel of the amplifier box is shown in Fig. 3 and the photographs but again this may be varied to suit the size of the box used. Note that two wander plug type sockets (SK1) for the microphone lead are mounted on the side of the case. A miniature jack or similar two-pin connection could be used instead but the earthed connection must be from the screening braid of the microphone cable (black socket to screen). The wiring between the various components mounted in the case is shown in Fig. 3.

All that remains is to mount the crystal microphone in its box (Fig. 4) and connect it to the sockets on the side. (A jack or two-pin connection could also be used here instead of wander

Fig. 1. Circuit diagram of the Baby Alarm. The part of the circuit enclosed by the dotted line box is the Newmarket PC2 amplifier module.

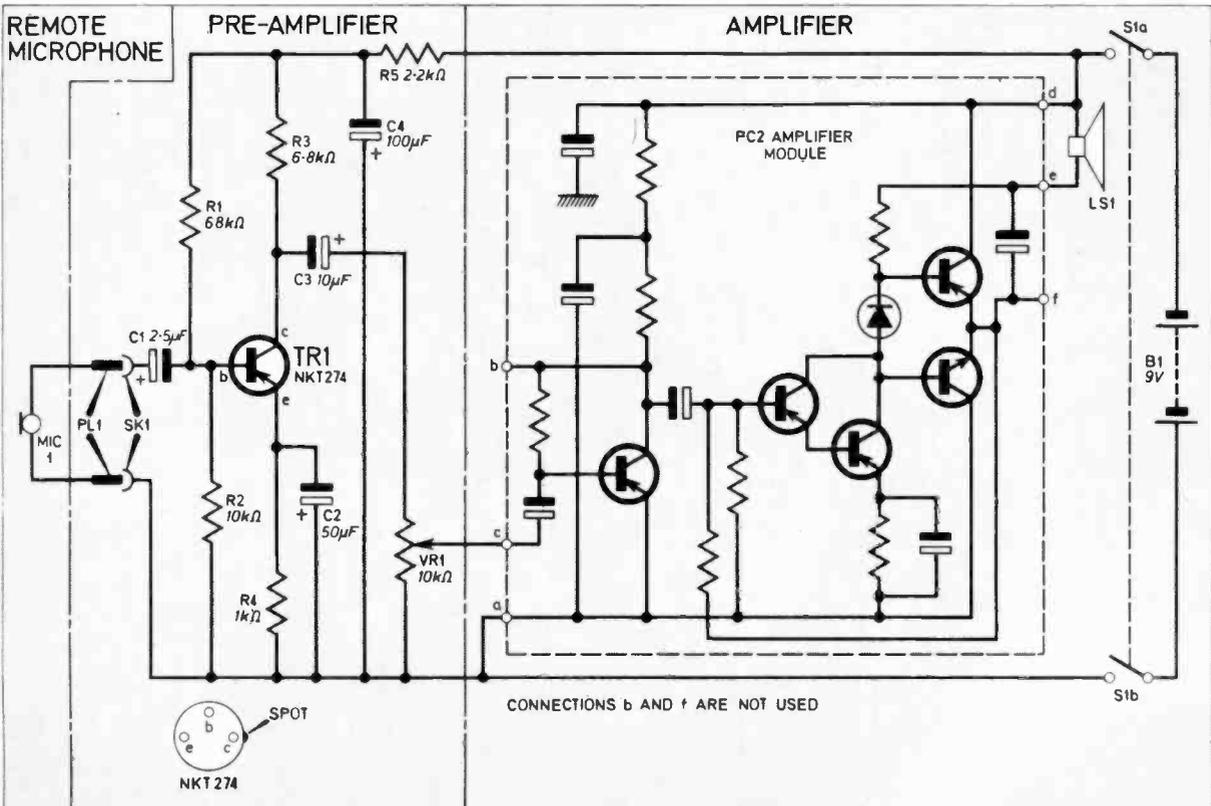

Baby Alarm

Fig. 4. Microphone wiring for box mounting.


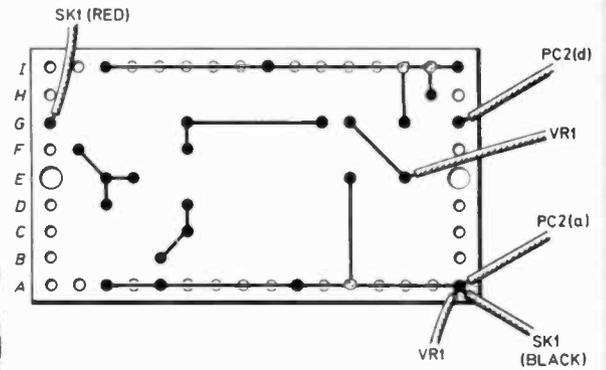
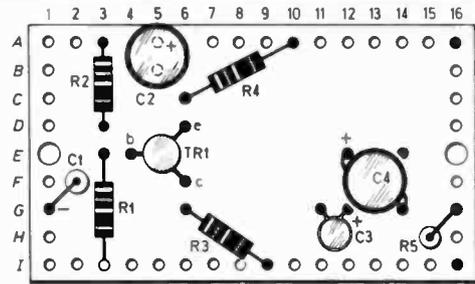
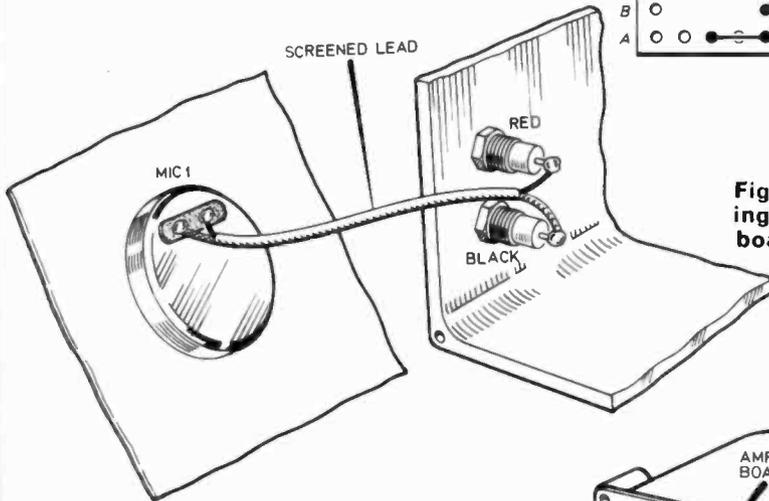


Fig. 2. (Above) Layout and wiring of the component mounting board.

Fig. 3. (Below) Interwiring of the amplifier box of the Baby Alarm.

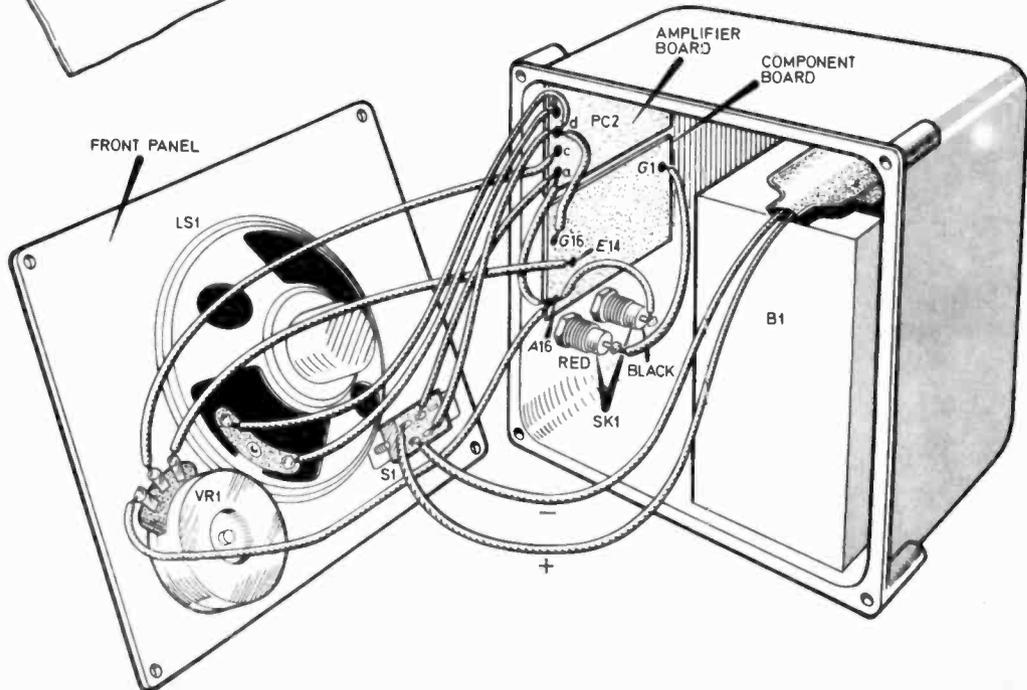

Components....

Resistors

- R1 68k Ω
- R2 10k Ω
- R3 6.8k Ω
- R4 1k Ω
- R5 2.2k Ω
- $\frac{1}{4}$ W \pm 10% carbon

SEE
**SHOP
TALK**

Capacitors

- C1 2.5 μ F elect. 12V
- C2 50 μ F elect. 12V
- C3 10 μ F elect. 12V
- C4 100 μ F elect. 12V

Potentiometer

- VR1 10k Ω log. carbon

Transistor

- TR1 NKT 274 germanium *pnp*

Miscellaneous

- S1 Double-pole single-throw slide or toggle switch
- B1 9V PP9 battery
- PC2 Newmarket amplifier module
- MIC1 Crystal microphone insert (any small type or complete microphone)
- SKI, PLI wander plugs and sockets (2 red, 2 black of each)
- LS1 Miniature 2 $\frac{1}{2}$ in. to 3 $\frac{1}{2}$ in. 15 or 25 Ω loudspeaker


Screened lead (length as required), plain perforated 0.15 inch matrix Veroboard 2 $\frac{1}{2}$ in. \times 1 $\frac{1}{2}$ in. 6 BA fixings, connecting wire, plastic cases (see text), control knob.

plug sockets.) It does not matter which way round the leads to the microphone insert are connected. The screening cable should preferably be screened light-weight microphone cable. The baby alarm units may be permanently mounted if required or, the microphone may simply be placed a few feet away from the cot, the cable led to the living room and the amplifier connected up. The whole can be quickly gathered up and put away when it is not in use.

In operation the unit is quite sensitive and with the microphone even 6 feet away from a crying baby the sound from the loudspeaker at half to full volume setting will be as loud as if the baby were in the same room.

SAFETY

The alarm is inherently safe due to its being battery operated. There is no d.c. present at the microphone end and hence even if the baby removes the leads and puts them in its mouth no harm can come of it, provided the plugs are securely fixed. The box used to house the microphone is also harmless to a baby and quite tough; if a complete microphone is used this should be taken into account when purchasing.

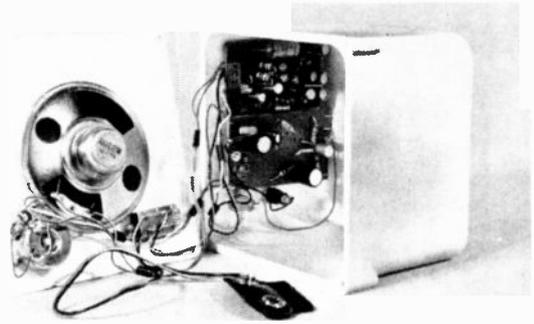


Due to the high impedance of the microphone the length of lead used to connect the two units should be kept as short as possible to avoid unnecessary noise or oscillation. The prototype was tested with a 15 yard length of screened lead and gave satisfactory results, suggesting that a reasonable increase on this length could be used without any major problems. To keep lead length within reason the wire could be fed from an upstairs room to a ground floor room via the windows instead of running it down a staircase. Routing the connecting wire parallel with mains wiring should also be avoided as this will induce hum in the circuit.

CHECKING THE UNIT

The standing current consumed by the amplifier with no signals is approximately 10mA so do not leave the unit running longer than is necessary. To test for operation, short circuit the microphone sockets and turn the volume control full on. A soft hiss should be heard from the loudspeaker. Place the microphone in another room to prevent feedback, which will occur if the microphone is near the speaker, and check by getting someone to speak quietly into the microphone. A good signal should be obtained from the speaker.

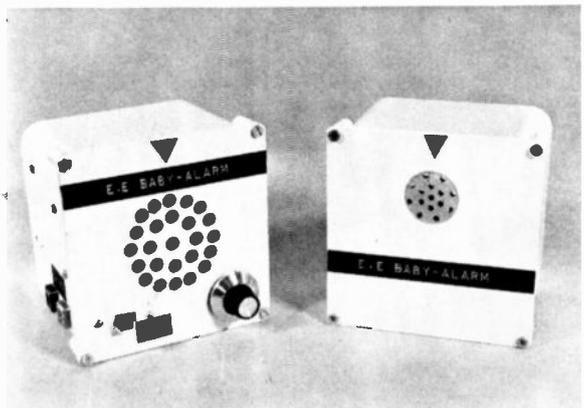The unit is now ready for use and can either be permanently installed or placed in position as necessary. □



Fifty years of British Broadcasting

FIFTY years ago British broadcasting was born in an ex-army hut near Chelmsford in Essex, when on February 14, 1922 a group of Marconi engineers began a series of regular experimental transmissions. Every Tuesday evening from a rigged-up transmitter, call sign 2MT Writtle, or more affectionately to its listeners, Two Emma Tock. They transmitted programmes whose original purpose was entirely technical. Shortly afterwards, in May, another transmitter, later to be even better known, was opened up by the company at Marconi House in the Strand in London. This was the famous 2LO station that provided the foundation from which the British Broadcasting Company grew after its formation on November 14 of the same year.

Two Emma Tock provided the first regular broadcast service in this country, and incidentally broadcasting's first audience, an audience which in its enthusiasm for the pioneering programmes, generated the original demand for public service broadcasting. The 2MT transmitter was set up for use in a series of experiments designed to establish the effective range of a wireless telephony transmitter. At the same time a number of radio amateurs were appearing, largely young ex-

servicemen who had learnt about radio during the 1914-18 war, who had put together their own receiving sets, and who wanted transmissions to receive. Earlier experiments with entertainment had shown that there was a potential for wireless telephony outside official communication and navigation usage, but the official attitude had been discouraging.

2MT opened regular broadcasts officially on behalf of the amateurs who needed a source against which they could calibrate their receivers, and to begin with its programmes were not very much more interesting than early 1920 transmissions made before the government clamp-down, when W. T. Ditcham read from Bradshaw's railway timetable, but the enthusiasm and gaiety of the young Marconi engineers who ran it very soon turned it into a half-hour's entertainment in its own right.

The names of those men read like a roll-call of some of the great names in Broadcasting. In charge of the project was Captain P. P. Eckersley, who later went to the new British Broadcasting Company as its first Chief Engineer. It was his infectious and spontaneous humour which gave 2MT its unique flavour; he had a gift for ad-libbing that constantly alarmed those of a less adventurous disposition who worked with him. Others in the team were Noel Ashbridge, later Sir Noel, who was the BBC's first technical director, R. T. B. Wynn, a later Chief Engineer of the BBC

and B. N. MacLarty, who became Head of the BBC's Design and Installation team.

By contrast, Marconi's 2LO station, granted its licence in May, began a rather staid existence, a happy coincidence for the pioneers of 2MT, as it gave them an opportunity to provide skits and lampoons which were much appreciated by their listeners. 2LO operated on conditions of restricted timing, at first even no music, and low power, beginning with 100 watts, later raised to 1½kW.

By this time many wireless societies had been formed and more and more the demand for radio receivers was being felt. In the United States since 1919 "wireless" had become fashionable, but with no constitutional control of the use of wavelengths, chaos reigned in a commercially sponsored free-for-all. The British Government, seeking a way from the dilemma posed by popular demand on the one hand and a justifiable reluctance to allow free access to the air on the other, set up the Wireless Sub-Committee of the Imperial Communications Committee in April of 1922. After consideration, their recommendation to set up a single broadcasting company was accepted and in November 1922 the British Broadcasting Company was formed from six commercially interested companies with £100,000 share capital.

2MT Writtle continued to transmit until the following January, when it finally closed down.

In-Store Watch-dog

ST MICHAEL now has an electronic watch-dog to help with quality control.

Marks & Spencer's St Michael brandname has long been a by-word for dependability and has recently been developing in the foods market. As part of their quality control effort in this sensitive area, Marks are using a GEC-Elliott instrument in their shops, to check that chilled and frozen goods are maintained at the optimum temperatures for freshness and quality.

The equipment consists of a portable temperature measuring and recording system. It enables

spot checks to be made at a moment's notice, or can operate continuously after the store has closed to record changes throughout the day, overnight or during the weekend. Although the company has supplied similar static

equipment for cold stores, warehouses and refrigerated ships, this is the first portable system for the retail trade. The system is trolley mounted, so that it can be moved from counter to counter, or store to store.



So many of the components you want for EE designs are in the Electrovalue catalogue. Good service, delivery and discounts

ELECTROVALUE

Electronic Component Specialists

THIS MONTH'S SELECTION OF POPULAR ITEMS FROM THE ELECTROVALUE CATALOGUE

TRANSISTORS

(Sil. = Silicon. Ger. = Germanium)

No.	Type	Purpose	Price
2N697	Sil. NPN	General	18p
2N1304	Ger. NPN	"	28p
2N1305	PNP	"	28p
2N2646	Sil. UJT	Oscillator, SCR driver	47p
2N2924	NPN	Small sig. amp	11p
2N3056	NPN	High power	60p
2N3702	PNP	Low power	13p
2N3704	NPN	Low power	13p
AC128	Ger. PNP	Small sig./driver	20p
AC129	PNP	Low power	20p
AD149	PNP	High power	58p
AC178	NPN	Low power	16p
*AD161	NPN	Med. power	33p
*AD162	PNP	Med. power	36p
BC108	Sil. NPN	Small signal	11p
BC109	NPN	Low noise	12p
BC133	NPN	Small signal	10p
BC189	NPN	Low noise	11p
BF194	NPN	RF amp.	14p
BFT51	NPN	Med. current	20p
OA90	Ger. diode	RF detector	6p
OA91	"	General	5p
ED1	"	Silicon Rectifier 1 amp	10p
W02	"	Silicon bridge 1 amp	40p
*Matched pair AD161/AD162			60p

CAPACITORS

Non-polarised

Electrolytic



Polystyrene

10pF	3p	1mF 40V	6p
22pF	3p	5mF 64V	6p
100pF	3p	10mF 64V	6p
220pF	3p	20mF 64V	6p
470pF	3p	25mF 25V	6p
1000pF	3p	50mF 25V	6p
2200pF	3p	80mF 25V	6p
4700pF	4p	100mF 25V	7p
		220mF 25V	10p
		470mF 25V	12p
		1000mF 25V	20p
		2000mF 25V	30p
		5000mF 25V	62p

Polyester M K T

0.01mF	5p	Many other higher and lower ratings will be found in the catalogue. Close tolerance and high stability types also.
0.02mF	5p	
0.047mF	6p	
0.1mF	6p	
0.22mF	6p	
0.47mF	10p	
1mF	14p	

VOLUME CONTROLS, ETC.

Very wide ranges carried including the following popular types:—

4-7Kohms, 10Kohms, 22 Kohms, 47, 100, 220, 470 Kohms; 1 Megohm, 2-2 Megohms.



Log or linear tracks

MONO 12p each: STEREO (matched tracks) 42p

Any type with double pole mains switch—12p extra

DUAL CONCENTRIC

In any combination of above values 60p, with switch 72p

STEREO BALANCE CONTROLS
Log/Antilog. 10K, 47K, 1M
Dual antilog 10K only.

MAIN LINE AMPLIFIERS

70 watt power amplifier in module form ready to build into any system. With full instructions.

Amplifier module kit	nett £12.60
Power supply kit	nett £6.00
Matching pre-amplifier kit (for magnetic or ceramic pick-up) less panel, knobs and chassis	nett £3.30

Note—All the above prices are for mono.

FOR STEREO for building into your own cabinet. Two amplifier modules and pre-amp kits are required with matched controls plus one power supply kit, nett price £38.40

MISCELLANEOUS ITEMS

INDICATOR LAMPS

NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C 24p. Neon, square red type LS5C/P, 18p; amber type LS5C/A, 18p; clear type LS5C/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type LS5C/R-6V, 30p; 6V 0.04A amber type LS5C/A-6V, 30p; 6V 0.04A clear type LS5C/C-6V, 30p; 6V 0.04A green type LS5C/G-6V, 30p; 12V 0.04A LS5C/R-12V, 34p; 28V 0.04A LS5C/R-28V, 43p.

KNOBBS—NUTS, SCREWS, WASHERS — TERMINALS AND MANY OTHER ESSENTIAL ITEMS — see Catalogue

COLVERN 3 watt Wire-wound Potentiometers: 10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1K, 1.5K, 2.5K, 5K, 10K, 15K, 25K, 50K, 32p each

DIN CONNECTORS

Loudspeaker	2-pole	plug	socket
Audio	3-pole	12p	10p
Audio	4-pole	13p	10p
Audio	4-pole	14p	12p
Audio	5-pole 180 deg	15p	12p
Audio	5-pole 240 deg.	15p	12p
Audio	6-pole	15p	13p

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES, 40p.

HANDBOOK OF TESTED TRANSISTOR CIRCUITS, 40p.
COLOUR CODE WALL CHART, 15p. (Add 3p for P/P if any of above three items are ordered separately.)

OVERSEAS CUSTOMERS WELCOME

COMPONENTS DISCOUNTS

allowed on all items other than those at NETT prices.

10% on orders for £5 or more

15% on orders for £13 or more

POSTAGE & PACKING FREE on orders for £2.00 or more. Please add 10p if under. Overseas orders welcomed. Prices subject to alteration without prior notice. Terms of business — C.W.O. as in catalogue

10p CATALOGUE FREE, IF REQUIRED, WITH ORDERS FOR £1.00 OR MORE

The Electrovalue catalogue (64 pages and cover, 8 1/2 x 5 1/2 ins) is crammed with money saving items, and illustrated technical information. FREE with orders for £1.00 or more. Sent separately it costs you 10p post free. Write your order on a sheet of paper with coupon attached

ELECTROVALUE

28 ST. JUDES ROAD, ENGLEFIELD GREEN
EGHAM, SURREY, TW20 OHB

Hours 9-5.30 : Sat. 1.0 p.m.

Telephone: Egham 5533 & 4757 (STD 0784-3)

Telex: 264475

To ELECTROVALUE, ENGLEFIELD GREEN, EGHAM, SURREY
Please send a Goods to value of £..... as detailed on sheet attached, plus FREE copy of catalogue.
b Copy of catalogue, 10p.
(strike out item which does not apply)

NAME

ADDRESS

Enclosed please find £..... cash/cheque/money order.

EE.6

BODINE TYPE N.C.I. GEARED MOTOR



(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 50 cycle, 0-38 amp (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p. 50 cycle, 0-28 amp. 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p P. & P. or less transformer £2.15 plus 27p P. & P.

1 1/2 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of approx. 125 RPM. Size 4 1/4" x 2 1/2" dia. Price 95p inc. post.



230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gear-box. 1 R.P.M. cw 1 R.P.H. A/cw 10 R.P.H. A/cw 2 R.P.H. cw 15 R.P.H. A/cw 60 R.P.M. cw 3 R.P.H. A/cw 20 R.P.H. cw 6 R.P.H. cw 30 R.P.H. cw

cw = Clockwise. A/cw = Anti-clockwise rotation. Fraction of makers' price. All at 75p incl. P. & P.

G.E.C. 12 WAY 15 AMP. CONNECTORS

NEW in maker's carbon BAKELITE £1.25 per doz. FLEXIBLE £1.50 per doz. Post paid (Minimum 1 doz.)



PROGRAMME TIMERS

(Mfr. by 'Magnetic Devices Ltd.'). 240V A.C. 5 r.p.m. 'Cruzet' motor. Drives 15 cams, each operating a cam c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW PRICE: £5.75. P. & P. 25p.



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1.5V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tones. Price £3.00. P. & P. 22p.

50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 54-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instruction. £1.75 inc. post.

VENNER Electric Time Switch

200/250V Ex. G.P.O. Tested. Manually set. 2 on, 2 off every 24h. Overcurrent switch: 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.

MICRO SWITCH

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 inc. post. (Min. order 20)

"HONEYWELL" LEVER OPERATED MICRO SWITCH

15 amps. 250 volt A.C. c/o contacts. NEW in maker's Carton. Price: £1.00 for £1.90 incl. P. & P.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/140V a.c. 50/60 OUTPUT VARIABLE 0.260V All Types (and Spares) from 1/2 to 50 amp from stock.



SHROUDED TYPE
1 amp, £7.00 2-5 amp, £8.05
5 amp, £11.75
10 amp, £22.50 20 amp, £49.00
15 amp, £25.00 25 amp, £58.00
37.5 amp, £82.00 50 amp, £98.00
All plus £1.00 carr. where not specified.
OPEN TYPE (Panel Mounting) 1/2 amp, £4.75.
1 amp, £7.00 2 1/2 amp, £8.05. Carr. 40p on open type.

Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2-5 kΩ, 2A; 5 kΩ, 140 mA. Diameter 3 1/2" Shaft length 3 1/2" dia. 1/2" in. All at £1.50 each. P. & P. 5p.
50 WATT. 1/5/10/25/50/100/250/500/1/1-1/2-5/5kΩ. All at £1.12 each. P. & P. 11p.
25 WATT. 10/25/50/100/250/500/1/1-1/2-5/3-5/5kΩ. All at 78p each. P. & P. 15p.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard, S.C.R. Unijunction Xenon Tube and instructions £6.30, plus 25p P. & P.
NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-50 f.p.s. Price £10.50. P. & P. 50p.

HY-LYGHY STROBE MK 111
This strobe has been designed and produced for use in large rooms, halls and the photographic field and utilises a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12.00. P. & P. 50p.
SPECIALLY DESIGNED, FULLY VENTILATED METAL CASE, including reflector. £4.00 P. & P. 45p Post paid with kit.

THE 'SUPER' HY-LYGHY KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:

- Heavy duty power supply
 - Variable speed from 1-25 flash per sec.
 - Reactor control circuit producing an intense white light. The brilliant light output of the "SUPER" HY-LYGHY gives fabulous effects with colour filter.
- Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £26 plus 75p P. & P. & P. 50p.
ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Lyght Kit including reflector £7.00 P. & P. 45p.
7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.

RELAYS New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

1	2	3	4	1	2	3	4
45	6-9	2 HD	M 50p	700	15-35	2 c/o HD	73p*
185	12-18	4 c/o	73p	700	16-24	6M	65p*
280	9-12	2 c/o	73p*	1,250	24-36	4 c/o	63p*
600	18-32	4 c/o	78p*	2,500	36-45	6M	63p*
700	16-24	4M 2B	63p*	2,400	30-48	4 c/o	50p*
700	16-24	4 c/o	78p*	9,000	40-70	2 c/o	50p*
700	12-24	2 c/o	63p*	15k	85-110	6M	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contracts; (4) Price (HD) Heavy Duty. All Post Paid. *Including Base.

12 VOLT D.C. RELAY

Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)

'DIAMOND H' 230 VOLT A.C. RELAYS (UNUSED)

Three sets c/o contacts rated at 5 amps. Price: 50p P & P 10p. (100 lots £40.00 incl. P. & P.)

'KEY SWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. BOXED. Price: 40p. P & P 5p. (100 lots £32.00 incl. P. & P.)

230 VOLT A.C. SOLENOID OPERATED L.P. VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1" b.s.p. inlet/outlet. Precision made, British mfg. Price £1.75. P. & P. 20p. Special quotation for quantity.



INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.00 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC.. UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.00 post paid.

MAIL ORDER ONLY. S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

8a, LICHFIELD STREET, WALSAIL, STAFFS. WS1 1UZ

EX COMPUTER PRINTED CIRCUIT PANELS
2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 26 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 80p, P. & P. 6p.

9 OA6, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1. P. & P. 25p.

709C OPERATIONAL AMPLIFIER TOS
8 lead I.C. 1 off 50p. 50 off 85p. 100 off 80p.

250 MIXED RESISTORS 62p
1/2 and 1 watt.

150 MIXED HI STABS 62p
1/2, 1 and 1 watt 5% and better.

QUARTZ HALOGEN BULBS
With long leads. 12V 55W for car spot lights, projectors, etc. 80p each, P. & P. 5p.


GPO EXTENSION TELEPHONES
with dial but without bell. 96p each, P. & P. 30p. £1.75 for 2, P. & P. 80p.

BARGAIN RELAY OFFER
Single pole change over silver contacts 25V to 80V. 2-8k Ω coil. 8 for 80p, P. & P. 8p.

KEYTRONICS mail order only
44 EARLS COURT ROAD
LONDON, W.8 01-478 8499

SERVICE TRADING CO

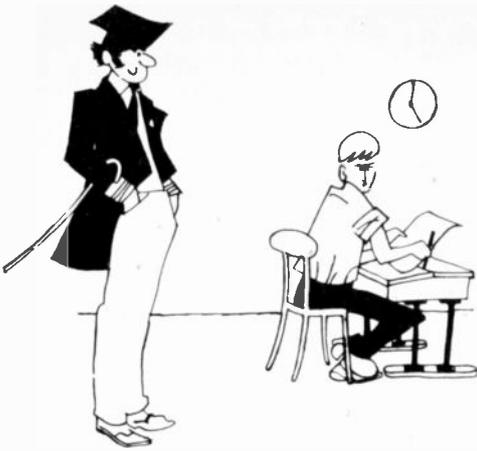All Mail Orders—Also Callers—Ample Parking Space
Dept. E.E. 57 BRIDGMAN ROAD, LONDON, W4 5BB
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.
Personal callers only. Open Sat.
9 LITTLE NEWPORT ST.
LONDON WC2H 7JJ 01-437 0579



TEACH-IN

Half term test

It is always fun to prove to yourself how much you know, hence we have devised this test at the half way point of Teach-In. Do not worry if you are unable to answer all the questions, it simply means that you have not taken in all the information we have given. We will publish full answers next month so do not write to us with your answers or queries.







We have tried to set the sort of questions that will probably come up when you are actually involved in sorting out practical designs. Ultimately you ought to be able to answer them all from memory of the principles involved.


- (1) In an electric circuit do electrons flow from the positive to the negative terminal of the battery or vice versa?
- (2) Which of the following abbreviations are used to describe the magnitude of current:
(a) mV, (b) μ A, (c) pF, (d) μ F, (e) A, (f) nV, (g) k Ω .
- (3) What would you expect the potential difference across a 2.2 kilohm resistor to be if 0.01 amperes were flowing through it.
- (4) We can make a voltmeter by putting a resistor in series with a sensitive ammeter. Does it matter if the resistor is connected between the positive terminal of the meter and the battery's positive terminal or between the respective negative terminals?
- (5) What current do you think would be flowing through R1 in Fig. 1? If you put another resistor in parallel with R2 would the current through R1 increase or decrease?
- (6) What would be the minimum power rating of devices you would use for R1, R2 and R3 shown in Fig. 2?
- (7) What would be the maximum power dissipation of the potentiometer shown in Fig. 3?
- (8) The colour codes on resistors are as follows: what are the ohmic values and tolerances?
(a) Yellow, Violet, Red, Silver.

- (b) Red, Red, Orange, Gold.
- (c) Brown, Black, Yellow, Silver.
- (9) Generally speaking if you wanted a 16 μ F electrolytic capacitor having a working voltage of 25V and the shopkeeper did not have one exactly as specified; which of the following alternatives would you choose as being the most suitable.
(a) 16 μ F 12V, (b) 20 μ F 40V, (c) 20 μ F 15V, (d) 12 μ F 25V.
- (10) You ask the shopkeeper for a 0.15 μ F capacitor and he gives you one with no markings other than three coloured bands—reading from the top down to the black band, Brown, Red, Yellow. Would you (a) accept it as being correct, (b) reject it politely?
- (11) In Fig. 4 which capacitor will charge up fastest when the switch is closed C1, C2 or C3?
- (12) Again in Fig. 4 which capacitor will take the longest time to charge?
- (13) Is D1 in Fig. 5 forward or reverse biased?
- (14) In Fig. 6 S1 is a reversing switch that effectively changes the polarity of the supply voltage from the battery. Assuming it can be set in either position calculate the peak reverse breakdown voltage and forward current the diode D1 must be capable of withstanding.
- (15) If a design called for a diode having a peak inverse voltage of 75V and a forward current of 0.1 amperes; which of the following specified devices could be used with safety?

	Reverse voltage	Forward current
(a)	100V	50 mA
(b)	50V	50 mA
(c)	50V	150 mA
(d)	100V	150 mA

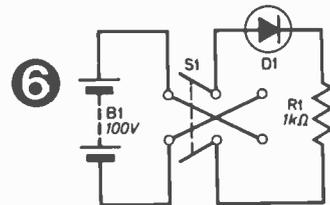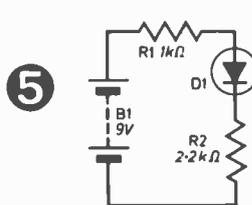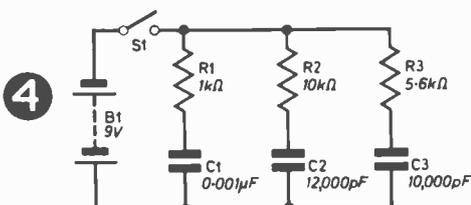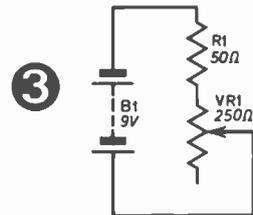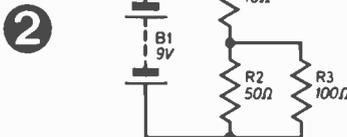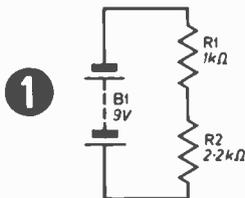- (16) If D1 in Fig. 5 was a silicon device and you measured the voltage across it with a high resistance voltmeter; would you expect the voltmeter to read:
(a) 9V, (b) 0.6V, (c) zero volts?



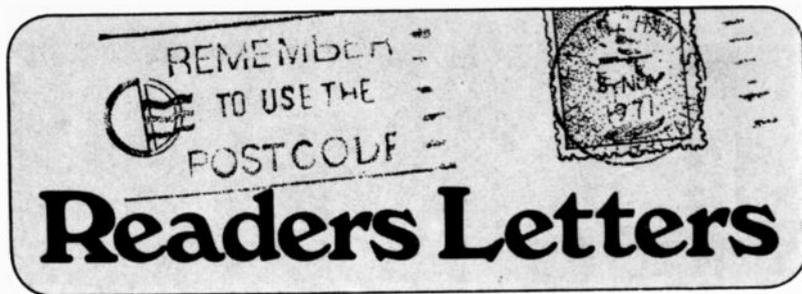

From Abroad

I have now had the first three issues of your publication and find it very interesting. They are on sale here exactly a month after publication, which seems a long time. Also it is difficult to get the required components as we only have one stockist in town. Is it possible to have a parcel of all components for a project sent direct from England?

I have made the *Demo Deck* and tried the experiments on page 151, January *EVERYDAY ELECTRONICS*. According to your diagrams the positive terminal of the meter is connected to the positive terminal of the battery. By doing this I find the needle shooting across the dial of the meter. However, by connecting the positive battery terminal to the resistors then to the meter positive terminal I get the correct readings.

If the current goes from positive to negative then surely the resistors should come before the meter, and if this is the case, then the positive sign on the diagrams should be on the other side of the battery. Please explain.

D. A. Watson
South Africa.

It would seem that you have inadvertently connected your Demo Deck meter across the battery with no resistors in circuit. As the current flows around the whole circuit from positive to negative battery terminals and the resistors merely limit the flow it does not matter where in the circuit they are.

Thanks for a great new magazine, will be making most of your projects shown. Envy your low low prices. OC71 costs £3 here!!!!

J. Koppard
Wellington, N. Zealand.

At those prices it may be cheaper to buy from one of the British suppliers. Unfortunately we are unable to show the beautiful grass-skirted Tahitian girl on the front of the postcard from this reader!

Constructive—Helpful!

As a regular subscriber to "big brother" *Practical Electronics*, permit me to add my quota of appreciation of particular features in the welcome appearance of the new member of the "practicals" family.

First, I note the very commendable provision of space for readers' letters. The growth of such a feature can provide a fraternal, club-like air. Both constructive and controversial writers therein can be respectively helpful or entertaining.

Myself an octogenarian who has followed the present hobby since the first days of the crystal detector and early usage of the now archaic term "wireless", which many qualified speakers and writers still use, I would like here to submit a small specially chosen item appropriate to the purpose of the *Teach-In* feature. It is with reference to the definition of alternating current as frequently seen in text books and other sources of instruction in basic electricity.

The virtually stereotype explanation says, "a current which flows this way and then that." To the uninformed, the nature of such expression at once conveys a relatively slow change without a precise frequency as required for practical use.

Still, with newcomers and beginners in mind, I would like here to repeat my comment, earlier published in *Practical Electronics*, which deplored the continued proliferation of semiconductors listed by retailers.

With every sympathy and understanding of the advertisers' problems in this matter, a list of over one thousand code markings for the identity of the devices being offered will serve only those readers who already know precisely that which they require. They may at the same time be aware of the many equivalents given in a list. It follows therefore that the ordinary active amateur constructor is saved frustration only by the authors of the constructional projects stipulating not only the preferred type of device, but also where possible, other

alternatives, all of which point to the need for progressive enthusiasts to avail themselves of comprehensive data on solid-state products.

In good humour and intention, I now turn to the question of two essentially familiar components—variable resistors and capacitors. The more experienced followers of the electronics cult must have noticed that many suppliers who regardless of its specific use, persist in calling the former article a "volume control", while others continue to call the latter "condensors" or "condensers".

Lastly, for those who may not be aware, there is an excellently produced, colour illustrated, twenty-four page booklet issued by Joseph Lucas Ltd. under the title, "The Story of Semiconductors." Whether one knows it all or not, the lucid manner of presentation is a pleasure to read. To conclude, do I hear electronically simulated laughter at my laboured views?

P. Ashdown
Cheshire.

No laughter from us! We hope our booklet in the next issue will help with transistor data.

Commercial Equipment

I have followed with interest your magazine since the first issue and have found it most helpful and informative. Your *Teach-In* articles are an excellent idea, and in particular I would commend the *Shop Talk* articles. These fulfil the purpose of providing the newcomer with what he needs to know about component buying, something that other magazines seem to think he knows already.


However, there is one "gap" I think you could yet fill. Your projects at present are all on the same theme—construction of simple self-contained electronic devices.

No doubt many readers are interested in these, in particular the devices for cars such as the *Auto Alert* I would consider most useful since it is not easy to obtain proprietary devices at reasonable cost to serve the same purpose. But I would be interested to see some articles about ordinary household apparatus, and simple repairs and modifications to them. For instance: What common faults can one expect to develop in a radio set and how can one deal with them?

How can one suppress electrical apparatus that is causing interference. How to fit a socket to a television set to make tape

Everyday Electronics, April 1972

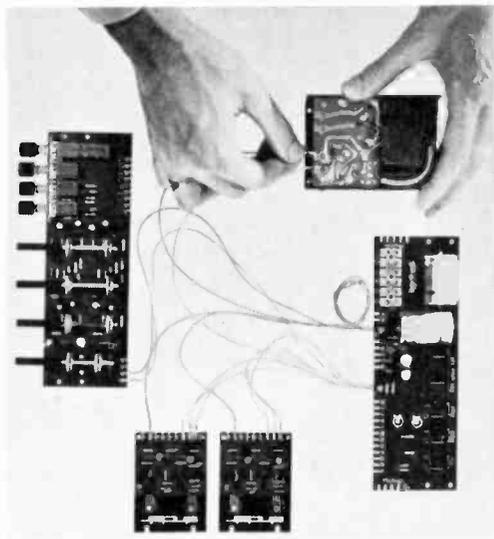Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same — there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative — Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one — Masterlink — which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together — the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

Guarantee

If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

sinclair

Sinclair Radionics Ltd., London Road,
St. Ives, Huntingdonshire PE17 4HJ.
Telephone: St. Ives (04806) 4311

Specifications

Output — 30 watts music power (10 watts per channel R.M.S. into 3 Ω).

Inputs — Mag. P.U. — 3mV correct to R.I.A.A. curve 20—25,000 Hz ± 1dB. Ceramic pick-up — 50mV. Radio — 50 to 150mV. [Aux. adjustable between 3mV, and 3V.

Signal to noise ratio — Better than 70dB.

Distortion — better than 0.2% under all conditions.

Controls — Press buttons for on-off, P.U., radio and aux. Treble +15 to -15 dB at 10 kHz. Bass +15 to -15 dB at 100 Hz. Volume. Stereo Balance.

Channel matching within 1dB.

Front panel — brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

£29.95

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE174HJ

Please send Project 605 post free Details and list of stocklists

Name

Address

for which I enclose £29.95 cheque/money order/cash.

E.E.6B

**BRAND NEW
GUARANTEED**

**LARGEST SELECTION OF SEMICONDUCTORS
COMPONENTS**

**RETURN OF POST
SERVICE**

TRANSISTORS

2G301	2N3404	40310	45p	BC212L	15p	B8X28	25p	NKT281	27p
2G302	2N3405	40311	45p	BCY30	27p	B8X50	25p	NKT401	27p
2G303	2N3414	40314	47p	BCY31	30p	B8X51	25p	NKT402	27p
2G304	2N3416	40316	47p	BCY32	30p	B8X76	25p	NKT403	27p
2G305	2N3417	40317	47p	BCY33	30p	B8X77	27p	NKT404	27p
2G306	2N3417	40317	47p	BCY34	30p	B8X78	27p	NKT405	27p
2G307	2N3570	40324	47p	BCY35	40p	B8Y10	27p	NKT406	27p
2G308	2N3572	40328	47p	BCY39	60p	B8Y11	27p	NKT481	27p
2G309	2N3606	40329	30p	BCY40	50p	B8Y24	15p	NKT482	27p
2G310	2N3606	40329	30p	BCY41	50p	B8Y25	15p	NKT483	27p
2G311	2N3607	40347	57p	BCY43	15p	B8Y26	17p	NKT603F25	27p
2G312	2N3702	41034	48p	BCY44	23p	B8Y27	17p	NKT613F	27p
2G313	2N3703	41036	48p	BCY45	23p	B8Y28	17p	NKT674F	27p
2G314	2N3704	41038	47p	BCY59	23p	B8Y29	17p	NKT677F	27p
2G315	2N3705	40370	23p	BCY60	27p	B8Y32	30p	NKT715	27p
2G316	2N3706	40406	57p	BCY70	20p	B8Y36	25p	NKT781	27p
2G317	2N3707	40407	40p	BCY71	20p	B8Y37	25p	NKT10410	27p
2G318	2N3708	40407	40p	BCY72	17p	B8Y38	22p	NKT10439	27p
2G319	2N3709	40408	48p	BCZ10	27p	B8Y39	23p		
2G320	2N3710	40410	23p	BCZ11	48p	B8Y40	23p	NKT10619	27p
2G321	2N3711	40487A	57p	BD116	41-18	B8Y51	23p		
2G322	2N3712	40488A	57p	BD121	60p	B8Y52	23p	NKT20329	27p
2G323	2N3713	40489	57p	BD122	60p	B8Y53	23p	NKT20330	27p
2G324	2N3714	40490	57p	BD123	60p	B8Y54	23p	NKT20331	27p
2G325	2N3715	40491	57p	BD124	60p	B8Y55	23p	NKT20332	27p
2G326	2N3716	40492	57p	BD125	60p	B8Y56	23p	NKT20333	27p
2G327	2N3717	40493	57p	BD126	60p	B8Y57	23p	NKT20334	27p
2G328	2N3718	40494	57p	BD127	60p	B8Y58	23p	NKT20335	27p
2G329	2N3719	40495	57p	BD128	60p	B8Y59	23p	NKT20336	27p
2G330	2N3720	40496	57p	BD129	60p	B8Y60	23p	NKT20337	27p
2G331	2N3721	40497	57p	BD130	60p	B8Y61	23p	NKT20338	27p
2G332	2N3722	40498	57p	BD131	60p	B8Y62	23p	NKT20339	27p
2G333	2N3723	40499	57p	BD132	60p	B8Y63	23p	NKT20340	27p
2G334	2N3724	40500	57p	BD133	60p	B8Y64	23p	NKT20341	27p
2G335	2N3725	40501	57p	BD134	60p	B8Y65	23p	NKT20342	27p
2G336	2N3726	40502	57p	BD135	60p	B8Y66	23p	NKT20343	27p
2G337	2N3727	40503	57p	BD136	60p	B8Y67	23p	NKT20344	27p
2G338	2N3728	40504	57p	BD137	60p	B8Y68	23p	NKT20345	27p
2G339	2N3729	40505	57p	BD138	60p	B8Y69	23p	NKT20346	27p
2G340	2N3730	40506	57p	BD139	60p	B8Y70	23p	NKT20347	27p
2G341	2N3731	40507	57p	BD140	60p	B8Y71	23p	NKT20348	27p
2G342	2N3732	40508	57p	BD141	60p	B8Y72	23p	NKT20349	27p
2G343	2N3733	40509	57p	BD142	60p	B8Y73	23p	NKT20350	27p
2G344	2N3734	40510	57p	BD143	60p	B8Y74	23p	NKT20351	27p
2G345	2N3735	40511	57p	BD144	60p	B8Y75	23p	NKT20352	27p
2G346	2N3736	40512	57p	BD145	60p	B8Y76	23p	NKT20353	27p
2G347	2N3737	40513	57p	BD146	60p	B8Y77	23p	NKT20354	27p
2G348	2N3738	40514	57p	BD147	60p	B8Y78	23p	NKT20355	27p
2G349	2N3739	40515	57p	BD148	60p	B8Y79	23p	NKT20356	27p
2G350	2N3740	40516	57p	BD149	60p	B8Y80	23p	NKT20357	27p
2G351	2N3741	40517	57p	BD150	60p	B8Y81	23p	NKT20358	27p
2G352	2N3742	40518	57p	BD151	60p	B8Y82	23p	NKT20359	27p
2G353	2N3743	40519	57p	BD152	60p	B8Y83	23p	NKT20360	27p
2G354	2N3744	40520	57p	BD153	60p	B8Y84	23p	NKT20361	27p
2G355	2N3745	40521	57p	BD154	60p	B8Y85	23p	NKT20362	27p
2G356	2N3746	40522	57p	BD155	60p	B8Y86	23p	NKT20363	27p
2G357	2N3747	40523	57p	BD156	60p	B8Y87	23p	NKT20364	27p
2G358	2N3748	40524	57p	BD157	60p	B8Y88	23p	NKT20365	27p
2G359	2N3749	40525	57p	BD158	60p	B8Y89	23p	NKT20366	27p
2G360	2N3750	40526	57p	BD159	60p	B8Y90	23p	NKT20367	27p
2G361	2N3751	40527	57p	BD160	60p	B8Y91	23p	NKT20368	27p
2G362	2N3752	40528	57p	BD161	60p	B8Y92	23p	NKT20369	27p
2G363	2N3753	40529	57p	BD162	60p	B8Y93	23p	NKT20370	27p
2G364	2N3754	40530	57p	BD163	60p	B8Y94	23p	NKT20371	27p
2G365	2N3755	40531	57p	BD164	60p	B8Y95	23p	NKT20372	27p
2G366	2N3756	40532	57p	BD165	60p	B8Y96	23p	NKT20373	27p
2G367	2N3757	40533	57p	BD166	60p	B8Y97	23p	NKT20374	27p
2G368	2N3758	40534	57p	BD167	60p	B8Y98	23p	NKT20375	27p
2G369	2N3759	40535	57p	BD168	60p	B8Y99	23p	NKT20376	27p
2G370	2N3760	40536	57p	BD169	60p	B8Y00	23p	NKT20377	27p

Post & Packing 13p per order. Europe 25p. Commonwealth (Air) 65p (MIN.)
Matching charge (audio transistors only) 15p extra per pair.
Prices subject to alteration without prior notice.

TTL LOGIC I.C. NEW PRICES

1-11 18-84		1-11 18-84		1-11 18-84	
SN7400	8p	SN7433	8p	SN7472	8p
SN7401	0.90 0.18	SN7437	0.64 0.06	SN7473	0.43 0.41
SN7402	0.90 0.18	SN7438	0.64 0.06	SN7474	0.43 0.41
SN7403	0.90 0.18	SN7440	0.64 0.06	SN7475	0.45 0.44
SN7404	0.90 0.18	SN7441A	0.67 0.03	SN7476	0.45 0.44
SN7406	0.90 0.18	SN7442	0.65 0.01	SN7478	0.70 0.68
SN7407	0.90 0.18	SN7443	0.65 0.70	SN7481	1.40 1.38
SN7408	0.90 0.18	SN7444	0.90 0.18	SN7482	0.87 0.85
SN7409	0.90 0.18	SN7445	0.50 0.40	SN7483	0.87 0.85
SN7410	0.90 0.18	SN7446	1.00 0.95	SN7484	3.00 1.85
SN7411	0.90 0.18	SN7447	1.00 0.95	SN7485	3.00 1.85
SN7412	0.45 0.40	SN7448	1.00 0.95	SN7486	0.33 0.30
SN7413	0.45 0.38	SN7449	1.00 0.95	SN7490	0.37 0.34
SN7420	0.90 0.18	SN7450	0.90 0.18	SN7491A	1.31 1.10
SN7423	0.51 0.47	SN7451	0.90 0.18	SN7492	0.87 0.84
SN7427	0.45 0.45	SN7453	0.90 0.18	SN7493	0.87 0.84
SN7428	0.90 0.18	SN7454	0.90 0.18	SN7494	0.87 0.84
SN7430	0.90 0.18	SN7460	0.90 0.18	SN7495	0.87 0.84
SN7432	0.45 0.45	SN7470	0.40 0.38	SN7496	0.87 0.84

MULLARD SUB-MIN ELECTROLYTIC

C485 range axial lead 8p each
Values: (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/8; 4/10; 4/6; 5/6; 6/4; 8/4; 8/4; 10/4; 10/4; 10/4; 12.5/20; 16/40; 20/16; 20/16; 25/16; 25/16; 25/16; 32/40; 32/40; 40/16; 50/8; 40/25; 50/40; 50/40; 80/25; 80/16; 80/25; 100/8; 125/10; 125/16; 200/4; 200/10; 320/4.

SILICON RECTIFIERS

PIV	50	100	200	400	600	800	1000	1200
1A	8p	8p	10p	11p	13p	15p	18p	21p
2A	15p	—	—	23p	—	—	—	—
6A	—	—	25p	30p	33p	35p	—	—
10A	—	—	33p	40p	45p	47p	51p	51-55
16A	—	—	37p	45p	51p	57p	61-65	61-67
32A	—	—	51p	61p	65p	71p	75-80	—

1 amp and 8 amp are plastic encapsulation.

DIODES & RECTIFIERS

IN34A	10p	A4119	7p	BAX16	12p	FRTS/4	22p
IN914	7p	AA129	15p	BAY18	17p	OA5	17p
IN916	7p	AA129	15p	BAY31	17p	OA10	30p
IN6007	20p	AA218	13p	BAV35	25p	OA9	10p
1844	7p	AA127	10p	BT100	15p	OA7	8p
18113	15p	BA100	15p	BT103	25p	OA70	7p
18120	15p	BA102	25p	BY122	47p	OA73	10p
18121	14p	BA110	25p	BY124	15p	OA79	7p
18130	8p	BA114	15p	BY126	15p	OA81	8p
18131	10p	BA115	7p	BY127	17p	OA88	15p
18132	15p	BA141	17p	BY184	87p	OA90	7p
18920	7p	BA142	17p	BY110	22p	OA91	7p
18923	8p	BA144	15p	BZ100	25p	OA95	7p
18923	15p	BA145	17p	BZ111	25p	OA90	7p
18940	8p	BA154	15p	BZ121	30p	OA202	10p
		BAX13	8p	BZ131	25p	TIV307	60p

**"SCORPIO" CAP
DISCHARGE IGNITION
SYSTEM**
(As printed in P.E. Nov.
71). Complete kit £10.00
P. & P. 50p.

BRIDGE RECTIFIERS

A. PIV	1	100	87p	4	50	80p
1	1.140	87p	4	100	70p	
2	50	23p	6	400	80p	
2	200	41p	6	200	80p	
2	400	46p	6	400	81-10	

THYRISTORS (SCR)

PIV	50	100	200	300	400
1A	25p	27p	27p	40p	47p
4A	47p	55p	77p	—	77p
7A	—	87p	100p	—	—

TIC47 0.6 amp. 300 PIV 50p.
Also 12 amp. 100 PIV 75p.
2N3028 at £1.15p

MULLARD C280 M/FOIL CAPACITORS

0.01, 0.022, 0.033, 0.047	3p each
0.06, 0.1	4p each
0.15, 0.22, 0.33	4p each
0.47	—

recordings from the sound channel? How does one acquire circuit diagrams and service sheets for radio sets etc?

Another point in the diagrams accompanying the projects, the dimensions in inches, quarters and eighths strike me as a bit archaic, in view of the fact that most of the electronics industry works in metric units. If you must use inches, could you not use decimal fractions, e.g. 2.7in.

Finally, I would like to record my appreciation of the excellent drawings, photographs and general layout of the magazine.

Wishing your magazine every success,

M. D. McMahon
Middlesbrough.

The subject of servicing, repair and alteration of commercial equipment is a vast one and often individual items must be described separately. Thus we cannot and will not be able to cover such subjects.

Taking your point about metric measurement, we feel that most readers would prefer to use the conventional system, but we are always pleased to receive comment—so what do other readers feel?

When I saw the title of your magazine on the bookstall I—foolishly as it turned out—assumed that it would contain some reference to “electronic-flash” a piece of apparatus used by thousands of photographers both amateur and professional.

But nowhere in your pages—either editorial or advertisement—is there the slightest hint that such things as flash-guns exist. Of course your magazine is not the only offender. I wonder whether there is some conspiracy to keep circuit diagrams and maintenance of electronic flash systems out of reach of the public so that “repairers” can go on fleecing us.

As you undoubtedly know there is a tremendous sale on these relatively simple pieces of equipment. Consequently there must be many people like myself who use them and would welcome some details of construction and maintenance and the names of suppliers who could provide the necessary components.

I do not know whether my letter is useful as a contribution to your letters from readers page.

H. A. Williams
Swansea.

Designs for flash guns are within our scope but supply of the flash tubes is not so easy at present. We are not able to cover the design and maintenance of commercial flash guns.

Everyday Electronics, April 1972

Capacitors

I have just completed my first circuit—your *Snap Sequence Indicator*—and, guess what? It worked! Thanks mainly to your helpful *Teach-In* series.

As a complete beginner I have managed to understand what has been said so far, but then came Capacitors and there my enthusiasm cooled down a bit.

I am not mathematically-minded and think it would be helpful if you printed a few sums in full to show how to arrive at for example, $0.01\mu\text{F}$, as I am not sure how to change pF's into μF 's etc. Also I have not seen nF on a capacitor but in my catalogue a lot of capacitors are shown in mF. Please advise me what this stands for as I can find no mention of same in your *Teach-In* series.

Please could you advise me whether metallised polyester capacitors are suitable for all applications where electrolytic capacitors are not specified.

I hope you may be able to consider this letter for your letter page as I am sure there are a lot of home-constructors who, like me, find looking for the right capacitor in a catalogue extremely difficult owing to the wide range of types, voltages, etc. available.

B. Way
Isle of Wight.

Capacitors are usually designated in μF , nF and pF, these are millionths of Farads (+1,000,000) thousandths of millionths of Farads (+1,000,000,000) and billionths of Farads (+1,000,000,000,000). Thus to change from pF to μF divide by 1,000,000; hence $10,000\text{pF} = 0.01\mu\text{F}$. To change from μF to pF multiply by 1,000,000; hence $0.15\mu\text{F} = 150,000\text{pF}$. The use of nF is rather restricted and will probably be seldom encountered. If a manufacturer or supplier quotes mF he means μF .

Metallised polyester types are suitable for all our projects unless specific types are given and providing the specified value is available.

Q. and A.

As a follow up to D. Hill's letter in the February issue of EVERYDAY ELECTRONICS, I wish to endorse his suggestion of a Question and Answers section. *Readers' Letters and Shop Talk* are most helpful, but with a Question and Answer section short and to the point, more information could be conveyed, e.g. your abbreviations section is a perfect example as, to a beginner such as myself, a quotation such as s.r.b.p. is double dutch.

Belated congratulations on your magazine, which through the *Teach-In* series gives a welcome lead-in to electronics.

W. McLintock
Londonderry, N. Ireland.

It seems that a number of readers would like such a page and we will be looking into the possibility of including this item in future.

No Waa!

I am writing to you to see if you could possibly help me. In this month's edition of EVERYDAY ELECTRONICS, you featured a circuit for a *Waa-Waa Pedal*, which I have built, but unfortunately I cannot get it to function properly. Every time I press the pedal down, all that happens is that I get a very slight increase in volume, and when I bring the pedal back, I get a slight decrease in volume.

I have checked the circuit that many times now that I am beginning to give up hope.

R. Templeton
Melton Mowbray.

If you have checked out the circuit, paying special attention to transistor lead connections and capacitor polarities, and everything is correct, then we suggest that you experiment with the value of capacitor C2 (part of the filter network) as its value is critical.

If, for example, its value is too low due to a high tolerance figure, then the peak of the filter characteristic curve, Fig. 1 will be at too high a frequency—beyond or at the top end of the guitar upper scale.

Try increasing the value of C2 in small steps. This can be done by placing a capacitor across the one already in circuit. Capacitors in parallel are additive.

Astron

May I as a complete stranger to the world of electronics, congratulate you on your magazine EVERYDAY ELECTRONICS. I have followed with interest your magazine from its conception, especially your *Teach-In*. I dared not experiment with anything you published in case I made a hash of it. But after following your instructions on how to build the Astron radio I was honestly surprised with the results I achieved.

James McFadden
Belfast.

YATES ELECTRONICS (FLITWICK) LTD.

RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4VW
Erie wire wound. 1/2W 2% Electrofil TR.5.

Power	Tolerance	Range	Values available	Price
1/2	5%	4-7Ω-2-2MΩ	E24	1-99 100+
1/2	10%	3-3MΩ-10MΩ	E12	1-0p 0-8p
1/2	2%	10Ω-1M	E12	3-5p 3-0p
1/2	10%	1Ω-3-9Ω	E12	1-0p 0-8p
1/2	5%	4-7Ω-1MΩ	E12	1-0p 0-8p
1/2	10%	1Ω-10Ω	E12	6p 5-5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4-7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0-1 matrix).
Sub-miniature 0.1W, 3p each. Miniature 0.25W, 6p each.

SEMICONDUCTORS

AC107 13p	BC108 10p	BFY52 22p	OC71 12p	IN4006 12p
AC126 13p	BC109 10p	BY127 12p	OC72 12p	IN4007 12p
AC127 12p	BC147 13p	BZ10 20p	OC81 12p	2N2926R 9p
AC128 12p	BC148 13p	BZ13 20p	OC82 12p	2N2926G 9p
AC131 12p	BC149 13p	OA85 7p	OC82D 12p	2N2926G 9p
AD140 50p	BC157 14p	OA90 5p	ORP12 50p	2N2926G 10p
AF114 20p	BC158 14p	OA91 5p	IN4001 6p	2N3055 60p
AF115 20p	BC159 14p	OA202 7p	IN4002 10p	2N3702 13p
AF116 20p	BF179 32p	OC26 45p	IN4003 10p	2N3703 11p
AF117 20p	BFY50 22p	OC44 12p	IN4004 10p	2N3707 13p
BC107 10p	BFY51 22p	OC45 12p	IN4005 12p	2N3711 10p

ZENER DIODES

400mW 5% 3-3V to 30V, 15p.

LINEAR IC's (DIL)

709 50p	741 50p	14 and 16 pin
710 50p	748 50p	16p

DIL SOCKET

BRUSHED ALUMINIUM PANELS

12in x 6in—25p; 12in x 2 1/2in—10p; 9in x 2in—7p.

DEPT. E.E.
ELSTOW STORAGE DEPOT,
KEMPSTON HARDWICK,
BEDFORD.

C.W.O. PLEASE. POST AND PACKING,
PLEASE ADD 10p TO ORDERS UNDER £2.
Catalogue which contains data sheets for most of the
components listed will be sent free on request.
5p stamp appreciated.
10% DISCOUNT TO ALL CALLERS ON SATURDAYS

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2 1/2p, 0.0068μF, 0.01μF,
0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7 1/2p,
0.33μF, 11p, 0.47μF, 13p.

160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3 1/2p, 0.15μF,
4p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7 1/2p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF
3 1/2p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6 1/2p, 0.47μF, 8 1/2p, 0.68μF, 11p, 1.0μF, 13p
1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V,

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF,
2 1/2p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

(μF/V) 10/2-5, 40/2-5, 80/2-5, 160/2-5, 320/2-5, 500/2-5, 8/4, 32/4, 64/4, 125/4, 250/4,
400/4, 6-4/6-4, 25/6-4, 50/6-4, 100/6-4, 200/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10
125/10, 200/10, 2-5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1-6/25, 6-4/25, 12-5/25,
25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64
20/64, 32/64.

MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6-4, 800/4, 1000/2-5, 9p, 100/64, 160/40, 250/25,
400/16, 640/10, 1250/4, 1000/6-4, 1600/2-5, 12p, 160/64, 250/40, 400/2-5, 640/16,
2000/4, 1000/10, 1600/6-4, 2500/2-5, 15p, 250/64, 400/40, 640/25, 3200/4, 1000/16,
1600/10, 2500/6-4, 4000/2-5, 18p.

ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V) 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25, 5p each.

VEROBOARD

2 1/2 x 3 1/2	22p	0-15
2 1/2 x 5	24p	21p
3 1/2 x 3 1/2	24p	21p
3 1/2 x 5	28p	25p
1 1/2 x 2 1/2	17p	57p
1 1/2 x 3 1/2	100p	78p
1 1/2 x 5 (plain)	—	82p
1 1/2 x 3 1/2 (plain)	—	60p
1 1/2 x 2 1/2 (plain)	—	42p
2 1/2 x 5 (plain)	—	11p
2 1/2 x 3 1/2 (plain)	—	52p
Pin insertion tool	52p	
Spot face cutter	42p	
Pkt. 50 pins	20p	

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Pin. Socket 8p.
4 way screened cable 13p/metre
6 way screened cable 23p/metre

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-style drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

"EXCELLENT PUBLICATION"

"Thank you for the excellent publication: the best in form and type I have ever come across"

T.L.O., Shanklin

"READABLE AND INTERESTING"

"The Manuals are so readable and interesting that I do not think this magazine does full justice to the wonderful contents."

S.T.P., Bangor

"REAL HELP"

"I find the Basic Manuals the best in their class and a real help in my work in prototype electronics."

C.L.P., Cardiff

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50 Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. BASIC ELECTRONICS £5.40 Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY

BASIC ELECTRONICS

Prices include Postage and Packing.

Signature

(If under 21 signature required of parent or guardian)

NAME
BLOCK LETTERS

FULL POSTAL
ADDRESS

POST NOW FOR THIS OFFER!!

A TECH-PRESS PUBLICATION
338

Everyday Electronics, April 1972

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS
TYPESW.100
 100 x 80 mm.



50μA.....	\$3-60	20V. D.C.....	\$3-10
50-0-50μA	\$3-45	300V. D.C.....	\$3-10
100μA.....	\$3-50	1 amp. D.C.....	\$3-10
100-0-100μA	\$3-45	5 amp. D.C.....	\$3-10
500μA.....	\$3-55	300V. A.C.....	\$3-10
1mA.....	\$3-10	VU Meter.....	\$3-75

BAKELITE PANEL METERS
TYPE S-80
 80 mm. square fronts



50μA.....	\$3-30	50V. D.C.....	\$3-60
50-0-50μA	\$3-10	300V. D.C.....	\$3-60
100-0-100μA	\$3-10	1 amp. D.C.....	\$3-60
500μA.....	\$3-60	5 amp. D.C.....	\$3-60
1mA.....	\$3-60	300V. A.C.....	\$3-60
20V. D.C.....	\$3-60	VU Meter.....	\$3-77

"SEW" CLEAR PLASTIC METERS

Type MR.65P. 4 1/2 in. x 4 1/2 in. fronts.



50μA.....	\$3-60	50mA.....	\$3-60
50-0-50μA	\$3-10	100mA.....	\$3-60
100μA.....	\$3-10	500mA.....	\$3-60
100-0-100μA	\$3-10	1 amp.....	\$3-60
500μA.....	\$3-60	5 amp.....	\$3-60
1mA.....	\$3-60	15 amp.....	\$3-60
200μA.....	\$3-60	30 amp.....	\$3-60
500μA.....	\$3-60	20V. D.C.....	\$3-60
500-0-500μA	\$3-60	50V. D.C.....	\$3-60
1mA.....	\$3-60	300V. D.C.....	\$3-60
1-0-1mA.....	\$3-60	1 amp. D.C.....	\$3-60
5mA.....	\$3-60	5 amp. D.C.....	\$3-60
10mA.....	\$3-60	30 amp. A.C.....	\$3-60
30 amp. A.C.....	\$3-60	VU Meter.....	\$3-60

Type MR.65P. 2 1/2 in. square fronts.

50μA.....	\$3-10	10V. D.C.....	\$2-00
50-0-50μA	\$3-60	20V. D.C.....	\$2-00
100μA.....	\$3-60	50V. D.C.....	\$2-00
100-0-100μA	\$3-60	300V. D.C.....	\$2-00
500μA.....	\$3-60	15V. A.C.....	\$2-10
1mA.....	\$3-60	300V. A.C.....	\$2-10
10mA.....	\$3-60	8 Meter 1mA	\$2-10
50mA.....	\$3-60	VU Meter.....	\$2-60
100mA.....	\$3-60	1 amp. A.C.....	\$2-60
500mA.....	\$3-60	5 amp. A.C.....	\$2-60
1 amp.....	\$3-60	10 amp. A.C.....	\$2-60
5 amp.....	\$3-60	20 amp. A.C.....	\$2-60
		30 amp. A.C.....	\$2-60

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts.

50μA.....	\$3-37	10V. D.C.....	\$2-80
50-0-50μA	\$2-75	20V. D.C.....	\$2-80
100μA.....	\$2-75	50V. D.C.....	\$2-80
100-0-100μA	\$3-65	150V. D.C.....	\$2-80
200μA.....	\$3-65	300V. D.C.....	\$2-80
500μA.....	\$3-40	15V. A.C.....	\$2-30
500-0-500μA	\$2-80	50V. A.C.....	\$2-30
1mA.....	\$2-80	300V. A.C.....	\$2-30
10mA.....	\$2-80	500V. A.C.....	\$2-30
50mA.....	\$2-80	8 Meter 1mA	\$2-37
100mA.....	\$2-80	VU Meter.....	\$2-37
500mA.....	\$2-80	50mA A.C.....	\$2-30
1 amp.....	\$2-80	100mA A.C.....	\$2-30
5 amp.....	\$2-80	200mA A.C.....	\$2-30
10 amp.....	\$2-80	500mA A.C.....	\$2-30
15 amp.....	\$2-80	1 amp. A.C.....	\$2-30
20 amp.....	\$2-80	5 amp. A.C.....	\$2-30
30 amp.....	\$2-80	10 amp. A.C.....	\$2-30
5V. D.C.....	\$2-80	20 amp. A.C.....	\$2-30
		30 amp. A.C.....	\$2-30

***MOVING IRON—ALLOTHERS MOVING COIL**
 Please add postage

SEW EDUCATIONAL METERS



neter movement in easily accessible to demonstrate internal working. Available in the following ranges:

50μA.....	\$2-00	20V d.c.....	\$4-40
100μA.....	\$4-65	50V d.c.....	\$4-40
1mA.....	\$4-40	300V d.c.....	\$4-40
50-0-50μA.....	\$4-65		
1-0-1mA.....	\$4-40	Dual range	
1A d.c.....	\$4-40	500mA/5A d.c.	\$4-65
5A d.c.....	\$4-40	5V/50V d.c.	\$4-65
10V d.c.....	\$4-40		

Type MR.65P. 1 1/2 in. square fronts.

200μA.....	\$1-60	200mA.....	\$1-60
300μA.....	\$1-60	300mA.....	\$1-60
500μA.....	\$1-60	500mA.....	\$1-60
750μA.....	\$1-60	750mA.....	\$1-60
1 amp.....	\$1-60	1 amp.....	\$1-60
2 amp.....	\$1-60	2 amp.....	\$1-60
5 amp.....	\$1-60	5 amp.....	\$1-60
10 amp.....	\$1-60	10 amp.....	\$1-60
3V. D.C.....	\$1-60	10V. D.C.....	\$1-60
10V. D.C.....	\$1-60	15V. D.C.....	\$1-60
20V. D.C.....	\$1-60	20V. D.C.....	\$1-60
100V. D.C.....	\$1-60	100V. D.C.....	\$1-60
500μA.....	\$1-65	150V. D.C.....	\$1-60
500-0-500μA	\$1-60	300V. D.C.....	\$1-60
1mA.....	\$1-60	500V. D.C.....	\$1-60
1-0-1mA.....	\$1-60	750V. D.C.....	\$1-60
2mA.....	\$1-60	15V. A.C.....	\$1-70
5mA.....	\$1-60	50V. A.C.....	\$1-70
10mA.....	\$1-60	150V. A.C.....	\$1-70
20mA.....	\$1-60	300V. A.C.....	\$1-70
50mA.....	\$1-60	500V. A.C.....	\$1-70
100mA.....	\$1-60	8 Meter 1mA	\$1-70
150mA.....	\$1-60	VU Meter.....	\$2-10

Type MR.65P. 2 in. square fronts.

50μA.....	\$2-25	5 amp.....	\$1-70
50-0-50μA	\$2-10	10V. D.C.....	\$1-60
100μA.....	\$2-10	20V. D.C.....	\$1-60
100-0-100μA	\$1-37	50V. D.C.....	\$1-60
200μA.....	\$1-37	300V. D.C.....	\$1-60
300-0-300μA	\$1-70	15V. A.C.....	\$1-80
1mA.....	\$1-70	300V. A.C.....	\$1-80
5mA.....	\$1-70	8 Meter 1mA	\$1-85
10mA.....	\$1-70	VU Meter.....	\$2-25
50mA.....	\$1-70	1 amp. A.C.....	\$1-70
100mA.....	\$1-70	5 amp. A.C.....	\$1-70
300mA.....	\$1-70	10 amp. A.C.....	\$1-70
1 amp.....	\$1-70	20 amp. A.C.....	\$1-70
		30 amp. A.C.....	\$1-70

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts.

25μA.....	\$3-50	1 amp.....	\$1-95
50μA.....	\$3-50	2 amp.....	\$1-95
50-0-50μA	\$3-35	5 amp.....	\$1-95
100μA.....	\$3-35	15 amp.....	\$1-95
100-0-100μA	\$3-35	30 amp.....	\$1-95
500μA.....	\$3-30	50 amp.....	\$1-95
1mA.....	\$1-95	5V. D.C.....	\$1-95
1-0-1mA.....	\$1-95	10V. D.C.....	\$1-95
5mA.....	\$1-95	20V. D.C.....	\$1-95
10mA.....	\$1-95	50V. D.C.....	\$1-95
100mA.....	\$1-95	150V. D.C.....	\$1-95
500mA.....	\$1-95	300V. D.C.....	\$1-95
		30V. A.C.....	\$1-85
		50V. A.C.....	\$1-85
		150V. A.C.....	\$1-95
		300V. A.C.....	\$1-95
		500mA A.C.....	\$1-95
		1 amp. A.C.....	\$1-85
		5 amp. A.C.....	\$1-85
		10 amp. A.C.....	\$1-95
		20 amp. A.C.....	\$1-95
		30 amp. A.C.....	\$1-95
		50 amp. A.C.....	\$1-95
		VU Meter.....	\$2-10

EDGWISE METERS



Type PE.70. 3 1/2 in. x 1 1/2 in. x 1 1/2 in. deep.

50μA.....	\$3-10	500μA.....	\$2-75
50-0-50μA	\$3-00	1mA.....	\$2-45
100μA.....	\$3-00	100μA.....	\$3-00
100-0-100μA	\$3-90	300V. A.C.....	\$3-45
200μA.....	\$3-90	VU Meter.....	\$3-40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

MULTIMETERS for EVERY purpose!

ROUND SCALE TYPE PENCIL TESTER MODEL TS 48

Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY \$1-97 P. & P. 13p

HIOKI MODEL 720K
 \$0,000 O.P.V.
 Overload protection.
 5/25/100/500/1000 VDC.
 10/50/250/1000 VAC.
 50 mA/250 mA. 20K/2 meg ohm.
 \$4-97. P. & P. 15p.

SKYWOOD SW-500
 50K Ω/Volt. Mirror scale DC Volts 0.3/3/12/30/300/600. DC Current 20uA/5/600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels - 20 to + 87 db. \$7-50. P. & P. 15p.

Model S-100TR MULTI-METER TRANSISTOR TESTER
 100,000 o.p.v. MIRROR SCALE OVER-LOAD PROTECTION
 0/12-0-6/3/12/30/120/600 V DC.
 0/6/30/120/600 V. AC.
 0/12/600uA/12/300MA/12 Amp. DC.
 0/10K/1 MEG/100 MEG.
 -20 to + 30 db.
 0-01 - 2 μh.
 Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. \$13-50, P.P. 25p.

370 WTR MULTI-METER
 Features A.C. current ranges. 20,000 o.p.v. 0/-.5/2-5/10/50/250/500 1000 V DC. 0/2-5/10/50/250/500/1000 V AC. 0/50uA/1/10/100MA/1/10 Amp DC. 0/100MA/1/10 Amp AC 0/5K/50K/500K/5MEG/50MEG. -20 + 62 db. \$16. P. & P. 25p.

TKM MODEL TW-50K 48 ranges, mirror scale, 50K/Volt.
 D.C. 1.5K /Volt A.C. D.C.: Volts 125, 25, 1.25, 3.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 28, 50uA, 2.5, 5, 25, 50, 250, 500amp, 100amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels - 20 to + 81.5 dB. \$8-50. P. & P. 17ip

TE22 SINE SQUARE WAVE AUDIO GENERATORS
 Sine: 20cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 6,000 ohms, 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. \$17-50. Carr. 37ip.

HT100B4 MULTI-METER
 Features A.C. current ranges. 100,000 o.p.v. Mirror Scale, Overload protection. 0/-.5/2-5/10/50/250/500/1000 V DC. 0/2-5/10/50/250/1000 V AC. 0/10/250uA/2-5/25/250 MA/10 Amp DC. 0/20K/200K/2MEG/20 MEG -20 + 62 db. \$12-50. P. & P. 25p.

TE-20D RF SIGNAL GENERATOR
 Accurate wide range signal generator covering 120 KC/s-500 Mc/s on 6 bands. Directly calibrated Variable R.P. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$18. Carr. 37ip. Size 140 x 215 x 176 mm.

RUSSIAN 22 RANGE MULTIMETER
 Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 uA/1/10/100mA/1A. Resistance 300 ohm/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$5-97 P. & P. 25p.

BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR
 New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 218mm x 130mm x 120mm. Price \$37-50. Carr. 25p.

TO-3 PORTABLE OSCILLOSCOPE
 3in. tube. V amp. Sensitivity 0.1v p-p/C. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω 25pF X amp. sensitivity 0.6v p-p/C. Bandwidth 1.5 cps - 800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal. external. Illuminated scale 140 x 215 x 350 mm. Weight 151 lb. 220/240V. A.C. Supplied brand new with handbook. \$37-50. Carr. 50p

340° Wide Angle Ima Meters
 MW1-6 60mm square \$3-97
 MW1-8 80mm square \$4-97
 P. & P. extra

HONEYWELL DIGITAL VOLTMETER VT.100
 Can be panel or bench mounted. Basic meter measures 1 volt DC but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2. 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 9 1/2 in. x 2 1/2 in. x 4 3/4 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. \$49-97. Carr. 50p.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE
 A new portable bridge offering excellent range and accuracy at low cost. Ranges: R 1Ω-11.1 meg Ω. 5 Ranges ± 1% 5 Ranges ± 1% 1 μ H - 11 μ H. HENRY'S 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 7 in. \$20. P. & P. 25p

G. W. SMITH & CO (RADIO) LTD.
 Also see next two pages

330V/240V SMITHS SYNCHRONOUS GRATED MOTORS
 Built in gearbox. All brand new and boxed 60 RPM CW; 30 RPM CW; 2R/HR ACW; 2R/HR CW; 8R/DAY CW; 10 RPM CW; 50p each. Post 120.

SEMI-CONDUCTOR VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	22p	2N5458	35p	BC114	15p	BFW90	22p	BT219	30p
	2N3416	27p	2N5459	50p	BC115	15p	BFW91	22p	BT220	30p
2Q301	20p	2N3417	22p	2N5460	50p	BC116	15p	BFX10	22p	NKT224
2Q302	20p	2N3439	130p	2B103	25p	BC118	15p	BFX13	22p	NKT225
2Q303	20p	2N3440	97p	2B104	25p	BC119	30p	BFX29	25p	NKT229
2Q306	30p	2N3564	17p	2B301	50p	BC121	20p	BFX30	25p	NKT237
2Q308	30p	2N3565	15p	2B302	50p	BC122	20p	BFX37	30p	NKT238
2Q309	30p	2N3566	22p	2B303	60p	BC123	20p	BFX44	37p	NKT240
2Q371	15p	2N3568	25p	2B304	75p	BC125	25p	BFX45	37p	NKT241
2Q372	20p	2N3569	25p	2B305	20p	BC126	15p	BFX84	25p	NKT242
2Q381	22p	2N3570	125p	2B502	35p	BC135	12p	BFX85	25p	NKT243
2N388A	49p	2N3572	97p	2B503	27p	BC136	15p	BFX86	25p	NKT244
2N404	20p	2N3605	27p	3N83	40p	BC137	15p	BFX87	25p	NKT245
2N496	15p	2N3606	27p	3N128	70p	BC138	20p	BFX88	20p	NKT261
2N497	15p	2N3607	22p	3N140	77p	BC140	30p	BFX89	62p	NKT262
2N498	15p	2N3638	18p	3N141	72p	BC141	30p	BFX93A	70p	NKT264
2N499	15p	2N3639	20p	3N142	65p	BC142	15p	BFX94	62p	NKT273
2N706	15p	2N3644	18p	3N143	67p	BC148	10p	BFY11	42p	NKT292
2N706A	18p	2N3642	18p	3N152	67p	BC149	12p	BFY19	25p	NKT294
2N706	15p	2N3643	20p	40050	55p	BC152	17p	BFY21	42p	NKT275
2N708	45p	2N3644	25p	40280	50p	BC153	20p	BFY24	45p	NKT276
2N718	25p	2N3645	25p	40291	32p	BC154	20p	BFY29	40p	NKT281
2N718A	30p	2N3691	10p	40309	32p	BC157	15p	BFY30	40p	NKT401
2N726	25p	2N3692	18p	40310	45p	BC158	11p	BFY41	50p	NKT402
2N727	25p	2N3693	20p	40311	45p	BC159	12p	BFY43	62p	NKT403
2N914	17p	2N3694	18p	40312	47p	BC160	35p	BFY46	20p	NKT404
2N916	17p	2N3702	10p	40314	37p	BC167	11p	BFY51	20p	NKT405
2N918	30p	2N3703	10p	40315	37p	BC168B	12p	BFY52	20p	NKT406
2N929	22p	2N3704	12p	40316	47p	BC168C	15p	BFY53	15p	NKT451
2N930	30p	2N3705	10p	40317	37p	BC169B	14p	BFY56A	57p	NKT452
2N937	52p	2N3706	10p	40320	47p	BC170	12p	BFY71	45p	NKT453
2N1090	20p	2N3707	10p	40323	32p	BC171	15p	BFY90	65p	NKT713
2N1091	22p	2N3708	10p	40324	32p	BC172	15p	BFY95	65p	NKT717
2N1131	25p	2N3709	10p	40324	32p	BC173	15p	BFY96	65p	NKT734
2N1132	25p	2N3710	10p	40326	37p	BC175	22p	BFY20	15p	NKT736
2N1302	17p	2N3711	10p	40329	30p	BC177	20p	BHX21	20p	NKT773
2N1303	17p	2N3713	18p	40344	27p	BC178	20p	BHX26	45p	NKT778
2N1304	25p	2N3714	18p	40345	27p	BC179	20p	BHX27	45p	NKT787
2N1305	25p	2N3715	25p	40348	52p	BC182	12p	BHX28	12p	OC19
2N1306	25p	2N3716	25p	40360	40p	BC182L	10p	BHX80	82p	OC20
2N1307	25p	2N3717	25p	40361	40p	BC183	9p	BHX81	62p	OC22
2N1308	25p	2N3721	27p	40362	50p	BC183L	9p	BHX76	15p	OC23
2N1309	25p	2N3819	34p	40370	32p	BC184	11p	BHX77	20p	OC24
2N1507	17p	2N3820	55p	40406	47p	BC184L	11p	BHX78	25p	OC24
2N1513	24p	2N3825	55p	40528	72p	BC189	15p	BRY24	15p	OC28
2N1631	35p	2N3854	27p	40408	52p	BC187	27p	BRY25	15p	OC28
2N1632	30p	2N3854A	27p	40409	55p	BC212L	12p	BRY26	17p	OC29
2N1637	30p	2N3855	27p	40410	62p	BC213L	12p	BRY27	18p	OC30
2N1638	27p	2N3855A	30p	40412	50p	BC214L	15p	BRY28	17p	OC36
2N1639	27p	2N3856	30p	40478A	57p	BCY10	27p	BRY29	17p	OC41
2N1701	15p	2N3856A	35p	40488A	35p	BCY30	30p	BRY32	25p	OC41
2N1711	24p	2N3858	25p	40528	72p	BCY31	40p	BRY36	25p	OC44
2N1889	32p	2N3858A	30p	40600	57p	BCY32	60p	BRY37	25p	OC45
2N1893	37p	2N3859	27p	40603	50p	BCY33	30p	BRY38	20p	OC46
2N2147	72p	2N3859A	32p	AC107	30p	BCY34	35p	BRY39	22p	OC70
2N2160	72p	2N3860	30p	AC126	30p	BCY38	45p	BRY43	25p	OC71
2N2193	40p	2N3866	150p	AC127	24p	BCY39	60p	BRY51	32p	OC72
2N2193A	45p	2N3877	40p	AC128	27p	BCY40	60p	BRY52	32p	OC72
2N2194	27p	2N3877A	40p	AC151	18p	BCY41	15p	BRY53	37p	OC74
2N2194A	30p	2N3900	37p	AC152	22p	BCY42	15p	BRY54	40p	OC75
2N2217	25p	2N3900A	40p	AC154	22p	BCY43	15p	BRY56	90p	OC76
2N2218	20p	2N3901	97p	AC176	20p	BCY54	32p	BRY79	45p	OC77
2N2219	20p	2N3903	20p	AC187	25p	BCY58	22p	BRY90	57p	OC78
2N2220	25p	2N3904	25p	AC188	25p	BCY59	22p	BRY95A	18p	OC81
2N2221	25p	2N3907	40p	AC177	27p	BCY60	97p	CA2	15p	OC81D
2N2222	20p	2N3906	25p	ACY18	24p	BCY70	15p	CA50	15p	OC82
2N2222A	25p	2N4088	12p	ACY19	24p	BCY71	20p	GET102	35p	OC82D
2N2287	30p	2N4089	10p	ACY20	20p	BCY72	15p	GET113	25p	OC83
2N2368	15p	2N4090	12p	ACY21	20p	BCY78	30p	GET114	20p	OC84
2N2369	15p	2N4091	12p	ACY22	10p	BCY79	30p	GET118	20p	OC139
2N2369A	15p	2N4092	12p	ACY23	17p	BCZ10	27p	GET120	25p	OC140
2N2410	42p	2N4093	15p	ACY24	17p	BCZ11	40p	GET183	12p	OC170
2N2483	27p	2N4248	15p	ACY40	14p	BD112	50p	GET880	45p	OC171
2N2484	32p	2N4249	15p	ACY41	15p	BD116	112p	GET887	15p	OC200
2N2539	22p	2N4250	18p	ACY44	25p	BD121	65p	GET889	22p	OC201
2N2540	22p	2N4254	42p	AD140	47p	BD123	80p	GET890	22p	OC202
2N2613	35p	2N4255	42p	AD149	47p	BD124	78p	GET896	22p	OC203
2N2614	30p	2N4284	17p	AD150	47p	BD131	75p	GET897	22p	OC204
2N2646	47p	2N4286	17p	AD161	35p	BD132	80p	GET898	22p	OC205
2N2711	25p	2N4286	17p	AD162	35p	BDY10	125p	MAT100	25p	OC206
2N2712	25p	2N4287	17p	AF109	45p	BDY20	125p	MAT101	25p	OC207
2N2713	27p	2N4288	15p	AF114	25p	BDY61	125p	MAT120	25p	OCP71
2N2714	30p	2N4289	12p	AF115	25p	BDY62	100p	MAT121	25p	ORP12
2N2904	20p	2N4290	12p	AF116	25p	BF115	25p	M4060	107p	ORP60
2N2904A	25p	2N4291	15p	AF117	20p	BF117	47p	MJ489	80p	ORP81
2N2905	25p	2N4292	15p	AF118	44p	BF152	28p	MJ421	80p	P346A
2N2905A	20p	2N4294	17p	AF121	30p	BF154	20p	MJ430	102p	RT140
2N2906	20p	2N4303	47p	AF124	22p	BF158	15p	MJ440	95p	RT141
2N2906A	25p	2N4364	16p	AF125	19p	BF159	35p	MJ480	97p	TR334
2N2907	25p	2N4365	18p	AF126	18p	BF163	35p	MJ481	125p	TR843
2N2907A	15p	2N5027	52p	AF127	15p	BF167	25p	MJ492	82p	TR844
2N2924	15p	2N5028	47p	AF139	28p	BF170	35p	MJ491	137p	TR845
2N2925	15p	2N5029	47p	AF178	42p	BF173	30p	MJE340	80p	TR846
2N2926G	12p	2N5030	42p	AF179	45p	BF177	30p	MJE370	80p	TR847
2N2926Q	12p	2N5172	12p	AF180	50p	BF178	25p	MJE371	80p	TR848
2N2926V	12p	2N5174	52p	AF181	40p	BF179	20p	MJE520	75p	TR849
2N3011	20p	2N5175	52p	AF186	30p	BF180	35p	MP621	70p	TR850
2N3012	20p	2N5176	52p	AF187	30p	BF181	35p	MP622	70p	TR851
2N3053	20p	2N5232A	30p	AF279	47p	BF182	30p	MPF103	35p	TR852
2N3054	49p	2N5245	45p	AF280	47p	BF184	20p	MPF104	37p	TR853
2N3055	72p	2N5246	42p	AF211	32p	BF185	20p	MPF105	37p	TR812
2N3133	25p	2N5249	47p	AFY26	25p	BF194	15p	MP83638	32p	XC141
2N3134	30p	2N5265	32p	AFY27	30p	BF195	15p	NKT124	42p	ZTX107
2N3135	25p	2N5306	37p	AFY28	24p	BF196	15p	NKT125	27p	ZTX108
2N3136	25p	2N5307	37p	AFY29	27p	BF197	15p	NKT126	27p	ZTX109
2N3390	25p	2N5307	37p	AFY50	25p	BF198	15p	NKT		

HI-FI EQUIPMENT

SAVE UP TO
33% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!



RECORD DECKS

B.S.R.			
Mini Mono†	£4.97	SP25 III	£10.50
C129†	£6.70	SL55B	£13.45
MP60	£10.75	A175	£18.90
510	£14.65	SL72B	£23.95
510	£11.85	SL75B	£28.50
310	£9.65	SL95B	£32.95
810	£34.47		£29.95
MP60 TPD†	£17.65	ZERO 100A	£45.95
MP60 TPD†	£18.85	ZERO 100B	£42.95
610 T.P.D.†	£20.75	GOLDRING	
510 T.P.D.†	£18.75	GL59/2	£18.97
210 Package*	£9.85	GL169/2P	£24.95
H.T.70	£15.55	GL72	£22.95
H.T.70 Pack.	£22.50	GL72P	£29.95
THORENS		GL75	£28.85
TD125	£59.85	GL75†	£35.95
TD125AB	£84.25	LID 75	£37.75
TX35	£6.75	LID 75	£37.95
TD150AII	£34.50	GL85	£47.95
TD150ABII	£40.25	GL85P	£55.95
TX11	£3.77	LID 85	£4.85
GARRARD		G101	£22.80
2025 T/C*	£8.50	G95	£19.95
3000*	£7.50	PIONEER	
3500*	£9.75	PL12AC	£36.50

† Mono. * Stereo Cartridge
All other models less Cartridge
Carriage 50p extra any model.

RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge. Garrard

2025 T/C with Sonotone 9TA1CD	£13.95
Garrard SP25 Sonotone 9TA1CD	£15.95
Garrard SP2511I Goldring G800	£18.95
Garrard AP76 Goldring G800	£29.95
Garrard SP2511I/Shure M75-6	£19.95
Garrard AP76/Shure M75-6	£20.95
BSR MP60 Audio Technica AT 55	£21.00
Goldring GL72 Goldring G800	£37.50
Goldring GL75 Goldring G800	£42.50
Goldring GL75 Goldring G800E	£46.85

Carriage 50p extra any model.

★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6.37. P. & P. 12p. Stereo multiplex adaptors £4.97.

SINCLAIR EQUIPMENT



Project 60. Package offers.
2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. £16.75 Carr. 37p. Or with PZ6 power supply £18.95 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. £20.25 Carr. 37p.
Transformer for PZ8. £2.97 extra.
Add to any of the above £4.87 for active filter unit and £13.90 for pair of Q16 speakers.
Project 60 FM Tuner £16.95. Carr. 37p.
All other Sinclair products in stock.
2000 Amp £23.75 Carr. 37p.; 3000 Amp £31.50 Carr. 37p.; Neoteric Amp £43.95 Carr. 37p.; 1C10/1C12 £2.50.
NEW PROJECT 60s £20.97 Carr. 37p.

LATEST CATALOGUE


Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

SEND NOW

ONLY
37 1/2 p
P & P
10p




TELETON SAQ-206B STEREO AMPLIFIER

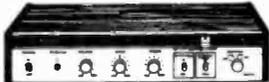

Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List £32.50 OUR PRICE £19.95 Carr. 37p.

TELETON SPECIAL OFFER!

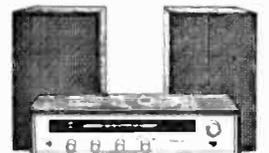

CR101 AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR OF SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception, AFC, built-in MPX, Cer/XTAL input. Total List **£50.25**. OUR PRICE £29.75 Carr. 62p. Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired £36.50. Carr. £1.00.

LAFAYETTE LA. 324 STEREO

AMPLIFIER 12.5 + 12.5 watt R.M.S. Mag/Cer/Tuner /Tape Inputs. Excellent performance. Completes with amplifiers up to £40.

OUR PRICE £24. Carr. 37p.

TAPE CASSETTES

Top quality in plastic library boxes.
C90 60 min 30p. 3 for 85p.
C60 90 min 42p. 3 for £1.10
C120 120 min 52p. 3 for £1.35
Cassette Head Cleaner 30p. Post Extra

TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 01/003/1/3/1/3/10/30/100/300V. R.M.S. 4cps. 1-2 Mc/s. Decibels -40 to +80dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.50. Carr. 25p.

TMK MODEL 117 P.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0-3. 1200V. AC VOLTS 3-300V R.M.S. 8.0-800V P.P.S. DC CURRENT -12-12mA.

Resistance up to 2000M ohm. Decibels -20 to +81 db Complete with leads/instructions. £17.50. P. & P. 20p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40). Quantities available.

PRS-2 PHOTO ELECTRIC RELAY SYSTEM

Inexpensive warning or counting system consisting of an exciter and relay unit. Relay unit has variable sensitivity control and switch for intermittent alarm operation. Exciter unit has removable infra red filter and A.C. outlet socket to operate bells, counters, etc. 240V A.C. Complete with cables and instructions. £9.97 P. & P. 25p.

HOMER INTEROOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station £2.97. P. & P. 15p.
3 Station £5.25. P. & P. 15p.
4 Station £8.62. P. & P. 17p.

EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt R.M.S. Available 8 or 15 ohms. £7.50 each. P. & P. 37p.
Model 450. 13" x 8" with twin tweeters/crossover. 55-13,000 Hz. 8 watt R.M.S. Available 8 or 15 ohms. £3.50 each. P. & P. 25p.

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET. Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1.97. P. & P. 15p.

M27 MIXER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mic: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8.97. P. & P. 20p.

HOSIDEN DH-025 STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY £2.37. P. & P. 12p.

1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2.25. P. & P. 15p.

RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 2 sec to 100 mill sec/cm. Supplied complete with all accessories and instructions £87. Carr. paid.

W4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 687 o.p.v. 6/3/1.5/7.5/30/60/150/300/600/900 VDC and 75mV. 0/1/3/15/7.5/30/60/150/300/600/900VAC. 0/300uA/1.5/5/10/50/100/150/600mA/1.5/5 AMP. D.C. 0/1/5/6/15/60/150/600mA/1.5/5 AMP. A.C. W/250 12/3K/30K Ω. Accuracy DC 1%, AC 1.5%. Knife, edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9.50 plus P. & P. 25p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s-30mc/s. FET. 8 Meter, Variable BFO for 88B, Built-in Speaker, Bandspread, Sensitivity Control. 220/240v. A.C. or 12v. D.C. 12 1/2" x 4 1/2". Brand new with instructions. £25. Carr. 37p.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter, Bandspread, RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £45. Carr. 50p.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2CF8.1 MHz. Input imp. 2 meg Ω 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with hand-book. £22.50. Carr. 50p.

TE-16A Transistorised Signal Generator. 5 ranges 400kHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800kHz modulation. 6 1/2" x 5 1/2" x 3 1/2". Complete with instructions and leads. £7.97. P. & P. 20p.

TE-1035 STEREO HEADPHONES

Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable headband. 8 ohm impedance. 25-18,000 Hz. With lead and stereo jack plug. ONLY £1.97. P. & P. 12p.

MCA. 220 AUTOMATIC VOLTAGE STABILISER

Input 88-125 VAC or 170-250VAC. Output 120VAC or 240VAC. 200VA rating. £11.97. Carr. 50p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. In. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. £7.2p. P. & P. 71p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.05 P. & P. 71p. 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £1.37 P. & P. 71p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

S-260 General Purpose Bench Mounting		S-260B Panel Mounting	
1 Amp	£7.00	1 Amp	£7.00
2.5 Amp	£8.05	2.5 Amp	£8.05
5 Amp	£11.75		
8 Amp	£15.95		
10 Amp	£22.50		
12 Amp	£23.60		
20 Amp	£46.00		

Please add postage ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS. Special discounts for quantity

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to -
11-12, Paddington Green,
London W.2
Tel: 01-262 6562

Everyday Electronics Classified Advertisements

RATES: 7p per word (minimum 12 words). Box No. 7p. extra. Semi-display—£4.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

SERVICE SHEETS

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

RECEIVERS and COMPONENTS

NEW BRANDED GUARANTEED TOP QUALITY

MICROCIRCUITS and TRANSISTORS ALL COMPLETE WITH DATA

2N3055 48p; 741 36p; 723 75p
SOLDERCON I.C. Pin Sockets—0.7p per pin in strips any length.

Send for List and a 2N2926 (Green) **FREE** during **APRIL 1972**

JEF ELECTRONICS (E.E.4)

York Hse., 12 York Dr., Grappenhall, Warrington WA4 2EJ.

Mail Order Only. C.W.O. P&P 7p per order. O/seas 65p. Money back if not satisfied. Discounts begin at 10 off.

COMPUTER PANELS 5-BC108, DIODES 15p, post 5p. 4-50p, Post 10p. **AMERICAN PANELS TOTAL AT LEAST 80 TRANSISTORS, FIRST GRADE COMPONENTS.** 4-55p, Post 10p. **ASSORTED PANELS 6-75p, Post 15p. UNIT WITH 4 LAS POT CORES Plus 11 2% CAPACITORS** 50p, Post 12p. **SINGLES** 80p c.p. **ORPIS ON PANEL EX EQUIPT.** 80p c.p. **FERRITE ROD 7 x 1 1/2p, Post 8p each.** Post for 5 27p. **ICs 7400 SERIES ON PANELS** 10-75p, Post 10p. **'FALL OUTS'** 5-10p, Post 3p. **COPPER CLAD PAXOLIN RINGLE SIDED 8 x 5, 10p, Post 5p each, 13 x 1 1/4, 30p, Post 8p each.** **SMALL SYNCHROUS MOTOR WITH GEAR TRAIN 200-250V.** 30p c.p. **ELECTROLYTICS 5,000 MFD, 25V, 50p c.p. 25 POSITION SLIDING SWITCH AC MAINS OPERATED, WITH MAINS RESET.** 80p, Post 12p. **BANK 10 WIRE ENDED WEAWS** 30p, Post 7p. **ASSORTED TRIMMERS, PRESETS AND MIN. POTS 15-50p c.p. ASSORTED POTS 1" SPINDLES SINGLE AND GANGED 15-50p c.p. TRANSFORMER IN DIE CAST BOX MAINS PRIM. SEC 250-0-25 AT 0.65 AMP 11.** Post 25p. **SEND LARGE S.A.E. FOR LIST OF PANELS, ETC.**

31b ASSORTED PANELS 75p c.p. CONTAIN RES, CAPS, DIODES INDUCTORS, ETC.

J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCs
MAIL ORDER ONLY

Send now for our
ILLUSTRATED COMPONENT EQUIPMENT CATALOGUE
SLIDE AND ROTARY LAMP DIMMER CATALOGUE

10p each—post free
YOUNG ELECTRONICS
54 Lawford Rd., London, NW5 2LN
01-267-0201

DO-IT-YOURSELF ... we stock a large range of audio and electronic components at very competitive prices, e.g.: Chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale & Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for **FREE** list. (2 x 3p stamps for fabric samples.) Mail-order **ONLY**. No callers please.

AUDIOSCAN Dept. EE472
4, PRINCES SQUARE, HARROGATE, YORKS.

BRAND NEW G.P.O. TYPE 3000 RELAYS

2000 Ohm Coil, 1 X Normally Closed Contact, 60p P. & P. 10p
2000 Ohm Coil, 1 X Normally Closed Heavy Duty Contact 75p, P. & P. 18p
1000 Ohm Coil, 2 X Change-over Light Duty Contacts 75p, P. & P. 18p

We can supply any type of G.P.O. 3000 Relays. Component parcels include Plugs, Sockets, Capacitors, etc. etc., 4 lb. nett weight, £1.00, P. & P. 30p

ELEKON ENTERPRISES

12A TOTTENHAM STREET, LONDON, W1P 9PQ
Tel. 01-580-7881

EDUCATIONAL

TECHNICAL TRAINING in Radio, TV & Electronics through world-famous ICS. For details of proven home-study courses write: ICS (Dept. 566), Inter-text House, London, SW8 4UJ.

MEN! You can earn £50 p.w. Learn computer operating. Send for FREE brochure—London Computer Operators Training Centre, G22 Oxford House, 9-15 Oxford Street, London, W.1.

FREE

TO ENGINEERS

Whatever your age or experience you must read **New Opportunities**. It describes the easiest way to pass A.M.S.E., A.M.I.M.I., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering: Mechanics, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book.

Send for your copy today—**FREE!**

B.I.E.T. B125, Aldermaston Court, Reading, RG7 4PP

Accredited by the Council for the Accreditation of Correspondence Colleges

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

MISCELLANEOUS

PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN. **TRIAL KIT** (36 sq. in.) .. £1.28 carr. pd. **No. 1. KIT** (54 sq. in.) .. £1.88 carr. pd. **No. 2. KIT** (72 sq. in.) .. £2.39 carr. pd. **MPE Ltd., Dpt D.E. Bridge St. Clay Cross, Derbys**

Build your EE circuit on a NIPPIBOARD

Printed wiring board for transistor circuits

EE Windscreen Wiper Control	—Type 1B
EE Fuzz Box	—Type 1A
EE Astron Medium Wave Receiver	—Type 1A
EE Remote Temperature Comparator	—Type 1A
EE Soil Moisture Meter	—Type 1A
EE Darkroom Timer	—Type 2A
EE Wea-Waa Pedal	—Type 2A
EE Rain Sensor	—Type 1A

Also suitable for other E.E., P.E., P.W. projects
S.R.B.P. FIBREGLASS

1A	15p	2AS	28p	1B	18p	2BS	34p
2A	28p	4AS	44p	2B	34p	4BS	52p
3A	38p	6AS	60p	3B	43p	6BS	72p
5A	52p	10AS	90p	5B	62p	10BS	£1.10

NIP Electronics

DEPT. NB/EE, P.O. BOX 11, ST ALBANS, HERTS

A CATALOGUE

Is the first step to a successful electronic building project. Beginners and experts alike can select their needs from a catalogue which shows the wealth of Professional components distributed by R.S. Components Ltd. (formerly Radiospares). Every Radiospares Item specified in constructional features can be supplied, just as quickly as the postman can get to your home.

ALL LISTED COMPONENTS ARE POST PAID TO YOUR HOME IN THE U.K. STRICTLY MAIL ORDER ONLY.

SEND ONLY 25p FOR YOUR COPY OF THIS INVALUABLE 96-PAGE CATALOGUE TO:—

CELECTRON-E

P.O. BOX NO. 1,
LLANTWIT MAJOR, GLAMORGAN CF6 9YN

WILSIC SOUND EFFECTS KITS WAH-WAH PEDAL KIT (illustrated)



Kit comprises a **SELECTIVE AMPLIFIER MODULE KIT** to convert the **FOOT VOLUME CONTROL PEDAL** (as photo) to Wah-Wah operation. Amplifier module £1.75, pedal unit £5.13, **COMPLETE KIT £6.50** add 30p for assembly of module, but please note we cannot supply kits fully built.

REVERBERATION UNIT KIT. For dimension effect. Connects between sound source, mic., etc., and amplifier. Battery powered. **COMPLETE KIT £9.20** (excluding case £7.50). Assembled in slimline cabinet £12.50.

VIBRATO UNIT KIT. Foot pedal unit with variable speed and depth controls. **COMPLETE KIT £5.25.**

SEND 15p for the WILSIC PLANS BOOK, with full details of these kits; circuits, drawings and price lists.

LATEST CATALOGUE 5p (stamps)

WILSIC ELECTRONICS LTD.

6 COPLEY ROAD, DONCASTER, YORKS.

MISCELLANEOUS—continued

RECORD TV SOUND using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. **CROWBOROUGH ELECTRONICS (E.E.)**, Eridge Road, Crowborough, Sussex.

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW
S.A.E. for details

TO: BOFFIN PROJECTS'
DEPT. KEE.
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY

CASSETTE BARGAINS. Paros recorder Mains/battery complete for only £17 post free. Low-noise tape cassettes, C60-32p, C90-50p, C120-70p. Musicassettes—£1.25 & £1.50, post free. Write for other bargains. Hargreaves Electric, 4 Roman Way, Dordon, Tamworth, Staffordshire.

JOHN SAYS...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable FI/F2 rejection. Module £7. Unit £8-90. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. Only £2-95. AUTO RHYTHM from Dewtron modules. Simple unit for waltz, fox trot etc. costs £18-00 in modules. SYNTHESISER MODULES and other miracles. Send 15p for illust. list. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

KASPEN

Why not build your projects in modern looking cases made of Perspex? Besides being robust & weatherproof, Perspex is available in a variety of bright colours, transparent and opaque. Cases are available in kit form for the following:-

- ASTRON £1-40 REMOTE TEMP. COMP. £1-30
 - HOME SENTINEL £0-90 RAIN ALARM £0-90
 - BARRROOM TIMER £1-30 MOISTURE METER £1-00
(STATE DIA. OF METER HOLE WHEN ORDERING)
all prices include p & ph.
- cash - with - order

10, SEYMOUR ROAD, TILBURY, ESSEX RM10 7AP

CHROMASONIC electronics

SL403D £1-50, SN76013 £1-25, MFC4000 52p, AD161/162 pair 60p, A.M. Coil set with ferrite rod £1 (p. & p. 6p all orders). Carbon Track pots 12p + Switch 24p. Fully illustrated 1972 Catalogue 20p post free.

56 Fortis Green Rd, London N10 3HN

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts. 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised. Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3.30** post paid
or in kit form **£2.90**

Easy to construct
SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire Large S.A.E. for lists

"I'D LIKE TO TEACH THE WORLD TO PLAY"

So I've designed an Electronic Automatic Chord selector which can be fitted to most organs or which can be made into an Accompliment Instrument ideal for groups, singers, arrangers or as an instrument which all the family can play.

Send for details to:
J. MOLLOY
Elm Road, Tokers Green, Reading, Berks.

SOUND SUPPLIES (LOUGHTON) CO. LTD.

for Eagle International and International Rectifier Products TOA P.A. Equipment and Mikes. Capacitors, Resistors, Plugs, Sockets, Cables, Audio Leads, Semiconductor, Valves, Vero Board, etc., for the constructor.

ELECTRONICS DEPT. Tel. 01-508-2715
12 Smaris Lane, Loughton, Essex.
Hours: 9.30 a.m.-1 p.m., 2-6 p.m. Mon., Tues. Wed. and Fri.; 9.30 a.m.-1 p.m., 2-5.30 p.m. Sat. Closed all day Thursday.

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

NEW LINES !!!!!

E.M.I. Speakers with twin tweeters	£3-75
8 watt amplifiers complete	£2-80
Cassette Tapes: C60, 57p; C90 75p; C120, 90p	
GOLDRING MAGNETIC CARTRIDGES (GB50)	£4-75
Cardioid Ball type Mikes (usually £6-60)	£3-75
Intercom with Battery & Lead	£2-50
Neons, with resistor and 2 ft lead	3p
Speakers, 8 ohm, 2 1/2 in	45p
MULLARD DATA BOOK FOR 1972	30p

TRANSISTOR EQUIVALENT BOOK, LATEST EDITION 40p

Mikes, Low impedance, dynamic stick type with on/off switch	£1-00
" Crystal, hand	20p
" Crystal, Inserts with bracket	£1-25
Lockable car aerials	98p
Dee-Gez 25 watts pencil bit soldering irons	50p
Speakers, 2 1/2 in, 8 ohms	3p
Insulating Tape, 1/2 in wide, 10 yard rolls	12p
Miniature Output Transformers	15p
Rotary Switches, 4 pole 3 way or 2 pole 6 way	50p
Switch cleaner, aerosol cans	50p

Electrolytic Capacitors		Miniature type. Both wires same end.	
2,000 µf 25 volt Rev.	25p	5 µf 10 volt	} 3p each
1,000 µf 70 volt	35p	250 µf 25 volt	
10,000 µf 35 volt	50p	10 µf 10 volt	
10,000 µf 25 volt	35p	30 µf 10 volt	
2,000 µf 18 volt	20p	50 µf 10 volt	
60µf ... 200µf 300 volt	30p	Axial leads	
400 µf 275 volt	25p	250 µf 25 volt	10p
10µf 6 volt	2p	500 µf 25 volt	13p
10µf 25 volt	4p	1,000 µf 25 volt	16p
16µf 250 volt	8p	2,000 µf 25 volt	25p
32 µf 275 volt	8p	400 µf 40 volt	20p

STOCK TAKING CLEARANCE! IMPOSSIBLE TO REPEAT!
We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.

Gross weight 2 lb £1 (postage 20p)
Gross weight 5 lb £2 (postage 30p)

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.

UNBEATABLE PRICE !!!!!

LINEAR INTEGRATED CIRCUITS. Direct from manufacturer, all 100% to specification.

709C	35p	100 up	24p
741C	50p	100 up	35p

VEROBOARD

2 1/2 in x 1 in x 0.15 in 6p	5 in x 3 1/2 in x 0.15 in 28p	3 1/2 in x 3 1/2 in x 0.1 in 24p
2 1/2 in x 2 1/2 in x 0.15 in 16p	17 in x 2 1/2 in x 0.15 in 55p	5 in x 2 1/2 in x 0.1 in 23p
3 1/2 in x 3 1/2 in x 0.15 in 20p	17 in x 3 1/2 in x 0.15 in 74p	5 in x 3 1/2 in x 0.1 in 28p
5 in x 2 1/2 in x 0.15 in 20p	3 1/2 in x 2 1/2 in x 0.1 in 21p	

Spot Face Cutter 38p, Pin Insert Tool 48p, Terminal Pins (0-1 or 0-15) 36 for 18p, Special Offer Pack consisting of 5 2 1/2 in x 1 in boards and a Spot Face Cutter—50p.

RECORD PLAYER CARTRIDGES. Well below normal prices!
G90 Magnetic Stereo Cartridges, Diamond Needle, 6mV output, £2-75. ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible, Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1-25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1-63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1-50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1-88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1-25.

TRANSISTORISED FLUORESCENT LIGHTS, 12 volt. All with reverse polarity protection. 8 watt type with reflector, suitable for tents, etc., £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch, 2 1/2 in x 2 in x 1 in £3. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.

MULLARD POLYESTER CONDENSERS
1,000pf, 1,200pf, 1,500pf, 1,800pf, 2,200pf, 15p per dozen (all 400V working). 0.15µf, 0.22µf, 0.27µf, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

RESISTORS
1/4 and 1/2 watt. Most values in stock, 75p per 100. 10p per dozen of any one value. **WIRE WOUND MAINS DROPPERS.** Hundreds of values from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

TRANSISTORS

A SELECTION FROM OUR LIST

AA730 10p	BD115 75p	OC16 50p	2N1303 18p
AA742 15p	BD123 85p	OC20 85p	2N1304 22p
AAZ13 10p	BD124 80p	OC22 50p	2N1305 22p
AAZ15 10p	BD131 75p	OC23 60p	2N1306 25p
AAZ17 10p	BD132 80p	OC24 60p	2N1307 25p
AC737 35p	BDY11	OC25 40p	2N1307 25p
AC126 30p	BDY17	OC26 25p	2N1308 25p
AC127 25p	BDY38 65p	OC28 60p	2N1309 25p
AC127Z 50p	BDY60	OC29 60p	2N1613 20p
AC176 20p	BDY60	OC35 50p	2N2147 75p
AC187 25p		OC36 60p	2N2160 60p
AC189 25p		OC42 40p	2N2217 25p
AC187 30p	BF115 25p	OC43 40p	2N2218 20p
AC197 25p	BF154 20p	OC44 15p	2N2218 20p
AC198 25p	BF158 15p	OC45 12p	
AC199 25p	BF159 35p	OC70 12p	2N2219 20p
AC200 25p	BF180 35p	OC71 12p	2N2219 20p
AC21 20p	BF180 35p	OC72 20p	
AC22 10p	BF194 15p	OC73 25p	2N2220 25p
AC23 55p	BF195 15p	OC77 25p	2N2221 20p
AC24 40p	BF196 15p	OC77 25p	2N2221 20p
AC24 15p	BF197 12p	OC81 20p	
AD144 25p	BFX13 25p	OC81Z 20p	2N2222 20p
AD149 50p	BFX29 25p	OC81Z 20p	2N2222A
AD161 35p	BFX34 25p	OC83 25p	
AD162 35p	BFX56 30p	OC84 25p	2N2369 15p
AF114 45p	BFY85 15p	OC89 40p	2N2369A
AF116 25p	BFY87 25p	OC141 60p	2N2446 40p
AF116 25p	BFY88 20p	OC170 25p	2N2904 20p
AF117 20p	BFY18 25p	OC171 30p	2N2904A
AF118 60p	BFY50 20p	OC200 40p	
AF124 25p	BFY51 20p	OC201 75p	2N2905 25p
AF125 20p	BFY52 20p	OC202 80p	2N2905A
AF126 20p	BFY53 20p	OC203 80p	2N2905B
AF127 20p	BFY90 65p	OC271 97p	
AF139 30p	BRX30 15p	ORP12 50p	2N2906A
AF180 50p	BRX21 20p	ORP60 40p	
AF181 45p	BRX27 15p	RT140 15p	2N2907 23p
AF185 60p	BRT95A 12p	RT141 20p	2N2907A
AF186 40p	BRT95 12p	TIP29A 50p	2N2925 25p
AF195 45p	BT105 25p	TIP30A 60p	2N2926 15p
ABY26 35p	BT100 15p	TIP31A 60p	2N2906 20p
ABY27 30p	BY126 12p	TIP32A 70p	2N3011 20p
ABY28 25p	BY124 15p	TIP33A	2N3003 20p
ABY29 30p	BY182 90p		2N3004 50p
ABZ21 55p	BYZ10 85p	TIP34A	2N3055 75p
BA109 15p	BYZ12 30p		2N3025
BA102 25p	BYZ13 25p	TI843 40p	2N3625
BA117 25p	BYZ13 25p	TI850 12p	2N3614 55p
BA118 7p	BYZ10 85p	TI851 10p	2N3702 10p
BA119 5p	BYZ10 85p	TI852 10p	2N3703 10p
BA116 7p	GET105 25p	TI860 15p	2N3704 12p
BA131 7p	GET111 45p	TI861 20p	2N3705 10p
BA132 15p	GET112 25p	TI862 25p	2N3707 12p
BC107 10p	GET105 25p	TI90A 60p	2N3708 12p
BC108 10p	GET115 50p	VR525 35p	2N3714
BC109 10p	GET116 55p	WO1 30p	
BC109C 12p	GET880 45p	WO6 45p	2N3715
BC113 10p	GET882 30p	ZTX107 15p	
BC114 20p	GET886	ZTX108 12p	2N3716
BC115 20p	GM378A 15p	ZTX109 15p	2N3717
BC116 20p	MAT101 25p	ZTX302 20p	2N3771
BC117 20p	MAT121 25p	ZTX302 20p	2N3772
BC118 20p	MC724P 80p	ZTX303 20p	
BC119 30p	MJ420 80p	ZTX304 25p	2N3773
BC120 30p	MJ421 80p	ZTX600 15p	2N3774
BC135 15p	MJ2901	ZTX601 15p	2N3781
BC136 20p	MJ2901	ZTX602 20p	2N3782
BC137 30p	MJ2901	ZTX603 17p	2N3816 35p
BC138 30p	MJ2901	ZTX604 40p	2N3820 55p
BC147 12p	MJE340 80p	ZTX631 20p	2N3823 50p
BC148 10p	MJE370 80p	IN914 7p	2N3824 95p
BC149 12p	MJE371 80p	IN916 10p	2N3903 20p
BC153 20p	MJE520 75p	IN1418 7p	2N3906 25p
BC154 20p	MJE521 75p	IR44 7p	2N4058 12p
BC167 15p	MJE2955	IR921 7p	2N4061 12p
BC169 12p		IR922 6p	2N4062 12p
BC169C 15p	MJE3055	2Q301 25p	2N4289 12p
BC177 20p		2Q302 30p	2N4290 12p
BC178 20p	MP8A06 25p	2Q303 35p	2N4871 35p
BC179 20p	MP8A58 80p	2N404 20p	2N5457 30p
BC182L 10p	MP8U10 15p	2N696 15p	2N6458 35p
BC183L 10p	MP8U06 50p	2N697 15p	2N6459 35p
BC184L 12p	MP8U56 55p	2N698 30p	40250 50p
BC212L 12p	NKT714 20p	2N706 10p	40260 40p
BC213L 12p	NKT715 35p	2N706A 12p	40361 40p
BC214L 15p	NKT403 75p	2N708 15p	40362 50p
BCY30 25p	NKT404 55p	2N930 20p	40430 60p
BCY31 30p	OA5	2N987 40p	40443 65p
BCY32 30p	OA10 25p	2N1171 25p	40594 60p
BCY33 30p	OA47 10p	2N1132 25p	40595 60p
BCY34 30p	OA70 10p	2N1302 18p	40638 60p
BCY35 45p	OA79 10p		
BCY39 45p	OA81 8p		
BCY40 45p	OA90 8p		
BCY41 45p	OA91 8p		
BCY42 45p	OA95 7p		
BCY71 20p	OA200 7p		
BCY72 15p	OA202 10p		

Full transistor list available—send for free copy today!

HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW FULL SPECIFICATION TTL74 SERIES

BRANDED FAIRCHILD, I.T.T. AND TEXAS

DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICES

No.	Description	1-11	12-24	25-90	100+	250+
7400	Quad 2-input NAND gates	20p	18p	14p	14p	12p
7401	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7402	Quad 2-input NOR gates	20p	18p	14p	14p	12p
7403	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7404	Hex inverters	20p	18p	14p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	14p	14p	12p
7410	Triple 3-input NAND gates	20p	18p	14p	14p	12p
7413	Dual 4-input Schmitt triggers	30p	27p	25p	22p	20p
7420	Dual 4-input NAND gates	20p	18p	14p	14p	12p
7430	Single 8-input NAND gates	20p	18p	14p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	14p	14p	12p
7445	Dual 4-input NAND buffer driver	75p	72p	70p	60p	55p
7448	BCD-Decimal decoder (4-10-line) TTL O/P	75p	72p	70p	60p	55p
7449	Excess 3-Decimal decoder TTL outputs	\$1.00	90p	90p	80p	70p
7447	BCD-Decimal 7 seg. decoder/indicator driver	\$1.75	\$1.60	\$1.45	\$1.30	\$1.15
7448	BCD-Decimal 7 seg. decoder/driver TTL O/P	\$1.75	\$1.60	\$1.45	\$1.30	\$1.15
7450	Expand dual 3-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7452	Quad 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7454	4-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7460	Dual 4-input expanders	20p	18p	14p	14p	12p
7470	Single J-K flip-flop (gated inputs)	20p	27p	25p	22p	20p
7472	Single J-K flip-flop (gated inputs)	30p	27p	25p	22p	20p
7473	Dual J-K flip-flop	40p	37p	35p	32p	30p
7474	Dual D flip-flop	40p	37p	35p	32p	30p
7475	Quad J-K flip-flops with Preset and Clear	45p	42p	40p	38p	35p
7480	Gated Full Adder	80p	72p	67p	59p	55p
7481	16-bit read/write memory	\$1.25	\$1.15	\$1.10	\$1.00	90p
7482	2-bit binary Full Adder	87p	80p	70p	65p	60p
7483	4-bit binary Full Adder	\$1.00	90p	80p	70p	65p
7484	16-bit RAM with gated write inputs	90p	85p	80p	75p	72p
7486	Quad 2-input Exclusive OR gates	45p	42p	40p	38p	35p
7490	BCD decade counter	75p	70p	65p	60p	55p
7491	8-bit shift register	\$1.00	95p	90p	80p	70p
7492	Divide twelves counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	75p	70p	65p	60p	55p
7494	Dual entry 4-bit shift register	80p	75p	70p	65p	60p
7495	4-bit up-down shift register	80p	75p	70p	65p	60p
7496	5-bit parallel/inhibit/out shift register	\$1.00	97p	95p	80p	83p
7413	8-bit bistable decoder	\$2.50	\$2.30	\$2.00	\$1.75	\$1.50
74118	Hexuple Set-Reset latches	\$1.00	95p	90p	80p	70p
74121	Monostable multivibrators	60p	55p	50p	46p	41p
74141	BCD-Decimal decoder/Nixie driver	\$1.00	95p	90p	80p	70p
74150	BCD-Decimal decoder (4-10-line) TTL O/P	\$1.50	\$1.40	\$1.30	\$1.10	\$1.00
74151	16-bit data selector/multiplexer	\$3.35	\$3.20	\$2.95	\$2.15	\$2.05
74152	8-bit data selector/multiplexer	\$1.35	\$1.27	\$1.20	\$1.15	\$1.10
74153	Dual 4-line to 16-line data selector/multiplexer	\$2.00	\$1.75	\$1.55	\$1.30	\$1.05
74154	16-bit decoder/demultiplexer	\$1.55	\$1.47	\$1.35	\$1.10	\$1.05
74155	Dual 2-line to 4-line decoder/demultiplexer	\$1.55	\$1.47	\$1.35	\$1.10	\$1.05
74156	Dual 2-line to 4-line decoder/demultiplexer	\$1.95	\$1.85	\$1.75	\$1.60	\$1.50
74190	Rsync decade up-down counter, 1-line mode	\$2.00	\$1.90	\$1.80	\$1.65	\$1.55
74191	Rsync 4-bit up-down counter, 1-line mode	\$1.95	\$1.85	\$1.75	\$1.60	\$1.50
74192	Rsync decade up-down counter, 2-line mode	\$2.00	\$1.90	\$1.80	\$1.60	\$1.40
74193	Rsync 4-bit up-down counter, 2-line mode	\$2.00	\$1.90	\$1.80	\$1.60	\$1.40
74197	Asynchronous presettable decade counter	\$1.50	\$1.40	\$1.30	\$1.10	\$1.00
74198	Asynchronous presettable 4-bit binary counter	\$1.50	\$1.40	\$1.30	\$1.10	\$1.00

Complete data on the above in booklet 20 pages, Ref. 29, issue 2 at 15p post paid.
 Texas I.C. Handbook. Complete information on 100 types. 40p. Post 10p.
 Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 30p.

INTEGRATED CIRCUITS

MFC4000P	55p
MFC4010P	60p
IC12	\$2.50
PA245	\$1.50
TAD100	\$1.50
TAD110	\$1.50
MC724P	60p
709C (T05)	45p
709C (T05)	45p
709C (D.I.L.)	45p
723C (T05)	\$1.00
741C (T05)	80p
MC1303P	\$2.00
MC1304P	\$2.20
81403D	\$1.50
741C (D.I.L.)	75p
914 (T05)	40p
923 (T05)	40p
TOHIBA	40p
20 watt amp.	24-47
TOHIBA	40p
Pre amp	\$1.50

PLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier

IC403D
 Complete with 8-page booklet, circuits and data
£1.50



ZENER DIODES

1-25	100	500	1000
24	+	+	+

600m/w

BZY 88 series*	12p	10p	8p	7p	6p
11 watt					
12Z series	25p	23p	20p	17p	15p
3 watt					
3TZ series	30p	27p			

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS AND AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. Switched Ear-piece Socket complete, with Earpiece, 10 Transistors plus 3 Diodes. 8" x 5 1/2" Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)



ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL




7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 8" x 5 1/2" Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)

ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 5" heavy duty speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.

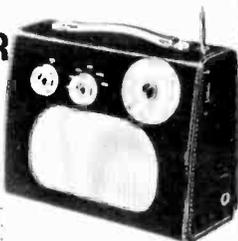
Total building costs **£5-98** P. P. & Ins. 41p. (Overseas P. & P. £1)



ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra MW band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—8 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

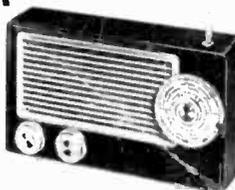Total building costs **£3-98** P. P. & Ins. 26p. (Overseas P. & P. £1)



POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 21p. (Overseas P. & P. 63p)



TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 22p. (Overseas P. & P. 63p)




TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

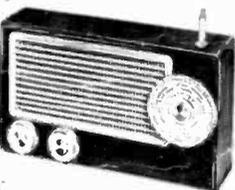Total building costs **£4-48** P. P. & Ins. 31p. (Overseas P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT COMPONENTS INCLUDE:

Tuning Condenser; 2 Volume Controls; 2 Slider Switches; 4"x2 1/2" Speaker; Terminal Strip; Ferrite Rod Aerial; 3 Plugs and Sockets; Battery Clips; 4 Tag Boards; Balanced Armature Unit; 10 Transistors; Diodes; Resistors; Capacitors; Three 1" Knobs.

Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including Case and Plans **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)



FULL AFTER SALES SERVICE

• Callers side entrance Barratts Shoe Shop
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN ROAMER SEVEN
ROAMER EIGHT TRANS EIGHT
TRANSONA FIVE ROAMER SIX
POCKET FIVE EDU-KIT

Parts price list and plans for

Name

Address

(Dept. E.E.6.)

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · ELECTRONIC COMPONENTS · TEST PA · DISCOTHEQUE · LIGHTING · MAIL ORDER

10th EDITION CATALOGUE



350 pages fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

PRICE 55p POST PAID (40p FOR CALLERS)

10,000 Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. EE), 3 Albemarle Way, London, E.C.1—for catalogue by post only.

All other mail and callers to "309", see below HENRY'S CATALOGUE IS A MUST FOR ELECTRONIC COMPONENTS OF ALL TYPES

TEST EQUIPMENT

Huge range in stock—too much to list here. It's all in the latest catalogue—prices—specifications etc. Also Panel Meters and Edge Meters.



GARRARD McDONALD GOLDRING TURNTABLES

CHASSIS (Post 50p)
 SP25/3 £11.30 H770 £16.60
 MP60 £11.30 MP610 £15.15
 AP76 £20.50 Zero 1005 £41.97

With PLINTH/COVER (Post 70p)
 MP60 PC £17.65
 HL75 PC £37.35
 HT70 PC £23.50
 GL72P £32.95
 CART/PLINTH/COVER (Post 70p)
 GL72PC/G800 £35.95
 MP60 PC/G800 £29.95
 HT70 PC/G800 £29.95
 MP60 PC/SC5M £17.50
 (HL)SP25/3/G800H £19.95
 (HL)2025 TC/9TAHCD £14.95

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.
PRICE PAIR £5.90 Post 10p

POWER INTEGRATED CIRCUITS

SL403D—3 watt with 8 page data, layouts & circuits £1.50
 P.C. Board 60p; Heat Sink 14p
 IC12—6 watt with data and circuits £2.50
 TOSHIBA—20 watt Power Amp Module £4.57
 TOSHIBA—IC Preamplifier £1.50
 TOSHIBA—Data / Circuits Book No. 42 10p

TEXAS PUBLICATIONS

1-100 watt Amplifiers and PreAmp. Layouts and data £1.25 Price list No. 48A FREE
 700 page IC Data Book (No. 2) 60p
 420 page Transistor Data (No. 3) 60p
 340 page Transistor Data (No. 4) 60p
 (Post etc. 15p each, 20p per 2 or 3 books)

NIXIE TUBES

(Post 15p per 1 to 6)
 XN3, XN13, GN6 0-9. Side view with data 95p
 GNP-7, GNP-8 0-9. Side view with decimal points and data 95p
 GN4 0-9 End view with socket and data £1.65

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150 TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.95. Post 25p.
TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7.70. Post 28p.

POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

HIGH POWER AMPLIFIER MODULES

Quality transformerless low noise amplifiers suitable for all Audio, PA and Hi-Fi use. Modern compact designs. PA25 and PA50 supplied with plug harness for use with MU442 Power Supply.
 MPA12/3 18v. 0-8A. 12W. 3-4 ohm. £4.50
 MPA12/15 30v. 0-5A. 12W. 12-16 ohm. £5.25
 MU24/40 Mains unit for 1 or 2 MPA12/3 or 15. £4.50
 PA25 22-0-22v. 1A. 25W. 8 ohm. £7.50
 PA50 22-0-22v. 2A. 50W. 3-4 ohm. £9.50
 MU442 Mains unit for 1 or 2 PA25 or 1 only PA50. £6.00

ALL SILICON-FET PREAMPLIFIER AND MIXER SELF POWERED

All inputs. Adjustable input and output. DIN sockets. Tape in and out. Microphone mixing. Suitable up to 4-PA25 or 2-PA50.
PRICE £10.50 Post 30p

300mW TRANSISTOR AMPLIFIER MODEL 4-300

Fully assembled 5TR Amplifier. Size 5 1/2" x 3 1/2" x 1 1/2". 1-10mV adjustable sensitivity. Output 3-8 ohms. Fitted Vol. control, 9 volt operated. Thousands of uses plus low cost.
 Price £1.75, p.p. 15p (or 2 for £3.25, p.p. 15p)

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO
 A popular VHF FM Tuner for quality A and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.
TOTAL £6.97, p.p. 20p. Cabinet 100p. Decoder Kit £5.97.
 Tuning meter unit £1.75
 Mains unit (optional) Model PS900 £2.47. Post 20p
 Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p

SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!

Z30 £3.60 Z50 £4.38
 STEREO PZ5 £3.98
 60 £7.98 PZ8 £5.97
 PZ6 £6.38

Transformer for PZ8 £2.95
 Active Filter Units £4.75
 Stereo FM Tuner £20.25
 IC12 £2.50; Q16's £8 ea.
 Post etc. 20p per item
ALSO IN STOCK
 2000 £3.75; 3000 £31.50
 Post 50p each

"BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/JF Module. Medium and Long Wave bands plus Medium Wave Bandsread for extra selectivity. Also slow motion geared tuning, 600 mV push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.
TOTAL COST TO BUILD £7.98, p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2.
"77" MEDIUM AND LONG WAVE PORTABLE (as previously advertised) £6.98, p.p. 35p from stock—Leaflet No. 1.

SLIDER CONTROLS. Top quality 60mm singles and gangs complete with knobs. (Post 1-5 15p; 6 or more 20p)
 5K, 10K, 25K, 50K, 100K, 500K, 1 Meg. Log and Lin 45p each
 10K, 25K, 50K, 100K, Log and Lin ganged. 75p each

F2000 SYSTEM

Teleton F2000 Med/Stereo FM Tuner Amplifier, Garrard SP25/3, Goldring G800H, Auto with plinth and cover. Pair matching speakers K60. Size 16 x 9 1/2 x 6 1/2 in. All leads etc.
 List £54.65 Carr. £2.93
 or with MP60/SC5MD Single Player £57.50. Carr. £2.

2200 SYSTEM

Rota 10 + 10 watts Stereo Amplifier, Garrard SP25/3, Goldring G800H, plinth and cover, pair of speakers SDL2 (or KN800) Size 18 x 10 1/2 x 7 1/2 in. All leads etc.
 List £65.50 Carr. £2.94

2200 SYSTEM

Rota 10 + 10 watts Stereo Amplifier, Garrard SP25/3, Goldring G800H, plinth and cover, pair of speakers SDL2 (or KN800) Size 18 x 10 1/2 x 7 1/2 in. All leads etc.
 List £65.50 Carr. £2.94

206B SYSTEM

Teleton SAQ206B8 + 8 watts Stereo Amplifier, Garrard SP25/3, Goldring G800H, plinth and cover. Pair of speakers SDL1 (or K80). Size 15 x 10 1/2 x 7 1/2 in. All leads etc.
 List £55.95 Carr. £2.90
 or with 2025TC/9TAHCD and K60 Speakers 16 x 9 1/2 x 6 1/2 in. £49.95. Carr. £2.

ROTEL SYSTEM

RX 150 B + 8 watt Med/FM/Hi-Fi stereo Tuner Amplifier, pair of SDL2 Speaker Systems 18" x 10 1/2" x 7 1/2". Garrard SP25/3/11/Plinth/Cover/Goldring G800H cart. All leads etc.
 List £99.95 Carr. £2.50
 £133

FREE

Latest Hi Fi & Tape Recorder 12 page Stock Discount List plus over 100 Stereo Systems. Ref. 16/17.

PUBLIC ADDRESS, LIGHTING & DISCOTHEQUE EQUIPMENT

DJ1055 30 watt rms Amplifier, 4 Inputs, master tone and volume controls etc. 8 ohm output. Cased portable. £33.50. Post 40p.
 DJ705 70 watt rms version. Cased portable. £53.00. Post 40p.
 DISCOAMP 100 watt rms to 8 ohms. 4 inputs, separate bass and treble controls, PFL, etc. Cased for cabinet or rack mounting £76.50. Post 40p.
 McDONALD MP60 fitted to plinth with cover, SC5MD cartridge to match above amplifiers. £17.50. Post 70p.
 DJ301.11 3 channel light control unit for above amplifiers. 3 x 1 K Watt. Treble, Bass and Mid range. £33.50. Post 35p.
 EFFECTS PROJECTORS—Coloured rotating light patterns.
 DISCO-COLT 250w Tungsten £22.50
 LIQ150—50 watt Q.I. £32.50
 LIQ150—150 watt Q.I. £50.00

FULL RANGE OF LIGHTING IN STOCK

High Fidelity Sales & Demonstrations Centre
 354 EDGWARE ROAD, LONDON, W.2.
 Tel: 01-402 5854

SPECIAL! Anti-Feedback Microphone designed and made for Henry's for all PA/Disco Equipment. £11.50
LIGHT GUIDE 64 fibres sheathed £1 per yd.
 Mono (0-001") £1.50 per 25 metre reel.
 COMPLETE RANGE OF DISCO/PA AND LIGHTING ON DISPLAY AT "309".
 Call, write or phone for details and lists.

P.A., Disco & Lighting Centre
 309 EDGWARE ROAD, LONDON, W.2.
 Tel: 01-723 6263

Mail Orders. Special Bargain Shop, Industrial Sales
 303 EDGWARE ROAD, LONDON, W.2.
 Tel: 01-723 1008/9

"309", "354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY