



An exciting hobby.... for everyone

everyday electronics

JUNE 72


15p

**GUIDE TO CIRCUIT SYMBOLS
PART 1**

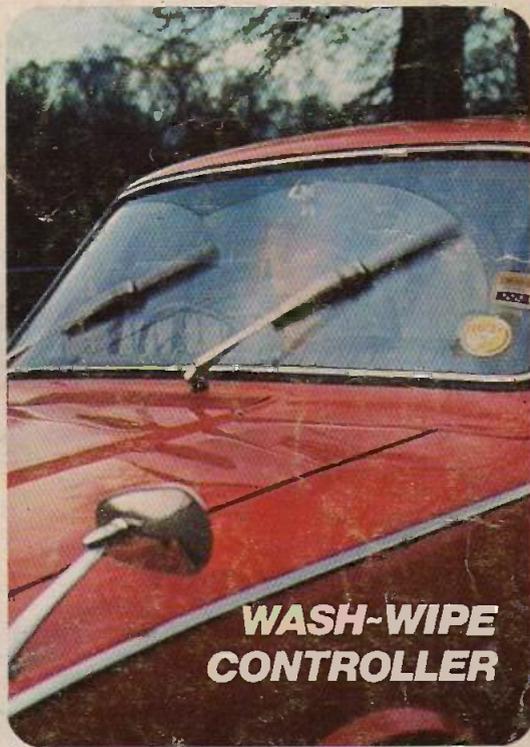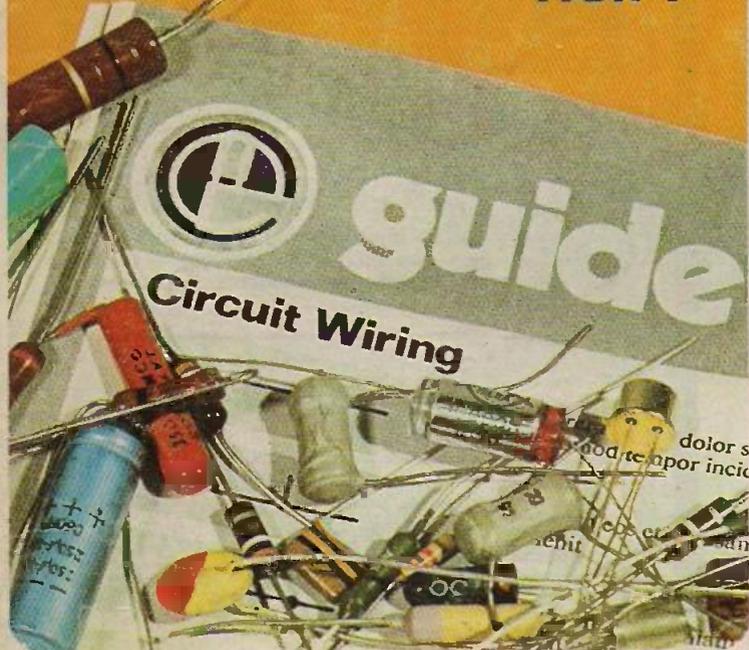

**WASH-WIPE
CONTROLLER**

**LIGHT
TO
SOUND
CONVERTER**

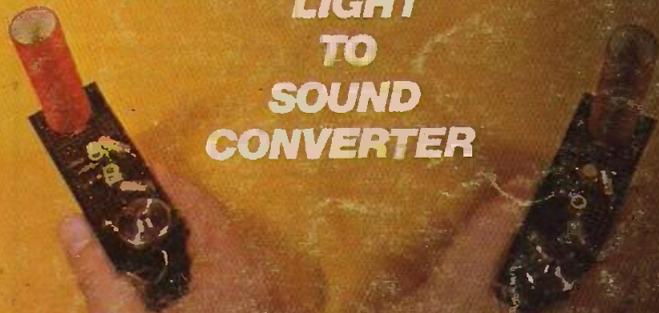

SIMPLE MULTIMETER

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits

(illustrated) available

COPPER

B 38 $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{4}$ " — 4.75 mm EYELLET BIT

B 58 $\frac{1}{2}$ " — 6.3+ mm CHISEL FACE

LONG LIFE


B 42 LL $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

PRICE
£1.85

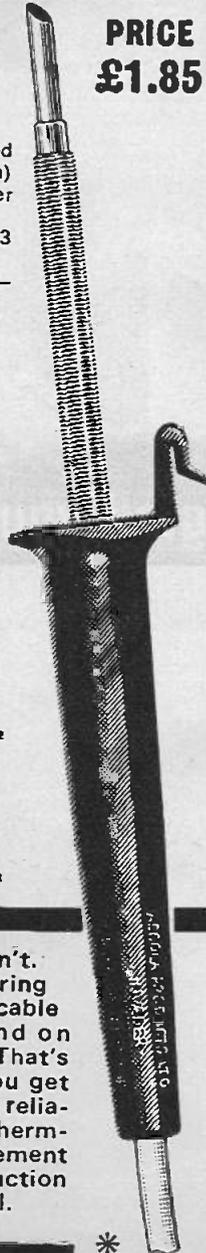

Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



* Write for price list and catalogue

ADCOLA PRODUCTS LTD.,
(Dept. Y), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-872 8251/3 - Telegrams: Seljeat Leadia Telex - Telex: Adcola London 21851

SAFEBLOC

of robust construction


Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

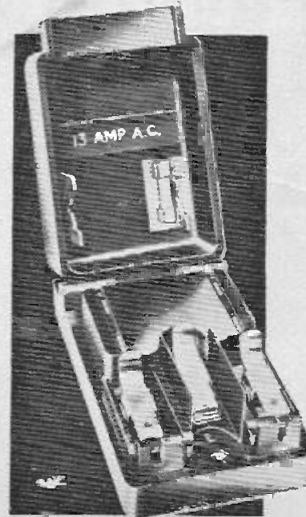Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.



If ordering by post, send cash with order.

PRICE £2.60+10p P.&P. EACH

Special bulk order wholesale and industrial rates on application



RENDAR®

Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex. Tel. Burgess Hill 2642

BARGAIN PRINTED CIRCUIT OFFER

Circuit Board with all holes drilled, 7 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ ". Central hole 1 $\frac{1}{2}$ " for speaker magnet and cut out for PP3 batt.; Rocker w/change switch and mounting bracket; 2 gaur. tuning capacs.; 3 I.F.S. Osc. Coil, Ferrite rod with coils and holder. Potentiometer and knob; Circuit Booklet, showing component values and positions. All for £1.75 (25p Post). Worth £5.

BATTERY CHARGER

5 $\frac{1}{2}$ " x 3" x 3" with fixing feet. 12V 2amp. On-off Indicator, 2 yds. Mains and 2 yds. Battery Leads; Battery Clips. £1.50 (25p. Post).

PANEL METERS—70mm square. Minus 10A. to Plus 20A. D.C. £1 (15p Post); Ditto 0-25V. A.C. and D.C. £1 (15p. Post); 2 $\frac{1}{2}$ " dia. 0-40V. D.C. 50p (15p Post);

ELECTROSTATIC VOLTMETER 3 $\frac{1}{2}$ " dia. 0-1000V. £2 (15p Post).


STEREO AMPLIFIER Type SHV—2 x 3 watts

Fully built. Separate vol., bass and treble controls each channel; 12 x 4 $\frac{1}{2}$ x 6in high. 2 x BY127, 60CR5, 2 x ECL86 valves. O.P. trans. for 3-ohm speakers. Double wound mains trans. Suitable for crystal, ceramic cartridge, tuner, etc. 200-250V. A.C. mains. 28 (P. & P. 50p)



MONO GRAM CHASSIS 3 WATT

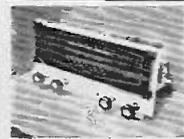3 Wave band long-med-short, Gram., 200-250V. A.C. Ferrite aerial. Chassis 13 x 7 x 6in. Dial 13 x 4in. Double wound mains transformer 5 valves ECH81, 6X9, 6BQ5, 6X4, 6Z50. Price £10.53. (37p P. & P.) Output trans. for 3-ohm speaker. Soudc slightly tarnished at £10 carr. pd.



MAINS TRANSFORMERS (240-250V input)

Postage In brackets. 6-3V at 2A. 40p (16p)
280-0-280V 60MA. 6-3V 2A. 6-3V 700MA. £1 (27p)
250V at 50mA and 6-3V at 1A. 50p (20p)
22V at 1A. 6-2V at 2A and 250V at 50mA. 75p (25p)
90V at 20mA and 1-4V at 250mA. 50p (15p)
13V at 1A. 40p (16p).

Deduct 10 per cent from total bill for more than one transformer.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, HANTS.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22340. CLOSED WEDNESDAY. S.A.E. for enquiries please.

Would YOU pay 50 pence for a components catalogue?



You'll be glad you did
when you get THIS one!

A components catalogue is so vital to any keen constructor that it simply does not pay to make do with less than the best. True, the best may cost a little more . . . but it's the cheapest in the end. So invest in a *Home Radio Components Catalogue*, listing over 8,000 items, more than 1,500 of them illustrated. If you call at our shop the catalogue is yours for just 50 pence. If you order by post—70 pence, including postage and packing. You also get 10 Vouchers, each worth 5 pence when used as instructed—so you can get the cost of the catalogue back in any case!

Ask for details of our Credit Account Service.

24-hour Phone Service. Ring 01-648 8422

POST THIS COUPON with your cheque or postal order for 70p



Please write your Name and Address in block capitals

NAME

ADDRESS



The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

HOME RADIO (COMPONENTS) LTD., Dept. EE,
234-240 London Road, Mitcham, Surrey CR4 3HD.

THIS FANTASTIC OFFER ONLY FROM US! Fabulous BRAND NEW **SAVE £20.25 NOW!** **SOLID STATE** This equipment's got EVERYTHING!

BATTERY/MAINS AC/DC

Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



RECOMMENDED RETAIL PRICE £44

OUR PRICE £23.75 CARR. ETC. 35p

WITH REMOTE CONTROL MICROPHONE

Latest sensation in the world of sound! First-class makers. Fabulous V.H.F. AM/FM Radio AND Cassette Tape Recorder and Player combined, AND runs off standard batteries or mains (plug in the 220/240v. AC line cord). Record, play back anything, anywhere! Even tape direct from Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44. WE OFFER AT ALMOST HALF PRICE!** Wonderful features: * Press button Keyboard Control panel or latest **MASTER SWITCH CONTROL!** * "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic leveller. * Separate ON/OFF, HI-LO volume control! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case with carry handle. **DESIGNS VARY SLIGHTLY.** Takes standard 30, 60, 90 or 120-minute Philips Cassette Tapes obtainable everywhere. The amazing built-in full circuit V.H.F. AM/FM Radio gives you superb clarity of tone, incredible station selection—Unique rotating "Station Selector Dial"—get all local city and regional stations in every part of the country plus BBC, National V.H.F. Picks up dozens of foreign stations. Also fabulous in car! You could pay ££££'s more for a Car Radio or Car Cassette player ALONE! **£23.75, CARR. 35p.** Simple instructions, remote control microphone with on/off switch and microphone stand. **BONUS—Standard Batteries and Cassette Tape 25p extra if required.** Send or call

RUSSIAN WORLD BEATER! **WORLD WIDE RECEPTION** THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

JUST ARRIVED! THE FABULOUS BRAND NEW **VEF 204** THIS OFFER ONLY FROM US!

8 WAVEBAND **10 TRANSISTOR** PLUS 1000'S OF **PORTABLE RADIO**

AND NOW WITH **SHIP-TO-SHORE MARINE BAND** NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

BATTERY MODEL £13.97p BATTERIES ETC. 50p **MAINS/BATTERY ELIMINATOR £1.48p Extra.**



WE COULD NOT EVEN MAKE THEM FOR OUR FANTASTIC PRICE! *COMPARE IT'S PERFORMANCE WITH £42 RADIOS!

Important! This very latest model incorporates all latest technological improvements and surpasses all earlier models! Yes, **DESIGNED FOR WORLD-WIDE RECEPTION**—it'll probably make your present radio seem like a "crystal set"! It even incorporates a special **MARINE WAVEBAND** to receive spoken communications from ship-to-shore! We're almost giving them away at only £13.97p—a mere fraction of even today's Russian miracle price! Compare performance with £42 radios! *Refund if not satisfied! Purer and sweeter tone than ever! Wider band spread for "pin-point" station selection! The Russians have really surpassed themselves this time, proving again their ability in the field of space communications. Yes, 8 separate wavebands, including Standard Long, Medium and Short Waves to cover the world, PLUS special "ship-to-shore" **MARINE BAND!** Thousands of different transmissions and stations at your fingertips 24 hours a day, including ships at sea, etc., and messages from all over the world. You must hear it to believe it! Superb sweet tone—controlled from a whisper to a roar! Push-pull output! Separate ON/OFF volume & Treble/Bass tone controls! Press-button dial Illumination! Take it anywhere—runs economically on standard batteries, or through battery eliminator from 220/240v. AC mains, internal ferrite rod plus telescopic aerial. It's also a fabulous **CAR RADIO!** Black and chrome case 11" x 9" x 3 1/2" overall approx. Made to give years of perfect service. Complete with **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £13.97p** (with mains/battery eliminator £1.48 extra). **POST 50p.** Standard batteries 38p extra. Can also be used through extension amplifier, tape recorder or public address system. (SORRY—we cannot change these new radios for any earlier model already purchased!) **NOTE:—The Ministry of Post & Telecommunications has pointed out that licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.**

SHOPERTUNITIES LTD. SIL Dept. EE/8, 164 UXBRIDGE ROAD, LONDON W12 8AQ (facing Shepherds Bush Green) (THURSDAY 1, FRIDAY 7). Also at 37/39 High Holborn, LONDON, W.C.1. (Thurs. 7). Both stores open from MONDAY-SATURDAY 9 a.m.-6 p.m.

The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (25p P & P) ALSO AVAILABLE
SINGLE VICE: £3.37 1/2 (21p P & P)

COVENTRY MOVEMENT CO LTD.
Dept. E5
BURNSALL ROAD, COVENTRY CV5 6BU STD O203-74363

Introduction to Electricity

L. T. AGGER

This comprehensive introduction to electrical science is designed to meet the requirements of courses leading to the Ordinary National Certificate and Diploma, and of the City and Guilds Technicians' courses. Chapters dealing with applications include sufficient relevant general science to make the book self-contained, and it is therefore equally suited for use by the student working on his own. In the general treatment of electrical science, physical explanations are widely used, and the mathematical standard is set no higher than is strictly necessary. A graded set of problems is appended to each chapter. SI units are used consistently throughout the text, and brief notes on absolute units are also given. 331 text figures £6 paper covers £3

OXFORD UNIVERSITY PRESS

Vary the strength of your lighting with a **DIMMASWITCH**



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt £3.20. Kit Form £2.70
300 Watt £2.70. Kit Form £2.20

All plus 10p post and packing. Please send C.W.O. to:

DEXTER & COMPANY
5 ULVER HOUSE, 19, KING STREET, CHESTER CH1 2AH Tel: 0244-25883, As supplied to H.M. Government Departments.

£25

takes the wraps off
UNISOUND
 a new concept in stereo




The whole system is complete including superb cabinets in simulated teak—just simply screw together the components and you save pounds! Amplifier is based on the famous Mullard Unilex system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13" x 8" EMI speakers ready for mounting in their elegant cabinets which simply need screwing & gluing together. Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound. Output—5 watts R.M.S. per channel into 8-15Ω.

£25 complete plus £2.80 p. & p.
 Power output: 4 watts per channel into 8 ohms
 Input: 120 mV (for ceramic cartridge)



UNISOUND MODULES ONLY-£6.95

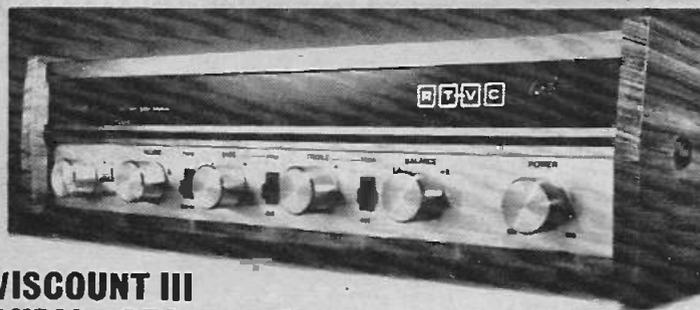If you prefer, you can buy the three modules—pre-amplifier, power supply/dual power amplifier and control panel—by themselves for only £6.95. P. & P. 50p extra. Their overall specification is the same as shown for the complete Unisound console. See below for address.



A QUARTER TURN RIGHT!

...opens a world of
 real stereo sound

VISCOUNT III AUDIO—£52 complete

PRICES	
SYSTEM 1	
Viscount III R 101 amplifier	£22.00 + 90p p&p
2 x Duo Type II speakers	£14.00 + £2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
Total	£59.00
Available complete for only £52 + £3.50 p&p	
SYSTEM 2	
Viscount R101 amplifier	£22.00 + 90p p&p
2 x Duo Type III speakers	£32.00 + £3 p&p
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23.00 + £1.50 p&p
Total	£77.00
Available complete for only £69 + £4 p&p	

14+ 14W per channel 40Hz to 40kHz ± 3dB.

Total distortion @ 10W @ 1kHz — 0.1%.

2 complete stereo systems using the Viscount III amplifier. FET'S are incorporated on the input stages, just like top priced units to give you more of the signal you want and almost none of the hiss you don't. Output sockets for 'phones and tape recorder.

The exclusive Duo loudspeaker systems are large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

Speakers Duo Type II

Size approx. 17" x 10 3/4" x 6 3/4". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 8 ohms. Simulated teak cabinet. £14 pair + £2 p&p.

Duo Type III. Size approx. 23 1/2" x 11 1/2" x 9 1/2". Drive unit 13 1/2" x 1 1/2" with H.F. speaker. Max power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

Specification

14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms). Total distortion @ 10W @ 1kHz 0.1% P.U.I. (for ceramic cartridges) 150mV. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. (Radio 150mV. Tape out facilities: headphone socket. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: P.U.1 and radio — 65dB. P.U.2, +58dB. Cross talk better than — 35dB on all inputs. Size approx 13 3/4" x 9" x 3 3/4". Goods not despatched outside U.K.




R+TV

Radio and TV Components (Acton) Ltd., 21c High Street,
 Acton, London G3 6NG, 323 Edgware Road, London W2.
 Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.

BSR LATEST SUPERSLIM STEREO AND MONO

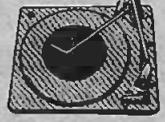
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 12 1/2 x 11 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL MONO-COMPATIBLE Plays all records



£8-75 Post 25p.
£7-75 Post 25p.

BGS 3 WATT AMPLIFIER Ready made tested. 3-stage triode pentode valve UCL82. 3 watts output. Tone and volume controls. Rectifier valve UY35. Kinks. With high performance Loudspeaker. Response 50-12,000 cps. Sensitivity 200mV. Post 25p **£4**

R.C.S. PORTABLE PLAYER CABINET

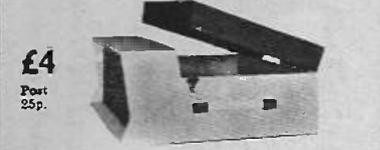

Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18 x 15 x 5 in. Metal finishes. Carrying handle. Popular colours. Two-tone varnished. **£4** Post 25p.

GARRARD SINGLE PLAY TA MK II Complete with stereo mono plug in head. Ideal Discotheque or Hi-Fi. **£10**

GARRARD AUTOCHANGERS with Sonotone Cartridges Stereo Diamond and Mono Sapphire. Model 1025 £10. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

BSR JUNIOR SINGLE PLAYER Turntable, 4-speed motor and separate pick-up **£4-50**

EMI PICK-UP ARM with mono xtal and stylus £1-25. **HI-FI PICK-UP CARTRIDGES** Diamond LP/Stereo Stereo/Mono £24 £25.00; GP34 £2.50; GP33 £2.00; Sapphire Mono GP31 £1.50; Power-point LP/78. 60p.

E.M.I. WOOFER AND TWEETER KIT £5-75 Post 25p

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 44oz. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Impedance Standard 8 ohms Maximum Power 12 watts Useful Response 35 to 18,000 cps Base Resonance 45 cps **SUITABLE ENCLOSURE 20 x 13 x 9 in, £9 POST 25p**

WEYRAD P50 - TRANSISTOR COILS

RA5V Ferrite Aerial... 72p	Spare Cores
Loc. P50/LAC... 33p	Driver Trans. LYDTA... 58p
LF. P50/200 470 kfs. 38p	Printed Circuit, P50A1... 58p
3rd LF. P50/30C... 38p	J.B. Tuning Gang... 65p
P51/L or P51/2... 38p	Wayrad Booklet... 10p
P50/37... 38p	OFTI... 58p

Melbard Ferrite Rod 3 x 1/2 in. 20p, 6 x 1/2 in. 20p.

VOLUME CONTROLS 800ohm Coax 4p. rd. **BRITISH AERIALITE AERIAL-AIR SPACED** 40 yd. £1.40; 60 yd. £2. FRINGS LOWLOSS 10p yd. Ideal 625 and colour.

8in ELAC HI-FI SPEAKERS Dual cone plasticized roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts music power. **£4-80**

BLANK ALUMINIUM CHASSIS 18 s.w.g. 8in. sides 7 x 4in. 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 8in. 90p; 14 x 11in. 95p; 15 x 14in. 95p; 11 x 8in. 50p; 16 x 10in. 41p. **ALUMINIUM PANELS** 18 s.w.g. 6 x 4in. 9p; 8 x 6in. 16p; 14 x 3in. 16p; 10 x 7in. 15p; 12 x 6in. 20p; 12 x 8in. 28p; 16 x 6in. 25p; 14 x 9in. 24p; 12 x 12in. 40p; 16 x 10in. 50p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2 p. 2-way, or 3 p. 6-way or 3 p. 4-way 25p each. 1 p. 18-way, or 4 p. 2-way, or 4 p. 3-way 25p.

TOGGLE SWITCHES, sp. 14p; dp. 18p; dp. dt. 23p.

"THE INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER 200/250v. A.C. £2-35 Post 15p

HI-FI STOCKISTS RETURN OF POST DESPATCH **RADIO COMPONENT SPECIALISTS** MINIMUM POST AND PACKING 15p **CUSTOMERS FREE CAR PARK** CALLERS WELCOME **337 WHITEHORSE ROAD, CROYDON** Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) Radio Books & Component Lists 5p. Written guarantees. (Export; Remit cash and extra postage.) Buses 50, 68, 159 Rail Selhurst. Tel. 01-684-1665

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Filtered Circuit, Bridge Rectifier and Double Wound Mains Transformer input 200/240v. AC. Output voltages available 6 or 9 or 12 or 16 or 18 or 20v. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST FREE Details S.A.E. Size 3 1/2 x 1 1/2 in.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 8-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 in. Response 25 cps to 25 Kc/s. 26db gain. For use with valve or transistor equipment. 90p Post Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS

2/850V... 14p	250/25V... 14p	50+50/350V... 35p
4/350V... 14p	500/25V... 20p	60+100/350V... 58p
8/450V... 14p	1000/25V... 35p	32+32/250V... 18p
16/450V... 15p	1000/50V... 47p	32+32/450V... 33p
32/450V... 20p	5+3/450V... 18p	350+50/325V... 50p
25/25V... 10p	5+18/450V... 20p	32+32+32/350V... 43p
50/50V... 10p	16+18/450V... 25p	100+50+50/350V... 745p
100/25V... 10p	32+32/350V... 25p	

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 12V. 15p; 25V. 20p; 50V. 30p.
1000mF. 12V. 17p; 25V. 25p; 50V. 47p; 100V. 70p.
2000mF. 6V. 25p; 25V. 42p; 50V. 57p.
2500mF. 50V. 82p; 3000mF. 25V. 47p; 50V. 65p.
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p.

CERAMIC 1pF to 0.01 mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p. 0-8 18p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 5p; 0.47 25p.

SILVER MICA Close tolerance 1 p, 2-5-500pF 5p; 500-2-200 pF 10p; 2-700-4-600pF 20p; 6-300pF 0-01, mid 20p; each. **TWIN GANG** 10 or 20pF x 170V. 45p; slow motion drive 385+385 with 25+25pF 50p 500pF slow motion, standard 45p; small 3-gang 500pF £1.60.

SHORT WAVE, SINGLE 10pF 30p; 25pF 55p; 50pF 55p. **NEON PANEL INDICATORS** 250V AC/DC Red or Amber 20p. **RESISTORS** 1 w., 1/2 w., 20% 1p; 2 w. 5p 10 ohms to 10 meg HIGH STABILITY 1 w. 2%, 10 ohms to 1 meg. 10p. Ditto 5% Preferred values 10 ohms to 10 meg. 4p. **WIRE-WOUND RESISTORS** 5 watt, 10 watt, 15 watt 10 ohms to 100K. 10p each; 2 1/2 watt, 1 ohm to 8-2 ohms 10p.

DECCA DECCAED GARRARD MOTOR UNIT MKII



Single play Stereo Mono Derram transcription head and arm. Four speeds. 10 1/2 in. turntable. Anti-rumble filter. Bias compensation. Laboratory motor. **SPECIAL PRICE £18-50** Post 25p

METAL PLINTH & PLASTIC COVER Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 x 7 1/2 in. **£5-50** Post 25p

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH AT SAME PRICE

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp.	£1-60
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£2-50
250-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£3-00
300-0-300 v. 150 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a.	£3-25
MINI-TUNER 200 v. 200 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in.	75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in.	90p
MINI-MAINS 50v. 100mA. 1 1/2 x 1 1/2 in.	50p
HEATER TRANS. 6.3 v. 3 a.	60p
Ditto tapped sec. 1.4 v. 2.3 a. 5.6 v. 1 1/2 amp.	80p

GENERAL PURPOSE LOW VOLTAGE, Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. 25 25 1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, 25 25 2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, 25 25 5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, 25 25 **AUTO TRANSFORMERS** 115v. to 230v. or 230v. to 115v. 100w. £2-25; 500w. 25-25; 750w. £10; 1000w. £14. **CLARION TRANSFORMERS** 100/250/500. 10p for 8 or 12v. 16in. £1-50; 2 amp £1-80; 4 amp £2-50. **FULL WAVE BRIDGE CHARGER RECTIFIERS:** 6 or 12v. outputs, 1 amp. 40p; 2 amp. 55p; 4 amp. 85p. **LUCAS 2DS500 Bridge 70V 5 amp £1.**

E.M.I. 13 1/2 x 8in. LOUDSPEAKERS

With twin tweeters and crossover, 10 watt. Size 8 or 8 or 15 ohm. (As illustrated) **£4-25** Post 15p

With fitted tweeter cone and ceramic magnet. 10 watt. Base res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. **£2-75** Post 15p

Teak Cabinet Size 16 x 10 x 9in. Post 25p £5

ALL MODELS "BAKER SPEAKERS" IN STOCK BAKER 12in. MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 n.p.s. Rated 30 watts. Voice coils 3 or 8 or 15 ohms. Post Free

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11-50**

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch 25 watt	12 inch 35 watt	15 inch 50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TRAK HI-FI SPEAKER CABINETS Plated wood front For 12in. or 10in. dia. speaker 20 x 18 x 9in. £9. Post 25p For 12 x 8in. or 8in. speaker 16 x 10 x 9in. £5. Post 25p For 10 x 6in. or 6in. speaker 16 x 8 x 6in. £4. Post 25p. **LOUDSPEAKER CABINET WADDING** 14in. wide, 15p ft.

GOODMANS 6 1/2 in. HI-FI WOOFER 8 ohm, 10 watt. Large ceramic magnet. Special Cambridge cone surround. Frequency response 80-12,000 cps. Ideal P.A. Column, Hi-Fi Enclosures Systems, etc. **£4**

ELAC CONE TWEETER The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 3,000 cps to 12,000 cps. Size 3 1/2 x 2 1/2 in. dia. Rating 10 watts. 3 ohm or 15 ohm models. **£1-90** Post 10p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kfs, 10W 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-18 kfs, 16W, 15W, 15 ohm £3. **TWO-WAY 3000cps CROSSOVERS** 2 or 3 or 15 ohm 50p. **SPECIAL OFFER:** 80 ohm 2 1/2 in.; 2 1/2 in.; 35 ohm, 2 1/2 in.; 3in 25 ohm, 2 1/2 in. dia.; 3in dia.; 8 x 4 in.; 8 x 6 in. £1 EACH TYPE 8 ohm, 2 1/2 in. 3in, 5 in.

LOUDSPEAKERS P.M. 8 OHMS 7 x 4in. £1-25; 6in. £1-50; 8 x 5in. £1-60; 8 x 2 1/2 in. 80p. 8in. £1-10; 6 x 4in. £1-10.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 8 watt 3 or 8 or 15 ohm models £2.00 each. Post 15p. **VALVE OUTPUT TRANS.** 25p; **MIKE TRANS.** 50-1 25p. **5 WATT MULTI-RATIO.** 3, 8 and 15 ohms 80p.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 input speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. **£39** Post Free

GARRARD AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **£4-50**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **STEREO VERSION OF ABOVE 24-50. £3-50**

BARGAIN FM TUNER 88-108 Mc/s. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch **£12-50**

BARGAIN FM TUNER as above less cabinet **£8-85**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **£3-50**

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LIFE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p. BATTERED TWIN FEEDERS 5p yd. 50 ohms or 300 ohms. JACK SOCKET 3rd. open-circuit 14p. closed circuit 23p; Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS 8in. DMM Plugs; 3 6mm Chrome 14p. DMM SOCKETS Chassis 5-pin 10p; 5-pin 10p. DIT SOCKETS Lead 3-pin 15p; 5-pin 55p. DIN Plug 3-pin 15p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 5p; CASE 5p.

E.M.I. TAPE MOTORS Post 15p. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. **£1-25** Size 2 1/2 x 2 1/2 in. (Illustrated).

BALFOUR GRAM MOTORS 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1 x 3/32. Size 2 1/2 x 2 1/2 in. **Post 15p 85p**

FOR RAPID SERVICE

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

TRANSISTORS

AC127	17p	BFX29	38p
AC128	18p	BFX84	25p
AC176	22p	BFX88	30p
AC187	28p	BFY50	21p
AC188	27p	BFY51	21p
ACY19	23p	BFY52	22p
AD149	47p	MAT100	25p
AD161/162	73p	MAT101	29p
ADT140	62p	MAT120	25p
AF118	45p	MAT121	29p
AF124	22p	OC28	58p
AF125	19p	OC35	48p
AF126	20p	OC44	12p
AF127	19p	OC45	12p
AF178	67p	OC71	11p
AF179	66p	OC72	12p
AF180	45p	OC75	20p
AF239	32p	OC200	27p
BC107	11p	OC201	38p
BC108	11p	OC771	42p
BC109	11p	ST140	15p
BC147	12p	ST141	23p
BC148	12p	UT46	35p
BC149	12p	2N696	15p
BC157	15p	2N706A	12p
BC158	14p	2N2926G	14p
BC159	14p	2N2926Y	13p
BD131	75p	2N2926O	12p
BB132	75p	2N3053	25p
BF115	25p	2N3054	60p
BF178	32p	2N3055	72p
BF179	56p	2N3702	15p
BF180	30p	2N3703	14p
BF181	32p	2N3704	15p
BF184	30p	2N3705	14p
BF185	32p	2N3706	14p
BF194	14p	2N3711	14p
BF195	14p	2N3819	35p
BF196	28p	2N4058	17p
BF197	15p	2N5459	60p
BFW10	70p		

DIODES

AA119	11p	OA202	10p
OA47	7p	BY100	15p
OA90	7p	BY127	22p
OA91	6p	BY212	22p

ZENER DIODES

From 2 to 33 volts.
400mW, 15p; 1.5W, 22p

SILICON BRIDGE RECTIFIERS

40 P.I.V., 1.5A
200 P.I.V., 2.0A

MISCELLANEOUS ITEMS

Mercury Switch, 2 Amp., 25p
B9A valve bases, 2p
5k Ω edge control, fits most small, imported radios, 7p
20 Ω volume control for 3 Ω speakers, 20p
Antex CN240, 15W miniature soldering iron, £1.70
Valve and Transistor Data book, 9th edition, 75p
Transistor equivalent book, BPI, 40p

PANEL FUSEHOLDERS

For 1 1/2in. fuses 18p
For 20mm fuses 15p

CONTROLS, Log. or Lin.

Single, less switch, 15p
Single, D.P. switch, 24p
Tandem, less switch, 40p
5k Ω , 10k Ω , 25k Ω , 50k Ω , 100k Ω , 250k Ω , 500k Ω , 1M Ω , 2M Ω

RESISTORS

Carbon
All 5% high-stability, E12 values, 1W, 1p, 1W, 1p; 1W, 4p; 2W, 6p
Wire-wound
5W, 10p; 10W, 12p

ELECTROLYTICS

1 μ F	450V	19p	1,000 μ F	25V	27p
2 μ F	500V	20p	1,000 μ F	50V	39p
4 μ F	350V	14p	2,000 μ F	25V	36p
8 μ F	450V	16p	2,000 μ F	50V	53p
16 μ F	450V	17p	2,500 μ F	25V	45p
25 μ F	50V	8p	2,500 μ F	50V	60p
32 μ F	450V	24p	3,000 μ F	25V	44p
50 μ F	50V	10p	5,000 μ F	25V	53p
100 μ F	25V	10p	5,000 μ F	50V	98p
100 μ F	50V	10p	8-8 μ F	450V	18p
250 μ F	25V	12p	8-16 μ F	450V	20p
250 μ F	50V	17p	16-32 μ F	450V	27p
500 μ F	25V	18p	16-32 μ F	450V	63p
500 μ F	50V	25p	32-32 μ F	450V	49p
			50-50 μ F	350V	38p

MINIATURE ELECTROLYTICS

1 μ F	25V	10 μ F	64V
2 μ F	64V	16 μ F	40V
4 μ F	40V	25 μ F	25V
5 μ F	64V	30 μ F	15V
8 μ F	15V	50 μ F	15V
8 μ F	40V	100 μ F	15V
10 μ F	15V		

VARIABLE POWER SUPPLY

Input: 240V, a.c.
Output: Switched 3, 4-5, 6, 7-5, £4.20
9,12 volts d.c. at 500mA

NEW ILLUSTRATED 1972-73 CATALOGUE

Post Free 15p

VEROBOARD

Size	0-1 matrix	0-15 matrix
2 1/2in x 3 1/2in	22p	16p
2 1/2in x 5in	24p	25p
3 1/2in x 3 1/2in	24p	25p
3 1/2in x 5in	27p	29p
1 7/8in x 2 1/2in	75p	57p
1 7/8in x 3 1/2in	£1	75p

Pins—both sizes: packet of 36, 18p

ALUMINIUM BOXES with lids and screws

Type	Length	Width	Depth	Price
GB7*	2 1/2in	5 1/2in	1 1/2in	38p
GB8*	4in	4in	1 1/2in	38p
GB9*	4in	2 1/2in	1 1/2in	38p
GB10*	4in	5 1/2in	1 1/2in	44p
GB11	4in	2 1/2in	2in	38p
GB12	3in	2in	2in	33p
GB13	6in	4in	2in	52p
GB14	7in	5in	2 1/2in	63p
GB15	8in	6in	3in	81p
GB16	10in	7in	3in	92p

* These sizes fit standard Veroboards.

CASSETTE OWNERS!

For Philips and similar cassette recorders.
PU12 Power unit for connection to 12V + or - car electrical systems. £3.25
giving 7 1/2W, stabilised output.

PP75 Mains power supply, output 7 1/2V, d.c.
Both units are complete with cable and 5 pin D.I.N. plug. £1.95

BONDED ACRYLIC FIBRE

B.A.F. wadding, 1.8in wide, 1in thick. The ideal lining for speaker enclosures. 25p per yard.

LOW-OHM RESISTORS

2 1/2 watt wire-wound.
1 Ω , 1-8 Ω , 2-7 Ω , 3-3 Ω , 3-9 Ω , 4-7 Ω , 5-6 Ω , 6-8 Ω , 8-2 Ω

CAPACITORS

2.2pF	500V	SJM	7 1/2p	0.0027 μ F	500V	SJM	15p
3.3pF	500V	SJM	7 1/2p	0.003 μ F	500V	Cer.	5p
5pF	500V	SJM	7 1/2p	0.0033 μ F	125V	P.S.	6p
10pF	125V	P.S.	5p	0.0033 μ F	500V	Poly.	6p
10pF	500V	SJM	7 1/2p	0.0033 μ F	1,000V	MDC	6p
15pF	125V	P.S.	5p	0.0036 μ F	500V	SJM	15p
15pF	500V	SJM	7 1/2p	0.0047 μ F	125V	P.S.	9p
15pF	500V	Cer.	5p	0.0047 μ F	500V	Poly.	6p
18pF	500V	SJM	7 1/2p	0.0047 μ F	500V	SJM	20p
22pF	125V	P.S.	5p	0.0047 μ F	1,000V	MDC	6p
22pF	500V	SJM	7 1/2p	0.005 μ F	100V	Mylar	3p
25pF	500V	SJM	7 1/2p	0.005 μ F	500V	MDC	7p
27pF	500V	Cer.	4p	0.0063 μ F	125V	P.S.	10p
33pF	125V	P.S.	5p	0.0063 μ F	500V	SJM	30p
33pF	500V	SJM	7 1/2p	0.0063 μ F	500V	Poly.	6p
39pF	500V	SJM	7 1/2p	0.0082 μ F	125V	P.S.	10 1/2p
47pF	125V	P.S.	5p	0.0082 μ F	500V	SJM	30p
47pF	500V	Cer.	4p	0.01 μ F	18V	Disc	5p
50pF	500V	SJM	7 1/2p	0.01 μ F	125V	P.S.	10 1/2p
56pF	500V	SJM	7 1/2p	0.01 μ F	160V	Poly.	4p
68pF	125V	P.S.	5p	0.01 μ F	250V	M.F.	3p
68pF	500V	SJM	7 1/2p	0.01 μ F	400V	Poly.	5p
75pF	500V	SJM	7 1/2p	0.01 μ F	500V	Cer.	5p
82pF	500V	SJM	7 1/2p	0.01 μ F	500V	SJM	30p
100pF	125V	P.S.	5p	0.01 μ F	600V	MDC	7p
100pF	500V	SJM	7 1/2p	0.015 μ F	1,000V	MDC	9p
100pF	500V	Cer.	5p	0.015 μ F	160V	Poly.	3p
120pF	500V	SJM	7 1/2p	0.015 μ F	400V	Poly.	3p
150pF	125V	P.S.	5p	0.022 μ F	100V	Mylar	3p
150pF	500V	SJM	7 1/2p	0.022 μ F	18V	Disc	5p
180pF	500V	Cer.	5p	0.022 μ F	250V	M.F.	3p
200pF	500V	SJM	7 1/2p	0.022 μ F	400V	Poly.	3p
220pF	125V	P.S.	5p	0.022 μ F	600V	MDC	7 1/2p
220pF	500V	Cer.	5p	0.022 μ F	1,000V	MDC	9p
250pF	500V	SJM	8p	0.033 μ F	250V	M.F.	4p
270pF	500V	Cer.	5p	0.033 μ F	400V	Poly.	4p
300pF	500V	SJM	8p	0.047 μ F	12V	Disc	6p
330pF	125V	P.S.	5p	0.047 μ F	160V	Poly.	3p
330pF	500V	SJM	8p	0.047 μ F	250V	M.F.	3p
390pF	500V	SJM	8p	0.047 μ F	400V	Poly.	4p
470pF	125V	P.S.	5p	0.047 μ F	400V	MDC	10p
470pF	750V	Disc	5p	0.1 μ F	30V	Disc	6p
500pF	500V	SJM	8p	0.1 μ F	400V	Poly.	5p
560pF	500V	SJM	8p	0.1 μ F	400V	M.F.	4p
680pF	125V	P.S.	5p	0.1 μ F	600V	MDC	10p
680pF	500V	SJM	8p	0.1 μ F	1,000V	MDC	13p
820pF	500V	SJM	8p	0.15 μ F	250V	M.F.	5p
0.001 μ F	100V	Mylar	3p	0.22 μ F	160V	Poly.	6p
0.001 μ F	125V	P.S.	6p	0.22 μ F	250V	M.F.	5p
0.001 μ F	400V	Poly.	3p	0.22 μ F	400V	Foil	10p
0.001 μ F	500V	SJM	10p	0.22 μ F	1,000V	MDC	15p
0.001 μ F	500V	Cer.	5p	0.33 μ F	250V	M.F.	8p
0.001 μ F	1,000V	MDC	6p	0.47 μ F	250V	Foil	8p
0.0015 μ F	400V	Poly.	3p	0.47 μ F	400V	Foil	15p
0.0015 μ F	500V	SJM	10p	0.47 μ F	1,000V	MDC	20p
0.0015 μ F	500V	Cer.	5p	1.0 μ F	250V	M.F.	15p
0.0018 μ F	500V	SJM	10p				
0.002 μ F	100V	Mylar	3p				
0.002 μ F	500V	Cer.	5p				
0.0022 μ F	125V	P.S.	6p				
0.0022 μ F	500V	SJM	10p				
0.0022 μ F	1,000V	MDC	6p				

Note:
SJM—silver mica 1% tol.
P.S.—polystyrene 2 1/2% tol.
MDC—a.c. rating=300V.
M.F.—Mullard min. foil.
Cer.—ceramic.

PLUGS

Car aerial	14p
Co-axial	8p
D.I.N. 2 pin (speaker)	10p
D.I.N. 3 pin	13p
D.I.N. 4 pin	13p
D.I.N. 5 pin, 180°	13p
D.I.N. 5 pin, 240°	15p
D.I.N. 6 pin	13p
Jack, 2 1/2mm unscreened	9p
Jack, 2 1/2mm screened	10p
Jack, 3 1/2mm unscreened	8p
Jack, 3 1/2mm screened	12p
Jack, 4 1/2mm unscreened	12p
Jack, stereo, unscreened	20p
Jack, stereo, screened	35p
Phono, plastic top	3p
Phono, plated metal	12p
Phono, fitted 4ft lead	8p
Wander, red or black	3p
Banana 4mm, red or black	6p

SOCKETS

Car aerial	8p
Co-axial, surface	8p
Co-axial, flush	9p
O.I.N. 2 pin (speaker)	10p
D.I.N. 3 pin	10p
D.I.N. 3 pin, 180°	9p
D.I.N. 3 pin, 240°	9p
Jack, 2 1/2mm	10p
Jack, 3 1/2mm	10p
Jack, 4 1/2mm	10p
Jack, stereo, switched	17p
Phono, single	5p
Phono, 2 on a strip	7p
Phono, 3 on a strip	9p
Phono, 4 on a strip	10p
Wander, single, red or black	3p
Wander, twin strip	3p
Wander, 4 on a strip	6p

MAIL ORDERS: C.W.O. only. Please include 12p P. & P. (Overseas extra). S.A.E. with all enquiries please. Telephone 01-692 4412

DISCOUNTS UP TO

60% OFF ON BRANDED GOODS

ALL BRAND NEW
in manufacturer's sealed cartons.
GUARANTEED 12-MONTHS.

SPECIAL OFFER £17-95

Garrard SP25 Mk. III
Goldring G800
Teak pinth and tinted cover. All leads supplied.
Please add £1-25 for P. & P.

TURNTABLES

Please add 75p for P. & P.

Garrard SP25 Mk. III	£9-45
Garrard AF76	£18-75
Garrard SL65B	£12-95
Garrard 401	£26-50
Garrard Zero 100 (Auto)	£38-95
Garrard Zero 100 (Single)	£36-75
Garrard SL72B	£23-50
Garrard SL75B	£25-50
Garrard SL95B	£34-25
BSR MP60	£9-45
Goldring GL72	£21-95
Goldring GL72IP	£27-95
Goldring GL75	£25-75
Goldring GL75IP	£34-25
Wharfedale Linton & cart.	£27-25
Thorens TD125	£57-00
Thorens TD125AB	£88-50
Thorens TD150 Mk. II	£26-00
Thorens TD150A Mk. II	£33-25

AMPLIFIERS

Please add 75p P. & P.

Armstrad 8000 Mk. II	£16-25
Armstrad IC2000	£27-45
Armstrong 521 (teak cased)	£43-90
Alpha Highgate 212	£25-00
Alpha Highgate FA300	£27-95
Alpha Highgate FA400	£31-95
Leak Delta 30	£47-95
Leak Delta 70	£55-95
Metrosound ST20E	£24-50
Metrosound ST60	£45-95
Pioneer SA600	£58-00
Pioneer SA700	£66-50
Pioneer SA800	£73-95
Pioneer SA900	£92-00
Pioneer SA1000	£94-00
Rogers R/brook (Chassis)	£45-00
Rogers R/brook (Cased)	£37-00
Rogers R/bourne (Chassis)	£41-95
Rogers R/bourne (Cased)	£47-50
Sinclair PRO60 2 x 230/PZ5	£14-95
Sinclair PRO60 2 x 230/PZ6	£17-00
Sinclair PRO60 2 x Z50/PZ8/Trans	£21-25
Sinclair AFU (Filter Unit)	£4-40
Sinclair 605	£18-50
Sinclair 2000 Mk. II	£21-50
Sinclair 3000 Mk. II	£29-25
Wharfedale Linton	£37-50
Goodmans Max Amp	£37-95
Teleon 5AQ206B	£20-50
Teleon 5AQ306B	£22-50
Europhon 10 = 10	£16-95

All prices correct at time of press F & O.F.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE8) 774 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 - minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

TUNERS

Please add 75p P. & P.

Armstrong 253	£39-50
Armstrong 524	£30-95
Rogers Ravensbrook FET4 (Chassis)	£31-00
Rogers Ravensbrook FET4 (Cased)	£35-00
Rogers Ravensbourne FET4 (Chassis)	£43-00
Rogers Ravensbourne FET4 (Cased)	£48-00
Sinclair PRO60 (Module)	£17-95
Sinclair 2000/3000 Tuner	£32-75
Philips RH690	£33-00
Leak Delta FM (Cased)	£54-75
Leak Delta AM/FM (Cased)	£64-50

TUNER/AMPLIFIERS

Please add 75p for P. & P.

Alpha Highgate 150	£44-25
Armstrong 525 (Teak cased)	£67-95
Armstrong 526 AM/FM (Teak cased)	£77-75
Leak Delta 75	£127-95
Philips RH781	£50-00
Philips RH702	£82-50
Teleon 2100	£29-95
Goodmans One Ten	£99-50
Rogers R/brook (Teak)	£78-50
Rogers R/brook (Chassis)	£72-75

SPEAKERS

Please add £1-25 P. & P. per pair

Armstrad 138	£15-95
Wharfedale Denton 2	£28-40
Wharfedale Linton 2	£35-95
Wharfedale Melton 2	£47-45
Wharfedale Dovedale 3	£60-50
Celestion Dittion 120	£39-50
Celestion Dittion 15	£23-50
Celestion Dittion 25	£87-00
Goodmans Double Maxim	£48-25
Goodmans Mezzo 3	£44-95
Goodmans Magister	£74-00
Sinclair Q16	£12-50

£3-20*

Plus 35p p. & p. Finished in teak veneer with tinted dust cover fully assembled. For Garrard SP25, 2025TC, 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B; £4-20 plus 55p P. & P. Also finished in walnut to match Japanese equipment—at no extra.

CARTRIDGES

Please add 10p for P. & P.

Goldring G850	£3-45
Goldring G800	£5-95
Goldring G800E	£9-75
Goldring G800 Super E	£15-00
Shure M3D	£4-15
Shure M44E	£5-70
Shure M55E	£5-85
Shure M75E Type 2	£10-75
Sonotone 9TAHC	£1-43

C. R. HADLEY 24 WOODHILL, HARLOW, ESSEX.

Add 5p P. & P. Catalogue 5p stamp or free with order. All our stocks are brand new with money back GUARANTEE.

TRANSISTORS									
AC 107	15p	BC 108	8p	ME 0402	18p	OC 140	17p	2N 3705	12p
AC 126	13p	BC 109	8p	ME 0404	14p	OC 170	23p	40636	55p
AC 127	16p	BC 164	20p	ME 4101	10p	OC 171	23p		
AC 128	12p	BC 168	10p	ME 4102	12p	OC 200	25p	Rectifiers	
AC 176	22p	BC 169	11p	ME 8002	14p	OC 23	30p	1N 4001	5p
AC 141	16p	BC 148	10p	ME 6101	14p	OC 25	25p	1N 4002	5p
AC 142	16p	BC 149	10p	ME 6102	14p	OC 28	30p	1N 4003	6p
AC 141K	20p	BC 182L	8p	MP 8111	32p	OC 29	38p	1N 4004	8p
AC 142K	20p	BC 183L	8p	MP 8113	34p	OC 35	28p	1N 4005	11p
AD 142	39p	BC 184L	8p	MP 8511	84p	OC 36	38p	1N 4006	12p
AD 149	40p	BC 212L	8p	MP 8513	45p	2N 697	18p	1N 4007	13p
AD 150	44p	BC 213L	8p	OC 44	13p	2N 1177	24p	W065	30p
AD 140	40p	OC 214L	8p	OC 44	13p	2N 1304	25p	W02	35p
AD 161	m/p	BD 121	50p	OC 45	13p	2N 1305	28p	OA 90	8p
AD 162	56p	BD 123	60p	OC 71	13p	2N 2646	47p	OA 91	8p
AL 102	58p	BD 130	46p	OC 72	13p	2N 2926	51p	1N 4148	4p
AL 103	49p	BFY 50	18p	OC 81	13p	2N 3053	20p	400mW Zeners	
AL 103	53p	BFY 51	12p	OC 81D	18p	2N 3056	49p	3-3-30V	10p
AL 111	85p	BFY 82	12p	OC 83	20p	2N 3702	15p		
BC 107	8p	BSY 35A	15p	OC 139	13p	2N 3704	15p		

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0-01µF, 0-015µF, 0-022µF, 3p, 0-033µF, 0-047µF, 0-068µF, 3p, 0-1µF, 4p, 0-15µF, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 8p, 0-68µF, 11p, 1-0µF, 13p, 1-5µF, 20p, 2-2µF, 24p.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES 6p each. (µF/V) 10/2-5, 40/2-5, 80/2-5, 160/2-5, 320/2-5, 500/2-5, 80/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6-4/6-4, 8-4/6-4, 50/6-4, 100/6-4, 200/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2-5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1-6/25, 6-4/25, 12-5/25, 25/25, 50/25, 80/25, 114/25, 440/25, 8/40, 16/40, 32/40, 50/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64, 20/64, 32/64.

SILVERED MICRA. 500V d.c. 6p each
Values (PF): 2-2, 5, 8-2, 10, 12, 15, 18, 22, 24, 27, 30, 33, 35, 39, 47, 50, 56, 68, 75, 82, 100, 120, 150, 180, 200, 220, 250, 7p each.—270, 300, 330, 390, 400, 470, 500, 556, 680, 800, 10p each.—1000, 1500, 1800, 2200, 16p each.—2700, 3600, 20p each.—4700, 5000, 30p each.—5600, 6800, 8200, 10000.

RESISTORS
½ watt 10% carbon 1p each
½ watt 10% carbon 1p each
Range 2-2 ohms to 10 meg.
TR5 triple rated at ½ + ½ + ½ watt
tin oxide resistor ±2% 3p each.
Range 10 ohms-1 meg ohm.

SLIDE SWITCH
3 55T 10p each
3P Three Position 12p each

MINIATURE NEON LAMPS
240v or 110v 1-4 5p, 5 plus 44p each.

LINEAR IC's
709C 28p
709C DIL 28p
741C TO99 6p
741C DIL 36p

BARGAIN TTL's at 15p each
7400, 7401, 7402, 7403, 7404, 7410, 7420, 7430, 7440, 7450, 7451, 7453, 7454.
35p each:
7442, 7470, 7472, 7473, 7474, 7476, 7485.

— AND LOTS MORE —

SOUND BARGAINS



BEST OF ALL WORLDS
VHF, FM, AM, AFC, AIR BAND, PUBLIC SERVICE BANDS, WEATHER BANDS.

GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER
WITH 8 IN 1 A.C./D.C. POWER SUPPLY SYSTEM
MANS, BATTERY AND BUILT-IN BATTERY BOOSTER

OUR PRICE £10-50
+40p P. & P.

THIS NEW 1978 RADIO. No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop, Prizes, Taxicabs, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHER-BAND. Frequency ranges: MW540-1600 KHZ, PM88-138MHz, Airband 108-145 MHz, VHF 145-176MHz, 23 semi-conductors—12 transistors. 11 diodes and the automatic frequency control. 31° telescopic aerial. Runs off mains AC 230/250 volts or off 4 U2 batteries, or use re-chargable nickel alkal cell. Finished in strong leather grained case with carrying handle. Approx. size 10½" x 6½" x 3½". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries FREE. HURRY! Limited quantity only from Marktyme. Money back guarantee.



OUR PRICE £28-95
+50p P. & P.

Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; 14 resistors. Integral ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350Kc. Medium 453-1800Kc. Marine 1-6-45Mcs. Short Wave 12-24Mcs. VHF/VHF 88-108Mcs. Aircraft 108-135 Mcs. PUBLIC SERVICE BANDS 135-174Mcs. Fully guaranteed.

MARKTYME (Dept. ED1), 372 EDGWARE ROAD, LONDON, W.3. Tel. 01-723 0694.
Callers welcome Monday to Saturday 9 a.m.-6 p.m.



CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price £1.70

CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price £1.70

G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price £1.83.




CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety: fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. Price £1.80

CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price £1.95



E.240 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price £1.80.

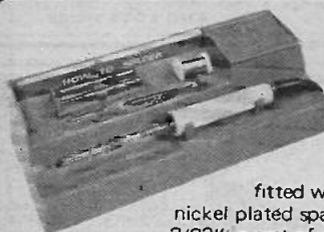ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price £1.83



SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price £2.75



SK.2 SOLDERING KIT

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price
£2.40.



MES.12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price £1.95.

sign here

to answer all your soldering problems

I enclose cheque/P.O./Cash
(Giro No. 2581000)

Name _____
Address _____

E.E. 6

Please send the Antex
colour catalogue.

Please send the following:



from electrical, radio or car accessory
shops or from **Antex Ltd.,** Freepost
(no stamp required) **Plymouth**
PL1 1BR Telephone 0752 67377/8

BI-PRE-PAK



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 50p

COMPLETE TELEPHONES

EX-G.P.O. NORMAL HOUSEHOLD TYPE



95p EACH
P. & P. 35p each.

TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V. 0-5 to 2mA.	50p
B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weights	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H28	20	OC200/1213 PNP Silicon uncodded TO-5 can	50p
H30	20	1 Watt Zener Diodes. Mixed Voltages 5.8 - 43V.	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types.	50p

UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. class type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200; OA202	50p
B86	50	Sil. Diodes sub. min. 1N914 and 1N916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/12N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		6p	
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-20	2G303	0-13
ACV17	0-20	2G303	0-13
AF239	0-30	2N711	0-50
AF196	0-20	2N1302-3	0-15
AF139	0-30	2N1304-5	0-17
BC154	0-10	2N1306-7	0-20
BC107	0-20	2N1308-9	0-22
BC108	0-10	2N3819FET	0-45
BC109	0-10		
BF194	0-15	Power Transistors	
BF274	0-20	OC20	0-30
BFY50	0-15	OC23	0-30
BSY25	0-13	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-10	AD149	0-30
OC41	0-15	AUY10	1-25
OC44	0-13	25034	0-25
OC45	0-10	2N3055	0-50
OC71	0-10	Diodes	
OC72	0-10	AA142	0-10
OC81	0-13	CA95	0-07
OC81D	0-13	OA79	0-07
OC83	0-18	OA81	0-07
OC139	0-13	IN914	0-06
OC140	0-15		

F.E.T. PRICE BREAKTHROUGH !!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3B23E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/B, BSY26-29, BSY95A, BCY70, etc. £4.25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4.25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4.50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4.25 per 500; £8 per 1,000.

OC44, OC35 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3B23E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:

1N4001, 500+ at 4p each; 1,000+ at 3p each.
1N4004, 500+ at 5p each; 1,000+ at 4p each.
1N4006, 500+ at 6p each; 1,000+ at 5p each.
1N4007, 500+ at 8p each; 1,000+ at 7p each.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

8 RELAYS FOR VARIOUS TYPES P & P 25p £1

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500, valves. As removed from colour receivers at the factory.

NOW ONLY 50p each post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested			
Unmarked	5p	5p	4p
Matched Sets 1-OC45 and 2-OC45's. Per Set.	25p	20p	15p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

5L403D Audio Amp., 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	25p	20p	15p
Gates, Factory Marked and Tested by A.E.I.	10p	9p	8p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	20p	18p	15p
SN7490 Decade Counter	50p	45p	40p
UL914 Dual 2 1/2 Gate	40p	35p	30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each

16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines: B.P.I Transistor Equivalents and Substitutes;

This includes many thousands of British U.S.A., European and C.V. equivalents. The Iliffe Radio Valve & Transistor Data Book 9th Edition; Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. E 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

BUDGET HIGH-FIDELITY STEREO SYSTEMS



FREE
LEADS
AND PLUGS
SUPPLIED
WITH ALL
SYSTEMS

PREMIER STEREO SYSTEM "ONE" Consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo/mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off, Mono/Stereo switch, Stereo Headphone socket. Black leatherette cabinet with aluminium front panel. Size: 12 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ ". (Amplifier available separately if required £15.00. Carr. 50p).

PREMIER STEREO SYSTEM "TWO", as above but with Garrard SP25 MK III and magnetic cartridge. **ONLY £45.** Carr. £1.75.

ONLY
£40-95
carr. £1.75



METER BARGAINS

MODEL GT-800 MULTIMETER
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 10, 50, 250, 1,000V (1,000 ohm/V). AC Voltages: 10, 50, 250, 1,000V (1,000 ohm/V). DC Current: 1mA, 100mA. Resistance: 0-150K ohms. Decibel: —10 to +29.1b (at AC 10V range) £2.47. P. & P. 25p.



MULTIMETER 20,000 O.P.V.
Features large easy-to-read meter, wide choice of ranges. With test leads, battery and manual. Size 4 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " x 1". RANGES D.C. Voltages 0-5-25-50-250-500-2500V. A.C. Voltages 0-15-50-100-500-1000V. D.C. Current: 0-50 μ A-2.5mA-250mA. Resistance: 0-8000 ohms 0-6 megohms (300 ohms and 30 Kohms, at centre scale). Capacity: 10 μ F to 0.01 μ F, 0.01 μ F to 1 μ F. Decibels —20 to +22dB. £4.90. P. & P. 25p.



MODEL CT-620 MULTITESTER
RANGES—DC Voltages: 0, 5, 25, 100, 500, 1,000V (20,000 ohms/V). AC Voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). DC Current: 0, 50 μ A, 0, 5, 50, 500mA. Resistance: 0, 6K, 600K, 6M, 60M ohms. Decibels: —20 db to +62 db in 5 ranges. £5.62. P. & P. 25p.



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 160/140 °C. P. & P. watt. 240 volt A.C. **£3.95** 50p



"Markeman" Soldering Iron. Lightweight, pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. £1.50 P. & P. 10p

VERITAS V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds. **£1.72** P. & P. 15p.

"VERITONE" RECORDING TAPE


SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSURED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped attractively boxed.

LP3 3" 250'	P.V.C.	28p	LP8 5 $\frac{1}{2}$ " 1200'	ACETATE	75p
TT3 3" 450'	POLYESTER	87p	DT6 5 $\frac{1}{2}$ " 1800'	POLYESTER	£1.18
DT3 3 $\frac{1}{2}$ " 600'	POLYESTER	87p	TT6 5 $\frac{1}{2}$ " 2400'	POLYESTER	£1.87
SP5 5" 600'	P.V.C.	42p	8P7 7" 1200'	P.V.C.	62p
LP6 6" 900'	ACETATE	50p	LF7 7" 1800'	ACETATE	75p
DT6 5" 1200'	POLYESTER	75p	DT7 7" 2400'	POLYESTER	£1.25
			TT7 7" 3600'	POLYESTER	£2.50

TAPE SPOOLS 8" 5p, 5", 6 $\frac{1}{2}$ ", 7" 9p.
Post and Packing 3" 5p, 5 $\frac{1}{2}$ ", 6 $\frac{1}{2}$ ", 7" 10p (3 reels and over Post Free).

PREMIER HI-FI OFFERS

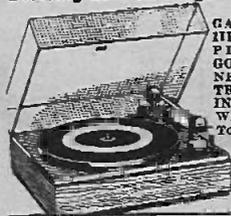- Rogers Ravensbrook II Stereo Amplifier teak **£38.50**
- Rogers Ravensbourne Stereo Amplifier teak **£49.00**
- Metrosound ST20E Stereo Amplifier teak **£25.50**
- Golding GL72 less cartridge **£22.00**
- Garrard SP25 III with Goldring G800 cartridge **£15.00**



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE COMPLETE IN TEAK PLINTH WITH COVER. Total list price over £34.

PREMIER PRICE **£18.50** P. & P. 50p.

Garrard AP76 with G800, ready wired to 5 pin Din in plinth with cover **£29.50**

Garrard AP76 less cartridge **£18.80**

Garrard 401 Transcription Unit List £40.15) **£27.40**


Garrard 2025 T/C with Stereo Ceramic Cartridge **£8.50**
Garrard 2025 T/C with Stereo Ceramic Cartridge ready wired in teak plinth with cover **£12.45**

Carriage and Insurance 60p extra any item.

CARTRIDGE BARGAINS!
Golding G800M £5.00; G800 £5.50; G800E £9.50; SHURE M3D £4.00; M44E £5.75; M55E £6.50; MYSEII £10.90. P. & P. 10p



PREMIER 800 STEREO AMPLIFIER

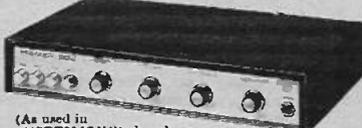

(As used in SYSTEM "ONE" above)
A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ ".

ONLY £15.00 Carr. 50p.
Mk. II Version available with Teak Finish Cabinet. £16.25. Carr. 50p.



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 $\frac{1}{2}$ in. speaker units with soft padded ear muffs. Adjustable headband. 1 ohms impedance. Complete with 6ft lead and stereo jack plug. **£2.47** P. & P. 25p.

STEREO STETHOSCOPE SET Low imp. £1.25 P. & P. 10p
MONO STETHOSCOPE SET Low imp. 53p. P. & P. 10p



E.M.I. 13 x 8in. HI-FI SPEAKERS

Fitted two 2 $\frac{1}{2}$ in. tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new. **£3.47** P. & P. 50p



VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 db. Standard jack plug socket inputs, phono plugs output. Attractive teak wood grain finish case. **MONO MODEL £3** **STEREO MODEL £3.47** P. & P. 15p



TAPE CASSETTES

C60 (60 min.)	29p	3 for 81p
C90 (90 min.)	40p	3 for £1.11
C120 (120 min.)	52p	3 for £1.40

P. & P. 10p.

FREE Cassette Head Cleaner with every 10 cassettes

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



A fascinating foundation for your child's future...

In Radio & Electronics with



Radionic Construction Kits



**NO SOLDERING
BATTERY OPERATED**

A teenager will enjoy many exciting hours constructing experiments with his Radionic Kit.

Not only is it entertaining and absorbing but the knowledge gained of the principles of electronics is invaluable in helping with general studies for higher education.

So simple and practical to use—and there is no soldering whatsoever.

You couldn't choose a better gift for any occasion—or why not just buy one anyway?

Radionic Products Limited

St. Lawrence House, Broad Street,
Bristol BS1 2HF Tel: 0272 25351

A member of the ESL BRISTOL Group of Companies

PHILIPS

Please send me literature on Radionic radio and electronics construction kits

NAME _____

ADDRESS _____

EE

gspk (sales)

quite simply—the best

RESISTORS

FULL RANGE OF ISKRA CARBON FILM RESISTORS

1/8 W (range 4.7 ohms to 470K) 1p each
1 W and 1/2 W (range 4.7 ohms to 10 Megs) 1p each
1 W (range 4.7 ohms to 10 Meg) 2p each
2 W (range 4.7 ohms to 10 Meg) 3p each

ISKRA MINIATURE HIGH STABILITY CARBON FILM RESISTORS WITH NEGLIGIBLE NOISE FACTOR.

All Resistors $\pm 5\%$ (except values over 4.7 Meg). These Resistors are even lower in price than most 10% and older carbon composition types.

PRE-SET POTENTIOMETERS

Standard values of pre-sets from 100 ohms to 5 Meg. Standard/miniature 7p each Sub-miniature 5p each

SIEMENS PROFESSIONAL CAPACITORS

POLYCARBONATE AND POLYESTER ELECTROLYTIC

Voltage	Capacitance	Price	Voltage	Capacitance	Price
100v	0.1 μ F	6p	10v	22 μ F	7p
100v	0.15 μ F	6p	10v	47 μ F	11p
100v	0.22 μ F	6p	16v	47 μ F	7p
100v	0.33 μ F	9p	25v	10 μ F	7p
100v	0.47 μ F	16p	25v	100 μ F	9p
100v	0.68 μ F	15p	33v	220 μ F	11p
250v	0.01 μ F	5p	25v	170 μ F	14p
250v	0.015 μ F	5p	25v	1000 μ F	22p
250v	0.022 μ F	5p	25v	2200 μ F	42p
250v	0.033 μ F	6p	35v	4.7 μ F	7p
250v	0.047 μ F	6p	35v	220 μ F	14p
250v	0.068 μ F	6p	100v	10 μ F	8p
250v	0.1 μ F	6p	100v	22 μ F	9p
			100v	47 μ F	14p

SPECIAL INTRODUCTORY OFFER

FREE with all orders value £5 or over we will give absolutely free one GSPK P.C. Kit for making your own printed circuits (normal retail price £1.95). Hurry! Offer valid for limited period only.



SEMICONDUCTORS

Here are just a few examples of our LOW Semiconductor prices. Many more semiconductors available all at equally sensational prices... NOW.

AC127	24p	22p	BZY88C	1+	25+	OC76	+1	25+
AC128	15p	16p	Series E12			OC170	23p	21p
AC176	15p	13p	(2.7V-30.0V)	10p	8p	1N4001	6p	5p
ACV18	18p	15p	NKT210	24p	19p	1N4002	6p	5p
AD161	27p	25p	NKT211	24p	19p	1N4003	7p	6p
AD162	27p	25p	NKT212	24p	19p	1N4004	8p	7p
AF139	28p	28p	NKT213	24p	19p	1N4005	10p	9p
BC107	8p	8p	NKT214	19p	17p	1N4006	12p	11p
BC108	8p	7p	NKT218	24p	19p	1N4007	16p	16p
BC109	9p	8p	NKT219	24p	19p	1N4148	4p	3p
BC147	8p	7p	NKT223	26p	20p	2N1302	16p	16p
BC148	8p	7p	NKT224	21p	19p	2N1304	21p	20p
BC149	8p	7p	NKT242	14p	12p	2N1613	14p	13p
BC170	14p	13p	NKT243	81p	77p	2N1711	15p	14p
BCV71	20p	19p	NKT401	70p	58p	2N2904	29p	28p
BCV72	14p	12p	NKT402	75p	59p	2N2905	24p	23p
BDY20	81p	73p	NKT403	64p	50p	2N2906	19p	18p
BFX29	24p	23p	NKT453	41p	33p	2N2907	22p	21p
BFX30	24p	23p	OA47	6p	5p	2N3053	17p	16p
BFX50	18p	15p	OA79	6p	5p	2N3054	49p	47p
BFX51	18p	17p	OA90	5p	4p	2N3055	57p	52p
BFX52	19p	18p	OC70	12p	12p	(BD130)		

NUMEROUS OTHER ITEMS AVAILABLE INCLUDE :

Switches Comprehensive range of N.E.F. Toggle switches and Rotary Wafers switch kits (to enable you to make your own switch to your own specification). Copper laminates and all materials available to make your own printed circuit boards. Lamps and lampholders for every requirement. Ready Built Circuits and Modules. Freezer and Cleaner aerosol sprays. Jack Plugs and sockets. Variety of speciality products.

All orders value £2 or over post free. Other orders please add 10p p & p. We only sell new products—do not confuse with 'seconds' or surplus stock. Because of our keen prices we regret the prices apply to U.K. and B.F.P.O. addresses only. Please fill in the coupon and send with 10p (refundable on ordering) for catalogue.

ALL CALLERS WELCOME
To GSPK (SALES) LIMITED, Dept. E.E.
Head Office, Hookstone Park, Harrogate, Yorkshire,
HG2 7BU.

MON.

TU.

FRI.


9-5.00

Name _____

Address _____

E.E.

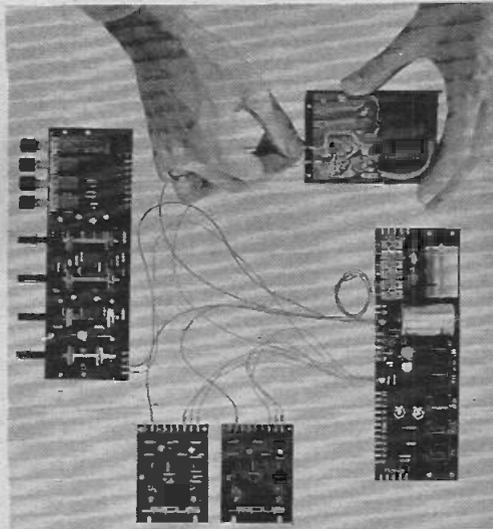Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same - there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative - Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one - Masterlink - which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together - the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

Guarantee If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

sinclair

Sinclair Radionics Ltd., London Road.,
St. Ives, Huntingdonshire PE17 4HJ.
Telephone: St. Ives (04806) 4311

Specifications

Output - 30 watts music power (10 watts per channel R.M.S. into 3Ω)

Inputs - Mag. P.U. - 3mV correct to R.I.A.A. curve 20-25,000 Hz ± 1dB. Ceramic pick-up - 50mV. Radio - 50 to 150mV. [Aux. adjustable between 3mV, and 3V.

Signal to noise ratio - Better than 70dB.

Distortion - better than 0.2% under all conditions.

Controls - Press buttons for on-off, P.U., radio and aux. Treble +15 to -15 dB at 10 kHz. Bass +15 to -15 dB at 100 Hz.

Volume, Stereo Balance.

Channel matching within 1dB.

Front panel - brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

£29.95

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ

Please send Project 605 post free Details and list of stockists

Name

Address

for which I enclose £29.95 cheque/money order/cash.

E.E.T.B

everyday electronics

PROJECTS....
THEORY.....

GETTING FAMILIAR

It is our aim to dispel the mystique of electronics.

One of the very first steps the beginner must take is to become fully acquainted with the symbols used in circuit diagrams. He must also familiarise himself as soon as possible with the more commonly used components—their general physical form and any peculiar or distinguishing features.

We make this point deliberately, knowing that numerous people are now becoming attracted to electronics for the first time. It is probable that the majority of such new recruits will not previously have handled or even seen at close quarters a resistor, capacitor, or transistor—the very stuff electronics is made of. To ease the task of familiarisation we have planned a *Guide to Circuit Symbols* and the first part appears this month.

SYMBOLIC AND REAL

In this guide, the symbol is shown with an outline drawing of a typical component of that class, so aiding rapid identification of the actual part. Included against each symbol is its Circuit Reference. This provides a link between the theoretical circuit diagram and the practical component layout and wiring diagrams which are included in all our constructional articles. Also, this reference is a convenient "shorthand" label for use in the accompanying text and, of course, in the components list.

Our July issue will be published on Friday, June 16

NO MALE MONOPOLY


Our slogan is electronics . . . for everyone.

Electronics is not entirely a man's world. As we had suspected, this hobby has its keen followers amongst members of the fair sex. This month we are pleased to include letters from two lady enthusiasts who responded to our appeal a couple of months ago. By this token there must be a number of other electronic Eves who are reluctant or too shy to reveal themselves.

To exploit electronics in and around the home—for everyone's benefit—we look particularly to the womenfolk to suggest some new applications. The man of the house may believe he knows all the answers, but the housewife must often encounter situations that her mate is oblivious of. Some of these give rise to problems or needs that could perhaps be solved or satisfied by some simple electronic gadget.

HOUSEWIFE'S CHOICE

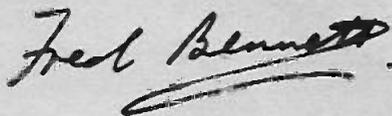So think about it all you lady readers, and let us have your suggestions. All will be carefully investigated and those capable of being carried out efficiently and effectively by relatively simple electronics will, it is hoped, be presented in due course as constructional projects in this magazine.



EDITOR F. E. BENNETT • M. KENWARD • B. W. TERRELL B.Sc.

ART EDITOR J. D. POUNTNEY • P. A. LOATES • S. W. R. LLOYD


ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Subscription Rates including postage for one year, to any part of the world, £2.35.

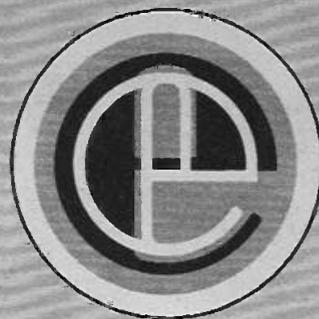Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



..EASY TO CONSTRUCT
..SIMPLY EXPLAINED

VOL. 1 NO. 8

JUNE 1972

CONSTRUCTIONAL PROJECTS

- SIMPLE MULTIMETER** For all constructors and beginners by Mike Hughes 414
LIGHT TO SOUND CONVERTER Simple experimental project by Gerry Brown 423
WASH WIPE CONTROLLER Automatic windscreen washing for most cars by D. G. Howells 437

GENERAL FEATURES

- EDITORIAL** 412
JOURNEY TO JUPITER Man's first venture to the outer reaches of the solar system by David Stefan 418
BRIGHT IDEAS A readers' constructional hint 422
RUMINATIONS by Sensor 422
PLEASE TAKE NOTE 426
GUIDE TO CIRCUIT SYMBOLS Part 1, Identification of symbols and components 427
TEACH-IN Part 8—Multivibrators by Mike Hughes 430
SHOP TALK Component buying by Mike Kenward 436
THEY MADE THEIR MARK No. 2—Volta by J. E. Gregory 445
READERS LETTERS Comment and criticism from you 446, 449

**Sorry—but no
back numbers**

The publishers regret to advise readers that copies of past issues are no longer available. Nor will they be able to supply back-numbers in the future.

Sorry about this—but to avoid possible disappointment we can only urge our readers to place a regular order with their normal supplier; or alternatively to take out an annual subscription (for details see foot of facing page).

EVEN though you may be a beginner you are sure to need an instrument to measure voltages. Sometimes the most simple circuit will not work first time—this is usually caused by a wiring error. A few quick checks on voltage levels frequently solves the problem; even if it was simply that the battery was flat!

The instrument to be described can be made by the absolute beginner and is capable of measuring most of the usual levels one is likely to encounter. You can make several versions of the meter depending on the quality you want and the amount you can afford.

This article will detail construction of the cheapest version but it is straightforward to follow the data given and make a better quality version. Variables are: (a) size of meter (b) sensitivity—ohms per volt (c) accuracy of reading to be expected.

Those who want to make the meter for odd jobs about the house or on the car are advised to make the cheap version but those who really want to use the instrument to measure “electronic” levels should preferably go for the higher sensitivity and best accuracy.

RANGES

Construction has been kept as simple as possible—using sockets to select ranges instead

Simple Multimeter

By Mike Hughes

A basic design for
beginners and constructors

Components....

Resistors

R1	10k Ω
R2	10k Ω
R3	100k Ω
R4	100k Ω
R5	1M Ω
R6	47k Ω
R7	470k Ω
R8	2.2k Ω

All $\pm 1\%$ or $2\% \frac{1}{2}W$ high stability. See Table 1 for alternative sensitivity values.

Variable Resistor

VR1 2k Ω or 2.5k Ω linear carbon or wirewound

Diodes

D1	1N 4006
D2	1N 4001

Meter

500 μA f.s.d. moving coil meter SEW type MR52P. See Table 1 for alternative types.

Miscellaneous

B1 1.5V HP7 battery and holder (Eagle type—see text)

SK1-SK9 Wander plug sockets 9 off (colours as required).

Battery connector, suitable metal or plastic case—see text. Wander plugs, wire and test probes for test leads (one black, one red set of each). 22 s.w.g. tinned copper wire for connections.

SEE
**SHOP
TALK**



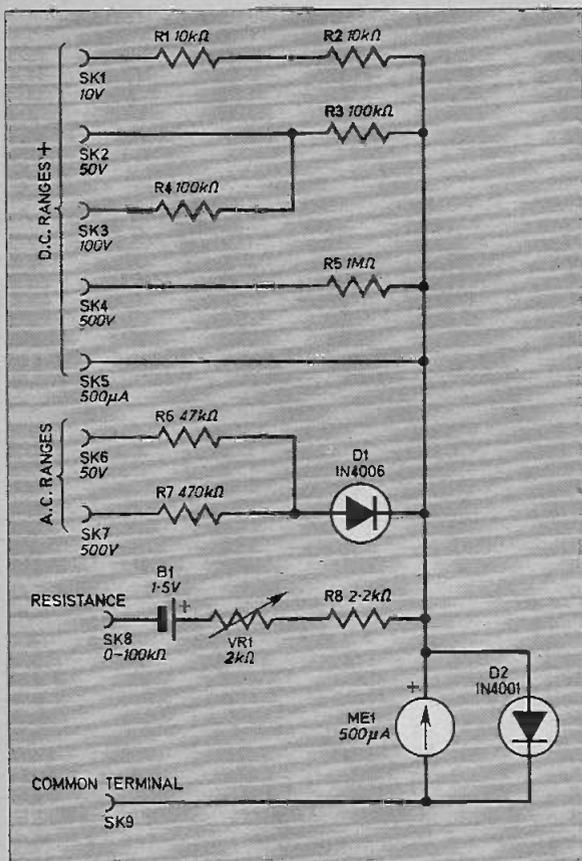


Fig. 1. Circuit diagram of the complete multi-meter using the $500\mu\text{A}$ meter movement. For the more sensitive design Table 1 gives alternative resistor values.

of the usual switch; this is at the expense of more ranges and the ability to measure currents—other than that given by the basic meter movement. Ranges are; d.c. volts 10V, 50V, 100V, 500V; a.c. volts 50V, 500V; d.c. current—basic meter movement ($500\mu\text{A}$ or $50\mu\text{A}$); resistance 0-100 kilohms. Sensitivity of the cheaper unit is 2,000 ohms per volt and the better quality version 20,000 ohms per volt.

The values of components shown in Fig. 1 are for the cheaper unit; see Table 1 for alternative values for higher sensitivity. For either unit it is not possible to obtain a preferred value resistor for the 10V and 100V ranges so use is made of two resistors in series to make up the correct value. One of the series resistors for the 100V range (R5) is used to provide a 50V input.

The a.c. ranges use a single diode giving half wave rectification—this is not conventional but helps simplify construction. You should not expect absolute accuracy when measuring a.c. because the meter will be measuring an approximate root mean square value the precise display of which will depend to some extent on the mechanics of the movement itself; nevertheless it is sufficiently accurate for checking the approximate level of mains voltage and transformer output voltage.

Resistors R1 to R5 are series connected for d.c. voltage ranges, R6 and R7 likewise for a.c. Full scale deflection for zero ohms is effected by R8 and VR1. Diode D2 is a silicon device and prevents the potential difference across the meter exceeding 600mV hence affording some degree of protection.

ACCURACY

Ultimate accuracy depends on the tolerances of resistors selected. For those requiring the best make sure that 1 per cent tolerance devices are used. To cut costs you can use 2 per cent, 5 per cent or even 10 per cent resistors, but remember the reading will only be as accurate as the resistors used.

The size of the meter movement will have an indirect bearing on the accuracy—the larger the meter the easier it is to read. The actual physical size used will not change the values of any of the components. The approximate cost of components given for the meter is based on the cheapest design using ± 2 per cent resistors.

Remember that the diode you use for D1 must be capable of withstanding the peak reverse voltage of the supply you are measuring (for 500 volts r.m.s. (root mean square) this would be 750V). The prototype uses an 800V device for both a.c. ranges—a 1N4006.

CONSTRUCTION

The prototype meter is housed in a commercial case measuring $6\frac{1}{2} \times 4 \times 4$ inches. The smallest case size would be approximately $6\frac{1}{2} \times 4 \times 2$ inches, and if a larger size meter is used

Approximate cost of components
£3.75 including leads, less case



Simple Multimeter

Photograph showing front panel designations.

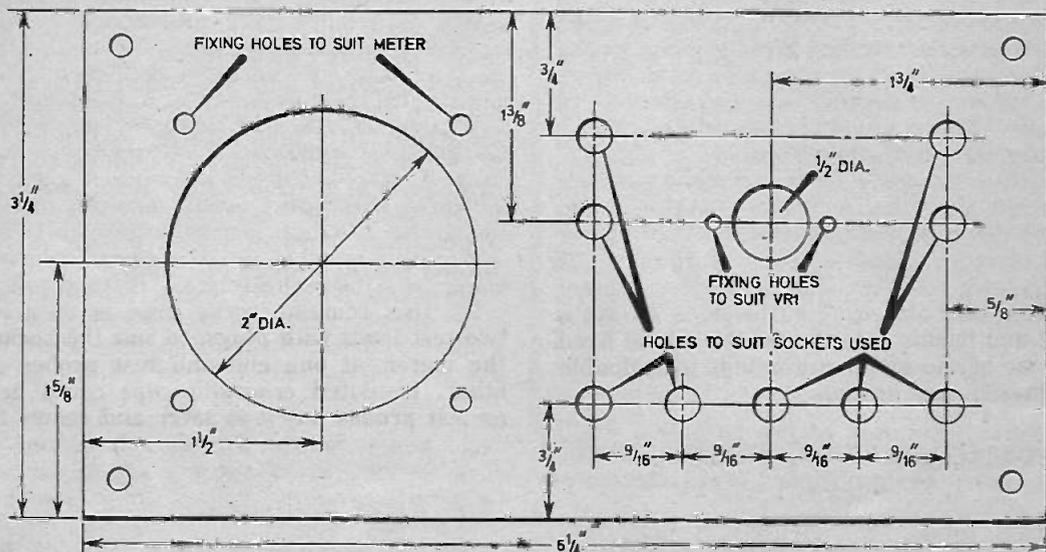


Fig. 2. Layout and drilling details of the Multimeter front panel. A larger panel would be required for larger type meters.

FRONT PANEL

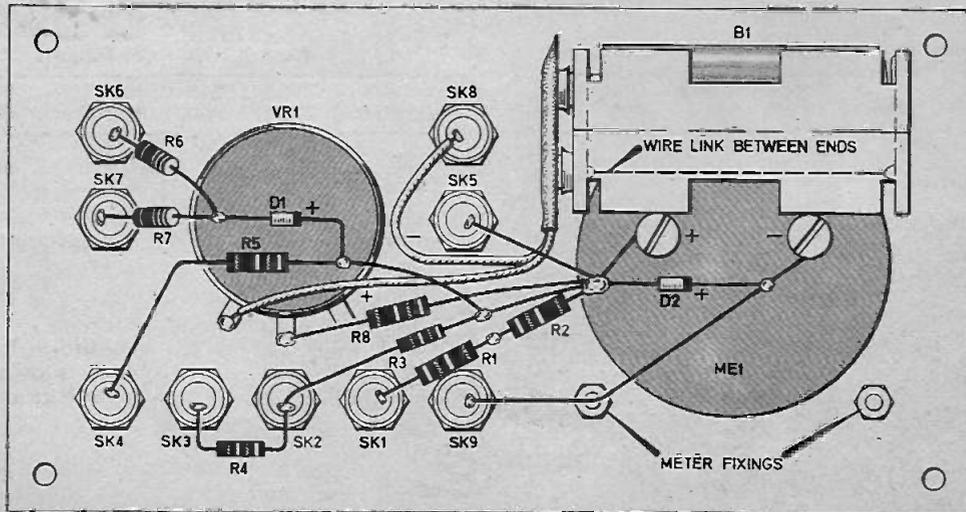


Fig. 3. Layout and wiring of the complete Multimeter. Note the wire link on the battery holder.

this case size would need to be increased. The case can be any suitable plastic or metal type. Construction enables all the wiring to be supported on the front panel, the drilling details for this panel are shown in Fig. 2. Very few flying leads are used as the resistor leads are—on the whole—long enough to go from point to point, see Fig. 3.

The wires may be sleeved if required but this is not essential as the wiring is fairly robust and provided care is taken during assembly to keep a sensible distance between wires there should be no problem with short circuits. When connecting D1 in series with the respective resistors cut the lead of each to about half an inch, lay these leads side by side giving an overlap and quickly solder them together then solder the other ends of the resistors to their respective sockets keeping them as close to the sockets as possible. The sockets can be of different colours to provide easy identification of the ranges. The front cover illustration shows the colours used in the prototype.

Alternative makes of moving-coil meter can be used but the drilling layout may vary. The 1.5V pen torch cell is held in a plastic battery holder. As only one cell is used, the connections for the second cell (in this particular holder) are shorted out. Mounting batteries is always a problem and in this case the holder can be fixed to the rear of the meter movement with double sided adhesive tape or glue.

CALIBRATION

Calibration is quite straightforward. There is no need to have a standard instrument or standard cell provided you are confident in the meter movement purchased and that all the resistors were bought new.

If one of the specified movements is used carefully remove the front cover and by undoing the two small screws remove the dial. Take a wooden cocktail stick; moisten one end and "fluff" it up into a stiff brush then using this brush with a small amount of household abrasive powder and water you can work on the silk screened lettering until it is removed.

Remove all numbers and lettering but leave the scale untouched. Using a compass you can draw in the extra concentric arcs for the different scales and then mark in the designations and calibrations as shown in the photograph opposite. Use Letraset for the printing; colour can be added with water colour or felt tip pens if required.

The resistance scale is calibrated at a few points by trial with a few known 1 per cent resistors. Sockets SK8 and SK9 should be shorted together and VR1 adjusted to give a full scale reading before measuring any resistance values.

You can check calibration of the 10V scale using a new multitap 9V battery but remember that a new battery will read slightly high. Provided this scale reads correctly the other scales should automatically do so.


The front panel of the meter can be designated using Letraset as shown in the photographs.

All that remains to be done is to make up two test leads with plugs, to suit the sockets on the meter, at one end and test probes at the other. Insulated crocodile clips could be used as test probes but it is safer and easier to buy some proper insulated probes. Insulated probes of some kind must always be used where high voltages are employed e.g. on mains powered equipment.


The test leads should be red and black for easy polarity observation—the black lead will always be used in the common socket SK9. ▣

Table 1. RESISTANCE VALUES AND METER TYPES FOR DIFFERENT SENSITIVITIES

Sensitivity	MEI (SEW Meter Type)										
	R1	R2	R3	R4	R5	R6	R7	R8	VR1	MR52P 2 $\frac{3}{8}$ "	MR65P 3 $\frac{3}{8}$ "
2,000 Ω /V	10k Ω	10k Ω	100k Ω	100k Ω	1M Ω	47k Ω	470k Ω	2.2k Ω	2k Ω	500 μ A	500 μ A
20,000 Ω /V	100k Ω	100k Ω	1M Ω	1M Ω	10M Ω	470k Ω	4.7M Ω	22k Ω	20k Ω	50 μ A	50 μ A

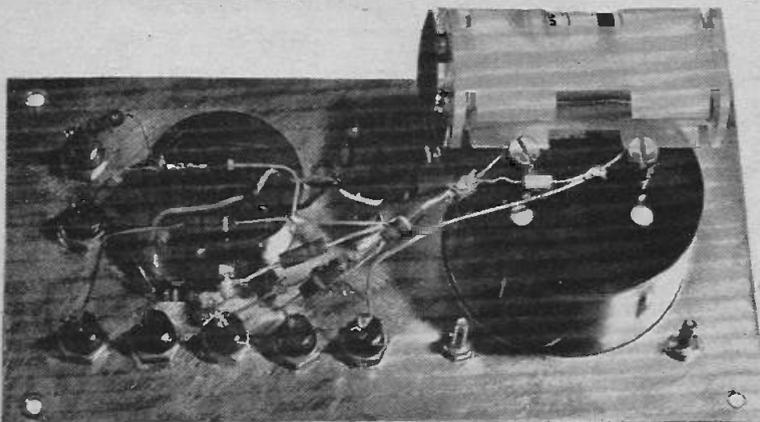

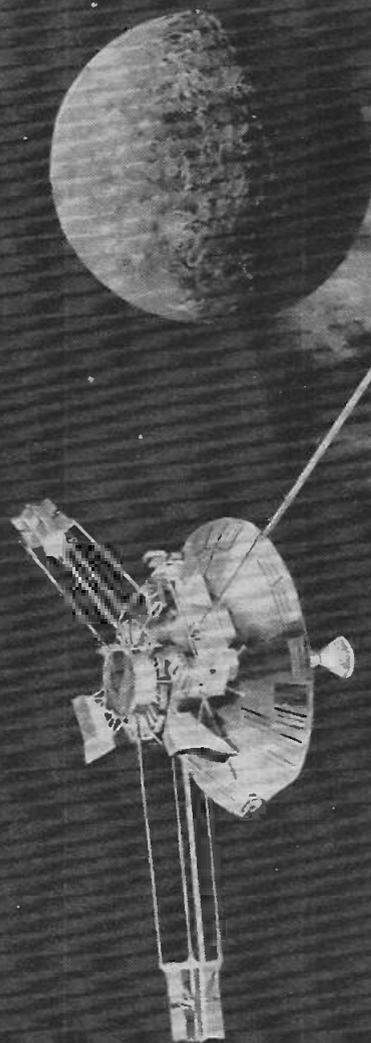Photograph of the complete multimeter showing the construction.



Journey to Jupiter

by David Stefan

AFTER 15 years of space exploration, the world has just embarked on its first-ever venture to the outer reaches of the solar system. America's unmanned research spacecraft, Pioneer 10, which was launched from Cape Kennedy on March 3, is now settling down to a 620 million mile journey to the giant planet Jupiter.

The voyage will last for nearly two years and is expected to set a number of new records, particularly in the field of space communications. There will be hazards too; to accomplish its main task of providing scientists with the first close-up look at Jupiter, Pioneer 10 has to penetrate the 150 million-mile-wide asteroid belt beyond the orbit of Mars, where 50,000 bodies more than a

mile in diameter, as well as countless bits of space rock, circle the sun.

If it manages to avoid all these obstacles it will spend four days collecting information as it flies past Jupiter at a distance of 100,000 miles. But that will not be the end of this ambitious mission. Providing all systems are still "go", Pioneer 10 will continue to speed away from earth, eventually becoming the first spacecraft to escape completely from the solar system.

COMMUNICATIONS

The success of the Pioneer mission will hinge on the craft's ability to transmit its data back to earth. Jupiter is so far away that radio messages moving at the speed of light will take 45 minutes

in each direction and this fact alone will demand planned command operations. Pioneer has been designed so that it can store five commands, but as it nears its target it will be controlled by frequent instructions from earth.

The spacecraft's communications system, incorporating the "travelling wave-tube" amplifier, transmits with an 8-watt signal to the 210 ft. dish antennas of NASA's deep space network. But because of the distance involved, these great aerials will be strained to the limit to pick up the weakened signals. To give an example in layman's terms, the signal from Pioneer 10, by the time it reaches the antennas, will have the power of only one trillionth of a watt. If this amount of energy was collected for 19 million years, it would just be enough to light a 7½-watt Christmas tree bulb for one-thousandth of a second.

In practical terms it means that whereas Mariner 9, now concluding its remarkable picture-taking mission from Martian orbit, can send back 16,000 "bits" of information on its four experiments, Pioneer can transmit only 1,000 per second on its 11 experiments.



RADIO NOISE

Another possible difficulty is that Jupiter itself is the centre of intense electrical activity. From time to time it emits huge surges of radio noise. Its magnetic field appears to be similar in shape to earth's, but far stronger, and its radiation belts are estimated to be a million times more intense.

All this adds up to forces which could seriously interfere with the spacecraft's electronics, but project officials are confident that Pioneer will come through with flying colours. They have gone as far as to say that the probe may remain in radio contact for seven years, when it will be one and a half thousand million miles from earth. The radio signals from Pioneer 10 cannot be received once the spacecraft has passed this distance.

On board Pioneer 10, communications and control are served by three antennas—a 9ft. dish which will be locked on earth like a big eye throughout the mission, a forward-facing medium-gain horn, and a single-spiral, low-gain antenna, mounted at the rear.

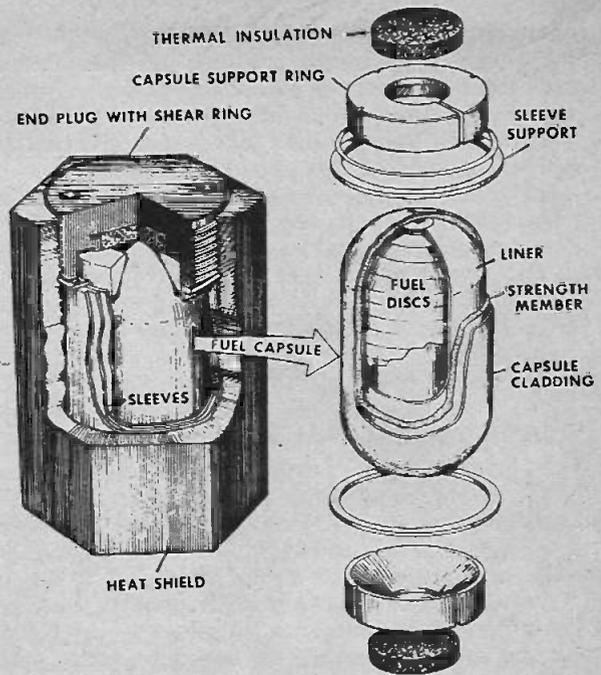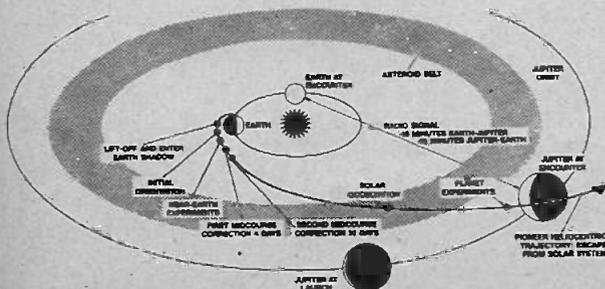The flight path of Pioneer 10 from earth to Jupiter.



Cutaway view of the plutonium 238 fuel capsule of the SNAP 19 radioisotope thermoelectric generator (atomic battery). Four of these Atomic Energy Commission-developed generators provide a total of 120 watts of electrical power in the Pioneer 10.

SELF-REPAIRING COMPUTER

The spacecraft will be guided on its long journey by a computer that realises when it makes a mistake and can fix itself if it needs repairing. This is a STAR (self-test and repair) computer. In operation, if it finds that it has made a mistake, it turns back and recycles, in order to undo the damage. The STAR computer carries spare parts, and in the event of an equipment failure is capable of patching itself up.

Another feature of Pioneer 10 is a thermonuclear generator which provides power for its instruments. This device converts heat from plutonium fuel directly into electricity with no mechanical processes in between. It is part of the spacecraft's equipment because radiation from the Sun is too weak at Jupiter for an efficient solar-powered system to be used.

Though Pioneer 10 bears scant resemblance to America's earlier probes of the same name, it retains many tested sub-systems of its predecessors, Pioneer 6 to 9. (Incidentally, all four of these craft are still operating in interplanetary space. Pioneer 6 is in its seventh year.)

"CAMERA"

Pioneer 10 is spin-stabilised, so that its instruments have a full-circle scan. This will be especially important to the craft's "camera," a versatile instrument known as an imaging photopolarimeter, which will take images of Jupiter

that can be built into photographs of the planet. This camera-like device will use the spin of the spacecraft to scan the planet in narrow strips in both red and blue light. Back on earth investigators will put the elements together to make composite pictures of the planet, taking about one each hour. It may prove possible to superimpose elements taken with the red and blue filters to make colour pictures of Jupiter.


The "camera" will get its first test earlier in the mission when it is used in interplanetary space to measure zodiacal light, and changes in light reflected by the planet which should indicate characteristics of Jupiter's surface.

INSTRUMENT PACKAGE

Pioneer's camera and 10 other instruments make up the most comprehensive scientific payload ever sent towards another planet. But they are relatively light in weight, accounting for only 65lb. of the spacecraft's total weight of 565lb.

The instrument package is designed to conduct 13 different experiments which between them should provide a wealth of new knowledge, not only about Jupiter, but on the outer solar system and the Milky Way galaxy. Specifically they will study and report on the possible hazards of flying through the asteroid belt (a section of the journey that will last for six months); they will make the first report on Jupiter's twilight side, which cannot be seen from earth, and make 20

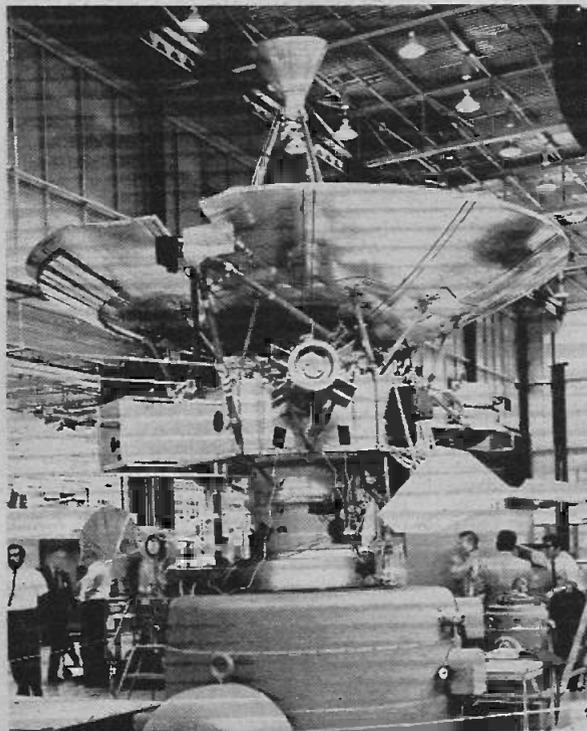Test model of the Pioneer 10 mounted on a shake table.



types of measurements to send back data on the planet's atmosphere, radiation belts, heat balance, magnetic fields and moons.

Pioneer 10's instruments will also gather information on the heliosphere, the region of space that is influenced by the Sun. They will look for the boundary where the heliosphere ends and galactic space begins to give scientists a better understanding of the effects of the heliosphere on the earth.

Radio signals figure in one of the spacecraft's two passive experiments. This is Pioneer's S-band occultation research project, in which the analysis of signals cut off as the spacecraft swings behind the planet may provide information on the atmosphere. The other passive experiment involves a study of the craft's trajectory to define more accurately the known position of the planets.

FASTEST EVER


Right at the start of its journey, Pioneer 10 became the fastest-ever spacecraft, when it was accelerated to 32,400 miles an hour to escape the pull of the earth's gravity without first going into orbit. Usually spacecraft first take up a position in orbit round the earth and are then given an extra boost to put them on a trajectory for their target in space.

To give Pioneer 10 the necessary extra power, however, an upper third stage was added to the Atlas-Centaur rocket, which the United States now uses for most of its deep space flights. This was enough to send the compact spacecraft hurtling from the earth's atmosphere at a greater speed than any other craft has flown. Eleven hours after launch Pioneer had intersected the orbit of the Moon, a journey which takes the Apollo astronauts nearly three days. In the first week of its journey it travelled over half a million miles a day.

With most of its propulsion needs taken care of in that initial powerful thrust, little else in the way of fuel was needed on board. Only a few small jets are needed to control the spin rates which stabilise the vehicle and to align the antenna, a task which increases in difficulty as the distance from earth increases.

SPECTACULAR PLANET

Jupiter, the fifth planet from the sun, is among the most spectacular of heavenly bodies. It appears to have its own internal energy source and is so massive that it is almost a small star. It generates more heat than it receives from the distant sun and may have the necessary ingredients to produce life. Its volume is 1,000 times that of earth, and it has more than twice the mass of all the other eight planets combined. Striped in glowing yellow-orange and blue-grey, Jupiter floats in space like a bright-coloured rubber ball. It has a huge red "eye" in its southern

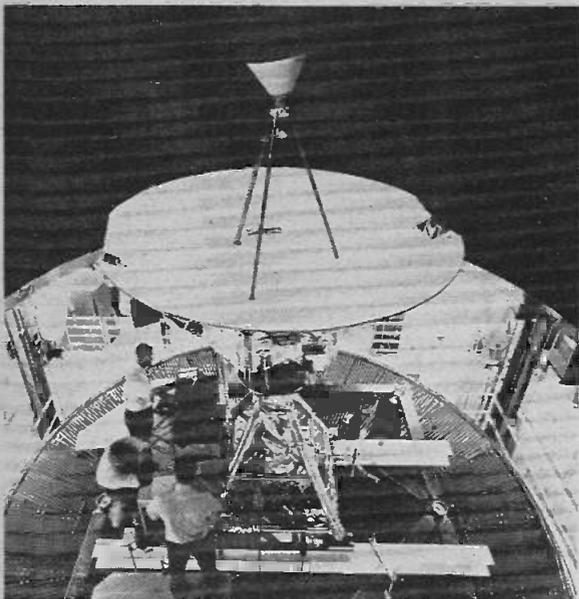

Before launch Pioneer 10 was tested in a simulation chamber which reproduced the conditions of heat, cold, vacuum and radiation expected on the flight to Jupiter and beyond.

hemisphere and spins more than twice as fast as earth.

Jupiter has 12 moons, including three—Ganymede, Io and Callisto—which are larger than the earth's moon. But the planet itself is little understood. Earth-based studies have not yet revealed whether the surface is solid, liquid or gas.

It broadcasts predictably modulated radio signals of enormous power. Though it has only 1/1000th the mass of the Sun, it may have Sun-like internal processes, apparently radiating about four times as much energy as it receives from solar radiation.

The planet's atmosphere is made up of hydrogen with small amounts of ammonia, methane, helium, and probably water—ingredients believed to have produced life on earth about 4,000 million years ago. Because of Jupiter's internal heat source, many scientists believe that large regions below the frigid cloud are around room temperature. These conditions could allow the planet to produce living organisms despite the fact that it receives only 1/27th of the solar energy received by the earth.

Jupiter itself is probably more than 75 per cent hydrogen, the main constituent of the universe. The planet may have no solid surface. Due to its high gravity, it may go from a thick gaseous atmosphere down to oceans of liquid hydrogen, to a slushy layer, and then to a solid hydrogen core. Ideas of how deep beneath its striped cloud layers any solid hydrogen "icebergs" or "continents" might lie, vary by thousands of miles.

Astronomers have long seen violent circulation of the planet's large-scale cloud features. A point

on Jupiter's equator moves at 22,000 m.p.h., compared with 1,000 m.p.h. for a similar point on earth's equator.

EYE


The most bizarre feature of the planet is the Great Red Spot, known as the "Eye of Jupiter." This huge oval is 30,000 miles long and 8,000 miles wide, large enough to swallow up several earths with ease. The Red Spot may be an enormous standing column of gas, or, says one scientist, a "raft" of hydrogen ice floating on a bubble of warm hydrogen in the cooler hydrogen atmosphere, and bobbing up and down at 30-year intervals, so that the Spot disappears and reappears. The Spot appears to rotate at a different speed from the planet. Its red colour may be due to the presence of organic compounds found in a gigantic lightning charge in the Jovian atmosphere, according to one theory.

TWIN SPACECRAFT


Shortly after Pioneer 10 leaves the asteroid belt next April, an identical spacecraft will be launched on a similar mission. These two spacecraft, their scientific instruments, and data processing and analysis, will cost about 100 million dollars.

According to project officials, potential benefits include increased knowledge of what they call the "collisionless plasmas" of the solar wind. This bears directly on the "ultimate" clean system for electric power production, controlled hydrogen fusion. The findings may also lead to better understanding of earth's weather cycles, and to insights into earth's atmosphere. There may also be indications of Jovian resources, such as perhaps a quantity of petrochemicals equivalent to earth's consumption for a million years.

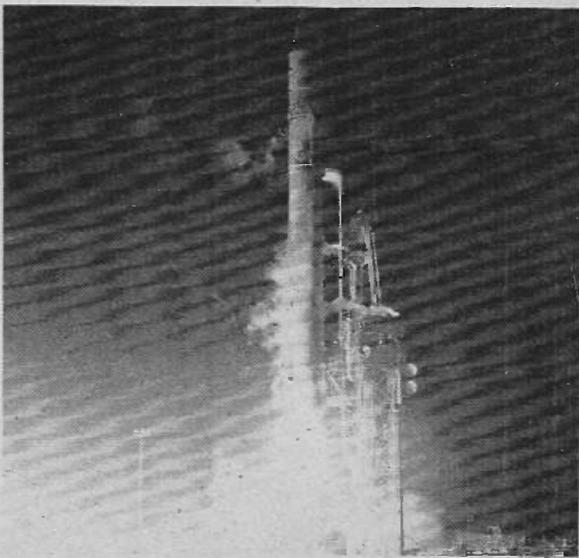Photographs: United States Information Service.



BRIGHT IDEAS

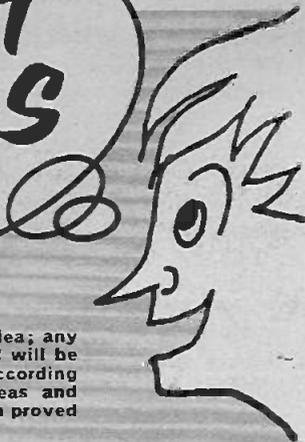

A readers' Bright Idea; any idea that is published will be awarded payment according to its merit. The ideas and designs have not been proved by us.

Most electronic projects featured in E.E. pages are made up on strips of Veroboard, which makes a very neat and compact unit in itself but does not seem to have provided any immediate means for attaching to a chassis, box, model or whatever. Bolts are clumsy inconvenient fixtures, edge connectors rather expensive items and often not justified for four or five connections.


Most stationers now sell a plastic "V" shaped strip for holding papers together or the same thing is sold in longer lengths at Ironmongers as saw-guards, in both cases it

costs about 4p a foot.

This plastic forms a holder into which Veroboard may be slid and held securely, either vertically or from the side of a chassis or using two strips one on either side, as runners into which completed boards may be slid.

The back of the clip is flat and is of a type of plastic into which self-tapping screws may be successfully driven, so that it is a simple matter to fix the plastic clip to a framework with binders.

G. E. Dunning
Surrey.

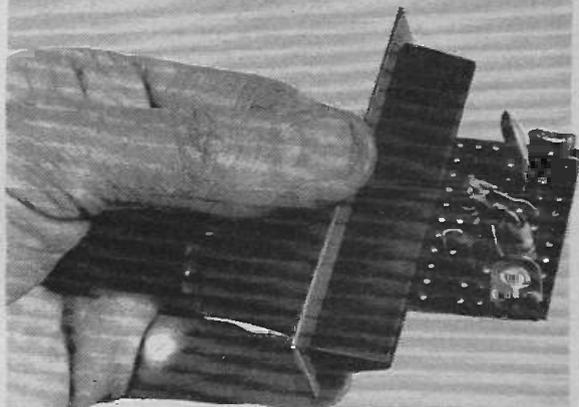

Ruminations By Sensor

Sic transit gloria

REDEVELOPMENT schemes are taking place all around us these days and the glass and concrete structures rising in our towns and cities are, usually, far less interesting than the buildings they replace.

The other day I noticed that yet another row of shops was to be demolished and amongst these was an old style "Cycle and Wireless" shop. I stopped and looked in the window; amongst the bicycle pumps, spanners, spoke keys and oil cans, lay some treasures from the past. There were gramophone sound boxes and clockwork springs, "loudtone" needles and banjo strings, pram hood corners and oil lamp wicks, spade-end terminals and fire lighter bricks.

"Everything must be cleared" declared the painted notice on the window, I had to go in.

Inside the shop, a faint aroma of bicycle oil with admixtures of rubber, paint and leather excited my nostrils. A woman came from the back of the shop and invited me to look around. She explained that the property had been subject of a compulsory purchase order and that she and her husband were, therefore, forced to sell up, much against their wishes.

Condensers

It was clear that the "wireless" side of the business must have started to run down some forty years ago—I found a box of bakelite five pin and four pin valveholders, the baseboard type with screwed terminals. In a glass fronted cabinet, a few variable "condensers" and "h.f. chokes" lay forlornly—overtaken, like the shop itself, by the pace of technology.

What else lay in all those drawers and cupboards? Was there a set of plug-in honeycomb coils, long and medium wave, for h.f., reaction and detector?

I remember finding such a set of coils in a box of my father's old junk; each coil carried a

label showing the wavelength range covered when tuned by a 0.0005 μ F "condenser", and the legend "what are the wild waves saying" was printed across the top of the label.

No doubt, the shop had at one time had a battery charging installation like the one I saw advertised in a church bazaar recipe book, printed about fifty years ago. The advertisement invited customers to "see your accumulators charged in our modern battery charging station". 120 volt h.t. batteries could be bought for 1 shilling per week and the proud possessor of a "wet h.t." i.e. a bank of small accumulators, series connected, could have these recharged at a "very reasonable price".

When domestic electric installations became more common (there are limits to what can be done by gas) the h.t. battery was replaced by an "eliminator" which often had provision for trickle charging the accumulator. It was then but a short step to the "all-mains set" with its indirectly heated cathodes and 4 volt heaters. And now, with transistor radios, we are back to batteries.

LIGHT TO SOUND CONVERTER

By Gerry Brown



An experimental device providing an audio output, the frequency of which depends on the light falling on a light dependent resistor.

This Light to Sound Converter is intended as an experimental device and could have many novel applications. If fitted with a simple lens system it could provide an aid for the blind for sensing heights of liquids or changes in contrast or light levels. Alternatively it can be treated purely as a novel exercise in electronics or as a party game device which could be used for detection of objects or people whilst blind-folded.

Since the feature is experimental in its application no specific case design has been given. Suggestions for a case and simple optical accessories are given in the text.

PRINCIPLE OF OPERATION

The circuit of the Light to Sound Converter is shown in Fig. 1. Transistors TR1 and TR2, plus their associated components, form a simple multivibrator the output frequency of which is essentially determined by the values of C1, R2, R3, R4, C2, and PCC1; thus the frequency can be varied by the amount of light falling on the light dependent resistor (l.d.r.) PCC1. Basic operation of the circuit can be best understood with PCC1 and R3 shorted-out, such that the junction of R2, R4 is taken to the positive supply rail. Immediately power is applied, one tran-




Approximate
cost of
components
£1.70 inclusive

sistor, or the other will conduct (in a circuit of this kind the initial process is an effectively random one). Assuming TR1 was the first to conduct, then C1, which would have charged almost simultaneously with application of power to the circuit, will begin to discharge through R2 at a rate equivalent to C1, R2. During this time TR2 will be turned off. When the junction of C1, R2 reaches approximately 0.6 volts, TR2 will conduct and C2, which charged when TR1 began conducting, will begin to discharge through R4. At this time the junction R4, C2 will be negative and hence TR1 will be cut-off, thus C1 will re-charge almost instantaneously via R1. Once the junction R4, C2 reaches 0.6V, TR1 will again conduct and the process repeats. The action of the circuit is somewhat like that of a rapid see-saw, indeed, some of the earlier versions of this circuit were actually referred to as such.

SENSITIVITY

Since with any photo-resistor there will be a light level above which there will be no further drop in its resistance (i.e. saturation) there will naturally be conditions where the aids' value could be questionable. On the other hand, in

Fig. 1. Circuit diagram of the Light to Sound Converter. The frequency of the multivibrator formed by TR1 and TR2 is varied by light falling on PCC1—the light dependent resistor.

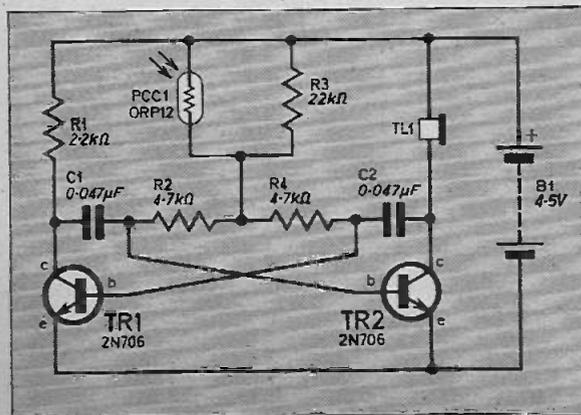

Components....

Resistors

- R1 2.2k Ω
- R2 4.7k Ω
- R3 22k Ω
- R4 4.7k Ω
- All $\frac{1}{4}$ W $\pm 10\%$ carbon

Capacitors

- C1 0.047 μ F
- C2 0.047 μ F

Transistors

- TR1 2N706 silicon npn
- TR2 2N706 silicon npn

Miscellaneous

- PCC1 ORP12 light dependent resistor
- TL1 Earphone magnetic, type 100-250 Ω impedance
- B1 4.5V battery
- Veroboard 0.1in. matrix, 3 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in., connecting wire, plastic or s.r.b.p. tube for light shield—approximately $\frac{1}{2}$ in. diameter by 2 $\frac{1}{2}$ in. long.

SEE
**SHOP
TALK**

totally dark surroundings PCC1 would have an extremely high resistance, so high that oscillator instability could occur resulting in a "chirping" or wavering in pitch. To overcome this disadvantage, R3 is included to provide some parallel limiting resistance; this addition only barely affects the overall sensitivity.

To maintain simplicity of the device, no special amplifier is employed and the earphone, which has the role of a miniature loudspeaker, is driven direct as the collector load of TR2.

CONSTRUCTION

In its prototype form, the converter was constructed on a piece of 0.01 inch Veroboard, as shown in Fig. 2. The transistors should be the final components to be soldered in position (using a heat shunt on each lead), thus preventing damage when fitting other items. Cutting breaks in the copper strips should be performed prior to fitting adjacent parts.

The earpiece TL1 can be mounted in position with impact adhesive, applied to both it and the circuit board. The same method can be used for the l.d.r. hood which will probably be employed initially. This tubular shield can be of any suitable material and should be painted matt black on the inside to prevent unwanted light reflection. Before the device is connected to a battery, it is wise to ensure that all the connections that have been made are correct.

A suitable case for the unit could be constructed from an old torch case with the photo-cell situated in place of the bulb and the earphone arranged so that the sound emits from a

LIGHT TO SOUND CONVERTER


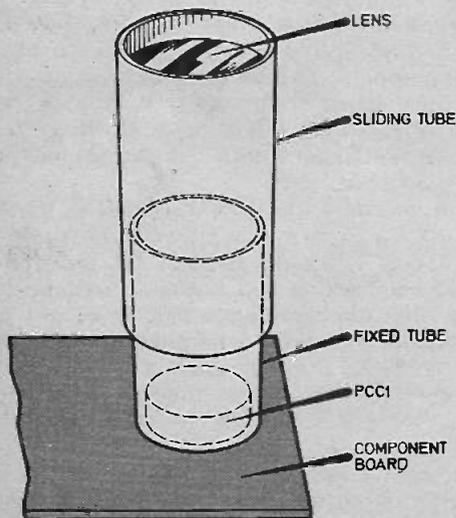
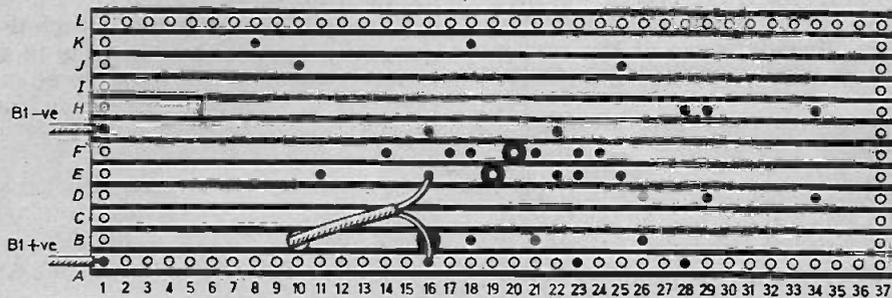


Fig. 2. Layout and wiring of the Veroboard, top and underside, showing the complete Light to Sound Converter less battery.

Fig. 3. A simple method of improving the sensitivity of the Light to Sound Converter by adding an optical system. The system shown allows the lens to be focussed by moving the sliding tube.

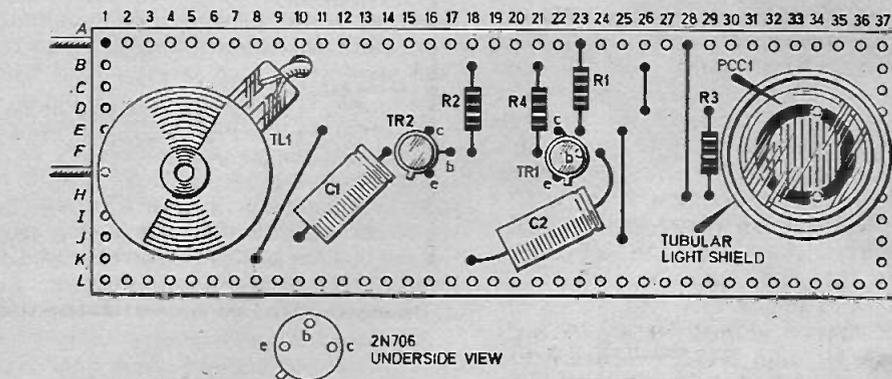

Photograph showing the prototype unit with a simple light shield.

grille at the other end of the "torch". If such a case is used three 1½ volt pen torch batteries wired in series can be used for the power supply and a small s.p.s.t. switch inserted in the positive lead to turn the unit on and off.

If the unit is to be used experimentally without a case the underside of the Veroboard should be protected in some way to prevent alteration of the output frequency by possible bridging of the copper strips with the hand. A layer of insulation tape covering the strips is suitable for this purpose.

OPTICS

In its prototype form the Light to Sound Converter carries no proper optical accessories and employs just a simple tubular light hood to limit slightly the l.d.r.'s angle of view. This scheme, nonetheless, proves to be extremely satisfactory for most general purposes and permits easy detection of small changes in the level of ambient lighting.

For specific tasks the device ideally requires the use of lenses. Such lenses might be obtained from an optician, one of the London-based optical manufacturers, or even the plastic lenses from an old pair of children's binoculars or a plastic magnifying glass.

Such a lens should be fitted in a sliding tube, as shown in Fig. 3, so that the distance between the lens and the l.d.r. is the image distance of the lens. A simple way of determining the approximate distance required is to focus the sun on a piece of card and measure the distance between the card and the lens; this distance can then be made the minimum distance between the lens and PCC1.

By sliding the lens in and out while pointing the unit at a distance light source a position can be found where the unit is most sensitive. Further experimentation with an optical system is left to the ingenuity of the constructor.

EXPERIMENTAL TEST

Ideally, the aid should be used with reflected light and not "look" at direct sunlight or electric lamps, resulting in saturation of the photo-sensor; this cannot damage the circuit but sensitivity will not be so good in this mode. To check correct operation of the device, place it with the l.d.r. away from a window and slowly wave a sheet of white paper in front, about 6 inches from the light shield. This ought to result in an increase in the pitch of the signal from the ear-phone, always assuming, of course, that this experiment is performed during daylight hours!

Choice of lenses must naturally be left to the constructor, but he/she may find it interesting to experiment with colour filters and polarising elements. Indeed, if either a dichroic (two-way) mirror or fibre optics can be obtained, they could be employed to permit simultaneous illumination and "viewing" of an object by the photo-sensor.

Whatever the ultimate sophistication of the aid, one is likely to achieve some degree of satisfaction from knowing that at least its primary application could be in helping others less fortunate than ourselves. In a world like ours this, surely, cannot be a bad thing! □


PLEASE TAKE NOTE

We regret that the coil winding details of the Metal Locator, published last month, were omitted. The coil consists of 40 turns of 26 s.w.g. enamelled or cotton covered copper wire.

We apologise to readers and to Mr. Bollen for this omission.

In the Constructors Companion booklet given free with last month's issue, the NKT 125 should not have been given as a substitute to the 2N 1091 on page 20.

what they look like

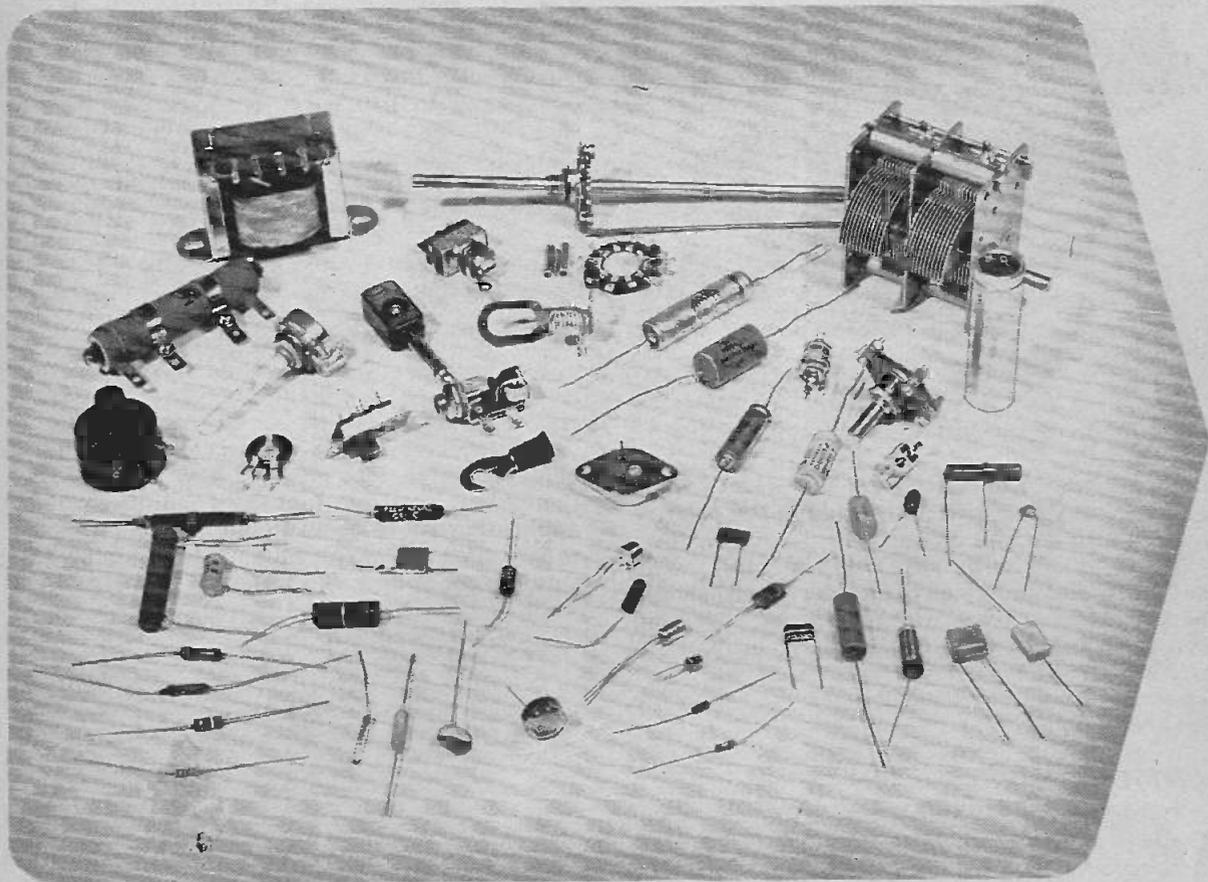

The first part of a series showing the various signs and designations used in electronics, explaining briefly what they represent and showing typical components.

The photograph above shows a range of components. **Top left:** transformer, various switches, connectors, lamp holder, reed relay and a reed switch and magnet. **Lower left:** range of resistors including a mains dropper, normal and preset potentiometers. **Lower centre:** thermistor, voltage dependent resistors, light dependent resistor, some transistors and two diodes. **Right:** selection of capacitors including variable and preset types.




guide to circuit symbols



guide to circuit

Circuit Wiring

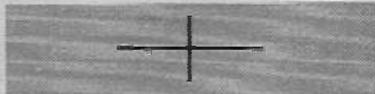


Two conductors crossing on a circuit diagram—no connection.



Junction or connection of two conductors on a circuit diagram.



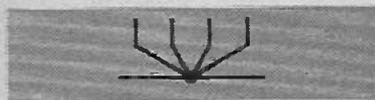Junction or connection of three adjacent conductors on a circuit diagram.



Common junction or connection of four conductors on a circuit diagram to a common point.



Continuous coaxial line.



Coaxial line split at one end into two terminals.



Earthed outer conductor of coaxial line.



Boundary line around part of a circuit diagram.




Earth connection.



Connection to frame, chassis or case, not necessarily earthed.






Batteries

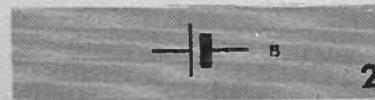

Primary or secondary cell. Long line represents positive terminal.








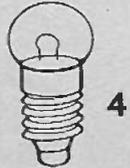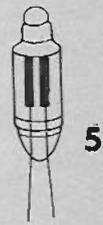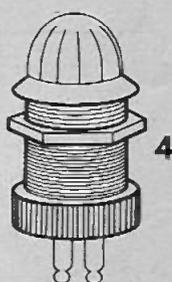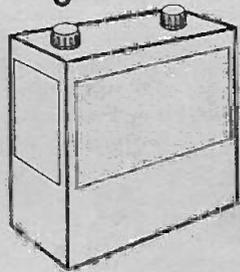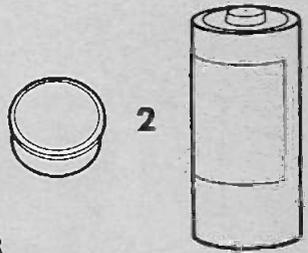Battery of primary or secondary cells marked with voltage. Long line represents positive terminal.




symbols . . . part 1


Indicating Devices

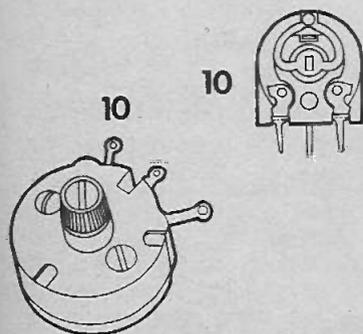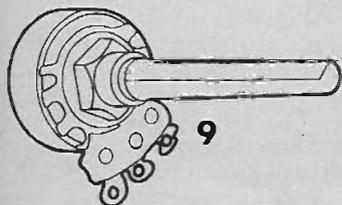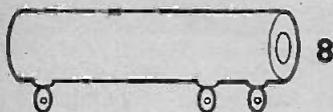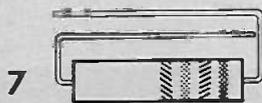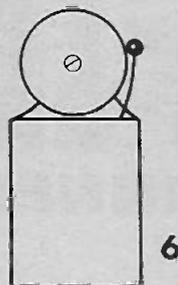

Signal or indicating lamp.

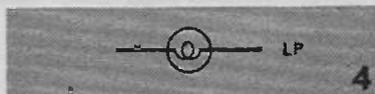

Filament illuminating lamp.

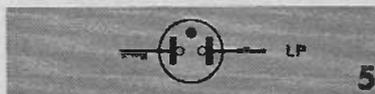

Neon lamp or indicator.




Electric bell.



Electric buzzer.

Resistive Devices

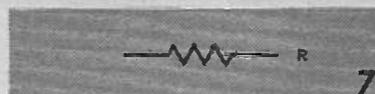

Fixed value resistor.



Fixed value resistor with tapping.



Resistive heating element.




Variable resistor.



Potentiometer with control knob.



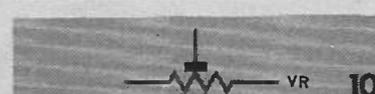Variable resistor with preset adjustment.



Potentiometer with preset adjustment.



TEACH-IN

... FOR BEGINNERS

By Mike Hughes M.A.

8

MULTIVIBRATORS

WHEN dealing with circuits, most books start with amplifiers; this pre-supposes you have something to amplify but if you haven't it can be frustrating making an amplifier you cannot check.

Because of this—and because we're all human and like to see things working right away—we will leave amplifiers to start with, and concentrate this month on a very important basic circuit having the grandiose name "astable multivibrator".

It is such a frequently used circuit that one does not even have to read the Editor's mind to estimate that it will feature in several projects per annum. We are going to make it flash lights and produce an audible sound.

We'll keep to our word and not dive in at the deep end but will slowly develop the full circuit in easy stages. Follow the text and figures carefully.

BASE CURRENT

The circuit of Fig. 1 is similar to one shown last month. If we connect the free end of R1 to the positive rail we will pass base current, and provided it is great enough, the transistor will conduct "heavily" and the lamp will light.

Although the specification for the BC108 says it has an h_{FE} of 240, there is likely to be some variation between devices; as we want to ensure that the lamp comes on at its brightest we will assume that the gain of the device to hand is

considerably less than this when it comes to calculating the value of R1.

We will assume, rather pessimistically, that the actual gain of our device is 120 (it does not matter if it happens to be higher). We will also overstate the current our bulb will draw, say 100mA. It can't be more than this because we would exceed I_{max} for the transistor.

Thus we can calculate the base current required.

$$I_b = \frac{I_c}{h_{FE}} = \frac{100}{120} = 0.83\text{mA}$$


R1 is found by dividing the voltage drop of the transistor by the base current required.

Therefore

$$R1 = \frac{9 - 0.5}{0.00083} = 10,200 \text{ ohms.}$$

The nearest preferred value to this is 10 kilohm.

Fig. 1. Connecting the free end of R1 as shown causes TR1 to conduct sufficiently to light LP1 brightly.

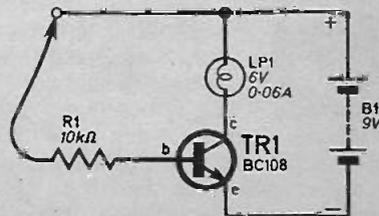

CAPACITOR CHARGING/ DISCHARGING

Now look at Fig. 2(a). Strange as it may seem, D1 does not take an active part in our description because it is there only to protect the base emitter junction from high reverse voltages that we shall be applying (V_{eb} for the BC108 must not exceed 5V, remember?). You'll see how this comes about shortly.

Let's assume we connect the free end of C1 to the positive rail with the link to the negative rail disconnected and switch on. The capacitor can be considered as being "charged" because

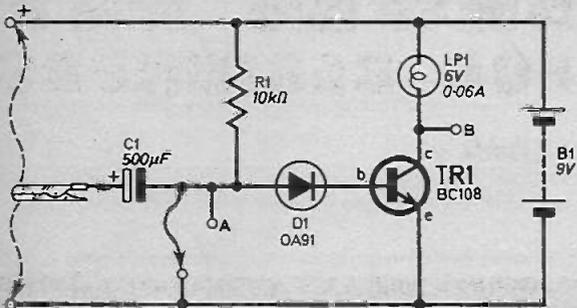


Fig. 2(a) (above). The circuit diagram to illustrate the switching action of a transistor.

Fig. 2(b) (top right). The circuit of Fig. 2(a) wired up on the Demo Deck.



the positive plate immediately rises to +9V but the negative plate stays momentarily at zero.

Forget the battery, transistor and diode for a moment and just consider C1 and R1. The 9V potential difference across the plates will cause a discharge current to pass through R1 and the potential of the negative plate will try to approach that of its counterpart.

Now look at the circuit as a whole with a voltmeter connected between "ground" (the negative rail) and point A. Going through the same argument, the voltage we would see initially is zero but will rise in a positive direction as C1 discharges. When the potential reaches about +500mV the discharge will stop because TR1 starts to draw base current; this prevents the potential rising any further but I_b will flow through R1 and D1. This turns the transistor on and the lamp lights. You can see this effect on the Demo Deck.

TRANSISTOR SWITCH

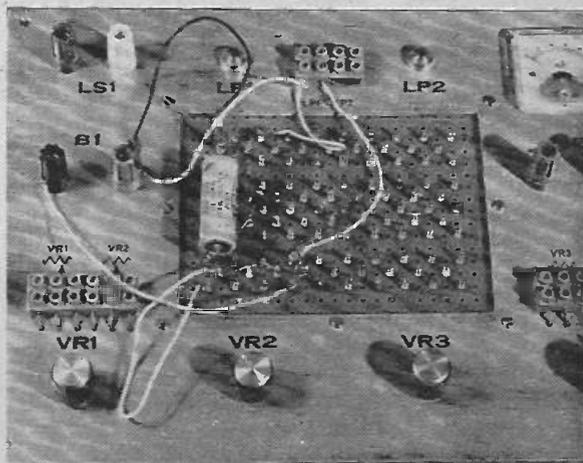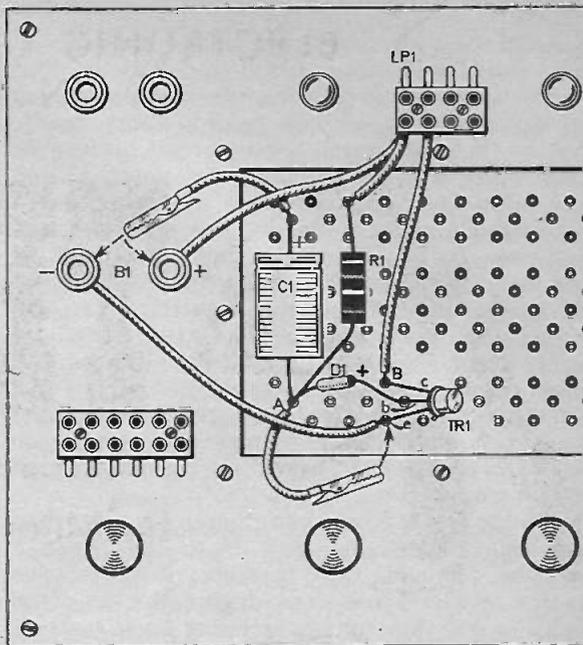To start the cycle make sure C1 is fully charged by shorting point A to ground; the lamp goes out immediately. When you remove the short circuit there will be a short delay (about 1 second) before the lamp comes on again—monitor point A while this is happening and you will see that the lamp lights just as the voltage reaches about 500mV. The delay is caused by the time it takes the potential dif-



Photograph of the Demo Deck wired up according to the circuit diagram of Fig. 2(a).

ference across the capacitor to decay from 9V to about 8.5V.

An important note to Demo Deck users: you can still use our simple circuit for a 10V range meter, (1 kilohm resistor in series with the Demo Deck meter) but its sensitivity is so poor (1,000 ohms per volt) that you will now start to read voltage levels rather less than those detailed above and its low internal resistance will start to affect the charge and discharge rates of the capacitors. Now is the time to start thinking about buying or making a 20,000 ohm per volt meter (see the *Simple Multimeter* article on page 414).

Discard the shorting link at point A and revert to a flying lead from the free end of C1. First touch the lead on to the positive

rail then watch the meter with one eye, the bulb with your other and if you have a third eye or a helper, quickly transfer the flying lead to the negative rail and hold it there firmly. Notice that the meter tries to read backwards (indicating a negative voltage at point A) and the lamp goes out and stays out for about 4 seconds. Repeat the experiment several times remembering to return the flying lead back to the positive rail between times (ignore the slight flash from the bulb when you do this). You will notice that the lamp turns on after a definite delay and always when the potential at point A finds its way back to +500mV.

"What happened to this potential when the lamp was out?" Well, reverse the meter connections and see by repeating the experiment a few more times.

If your eye is quick, you should see that when you touch the flying lead on to the negative rail the potential falls to minus 8.5V relative to the negative rail, and during the time the lamp is out this voltage is rising back towards zero and ultimately back to +500mV.

Before we talk about what causes the longer delay time let's find out why the potential can go negative.

NEGATIVE POTENTIAL

At the start point of our cycle, point A was at +0.5V and the other side of the capacitor at +9V. When we move the flying lead to the negative rail we effectively change the potential on the positive plate by 9V in a negative going direction. You might think that this would virtually cause the capacitor to be discharged with only 0.5V being left across it. This is not true because no discharge current has been seen to flow yet. Discharge current does, however, flow and the only way is through R1.

If the discharge current through R1 now increases suddenly (it flows from the positive plate of the capacitor through the battery and R1 and back to the capacitor) the potential difference across R1 must increase—but it was already 8.5V (point A was at +0.5V). The instantaneous change in current will cause the potential difference across R1 to increase by the same amount as the change in potential we applied to the positive plate. This means that the drop across R1 must increase from 8.5V to $(8.5+9)V=17.5V$.

As one end of R1 is well and truly fixed at the +9V battery potential it means that the other end must fall to $(9-17.5)V=-8.5V$. This is exactly what happens to point A and is why we have to protect the base/emitter junction of the transistor with D1.

With the positive plate at zero volts and point A at -8.5V the only discharge path is through R1. The potential at point A will rise slowly as it tries to reach +9V (see Fig. 3(a)) but this is

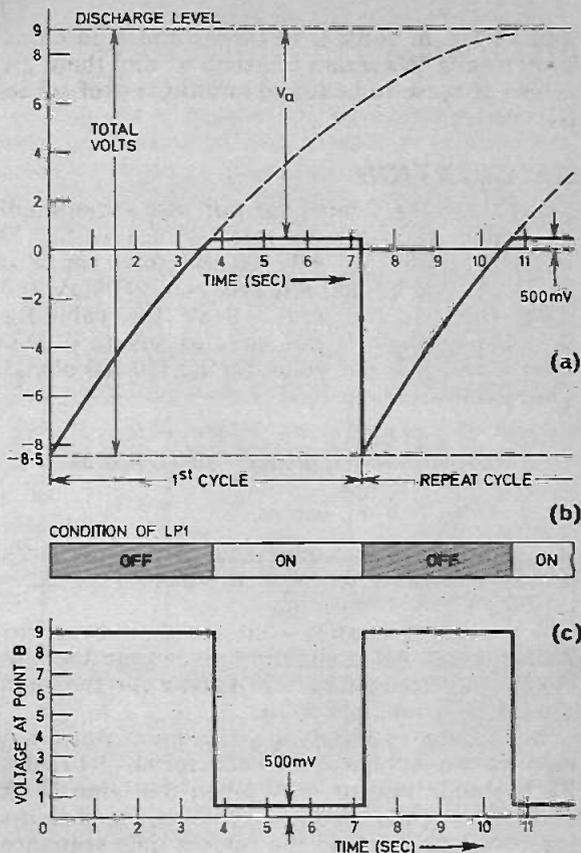


Fig. 3. (a) The graph obtained by plotting voltage at point A against time. (b) The state of LP1 with time. (c) The output voltage at point B of Fig. 2(a).

prevented by the transistor starting to draw base current (when the potential reaches 500V) so the graph suddenly levels off at +500mV.

The dotted part of the graph shows what would have happened had the transistor not been in circuit. Fig. 3(a) shows the graph for two consecutive cycles of our experiment.

CAPACITOR CHARGING TIME

The time it takes for a capacitor to discharge through a resistor is controlled by the value of the capacitor, the resistor and the voltage range through which it is discharging. We can even predict how long it will take to achieve partial discharge (as is the case for us). Let us say the capacitor wants to discharge completely through a voltage range of V_{total} (measured in volts), and we want to find how long it takes to discharge to a level of V_a volts from the final discharge level; the time taken is calculated from the following equation:

$$t = \log_e \frac{V_{total}}{V_a} \times C \times R$$

where t is the time measured in seconds, V_{total}

and V_a are in volts, C in farads and R in ohms. \log_e means "Naperian Logarithm" and there are tables of these to be found in most sets of school log. tables.

CALCULATION

Let's use the figures for our own experiment to see how the formula works. V_{total} (see Fig. 3) is from $-8.5V$ to $+9V$ so the total range is $17.5V$. V_a will be that left between $+500mV$ and $+9V$ which, of course, is $+8.5V$. Our value for C is $500\mu F$ which is the same as saying 0.0005 farads, and R is our value for R_1 ($10,000$ ohms). Therefore,

$$t = \log_e \left[\frac{17.5}{8.5} \right] \times 0.0005 \times 10,000 \text{ seconds}$$

$$= \log_e 2.06 \times 5 \text{ seconds}$$

If you look up $\log_e 2.06$ in your tables it is given as approximately 0.72 . So the answer becomes $t = 0.72 \times 5 = 3.6$ seconds.

Is this approximately what you got in practice? Probably you got a slightly longer time because electrolytic capacitors are usually on the high side of their nominal value.

Repeat the experiment a few more times but monitor the voltage at the collector of TR_1 (point B). It should rise to $+9V$ when the lamp is off and fall to nearly zero when it is on. Fig. 3 shows these voltage levels in the correct time sequence with what was happening at point A.

caused by the comparatively "heavy" currents we are switching. Now watch both bulbs and transfer the flying lead to ground.

As you would expect LP_1 goes out; TR_1 collector goes to $+9V$ which makes LP_2 go on (as it was already on there will be no change). Keep the lead firmly held on the ground line and keep watching. After about 4 seconds LP_1 comes on again and TR_1 collector falls to near zero. This forces TR_2 out of conduction and LP_2 now goes out. Keep watching. After another 4 seconds LP_2 comes on again just as we have seen for the first stage. We are now back where we started and nothing else will happen unless you return the flying lead back to the 100 ohm resistor (ignore the odd flash while doing this but allow time to stabilise) and repeat the cycle.

Now connect the flying lead to the collector of TR_2 and feedback the voltage changes of the second stage to control the first stage. The electronics now takes over from you and the lamps will continue their 4 second flashing cycles automatically!

You have made an "astable multivibrator"—one of a group of circuits called "oscillators". An oscillator produces changes of voltage levels (or controls current) in a regular repetitive manner for indefinite periods. You can monitor its "waveform" by looking at the voltage of one of the collectors. It is, of course a regular form of Fig. 3(c). Because of its rectangular shape we call it a "square wave".

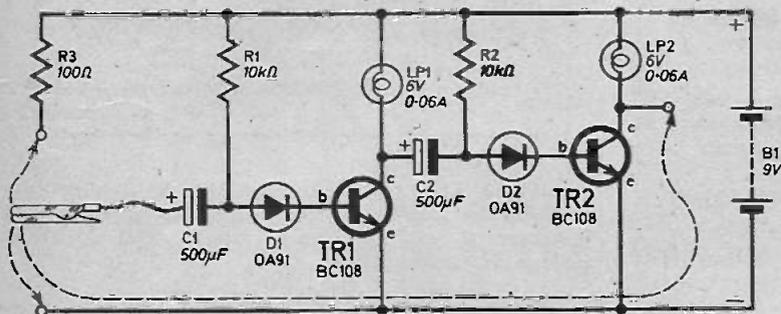



Fig. 4(a) (left). The basis of the astable multivibrator. When the positive end of C_1 is connected to TR_2 collector, the circuit operates automatically.

Fig. 4(b) (below). The circuit of Fig. 4(a) wired up on the Demo Deck.

THE ASTABLE MULTIVIBRATOR

Now build the circuit of Fig. 4(a) on the Demo Deck. You can see it is made up of two circuits each identical to that we have just analysed in depth. Instead of a flying lead at the capacitor of the second stage we will connect C_2 direct to the collector of TR_1 . The voltage swings at its collector will do exactly the same as our flying lead would have done. We will, however, keep a flying lead on C_1 .

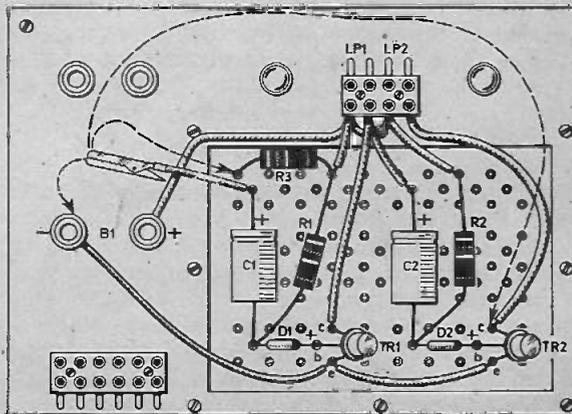Connect this lead through a 100 ohm resistor to the positive rail, switch on and wait a few moments. After a short while both lamps will be alight. You need not worry about the 100 ohm resistor, it is there simply to prevent a side effect



From the point of "just" going to +9V for the first time to when it just goes to +9V the second time is called a "cycle".


The dwell time at +9V is called the "off time" and the dwell at zero volts is the "on time". The total length of time of one cycle is called the "period".

The number, or fractions, of cycles that occur in a second is called the "frequency" and this is measured in "hertz" (abbreviation Hz).

In our case the period is 8 seconds so the frequency is $\frac{1}{8}$ Hz or 0.125Hz.

For a square wave the ratio between on and off times is called the "mark to space ratio". In our case it is "one-to-one" or unity mark space ratio. You can change this ratio by altering the values of either R1 or R2. Try making each in turn 1 kilohm and then both 1 kilohm. Notice the change in mark/space ratio and also the frequency!

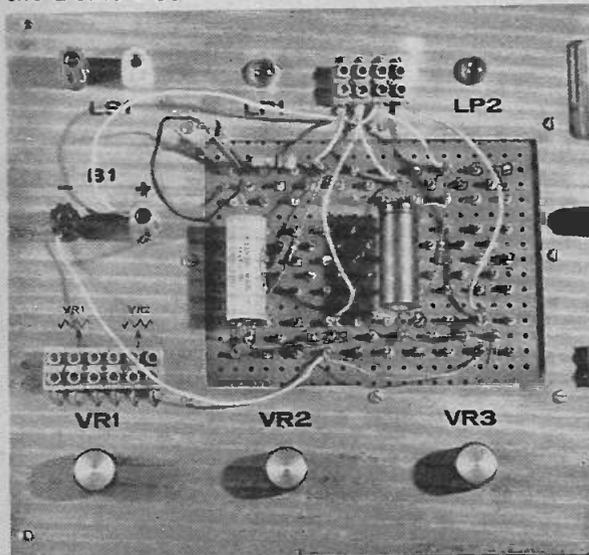Photograph of the circuit of Fig. 4(a) wired up on the Demo Deck.



OUTPUT FREQUENCY

If you keep the circuit symmetrical so that $R1=R2$ and $C1=C2$, the formula for calculating the period is

$$t = 2 \times 0.7 \times C1 \times R1 = 1.4 \times C1 \times R1 \text{ seconds}$$

$$\text{hence, frequency} = 1/t = \frac{1}{1.4 \times C1 \times R1} \text{ hertz (1)}$$

The term $R \times C$ is frequently come across in electronics and is called the "time constant".

Using the above equation we can design our multivibrator to oscillate at any frequency from a fraction to tens of kilohertz (kHz). Musical pitches are determined by the frequency of sound vibrations and 700Hz is about that of "Top F" on a piano keyboard. Let's see if we can make this note electronically!

AUDIBLE OUTPUT

To hear the note we shall use a "loudspeaker". This consists of a coil of wire suspended between the poles of a very strong magnet and the coil has a fabric cone fixed to it. If we pass current through the coil it will move one way or the other and flex the cone at the same time. The latter sets up changes of air pressure which registers on our ears as sound.

We shall use the Demo Deck loudspeaker which has a coil resistance of 35 ohms but provided it is in the range 20 to 70 ohms any loudspeaker will do. Although there is more to it, we shall assume that the coil of the loudspeaker is, to all intents and purposes, a resistor when it comes to our calculations.

The oscillating current in the multivibrator flows between collector and emitter of either of the transistors. We will therefore replace one bulb with our loudspeaker. Unfortunately the resistance, being only 35 ohms, would allow too much collector current to flow and we would exceed I_{max} for the transistor; we must therefore put another resistor in series—see Fig. 5.


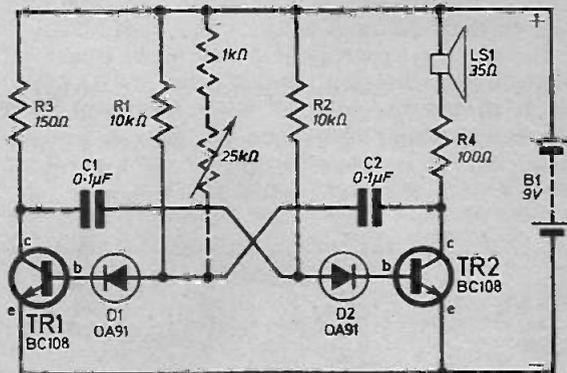


Fig. 5(a) (above). The astable multivibrator circuit for producing an audible output. To produce a variable tone, replace R1 by the dotted combination.

Fig. 5(b) (below). The above circuit wired on the Demo Deck.

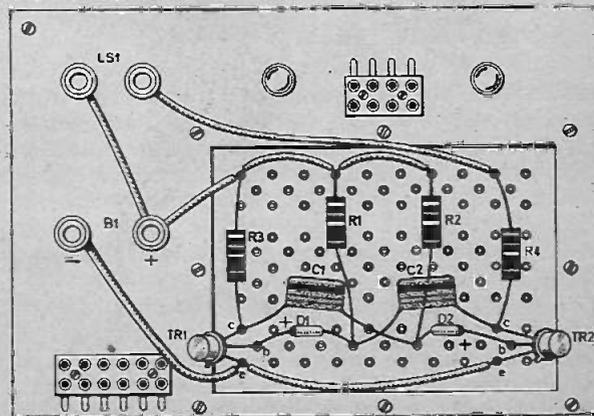

The value of the resistor plus the loudspeaker should be high enough to prevent any current in excess of 100mA (i.e. the total collector load should not be less than 90 ohm). Let's play safe and make R4 100 ohms then even if you accidentally short circuit the loudspeaker no damage will be done.

Similarly we shall make the collector load to the other transistor (R3) 150 ohm—to keep the symmetry about right. Both of these resistors must have half-watt ratings.

SELECTION OF FREQUENCY

As these loads are almost the same as the bulbs (resistively speaking that is) we can leave R1 and R2 at 10 kilohm each. All we have to do now is calculate the values of C1 and C2 to give a frequency of 700Hz.

Using equation (1),

$$700 = \frac{1}{1.4 \times R \times C} = \frac{1}{1.4 \times 10,000 \times C}$$

$$\text{therefore } C = \frac{1}{14,000 \times 700} \text{ farads}$$


giving an approximate value for C of 0.000001 farads (0.1µF).

So make C1 and C2, 0.1µF each, connect up and switch on. If you have a piano, see how close you were to the right note. Don't expect perfection because you must remember resistors and capacitors have tolerances. If you want to you can make one half of the multivibrator variable by substituting R1 with a 1 kilohm resistor in series with VR3 of the Demo Deck (25 kilohm).



Next month: Alternating current. Components used in next months Teach In: Friedland Bell transformer, mains/8V; Resistors, 22 kilohm, 10 kilohm; Capacitors, 500µF elect. 12V, 0.22µF; Diodes, IN4004 (4 off).

Everyday Electronics, June 1972

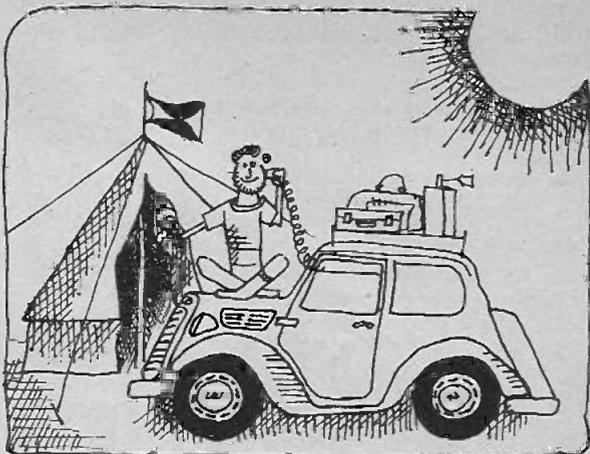


Shave anywhere with the Shaver Inverter

Well almost anywhere! The inverter provides 240volts 50Hz a.c. output, at a power of approximately 10 watts from a 12V car battery.

Horses for Courses

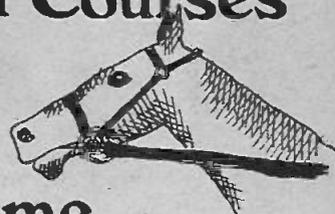The application of a simple circuit, demonstrating genetics, to a family table top game of horse breeding and racing.



Electronome

It's not a miniature electronic man but an electronic metronome. The pulse frequency is continuously variable from 40 to 225 beats per minute.

Teach-In

Next month we introduce alternating currents and transformers.

All in the July issue of



On sale Friday, June 16.

WORKING with electronic gadgets all the time it is not very often that we actually visit a shop to purchase a few odd items, normally we buy a stock from one of the manufacturers or distributors. However, we decided to go out with a list of about 30 items to cover two projects just to see what was involved.

After looking through our catalogues we decided that one supplier could provide all the parts required. The first thing that happened was that the shopkeeper took one look at the list (it was on E.E. headed notepaper by the way) and said we would have to leave it for at least an hour. Well, 1½ hours later, he gave the list back with some components saying that he could not supply those marked.

We checked the items and asked why, for instance, he could not supply the relay asked for—after all it was in his latest advert in E.E.? Well, the advert went in about six weeks ago and since then he had sold out. How about the transistors and the integrated circuit and holder? Apparently he does not keep large quantities of these items and they were out of stock—waiting delivery from the distributors and no telling when that may be!

Fair enough there does not seem to be much he can do about those things. However, when we checked the parts back at the office we found that two of the items supplied from the list were completely wrong.

The motto from all this? We are sure most suppliers do their best to keep stocks of advertised components but the supply from manufacturers and distributors is far from speedy and regular, in some cases. This means that suppliers may have to wait anything up to a few months before they receive their orders and, if this happens to one it can happen to them all, so very often you will find one particular item is difficult to get anywhere.

This magazine can create a demand which the suppliers cannot cope with, for instance the SEW type meter used in the *Demo Deck*. Most suppliers would keep a few and perhaps sell one or two a week; however, we publish the *Demo Deck* design and suddenly they sell ten or more in a week. This happens all over the country and all the shops order



more—perhaps a larger quantity than before—the distributors are hard pushed to cope with the demand and, in fact, in this case, the importers of the meter went completely out of stock and had to order more from Japan; hence a long delay for some readers. A similar thing happened with the loudspeaker and more had to be made to meet the orders.

Unfortunately there is little we can do about this situation and in some cases all we can say is, be patient or try to find an alternative.

We are sure most readers are sensible enough, unlike us, to check items bought before leaving the shop. We all make mistakes and the person who made up the order was probably in a hurry and put his hand in the wrong box. Incidentally, the shop was only too willing to change the incorrect items, and the advert for the relay did not appear the following month. Taking into account what we have just said let us now look at the more obvious supply difficulties that may be encountered when buying for this month's constructionals.

Light to Sound Converter

Judging by the response to the *Electrolaugh*, many readers will want to make up the *Light to Sound Converter* just to experiment with and, as far as we can see, there are not likely to be any supply problems.

Two points worth noting however; the earpiece used is a small magnetic type and these are generally available for about 50p. This earpiece could be replaced by

a miniature loudspeaker provided its impedance is greater than about 75 ohms. The cost of such a speaker should be similar to that of the earpiece.

The simple light shield shown on the prototype unit is made of plastic tubing and some samples of this material and a price list have recently been sent to us from NCF Systems, 21A Bramble Street, Coventry, CV1 2HU. Telephone Coventry 26825. This firm will supply round or oval section white p.v.c. tube in one foot lengths; a list of various types of tube, together with prices is available from the above address, provided the request is accompanied by a s.a.e. The prices are reasonable; 5/8 inch diameter round section costs 7p per foot, and end caps for this size, should they be required, are 3p each.

The p.v.c. tubing is easier to work than s.r.b.p. tube, has a better finish and appears to be much cheaper.

Simple Multimeter

The cost of the resistors used in the *Simple Multimeter* is determined mainly by the tolerance used. Most people will find that +2 per cent types are suitable and, unless a large scale higher sensitivity meter is used there is little point in employing ±1 per cent resistors.

There should not be any difficulty in component supply—unless the demand causes a lack of meters again. The case we have used is generally available but a shallower style will provide a more compact, better looking meter if you can find a suitable size. Plastic cases, provided they are fairly tough, are eminently suited for this purpose. We would advise you to buy a good pair of test probes to make the leads up, there are a number of types available.

Wash Wipe

As stated in the text of the *Wash Wipe* article the relay used is fairly critical and the one specified should be obtained if possible, as we know that this one will work well in the circuit shown; Henry's Radio can supply this relay. If you resort to a similar type make sure it will work from 6 to 12 volts and that the coil resistance is not less than 120 ohms nor greater than about 500 ohms the contacts used should be suitably rated. After some requests for 6V operation car devices we have specifically modified this circuit so that with a minor alteration it will work with a supply as low as 5 volts (with the specified relay).

All other components for this item are readily available.

Automatic wiper operation when washers are used. For all 6 and 12V cars fitted with washers and self-parking wipers.

In these days of traffic jams, frequent road works and liberally salted roads, it has become essential to have some form of wind-screen washing device to avoid developing an opaque film over the whole of the screen. Furthermore, it is important to be able to operate the washer and the wiper simultaneously, and without fumbling for badly located switches. Unfortunately, very few cars have a combined switch or stalk for both functions, and even fewer allow both functions to be performed by a single movement of such a stalk.

The device described in this article controls both wiper and washers simultaneously from one spring-loaded electric washer switch or manual washer pump. More important, when the switch or pump is released, the washer stops but the wiper continues for a pre-determined number of strokes (which can be preset by a suitably located control). It is one of those accessories which, when fitted, makes you wonder how you ever managed without it!

OPERATION

The washer is operated directly by the hand-switch, in the case of electric types, or the hand pump. The wiper however, is controlled by a transistor circuit which is triggered on by the hand-switch or a microswitch operated by the pump, but which will not switch off until a certain preset time period has elapsed. The wiper must be of the self-parking type, and can of course, be operated independently by means of the normal wiper switch. The circuit will work on both 6V and 12V cars with only the minor modification which is described later.

DELAY CIRCUIT

The circuit diagram shown in Fig. 1 (excluding

WASH WIPE controller

By D.G. Howells

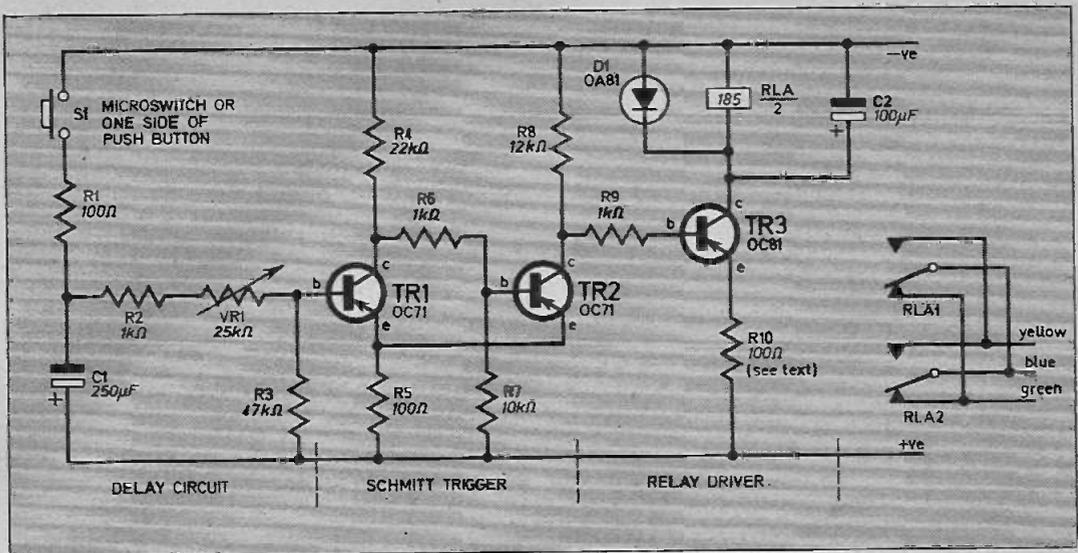


Fig. 1. Complete circuit diagram of the Wash Wipe Control. R10 is removed for 6V operation.

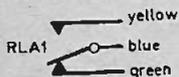


Fig. 2. Diagram showing how the relay contacts are shown in following Figs.


12 volt operation but can be modified for 6 volt operation if required. It can be considered as having three parts, as shown. The delay circuit feeds a Schmitt trigger which operates a relay driving transistor and hence the relay controlling the wipers.

When the washer switch or microswitch operated by the pump is closed, capacitor C1 charges rapidly via R1. Since the switch-on voltage of the Schmitt trigger is low, the trigger switches and the collector voltage of TR2 drops causing TR3 to switch on, thus operating the relay and hence the wipers.

When the hand-switch or pump is released, C1 can only discharge through R2, VR1, R3 and TR1 base, so that a short period, determined by the setting of VR1, elapses before the circuit reverts to its "normal" state. During this period TR3 is conductive, holding the relay on.

The value of VR1 determines the delay period

Fig. 3a. Wiring diagram of a single speed field coil wiper motor.

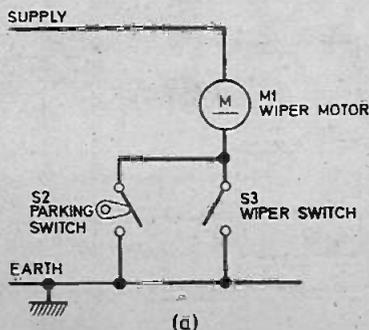

of the circuit and this can either be pre-set or variable, in which case it can be located on the fascia of the car to provide a control over the number of sweeps performed by the wiper. The time delay available is from approximately 1 second to 25 seconds; this could be increased by increasing the value of C1 or VR1 if required.


RELAY WIRING

Relay RLA1, used in the circuit is fairly critical and the recommended type should be used. This relay will work on a supply from 6 to 12 volts and resistor R10 is included in the circuit of the 12 volt system to limit the voltage applied. If this resistor is not fitted the relay may not turn off due to a small voltage across it.

The specified relay and circuit components will work on a supply as low as 5 volts provided R10 is left out and the emitter of TR3 connected to the positive supply. By altering the circuit in this way it can be used on cars with 6 volt electrical systems.

The contacts of the specified relay are rated at 2 amps and both sets are wired in parallel to

Fig. 3b. Method of connecting the controller to the circuit of 3a.

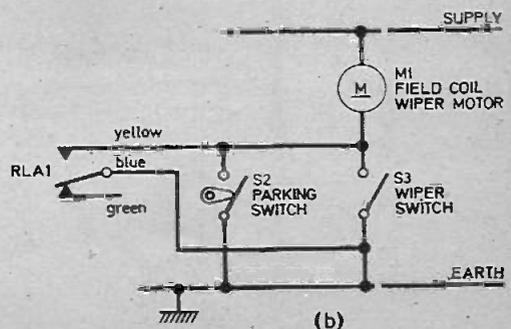

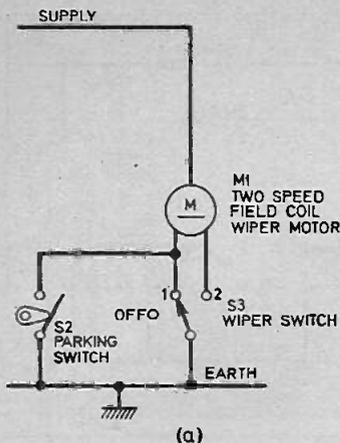


Fig. 4a. Wiring diagram of a 2 speed field coil wiper motor.

switch the wiper motor. Although some motors will draw more than 4 amps the relay is hardly ever used to break the connection as the self parking switch will carry the supply to the wipers until they are in the park position. Hence the contacts have been found to be adequate.

The circuit diagram of Fig. 1 shows both sets of contacts wired in parallel but to avoid unnecessary complication the following wiring diagrams will only show one set of contacts as in Fig. 2.

One point about the circuit is that it is switched on all the time the ignition is on, however current drain in the "standby" state is only 3mA and the life expectancy of the circuit in this state is extremely long. The supply must be taken from a point that is switched by the ignition switch.

WIPER MOTOR CIRCUIT

Not all self-parking wiper motors use the same circuit. Four common examples are shown in Fig. 3a, 4a, 5a and 6a. Fig. 3a shows a circuit

Fig. 5a. Circuit of a single speed permanent magnet wiper motor.

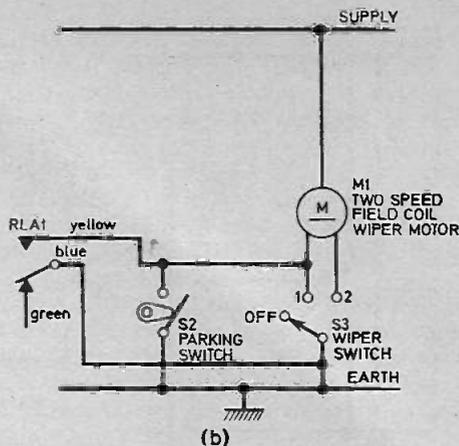
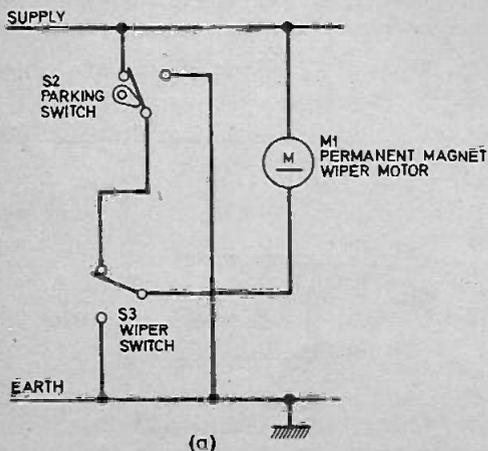


Fig. 4b. Method of connecting the controller to the circuit of Fig. 4a.

commonly used with single speed field coil motors—most cars over 3 years old use such a system. The self-parking switch operates in parallel with the hand-switch. If this type of motor is fitted, the relay should be connected as shown in Fig. 3b.


The circuit of Fig. 4a is used with a two-speed field coil motor. The control is wired up in a similar manner to Fig. 3b but only one speed can be used. The wiring is shown in Fig. 4b.

More recent cars (generally less than three years old) are fitted with permanent magnet wiper motors that have to be shorted to stop them quickly, Fig. 5a shows a common wiring system of a single speed permanent magnet wiper motor and Fig. 5b shows how it is wired to the Wash Wipe control.

Two speed permanent magnet motors are normally wired up as shown in Fig. 6a, the method for connecting the relay to this system is shown in Fig. 6b—the control can only be used with the first switched speed in this case.

It is particularly important that the contacts

Fig. 5b. Method of connecting the controller to the circuit of Fig. 5a.

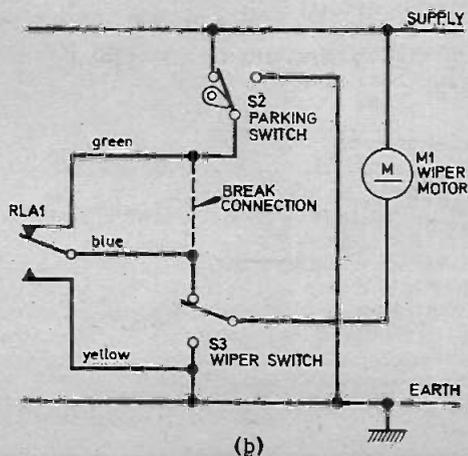

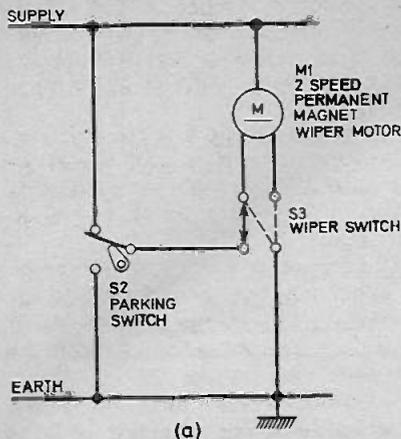


Fig. 6a. Circuit of a 2 speed permanent magnet wiper motor.

made to a permanent magnet wiper motor are correct, as the electrical system could be shorted out if the unit is fitted wrongly. Incidentally, it has been found that many garages and some manufacturers may give incorrect information concerning the type of motor fitted, this should be checked with the car manual and a wiring diagram if possible.

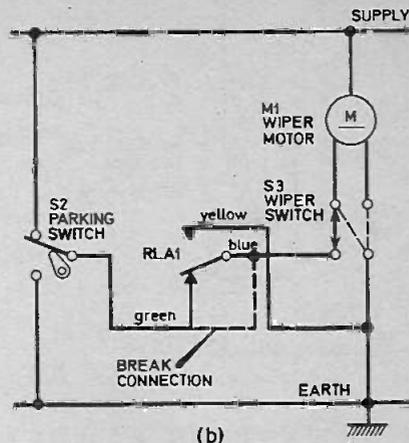


Fig. 6b. Method of connecting the controller to the circuit of Fig. 6a.

It is not possible to use the accessory satisfactorily with wipers that are controlled by a switch with a park position and do not park fully automatically, nor can it be satisfactorily used with wipers that are not self-parking.

If the previously published Wiper Control has been fitted the green, blue and yellow wires on both these devices can be connected together i.e. green to green etc., and both units can be used independently or the washer will override the delayed timing of the Wiper Control if both are used together.

Components....

Resistors

R1	100Ω
R2	1kΩ
R3	47kΩ
R4	22kΩ
R5	100Ω
R6	1kΩ
R7	10kΩ
R8	12kΩ
R9	1kΩ
R10	100Ω
All	±10%, ¼W. carbon

Capacitors

C1	250μF elect. 16V
C2	100μF elect. 16V

Semiconductors

TR1	OC71 germanium <i>pnp</i>
TR2	OC71 germanium <i>pnp</i>
TR3	OC81 germanium <i>pnp</i>
D1	OA81

Miscellaneous

S1	s.p.s.t. microswitch or d.p.s.t. press to make switch (see text)
VR1	25kΩ preset or log. variable potentiometer (see text)
RLA	PC2 CBB/12, 6/12V operated, 185Ω coil relay with 2 sets of changeover contacts. Connection blocks, 3 way 1 off and 6 way 1 off, Veroboard 0.15in matrix, 2½in x 1½in, connecting wire, metal for case or bracket and microswitch mounting—if used, 6BA fixings, stiff wire to operate microswitch.

SEE
**SHOP
TALK**

CONSTRUCTION

The delay circuit is wired on a piece of 0.15 inch matrix Veroboard approximately 2¼ inches by 1⅝ inches, as shown in Fig. 7. This can be mounted in a small aluminium box or on a bracket as shown, together with the relay and two connection blocks. All leads from the circuit board are taken to a plastic connecting strip. The leads should be of standard connecting wire, but of different colour combinations to assist identification. Leads from the relay to the connecting strip and from the strip to the wiper motor, should be of heavy gauge car connecting wire (green, blue and yellow wires).

The circuit panel should be made up first with all components and short (6 inch) flying leads attached—solder in the transistors last and use a heat shunt on each wire to protect the device from the heat of the soldering iron. Next, drill the bracket or box to hold the board and the two connecting strips, attach the flying leads to the board connecting strip and fix the board and strip in place using 6BA bolts with stand-off bushes under the board (Fig. 8).

Solder the connections to the relay RLA using heavy gauge car connecting wire, and affix the diode using a heat shunt and observing polarity. Glue the relay to the case or bracket and connect the green, blue and yellow wires to the relay connecting strip—fix this strip to the unit and

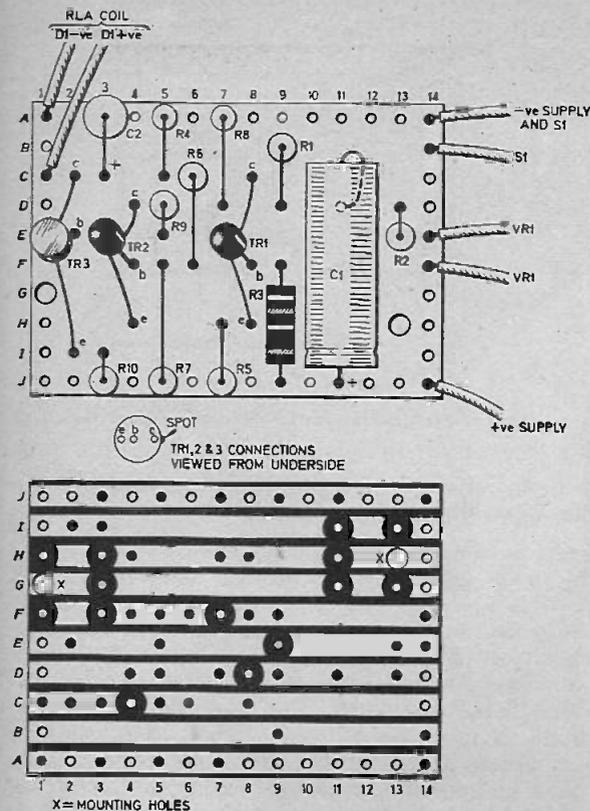


Fig. 7. Construction of the circuit board for the Wash Wipe Control.

all that remains to be done is to wire the unit to VR1, S1, the supply and the wiper motor circuit—again use heavy duty wire for the connections to the wiper motor.

When connecting the unit to an electric washer

system the existing washer switch should be replaced by a double-pole, single throw type, one side of this switch is used to control the washers and the other side is used to control the Wash Wipe.

The layout shown in Fig. 7 is for a 12V system. For a 6V system omit R10 and solder the collector wire of TR3 into hole J2 instead of hole I2. Then wire up the unit in the same way as for a 12V system.

The circuit board is bolted or screwed down wherever space can be found behind or near the facia. Make sure, however, that hot or cold air from the heater or vents is not directed around the unit and do not mount the unit in the engine compartment—no temperature compensation components are included in the circuit.


The hand-switch used for electric washers must be of the self-cancelling d.p.s.t. type (a spring loaded stalk-switch or push button can be bought at any good car accessory store),

If a manual pump system is used the micro-switch can be fitted under the dash panel and operated by a wire or lever that is depressed when the pump is fully depressed. An operating wire can be formed to a shape suitable for the particular system from a large paper clip.

The sweep control can be either a pre-set potentiometer fitted in the case or on the bracket or a variable control with knob, fitted in a convenient position on the dash panel. If a variable control is used a logarithmic type is recommended as this makes control easier over a short time period.

OPERATION

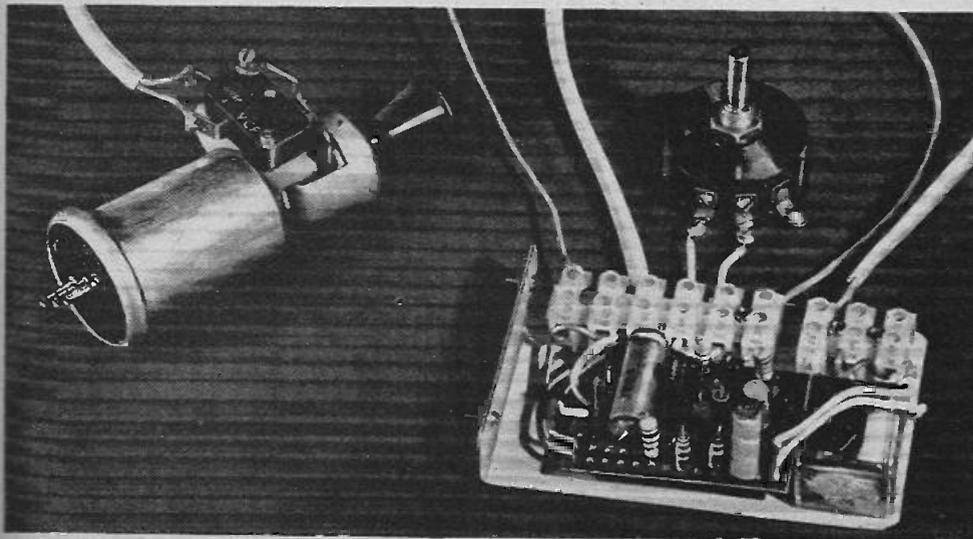Because of the variation in the characteristics of different OC71 transistors, the overall time delay available may vary but should be able to provide more than enough sweeps after the washer jet has stopped. □



The complete unit ready for installing in the car.

WASH- WIPE Controller



Approximate
cost of
components
£2.20 plus case

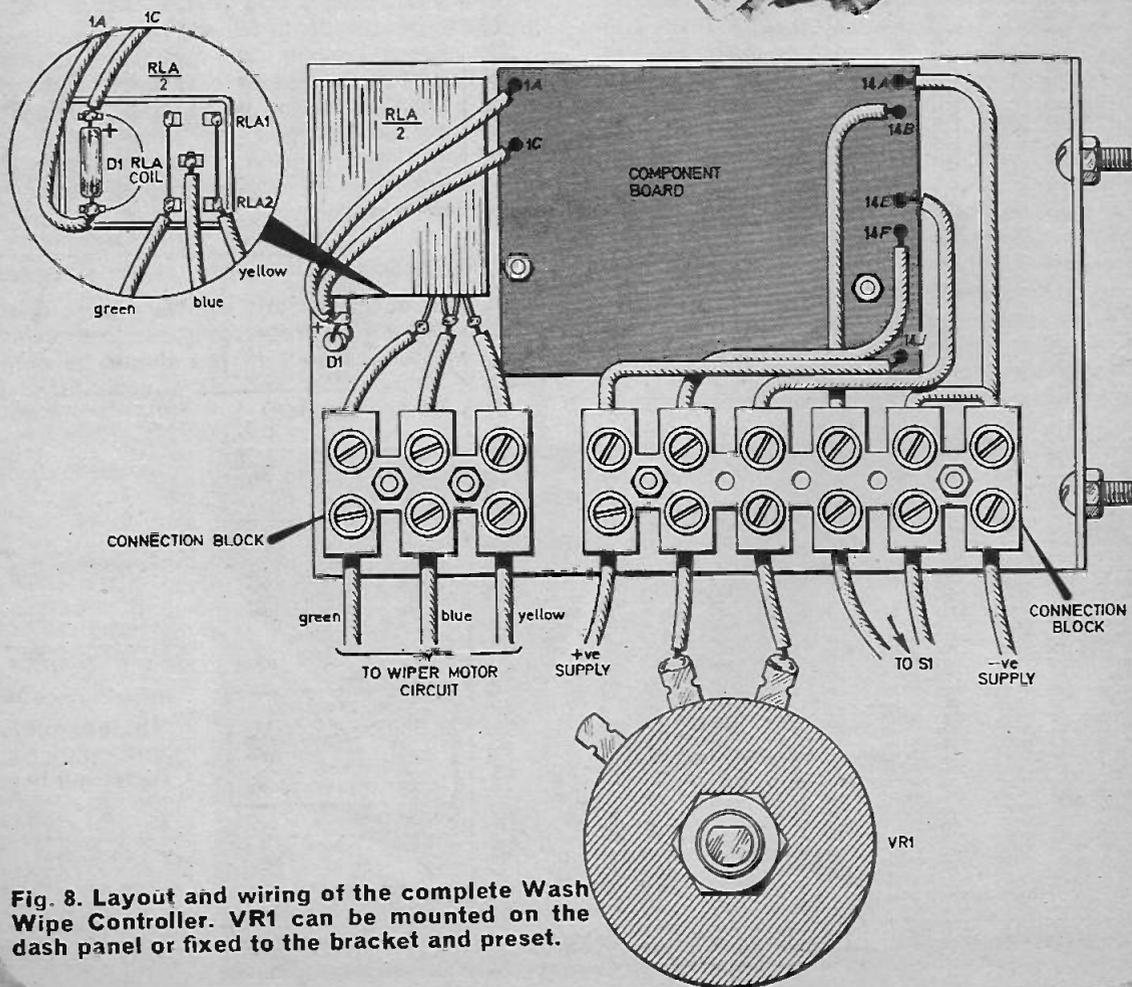
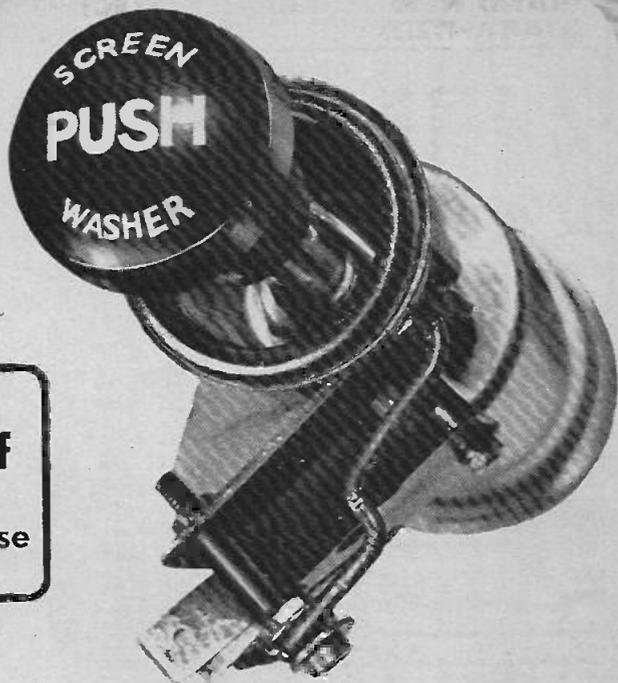


Fig. 8. Layout and wiring of the complete Wash Wipe Controller. VR1 can be mounted on the dash panel or fixed to the bracket and preset.

**BRAND NEW
GUARANTEED**

**LARGEST SELECTION OF SEMICONDUCTORS
COMPONENTS**

**RETURN OF POST
SERVICE**

TRANSISTORS

2C301	20p	2N3404	32p	40310	45p	BC121L	18p	8BX28	32p	NKT281	27p
2C302	20p	2N3405	32p	40311	45p	BC122	18p	8BX30	32p	NKT281	27p
2G303	20p	2N3414	22p	40312	47p	BCY31	30p	8BX61	62p	NKT402	30p
2G306	42p	2N3415	22p	40314	37p	BCY32	50p	8BX76	22p	NKT403	75p
2G303	30p	2N3416	27p	40320	27p	BCY33	25p	8BX77	27p	NKT404	62p
2G309	30p	2N3417	37p	40323	32p	BCY34	30p	8BX78	27p	NKT405	75p
2G371	15p	2N3470	11.25	40324	47p	BCY38	40p	8BX10	27p	NKT406	62p
2G374	15p	2N3471	11.25	40325	37p	BCY39	30p	8BX19	27p	NKT451	62p
2G381	22p	2N3605	27p	40329	30p	BCY40	50p	8BY24	15p	NKT452	62p
2N404	22p	2N3606	27p	40344	27p	BCY42	15p	8BY25	15p	NKT463	47p
2N696	20p	2N3607	22p	40347	57p	BCY43	15p	8BY26	17p	NKT603F32p	
2N697	17p	2N3702	11p	40348	57p	BCY54	32p	8BY27	17p	NKT618F32p	
2N698	25p	2N3703	10p	40360	42p	BCY58	22p	8BY28	17p	NKT674F30p	
2N705	15p	2N3704	11p	40317	47p	BCY72	22p	8BY29	17p	NKT777F30p	
2N705A	15p	2N3708	10p	40362	57p	BCY60	97p	8BY32	25p	NKT781F30p	
2N708	15p	2N3706	09p	40370	82p	BCY70	20p	8BY36	25p	NKT781F30p	
2N709	62p	2N3707	11p	40406	37p	BCY71	25p	8BY37	25p	NKT1041030p	
2N718	25p	2N3708	07p	40407	40p	BCY72	17p	8BY39	22p	NKT10439p	
2N726	30p	2N3709	09p	40408	52p	BCZ10	27p	8BY39	22p		37p
2N727	30p	2N3710	09p	40410	62p	BCZ11	42p	8BY40	32p	NKT10519	32p
2N914	17p	2N3814	15p	40467A	37p	BD116	41-12p	8BY41	32p	NKT20339p	32p
2N916	17p	2N3715	11.25	40488A	85p	BD121	85p	8BY52	32p		
2N918	30p	2N3716	11.30	40600	57p	BD123	82p	8BY53	37p		47p
2N929	22p	2N3791	12.08	AC107	30p	BD124	80p	8BY54	40p	NKT20339p	37p
2N930	27p	2N3819	35p	AC126	20p	BD131	75p	8BY56	90p		37p
2N1090	22p	2N3823	37p	AC127	25p	BD132	85p	8BY58	47p	NKT80111	37p
2N1091	22p	2N3854	27p	AC128	25p	BD170	41-21	8BY59	50p	NKT80112	37p
2N1131	25p	2N3854A	27p	AC154	22p	BD111	41-62	8BY82	52p	NKT80113	37p
2N1132	25p	2N3855	27p	AC176	25p	BDY17	11-50	8BY90	57p		97p
2N1302	17p	2N3855A	30p	AC187	62p	BDY18	11-75	8BY95A	42p	NKT80113	11.12
2N1303	17p	2N3856	30p	AC188	67p	BDY19	11-97	8BY94	12p		11.12
2N1304	25p	2N3856A	35p	AC177	27p	BDY20	11-121	8BY97	27p	NKT8021	92p
2N1305	25p	2N3857	30p	AC178	25p	BDY21	11-121	8BY97	27p	NKT80212	92p
2N1306	25p	2N3858A	30p	AC199	25p	BDY60	41-25	C424	27p		92p
2N1307	35p	2N3859	27p	ACY20	25p	BDY61	41-25	C425	55p		92p
2N1308	30p	2N3859A	32p	ACY21	25p	BDY62	41-00	C426	40p	NKT80213	92p
2N1309	30p	2N3860	30p	ACY22	30p	BF116	25p	C428	37p		92p
2N1307	30p	2N3860	11.50	ACY28	20p	BF117	47p	C744	30p	NKT8021	92p
2N1613	92p	2N3914	15p	ACY161	35p	ACY161P1	35p	DI16P1	35p	NKT80215	92p
2N1631	35p	2N3877A	40p	ACY41	25p	BF167	18p	DI16P2	40p	NKT80215	92p
2N1632	30p	2N3900	37p	ACY44	40p	BF173	18p	DI16P3	37p	NKT80216	92p
2N1638	27p	2N3900A	40p	AD140	52p	BF177	30p	DI16P4	40p	NKT80216	92p
2N1639	27p	2N3901	37p	AD149	57p	BF178	30p	GET102	30p		92p
2N1671B	41.00	2N3903	35p	AD150	62p	BF179	30p	GET113	20p		75p
2N1711	25p	2N3904	35p	AD161	62p	BF180	30p	GET114	20p		75p
2N1789	32p	2N3905	37p	AD162	87p	BF181	32p	GET118	20p		75p
2N1893	37p	2N3906	37p	AF106	42p	BF184	25p	GET119	20p		75p
2N2147	82p	2N4058	17p	AF114	25p	BF185	42p	GET120	52p		62p
2N2148	57p	2N4059	10p	AF115	25p	BP194	17p	GET126	27p		62p
2N2150	57p	2N4060	13p	AF116	25p	BP195	15p	GET180	30p		62p
2N2193	42p	2N4061	13p	AF117	25p	BP196	15p	GET181	30p		62p
2N2193A	42p	2N4062	15p	AF118	62p	BP197	42p	GET189	22p		62p
2N2194A	30p	2N4244	47p	AF119	25p	BF198	42p	GET190	22p		62p
2N2217	27p	2N4285	17p	AF124	22p	BP200	52p	GET196	22p		62p
2N2218	27p	2N4286	17p	AF125	20p	BP224	14p	GET197	22p		62p
2N2219	27p	2N4287	17p	AF126	20p	BP225	18p	GET198	22p		62p
2N2220	27p	2N4288	17p	AF127	22p	BP246	22p	GET206	11.50		62p
2N2221	25p	2N4289	17p	AF139	37p	BF238	23p	MJ420	11-121		62p
2N2222	30p	2N4290	17p	AF178	42p	BF244	23p	MJ421	11-121		62p
2N2270	47p	2N4391	17p	AF179	72p	BFW61	47p	MJ430	41-02		62p
2N2297	30p	2N4292	12p	AF180	52p	BFX12	22p	MJ440	95p		62p
2N2298	17p	2N4303	47p	AF181	42p	BFX13	22p	MJ480	97p		62p
2N2369	27p	2N4304	47p	AF182	42p	BFX32	30p	MJ481	11-35		62p
2N2369A	17p	2N6025	57p	AF279	47p	BFX30	30p	MJ480	10p		62p
2N2410	42p	2N6029	47p	AF280	62p	BFX42	37p	MJ491	41-87		62p
2N2483	27p	2N6030	42p	AF211	22p	BFX44	37p	MJ1800	42-17		62p
2N2484	32p	2N6173	12p	AFY26	25p	BFX68	67p	MJE340	62p		62p
2N2529	22p	2N6174	52p	AFY27	37p	BKX84	35p	ME620	60p		62p
2N2540	22p	2N6175	52p	AFY28	37p	BKX85	35p	ME625	60p		62p
2N2613	35p	2N6176	52p	AFY29	27p	BFX86	25p	MFF102	45p		62p
2N2614	30p	2N6242A	40p	AFY38	25p	BFX87	27p	MFF103	37p		62p
2N2634	62p	2N6245	45p	AFY50	25p	BFX88	25p	MFF104	37p		62p
2N2636	32p	2N6246	42p	AFY51	32p	BFX89	25p	MPP105	37p		62p
2N2711	25p	2N6249	67p	AFY54	25p	BFX93A	70p	MPP3638	32p		62p
2N2712	25p	2N6256	42p	AFY55	25p	BFY10	82p	NKT213	47p		62p
2N2713	30p	2N6266	42.75	AD103	41.25	BFY11	48p	NKT123	27p		62p
2N2714	30p	2N6267	42.82A	ASZ21	42p	BFY12	22p	NKT125	27p		62p
2N2865	62p	2N6305	37p	BC107	10p	BFY18	32p	NKT126	27p		62p
2N2904	30p	2N6306	40p	BC108	10p	BFY19	32p	NKT128	27p		62p
2N2904A	32p	2N6307	37p	BC109	10p	BFY20	42p	NKT135	27p		62p
2N2905	37p	2N6308	37p	BC113	15p	BFY21	42p	NKT137	32p		62p
2N2905A	47p	2N6309	42p	BC115	15p	BFY24	45p	NKT210	30p		62p
2N2906	25p	2N6310	48p	BC116A	15p	BFY25	25p	NKT211	30p		62p
2N2906A	27p	2N6314	27p	BC118	10p	BFY26	20p	NKT212	30p		62p
2N2907	30p	2N6335	27p	BC121	20p	BFY29	50p	NKT213	30p		62p
2N2923	15p	2N6368	32p	BC122	20p	BFY30	50p	NKT214	22p		62p
2N2924	15p	2N6369	32p	BC125	20p	BFY41	50p	NKT215	22p		62p
2N2925	15p	2N6368	32p	BC126	20p	BFY43	62p	NKT216	22p		62p
2N2926	15p	2N6367	32p	BC140	47p	BFY50	20p	NKT217	42p		62p
2N2926	15p	2N6368	32p	BC141	47p	BFY51	20p	NKT219	30p		62p
2N2926	15p	2N6369	32p	BC148	10p	BFY52	20p	NKT223	27p		62p
2N2926	15p	2N6370	32p	BC149	12p	BFY73	17p	NKT224	27p		62p
2N2926	15p	2N6371	32p	BC152	15p	BFY86A	57p	NKT225	27p		62p
2N2926	15p	2N6372	32p	BC157	20p	BFY87	20p	NKT226	27p		62p
2N2926	15p	2N6373	32p	BC158	11p	BFY78	42p	NKT227	35p		62p
2N2926	15p	2N6374	32p	BC159	12p	BFY77	57p	NKT238	35p		62p
2N2926	15p	2N6375	32p	BC160	62p	BFY90	67p	NKT340	27p		62p
2N2926	15p	2N6376	32p	BC167	11p	BFY90	67p	NKT341	27p		62p
2N2926	15p	2N6377	32p	BC168	10p	BFY91	17p	NKT342	27p		62p
2N2926	15p	2N6378	32p	BC169C	10p	BFY90	67p	NKT343	27p		62p
2N2926	15p	2N6379	32p	BC170	12p	BFY95	11p	NKT344	27p		62p
2N2926	15p	2N6380	32p	BC171	12p	BFY95	11p	NKT345	27p		62p
2N2926	15p	2N6381	32p	BC172	15p	BFY95	11p	NKT346	27p		62p
2N2926	15p	2N6382	32p	BC173	15p	BFY95	11p	NKT347	27p		62p
2N2926	15p	2N6383	32p	BC174	15p	BFY95	11p	NKT348	27p		62p
2N2926	15p	2N6384	32p	BC175	15p	BFY95	11p	NKT349	27p		62p
2N2926	15p	2N6385	32p	BC176	15p	BFY95	11p	NKT350	27p		62p
2N2926	15p	2N6386	32p	BC177	15p	BFY95	11p	NKT351	27p		62p
2N2926	15p	2N6387	32p	BC178	15p	BFY95	11p	NKT352	27p		



Photograph: Science Museum London

LAST month in the introduction to the series we saw that electric current as we now understand it was unknown and, that electrical experiments were based on the forces of attraction and repulsion. Then in 1798 Alessandro Volta, an Italian Physicist, after whom the Volt (see Table 1) is named, produced his galvanic battery. But first, like Volta, we must hear the legend of the "frogs thighs".

GALVANI'S DINNER

One evening in 1790 Aloisio Galvani, Professor of Medicine at Bologna was patiently waiting for his wife to finish preparing his favourite dinner, a delicacy of frogs thighs. To skin the frogs the good lady had borrowed one of her husbands instruments. As she was finishing the last thigh the scalpel fell from her hand on to the rear nerve of the frog's thigh and at the same time touched the plate. Immediately the skinned thigh stretched and jumped away, Senora Galvani repeated her actions several times before drawing her husbands attention to the mystery, he immediately "took charge" and exclaimed "I have discovered animal electricity the primary source of life". As news of this incident spread no frog was safe as experiments with them became the rage of Bologna.

Volta at that time, Professor of Physics at Pavia, did not believe in Galvani's animal electricity, he reasoned that the frogs legs played no part in the phenomenon other than providing moisture and that the electricity was produced by the steel of the scalpel and the tin plate set in a moist medium.

Everyday Electronics, June 1972

THEY MADE THEIR MARK NO2 VOLTA

By J. E. Gregory

Table 1. THE VOLT (V)

The volt is the unit of electrical potential or "pressure". It can, perhaps, be most clearly understood by comparing it with water pressure. The higher a water tank is from a tap, the greater the water pressure at the tap. Similarly, with electricity the higher the voltage of a battery or generator, the higher the electric pressure at its output terminals. The unit was named after Volta in 1836 and was adopted very slowly until it received international recognition in 1881, when it was one of the first practical units to be approved by the International Electrotechnical Committee.


Volta pondered on his discovery and set about reproducing and multiplying the effect, he piled a large number of zinc and copper discs separated by moistened cardboard discs on top of one another so that the zinc of each pair was in direct contact with the copper of its neighbour. Volta found the pile gave a shock when opposite ends were touched simultaneously.

The modest Volta called his pile the Galvanic Battery after the old Professor. This pile which generated electricity without any external aid was the start of a new era in electrical science, and was the first electric battery in the modern sense.

Volta's fame grew and he constantly travelled throughout Europe demonstrating his electrical experiments. In 1801 Napoleon fresh from his conquests of the Austrian forces summoned him to Paris, so impressed was Napoleon that he had a special medal struck in Volta's honour. Other honours quickly followed. Senator of the Kingdom Lombardy, the Copley medal of the Royal Society, and in 1815 the Emperor of Austria made him a director of the faculty of Padua.

BRITISH ASSOCIATION

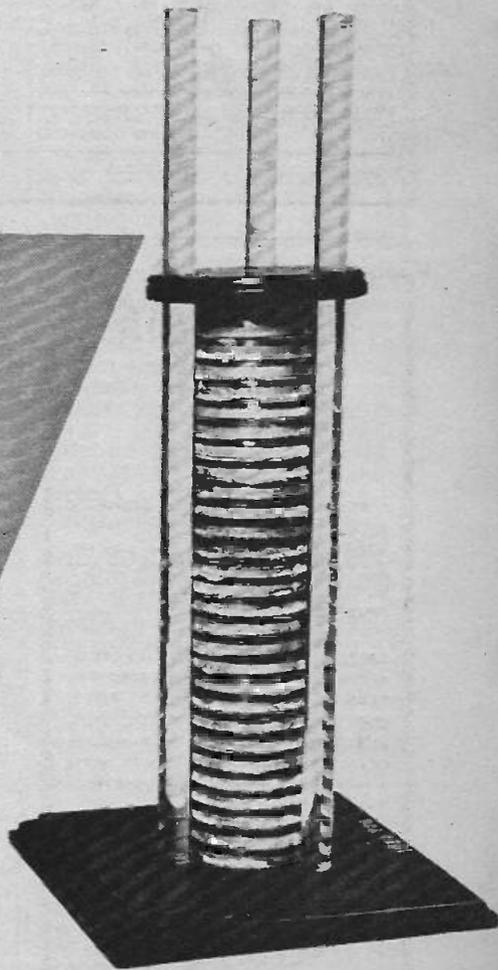Before he died Volta made a journey to London to attend a British Association Meeting at which he presented a Voltaic pile to Michael Faraday, but more of him and the farad in a later article.



Volta's Pile.

Photograph Crown Copyright Science Museum London

REMEMBER
TO USE THE
POSTCODE



Readers Letters

Electronic Lib

I am writing in response to your appeal to hear from some lady enthusiasts. I have been working in electronic factories for the past five years assembling printed circuit boards and doing point to point wiring, but in the last year or so I have become quite suddenly very interested in electronics (if you get my meaning). Since then I have been searching my local library for books on electronics that were not too advanced, and having got through the few that were there, I was just beginning to think that it was the end of the road in my quest to learn and understand electronics, when along came the first issue of EVERYDAY ELECTRONICS.

Here at last a magazine that was starting right at the beginning and, what was more important, one I could understand. So far I have had all issues and will continue to do so. I have not yet attempted any of the projects but I am hoping to do so in the near future, for having just taken advantage of your electronic tool-kit offer I am just about ready to venture into the very exciting world of electronics.

Many thanks for such an interesting and worthwhile magazine.

Miss J. Pledger
Basingstoke, Hants.

You have obviously got a great advantage over many "beginners" as, in the constructional techniques, you are a professional! We wish you success with future projects.

And Daughter

I have just managed to get hold of my April 1972 copy of your magazine (yes! in future it will be ordered) and read with interest a wife's view of her husband's hobby (*Wifely Woes*—June Burn). I will have to try and persuade my husband to present his side as I am the enthusiast in this family. I started evening classes for Radio and T.V. (Beginners) in September last year and found myself at sea among a lot of men who, though calling themselves

beginners, obviously had a good background of knowledge which I lacked. I saw the first copy of your magazine and realised that this was just what I was looking for—instruction and constructional projects.

Last week I completed the *Snap Sequence Indicator* (even made a wooden box for it!) and it works—to the delight of my family and the incredulous amusement of our friendly neighbourhood electrician who helped me to get the components.

By the way, my enthusiastic assistant in this has not been my husband or son, but my ten year old daughter Lizzie.

Mrs. J. V. Devaney,
Lee, S.E.12.

These two letters show that the hobby is not one sided—we wish all ladies success.

15p Effort

I have purchased so far all four copies of your new magazine, and find them most interesting. I have completed the *Signal Injector* in one afternoon and it gives good service. I was very disappointed in your answer to Mr. M. D. McMahon's letter (April issue).

Your magazine should include articles about servicing and modification, improvements and additions to commercial or any available equipments. Also, you have not given an answer to the questions raised in the letter. As you stated, the servicing problem is a vast one, but you could give helpful advice or information to amateurs. The servicing trade is slow and expensive and other radio magazines have articles about maintenance.

Your categorical statement that "you" cannot and will not include such articles led me to the decision, that I cannot and will not be interested to have a subscription of your magazine unless you make an effort for the 15p.

The metrication is on the way for this country, and if you or readers like it or not, eventually you will have to learn it.

W. A. Alexander
Bristol.

More Metric

May I add my plea to that of M. D. McMahon's for metric sizes, most B.S. specifications have already been metricized and we shall all have to use metric in the near future; clearly the shorter transition period the better, magazines such as yours could help in this respect.

Naturally no magazine cares to risk upsetting their readers but as I see it anyone unable to readily understand and appreciate anything so simple as metric measurements would not be able to understand the subject matter of your or any other book and would presumably not buy them in the first place.

F. Trusson
Essex.

May I just say how much I have enjoyed reading your magazine EVERYDAY ELECTRONICS right from the first issue. The magazine arrived on the bookstalls exactly at the right time for me. I started my first year at evening classes for O.N.C. last September, and as I do not work in the electrical field the practical aspect of E.E. is just what I require to put principles into practice.

I would like to compliment you on the excellent way in which the *Teach-In* feature is progressing, it has been a great help.

I would also like to second the suggestion made last month that S.I. units can be used throughout E.E. in future.

J. E. Farrer
London, E.6.

With regard to the comment made by M. D. McMahon in the April 1972 edition of EVERYDAY ELECTRONICS, I agree entirely about the use of metric measurement. At school, it is almost a crime to use inches and feet, or pounds and ounces, in the Maths or Physics lesson. Thus, I am completely lost when doing calculations using these units. Also throughout my components catalogues centimetres and millimetres are used for dimensions of components, this can be annoying when looking for the right size component.

I have successfully completed your *Signal Injector*. As relatively new to electronics, I hope to do either the *D.C. Power Supply* or the *Audio Tone Generator* next, depending on costs. The costs are my main problem, as a schoolboy it is not easy to find £5. I do appreciate when something, like the signal injector, comes up which is cheap and the case costs nothing, also I must commend you on an ability to create attractive and purposeful cases at reasonable costs.

The *Baby Alarm* which is
Everyday Electronics, June 1972

NATION WIDE SERVICE + ATTRACTIVE DISCOUNTS

ELECTROVALUE—an independent company since its establishment in 1965

ELECTROVALUE

Electronic Component Specialists

SEMI-CONDUCTORS

Brand new, guaranteed to spec. No seconds or surplus.

1B40K10	175p	2N2925	18p	2N5165	30p	AD142	50p	BC149	10p	BF167	18p	NKT212	25p
1N914	5p	2N5226	11p	2N5172	30p	AD149	50p	BC163	15p	BF173	19p	NKT213	25p
1N316	10p	2N3053	27p	2N5191	70p	AD150	60p	BC164	15p	BF277	25p	NKT214	25p
1N1763A	24p	2N3054	45p	2N5196	90p	AD161	25p	BC167	12p	BF178	31p	NKT217	50p
1N3754	20p	2N3055	60p	2N5457	30p	AD162	38p	BC168	11p	BF184	14p	NKT261	21p
1N5399	24p	2N3225	51p	2N5459	30p	*AD161/162	60p	BC159	12p	BF195	15p	NKT271	18p
1N5402	25p	2N3405	40p	49250	71p	AF114	24p	BC167	11p	BF244	30p	NKT274	18p
1N5407	35p	2N3662	65p	40251	89p	AF115	24p	BC168	10p	BF254	14p	NKT275	25p
1844	5p	2N3702	10p	40361	45p	AF116	45p	BC169	11p	BF265	15p	NKT403	65p
18940	5p	2N3703	10p	40362	45p	AF117	45p	BC177	12p	BF289	18p	NKT404	81p
2N696	17p	2N3704	10p	40406	58p	AF118	82p	BC178	12p	BF294	30p	NKT603F	70p
2N697	18p	2N3705	10p	40408	54p	AF124	24p	BC179	11p	BF339	25p	NKT612F	30p
2N706	12p	2N3706	10p	40412	67p	AF125	24p	BC182L	11p	BF365	35p	NKT612F	30p
2N990	21p	2N3707	8p	40430	122p	AF126	20p	BC188	10p	BF387	29p	NKT674P	24p
2N1181	25p	2N3708	8p	40432	180p	AF127	22p	BC194L	11p	BF388	26p	NKT677F	22p
2N1182	25p	2N3709	10p	40512	179p	AF129	22p	BC186	32p	BF390	25p	NKT713	30p
2N1302	19p	2N3710	10p	40602	47p	AF239	36p	BC192L	14p	BF391	26p	NKT773	25p
2N1303	19p	2N3711	10p	40669	120p	AL102	77p	BC213L	15p	BF392	23p	OA47	8p
2N1304	20p	2N3731	180p	AC107	44p	AY26	27p	BC214L	14p	BF393	30p	OA90	6p
2N1306	20p	2N3810	15p	AC126	22p	AY27	36p	BC287	9p	BF394	16p	OA91	5p
2N1307	35p	2N3820	52p	AC128	30p	AY28	37p	BC288	8p	BF395	16p	OA95	6p
2N1308	36p	2N3904	18p	AC141H	84p	AT111	87p	BC267	17p	BF398-300	37p	OC19	10p
2N1309	36p	2N3906	20p	AC141HK	77p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N1906	76p	2N4036	42p	AC142H	25p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N1909	76p	2N4058	13p	AC142HK	25p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N1913	20p	2N4059	11p	AC153K	16p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N1917	26p	2N4060	11p	AC176	17p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N1893	54p	2N4061	11p	AC176K	17p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2147	114p	2N4062	11p	AC187K	17p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2218	33p	2N4124	16p	AC188K	23p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2218A	44p	2N4126	22p	*AC187K/188K	40p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2219	39p	2N4284	15p	AC17	31p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2219A	51p	2N4288	15p	AC17	31p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2270	62p	2N4289	15p	AC17B	19p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2369A	19p	2N4291	15p	AC17C	23p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2483	35p	2N4292	15p	AC17D	20p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2484	42p	2N4410	24p	AC17E	21p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2486	47p	2N4483	89p	AC17F	18p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2904	38p	2N4906	27p	AC17G	63p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2904A	42p	2N4916	27p	AC17H	17p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2905	44p	2N4991	44p	AC17I	18p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2906A	47p	2N5062	42p	AC17J	16p	B30C250/300	34p	BC269	49p	C762	17p	OC25	42p
2N2924	16p	2N5088	48p	AD140	65p	BC148	9p	BF113	28p	NKT211	25p	* Matched pair	

1972 ELECTROVALUE CATALOGUE (No.6)

Biggest and best edition yet—96 pages, plus covers. Well printed and generously illustrated, packed with hundreds of items at keen prices, valuable information and diagrams post free 10p.

DISCOUNTS

allowed on all items other than those at NETT prices.

10% on orders for £5 or more 15% on orders for £15 or more

POSTAGE & PACKING FREE on orders for £2.00 or more. Please add 10p if under. Overseas orders welcomed. Prices subject to alteration without prior notice.

Terms of business—C.W.O. as in catalogue

We are now approved distributors for ELMCO SOLDERSTAT SOLDERING IRONS

A popular and beautifully made lightweight example from a wide and versatile range of soldering irons of exceptional quality. Type HM5 for 16 or 24 watts, A.C. mains. £1.85

Solderstat Infinitely Variable Temperature Controlled Soldering Iron. Stays constant at desired temperature. For printed circuits, delicate work etc. complete £8.40. De soldering braid per 6 ft.—47p.

SLIDER POTENTIOMETERS

In usual values from 47K to 1 megohm, log or linear. Robust construction, smooth action, etc. 26p. Slider control knobs—Black/Red/Yellow/Green/Blue/Lt Gray/Dk Grey/White, each 5p.

CAPACITORS

SIEMENS 5% TOLERANCE POLYCARBONATE 250V. up to 0.1µF: 100V 0.1µF and above. 0-01; 0-012; 0-015; 0-018; 0-022; 0-027; 0-033; 0-047; 0-056, each 3p. 0-068; 0-082; 0-1; 0-12; 0-15 each 4p. 0-018; 0-22; 0.45; 0.5p; 0-27; 0-33; 6p; 0-39 7p; 0-47; 8p; 0-56; 10p; 0-68; 11p; 1µF 13p.

SIEMENS ELECTROLYTIC with axial leads: Values in µF/V m 0-47/100; 1/100; 2/263; 4/735; 10/25; 22/16; 47/10; 47/25; 100/10; 220/3; each 5p. 10/63; 22/35; 47/35; 100/16; 100/25; 220/6; 220/10; 220/16; 470/3, each 6p. 47/50; 47/63; 100/35; 470/10, each 7p. 100/50; 220/35; 9p; 100/63; 470/25; 100/10, ea. 10p. 220/63; 470/35; 1000/16, ea. 14p. 1000/25; 16p; 470/63; 1000/35; 19p; 2000/200; 29p; 1000/63; 2200/35; 4700/16, ea. 13p.

MULLARD SUB-MIN ELECTROLYTICS C426 range, axial lead 6p each Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/10; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/3.2; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 152/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

LARGE CAPACITORS High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, 114p; 2500/64, 77p; 2500/70, 98p; 5000/25, 62p; 5000/50, 110p; 5000/100, 129p.

Simple to Build, Astonishingly Good 10W/150 BAXENDALL SPEAKER

As originally designed by P. J. Baxendall and described in Wireless World. 10 watt/15 ohm loudspeaker with equaliser network speaker unit and specially designed cabinet in kit form. Size when built approx. 18" x 12" x 10". Price inc. carriage paid in U.K. Nett £13.81.

Speaker unit and equaliser kit with instructions £4.81 Cabinet kit, all parts cut to size ready to assemble, in natural teak finish £9.00

HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES

40p. HANDBOOK OF TESTED TRANSISTOR CIRCUITS (H. Nass), 40p. RADIO & ELECTRONICS Colour codes & data wall chart. 15p. ENGINEERS REFERENCE HANDBOOK & TABLES 20p. (Add 3p. for postage on each of above if bought separately.)

CARBON TRACK POTENTIOMETERS, long spindle

Double wipers SINGLE GANG linear 100 Ω to 2.2M Ω, 12p; Single gang 0.6-4.7K Ω to 2.2M Ω, 12p; Dual gang linear 4.7K Ω to 2.2M Ω, 42p; Dual gang log. 4.7K Ω to 2.2M Ω, 42p; IM Ω only 42p; Dual antilog, 10K only, 42p. Any type w/ 2A D.P. mains switch, 12p extra.

Only Decades of 10, 22 & 47 available in ranges quoted. DUAL CONCENTRIC in any combination of above values. 60p; with switch, 72p.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only: 100 Ω, 220 Ω, 470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω. Vertical or horizontal mounting, 5p each.

ZENER DIODES 5% full range E24 values: 400mW: 2-7V to 36V, 15p each; 1W, 6-8V to 82V, 27p each; 1-5W: 4-7V to 75V, 48p each.

Clip to increase 1-5W rating to 3 watts (type 266F). 4p.

RESISTORS—10%, 6%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	9	0-8	7
C	1/8W	5%	4.7 Ω-470K Ω	E24	1	0-8	0-7
C	1/4W	10%	4.7 Ω-10M Ω	E12	1	0-8	0-7
C	1/2W	5%	4.7 Ω-10M Ω	E24	1-2	1	0-9
C	1W	10%	4.7 Ω-10M Ω	E12	2-5	2	1-8
C	1W	2%	10 Ω-1M Ω	E24	4	3	2net
MO	1/2W	10%	0.22 Ω-3.9 Ω	E12	7	7	6
WW	3W	5%	1 Ω-10K Ω	E12	7	7	6
WW	7W	5%	1 Ω-10K Ω	E12	7	7	8

Codes: C = carbon film, high stability, low noise. MO = metal oxide, Electroisil TRS, ultra low noise. WW = wire wound, Plessey. Values in series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

NEW MARKET LINEAR I.C.s IC 709 C/14 Dual in line 34p. IC 741 C/14 Dual in line 40p.

.C. SOCKETS (low cost) 14 way 14p; 16 way 15p. In-line or staggered pin arrangements available

MAIN LINE AMPLIFIER KITS 70 watt power amp, module kit. £12.60 nett. Power supply kit, £6.50 nett. Matching pre-amp kit, £3.30 nett. (Above prices for mono.) Stereo kit, 2 power amps, pre-amp kit, power supply kit and matched controls for building into your own cabinet, £38.90 nett.

THERMISTORS VAI039, VAI040, VAI055, VAI066, VAI077, CZ-6, K151-IK, VAI100, 15p. R24, R53, R54, £1-35.

INSULATED SCREW TERMINALS in range of seven colours, each 11p. Matching plugs: 2mm, each 4p; 4mm, each 6p.

MINIATURE TOGGLE SWITCHES 2A/250V. DP/DT 48p.

ELECTROVALUE

DEPT. EE572, 28 St. Judes Road, Englefield Green, Egham, Surrey. TW20 0HB
Hours: 9-5.30, 1.0 p.m. Saturdays.
Phone: Egham 5533 and 4757 (STD 0784-3) Telex 264475

DISTRIBUTION PANELS

Just what you need for work bench or lab 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2-25 plus 25p P. & T.

MULTI-SPEED MOTOR
Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000; 12,000 & 16,500 r.p.m. shaft is 1/2 in. diameter 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price 88p plus 25p postage and insurance.

MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.

TELEPHONE HAND SET

Ex-G.P.O. Perfect order. 50p each + 20p P. & P.

12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 250/240V mains transformer with full wave rectifier and 2000 mfd/50 smoothing. Price £1-50 plus 20p post & packing.

NEW LIGHT DIMMER

This uses the latest technique from America, a self triggering device known as the thermo tab and has enabled us to produce a really reliable dimmer at a remarkably low price—namely £2-60 each or 10 for £22-50.

DRY FILM LUBRICANT

Dry Film Lubricant. In aerosol can for easy application and for putting lubricant into places where the normal oil can cannot reach. Home and everyday use. We have purchased a large quantity of these from the Liquidator and are able to offer them to you for about half of the original list price. 20p per (8 oz.) can or 12 cans for £3 post paid. The lubricant is I.C.I. fluid L169.

CARD OPERATED SAFE

All electronic parts to make this £4-50.

AMPLIFIER CASE

Teak veneer on 1/2 ply, modern appearance and design. Size—front 13" x 4 1/2" deep x 8 1/2". Limited quantity £1-25 each plus 25p post and insurance.


KITS FOR PREVIOUS PROJECTS

Unless otherwise stated, kits contain electronic parts only. The case and special items can be obtained locally. Also batteries are not included. Kits may be returned for refund if construction has not been started. We reserve the right to substitute components should deliveries be protracted so as to avoid undue delay.

HOME SENTINEL INTRUDER ALARM	£3-75
SNAP INDICATOR	75p
WINDSCREEN WIPER CONTROL	£2-00
RECORD PLAYER	£5-50
(amplifier components only)	
DEMO DEC	£6-75
FUZZ BOX	£1-85
PHOTOGRAPHIC COLOUR TEMPERATURE METER	£2-65
ASTRON RADIO	£3
REMOTE TEMPERATURE COMPARATOR	£4-25
ELECTRO LAUGH	£2
TRANSISTOR MICROPHONE	£1-70
AUTO ALERT	£2-50
RAIN WARNING ALARM	£1-80
WA-WA PEDAL	£2-90
DARKROOM TIMER	£4-50
SIGNAL INJECTOR	80p
SOIL MOISTURE METER	£3-00
SIMPLE CALCULATOR	£2-20
DC POWER SUPPLY	£5-00
BABY ALARM	£4-00
AUDIO TONE GENERATOR	£2-60
METAL LOCATOR	£4-00

MAINS TRANSISTOR POWER PACK

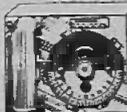Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 300mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 83p, plus 20p postage.



24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. £2-50 post and ins. 25p. Additional time contacts 60p pair.

TREASURE TRACER MARK II

Complete Kit (except wooden battens) to make the metal detector similar to that described editorially in Practical Wireless August issue. £2-95 plus 20p post and insurance.

MULLARD I.F. MODULE

This is a fully screened intermediate frequency module for amplification and detection of f.m. signals at 10-7MHz and a.m. signals at 470KHz. The first stage is used as an i.f. amplifier for f.m. and a self oscillating mixer for a.m. operation, in conjunction with an external oscillator coil. 75p each, 10 for £2-75. 100 for £2-50. With connection disc.

COMPUTER TAPE

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in. wide £1-00 plus 33p post and insurance, with cassette. 1/2 in. wide £1-00 plus 30p post and insurance with cassette. 3/4 in. wide 85p plus 25p post and insurance with cassette. Spare spools and cassettes—1in 75p, 1/2 in 75p each plus 20p post and insurance.

THIS MONTH'S SNIP

HONEYWELL THERMOSTAT

Made by Honeywell for normal air temperatures 40°-80°F (5°-25°C). This is a precision instrument with a differential which can be adjusted to better than 1/3°F. A mercury switch breaks on temp. rise—the switch is operated by a coiled bi-metal element and adjustable heater is incorporated for heat anticipation. Elegantly styled and encased in an ivory plastic case with clear plastic windows thermometer above and switch setting scale below—size approx 3-8" x 2-2" x 1-4" deep—can be mounted on conduit box or directly on wall. Price £1-25 each or ten for £11-25.

CENTRIFUGAL FAN

Mains operated, turbo-motor type. Pressed steel housing contains motor and aluminium impeller. Motor is 1/10th hp giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2" wide by 12" dia. Outlet into trunking 10 1/2" x 4 1/2". £4-95 + £1.

THE FULL-FI STEREO SIX

THE AMPLIFIER

EXCEPTION OF THE YEAR
You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal chassis ready for mounting on plinth this state circuit uses an integrated solid state circuit with an output power of 6W R.M.S. split over the two channels. The amplifier is ideal for

use with normal pick-ups and tuners. It has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. UNREPEATABLE PRICE is £6-50 plus 20p post and insurance. Simulated Teak cabinet ready for mounting amplifier £1-95 (posted free when ordered with chassis).

WASH AND WIPE MULTI METER LIGHT TO SOUND CONVERTER

To receive prices for these and other featured projects send the estimated cost any differences will be adjusted.

P.E. GEMINI

Dual purpose twin 30 watt stereo amplifier for exceptional performance. Complete kit of parts less case £45 or reprint of data & parts list 55p.

DIAL THERMOMETER

Reading from 20°-520° used on Tricity and other cookers. This has a range and can be mounted through a 1 1/2" hole or alternatively it can just be rested on the object whose temperature it is required to measure. Size 2" x 1" overall diameter. Depth 1" below and 1" above mounting panel. Price 80p each or 10 for £7-20p.

MULLARD, AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into 8 ohms speaker. Input suitable for crystal mic, or pick-up. 9V battery operated. Size 2in long x 1 1/2in wide x 1in high. SPECIAL SNIP PRICE 60p each. 10 for £5-40, 100 for £50.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for an improved and even more efficient version (Practical Wireless, June). Price £4-95 plus 20p. Special Snip Price £2-95 plus 20p.

ELECTRONIC IGNITION

20p post. When ordering please state whether for positive or negative systems. Also available, ready made ignition systems for 6V vehicles £5-25 plus 20p.

RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2—twin stethoeth instead of earpiece 75p extra—post and ins. 20p.

QUICK CUPPA

Mini Immersion Heater. 350w 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1-25, post and insurance 14p. 12v. car model also available same price. Jug heater £1-50 plus p. & p. 14p



MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1" pull—approx. size 1 1/2" x 1 1/2" 60p.
Model 600/1 1/2" pull. Size 2 1/2" x 1 1/2" 75p.
Model 600/1 1/4" pull. Size 3 x 2 1/2" 91p £1-80 plus 20p post and ins.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amperes. Operating coil wound for 240V. O.C. Good British Make. Unused. Size approx. 1 1/2" x 1". Open construction. Single pole 25p each 10 for £2-25 Double pole 35p each 10 for £3-15

DRILL CONTROLLER

NEW IKW MODEL
Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-50 plus 15p post and insurance. Made up model also available. £2-25 plus 13p post & p.



SLIDE SWITCHES

Slide Switch. 2-pole changeover panel mounting by two 6BA screw. Size approx. 10 x 1in rated 250V lamp. 6p each. 10 for 54p, 100 for £5-10, 500 for £24. Ditto as above but for printed circuit 5p each 10 for 45p, 100 for £4-25. 8ub Miniature Slide Switch. DPDT 19mm (1in approx.) between fixing centres. 12p. each or 10 for £1-08.

LIGHT CELL

Almost Zero resistant in sunlight increases to 10 K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1in dia. by 1/2in thick. Rated at 600 MW, wire ended. 48p with circuit. Also ORP12 light cell 45p.

TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—5 sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA. PCB. 88p. KNUCKLED MODEL FOR F.M. 50p.

0.8 AMMETER

2in square full vision for flush mounting. Moving iron instrument. Ideal for charger. Price 43p each. 10 for £3-90.

EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan switch, mains connector, and fixing brackets, £2 plus 26p post and ins.

BALANCED ARMATURE UNIT

600 ohm, operates speaker or microphone, so useful in intercom or similar circuits. 23p each, £3-50 doz.

MICRO SWITCH

5 A changeover contacts. 9p each. £1 doz. 16 amp. Model 10p each or £1-95 doz.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—3 pole 6 way—1 pole. 12 way. All at 20p each. £1-80 for ten, your assortment.

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

J. BULL (ELECTRICAL) LTD.

(Dept. E.E.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

Everyday Electronics, June 1972

featured in the April edition; could it be used as a one way intercom? (i.e. is the sound produced by speaking into it audible in the loudspeaker?).

C. J. Radford
Bournemouth.

The Baby Alarm would make a one way intercom but we will be publishing a proper intercom design in the future.

Supply Abroad

When I saw your magazine advertised in our local paper I took interest in it and made my first electronic device—*Wind-screen Wiper Control*. After a few failures it worked.

In your second issue I followed your *Demo Deck*. But trouble started: parts! It took me three weeks to buy a loudspeaker of 40Ω—4 inch diameter, as the one you mentioned is not obtainable in New Zealand. Also, then I was advised by several people experienced in "electronics" to change over to another magazine, preferably an Australian one, as the parts you quote for your circuits are very hard to get, very dear, or never heard of, or not used in New Zealand. But however, I carried on and made the *Demo Deck*.

In your January 1972 issue, my boys took a liking to the *Astron* m.w. receiver. So I went to the shops to find out the costs. First: the semiconductors: ZTX 100, 501 and 300—"never heard of", "not in our catalogues",—"oh, that magazine again." Everywhere the same: "Sorry Sir, cannot help you." The same with the loudspeaker! In the component parts: R9 not mentioned.

So you see, all in all, all very disheartening. And the transistors in the *Electro-Laugh* are, if obtainable, about \$3.00 (N.Z.) each.

What am I to do? Give it up?—no—another magazine, but then what about my *Demo Deck*? One firm suggested to write to you and ask for different circuit diagrams, or the equivalent of transistors and loudspeakers as he says: "The *Teach-In* course is good and practicable."

Your February issue is not on sale yet. So you see, problems, problems.

So, can you help your New Zealand customers and is there any way to get your magazine sooner than three months after due dates? I am very much obliged for your help and remain.

F. Van Waelsden
Christchurch, N.Z.

We cannot give alternatives for you as we do not know what is available in New Zealand. We think it would be better if you

Everyday Electronics, June 1972

bought your components from a supplier in this country and paid for them to be posted to you. As far as three months for an issue goes—if you take out a subscription it should be quicker.

Back Issues

After reading your *Readers Letters* I realise how many other people had the same feelings as I; namely that electronics would always be for the experts and beyond most of us, but as your magazine explains things, and sets out wiring diagrams etc, it is not now so mysterious. I have built myself a *Demo Deck* and find the practical experiments you present most helpful.

I had great success with the *Signal Injector*. This helped me to locate a fault in a transistor radio. One favour I would like to ask is it possible for me to obtain a copy of the first issue (November) I have the others but missed the first one. It is annoying to keep reading references to *Snap Sequence Indicator* and *Home Sentinel* and not know what they are.

Thank you for an interesting magazine.

R. Brown
Burton-on-the-Wold
Leicester.

Unfortunately we are no longer able to supply any back issues (see page 413). Thus it is now more important that all readers place a regular order or take out a subscription—details on page 412.

Red Flash

Despite the fact that I have been interested in electronics and radio in particular for over two years I am still not far out with the "beginner" class and find your articles interesting and helpful. Despite that it angers me to see such letters as H. A. Williams' letter of the April issue.

It seems to me that he is very narrow minded in his outlook since to me, electronics means electronics in its widest field, computers, radio, electronic music modules such as waa-waa and fuzz as well as the other circuits you print. To suggest that an electronics magazine should print circuits as flash every month and to have the insolence to suggest that such magazines should be printed to cover only one narrow subject makes me see red. Why not take it as it is and try all the circuits?

My interest is radio but I find your articles and circuits very interesting; thank you.

D. Burgess
Ross-shire.

Bee Counted

I was very pleased to see that in the May copy of E.E., you would be making a *Bee-Counter*. As a bee keeper I am very pleased to see that electronics can help me. I just hope I can build my *Bee-Counter* before they go out to pollenate.

Well, as a bee keeper E.E. is going to help me. So I wonder if you could now help me as a goat keeper as well. In the summer my goats always jump over the fence, as the grass on the other side is always greener.

So please can you work out a circuit for a transistor electric fence unit to keep my goats in.

D. A. Cullum
Cambridge.

No promises, but this could be a future project; farmers and smallholders please note.

Understandable

Well done. At last we can obtain a magazine, though a month behind out here, that every one can understand, I have worked with electronics for some time now, never have I come across such clear detailed circuitry, the projects quite compelling—who wants a rain detector in drought stricken N.S.W.!? They all work too, "Cam's Comic" readers note!

Shop Talk, very good idea all budding inventors should not miss that page, I would like to endorse the editorial in the Feb. issue you feel a bit of a charles when you build a good bit of working gear and can't put it right when it does go wrong!

Just one point I hope in a year's time I can pick up *EVERYDAY ELECTRONICS* and see fine projects for the not so experienced still predominate in the magazine, leaving doppler radar gear etc., to the other magazines.

M. T. Cole
New South Wales

Electronics Taped

I find your magazine very interesting and instructive. I am wondering if any readers would be interested in exchanging ideas and comments about electronics projects and electronics in general on tape.

If you would be interested in exchanging tapes please write to me, at the address given, and I will give you further details. Please enclose 2½p stamp. If you prefer you can send a tape—two-track at 3½ i.p.s. speed.

John Bradley
1, Amblefield Way
Stafford.

BUILD 5 RADIO AND ELECTRONIC PROJECTS

only £2-45



Amazing Radio Construction set! Become a radio expert for £2-45. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeakers, personal phone, knobs, screws, etc. all you need. Presentation box 45p extra asillus. (if required) (parts available separately) no soldering necessary. Send £2-45 + 30p p. & p.

SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON



Only £2-75

CUTS OUT NOISE POLLUTION—SOOTHES YOUR NERVES! Don't underestimate the uses of this fantastic new device—the RELAXATRON (a basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 battery (current used so small that battery life is almost shelf-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, components, nuts, screws, wire, etc. no soldering. £2-75 + 25p p. & p. Parts available separately.

FIND BURIED TREASURE! Transistorised Treasure Locator



ONLY £2-85

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC. Extremely sensitive, will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY £2-85 + 25p p. & p. (Sectional handle as illustrated 35p extra). Parts available separately. Made up looks worth £15.

Eavesdrop on the exciting world of Aircraft Communications

V.H.F. AIRCRAFT BAND ONLY CONVERTER £2-85

Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding themselves on talk downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the International distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portables). NO CONNECTIONS WHATSOEVER NEEDED. SEND ONLY £2-85 + 25p p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

SHORTWAVE TRANSISTOR RADIO

only £2-75



Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 75 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2". Only £2-75 + 30p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY £3-25



CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SLEEPY SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Approx. size: 2 1/2" x 2 1/2" x 2 1/2". Price £3-25 + 25p p. & p. (parts available separately).

ELECTRONIC ORGAN


ONLY £3-25



Don't confuse with ordinary electronic organs that simply blow air over mouth-organs type reeds etc. Fully transistorised. FULLY OBTAINED LOUDSPEAKER. 15/16ths separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real live, portable electronic organ. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED. No soldering necessary. Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions. ONLY £3-25 + 25p p. & p. for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY £4-95

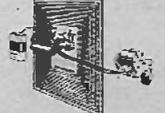

FULLY TRANSMITTER-CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORKS ABOUT 400'. Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN £4-95 + 30p cart. etc. (High quality Danish 8-ohm phone headphones £2-75 extra if required.) EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IF FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD. (EE6U) 8 Westbourne Grove, London, W.2. Callers welcome 9 a.m.—5.30 p.m. inc. Saturday

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.

No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N 9 803 1685

MIDGET FLEX CONNECTOR

Approx. 2 amp rating. Two-pin non-reversible midget flex connector. Approx. size: 2 1/2" x 2 1/2". Ideal for loudspeaker connections, etc. 5p plus 5p p. & p.

MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 60mA. 63V. @ 1A. This transformer is made to a very high standard and is a small size: 2 1/2" x 2 1/2" x 2 1/2". 63p plus 15p p. & p.

BRIDGE RECTIFIER

Plastic encapsulated. Texas Type No 1R40. K05 50v at 4 amp. Our Price 55p + 5p P. & P.

HIGH QUALITY IMPORTED HEADPHONES

1,000 Ohm per phone ... 95p TTC
2,000 Ohm per phone ... 105p G1105
Plus 10p P. & P. per pair.

COMPONENT CORNER

Veroboard Outputs 2 1/2" x 3 1/2" 17p
52" 17p
Plain Veroboard 1 1/2" x 3" 9p
Standard Toggle Switch, DPDT 18p
D.P.D.T. Slide Switch 13p
Experimental Transistor 7p
Holders, 3-pin and 4-pin 7p
I.C. Holders for 14 or 16 pin 20p
Please include 3p p. & p. per 2 items

SINGLE EARPIECES

Crystal or Magnet 3 ohm or 2.5 ohm (please state which type you require. Complete with lead. 20p plus 3p p. & p.

LOUDSPEAKER BARGAINS

E.M.E. 450 set 3. 8. 15 ohm £3-25 plus 3p p. & p.
E.M.I. 350 set 8 ohm. £7-00 plus 3p p. & p.

MINI LOUDSPEAKERS

2 1/2" (57mm) 8ohm — 50p each
2 1/2" (57mm) 40ohm — 50p each
2 1/2" (57mm) 80ohm — 50p each
Please include 5p p. & p. up to 3 Mini-Loudspeakers

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your transistor radio, amplifier, cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug you can select the voltage you require—6v, 7 1/2v or 9 volts. This means all your transistor power pack applications can be handled by this one unit. Approx. size: 2 1/2" x 2 1/2" x 2 1/2". Price £2-75p + 10p P. & P. Same model antistatically wired for the Philips Cassette — £3-00 + 10p P. & P.

ALUMINIUM CHASSIS

Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.

6 x 4—41p	12 x 3—55p	14 x 9—84p
6 x 4—45p	12 x 3—61p	10 x 6—88p
8 x 6—53p	12 x 8—83p	16 x 10—1-08p
10 x 7—68p	14 x 3—60p	

Please send 10p per chassis P. & P.

BULGIN OCTAL PLUG

Ideal for all those multi-way connections. This plug comes with a standard 8-pin valve holder. Plug — 12p Socket — 6p Please include 4p p. & p.

WAFER SWITCHES

1 pole 1 way	2 pole 2 way
2 pole 3 way	2 pole 4 way
2 pole 6 way	3 pole 4 way
4 pole 3 way	18p each. Please inc. 5p P. & P. up to 3 switches.

POTENTIOMETERS

All types 1" and less diameter.

SINGLES	DOUBLE
3K Log or 5K	10K Lin less 10K
25K Switch	25K Less
50K 12pea	50K Switch
100K	100K 40p.
250K	250K
500K	Pole 250K each
1M	Switch 1M
2M	Switch 2M

Up to 3 Pots. Please add 5p P. & P.

2N3055 POPULAR POWER TRANSISTOR

Now at our Low Price 50p each. Please include 5p P. & P.

BARGAIN S.C.R.

TESTED THYRISTOR 400 volt 3 amp. 45p each 5 for £2-00. Please include 5p P. & P.

PRINTED CIRCUIT BOARD

Everything for producing your own printed circuits. 21-40p plus 10p P. & P.

8 x 6—10p	10 x 8—15p
9 x 5—10p	12 x 12—30p

Please inc. 3p. per board P. & P.

EA1000 3 WATT AUDIO AMPLIFIER MODULE

An Audio Amplifier designed around the TAA621 Linear I.C.—

Supply Voltage	9—24V
Speaker Imp.	8—16 ohm
Frequency	50Hz—26kHz
Overall Size	2 1/2" x 3 1/2" x 1 1/2"

Ideal Amplifier for radios, record players, stereo units, etc. Full technical data and diagrams with each module. All guaranteed and a bargain at £2-63 + 5p P. & P.

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK • OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS

TYPE SW.100
100 x 80 mm.

50μA	\$2.90	20V. D.C.	\$3.10
50-0-50μA	\$2.45	50V. D.C.	\$3.10
100μA	\$2.45	300V. D.C.	\$3.10
100-0-100μA	\$3.35	1 amp. D.C.	\$3.10
500μA	\$2.80	5 amp. D.C.	\$3.10
1000μA	\$2.80	300V. A.C.	\$3.10
1mA	\$2.80	VU Meter	\$3.75

BAKELITE PANEL METERS

TYPE S-80
80 mm. square fronts

50μA	\$2.20	50V. D.C.	\$2.60
50-0-50μA	\$3.10	300V. D.C.	\$2.60
100μA	\$2.10	1 amp. D.C.	\$2.60
100-0-100μA	\$3.00	5 amp. D.C.	\$2.60
500μA	\$2.75	300V. A.C.	\$2.60
1mA	\$2.60	VU Meter	\$3.37

"SEW" CLEAR PLASTIC METERS

Type MR.55P. 4 1/2 in. x 4 1/2 in. fronts

50μA	\$2.60	10V. D.C.	\$2.90
50-0-50μA	\$2.60	20V. D.C.	\$2.90
100μA	\$2.10	50V. D.C.	\$2.90
100-0-100μA	\$2.90	300V. D.C.	\$2.90
500μA	\$2.90	15V. A.C.	\$2.10
1000-500μA	\$2.80	300V. A.C.	\$2.10
1mA	\$2.80	5 Meter 1mA	\$2.80
1-0-1mA	\$2.80	VU Meter	\$3.87
5mA	\$2.80	1 amp. A.C.*	\$2.80
10mA	\$2.80	5 amp. A.C.*	\$2.80
50mA	\$2.80	10 amp. A.C.*	\$2.80
100mA	\$2.80	20 amp. A.C.*	\$2.80
5 amp.	\$2.80	30 amp. A.C.*	\$2.80

Type MR.58P. 1 1/2 x 3 1/2 in. square fronts

50μA	\$2.10	10V. D.C.	\$1.90
50-0-50μA	\$1.90	20V. D.C.	\$1.90
100μA	\$1.90	50V. D.C.	\$1.90
100-0-100μA	\$1.75	300V. D.C.	\$1.90
500μA	\$1.65	15V. A.C.	\$1.90
1000-500μA	\$1.60	300V. A.C.	\$1.90
1mA	\$1.60	5 Meter 1mA	\$1.90
1-0-1mA	\$1.60	VU Meter	\$2.80
5mA	\$1.60	1 amp. A.C.*	\$1.90
10mA	\$1.60	5 amp. A.C.*	\$1.90
20mA	\$1.60	10 amp. A.C.*	\$1.90
50mA	\$1.60	20 amp. A.C.*	\$1.90
100mA	\$1.60	30 amp. A.C.*	\$1.90
150mA	\$1.60	VU Meter	\$2.10

"SEW" BAKELITE PANEL METERS

Type MR.55. 3 1/2 in. x 3 1/2 in. fronts

50μA	\$2.37	10V. D.C.	\$2.20
50-0-50μA	\$2.75	20V. D.C.	\$2.20
100μA	\$2.75	50V. D.C.	\$2.20
100-0-100μA	\$2.65	300V. D.C.	\$2.20
500μA	\$2.40	15V. A.C.	\$2.20
1000-500μA	\$2.20	300V. A.C.	\$2.20
1mA	\$2.20	5 Meter 1mA	\$2.20
5mA	\$2.20	VU Meter	\$3.87
10mA	\$2.20	1 amp. A.C.*	\$2.20
50mA	\$2.20	5 amp. A.C.*	\$2.20
100mA	\$2.20	10 amp. A.C.*	\$2.20
500mA	\$2.20	20 amp. A.C.*	\$2.20
1 amp.	\$2.20	30 amp. A.C.*	\$2.20
5 amp.	\$2.20		
10 amp.	\$2.20		
15 amp.	\$2.20		
20 amp.	\$2.20		
30 amp.	\$2.20		
50 amp.	\$2.20		
SV. D.C.	\$2.20		

***MOVING IRON— ALL OTHERS MOVING COIL**
Please add postage

SEW EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is demonstrated internal working. Available in the following ranges:

50μA	\$5.00	20V. d.c.	\$4.40
100μA	\$4.65	50V. d.c.	\$4.40
1mA	\$4.40	300V. d.c.	\$4.40
10-0-50μA	\$4.65		
1-0-1mA	\$4.40	Dual range	
1A d.c.	\$4.40	600mA/5A d.c.	\$4.65
5A d.c.	\$4.40	5V/50V d.c.	\$4.65
10V d.c.	\$4.40		

EDGWISSE METERS

Type PE.70. 3 1/2 x 1 1/2 x 1 1/2 in. x 2 1/2 in. deep.

50μA	\$2.10	600μA	\$2.75
50-0-50μA	\$3.00	1mA	\$2.45
100μA	\$2.90	300V. A.C.	\$2.45
100-0-100μA	\$2.90	VU Meter	\$3.40
200μA	\$2.90		

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

MULTIMETERS for EVERY purpose!

ROUND SCALE TYPE PENCIL TESTER MODEL TS.63

Completely portable, simple to use pocket sized tester. Ranges 0/5/30/300V AC and DC at 2,000 ohm p.v. Resistance 0-20K ohms. ONLY \$1-97 P. & P. 13p



SKYWOOD SW-600

50K ohm/Volt. Mirror scale. DC Volts 0.6/3/12/30/300/600. DC Current 20μA/5/600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +57 db. \$7.50. P. & P. 15p.



370 WTR MULTI-METER

Features A.C. current ranges. 20,000 o.p.v. 0/1-2-5/10/50/250/500 1000 V DC. 0/2-5/10/50/250/500/1000 V AC. 0/50mA/1/10/100mA/1/10 Amp DC. 0/100MA/1/10 Amp AC 0/5K/50K/500K/5MEG/50MEG. -20 to +82 db. \$15. P. & P. 25p.



TE2Z SINE SQUARE WAVE AUDIO GENERATORS

Since 80cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 6,000 ohms. 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. \$17.50. Carr. 371p



TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$18. Carr. 371p. Size 140 x 215 x 170 mm.



BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Size 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max to 10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price \$27.50. Carr. 25p.



240° Wide Angle Ima Meters

MW1-6 60mm square \$2.97 P. & P. extra
 MW1-8 80mm square \$4.97 P. & P. extra



TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R: 1Ω-100Ω. C: 6 pF to 1 μF. L: 1 μH to 100 mH. HENRY'S 6 Ranges ±2% = %C.10pF-1110mFD. 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter Indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 in. \$20. P. & P. 25p



230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed 60 RPM CW: 30 RPM CW; 2R/HE ACW; 2R/HE CW; 8R/DAY CW; 10 RPM CW; 60Y each. Post 12p.



HIOKI MODEL 720X

25,000 O.P.V. Overload protection. 5/25/100/500/1000 VDC. 10/50/250/1000 VAC. 50 mA/250 mA. 20K/2 meg ohms. -5 to +62db. \$4.97. P. & P. 15p.



Model 5-100TE MULTI-METER TRANSISTOR TESTER

100,000 o.p.v. MIRROR SCALE OVERLOAD PROTECTION 0/1/2...8/3/12/50/120/600 V DC. 0/6/30/120/600 V. AC. 0/12/600mA/12/300mA/12 Amp. DC. 0/10K/1 MEG/100 MEG. -20 to +50 db. 0.01 - 2 mfu. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. \$13.60. P.P. 25p.




MODEL 500 30,000 O.P.V.

with overload protection mirror scale 0/1-2-5/10/25/100/250/500/1,000 V. D.C. 0/2-5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/5K/50K/500K/5MEG/50MEG. \$8.71. Post paid.




HT100B4 MULTI-METER

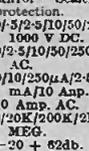Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection. 0/3-2-5/10/50/250/500/1000 V DC. 0/2-5/10/50/250/100 V AC. 0/10/250μA/2-5/25/250 mA/10 Amp. DC. 10 Amp. AC. 0/20K/200K/2MEG/20MEG. -20 to +82db. \$12.50. P. & P. 25p.



RUSSIAN 22 RANGE MULTIMETER

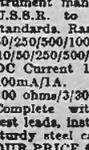Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Range: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 mA/1/10/100mA/1A. Resistance 300 ohms/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$25.97 P. & P. 25p.



TO-3 PORTABLE OSCILLOSCOPE

3in. tube. Y amp. Sensitivity 0-1v p-p/CM. Bandwidth 1-5 cps-1.5 MHz. Input imp. 2 meg-10 25pF X amp. sensitivity 0-1v p-p/CM. Bandwidth 15 cps-800KHz. Input imp. 2 meg 10 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 340 x 215 x 390 mm. Weight 15 lb. 220/240V. A.C. Supplied brand new with handbook. \$40.00. Carr. 50p




HONEYWELL DIGITAL VOLTMETER VT-100

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specifications: Accuracy: ± 0.2. 1 1/2 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg. ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing. Full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2 in. x 2 1/2 in. x 3 1/2 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. \$49.97. Carr. 50p.



G. W. SMITH & CO (RADIO) LTD.

Also see next two pages

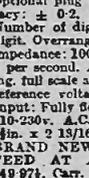

SEMI-CONDUCTOR VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	2N3416	2N3417	2N3499	2N3500
2N3415	2N3416	2N3417	2N3500	

Integrated Circuits	CA3000	CA3001	CA3002	CA3099	CA3100
CA3000	CA3001	CA3002	CA3100	

VALVES

Valves	6AR5	6AR6	6AR7	6AR8	6AR9	6AR10	6AR11	6AR12	6AR13	6AR14	6AR15	6AR16	6AR17	6AR18	6AR19	6AR20	6AR21	6AR22	6AR23	6AR24	6AR25	6AR26	6AR27	6AR28	6AR29	6AR30	6AR31	6AR32	6AR33	6AR34	6AR35	6AR36	6AR37	6AR38	6AR39	6AR40	6AR41	6AR42	6AR43	6AR44	6AR45	6AR46	6AR47	6AR48	6AR49	6AR50	6AR51	6AR52	6AR53	6AR54	6AR55	6AR56	6AR57	6AR58	6AR59	6AR60	6AR61	6AR62	6AR63	6AR64	6AR65	6AR66	6AR67	6AR68	6AR69	6AR70	6AR71	6AR72	6AR73	6AR74	6AR75	6AR76	6AR77	6AR78	6AR79	6AR80	6AR81	6AR82	6AR83	6AR84	6AR85	6AR86	6AR87	6AR88	6AR89	6AR90	6AR91	6AR92	6AR93	6AR94	6AR95	6AR96	6AR97	6AR98	6AR99	6AR100
6AR5	6AR6	6AR7	6AR8	6AR9	6AR10	6AR11	6AR12	6AR13	6AR14	6AR15	6AR16	6AR17	6AR18	6AR19	6AR20	6AR21	6AR22	6AR23	6AR24	6AR25	6AR26	6AR27	6AR28	6AR29	6AR30	6AR31	6AR32	6AR33	6AR34	6AR35	6AR36	6AR37	6AR38	6AR39	6AR40	6AR41	6AR42	6AR43	6AR44	6AR45	6AR46	6AR47	6AR48	6AR49	6AR50	6AR51	6AR52	6AR53	6AR54	6AR55	6AR56	6AR57	6AR58	6AR59	6AR60	6AR61	6AR62	6AR63	6AR64	6AR65	6AR66	6AR67	6AR68	6AR69	6AR70	6AR71	6AR72	6AR73	6AR74	6AR75	6AR76	6AR77	6AR78	6AR79	6AR80	6AR81	6AR82	6AR83	6AR84	6AR85	6AR86	6AR87	6AR88	6AR89	6AR90	6AR91	6AR92	6AR93	6AR94	6AR95	6AR96	6AR97	6AR98	6AR99	6AR100	

HI-FI EQUIPMENT

SAVE UP TO
33% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!



RECORD DECKS

BSR UA501	24.97	ZERO 100A	241.95
CI291	58.60	ZERO 100B	237.50
MP60	110.40	GOLDRING	
610	114.07	GL69/2/P	118.97
510	111.50	GL72	128.25
610	114.40	GL72/P	128.05
810	123.45	GL75	129.05
MP60 TFD1	117.12	GL75/P	124.95
MP60 TFD2	116.40	LD75	123.83
110 TPD1	120.35	LD72	123.65
110 TPD1	118.20	G99	119.30
210 Package*	129.55	GL85	148.50
HT 70	114.99	GL85/P	154.30
HT 70 Package		LD85	144.80
		G101	121.95
GARRARD		PIONEER	
2025 T/C*	28.50	PL12AC	135.15
40B*	28.25	PL16C	150.25
E-300*	28.50	PLA25	182.85
SP28 III	110.50	THORENS	
SP28/G800*	114.50	TD125	157.65
SL55B	113.45	TD125AB	191.15
AE76	118.85	TX25	28.40
SL76/G800*	122.80	TD190	127.90
SL72B	122.20	TD150A II	133.25
SL75B	128.00	TD150AB II	137.80
SL93B	122.50	TD150 Plinth	13.47
401	128.60	TX11	13.65

* Mono Stereo Cartridge
All other models less Cartridge
Carriage 50p extra any model.

RECORD DECK PACKAGES

Decks supplied with cartridge ready wired in toak veneered plinth with cover.

Garrard 2025TC/9TAHCD	112.95
Garrard SP25 III/9TAHCD	115.95
Garrard SP25 III/G800	118.60
Garrard SP25 III/MT75	119.50
Garrard SP25 III/M44-7	120.35
Garrard SP25 III/M44-E	122.30
Garrard SP25 III/G800 (Play on Plinth and Cover)	119.75
Garrard AP76/G800	123.60
Garrard AP76/MT75	123.65
Garrard AP76/M55E	123.95
Garrard AP76/MT75EJ	124.90
BSR McDonald MP60/AT55	119.25
Goulding GL72/G800	124.50
Goulding GL75/G800	129.70
Goulding GL75/G800E	124.15

Carriage 50p any item.


SINCLAIR EQUIPMENT



Project 60. Package offers.
2 x 230 amplifier, stereo 60 pre-amp, P23 power supply, £15.95 Carr. 37p. Or with P26 power supply £18.00 Carr. 37p. 2 x 250 amplifier, stereo 60 pre-amp, P23 power supply, £20.25 Carr. 37p.
Transformer for P28, £2.97 extra.
Add to any of the above £4.45 for active filter unit and £13.90 for pair of Q16 speakers.
Project 60 FM Tuner £18.95 Carr. 37p.
All other Sinclair products in stock.
2000 Amp £28.50 Carr. 37p.; 2000 Amp £30.95 Carr. 37p.; Neoteric Amp £49.95 Carr. 37p. 1012 £1.80 Post 10p.
NEW PROJECT 605 — £20.97 Carr. 37p.

LATEST CATALOGUE

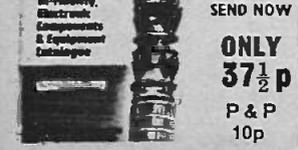Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT AND COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS



SEND NOW
ONLY 37½p
P & P 10p

TELETON SAQ-206B STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal. aux. lead. Volume, bass, treble, sliding balance, scratch filter and loudness controls.
OUR PRICE £18.60 Carr. 37p.

TAPE CASSETTES

Top quality Hi Fi Low Noise in Philips Library cases.
C60 3 for 75p 10 for £2.35 P. & P.
C90 3 for £1.05 10 for £3.30 10p
C120 3 for £1.85 10 for £4.20 extra.
Tape Head Cleaner 30p each

LAFAYETTE LA. 324 STEREO AMPLIFIER



OUR PRICE £24, Carr. 37p.

SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 8 bands 200-420 KHz and 55 to 20 MHz. Illuminated slide rule dial. Bandspread.
Aerial tuning. BFO. AVC. ANL. 8' meter. AM/CW/SS B. Integrated speaker and phone socket. Operation 220/240V AC or 12V DC. Size 925 x 266 x 150 mm. Complete with instructions and control.
£28.50. Carr. 50p

★ TRANSISTORISED FM TUNER




6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2 in. 3 I.F. stages. Double tuned discriminator. Simple output to feed most amplifiers. Operates on 9 V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. 28 37p. P. & P. 12 1/2p. Stereo multiplex adaptors 24-97 1/2p.

TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER



Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3 - 1200V. AC VOLTS 3 - 300V R.M.S. 8.0 - 800V P-P. DC CURRENT 12 - 120MA.
Resistance up to 2000 Ohm. Decibels -20 to +51 db Complete with leads/instructions. £17.50, P. & P. 20p.

230 VOLT A.C. 50 CYCLES RELAYS

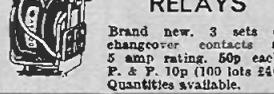


Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40). Quantities available.

PRS-2 PHOTO ELECTRIC RELAY SYSTEM



Inexpensive warning or counting system consisting of an exciter and relay unit. Relay unit has variable sensitivity control and switch for intermittent alarm operation. Exciter unit has removable infra red filter and A.C. outlet socket to operate bells, counters, etc. 240V AC. Complete with cables and instructions. £9.97 P. & P. 25p.
HOMER INTERCOMS

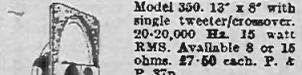
Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.
2 Station £2.97, P. & P. 16p.
3 Station £5.25, P. & P. 15p.
4 Station £8.62, P. & P. 17p.



EMI LOUDSPEAKERS
Model 390. 13" x 8" with single tweeter/cover. 20-20,000 Hz. 15 watt R.M.S. Available 8 or 16 ohms. £7.50 each. P. & P. 87p.
Model 450. 15" x 8" with twin tweeters/cover. 55-13,000 Hz. 8 watt R.M.S. Available 8 or 16 ohms. £3.50 each. P. & P. 25p.




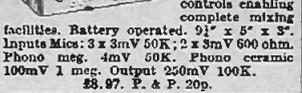TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET
Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms.
£1.97, P. & P. 15p.



MP7 MIXER PREAMPLIFIER
5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mics: 3 x 3mV 50K, 2 x 3mV 600 ohm. Phone neg. 4mV 50K. Phone ceramic 100mV 1 meg. Output 250mV 100K.
£8.97, P. & P. 20p.

HOSIDEN DH-025 STEREO HEADPHONES

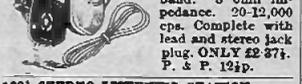

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY £2.77. P. & P. 12 1/2p.

1021 STEREO LISTENING STATION



For balancing and an excellent selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2.25, P. & P. 15p.


MCA. 220 AUTOMATIC VOLTAGE STABILISER




Input 88-125 VAC or 176-250VAC. Output 120VAC or 240VAC. 200VA rating.
£11.97, Carr. 50p.

SPECIAL OFFER!

SINCLAIR PROJECT 60 STEREO FM TUNER

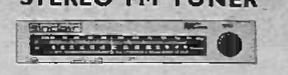

The first tuner in the world to use the phase lock loop principle—as used for receiving signals from space craft because of its vastly improved signal to noise ratio. Provides fantastic results even in difficult areas. Tuning range 87.5 to 108MHz. Automatic stereo indicator. Sensitivity: 2uV. APC range ± 200KHz. Signal to noise ratio: 65dB. Output voltage 2 x 150mV. Operating voltage 225-240V D.C. Size: 93 x 40 x 207 mm. REC. LIST PRICE £28.
OUR PRICE £16.95 P. & P. ONLY 25p
Unrepeatable offer—buy now and save over £8

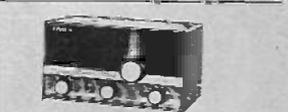


URE-30 RECEIVER
4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. £15.75. Carr. 37p.

LAFAYETTE HA-600 SOLID STATE RECEIVER



General coverage 150-400kc/s, 550 kc/s-30mc/s. PET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, S. Meter, Bandsread. RF Gain. 18" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12V. D.C. Brand new with instructions. 50p. Carr. 50p.

U4812 MULTIMETER

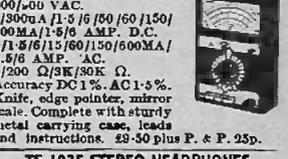

Extremely sturdy instrument for general electrical use. 607 o.p.v.
0-31.5/7.5/30/60/150/300/600/900 VDC and 75mV.
0-3/1.5/7.5/30/60/150/300 600/100 VAC.
0/300uA/1/5/16/50/150/600MA/1.5/8 AMP. D.C.
0/1/5/16/15/60/150/600MA/1.5/8 AMP. A.C.
0/200 0/3K/30K 0.
Accuracy DC 1%. AC 1.5%.
Knife, edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9.50 plus P. & P. 25p.

TE-1035 STEREO HEADPHONES




Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable headband. 8 ohm impedance. 25-18,000 Hz. With lead and stereo jack plug. ONLY £1.97. P. & P. 12 1/2p.

E.H.T. TESTER 0-30KV.



Completely self-contained with built-in voltmeter. Easy to read, very accurate, robust construction. An essential for colour television servicing, etc. Size 360mm long. 50mm. dia. £6.95. P. & P. 25p.

POWER RHEOSTATS

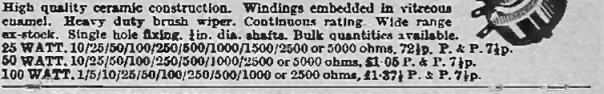

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiring. Continuous rating. Wide range ex-stock. Single hole fixing. 1/2 in. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 72 1/2p. P. & P. 7 1/2p.
50 WATT. 10/25/50/100/250/500/1000 or 5000 ohms. £1.06 P. & P. 7 1/2p.
100 WATT. 15/10/25/50/100/250/500/1000 or 2500 ohms. £1.87 1/2p. P. & P. 7 1/2p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS



Excellent quality. Low price. Immediate delivery
S-280 General Purpose Bench Mounting
1 Amp £7.00
2.5 Amp £8.05
5 Amp £11.75
8 Amp £15.90
10 Amp £22.50
12 Amp £23.60
20 Amp £49.00
S-280B Panel Mounting
1 Amp £7.00
2.5 Amp £8.05
Please add postage ALL MODELS
INPUT 230 VOLTS, 50/60 CYCLES.
OUTPUT VARIABLE 0-280 VOLTS.
Special discounts for quantity

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
31 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

Everyday Electronics Classified Advertisements

RATES: 7p per word (minimum 12 words). Box No. 7p. extra. Semi-display—£4.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

RECEIVERS and COMPONENTS

BEGINNERS! Build your project as cheaply as possible! We stock best components at give-away prices. SAE free list. Advice with orders if required. **NO CALLERS.** R. S. Green, 4 Colecroft Hill, Purley, Surrey.

COMPUTER PANELS 5BC108 diodes, 450p post 10p. PANELS WITH SILICON AND GERM/ TRANS. at least 50. 6—21.90 post 15p. UNIT WITH 4-LA2 POT CORES+11 2% CAPS 50p post 15p. ICs 7400 SERIES ON PANEL(S) 10—75p post 10p. FALLOUTS 5—13p. ORP12 on panel ex equip. 35p cp. BANK 20 WIRE ENDED NEONS 50p post 8p. SEND LARGE S.A.E. FOR LIST OF PANELS ETC. 7LB ASSORTED COMPONENTS £1.30 cp.

J.W.B. RADIO
75 HAYFIELD ROAD SALFORD 6 LANCs
MAIL ORDER ONLY

SERVICE SHEETS

SERVICE SHEETS (1925-1972) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

FOR SALE

FIELDEN 'TECTOR' proximity field capacity switches unused. Cost £28. Few only £4.50 each. Tel: WA 20144.

MISCELLANEOUS

UNIMIXER STUDIO 4 & 6 stereo mixers for professional work. (Slider faders, tone controls, PPM facilities.) Supplied directly at net prices from £86. Manufacturers: Soundex Ltd., 18 Blenheim Road, W4 1ES.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p post free.

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW
S.A.E. for details

TO: BOFFIN PROJECTS,
DEPT. KEE,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY

Cases for EVERYDAY ELECTRONICS Projects.

Specially made to suit actual specifications in EVERYDAY ELECTRONICS in two tone moulded plastic.

Examples—many others available	£
Moisture Meter	0.65
Darkroom Timer	0.75
Rain Alarm	0.65
Home Sentinel	0.65
Remote Temp. Control	0.75

Write (SAE) stating project required for Brochure and Price List.

M.P.E. Ltd., Dept. EE., Bridge Street, Clay Cross, Chesterfield, S45 9NU.

12 VOLT FLUORESCENT LIGHTS (as illustrated)



Beat power cuts, be Independent. Ideal for Caravans, Tent, Emergency Lighting, etc. Works anywhere where 12V is available. Guaranteed for six months, READY TO USE at:-

12ins 8watt £3.60 post paid
21ins 13watt £4.60 post paid

SALOP ELECTRONICS Callers welcome for lists or Enquiries Large S.A.E.
23 Wyle Cop Shrewsbury, Shropshire.

BEFORE BUYING Hi-Fi equipment; buy Audio Supply's new 105 page photographically illustrated catalogue (60p). Fair cash terms and service. Our associates manufacture records from customers' tapes. Specify requirements to Sound News, 18 Blenheim Road, London W4 1ES.

RECORD TV SOUND using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included £1 post free. **CROWBOROUGH ELECTRONICS (E.E.)**, Eridge Road, Crowborough, Sussex.

SOLID STATE C.ds. exposure meter—save pounds! Assemble our meter, all parts and simple instructions for your case. Photo-logic module ensures accuracy over 18 light valves. £5.47 or SAE for details. **Tranix**, 18 Wroxham Close, Shelton Lock, Derby.

ARE YOU BUILDING THE NIP-E BABY ALARM

in April Everyday Electronics or the DARKROOM TIMER in MARCH.

Make these on easy-to-use type 2A only 28p WIRING LAYOUTS SUPPLIED

See our advert last month for other projects on this multi-purpose printed wiring board. **SL403D i.c. REDUCED to £1.20**

NIP ELECTRONICS
DEPT NB/EE, P.O. BOX 11, ST. ALBANS, HERTS

SOUND SUPPLIES (LOUGHTON) CO. LTD.

for Eagle International and International Rectifier Products TOA P.A. Equipment and Mikra. Capacitors, Resistors, Plugs, Sockets, Cables, Audio Leads, Semiconductors, Valves, Vero Board, etc., for the constructor.

ELECTRONICS DEPT. Tel. 01-508-8715
12 Smarts Lane, Loughton, Essex.

Hours: 9.30 a.m.-1 p.m., 2-8 p.m. Mon., Tues. Wed. and Fri.: 9.30 a.m.-1 p.m., 2-5.30 p.m. Sat. Closed all day Thursday.

EDUCATIONAL

TECHNICAL TRAINING in Radio, TV & Electronics through world-famous ICS. For details of proven home-study courses write: ICS (Dept. 566), Inter-text House, London, SW8 4UJ.

MEN! You can earn £50 p.w. Learn computer operating. Send for FREE brochure—London Computer Operators Training Centre, G22 Oxford House, 9-15 Oxford Street, London, W.1.

FREE

TO ENGINEERS Whatever your age or experience you must read **New Opportunities**. It describes the easiest way to pass A.M.S.E., A.M.I.M.I., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering: Mechanics, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book.

Send for your copy today—FREE!
B.I.E.T. B32, Aldermaston Court, Reading, RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

If you have difficulty in obtaining

EVERYDAY ELECTRONICS

Please place a regular order with your news-
subscription or send 1 year's
subscription (£2.35) to

Subscription Department,
EVERYDAY ELECTRONICS,
Tower House,
Southampton Street,
London, W.C.2

KASPEX

16 SEYMOUR ROAD
TILBURY ESSEX RM18 7AP

Would you believe it, some people still house their constructed projects in tatty looking cases 'bashed out' from aluminium, tin plate, etc., or get involved in complicated carpentry.

No need for this any more !!!

We can supply cases in kit form to house most of your Everyday Electronics projects which will give them a touch of professionalism and a modern appearance with a mirror-like finish. Our cases, which are fabricated from Perspex, Oroglass and Acrylic Sheet (both in dense and transparent bright colours), are supplied in kit form, their construction being quick and easy and involving the minimum amount of work. Included with the kits are comprehensive assembly details and diagrams. Take the hard work out of making your cases and go MODERN with KASPEX.

ASTRON £1.40
DARKROOM TIMER £1.30
RAIN ALARM £0.90
METAL LOCATOR PLATES £1.20
BEE COUNTER WINDOWS £0.75

S.A.E. for free quotations on any other case designs

All prices include post and packing.
Mail Order only—Cash with order

AERIAL BOOSTERS

We make four types of Aerial Boosters. L45825 UHF, L12 VHF 405, L11 VHF Radio L10 M/W & S/W. Price L45, L12 & L11 £2.95, L10 £2.45

VALVE BARGAINS

Any 5—45p, 10—70p:
ECC82, ECL80, EF80, EF85, EF183, EF184, EBF89, EB91, EY86, PCC84, PCC89, PCL87, PCF80, PCF86, PCL82, PCL83, PCL88, PL36, PY33, PY82, PY800, PY801, 30L15, 30C15, 6-30L2.

19" TV £6.50

19" 405 Silmline Televisions in good working order, with complete set of spare valves.
Price £6.50. Carriage £1.50.

PRINTED CIRCUIT BOARD

2-8 Ins by 4 ins boards complete with etching compound and instructions—40p

500MFD CAPACITORS

500mfd-25V Brand New Electrolytic with long leads. 11p each.

POST & PACKING under £1.5p Over £1.10p.
S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

VELCO ELECTRONICS

62A Bridge Street, Ramsbottom,
Bury, Lancs.

B.H. COMPONENT FACTORS LTD.

For Eagle, Sinclear, Data Books and Components, 4w 5% resistors 1p, or 50p/100. Electrolytic C426 4/40, 4/40, 10/16, 32/10, 25/25, 100/6, all 4p. IN914 8p, 100y 1A Bridge 40p. Panel neon 15p. Main Transformer 32-0-32 @ 150 mA 50p. Bargain Electrolytics—Send for list. Electrolytic 100/50 10p, 500/50 12p, 1000/12 12p, 1000/25 25p, 1000/50 35p, uL914 30p, 7400/01/10/30 15p. Free list, C.W.O. p.p. U.K. 10p. Discount £10-10% Money back guarantee. Brand new to spec.

P.O. BOX 18, LUTON, BEDS, LU1 1SU
DEPT. EE

JOHN SAYS...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module £7. Unit £8.90. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. Only £2.95. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrot etc. costs £18-00 in model. **SYNTHESIZER MODULES** and other miracles. Send 15p for illust. list.
D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

BODINE TYPE N.C.I. GEARED MOTOR



(Type 1) 71 r.p.m. Torque 10 lb. inch. Reversible. 1/70th h.p. 50 cycle, 0.38 amp (Type 2) 28 r.p.m. Torque 20lb inch. Reversible. 1/80th h.p. 50 cycle, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.50 plus 35p P. & P. or less transformer £2.25 plus 27p P. & P.

12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of approx. 125 RPM. Size 4 1/2" x 2 1/2" dia. Price 95p inc. post.

230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox.
1 R.P.M. cw 1 R.P.H. A/cw 10 R.P.H. A/cw 2 R.P.H. cw 15 R.P.H. A/cw 60 R.P.M. cw 3 R.P.H. A/cw 20 R.P.H. cw 6 R.P.H. cw 30 R.P.H. cw

cw—Clockwise. A/cw—Anti-clockwise rotation. Fraction of maker's price. All at 75p incl. P. & P.

CONSTANT SPEED, PRECISION MADE 6 VOLT D.C. GOVERNED MOTOR

Seven pole armature, ballrace bearing. 2,750 r.p.m. Length 2 1/2". Dia. Shaft length 1/2". Shaft dia. 1/8". No load 40 mA. Normal load 350 mA. Ideal for portable recorders, etc., etc. Price £1.25 p & 10p

PROGRAMME TIMERS

(Mfr. by 'Magnetic Devices Ltd.'). 240V A.C. 5 r.p.m. 'C'rouzet motor. Drives 15 cams, each operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW PRICE: £5.75. P. & P. 25p.

50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instruction. £1.75 inc. post.

VENNER Electric Time Switch

200/250V Ex. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.

D.C. AMMETERS NEW!

1A, 5A, 15A, 20A, £1.75. 0-300V a.c., £1.90, incl. P. & P.

"HONEYWELL" LEVER OPERATED MICRO SWITCH

15 amps, 250 volt A.C. c/o contacts. NEW in maker's Carton. Price: 10p for £1.90 incl. P. & P.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 140V a.c. 50/60 OUTPUT VARIABLE 0.260V from 1/2 to 50 amp stock. SHROUDED TYPE

1 amp, £7.00 2.5 amp, £8.05
5 amp, £11.75 10 amp, £22.50 20 amp, £49.00
15 amp, £25.00 25 amp, £58.00
37.5 amp, £82.00 50 amp, £98.00
OPEN TYPE (Panel Mounting) 1 amp, £4.75.
1 amp, £7.00 2 1/2 amp, £8.05. All types carriage paid.



Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 2A; 5 kΩ, 140 mA. Diameter 3 1/2 in. Shaft length 3 in, dia. 1/2 in. All at £1-65 each. P. & P. 75p.
50 WATT. 1/5/10/25/50/100/250/500/1111/5/2.5/5kΩ. All at £1-15 each. P. & P. 75p.
25 WATT. 10/25/50/100/250/500/111/5/2.5/3/5/5kΩ. All at 90p each. P. & P. 75p.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. EXPERIMENTERS' ECONOMY KIT Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.30, plus 25p P. & P. NEW INDUSTRIAL KIT! Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p. HY-LYGT STROBE MK III

This Strobe has been designed and produced for use in large halls and utilises a silica tube printed circuit for easy assembly. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £17.00. P. & P. 50p. SPECIALLY DESIGNED. FULLY VENTILATED METAL CASE. Including Reflector. £4.00 P. & P. 45p. Post paid with kit.

THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:
● Variable speed from 1-23 flash per sec.
● Reactor control circuit producing an intense white light. The brilliant light output of the 'SUPER' HY-LYGT gives fabulous effects with colour filter.
Now before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P. ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Lyght Kit including Reflector £7.00 P. & P. 45p. 7-inch POLISHED REFLECTOR Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.
6 in colour wheel as used for disco lighting effects etc. £5.75 incl. P. & P. can be operated from our 1 rpm synchronous motor 75p incl. P. & P.

RELAYS New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

1	2	3	4	1	2	3	4
52	3-6	2 c/o	63p*	700	22-30	6 c/o	75p
400	10-18	4 c/o	73p*	700	15-35	2 c/o HD	73p*
600	12-24	4 c/o	78p*	700	16-24	6M	65p*
600	18-32	4 c/o	78p*	1,250	24-36	4 c/o	63p*
700	16-24	4M 2B	63p*	2,500	36-45	6M	63p*
700	16-24	4 c/o	78p*	2,400	30-48	4 c/o	50p*
700	12-24	2 c/o	63p*	9,000	6-12	6M	50p*
700	6-12	1 c/o HD 50*	15k	85-110	6M	50p*	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. *Including Base

12 VOLT D.C. RELAY 140 OHM COIL

Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)

'DIAMOND H' 230 VOLT A.C. RELAYS (UNUSED)

Three sets c/o contacts rated at 5 amps. Price: 50p P. & P. 10p. (100 lots £40.00 incl. P. & P.)

'KEY SWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. BOXED. Price: 40p. P. & P. 5p. (100 lots £32.00 incl. P. & P.)

230 VOLT A.C. SOLENOID OPERATED FLUID VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1/4" b.s.p. inlet/outlet. Precision made. British mfg. Price £1.75. P. & P. 20p. Special quotation for quantity.

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. E.E. 57 BRIDGMAN ROAD, CHISWICK, W4 5BB
Phone 01-795 1560 SHOWROOM NOW OPEN MON-FRI.

Personal callers only. Open Sat.
9 LITTLE NEWPORT ST.
LONDON WC2H 7JJ 01-437 0579

TRANSISTORS

A SELECTION FROM OUR LIST

AAV30 10p	BD115 75p	OC16 50p	2N1303 18p
AAV42 15p	BD123 85p	OC22 85p	2N1304 22p
AAZ13 10p	BD124 80p	OC22 50p	2N1305 22p
AAZ17 10p	BD132 80p	OC24 60p	2N1306 25p
AC107 35p	BDY11 1.50	OC25 40p	2N1307 25p
AC126 30p		OC28 25p	2N1308 25p
AC127 25p	BDY17 1.50	OC28 60p	2N1309 25p
AC127 50p		OC29 60p	2N1314 20p
AC128 20p	BDY28 45p	OC35 50p	2N1447 75p
AC176 20p	BDY60 1.00	OC36 60p	2N1610 40p
AC187 25p		OC42 40p	2N2217 25p
AC188 25p		OC43 50p	2N2218 20p
AC17 30p	BF115 25p	OC44 15p	2N2218A 25p
AC18 25p	BF154 20p	OC45 12p	2N2219 20p
AC19 25p	BF158 15p	OC70 12p	2N2219A 25p
AC20 20p	BF159 35p	OC71 12p	2N2220 25p
AC21 20p	BF180 35p	OC72 20p	2N2221 20p
AC22 10p	BF194 15p	OC75 25p	2N2222 20p
AC23 35p	BF195 15p	OC76 25p	2N2222A 20p
AC24 20p	BF196 15p	OC77 40p	2N2222B 20p
AC24 15p	BF197 15p	OC78 25p	2N2222C 20p
AD140 50p	BFX13 25p	OC81D 20p	2N2222D 20p
AD149 50p	BFX29 25p	OC81Z 40p	2N2222E 20p
AD161 35p	BFX30 25p	OC83 25p	2N2222F 20p
AD162 35p	BFX34 25p	OC84 25p	2N2222G 15p
AD174 25p	BFX35 25p	OC139 25p	2N2269A 15p
AF115 25p	BFX87 25p	OC141 80p	2N2646 40p
AF116 25p	BFX88 20p	OC170 25p	2N2904 20p
AF117 20p	BFY18 25p	OC171 30p	2N2904A 20p
AF118 60p	BFY50 20p	OC200 40p	2N2905 25p
AF124 25p	BFY51 20p	OC201 75p	2N2905A 25p
AF125 20p	BFY52 15p	OC206 95p	2N2906 20p
AF126 20p	BFY43 15p	OC206 95p	2N2906A 20p
AF127 20p	BFY90 65p	OC271 97p	2N2906B 20p
AF128 20p	BSX20 15p	ORP12 50p	2N2906C 20p
AF180 50p	BSX21 20p	ORP60 40p	2N2907 23p
AF181 45p	BSY27 15p	RT140 15p	2N2907A 20p
AF185 50p	BSY28 15p	RT141 20p	2N2907B 25p
AF186 40p	BSY29 15p	TIP29A 50p	2N2907C 25p
AF189 40p	BU105 £2.25	TIP30A 60p	2N2907D 15p
ASB26 25p	RV100 15p	TIP31A 60p	2N2926 10p
ASB27 30p	BY126 12p	TIP32A 70p	2N3001 20p
ASB28 25p	BY124 15p		2N3002 20p
ASB29 30p	BY125 15p		2N3003 20p
ASB31 25p	BY210 85p	TIP34A 1.00	2N3003 50p
BA100 15p	BYZ11 30p		2N3003 75p
BA102 30p	BYZ12 30p	TIP34A 1.00	2N3003 75p
BA110 25p	BYZ13 20p	TIP34A 1.00	2N3003 75p
BA115 7p	BYZ7821.00	TIP34A 1.00	2N3003 75p
BA118 5p	GET102 35p	TIP34A 1.00	2N3003 75p
BA121 7p	GET103 35p	TIP34A 1.00	2N3003 75p
BA131 7p	GET111 45p	TIP34A 1.00	2N3003 75p
BA138 15p	GET113 25p	TIP34A 1.00	2N3003 75p
BC107 10p	GET114 20p	TIP34A 1.00	2N3003 75p
BC108 10p	GET115 60p	TIP34A 1.00	2N3003 75p
BC109 10p	GET116 60p	TIP34A 1.00	2N3003 75p
BC109C 12p	GET117 12p	TIP34A 1.00	2N3003 75p
BC113 10p	GET118 12p	TIP34A 1.00	2N3003 75p
BC114 10p	GET119 12p	TIP34A 1.00	2N3003 75p
BC115 20p	GET120 12p	TIP34A 1.00	2N3003 75p
BC116 20p	GM378A 55p	TIP34A 1.00	2N3003 75p
BC116A 20p	MAT101 25p	TIP34A 1.00	2N3003 75p
BC117 20p	MAT191 25p	TIP34A 1.00	2N3003 75p
BC118 20p	MJ242 80p	TIP34A 1.00	2N3003 75p
BC119 30p	MJ420 80p	TIP34A 1.00	2N3003 75p
BC124 20p	MJ421 80p	TIP34A 1.00	2N3003 75p
BC125 15p	MJ2801 15p	TIP34A 1.00	2N3003 75p
BC126 20p	MJ290 1.10	TIP34A 1.00	2N3003 75p
BC127 20p	MJ290 1.10	TIP34A 1.00	2N3003 75p
BC128 20p	MJ290 1.10	TIP34A 1.00	2N3003 75p
BC129 20p	MJ290 1.10	TIP34A 1.00	2N3003 75p
BC147 12p	MJ340 50p	TIP34A 1.00	2N3003 75p
BC148 10p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC149 12p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC149 12p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC153 20p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC154 20p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC157 15p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC159 12p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC159C 15p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC177 20p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC178 20p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC179 20p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC182L 10p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC183 10p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC183L 10p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC184L 12p	MJ350 20p	TIP34A 1.00	2N3003 75p
BC212L 12p	NK7214 20p	TIP34A 1.00	2N3003 75p
BC213L 12p	NK7216 35p	TIP34A 1.00	2N3003 75p
BC214L 15p	NK7403 75p	TIP34A 1.00	2N3003 75p
BC230 35p	NK7404 50p	TIP34A 1.00	2N3003 75p
BC231 40p	OAP 40p	TIP34A 1.00	2N3003 75p
BC232 60p	OAI0 25p	TIP34A 1.00	2N3003 75p
BC233 30p	OAO7 10p	TIP34A 1.00	2N3003 75p
BC234 35p	OAO7 10p	TIP34A 1.00	2N3003 75p
BC235 30p	OAO7 10p	TIP34A 1.00	2N3003 75p
BC236 30p	OAO7 10p	TIP34A 1.00	2N3003 75p
BC240 50p	OAS1 8p	TIP34A 1.00	2N3003 75p
BOY70 15p	OAS7 7p	TIP34A 1.00	2N3003 75p
BCV71 20p	OAS9 7p	TIP34A 1.00	2N3003 75p
BCV72 15p	OAO22 10p	TIP34A 1.00	2N3003 75p

Full transistor list available—send for your free copy today!

HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW FULL SPECIFICATION TTL74 SERIES
 BRANDED FAIRCHILD, I.T.T. AND TEXAS
 DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICES

No.	Description	1-11	12-84	85-90	100+	250+
7400	Quadrate 2-input NAND gates	20p	18p	14p	14p	12p
7401	Quad 2-input open collector NAND gates	20p	18p	16p	14p	12p
7402	Quad 2-input NOR gates	20p	18p	18p	14p	12p
7403	Quad 2-input open collector NAND gates	20p	18p	18p	14p	12p
7404	Hexuple inverters	20p	18p	18p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	18p	14p	12p
7406	Triple 3-input NAND gates	20p	18p	18p	14p	12p
7413	Dual 4-input Schmitt triggers	30p	27p	25p	22p	20p
7420	Dual 4-input NAND gates	20p	18p	18p	14p	12p
7430	Single 8-input NAND gates	20p	18p	18p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	18p	14p	12p
7441	BCD-Decimal decoder/Nixie driver	75p	72p	70p	60p	55p
7442	BCD-Decimal decoder (4-10-line) TTL O/P	75p	72p	70p	60p	55p
7443	Excess 3-Decimal decoder TTL outputs	£1.00	95p	90p	80p	70p
7447	BCD-Decimal 7 seg. decoder/indicator driver	£1.75	£1.60	£1.45	£1.30	£1.15
7448	BCD-Decimal 7 seg. decoder/indicator driver TTL O/P	£1.75	£1.60	£1.45	£1.30	£1.15
7450	Expand dual 2-input AND-OR-INVERT gates	20p	18p	18p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	18p	14p	12p
7453	Quad 2-input expand AND-OR-INVERT gates	20p	18p	18p	14p	12p
7454	4-wide 2-input AND-OR-INVERT gates	20p	18p	18p	14p	12p
7460	Dual 4-input expanders	20p	18p	18p	14p	12p
7470	Single J-K flip-flop (gated inputs)	30p	27p	25p	22p	20p
7472	Single J-K flip-flop (gated inputs)	30p	27p	25p	22p	20p
7473	Dual J-K flip-flop	40p	37p	35p	32p	30p
7474	Dual D flip-flop	40p	37p	35p	32p	30p
7478	Quadrate bistable latch	45p	42p	40p	35p	30p
7476	Dual J-K flip-flops with Preset and Clear	40p	37p	34p	31p	28p
7480	Gated Full Adder	80p	72p	67p	59p	55p
7481	16-bit read/write memory	£1.25	£1.15	£1.10	£1.00	90p
7482	2-bit binary Full Adder	67p	60p	55p	48p	41p
7483	4-bit binary Full Adder	£1.00	90p	85p	75p	70p
7484	16-bit RAN with gated write inputs	40p	35p	32p	28p	25p
7488	Quadrate 2-Input Exclusive OR gates	85p	75p	70p	60p	55p
7490	BCD decade counter	75p	70p	65p	60p	55p
7491	8-bit shift register	£1.00	95p	90p	80p	70p
7492	Divide by two counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	75p	70p	65p	60p	55p
7494	Dual 4-bit shift register	80p	75p	70p	65p	60p
7495	4-bit up-down shift register	80p	75p	70p	65p	60p
7496	5-bit parallel/serial in/out shift register	£1.00	97p	95p	85p	80p
74100	8-bit bistable latch	£2.60	£2.30	£2.00	£1.75	£1.50
74118	Hexuple Set-Reset latches	£1.00	95p	90p	80p	70p
74121	Monostable multivibrator	60p	55p	50p	45p	40p
74141	BCD-Decimal decoder/Nixie driver	£1.60	£1.40	£1.30	£1.10	£1.00
74145	BCD-Decimal decoder (4-10-line) TTL O/P	£1.60	£1.40	£1.30	£1.10	£1.00
74151	8-bit data selector/multiplexer	£3.35	£3.20	£2.95	£2.15	£2.05
74152	8-bit data selector/multiplexer	£1.10	95p	90p	80p	70p
74153	Dual 4-line to 1-line data selector/multiplexer	£1.35	£1.27	£1.20	£1.15	£1.10
74154	16-bit decoder/demultiplexer	£2.00	£1.75	£1.55	£1.30	£1.05
74155	Dual 2-line to 4-line decoder/demultiplexer	£1.65	£1.47	£1.35	£1.10	£1.05
74156	Dual 2-line to 4-line decoder/demultiplexer	£1.65	£1.47	£1.35	£1.10	£1.05
74158	Dual 2-line to 4-line decoder/demultiplexer	£1.65	£1.47	£1.35	£1.10	£1.05
74159	8-bit decade up-down counter, 1-line mode	£1.85	£1.85	£1.75	£1.60	£1.50
74191	8-bit decade up-down counter, 1-line mode	£1.95	£1.85	£1.75	£1.60	£1.50
74192	8-bit decade up-down counter, 2-line mode	£2.00	£1.90	£1.80	£1.65	£1.55
74193	8-bit decade up-down counter, 2-line mode	£2.00	£1.90	£1.80	£1.65	£1.55
74198	8-bit decade up-down counter, 2-line mode	£2.00	£1.90	£1.80	£1.65	£1.55
74199	Asynchronous presetable decade counter	£1.50	£1.40	£1.30	£1.10	£1.00
74197	Asynchronous presetable 4-bit binary counter	£1.50	£1.40	£1.30	£1.10	£1.00

Complete data on the above is booklet 20 pages, Ref. 29, issue 2 at 15p post paid.
 Texas I.C. Handbook. Complete information on 100 types. 40p. Post 10p.
 Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 30p.

INTEGRATED CIRCUITS

MFC4000P	55p
MFC4010P	80p
IC12	£2.60
PAD246	£1.50
TAD100	£1.50
TAD110	£1.50
MC724P	50p
702C (T05)	75p
709C (D.I.L.)	45p
709C (D.I.L.)	45p
723C(T05)	£1.00
741C(T0	

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated Telescopic Aerial, for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 8" x 2 1/2" Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off. Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)

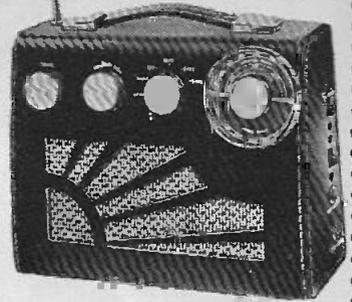

ROAMER EIGHT Mk I


NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 8" x 2 1/2" Speaker. Air spaced ganged tuning condenser. Volume on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)


ROAMER SEVEN MK IV

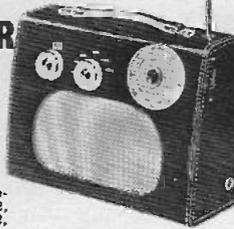

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 2 1/2in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.

Total building costs **£5-98** P. P. & Ins. 41p. (Overseas P. & P. £1)

ROAMER SIX

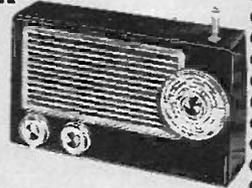

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3-98** P. P. & Ins. 26p. (Overseas P. & P. £1)

POCKET FIVE



3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 5 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 2 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 21p. (Overseas P. & P. 63p)

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 22p. (Overseas P. & P. 63p)

TRANS EIGHT

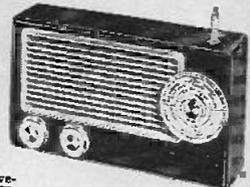

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and LW. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P. P. & Ins. 31p. (Overseas P. & P. £1)

NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY TO FOLLOW PAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4 "22" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: Diodes: Resistors: Capacitors: Three "J" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including Case and Plans **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)

FULL AFTER SALES SERVICE

• Callers side entrance Barratts Shoe Shop
• Open 10-1, 2.30-4.30 Mon.-Fri. 8-12 Sat.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for

Name

Address

(Dept. E.E.B.)

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · ELECTRONIC COMPONENTS · TEST · PA · DISCOTHEQUE · LIGHTING · MAIL ORDER

TEXAN



20 + 20 WATT I.C. STEREO AMPLIFIER

(As featured by "Practical Wireless" May/June 1972)

DEVELOPED BY "TEXAS" ENGINEERS FOR PERFORMANCE, RELIABILITY AND POWER

FEATURES INCLUDE: Low profile with specially designed Gardners Transformer. 6—i.c.'s, 10 Transistors, 4 Diodes, 2 Zeners. Fibre glass P.C. panel. Multi protection. Stabilised supply. DIN input/output. Complete chassis work.

FUNCTIONS: Separate Treble/Bass/Volume/Balance controls. Input selector. High-pa Radio, Tape in and out. Headphone socket. Scratch and rumble filters. Mono/Stereo switch.

SLIM DESIGN WITH SILVER TRIM—Chassis size overall 14" x 6" x 2" max.

TOTAL COMPONENT COST £32 (Parts list on request Ref. No. 20).

SPECIAL KIT PRICE £28.50, Post 45p.
(Optional Teak sleeve available July/August)

Henry's are sole U.K. trade and retail suppliers of the Texan—enquiries invited

TEXAS—HENRY'S VALUE & PERFORMANCE

LATEST EDITION CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

PRICE 55p
POST PAID
(40p FOR CALLERS)

10,000 Stock lines at Special Low Prices and Fully Guaranteed

Send to this address—Henry's Radio Ltd., (Dept. EE), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see below

PUBLIC ADDRESS, LIGHTING & DISCOTHEQUE EQUIPMENT

DJ105S 30 watt rms Amplifier, 4 inputs, master tone and volume controls etc. 8 ohm output. Cased portable. £33.50. Post 40p.

DJ70S 70 watt rms version. Cased portable. £49.75. Post 40p.

DISCOAMP 100 watt rms to 8 ohms. 4 inputs, separate bass and treble controls, PFL, etc. Cased for cabinet or rack mounting £67.50. Post 40p.

MCDONALD MP60 fitted to plinth with cover. SC5MD cartridge to match above amplifiers. £17.25. Post 70p.

DJ30L11 3 channel light control unit for above amplifiers. 3 x 1 K Watt. Treble, Bass and Mid range. £28.50. Post 35p. DJ40L as 30L plus mike £37.50

EFFECTS PROJECTORS—Coloured rotating light patterns.

DISCO-COLT 150w Tungsten £22.50

LIQ1 50—50 watt Q.I. £32.50

LIQ1 150—150 watt Q.I. £50.00

Complete range of Disco/PA/Lighting on display at "309"

TEST EQUIPMENT
Huge range in stock—too much to list here. It's all in the latest catalogue—prices—specifications etc. Also Panel Meters and Edge Meters.



GARRARD McDONALD GOLDRING TURNTABLES

CHASSIS (Post 50p)
SP25/3 £10.50 HT70 £15.00
MP60 £10.40 MP610 £14.15
AP76 £18.85 Zero 1005 £40.75

With PLINTH/COVER (Post 70p)

HL75 PC £17.20

MP60 PC £35.25

HT70 PC £21.60

GL72P £19.25

CART/PLINTH/COVER (Post 70p)

GL72PC/G800 £34.50

(HL)AP76/G800 £29.95

HT70 PC/G800 £27.00

MP60 PC/G800 £17.25

(HL)SP25/G800H £18.95

(HL)2025 TC/9TAHCD £13.50

ULTRASONIC TRANSISTOR TESTERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.

PRICE PAIR £5.90 Post 10p

POWER INTEGRATED CIRCUITS

5L403D—3 watt with 8 page data, layouts & circuits £1.50 P.C. Board 60p; Heat Sink 14p

IC12—6 watt with data and circuits £1.80

TH9013P—20 watt Power Amp Module £4.57

TH9014P—IC Preamplifier £1.50

Data / Circuits Book for No. 42 10p

TEXAS PUBLICATIONS

1-100 watt Amplifiers and Preamp. Layouts and data £1.25 (Price list No. 48A FREE)

700 page IC Data Book (No. 2) (All TTL IC's) 60p

420 page Transistor Data (No. 3) 60p

340 page Transistor Data (No. 4) 60p

(Post etc. 20p each.)

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)

XN3, XN13, GN6 0-9. Side view with data 85p.

GNP-7, GNP-8 0-9. Side view with decimal points and data 95p.

3015F 7-Segment £7 per 4 with data. New Digital Clocks Circuits, Nixie and 7 segment. Ref 31 15p

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.

TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.

TYPE 150 TC Twin cone version £2.75. Post 22p.

TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.85. Post 25p.

TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7.70. Post 28p.

POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

HIGH POWER AMPLIFIER MODULES

MPA12 Quality transformerless low noise amplifiers suitable for all Audio, PA and Hi-Fi use. Modern compact designs. PA25 and PA50 supplied with plug harness for use with MU442 Power Supply.

MPA12/3 18v. 0.8A. 12W. 3-4 ohm. £4.50

MPA12/15 30v. 0.5A. 12W. 12-16 ohm. £5.25

MPA2/40 Mains unit for 1 or 2 MPA12/3 or 15. £4.50

PA25 22-0-22v. 1A. 25W. 8 ohm. £7.50

PA50 22-0-22v. 2A. 50W. 3-4 ohm. £9.50

MU442 Mains unit for 1 or 2 PA25 or 1 only PA50. £6.00

Post 20p per unit

ALL SILICON-FET PREAMPLIFIER AND MIXER SELF POWERED

All inputs. Adjustable input and output. DIN sockets. Tape in and out. Microphone mixing. Suitable up to 4-PA25 or 2-PA50.

PRICE £10.50 Post 30p

PRICE £10.50 Post 30p