


An exciting hobby.... for everyone

everyday electronics


OCT. 72
15p




REACTOMATIC

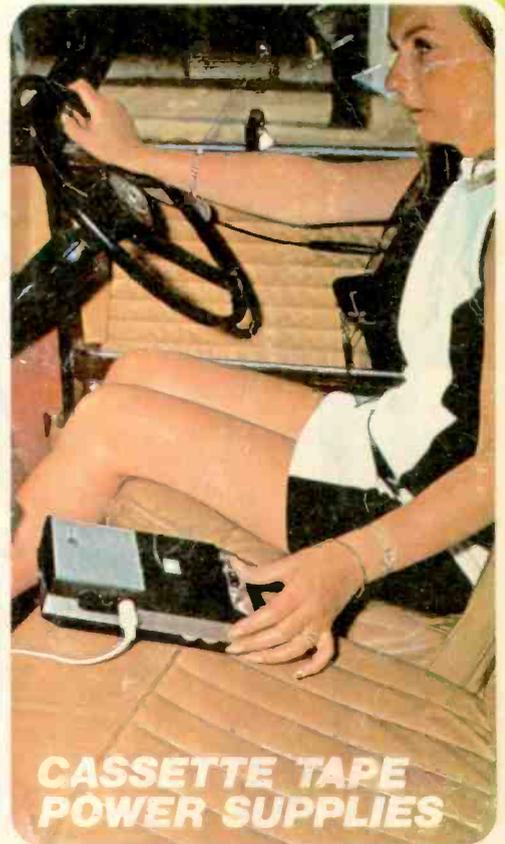

**CASSETTE TAPE
POWER SUPPLIES**

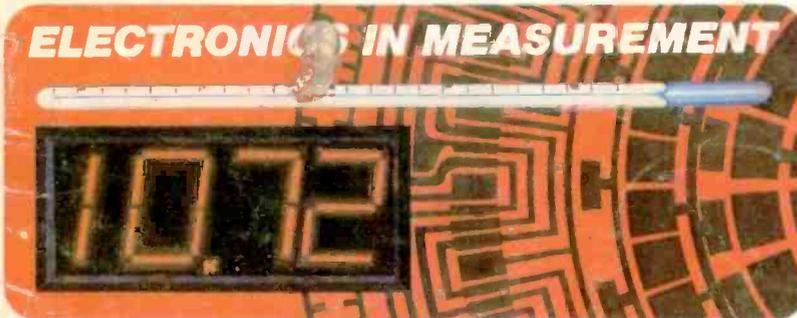

ELECTRONICS IN MEASUREMENT

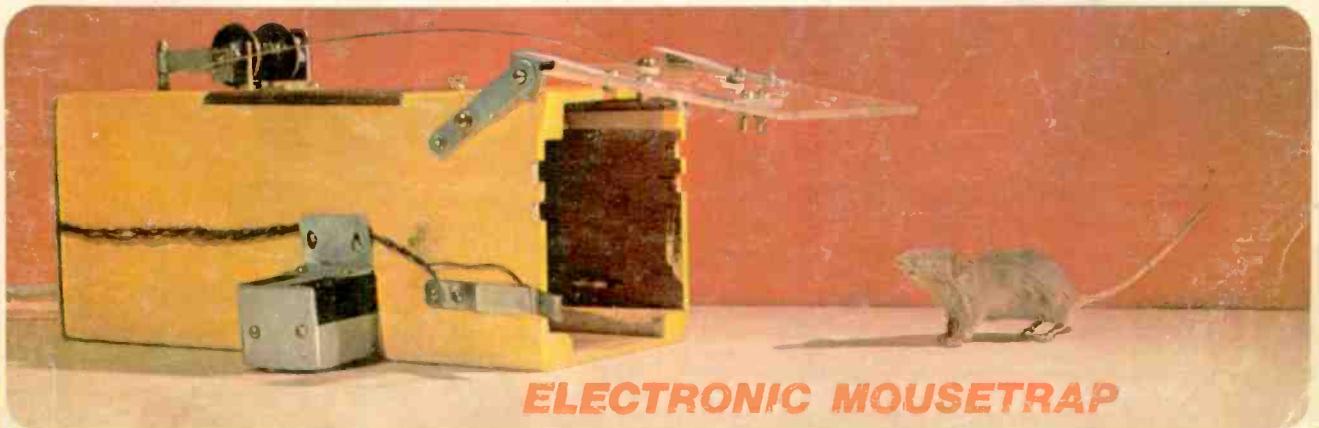

ELECTRONIC MOUSETRAP

ADCOLA

meet the precision
'INVADER' SOLDERING INSTRUMENTS

Precision instruments supplied with standard detachable copper chisel face bits. Standard temp. 360°C at 19/23/27 watts. Special temps. from 250°C/410°C.



L1076
BIT SIZE 1/4"
6.34 mm Dia.
27 watts.
£2.18

For perfection
in soldering

L646
BIT SIZE 3/16"
4.75 mm Dia.
23 watts.
£2.12

L706 →
BIT SIZE 1/8"
3.2 mm Dia.
19 watts.
£1.96



Don't take chances. We don't. All our ADCOLA Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get good service ... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this production tool. ADCOLA day after day.


Send for **NEW** catalogue today

ADCOLA PRODUCTS LTD. ADCOLA HOUSE GAUDEN ROAD LONDON, SW4 6LH
Postage, packing paid on orders over £2. under £2 add £0.10

Models required _____
Enclosing P/O or cheque for _____
Name _____
Address _____

EE4

Are you alright for Jacks?

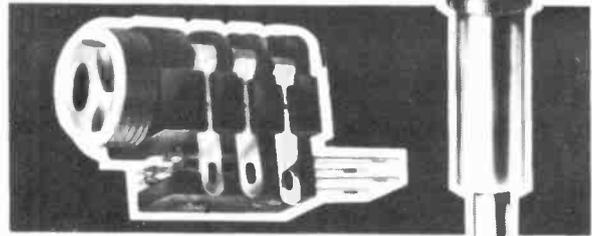

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes ... plugs in both screened and unscreened versions ... socket bodies in high melting point thermoplastic ... several unique features (some protected by UK and US Patents) ... Post Office and NATO specifications.

If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!



RENDAR®

Rendar Instruments Ltd., Victoria Road
Burgess Hill, Sussex. Tel. Burgess Hill 2642-4
Cables: Rendar, Burgess Hill

SOUND BARGAINS



GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER

WITH 3 IN 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

BEST OF ALL WORLDS

VHF FM, AM, AFC, AIR BAND, PUBLIC SERVICE AND WEATHER BANDS

OUR PRICE £10.50
+40p P. & P.

THIS NEW 1972 RADIO. No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHER-BAND. Frequency ranges: MW340-1600 KHZ, FM188-108MHZ, Airband 108-145 MHZ, VHF 145-175MHZ, 23 semi-conductors—12 transistors, 11 diodes and thermistors. Automatic frequency control. 31" telescopic aerial. Runs off mains AC 230/250 volts or off 4 U2 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10 1/2" x 6 1/2" x 3 1/2". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries FREE. **HURRY!** Limited quantity only from Marktyme. Fully guaranteed.

BATTERY CHECK INDICATOR

OUR PRICE £28.95
+50p P. & P.



Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 180-350Kcs. Medium 353-1605Kcs. Marine 1.6-4.5Mcs. Short Wave 12-24Mcs. FM/VHF 88-108Mcs. Aircraft 108-135 Mca. **PUBLIC SERVICE BANDS 135-174Mcs.** Fully guaranteed.

N.B.—The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

MARKTYME (Dept. ED5), 372 EDGWARE ROAD, LONDON, W.2. Tel. 01-723 0094.
Callers welcome Monday to Saturday 9 a.m.—6 p.m.

That's Summer that was!!



Summer was so late arriving this year that it nearly slipped by without our noticing it! Already we are tucking the lawn mower in for its winter hibernation, and once again "the nights are drawing in". HOORAY!—that means we can really get cracking on those electronic projects that have been buzzing around at the back of our minds.

The first step is to get the *components* lined up. And the best way to do that? Simple—get a copy of the Home Radio Components Catalogue. Then we can quickly and clearly see what we need and how much it costs. We'll know too that either by sending an order or by calling in at the Mitcham shop, we can get just what we want "off the shelf". The catalogue costs 70p, including post and packing, or 50p over the counter. Every copy contains 10 vouchers, totalling a value of 50p when used as instructed—so you can soon get back the cost of the catalogue. Over 8,000 items are listed, over 1,500 of them illustrated, and free supplements are supplied regularly to keep you up-to-date.

Post the coupon today, or call at our shop S.A.P.—we're open 9 to 5.30 Monday to Saturday, except Wednesday 9 to 1.

It would help us considerably if we knew whether this was your first Home Radio Components Catalogue. If it is, please place a tick in the box.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

Our CREDIT ACCOUNT SERVICE makes it so simple to purchase

Our customers find this service a very simple and convenient way of purchasing all their radio and electronic components. We supply pre-paid envelopes and order forms, and no matter how many orders you send us you make only one payment per month. There are several other advantages too—full details and entry forms are included in our catalogue.

Telephone
01-648 8422



**POST THIS
COUPON
with your
cheque or
postal order
for 70p**

This is my first H.R. Components Catalogue

Name _____

Address _____

HOME RADIO (COMPONENTS) LTD., Dept. EE
234-240 London Road, Mitcham, Surrey CR4 3HD.

INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY £3-25



CAN'T SLEEP AT NIGHTS DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP. AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. SEND £3-25 + 25p p. & p. (parts available separately).

BUILD 5 RADIO AND ELECTRONIC PROJECTS

ONLY £2-45



Amazing Radio Construction set! Become a radio expert for £2-45. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. Send £2-45 + 20p p. & p.

Eavesdrop on the exciting world of Aircraft Communications

V.H.F. AIRCRAFT BAND CONVERTOR ONLY £2-85



Listen in to AIR-LINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk down. Be ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over 19 years in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portable). NO CORRECTIONS WHAT-EVER NEEDED. SEND ONLY £2-85 + 20p p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

FIND BURIED TREASURE!

Transistorised Treasure Locator



This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL FINDS ETC. ETC. Extremely sensitive. Will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY £2-95 + 25p p. & p. (Sectional handle as illustrated 95p extra). Parts available separately. Made up looks worth £15.

SHORTWAVE

TRANSISTOR RADIO

only £2-75



Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2" ONLY £2-75 + 20p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHE YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost self-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, nuts, screws, wire, etc. no soldering £2-75 + 25p p. & p. Parts available separately.

ELECTRONIC ORGAN

ONLY £3-25



Don't confuse with ordinary electronic organs that simply blow air over mouth-organ type reeds etc. Fully transistorised. SELF CONTAINED LOUDSPEAKER. 17 (separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED. No soldering necessary. Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions. ONLY £3-25 + 25p p. & p. for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY £4-95



FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN £4-95 + 30p carr. etc. (High quality Danish Stethoscope headphones £2-75 extra if required.) EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDABLE IN FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD. (EE10U) 8, Westbourne Grove London W.2. Callers Welcome

Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression: 600 Watt £3-20. Kit Form £2-70 300 Watt £2-70. Kit Form £2-20

All plus 10p post and packing. Please send C.W.O. to:

DEXTER & COMPANY
5 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH Tel: 0244-25883,
As supplied to H.M. Government Departments.

INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2-60 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC.. UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2-60 post paid.

MAIL ORDER ONLY.

S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

38a, LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p. P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 1 1/2in x 4in. 4 for £1. P. & P. 25p.

709C OPERATIONAL AMPLIFIER TOS
8 lead I.C. 1 off 50p. 50 off 25p. 100 off 20p.

250 MIXED RESISTORS 62p
1/2 and 1 watt.

150 MIXED HI STABS 62p
1/2, 1 and 1 watt 5% and better.

QUARTZ HALOGEN BULBS
With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

GPO EXTENSION TELEPHONES
with dial but without bell. 95p each, P. & P. 30p. £1-75 for 2. P. & P. 50p.

BARGAIN RELAY OFFER
Single pole change over silver contacts 25V to 50V. 2-5k Ohm coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
44 EARLS COURT ROAD
LONDON, W.8 01-478 8499

PREMIER 800 STEREO AMPLIFIER



(As used in
SYSTEM '800')

A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1% Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 6½" x 2½".

ONLY £15.00 Carr. 50p.


Mk. 11 Version available with Teak Finish Cabinet. £16.25. Carr. 50p.

PREMIER HI-FI STEREO SYSTEMS

SYSTEM "800"

Consists of the Premier 800 Mk II all transistor stereo amplifier (described left) Garrard auto/manual record player unit fitted stereo/mono cartridge with diamond stylus and mounted in teak finish plinth with cover and two cloth front loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 800 Mk II amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch. Headphone socket. Power on/off. Teak finish cabinet with aluminium front panel. Size: 12½in x 6½in x 2½in.

£35.00
Carr. £1.75

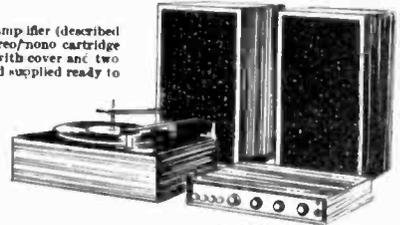

SYSTEM "TWO"

as above but with slotted front teak finish loudspeakers, Garrard SP25 Mk. III and magnetic cartridge.

£45.00
Carr. £1.75

SYSTEM "THREE"

This consists of KLINGER K0903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and Ceramic pick-up, tuner, tape in and out. Stereo headphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Ronotone 9TABCD diamond stereo cartridge. A pair of HMP Speakers size 16½" x 10½" x 9" fitted EM1 units complete the matching system.

£57.75
£1.75

FREE
LEADS
AND PLUGS
SUPPLIED
WITH ALL
SYSTEMS

PREMIER PARAGON STEREO HI-FI AMPLIFIER



Gives the best possible reproduction of records, radio and tape at a reasonable price.

Fitted with all the controls and facilities you're ever likely to want, the Paragon gives you a degree of sophistication that is usually only found with amplifiers costing twice its price. It has bass and treble slide controls, volume and balance knobs, and eight push-buttons. There's also a standard stereo jack socket on the front panel, plus a ceramic/magnetic cartridge switch and a mains outlet socket on the back panel.

Specifications: 10 + 10 watts into 8 ohms. Power/frequency response: 0dB 10 watts into 8 ohms -3dB 20Hz - 25KHz. Distortion typically less than 0.25%. Inputs for Magnetic phono (4mV) Crystal phono (66mV) Radio/Tape (100mV). High and low filters. Teak finish cabinet. Size: 12½" x 5½" x 10½".

£32.50 P. & P. 50p.



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 P. & P. watt. 240 volt A.C. £3.95 P. & P.

"Marksmen" Soldering Iron. Lightweight ½" pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. £1.50 P. & P. 16p.

VERITAS V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds.

£1.72
P. & P. 15p.



E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2½in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.

£3.47 P. & P. 50p

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILIBED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

| | | | | | |
|---------------|-----------|-----|---------------|-----------|-------|
| TT3 3' 450' | POLYESTER | 37p | DT6 5½' 1800' | POLYESTER | £1.12 |
| DT3 3½' 600' | POLYESTER | 87p | TT6 5½' 2400' | POLYESTER | £1.87 |
| SP5 5' 800' | P.V.C. | 42p | SP7 7' 1200' | P.V.C. | 62p |
| LP5 5' 900' | ACETATE | 50p | LP7 7' 1800' | ACETATE | 75p |
| DT5 5' 1200' | POLYESTER | 75p | DT7 7' 2400' | POLYESTER | £1.25 |
| LP6 5½' 1200' | ACETATE | 75p | TT7 7' 3600' | POLYESTER | £2.50 |

TAPE SPOOLS 3" 5p, 5", 5½", 7" 9p.
Post and Packing 3" 5p, 5", 5½", 8p, 7" 10p (3 reels and over Post Free).



PREMIER HI-FI OFFERS

Rogers Ravensbrook II Stereo Amplifier teak £38.50
Rogers Ravensbourne Stereo Amplifier teak £49.00
Metrosound ST20E Stereo Amplifier teak £25.50
Goldring GL72 less cartridge £22.00
Garrard SP25 III with Goldring G800 cartridge £15.00



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE. COMPLETE IN TEAK FINISH WITH COVER.
Total list price over £34.

PREMIER PRICE
£17.95
P. & P. 50p.

Garrard AP76 with G800, ready wired to 5 pin Din in plinth with cover £29.50

Garrard AP76 less cartridge £18.80

Garrard 401 Transcription Unit List £40.15 £27.40

Garrard 2025 T/C with Stereo Ceramic Cartridge £8.50
Garrard 2025 T/C with Stereo Ceramic Cartridge £12.45

ready wired in teak plinth with cover
Carriage and Insurance 60p extra any item.

CARTRIDGE BARGAINS!
Goldring G800H £5.00; G800 £5.50; G800E £9.50; P. & P. 10p



METER BARGAIN

MODEL GT-800 MULTIMETER
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 10, 50, 250, 1,000V (1,000 opV). AC Voltage: 10, 50, 250, 1,000V (1,000 opV). DC Current: 1mA, 100mA. Resistance: 0-150K ohms. Decibel: -10 to +22dB (at AC 10V range) £2.47. P. & P. 25p.



MODEL CT680
Ranges - D.C. voltages: 0 - 3 - 15 - 60 - 300 - 600 - 1,200V (30,000 O.P.V.)
A.C. voltages: 0 - 6 - 30 - 120 - 600 - 1,200V (15,000 O.P.V.)
D.C. Current: 0 - 0.03 - 3 - 30 - 300mA
Resistance: 0 - 16 M ohms.
Decibels: - 20 to + 63dB.
£7.00. P. & P. 25p.



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.
£2.47 P. & P. 25p.



VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2½in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono plugs output. Attractive teak wood grain finish case.
MONO £3 STEREO £3.47 P. & P. 15p



GENUINE EMI-TAPE COMPACT CASSETTES LOW NOISE BRAND NEW IN LIBRARY CASES

C86 (List 71p) 85p
C90 (List 98p) 88p
C120 (List £1.48) 90p
P. & P. 10p



VERITONE CASSETTES

In library cases—fully guaranteed

C60-29p (3 for 81p) C90-40p (3 for £1.11) C120-52p (3 for £1.40)

P. & P. 10p each (3 and over 15p)

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



**FOR
RAPID
SERVICE**

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

TRANSFORMERS

all with 0-250 Volt primaries
Miniature
 MM6 6V, 500mA + 6V, 500mA
 MM12 12V, 250mA + 12V, 250mA
 MM20 20V, 150mA + 20V, 150mA
 £1.29 plus 13p p. & p.

L.T.
 LT1 6.3V, 1.5A—75p plus 18p p. & p.
 LT2 6.3V, 3A—80p plus 26p p. & p.
 LT3 12V, 1.5A—80p plus 26p p. & p.
 LT4 12V, 3A—£1.12 plus 30p p. & p.

LTS 9-0-9V, 0.5A—75p plus 21p p. & p.
 LTS 12-0-12V, 1A—95p plus 26p p. & p.
 LTS 30-0-30V, 1A—£1.87 plus 30p p. & p.

Multi-tapped
 MT30/2 0-12-15-20-24-30V, 2A—
 £1.95 plus 30p p. & p.
 MT60/1 0-5-20-30-40-60V, 1A—
 £1.97 plus 30p p. & p.
 MT60/2 0-5-20-30-40-60V, 2A—
 £2.90 plus 34p p. & p.

Charger
 CT/01 2A—£1 plus 26p p. & p.
 CT/02 2A—£1.25 plus 30p p. & p.
 CT/03 4A—£1.50 plus 30p p. & p.
 Secondaries—0.5-1-1-17V.

Auto-transformers
 AT30 30V—£1.18 plus 30p p. & p.
 AT75 75V—£1.95 plus 30p p. & p.
 AT150 150V—£2.55 plus 34p p. & p.
 AT300 300V—£4.75 plus 42p p. & p.
 AT1000 1000V—£8.90 plus 62p p. & p.

All shrouded with terminal blocks.
 AT30 0-110-240V. All others 0-
 110-200-220-240V.

Speaker isolating transformer
 1:1 ratio for 3-15Ω, 2W—80p plus
 13p p. & p.

Speaker matching transformer
 Tapped 3, 8, 16Ω. Will match
 almost any speakers to any amplifier.
 15W max.—90p plus 20p p. & p.

ALUMINIUM BOXES

with lids and screws

| Type | L | W | D | Price p. & p. |
|------|----------|----------|----------|---------------|
| GB7 | 5 1/2 in | 2 1/2 in | 1 1/2 in | 38p 15p |
| GB8 | 4 in | 4 in | 1 1/2 in | 38p 15p |
| GB9 | 4 in | 2 1/2 in | 1 1/2 in | 38p 13p |
| GB10 | 5 1/2 in | 4 in | 1 1/2 in | 44p 18p |
| GB11 | 4 in | 2 1/2 in | 2 in | 38p 13p |
| GB12 | 3 in | 2 in | 1 in | 33p 13p |
| GB13 | 6 in | 4 in | 2 in | 52p 18p |
| GB14 | 7 in | 5 in | 2 1/2 in | 63p 19p |
| GB15 | 8 in | 6 in | 3 in | 81p 26p |
| GB16 | 10 in | 7 in | 3 in | 92p 26p |

* These sizes fit standard veroboards



EQUIPMENT CASES

with sloping front panel

| Type | H | W | D | Price p. & p. |
|------|------|----------|----------|---------------|
| SF1 | 2 in | 5 1/2 in | 2 1/2 in | 45p 12p |
| SF2 | 2 in | 7 1/2 in | 3 in | 60p 16p |
| SF3 | 2 in | 9 1/2 in | 4 in | 75p 19p |

Plain aluminium.
 Stove - enamelled silver-grey hammer finished. 20p extra.



CONSOLE CASES

in plain aluminium, ideal for mixers, instruments, etc.

| Type | W | A | B | C | D | Price p. & p. |
|------|-------|------|----------|------|------|---------------|
| GB20 | 8 in | 9 in | 3 1/2 in | 2 in | 3 in | £1.42 30p |
| GB21 | 10 in | 9 in | 3 1/2 in | 2 in | 3 in | £1.58 30p |
| GB22 | 12 in | 9 in | 3 1/2 in | 2 in | 3 in | £1.72 30p |



VEROBOARD

| Size | 0.1 matrix | 0.15 matrix |
|---------------------|------------|-------------|
| 2 1/2 in x 3 1/2 in | 22p | 16p |
| 2 1/2 in x 5 in | 24p | 25p |
| 3 1/2 in x 3 1/2 in | 24p | 25p |
| 3 1/2 in x 5 in | 27p | 29p |
| 1 7/8 in x 2 1/2 in | 75p | 57p |
| 1 7/8 in x 3 1/2 in | £1.75p | 75p |

Pins—either size, packet of 36, 18p

ELECTROLYTICS

| | | | | | |
|-------|------|-----|---------|------|-----|
| 1μF | 450V | 19p | 1,000μF | 25V | 27p |
| 2μF | 500V | 20p | 1,000μF | 50V | 39p |
| 4μF | 350V | 14p | 2,000μF | 25V | 36p |
| 8μF | 450V | 16p | 2,000μF | 50V | 53p |
| 16μF | 450V | 17p | 2,500μF | 25V | 45p |
| 25μF | 25V | 7p | 2,500μF | 50V | 60p |
| 25μF | 50V | 8p | 3,000μF | 25V | 48p |
| 32μF | 450V | 24p | 5,000μF | 25V | 55p |
| 50μF | 50V | 10p | 5,000μF | 50V | 98p |
| 100μF | 25V | 10p | 8-16μF | 450V | 18p |
| 100μF | 50V | 10p | 16-16μF | 450V | 20p |
| 250μF | 25V | 12p | 16-32μF | 450V | 27p |
| 250μF | 50V | 17p | 32-32μF | 450V | 63p |
| 500μF | 25V | 18p | 32-32μF | 450V | 49p |
| 500μF | 50V | 25p | 50-50μF | 350V | 38p |

MINIATURE ELECTROLYTICS

| | | | | | |
|-------|-----|----|-------|-----|----|
| 1μF | 63V | 6p | 10μF | 64V | 7p |
| 2.2μF | 63V | 6p | 10μF | 40V | 7p |
| 4μF | 40V | 7p | 30μF | 15V | 7p |
| 4.7μF | 63V | 6p | 47μF | 16V | 7p |
| 8μF | 15V | 7p | 47μF | 25V | 6p |
| 8μF | 40V | 7p | 68μF | 16V | 6p |
| 10μF | 25V | 6p | 100μF | 10V | 6p |

ENTIRE MULLARD 015 016 017 RANGE
 ALSO STOCKED

CASSETTE OWNERS!

For Philips and similar cassette recorders.
 PU12 Power unit for connection to
 12V + or - E car electrical
 systems, giving 7 1/2V, stabilised
 output. **£3.25**

PU14 As above but switched for
 6V, 7 1/2V or 9V output. **£5.10**

PP75 Mains power supply, output
 7 1/2V d.c. **£1.95**

All units are complete with cable and plug.

VARIABLE POWER SUPPLY

Input: 240V, a.c.
 Output: Switched 3, 4.5, 6, 7.5, 9,
 12 volts d.c. at 500mA **£4.20**

BATTERY ELIMINATORS

suitable for transistor radios and similar light
 current equipment
 PP6 Input 240V a.c. Output 6V d.c.
 PP9 Input 240V a.c. Output 9V d.c.
 Price £1.50 plus 12p p. & p.

NEW ILLUSTRATED 1972-73 CATALOGUE Post Free 15p

CONTROLS, Log. or Lin.

Single, less switch, 15p
 Single, D.P. switch, 24p
 Tandem, less switch, 40p
 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ,
 500kΩ, 1MΩ, 2MΩ

SLIDER CONTROLS, 87mm.

complete with knobs.
 Single, 44p; Tandem, 55p. 10kΩ, 25kΩ,
 50kΩ, 100kΩ, log. or lin.

RESISTORS

Carbon
 All 5%, high-stability, E12 values. 1W, 1p;
 1/2W, 1 1/2p; 1W, 4p; 2W, 6p
 Wire-wound
 5W, 10p; 10W, 12p

LOUDSPEAKERS

7in x 4in, 3Ω—£1.12, 8Ω—£1.12,
 15Ω—£1.40
 8in x 5in, 3Ω—£1.85, 8Ω—£1.77,
 15Ω—£1.70
 10in x 6in, 3Ω—£2.32, 8Ω—£2.32,
 15Ω—£2.32
 8in round, 3Ω—£2.10, 8Ω—£2.50,
 15Ω—£2.10
 Adastral "Hi-Ten" 10in, 10W, 8 or 15Ω—£3.40.
 Please add 20p p. & p. to all speakers.

BONDED ACRYLIC FIBRE

B.A.F. wadding, 18in wide, 1in thick. The
 ideal lining for speaker enclosures. 25p per
 yard.


PLUGS

Car aerial 14p
 Co-axial 9p
 D.I.N. 2 pin (speaker) 10p
 D.I.N. 3 pin 13p
 D.I.N. 4 pin 14p
 D.I.N. 5 pin, 180 13p
 D.I.N. 5 pin, 240 15p
 D.I.N. 6 pin 13p

Jack, 2 1/2mm unscreened 9p
 Jack, 2 1/2mm screened 10p
 Jack, 3 1/2mm unscreened 8p
 Jack, 3 1/2mm screened 12p
 Jack, 3 1/2mm unscreened 20p
 Jack, 3 1/2mm screened 20p
 Jack, stereo, unscreened 25p
 Jack, stereo, screened 25p
 Phono, plastic top 5p
 Phono, plated metal 12p
 Phono, fitted 4 ft lead 8p
 Wander, red or black 3p
 Banana 4mm, red or black 6p

LINE SOCKETS

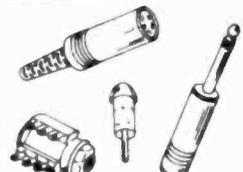Car aerial 14p
 Co-axial 9p
 D.I.N. 2 pin (speaker) 15p
 D.I.N. 3 pin 18p
 D.I.N. 5 pin, 180 16p
 D.I.N. 5 pin, 240 16p
 Jack, 3 1/2mm 15p
 Jack, 3 1/2mm screened 49p
 Jack, stereo, screened 30p
 Phono, plated metal 14p



SOCKETS

Car aerial 8p
 Co-axial, surface 8p
 Co-axial, flush 9p
 D.I.N. 2 pin (speaker) 10p
 D.I.N. 3 pin 9p
 D.I.N. 5 pin, 180 9p
 D.I.N. 5 pin, 240 9p
 Jack, 2 1/2mm 10p
 Jack, 3 1/2mm 10p
 Jack, 3 1/2mm unscreened 15p
 Jack, 3 1/2mm switched 17p
 Jack, stereo, switched 24p
 Phono, single 5p
 Phono, 2 on a strip 7p
 Phono, 3 on a strip 9p
 Phono, 4 on a strip 10p
 Wander, single, red or black 5p
 Wander, twin strip 7p
 Banana 4mm red, or black 6p

CAPACITORS

| | | | | | | | |
|----------|--------|-------|-----|----------|--------|-------|---------|
| 2.2pF | 500V | S/M | 7p | 0.0027μF | 500V | S/M | 15p |
| 3.3pF | 500V | S/M | 7p | 0.0033μF | 500V | Cer. | 3p |
| 5pF | 500V | S/M | 7p | 0.0033μF | 125V | P.S. | 6p |
| 10pF | 125V | P.S. | 5p | 0.0033μF | 1,000V | MDC | 6p |
| 10pF | 500V | S/M | 7p | 0.0036μF | 500V | S/M | 15p |
| 15pF | 125V | P.S. | 5p | 0.0047μF | 125V | P.S. | 9p |
| 15pF | 500V | Cer. | 4p | 0.0047μF | 500V | Poly. | 6p |
| 18pF | 500V | S/M | 7p | 0.0047μF | 500V | S/M | 20p |
| 22pF | 125V | P.S. | 5p | 0.0047μF | 1,000V | MDC | 6p |
| 22pF | 500V | S/M | 7p | 0.0051μF | 500V | Mylar | 3p |
| 25pF | 500V | S/M | 7p | 0.0051μF | 100V | Cer. | 5p |
| 27pF | 500V | Cer. | 4p | 0.0068μF | 125V | P.S. | 10 1/2p |
| 33pF | 125V | P.S. | 5p | 0.0068μF | 500V | S/M | 30p |
| 33pF | 500V | S/M | 7p | 0.0068μF | 500V | Poly. | 6p |
| 39pF | 500V | S/M | 7p | 0.0082μF | 125V | P.S. | 10 1/2p |
| 47pF | 125V | P.S. | 5p | 0.0082μF | 500V | M.F. | 3p |
| 47pF | 500V | Cer. | 4p | 0.011μF | 18V | Disc | 4p |
| 50pF | 500V | S/M | 7p | 0.011μF | 125V | P.S. | 10 1/2p |
| 56pF | 500V | S/M | 7p | 0.011μF | 160V | Poly. | 4p |
| 68pF | 125V | P.S. | 5p | 0.011μF | 250V | M.F. | 3p |
| 68pF | 500V | S/M | 7p | 0.011μF | 400V | Poly. | 3p |
| 75pF | 500V | S/M | 7p | 0.011μF | 500V | Cer. | 5p |
| 82pF | 500V | S/M | 7p | 0.011μF | 12V | Disc | 3p |
| 100pF | 125V | P.S. | 5p | 0.011μF | 600V | MDC | 7p |
| 100pF | 500V | S/M | 7p | 0.015μF | 1,000V | MDC | 9p |
| 100pF | 500V | Cer. | 5p | 0.015μF | 400V | Poly. | 3p |
| 120pF | 500V | S/M | 7p | 0.022μF | 100V | Mylar | 3p |
| 150pF | 125V | P.S. | 5p | 0.022μF | 18V | Disc | 3p |
| 150pF | 500V | S/M | 7p | 0.022μF | 400V | Poly. | 3p |
| 150pF | 500V | Cer. | 5p | 0.022μF | 600V | M.F. | 3p |
| 180pF | 500V | S/M | 7p | 0.022μF | 600V | MDC | 7p |
| 200pF | 500V | S/M | 7p | 0.022μF | 1,000V | MDC | 9p |
| 220pF | 125V | P.S. | 5p | 0.033μF | 250V | M.F. | 4p |
| 220pF | 500V | Cer. | 5p | 0.033μF | 400V | Poly. | 4p |
| 250pF | 500V | S/M | 8p | 0.047μF | 12V | Disc | 6p |
| 270pF | 500V | Cer. | 5p | 0.047μF | 160V | Poly. | 3p |
| 300pF | 500V | S/M | 8p | 0.047μF | 250V | M.F. | 3p |
| 330pF | 125V | P.S. | 5p | 0.047μF | 400V | Poly. | 4p |
| 330pF | 500V | S/M | 8p | 0.047μF | 600V | MDC | 8p |
| 390pF | 500V | S/M | 8p | 0.047μF | 1,000V | MDC | 10p |
| 470pF | 125V | P.S. | 5p | 0.1μF | 30V | Disc | 6p |
| 470pF | 750V | Disc | 5p | 0.1μF | 250V | M.F. | 4p |
| 500pF | 500V | S/M | 8p | 0.1μF | 400V | Poly. | 5p |
| 560pF | 500V | S/M | 8p | 0.1μF | 600V | MDC | 10p |
| 680pF | 125V | P.S. | 6p | 0.1μF | 1,000V | MDC | 13p |
| 680pF | 500V | S/M | 8p | 0.15μF | 250V | M.F. | 5p |
| 820pF | 500V | S/M | 8p | 0.22μF | 160V | Poly. | 6p |
| 0.001μF | 100V | Mylar | 3p | 0.22μF | 250V | M.F. | 5p |
| 0.001μF | 125V | P.S. | 6p | 0.22μF | 400V | Foil | 10p |
| 0.001μF | 400V | P.S. | 6p | 0.22μF | 1,000V | MDC | 15p |
| 0.001μF | 500V | S/M | 10p | 0.33μF | 250V | M.F. | 8p |
| 0.001μF | 500V | Cer. | 5p | 0.47μF | 250V | Foil | 8p |
| 0.0015μF | 1,000V | MDC | 6p | 0.47μF | 400V | Foil | 15p |
| 0.0015μF | 400V | Poly | 3p | 0.47μF | 1,000V | MDC | 20p |
| 0.0018μF | 500V | S/M | 10p | 1.0μF | 2 | | |

£25

takes the wraps off

UNISOUND a new concept in stereo



See below for address.

The whole system is complete including superb cabinets in simulated teak—just simply screw together the components and you save pounds! Amplifier is based on the famous Mullard Unilex system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13" x 8" EMI twin cone speakers ready for mounting in their elegant cabinets which simply need screwing & gluing together.

Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound.


£25 complete plus £2.80 p. & p.

Diamond Stylus £1.25 extra
Power output: 4 watts per channel into 8 ohms
Input: 120 mV (for ceramic cartridge). Stereo Headphones with adapter £4



UNISOUND MODULES ONLY-£6.95

If you prefer, you can buy the three modules—pre-amplifier, power supply/dual power amplifier, and control panel—by themselves for only £6.95. P. & P. 50p extra. Their overall specification is the same as shown for the complete Unisound console using the highly efficient I.C. monolithic power chips to ensure very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum.

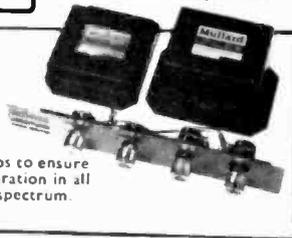

THE TOURIST PB PUSH BUTTON CAR RADIO KIT

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components, this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

Fully retractable, lockable car aerial £1.25 post paid

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. Four push-buttons for medium wave, one for long wave. It is permeability tuned

PRICE ONLY
£7.00 + p&p 50p

THE TOURIST PB CAN BE MOUNTED IN ANY STANDARD SIZE DASH PANEL AND IT HAS AN ILLUMINATED TUNING SCALE FOR EASY READING AT NIGHT. CHASSIS SIZE IS: 7" WIDE, 2" HIGH AND 4 1/8" DEEP (EXCLUDING FRONT PANEL, ETC.)

8 ohm speaker with baffle and fixing strips: £1.50 + p & p 25p post free if brought with the kit

* Car aerial £1.25 p.p.



ONLY
£7.00

and sturdily constructed. Output is a full 2.5 watts into an 8 ohm speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms. Power consumption is less than 1 amp.

* Circuit diagram and comprehensive instructions 50p, free with parts.

Radio & TV Components (Acton) Ltd.
21E High Street, Acton, London W3 6NG.
323 Edgware Road, London W2.

If you can solder on printed circuit board, you can build this push-button car radio kit.

It's simple—just follow the step-by-step instructions



Mail Orders to Acton. Terms C.W.O. All enquiries S.A.E. Goods not despatched outside U.K.

JUST ARRIVED! THIS YEAR'S NEW *RUSSIAN MIRACLE! COMPUTERISED?

BRAND NEW SPACE AGE model SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!

THE FABULOUS ASTRAD 17

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS STATIONS FROM THE FOUR CORNERS OF THE EARTH!

PORTABLE RADIO & COMMUNICATIONS RECEIVER

28 TRANSISTORS AND DIODES! WAVEBANDS: STANDARD LONG and MEDIUM Plus 5 SHORT WAVEBANDS Plus ULTRA SHORT WAVES (V.H.F. AM, FM, MW, LW, USW.)

***COMPARE ITS PERFORMANCE with £80 RADIOS!**

***NOW AVAILABLE WITH fabulOUS "COMPUTERISED" WORLD TUNING GUIDE! NO MORE GUESSWORK - INSTANT DATA at your fingertips - enables you to TUNE IN A FLASH to transmissions the world over!**

***MAGIC EYE" tuning level indicator**

£20.75 BOX POST ETC. 50p

MAINS/BATTERY ELIMINATOR £1.48 extra

Think of the year 1984 and what might be produced then—now get the fantastic ASTRAD 17 and see for yourself that the Russians have done it all NOW! This ONE SUPERSEDES ALL EARLIER MODELS! It will probably make your present radio seem like a 'crystal set'! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a fraction of today's Russian price! Compare performance with £80 radios! Test 7 days—refund instantly if not satisfied. Black and Chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures sweeter tone than ever! Volume controlled from a whisper to a roar. Wider bandwidth, for "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in space-age and satellite communications. Yes, EVERY WAVEBAND instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the Earth, including all normal transmissions, VHF, AM, FM, MW, LW, USW, plus local and new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER side control waveband selection unit (as used on expensive TV's!) Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output ON/OFF volume and separate Treble and Bass tone controls for better perfection of reproduction and tone! Press-button Illumination Takes it where—runs on batteries (obtainable everywhere) or through battery eliminator from 220/240v. AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins. approx. It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE 14ins. x 10 1/2ins. x 4 1/2ins. overall approx. Magnificently made to give years of perfect service. U.K. service facilities and spares available for years to come, if necessary! With ATTEN' GTEE, manual with simple operating instructions and circuit diagram. ONLY £20.75 (with main/battery eliminator £1.48 extra). BOX, POST, ETC., 50p. *BUT WAIT, for only 50p extra you get the sensational "COMPUTERISED" WORLD TUNING GUIDE. (It enables you to time, pinpoint and get transmissions the whole world over—even a child can do it!—It even lets you know when to tune into the U.K. when abroad. NO GUESSING! NO MESSING! PLUS Standard "long-life" batteries. PLUS ultra sensitive earphone for personal listening. (Sorry—We cannot change these for any earlier model purchased.)

FANTASTIC! Brand new from Eastern Europe—Incredible 2-in-1 Radio!

First class makers—because of our crazy price contract stipulates we must NOT mention name! Beautifully made 9"x5"x2 1/2", overall approx. Every up-to-date technological improvement! /15 SEMI-CONDUCTORS: 9 Transistors, 5 Diodes and Stabiliser! FOUR WAVEBANDS! Yes, VHF model with AM/FM Long and short Wavebands! Gets stations around world incl. Standard Long, Medium & Short Wave, also local and new stations not yet operational! Internal ferrite aerial plus 26 inch swivel telescopic aerial. On / off / volume and Tone Controls. Clear station Selector Dial! Waveband selector! Equally wonderful in CAR or HOME! TWO TUNING Dials for flat or upright use as illustrated. RUNS OFF 12 VOLT BATTERY! (AS A PORTABLE it runs on standard batteries). PLUG IN 12 VOLT ADAPTOR JACK PROVIDED and automatically cut out internal batteries, using car battery only! Miraculous! Span oceans! Hundreds of transmissions day and night including short wave—even in car! BUT WAIT simply remove radio from car, "snap on" optional carry handle AND YOU HAVE A DELUXE PORTABLE with additional upright tuning dial. WRITTEN G'TEE. Only £19.95, post 45p. *Sprung off metal matching detachable carry handle (as illus.) AND set of batteries 25p ex. if reqd. Test 7 days—refund if not delighted.

SHOPERTUNITIES LTD. Dept. EE/12, 164 UXBRIDGE RD. (facing Shepherd's Bush Green), LONDON, W12 8AQ (Thurs. 1, Fri. 7). Also: 33 High Holborn, London, WC1 (Thurs. 7). Both stores open Mon. to Sat. 9 a.m.—6 p.m.

DISCOUNTS UP TO 60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

SPECIAL OFFER £17.75

Garrard SP25 Mk. III
Goldring G800
Teak plinth and tinted cover. All leads supplied.
Please add £1.25 for P. & P.

TUNERS

Please add 75p P. & P.

| | |
|------------------------------------|--------|
| Amstrad Multiplex 3000 | £27.95 |
| Armstrong 523 | £39.50 |
| Armstrong 524 | £30.95 |
| Rogers Ravensbrook FET4 (Chassis) | £31.00 |
| Rogers Ravensbrook FET4 (Cased) | £35.00 |
| Rogers Ravensbourne FET4 (Chassis) | £43.00 |
| Rogers Ravensbourne FET4 (Cased) | £48.00 |
| Sinclair PRO60 (Module) | £16.50 |
| Sinclair 2000/3000 Tuner | £31.95 |
| Philips RH690 | £33.00 |
| Leak Delta FM (Cased) | £54.75 |
| Leak Delta AM/FM (Cased) | £64.50 |
| Alpha Highgate FT 150 | £34.95 |

TURNTABLE

Please add 75p for P. & P.

| | |
|---------------------------|--------|
| Garrard SP25 Mk. III | £10.25 |
| Garrard AP76 | £17.75 |
| Garrard SL65B | £12.65 |
| Garrard 401 | £26.00 |
| Garrard Zero 100 (Auto) | £38.75 |
| Garrard Zero 100 (Single) | £36.95 |
| Garrard SL72B | £30.95 |
| Garrard SL75B | £25.50 |
| Garrard SL95B | £34.25 |
| BSR MP60 | £9.45 |
| Goldring GL72 | £22.00 |
| Goldring GL72/P | £28.75 |
| Goldring GL72/P | £27.50 |
| Goldring 101 PC | £22.00 |
| Wharfedale Linton & cart. | £27.95 |
| Thorens TD125 | £57.50 |
| Thorens TD125AB | £92.00 |
| Thorens TD150 Mk. II | £27.50 |
| Thorens TD150A Mk. II | £33.50 |

AMPLIFIERS

Please add 75p P. & P.

| | |
|----------------------------------|--------|
| Amstrad 8000 Mk. II | £16.25 |
| Amstrad IC2000 | £27.50 |
| Amstrad Integra 40000 | £21.95 |
| Armstrong 521 (teak cased) | £43.95 |
| Alpha Highgate 212 | £24.95 |
| Alpha Highgate FA300 | £30.95 |
| Alpha Highgate FA400 | £31.95 |
| Leak Delta 30 | £47.65 |
| Leak Delta 70 | £55.95 |
| Metrosound ST20E | £24.45 |
| Metrosound ST60 | £45.95 |
| Pioneer SA600 | £58.00 |
| Pioneer SA700 | £66.50 |
| Pioneer SA800 | £73.95 |
| Pioneer SA900 | £92.00 |
| Pioneer SA1000 | £94.00 |
| Rogers R/brook (Chassis) | £35.00 |
| Rogers R/brook (Cased) | £37.00 |
| Rogers R/bourne (Chassis) | £41.95 |
| Rogers R/bourne (Cased) | £47.50 |
| Sinclair PRO60 2 x Z30/PZ5 | £14.95 |
| Sinclair PRO60 2 x Z30/PZ6 | £17.00 |
| Sinclair PRO60 2 x Z50/PZ8/Trans | £21.50 |
| Sinclair AFU (Filter Unit) | £21.50 |
| Sinclair 605 | £18.50 |
| Sinclair 2000 Mk. II | £21.50 |
| Sinclair 3000 Mk. II | £29.50 |
| Wharfedale Linton | £37.50 |
| Goodmans Max Amp | £37.95 |
| Teleton SAQ206B | £20.50 |
| Teleton SAQ307 | £22.50 |
| Rotel RA210 | £24.50 |
| Rotel RA 310 | £31.00 |
| Rotel RA 610 | £48.50 |

TUNER/AMPLIFIERS

Please add 75p for P. & P.

| | |
|----------------------------------|---------|
| Alpha Highgate 150 | £44.25 |
| Armstrong 525 (Teak cased) | £67.95 |
| Armstrong 526 AM/FM (Teak cased) | £77.75 |
| Leak Delta 75 | £124.75 |
| Philips RH781 | £50.00 |
| Philips RH702 | £82.50 |
| Teleton 2100 | £29.95 |
| Goodmans One Ten | £99.50 |
| Rogers R/brook (Teak) | £78.50 |
| Rogers R/brook (Chassis) | £72.75 |
| Alpha FR 3000 | £66.00 |

SPEAKERS

Please add £1.25 P. & P. per pair

| | |
|---------------------------|--------|
| Amstrad I38 | £15.95 |
| Wharfedale Denton 2 | £28.30 |
| Wharfedale Linton 2 | £35.90 |
| Wharfedale Melton 2 | £47.50 |
| Wharfedale Dovedale 3 | £39.50 |
| Celestion Ditton 120 | £37.45 |
| Celestion Ditton 15 | £52.00 |
| Celestion Ditton 25 | £87.00 |
| Celestion County New Prod | £55.95 |
| Goodmans Double Maxim | £48.25 |
| Goodmans Mezzo 3 | £44.95 |
| Goodmans Magister | £74.00 |
| Sinclair Q16 | £12.50 |

£3.30*

Plus 35p p. & p.
Finished in teak veneer with tinted dust cover fully assembled. For Garrard SP25, 2025TC, 3000, AT60, 2000, 2500, 3500, 5100, 1025, SL65B. Also for BSR McDonald MP60 and others. For AP76, AP75, SL72B, SL75; SL95B; £4.30 plus 35p P. & P. Also finished in walnut to match Japanese equipment—at no extra.

CARTRIDGES

Please add 10p for P. & P.

| | |
|-----------------------|--------|
| Goldring G850 | £3.25 |
| Goldring G800 | £3.75 |
| Goldring G800E | £8.50 |
| Goldring G800 Super E | £14.35 |
| Shure M3D | £3.85 |
| Shure M446 | £3.65 |
| Shure M55E | £5.85 |
| Shure M75E Type 2 | £10.35 |
| Sonotone 9TAHC | £1.75 |

GLOBAL AUDIO DISCOUNT WAREHOUSES

All prices correct at time of press E. & O.E.

Dept. (EE11) 174 Pentenville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.


MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

Why take the risk?

of damage to expensive transistors and integrated circuits, when soldering?

Use Antex low-leakage soldering irons

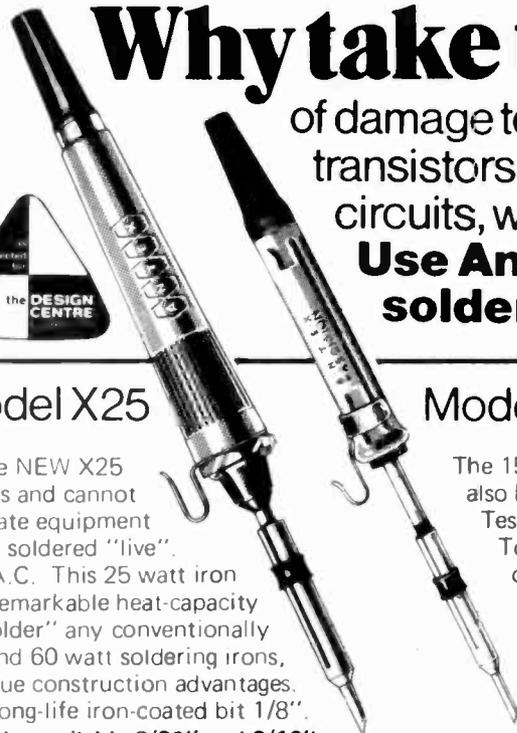

220-240 Volts or
100-120 Volts

Model X25

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".

Tested at 1500v. A.C. This 25 watt iron with it's truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8".
2 other bits available 3/32" and 3/16".

Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be removed

PRICE: £1.75 (rec. retail)
Suitable for production work and as a general purpose iron

Model CCN 220 volts or 240 volts

The 15 watt miniature model CCN. also has negligible leakage.

Test voltage 4000v. A.C.

Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"

4 other bits available
1/8", 3/16" 1/4" and 1/16"

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8"

PRICE: £1.95 (rec. retail)

A SELECTION OF OTHER SOLDERING EQUIPMENT.



MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 1/16" to 3/16". Voltages 240, 220, 110, 50 or 24
PRICE: £1.70 (rec. retail)

MODEL CN2


Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.
PRICE: £1.70 (rec. retail)



MODEL G

18 Watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.
PRICE: £1.83 (rec. retail)

MODEL SK.1 KIT

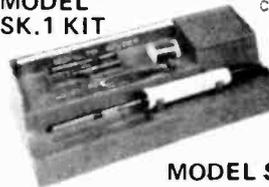

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £2.75
(Rec. retail)

MODEL SK.2 KIT

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32"

heat sink, solder and booklet "How to Solder"

PRICE £2.40
(Rec. retail)



MODEL MES. KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder."

PRICE £1.95
(Rec. retail)



From radio or electrical dealers,
car accessory shops or,
in case of difficulty direct from:-
ANTEX LTD. FREEPOST
(no stamp required) **Plymouth**
PL1 1BR Tel: 0752 67377


- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash
(Giro No. 2581000)

NAME _____

ADDRESS _____

EE10

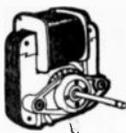

MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Selp at 65p. Postage 20p for first one then 10p for each one ordered.



MULLARD 4+4 STEREO AMPLIFIER

We demonstrate these daily and almost always a sale results; it really is a cracking amplifier. Only Mullard with their know how could have made it possible at this low price. SPEC: Mains operated. 4 watts music or speech per channel. Double wired power supply eliminates cross talk. Harmonic distortion less than 2%. Frequency response 50Hz-16KHz. Input suitable for pick up tuner or microphone. 6 months guarantee. Only 28-95p + 30p postage and insurance. Teak finished case 22-45

POCKET CIRCUIT TESTER

Test continuity of any low resistance circuit, home wiring, car electric. Tests polarity of diodes and rectifiers. Also ideal size for overconclusion to signal injector (circuit supplied). 30p or 2 for 60p post paid.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—3 pole, 4 way—3 pole, 4 way—3 pole 6 way—1 pole, 13 way. All at 80p each 1-80 for ten, your assortment.

COMPUTER TAPE

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in. wide 11-90 plus 35p post and insurance, with cassette, 1 in. wide 11-90 plus 30p post and insurance with cassette. 1in. wide 85p plus 25p post and insurance with cassette. Spare spools and cassettes—110 75p, 1in. 75p each plus 30p post and insurance.



TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover's and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 11W element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 22-50, 3kW Model as above except 2 kilowatts 22-60. Don't miss this. Control Switch 85p. P. & P. 40p.



SPARTAN Portable RADIO


£1-99 Only. Six transistor medium wave pocket loud-speaker radio. Loud and with good tone will make wonderful Christmas present. Buy while stocks last. Full money back guarantee.



RENITONE med. wave 7 transistors £1-95

ELECTRIC CLOCK WITH 20AMP. SWITCH

These units are as fitted to many top range medium wave cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another time or alarm—this may be set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price. 22-50, less than the value of the clock alone—post and ins. 18p.

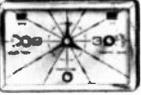

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 8 revs per min. Some of the many uses of this timer are Machine control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price 22-75 plus 25p post and insurance. Don't miss this terrific bargain.



THIS MONTH'S SNIP

TIMEAC 24 hour 15 amp Clock Switch. Self-contained unit for flex connection to the mains. Clock switches 2 on/off's per 24 hours Operates a 15 amp switch. All neatly made up in an ivory moulded case with outlet socket. The only snag is outlet socket is continental type. Plugs available in this country or put a connector strip in place of output socket. Overall size approx. 4 x 2 1/2 x 3 and the clock has a clear perspex cover which is easily removable for reprogramming. 22-75p



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 60p post free.

RESETTABLE FUSE

How long does it take you to reset a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Priced only £1 each or £11 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.



THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price 22-85, plus 30p post and insurance.



FLOURESCENT CONTROL KIT

Each kit comprises seven items—Choke, 2 tube ends, starter, holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-stent, mostly resin filled. Kit A—15-20 w. £1. Kit B—20-40 w. £1. Kit C—40-60 w. £1-30. Kit D—60-80 w. £1-50. Kit E—80-100 w. £1-75. Kit MF1 is for 6in., 9in. and 12in. miniature tubes £1. Kit MF3 for 21in. 13 w. miniature tube £1. Postage on Kits A and B 25p for one or two kits then 25p for each two kits ordered. Kit C, D and E 25p on first kit then 15p for each kit ordered. Kit F 25p then 25p for each kit ordered. Kit MF1 15p on first kit then 15p on each two kits ordered.

DOOR INTERCOM

Know who is calling and speak to them without leaving bed or chair. Output comprises microphone with call push button, connectors and master intercom. Simply plug together. Originally sold at £10. Special snip price 22-50 plus 30p postage.



SOLDER GUN

A must for every busy man, gives almost instant heat also illuminated job. 100 watt 22-85 plus post and ins. 20p. BIG JOB 250 watt model 24-75 plus post and ins. 40p.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 85p, plus 20p postage.

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1183 800m watt power output 75p. Model 1172 750m watt power output 85p. Model 1170 600m watt power output 85p. 10% discount if 10 or more ordered.

IMMERSION HEATERS BY REMPLOY

Standard fitting for domestic water tanks. Made by the famous Remploy Company. Complete with sealing washers suitable for 200-240 volts A.C. Depth into tank 11". 24 kw or 3 kw. 22 plus 40p each post and insurance.




TAPE POWER SUPPLY · ELECTRONIC MOUSE TRAP · REACTOMATIC

To receive components for these projects send the quoted approx. price. Any cash difference will be made up.

13 AMP TWIN GANG SOCKETS

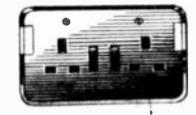Offered at less than wholesale price your opportunity to replace those dangerous adaptor—brown bakelite knob mounting—standard fitted. Unswitched 20p each, separately switched 30p each. Separately switched and with neon on/off indicators 45p each. Less 10% ten or more + 20p postage if order under



Where postage is not stated then orders over 25 are post free. Below 25 add 50p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

AMPLIFIER IN CASE WITH SPEAKER

Marketed by British Relay under the name Luxistor. This is in a very neat looking cabinet and is ideal around the home or in the workshop for trouble shooting or for testing out a quick lash up. Size approx. 9 1/2" x 6 1/2" x 3 1/2" deep. Input is via a matching transformer and volume control and amplifier may be powered by an internal 9v battery or an external 110v source. Speaker is an R-A elliptical 6" x 3 1/2" 10,000 Gauss. The amplifier proper is a Newmarket model ref. P.C.4. Price 22-50 each, 10 for 221-60. Post and insurance 20p.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs. etc. Price 45p each.



TELEPHONES

Complete as illustrated. Save your legs, time and temper, simply by putting in some telephones. E.R. G.P.O. not new but guaranteed in good condition and serviceable. Supplied with diagram and instructions showing how to connect. Price 75p each + 50p post or 2 for £2 post paid. Also available separately, dials and handsets 60p each + 20p post.



ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1" 6p each, 10 for 64p.

SLIDE SWITCHES

Slide Switch. 2-pole changeover panel mounting by two 6B.A. screws. Size approx. 1in x 1in rated 250V lamp. 6p each. 10 for 64p, 100 for 25-10, 500 for 224. Ditto as above but for printed circuit 6p each 10 for 64p, 100 for 2425. Sub Miniature Slide Switch. DPDT 19mm (1in approx.) between fixing centres. 18p. each or 10 for 21-06. SP Change over spring return 250v 1 amp. 10p.



EDUCATIONAL KITS—all with pictorial instructions

THIS BALANCE KIT FREE. Facile educational kits. Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 40p each post paid. Special price for all 8 kits 22-00 with free balance kit.

- KA2 Lens Kit. Eleven parts, including candle, one concave lens, one convex lens, stage and frame, etc. Watch light rays bend as they pass through different lenses.
- KA3 Water Pump Kit. Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working. Three types of pump may be made: lift pump, Force Pump and Force Pump with reservoir and nozzle.
- KA4 Buzzer Kit. Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer.
- KA5 8-Pole Motor Kit. Twenty-four parts including enamel wire, armature and pole pieces, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor.
- KA7 Electro-Magnet Kit. Fifteen parts, includes compass. Make two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.
- KA8 Current and Resistance Kit. Twenty-nine parts, including bench and light bulb. Conduct interesting and educational projects to learn the application of "OHMS LAW" and see the difference in current and resistance with different types and lengths of wire.
- KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.
- KA10 Morse Key buzzer and bell kit. 25 part kit easy to construct, simple to operate.

J. BULL (ELECTRICAL) LTD.

(Dept. E.E.) 7 Park Street, Croydon CRO 1YD
Callers to: 162/3 Tamworth Road, CROYDON

Everyday Electronics, October 1972

BI-PRE-PAK

COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH



TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 50p

POST & PACKING 15p

TESTED AND GUARANTEED PAKS

| | | | |
|-----|-----|--|-----|
| B3 | 4 | Photo Cells, Sun Batteries. 0-3 to 0-5V. 0-5 to 2mA. | 50p |
| B79 | 4 | IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic | 50p |
| B81 | 10 | Reed Switches, mixed types large and small | 50p |
| B99 | 200 | Mixed Capacitors. Approx. quantity, counted by weight | 50p |
| H4 | 250 | Mixed Resistors. Approx. quantity counted by weight | 50p |
| H7 | 40 | Wirewound Resistors. Mixed types and values. | 50p |
| H8 | 4 | BY127 Sil. Recs. 1000 PIV. 1 amp. plastic | 50p |
| H9 | 2 | OC771 Light Sensitive Photo Transistor | 50p |
| H12 | 50 | NKT155/259 Germ. diodes, brand new stock clearance | 50p |
| H28 | 20 | OC200/12/3 PNP Silicon uncodded TO-5 can | 50p |
| H30 | 20 | 1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V. | 50p |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked. | 50p |
| H38 | 30 | Short lead Transistors, NPN Silicon Planar types. | 50p |

UNMARKED UNTESTED PAKS

| | | | |
|-----|-----|--|-----|
| B66 | 150 | Germanium Diodes Min. glass type | 50p |
| B83 | 200 | Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ. | 50p |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202 | 50p |
| B86 | 50 | Sil. Diodes sub. min. IN914 and IN916 types | 50p |
| B88 | 50 | Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc. | 50p |
| B1 | 50 | Germanium Transistors PNP, AF and RF | 50p |
| H6 | 40 | 250mW, Zener Diodes DO-7 Min. Glass Type | 50p |
| H17 | 20 | 3 amp. Silicon Stud Rectifiers, mixed volts | 50p |
| H15 | 30 | Top Hat Silicon Rectifiers. 750mA. Mixed volts | 50p |
| H16 | 8 | Experimenters' Pak of Integrated Circuits. Data supplied | 50p |
| H20 | 20 | BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts. | 50p |
| H34 | 15 | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can. | 50p |

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

| 4p | | 6p | |
|--------|------|-------------------|------|
| AC107 | 0-15 | OC139 | 0-13 |
| AC126 | 0-15 | OC140 | 0-15 |
| AC127 | 0-17 | OC170 | 0-23 |
| AC128 | 0-15 | OC171 | 0-23 |
| AC176 | 0-20 | OC200 | 0-25 |
| AC177 | 0-20 | OC201 | 0-25 |
| AF239 | 0-30 | 2N1302-3 | 0-15 |
| AF186 | 0-20 | 2N1304-5 | 0-17 |
| AF139 | 0-30 | 2N1306-7 | 0-20 |
| BC154 | 0-20 | 2N1308-9 | 0-22 |
| BC107 | 0-10 | 2N3819FET | 0-30 |
| BC108 | 0-10 | 2N4416FET | 0-35 |
| BC109 | 0-10 | Power Transistors | 0-40 |
| BC148 | 0-12 | OC20 | 0-10 |
| BC169 | 0-15 | OC23 | 0-25 |
| BF194 | 0-15 | OC23 | 0-25 |
| BF274 | 0-20 | OC25 | 0-25 |
| BFY50 | 0-15 | OC26 | 0-25 |
| BSY25 | 0-13 | OC28 | 0-30 |
| BSY26 | 0-13 | OC35 | 0-25 |
| BSY27 | 0-13 | OC36 | 0-37 |
| BSY28 | 0-13 | AD149 | 0-35 |
| BSY29 | 0-13 | AU110 | 1-75 |
| BSY95A | 0-10 | 25034 | 0-25 |
| OC41 | 0-15 | 2N3055 | 0-40 |
| OC44 | 0-13 | Diodes | |
| OC45 | 0-10 | AAY42 | 0-10 |
| OC71 | 0-10 | OA95 | 0-07 |
| OC72 | 0-10 | OA79 | 0-07 |
| OC81 | 0-13 | OA81 | 0-07 |
| OC81C | 0-13 | OA95 | 0-07 |
| OC83 | 0-18 | IN914 | 0-06 |

F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+20p each.



A CROSS HATCH GENERATOR FOR £3.50!!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Oots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

8 RELAYS FOR VARIOUS TYPES £1

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each post and packing 23p.

| Quantity | 1-10 | 10-50 | 50+ |
|---|------|-------|-----|
| 8B105 Varicap Diodes | 10p | 8p | 6p |
| OC71 or 72 Fully Tested Unmarked | 5p | 5p | 4p |
| Matched Sets 1-OC44 and 2-OC45's, Per Set. | 25p | 20p | 15p |
| OA47 Gold-Bonded Diodes, Marked and Tested | 3p | 3p | 2p |
| 1-watt Zener Diodes 7.5, 24, 27, 30, 36, 43 Volts | 5p | 4p | 3p |
| 10-watt Zener Diodes 5-1 8-2, 11, 13, 16, 24, 100 Volts | 20p | 17p | 15p |
| Micro Switches, S/P, C/O | 25p | 20p | 15p |
| 1-amp Bridge Rec's 25-volt | 25p | 22p | 20p |

INTEGRATED CIRCUITS

| | | | |
|---|------|------|------|
| SL403D Audio Amp, 3-Watts | 1-50 | 1-37 | 1-32 |
| 709C Linear Op. Amp. | 25p | 20p | 15p |
| Gates, Factory Marked and Tested by A.E.I. | 10p | 9p | 8p |
| J. K. Flip-Flops Factory, Marked and Tested by A.E.I. | 20p | 18p | 15p |
| SN7490 Decade Counter | 65p | 60p | 55p |
| UL914 Dual 1/2 Gate | 40p | 35p | 30p |

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines: **B.P.1 Transistor Equivalents and Substitutes;** 40p

This includes many thousands of British U.S.A., European and C.V. equivalents. Postage and Packing 21p.

The Iliife Radio Valve & Transistor Data Book 9th Edition; 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DE
TELEPHONE: SOUTHEND (0702) 46344

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N-9 803 1685



**S. G. BROWN
"DIPLOMAT"
MONO/STEREO
HEADSET**
Finest quality British made Light-weight Headphones. Incorporate ceramic piezo electric transducers.
Specification:—
Frequency—20-17,500 CPB.
Impedance—Predominantly capacitive, at .001MFD per earpiece can be regarded as 150K at 1kcs.
Weight—3.5oz. (98 grams).
A Bargain at **£2-50p** each set. Please include 10p per set P.F.



**"CRESCENT"
DIGITAL
CLOCK KIT**
24 Hour Nixie Digital Clock Kit We Supply:
★ A complete set of components
★ A complete set of easy to follow instructions
★ Printed circuits made to make construction as simple as possible
★ A cabinet and front panel to give a professional finish.
All for the price of the components. **£22.50 + 50p P. & P.** Please send S.A.E. for more information.



TRI-VOLT BATTERY ELIMINATOR
Enables you to work your transistor radio, amplifier, or cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug you can select the voltage you require—6v, 7½v or 9 volts. This means all your transistor power pack applications can be handled by this one unit.
Approx. size: 2½" x 2½" x 3½". OUR PRICE—**£2-75p + 10p P. & P.** Same model suitably wired for the Philips Cassette—**£3-00 + 10p P. & P.**



TRI-VOLT CAR CONVERTER
Enables you to work your Transistor Radio, Amplifier or Cassette etc. from the 12 volt car supply positive or neg. earth.
This converter supplies 6, 7½ or 9 volts and is transistor regulated. Approx. size 2½" x 3½" x 2". Very easy to fit and a real money saving device for **£2-50 + 10p P. & P.**



WAFER SWITCHES
1 pole 12 way
2 pole 2 way
2 pole 3 way
2 pole 4 way
2 pole 5 way
3 pole 4 way
4 pole 3 way
18p each. Please inc. 5p P. & P. Up to 3 switches.

BRIDGE RECTIFIER
Plastic encapsulated. Texas Type No 1B40-K05 50v at 4 amp. Our Price 55p + 5p P. & P.

MINIATURE RELAY
6 volt 70 ohm. Single Pole Changeover. Approx. size—1½" x 1" x 1".
40p plus 5p P. & P.

ALUMINIUM CHASSIS
Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2½" depth.

| | | |
|------------|------------|---------------|
| 6 x 3—41p | 12 x 3—53p | 14 x 9—94p |
| 6 x 4—45p | 12 x 5—61p | 16 x 6—86p |
| 8 x 6—53p | 12 x 8—83p | 16 x 10—1.08p |
| 10 x 7—63p | 14 x 3—60p | |

Please send 10p per chassis P. & P.



HIGH QUALITY IMPORTED HEADPHONES
1,000 Ω per phone... **95p**
2,000 Ω per phone... **105p**
Plus 10p P. & P. per pair.

TTC G1105
£1-75 plus 13p P. & P.

EN3655 POPULAR POWER TRANSISTOR
Now at our Low Price **50p each**
Please include 5p P. & P.


PRINTED CIRCUIT KIT
Everything for producing your own printed circuits.
£1-40p plus 10p P. & P.

LOW VOLTAGE AMPLIFIER Few only at plus 13p P. & P.
5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.
With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.

LOUDSPEAKER BARGAINS
E.M.I. 450 set 3. 8. 15 ohm **£3-50 plus 38p P. & P.**
E.M.I. 350 set 8 ohm. **£7-00 plus 38p P. & P.**
MINI LOUDSPEAKERS
2½" (57mm) 8ohm — 50p each
2½" (57mm) 40ohm — 50p each
2½" (57mm) 80ohm — 50p each
Please include 5p P. & P. up to 3 Mini-Loudspeakers

BARGAIN S.C.B. TESTED THYRISTOR
400 volt. 3 amp. **45p each 5 for £2-00**
Please include 5p P. & P.

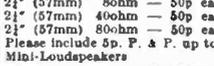PRINTED CIRCUIT BOARD
8 x 6—10p 10 x 6—15p
9 x 5—10p 12 x 12—30p
Please inc. 3p. per board P. & P.



EA1000 3 WATT AUDIO AMPLIFIER MODULE
An Audio Amplifier designed around the TAA621 Linear I.C.—
Supply Voltage ... 9-24V
Speaker Imp. ... 8-16 ohm
Frequency ... 60Hz-26k Hz
Overall Size ... 2½" x 3½" x 1½"
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at **£2-63** + 5p P. & P.

POTENTIOMETERS
All types 1" and less diameter. SINGLES DUAL
5K Log or 5K
10K Lin Less 10K
25K Switch 25K
50K Switch 50K
100K 12p ea, 100K Less
250K Double 250K 40p each
500K Pole 500K
1M Switch 1M
2M Pole 2M
24p ea.
Up to 3 Pots. Please add 5p P. & P.

MINIATURE RELAYS
Brand new range of British made Relays.
Size—1½" x 1" x 1"
All two changers with 250V. 1.5A contacts and suitable for fitting on 1mm Veroboard.
Type Volts Current Ohms.
27/A 12v 17mA 700 Ω
21/A 12v 28mA 430 Ω
12/A 6v 33mA 185 Ω
80p each.
Please include 5p P. & P up to 3 Relays.

The Pictorial Method

BASIC ELECTRICITY(5vols) ELECTRONICS(6vols) TELEVISION(3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.



The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

You have my firmest recommendation in favour of this method of Self Teaching.
B.W. Blackburn.
The best I have ever had: they are fantastic and everything your readers say.
P.L.W. Davenport.
I have made great use of the Basic Manuals.
B.C. Hendon.
I have found the Electronics volumes so interesting: please rush me Electricity.
C.A. Folkestone.

YOUR 100% GUARANTEE
Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....
BASIC ELECTRICITY 5 parts £4.50
BASIC ELECTRONICS 6 parts £5.40
BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.
YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS
FULL POSTAL.....
ADDRESS

POST NOW FOR THIS OFFER!

introducing

ARROW ELECTRONICS LTD.

an associate Company of LST ELECTRONIC COMPONENTS LTD.

'Service the way it ought to be'

When it comes to retail distribution we're head and shoulders above the rest!

We're a new Company but our experience and ability in electronic components goes back a long way...

Here at Arrow Electronics fast, reliable service is law!

We offer a rapid, same day turn round on all mail received up to 3 pm on any given weekday.

What's more, when we promise to clear all orders on receipt, we really mean it!

Our no fuss, no bother ordering system is a joy to behold. We'll give you all the forms and envelopes you could possibly need. Combine them with our simple Catalogue Coding and hey presto, you can order and order, time and time again without the slightest error or mistake.

You'll always be up to date with us—we're continually adding to our high quality stock range and we're always up-dating our catalogue.

Get to know us and you'll soon raise your hat to our customer discount—it's tops with a total order value discount of 10% on orders exceeding £4.00.

Now's your chance to get to know us better. Our brand new Catalogue is now awaiting you, hot from the presses.

NEW PRODUCTS

Products featured in the Arrow Electronics Mail Order Catalogue include the following—

- Extended ranges of Bridge Rectifiers, and Capacitors including Variable Capacitors.
- Low cost Integrated Circuit Mounting Pins.
- Instrument Knobs.
- Light Emitting Diodes.
- Magneto Resistors.
- Optically Coupled Isolators.
- Extended Range of Potentiometers.
- Medium current and High current Rectifiers.
- Temperature controlled Soldering irons.
- Extended Range of Thyristors.
- Many new types of Passive Components.
- Hardware and Accessories including tools, Chassis.
- Aluminium Boxes.
- An extended range of Opto Electronic Devices.
- A very wide range of new Semiconductors.
- Test Metals.

and many other items of great interest to the home constructor.

Arrow Electronics Limited
Dept EE1
7 Coptfold Road
Brentwood Essex
Tel: Brentwood 219435

NEW PRODUCT

The unique test instrument illustrated gives an instantly visible display of the Logic State of DIL Integrated circuits. The device automatically selects its power supply from the terminals of the IC's being inspected. Each Logic Checker is supplied complete with a set of clip-on Logic plates. For fuller details see the new Arrow catalogue.



NEW PRODUCT

Arrow are the first to offer the new double wound ring core chokes designed for RF interference suppression in Bi-Polar SCR and TRIAC circuits. The chokes are supplied as a kit including a Delta Capacitor. For details see the new catalogue.



**Shoot the
your
catalogue**

I enclose PO/Cheque for 10p
Name
Address
Arrow Electronics Limited
Dept EE1
7 Coptfold Road
Brentwood, Essex

everyday electronics

PROJECTS...
THEORY.....

THE GOAL

As a hobby, electronics offers the ordinary person opportunity for involvement at different levels. The mathematically-inclined applying themselves to the resolution of intricate points of circuit design from first principles, the experimenters seeking the same end but depending largely upon cut and try methods, and the constructors pure and simple relying entirely upon published designs—all of these derive enjoyment and satisfaction from their labours.

The initial approach to the subject may differ, but the final goal for all is the completion of some item of electronic equipment which will be a rewarding achievement in itself, as well as being a device of practical worth.

CONSTRUCTORS

EVERYDAY ELECTRONICS is chiefly concerned with the "constructors" (who should take no offence from the "pure and simple" definition given above!) and especially with those having little or no previous knowledge of electronics.

It is abundantly clear that there are thousands who have been fascinated by what they have read or heard concerning this all powerful, all embracing technology, and who have eagerly seized the opportunity provided by EVERYDAY ELECTRONICS to use their hands and develop some skill in this branch of light engineering, so admirably suited to table top operators.

NOT DESIGNS, ALONE

We referred to three classes of enthusiasts in


our opening paragraph. This division is of course a broad generalisation, but is substantially true. Our concern for the constructors does not end with the publication of designs with every detail clearly laid out. We appreciate the need for simple yet authoritative explanations of circuit theory. A sound knowledge of at least elementary theory is desirable, even for those whose chief interest is in the practical assembly work.

The *Teach-In* series which concludes with this month's article has been widely acclaimed in our post bag. This series has undoubtedly opened the door of electronics to thousands of novices. The awareness of what is happening in a circuit gives extra interest to the subject, and often will provide the urge to learn more. And that's not a bad thing.

PERSONAL CHOICE

We do always remember however that a hobby is first and foremost an activity indulged in for pleasure and recreation. How much time one is able or prepared to devote to it and how seriously one takes it, are all matters for each individual to decide for himself.

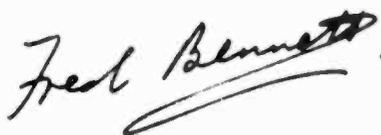It is this freedom of choice, and the absence of rules and constraints governing one's activity which sets a hobby apart from a routine job of work.



Our November issue will be published on Friday, October 15

EDITOR F. E. BENNETT • M. KENWARD • B. W. TERRELL B.Sc.
ART EDITOR J. D. POUNTNEY • P. A. LOATES • S. W. R. LLOYD
ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.
All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.
Subscription Rates including postage for one year, to any part of the world, £2.35.
Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



EASY TO CONSTRUCT SIMPLY EXPLAINED

VOL. 1 NO. 12

OCTOBER 1972

CONSTRUCTIONAL PROJECTS

- CASSETTE TAPE POWER SUPPLIES** Two supplies to power a cassette recorder by Mike Hughes 638
REACTOMATIC Reaction testing game by D. Smith 650
ELECTRONIC MOUSE TRAP Humane trap to catch mice alive by F. C. Judd 662

GENERAL FEATURES

- EDITORIAL** 636
SHOP TALK Component buying and new products by Mike Kenward 643
ELECTRONICS IN MEASUREMENT by Jon H. Talbot 644
BRIGHT IDEAS A reader's idea 649
TEACH-IN Part 12—Amplification by Mike Hughes 654
RUMINATIONS by Sensor 660
THEY MADE THEIR MARK No 6—Faraday (Part 1) by J. E. Gregory 669
TEACH-IN END OF TERM TEST Test your knowledge 670
READERS' LETTERS Controversial comment and news from you 673
Due to pressure on space **Guide To Circuit Symbols Part 5** is held over to next month

EXTRA NEXT MONTH!
See page 661 for details





Cassette Tape POWER SUPPLIES



Approximate
cost of
components
£2.00 (mains)
£1.10 (car)

Two units to power a cassette machine from the mains
or from a car battery by Mike Hughes

THE thousands of users of cassette tape recorders will know how useful it is to have a battery operated unit but will also be aware of the cost and comparatively short life of the internal battery supply. The recorder manufacturers have gone a long way to relieving the situation with clever design to keep current consumption to a minimum; nevertheless ten hours of intermittent operation seems to be a typical endurance.

This article describes two forms of auxiliary supply which are both simple to make and give excellent results; the first is a straightforward mains powered "battery eliminator" and the second provides a stabilised supply from a 12V car electrical system (operating from positive and negative earthed systems).

OUTPUT

Both units are designed to give a nominal output of 7.5V at currents up to about 200mA. This is the typical supply requirement of the Philips range of small cassette recorders. It is quite likely that the units could power other makes of equipment but the reader should read the manufacturers literature carefully to double check the voltage and current required.

The unit that interfaces with the car electrical system has the ability of providing a range of output voltages (from 7V to 9V at 200mA) hence is comparatively versatile and will probably drive most forms of transistorised radio, tape recorder or record player.

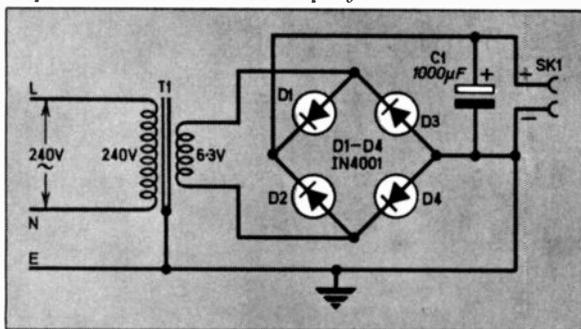


Fig. 1. Complete circuit diagram of the mains powered Cassette Tape Power Supply.

MAINS UNIT

The circuit for the mains unit is shown in Fig. 1 and is a simple unstabilised "sagging" supply. We call it sagging because the output voltage is to some extent dependent on the amount of current being drawn. Up to 200mA no noticeable effect on reproduction quality should be experienced.

Transformer T1 is a small 6.3V heater transformer the output of which is full-wave rectified by the diode bridge D1, 2, 3 and 4. Theoretically the output voltage of the bridge (when smoothed by capacitor C1) will equal the

peak voltage ($6.3 \times 1.4 = 8.8V$); this is in excess of that required. However we are using silicon rectifiers for the bridge and these will introduce a forward voltage drop bringing the output voltage down to between 7.5 and 8.0V. By the time a load is applied the output will fall to a nominal value of about 7.5V.

With the cassette recorder operating on its own internal speaker no hum is noticed even though the smoothing capacitor C1 is only 1,000µF. If, however, the audio output is to be amplified through a higher quality amplifier it would be worth considering increasing the value of C1 to about 5,000µF.

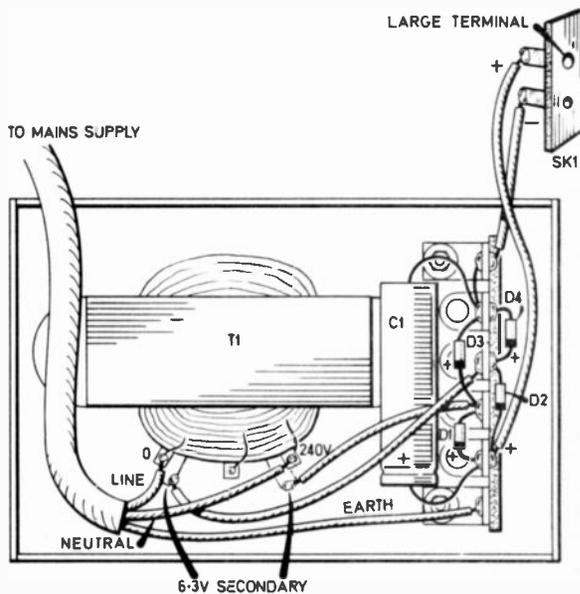


Fig. 2. Construction of the mains unit. Both the case and the negative supply rail are earthed via the earth wire in the mains lead.

CONSTRUCTION

Construction is shown in Fig. 2. The prototype case is a commercial design but could easily be fabricated out of 20 s.w.g. aluminium. Make absolutely sure that the terminations of the transformer do not touch the inside of the lid and ensure that an earth lead is provided. The negative side of the output should also be connected back to the chassis—and hence earth—for safety reasons. No on/off switch or indicator light was fitted on the prototype but these could be installed on the mains side of the transformer (a mains neon indicator may be used for the lamp) if required.

The output voltage is made available at a polarised output socket (i.e., one which will accept a plug one way round only) the type used in the prototype is a simple extension loud-speaker socket—the large contact being taken as positive.

Cassette tape POWER SUPPLIES

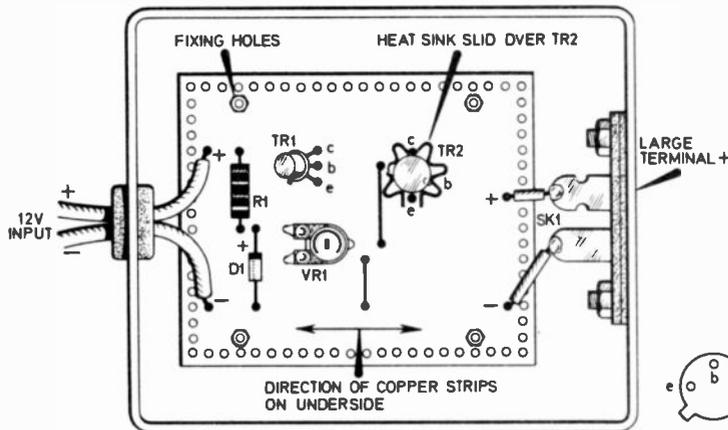


Fig. 4. The components mounted in position on the Veroboard inside the prototype case (Fig. 5.) Note the direction of the copper strips of the Veroboard—there are no cut-outs on these strips.

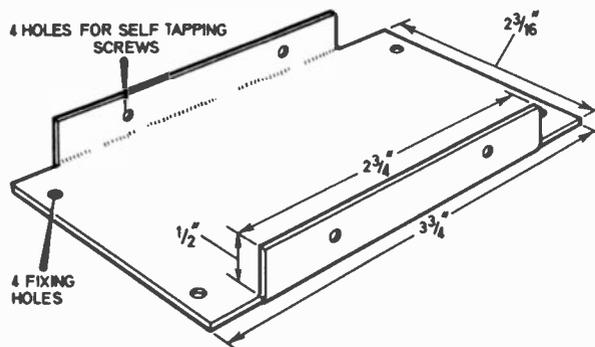
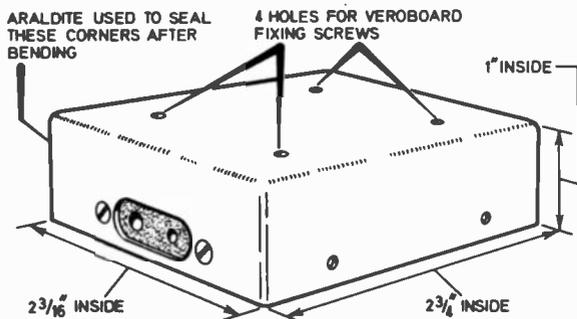


Fig. 5 (above). Dimensions and details of the prototype case used for housing the car unit. A suitable material is 20 s.w.g. aluminium.

Photograph of the assembled car unit with base removed.


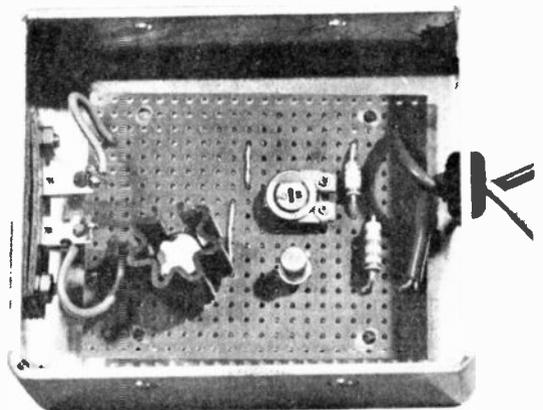


Fig. 6 (below). Details of the supply connection to a 5-pin DIN plug.

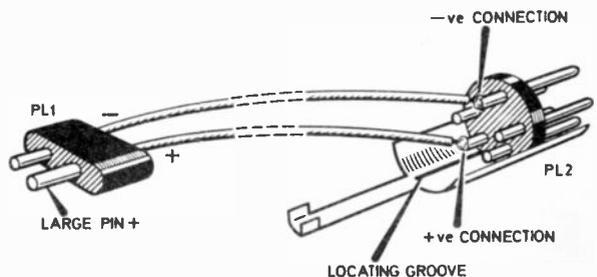

Components SEE

SHOP TALK

Mains Supply

Diodes

- D1 1N4001
 - D2 1N4001
 - D3 1N4001
 - D4 1N4001
- or any 1A, 50 p.i.v. silicon rectifier diodes

Transformer

- T1 240V primary, 6.3V 1A secondary (small heater transformer)

Capacitor


- C1 1,000 μ F elect. 12V (see text)

Miscellaneous

SK1 polarised panel mounting socket (loudspeaker type) Aluminium case (approx. 4in x 2½in x 2in—depending on transformer size), tag strip with 4 insulated and 2 grounded tags, ⅜in grommet, mains lead and three pin plug fused at 2A, connecting wire, 4BA fixings.

Components Common To Both Projects

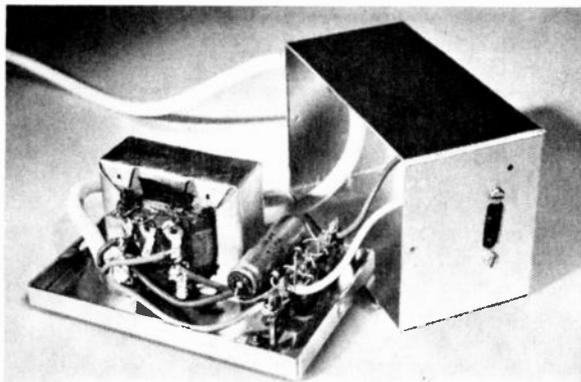Polarised loudspeaker plug (to suit SK1), 5 pin, 240 degree, DIN plug (for connection to recorder), two core connecting wire (length as required).



The construction of the mains unit.

CAR UNIT

The problem with running anything from a car's electrical system is that the voltage level (nominally 12V) varies quite considerably depending on the state of charge of the accumulator and the rate of charge from the generator or alternator.

Sometimes it might rise to as high as 15V. Thus we have to introduce some form of stabilisation as well as drop the level to that required by our equipment. We will use the circuit shown in Fig. 3. On the face of it, it may look extravagant using two transistors as well as a Zener diode but all the components are relatively

cheap and using a second transistor enables us to use a preset variable potentiometer (VR1) to set any output voltage we require between zero and 9V.

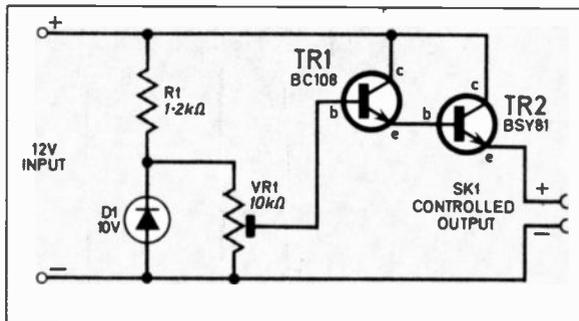


Fig. 3. Complete circuit diagram of car Cassette Tape Power Supply.

OPERATION

The Zener diode that supplies the reference voltage should have a value of approximately 10V. Certainly its value should not be greater than 10.5V and if less than 10V it will not be possible to get output voltages as high as 9V. Preset potentiometer VR1 provides a well defined reference voltage that can be set between zero and the full Zener level. This provides a small drive current into the base of TR1 the emitter current of which provides a much greater drive into the base of TR2 which is operating as a series stabiliser.

The combination of TR1 and TR2 in this configuration is sometimes called a Darlington pair. We need the intermediary action of TR1 because the current available from the Zener diode circuit—in particular when VR1 is set at a low voltage level—is small and the current gain of TR2 in isolation would not be sufficient if we wished to draw up to the 200mA specified.

No smoothing is required in this circuit because we are already operating from d.c. but if the stabiliser is to be used for powering a radio it might be worth incorporating a small capacitor (say 10 μ F) to prevent any breakthrough of car ignition interference. This should be connected across the power output leads of the unit. When the unit was used with a Philips cassette recorder no interference could be detected at all and the stabiliser even coped with the dramatic voltage drop of the car's electrical system while the starter was being operated.

CONSTRUCTION

All the components are mounted on Vero-board (Fig. 4); VR1 should be a flat mounting type so that it can be adjusted after the board has been installed in the box. Make sure that the Zener diode is connected the correct way round—the banded end should be connected to R1. A finned type of heatsink should be slipped

on to the can of TR2 (the can size is TO-5). Keep the leads of the components above the board as short as possible to prevent any mechanical vibration but at the same time do not overheat the components when soldering.

The box used in the prototype is formed from 20 s.w.g. aluminium the base being in the form of a flange (Fig. 5) which is used for fitting the unit to the bulkhead on the car. The Veroboard is bolted inside the lid on insulated spacers. Power input leads are taken out through a grommeted hole for permanent wiring to the car and the output connections terminated at a polarised socket identical to that described earlier—make sure that you keep to the same polarity convention!

Note that no electrical connections are made to the metal of the box; this enables the unit to work from either positive or negative earth cars. Before connecting up make sure you know your car's polarity otherwise you may permanently damage the transistors.

SETTING UP

Before connecting up to the tape recorder set VR1 to give the output voltage required by measuring the output with a voltmeter. If you cannot get the full 9V output it means that the Zener diode has a lower breakdown than that specified; check this by measuring the potential difference across the Zener. The output voltage will always be approximately 1V less than the reference voltage set by VR1 because of the forward voltage drops of the base/emitter circuits of TR1 and TR2.

Because of the maximum dissipation of TR2 the output voltages are limited to the range 7 to 9V at up to 200mA. However, if lower voltages are required, these can be obtained by setting VR1 accordingly but the current output will not be so high. For example 100mA at 2V would be permissible and approximately 150mA at 5V.

For Philips recorders it is not necessary to incorporate any switching in the recorder itself. Inserting the DIN plug automatically cuts out the internal batteries. This may or may not be the case with other equipment.

It is worth repeating the manufacturer's instructions that if you do not intend to use the batteries within the recorder for some period of time they should be removed to prevent any possible leakage and corrosion.

SUPPLY CONNECTION

To connect the supply to the recorder an accessory lead is made up using a polarised plug (to mate with the socket just described) and a 5-pin (240 degree) DIN plug that is accepted by the accessory input of the recorder. Make absolutely certain that you connect up to the correct pins as shown in Fig. 6.

This wiring is correct for the Philips equip-

ment and should apply to other manufacturers but you are advised to make absolutely sure by referring to the manufacturer's own leaflet or service sheet. Once this lead has been made up it can be used with either the mains or the car unit. □

Components SEE **SHOP TALK**

Car Battery Supply

Resistor

R1 1.2kΩ ¼W ±10% carbon

Variable Resistor

VR1 10kΩ skeleton preset (flat mounting type)

Semiconductors

TR1 BC108

TR2 BSY81, or BFY51,


D1 10V 400mW Zener diode

Miscellaneous

SK1 polarised panel mounting socket (loudspeaker type) Veroboard 2in x 1½in x 0.1in matrix, TO5 type heat sink (finned push on type), ⅜in grommet, material for case (see text), connecting wire, 6BA fixings

Components Common To Both Projects

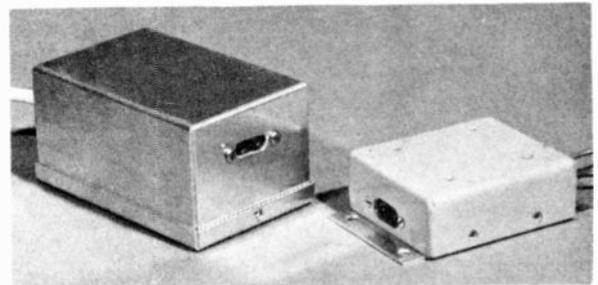Polarised loudspeaker plug (to suit SK1), 5 pin 240 degree DIN plug (for connection to recorder), two core connecting wire (length as required).



AUDIO FAIR

EVERYDAY ELECTRONICS and PRACTICAL ELECTRONICS will be exhibiting at this year's International Audio Festival and Fair, Olympia London, October 23-28.

See us on Stand 19, Ground Floor.

Sound Synthesis For The Amateur is the title of a lecture/demonstration to be given by D. Shaw, contributor to PRACTICAL ELECTRONICS, on Tuesday, Oct 24 and Saturday, Oct 28 at 2 p.m.

ONCE again this month we have a couple of new products well worthy of mention so we will deal immediately with buying problems and then take a look at the products.

Just a couple of points concerning the *Weather Station* (August issue); first G. W. Smith have now informed us that they do not supply the case for the monitor unit and unfortunately we have been unable to find a supplier. However Garland Bros. Ltd., who advertise in our pages can supply a slope fronted case in plain aluminium. The second point is that the GL23 thermistor is available from Henry's Radio, who also take space in our issues.



Mouse Trap

A very unusual project—the *Mouse Trap*—but surprisingly enough one that has been in demand amongst our staff ever since the prototype was given to us by Fred Judd. Even those people who did not think they had mice (like me) have found that the *Mouse Trap* will catch any that are around; perhaps they are attracted by the light inside!

As far as we can see there should be no buying problems for this project. The Perspex should be available locally at a good hardware shop or from a small firm that uses it e.g. sign makers. Incidentally the door retaining wire can be made from one of the EE binder retaining wires (what a good sales gimmick!)

Easi-Binders to hold 12 issues of EVERYDAY ELECTRONICS are available from Binding Dept., IPC

Everyday Electronics, October 1972

Magazines Ltd., Carlton House, 68 Great Queen Street, London W.C.2. These binders are well worth having even if you are not building the *Mouse Trap*, they are finished in orange de luxe Balacon (similar to p.v.c. in appearance) and cost 88p including postage and packing.

Reactomatic

Few buying problems should be encountered when getting parts for the *Reactomatic*. Two things to note are that the control knob should not have any markings on it and that the lamps used are easily visible in daylight when illuminated. Those shown on the prototype proved rather difficult to see and larger types with enclosed bulbs and bigger lenses may well be better. None of the other components should be difficult to get, any type of push-to-make push button can be used.

Cassette Tape Power Supplies

The two *Cassette Tape Power Supplies* described are likely to be among the most popular designs we have yet published—judging by the correspondence we receive requesting such devices. They have been kept very simple in design and all the parts are easy to obtain.

The case shown for the mains unit is a "Norman case" which was purchased from Radio Component Specialists who advertise in our pages. The car unit could be put in a similar case although this is larger (4in x 2½in x 2in) than that shown in the article.

If you have any difficulty getting the polarised plugs and sockets, most car accessory shops can supply them.

New Products

A new "Cassette Re-Record Kit" has recently been introduced by Bib who already make a vast range of audio accessories. The kit is designed to enable pre-recorded cassettes to be used to record on when the original material becomes outdated.

The kit contains 20 plastic inserts to press into the holes at the back of the cassette, 27 labels to stick over the existing title labels, and a tab removing tool to remove the plastic inserts on existing recorded cassettes, or the inserts in the kit, so that the



cassette can be preserved without the risk of accidental erasure after it has been recorded or re-recorded (if you can follow that).


The kit is available from most hi-fi and audio shops. The recommended retail price is 44p and full instructions for using the kit are printed on the back of the header card.

Another new product from West Hyde Developments—whose cases were mentioned last month—is what they term as a "throw away" multimeter. Primarily intended to be issued to engineers, the meter may well appeal to constructors as a cheap portable meter. The ranges are 15, 150, 1000V a.c., 15, 150, 1000V d.c., 1, 150mA d.c. current, and a resistance range capable of reading values from 100Ω to about 30kΩ, sensitivity is 1,000Ω/V and the meter costs £2.

The beauty of the meter is its compact size—about 3½ x 2¼ x 1 inch, it is made in Japan and is sold with test leads and a brief, quaintly translated, instruction sheet. The photograph below gives a good idea of the size of the meter.

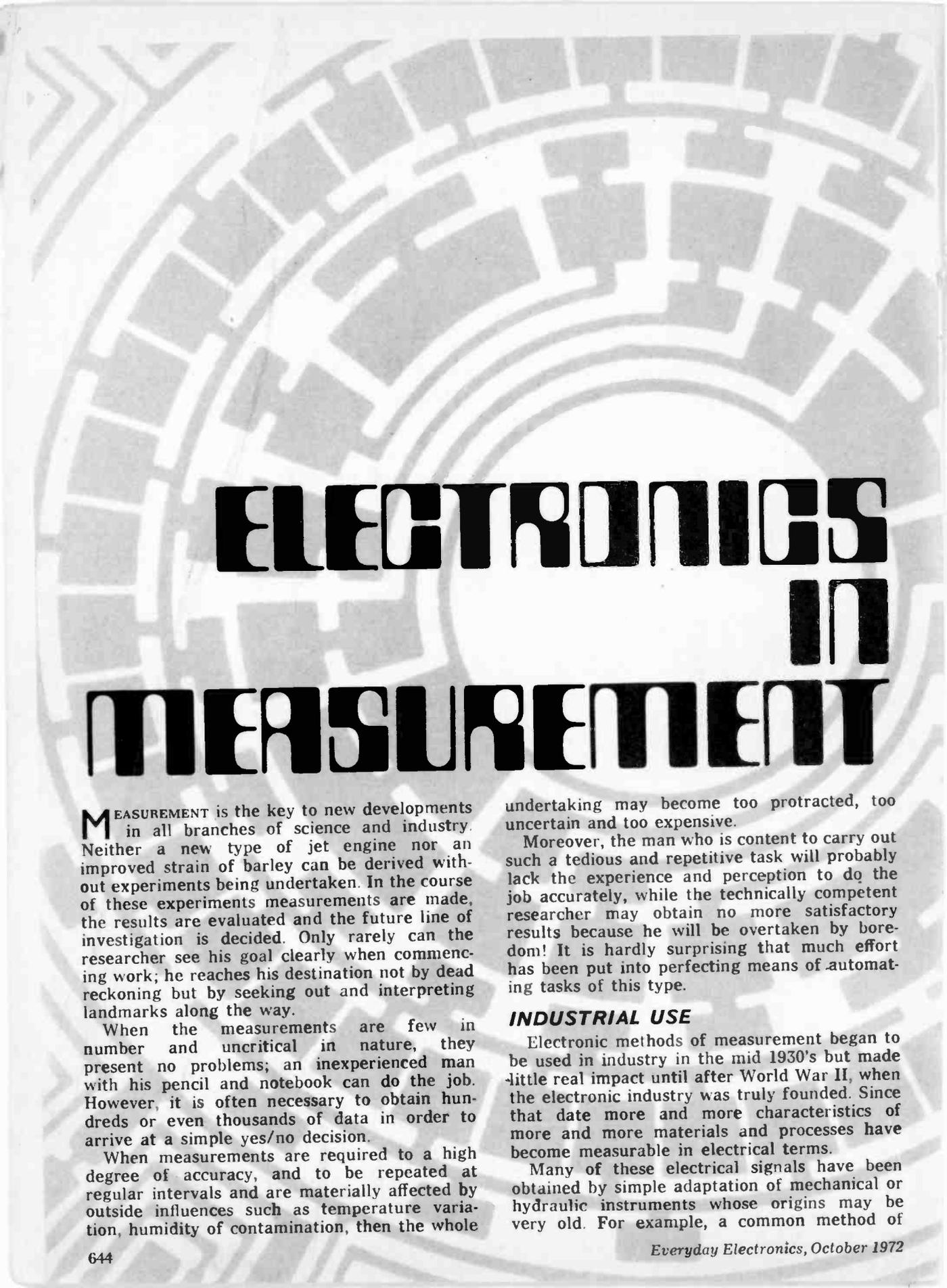The meter is available from West Hyde Developments Ltd., Ryfield Crescent, Northwood Hills, Northwood, Middlesex, HA6 1NN.





ELECTRONICS IN MEASUREMENT

MEASUREMENT is the key to new developments in all branches of science and industry. Neither a new type of jet engine nor an improved strain of barley can be derived without experiments being undertaken. In the course of these experiments measurements are made, the results are evaluated and the future line of investigation is decided. Only rarely can the researcher see his goal clearly when commencing work; he reaches his destination not by dead reckoning but by seeking out and interpreting landmarks along the way.

When the measurements are few in number and uncritical in nature, they present no problems; an inexperienced man with his pencil and notebook can do the job. However, it is often necessary to obtain hundreds or even thousands of data in order to arrive at a simple yes/no decision.

When measurements are required to a high degree of accuracy, and to be repeated at regular intervals and are materially affected by outside influences such as temperature variation, humidity of contamination, then the whole


undertaking may become too protracted, too uncertain and too expensive.

Moreover, the man who is content to carry out such a tedious and repetitive task will probably lack the experience and perception to do the job accurately, while the technically competent researcher may obtain no more satisfactory results because he will be overtaken by boredom! It is hardly surprising that much effort has been put into perfecting means of automating tasks of this type.

INDUSTRIAL USE

Electronic methods of measurement began to be used in industry in the mid 1930's but made little real impact until after World War II, when the electronic industry was truly founded. Since that date more and more characteristics of more and more materials and processes have become measurable in electrical terms.

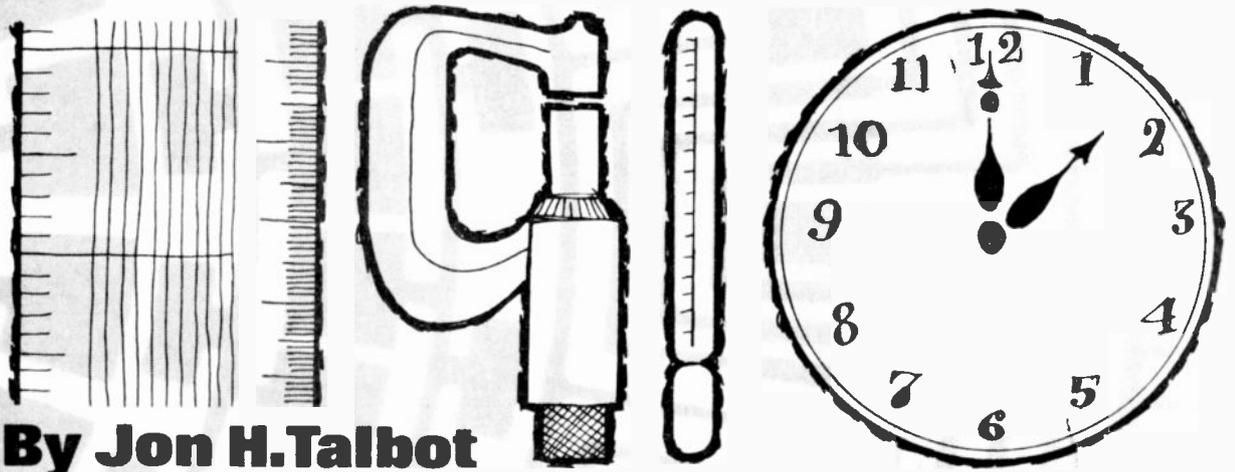Many of these electrical signals have been obtained by simple adaptation of mechanical or hydraulic instruments whose origins may be very old. For example, a common method of



By Jon H. Talbot

measuring the pressure of a liquid in a pipe is to take a tapping via a small bore tube terminated in a seamless metal bellows. As the pressure rises the bellows becomes distended and moves the pointer of an indicator.

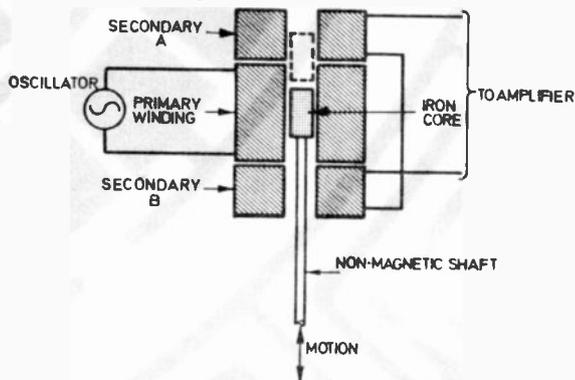


Fig. 1. Schematic diagram of a Differential Transformer (displacement measurement). The cone movement direction is determined by the amplifier by comparing the phase of the received signal with that from the oscillator.

To make this simple pressure gauge generate an electrical signal we can make use of a differential transformer. An iron core is attached to the rod which formerly drove the pointer and this core is located centrally inside a cylindrical coil. The coil is energised by an a.c. signal and is in close proximity to two other coils which are located at either end. As the core rises and falls with increasing and decreasing pressure it causes a larger voltage to be induced in one secondary coil and a smaller voltage in the other (Fig. 1). The magnitudes of these induced signals are a measure of the displacement of the bellows.

ANALOGUE TRANSDUCER

The pressure gauge described above is an analogue transducer: a device producing a signal which varies steadily with the parameter being measured (in this case, pressure) and, in theory at least, it has infinite resolution i.e. an infinitely small change in pressure results in an infinitely small change in electrical output. In practice, of course, the mechanical characteristics of the

moving parts will result in the output changing in tiny jerks so the resolution, while fine, is not infinite.

NEW ELEMENTS

Some of the early measuring instruments did not lend themselves readily to such adaptations and entirely new primary elements had to be devised. These new instruments were often designed and developed throughout by electronic firms and as a result were more readily incorporated into complete electronic systems.

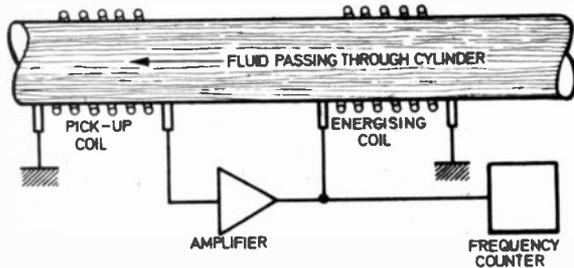


Fig. 2. A cross-sectional diagram of a vibrating cylinder density transducer.

The physical linkages between the medium being measured and the electrical circuit were simpler and more direct, eliminating some of the sources of inaccuracy. An example is the vibrating cylinder density transducer (Fig. 2). An amplifier drives a coil which sets up vibrations in a tube through which a gas or liquid is flowing. When the density of the fluid increases it raises the mechanical loading on the tube and reduces the resonant frequency of what is really a mechanical tuned circuit (rather like a tuning fork). The vibration is detected by a pick-up coil and the frequency of the energising signal is

Assembling and testing transducers for gas density measurement.

(Solar Electronic Group Ltd)



changed in sympathy. This means that the natural frequency of oscillation of the electro-mechanical circuit is a measure of the fluid density.

This density transducer is, for obvious reasons, described as a frequency-domain device.

DIGITAL TRANSDUCER

There is a third type of transducer which is more limited in application but possesses the advantage that it needs no calibration as such, while the desired resolution is defined when the instrument is made. This is the digital transducer, of which by far the commonest example is the encoding disc.

In appearance it is similar to a series of stroboscope rings such as those used to check the speed of a gramophone turntable. The centre ring has a small number of segments while the other rings have progressively more segments as their circumference increases.

If the disc is fixed onto a shaft, then the angular position of the shaft at any instant, whether it is moving or stationary, can be detected by examining the position of the segments by photo-electric or mechanical means. An example of such a disc is shown on the front cover and the pattern is also used in the heading of this article.



Checking the finish of a lens with the Talyrond 73 roundness measuring system. This system which can detect surface irregularities of the order of one millionth of an inch, uses a special purpose computer to correct for inaccuracies in work positioning etc. Defects of the work piece are recorded on a rotating chart. (Rank Precision Industries Ltd.)

The disc is often made in the form of a printed circuit board so that its position can be ascertained by picking up an electrical output from stationary brushes.

There is a great need for better transducers. This has been highlighted by the increasing importance of detecting pollutants in air and

water, yet it is still only possible to isolate certain poisonous substances by carrying out a chemical analysis manually.

DATA LOGGING

The process of automatically collecting and recording information from a number of transducers is called data logging. In its simplest form, a data logger comprises a scanner, an analogue-to-digital converter and an output device (Fig. 3).

The scanner is a series of relays which are operated sequentially such that the output from a number of analogue transducers is connected to the converter in turn. The converter samples each signal and feeds the result of its measurement in digital form (binary or binary-coded decimal) to the output driver.

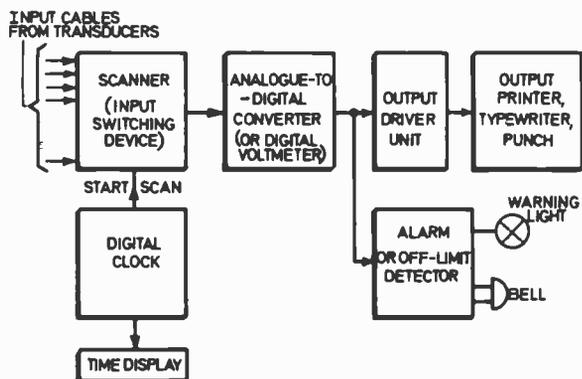


Fig. 3. Block diagram of a typical data logging system.

The output machine may be a strip printer, which prints the results on a tear-off strip for the convenience of the plant operator; it may be an electric typewriter which produces a record in tabular form suitable for binding into a log-book, or it may be a punch, which produces perforated paper tape for subsequent computer analysis.

A more elaborate logger will include a digital clock, which enables the readings to be repeated at accurately determined time intervals, and an alarm detector that flashes a light and rings a bell if a reading is taken that is outside prescribed limits.

APPLICATIONS

The applications of data logging are not restricted to research alone. Frequently the information which has been obtained by a data logger is used to set the controls in a process plant. An obvious development is to use signals from the logger to operate relays, valves and motors controlling the plant, thus avoiding the need for intervention by the plant operator.

In the case of a small electric furnace, where close temperature control may not be needed,

this can be achieved easily. If the logger detects that the temperature is too low then the alarm detector energises a relay that switches on the heating elements. When the logger returns to that measuring point (or channel) and finds that the temperature is now too high, then the relay is relaxed and power is removed from the furnace.

If the temperature is to be maintained within close limits a much more refined control system will be needed. A complicated industrial operation may involve a hundred or more variables, not only temperatures but pressures, flows, densities and levels as well.

Many variables are closely interrelated with others and are subject to disturbances of a random nature, so the only means of running the plant is to entrust the whole operation to a digital computer.

However, the largest and fastest computer, controlled by comprehensive programmes, is ultimately dependant upon the information it is given. The plant may produce nothing but waste output if the transducers are badly sited or the scanning system is poorly conceived.

VOLUME MEASUREMENT

There are many fields of measurement which are more complex than they at first appear.

When a petrol tanker discharges at a filling station the driver sometimes checks the level of liquid by means of a dipstick—a convenient and simple tool. At the oil refinery the level of liquid in the huge storage tanks is often checked in a similar manner: a float moves a cable or tape, made of low-expansion alloy, and this drives a remote indicator. The depth of liquid can be measured accurately, but petrol and oil are sold by the gallon—by volume. The relationship between the two types of measurement is not simple.

Oil storage tanks are made of steel and concrete, but they are not as rigid as they appear. When an empty tank is filled, the effect is not unlike that of filling a plastic bucket; the bottom becomes concave and the sides become slightly barrel-shaped, so that each additional

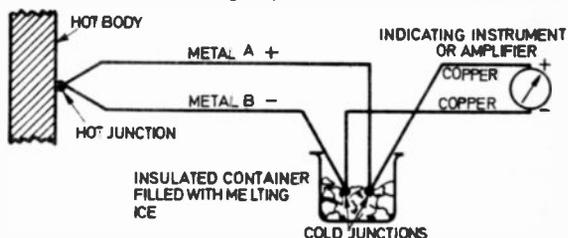


Fig. 4. A schematic diagram of a thermocouple—used for temperature measurement. The thermocouple utilises the principle that if two dissimilar metal wires are joined at their ends, and each function subjected to a different temperature then a current flows, its magnitude being proportional to temperature difference of junctions.

foot of depth represents a different quantity of oil.

The volume of oil is also affected greatly by temperature and barometric pressure; the value of the contents of the largest size of tank is over £1000 more on a hot, sunny day than on a cold, overcast day (there are some anxious moments when the Inland Revenue inspector calls to determine the duty payable!)

Fig. 5 (top). Appearance of a typical strain gauge element. (Bottom) Shows the insertion of the element into a Wheatstone bridge. Utilises change of resistance with element geometry.

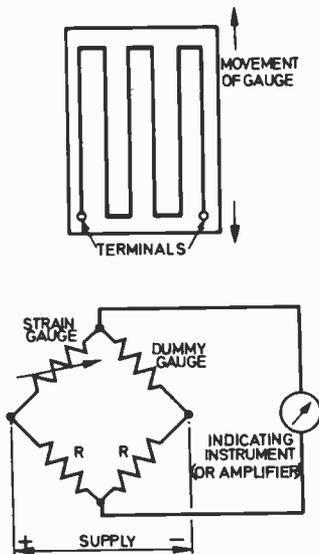


Table 1: Transducers used for measurement in industry

| Parameter | Transducers and associated equipment |
|---------------------|--|
| Temperature | Resistance thermometer Thermocouple Thermistor (temperature-sensitive resistor) |
| Light | Photo-electric cell Photo-multiplier tube |
| Acidity | pH electrode (measures hydrogen ion concentration) |
| Properties of Gases | Infra-red source and Detector Colorimetric Analyser (measurement of transmission of light of various frequencies) |
| Hardness | Diamond pyramid tester and differential transformer |
| Magnetic field | Hall-effect element |
| Mechanical strain | Resistance strain gauge Load Cell |
| Proximity | Capacitance proximity detector Ultrasonic source and detector |
| Displacement | Differential transformer |

The only way of obtaining a direct reading of the contents, which is corrected to normal temperature and pressure, is to use what is in effect a special-purpose computer that is connected to temperature and pressure sensors and to a depth transducer. This machine combines their outputs by correcting the depth reading according to ambient conditions and to a preset programme which corrects for mechanical distortion of the tank.

Instruments of this type have been made experimentally and will undoubtedly come into common use, but at present they are too expensive to compete with existing equipment.

Many of the potential benefits of electronics in measurement have not been realised in the past because electronics men have concerned themselves more with "pure" rather than applied electronics, while established industries have been slow to adopt new techniques. The alchemists and luddites have their counterparts in modern times!


MACHINE TOOLS

One of the slowest industries to adopt electronic methods was that of machine tools, yet precision machining of metals lends itself well to digital measurement techniques. A problem here was that the tools had to be designed around the transducers; it was not enough to add electronic appendages to existing machines.

Nowadays all types of machine-shop work, from the finishing of rough castings to the repetitive milling of complex mechanical structures from the solid, is carried out under the control of signals from magnetic or punched paper tape.

The machine work-table is fed upwards, sideways and forwards, tools are changed and feed rates are monitored and adjusted under electronic control. Here the measurement devices are "closing the loop"—they confirm that a certain operation is being carried out exactly as required by the directions on the tape, and correct for factors such as tool wear that cannot be assessed in advance.

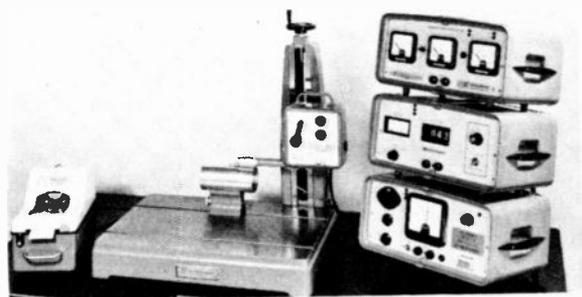The Talysurf 4 system which counts the irregularities in a machined surface and enables the texture of the finish to be evaluated quantitatively. (Rank Precision Industries Ltd.)



DYNAMICS

There is increasing interest in measurement that is dynamic rather than static, for time delays are important in many processes. For example, the spring rate of a valve spring for the engine of a motor car can be determined by loading it with a weight and measuring the amount of compression with a rule. This, however, offers very little data on what happens when it is compressed 4000 times a minute in a working engine.

It is more instructive to compress the spring, release it in 1/4000th. of a minute, and then measure how long it takes to come to rest.

It is the transfer function, the relationship between stimulation and response that matters, and this has led to the spawning of a whole new generation of dynamic analysis instruments. These can either simulate an operation electrically on the bench or be coupled temporarily into a working system to cause known perturbations which can be analysed automatically.



Using a Transfer Function Analyser to determine the relationship between respiration and work done by humans. (Solartron Electronic Group Ltd)

A new dimension has been added to the science of measurement and provides a fresh view of concepts that had been developed as far as our previous static assessment would allow. □

Everyday Electronics, October 1972

BRIGHT IDEAS


A readers' Bright Idea; any idea that is published will be awarded payment according to its merit. The ideas have not been proved by us.

I have found a way of making test probes for equipment that are cheap, insulated and rugged.

The parts needed are the red and black bodies of two "Scripto" or "Venus Gem Writer" type of felt tip pens that have been used up, a piece of stiff wire such as that used to make coat hangers and two lengths of red and black connecting wire.

To make the probe, remove the ink felt and fibre tip by pulling off the white end and the tip cap. Cut a length of stiff wire—about 6 inches long and file one end to fit into the plastic tip. Cut a small hole in the white cap, pass a connecting wire through the cap, solder it to the stiff wire, and reassemble the pen. The photograph shows the construction and the finished probe.

E. R. Wall,
Chalton, S.E.7.

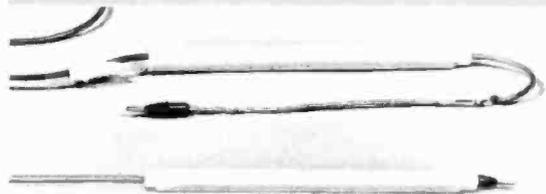

Please Note: this column is intended for constructional ideas and ideas relating to electronic construction. It is not our intention to publish circuits of any description.

All items submitted should be original and not previously published.

A reaction testing game that can also be converted to a quiz answering indicator.

By D. Smith

REACTOMATIC



Approximate
cost of
components
£3.00 plus case

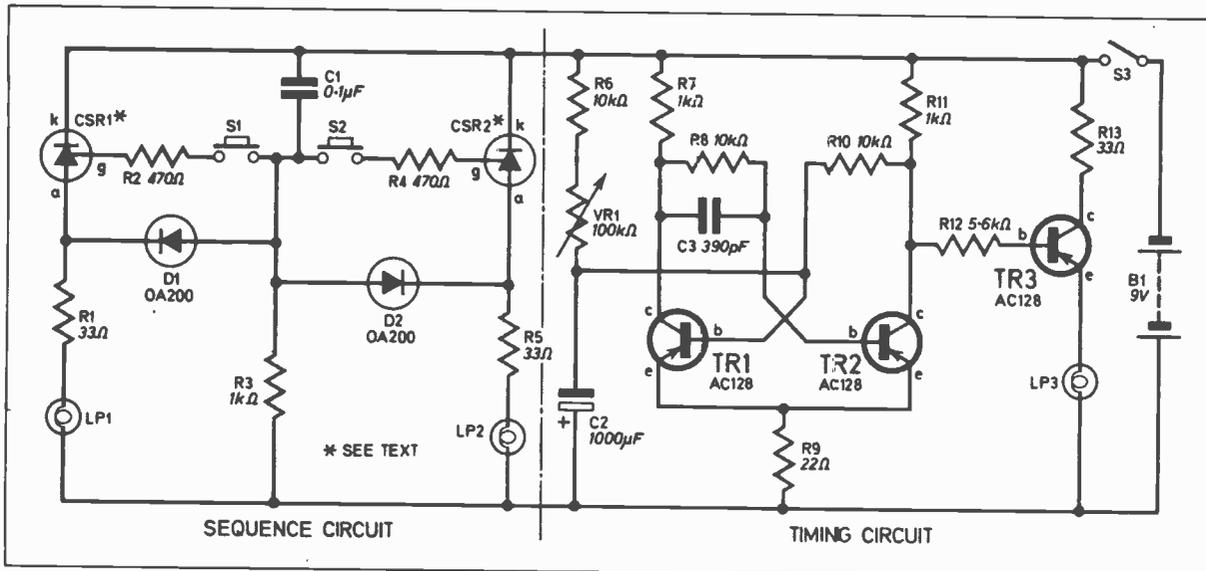


Fig. 1. Complete circuit diagram of the Reactomatic.

THE REACTOMATIC is a game of fun and skill for young and old alike. Being portable, it is ideal to take to parties or clubs. The basic sequence indicator can also be used, with a number of push-buttons, for quiz game answering.

At home it will keep two people amused for hours, testing their skill against each other and, being a silent game (using only bulbs), will not distract the other members of the family.

Since the unit uses batteries there is no risk of shock, it is light in weight, portable and is cheap to build.

CIRCUIT DESCRIPTION

The circuit (Fig. 1) can be broken down into two main parts; the timer circuit, consisting of TR1, TR2, TR3, and their associated components, and the sequence circuit.

If we take the timer circuit first, it will be seen that TR1 and TR2 form a bistable and TR3 is an electronic switch. When the unit is switched on by S3, the bistable flips into "mode one". (TR1 off, TR2 on). A negative charge is then allowed to build up on the base of TR1, via R6, VR1 and C2.

When a certain amount of voltage has built up across C1, it will switch on TR1 which will then, via R8 and C3, switch off TR2. Therefore the voltage at the collector will go negative.

This negative voltage is passed to the base of TR3 via R12. Hence TR3 is switched on and allows voltage to flow through it to light LP3. The time for this to happen is determined by the value of C2, R6 and VR4.

The values shown in the circuit will give a delay of between approximately 5 seconds and

30 seconds. The latter time is ideal to build up tension in the players as they wait for the light to come on.

It should be noted that the knob fitted to VR4 should not be marked in anyway to show the time that has been set. A plain knob should be used, the loser of the previous game, re-setting it to a different time delay.

A 33 ohm resistor has been inserted in series with each of the three bulbs shown in Fig. 1. This is because the supply voltage is 9V and the bulbs are 6V, the resistors reduce the voltage to approximately 6V.

SEQUENCE CIRCUIT

The second part of the circuit containing the controlled silicon rectifiers (thyristors) works as follows. The idea is, that as soon as LP3 lights up each player pushes his button (S1 or S2) and the first one to do so turns his light on (LP1 or LP2 respectively).

Once one light is on the other cannot operate, therefore it is obvious which player pressed first.



When S3 is operated, C1 is charged up via R3. Now when LP3 lights, S1—for example—is pressed first and the positive charge stored in C1 is fed via R2 to CSR1. As only a small pulse of current is needed to switch CSR1 on, LP1 will light and remain lit as the current flowing through CSR1 is more than its holding current.

Once CSR1 turns on, C1 is discharged through D1 and CSR1, hence there is no voltage left in C1 to turn on CSR2.

If S2 is operated first, the reverse will happen, C1 will switch CSR2, via R4, and C1 will be discharged through D2 and CSR2, thus leaving no positive charge to operate CSR1.

All this happens very quickly, but the first person to press his push button will light the respective light. There is no need to keep the

REACTOMATIC

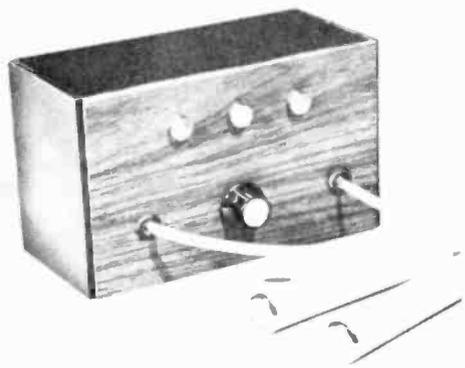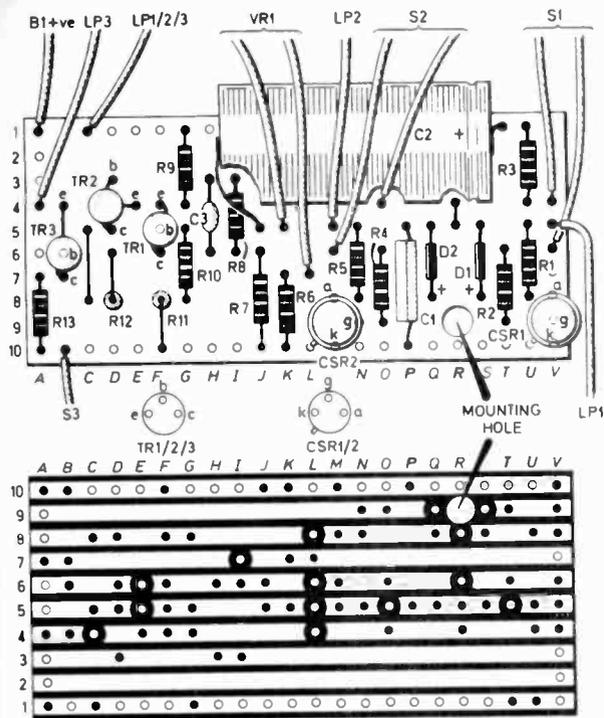

Photograph of the completed, unit ready for use.

Fig. 2 (above). The layout of the components on the top side of the Veroboard and the regions of copper strip to be removed from the underside.


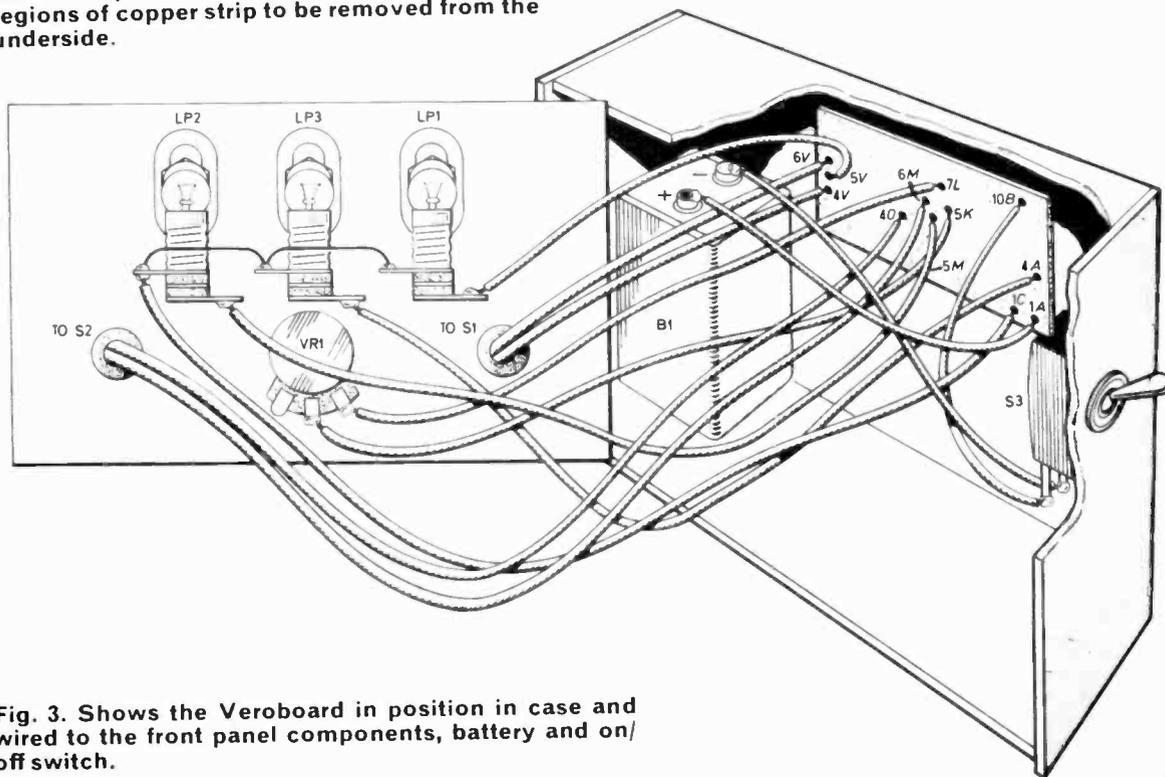


Fig. 3. Shows the Veroboard in position in case and wired to the front panel components, battery and on/off switch.

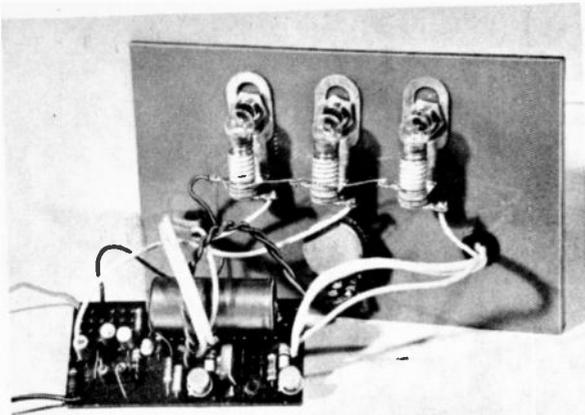

button pressed as the loser cannot possibly light his light, due to C1 being kept discharged all the time a light is on. Resistors R2 and R4 limit the current which switch CSR1 and CSR2 on.

Once the winner has been shown—by his light—S3 is turned off and then on again to restart the game. This allows C2 to discharge and CSR1 or CSR2 to turn off.

EXTRA PUSH BUTTONS

The sequence circuit can be increased in stages so that it may be used to indicate which of a number of players was first to press the button. To add on each additional lamp, simply repeat the push button, CSR, gate current limiting resistance (R2), lamp, lamp current limiting resistance (R1) and the bypass diode (D1). Components C1 and R3 need not be repeated.

The timing circuit does not need to be included if not required but an on/off switch must be used to reset the circuit. It will not be necessary to increase the battery capacity since only one light in the sequence circuit can be on.

CONSTRUCTION

The prototype unit was housed in a small plastic case, but any suitable box will do; layout is not critical. The three lamps, two push button leads and timer control are all attached to the front panel. On the side of the case is the on/off switch, and the circuit board, on which most of the components are situated, is mounted together with the battery inside the case. The circuit board is fixed to the panel by a single screw and an insulated spacer.

In the prototype the push buttons were mounted in two pieces of plastic tubing such as that used for holding mains wire. Plastic Padding or a similar filler is used to block up the ends of the tube to prevent the wires being pulled out.

If alternative types of push button are used they can be mounted on small blocks of wood. The push button leads should be quite flexible as they have to take a lot of bending; electric razor lead was found to be ideal for this purpose.

The Veroboard should be cut and the components mounted as shown in Fig. 2. Care should

be taken not to let heat from the soldering iron travel up the wires of the transistors, thyristors or diodes. A suitable heat shunt should be used when soldering in these components. Once the circuit board has been wired up it can be mounted in the case together with the remaining components and the complete unit wired up as shown in Fig. 3.

PLAYING

To play the game each player holds a push button and one player switches the unit on. When LP3 operates, the first player to press his push button wins (indicated by the corresponding light). The loser is then allowed to vary VR1 to reset the time. If a player pushes before LP3 lights the other player is declared the winner. The battery will last a long time provided the game is switched off as soon as possible. □

Components

Resistors

| | |
|--------------------|-------|
| R1 | 33Ω |
| R2 | 470Ω |
| R3 | 1kΩ |
| R4 | 470Ω |
| R5 | 33Ω |
| R6 | 10kΩ |
| R7 | 1kΩ |
| R8 | 10kΩ |
| R9 | 22Ω |
| R10 | 10kΩ |
| R11 | 1kΩ |
| R12 | 5.6kΩ |
| R13 | 33Ω |
| All ½W ±10% carbon | |

SEE
**SHOP
TALK**

Capacitors

| | |
|----|--------------------|
| C1 | 0.1μF |
| C2 | 1,000μF elect. 12V |
| C3 | 390pF |

Semiconductors

| | |
|------|---|
| CSR1 | Any 50 p.i.v. 1A thyristor (controlled silicon rectifier) |
| CSR2 | Any 50 p.i.v. 1A thyristor |
| D1 | OA200 |
| D2 | OA200 |
| TR1 | AC128 germanium pnp |
| TR2 | AC128 germanium pnp |
| TR3 | AC128 germanium pnp |

Miscellaneous

| | |
|-----------|--|
| LP1, 2, 3 | 6V 0.2A bulbs and panel mounting lamp holders |
| S1, S2 | S.p.s.t. push to make push buttons |
| S3 | S.p.s.t. toggle switch |
| VR1 | 100kΩ lin. carbon potentiometer |
| B1 | 9V PP9 battery |
| Case | (approx 7in × 4in × 3in, any material) plain unmarked knob for VR1, connecting wire, material for mounting S1 and S2 (see text), Veroboard 3½in × 1½in × 0.15in matrix, battery connectors, 6BA fixing and spacer. |



ELECTRONIC CIRCUITS -
..... IN THEORY and PRACTICE

TEACH-IN

... FOR BEGINNERS

By Mike Hughes M.A.

12

AMPLIFICATION

LAST month some experimenters might have been a little disappointed with the output of the little microphone amplifier we made. This is very understandable, but one must bear in mind that only two transistors were used, one for voltage amplification and the other to provide a low output impedance. This month we shall put matters right and develop a low power amplifier that will produce about 0.5W output—perfectly adequate for a baby alarm etc. But first we must carry out some improvements to our voltage amplifier.

Last month's circuit suffered from the problem that we had to set the bias manually to match the gain of the transistor—a good example for demonstration purposes—but not very practicable.

There are two very commonly used circuits that we can use for biasing that are not so sensitive to variations in h_{FE} ; the first is simple, and if used carefully is very adequate, but the second we shall describe is more generally favoured and uses a few more components.

FEEDBACK BIASING

The first option is shown in Fig. 1(a) and is called a **feedback bias** circuit. As before we must decide the output quiescent voltage which we shall fix at mid-rail potential (+4.5V) and at the same time decide the quiescent collector current, say 0.5mA.

This immediately fixes the value of R_1 as $4.5/0.5$ kilohm (9,000 ohm); say 10 kilohm.

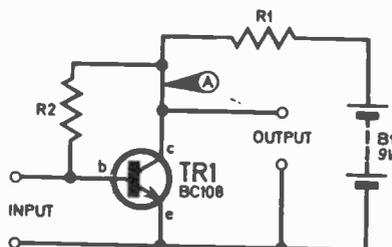


Fig. 1(a). Feedback biasing circuit. For experimental purposes make R_1 and R_2 equal to 10 kilohm and 1.5 megohm respectively. Check that the output voltage is approximately "mid-rail".

We shall use the potential at point "A" as the source of our base current—you'll see why in a moment—and we'll assume the gain of the transistor to be 200.

The base current for biasing should ideally be

$$\frac{I_c}{h_{FE}} = \frac{0.5}{200} = 0.0025\text{mA}$$

Assuming that the potential at point "A" is 4.5V we can therefore calculate the required value for R_2 . It will be

$$\frac{4.5 - 0.6}{0.0025} \text{ kilohm} = 1.56 \text{ megohm}$$

The nearest preferred value is 1.5 megohm. Make this circuit up on Demo Deck and verify that the quiescent voltage at "A" is approximately 4.5V. Try substituting different BC108's and you should find no appreciable change.

This circuit is self compensating as far as bias is concerned. Imagine you had a transistor with a low gain; initially the base current available from point "A" (assuming it was 4.5V) would not be sufficient to turn the transistor on hard enough to make point "A" fall to 4.5V so therefore "A" could not have been 4.5V—it would have been higher in potential.

If it had been at a higher potential then the base current would have increased thus bringing about a reduction in the voltage at "A."

In effect the circuit around the transistor settles itself out so that the potential at "A" is just enough to supply sufficient base current to keep the potential at "A" stable.

If you think we are talking in circles you are quite correct because what we have described is a **negative feedback loop**. If we have carried out our calculations correctly a very small increase in potential at "A" is all that is needed to provide that extra base current to compensate for a low gain transistor. This small increase will not present any major problems and will hardly be noticeable under normal circumstances. The same argument applies to a transistor with higher gain only the output potential will settle to a slightly lower than mid-rail voltage.

MODIFICATION

Modify your circuit slightly as shown in Fig. 1(b) and add the emitter follower output stage that we originated last month. Notice that instead of R2 we are using two resistors in series (470 kilohm and 1 megohm) and have introduced a variable resistor and capacitor.

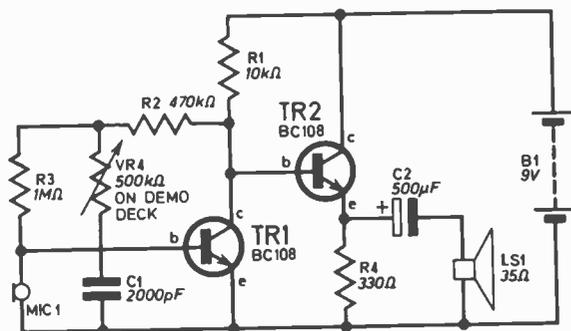


Fig. 1(b). A two-stage microphone amplifier, using a feedback biased stage followed by an emitter follower.

Initially set VR4 to maximum resistance, connect up the microphone, and you should find that the circuit works, but the output is not as great as last month's.

The reason for this is that the signal from the microphone is now appearing amplified at the collector of TR1, but because of the inverting property of the transistor, a certain proportion is being fed back through R2 and R3, 180 degrees out of phase (i.e. in a way that will

negate our input signal). Fortunately we can "catch" this fed back signal with C1.

Because the audio voltage is alternating it sees a low impedance in C1 and will be shorted out to the common rail—that is if VR4 is reduced to zero ohms. Try reducing the value of VR4 and you should find an appreciable increase in output from the loudspeaker.

POTENTIAL DIVIDE BIASING

The basic circuit of the second type of biasing system we shall cover is shown in Fig. 2(a). This can best be described as a **potential divide** type of circuit because the bias is dependent on the potential divide effect of resistors R2 and R3.

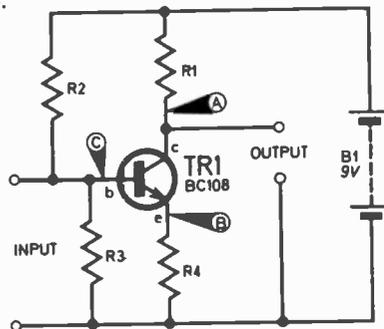


Fig. 2(a). Potential divide bias circuit. See text for the experimental resistor values.

Lets assume a mid-rail quiescent output at a collector current of 0.5mA; this makes R1 10 kilohm. Notice we have introduced a resistor (R4) into the emitter circuit. If current is flowing between collector and emitter (as it must) then the quiescent current of 0.5mA plus any base current, will flow through R4 giving rise to a voltage drop across it. In this article we can ignore the contribution of the base current as it is bound to be small compared with I_c .

The potential at point "B" must not be too high otherwise we will be unable to obtain wide voltage swings at the collector and it is usual to set this emitter voltage at 1V. This means that R4 will be approximately

$$\frac{1}{I_c} = 2,000 \text{ ohms}$$

Let's say 2.2 kilohm as the nearest.

For base current to flow the base must be made 0.6V more positive than the emitter (for a silicon npn device); this means that the potential at point C will be +1.6V.

STABILITY

The base current we require (still assuming an h_{FE} of 200) will again be 0.0025mA and this will have to be provided through R2. The values of R2 and R3 are arranged so that they form a potential divide that maintains the base potential at the 1.6V we require. For stability reasons it is usual to have a standing current through

150,000 Ω 

R2 and R3 that is 4 or 5 times the base current. Let's say we will make 4 times the base current flow through R3 and at the same time maintain 1.6V drop across the resistor; the value for R3 will be

$$\frac{1.6}{4 \times 0.0025} \text{ kilohm} = 160 \text{ kilohm}$$

The current for R3 has to pass through R2, but R2 also has to provide the base current; therefore the total current flowing through R2 will be five times I_b . The drop across the resistor will be $(9-1.6)V=7.4V$, so the value for R2 is

$$\frac{7.4}{5 \times 0.0025} \text{ kilohm} = 590 \text{ kilohm}$$


The nearest readily available values for R2 and R3 will be 560 kilohm and 150 kilohm respectively. Make up the circuit and measure the potentials at points "A" "B" and "C." Again the substitution of different BC108s should not cause the output voltage to vary significantly.

TRANSISTOR GAIN VARIATION

If a transistor of low gain was used, I_c would not be the anticipated 0.5mA initially, therefore the potential at point "B" will fall below the assumed 1V. This provides a more attractive set of circumstances for base current to be drawn through R2 so the current through R2 will increase, the potential at "C" will decrease and the current through R3 will decrease. The extra current flowing through R2 passes into the base of the transistor thus increasing the base current and this helps bring the quiescent collector current almost back to normal.

Again we have negative feedback effectively between the base and emitter circuits which self stabilises the biasing. For a transistor having higher gain the opposite will happen.

Fig. 2(b). The circuit diagram of a two-stage microphone amplifier using potential divide biasing.

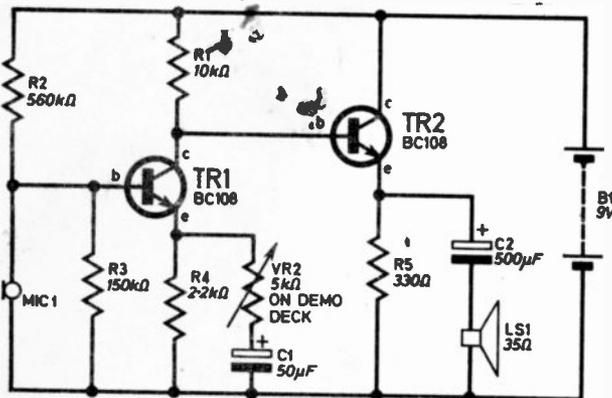

DRIVING THE LOUDSPEAKER

To complete the experiment make-up the com-

plete circuit of Fig. 2(b) and see that we can drive the loudspeaker. Notice the introduction of VR2 and C1. Initially set VR2 to maximum resistance; the output will be very poor indeed.

The reason is that TR1 is acting in part as an emitter follower. Any "overpotential" we apply at the base in the way of signal will appear at the emitter; thus we will not be producing much in the way of potential difference between base and emitter and hence not cause as much increase in base current as we might have expected. Ideally we want any current from the microphone to add to the base current in its entirety; this we can arrange by again using the fact that our signal will be alternating.

Connecting a large value capacitor between the emitter of TR1 and ground will present a low impedance path for the signal current to flow through without affecting the d.c. bias conditions. You can introduce C1 gradually by reducing the value of VR2 and will notice a dramatic improvement in output signal. We call C1 an emitter decoupling—or by-pass—capacitor; the maximum value of it is unimportant—but it must always be "greater than" a certain value.

Try replacing it with a 0.1µF capacitor; the circuit will work but with less output and any bass response which might have been there originally will be lost because the low value capacitor will only effectively decouple at high frequencies.

A problem with this circuit in our application is that the introduction of two resistors of comparatively low values (R2 and R3) in the bias circuit effectively reduces the input impedance of our voltage amplifier, hence, a lot of microphone signal will be shunted out to the power rails. Do not, therefore, expect quite as high an output as for the previous feedback biasing circuit.

We make no apologies for the comparatively low output powers of all these experimental amplifiers so far. It is easier to understand things if you concentrate on only one point at a time; therefore we deliberately made the power output stage as simple as possible so that we could concentrate on the important aspect of voltage amplification.

We hope that, from the two examples this month and the one last month, you appreciate there are several ways of producing the same effect; this happens all the way through electronics and is not limited solely to amplification. Follow other articles in EVERYDAY ELECTRONICS and you will soon see that different designers have different personal opinions and ideas as to what is the best circuit for the job and they may all be equally correct.

Some designs can be cheap but adequate, others expensive and full of special features that aid the quality of the design without altering the fundamental workings.

50,000 Ω

COMPLIMENTARY CLASS B BASICS

As promised we'll now show you how to get more power from the microphone amplifier and at the same time improve its quality. Firstly let's look at the fundamental circuit of what is called a class B complimentary symmetry output stage. This is shown in Fig. 3(a).

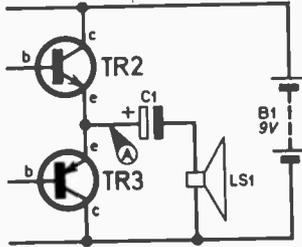


Fig. 3(a). The basics of a class B complimentary symmetry output stage; both an npn and a pnp transistor are used.

We are introducing a pnp transistor for the first time, TR3, but there is no need to worry too much about this except to remember it works just like an npn device with opposite polarity of supply voltage.

As shown in the circuit its collector goes to the common or negative rail and to make it turn on we must make its base go negative with respect to the emitter.

Both TR2 and TR3 are working as grounded collector or emitter followers. Assume nothing is connected to the bases of these transistors; no base current will flow in either and hence no current can flow from the collector of TR2 out of its emitter, into the emitter of TR3 and down to ground through its collector (this is the flow path for conventional current). These transistors are to all intents and purposes "open circuit" and we can consider the point "A" as being isolated from either the positive or negative rails.

If we also assume that C1 was charged so that its positive plate was at, say, +4.5V, the capacitor will maintain its charge because there is nowhere it can leak away to.

If we were able to make the base of TR2 more positive than +5.1V (0.6V more positive than its emitter) current will flow through the collector/emitter circuit of TR2 and charge up the capacitor until the potential at "A" rises to a new level that is 0.6V below the base voltage. This charge current must also pass through the coil of the loudspeaker.

Now consider what happens if we leave TR2's base open circuit and make the base of TR3 less than 3.9V (0.6V negative with respect to its emitter). Transistor TR3 will now act as an emitter follower and the capacitor will discharge through the emitter and collector of TR3 until the voltage at "A" is just 0.6V more positive than the base. You might challenge the assumption that point "A" could have been at +4.5V

in the first place—this is a fair comment but we assume that no transistors are perfect (there is always a small amount of leakage) and the leakage current through TR2 and TR3 will be about the same and hence we get a sort of potential divide effect at minute currents giving us a "starting" potential at point "A."

DISTORTION

Move on to Fig. 3(b) where we have connected the bases of TR2 and TR3 together and then back to the collector of a feedback biased stage—the quiescent output potential of which is +4.5V. This voltage is not 0.6V more positive with respect to TR2's emitter nor more negative with respect to TR3's emitter, therefore neither transistor will conduct (apart from leakage) and the positive plate of C1 will stay at about +4.5V—unfortunately you cannot measure this without an extremely high resistance voltmeter.


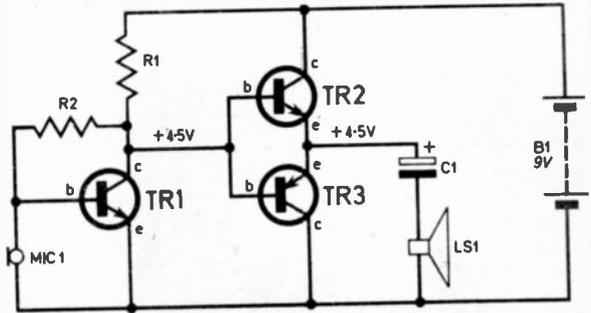


Fig. 3(b). A class B complimentary symmetry output stage preceded by a feedback biased stage.

If we whistled a perfect sine wave note into the microphone we know that the collector of TR1 would follow suit alternating by about 1V above and below +4.5V. As soon as we exceed +5.1V TR2 will start to conduct and charge current will flow through the loudspeaker; when we fall below 5.1V, TR2 will shut off and when we fall below +3.0V, TR3 will start to conduct

Fig. 4. These waveforms refer to Fig. 3(b) and show "crossover distortion."

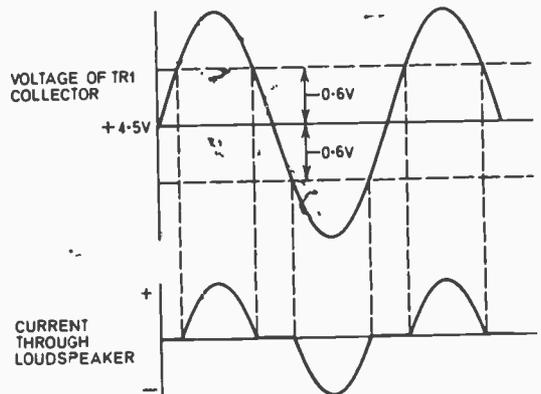

and discharge current flows through the loudspeaker in the opposite direction.

The only problem, so far, is that we are losing part of our signal. The current through the loudspeaker follows the voltage swings at TR1's collector only when we exceed certain limits; in between these limits it stops and we get a distorted current sine wave as shown in Fig. 4. This distortion is most undesirable and is called **crossover distortion** and is a classic problem with class B stages. Nevertheless it can be avoided as we shall see.

First of all take note of the important point that in the absence of any microphone signal no current at all is flowing through the output transistors—the transistors are dissipating no power.

This is a tremendous advantage over the simple emitter follower stage described last month which had a quiescent current almost as high as the amount of signal current fed to the loudspeaker which is wasteful on power and means that we have a static dissipation in the transistor which is serving no useful purpose (acoustically speaking) and limits the amount of power we can use as signal. This is a problem associated with the type of output stage known as class A.

CROSSOVER ELIMINATION

To overcome crossover distortion we have to arrange that the quiescent voltages at the bases of TR2 and TR3 are just on the threshold of taking the transistors into conduction. This is done by introducing an extra stage in our power amplifier called a driver. This is shown as TR1 in Fig. 5(a).

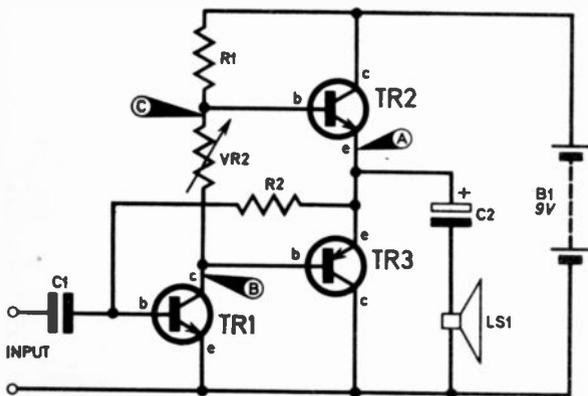


Fig. 5(a). By introducing a "driver" stage, TR1, crossover distortion can be eliminated.

Resistor R2 works like the feedback resistor in our voltage amplifier and by careful calculation we can ensure that the potential at "B" is just enough to start TR3 conducting; VR2 and R1 form the collector load of TR1, but VR2 also ensures that there is always twice 0.6V (1.2V) difference in potential between points "B" and

"C." Both TR2 and TR3 will be conducting slightly and point "A" will settle (aided by negative feedback from R2) to about +4.5V. Any negative going signal at the input capacitor will make TR2 go more into conduction, and vice versa for TR3.

This time we will have no crossover distortion provided VR2 is of a high enough value to maintain the quiescent voltage differential between points "B" and "C."

In Fig. 5(b) you will notice that in the practical circuit we are using a silicon diode (D1) in forward biased mode to help maintain the 1.2V difference—it also helps combat variations in temperature that affect the emitter/base forward voltage drops of the output transistors.

MATCHING

A final couple of points before describing Fig. 5(b); in a good quality piece of equipment the h_{FE} of the **complimentary output pair** of transistors (TR2 and TR3) should be accurately matched so that the current through the loudspeaker is symmetrical on the "charge" and "discharge" parts of the cycle. With the low price transistors we have specified this is not possible, but we can tolerate a reasonable amount of distortions at low powers.

Because the voltage across either of the output transistors—when they are conducting—never exceeds 4.5V, and in the quiescent condition no current is flowing, we now have the full current and power rating of each transistor at our disposal. We could, theoretically, charge over 4.5V with a peak current of 100mA which gives a peak power of 0.45W and discharge through TR3 at the same rate giving an overall power output of nearly 1 watt. This, of course, is an absolute maximum and actually exceeds the individual r.m.s. power ratings of the transistors; however this can be tolerated provided the power overload is only temporary.

When dealing with commercial power amplifiers you will find the power ratings quoted as r.m.s and peak—sometimes peak power is described as "music rating" and r.m.s power as "continuous rating."

MICROPHONE AMPLIFIER

Fig. 5(b) is our grand finale for the Teach-In series and represents a reasonable 0.5W r.m.s microphone amplifier that embodies many of the points we have covered in the latter part of the series.

Transistor TR1 is a potential divide biased voltage amplifier, TR2 the output driver and TR3 with TR4 gives us a class B complimentary output stage. The driver serves two purposes; it enables us to bias the output transistors but also, as a by-product, gives us a further stage of voltage amplification. This ensures that we can drive the output pair to "saturation" from


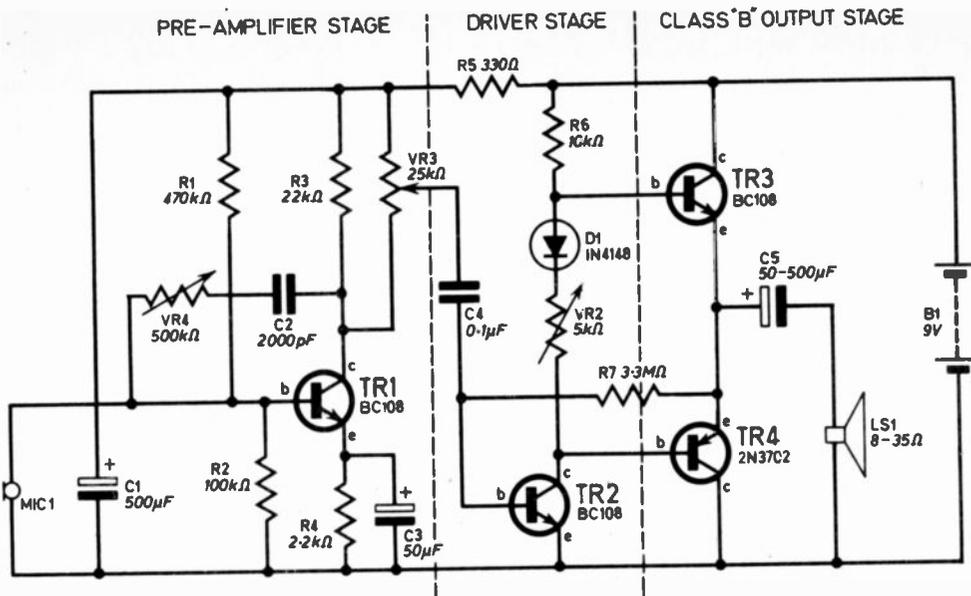


Fig. 5(b) (above). The circuit diagram of a 0.5 watt microphone amplifier using a potential divide biased first stage followed by a driver and class B complimentary symmetry output stage with several refinements.

Fig. 5(c) (right). The circuit of Fig. 5(b) shown wired up on the Demo Deck.

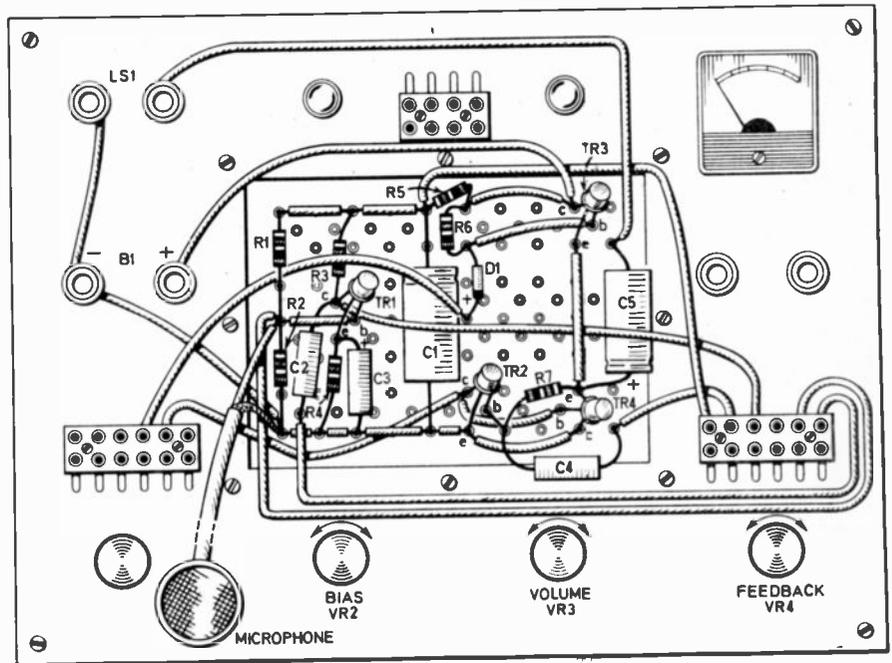

the microphone input should we so wish. In fact there is plenty of unrequired gain in hand. We can make use of this to add in a couple of refinements.

VOLUME CONTROL AND SELECTIVE FEEDBACK

The simplest is a volume control—shown as VR3 (of the Demo Deck) in parallel with a 22 kilohm collector load for TR1—that enables us to “tap off” lower proportions of variations in TR1’s collector potential. As this would affect the bias of TR2 we have to decouple the d.c. link between the wiper of VR3 and TR2’s base; this is done with capacitor C4 (we have introduced a.c. coupling).

There is still some gain in hand so we can introduce some frequency selective negative feedback between the collector and base of TR1 (with the aid of C2 and VR4). When VR4 is set to a high resistance value, very little feedback occurs and our signal strength will be high; by reducing the value of this potentiometer some feedback will take place but only at high frequencies (C2 still acts as a very high resistance to low frequencies). The more you decrease the value of VR4, the more you will suppress high frequencies and hence counter the rather poor frequency response we had previously—speech will become more “bassy” and appear to have more “body.” It may be necessary to increase the volume control to get the best effect.

DECOUPLING

The resistor/capacitor combination, R5 and C1, form what is called a **decoupler**; this prevents any variations in power line voltage caused by high currents being drawn through the output transistors affecting the first **amplifier stage**. Without these components the whole system could be subject to **positive feedback**, become unstable and oscillate—take them out and see!

SETTING UP THE AMPLIFIER


When setting up the amplifier, start with VR2 at minimum value and slowly increase it while speaking quietly into the microphone. You should initially hear the effect of cross over distortion (it is better heard than described) but stop increasing its value as soon as the distortion disappears. In normal circuits VR2 would be a preset component and VR4 would be of a fixed value determined by the designer.

The little loudspeaker in Demo Deck does not really do justice to this circuit and is of rather too high an impedance to get maximum power. If you have a larger 8 ohm loudspeaker try this in its place—you'll probably be very surprised with the difference. There is no reason why you should not replace the microphone with a crystal pick-up and make a record player amplifier.

LAST WORDS

We've come a long way since the "plumbing" in Part 2 and we hope you have been able to follow us. The subject is only a hobby but it can be great fun if you know some of the inside stories rather than "construct-in-the-dark."

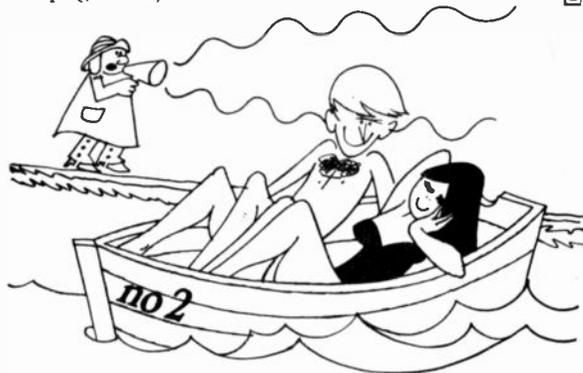You will find many more articles in months to come which will help fill some of the gaps and also venture on new territory. Ultimately the only way to become proficient at electronics is to make things, have successes and have failures but if you have a failure do not give up in disgust, try and find out what went wrong. Why not round off with the "End of Term Test" on page 670). □



Ruminations By Sensor

Having A Nose For It

I once knew a man (I'll call him John) who had an uncanny knack for fault diagnosis. He was not highly trained in electronics but had grown up with the science and accumulated a vast store, a practical experience which enabled him to find faults very quickly with a minimum of testing. When I first met John, he was working on Radar equipment but he had previously worked on domestic radio servicing; he transferred apparently without any difficulty to television fault diagnosis.

Although his theoretical knowledge was limited, his talent for quick diagnosis was admired and respected by all—even the most senior engineers. It must be remembered that he was dealing with new equipment straight from the production lines—receivers that had never worked before;

wiring faults and components of the wrong type and value made the business more complicated than normal servicing work.

Every engineer acquires this "instinct" for fault diagnosis, to a greater or lesser degree. It is an amalgam of keen observation, knowledge of components and their behaviour, the "stock" faults of various models—and a good memory. These factors do not compensate for lack of a sound knowledge of basic theory, which properly applied, will enable one to diagnose any fault, though probably not as quickly as John would have found it. A good beginner's series can help those who already have some "instinct" to develop their theory whilst those without either theoretical knowledge or "instinct" can quickly learn sufficient theory to enable them to begin to acquire an "instinct."


One-Upmanship

I once gained some kudos myself by using my required "instinct." I was watching a computer engineer who was looking for a fault. He had isolated the

trouble to one particular circuit board and had removed this board from the computer. While he collected together his tools, test-meter circuit diagram and wiring diagram of the particular board in preparation for detailed investigation, I picked up the board and idly glanced over it.

One resistor looked just a shade brighter in colour than the rest, I looked more closely and saw that the thin wax coating, that used to be applied to resistors in those days, was just beginning to soften. "Is that resistor the correct value?" I asked. We looked on the circuit diagram and found that the resistor ought to have been 470 kilohm; it was in fact 47 kilohm and was correctly colour coded. The computer engineer was most impressed!

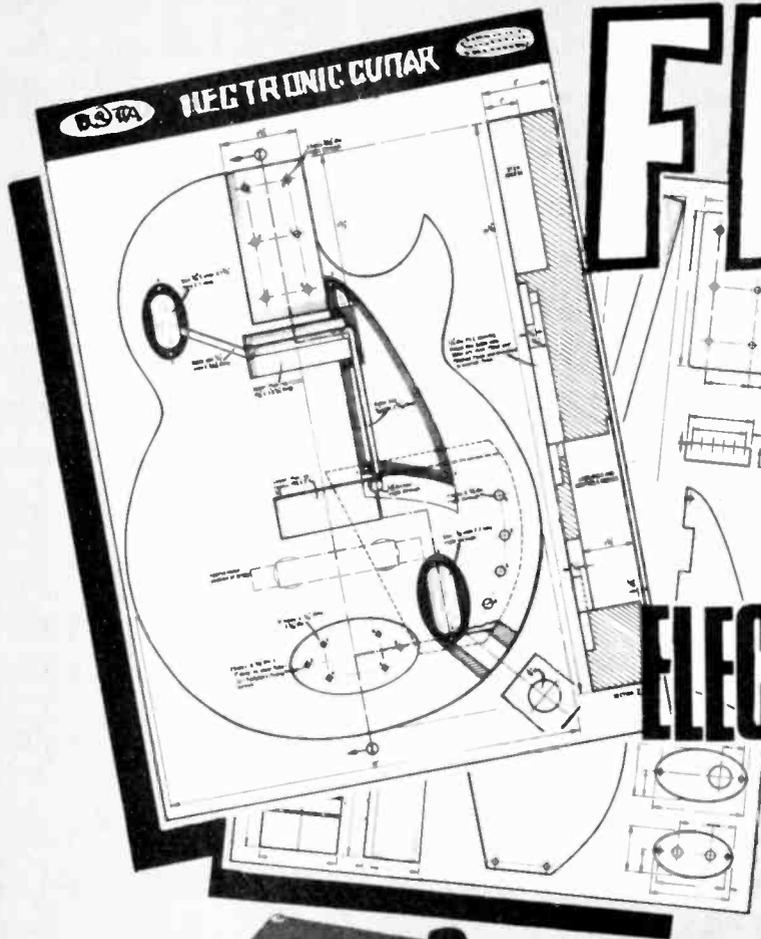Somewhere along the line the colour coding had been misinterpreted (orange and yellow can be quite close together in shade) and although there was not much current flowing in the circuit concerned, a change in resistor value of 10 times was sufficient to produce very slight overheating in the resistor and give me a clue to the trouble.



FREE!

IN THE NOV ISSUE BLUEPRINT FOR ELECTRONIC GUITAR

This double sided blueprint showing the construction of the Beta guitar combines with two articles to detail a modern solid guitar incorporating two electronic effects units.



TRANSISTOR TESTER

How often have you built a circuit only to find that it does not work. With the simple Transistor Tester you can quickly check most transistors and thus eliminate the use of "duds".

ALSO...

PART 1 OF A NEW BEGINNERS SERIES BASIC ELECTRICITY



Just PART of the
NOVEMBER Issue of
ON SALE OCTOBER 20



THE Electronic Mouse Trap described herein does not kill or injure a captured mouse. It catches the mouse alive so that it may be released in the local park or a field. This satisfies the R.S.P.C.A. and wildlife preservationists and all others opposed to "blood sports". Only the cats will be unhappy at the risk of being made redundant.

The trap has been well proven in use and has caught six mice during a few weeks of operation. Certain modifications have been made to the prototype due to the annoying habit of the mice to chew the connecting wires inside the trap.

PRINCIPLE OF OPERATION

The principle of operation is quite simple, although the trap may look a little complicated mechanically. The "electronics" consist of a

photo-conductive cell which operates a simple d.c. amplifier (Fig. 1), this in turn energising a solenoid (L1).


When the solenoid is energised it releases the door retaining spring. The door then promptly closes and at the same time switches off the supply via S1. The sequence is set off by the mouse which, on entering the trap to gain access to the "bait", carefully placed inside at the far end, has to pass through a beam of light shining on the photocell PCC1 from LP1. When the light beam is interrupted the photocell resistance increases and actuates the d.c. amplifier and solenoid.

There are only two ways, well three really, in which a mouse can evade being captured. One, if the mains supply fails or is switched off, two, it could jump over the beam of light or three, just not enter the trap anyway.

A proven design for a humane mouse trap.

By F. C. Judd

Electronic MOUSETRAP

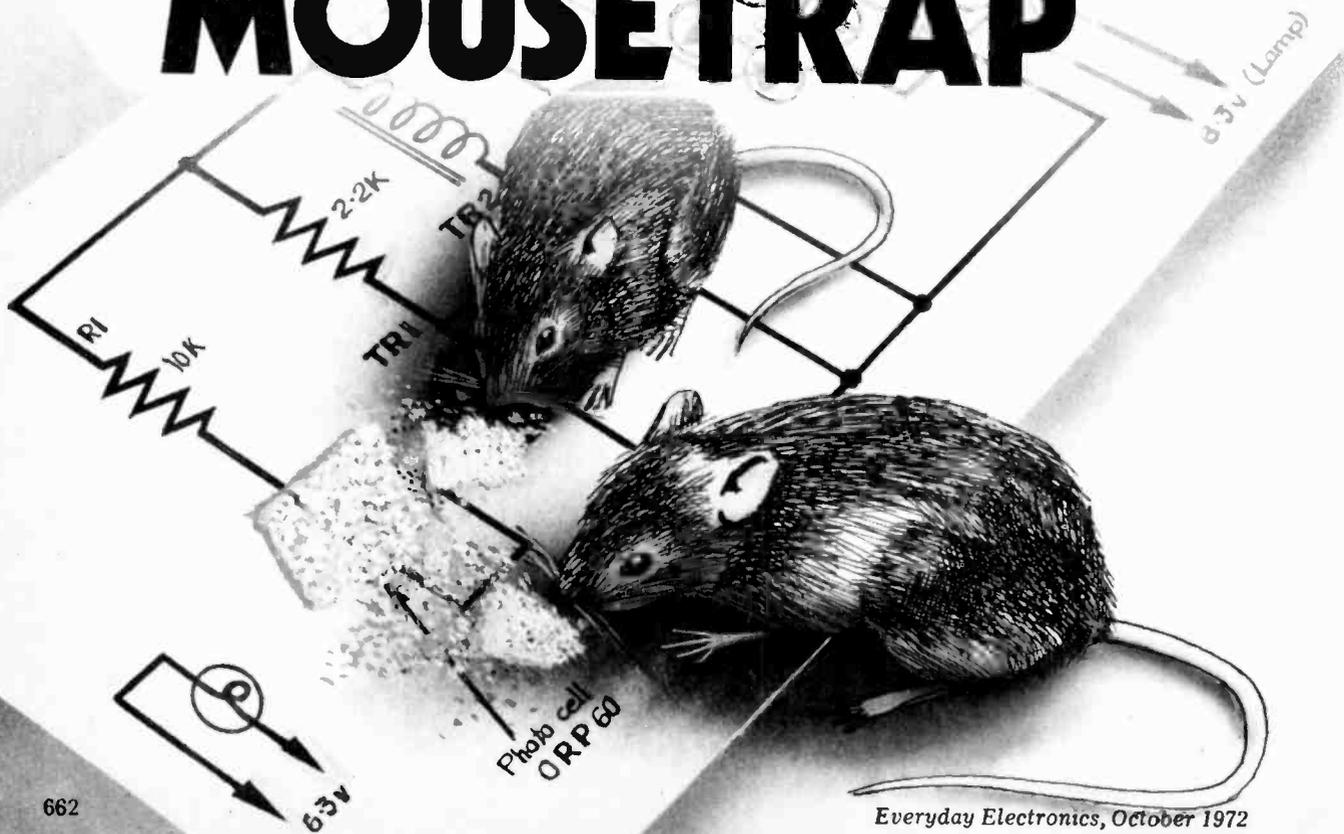

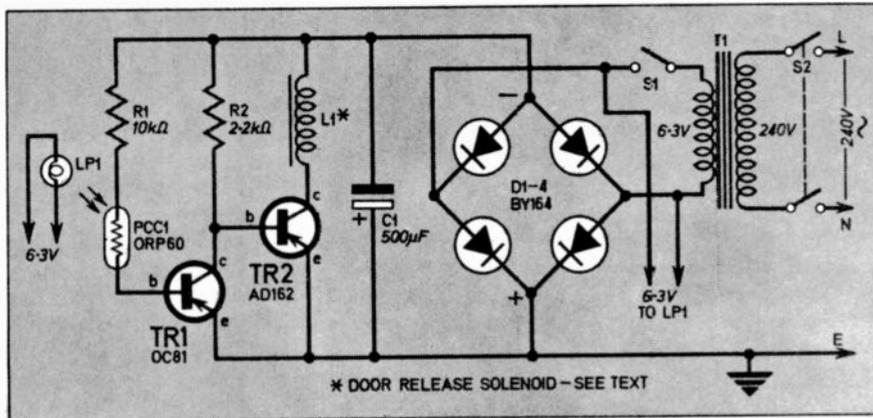


Fig. 1. Complete circuit diagram of the Electronic Mouse Trap.

CONSTRUCTION

The box can be made from hardboard or thin plywood with sides and top etc., held together with half-inch by half-inch battens pinned or glued. Details for the box are given in Fig. 2. Note that a hole is drilled each side of the box about $\frac{3}{4}$ in up from the bottom. These holes allow the light from the external 6.3V lamp (LP1) to shine through and across the box to the photocell opposite.

The trap door can be made from Perspex which enables one to see if a mouse has been caught. It could otherwise be made from hardboard but drill some holes in the door otherwise a caught mouse could die of suffocation!

It has been found that in an effort to escape the mice chew the wooden batten around the door so it is best to make these of the half-inch batten specified. The mice do not seem to want to chew the plywood sides.

The d.c. amplifier and power supply components are mounted on the aluminium panel that forms the rear end of the box and are separated from the captured mouse by an inner dividing wall. Without this wall a mouse could get to the mains supply and possibly electrocute itself.

The amplifier circuit is shown in Fig 1 and consists simply of a d.c. coupled pair of transistors but note that TR2 passes a large current when the light beam is interrupted. It is for this reason and because no heatsink is provided for TR2, that a contact (S1), operated by the door, opens and cuts off the secondary voltage of the transformer T1 when the door is closed. This also switches off the light, thus saving current when the trap has done its job.

SOLENOID



The solenoid is fairly easy to make and really amounts to a coil of wire with a steel bolt as the electromagnet. Details are given in Fig. 3.

The coil cheeks could be any insulating material, even stiff cardboard and the coil itself consists of enough 32 swg enamelled wire to

build up a winding of about $\frac{3}{4}$ in diameter between the cheeks that are fixed one inch apart on a $\frac{1}{4}$ in steel bolt. The d.c. resistance of the winding will be in the region of 20 to 30 ohms.

To make the solenoid cut out two discs 1 inch diameter for the end cheeks and drill two holes in one as shown in Fig. 3. Slide these cheeks onto the bolt—the undrilled one first—and screw on a nut so that the two discs are one inch apart.

Using 32 s.w.g. enamelled copper wire, pass one end out through the inner hole, cover the outer end with sleeving and with the uncovered wire wind on the turns evenly along the length

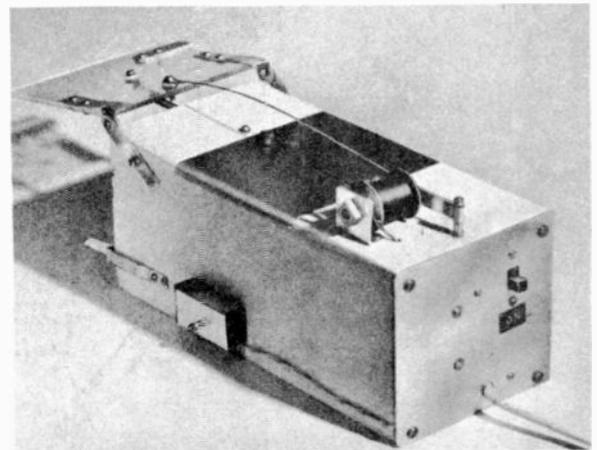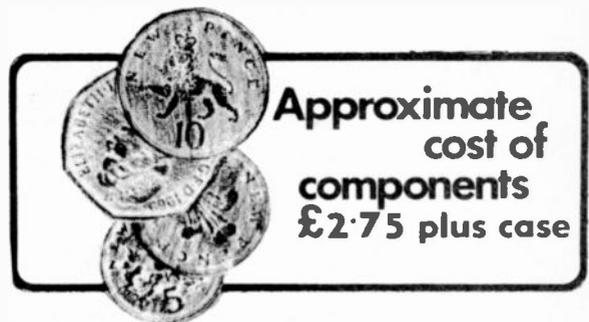


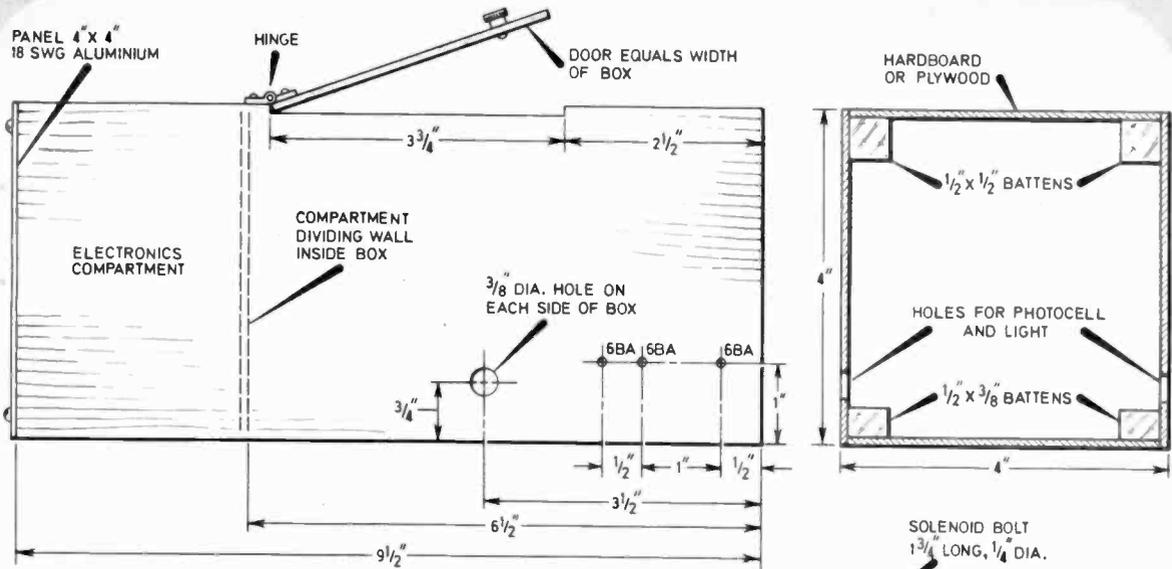
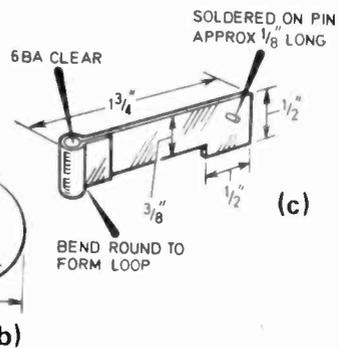


Fig. 2 (above). Details and dimensions of the wooden box as used for the prototype mousetrap showing the electronics compartment at the rear of the unit.

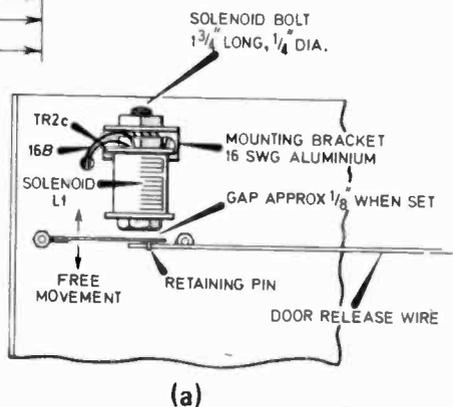

Electronic MOUSETRAP

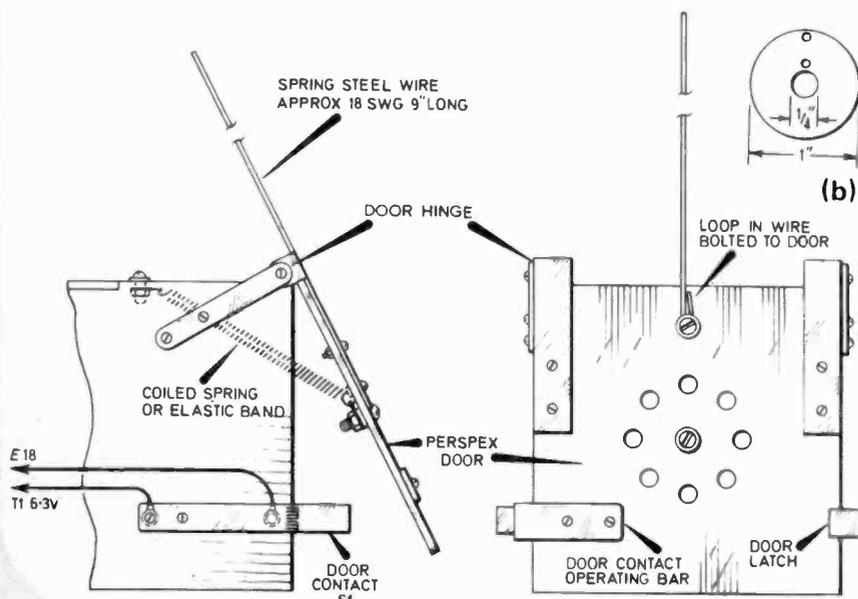


Fig. 3 (above) (a) A plan view of the solenoid arrangement on top of the unit. (b) Shows the dimensions of the cardboard cheeks of the solenoid. (c) Details of the operating arm.

Fig. 4 (left) Shows details of the Perspex door, door fittings and S1.

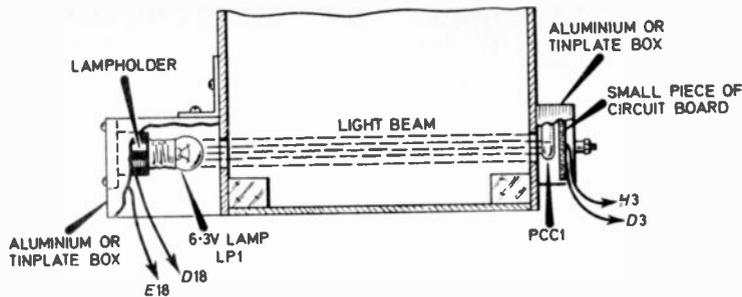


Fig. 5. The mounting and wiring of the lamp and photocell.

of the solenoid, layer upon layer until the winding is approximately $\frac{3}{4}$ in in diameter. Pass the other end of the wire through the outer hole, sleeve the wire and secure the winding with insulation tape.

The operating arm, which releases the door retaining wire must be made from tinfoil or thin mild steel. A piece cut from an empty tin box will do. A vertical loop is formed at one end as shown in Fig. 3, just large enough to slide over a 6BA screw which will form a bearing for the arm. The position of the arm relative to the solenoid is shown in Fig. 3.

TRAP DOOR

The door is hinged as shown in Fig. 4 and held closed by a light tension coil spring or an elastic band. The tension must not be too great but sufficient to bring the door down smartly from a near horizontal position so that it latches.

Attached to the middle of the door is a piece of springy steel wire long enough to reach back so that the end can be hooked under the pin on the solenoid arm (see Fig. 3). When the solenoid is energized the arm moves in and the door retaining wire is released.

When the door comes down it must break the contact which forms S1, this disconnects one side of the transformer secondary winding from the rectifier and the lamp. Details for the contact are given in Fig. 4 and the position of its operating bar is also shown.

The door fittings can be made from light gauge aluminium but the door contact must be springy i.e., made from tinfoil or thin brass. When the door is open the contact must make with the 6BA bolt on the side of the box as in Fig. 4.

Two wires, one from the contact and one from the bolt are taken along the outside of the box to the transformer and circuit board at the rear. The wires should not pass inside the trap as they will soon be chewed away by the captive mice. The door is also fitted with a simple latch to prevent the mouse from pushing it open and escaping.

LAMP AND PHOTOCCELL

The photocell is a type ORP60 which has its

sensitive element near the top end so this end must be in the light beam as in Fig. 5. The lamp housing consists simply of a small three sided box just large enough to take an MES lamp-holder (Fig. 5). This is bolted onto the side of the box so that the lamp is in line with the hole and adjusted so that maximum light will shine across onto the photocell.


The photocell can be mounted on a small piece of plain circuit board so that the light sensitive end "looks into the box" through the hole. This small assembly is attached to the outside of the box.

It is important that the holes in the box are not too large as the mice may tend to chew the surrounding wood.

AMPLIFIER

The two transistors and remaining com-

Fig. 6. Layout and wiring of the components mounted on the circuit board.

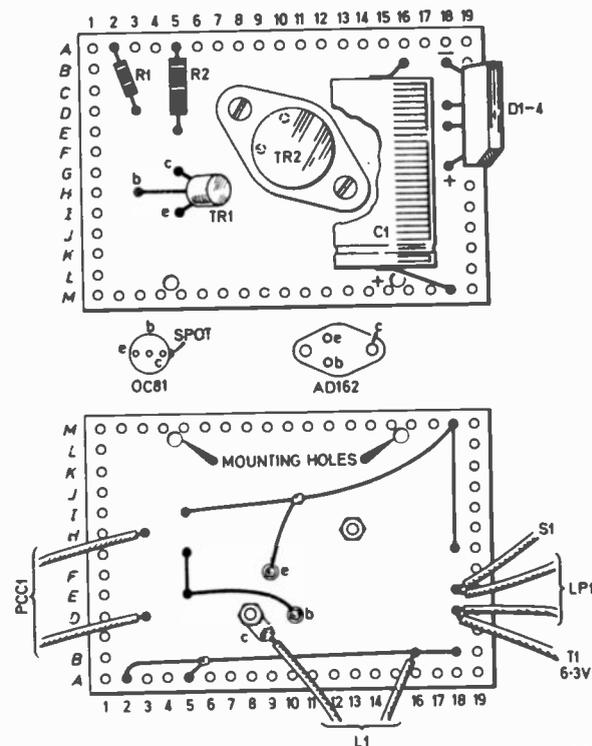

ponents, including the bridge rectifier, are mounted and wired on a piece of plain circuit board as shown in Fig. 6. Mount all the components on the circuit board after it has been cut to size and the mounting holes drilled. Solder the connections, using a heat shunt on the transistor leads and connect up the flying leads.

Leads are taken to the door switch (S1), lamp, photocell and to the solenoid as shown in Fig. 6. Note that the transformer T1 is a 6·3V 1 amp heater type. This transformer is mounted directly on the rear panel together with the circuit board and the mains switch as shown in Fig. 7. It is important that the aluminium panel is earthed via the mains lead.


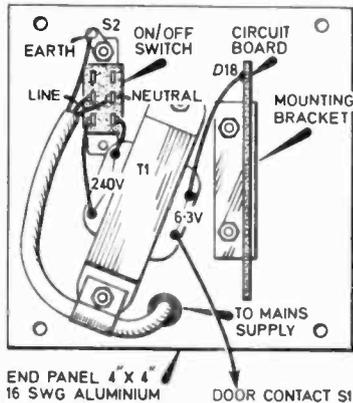


Fig. 7. Wiring of the components on the panel.

OPERATION

The trap door is set by releasing the catch, lifting it to a horizontal position and retaining it by hooking the long stiff wire under the pin on the solenoid arm. Check that it will release by pushing the arm in towards the face of the solenoid. Only slight pressure should be required.

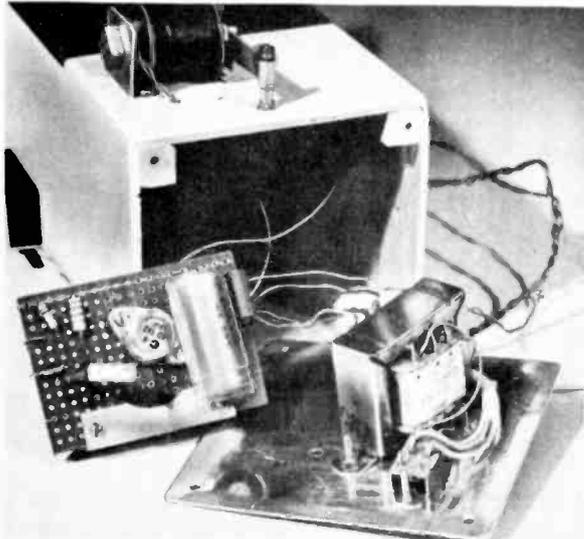Now switch on the amplifier, re-set the door, and check that the lamp lights when the door



Components....

Resistors

R1 10k Ω
R2 2·2k Ω } $\frac{1}{4}$ W \pm 10% carbon

Capacitor

C1 500 μ F elect. 12V

Semiconductors

PCC1 ORP60 photo conductive cell
D1-4 BY164 bridge rectifier or similar
IA 50 p.i.v. bridge
TR1 OC81 germanium pnp
TR2 AD162 germanium pnp


Miscellaneous

LP1 6V 0·2A bulb and holder
L1 32 s.w.g. enamelled copper wire wound on $\frac{1}{4}$ in \times 1 $\frac{1}{4}$ in steel bolt (see text).
S1 Door contact switch (see text)
S2 D.p.s.t. mains switch, slide or toggle
T1 6·3V 1A secondary mains transformer

Materials for case, door hinges, door latch, LP1 and PCC1 mounting boxes, solenoid arm, door retaining spring and end mounting panel (see text). Plain perforated Veroboard 3in \times 2 $\frac{1}{2}$ in \times 0·15in matrix, $\frac{1}{2}$ in \times $\frac{1}{2}$ in \times 2in aluminium angle for mounting bracket, mains lead and three pin plug, connecting wire, 6BA and 4BA fixings.

is in the retained position. Providing the photocell is fully illuminated the arm will not move, indicating that TR2 is cut off. Try rolling a cotton reel into the box to interrupt the light beam. This should cause the solenoid arm to move, release the retaining wire and allow the door to instantly close. At the same time the door contact S1 will open and cut off the supply voltage to the amplifier and lamp.

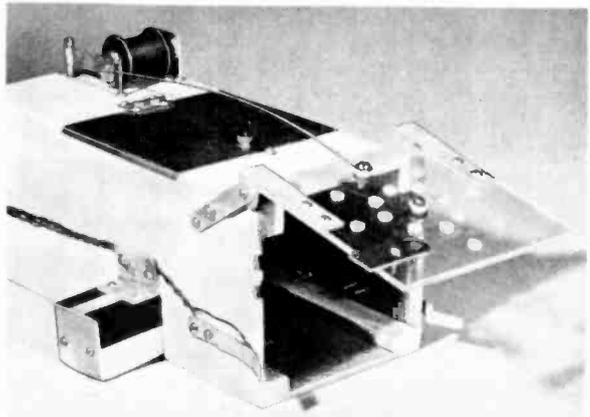With the door closed the lamp must go out. Should the door contact fail to break the circuit do not leave the amplifier operating as TR2 will be passing a large current and may destroy itself. Make sure that the light always goes out when the trap door closes. \square



BRAND NEW GUARANTEED

LARGEST SELECTION OF SEMICONDUCTORS COMPONENTS

RETURN OF POST SERVICE

TRANSISTORS

| | | | | |
|--------------|---------------|-------------|-------------|---------------|
| 2G301 0-15 | 2N3854 0-16 | BC108 0-11 | BFY50 0-16 | NKT613P 0 30 |
| 2G302 0-15 | 2N3854A 0-16 | BC109 0-12 | BFY51 0-16 | NKT674P 0 24 |
| 2G303 0-25 | 2N3855 0-16 | BC110 0-12 | BFY52 0-16 | NKT777P 0 32 |
| 2G306 0-30 | 2N3855A 0-16 | BC115 0-16 | BFY53 0-15 | NKT771S 0 30 |
| 2G309 0-30 | 2N3856 0-16 | BC116 0-16 | BFY56 0-34 | NKT771T 0 44 |
| 2G371 0-15 | 2N3856A 0-16 | BC116A 0-16 | BFY75 0-40 | NKT781 0 30 |
| 2G374 0-15 | 2N3858 0-16 | BC118 0-11 | BFY76 0-22 | NKT10419 0 30 |
| 2G381 0-25 | 2N3858A 0-16 | BC121 0-20 | BFY77 0-24 | NKT10439 0 30 |
| 2N404 0-25 | 2N3859 0-16 | BC125 0-15 | BFY90 0-45 | NKT10519 0 27 |
| 2N491 0-15 | 2N3859A 0-16 | BC126 0-20 | BFY39 0-38 | NKT20329 0 23 |
| 2N497 0-15 | 2N3860 0-16 | BC140 0-30 | B8X19 0-13 | NKT20339 0 36 |
| 2N498 0-25 | 2N3866 0-70 | BC147 0-10 | B8X20 0-14 | NKT80111 0 67 |
| 2N706 0-10 | 2N3877 0-25 | BC148 0-10 | B8X21 0-20 | NKT80112 0 84 |
| 2N708 0-13 | 2N3877A 0-25 | BC149 0-11 | B8X26 0-20 | NKT80113 0 84 |
| 2N709 0-26 | 2N3900 0-20 | BC157 0-09 | B8X27 0-24 | NKT80211 0 75 |
| 2N718 0-21 | 2N3900A 0-21 | BC158 0-10 | B8X28 0-25 | NKT80212 0 75 |
| 2N719 0-15 | 2N3901 0-22 | BC159 0-10 | B8X60 0-54 | NKT80215 0 75 |
| 2N816 0-17 | 2N3903 0-22 | BC160 0-11 | B8X61 0-15 | NKT80216 0 75 |
| 2N818 0-10 | 2N3904 0-22 | BC167B 0-11 | B8X77 0-15 | NKT80216 0 75 |
| 2N929 0-24 | 2N3905 0-21 | BC168B 0-10 | B8X78 0-20 | NKT80216 0 75 |
| 2N930 0-14 | 2N3906 0-22 | BC169C 0-11 | B8X79 0-25 | NKT80216 0 75 |
| 2N1090 0-30 | 2N4058 0-13 | BC169B 0-11 | B8Y24 0-30 | NKT80216 0 75 |
| 2N1091 0-22 | 2N4059 0-30 | BC170 0-11 | B8Y25 0-20 | NKT80216 0 75 |
| 2N1181 0-20 | 2N4060 0-11 | BC171 0-13 | B8Y26 0-20 | NKT80216 0 75 |
| 2N1192 0-20 | 2N4061 0-11 | BC172 0-11 | B8Y27 0-15 | NKT80216 0 75 |
| 2N1184 1-27 | 2N4062 0-11 | BC182 0-10 | B8Y28 0-15 | NKT80216 0 75 |
| 2N1302 0-16 | 2N4303 0-33 | BC182 0-10 | B8Y29 0-15 | NKT80216 0 75 |
| 2N1303 0-16 | 2N5172 0-09 | BC183 0-09 | B8Y39 0-15 | NKT80216 0 75 |
| 2N1304 0-20 | 2N5174 0-23 | BC184 0-11 | B8Y51 0-25 | NKT80216 0 75 |
| 2N1305 0-20 | 2N5175 0-23 | BC185 0-11 | B8Y52 0-25 | NKT80216 0 75 |
| 2N1306 0-22 | 2N5176 0-23 | BC186 0-11 | B8Y53 0-25 | NKT80216 0 75 |
| 2N1307 0-22 | 2N5245 0-43 | BCY31 0-40 | B8Y54 0-30 | NKT80216 0 75 |
| 2N1308 0-25 | 2N5459 0-33 | BCY32 0-40 | B8Y55 0-79 | NKT80216 0 75 |
| 2N1309 0-25 | 3N128 0-33 | BCY33 0-30 | B8Y76 0-40 | NKT80216 0 75 |
| 2N1507 0-30 | 3N140 0-76 | RCY34 0-35 | B8Y77 0-40 | NKT80216 0 75 |
| 2N1613 0-30 | 3N141 0-69 | RCY35 0-30 | B8Y78 0-40 | NKT80216 0 75 |
| 2N1681 0-35 | 3N142 0-64 | BCY39 0-60 | B8Y90 0-45 | NKT80216 0 75 |
| 2N1686 0-35 | 3N143 0-64 | BCY40 0-50 | B8Y96A 0-60 | NKT80216 0 75 |
| 2N1688 0-35 | 3N152 0-70 | BCY42 0-15 | C111 0-03 | NKT80216 0 75 |
| 2N1711 0-17 | | BCY43 0-15 | C424 0-15 | NKT80216 0 75 |
| 2N1893 0-34 | | RCY58 0-18 | C425 0-35 | NKT80216 0 75 |
| 2N2147 0-40 | | RCY59 0-18 | C426 0-35 | NKT80216 0 75 |
| 2N2148 0-70 | | BCV70 0-17 | C428 0-25 | NKT80216 0 75 |
| 2N2193 0-48 | | BCV71 0-22 | GET113 0-25 | NKT80216 0 75 |
| 2N2193A 0-61 | | BCV72 0-18 | GET114 0-20 | NKT80216 0 75 |
| 2N2194A 0-30 | 40050 0-50 | BCZ10 0-35 | GET119 0-35 | NKT80216 0 75 |
| 2N2219 0-20 | 40251 0-53 | BCZ11 0-50 | GET120 0-40 | NKT80216 0 75 |
| 2N2220 0-20 | 40309 0-26 | BD116 0-75 | GET873 0-15 | NKT80216 0 75 |
| 2N2221 0-20 | 40310 0-37 | BD121 0-75 | GET890 0-35 | NKT80216 0 75 |
| 2N2222 0-20 | 40380 0-25 | BD123 0-22 | GET897 0-30 | NKT80216 0 75 |
| 2N2222A 0-33 | 40381 0-37 | BD124 0-60 | GET898 0-35 | NKT80216 0 75 |
| 2N2368 0-11 | 40382 0-40 | BD131 0-75 | MJ400 0-78 | NKT80216 0 75 |
| 2N2369 0-12 | 40406 0-40 | BD132 0-75 | MJ420 0-85 | NKT80216 0 75 |
| 2N2369A 0-17 | 40407 0-21 | BDY10 1-25 | MJ421 0-88 | NKT80216 0 75 |
| 2N2046 0-45 | 40408 0-41 | BDY11 1-25 | MJ430 0-75 | NKT80216 0 75 |
| 2N2711 0-18 | 40410 0-58 | BDY17 1-50 | MJ440 0-71 | NKT80216 0 75 |
| 2N2712 0-13 | 40467A 0-57 | BDY18 1-75 | MJ480 0-75 | NKT80216 0 75 |
| 2N2713 0-17 | 40468 0-55 | BDY19 1-97 | MJ481 0-65 | NKT80216 0 75 |
| 2N2714 0-17 | AC107 0-35 | BDY20 1-00 | MJ490 0-75 | NKT80216 0 75 |
| 2N2904 0-18 | AC126 0-20 | BDY38 0-65 | MJ491 1-10 | NKT80216 0 75 |
| 2N2904A 0-29 | AC127 0-20 | BDY69 0-90 | MJ5340 0-47 | NKT80216 0 75 |
| 2N2905 0-26 | AC128 0-20 | BDY61 0-85 | MJ520 0-55 | NKT80216 0 75 |
| 2N2905A 0-26 | AC154 0-20 | BDY62 0-75 | MJ520 0-55 | NKT80216 0 75 |
| 2N2906 0-18 | AC176 0-16 | BF115 0-25 | MJ520 0-55 | NKT80216 0 75 |
| 2N2906A 0-28 | AC177 0-16 | BF117 0-43 | MJ520 0-55 | NKT80216 0 75 |
| 2N2907 0-18 | ACY18 0-15 | BF163 0-20 | MPP104 0-33 | NKT80216 0 75 |
| 2N2923 0-18 | ACY19 0-20 | BF164 0-20 | MPP105 0-33 | NKT80216 0 75 |
| 2N2924 0-18 | ACY20 0-20 | BF167 0-18 | MPP124 0-43 | NKT80216 0 75 |
| 2N2925 0-18 | ACY21 0-18 | BF173 0-18 | NKT128 0-38 | NKT80216 0 75 |
| 2N2926 0-18 | ACY22 0-18 | BF177 0-25 | NKT128 0-38 | NKT80216 0 75 |
| 2N2928 0-18 | ACY23 0-18 | BF178 0-21 | NKT135 0-26 | NKT80216 0 75 |
| 2N2928A 0-18 | ACY28 0-18 | BF179 0-28 | NKT137 0-28 | NKT80216 0 75 |
| Green 0-10 | ACY40 0-17 | BF180 0-35 | NKT210 0-26 | NKT80216 0 75 |
| Yellow 0-10 | ACY41 0-17 | BF181 0-35 | NKT211 0-25 | NKT80216 0 75 |
| Orange 0-10 | ACY42 0-17 | BF182 0-35 | NKT212 0-25 | NKT80216 0 75 |
| 2N3052 0-15 | AD140 0-55 | BF185 0-17 | NKT213 0-25 | NKT80216 0 75 |
| 2N3054 0-47 | AD148V 1-23 | BF186 0-17 | NKT214 0-15 | NKT80216 0 75 |
| 2N3055 0-60 | AD150 0-55 | BF190 0-14 | NKT215 0-21 | NKT80216 0 75 |
| 2N3090 0-30 | AD161 0-20 | BF195 0-15 | NKT216 0-46 | NKT80216 0 75 |
| 2N3391 0-20 | AD162 0-36 | BF196 0-15 | NKT217 0-50 | NKT80216 0 75 |
| 2N3391A 0-22 | AD161 PR 0-80 | BF198 0-18 | NKT219 0-25 | NKT80216 0 75 |
| 2N3392 0-13 | AD162 0-80 | BF200 0-40 | NKT223 0-17 | NKT80216 0 75 |
| 2N3393 0-12 | AP106 0-24 | BF224J 0-14 | NKT224 0-25 | NKT80216 0 75 |
| 2N3394 0-12 | AP111 0-25 | BF256J 0-19 | NKT225 0-21 | NKT80216 0 75 |
| 2N3402 0-17 | AP112 0-25 | BF257 0-22 | NKT229 0-29 | NKT80216 0 75 |
| 2N3403 0-19 | AP116 0-25 | BF259 0-22 | NKT237 0-31 | NKT80216 0 75 |
| 2N3404 0-24 | AP117 0-20 | BF244 0-16 | NKT238 0-18 | NKT80216 0 75 |
| 2N3405 0-27 | AP118 0-50 | BFX13 0-22 | NKT240 0-19 | NKT80216 0 75 |
| 2N3414 0-10 | AP124 0-24 | BFX19 0-22 | NKT241 0-20 | NKT80216 0 75 |
| 2N3415 0-10 | AP125 0-20 | BFX29 0-25 | NKT242 0-15 | NKT80216 0 75 |
| 2N3416 0-15 | AP126 0-20 | BFX30 0-25 | NKT243 0-33 | NKT80216 0 75 |
| 2N3417 0-21 | AP127 0-20 | BFX44 0-33 | NKT244 0-17 | NKT80216 0 75 |
| 2N3570 1-25 | AP139 0-33 | BFX68 0-30 | NKT245 0-18 | NKT80216 0 75 |
| 2N3572 0-97 | AP178 0-55 | BFX84 0-24 | NKT246 0-21 | NKT80216 0 75 |
| 2N3702 0-11 | AP179 0-65 | BFX86 0-24 | NKT262 0-19 | NKT80216 0 75 |
| 2N3703 0-10 | AP180 0-50 | BFX87 0-27 | NKT264 0-21 | NKT80216 0 75 |
| 2N3704 0-11 | AP211 0-55 | BFX89 0-25 | NKT271 0-18 | NKT80216 0 75 |
| 2N3705 0-10 | AP239 0-36 | BFX98 0-45 | NKT272 0-18 | NKT80216 0 75 |
| 2N3706 0-10 | AP279 0-47 | BFY10 0-35 | NKT374 0-18 | NKT80216 0 75 |
| 2N3707 0-11 | AP280 0-47 | BFY11 0-35 | NKT375 0-22 | NKT80216 0 75 |
| 2N3708 0-70 | AP280 0-47 | BFY19 0-35 | NKT401 0-70 | NKT80216 0 75 |
| 2N3709 0-90 | AP280 0-47 | BFY20 0-50 | NKT402 0-76 | NKT80216 0 75 |
| 2N3710 0-90 | AP280 0-47 | BFY29 0-40 | NKT403 0-85 | NKT80216 0 75 |
| 2N3711 0-90 | AP280 0-47 | BFY41 0-43 | NKT404 0-81 | NKT80216 0 75 |
| 2N3715 1-22 | AP280 0-47 | BFY43 0-85 | NKT406 0-30 | NKT80216 0 75 |
| 2N3716 1-30 | AP280 0-47 | | | NKT80216 0 75 |
| 2N3791 2-06 | AP280 0-47 | | | NKT80216 0 75 |
| 2N3819 0-26 | AP280 0-47 | | | NKT80216 0 75 |
| 2N3823 0-26 | AP280 0-47 | | | NKT80216 0 75 |

Post & Packing 13p per order. Europe 25p. Commonwealth (Air) 65p (MIN.)
 Matching charge (audio transistors only) 15p extra per pair.
 Prices subject to alteration without prior notice.

TTL LOGIC I.C. NEW PRICES

| 1-11 15-24 | | 1-11 15-24 | | 1-11 15-24 | |
|------------|------|------------|------|------------|------|
| 1p | 2p | 1p | 2p | 1p | 2p |
| SN7400 | 0 20 | SN7433 | 0 80 | SN7472 | 0 33 |
| SN7401 | 0 20 | SN7434 | 0 80 | SN7473 | 0 33 |
| SN7402 | 0 20 | SN7438 | 0 80 | SN7474 | 0 33 |
| SN7403 | 0 20 | SN7440 | 0 33 | SN7475 | 0 33 |
| SN7405 | 0 20 | SN7441A | 0 87 | SN7476 | 0 33 |
| SN7406 | 0 30 | SN7442 | 0 85 | SN7480 | 0 70 |
| SN7407 | 0 20 | SN7443 | 0 86 | SN7481 | 1 40 |
| SN7408 | 0 20 | SN7444 | 0 86 | SN7482 | 0 87 |
| SN7409 | 0 20 | SN7445 | 0 86 | SN7483 | 0 87 |
| SN7410 | 0 20 | SN7446 | 1 00 | SN7484 | 2 00 |
| SN7411 | 0 22 | SN7447 | 1 00 | SN7485 | 3 00 |
| SN7412 | 0 48 | SN7448 | 1 00 | SN7486 | 3 33 |
| SN7413 | 0 40 | SN7449 | 1 00 | SN7490 | 0 87 |
| SN7420 | 0 20 | SN7450 | 0 20 | SN7491A | 1 21 |
| SN7423 | 0 51 | SN7451 | 0 20 | SN7492 | 0 87 |
| SN7427 | 0 48 | SN7453 | 0 20 | SN7493 | 0 87 |
| SN7428 | 0 30 | SN7454 | 0 20 | SN7494 | 0 87 |
| SN7430 | 0 22 | SN7460 | 0 20 | SN7495 | 0 87 |
| SN7432 | 0 48 | SN7470 | 0 40 | SN7496 | 0 87 |

SUB-MIN ELECTROLYTIC

range axial lead 6p each
 Value: (µF/V): 0-64/64; 1/40; 1-6/25; 2-5/10; 2-2/63; 4/10; 4/40;
 6-4/6; 6-4/25; 10/16; 10/64; 16/40; 20/16; 20/64; 25/6-4; 25/25; 32/10;
 32/40; 32/64; 40/16; 50/6-4; 50/25; 50/40; 64/10; 80/16; 80/25; 100/6-4;
 125/10; 125/16; 320/6-4.

SILICON RECTIFIERS

| PIV | 50 | 100 | 200 | 400 | 600 | 800 | 1000 | 1200 |
|-----|-----|-----|-----|--------|--------|--------|--------|------|
| 1A | 8p | 9p | 10p | 11p | 12p | 15p | 30p | — |
| 3A | 17p | 17p | 20p | 25p | 25p | 27p | 30p | 35p |
| 6A | — | — | 25p | 30p | 32p | 35p | — | — |
| 10A | 30p | 35p | 40p | 47p | 55p | 65p | 75p | — |
| 15A | 35p | 45p | 48p | 55p | 65p | 75p | — | — |
| 35A | 70p | 80p | 90p | \$1.00 | \$1.40 | \$1.70 | \$3.75 | — |

1 amp and 3 amp are plastic encapsulation.

DIODES & RECTIFIERS

| | | | | |
|-------|-----|-------|----|-----|
| IN34A | 10p | AA119 | 7p | BAX |
|-------|-----|-------|----|-----|

GSPK (sales)

quite simply-the best

RESISTORS

FULL RANGE OF CARBON FILM RESISTORS

1/5 W (range 4.7 ohms to 470K) 1p each
 1/2 W and 1/2 W (range 4.7 ohms to 10 Mega) 1p each
 1 W (range 4.7 ohms to 10 Meg) 5p each
 2 W (range 4.7 ohms to 10 Meg) 8p each

These Miniature High Stability carbon Film Resistors have negligible noise factor.

All Resistors $\pm 5\%$ (except values over 47 Meg). These Resistors are even lower in price than most 10% and older carbon composition types.

PRE-SET POTENTIOMETERS

Standard values of pre-sets from 100 ohms to 5 Meg. Standard/miniature 7p each Sub-miniature 5p each

SIEMENS PROFESSIONAL CAPACITORS

| Voltage | Capacitance | Price | Voltage | Capacitance | Price |
|---------|--------------|-------|---------|--------------|-------|
| 100v | 0.1 μ F | 6p | 10v | 22 μ F | 7p |
| 100v | 0.15 μ F | 6p | 10v | 47 μ F | 11p |
| 100v | 0.22 μ F | 6p | 16v | 47 μ F | 7p |
| 100v | 0.33 μ F | 9p | 25v | 10 μ F | 7p |
| 100v | 0.47 μ F | 10p | 25v | 100 μ F | 9p |
| 100v | 0.68 μ F | 15p | 25v | 220 μ F | 11p |
| 250v | 0.1 μ F | 8p | 25v | 470 μ F | 14p |
| 250v | 0.15 μ F | 8p | 25v | 1000 μ F | 22p |
| 250v | 0.22 μ F | 8p | 25v | 2200 μ F | 42p |
| 250v | 0.33 μ F | 8p | 35v | 4.7 μ F | 7p |
| 250v | 0.47 μ F | 8p | 35v | 220 μ F | 14p |
| 250v | 0.68 μ F | 8p | 100v | 10 μ F | 8p |
| 250v | 0.1 μ F | 8p | 100v | 22 μ F | 9p |
| | | | 100v | 47 μ F | 14p |

SPECIAL INTRODUCTORY OFFER

FREE with all orders value £5 or over we will give absolutely free one GSPK P.C. Kit for making your own printed circuits (normal retail price £1.95). Hurry! Offer valid for limited period only.



SEMICONDUCTORS

Here are just a few examples of our LOW Semiconductor prices. Many more semiconductors available all at equally sensational prices... NOW.

| 1+ | 25+ | 1+ | 25+ | 1+ | 25+ |
|-------|-----|--------------|-----|--------|-----|
| AC127 | 24p | BZY88C | 10p | OC76 | 22p |
| AC128 | 19p | Series E12 | 10p | OC170 | 24p |
| AC176 | 15p | (2.7v-30.0v) | 10p | 1N4001 | 8p |
| ACY18 | 18p | NKT210 | 24p | 1N4002 | 8p |
| AD161 | 27p | NKT211 | 24p | 1N4003 | 7p |
| AD162 | 27p | NKT212 | 24p | 1N4004 | 8p |
| AF139 | 28p | NKT213 | 24p | 1N4005 | 10p |
| BC107 | 8p | NKT214 | 19p | 1N4006 | 12p |
| BC108 | 8p | NKT218 | 24p | 1N4007 | 15p |
| BC109 | 9p | NKT219 | 24p | 1N4148 | 4p |
| BC147 | 8p | NKT223 | 25p | 2N1302 | 16p |
| BC148 | 8p | NKT224 | 21p | 2N1304 | 21p |
| BC149 | 8p | NKT242 | 14p | 2N1613 | 14p |
| BCY70 | 14p | NKT243 | 81p | 2N1711 | 15p |
| BCY71 | 20p | NKT401 | 70p | 2N2904 | 22p |
| BCY72 | 14p | NKT402 | 75p | 2N2905 | 24p |
| BDY20 | 91p | NKT403 | 64p | 2N2906 | 19p |
| BFX29 | 24p | NKT403 | 41p | 2N2907 | 22p |
| BFX30 | 24p | OA47 | 6p | 2N3053 | 17p |
| BFY50 | 19p | OA79 | 6p | 2N3054 | 49p |
| BFY51 | 19p | OA90 | 8p | 2N3055 | 57p |
| BFY52 | 19p | OC70 | 12p | 2N3055 | 57p |

NUMEROUS OTHER ITEMS AVAILABLE INCLUDE :

Switches Comprehensive range of N.S.F. Toggle switches and Rotary Water switch kits (to enable you to make your own switch to your own specification).
 Copper laminate and all materials available to make your own printed circuit boards.
 Lamps and lampholders for every requirement. Ready Built Circuits and Modules.
 Freezer and Cleaner aerosol sprays.
 Jack Plugs and sockets.
 Variety of speciality products.
 Recording Tape

All orders value £2 or over post free. Other orders please add 10p p. & p. We only sell new products—do not confuse with 'seconds' or surplus stock. Because of our keen prices we regret the prices apply to U.K. and B.F.P.O. addresses only. Please fill in the coupon and send with 10p (refundable on ordering) for catalogue.

ALL
CALLERS
WELCOME

To GSPK (SALES) LIMITED, Dept. E.E.
Head Office, Hookstone Park, Harrogate, Yorkshire,
HG2 7BU.

MON.
TO
FRI.
9-5.00

Name

Address

..... E.E.

B.H. COMPONENT FACTORS LTD.

DEPT. E.E., P.O. BOX 18, LUTON, BEDS. LU1 1SU

POLYESTER CAPACITORS MULLARD C280, 250 volts.
 0.01 μ F, 0.015, 0.047, 3p, 0.068, 0.1, 0.15, 4p, 0.22, 5p, 0.68, 10p, 1.5 μ F 20p.
MINIATURE ELECTROLYTIC MULLARD C426.
 4 μ F/40V, 8/40, 10/16, 16/40, 25/25, 100/6.4, 32/10, 4p.; 200 μ F 6-4V, 40/16, 80/25, 0.64/6.4, 10/6.4, 20/6.4, 32/6.4, 5p.; C437, 640/6.4, 1600/6.4, 160/25, 160/40, 9p.

| Electrolytic Capacitors | | | | IN4001 | | | | IN4002 | | | | IN4003 | | | | IN4004 | | | |
|-------------------------|----|-----|-----|---------------|-----|-----|-----|-------------------|-----|-----|-------|--------|----|-------|-----|--------|-------|-----|-----|
| mF | V | 2p | 8p | mF | V | 8p | 10p | mF | V | 8p | 10p | mF | V | 8p | 10p | mF | V | 8p | 10p |
| 0.64 | 50 | 2p | 8p | 640 | 10 | 8p | 10p | 1000 | 3 | 6p | 8p | 1000 | 3 | 6p | 8p | 1000 | 3 | 6p | 8p |
| 1 | 6 | 2p | 8p | 1000 | 3 | 6p | 8p | 1000 | 3 | 6p | 8p | 1000 | 3 | 6p | 8p | 1000 | 3 | 6p | 8p |
| 2 | 15 | 2p | 8p | 1000 | 6 | 8p | 10p | 1000 | 6 | 8p | 10p | 1000 | 6 | 8p | 10p | 1000 | 6 | 8p | 10p |
| 2.5 | 50 | 3p | 10p | 1000 | 12 | 10p | 15p | 1000 | 12 | 10p | 15p | 1000 | 12 | 10p | 15p | 1000 | 12 | 10p | 15p |
| 4 | 10 | 3p | 10p | 1000 | 25 | 15p | 20p | 1000 | 25 | 15p | 20p | 1000 | 25 | 15p | 20p | 1000 | 25 | 15p | 20p |
| 6.4 | 50 | 3p | 10p | 1000 | 50 | 35p | 45p | 1000 | 50 | 35p | 45p | 1000 | 50 | 35p | 45p | 1000 | 50 | 35p | 45p |
| 10 | 40 | 4p | 12p | 2000 | 12 | 10p | 15p | 25 | 750 | 2p | 0.01 | 350 | 2p | 0.022 | 30 | 2p | 0.047 | 30 | 2p |
| 10 | 50 | 4p | 12p | 2000 | 25 | 15p | 20p | 25 | 750 | 2p | 0.01 | 160 | 2p | 0.015 | 160 | 2p | 0.022 | 160 | 2p |
| 16 | 15 | 3p | 10p | 2500 | 12 | 10p | 15p | 40 | 750 | 2p | 0.015 | 160 | 2p | 0.022 | 160 | 2p | 0.047 | 30 | 2p |
| 16 | 25 | 3p | 10p | 2500 | 25 | 15p | 20p | 75 | 750 | 2p | 0.022 | 160 | 2p | 0.047 | 30 | 2p | 0.075 | 30 | 2p |
| 20 | 25 | 3p | 10p | 2500 | 25 | 15p | 20p | 100 | 750 | 2p | 0.022 | 160 | 2p | 0.047 | 30 | 2p | 0.075 | 30 | 2p |
| 25 | 15 | 3p | 10p | 2500 | 25 | 15p | 20p | 120 | 750 | 2p | 0.033 | 160 | 2p | 0.047 | 30 | 2p | 0.075 | 30 | 2p |
| 25 | 25 | 3p | 10p | 2500 | 25 | 15p | 20p | 220 | 750 | 2p | 0.047 | 160 | 2p | 0.075 | 30 | 2p | 0.1 | 160 | 2p |
| 32 | 50 | 4p | 12p | 2500 | 25 | 15p | 20p | 1000 | 50 | 2p | 0.68 | 150 | 4p | 0.047 | 30 | 2p | 0.075 | 30 | 2p |
| 40 | 6 | 3p | 10p | 2500 | 25 | 15p | 20p | 4700 | 30 | 2p | 0.68 | 150 | 4p | 0.047 | 30 | 2p | 0.075 | 30 | 2p |
| 50 | 10 | 3p | 10p | 2500 | 25 | 15p | 20p | 0.01 | 30 | 3p | 10 | 160 | 6p | 0.047 | 30 | 2p | 0.075 | 30 | 2p |
| 50 | 10 | 3p | 10p | 2500 | 25 | 15p | 20p | all values, 2-13V | | | | | | | | | | | |
| 50 | 50 | 7p | 25p | | | | | 5p each | | | | | | | | | | | |
| 64 | 10 | 4p | 12p | | | | | | | | | | | | | | | | |
| 64 | 25 | 4p | 12p | | | | | | | | | | | | | | | | |
| 64 | 40 | 5p | 15p | | | | | | | | | | | | | | | | |
| 100 | 6 | 3p | 10p | 2N706 | 10p | | | | | | | | | | | | | | |
| 100 | 6 | 3p | 10p | 2N708 | 13p | | | | | | | | | | | | | | |
| 100 | 50 | 8p | 25p | 2N1303 | 17p | | | | | | | | | | | | | | |
| 250 | 6 | 4p | 12p | 2N3866 | 80p | | | | | | | | | | | | | | |
| 250 | 10 | 4p | 12p | 2N3055 | 60p | | | | | | | | | | | | | | |
| 250 | 15 | 6p | 15p | BC108 | 11p | | | | | | | | | | | | | | |
| 250 | 25 | 8p | 20p | BCY30 | 22p | | | | | | | | | | | | | | |
| 250 | 25 | 8p | 20p | BFY51 | 20p | | | | | | | | | | | | | | |
| 400 | 10 | 5p | 12p | BSX21 | 16p | | | | | | | | | | | | | | |
| 500 | 10 | 5p | 12p | OC35 | 40p | | | | | | | | | | | | | | |
| 500 | 12 | 8p | 20p | OC36 | 43p | | | | | | | | | | | | | | |
| 500 | 25 | 10p | 25p | μ L914 | 30p | | | | | | | | | | | | | | |
| 500 | 50 | 12p | 30p | 7400/01/10/30 | 30p | | | | | | | | | | | | | | |

BARGAIN PACKS
 14/0076 PCV wire 5 x 10 yds 30p
 7/0076 PVC wire 5 x 10 yds 30p
 5 Small Multi-cable 4 way 10 yds 50p
 Gen. purpose switching diode 25 for 25p
 80V Neon wire ends 5 for 20p
 Miniature Pushbutton 2 for 20p
 Transformer 32-0-32 at 150mA 50p
 Red Panel Neon 1 for 10p

MINIATURE R.F. CHOKES
 0.22 μ H, 2.2 μ H, 12 μ H, 8p each

\pm W. 5% Resistors 1p each or 100 Mix 60p 10 Ω -1M

TRANSISTOR EQUIVALENTS BOOK 40p

TERMS: Cash with order. P. & P. please add 10p for orders below £5. Overseas extra. Discount: £10-10%. All goods carry our money back guarantee if not satisfied. We have many components not listed, enquiries welcome. List 5p stamp. Trade enquiries welcome.

C. HADLEY 24, WOODHILL, HARLOW, ESSEX

Add 5p. P. & P. Price list S.A.E. No callers please

All our stocks are brand new with money back guarantee

| | | | | | | | | | |
|--------|--------|--------|-----|--------|-----|--------|-----|--------|-----|
| AC107 | 15p | BC108 | 8p | BFY51 | 12p | OC72 | 12p | 2N2646 | 47p |
| AC126 | 13p | BC109 | 8p | BSY85A | 15p | OC81 | 13p | 2N2926 | 10p |
| AC127 | 13p | BC154 | 20p | ME4042 | 18p | OC81D | 13p | 2N3053 | 20p |
| AC128 | 13p | BC168 | 10p | ME4044 | 14p | OC83 | 20p | 2N3055 | 49p |
| AC176 | 25p | BC189 | 11p | ME4101 | 10p | OC170 | 24p | 2N3702 | 11p |
| AC141K | 20p | BC182L | 8p | ME4102 | 12p | OC200 | 25p | 2N3704 | 13p |
| AC142K | 20p | BC183L | 8p | ME4002 | 14p | OC201 | 25p | 2N3703 | 11p |
| AD149 | 40p | BC184L | 8p | ME4101 | 14p | OC25 | 25p | 40K36 | 55p |
| AD150 | 44p | BC212L | 8p | ME8102 | 15p | OC28 | 30p | 1N4001 | 4p |
| AD161 | M/P56p | BC214L | 8p | MP8111 | 32p | OC29 | 36p | 1N4002 | 4p |
| AD162 | M/P56p | BD116 | 70p | MP8511 | 34p | OC35 | 25p | 1N4003 | 5p |
| AF114 | 15p | BD121 | 60p | MP8513 | 45p | OC38 | 36p | OC202 | 7p |
| AF115 | 15p | BD130 | 46p | OC41 | 13p | 2N697 | 15p | OA90 | 6p |
| AF116 | 15p | BD131 | 59p | OC44 | 13p | 2N1171 | 24p | OA91 | 6p |
| AF117 | 15p | BF194 | 15p | OC45 | 13p | 2N1304 | 25p | 1N4148 | 4p |
| BC107 | 8p | BFY50 | 15p | OC71 | 12p | 2N1306 | | | |



THEY MADE THEIR MARK

NO6 Faraday

(Part 1)

By J. E. Gregory

Table I: FARAD (F)

The farad is the unit of electric capacitance. A capacitor has a capacitance of one farad when a charge of one coulomb raises the potential between its plates to one volt, hence farads = $\frac{\text{coulombs}}{\text{volts}}$

For everyday use the farad is too large a unit, and smaller units called microfarads (symbol $\mu\text{F} = 10^{-6}\text{F}$), nanofarads (symbol $\text{nF} = 10^{-9}\text{F}$) and picofarads (sometimes called "puffs"—symbol $\text{pF} = 10^{-12}\text{F}$) are used.

The unit was first suggested in 1867 by Latimer Clark, the English engineer and electrician, who besides inventing the Clark standard cell took a leading part in the movement for the systemisation of electrical standards. The farad was adopted as the unit of electric capacitance, at the first meeting of the International Electrotechnical conference in 1881.

In this, the first half of a two-part article, we meet the man once described as "the Columbus of electricity"—Michael Faraday—who discovered how to make electricity by mechanical means, and gave his name to the unit of electric capacitance (see Table 1).

Michael Faraday was born at Newington, Surrey, on September 22, 1791, the third son of a Yorkshire blacksmith who had migrated to London. At the age of fourteen Michael was apprenticed to one Riebeau, a book-binder, who gave young Michael time to study the many learned books they were binding. Michael was a good worker, with an aptitude for learning and as a reward Mr. Riebeau took him to a series of lectures, on chemistry given by Sir Humphrey Davy of miner's safety lamp fame.

GREATEST DISCOVERY

The young Faraday was spell-bound not only by Davy but by the content of the lectures, so much so that he made notes, bound and illustrated them, and sent them to Davy requesting an interview as an assistant, although impressed Davy wrote to Faraday saying that he should stick to his trade of bookbinding, "Science is too precarious for a young man".

Then fate took a hand, Davy's assistant was dismissed and Faraday was offered a job, and Davy made what he later described as "My greatest discovery". The man who in later years was to succeed him as Director of the Royal Institute.

ROYAL INSTITUTE

Faraday started work at the Royal Institute on March 1, 1813, in a humble capacity assisting lecturers and keeping the apparatus polished, soon he became Davy's experimental assistant, and together from October 1813 to April 1815, they toured Europe lecturing.

On June 12, 1821, Faraday married Sarah Barnard and they moved to apartments at the Royal Institute where he had been promoted to 'superintendent.

Taking up original work in chemistry Faraday made a number of discoveries among them benzol, and two new chlorides of carbon, he was also much in demand as a lecturer.

Gradually his work in chemistry was eclipsed by his electrical discoveries.

Faraday proved that a conductor carrying a current also induced currents in neighbouring conductors. On a wooden core he wound two coils of insulated wire, and sent electricity through one, while the other was connected to a meter which measured the current. He noticed that while the battery current flowed steadily through the coil, the meter did not move, but when the current was started or stopped, the needle jerked back and forth.

Picking up where Ampère left off he concluded that since electricity produced magnetism, so magnetism might produce electricity. He discovered that if a magnet is thrust into a coil of wire an electric current is "generated" in the coil, when the magnet is withdrawn the current direction is reversed proving that movement can produce electricity. This great discovery—that electricity could be produced by magnetism—was dated in Faraday's notebook as August 29, 1831.

He made a small dynamo in which a current was produced by rotating a loop of wire between the two poles of a magnet. At each half turn of the wire loop the direction of the current was reversed so that it flowed back and forth (a.c.). Faraday eventually fitted a commutator to turn the a.c. into d.c. He demonstrated his dynamo and reported his two discoveries of electrodynamic induction and magnetolectric induction to the Royal Society in November 24, 1831.

This is generally regarded as the birth of the modern dynamo and transformer, and led to the development of the electric motor.

But Faraday had not finished yet as we shall be seeing in Part 2, next month.






TEACH-IN


End of term test

To wind up the *Teach-In* series we have devised the following questionnaire which should help emphasise some of the more important points covered. We shall be publishing detailed answers next month so please do not send your answers in to us.

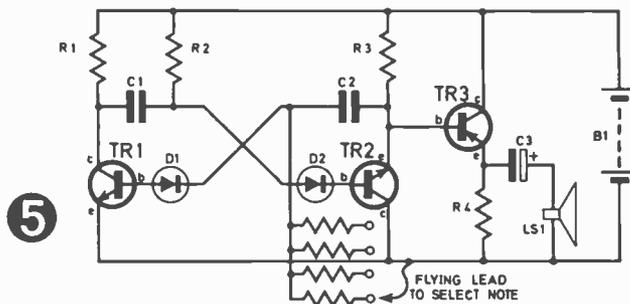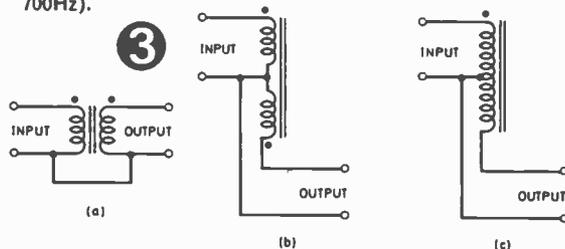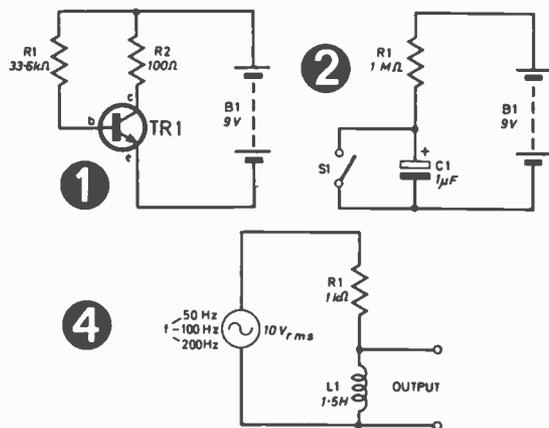- (1) To make a silicon *npn* transistor conduct between collector and emitter must we make the base: (a) 300 mV positive, (b) 300mV negative, (c) 600mV positive or (d) 600mV negative with respect to the emitter.
- (2) Generally speaking, and assuming all important parameters such as h_{FE} , breakdown voltages, junction capacitance, current and power ratings and manufacturing materials are the same, do you think you could substitute *pnp* for *npn* transistors in a circuit and simply reverse the polarity of the power supply?
- (3) Calculate the quiescent power dissipation of TR1 in Fig. 1. Assume TR1 is a silicon transistor and its h_{FE} is exactly 200; the resistors are precise values and the base/emitter voltage drop is exactly 600mV.
- (4) (a) How long will it take C1 to charge up to +4V when S1 in Fig. 2 is opened?
(b) If C1 was a "leaky" capacitor, would it take more or less time to charge to the same potential?
(c) Alternatively, if 18V was applied to the circuit, would the charging time be greater or less than in (a) above?
- (5) Why is it sometimes necessary to put a diode in series with the base of each transistor in an astable multivibrator?
- (6) A square wave has a mark/space ratio of 10 : 1. The off time is 50mS and represents the "mark". How long is the on time and what are the period and frequency of the waveform?
- (7) What are the absolute values of positive and negative peaks of a sine wave having an amplitude of 4V r.m.s. about a d.c. level of +2V?
- (8) Would you prefer to use a silicon or germanium diode as a half-wave meter rectifier when the meter has a full scale reading of 5V? There is a good reason for not using one type! What is the reason?
- (9) Fig. 3 shows three ways in which a transformer could be drawn in a simple circuit. In two cases the output voltage is in phase with the input. In one case it is out of phase. Which is the latter?
- (10) If you are going to buy a transformer to make a simple battery eliminator power supply with a d.c. output in the range 8V to 9V, would you select one with an r.m.s. secondary of: (a) 6.3V, (b) 9V, or (c) 12V?
- (11) What would you expect the r.m.s. output voltage from Fig. 4 to be for input frequencies of 50Hz, 100Hz and 200Hz having equal amplitudes of 10V r.m.s.?
- (12) To obtain best power efficiency with least drain on batteries, would you use a class A or class B output stage in a transistor radio?
- (13) Why do you think that many hi-fi purists prefer a class A output?
- (14) If you connect a crystal microphone to the low impedance sockets of an amplifier, would you have: (a) uniform frequency response, (b) loss of bass frequencies, or (c) loss of high frequencies?
- (15) You have a new amplifier that needs a loudspeaker having 7 ohms impedance. You have two loudspeakers having impedances of 3 ohms and 15 ohms respectively and you desperately want to try out the amplifier. Which loudspeaker could you use without fear of damaging the amplifier?
- (16) Fig. 5 is the basic circuit of a simple four note electronic organ—no component values are given and there are 5 deliberate mistakes in the fundamental circuitry—assume the battery polarity is correct as shown. See how many of the mistakes you can find and then try and work out the values of all the components to make the circuit work. (Frequencies should be in the range of 300 to 700Hz).



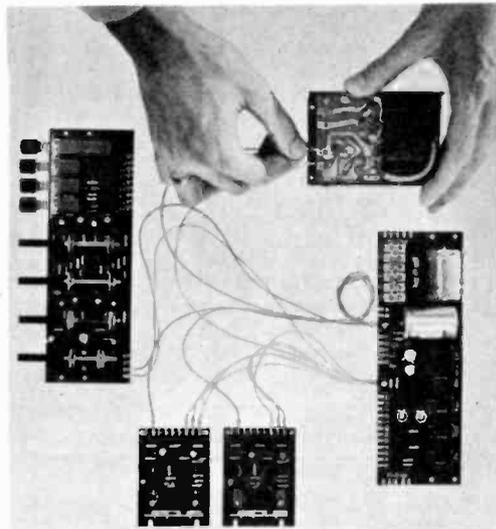Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same - there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative - Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one - Masterlink - which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together - the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

Guarantee If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

sinclair

Sinclair Radionics Ltd., London Road.,
St. Ives, Huntingdonshire PE17 4HJ.
Telephone: St. Ives (04806) 4311

Specifications

Output - 30 watts music power (10 watts per channel R.M.S. into 3Ω).

Inputs - Mag. P.U. - 3mV correct to R.I.A.A. curve 20-25,000 Hz ± 1dB. Ceramic pick-up - 50mV. Radio - 50 to 150mV.

|Aux. adjustable between 3mV. and 3V.
Signal to noise ratio - Better than 70dB.

Distortion - better than 0.2% under all conditions.

Controls - Press buttons for on-off, P.U., radio and aux. Treble +15 to -15 dB at 10 kHz, Bass +15 to -15 dB at 100 Hz. Volume. Stereo Balance.

Channel matching within 1dB.

Front panel - brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

£29.95

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ
Please send Project 605 post free Details and list of stockists

Name

Address

for which I enclose £29.95 cheque/money order/cash. E.E.9B.

YATES ELECTRONICS (FLITWICK) LTD

DEPT. E.E., ELSTOW STORAGE DEPT.
KEMPSTON HARDWICK,
BEDFORD.

C.W.O. PLEASE. POST AND PACKING,
PLEASE ADD 10p TO ORDERS UNDER £1.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

RESISTORS

½W Iskra high stability carbon film—very low noise—capless construction.
¼W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. ¼W 2%
Electrosil TR5.

| Power watts | Tolerance | Range | Values available | Price |
|----------------|-----------|------------|---------------------|-----------|
| ½ | 5% | 4.7Ω-2.2MΩ | E24 | 1-99 100+ |
| ½ | 10% | 3.3MΩ-10MΩ | E12 | 1-0p 0-8p |
| ¼ | 2% | 10Ω-1M | E24 | 3-5p 3-9p |
| ¼ | 10% | 1Ω-3.9Ω | E12 | 1-0p 0-8p |
| ¼ | 5% | 4.7Ω-1MΩ | E12 | 1-0p 0-8p |
| ¼ | 10% | 1Ω-10Ω | E12 | 6p 5-5p |

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ½W, lin ¼W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

TRANSISTORS

| | | | | | | | | | |
|-------|-----|-------|-----|-------|-----|---------|------|--------|-----|
| AC107 | 15p | BC107 | 10p | BF195 | 15p | OC81 | 12p | 2N3703 | 12p |
| AC126 | 12p | BC108 | 10p | BFY50 | 22p | OC82D | 12p | 2N3704 | 13p |
| AC127 | 12p | BC109 | 10p | BFY51 | 22p | OC971 | 40p | 2N3705 | 12p |
| AC128 | 12p | BC147 | 10p | BFY52 | 22p | ORP12 | 50p | 2N3706 | 11p |
| AC131 | 12p | BC148 | 13p | BSY36 | 32p | 2N369 | 16p | 2N3707 | 12p |
| AC132 | 12p | BC149 | 13p | OC26 | 45p | 2N2646 | 60p | 2N3708 | 10p |
| AD140 | 50p | BC157 | 13p | OC28 | 45p | 2N2926R | 9p | 2N3709 | 11p |
| AD161 | 33p | BC158 | 13p | OC35 | 45p | 2N2926G | 9p | 2N3710 | 11p |
| AD162 | 36p | BC159 | 13p | OC42 | 12p | 2N2926Y | 9p | 2N3711 | 11p |
| AF114 | 20p | BD131 | 75p | OC44 | 12p | 2N2926G | 10p | 2N4062 | 12p |
| AF115 | 20p | BD132 | 75p | OC45 | 12p | 2N3054 | 58p | ZTX302 | 15p |
| AF116 | 20p | BF179 | 32p | OC70 | 12p | 2N3055 | 60p | ZTX500 | 16p |
| AF117 | 20p | BF181 | 25p | OC71 | 12p | 2N3442 | 140p | ZTX503 | 16p |
| AF118 | 38p | BF194 | 15p | OC72 | 12p | 2N3702 | 13p | 40362 | 58p |

ZENER DIODES

400mW 5% 3.3V to 30V, 15p.

LINEAR IC'S (DIL)

709 50p 741 50p
710 50p 748 50p

DIL SOCKET

14 and 16 pin
16p

DIODES

RECTIFIER

| | | | |
|--------|-------|----|-----|
| BY127 | 1250V | 1A | 12p |
| BZY10 | 800V | 6A | 25p |
| BZY13 | 200V | 6A | 20p |
| IN4001 | 50V | 1A | 7p |
| IN4004 | 400V | 1A | 8p |
| IN4007 | 1000V | 1A | 12p |

SIGNAL

| | |
|--------|----|
| OA85 | 7p |
| OA90 | 5p |
| OA91 | 5p |
| OA202 | 7p |
| IN4148 | 5p |
| BA114 | 8p |

BRUSHED ALUMINIUM PANELS

12in x 6in—25p; 12in x 2½in—10p; 9in x 2in—7p.

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K log. or lin. 40p.

DUAL GANG, 10K + 10K etc. log. or lin. 60p.

KNOB FOR ABOVE 12p.

FRONT PANEL 65p

18 Gauge panel 12" x 4" with slots cut for use with slider pots. Grey or matt
black finish complete with fixings for 4 pots.

MULLARD POLYESTER CAPACITORS C2% SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2½p, 0.0068μF, 0.01μF,
0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7½p,
0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3½p, 0.15μF,
4½p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7½p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF
3½p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6½p, 0.47μF, 8½p, 0.68μF, 11p, 1.0μF, 13p
1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V,

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF
2½p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3½p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

6p each
(μF/V) 10/2.5, 40/2.5, 80/2.5, 160/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4,
400/4, 6.4/6.4, 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 4/10, 16/10, 32/10, 64/10
125/10, 200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1.6/25, 6.4/25, 12.5/25,
25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.64/64, 2.5/64, 5/64, 10/64
20/64, 32/64.

MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6.4, 800/4, 1000/2.5, 9p, 100/64, 160/40, 250/25,
400/16, 640/10, 1250/4, 1000/6.4, 1600/2.5, 12p, 160/64, 250/40, 400/2.5, 640/16,
2000/4, 1000/10, 1600/6.4, 2500/2.5, 15p, 250/64, 400/40, 640/25, 3200/4, 1000/16,
1600/10, 2500/6.4, 4000/2.5, 18p.

ELECTROLYTIC CAPACITORS Miniature P.C. mounting

5p each.
(μF/V) 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

VEROBOARD

0.1 0.15

2½ x 3½ 22p 17p

2½ x 5 24p 21p

3½ x 3½ 24p 21p

3½ x 5 28p 28p

17 x 2½ 75p 57p

17 x 3 100p 82p

17 x 5 (plain) — 82p

17 x 3½ (plain) — 60p

17 x 2½ (plain) — 42p

2½ x 5 (plain) — 12p

2½ x 3½ (plain) — 11p

Pin insertion tool 52p

Spot face cutter 42p

Pkt. 50 pins 20p

JACK PLUGS AND SOCKETS

Standard screened 18p

Standard insulated 12p

Stereo screened 35p

Standard socket 15p

Stereo socket 18p

3.5mm socket 8p

3.5mm socket 8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin

Plug 12p, Socket 8p.

4 way screened cable 15p/metre

6 way screened cable 22p/metre

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

THERMISTORS

VA10555 15p

VA10665 15p

VA1077 15p

R53

£1.35

COMPACT CASSETTES—IN PLASTIC LIBRARY BOX

C90 65p

C120 85p

LARGE (CAN) ELECTROLYTICS

1600μF 64V 74p

2500μF 40V 74p

2500μF 50V 58p

2500μF 64V 80p

2800μF 100V £3.00

3200μF 16V 50p

4500μF 16V 50p

4500μF 25V £1.68

5000μF 50V £1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p

0.022μF 12p

0.047μF 13p

0.1μF 16p

0.22μF 20p

0.47μF 23p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series values 4p each.

Peerless HIGH FIDELITY LOUDSPEAKERS

..... Acclaimed by the Experts

Chassis Units (Dual Cone,
Coaxial, Woofers, Tweeters,
etc.) plus Multi-unit systems
in Kit Form from Scandina-
via's largest manufacturer.



P. F. & A. R. Helma Ltd. (Dept. EE10)
Summerbridge, Harrogate HG3 4DR Yorks.
Tel: Darley 279 (STD 0423-72)

Matching
Cabinet Kits
also available.

AERIAL BOOSTERS

We make four types of Aerial Boosters. L45625 UHF, L12 VHF405, L11 VHF Radio
L10 M/W & S/W. Price L45 £2.95, L12 & L11 £2.95, L10 £2.45.

VALVE BARGAINS

Any 5—45p. 10—70p:

EC82, ECL80, EF80, EF85, EF183, EF184, EBF89, EB91, EY86, PCC84, PCC89,
PC97, PCF80, PCF86, PCL82, PCL83, PCL84, PCL85, PL36, PY33, PY82, PY800,
PY801, 30L15, 30C15, 6-30L2.

19" UHF/VHF TV £7.50

THORN 850 SERIES

Untested but with complete set of spare valves. Price £7.50. Carriage £1.50.

100 MIXED RESISTORS 60p


From ½ watt to 2 watt and from 10-ohms to 10 m-ohms our choice. Price 60p

100 MIXED CAPACITORS £1

From 220PF to 200MFD and from 12V/w to 500V/w—our choice £1.
PDST & PACKING under £1.5p. Over £1.10p, S.A.E. for leaflets on all items.
Money back guarantee if not completely satisfied.

VELGO ELECTRONICS

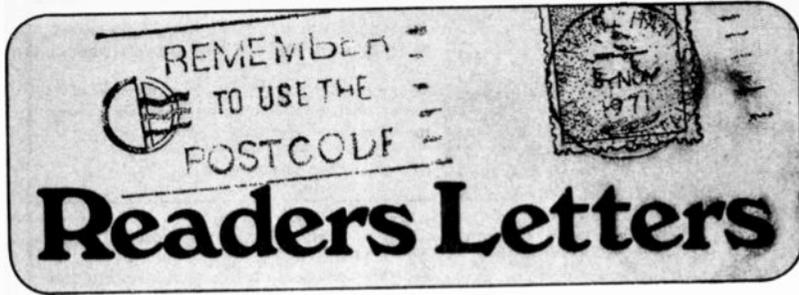62A Bridge Street, Ramsbottom, Bury, Lancs.



That Convention

Ref. your reply to Mr. Robinsons comment (July issue) on conventional and electron current, may I point out the following.

- (a) Conventional current is no longer in common usage; all secondary schools, at least in Scotland, teach the basics of electricity and magnetism with reference to electron flow.
- (b) All the basic laws of electricity and magnetism are not in terms of conventional current, electron current is now used and has been for some time.

To sum up, electron current has now become conventional, and the basic rules of electricity and magnetism not only remain as they always were, but they are now much more realistic. Readers still using conventional current may be brought up to date as far as electro-magnetics is concerned if they simply use electron current and interchange Flemings right and left hand rules.

In closing, may I congratulate you and your colleagues for an excellently produced magazine; I am sure that you have given much pleasure to the professional as well as the beginner in electronics.

Michael F. I. McVoy
Port Glasgow

Our Teach-In author, Mike Hughes, replies:

Thank you for Mr. McVoy's letter which is very interesting. Here is my reply which you might like to publish as I think his comments are quite controversial.

Mr. McVoy's comments are very interesting but I think that a unilateral decision to drop conventional current teaching could be very dangerous. Certainly in most parts of England the policy of teaching is to stay with conventional current—this is the accepted requirement for the London University Schools' Examination Board when they come to mark GCE papers.

Of course, all established physics and electronics books are written in terms of conventional current and the more recent ones in my possession still maintain this standard. Provided the student is aware of the definition

I do not think there is any great harm in maintaining the situation.

I cannot agree with Mr. McVoy's statement regarding Flemings "left" and "right" hand rules. Flemings rules were devised assuming current flow from positive to negative; if you change the convention they can no longer be called "Fleming's" rules, but worse still; I have great difficulty remembering which hand applies to what at the moment; introduce a reversal in sense of flow and I bet—as with a pair of swing doors—I will get the right set of circumstances on the last attempt!

What happens to the "Corkscrew" rule (left hand thread screws?) and those nice twirly N's and S's to tell me which end of a solenoid is the north pole? All transistor and diode symbols have a built in "arrow" which depicts the direction of conventional flow; if we changed the convention sooner or later someone would come along and say the symbols should be changed round. Anyone then referring back to old copies of E.E. would no doubt be reading npn for pnp types!

I have every sympathy with the beginner who may be mesmerised by the apparent nonsense of the convention, but I think it is simpler to stick with it than change it lightly.

Mike Hughes

Clubbed!

I have been interested in electronics for some years but until your magazine came out I had not done anything practical. Now I have built a couple of your projects, due to your magazine

making it simple and basic, and my interest has increased.

I would like to join a radio or electronics club to further my interest, but I'm a bit hesitant as being a near beginner I'm not certain if I'd be eligible. If you could suggest a suitable club in my area I would be very grateful.

H. Wagg
Cheshire

We do not know of a club in your area, but there may be a course at a local technical college or an evening course at a school. Otherwise see the following letter.

Thanks to your advice in reply to Mr. Milligan's letter (July issue) I have since joined the British Amateur Electronics Club and found that it fulfils all my requirements. As for a national exhibition this year's has already taken place at Penarth, Glamorgan on July 22 to 29. Amongst the exhibits was a random letter generator, designed by some of our more experienced members, and constructed by any members who were willing to help.

Although our projects sound rather ambitious (the next being a small computer) all attempts are made to help newcomers to the electronics field. Nearly half the quarterly newsletter is devoted to comment and articles to help the beginner, and give that beginner the knowledge he needs to become proficient in pursuance of his hobby, so, if anyone is interested, I am sure Mr. Margetts will send you details. (No, I don't get commission!)

Andrew Cash
Bristol

Weather Coupling

"E.E. Constructionairs" may find this tip useful for the wind generator spindle coupling in the Weather Station (August issue). By cutting away the plastic surround of a 2 amp plastic terminal block, the metal inserts make a suitable spindle coupling for a small model makers motors.

R. A. Lygo
Oxford

If you write to us for advice, and wish to have a personal reply you must include a s.a.e. Unfortunately, we cannot prepare special designs, circuits or wiring diagrams, to meet individual requirements nor can we supply back issues or answer queries concerning commercial equipment, or subjects or designs not published by us.

For all technical and editorial matters, write to: The Editor, Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone 01-634 4452.

For all enquiries concerning advertisements or advertisers write to: The Advertisement Manager, Everyday Electronics, at the above address. Phone 01-634 4202.

BSR LATEST SUPERSLIM

STEREO AND MONO

Plays 12", 10" or 7" records, Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2" x 11 1/2". Above motor board 3 1/2". Below motor board 2 1/2". With STEREO and MONO XTAL MONO-COMPATIBLE. Plays all records



£8.75 Post 25p.
£7.75 Post 25p.

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made tested. Printed circuit. 3 watts output. Tone and volume controls. Complete with two knobs, output valve and rectifier and high performance loudspeaker. Double wound fully isolated mains transformer. AC Mains 200/250V. Response 50-12,000 cps. Sensitivity 300mV. £4 Post 25p.

GARRARD DISCO DECK

£10 POST FREE

4 speeds. Plays all sizes of records. 4 pole heavy duty motor. 9in. steel turntable. Flux in head complete with stereo/mono cartridge. Adjustable stylus pressure. Auto-stop. Brown and Cream finish. AC mains 110/240V. Base plate size 12in. x 8in. Operating area 14in. x 12in. Above motor board 3in., below motor board 2 1/2in. Ideal for Home Hi-Fi or Discotheque.



GARRARD AUTOCHANGERS with Sonotone Cartridges Stereo Diamond and Mono Sapphire. Model 1025 210. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

BSR JUNIOR SINGLE PLAYER Turnable, 4-speed motor and separate pick-up £4.50

HI-FI PICK-UP CARTRIDGES. Diamond LP/Stereo Stereo/Mono PTA £2.50; GP94 £2.50; GP93 £2.00; Sapphire Mono GP91 £1.50; Power-point LP/78. 80p.

E.M.I. WOOFER AND TWEETER KIT

£5.75 Post 25p

Comprising a fine example of a Woofer 10 1/2" x 8 1/2" with a massive Ceramic Magnet, 44oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2" square has a special lightweight paper cone and magnet flux, 10,000 lines. Crossover condenser included. Impedance Standard 8 ohms Maximum Power 12 watts Useful Response 35 to 18,000 cps Base Resonance 45 cps



SUITABLE ENCLOSURE 20 x 13 x 9in. £9 POST 25p MODERN TEAK DESIGN

WEYRAD P50—TRANSISTOR COILS

| | |
|---|------------------------------|
| RA2W Ferrite Aerial... 72p | Spare Cores... 3p |
| Osc. P50/1AC... 33p | Driver Trans. LFD4... 58p |
| I.F. P50/BCC 470 kc/s... 38p | Printed Circuit, PCAL... 58p |
| 3rd I.F. P50/3CC... 38p | J.B. Tuning Gang... 65p |
| P51/1 or P51/2... 38p | Weyrad Booklet... 10p |
| P50/3V... 38p | OPTI... 58p |
| Mullard Ferrite Rod 8 x 1in. 20p. 6 x 1in. 20p. | |

VOLUME CONTROLS 80ohm Coax 4p. BRITISH AERIALITE AERIAL-AIR SPACED 40p. £1.40; 60yd. £2. FERRING LOW LOSS IDEAL 625 and colour. 10p. Prd.

8in ELAC HI-FI SPEAKERS

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts music power.



£3.75

E.M.I. 1 1/2" x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 25p. £4.25

With flared tweeter cone and ceramic magnet, 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p. £2.25

TEAK CABINET

18 x 10 x 9in Fluted front. £5 Post 25p

BLANK ALUMINIUM CHASSIS 18 x w.x. 2in. sides. 7 x 4in. 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 95p; 15 x 14in. 90p; 11 x 3in. 60p; 16 x 10in. £1. ALUMINIUM PANELS 18 x w.x. 6 x 4in. 5p; 8 x 6in. 15p; 14 x 8in. 15p; 10 x 7in. 15p; 13 x 6in. 20p; 18 x 8in. 25p; 16 x 6in. 25p; 14 x 9in. 34p; 12 x 12in. 40p; 18 x 10in. 50p

RADIO COMPONENT SPECIALISTS

Radio Books & Component Lists 5p. Written guarantee. (Export: Ramit cash and extra postage.)

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V. AC. Output voltages available 5 or 9 or 12 or 15 or 18 or 20V. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST FREE Details S.A.E. Size 3 1/2" x 1 1/2" x 1 1/2".

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2" x 1 1/2" x 1". Response 25 c.p.s. to 25 Kcs. 26db gain. For use with valve or transistor equipment. 90p Post Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS CAN TYPES

| | | |
|----------------|-------------------|-----------------------|
| 2/360V... 14p | 250/25V... 14p | 50+50/350V... 35p |
| 4/360V... 14p | 500/25V... 20p | 80+100/350V... 58p |
| 8/450V... 14p | 100/25V... 35p | 32+32/250V... 18p |
| 16/450V... 18p | 100/50V... 47p | 32+32/450V... 33p |
| 32/450V... 20p | 8+8/450V... 18p | 250+50/325V... 50p |
| 25/25V... 10p | 8+16/450V... 20p | 32+32+32/350V... 43p |
| 50/50V... 10p | 16+16/450V... 25p | 100+50+50/850V... 48p |
| 100/25V... 10p | 32+32/350V... 25p | |

LOW VOLTAGE ELECTROLYTICS

| |
|---|
| 1. 2. 4. 5. 8. 16. 25. 30. 50. 100. 200mF. 15V. 10p |
| 500mF. 12V. 15p; 25V. 20p; 50V. 30p. |
| 1000mF. 12V. 17p; 25V. 35p; 50V. 47p; 100V. 70p. |
| 2000mF. 6V. 25p; 25V. 42p; 50V. 57p. |
| 2500mF. 50V. 62p; 8000mF. 25V. 47p; 50V. 65p. |
| 5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 50V. 85p; 50V. 95p |

CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-01 4p. 0-5 13p; 1mF 15p; 2mF 150V 15p. 500V-0-001 to 0-05 4p; 0-1 5p; 0-25 8p; 0-47 25p.

SILVER MICA. Close tolerance 1% 2-2500pF 8p; 500-2-200 pF 10p; 2,700-6,800pF 20p; 6,800pF-0.01. mfd 30p; each. TWIN GANG. "A" or 208pF-170pF. 85p; Slow motion drive 365+365 with 25+25p; 50p; 500pF slow motion, standard 45p; small 3-gang 500pF £1.80.

SHORT WAVE, SINGLE. 10pF 30p; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS. 1/4 w., 1/2 w., 20% 1p; 2 w. 5p 10 ohms to 10 meg HIGH STABILITY. 1 w. £ 25. 10 watts to 1 meg., 10p. Ditto 5% Preferred values 10 ohms to 10 meg., 5p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 8-2 ohms 10p.

GARRARD DECADEC SP25 MK II RECORD PLAYER

With Stereo/Mono Derram Cartridge transcription head and arm Four speeds. 10 1/2in. turntable. Anti-rumble filter Bias compensation. Laboratory motor.



SPECIAL £18.50 Post 25p PRICE

METAL PLINTH & PLASTIC COVER

Cut out for most Garrard or B.S.R. Will go with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 1/2 x 14 1/2 x 7 1/2in. POST 25p

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3v. 4 amp £1.50
250-0-250 80 mA. 6.3v. 3.5a. 6.3v. 1a. or 5v. 2a. £2.50
350-0-350 80 mA. 6.3v. 3.5a. 6.3v. 1a. or 5v. 2a. £3.00
300-0-300V. 120mA. 6.3v. 4a. C.T. 6.3v. 2a. £3.25
MINIATURE 200v. 200mA. 6.3v. 1a. 2 1/2 x 2 1/2 x 2in. 75p
MIDTAP 230v. 45 mA. 6.3v. 2a. 2 1/2 x 2 1/2 x 2in. 90p
MINI-MIDS 20v. 100mA. 1 1/2 x 1 1/2 x 1 1/2in. 50p
HEATER TRANS. 6.3v. 3a. 2 1/2 x 2 1/2 x 2in. 60p
Ditto tapped sec. 1.4 v. 2. 3. 4. 5. 6.3 v. 1 1/2 amp. 95p
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3. 4. 5. 6. 8. 9. 10. 12. 15. 18. 24 and 30 v. £2.25
1 amp. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60. £2.25
2 amp. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60. £2.25
3 amp. 6. 8. 10. 12. 16. 18. 20. 24. 30. 36. 40. 48. 60. £2.75
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 150w. £2.25; 500w. £2.25; 750w. £10; 100w. £14.
CHARGER TRANSFORMERS. Input 200/250V. For 6 or 12v., 1 1/2 amp., £1.60; 2 amp. £1.80; 4 amp. £2.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p
LUCAS 2DS500 Bridge 70V 5 amp. £1.

MAINS ISOLATING TRANSFORMER (Primary 0 - 110 - 240V. Secondary 0 - 240V. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make. BARGAIN OFFER £10, Carriage 50p.

1 1/2 inch DIAMETER WAVE-CHANGING SWITCHES 25p. 2 p. 2-way, or 2 p. 6-way or 2 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.
TOGGLE SWITCHES. sp. 14p; dp. 18p; dp. dt. 23p.

'THE INSTANT' BULK TAP ERASER & HEAD DEMAGNETISER 200/250V. A.C. £2.35 Post Leaflet S.A.E.

MINIMUM POST AND PACKING 15p

ALL MODELS "BAKER SPEAKERS" IN STOCK HI-Fi Enclosure Manual containing 20 plans, crossover data and cubic tables. 42p Post Free.

BAKER 12in. MAJOR £9

30-14,500 c.p.s., 12in. Double cone, woofer and tweeter together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 30 watts. Voice coils 9 or 8 or 15 ohms. Post Free

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50

BAKER "BIG-GROUP" SPEAKERS

| 'Group 25' | 'Group 35' | 'Group 50' |
|------------------|------------------|-------------|
| 12 inch £8 | 12 inch £9 | 15 inch £20 |
| 25 watt | 35 watt | 50 watt |
| 3 or 8 or 15 ohm | 3 or 8 or 15 ohm | 8 or 15 ohm |

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. or 10in. dia. speaker 20 x 13 x 9in. £5. Post 25p For 10 x 8in. or 8in. speaker 18 x 10 x 9in. £4. Post 25p For 10 x 6in. or 6in. speaker 18 x 8 x 6in. £4. Post 25p LOUSPEAKER CABINET WADDING 18in. width, 18p it

GOODMANS 6 1/2 in. HI-FI WOOFER 8 ohm, 10 watt. Large ceramic magnet. Special Cambria cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. HI-Fi Enclosures Systems, etc. £4.

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 x 2in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1.90 Post 10p

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 9-16k/s. 10W 8 ohm or 15 ohm £1.50. De Luxe Horn Tweeters 8-18 K/s. 15W, 15 ohm £2. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 85p. SPECIAL OFFER! 80 ohm 2 1/2in.; 2 1/2in.; 35 ohm. 2in.; 15 ohm. 2 1/2in. dia.; 3in. dia.; 6 x 4in.; 8 x 6in. £1 EACH 18 ohm. 3 1/2in. dia.; 6 x 4in.; 7 x 4in.; 3 ohm. 2 1/2in. 3in. 5 x 3in.

LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in. £1.25; 6 1/2in. £1.50; 8 x 6in. £1.60; 8 x 2 1/2in. 90p 8in. £1.75; 10 x 6in. £1.90

RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in. dia. 4 watt; 10in. dia. 6 watt; 1 1/2in. dia. 6 watt 3 or 8 or 15 ohm models £2.00 each. Post 15p

VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO. 3, 8 and 15 ohms 80p.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 Input speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass Controls. Guaranteed. Details S.A.E. £49 Post Free

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.50

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. With mix Microlens, records, tape and tuner with separate controls into single output. Post 15p. STEREO VERSION OF ABOVE £4.50

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Callibr. slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4inches. £12.50

BARGAIN FM TUNER as above less cabinet £8.85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.50

COAXIAL PLUG 5p. PANEL SOCKETS 5p. LINE 18p. OUTLET BOXES. SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p. yard. 300 ohms. JACK SOCKET 34p. open-circuit 14p. closed circuit 25p. Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS 84d. Chrome 15p; 3.5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. 8p. CERAMIC 8p; CAN5 8p.

E.M.I. TAPE MOTORS Post 15p. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. Size 3 1/2 x 2 1/2 x 1 1/2in. (Illustrated) £1.25

BALANCED G.M.C. MOTORS 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1/8 x 3/8. Size 2 1/2 x 2 1/2 x 1 1/2in. Post 15p 85p

CUSTOMERS FREE CAR PARK CALLERS WELCOME 337 WHITEHORSE ROAD, CROYDON Ocen 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-3 p.m.) Buses 50, 68, 159 Rail Selhurst. Tel. 01-484-1645

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS



TYPES W.100
 100 x 80 mm.

| | | | |
|------------------|--------|-----------------|--------|
| 50μA..... | \$2-60 | 20V. D.C..... | \$2-10 |
| 50-0-50μA..... | \$2-45 | 50V. D.C..... | \$2-10 |
| 100μA..... | \$2-45 | 300V. D.C..... | \$2-10 |
| 100-0-100μA..... | \$2-35 | 1 amp. D.C..... | \$2-10 |
| 500μA..... | \$2-30 | 5 amp. D.C..... | \$2-10 |
| 1mA..... | \$2-10 | 300V. A.C..... | \$2-10 |
| | | VU Meter..... | \$2-75 |



TYPE S-80
 80 mm.
 square fronts

| | | | |
|------------------|--------|-----------------|--------|
| 50μA..... | \$2-20 | 50V. D.C..... | \$2-60 |
| 50-0-50μA..... | \$2-15 | 300V. D.C..... | \$2-60 |
| 100μA..... | \$2-10 | 1 amp. D.C..... | \$2-50 |
| 100-0-100μA..... | \$2-00 | 5 amp. D.C..... | \$2-60 |
| 500μA..... | \$2-75 | 300V. A.C..... | \$2-60 |
| 1mA..... | \$2-60 | VU Meter..... | \$2-87 |
| 20V. D.C..... | \$2-60 | | |

"SEW" CLEAR PLASTIC METERS



Type MR.52P. 4 1/2 in. x 4 1/2 in. fronts.

| | | | |
|------------------|--------|--------------------|--------|
| 50μA..... | \$2-60 | 100μA..... | \$2-60 |
| 50-0-50μA..... | \$2-60 | 500μA..... | \$2-60 |
| 100μA..... | \$2-60 | 1 amp..... | \$2-60 |
| 100-0-100μA..... | \$2-60 | 5 amp..... | \$2-60 |
| 500μA..... | \$2-60 | 15 amp..... | \$2-60 |
| 1mA..... | \$2-60 | 30 amp..... | \$2-60 |
| 50μA..... | \$2-60 | 20V. D.C..... | \$2-60 |
| 50-0-50μA..... | \$2-60 | 50V. D.C..... | \$2-60 |
| 100μA..... | \$2-60 | 300V. D.C..... | \$2-60 |
| 100-0-100μA..... | \$2-60 | 15V. A.C..... | \$2-60 |
| 500μA..... | \$2-60 | 300V. A.C..... | \$2-60 |
| 1mA..... | \$2-60 | 8 Meter 1mA..... | \$2-87 |
| 50μA..... | \$2-60 | VU Meter..... | \$2-87 |
| 50-0-50μA..... | \$2-60 | 15V. A.C..... | \$2-60 |
| 100μA..... | \$2-60 | 5 amp. A.C.*..... | \$2-60 |
| 100-0-100μA..... | \$2-60 | 10 amp. A.C.*..... | \$2-60 |
| 500μA..... | \$2-60 | 20 amp. A.C.*..... | \$2-60 |
| 1mA..... | \$2-60 | 30 amp. A.C.*..... | \$2-60 |

Type MR.52P. 2 1/2 in. square fronts.

| | | | |
|------------------|--------|--------------------|--------|
| 50μA..... | \$2-10 | 10V. D.C..... | \$2-60 |
| 50-0-50μA..... | \$2-60 | 20V. D.C..... | \$2-60 |
| 100μA..... | \$2-60 | 50V. D.C..... | \$2-60 |
| 100-0-100μA..... | \$2-60 | 300V. D.C..... | \$2-60 |
| 500μA..... | \$2-60 | 15V. A.C..... | \$2-60 |
| 1mA..... | \$2-60 | 300V. A.C..... | \$2-60 |
| 50μA..... | \$2-60 | 8 Meter 1mA..... | \$2-10 |
| 50-0-50μA..... | \$2-60 | VU Meter..... | \$2-30 |
| 100μA..... | \$2-60 | 1 amp. A.C.*..... | \$2-60 |
| 100-0-100μA..... | \$2-60 | 5 amp. A.C.*..... | \$2-60 |
| 500μA..... | \$2-60 | 10 amp. A.C.*..... | \$2-60 |
| 1mA..... | \$2-60 | 20 amp. A.C.*..... | \$2-60 |
| 50μA..... | \$2-60 | 30 amp. A.C.*..... | \$2-60 |

Type MR.52P. 3 1/2 in. x 3 1/2 in. fronts.

| | | | |
|------------------|--------|--------------------|--------|
| 50μA..... | \$2-37 | 10V. D.C..... | \$2-60 |
| 50-0-50μA..... | \$2-75 | 20V. D.C..... | \$2-60 |
| 100μA..... | \$2-75 | 50V. D.C..... | \$2-60 |
| 100-0-100μA..... | \$2-65 | 150V. D.C..... | \$2-60 |
| 500μA..... | \$2-65 | 300V. D.C..... | \$2-60 |
| 1mA..... | \$2-60 | 15V. A.C..... | \$2-60 |
| 50μA..... | \$2-60 | 50V. A.C..... | \$2-60 |
| 50-0-50μA..... | \$2-60 | 150V. A.C..... | \$2-60 |
| 100μA..... | \$2-60 | 300V. A.C..... | \$2-60 |
| 100-0-100μA..... | \$2-60 | 500V. A.C..... | \$2-60 |
| 500μA..... | \$2-60 | 8 Meter 1mA..... | \$2-87 |
| 1mA..... | \$2-60 | VU Meter..... | \$2-87 |
| 50μA..... | \$2-60 | 15V. A.C..... | \$2-60 |
| 50-0-50μA..... | \$2-60 | 5 amp. A.C.*..... | \$2-60 |
| 100μA..... | \$2-60 | 10 amp. A.C.*..... | \$2-60 |
| 100-0-100μA..... | \$2-60 | 20 amp. A.C.*..... | \$2-60 |
| 500μA..... | \$2-60 | 30 amp. A.C.*..... | \$2-60 |

*MOVING IRON—ALLOTHERS MOVING COIL
 Please add postage

SEW EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm.
 A new range of high quality moving coil instruments ideal for school experiments and other bench applications.
 3" mirror scale. The meter movement is readily accessible to demonstrate internal working. Available in the following ranges:

| | | | |
|----------------|--------|-----------------|--------|
| 50μA..... | \$2-60 | 20V. d.c..... | \$4-40 |
| 100μA..... | \$2-65 | 50mA A.C..... | \$4-40 |
| 1mA..... | \$4-40 | 300V. d.c..... | \$4-60 |
| 50-0-50μA..... | \$4-65 | | |
| 1-0-1mA..... | \$4-40 | Dual range | |
| 1A d.c..... | \$4-40 | 500mA/5A d.c. | \$4-65 |
| 8A d.s..... | \$4-40 | 5V/50V d.c..... | \$4-65 |
| 10V d..... | \$4-40 | | |

Type MR.52P. 1 1/2 in. square fronts.

| | | | |
|------------------|--------|------------------|--------|
| 200mA..... | \$1-60 | 5 amp..... | \$1-60 |
| 300mA..... | \$1-60 | 10V. D.C..... | \$1-60 |
| 500mA..... | \$1-60 | 20V. D.C..... | \$1-60 |
| 750mA..... | \$1-60 | 50V. D.C..... | \$1-60 |
| 1 amp..... | \$1-60 | 100V. D.C..... | \$1-60 |
| 2 amp..... | \$1-60 | 200V. D.C..... | \$1-60 |
| 5 amp..... | \$1-60 | 500V. D.C..... | \$1-60 |
| 10 amp..... | \$1-60 | 300V. D.C..... | \$1-60 |
| 3V. D.C..... | \$1-60 | 500V. D.C..... | \$1-60 |
| 10V. D.C..... | \$1-60 | 750V. D.C..... | \$1-60 |
| 15V. D.C..... | \$1-60 | 15V. A.C..... | \$1-70 |
| 20V. D.C..... | \$1-60 | 50V. D.C..... | \$1-70 |
| 50μA..... | \$2-10 | 100V. D.C..... | \$1-60 |
| 50-0-50μA..... | \$1-90 | 200V. D.C..... | \$1-60 |
| 100μA..... | \$1-90 | 500V. D.C..... | \$1-60 |
| 100-0-100μA..... | \$1-75 | 300V. D.C..... | \$1-60 |
| 200μA..... | \$1-75 | 500V. D.C..... | \$1-60 |
| 500μA..... | \$1-45 | 15V. A.C..... | \$1-70 |
| 500-0-500μA..... | \$1-60 | 300V. A.C..... | \$1-70 |
| 1mA..... | \$1-60 | 5 Meter 1mA..... | \$1-85 |
| 1-0-1mA..... | \$1-60 | VU Meter..... | \$2-25 |
| 2mA..... | \$1-60 | 15V. A.C..... | \$1-70 |
| 5mA..... | \$1-60 | 50V. D.C..... | \$1-70 |
| 10mA..... | \$1-60 | 100V. D.C..... | \$1-70 |
| 20mA..... | \$1-60 | 200V. D.C..... | \$1-70 |
| 50mA..... | \$1-60 | 500V. A.C..... | \$1-70 |
| 100mA..... | \$1-60 | 300V. A.C..... | \$1-80 |
| 1000mA..... | \$1-60 | 5 Meter 1mA..... | \$2-10 |
| 1500mA..... | \$1-60 | VU Meter..... | \$2-10 |

Type MR.52P. 5/8 in. square fronts.

| | | | |
|------------------|--------|------------------|--------|
| 50μA..... | \$2-25 | 5 amp..... | \$1-70 |
| 50-0-50μA..... | \$2-10 | 10V. D.C..... | \$1-70 |
| 100μA..... | \$2-10 | 20V. D.C..... | \$1-70 |
| 100-0-100μA..... | \$1-87 | 50V. D.C..... | \$1-70 |
| 200μA..... | \$1-87 | 100V. D.C..... | \$1-70 |
| 500μA..... | \$1-75 | 200V. D.C..... | \$1-70 |
| 500-0-500μA..... | \$1-70 | 500V. D.C..... | \$1-70 |
| 1mA..... | \$1-70 | 15V. A.C..... | \$1-80 |
| 5mA..... | \$1-70 | 300V. A.C..... | \$1-80 |
| 10mA..... | \$1-70 | 5 Meter 1mA..... | \$1-85 |
| 20mA..... | \$1-70 | VU Meter..... | \$2-25 |
| 50mA..... | \$1-70 | 15V. A.C..... | \$1-70 |
| 100mA..... | \$1-70 | 50V. D.C..... | \$1-70 |
| 500mA..... | \$1-70 | 100V. D.C..... | \$1-70 |
| 1 amp..... | \$1-70 | 200V. D.C..... | \$1-70 |
| | | 500V. A.C..... | \$1-70 |

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts.

| | | | |
|--------------------|--------|--------------------|--------|
| 1 amp..... | \$1-95 | 10V. D.C..... | \$1-95 |
| 2 amp..... | \$1-95 | 20V. D.C..... | \$1-95 |
| 5 amp..... | \$1-95 | 50V. D.C..... | \$1-95 |
| 15 amp..... | \$1-95 | 100V. D.C..... | \$1-95 |
| 30 amp..... | \$1-95 | 200V. D.C..... | \$1-95 |
| 50 amp..... | \$1-95 | 500V. D.C..... | \$1-95 |
| 5V. D.C..... | \$1-95 | 300V. D.C..... | \$1-95 |
| 10V. D.C..... | \$1-95 | 500V. D.C..... | \$1-95 |
| 20V. D.C..... | \$1-95 | 150V. D.C..... | \$1-95 |
| 50V. D.C..... | \$1-95 | 300V. D.C..... | \$1-95 |
| 100V. D.C..... | \$1-95 | 500V. A.C.*..... | \$1-95 |
| 200V. D.C..... | \$1-95 | 100V. A.C.*..... | \$1-95 |
| 500V. D.C..... | \$1-95 | 150V. A.C.*..... | \$1-95 |
| 150V. D.C..... | \$1-95 | 300V. A.C.*..... | \$1-95 |
| 300V. D.C..... | \$1-95 | 500mA A.C.*..... | \$1-95 |
| 500V. A.C.*..... | \$1-95 | 1 amp. A.C.*..... | \$1-95 |
| 150V. A.C.*..... | \$1-95 | 5 amp. A.C.*..... | \$1-95 |
| 300V. A.C.*..... | \$1-95 | 10 amp. A.C.*..... | \$1-95 |
| 500mA A.C.*..... | \$1-95 | 20 amp. A.C.*..... | \$1-95 |
| 1 amp. A.C.*..... | \$1-95 | 30 amp. A.C.*..... | \$1-95 |
| 5 amp. A.C.*..... | \$1-95 | 50 amp. A.C.*..... | \$1-95 |
| 10 amp. A.C.*..... | \$1-95 | VU Meter..... | \$2-10 |



EDGWISE METERS

| | |
|---|--------|
| Type PE.70. 3 1/2 in. x 1 1/2 in. x 2 1/2 in. deep. | |
| 50μA..... | \$2-10 |
| 50-0-50μA..... | \$2-10 |
| 100μA..... | \$2-10 |
| 100-0-100μA..... | \$2-10 |
| 200μA..... | \$2-10 |
| 500μA..... | \$2-75 |
| 1mA..... | \$2-45 |
| 300V. A.C..... | \$2-45 |
| VU Meter..... | \$2-40 |

Send for illustrated brochure on SEW Panel Meters—discuss quantities.

MULTIMETERS for EVERY purpose!




HOKI MODEL 780X
 20,000 O.P.V.
 Overload protection.
 5/25/100/500/1000 VDC.
 10/50/250/1000 VAC.
 50 mA/250 mA. 20KΩ meg ohm -2 to +62db.
 \$4-97. P. & P. 15p.




MODEL PL436
 20kΩ/Volt D.C.
 8kΩ/Volt A.C.
 Mirror scale.
 -6/3/12/30/120/600V
 D.C. 3/30/120/600V
 A.C. 50/600mA/60/
 600 mA. 10/100K/
 1 Meg 10 Meg Ω.
 -20 to +46db. \$8-97/P & P 12p



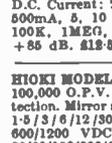
MODEL 5025 67 Ranges,
 Giant 5 1/2 in. Meter, Polarity
 Reverse Switch.
 Sensitivity: 50K/Volt D.C.
 5K/Volt A.C. D.C. Volts:
 -125, -25, -125, -10, 25,
 50, 125, 250, 500, 1,000V.
 A.C. Volts: 1-5, 3, 5, 10, 25,
 50, 125, 250, 500, 1,000V.
 500mA, 5, 10 amp. Resistance: 2K, 10K,
 100K, 1MEG, 10MEG. Decibels: -20 to
 +85 db. \$18-50. P. & P. 17p



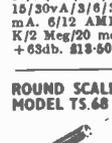
HOKI MODEL 700X
 100,000 O.P.V. Overload protection.
 Mirror scale. 3/6/12/2/1-5/3/6/12/30/60/120/300/600/1200 VDC. 1-5/3/6/12/30/60/120/300/600/1200 VAC. 15/30V A/3/6/30/60/150/300 mA. 6/12 AMP DC. 2K/20K/2 Meg/20 megohm. -20 to +63db. \$18-50. P. & P. 20p.



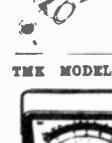
ROUND SCALE TYPE PENCIL TESTER
 MODEL TS.68
 Completely portable, simple to use pocket sized tester.
 Range: 0/5/30/300V AC and DC at 2,000 ohms.
 Resistance 0-20K ohms.
 ONLY \$1-97 P. & P. 13p



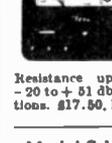TMK MODEL 117 P.E.T. ELECTRONIC VOLTMETER
 Battery operated,
 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2".
 DC VOLTS 0-3-1200V. AC VOLTS 3-300V RMS. 8-0-300V P-P. DC CURRENT -12-125mA.
 Resistance up to 2000K ohm. Decibels -20 to +51 db. Complete with leads/instructions. \$17-50. P. & P. 20p.



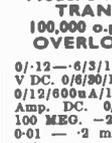Model S-100TR MULTIMETER
 TRANSISTOR TESTER
 100,000 O.P.V. MIRROR SCALE
 OVERLOAD PROTECTION
 0/12-6/3/12/30/120/600 VDC. 0/6/30/120/600 VAC. 0/12/600mA/12/300MA/12 Amp. DC. 0/10K/1 MEG/100 MEG. -20 to +50 db. 0-01 -2 mfd. Transistor tester measures Alpha, Beta and Ico. Complete with batteries, instructions and leads. \$18-50. P/P 25p.




TE22 SINE SQUARE WAVE AUDIO GENERATORS
 Sine: 20cps to 200 kc/s on 4 bands.
 Square: 20cps to 30 kc/s. Output impedance 5,000 ohms. 200/250V. A.C. operation.
 Supplied brand new and guaranteed with instruction manual and leads. \$17-50. Carr. 37p



TE-20RF SIGNAL GENERATOR
 Accurate wide range signal generator covering 120 kc/s-360 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V. A.C. Brand new with instruction manual and leads. \$18. P. & P. 37p. S.A.E. for details.



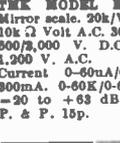MODEL LT.101 1000 O.P.V.
 0/10/50/250/1000 V. D.C.
 0/10/50/250/1000 V. A.C.
 0/1/100 M.A. 0/150 K ohms.
 \$1-97. P. & P. 15p.



TMK MODEL MD.180
 Mirror scale. 30kΩ/Volt D.C.
 10kΩ/Volt A.C. 30/60/300/
 600/5,000 V. D.C. 6/120/
 1,200 V. A.C.
 Current 0-60mA/0 -12/0
 300mA. 0-60K/0-6 Meg Ω.
 -20 to +43 db. \$4-65P.
 P. & P. 15p.



MODEL 500 30,000 O.P.V.
 with overload protection
 mirror scale 0/5/3/6/10/25/
 100/250/500/1,000 V. D.C.
 0/3/6/10/25/100/250/500/
 1,000V. A.C. 0/500A/5/50/
 500mA. 12 amp. D.C.
 0/60K/6 Meg./60 Meg Ω.
 \$2-87P. Post paid.



TMK LAB TESTER.
 100,000 O.P.V. 6 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: 5-2.5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 10, 50, 50, 250, 500, 1,000V. D.C. Current: 10, 100μA, 10, 100, 500mA. 2-5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100 MEG Ω. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size 7 1/2 in. x 6 1/2 in. x 3 1/2 in. \$18-90. P. & P. 2

HI-FI EQUIPMENT

SAVE UP TO
33 1/3% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!



RECORD DECKS

| | | |
|--------------|----------|--------|
| BER | 401..... | £26-60 |
| UA50† | £4-97 | |
| C129† | £6-50 | |
| MP60 | £10-40 | |
| 610 | £14-07 | |
| 610 | £11-50 | |
| 610 | £9-40 | |
| 610 | £33-45 | |
| MP60/ | | |
| 9800* | £12-90 | |
| MP60 TPD1 | £17-18 | |
| MP60/TPD1/ | | |
| 6800* | £19-50 | |
| MP60 TPD2 | £15-40 | |
| 610 TPD1 | £29-55 | |
| 610 TPD1 | £19-80 | |
| 610 Package* | £9-55 | |
| HT 70 | £14-99 | |
| HT70/ | | |
| 9800* | £17-85 | |
| HT 70 Pack | £21-60 | |
| HT70/Pack/ | | |
| 9800* | £23-65 | |

| | | |
|----------|--------|--|
| GARRARD | | |
| 3025 7C* | £3-60 | |
| 402* | £2-95 | |
| SP25 III | £10-95 | |
| SL65B | £13-45 | |
| AP76 | £18-95 | |
| SL72 | £23-95 | |
| SL95B | £23-60 | |

† Mono * Stereo Cartridge
All other models less Carriage
Carriage 50p extra any model.

RECORD DECK PACKAGES

Decks supplied with cartridge ready wired in teak veneered plinth with cover.

| | |
|-------------------------|--------|
| Garrard 3025TC/9TAHCD | £12-95 |
| Garrard SP25 III/9TAHCD | £16-95 |
| Garrard SP25 III/G800 | £18-50 |
| Garrard SP25 III/M75-6 | £19-50 |
| Garrard SP25 III/M44-7 | £19-75 |
| Garrard SP25 III/M44-E | £20-95 |
| SP25 III/G800 Play on C | £19-75 |
| Garrard AP76/G800 | £23-75 |
| Garrard AP76/M75-6 | £20-25 |
| Garrard AP76/M55E | £22-25 |
| Garrard AP76/M75EJ | £24-25 |
| Garrard AP76/G800E | £20-75 |
| BRR McDonald MP60/G800 | £19-95 |
| BRR McDonald MP60/M44-7 | £20-95 |
| BRR McDonald MP60/M44-E | £21-90 |
| Golding GL72/G800 | £24-50 |
| Golding GL75/G800 | £41-95 |
| Golding GL75/G800E | £44-95 |

Carriage 80p any item.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R: 10-11.1 megΩ, 6 Ranges ±1%, L: 1 μH - 111 HENRYs 6 Ranges ±1%, C: 10pF ± 1110mF, 6 Ranges ±2%, TURNS RATIO 1:1/1000-1:11100, 6 Ranges ±1%, Bridge voltage at 1,000 cps. Operated from 9 volts, 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. £20. P. & P. 25p

LATEST CATALOGUE

Our 7th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 60p



SEND NOW

ONLY
40p
P & P
10p

KEYWOOD CX200 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 KHz and 55 to 30 MHz. Illuminated slide rule dial. Bandspread Aerial tuning. BFO. AVC. ANL. '8' meter. AM/CW/SSB. Integrated speaker and phone socket. Operation 220/240v AC or 12v DC. Size 325 x 268 x 150 mm. Complete with instructions and circuit. £28-50. Carr. 50p

TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/ Amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/Cer phono inputs. AFC/Built-in MPX. List £51. OUR PRICE £28-75. Carr. 50p.

* TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6-87 1/2. P. & P. 12 1/2p. Stereo multiplex adaptors £4-97 1/2.

MP7 MIXER PREAMPLIFIER

6 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2 x 5 x 3". Inputs Mics: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV V. £8-97. P. & P. 20p.

SINCLAIR IC-12

List Price £2-98
OUR PRICE £1-80
P. & P. 10p

NS-1600W STEREO AMPLIFIER

Exceptional budget price amplifier. All silicon transistor. Handsome Walnut case. Switched input selector, separate balance, volume, treble, bass controls. Output 2 x 6W RMS. Inputs Mag. Tape, Xtal. Tuner, Tape Out. £14-75. Carr. 37p.

SH.801 HEAD-SET AND BOOM MICROPHONE
Moving coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms £4-82. P. & P. 15p.

WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5" dia. Impedance 4/8 ohms. High flux ceramic magnet. 20 watts r.m.s. Brand new £1-50. Carr. 37p.




MCA. 230 AUTOMATIC VOLTAGE STABILISER

Input 88-125 VAC or 174-250VAC. Output 120VAC or 240VAC. 200VA rating. £11-97. Carr. 50p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

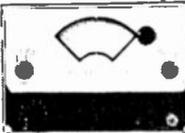9in 1R - 200,000 Hz; Square 18 - 50,000 Hz Output max. + 10 dB (10 K ohms). Operation internal batteries Attractive 2-tone case 7 1/2 x 5 x 2". Price £17-50. Carr. 17p.



SINCLAIR EQUIPMENT

Project 60. Package offers.



2 x Z30 amplifier, stereo 60 pre-amp, PZS power supply. £15-95 Carr. 37p. Or with PZ6 power supply £18-00 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. £20-55 Carr. 37p. Transformer for PZ8. £3-97 extra. Add to any of the above £4-45 for active filter unit and £18-80 for pair of Q16 speakers. Project 60 FM Tuner £18-75. Carr. 37p. All other Sinclair products in stock. 2000 Amp £31-95 Carr. 37p. 3000 Amp £36-50 Carr. 37p. 4000 Amp £43-95 Carr. 37p. IC12 £1-80 Post 10p NEW PROJECT 605 - £20-97. Carr. 37p.

220V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 60 RPM CW; 30 RPM CW; 2R/HR ACW; 2R/HR CW; 10 RPM ICW; 20R/HR ACW. 50p each Post 12p.



SDH 8V HI-FI PHONES

Input 8-16Ω Frequency 20-18,000 Hz stereo or mono switch, separate volume controls each earpiece, padded headband. £3-97. P/p 20p



HELICAL POTENTIOMETERS 1TT MCPM15 10 TURN 2 1/2 WATTS

Available 500 ohm, 1K, 5K ohm. £1-25 each P. & P. 15p.



340° Wide Angle 1mA Meters
MW1-6 60mm square £3-97 1/2
MW1-8 60mm square £4-97 1/2
P. & P. extra

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating Wide range exact. Single hole fixing, 1in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 90p. P. & P. 7 1/2p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1-15 P. & P. 7 1/2p. 100 WATT. 15/10/25/50/100/250/500/1000 or 2500 ohms. £1-85 P. & P. 7 1/2p.



"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

| | |
|--------------------------------------|----------------------|
| 8-900 General Purpose Bench Mounting | 5-260 Panel Mounting |
| 1 Amp | £7-00 |
| 2.5 Amp | £8-00 |
| 1 Amp | £7-00 |
| 2.5 Amp | £8-00 |
| 5 Amp | £11-75 |
| 8 Amp | £15-90 |
| 10 Amp | £23-50 |
| 12 Amp | £23-50 |
| 20 Amp | £40-00 |

Please add postage ALL MODELS INPUT 220 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS. Special discounts for quantity

SPECIAL OFFER! SINCLAIR PROJECT 60 STEREO FM TUNER




The first tuner in the world to use the phase lock loop principle—as used for receiving signals from space craft because of its vastly improved signal to noise ratio. Provides fantastic results even in difficult areas. Tuning range 87.5 to 108MHz. Automatic stereo indicator. Sensitivity: 2μV. AFC range ± 200KHz. Signal to noise ratio: 65dB. Output voltage 2 x 150mV. Operating voltage 25-30V. D.C. Size: 9 1/2 x 4 1/2 x 207 mm. REC. LIST PRICE £25.

OUR PRICE ONLY **£15-75** P. & P. 25p

Unrepeatable offer—buy now and save over 60

PS14 REGULATED POWER SUPPLY

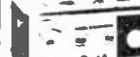Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240v AC. Size 185 x 85 x 105mm. £8-97. P. & P. 25p.




PS.1000B REGULATED POWER SUPPLY

Solid state. Output 0, 5 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240v AC. Size 4" x 3 1/2" x 6 1/2". £11-97. P. & P. 25p.



LAFAYETTE HA-600 SOLID STATE RECEIVER

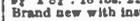General coverage 150-400kc/s. 550 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O. noise limiter. S. Meter. Bandspread. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £50. Carr. 60p.



UNR-90 RECEIVER

4 Bands covering 850kc/s-30mc/s. B.F.O. Built-in Speaker 220/240v. A.C. Brand new with instructions. £15-75. Carr. 37p.



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

| | | |
|---------|--------|-------------|
| 50 W. | £2-10 | P. & P. 18p |
| 150 W. | £2-70 | P. & P. 18p |
| 300 W. | £3-60 | P. & P. 25p |
| 500 W. | £5-25 | P. & P. 35p |
| 1000 W. | £7-50 | P. & P. 38p |
| 1500 W. | £10-80 | P. & P. 45p |
| 2250 W. | £17-25 | P. & P. 60p |
| 5000 W. | £26-00 | P. & P. 81 |

G.W. SMITH & CO. (RADIO) LTD

10 TOTTENHAM CT. RD. LONDON, W.1
27 TOTTENHAM CT. RD. LONDON, W.1
257/258 TOTTENHAM CT. RD. LONDON, W.2
3 LISLE STREET, LONDON, W.C.2
34 LISLE STREET, LONDON, W.C.2
311 EDGWARE ROAD, LONDON, W.2

Tel: 01-637 2232
Tel: 01-636 3715
Tel: 01-580 0670
Tel: 01-437 8204
Tel: 01-437 9155
Tel: 01-262 0387

CALLERS WELCOME MONDAY TO SATURDAY 9AM-6PM

All Mail Orders to 11-12, Paddington Green, London W.2. Tel: 01-262 6562

Everyday Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 10p. extra. Semi-display—£8.00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisements Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

SERVICE SHEETS

SERVICE SHEETS (1925-1972) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex. Tel: Hastings 29066.

RECEIVERS and COMPONENTS

COMPONENT CATALOGUE AND DISCOUNT VOUCHERS

25p POST FREE (UK)

W.E.C. LTD
HIGH STREET, RIPLEY, SURREY.

SOUND SUPPLIES

(Electronics) Co. Ltd.
P.A. EQUIPMENT, Marshall amps, instruments and guitars, etc. TOA and Eagle amps and accessories. Reslo mics, etc.
COMPONENTS. Resistors, capacitors, plugs, sockets, cables, audio leads, semiconductors, valves, vero board, etc., for the constructor. Power packs and car droppers for the cassette recorder or radio.
S.A.E. for list and enquiries. P.A. list 15p.
12 Smarte Lane, Loughton, Essex
Tel. 01-508 2715 Closed all day Thursday

TRANSISTORS: mint, branded top grade AD161/162 c.p.r., 60p; BC107B, 12p; BC169C, 10p; 2N2926G, 12p; 2N3702, 10p; 2N3704, 10p. Diodes: OA90, 6p; IN4002, 5p. Mail order only, UK postage 5p. **AMATRONIX LTD.**, 396 Selsdon Rd., South Croydon, Surrey, CR2 0DE.

C. F. COLE

153 Western St., Swansea
SA1 3JY

RS (Radiospares) COMPONENTS

Quotation by return

COMPUTER PANELS 58C108, diodes, 4-50p post 10p. **PANELS WITH SILICON AND GERM/TRANS.** at least 50. 6—£1.00 post 15p. **UNIT WITH 4-LA2 POT CORES CAPS** 50p post 15p. **ICs 7400 SERIES ON PANEL(S)** 10—75p post 10p. **FALLOUTS** 5—13p. **ORP12** on panel ex equip. 35p cp. **WIRE ENDED NEONS** 10—45p, 20—75p post 5p. **SEND LARGE S.A.E. FOR LIST OF PANELS ETC.**
7LB ASSORTED COMPONENTS £1.30 cp.
J.W.B. RADIO
75 HAYFIELD ROAD SALFORD 8 LANCS
MAIL ORDER ONLY

NEW MODEL V.H.F. KIT Mk 2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 + p. & p. 10p U.K. only.

Illustrated catalogue of selected kits and components. 15p P. & P. free.

Galleon Trading Co., Dept E.E.
12 Burs Way,
Coringham,
Stanford-le-Hope, Essex.

EXPRESS COMPONENTS

17 Albert Square, Stratford,
London E15 1HJ

ELECTRONIC KITS FOR E.E. PROJECTS

Have you waited weeks (or months) in the past for your electronic components to arrive??? Well you won't have to any more—not if you order from us!!! It is our intention to satisfy our customers—quickly and completely!!! This month's bargains are:—

| | |
|----------------------------------|-------|
| HORSES FOR COURSES | £2.00 |
| WASH/WIPE CONTROLLER | £2.10 |
| SIGNAL INJECTOR | £0.75 |
| ELECTRONOME | £1.65 |
| SHAVER INVERTER (20 watt) | £3.75 |
| INFRARED BURGLAR ALARM | £3.30 |

These kits comprise all electronic components to complete the project.

OTHER COMPONENTS Transistors: AD142 (similar characteristics to OC28, OC28, OC29 OC35). 35p each; Relays: 185Ω 2-pole change over 5A contacts. £1.00 each; Wafer switches: 1-pole 12-way, 4-pole 3-way, 3-pole 4-way. 20p each; Microswitch: S.P.C.O. 19p each; Potentiometers: 25kΩ log. .12p each, 250kΩ log with D.P.D.T. switch. .20p each; Mains neons (with resistor). .20p each.

Orders over 50p post free, others add 5p.

MAIL ORDER ONLY

EDUCATIONAL

TECHNICAL TRAINING in Radio, TV & Electronics through world-famous ICS. For details of proven home-study courses write: ICS (Dept. 566), Inter-text House, London, SW8 4UJ.

MEN! You can earn £50 p.w. Learn computer operating. Send for FREE brochure—London Computer Operators Training Centre, G22 Oxford House, 9-15 Oxford Street, London, W.1.

FREE

TO ENGINEERS

Whatever your age or experience you must read New Opportunities. It describes the easiest way to pass A.M.S.E., A.M.I.M.I., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering Mechanics, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book.

Send for your copy today—FREE!

B.I.E.T. B32, Aldermaston Court,
Reading, RG7 4PF

Accredited by the Council for the
Accreditation of Correspondence Colleges

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

CASSETTES

TOP QUALITY, low noise audio magnetics cassettes with fitted screws, in library case, C60 30p, C90 40p, C120 50p, P&P 15p. Ingo Ltd., 72 West End Lane, London, NW6.

MISCELLANEOUS

RECORD TV SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. **CROWBOROUGH ELECTRONICS (E.E.)**, Eridge Road, Crowborough, Sussex.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p post free.

"SHORTWAVE VOICES OF THE WORLD." £1.55. An exceptional book. "World Radio TV Handbook," December 1971, £2.80. "How to Listen to the World," 1971, £1.35. Under £2, postage 10p. Deliveries first class mail, ask for price list. CWO or send no money—COD 25p. **DAVID MCGARVA**, Box 114a, Edinburgh EH1 1HP.

MUSICAL MIRACLES

KITS to build quality accessories:—

WAA-WAA all parts, electronic & mech. £2.95
FUZZORAMA quality fuzz box £4.75
BASS PEDAL 16' and 8' tones £33

BUILD A SYNTHESIZER OR AUTO RHYTHM from Dewtron professional modules

Cat. 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AR

BEGINNERS

You can soon be designing your own circuits with **ELECTROLEARN** kits as used in Universities, Colleges and Schools.

Unique circuit board eliminates soldering. Completely self contained, no additional components or textbooks required.

KIT 1

Basic electricity; diodes; transistors; switching and computer circuits introduced through 26 graded experiments.

£9.75 including a MULTIRANGE TESTMETER.

KIT 2

Extends Kit 1 to amplifier, oscillator and radio circuits.

£7.75 including a SIGNAL GENERATOR.

Post and package 25p per kit.

ELECTROLEARN

88 HILTINGBURY ROAD, BARTLEIGH, HANTS.
Money refunded if kits are returned within 7 days.

OMNI-DETECTORS

(Featured ★ TV ★ Radio ★ National Press)
Ancient art of Dowsing in Modern Guise. Experience thrill of the old days of Wireless in this overlooked aspect of the Electro-Magnetic Spectrum. A LABORATORY IN A SINGLE PAGE. If you enjoy Treasure Hunting, use **OMNI-DETECTORS** to:—

- ★ Locate ANY buried substance, ANY depth.
- ★ Save hours of fruitless searching—MAP-DOWSING pinpoint search area before you leave home.
- ★ Analyse ground under your feet without even scratching the surface.
- ★ Limitless other uses involving health, food, sex, money. **YOU WILL BE FASCINATED.**

Send only £2.80 + 15p p & p for unique pack of 4 dowsing instruments (non-electronic) and explicit 60-page manual to sole suppliers: **OMNI-DETECTOR CO.** (Dept. EE), 27 Latham Road, Twickenham, Middx. TW1 1BN.

12 VOLT FLUORESCENT LIGHTS

(as illustrated)



Beat power cuts, be independent. Ideal for Caravans, Tent, Emergency Lighting, etc. Works anywhere where 12V is available. Guaranteed for six months. **READY TO USE** at:—

12ins 8watt £3.60 post paid
21ins 13watt £4.60 post paid

SALOP ELECTRONICS
23 Wyle Cop
Shrewsbury,
Shropshire.

Callers welcome for lists or Enquiries Large S.A.E.

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW
S.A.E. for details

TO: BOFFIN PROJECTS,
DEPT. KEE,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY

Please mention EVERYDAY ELECTRONICS

when replying to Advertising

IT COSTS NO MORE

To use guaranteed professional components. Don't risk failure in your building projects by using suspect junk-box items. We are able to supply, mostly by return of post, the entire range distributed by R. S. Components Ltd.



Printed Circuit type CAPACITORS, electrolytic, low voltage, small size, in the following $\mu\text{F/V}$: 0-47/63, 1/63, 4-7/40, 10/63, 22/40, 100/10, at 7p each, 42/40 at 18p each, 100/63, 22/40 at 470/16 at 13p each, 1000/16 at 18p each.

Phenolic Resin Boards, 172 x 133 x 1.57mm, punched 6.3mm grid, as used for Demo Deck, at 22p each. Turret Tags for above Boards, at 85p per pack of 144.



Miniature Moulded Bridge RECTIFIERS for printed circuit mounting. REC 60, 800 volts, 0.9 amp, 38p each. REC 65, 800 volts, 1.3 amps, 45p each.

All of the above and many, many other high grade components, are shown in our CATALOGUE. Price 25p by return of post.

All prices POST FREE in U.K.
Mail Order Only From—

NEW

15 watt Hi Fi AMPLIFIERS

Frequency response 15 to 19,000cs. Signal to noise > 70db. Input sens. 750mV into 2k.

HI ELECTRONICS
105, GRANGE ROAD, LONDON S.E. 25

£3.75 each
plus 25p p&p

BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 20 cycle, 0.38 amp (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.50 plus 35p P. & P. or less transformer £2.25 plus 27p P. & P.

CONSTANT SPEED, PRECISION MADE 6 VOLT D.C. GOVERNOR MOTOR

Seven pole armature, ballrace bearing. 2,750 r.p.m. Length 2H. Dia 1/2. Shaft length 1/2. Shaft dia. 5/64. No load 40 mA. Normal load 350 mA. Price £1.25 P. & P. 10p.

230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox. 5 R.P.M. A/cw 1 R.P.H. A/cw 6 R.P.H. cw 2 R.P.H. A/cw 3 R.P.H. A/cw 3 R.P.H. cw 3 R.P.H. A/cw 3 R.P.H. cw

60 R.P.M. cw 3 R.P.H. A/cw 30 R.P.H. cw cw = Clockwise. A/cw = Anti-clockwise. Fraction of makers' price. Allat 75p incl. P. & P.

"HONEYWELL" LEVER OPERATED MICRO SWITCH

15 amps. 250 volt A.C. c/o contacts. NEW in maker's Carton. Price: 10 for £1.90 incl. P. & P.

PROGRAMME TIMERS

240V A.C. 5 r.p.m. motor. 2 models available with either 10 cams or 15 cams. Each cam operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW 10 cam £4.75 p. & p. 25p. 15 cam £5.75 p. & p. 25p.

Simple 9 cam programme 9 x 5 amp 1M, 1B Microswitches driven by 115/230V A.C. 15 r.p.m. motor. Solid fibre cams adjustable. Price £3.50 p. & p. 25p.



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2 batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.00. P. & P. 22p.

50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instruction. £1.75 incl. post.

VENNER Electric Time Switch

200/250V Ex. GPO. Tested. Manually set on, 2 off every 24h. Override switch: 10A £2.75, 15A £3.25, 20A £3.75, 30A £3.95. P. & P. 20p. Also available with solar dial on dusk, OFF dawn. Price as above.

PARVALUX TYPE SD2. 200/250 VOLT A.C. D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated adjacent. PRICE: £1.75 P. & P. 25p

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/140V a.c. 50/60 OUTPUT VARIABLE 0.260V from 1/2 to 50 amp stock. SHROUDED TYPE
1 amp, £7.00 2.5 amp, £8.05
5 amp, £11.75
10 amp, £22.50 20 amp, £49.00
15 amp, £25.50 25 amp, £38.00
37.5 amp, £82.00 50 amp, £98.00
OPEN TYPE (Panel Mounting) 1 amp, £4.75.
1 amp, £7.00 2 1/2 amp, £8.05. All types carriage paid.



Superior Quality Precision Made

NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 165mA 5 kΩ, 140mA. Diameter 3/4in Shaft length 1/2in, dia. 1/8in. All at £1.65 each. P. & P. 7p.
50 WATT. 1/5/10/25/50/10C/250/500/1k/1.5k/2.5k/5kΩ. All at £1.15 each. P. & P. 7p.
25 WATT. 10/25/50/100/250/300/500/1k/1.5k/2.5k/3.5kΩ. All at 90p each. P. & P. 7p.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.
EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 36 Flash per sec. All electronic components including Varoboard S.C.R. Unijunction Xenon Tube and instructions £6.30, plus 25p P. & P.
NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.
HY-LIGHT STROBE *MK III!
Designed and produced for use in large halls and utilises a silica tube printed circuit. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12.00. P. & P. 50p.
SPECIALLY DESIGNED. FULLY VENTILATED METAL CASE. Including reflector. £4.00 P. & P. 45p. Post paid with kit.

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe. Incorporating:
● Variable speed from 1-23 flash per sec.
● Reactor control circuit producing an intense white light. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.
ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Light Kit including reflector £7.00 P. & P. 45p.
7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 53p, P. & P. 13p or post paid with kits.
6 in colour wheel as used for disco lighting effects etc. £5.75 incl. P. & P. can be operated from our 1 rpm synchronous motor 75p incl. P. & P.

RELAYS New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

| 1 | 2 | 3 | 4 | 1 | 2 | 3 | 4 |
|-----|-------|----------|------|-------|--------|----------|------|
| 52 | 3-6 | 2 c/o | 63p* | 700 | 15-35 | 2 c/o HD | 73p* |
| 280 | 9-12 | 2 c/o | 73p* | 700 | 16-24 | 6M | 65p* |
| 410 | 10-18 | 4 c/o | 73p* | 1,250 | 24-36 | 4 c/o | 63p* |
| 700 | 16-24 | 4M 2B | 63p* | 2,500 | 36-45 | 6M | 63p* |
| 700 | 16-24 | 4 c/o | 78p* | 2,400 | 30-48 | 4 c/o | 50p* |
| 700 | 12-24 | 2 c/o | 63p* | 9,000 | 40-70 | 2 c/o | 50p* |
| 700 | 6-12 | 1 c/o HD | 50p* | 15k | 85-110 | 6M | 50p* |
| 700 | 22-30 | 6 c/o | 73p* | | | | |

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. *Including Base.

12 VOLT D.C. RELAY 140 OHM COIL

Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)

'DIAMOND H' 230 VOLT A.C. RELAYS

Three sets c/o contacts rated at 5 amps. Price: 50p P. & P. 10p. (100 lots £40.00 incl. P. & P.) (UNUSED)

'KEY SWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. BOXED. Price: 40p. P. & P. 5p. (100 lots £32.00 incl. P. & P.)

MINIATURE LATCHING RELAY

Manufactured by Clare-Elliott Ltd. (Type F). 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size 1" high 1" wide, 1" thick. Complete with 3' leads. New 73p. incl. P. & P.

MICRO SWITCH—very special offer

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 incl. post. (Min. order 20)

600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3 incl. P. & P.

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. E.E. 57 Bridgman Road, Chiswick, London, W4 5BB
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.
Personal callers only. Open Sat.
9 LITTLE NEWPORT ST.
LONDON WC2H 7JJ 01-437 0576

HENRY'S - Your complete Semi-Conductor Store!

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIR-CHILD

| Type | 1/11 | 12/24 | 25/99 | Type | 1/11 | 12/24 | 25/99 | Type | 1/11 | 12/24 | 25/99 |
|--------|------|-------|-------|---------|------|-------|-------|---------|------|-------|-------|
| BN7400 | 0.20 | 0.18 | 0.16 | BN7450 | 0.20 | 0.18 | 0.16 | BN74145 | 1.50 | 1.40 | 1.30 |
| BN7401 | 0.20 | 0.18 | 0.16 | BN7451 | 0.20 | 0.18 | 0.16 | BN74150 | 3.85 | 3.95 | 2.18 |
| BN7402 | 0.20 | 0.18 | 0.16 | BN7453 | 0.20 | 0.18 | 0.16 | BN74161 | 1.10 | 0.95 | 0.90 |
| BN7403 | 0.20 | 0.18 | 0.16 | BN7454 | 0.20 | 0.18 | 0.16 | BN74153 | 1.85 | 1.87 | 1.20 |
| BN7404 | 0.20 | 0.18 | 0.16 | BN7460 | 0.20 | 0.18 | 0.16 | BN74154 | 2.00 | 1.75 | 1.55 |
| BN7405 | 0.20 | 0.18 | 0.16 | BN7470 | 0.20 | 0.27 | 0.25 | BN74155 | 1.55 | 1.47 | 1.35 |
| BN7406 | 0.20 | 0.27 | 0.25 | BN7472 | 0.30 | 0.27 | 0.25 | BN74156 | 1.55 | 1.47 | 1.35 |
| BN7407 | 0.20 | 0.27 | 0.25 | BN7473 | 0.40 | 0.37 | 0.35 | BN74157 | 1.60 | 1.70 | 1.50 |
| BN7408 | 0.20 | 0.19 | 0.18 | BN7474 | 0.40 | 0.37 | 0.35 | BN74160 | 2.60 | 2.40 | 2.25 |
| BN7409 | 0.45 | 0.42 | 0.35 | BN7475 | 0.55 | 0.52 | 0.50 | BN74161 | 2.60 | 2.40 | 2.25 |
| BN7410 | 0.20 | 0.18 | 0.16 | BN7476 | 0.55 | 0.48 | 0.39 | BN74162 | 3.40 | 3.25 | 2.70 |
| BN7411 | 0.22 | 0.22 | 0.20 | BN7480 | 0.80 | 0.75 | 0.67 | BN74163 | 3.40 | 3.25 | 2.70 |
| BN7412 | 0.42 | 0.40 | 0.35 | BN7481 | 1.25 | 1.15 | 1.10 | BN74164 | 2.75 | 2.80 | 2.10 |
| BN7413 | 0.30 | 0.27 | 0.25 | BN7482 | 0.87 | 0.80 | 0.70 | BN74165 | 4.00 | 3.80 | 3.00 |
| BN7416 | 0.30 | 0.27 | 0.25 | BN7483 | 1.00 | 0.90 | 0.85 | BN74166 | 1.60 | 1.85 | 1.80 |
| BN7417 | 0.30 | 0.27 | 0.25 | BN7484 | 0.90 | 0.85 | 0.80 | BN74167 | 9.25 | 9.00 | 6.10 |
| BN7420 | 0.20 | 0.18 | 0.16 | BN7486 | 0.45 | 0.41 | 0.38 | BN74170 | 4.10 | 3.85 | 3.05 |
| BN7422 | 0.48 | 0.44 | 0.40 | BN7490 | 0.75 | 0.70 | 0.65 | BN74174 | 2.00 | 1.75 | 1.80 |
| BN7423 | 0.48 | 0.44 | 0.40 | BN7491 | 1.00 | 0.95 | 0.90 | BN74175 | 1.85 | 1.87 | 1.15 |
| BN7425 | 0.48 | 0.40 | 0.35 | BN7492 | 0.75 | 0.70 | 0.65 | BN74176 | 1.60 | 1.85 | 1.20 |
| BN7427 | 0.30 | 0.27 | 0.25 | BN7493 | 0.75 | 0.70 | 0.65 | BN74177 | 1.60 | 1.85 | 1.15 |
| BN7428 | 0.50 | 0.45 | 0.42 | BN7494 | 0.80 | 0.75 | 0.70 | BN74180 | 1.60 | 1.85 | 1.15 |
| BN7430 | 0.20 | 0.18 | 0.16 | BN7495 | 0.90 | 0.75 | 0.70 | BN74181 | 7.00 | 6.00 | 5.60 |
| BN7432 | 0.42 | 0.39 | 0.35 | BN7496 | 1.00 | 0.97 | 0.95 | BN74182 | 2.00 | 1.80 | 1.60 |
| BN7433 | 0.42 | 0.39 | 0.35 | BN7497 | 6.25 | 5.50 | 5.00 | BN74184 | 2.40 | 2.00 | 1.80 |
| BN7437 | 0.65 | 0.60 | 0.50 | BN74100 | 2.50 | 2.30 | 2.00 | BN74185 | 4.00 | 3.00 | 1.80 |
| BN7438 | 0.65 | 0.60 | 0.50 | BN74105 | 1.45 | 1.35 | 1.20 | BN74190 | 1.95 | 1.85 | 1.75 |
| BN7440 | 0.20 | 0.18 | 0.16 | BN74105 | 1.45 | 1.35 | 1.20 | BN74191 | 9.55 | 9.50 | 7.75 |
| BN7441 | 0.75 | 0.72 | 0.70 | BN74107 | 0.50 | 0.45 | 0.40 | BN74192 | 2.00 | 1.90 | 1.80 |
| BN7442 | 0.75 | 0.72 | 0.70 | BN74110 | 0.80 | 0.70 | 0.60 | BN74193 | 2.00 | 1.90 | 1.80 |
| BN7443 | 1.00 | 0.95 | 0.90 | BN74118 | 1.00 | 0.95 | 0.90 | BN74194 | 2.50 | 2.25 | 1.90 |
| BN7445 | 2.00 | 1.75 | 1.60 | BN74119 | 1.90 | 1.78 | 1.65 | BN74195 | 1.85 | 1.70 | 1.60 |
| BN7446 | 2.00 | 1.75 | 1.60 | BN74121 | 0.80 | 0.65 | 0.50 | BN74198 | 1.50 | 1.40 | 1.30 |
| BN7447 | 1.75 | 1.60 | 1.45 | BN74123 | 2.70 | 2.55 | 2.47 | BN74197 | 1.50 | 1.40 | 1.30 |
| BN7448 | 1.75 | 1.60 | 1.45 | BN74141 | 1.00 | 0.85 | 0.90 | BN74198 | 4.60 | 3.70 | 3.25 |

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
TEXAS HANDBOOK NO. 2. I.C. 700 PAGES DATA 60p. POST 20p.
HIGH POWER 5M 74 LOO } Now in stock—send
LOW POWER 5M 74 LOO } for list No. 36

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

| | | | | | |
|------------|------------|-------------|--------------|--------------|--------------|
| AA Y30 10p | BC147 12p | BU105 25p | OC44 15p | T1843 35p | 2N3055 55p |
| AA Y42 15p | BC169C 12p | BY100 15p | OC45 15p | V4054 25p | 2N3440 75p |
| AA Z13 10p | BC192 10p | BY120 15p | OC67 50p | ZX108 15p | 2N3442 125p |
| AC107 35p | BC214 15p | BY127 15p | OC71 15p | ZX300 15p | 2N3825 75p |
| AC126 25p | BCY32 75p | BYZ13 35p | OC72 25p | ZX301 15p | 2N3816 50p |
| AC127 25p | BCY34 35p | CI06D 65p | OC77 45p | ZX302 15p | 2N3615 75p |
| AC128 25p | BCY39 1.00 | GET111 55p | OC81 25p | ZX341 20p | 2N3702 10p |
| AC176 25p | BCY42 30p | GET115 55p | OC83 25p | ZX500 15p | 2N3704 10p |
| AC187 25p | BCY43 25p | GET180 45p | OC140 55p | ZX503 17p | 2N3705 10p |
| AC188 25p | BCY55 2.50 | LM309K 25p | OC170 25p | Z0301 30p | 2N3714 1.80 |
| ACY17 30p | BCY70 1.80 | (T03) 1.87 | OC171 30p | 2N404 25p | 2N3771 1.75 |
| ACY20 30p | BCY71 20p | MAT121 25p | OC200 45p | 2N527 35p | 2N3773 2.00 |
| ACY21 20p | BCY72 15p | MJE340 50p | OC201 75p | 2N696 15p | 2N3790 2.25 |
| ACY39 55p | BCY87 2.99 | MJE370 70p | OC202 80p | 2N697 15p | 2N3819 35p |
| AD140 50p | BCZ11 50p | MJE520 75p | OC203 50p | 2N706 15p | 2N3820 50p |
| AD149 50p | BD134 80p | MJE295 1.10 | OC271 1.25 | 2N707 20p | 2N3868 85p |
| AD161 25p | BD131 75p | MJE295 1.10 | OP112 50p | 2N987 45p | 2N3903 15p |
| AD162 25p | BD132 80p | MJE3055 75p | OP60 40p | 2N1131 25p | 2N3904 12p |
| AF117 30p | BF115 25p | MPF105 40p | P346A 20p | 2N1132 25p | 2N4061 12p |
| AF118 50p | BF167 25p | MPP105 40p | RAB310A* 45p | 2N1302 18p | 2N4062 12p |
| AF124 25p | BF173 25p | NK1214 20p | RAB508A* 45p | 2N1304 22p | 2N4126 15p |
| AF139 30p | BF179 30p | NK2716 40p | TA A263 75p | 2N1305 22p | 2N4871 35p |
| AF186 40p | BF180 30p | NK2717 55p | TIL209 39p | 2N1307 25p | 2N4857 75p |
| AF239 40p | BF194 15p | NKT403 70p | TIP29A 50p | 2N1308 25p | 2N5777 50p |
| ABY27 30p | BF195 15p | NKT404 50p | TIP29B 50p | 2N1613 20p | 28001 1.00 |
| ABY28 25p | BF861 25p | OAS 50p | TIP30A 80p | 2N1671 1.00 | 28012 1.00 |
| BA102 30p | BF898 25p | OA10 35p | TIP31A 60p | 2N2147 75p | 28018 6.25 |
| BA115 7p | BFX13 25p | OA81 10p | TIP32A 70p | 2N2149 50p | 28026 8.90 |
| BA145 15p | BFX34 75p | OA81 7p | TIP33A 70p | 2N2217 25p | 28301 50p |
| BAK13 6p | BFX37 30p | OA200 7p | TIP33A 1.00 | 2N2221 20p | 28303 65p |
| BAK16 7p | BFX84 80p | OA202 10p | TIP34A 25p | 2N2222A 25p | 28324 95p |
| BC107 10p | BFY50 20p | OC16 75p | TIP34A 1.50 | 40250 50p | 40360 40p |
| BC108 10p | BFY51 20p | OC20 95p | TIP35A 1.50 | 40361 40p | 40362 50p |
| BC109 10p | BFY52 20p | OC23 85p | TIP35A 2.50 | 2N2906 20p | 2N2926 (all) |
| BC109C 12p | BFY54 50p | OC25 40p | TIP35A 3.00 | 2N2926 (all) | 40408 75p |
| BC113 15p | BFY90 50p | OC28 65p | TIP41A 75p | 2N3053 20p | 40486 1.10 |
| BC113 15p | BLY36 8.00 | OC35 65p | TIP42A 85p | 2N3054 50p | 40430 1.00 |
| BC117 20p | BRX20 10p | OC36 65p | | | |
| BC143 35p | BSY27 15p | OC42 40p | | | |

INTEGRATED CIRCUIT SOCKETS

LOW PROFILE PLATED PINS



(16 Lead D.I.L.) 17p
(14 Lead D.I.L.) 15p
(8 Lead D.I.L.) 15p

QUANTITY DISCOUNTS

10% 12+ : 15% 25+ : ANY ONE TYPE
20% 100+ : 25% 250+ :

From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value \$1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

| | | | |
|-------------------|-----|------------------------------|-------------|
| BFY90 1000 MC/S | 59p | 2N2926 10p | All Colours |
| 25 + 20p | | 25 + 9p | |
| 100 + 17p | | 100 + 6p | |
| 500 + 15p | | 500 + 6p | |
| | | 1000 + 5p | |
| AF117 Mullard 25p | | 2N319 Texas 35p | |
| 25 + 17p | | 25 + 30p | |
| 100 + 15p | | 100 + 25p | |
| 500 + 12p | | 500 + 20p | |
| | | 1000 + 15p | |
| OC170 Mullard 25p | | BC107, BC108, BC109 10p each | |
| 25 + 20p | | All Makes | |
| 100 + 18p | | 25 + 8p | |
| 500 + 15p | | 100 + 7p | |
| 1000 + 13p | | 500 + 6p | |
| | | 1000 + 5p | |
| BY127 Mullard 15p | | AD161, AD162 35p each | |
| 25 + 12p | | 25 + 32p | |
| 100 + 10p | | 100 + 28p | |
| 500 + 9p | | 500 + 25p | |
| 1000 + 8p | | 1000 + 22p | |
| OA202 10p | | 2N3053 20p | |
| 25 + 8p | | 25 + 18p | |
| 100 + 6p | | 100 + 15p | |
| 500 + 5p | | 500 + 10p | |
| 1000 + 5p | | 1000 + 10p | |
| OC35 Mullard 50p | | 2N3055 55p | |
| 25 + 45p | | 25 + 50p | |
| 100 + 40p | | 100 + 45p | |
| 500 + 35p | | 500 + 38p | |
| 1000 + 30p | | 1000 + 33p | |

ZENER DIODES

400 M/W 5% Miniature
BZY 88 Range
All voltages 3-3-33 Volt
10p each.

25+ 9p
100+ 8p
500+ 8p
1000+ 8p

Any one type.

1 1/2 Watt 5% Wire Ends Metal Case
All voltages 6-8-100 Volts
20p each

25+ 18p
100+ 18p
500+ 18p
1000+ 10p

Any one type.

3 Watt Plastic Wire Ends 5% 8EZ Range
All voltages 6-8-100 Volts
30p each.

25+ 18p
100+ 18p
500+ 18p
1000+ 10p

Any one type.

3 Watt Plastic Wire Ends 5% 8EZ Range
All voltages 6-8-100 Volts
30p each.

25+ 18p
100+ 18p
500+ 18p
1000+ 10p

Any one type.

LINEAR (O/P AMPS)

702C TO5 75p
709C TO98 35p
709C D.I.L. 35p
725C TO99 1.00
725C D.I.L. 85p
725C TO99 4.50
741C TO99 55p
741C D.I.L. 55p
747C TO99 1.10
747C D.I.L. 1.10

7274P D.I.L. 80p
7274P D.I.L. 80p
BINCLAIR IC12 1.50

TOSHIBA TH9013P
20 WATT AMP
\$4.47 POST PAID
TH9014P Pre Amp \$1.60

DATA AND CIRCUITS REF. 42 10p

FREE WITH PURCHASES

TRANSISTORS, IC's, TRIACS, BRIDGES, SCR's, LDR's

5 Watt Plastic Wire Ends 5% 8EZ Range
All voltages 6-8-100 Volts
30p each.

25+ 18p
100+ 18p
500+ 18p
1000+ 10p

Any one type.

3 Watt Plastic Wire Ends 5% 8EZ Range
All voltages 6-8-100 Volts
30p each.

25+ 18p
100+ 18p
500+ 18p
1000+ 10p

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated Telescopic Aerial, for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)



ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Overseas P. & P. £1

ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.

Total building costs **£5-98** P. P. & Overseas P. & P. £1

ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpieces with plug and switched socket for private listening 80p extra.

Total building costs **£3-98** P. P. & Overseas P. & P. £1

POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-29** P. P. & Overseas P. & P. 65p

TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES
3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Overseas P. & P. 43p

TRANS EIGHT

8 TRANSISTORS and 3 DIODES
6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P. P. & Overseas P. & P. £1

NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.
COMPONENTS INCLUDE:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 3 inch Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 7" Knobs.
Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction

All parts including **£5-50** P. P. & Case and Plans Ins. 31p (Overseas P. & P. £1)

FULL AFTER SALES SERVICE

Callers side entrance Barratts Shoe Shop
Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Parts price list and plans for

Name

Address

(Dept. E.E.12.)

U.K.'s LARGEST ELECTRONICS CENTRES!

HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381/8382
 354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736
 309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963
 303 BARGAIN STORE SPECIAL OFFERS 01-723 1008 All Mail to: 303, Edgware Rd., London, W.2.
ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

BUILD THE TEXAN

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

★ **FREE TEAK CABINET** with complete kits!

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners, special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.
HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.
FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).



As featured in "Practical Wireless" May to August 1972

SPECIAL KIT PRICE


£28.50 P & P 45p

COMPLETE WITH FREE TEAK CABINET
 Designer approved kits only available from Henry's

★ **SLIM DESIGN WITH SILVER TRIM**
 Overall chassis size 14 1/2" x 6" x 2" high

LOW COST HI-FI SPEAKERS

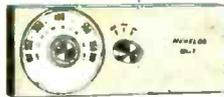E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150 TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.
POLISHED CABINETS 150, 150TC 450 £4.60. Post 30p.



ML-3 MW/LW TUNER TO BUILD

Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". **TOTAL COST TO BUILD** £4.85. Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD


Primed circuit all transistor design using Mullard RF/IF Module. Medium and long Wave bands plus Medium Wave. Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. **TOTAL COST TO BUILD** £7.98. p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE **55p** Post Paid (40p for CALLERS)
PLUS! FIVE 10p VOUCHERS

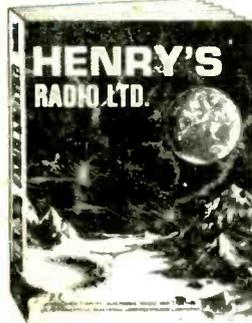Send to this address—HENRY'S RADIO LTD. (Dept. EE) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to "303" see below.



TEST EQUIPMENT

- SE250B Pocket Pencil Signal Injector £1.90
- SE500 Pocket Pencil Signal Tracer £1.50
- TE15 Grid Dip Meter 440 KHz-280 mHz £13.45
- 500 30 K/V Multimeter £9.25
- With leather case £10.50
- 200H 20K/V Multimeter £4.20. With case £4.95
- AF105 50K/V Multimeter £8.50. With case £9.50
- U43:1 A/C/D/C Multimeter with transistor tester with steel case £10.50
- TE20D RF Generator 120KHz-500MHz £15.95. Carr. 35p
- TE22D Audio Generator 20KHz-200KHz £17.50. Carr. 35p
- TO3 3" Scope 1 1/2Hz-1 1/2MHz £39.00. Carr. 50p
- CL-5 3" Pulse Scope 10Hz-10MHz £39.00. Carr. 50p
- TE65 Valve Voltmeter 28 ranges £17.50. Carr. 40p



PA-Disco-Lighting

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

- DJ30L 3 Channel sound to light unit, 3kw £28.50
- DJ40L 3 Channel Mic (Built in) to light, 3kw £37.50
- DJ70S 70 watt Disco amp/mixer £49.75
- D/SCOAMP 100 watt Disco amp/mixer £67.50
- DJ105S 30 watt Disco amp/mixer £31.00
- Anti-Feedback Quality Mic. £11.50
- SDL 12" 50 watt 8 ohm Full range speaker £12.95
- DECKS. Use MP60 or SP25/3 see above
- Matching cartridge 5CSM £2.62
- FIBRE OPTICS, LIGHTING EFFECTS, PROJECTORS, DIMMERS, MIXERS. Everything for PA—Disco—Lighting. FREE Stock List Ref. No. 18.



BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO
 A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.
TOTAL £6.97, p.p. 20p. Decoder Kit £5.97.
 Tuning meter unit £1.75
 Mains unit (optional) Model P5900 £2.47. Post 20p
 Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p



SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!

- Z30 £3.57; Z50 £4.37
- STEREO 60 PZ5 £3.97
- £7.97; PZ8 £4.77
- PZ6 £6.37;

Transformer for PZ8 £2.95
 Active Filter Unit £4.45
 Stereo FM Tuner £16.95
 IC12 £1.80; Q16's £15 pr.
 Post etc. 20p per item



PACKAGE DEALS

- Post 25p
- 2xZ30, Stereo 60, PZ5 £15.95
- 2xZ30, Stereo 60, PZ6 £18.00
- 2xZ50, Stereo 60, PZ8 £20.25
- Transformer for PZ8 £2.95
- PROJECT 605 KIT £19.95

RECORD DECKS

- CHASSIS (Post 50p)
- SP25/3 £10.75 HT70 £15.00
- MP60 £10.40 MP610 £14.15
- AP76 £18.95 GL72 £22.25
- WITH PLINTH/COVER (Post 70p)
- MP60 £17.20 TD150AB £41.45
- HT70 £21.60 PL12AC £35.25
- HL(GL75) £23.25
- MP610 £20.35 BD £32.25
- CART/PLINTH/COVER (Post 70p)
- (HL) AP76/G600/PC £29.95
- (HL) SP25-3/G800/PC £18.95
- HT70/G800/PC £37.00
- (HL) 2025TC/9TAHCD/PC £13.50
- MP60/5CSMD/PC £17.25
- (HL) GL75/G800E/PC £44.15
- (HL) GL72/800/PC £35.50

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits. £5.90 per pair. Post 10p

MARJOT TAPE HEADS

- 4 TRACK MC NO OF 2 TRACK STEREO
- '17' High Impedance £2.00
- '18' Med. Impedance £2.00
- '36' Med.-Low Imp. £3.50
- Erase Heads for above 75p
- '63' 2 track mono- £1.75
- Hi Imp.
- '43' Erase Head for above 75p

POWER INTEGRATED CIRCUITS

Plessey 5L403D—3 watt with 8-page data, layouts and circuits £1.50. P.C. Board 60p. Heat Sink 14p. Sinclair IC12—6 watt with data and circuits £1.80. TH9013P—20 watt Power Amp Module £4.57. TH9014P—IC Preamp £1.50. Data Circuits for above No. 42 10p

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
 XN3, XN13, GNE 0-9 side view with data. 85p.
 GNP-7, GNP-8 0-9 side view with decimal points and data. 95p.
 3015F 7 seg £2 each. £7 per 4 with data.
 12 and 24 hour clock circuits for above Ref. No. 31 15p.

Miniature Amplifier

5 transistor. 300mW o/p. Fitted volume and sensitivity control, 9 volt. operated. £1.75 each P/P 15p.

Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 500K. 1 meg. Log and Lin. 45p each, 10K, 25K, 50K, 100K, Log and Lin ganged. 75p each.

Hi-Fi & Tape Equipment

Acknowledged as U.K.'s Largest Stockists with Lowest Prices Plus 12 months Guarantee. Write or call for FREE 16 page lists (Ref. 16/17)

Transistors—IC's—5CR's—Rectifiers—Triacs, etc. NEW FREE LISTS Ref. No. 36 on request.

MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S
 All the parts you need plus Data and Circuits — Get a Catalogue — it's all in there!

Prices subject to change without notice E. & O.E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H