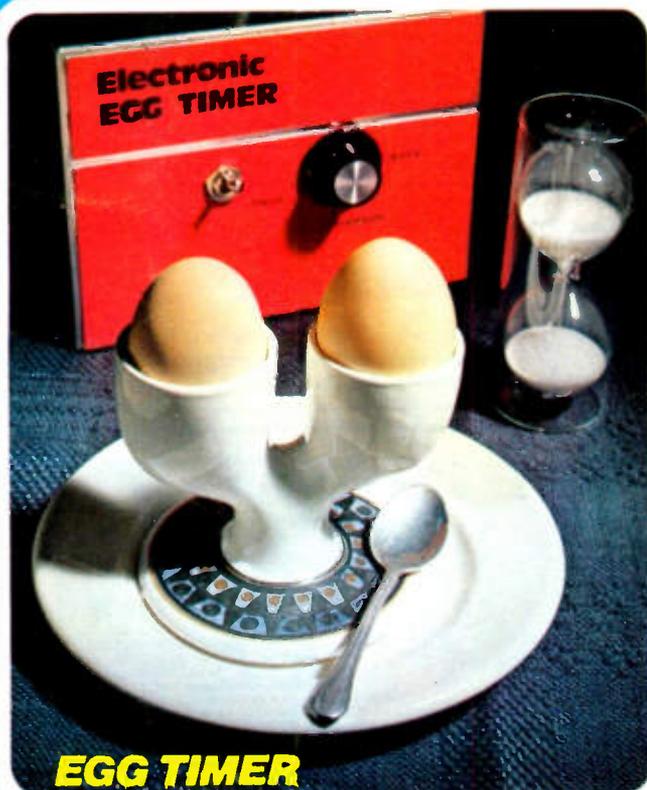



An exciting hobby.... for everyone

everyday electronics

MAR 73
15p




EGG TIMER

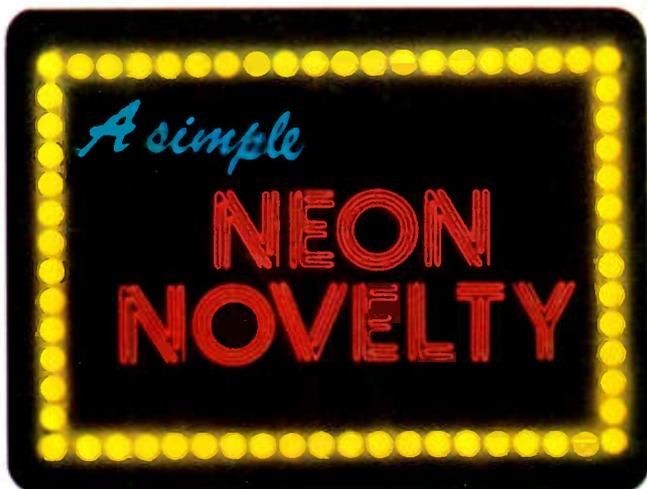


A simple

**NEON
NOVELTY**

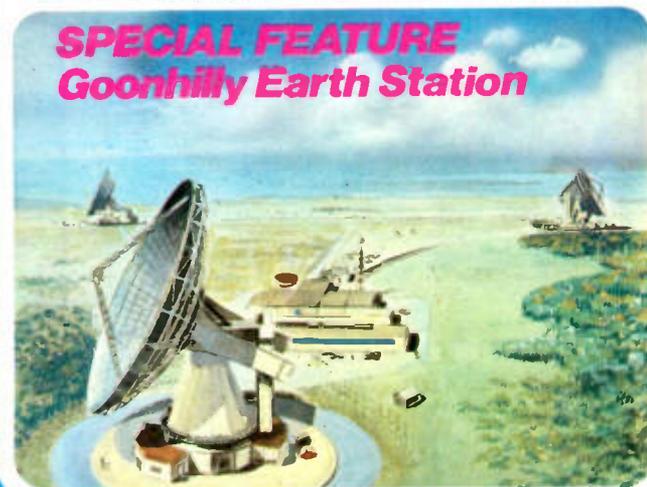

SPECIAL FEATURE
Goonhilly Earth Station

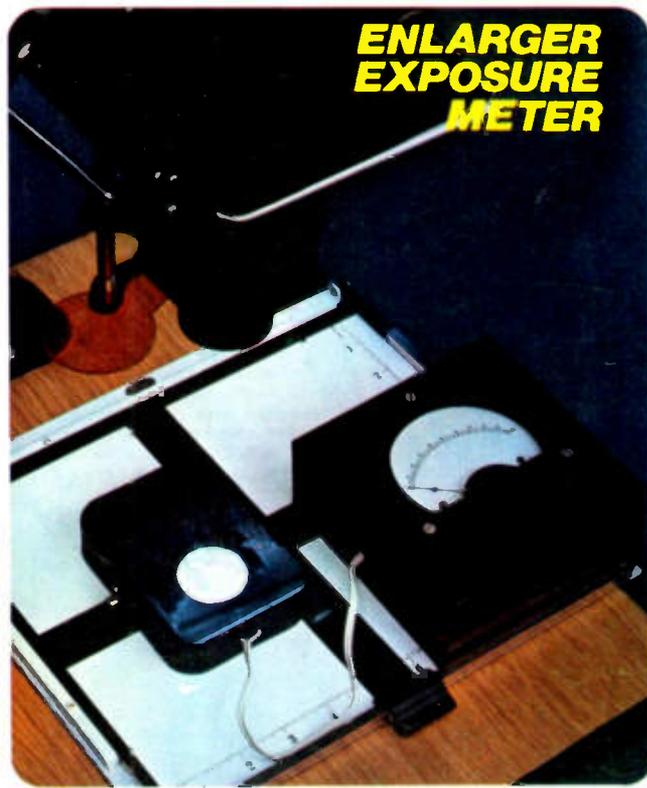

**ENLARGER
EXPOSURE
METER**

ADCOLA

meet the precision
'INVADER' SOLDERING INSTRUMENTS

Precision instruments supplied with standard detachable copper chisel face bits. Standard temp. 360°C at 19/23/27 watts. Special temps. from 250°C/410°C.



L1076
BIT SIZE 1/4"
6.34 mm Dia.
27 watts.
£2.18

For perfection
in soldering

L646
BIT SIZE 3/16"
4.75 mm Dia.
23 watts.
£2.12

L706 →
BIT SIZE 1/8"
3.2 mm Dia.
19 watts.
£1.96

Don't take chances. We don't. All our ADCOLA Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this production tool. ADCOLA day after day.

Send for **NEW** catalogue today


ADCOLA PRODUCTS LTD. ADCOLA HOUSE GAUDEN ROAD LONDON SW4 6LH
Postage, packing paid on orders over £2. under £2. add £0.10

Models required
Enclosing P/O or cheque for

Name
Address

EE9

Are you alright for Jacks?

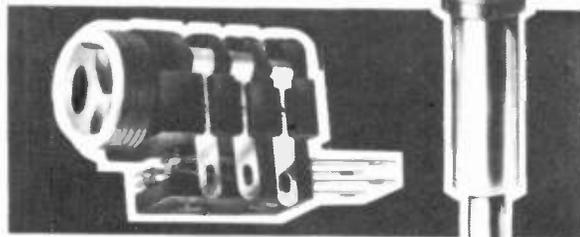

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes... plugs in both screened and unscreened versions... socket bodies in high melting point thermoplastic... several unique features (some protected by UK and US Patents)... Post Office and NATO specifications.

If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!



RENDAR®

Rendar Instruments Ltd., Victoria Road
Burgess Hill, Sussex. Tel. Burgess Hill 2642-4
Cables: Rendar, Burgess Hill



BEST OF ALL WORLDS


GIANT POWER MULTI-WAVEBAND BROADCAST RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE +40p P. & P. £10-50

No less than 3 VHF BANDS, picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHER-BAND. Frequency ranges: MW540-1600KHZ, FM88-108MHZ Airband 108-145 MHZ, VHF 145-175MHZ, 23 semi-conductors—12 transistors, 11 diodes and thermistors. Automatic frequency control. 31" telescopic aerial. Runs off mains AC 230/250 volts or off 4 U11 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10 1/2" x 6 1/2" x 3 1/2". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries FREE. HURRY! Limited quantity from Sonic Sound. Fully guaranteed.

OUR PRICE £28-95 +50p P. & P

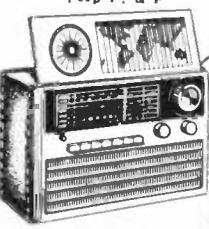


8 WAVE BANDS AND WORLD MAP TUNE ZONE DIAL

Tune into the world with this amazing world radio. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220/240 volt domestic mains supply. 14 Transistors; 9 diodes; 1 thermistor. Integral ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with earphone for personal listening. Frequency ranges: Long wave 150-350Kcs. Medium 350-1805Kcs. Marine 1.6-4.5Mcs. Short Wave 12-24Mcs. FM/VHF 88-108Mcs. Aircraft 108-135 Mcs. PUBLIC SERVICE BANDS 135-174 Mcs. Fully guaranteed.

N.B.—The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

SONIC SOUND AUDIO LTD. (Dept. ED8), 372 EDGWARE ROAD, LONDON, W.2. Tel. 01-723 0094. Callers welcome Monday to Saturday 9 a.m.—6 p.m.

The Catalogue you **MUST** have!

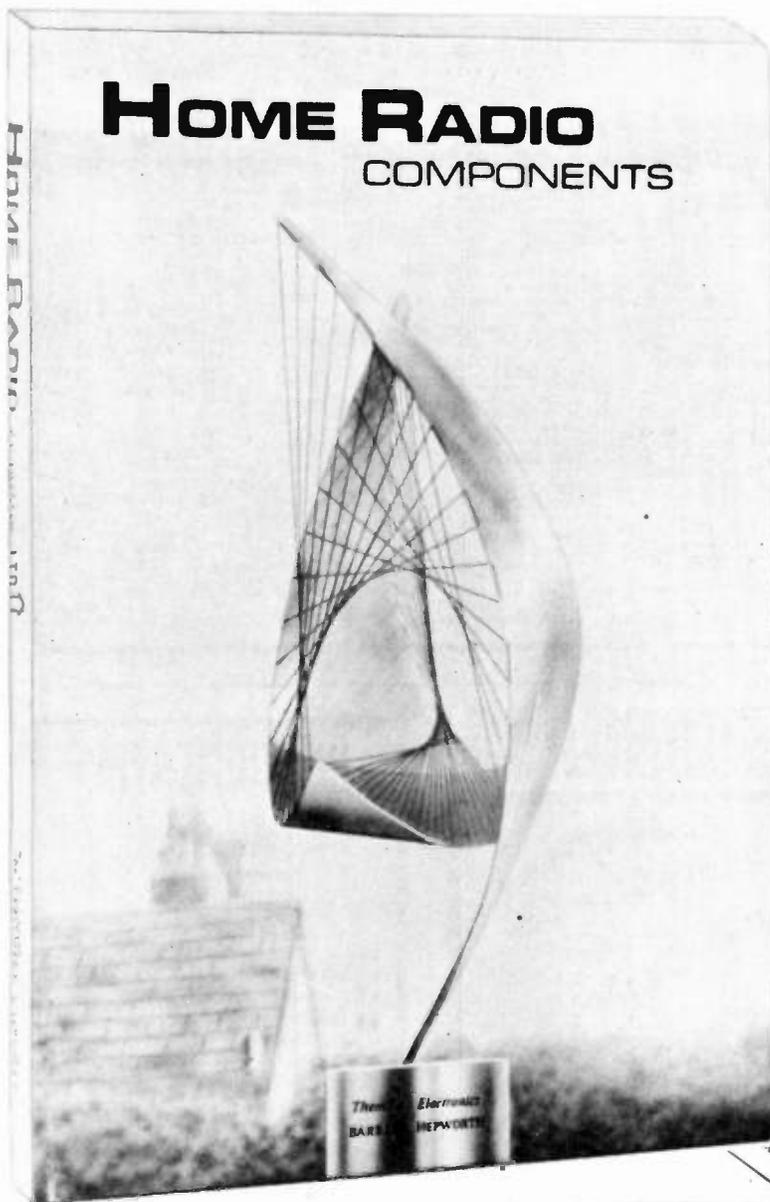

250 pages 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ "

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p. plus 20p **POST AND PACKING**

POST THIS ORDER

TRANNNIES

24, WOODHILL,
HARLOW, ESSEX

Add 5p P. & P. Price list B.A.E.
No callers please.

Phone: HARLOW 37739

(Formerly C. R. HADLEY)

All our stocks are brand new with money back refund.

TRANSISTORS

AC107	15p	AL102	50p	BD110	45p	OC14	13p	TIP33A	95p	2N3711	10p
AC126	11p	AL103	40p	BD131	50p	OC71	15p	TIP34A	11.80	40261	50p
AC127	11p	AU103	85p	BF194	10p	OC72	12p	2N697	15p	40636	50p
AC128	11p	AU111	95p	BFY50	10p	OC81	13p	2N1171	24p		
AC176	25p	BC107	8p	BFY51	12p	OC81D	13p	2N1304	25p		
AC141K	20p	BC108	8p	BSY95A	15p	OC82	20p	2N1305	25p		
AC142K	20p	BC109	8p	ME0402	18p	OC170	24p	2N2826	47p		
AD14	40p	BC154	20p	ME0404	14p	OC200	25p	2N3053	20p	1N4001	4p
AD150	44p	BC168	10p	ME4401	10p	OC201	25p	2N3055	40p	1N4002	4p
AD161		BC169	11p	ME4102	12p	OC25	25p	2N3702	12p	1N4003	5p
AD182 M/P 55p		BC182L	8p	ME6002	14p	OC28	30p	2N3703	12p	1N4004	7p
AF114	15p	BC183L	8p	ME8101	14p	OC29	30p	2N3704	12p	OA90	6p
AF115	15p	BC184L	8p	ME9102	15p	OC35	25p	2N3705	12p	OA91	6p
AF116	15p	BC212L	8p	MV9111	35p	OC36	30p	2N3706	10p	OA200	10p
AF117	15p	BC214L	8p	MP8511	34p	TIP29A	45p	2N3707	10p	OA202	8p
				MP8513	45p	TIP30A	55p	2N3708	9p	1B44	10p
				OC41	13p	TIP31A	58p	2N3709	10p	1N4149	4p
						TIP32A	60p	2N3710	10p	WQ2	32p

CAPACITORS

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0.01 μ F, 0.015 μ F, 0.022 μ F, 3p, 0.033 μ F, 0.047 μ F, 0.068 μ F, 8p, 0.1 μ F, 4p, 0.15 μ F, 0.22 μ F, 5p, 0.33 μ F, 6p, 0.47 μ F, 8p, 0.68 μ F, 11p, 1.0 μ F, 12p, 1.5 μ F, 20p, 2.2 μ F, 24p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0.001 μ F, 0.0015 μ F, 0.0022 μ F, 0.0033 μ F, 0.0047 μ F, 2p, 0.0068 μ F, 0.01 μ F, 0.015 μ F, 0.022 μ F, 0.033 μ F, 3p, 0.047 μ F, 0.068 μ F, 0.1 μ F, 4p, 0.15 μ F, 6p, 0.22 μ F, 7p, 0.33 μ F, 11p, 0.47 μ F, 13p.

160V: 0.01 μ F, 0.015 μ F, 0.022 μ F, 0.033 μ F, 0.047 μ F, 0.068 μ F, 3p, 0.1 μ F, 3p, 0.15 μ F, 4p, 0.22 μ F, 5p, 0.33 μ F, 6p, 0.47 μ F, 7p, 0.68 μ F, 11p, 1.0 μ F, 13p.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES 6p each
(μ F/V) 10/2.5, 20/2.5, 80/2.5, 160/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 5/4.6/4, 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1.6/25, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.63/64, 2.5/64, 5/64, 10/64, 20/64, 32/64.

MULLARD C437 SERIES
100/40, 160/25, 250/16, 400/10, 540/6.4, 800/4, 1000/2.5, 9p, 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1000/6.4, 1600/2.5, 12p, 160/64, 250/40, 400/2.5, 640/16, 2000/4, 1000/10, 1600/6.4, 2500/2.5, 15p, 250/64, 400/40, 1000/16, 640/25, 3200/4, 1000/16, 1600/10, 2500/6.4, 4000/2.5, 18p.

Miniature Vized Ceramic Plate, 3p each.
Preferred values from 1.8pfl to 10,000pfl.

MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0-9 and decimals
(Data Sheet on request)

ONLY £1-50

for one month only

16 DIL Socket
Driven by 7447

30p
95p

SUPER LOW
PRICED LINEAR I.C.'S

301A	To99	49p
301A	DIL	45p
709C	To99	25p
709C	DIL	30p
723C	To99	87p
723C	DIL	90p
741C	To99	25p
741C	DIL	34p
741C	8p in DIL	34p
747D	DIL	40p
748C	To99	38p

VOLUME CONTROLS

Potentiometers
Carbon track 500 Ω to 2.2M Ω
Log or Linear
Single 12p. Dual gang (stereo) 40p.
Single type only with D.P. Switch 12p extra.

RESISTORS
1 watt 5% carbon 1p each
1/2 watt 10% carbon 1p each
range 2.7 Ω to 10M Ω type TR5
triple rated 1/2-1/2, tin oxide x 2%
range 10 Ω to 1M Ω . 3p each

SLIDE SWITCH
SP3T 10p each
SP Three Position 12p each

MINIATURE NEON LAMPS
240v or 110v 1-4 5p, 5 plus 41p each

CARBON SKELETON PRE-SETS
Small high quality, type PR, linear only:
100 Ω , 220 Ω , 470 Ω , 1K, 2K2, 4K7,
10K, 22K, 47K, 100K, 220K, 470K,
1M, 2M2, 4M7, 10M Ω . Vertical or
horizontal mounting, 5p each.

VEROBOARD

	0-15	01
	Matrix	Matrix
2 1/2 x 3 1/2in	17p	23p
2 1/2 x 5in	25p	25p
3 1/2 x 3 1/2in	25p	25p
3 1/2 x 5in	30p	25p
5 x 17in (Plain)	83p	—
Vero Plus (Bag of 36)	20p.	
Vero Cutter	45p.	
Pin Insertion Tools (1 and .15 matrix)	at 55p.	

ZENER DIODES

400mW 5% 3-3V to 30V, 10p.

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 13p each.

16 pin type at 16p each.

TRANSISTOR EQUIVALENTS BOOK 40p


Pack of 20 1N4148	50p	Mix Pack of 20 1N4000 Series Diodes	50p
AC127 & AC128 1-9 10 plus 100 plus	13p 11p 13p	AD161, AD162 M/P	1-9 10 plus 52p 48p
1-9 10 plus	2N3055 49p 46p	BC107-BC108 BC109	1-9 10-99 100 plus 8p 7p 6p
Pack of 10 2N2926G	50p	Pack of 10 Plastic BC109	50p
unbranded but tested		Unmarked but fully tested	
Unmarked but fully tested		TBA800	5 watt AF power Amp. £1.40 each
1-9 10 plus	2N3055 30p 25p		

Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the

VEROBOARD

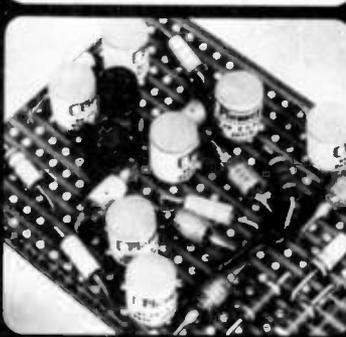

VEROBOARDS GIVE A PROFESSIONAL
FINISH TO YOUR WORK

INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY. (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.

MAIL ORDER ONLY.

S.A.E. ALL ENQUIRIES.

ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! Send quickly, after receiving goods test 7 days refund if not astounded. Elegant black & chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions VHF: FM/USW, AM: LW, MW, SW, Gats, locally, plus local and new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. SIZE 14ins x 10½ins x 4½ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities and spares available for years and years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions and circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra) **BOX, POST, ETC. 50p.** ***BUT WAIT,** for only 55p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (It enables you to time, pinpoint and get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) PLUS Standard 'longlife' batteries PLUS ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) **HURRY! SHOPERTUNITIES SAVE YOU £6!**

JUST ARRIVED! **THIS YEAR'S NEW *RUSSIAN MIRACLE! COMPUTERISED?**

BRAND NEW SPACE AGE model SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!

THE FABULOUS ASTRAD 17

THIS OFFER ONLY FROM US!

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!

PORTABLE RADIO & COMMUNICATIONS RECEIVER

28 TRANSISTORS AND DIODES! WAVEBANDS: STANDARD LONG and MEDIUM Plus 5 SHORT WAVEBANDS Plus ULTRA SHORT WAVES (V.H.F. AM, FM, MW, LW, USW.)

***COMPARE ITS PERFORMANCE with £80 RADIOS!**

FIRST TIME EVER!

***NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE!**

NO MORE GUESSWORK—INSTANT DATA at your fingertips—enables you to TUNE IN A FLASH to transmissions the world over!



BATTERY MODEL £20.75 **BOX POST ETC. 50p**
MAINS/BATTERY ELIMINATOR £1.48 extra

BUY ONE FROM US! SAVE £20.25 NOW!

Fabulous BRAND NEW SOLID STATE
BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE £44
OUR PRICE £23.75 **CARP ETC. 35p**

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined and it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play back anything, anywhere! **RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! ★ Separate ON/OFF and Hi-LO volume control! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker sockets! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY). Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. AND the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets locally, city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £ £ £'s more for a Car Radio or Car Cassette player. **ALONE! OUR FANTASTIC PRICE ONLY £23.75, CARP, ETC. 35p.** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, after receiving goods test 7 days—refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 25p extra if required.

FIRST TIME EVER! *SAVE £14.48!
BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER

With remote control microphone.



FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26.97!

OUR PRICE £12.49 **POST ETC. 31p**

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb deluxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £12.49!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on standard batteries AND 220/240V. AC mains. Separate jacks for remote control microphone, etc. Size 9½in. x 5½in. x 2½in. approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. **ONLY £12.49** post, etc., 31p. *Refund if you don't agree we could charge up to **£26.97! BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries, AND microphone stand all for 50p extra, if req. Send quickly, after receiving goods test 7 days—refund if not delighted.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE! NOTE: Merchandising office at Holborn Store.)

Dept. EE/17 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) **BOTH STORES OPEN FROM MONDAY TO SATURDAY FROM 9 A.M. UNTIL 6 P.M.**

SHOPERTUNITIES LTD.

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you


"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

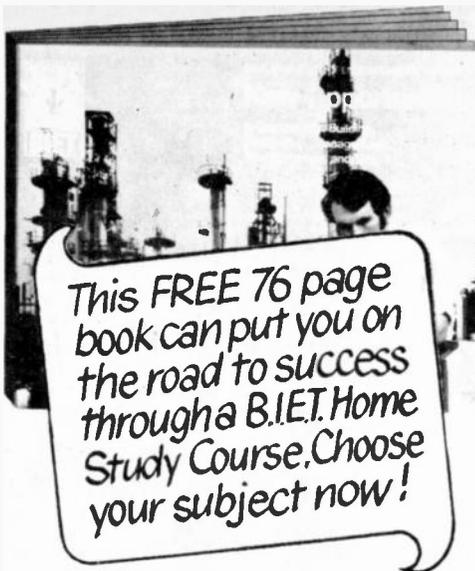These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BEE14, Aldermaston Court, Reading RG7 4PF



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

MECHANICAL A.M.S.E. (Mech.) Boiler Inspection & Operation C & G Eng. Crafts C & G Fabrication Diesel Eng. Eng. Inspection Inst. Eng. & Tech. Inst. Motor Ind. Maintenance Eng. Mechanical Eng. Sheet Metal Work Welding	Man. Prod.—cont. Salesmanship Storekeeping Work Study Works Management DRAUGHTSMANSHIP A.M.I.E.D. Design of Elec. Machines Die & Press Tool Design Electrical Draughtsmanship Gen. Draughtsmanship Jig & Tool Design Technical Drawing	Constructional-cont. Building Drawing Building Foreman Carpentry & Join. Civil & Municipal Engineering Constructional A.M.I.E.D. Construction Surveyors Institute Clerk of Works Council Eng. Geology Health Eng. Heat & Vent. Hydraulics Inst. of Builders Inst. Clerk of Works Inst. Works & Highway Supers. Painting & Dec. Public Hygiene Road Engineering Structural Eng. Surveying
ELECTRICAL & ELECTRONIC A.M.S.E. (Elec.) C & G Elec. Eng. C & G Elec. Inst. C & G Elec. Tech. Computer Elect. Elec. Maths Elec. Science Electronic Eng. Electrical Eng. Install. & Wiring Meters & Measuring Instruments	RADIO & TELE-COMMUNICATIONS Colour TV C & G Radio/TV/ Electronics C & G Telecomm. Tech. Prac. Radio & Elec. (with kit) Radio Amateurs Exam Radio Servicing & Repairs Radio & TV Eng. Transistor Course TV Main. & Serv.	GENERAL Agricultural Eng. Council of Eng. Inst. Farm Science General Education Gen. Plastics Pract. Maths Pract. Slide Rule Pure & Applied Maths Refrigeration Rubber Technology Sales Engineers Tech. Report Writing Timber Trade University Ent.
MANAGEMENT & PRODUCTION Automatic Control Computer Prog. Electronic Data Processing Estimating Foremanship Inst. Cost & Works Accountants Inst. Marketing Management Metrication Motor Trade Man. Network Planning Numerical Control Operational Research Personnel Man. Planning Eng. Production Eng. Quality Control	AUTO & AERO Aero Eng. A.M.I.M.I. A.R.B. Cert. Auto Engineering Auto Repair C & G Auto. Eng. Garage Management MAA/IMI Diploma Motor Vehicle Mechanics CONSTRUCTIONAL A.M.S.E. (Civil) Architecture Building	G.C.E. 58 'O' & 'A' LEVELS SUBJECTS Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

CU BEE14



BIET

NAME _____
 Block Capitals Please
 ADDRESS _____

SUBJECT OF INTEREST _____

AGE _____

Accredited by the Council for the Accreditation of Correspondence Colleges.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

PREMIER 800 STEREO AMPLIFIER



(As used in SYSTEM '800')

A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30,000 Hz = 2 db. Distortion: 1% Output Impedance 8 ohms nom. Inputs equalised to E.I.A. A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 100mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 6½" x 2½"

ONLY £15.00 Carr. 50p.

Mk. 11 Version available with Teak Finish Cabinet. £16.25. Carr. 50p.

PREMIER PARAGON STEREO HI-FI AMPLIFIER



Gives the best possible reproduction of records, radio and tape at a reasonable price.

Fitted with all the controls and facilities you're ever likely to want, the Paragon gives you a degree of

sophistication that is usually only found with amplifiers costing twice its price. It has bass and treble slide controls, volume and balance knobs, and eight push-buttons. There's also a standard stereo jack socket on the front panel, plus a ceramic/magnetic cartridge switch and a mains outlet socket on the back panel. Specifications 10 + 10 watts into 8 ohms. Power/frequency response: 0dB 10 watts into 8 ohms -3dB 20Hz - 25KHz. Distortion typically less than 0.25%. Inputs for Magnetic phono (4mV) Ceramic phono (66mV) Radio/Tape (100mV). High and low filters. Teak finish cabinet. Size: 12½" x 6½" x 10½"

£32.00 P. & P. 50p.

PREMIER STEREO SYSTEM '69'


Consists of the Premier Paragon Stereo Amplifier, Garrard SP25 III in teak finish plinth with cover and fitted Goldring 9800 stereo magnetic cartridge plus a pair of Marsden Hall Annex 100 Loudspeaker Systems. Complete with Free leads and plugs. £69 Insurance £1.75

VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono inputs output. Attractive teak wood grain finish case.



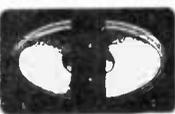MONO MODEL £3 STEREO MODEL £3.47 P. & P. 50p



E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2½in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new. £3.47 P. & P. 50p

QUALITY RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth cut out throughout the entire audio range. Double wrapped—actively boxed.

TT3 3" 450'	POLYESTER 37p	DT6 6" 1800'	POLYESTER £1.18
DT8 3½" 600'	POLYESTER 37p	TT6 6" 2400'	POLYESTER £1.87
SP5 4" 600'	P.V.C. 42p	SP7 7" 1200'	P.V.C. 62p
LP6 5" 900'	ACETATE 50p	LP7 7" 1800'	ACETATE 75p
DT5 5" 1200'	POLYESTER 75p	DT7 7" 2400'	POLYESTER £1.25
LP6 6" 1800'	ACETATE 75p	TT7 7" 3600'	POLYESTER £2.50

TAPE SPOOLS 8" 5p, 5½" 7" 8p. Post and Packing 3" 5p, 5½" 8p, 7" 10p (3 reels and over Post Free).


PREMIER HI-FI STEREO SYSTEMS

SYSTEM "800"

Consists of the Premier 800 Mk II all transistor stereo amplifier (described left) Garrard auto/manual record player unit fitted stereo/mono cartridge with diamond stylus and mounted in teak finish plinth with cover and two cloth front loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 800 Mk II amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Headphone socket. Power on/off. Teak finish cabinet with aluminium front panel. Size: 12½in x 6½in x 2½in.

£35.00

Carr. £1.75

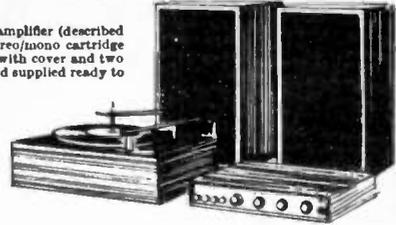

SYSTEM "TWO"

as above but with slotted front teak finish loudspeakers. Garrard SP25 Mk. III and magnetic cartridge.

£45.00

Carr. £1.75

SYSTEM "THREE"

This consists of KLINGER KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls Inputs for Magnetic and Ceramic pick-up, tuner, tape in and out. Stereo headphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of HMP Speakers size 16½" x 10½" x 9" fitted EMI units complete the matching system.

£57.75

FREE

LEADS AND PLUGS SUPPLIED WITH ALL SYSTEMS

NEW PREMIER COMPACT STEREO SYSTEM



All transistor stereo amplifier mounted into teak finish plinth with cover and Garrard 2025 T/C autochanger and a pair of matching teak finish cloth front speaker systems.

- ★ Output 4 watts rms per channel.
- ★ Separate volume, bass, treble and balance controls.
- ★ Stereo/Mono ceramic cartridge.
- ★ Tape/Tuner input and Tape output sockets.
- ★ Complete with all leads ready to use.

PREMIER PRICE ONLY £30 Carr. & Ins. £1.50



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE. COMPLETE IN TEAK PLINTH WITH COVER. Total list price over £34.

PREMIER PRICE £17.95 P. & P. £1

METER BARGAIN

MODEL GT-800 MULTIMETER A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 10, 50, 250, 1,000V (1,000 opV). AC Voltage: 10, 50, 250, 1,000V (1,000opV). DC Current: 1mA, 100mA. Resistance: 0-100K ohms. Decibel: -10 to +24db (at AC 10V range) £2.47, P. & P. 25p.



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.

£2.47 P. & P. 25p.

ROGERS RAVENSBROOK SEMI-PROFESSIONAL MODEL (as illustrated). (List £18.50). OUR PRICE £12.00. AKAI ASE95 £5.25. SENHEISER HD414 £8.50 P. & P. 25p each



E.M.I. LOW NOISE CASSETTES in library cases

C60 (List 71p) 45p
C90 (List 98p) 65p
C120 (List £1.48) 85p P. & P. 10p



LOW-NOISE COMPACT CASSETTES

Screw fixing—fully guaranteed. In Library cases.

	EACH	3 for	6 for	10 for
C60	29p	81p	£1.56	£2.50
C90	40p	£1.11	£2.16	£3.50
C120	52p	£1.40	£2.76	£4.50

P. & P. 10p each (3 and over 15p)

WELLER "EXPERT" SOLDER GUN.

Simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. £3.95 P. & P. 50p



"Litesold" Soldering Iron. Lightweight ¼" pencil bit. Ideal for regular beach use and around the home. 25 watts. 240 volt A.C. £1.50 P. & P. 10p.

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N-9 803 1685

7" x 4" LOUSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in. x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12k Hz. Power handling: 5W. Unbeatable. Price: £1.80. Free postage on this item.

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN GAE AERIAL

5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
complete with Fixing Bracket and £5.75 plus 5p P. & P.
Control Switch £5.75 plus 5p P. & P.

S. G. BROWN "DIPLOMAT" MONO/STEREO HEADSET

Finest quality British made Lightweight Headphones. Incorporate ceramic piezo electric transducers.
Specification:—Frequency—20-17,500 CPS.
Impedance—Predominantly capacitive, at 00MFD per earpiece can be regarded as 100K at 1000.
Weight—3.5oz. (98 grams).
Please include 10p per set P.P. A bargain at £1.50 each set

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. £1.75 plus 13p P. & P.

"CRESCENT" DIGITAL CLOCK KIT

24 Hour Nixie Digital Clock Kit. Apply:
★ A complete set of components
★ A complete set of easy to follow instructions
★ Printed circuits made to make construction as simple as possible
★ A cabinet and front panel to give a professional finish.
All for the price of the components. £22.50 + 50p. P. & P. Please send S.A.E. for more information.

MINIATURE RELAY

6 volt 70 ohm.
Single Pole Changerover.
Approx. size 1 1/2" x 1" x 1".
40p plus 5p P. & P.

40p plus 5p P. & P.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your transistor radio, amplifier, or cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug you can select the voltage you require—6v, 7 1/2v or 9 volts. This means all your transistor power pack applications can be handled by this one unit. Approx. size: 2 1/2" x 2 1/2" x 3 1/2". OUR PRICE—£2.75p + 10p. P. & P. Same model suitably wired for the Philips Cassette—£3.00 + 10p. P. & P.

ALUMINIUM CHASSIS

Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.
6 x 3—41p 12 x 3—53p 14 x 9—94p
8 x 4—45p 12 x 5—61p 16 x 6—86p
8 x 6—33p 12 x 8—58p 18 x 10—1.08p
10 x 7—63p 14 x 8—80p
Please send 10p per chassis P. & P.

POWER TRANSISTOR HEAT SINKS

Extruded aluminium:
Approx. size: 6" x 4 1/2" x 1 1/2".
A few only at this low price—40p each + 5p P. & P.

INTEGRATED CIRCUIT SOCKETS

A must for the experimenter interested in I.C.s. 14 pin, 16p each. 16 pin, 16p each. Please include 5p P. & P. per 3 sockets.

EA1000 3 WATT AUDIO AMPLIFIER MODULE

An Audio Amplifier designed around the TAA621 Linear I.C. Supply Voltage 9-24V Speaker Imp. 8-16 ohm Frequency 50Hz-25kHz Overall Size 2in x 3in x 1in Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at £2.63 + 5p P. & P.

TRI-VOLT CAR CONVERTER

Enables you to work your Transistor Radio, Amplifier or Cassette etc. from the 12 volt car supply positive or neg. car. This converter supplies 6, 7 1/2 or 9 volts and is transistor regulated. Approx. size 2 1/2" x 3 1/2" x 2". Very easy to fit and a real money saving device for £2.50 + 10p. P. & P.

WAFER SWITCHES

1 pole 12 way
2 pole 2 way
2 pole 3 way
2 pole 4 way
2 pole 6 way
3 pole 4 way
4 pole 3 way
18p each. Please inc. 6p P. & P. Up to 3 switches.

POTENTIOMETERS

All types 1" and less diam. SINGLES DUAL
5K Log or 5K
10K Lin Less 10K
25K Switch 25K Less
50K 12p ea, 100K 40p.
100K Double 250K
500K Pole 500K each
1M Switch 1M
2M Switch 2M
24p ea.
Up to 3 Pots. Please add 6p. P. & P.

MINIATURE RELAYS

Brand new range of British made Relays. Size—1 1/2" x 1" x 1/2". All two changovers with 250V, 1.5A contacts and suitable for fitting on 1in Veroboard. Type Volts Current Ohms. 27/A 12v 17mA 700 Ω 21/A 12v 28mA 430 Ω 12/A 6v 33mA 185 Ω 80p each. Please include 5p P & P up to 3 Relays.

The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....
BASIC ELECTRICITY 5 parts £4.50
BASIC ELECTRONICS 6 parts £5.40
BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.
YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS
FULL POSTAL.....
ADDRESS



WHAT READERS SAY

They have an easy approach to learning that a mathematical idiot like myself can easily understand. K.L.Y. Ashton-u-Lyme.

Thank you for the excellent publication: the best in form and type I have ever come across. T.L.O. Shanklin.

I find the Basic Manuals the best in their class and a real help in my work in photo-type electronics. C.L.P. Cardiff.

I was amazed how easy it was to read and learn. L.Y.C. Addington.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

POST NOW FOR THIS OFFER!

SAXON ENTERTAINMENTS.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES
FOR DOMESTIC & COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2.95 carr. free

25 WATTS RMS. 7 transistors or 7 diodes

SA35 £4.45 carr. free

35 WATTS RMS. 7 transistors or 7 diodes

SA100 £10.90 carr. free

100 WATTS RMS. 11 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000 Hz \pm 1dB
Distortion	0.2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	25-45 volts SA25/35 40-70 volts SA100
Size	4 1/2" x 4" x 1" (SA100) 4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilized supply for 2 SA25/35	£4.90
PU70	Unstabilized supply for one or two SA100	£7.75 carr. 40p
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
Stab PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
MT70	Transformer for PS70	£4.90 carr. 40p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free

ALL MODULES ARE BUILT ON
GLASS FIBRE P.C. BOARD
AND ARE SUPPLIED FULLY TESTED

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE £13.90 + 20p carr. or with supply
£18.95 + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

SPECIFICATION

Power output	120 watts into 8 ohms
Freq. response	20-20,000 HZ \pm 2dB
Input sensitivity	200 mV into 10K
Construction	Fibreglass board
Size	8" x 4" x 4" (5" with supply)
Load	Low distortion parallel push-pull output stage.




NEW 160 watt version & supply **£27.90**

SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

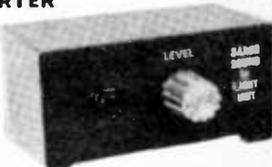Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



£8.90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue hooded cover. Fully guaranteed.



£19.75 carr. 30p

MONO VERSION £6.50 carr. 20p (As illustrated, S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



£15.80 carr. 30p


SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. **THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic input.)

COMPLETE AMPLIFIERS

The **CSE 100**, £34.90 carr. free

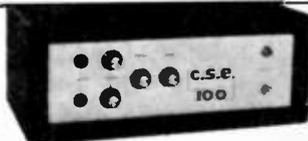This versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.



The **SAXON 100** £48.50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms **£5.95** carr. 30p, 15" 50W 8/15 ohm **£14.50** carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm **£11.50** carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use.

D11DHL rrp **£11.00** our price **£9.45** post free
D190C High Z rrp **£21.50** our price **£17.45** post free
D1000C 24 ct gold plate rrp **£37.00** our price **£32.00** post free

SEND SAE FOR OUR AKG PRICE LIST. DISCOUNTS ON ALL MICS.

CALLERS & MAIL ORDER:

351 Whitehorse Road,
Thornton Heath, Surrey.
91-689 3885

CALLERS ONLY:

OUR NEW DISTRIBUTORS

CIRCLE SOUND,
328-330 The Banks, Rochester.
Medway 404199

BUSINESS HOURS:

9.30 a.m.
to 5.30 p.m.

TERMS OF BUSINESS:

C.W.O. or C.O.D. (35p extra)
All cash in regd. envelopes please!
Telephone orders to our **CROYDON BRANCH.**
TRADE & EXPORT enquiries invited.

Would you spend an hour a day to earn more money in Electronics- Television-Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and our wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics - in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments).

With ICS you study at home - at your own pace, when you choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

ICS your key to the door
of opportunity

Tick or state subject of interest and post to:
International Correspondence Schools, Dept. 231D,
Intertext House, Stewarts Road, London SW8 4UJ.

Subject of interest _____

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name _____

Address _____

Occupation _____

Age _____

Accredited by the Council for the Accreditation of Correspondence Colleges

ELECTROKIT

DRILL SPEED CONTROLLER (E.E. Aug. 1972)
Complete kit includes MK box, plate and socket £2.30

BIT SAVER (E.E. Dec. 1972)
Kit includes all the parts less the Microswitch lever £1.70

MIGHTY MIDGET (P.W. Jan. 1973)
Kit includes all parts less the Battery, the Box or Knob £2.25

"SCORPIO" CAPACITOR DISCHARGE

IGNITION SYSTEM (P.E. Nov. 1971)
Complete kit with construction data £9.50

LIGHT DIMMER:
Complete kit including MK plate and full construction data £2.10

We are offering various other kits published in most other popular Electronics magazines and will be pleased to forward details on receipt of a stamped addressed envelope.

FREE POST AND PACKING

ELECTROKIT

12 Lauderdale Road, London, W.9
Telephone 01-286 0011

MON.-FRI. 9.30-5.30
THURS. 9.30-6.30

A complete Stereo System for ONLY £29.32p!

The
Heathkit
Stereo
Record
Player
SRP-1 Kit

(carr. £1 extra)



Enjoy the stirring realism of full stereo sound plus do-it-yourself savings. So easy to build, too!

The step-by-step manual tells you how. Compact styling - turntable folds away when not in use, with a choice of simulated teak or black and grey Rexine.

This is only one of many bargains in the Heathkit Hi-Fi/Audio/Instrumentation range. We even supply Metal Detectors, SW Receivers, Portable Radios, Battery Chargers in kit form too. Send coupon now for a FREE copy of the comprehensive Heathkit catalogue.

SEND TODAY FOR OUR LATEST CATALOGUE AND DETAILS OF NO DEPOSIT TERMS AND BUDGET PLAN

Please send me a FREE Heathkit catalogue

Name _____

Address _____



HEATH

Heath (Gloucester) Ltd.,
Dept. EE/3/73, Gloucester GL2 6EE.

ZN414 £1.25 POST FREE

The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets

Dual in-line or Zig-Zag (DUAL), 14 and 16 pin
Our Price 1p per pin

Slider Pots

Single	Dual	log
10K	10 + 10K	or
25K	25 + 25K	lin
50K	50 + 50K	
100K	100 + 100K	Knobs
30p	50p	10p.

VDR's & Thermistors

A158 75p	GL23 £1.00	VA1005 15p
C21 15p	R63 £1.32	VA1026 13p
C24 13p	R54 £1.46	VA1033 13p
C213A 13p		VA1040 10p
E298 ED/A258 10p		VA1053 10p
E298 Z/06 10p		VA1055S 10p
GL16 £1		VA1034 10p

Resistors

1/2 watt 5% Carbon Film - low noise
Hi-Stable
All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value.

1W 10% Carbon Composition 3p each
2W 10% Carbon Composition 6p each
2.1W 5% Wire wound 9p each
5W Wire wound 9p each
10W Wire wound 10p each
plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25.

Potentiometers



5KΩ	50KΩ	500KΩ	
10KΩ	100KΩ	1MΩ	
25KΩ	250KΩ	2MΩ	

log or lin less switch (& 1KΩ lin) 12p
log or lin with switch 24p
dual less switch 40p
dual with switch 10K, 100K & 1M log only 52p
10K log + 10K antilog less switch 40p

Eliminators



9 volt @ 20mA (PP3) £1.25
6 volt @ 50mA £1.50
9 volt @ 50mA £1.50
6 + 6 volt, 50mA £2.50
9 + 9 volt, 50mA £2.50
7 1/2 volt for cassette recorders £2.00
6.7 1/2 or 9 volt £3.00
3, 4.5, 6, 7.1, 9, 12 @ 500mA (Illus.) £3.99
Car Battery Converter fully stabilised to provide 6.7 1/2 or 9 volts (p. & p. 15p on all types) £4.99

Capacitors

disc ceramic

0.1μF 18v	5p	low voltage	0.1μF 30v	5p
0.22μF 18v	5p	0.22μF 5v	5p	
0.47μF 12v	5p	0.47μF 3v	5p	

ceramic plate

1000pf	10p	4700pf	10p
2200pf	10p	10,000pf	10p

Ceramic - plate 63V (C333)

1.8pf	8.2pf	33pf	120pf
2.2pf	10pf	39pf	150pf
3.3pf	12pf	47pf	180pf
3.9pf	15pf	56pf	220pf
4.7pf	18pf	68pf	270pf
5.6pf	22pf	82pf	330pf
6.8pf	27pf	100pf	

mylar film 100V

1000pf 2p	0.1μF 3p	0.68μF 4p
2000pf 2p	0.2μF 3p	1μF 4p
5000pf 2p	0.4μF 3p	2μF 5p
	0.5μF 3p	

polyethylene 160V

10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallised polyester 250V (C280)

0.1μF 3p	0.68μF 3p	47μF 8p
0.15μF 3p	1μF 4p	68μF 11p
0.22μF 3p	1.5μF 4p	1μF 13p
0.33μF 3p	2.2μF 5p	1.5μF 20p
0.47μF 3p	3.3μF 6p	2.2μF 24p

metallised polyester 400V (C281)

0.1μF 4p	0.47μF 6p	2.2μF 10p
0.15μF 4p	0.68μF 6p	3.3μF 14p
0.22μF 4p	1μF 7p	4.7μF 15p
0.33μF 5p	1.5μF 8p	

silvered mica 1% (>50pf) 500V

2.2pf-820pf	7p	4.7nF-5600pf	18p
1nF-2.2nF	9p	6800pf-0.1μF	25p
2.7nF-3.6nF	16p		

mixed dielectric 600V

0.1μF 7p	0.47μF 7p	2.2μF 16p
0.22μF 7p	0.68μF 8p	4.7μF 24p
0.33μF 7p	1μF 8p	1μF 33p

NEW LISTS

LOUDSPEAKERS No. 4
COILS AND INDUCTORS No. 5
TRANSFORMERS No. 6
(postage 5p)

Diodes & Rectifiers

AA119 9p	BA156 15p	BY176 £1.50
AA120 9p	BA243 56p	BY182 £1.50
AA129 9p	OA47 10p	BY250 23p
BA102 25p	OA79 9p	IN4001 6p
BA115 17p	OA90 7p	IN4002 6p
BA130 10p	OA91 7p	IN4003 8p
BA145 20p	OA200 10p	IN4004 8p
BA148 20p	BY100 15p	IN4005 12p
BA154 13p	BY126 15p	IN4006 12p
BA155 14p	BY127 15p	IN4007 15p

SGS

EA1000



3 Watt Audio Amplifier
Our Price inc. handbook £2.49

5 Watt Audio Amplifier
Our Price £3.99
Less quantity discount

Presets

Vertical or Horizontal

0.1 watt 5p	0.25 watt 7p
100 1KΩ	10KΩ 100KΩ 1MΩ
250 2.5KΩ	25KΩ 250KΩ 2.5MΩ
500 5KΩ	50KΩ 500KΩ 5MΩ

MAIL ORDERS: Where no p. & p. change is shown, a minimum of 7p applies, p. & p. on overseas orders is charged at cost.

ADDRESS TO: M. O. Dept.
56, Fortis Green Road, London N10 3HN
Telephone 01-833 3705

FM TUNER

chassis fully transistorised
9 volt operation
OUR PRICE £4.99

Matching stereo decoder £4.97
Ask for model list No. 11.




3 Watt Audio Amplifier



Our Price inc. handbook £2.49

Vertical or Horizontal Presets

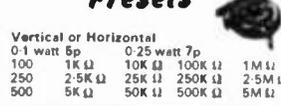


MAIL ORDERS: Where no p. & p. change is shown, a minimum of 7p applies, p. & p. on overseas orders is charged at cost.

ADDRESS TO: M. O. Dept.
56, Fortis Green Road, London N10 3HN
Telephone 01-833 3705

CHROMASONIC electronics

Heat Sinks

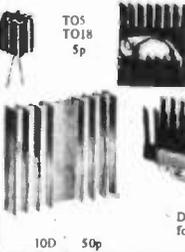

TOS TO18 5p
TO66 TO3 14p
Power Tab 13p
DIP10/2 for SL403D 15p
10D 50p

Transistors & Integrated Circuits

AC107 25p	BC147 10p	BF196 15p	OC81 15p	2N1304 22p	2N3978 15p
AC126 15p	BC148 10p	BF197 15p	OC140 20p	2N1711 25p	8ZV88 10p
AC127 15p	BC149 10p	BF272 50p	OC170 23p	2N1993 30p	ZENERS SERIES ea.
AC128 15p	BC167 10p	BFY50 24p	OC171 11p	2N3026 all 15p	LO08T1 £1.50
AC176 15p	BC156 10p	BFY51 21p	ETX107 11p	2N3053 25p	LO08T1 £1.50
AC187 25p	BC159 12p	BR39 30p	ETX108 12p	2N3054 50p	LO37T1 £1.50
AC187K 25p	BC169 15p	BSX21 24p	ETX109 15p	2N3055 50p	MC1303L £1.75
AC188 25p	BC268 15p	BSY95A 41p	TX3001 17p	2N3702 12p	MC1330 8p
AC188A 25p	BD115 67p	BU105/02 61.75	TX3001 15p	2N3703 12p	MC1330 7.5p
AC270 20p	BD131 70p	MJ340 67p	TX3002 20p	2N3704 18p	MC1330 7.5p
AO146 40p	BD132 70p	MPF192 40p	TX3003 20p	2N3705 18p	MC1352 £1.00
AO149 40p	BD137/EM.P. 13p	MPF103 37p	TX3004 25p	2N3706 18p	MFC4008B 50p
AD101 60p	BF190 81p	MPF104 37p	TX3011 20p	2N3707 15p	MFC4010A 50p
AD102 60p	BF190 81p	MPF105 40p	TX3001 15p	2N3708 12p	LM380 £1.40
AF114 18p	BF167 20p	MPF106 45p	TX3001 15p	2N3709 12p	SL403D £1.50
AF115 18p	BF173 20p	OC28 40p	TX3002 20p	2N3710 12p	TAD100 £1.50
AF116 18p	BF180 25p	OC35 40p	TX3003 17p	2N3711 12p	
AF117 18p	BF181 30p	OC44 15p	TX3004 50p	2N3819 35p	
AF139 20p	BF184 25p	OC45 15p	TX3531 25p	2N3903 25p	μA709C 45p
BC107 10p	BF185 25p	OC71 11p	EN067 18p	2N3904 17p	μA710 45p
BC108 10p	BF194 15p	OC72 17p	2N708 12p	2N3905 21p	μA723C £1.00
BC109 10p	BF195 15p	OC76 15p	2N708 15p	2N3906 12p	μA741C 30p

Mixed dielectric 1000V

1000pf 6p	6800pf 9p	1μF 12p
2200pf 6p	0.1μF 9p	2.2μF 22p
3300pf 6p	0.22μF 9p	4.7μF 30p
4700pf 6p	0.47μF 12p	

Ceramic

12KV d.c. 8KV d.c. MI-K 750V

10p	200p	9p	1000pf	5p
15p	9p	220p	9p	1500pf
22p	9p	250p	9p	2000pf
68p	9p	270p	9p	3000pf
82p	9p	300p	9p	5000pf
100p	9p	750V DISC	10,000pf	5p
120p	9p	470p	5p	feed-
140p	9p	1000p	5p	through
150p	9p	5000p	5p	
180p	9p	10,000p	5p	1000pf 5p

Veroboard

Copperclad Plain

0.1"	0.15"	0.15"
------	-------	-------

2 1/2" x 1"	6p	6p	
2 1/2" x 3 1/2"	20p	16p (9)	10p
2 1/2" x 5"	24p	21p (7)	12p
3 1/2" x 3 1/2"	24p	21p (8)	
3 1/2" x 5"	27p	27p (10)	17p
17" x 2 1/2"	67p	50p	37p
17" x 5"	90p	70p	52p
17" x 5"			75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

ADCOLA INVADER

ROTARY MAINS SINGLE WAFER ROTARY



Coax Plug 15p
Phono Socket 4p
Din Plug 15p
Din Socket A, B or C 15p
Coax (Surface Socket) 5p
Phono Plug 5p
Insulated TERMINALS 13p each
Loudspeaker Plug 10p
Loudspeaker Socket 10p

Coax L706 4p (Fluke)
Socket L646 1/2 8p
£1.70 p. & p. 10p
£1.85 p. & p. 10p

Available in Red, Black, Green, White, Yellow, Blue and Grey.

Socket Solder Dispenser: Contains 12 P. of called 18 s.w.g. Enlin Multi-colour Sock-it Alloy. 18p each

SLIDE D.P.D.T 17p
S.P.S.T. 250V, 1A 18p
TOGGLE D.P.D.T. 250V, 1A 26p

Mullard B Siemens Electrolytics

CAP μF	VOLTAGE			
	4	6.3	10	16 25 40 63
1	—	—	—	— 6p
1.8	—	—	—	— 6p
2.2	—	—	—	— 6p
3.3	—	—	—	— 6p
4.7	—	—	—	— 6p
6.8	—	—	—	— 6p
10	—	—	—	— 6p
15	—	—	—	— 6p
22	—	—	—	— 6p
33	—	—	—	— 6p
47	—	—	—	— 6p
58	—	—	—	— 6p
100	—	—	—	— 10p
150	—	—	—	— 10p
220	—	—	—	— 10p
330	—	—	—	— 10p
470	—	—	—	— 10p
680	—	—	—	— 10p
1000	—	—	—	— 10p
1500	—	—	—	— 10p
2200	—	—	—	— 10p
3300	—	—	—	— 10p
4700	—	—	—	— 10p

Quantity Prices on application.

NEW LISTS

BOXES, CHASSIS, etc. (soon)

TRANSISTORS, I.C.'s, etc. (postage 5p)

Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. A p.
(7)	2 1/2"	5 1/2"	1 1/2"	35p	8p
(8)	4"	4"	1 1/2"	35p	8p
(9)	4"	2 1/2"	1 1/2"	35p	8p
(10)	4"	5 1/2"	1 1/2"	40p	8p
11	4"	2 1/2"	2"	35p	8p
12	3"	2"	1"	32p	9p
13	6"	4"	2"	50p	10p
14	7"	5"	2 1/2"	58p	12p
15	8"	6"	3"	75p	18p
16	10"	7"	3"	85p	20p

Hi-Volt Electrolytics

1.2, 4, 6μF 450V	14p	22μF 450V	20p
16μF 450V	15p	50μF 350V	20p
8+8μF 450 V.W	18p	32+32μF 350 V.W	25p
8+18μF 450 V.W	20p	32+32μF 450 V.W	30p
16+16μF 450 V.W	25p	50+50μF 350 V.W	45p

MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2 1/2". £1.50 each.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 7p each. — for 50p. Plastic pushrod switch for operating. 5p each. 10 for 45p.



CAR PANEL SWITCH

Our Ref. No. 802. Arcs made. Has long flat ended toggle, black and chrome finish. Rated 2A at 250V and is double pole on/off. Listed at 45p. Our price 22p each.



CAR PANEL AUTO SWITCH

Ref. No. 800. Again a flat ended toggle. Made by Arrow. A 3 position double pole changeover switch centre off for auto serials, reversing motors, etc. 30p each.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip only £1.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 20p each £1.80 for ten, your assortment.

PORCELAIN FUSE AND CARRIER



20A 250V MEM Ref. No. 18LBB/15LRHW. Make your own fuse board. Price 20p per pair.

FLUORESCENT TUBES

Standard types—Bipin ends. Ideal pelmet lighting as well as for standard replacements—18in 15W, 24in 40W, 36in 40W, 39in 40W. All first grade tubes offered at one price—£3.50 per box of 24—i.e. less than 15p each. If not collecting then please add 50p per box per 200 miles.


MULTI-SPEED MOTOR

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000; 12,000 & 15,500 r.p.m. shaft is 1/4 in. diameter 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price 89p plus 25p postage and insurance.



MAINS MOTOR

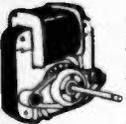Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. 81up at 65p. Postage 20p for first one then 10p for each one ordered. 1" stackmotor 89p. 1 1/2" stackmotor £1.



PANEL NEON INDICATOR

Our Ref. No. P101. Oblong type self-fixing into oblong hole. Suitable for 200/250V. Price 13p each.



FLUORESCENT CONTROL KIT

Each kit comprises seven items—Choke, 2 tube ends, starter, holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. £1. Kit B—30-40 w. £1. Kit C—80 w. £1.20. Kit D—125 w. tube £1.75. Kit MF1 is for 6in., 9in. and 12in. miniature tubes £1. Kit MF2 for 21in. 13 w. miniature tube £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23p on first kit then 18p for each kit ordered. Kit F 33p then 23p for each kit ordered. Kit MF1 18p on first kit then 15p on each two kits ordered.



HEAT & LIGHT LAMP

Plugs into a lamp holder. Ideal in bathroom, toilet, over bed, etc. 90p plus 20p P. & P.

12 WAY SUB-MINIATURE MULTI-CORE CABLE

Made by Smiths. Complete with control knob and calibrated dial. Useful in kitchen, office, dark-room, etc. Bargain at 50p.



MIGHTY MIDGET

Probably the finest possible radio, as described in Practical Wireless, January 73. All electronic parts £2 post paid.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work, £2.25 plus 23p P. & 1




HORSTMANN "TIME & SET" SWITCH

(A30 Amp Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc. up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50 Post and ins. 23p.



4 WATT AUDIO AMPLIFIER

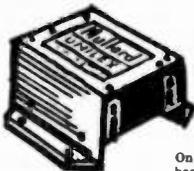

Works off dry batteries, car battery or mains power pack.

Only £1.65. This low price possible only because the make is over produced.


Unrepeatable once stocks are cleared.

Made by the famous Mullard company and carries their full guarantee. Complete in dustproof case, amplifier may be used for Mono or Stereo, music or speech. Hundreds of applications. Frequency response 50Hz-16KHz. Supplied complete with connection diagram and operating notes.

FREE all purchasers receive Mullard booklet "Do It Yourself Stereo" tells all you need to know to build your own stereo system. Write today to avoid missing this terrific offer.

RADIO STETHOSCOPE

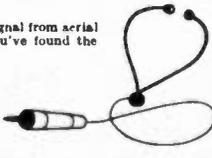Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2—twin stethoscope instead of earpiece 75p extra—post and ins. 20p.



24hr. REPEATING TIME SWITCH

Made by Smiths these are A.C. mains operated. NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours. 5 amp change-over contacts will switch circuit on or off during these periods £2.50 post and ins. 23p. Additional time contacts 50p pair.



ATLAS TWENTYLITE

Fluorescent lighting units with polyester choke and finished white enamel. 2ft. model. Ideal kitchen, bedroom, hallway, porch, loft etc. With tube assembled ready to install. £1.98 + 40p postage.




HONEYWELL THERMOSTAT

Made by Honeywell for normal air temperatures 40°-80°F (5-25°C). This is a precision instrument with a differential which can be adjusted to better than 1.5°F. A mercury switch breaks on temp. rise—the switch is operated by a coiled bi-metal element and adjustable heater is incorporated for heat anticipation. Elegantly styled and encased in an ivory plastic case with clear plastic windows thermometer above and switch setting scale below—size approx. 3-8" x 3-2" x 1-4" deep—can be mounted on conduit box or directly on wall. Price £1.25 each for ten for £11.25.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment on fitting into a cooker hood, fume drying cabinet or for removing fume smoke when soldering etc. etc. A real bargain at £1.85.

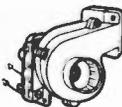

BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nickel—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £2.80 plus 20p postage.



SNAP ACTION SLIDE SWITCH

Rated 5a. 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuum, etc. 5p each. 10 for 45p.



BATTERY CHARGER KIT

Comprising 3 amp 12V mains tra. and rectifier with wiring diagram. £1.25 + 25p P. & P.

BLACK HEAT ELEMENTS

Ideal for making convector and similar devices. Two joined in series approx. 1KW. Price 79p per pr. + 20p postage.



EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2.50 + 20p P. & P.

CD CAR IGNITION

This system which has proved to be amazingly efficient. We offer kit of parts as P.W. Circuit £5.95 plus 20p P. & P. Deluxe model with prepared circuit board £8.95. When ordering please state whether for positive or negative systems.

ELECTRONIC IGNITION

EXIT SIGNS



One of our customers has pointed out how easily our box signs can be converted to exit signs. These are illuminated fluorescent lamp with associated control gear. The front is very thick clear plastic. Directly onto this you can stick down the letters available at most stations. There is room inside the box for a battery and low volt lamp in the case of power failure. Size of sign is 2 1/2" high x 1 1/4" wide x 5/16" deep. Solidly made from sheet steel and hammer finished in enamel. Price £3.50 plus 50p carriage per 200 miles.

SPIT MOTOR



200-250V induction motor, driving a Carter gearbox with a 1 1/2" output drive shaft running at 5 revs p.m. Intended for roasting chickens, also for driving models—windmills, coloured disc lighting effects, etc. £1.85 plus 20p post and ins.

SOLDER GUN



A must for every busy man, gives almost instant heat, also illuminated. 100 watt £2.25 plus post and ins. 20p. BIG 100W watt model £4.75 plus post and ins. 40p.

TELESCOPIC AERIAL



for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2" to 47in. Hole in bottom for 6BA screw. 38p. KNUCKLED MODEL FOR P.M. 50p

TREASURE TRACER



Complete Kit (except wood batten) to make the metal detector as the circuit in Practical Wireless, August issue. £2.95 plus 20p post and insurance

MINIATURE ROCKER SWITCH

Our Ref. R501. 10A 240V. Self-fixing into hole size approx. 1in x 1in by famous French maker Runsmburgh. Price 10p each.



MAINS OPERATED SOLENOIDS




Model 77R—small but powerful 1 1/2" pull—approx. size 1 1/2" x 1 1/2" 60p. Model 400/1 1" pull Size 2 1/2" x 2" x 1 1/2" 75p.

Model TT10 1 1/2" pull size 3 x 2 1/2 x 2" £1.80 plus 20p post and insurance.

RESETTABLE FUSE

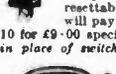How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (no circuit breaker) will pay for itself. Price only £1 each or 10 for £9.00 specify 5, 10 or 15 amp—simply fit in place of switch.



LIGHT CELL

Almost zero resistant in sunlight increases to 10 K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1in. dia by 1in. thick. Bated at 500 MW, wire ended. 60p with circuit. Also ORP 12 light cell 60p.



TAPE HEADS
We are gradually obtaining more information about the Truvox tape heads we have, we are told that these have been wound in a very ingenious way so that winding may be copied either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and no offer these in pairs, 1 record and 1 erase head. Price of the 2 track 45p per pair, 4 track 75p per pair. Fair mounted on plate 45p extra.


I R.P.H. MOTOR
Made by the famous Smiths Company. 240v 50 cycle mains working. Ideal motor to drive clock mechanisms. Price £1 each or 10 for £9.



CONTROL DRILL SPEEDS
DRILL CONTROLLER NEW 1KW MODEL
Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 15p post and insurance. Made up model also available. £2.25 plus 13p post & p.

HIGH ACCURACY THERMOSTAT
Uses differential comparator I.C. with thermostat as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack £5.50.

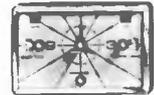WATERPROOF HEATING ELEMENT
26 yards length 70W. Self-regulating temperature control. 50p post free.



ISA ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory timer. A beautiful unit. Price £1.95 + 20p p & p or with glass front chrome bezel 75p extra.

INSTANT START UNITS
For 2ft tubes, Phillip's or Smart & Brown in a tray complete with tube clips and tube ends. Price £1.50 each or 10 for £13.50.

EDUCATIONAL KITS—all with pictorial instructions



THIS BALANCE KIT FREE

Eagle educational kits. Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 40p each post paid. Special price for all 8 kits £3.00 with free balance kit.

KA2 Lens Kit. Eleven parts, including candle, one concave lens, one convex lens, stage and all frame, etc. Watch light rays bend as they pass through different lenses.

KA3 Water Pump Kit. Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working. Three types of pump may be made: Lift pump, Force Pump and Force Pump with reservoir and nozzle.

KA4 Buzzer Kit. Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer.

KA5 2-Pole Motor Kit. Twenty-four parts including enamel wire, armature and pole piece, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor.

KA7 Electro-Magnet Kit. Fifteen parts, includes compass. Makes two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.

KA8 Current and Resistance Kit. Twenty-nine parts, including bench and light bulb. Conduct interesting and educational projects to learn the application of "OHM'S LAW" and see the difference in current and resistance with different types and lengths of wire.

KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.

KA10 Morse Key buzzer and bell kit. 25 part kit easy to construct, simple to operate.

ELECTRONIC EGG TIMER ENLARGER EXPOSURE METER NEON NOVELTY

To receive parts for these and other projects featured in this issue send quoted approximate amount any cash adjustment can be made later.

THYRISTOR LIGHT DIMMER

For any lamp up to 600 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price £2.95 plus 20p post and insurance.



TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £3.50. 2kW. Model as above except 2 kilowatts £2.50. Don't miss this. Control Switch 35p. P. & P. 40p.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fuse! plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.25 plus 23p P. & A

THIS MONTH'S SNIP 5 AMP VARIAC FOR £3

This heading is not quite accurate because it is not a variable transformer for we are offering but a solid state device which serves the same purpose in almost all applications and, of course, much smaller. Made by Ultra Electronics, can be fitted into ordinary switch box. Engrave a circle on the front plate, mark this off in divisions, fit a pointer knob, calibrate with your voltmeter (you will find the scale almost linear) you now have a power controller equal to a 5 amp variac costing £12 or more.

BARGAIN PARCEL OF SEVEN MOTORS FOR £1

A bargain parcel of 7 motors for £1. Some not as large as a postage stamp and only 1" thick, largest is 1 1/2" x 1 1/2" dia. Some work off 1 1/2 some as high as 18v. These motors are used in racing cars, power toys etc. The largest is so powerful that it will drive a Mini drill motor lathe, or similar. This is a 4 pole motor, optimum working 16 1/2 but very powerful even as low as 4 1/2. Don't miss this wonderful snip.



STANDARD WATER SWITCHES

Standard size 1 1/2" water—silver-plated 5-amp contact, standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	40p							
3 poles	40p	40p							
4 poles	40p	40p							
6 poles	40p	40p	40p	70p	95p	95p	95p	£1.45	£1.45
6 poles	40p	40p	40p	70p	95p	95p	95p	£1.70	£1.70
7 poles	70p	70p	70p	95p	£1.20	£1.20	£1.20	£1.95	£1.95
8 poles	70p	70p	70p	95p	£1.20	£1.20	£1.20	£2.20	£2.20
9 poles	70p	70p	70p	95p	£1.45	£1.45	£1.45	£2.45	£2.45
10 poles	70p	70p	70p	95p	£1.20	£1.45	£1.45	£2.70	£2.70
11 poles	70p	70p	70p	95p	£1.20	£1.70	£1.70	£2.95	£2.95
12 poles	70p	95p	95p	£1.20	£1.70	£1.70	£1.70	£3.20	£3.20

PAPST MOTORS

Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. £1.50 each. Postage one 23p, two 33p, 230V model £3.



BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners. This is a very strong case suitable to house instruments and special rigs, etc. Price 45p each. Fax lid 10p extra.

50 MICRO AMMETER Square, panel mounting type. £3

INTEGRATED CIRCUIT BARGAIN
A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect. First-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only £1 post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

CHIP RADIO

Ferranti's latest device ZN414 gives results better than superb. Supplied complete with technical notes and circuits. £1.25 each. 10 for £11.

12 VOLT 1 1/2 AMP POWER PACK
This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/50V smoothing. Price £1.95, plus 20p post & packing.

250 WATT POWER PACK
9-50 volts, 20-5 amp using full wave and half wave circuits voltage changes by inter connection of push-on tag. Price £5.50 + 50p p & p. N.B. Note these make excellent car battery chargers.

AMPLIFIER IN CASE WITH SPEAKER
Marketed by British Relay under the name Luxitor. This is in a very neat looking cabinet and is ideal around the home or in the workshop for trouble shooting or for testing out a quick lash up. Size approx. 9 1/2" x 6 1/2" x 3 1/2" deep. Input is via a matching transformer and volume control and amplifier may be powered by an internal 9v battery or an external 110v source. Speaker is an R-A elliptical 8" x 3 1/2" 10,000 Gauss. The amplifier proper is a Newmarket model ref. P.C.4. Price £3.50 each. 10 for £31.50. Post and insurance 20p.

TELEPHONES
Complete as illustrated. Save your legs, time and temper, simply by putting in some telephones. Ex. G.P.O. not new—but guaranteed in good condition and serviceable. Supplied with diagram and instructions showing how to connect. Price £1.00 each + 50p post or 2 for £2.50 post paid. Also available separately: dials and bandsets 50p each + 20p post.

ROCKER SWITCH
13 amp self-fixing into an oblong hole, size approximately 1" x 1" 5p each. 10 for 72p.

SLIDE SWITCHES
Slide Switch, 2-pole changeover panel mounting by two 0B.A. screws. Size approx. 1 1/2" x 1 1/2", rated 250V 15amp. 7p each. 10 for 83p, 500 for £24. DITto as above but for printed circuit 5p each 10 for 45p, 100 for £4.25. 50 Miniature Slide Switch. DPDT 19mm (pin approx.) between fixing centres. 18p each or 10 for £1.08. 8P Change over spring return 250V 1 amp. 10p.

KITS FOR PREVIOUS PROJECTS

Unless otherwise stated, kits contain electronic parts only. The case and special items can be obtained locally. Also batteries are not included. Kits may be returned for refund if construction has not been started. We reserve the right to substitute components should deliveries be protracted so as to avoid undue delay.

HOMESENTINEL INTRUDER ALARM	£3.75
SNAP INDICATOR	75p
WINDSCREEN WIPER CONTROL	£2.25
RECORD PLAYER	£5.50
(amplifier components only)	
DEMO BOX	£7.00
FUZZ BOX	£1.85
PHOTOGRAPHIC COLOUR	
TEMPERATURE METER	£2.45
ASTRON RADIO	£3
REMOTE TEMPERATURE	
COMPARATOR	£4.25
ELECTRA LAUGH	£2
RAIN WARNING ALARM	£1.80
WA-WA PEDAL	£2.90
SIGNAL INJECTOR	80p
SOIL MOISTURE METER	£3.00
SIMPLE CALCULATOR	£2.20
DC POWER SUPPLY	£5.00
BABY ALARM	£4.00
AUDIO TONE GENERATOR	£2.60
METAL LOCATOR	£4.00
LIGHT TO SOUND CONVERTER	£1.70
THRU LENS LIGHTMETER	£3.50
DRILL SPEED CONTROLLER	£2.00
ELECTRONOME	£1.75
SHAYER INVERTER	£3.75
I.R. BURGLAR ALARM	£3.50
L & M RADIO TUNER	£2.50
TAPE POWER SUPPLY MAINS	£2.00
CAR	£1.10
ELECTRONIC MOUSE-TRAP	£2.75
REACTORMATIC	£3.00
RADIO CONTROL RECEIVER	£3.00
RADIO CONTROL TRANSMITTER	£5.50
BIT SAVER	£1.50
ICE WARNING DEVICE	£1.40
BETA TREBLE BOOST & FUZZ	£6.00
AUDIO COLOUR UNIT	£6.50
DAMP LOCATOR	£1.25
UHF AERIAL less boom	£1.50

J. BULL (ELECTRICAL) LTD.
(Dept. E.E.), 7 Park Street, Croydon CRO 1YD
Callers to: 192/3 Tamworth Road, CROYDON.

everyday electronics

PROJECTS...
THEORY.....

THE HEART OF IT ALL

A hobby for all ages, catering for all inclinations: this is present day electronics, thanks to the transistor. Young people naturally enough accept the transistor for what it has become—the heart of electronics, upon which all circuits depend. Yet it was not always so, as older constructors will recall.

The transistor first appeared on the scene twentyfive years ago. Prior to that event, the valve was the vital active component and things were very different. Electronics extended very little beyond the fields of radio communication and sound amplification. The home constructor of the pre-transistor era was likewise limited to those two traditional areas, apart from a rare excursion into a "non-electronic area" as exemplified, perhaps, by the building of a simple timer for photographic purposes.

ENTER THE TRANSISTOR

The transistor changed all that, and how! Let us briefly recall the pattern of development.

Tiny in size relative to the valve, the semiconductor device needed but a modest power supply. Thus as equipment became "transistorised" it became physically smaller and lighter in weight. Electronic equipment composed of quite complex and extensive circuitry was no longer restricted to more-or-less permanent installations. It could now be installed or used in environments and situations never before practical or accessible.

Twentyfive years ago saw the start of the emancipation of electronics. The following years brought forth great and exciting developments in circuit design. These circuits were often based upon ideas that were not always new in themselves, but which had been denied practical realisation in the days of valves, because of the physical encumbrances inseparable from thermionic devices.

SOLID STATE REVOLUTION

The transistor proved to be just the beginning of a solid state revolution. Soon it was followed by a whole family of different, but related semiconductor devices. Some, for example, were designed for detecting heat and light radiation, others for controlling large amounts of electrical power.

Thanks to the versatility of these semiconductor devices the possible uses for electronic circuits grew steadily. And men of ideas soon started to apply electronics to fields far remote from those of the valve days. Today, possible applications of electronic circuits are far from exhausted. The future holds even greater promise.



Our April issue will be published on Friday, March 16

EDITOR F. E. Bennett ● ASSISTANT EDITOR M. Kenward ● B. W. Terrell B.Sc.
ART EDITOR J. D. Pountney ● P. A. Loates ● S. W. R. Lloyd
ADVERTISEMENT MANAGER D. W. B. Tilleard

© IPC Magazines Limited 1973. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.35.

Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



..EASY TO CONSTRUCT
..SIMPLY EXPLAINED

VOL. 2 NO. 3

MARCH 1973

CONSTRUCTIONAL PROJECTS

EGG TIMER <i>A simple timer with audible warning</i> by R. Gwinn	126
NEON NOVELTY <i>Interesting, modern ornamental project</i> by B. C. Macdonald	139
ENLARGER EXPOSURE METER <i>For the d.i.y. photographer</i> by J. M. Bartlett	144

GENERAL FEATURES

EDITORIAL	124
GOONHILLY <i>Britain's earth station</i> by Tony Ford	130
RUMINATIONS by Sensor	134
BASIC ELECTRICITY <i>Part 5—Motors, Generators and Alternators</i> by Maureen Birch	135
SHOP TALK <i>Component buying and new products</i> by Mike Kenward	143
THE FIRST TRANSISTOR <i>Twentyfive years ago</i>	149
PLEASE TAKE NOTE	153
DEMO CIRCUITS <i>4 The Grounded Base Amplifier</i> by Mike Hughes	154

We continually get requests for back numbers, unfortunately we are simply unable to supply any. To make sure you receive all our issues, we suggest that you place a regular order with your newsagent.





EGG TIMER

by R. Gwinn

of the mains cycle, C2 is charged through D2 to 9V. In the negative half cycle, C3 is charged through D3 to 9V. As these capacitors are in series, 18V appears across the d.c. power supply rails of the circuit.

When the circuit is first switched on, C1 is completely discharged as it is shorted out when the timer is off. The gate of the field effect transistor (f.e.t.) TR1 does not take any current, so all the current flowing through the series combination of VR1 and R1 flows into the capacitor C1 and charges it slowly, hence the voltage on the gate of TR1 rises slowly.

When the gate of a f.e.t. is very negative with respect to its other electrodes, very little current flows through them as it is "pinched off" by the depletion region, an area in which virtually no current flows and whose size is controlled by the gate potential; the f.e.t. is in this state when the timer is first switched on.

As the gate becomes more positive with respect to earth (less negative with respect to the drain electrode) this region becomes smaller and more current is allowed to flow through TR1, R2 and VR2. This causes the voltage across VR2 and on TR2 base to rise.

When the voltage on the base exceeds that of the emitter by 600mV, base current, and hence collector current, begins to flow. When there is sufficient current to pull in the relay, its contacts apply 6.3V a.c. to the buzzer WD1.


Switching off removes the mains and shorts C1 ready to begin another timing cycle.

A simple design to enable eggs to be boiled to your satisfaction.

CONVENTIONAL egg timers have one major drawback, there is no positive indication that timing has stopped. It is infuriating to turn around and look at the egg timer, only to find all the sand in the bottom and a very hard egg in the saucepan. The electronic Egg Timer provides an audible warning.

CIRCUIT DESCRIPTION

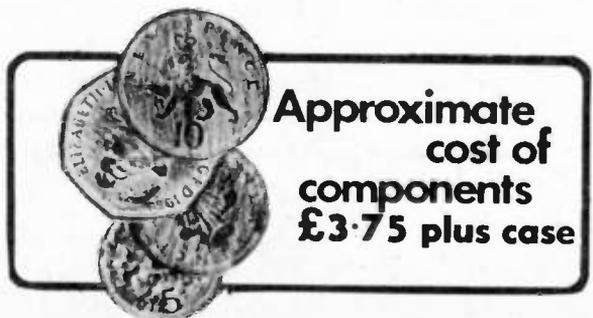The complete circuit diagram of the Egg Timer is shown in Fig. 1. During the positive half



**Approximate
cost of
components
£3.75 plus case**

EGG TIMER


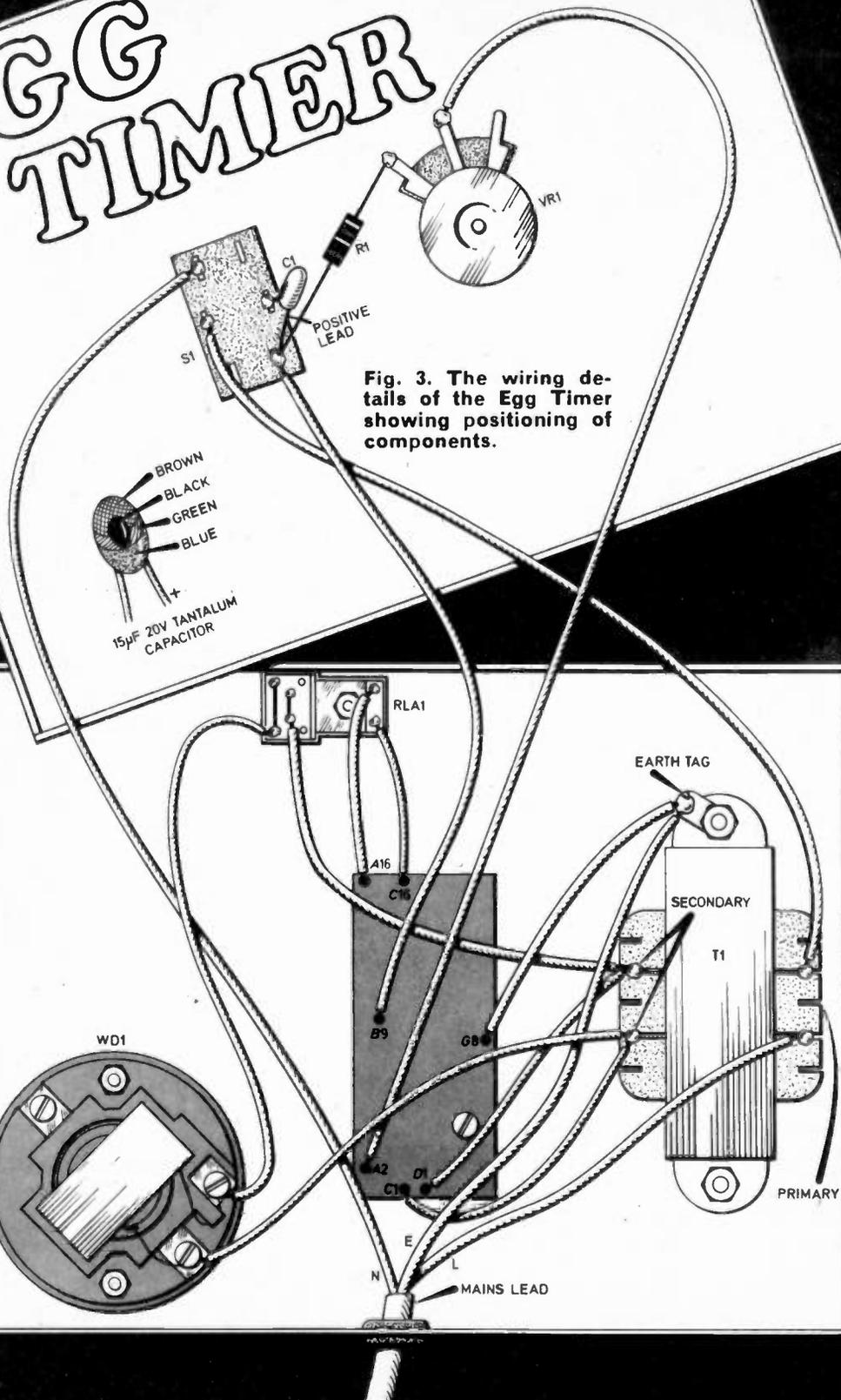


Fig. 3. The wiring details of the Egg Timer showing positioning of components.

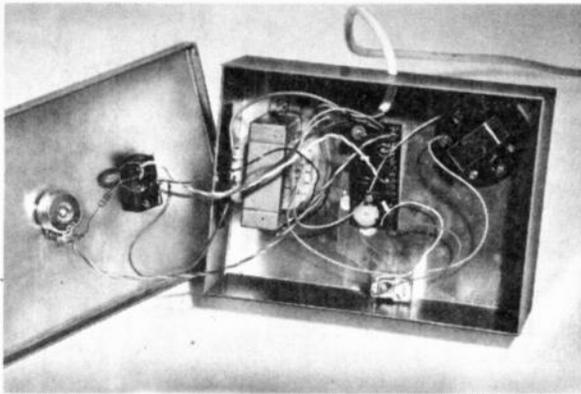BROWN
BLACK
GREEN
BLUE
+
15µF 20V TANTALUM
CAPACITOR



Photograph of the inside of the completed Egg Timer.

25mA (coil resistance greater than 700 ohms) will be suitable. The higher the resistance of the relay coil, the more accurate the timing interval is likely to be.

It may not be possible to obtain a relay with only one-pole make contact as is required, but this should present no problem as any contact arrangement can be easily adapted for this particular purpose, as in the prototype.

TESTING AND SETTING UP

Thoroughly check out the wiring and make sure the component board does not touch the metal case. It may be a good idea to glue a piece of foam rubber between the board and case so that the board is additionally supported and protected. This may be found necessary after testing due to the vibration of the unit when the buzzer is activated. Also check that the on/off switch does not touch any components inside the case when the lid is placed in position, insulating tape may be used as an extra safeguard.

Disconnect the buzzer and wire a 6V bulb in its place.

When you are completely satisfied that the wiring is correct, plug into the mains via a fused plug containing a 1A fuse.

When carrying out the setting up details given below, you should be extremely careful not to touch any wiring because mains voltages are on some wires and will give a nasty electric shock.

Adjust VR1 so that it is at its maximum, i.e. fully clockwise. With VR2 set to minimum resistance (fully anticlockwise), switch on via S1 and time for 7 minutes.

At this time, carefully (and quickly) adjust VR2 turning clockwise until the bulb glows. Now switch off via S1 (this discharges capacitor C1) for a few seconds and then switch on and record the time it takes for the bulb to switch on. It should be 7 minutes. If this is so, place a blob of glue on VR2 to secure it in this position, and mark the pointer position of VR1 on the lid to this effect. If the recorded time is not 7 minutes

adjust VR2 further until this time is achieved and then secure VR2 as above.

Now set VR1 to minimum position (fully anticlockwise) and measure the time from switch-on to the bulb glow and mark this time alongside VR1 point on the lid. This should be about 1½ minutes.

Intermediate times can be marked around VR1 knob by trial and error methods.

Required egg condition, i.e. soft, semi-hard and hard can be marked alongside the correct time if so desired as shown in front cover photograph, but this depends on many things such as size of egg, temperature of water, whether the egg has been stored in a refrigerator or not and is best done by trial and error.

Now replace the bulb with the buzzer and screw on the lid. The unit is now complete.

USING

When using the unit in the kitchen it is essential that a good earthing connection is available at the mains socket. The electronic Egg Timer, because it is using a mains supply, should be kept well away from any source of water or steam and not handled with wet hands.

To use the unit, select the "egg cooking time" required and switch on at the commencement of this time. The buzzer will sound when the set interval has elapsed. □

Components....

Resistors

- R1 5.6M Ω ½ watt carbon $\pm 10\%$
R2 18K Ω

Potentiometers

- VR1 4.7 M Ω carbon linear
VR2 1K Ω preset

Capacitors

- C1 15 μ F 25V tantalum bead type
C2 100 μ F elect 16V
C3 100 μ F elect 16V

Semiconductors

- TR1 2N3819 *n* channel f.e.t.
TR2 BC108 silicon *npn*
D1 1N914
D2 1N4001
D3 1N4001

Miscellaneous

- T1 Mains transformer, 240V primary, 6.3V 2A secondary
S1 Double-pole changeover toggle
WD1 Friedland 182 buzzer
RLA see text—suitable type STC 4189GD
Veroboard 0.15in. matrix size 16 x 7 holes; metal case, size 5in. x 7in. x 2½in.; three core mains cable; three pin fused plug; rubber grommet; 6V bulb—for test purposes only (see text).

SEE
**SHOP
TALK**

THE development of communications by space satellite is one of the most dramatic and fast moving chapters in the history of man's technological progress. Today, about 60 per cent of the world's inter-continental telephone traffic is carried by satellites stationed 22,300 miles out in space. Millions of people watch worldwide TV transmissions relayed by satellites positioned over the Atlantic, Indian and Pacific Oceans.

Yet it was as recently as 1962 that communication by satellite began when the first 'phone calls and TV pictures were beamed across the Atlantic via the pioneer satellite, Telstar. The historic signals were picked up at the Post Office satellite earth station at Goonhilly, Cornwall, a few miles from Lands End.

DEVELOPMENT

Since then Britain and Goonhilly have figured prominently in the rapid and exciting development of satellite communications. From the first commercial operations in 1965 with a single giant aerial focused on to a satellite, known as Early Bird, over the Atlantic, Goonhilly has become one of the busiest earth stations in the world. There are now three aerials at Goonhilly—the latest aerial coming into operation last year (1972)—which is the first earth station to have three aerials in simultaneous commercial operation to three satellites (two over the Atlantic and one over the Indian Ocean).

Developed at a total cost (at the end of 1972) of about £14m, Goonhilly has become the pattern for virtually all the world's satellite

earth stations—more than 70—which have mushroomed in the past decade. The huge aerials on the lonely Cornish moor have, therefore, helped realise a technological dream.

CABLE OR SATELLITE

It is necessary to define the role of satellites before looking in detail at the development of satellite communications. Will, for example, satellites eventually replace the other and traditional means of inter-continental telecommunications, undersea cables?

The short answer is no. The demand for international telecommunications service is doubling every four years and both cables and satellites are needed to meet the demand. Cables are ideal for busy or short routes and are still directly competitive over transatlantic routes. New developments in undersea cable technology (reviewed in *EVERYDAY ELECTRONICS*, September 1972, now no longer available) are dramatically increasing the communications circuit capacity of modern submarine cables.


The satellite has, however, one major advantage over the cable. It makes possible inter-communication between many different and widely scattered countries through a single piece of equipment—the satellite. Importantly too the satellite is the only way of providing inter-continental TV. In addition, the service provided by a satellite is flexible and can easily be adjusted to meet changes in demand.

The only other contender in the field of international communication is high frequency



Britain's Earth Station ...GOONHILLY

By TONY FORD

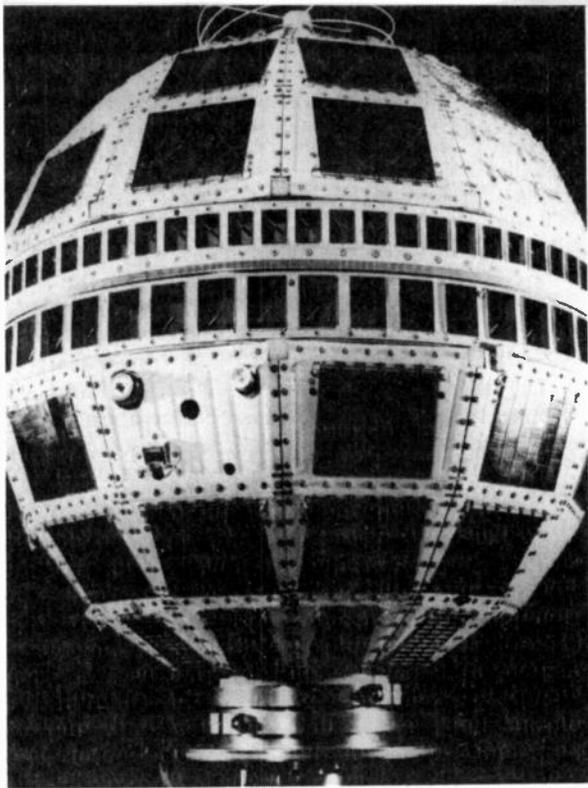

Shown above is the Mark II version of the original Telstar satellite.

radio which does not possess the capacity, reliability or quality of service needed for modern communication. In a remarkably short time, therefore, satellites have assumed a commanding and vital position in the expansion of global communications.

OPERATIONAL CONCEPT

Yet even during the brief space communications era there has been a fundamental change in the operational concept of satellites. In 1962 when the Telstar satellite was launched and USA, France and Britain took part in the first experiments it was envisaged that communications satellites would orbit in series and earth station aerials would track the satellites as they passed. Consequently during the Telstar experiments Goonhilly was only operational between the time the satellite appeared over one horizon and disappeared below the opposite horizon on its way around the earth—a period of only 20 minutes or so every two-and-a-half hours.

Barely had the feasibility of satellite communications been proved by Telstar when it became possible through the development of more powerful launching rockets, to place a satellite so far out in space that its orbit coincided with the Earth's rotation. At this distance, 22,300 miles above the Earth, the satellite appears to remain stationary—an orbit that is described as geo-stationary.

Everyday Electronics, March 1973

Earth stations could now focus permanently on the satellite and the complications involved in swiftly picking up and locking on to lower orbiting satellites and tracking them across the sky were removed.

INTELSAT

The global communications scenes then began to move swiftly. A group of 11 major countries, Britain included, signed an agreement in 1964 to form INTELSAT, the consortium responsible for providing the satellites and associated tracking and control facilities. This responsibility, described as the "space segment", does not include Earth stations which are the sole concern of the satellite users. Subsequently the number of INTELSAT members has grown to a total of 83 countries.

With the advent of the geo-stationary satellite whole new frontiers of technology were revealed. The science of space communications had to be created and perfected—the satellites, the aerials, ancillary earth station controls and telecommunications links to and from the earth stations and their national internal networks. One major problem was the maintenance of signal strength. The satellite picks up the signal beamed from the aerial, increases its strength and re-transmits it to a second earth station which means that the signal travels a total of about 45,000 miles.

Transmission and reception are simultaneous but the signals do not clash because different frequencies are used. The time taken for the signal to travel from earth to satellite and back to earth is about a quarter of a second.

When the signal arrives back on earth it is, however, so faint that it could be swamped even by the small amount of "thermal noise" made by the receiving equipment. To overcome this problem the receiving equipment at Goonhilly is cooled to minus 256 degrees Centigrade. This minimises molecular activity in the receiving equipment and enables the incoming signal from the satellite to be received with great clarity. The signal is then amplified in a series of steps until it is strong enough for ordinary transmission over the telephone network.

ACCESS

The amplified signal is, in the case of Goonhilly, carried by a microwave radio link in the 6000MHz band which connects the earth station with the international switchboard through the Post Office Tower in London. This link is routed via Plymouth and Bristol and a reserve system can be used for TV transmission simultaneously with telephony.

Since Goonhilly has multi-access to three satellites it has to break down the channel capacity of the baseband content of the inland microwave link to component super-groups and where necessary, to individual groups of chan-

nels, and then reassemble them in required channel content for transmission to the satellites. The same process must also be carried out in reverse for signals received from the satellite. This function is performed at Goonhilly by multiplex equipment which also provides pilot-frequency monitoring as a check on system performance.

The below baseband (0-12kHz) spectrum of each satellite carrier is used to provide engineering service order wires, both voice and teleprinter, which are separated from the traffic baseband before it reaches the multiplex equipment. Translation of these circuits is separately made in another, specially designed, multiplex equipment installation.

CONTROL

Operational control of the Goonhilly earth station is centralised in a main building separate from the three aerials. A console suite contains the engineering control of the aerial steering systems in addition to associated communications equipment. The console also allows monitoring of the continuity of traffic signals through the system.

For both colour and monochrome television there is a separate control and monitoring suite. Complementing this control there are speech and teleprinter engineering service circuits and two switchboards. From these the controller can maintain contact, through the satellite, with engineers at distant earth stations and their operational control centres. The entire working station is duplicated and there is automatic change-over when any unit fails. Manual change-over can also be made if necessary.

The main control console for all three aerials at Goonhilly.



SITE

The planning for Goonhilly earth station began with the initial choice of the site for the station. It had to be in the west of the country for maximum mutual visibility to the, then, low altitude satellites working with a station in the USA. It also had to be in the south because 95 per cent of the world's telephone users are to the south of Britain (and, therefore, satellite systems were also likely to be in the south).

The sub-strata had to be stable enough to support the weight of the aerials (about 1,000 tons each in the case of the first two aerials) and there had to be an all-round clearance elevation above about five degrees. Goonhilly easily meets both criteria. The earth station site has a rock base hundreds of feet thick and is on a plateau with an all-round clearance of half a degree in elevation.

Goonhilly is reasonably close to inland communications links, is also free from radio interference and does not cause interference to other communications systems.

The weather in the area had to be considered, for with three aerials whose dishes range from 85ft to 97ft in diameter on such an exposed site 350ft above sea level, wind damage could be calamitous. In fact, wind speeds at Goonhilly rarely exceed 60 mph, but to be on the safe side the aerials have been designed to survive wind speeds well over 100 mph and even, in the case of the third and latest aerial, up to 130 mph. Finally, heavy snowfalls, which could build up and overload the aerial structures, are rare at Goonhilly while rainfall, although frequent, is not unduly heavy.

An engineer checks pictures at the television control and monitoring console.



SATELLITES

After choosing the ideal site and spending, to date, about £14m on developing Goonhilly, the Post Office has also spent some further £12m towards the purchase and launching of satellites by INTELSAT. The money, together with that from other INTELSAT member countries, has provided for the development of a series of satellites each more sophisticated than the last.

Since the first days of the INTELSAT consortium in 1964, four series of satellites have been built. From a single Early Bird satellite (Intelsat I) with 240 circuits and point-to-point access only, in 1965, the system progressed to a multiple-access global service in mid-1969 using Intelsat III series satellites and then to Intelsat IV service by mid-1972.

Compared with the single links in 1965 from the USA to the UK or France or Germany there is now a global network of about 200 simultaneous links between pairs of earth stations.

Today's satellites, Intelsat IV's, are able to handle up to 5,000 communications circuits at once plus separate TV transmission facilities. They weigh almost one-and-a-half tons at launch, are taller than a double-decker bus and cost £6m each, plus about £7m for each launch. America's National Aeronautical and Space Administration (NASA) launches all INTELSAT's satellites and the powerful Atlas Centaur rocket is used to launch the Intelsat IV which has a design life of about seven years.

The Intelsat IV satellites have two important new features which make them more efficient to operate compared with earlier satellites. In addition to providing global coverage with its signals the Intelsat IV is able to concentrate

part of its power in two spot beams focused on the busy routes such as North America and Canada in the east and Britain, Europe and North Africa in the west.

Part of Intelsat IV's capacity can also be reserved for "demand assignment". This new system will allow a country with several light traffic routes to use, say, two or three access channels to cover them all where previously one pre-assigned circuit was required for each route.


Since January 1971, four Intelsat IV satellites have been launched and between them they carry all the INTELSAT traffic. Another four Intelsat IV satellites will be launched to provide spares-in-orbit over the three operating regions—the Atlantic, Indian and Pacific Oceans.

It should be explained that Russia is not a member of INTELSAT as they have their own and separate satellite communications system known as ORBITA which employs satellites in orbits quite different from those used by INTELSAT but which are especially suited to the coverage of the whole of Russia.

DEMAND

Despite the greater capacity for circuits provided by the latest satellites, demand is growing so rapidly that it is likely that by about 1975 still more capacity will be needed and even bigger satellites may be required. The growth in the number of circuits used by satellites has been startling. In mid-1967 the number of satellite circuits in use totalled 100. Today the global total is about 3,500 plus 5 to 10 per cent added for "occasional" use such as TV programmes. In the Atlantic region alone the

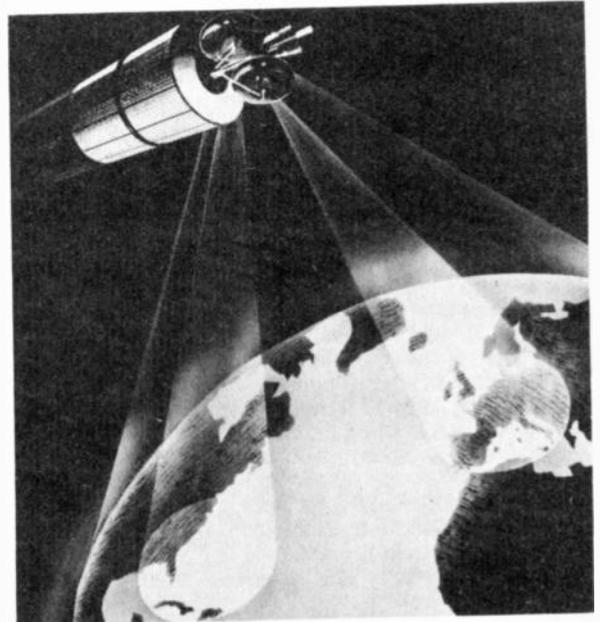
Part of the Intelsat IV's power is concentrated in two spot beams.



number of satellite circuits in use is more than 2,000, of which just under 500 are via Goonhilly. (In addition just over 600 UK-Atlantic circuits go by undersea cable.)

The three aerials at Goonhilly provide direct communication via satellite with 34 countries. Aerial Two (built in 1968) and Aerial Three (built in 1972 at a cost of £2¼m) are linked to 18 countries by satellites over the Atlantic. Aerial One (built in 1965 and re-equipped in 1969) operates to 16 other countries via a satellite over the Indian Ocean. Within the next few years a further 20 or more countries will join the INTELSAT system. At present Goonhilly has almost 700 long distance telephone circuits in operation.

Of all the statistics underlining the impressive growth of international telecommunications perhaps one of the most satisfying relates to the decreasing cost to the user. Today a phone call to North America can be made on international subscriber dialling for as little as 50p a minute. Yet when transatlantic 'phone services were begun 45 years ago the minimum charge for a similar call was £15—in those days the equivalent of several weeks' wages. Such dramatic cost reductions have not stemmed wholly from the advent of satellites, but their use has allowed countries to expand their international communications links more cheaply than if there had been no alternative to the laying of trans-oceanic cables. □

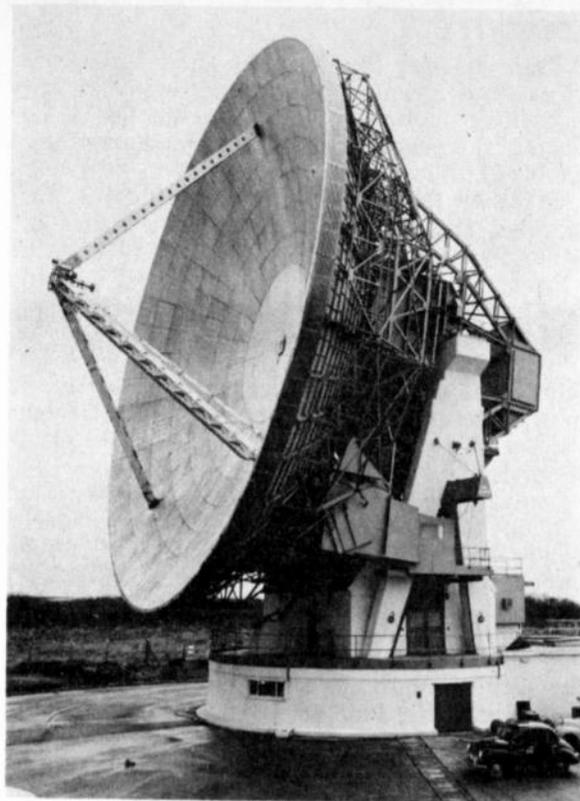

Aerial One built in 1965 and re-equipped in 1969. It operates to 16 countries via a satellite over the Indian Ocean.

Ruminations

By Sensor

Self-help

Most of us take our television for granted. In most parts of England good quality colour television programme reception is enjoyed but what about the folk in more isolated places who cannot get a decent black and white picture? For example, north of Inverness and in North West Scotland it is impossible to receive BBC 2 transmissions and ITA reception is poor. The BBC 1 signal is not always received—particularly, if there is a mountain between one's home and the transmitter.

In December 1972 BBC 1 colour programmes became available to viewers in the Inverness area from the transmitter at Rosemarkie, and a low power relay

station further south at Rosehearty helps to extend the area of the Aberdeenshire transmitter and the new station at Rosemarkie. The BBC plan to build many more of these low power relay stations, like the one at Rosehearty but it will be well into the 1980's before these are completed. Even then, there will always be many areas which cannot be reached because of the mountainous terrain.

The inhabitants of one village may enjoy relatively good reception whilst their neighbours only a mile away may receive nothing at all. Of course, the capital cost involved in providing even BBC 1 black and white pictures to certain parts of the Highlands would be quite prohibitive. However many communities have subscribed sufficient funds to erect their own communal mast on some suitable hill in order to enjoy their "telly". In one such village viewers pay £25 a year plus £4 maintenance costs into a television "club", in addition to their

licence fee and rental payments, for their piped television.

Deprived

Many people living in these remote areas feel that they are deprived in so many other respects such as libraries, further education facilities, cinemas and theatres, and yet, they are expected to pay the full licence fee even though they will not receive the full range of BBC and ITA services. It is natural that they should feel that a graded licence system ought to be introduced for areas of this kind.

Of course, all will be well when we each have our own satellite receiver. The thrifty Highlander will quickly learn to construct his reflector dish from old oil drums, driftwood and rubbish left by the English tourist and, with true Highland hospitality, will invite his "bed and breakfast" guests to watch the Highland Games in full colour whilst they are gathered around the peat fire. But that's nae yet!

BASIC

5 Electricity

Motors, Generators, Alternators By Maureen Birch

WE HAVE seen that a current flowing through a coil of wire that is suspended in a magnetic field produces movement of the coil. The coil always tends to align its axis with the field because the current flowing through it makes it behave like a magnet with its own north and south poles. These poles attract or repel the poles of the fixed magnet (producing the field) and the combination of these forces rotates the coil until it reaches a stable position—its axis in line with the field. This simple principle is adapted and refined to drive motors which in turn drive machines.

CONTINUOUS ROTATION

Continuous rotation of the coil can be achieved by arranging that just as the axis of the coil lines up with the field, the current flowing is momentarily stopped and the inertia of the coil is allowed to carry it past "top dead centre." The current is then reversed so that the poles that were attracting each other are now repelling each other, and vice versa.

Provided this is done every time the coil is about to line up with the fixed magnetic field continuous motion can be obtained. To turn the attractive forces to ones of repulsion we must either reverse the north/south direction of the fixed magnetic field, or, as is more usual, the direction of current flow through the coil.

COMMUTATOR

This reversal is accomplished by means of a commutator. It consists of a copper tube over an insulated cylinder that is fitted on the shaft that pivots the coil. The tube is fastened to the cylinder and is cut into two parts by two diametrically opposite saw cuts along its length.

The wires from the coil are each connected to one of the halves of the commutator and current is fed to the coil via brushes made of

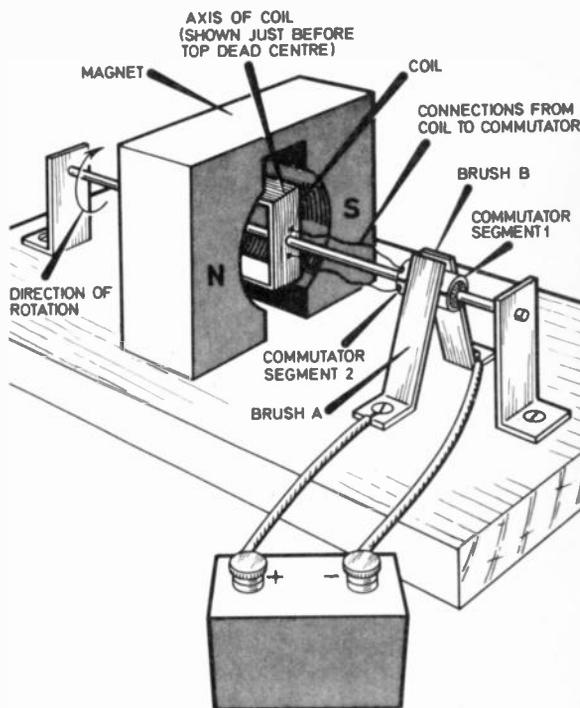


Fig. 5.1. A simple two-pole permanent magnet motor.

springy material (or in larger motors, carbon) that make contact with the commutator.

If a source of direct current is connected across the brushes the current will always enter by brush A (Fig. 5.1) and leave by brush B. When section 1 of the commutator is in contact with A, the current will flow through the coil in one direction and the coil turns until top dead centre is reached; the current flow is then momentarily broken and section 2 of the commutator makes contact with brush A. The direction of current flow is thus reversed and the coil continues to swing round towards top dead centre in the opposite direction.


ARMATURE

The forces acting on the coil are considerably increased if the coil is wound on a core of soft iron. This core, called an **armature**, is usually built up of thin sheet stampings that are electrically insulated from each other by thin paper. This reduces what are known as **eddy currents** which are induced in any metal object that moves in a magnetic field and in such a direction that they try to oppose the motion that is taking place.

The torque (twist) produced by the current and field is greatest when the axis of the armature is at right angles to the field and becomes zero at the top dead centre position. Because of remanence effects a simple two-pole motor like the one described will usually stop with the armature in the top dead centre position and therefore when current is re-applied there will be no torque and the motor will not start by itself unless spun by hand. This leads to the device of winding several coils on one armature, most commonly in the case of small model motors, three coils are used on a three-pole armature, see Fig. 5.2. There must be as many commutator segments as there are coils so that current can be made to change direction and be applied to the right set of coils at the right time.

The advantage of a three-pole motor is that there can never be a time when all three poles are at top dead centre and therefore there will always be some torque when current is applied and the motor is thus self starting.

Fig. 5.2. (a) Two pole, (b) three pole armatures and commutators.

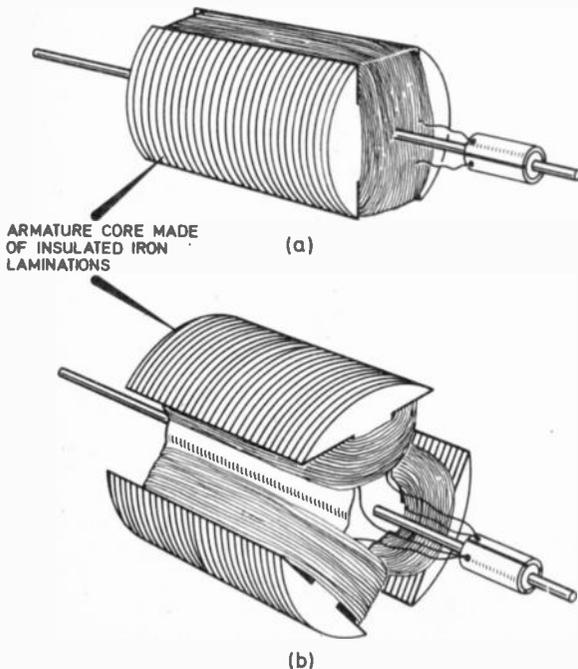

FIELD WINDING

In the case of small model motors the magnetic field is usually provided by a strong permanent magnet, but in the case of powerful machine motors, the field is produced by a separate coil called a **field winding**. The field winding can be connected in series with or in parallel with the brushes, see Fig. 5.3.

When series connected, one obtains very high starting torque but the speed of running is load dependent; with the parallel connection not so much torque is produced at switch on, but is better for running at constant speed under varying load conditions. Very powerful motors—as used for traction purposes—often have a switch which is used to convert them from series to parallel (sometimes called shunt) connection thus giving the driver the best of both worlds.

GENERATOR

One of the most momentous discoveries of the past was that of producing an electric current in a circuit without the aid of a battery. The principle of the **generator** is very simple. Whenever a wire, that forms part of a closed circuit is *moved* in a magnetic field, an electromotive force is induced and this causes a current to flow through the circuit of the wire.

If the wire is in the form of a coil, preferably on an iron core, the effect is greatly enhanced.

SIMPLE EXPERIMENT

If you have a radio with auxiliary record player input connections or a small amplifier, you can see what we mean, by connecting our electromagnet (from last month) straight across the record player input and then bring a small permanent magnet up in contact with the poles of the electromagnet, Fig. 5.4. This is the same as moving the coils of the electromagnet in a field.

Let the permanent magnet touch the pole of our home-made magnet; if you have the amplifier (radio) turned up sufficiently you will hear a "clunk" in the loudspeaker. This clunk is caused by the sudden increase in field strength of the permanent magnet inducing a voltage in the windings of our electromagnet. The radio serves only to amplify the voltage so that we can hear the effect in the loudspeaker. **Under no circumstances try this experiment unless your radio or amplifier has properly installed record player inputs.**

RATE OF CHANGE

This remarkable ability of magnetism to cause a flow of electrons is something we just have to accept. A wire, or coil, moving so that it cuts lines of magnetic force has this voltage induced across it and when moved in the opposite direction the e.m.f. polarity is reversed. The interest-

ing thing is that there is no induced e.m.f. unless the coil is moving, and the faster the coil moves the higher the e.m.f. Alternatively the coil could be kept still and the strength of the influencing magnetic field varied to get the same effect. The induced e.m.f. is proportional to the rate of change of magnetic flux crossing the wire or coil. The e.m.f. is also directly proportional to the length of wire (provided all the wire is subjected to the same change in flux) or, in the case of a coil, the number of turns of wire on the coil.

REGULAR A.C. OUTPUT

Our experiment produced an e.m.f. but it was very hit and miss and could not under any circumstances be called a steady voltage. To get a regularly produced e.m.f. it is usual to suspend a coil on a pivot in a fixed magnetic field and rotate the coil.

The current produced in this way is not steady, it is greatest when the coil's axis is perpendicular to the direction of the field since this is the position where the coil cuts straight


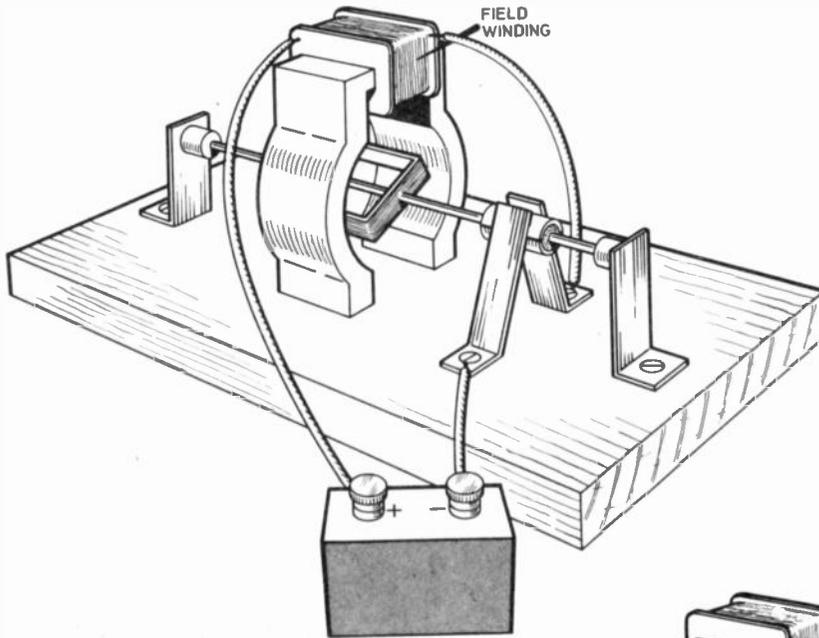


Fig. 5.3 (left). Shows a simple two-pole electromagnetic motor with series connected field winding. Below shows the parallel or shunt connection.

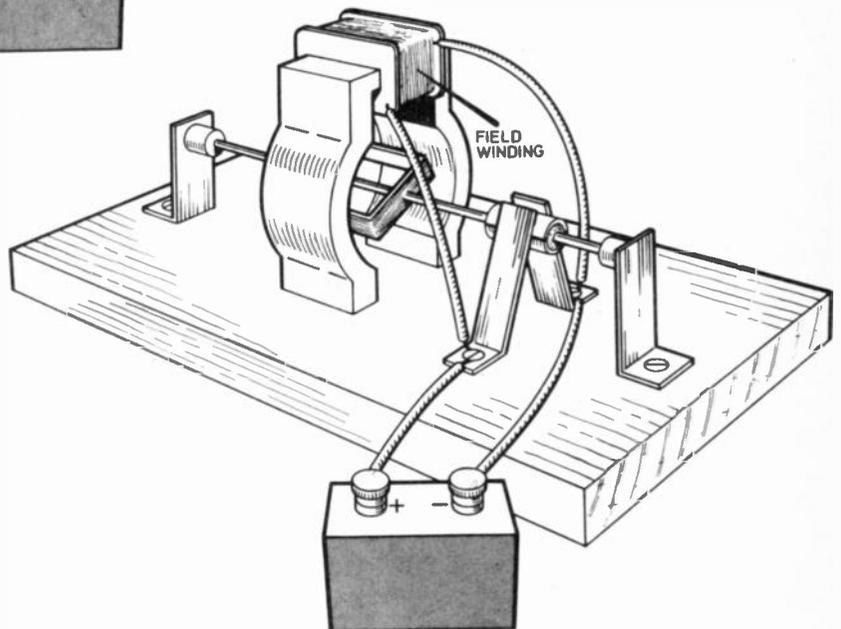

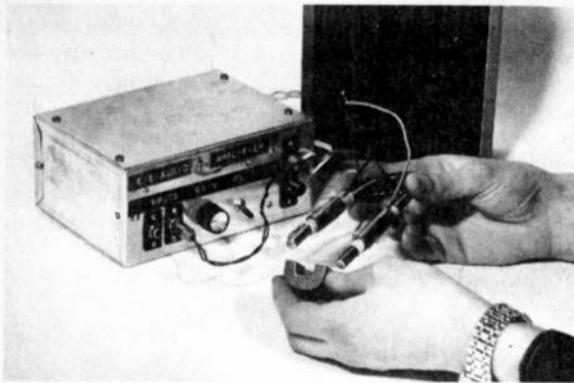


Fig. 5.4. Experiment to demonstrate electromagnetic induction.

across the lines of force. No current is produced in the top dead centre position because in this position the coil is tending to move along the lines of force and is not actually cutting across any.

If we follow one side of the coil as it rotates, Fig. 5.5, we see that for almost half of each revolution it is moving *up* through the lines of force but for most of the other half is moving *down*. As a result the current changes direction once in complete revolution; we say the current is alternating (a.c.).

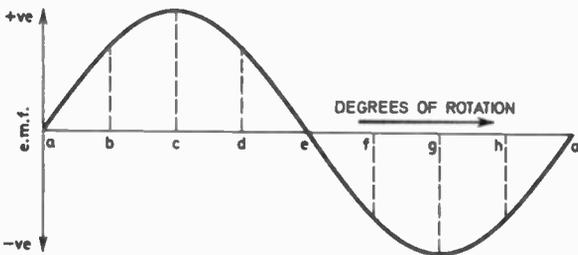
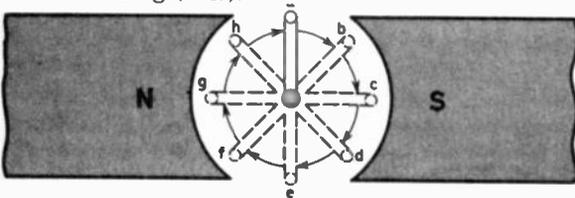


Fig. 5.5. Graphic display of generated e.m.f. as a function of rotation angle.

To get the induced current from the armature windings we use a form of commutator (Fig. 5.6) called a slip ring. Notice there are two slip rings and there is no split in either. The alternating current is picked up by brushes running in contact with the slip rings. This type of device is called an **alternator** and the 50Hz a.c. mains fed to our homes is generated in a similar way.

A direct current generator uses the same principle of induction as an alternator but is


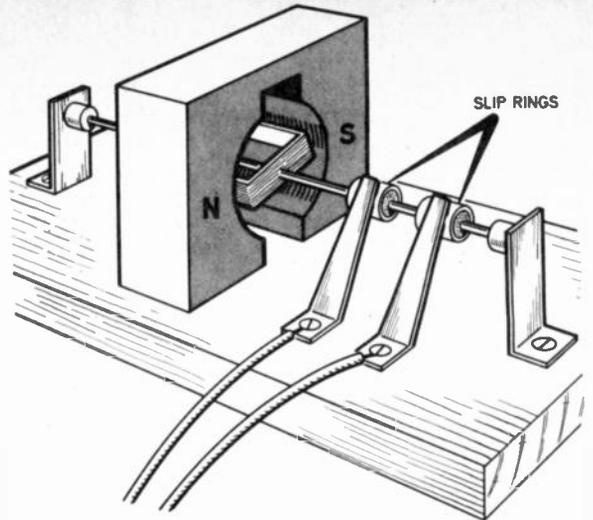
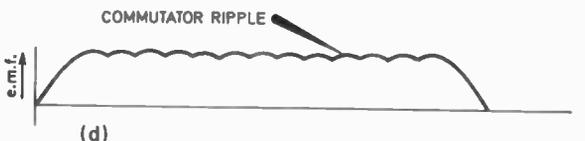
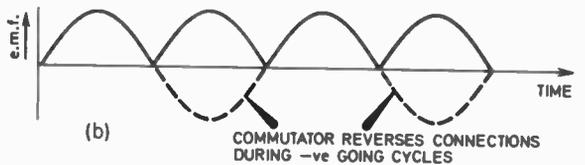


Fig. 5.6. Simple two-pole alternator.

built more along the lines of the d.c. motor. The output must be in one direction only and as steady as possible. By using a commutator instead of slip rings the negative half of each cycle is reversed and the result is a one directional pulsating output, see Fig. 5.7.


To reduce the level of the pulsations (or ripple) and so produce a more steady output more coils are introduced and the final output shows only small and rapid fluctuations.

Fig. 5.7. Outputs from (a) alternator (b) generator (c) multipole generator (d) effective output from (c).

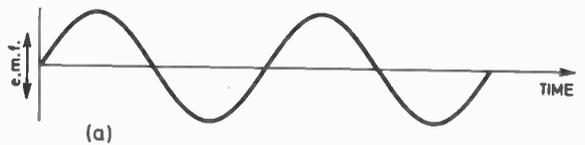

Next month: The transformer and simple household electricity.

NEON

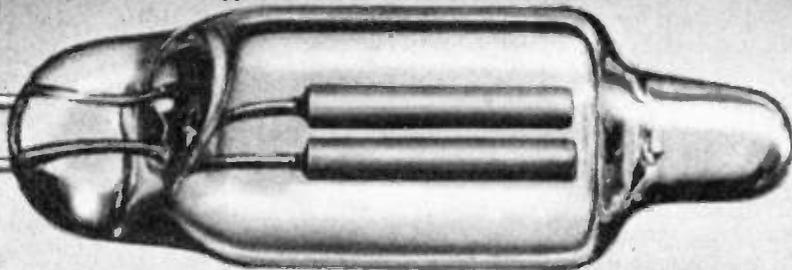

NOVELTY

An inexpensive, intriguing novelty for a youngster or for an unusual modern ornament.
By B. C. Macdonald

A SIMPLE novelty item can be made up using a number of flashing neons arranged in a small plastic case or by using two neons placed in the eyes of a child's toy animal. The first type of novelty—the "flashing block"—could make an interesting paper weight or modern ornament.

Both types of novelty are particularly interesting when viewed in the dark. The neons will continue to flash for a number of years because they drain on the battery, even with 8 neons, is only about 60 microamps. The neon bulbs flash independently of each other, the effect of the orange/red flashes is quite striking.

CIRCUIT DESCRIPTION

It will be seen from Fig. 1 that each neon is wired into a similar circuit, all of which are connected across a 90 volt battery. Each of these circuits operates independently. The basic circuit consists of a 10 megohm resistor (R1) in series with a 0.22μF capacitor (C1). A neon bulb (LP1) is connected in parallel with the capacitor.

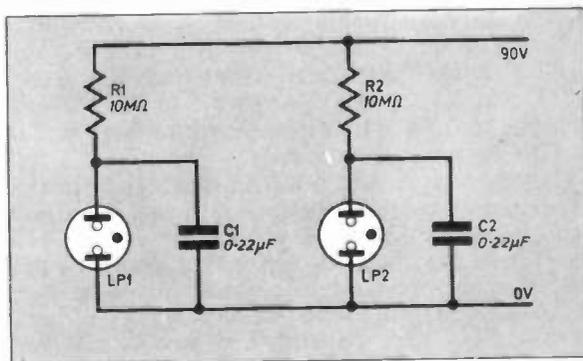


Fig. 1. Basic circuit diagram of Neon Novelty.

A characteristic of neon bulbs is that they do not light or draw any current except at a certain minimum voltage (about 80V for the type of neon used) and as soon as a holding voltage (about 60V) is no longer maintained the neons extinguish and become open circuit.

Consider one circuit only, since each works in the same way. The battery B1 charges capacitor C1 through R1. As the capacitor charges the voltage across it rises and will finally reach the battery voltage if not discharged. The rise in voltage is slowed down by the high value resistor R1, which restricts the current flow. As soon as the "firing" voltage of the neon is reached the neon lights but immediately goes out because in lighting it has discharged the capacitor and thereby reduced the voltage across it to less than the holding voltage. This charge and discharge then continuously repeats.



Approximate cost of components
£1.50 (8) 45p (2)
plus cases and batteries

The rate of flashing (charge and discharge of the capacitors) varies as the product of the capacitance and resistance, but to alter the flashing rate it is only necessary to alter the value of the resistor to vary the rate (reduce to increase the rate).

Although the value of the components is the same for each circuit each neon flashes at a slightly different rate, due to tolerances in the components. For this reason 20 per cent tolerance resistors will, in this case, provide a more varied display than closer tolerance types. As many neons as are required can be used in the circuit.

When six or eight neons are used together as in the unit shown, the effect is that of random flashing, since each bulb is flashing at a slightly different rate and no sequence is obvious. In the case of eight neons it may be found advantageous to vary the value of some of the resistors to alter the rates by a greater extent.

MODIFIED CIRCUIT

When using more than two neons it is possible to slightly modify the circuit to give a softer type of flashing which is, in fact, completely random. This is done by connecting one end of each capacitor together—see Fig. 2—by this means each flash is related to the state of charge in the capacitors, which is in turn related to the flashes of other neons.

The action of such a circuit is too complicated to try and explain fully and is, in fact, very difficult to see since each circuit is inter-related. Suffice to say that it works by the charging and discharging of the capacitors, is completely random and provides a longer "flash" of each neon; this circuit does in fact, provide the best type of display when all the values are similar.

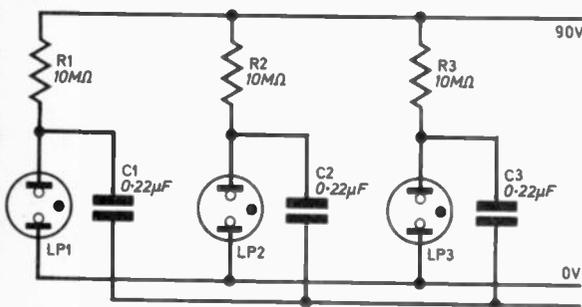


Fig. 2. Modified circuit for random flashing.

THE COMPONENTS

A 90 volt battery is required, such as the Ever Ready B126. Any type of 0.22μF capacitors may be used provided they have a working voltage in excess of about 100 volts. Any type of resistor may be used, but the ¼ or ½ watt carbon kind are of a convenient size (the colour coding of a 10 megohm resistor is brown, black, blue). The value of the resistors is by no means critical

and anything from 2 megohm to about 15 megohm will be satisfactory.

The correct type of neon is essential, this must be suited for operation from 70 to 90 volts, such as the Hivac 34L or the American type NE2 (these are direct equivalents). The bulb is in the form of an elongated glass capsule with thin flying leads.

A two pin or three pin plug will be required for making the connection to the battery. The polarity of the battery is not critical and therefore, the third locating pin on the connector is not required.

CONSTRUCTION

It was decided to use connector strip for the two neon circuit (animals eyes) since this requires no soldering and simplifies construction.

Obviously the leopard shown is a very suitable subject, but other animals could be used. In looking for a suitable animal model stuffed types were rejected because of the difficulty in inserting the eyes and connecting wires. A "nodding leopard" was finally used. These are sometimes seen in cars, the head nodding continually due to the motion of the car. The head is suspended in the body and can be easily removed. Both head and body are made of rubber and are hollow and so are quite easily adapted to the purpose required.

Do not cut the wires on the neons, but extend them by soldering short lengths of single plastic covered bell flex or similar wire to their ends. Now push short lengths of sleeving, just large enough to pass over the flex, right up to the neons so as to insulate the bare wires from each other. Secure the sleeving at the point farthest from the neon with a little plastic insulating tape.


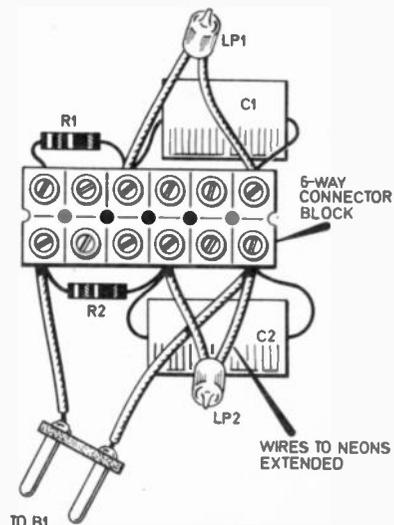


Fig. 3. Wiring for the two neon circuit.

NEON NOVELTY

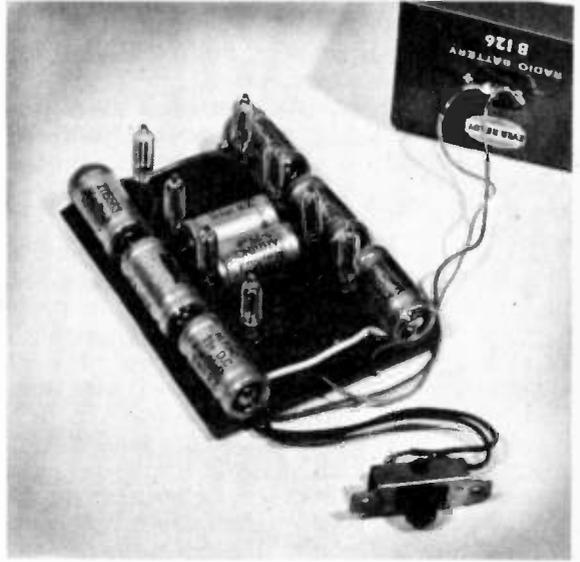

Photograph showing the completed circuit board and battery for an 8 neon "flashing block" unit.


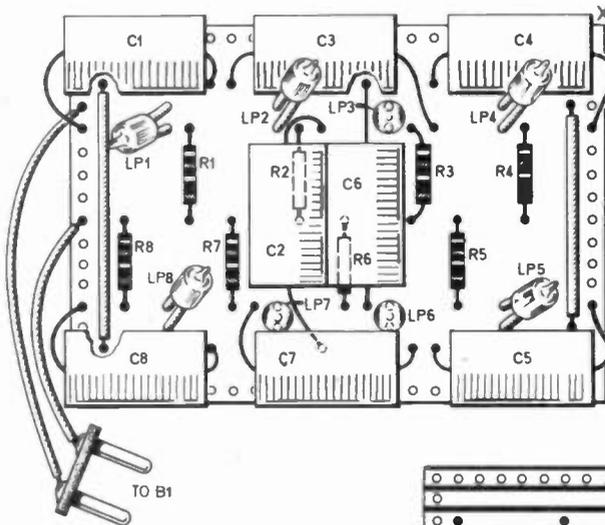


Fig. 4. Layout and wiring of the Vero-board for the 8 neon unit. The underside is shown below with cut aways and S1 wiring. To orientate the lower drawing find corner X on both views.

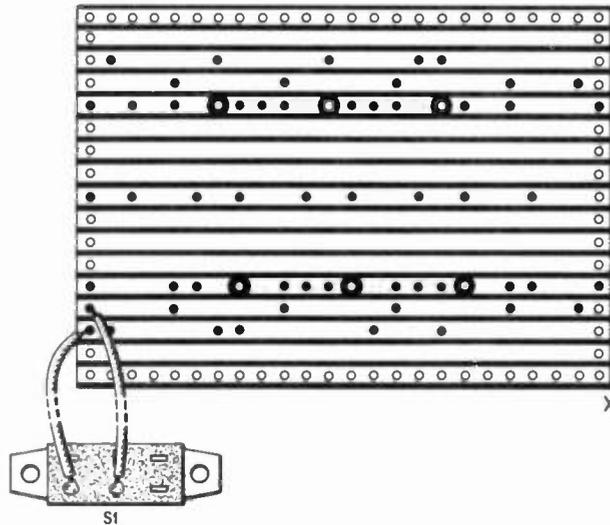


Fit the resistors, capacitors, the neon wires and the battery wires to the connector strip exactly as shown in the illustration (Fig. 3). Check carefully that all the connections are correct then push the plug into the battery. The neons should commence to flash.

Incidentally it is possible to get a shock from the battery although this is not normally dangerous.

HOUSING

Disconnect the neon wires from the connector strip. Pull out the eyes from the animal's head and insert the wires connected to the neons. Pull the wires through and finally push the neons right into the head so that only the end is showing. They must be secured with some kind of adhesive. Araldite adhesive was used and proved to be very satisfactory but no doubt other types, such as Evostik could be used. Immediately the eyes are in position in the head re-connect them to the connector strip and check if they still flash. This is a necessary precaution. The author found although the neons flashed before fitting they failed to flash after fitting. It was assumed that the very small current required by the eyes was short circuited and some of the plastic insulating tape was removed and the eyes flashed when re-fitted. This is why the sleeving should be taped only at the farthest point from the neons.

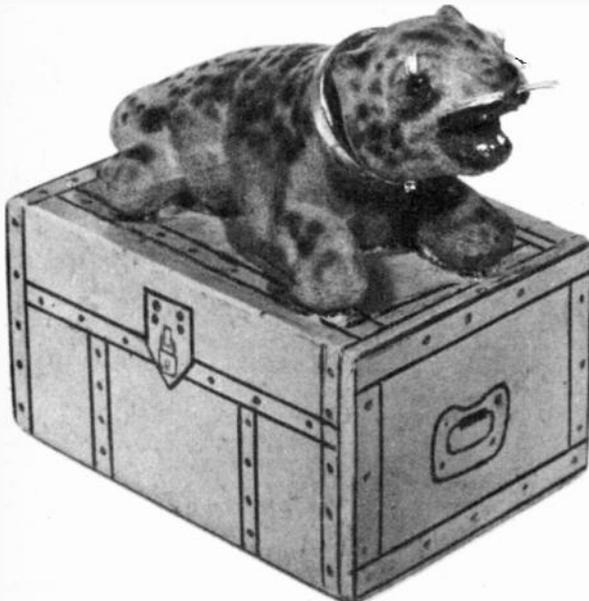Make or otherwise obtain a box of suitable size to easily house the battery and connector strip. A wood or plastic box is best.



The completed leopard lying on the box housing the battery.

Fit the leopard's head to the body, cementing it in place, and passing the wires into the body having previously made a hole in the base so

that they can emerge. Any convenient point will do, a hole in the leopard's paw was used in the prototype, the wires passing through this and also through a corresponding hole in the top of the box.

All the wires must be long enough to allow the connections to be made to the connector strip when it is outside the box. The next thing to do is to cement the leopard to the top of the box, using elastic bands to hold it in position while the cement sets.

FINISH

The battery and connector strip must be fitted in the box so that they will not move about and it is suggested that plastic bags should be crumpled up and used as packing and to separate the connector strip from the battery. Since access is not required over a number of years, the box may be closed, using cement but a small hole **must** be provided, otherwise there may be condensation inside the box, resulting in failure of the eyes to flash or pressure may build up as the battery is exhausted and the box may "explode." The box can be finally painted in suitable colours.

Two important points; solder the extension leads to the neon wires close to the ends of these wires and not near the glass. Do not try to light the neons by connecting directly to the battery; they will be destroyed if this is done. A 68,000 ohm series resistor must be used if the bulbs are connected **directly** to the battery. The resistor is replaced by R1 in the circuits.

BLOCK CONSTRUCTION

In order to make construction of the "flashing block" more easy a Veroboard layout is given (Fig. 4). This layout can be used for either circuit (Fig. 1 or Fig. 2) by operating switch S1.

Commence construction by inserting all the resistors, capacitors and wire links, including those to S1, in the Veroboard, cut the leads off and solder each connection. Next make the six breaks in the copper strips as shown and finally connect up the battery leads and solder in the neons so that the bottom of the two electrodes (inside) is about $\frac{1}{8}$ inch above the top of the highest components.

Connect the leads to the battery and check that all the neons operate, now operate switch S1 and compare the two types of display.

If only one type of display is required—a link could be put in place of the switch or both switch and link may be omitted. The unit can be housed in a wooden or plastic box with the neons showing through the top. Some Araldite around the base of each neon will hold them firmly and a Perspex cover could be made to fit over the top to protect the neons.

Continued on page 148

ONCE again we have run into supply difficulties on one particular component—the transformer used in the *Radio Control Receiver*—apparently Arden te are no longer in business and, as far as we know, all supplies of the transformer have now been exhausted. As we stated in the article, a larger type of transformer is available from Henry's Radio and this could be used if the board is extended by 0.6 inches at the TR5 end to hold the transformer, and the connections made using flying leads. If the receiver appears to suffer from lack of range try adjusting the value of C8.



Unfortunately we have been unable to find a transformer with exactly the same specification as the Arden te one and we are unable to give an alternative that will fit into the space on the board—the transformer available from Henry's is not that much larger than the original.

Egg Timer

The first "kitchen aid" that we have published; a design for the *Egg Timer*. A tantalum type capacitor must be used for C1 in this circuit since this type has a much lower leakage current than an electrolytic, which would not be able to charge due to the small current available through VR1 and R1.

Some difficulty may be experienced in obtaining the 4.7 megohm potentiometer specified

Everyday Electronics, March 1973

—Electrovalue of 28 St. Judes Road, Englefield Green, Egham, Surrey, can supply this pot. The cost of this item is 12p plus a small order surcharge of 10p (for orders under £2); this includes postage. Incidentally we do not take postage or any surcharge into account when we calculate the approximate cost of any of our projects.

The buzzer for the timer should be available through most electrical shops and the case of the prototype is a standard aluminium chassis available from many of the firms who advertise in our pages.

The relay used can be any fairly small type provided it has a coil resistance of at least 700Ω—the higher the value the better—and can work on 18V; the prototype unit used a 3000Ω 18V type. The relay should have at least one set of normally open contacts rated at 1.5 amp, alternatively two or more sets having a lower rating could be used, wired, in parallel.

Neon Novelty

There should be no buying problems with components for either *Neon Novelty* described. One point to watch is that the neons are the correct type—the voltage is the important point—and that the glass is not cracked or chipped.

Specific types of capacitor have been given in the components list simply because these types are relatively small in size and should fit easily on the board or the connection block. Any type of capacitor could be used provided its working voltage is greater than 100V.

This is one project where 20 per cent tolerance resistors are as good as—if not better than—the close tolerance types, so almost any high value (over about 6.8 megohm) carbon types will do.

Enlarger Exposure Meter

A project that should be popular with amateur photographers who do their own enlarging, the *Enlarger Exposure Meter* is a neat unit that should present few construction or buying problems.

The meter is the most expensive item and can be replaced by a multimeter if available. Alternatively buy a large type meter preferably 0-100μA with a scale marked 0-100 in single unit divi-

sions. The larger the scale length the better the accuracy but it is hardly worth getting a meter larger than 3½ or 4 inches across.

Other parts used in the exposure meter should be readily available.


New Products

What is claimed to be the "world's first cordless soldering iron" is now available in this country through Pact International Electronics Ltd., PO Box 19, Royston, Herts, SG8 5HH. The iron, which is made in the USA is automatically recharged from its stand when not in use. Once the iron is charged it can be used anywhere and heats up in 3 to 5 seconds at the touch of a button. The iron has a working light near the bit, which is said to be of the "indestructible iron plated type."

The iron costs £9.25 complete with stand and two bits.



Bib have introduced a Groov-Kleen for record changers, as opposed to single play decks. The "Changer Groov-Kleen Model 45" fits on the cartridge shell of the tracking arm and rests on the record near the stylus—see photo. The cleaner costs 98p plus purchase tax and will fit most pick-up arms by means of an adhesive black carrier plate, adaptors are provided for fixing to some cartridge carriers. Adjustment of the pick-up arm pressure can compensate for the additional weight on the stylus.

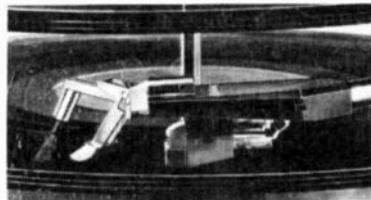

THIS article is of special interest to the photographer who does his own enlarging. It describes a light meter to determine the exposure required for satisfactory enlargements without the time consuming, and paper devouring, ritual of test strips. In practice the meter has been adequate for most normal work and variations required to optimise an enlargement have rarely fallen outside a 10 per cent change of the indicated exposure.

Owners of multimeters can use their meters on a low current range with the exposure meter circuit and hence save the cost of the most expensive component—the meter movement. Easy to make and operate, this is a project requiring very little technical knowledge, so is ideal for the home constructor.

BASIC BRIDGE

Consider a voltage V_a applied to two arms of a bridge, (Fig. 1), the left arm of R_a and R_3 , the right arm of $VR1$ and R_5 . In the left arm V_a will vary according to the values of R_a and R_3 , whilst in the right arm V_b will vary according to the values of $VR1$ and R_5 .

Each arm can be regarded as independent of the other for most practical purposes, and if V_a is equal to V_b , no current will flow in the meter and the bridge is said to be balanced. If, however, the resistance of R_a rises, the potential V_a falls and current flows from V_b to V_a .

If the current through the meter is very much smaller than the current in $VR1$ and R_5 , V_b will

remain virtually constant. Resistor R_4 is connected in series with the meter so that the full scale deflection (f.s.d.) current is not exceeded to such an extent that the meter is damaged.

The bridge equation is usually stated by saying that the bridge is balanced when $R_a \times R_5 = R_3 \times VR1$ but the action of the circuit is not so easy to see from this approach.

FULL CIRCUIT

Let us now consider the full circuit (Fig. 2). The right arm is $VR1$ and R_5 as before, with V_b set by the wiper of a subminiature potentiometer, and kept constant. Resistor R_3 is in the same position as before but R_a is now a field effect transistor (f.e.t.) with V_a appearing on its source.

As in the basic circuit when V_a is equal to V_b , the bridge is balanced and no current flows, but if V_a falls the current is passed through the meter from V_b to V_a .

LIGHT CELL

The light cell is a sensitive photoconductive cell (PCC1). In the dark its resistance rises to nearly 10 megohms falling to only a few hundred ohms in bright light. Under the enlarger it operates between about 1 megohm for a dense negative down to 100 kilohms for maximum meter deflection with a "thin" negative.

These values were determined with a wide variety of negatives, enlargements and stop values and although values outside this range

enlarger exposure meter

A light meter to determine the exposure required for satisfactory enlargements

By J. M. Bartlett


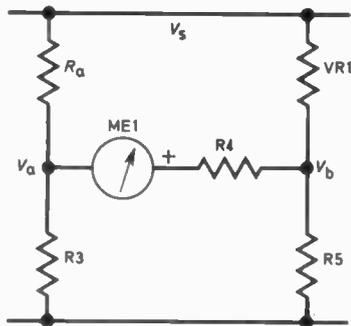


Fig. 1. Basic bridge circuit configuration.

Fig. 2. Circuit diagram of the Enlarger exposure meter.

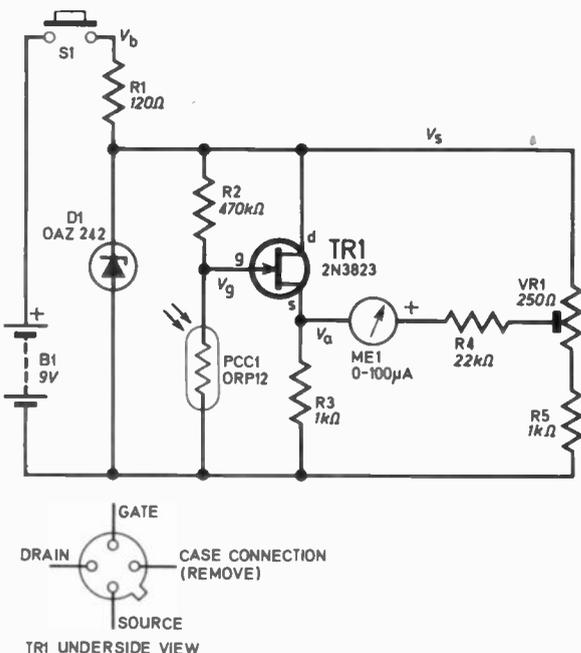

could be obtained they could be brought back into this working range by varying the stop position on the enlarger.

Incidentally these correspond to light values on the enlarger baseboard of 0.06 lux for a dense negative up to 0.8 lux for a thinner one. This is of purely academic interest but may be worth noting considering the difficulties involved in making such measurements.

In view of the high resistance involved the current passed through R2 and PCC1 is in the order of a few microamps, hence a field effect transistor (*n* channel) must be used as a voltage follower. As V_g falls so does V_a but the gate of the f.e.t. (at V_g) presents an input impedance of many megohms and can therefore be ignored; V_g therefore varies with the incident light and V_a follows this change.



In total darkness V_a is approximately 4.9 volts at which point VR1 is adjusted to give zero deflection on the meter. Under the enlarger the resistance of PCC1 falls, V_g falls, and V_a falls, following the change in voltage. V_a falls about 2.2 volts at the chosen light intensity so at this level of illumination we get $\frac{2.2V}{22k\Omega} = 100\mu A$. i.e. full scale deflection.

STABILIZER

To nullify the effects of battery ageing, a Zener diode together with R1 is used to derive a semistable voltage V_s , nominally 5.6V. For a variation in battery voltage of 6.5V to 9V the meter varies only one division at full scale. This does not affect the calibrated exposure to any significant degree.

A push button should be used to switch the circuit on so that the battery is only loaded when a reading is actually being taken.

MECHANICAL CONSTRUCTION

The diagrams and photographs are virtually self explanatory. Commence construction by cutting the board to size and cleaning up the edges with a file. There are no breaks in the copper strips of the board so the next step is to insert and solder up all the components as shown in Fig. 3. Connect the f.e.t. and l.d.r. after the other components and use a heat shunt to protect these components whilst soldering the leads.

The complete circuit except for the meter is mounted in a tin which formerly held Strepsil throat sweets. A one ounce tobacco tin is about the same size, or a die cast box could be bought, but it is not necessary to spend money on a fancy box.

Adhesive foam similar to draught excluding foam used on doors and windows holds the board firmly and a folded tissue on the bottom of the tin prevents the soldered joints from shorting on the tin. The meter leads are fed out through a small grommet.

A one inch diameter hole is cut in the case lid and a piece of diffusing material glued to the underside. It is worth mentioning that a small plywood box has some advantages:—

- (a) The soldered joints cannot be shorted.
- (b) Most handy-men can bore a one inch hole

enlarger exposure meter


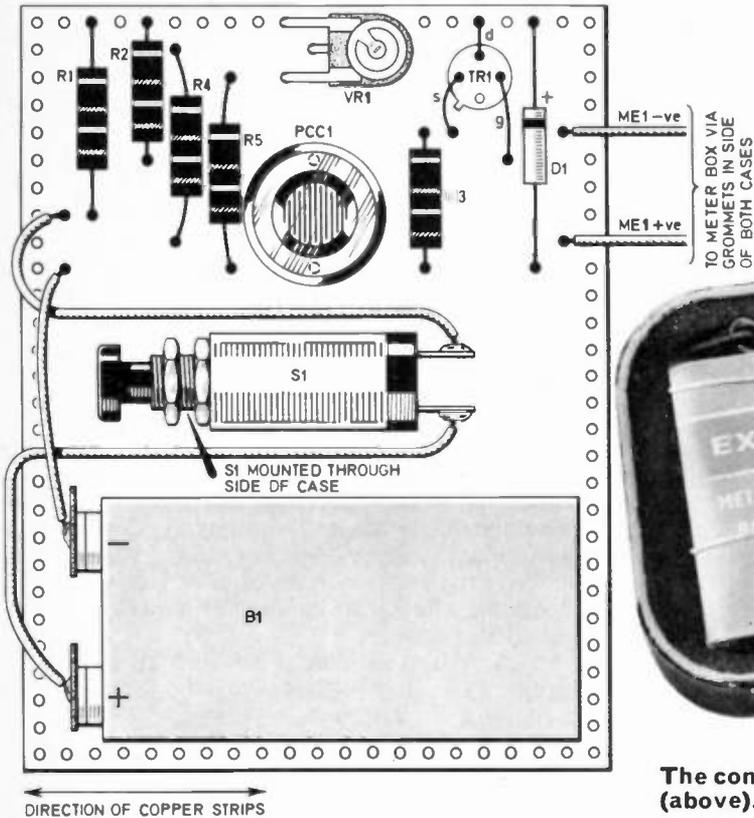


Fig. 3. Layout and wiring of the components mounted on the Veroboard. There are no breaks in the copper strips on the underside.

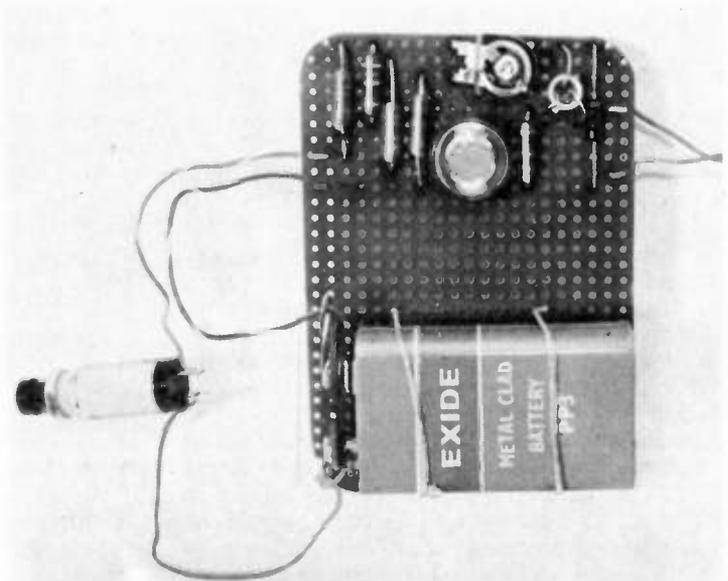

The completed sensor box with lid removed (above).

The Veroboard complete with all components. Note the mounting of TR1—upside down for easy lead connection. Also note the rounded corners of the board to enable it to fit inside the tin used for the case.



in wood whereas a "Q-max" cutter may not be available to cut the metal case.

(c) The case could be made the exact size to accommodate the Veroboard.

There is a choice of diffusing materials. Tracing paper is adequate but prone to damage. A stronger plastic tracing film could be used but Perspex is more durable and is the best choice. Clear Perspex can be diffused by lightly rubbing it with fine emery cloth.

An alternative is to use a clear window and



diffuse the projected image nearer to the enlarger lens. In this case a general reading is obtained of the whole negative.

The meter can be mounted in any suitable metal, plastic or wood case and connected to

the circuitry by a piece of twin core wiring flex—be sure to observe the correct polarity.

To finish the units they can both be painted matt black.

CALIBRATING THE METER

A calibration curve must be produced and this requires a few test strips to be made. The sensor is placed on the base board over the area of particular interest. The push button is operated and the deflection noted. A conventional test strip is made and the best exposure corresponding to that deflection is noted.

The enlarger stop is altered to give a new meter deflection and the best test strip exposure for this deflection is similarly recorded. This is repeated until 6 or 8 meter readings between, say, 10 and 100 with the corresponding exposures have been obtained. The deflection/time graph can be drawn and this is kept as the calibration curve. An example is shown in Fig. 4. Obviously there will be occasions when a difference in exposure is desirable to bring out special effects of shadows etc., but from past experience this has been found to be not more than ± 10 per cent of the indicated value.

VARIATIONS

Since we are dealing with a $100\mu\text{A}$ meter in this article, R_4 was chosen as 22 kilohms. Table 1 shows how R_4 varies with the meter used.

It is preferable to use the highest sensitivity meter but more important, it should be as large as possible. The meter must be read with the safe light off, using only the fringe lighting

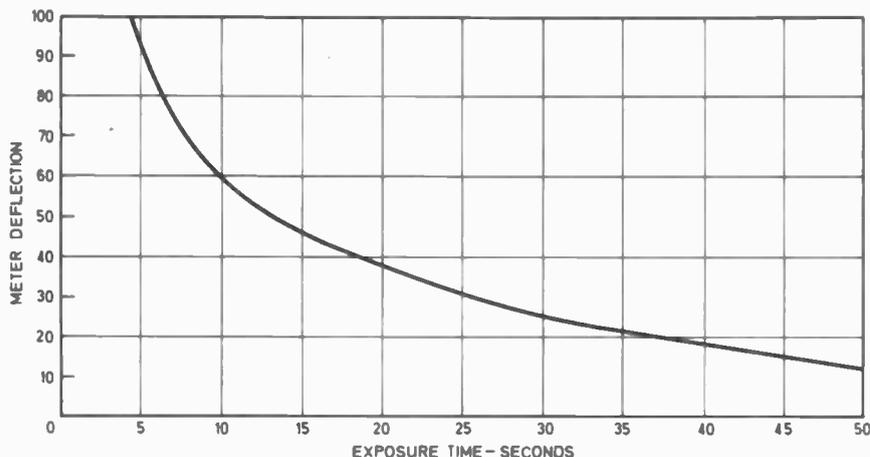


Fig. 4. Calibration curve for the prototype unit. A curve like this must be made for the meter.

Table 1: Resistance value for various meters


Meter f.s.d. (μA)	R_4 (calculated) ($\text{K}\Omega$)	Nearest preferred value ($\text{K}\Omega$)
50	44	47
100	22	22
150	14.6	15
200	11	12
250	9	10
500	4.5	4.7

from the enlarger, and since a calibration chart is used, meter sensitivity and linearity is less important.

If the meter reads very high all the time, it could be that a particularly bright lamp is fitted to the enlarger or consistently thin negatives are used. This is of no consequence since the sensor can be made less sensitive by increasing R4 from the original value. In this way the illumination has to be brighter to give a full scale reading.

Other variations include having the sensor (PCC1) on flying leads and fitting the bridge, battery and meter into one box. As a home project the exposure meter has several possibilities for the constructor to modify to his own requirements or to make as shown. □

The prototype unit.

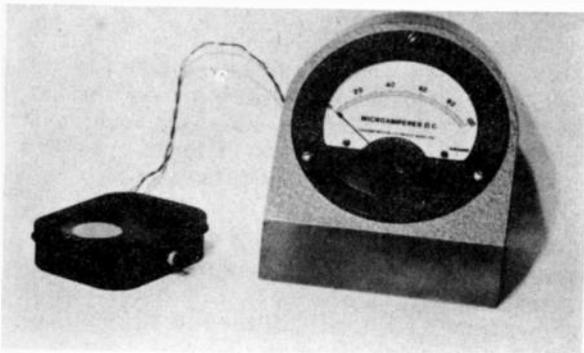

Components....

Resistors

R1	120 Ω
R2	470k Ω
R3	1k Ω
R4	22k Ω
R5	1k Ω

All $\frac{1}{2}$ W \pm 10% carbon

SEE
**SHOP
TALK**

Potentiometer

VR1 250 Ω subminiature skeleton preset

Semiconductors

PCC1 ORP12 light dependent resistor
D1 5.6V 400mW Zener diode
TR1 2N3823 n channel f.e.t.

Miscellaneous

S1 Single pole push to make pushbutton
B1 PP3 9V battery
ME1 0-100 μ A moving coil meter (or alternative—see text)

Veroboard 2.2 x 2.9 x 0.1 inch matrix, battery connectors, grommets, connecting wire, tracing paper or perspex for diffusing material, two cases (see text)

Continued from page 142

Since the unit can be expected to work for more than two or three years (possibly much longer) the box can be sealed up, but a small hole **must** be left as mentioned above; also the battery **must not** be a tight fit as it is likely to expand with old age.

ALTERNATIVE DISPLAY

An interesting alternative to the two projects described could be made for use with larger type toy animals. For this a six or eight neon configuration is used with the leads to the neons extended so that four neons form each eye providing a flickering effect in the eyes. □

Components....

Resistor

R1 10 M Ω
 $\frac{1}{2}$ W \pm 20% carbon (see text)

Capacitor

C1 0.22 μ F 100V or more working (polyester or polystyrene)

Neon


LP1 70 to 90V wire ended neon

Repeat all the above components for each flashing neon required.

Miscellaneous

B1 90V battery (type B126 or similar)
Veroboard (for 8 neon unit 2 $\frac{1}{2}$ x 3 $\frac{1}{2}$ x 0.15 inch matrix).
Six way connector (for two neon unit), connecting wire, two way or three way plug to suit battery. Materials for case and model animal—if used—see text.

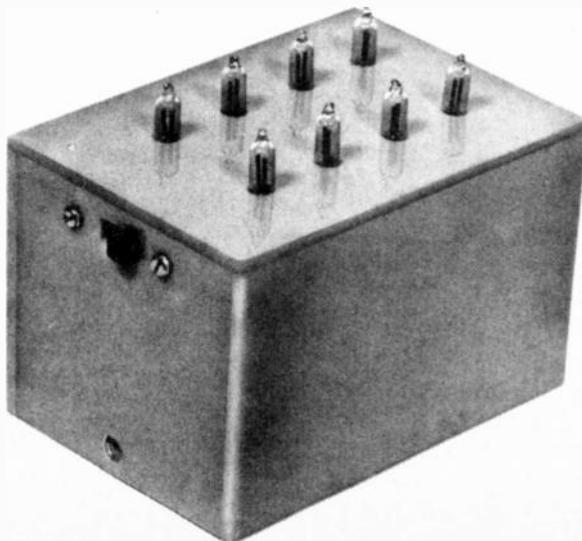Photograph of the completed "flashing block", incorporating two types of switched display.



The team behind the great technological breakthrough *left to right* John Bardeen, William Shockley and Walter Brattain.

The First Transistor



THE whole of electronics depends upon the amplification of electric current. The principal device employed for this function was originally the valve. During the last 15 years or so the transistor has taken over this role. The transistor, a solid state amplifying device, was invented *twenty-five years ago*.

There are interesting similarities in the histories of the valve and the transistor. The thermionic valve first appeared on the scene as a rectifier. It had two electrodes: a filament (cathode) and an anode, and it was known as a diode.

The usefulness of the valve was greatly increased when a third electrode called the grid was added around 1906. The result was a device capable of amplifying voltages and currents. It was called a triode.

ANCESTORS OF THE TRANSISTOR

The transistor has as its ancestors certain devices called solid state rectifiers. These have appeared in two different forms: (1) the crystal (point-contact) rectifier, first used as a detector of radio frequencies before the invention of the valve, (2) the plate or contact metal rectifier, used for producing direct current from alternating current supplies, which first appeared in practical forms around 1920.


Ever since the American Lee de Forest fitted the grid into Fleming's original diode, scientists have wished to emulate this in the field of solid state, that is with semiconductor materials.

Many attempts to make a solid state version of the amplifying valve must have been made during the last 50 years or so, but without success. This was mainly because the manner in which crystal and metal rectifiers functioned had not been clearly established. The world had to wait until 1947 for this wonder that was destined to revolutionise electronics and very soon the way of life for all.

THE BREAKTHROUGH

On December 24, 1947, two members of a research team at Bell Telephone Laboratories Inc., New Jersey, U.S., achieved the breakthrough. In the course of experiments with semiconductor crystals, John Bardeen and Walter Brattain placed two contacts onto a piece of germanium crystal, the contacts were close but separated from each other. With a third common contact made to the crystal, two separate external circuits were thus formed.

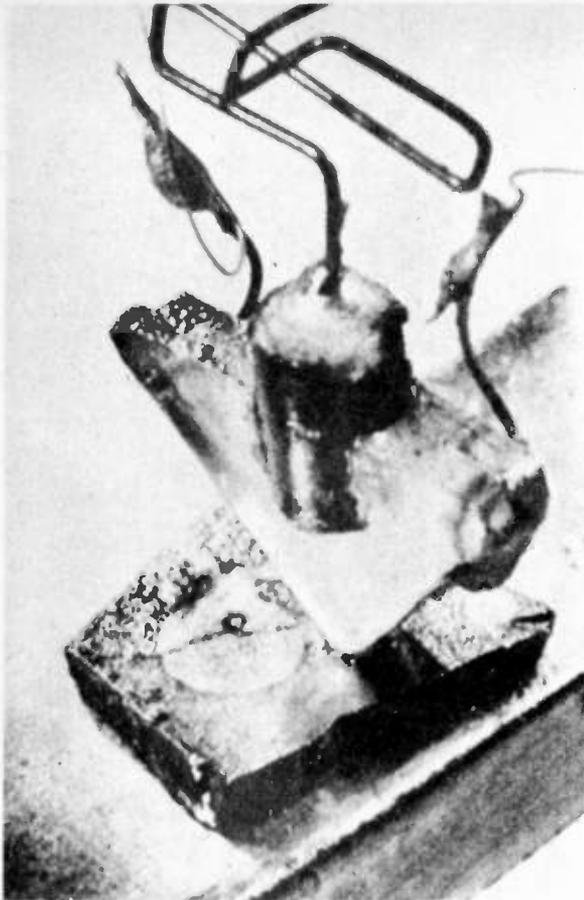A microphone was coupled to one circuit and it was found that an amplified version of speech current was produced in the second circuit. The crystal device had obviously introduced current



Photograph of the first original semiconductor amplifying device—the transistor.

gain, see Fig. 1. The name transistor was coined from the "transfer resistance" characteristic demonstrated by this device.

The full theory to account for the operation of this "point-contact transistor" was not worked out for some little time afterwards. It was during this theoretical investigation that the principle

INTERACTION BETWEEN TRANSISTOR ELECTRODES

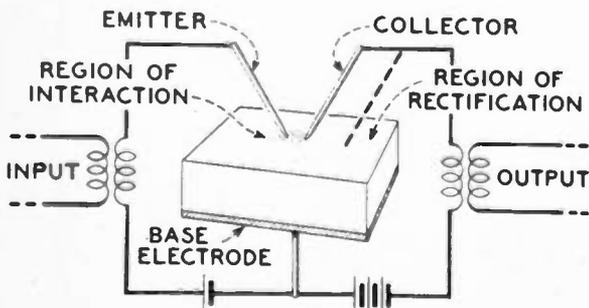


Fig. 1. The basis of the first transistor.

of the *junction* transistor was discovered by William Shockley, who was the leader of the team responsible for the initial transistor discovery.

As is well known, the junction type transistor soon proved to be superior to the point-contact transistor, and within a few years had entirely superseded the latter as a practical device suitable for large scale production. Undoubtedly though, the point-contact transistor provided the dramatic initial breakthrough and inspired subsequent research in this field. Thus it seems right and fair that honours should be shared equally between Bardeen, Brattain and Shockley. Indeed this is what the scientific world thought, because this trio were jointly awarded the Nobel prize in physics for 1956.

The junction transistor consists of a three-layer sandwich of *n* type and *p* type semiconductor material. There are thus two junctions. Alternative arrangements are possible, as indicated in Fig. 2.

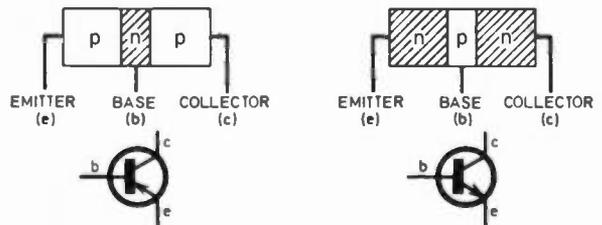


Fig. 2. Alternative arrangements of the junction transistor.

MANY VARIETIES

The ascendancy of the junction transistor was followed by a whole train of exciting and important technical developments. Silicon was introduced around 1960. By the 1960's, this semiconductor material had taken over almost entirely from germanium, the material originally used.

The bipolar junction transistor relies upon the injection of minority current carries (holes and electrons) across the base from one junction to the other. This theory has been applied extensively and a large number of different types of transistor have been developed since the first transistor made its appearance.

A wide range of bipolar *pnp* and *npn* devices specially designed for a.f., r.f. and high power operation have become available. Also switching devices such as the four layer *pnpn* silicon controlled rectifier or thyristor, capable of handling powers from a few milliamperes to hundreds of amperes, and at voltages ranging upwards to 1,000 or more. These four layer devices were invented by Shockley in the early 1950's.

A different principle is involved in the field effect transistor (*f.e.t.*)—also invented by Shockley in the early 1950's. This is a unipolar device—so called because majority carries alone are

introducing

ARROW ELECTRONICS LTD.

an associate Company of LST ELECTRONIC COMPONENTS LTD.

'Service the way it ought to be'

When it comes to retail distribution we stand and shoulders above the rest!

We're a new Company but our experience and ability in electronic components goes back a long way.

Here at Arrow Electronics fast, reliable service is vital.

We offer a rapid same-day turn round on all mail received up to 3 pm on any given weekday.

What's more, when we promise to clear all orders on receipt, we really mean it!

Our on-line, no bother ordering system is a joy to behold. We'll give you all the forms and literature you could possibly need. Combining them with our simple Catalogue Coding and key prints, you can order and order time and time again without the slightest error or mistake.

You'll always be up-to-date with us—we're continually adding to our high quality stock range and we're always updating our catalogue.

Get to know us and you'll soon raise your hat to our customer discount—it's tops with a total value discount of 10% on orders exceeding £4.00.

Now's your chance to get to know us better. Our brand new Catalogue is now awaiting you, hot from the presses.

NEW PRODUCTS

Products featured in the Arrow Electronics Mail Order Catalogue include the following:

- Extended ranges of Bridge Rectifiers and Capacitors including Variable Capacitors
- Low cost Integrated Circuit Mounting Film
- Mounting Knobs
- Light Emitting Diodes
- Motor car Beaters
- Optically Coupled Isolators
- Extended Range of Photoresistors
- Medium current and High current Rectifiers
- Temperature controlled Soldering Irons
- Extended Range of Thyristors
- Many new types of Passive Components
- Hot wire and Accessories including tools
- Chassis
- Mounting Boxes
- An extended range of Data Electronics
- and...
- A very wide range of new Semiconductors, resistors

and many other items of great interest to the home constructor.

NEW PRODUCT

The unique **Logic Checker** illustrated gives an instantly visible display of the Logic State of DTL Integrated circuits. The device automatically selects its power supply from the terminals of the IC's being inspected. The Logic Checker is supplied complete with a set of clip-on Logic plates. For other details see the new Arrow Catalogue.



NEW PRODUCT

Arrow are the first to offer the new double wound ring core chokes designed for HF impedance application in Bi-Polar TCR and TRIAC circuits. The chokes are packed as kits including a Delta Capacitor. For details see the new catalogue.



Shoot the
your
catalogue

Arrow Electronics Limited
Dept. EE 5
7 Capella Road
Barnet, Ed Essex
Tel: Barnetwood 215435

Name _____
Address _____
Postcode _____
Telephone No. (Area Code) _____
Arrow Electronics Limited
Dept. EE 5
7 Capella Road
Barnetwood, Essex

BI-PRE-PAK

COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH



TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 25p

POST & PACKING 15p

TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V. 0.5 to 2mA.	50p
B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short Lead Transistors, NPN Silicon Planar types.	50p
H39	10	Integrated Circuits: 6 Gates BMC 962, 4 Flip Flops BMC 945	50p
H40	20	BFY502, 2N696, 2N1613 NPN Silicon uncodded TO-5	50p

UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. 1N914 and 1N916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OVER 1,000,000 TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000

Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.

Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9 etc.

R.F. NPN and switching NPN.

Please state type of transistor required when ordering.

ALL AT 500 for £3, 1,000 for £5, 10,000 for £40 P & P 10p/1000

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.

TYPE "B" PNP Silicon, plastic encapsulation.

TYPE "E" PNP Germanium AF or RF.

TYPE "F" NPN Silicon plastic encapsulation.

TYPE "G" NPN silicon similar ZTX 300 range

TYPE "H" PNP silicon similar ZTX 500 range

POWER TRANSISTOR PRICE BREAKTHROUGH!

Plastic cased Silicon Power Transistors of latest design. 40watts and 90watts. PNP & NPN types. All types available at the most shatteringly low prices of all time. All are fully tested, marked and guaranteed!

1-12 13-25 26-50

40W NPN 20p 18p 16p

40W PNP 21p 19p 17p

90W NPN 24p 22p 20p

90W PNP 25p 23p 21p

PAK MP40

40W + 40W 50p 48p 46p

MP90

90W + 90W 40p 38p 36p



A CROSS HATCH GENERATOR FOR £3.50!!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

8 RELAYS FOR VARIOUS TYPES £1 P & P 25p

INTEGRATED CIRCUITS

Clocked Flip Flop	BMC931	20p	18p	16p
Ex. 2/4-input Buffer	BMC932	12p	11p	10p
2/4-input Expander	BMC933	12p	11p	10p
Hex. Inverter	BMC934	12p	11p	10p
Hex. Inverter	BMC935	12p	11p	10p
Hex. Inverter	BMC936	12p	11p	10p
Hex. Inverter	BMC937	12p	11p	10p
Hex. Inverter	BMC940	12p	11p	10p
Hex. Inverter	BMC941	12p	11p	10p
Type D Flip Flop	BMC942	20p	18p	16p
Ex. 2/4-input Power	BMC944	12p	11p	10p
Clocked Flip Flop	BMC945	20p	18p	16p
4/2 Input NAND Gate	BMC946	11p	10p	9p
Clocked Flip Flop	BMC948	20p	18p	16p
4/2 Input NAND Gate	BMC949	12p	11p	10p
Pulsed Trig. Binary	BMC950	20p	18p	16p
Monostable Multivib.	BMC951	25p	23p	21p
Dual J/K Flip Flop	BMC953	20p	18p	16p
Dual J/K Flip Flop	BMC955	20p	18p	16p
Dual J/K Flip Flop	BMC956	20p	18p	16p
Quad. 2-input Power	BMC958	12p	11p	10p
2/4-input Gate	BMC961	12p	11p	10p
3/3-input NAND Gate	BMC962	11p	10p	9p
3/3-input NAND Gate	BMC963	12p	11p	10p
Audio Amp. 3w. SL403D	£1.50	£1.40	£1.34	
Linear Op. Amp 709C	25p	20p	15p	
Decade Counter SN7490	45p	40p	35p	

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile
16 pin type at 16p each. J type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I Transistor Equivalents and Substitutes: 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.

The Iffla Radio Valve & Transistor Data Book 9th Edition: 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Postage and Packing 21p.

Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

Co. Regn. No. 820919
MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 10p post and packing per order.
OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD DEPT. E, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF
TELEPHONE: SOUTHEND (0702) 46344

involved in the mechanism by which these particular devices function.

The junction unipolar transistor (j.f.e.t.) was followed by the insulated gate field effect transistor also known as the metal-oxide semiconductor transistor (m.o.s.t.) on account of its form of construction.

The m.o.s.t. technique has been adopted for integrated circuit manufacture.

One type of bipolar transistor is, in fact, more correctly described as a double-base diode. This is the unijunction transistor (u.j.t.) it is essentially a switching device.

A wide variety of diodes based on the pn junction have been developed. They have use as signal and power rectifiers, as voltage regulators, as variable resistors (varistors) or capacitors (varactors); and as microwave oscillators.

OPTOELECTRONIC DEVICES

Both the single and the multiple pn junction have been widely applied in the field of optical radiation.

Devices which detect light are the photodiode and the photo transistor. Diode devices with large contact areas exploit the photovoltaic effect to produce electrical energy are commonly available as photocells or solar cells (or "batteries"—when used in groups).

Other pn junction devices convert electrical energy into light. Electroluminescent diodes consisting of a junction of p and n type gallium arsenide and gallium phosphide are becoming increasingly popular as red and green light emitters. This area of the technology is expanding dramatically with the demand for small direct readout systems.

INFRA-RED DEVICES

Much of the future development of semiconductor technology seems to lie in the field of infra-red. Exciting and sophisticated devices are likely to make their appearance in due course. Thus another part of the spectrum will become available for general exploitation through applied electronics. □

PLEASE
TAKE NOTE

Radio Control Receiver (Jan. 73) Fig. 2. A break should be made in the copper-strip at position J1. Transformer suppliers—see Shop Talk (page 143).

NEXT MONTH



INDICATOR AUDIBLE WARNING

Add this audible warning device to car indicators or dash-panel warning lights, e.g. oil pressure, engine temperature, etc., and your attention will be instantly drawn to the warning lamp.



CHILD'S BEDSIDE LAMP

A simple control to switch a lamp from full to half power.

GENERAL PURPOSE AMPLIFIER

A mono, audio amplifier of reasonable quality for use with radio tuners, audio oscillators, record decks or for electric guitar practise, etc.



These constructional projects and all the regular features in the April issue, on sale Friday, March 16.

DEMO CIRCUITS

By **MIKE HUGHES**

The Grounded Base Amplifier

THE experiment to be described demonstrates two points; first how to get maximum voltage amplification out of a transistor and secondly that a loudspeaker can act as a microphone—given the right set of circumstances.

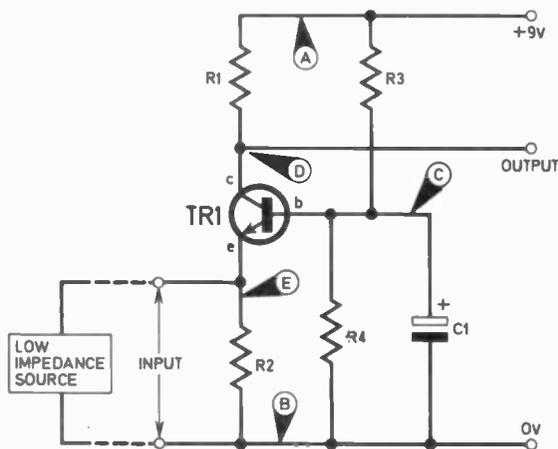


Fig. 4.1. Basic circuit of a grounded base stage.

BASIS OF OPERATION

At first sight the basic circuit for a grounded base stage (shown in Fig. 4.1) looks rather like a grounded emitter; but look closer. There is a large capacitor connected between the base of TR1 and the ground rail—this, in conjunction with the two resistors R3 and R4, keeps the base at a fixed potential with respect to the earth rail. This means that there is a fixed current flowing between base and emitter, controlled by the potential divide effect of R3 with R4 and the value of R2. Thus the collector current can flow through R1, the transistor and R2; by suitable selection of values for the components we can set the quiescent output voltage (output voltage with no input signal) at the collector of the transistor.

Provided C1 shows very low reactance to any alternating currents that may be superimposed on the d.c. levels in the circuit, the potentials at A, B and C are precisely defined and stable.

To work as an amplifier a signal that will cause current variations and generate variations in voltage at the collector must be injected. This is done by modulating the emitter current—applying the signal across R2.

The input is therefore between emitter and ground, and the output is between collector and ground; as the potential at the base is precisely defined as a d.c. level, the stage is termed a grounded base configuration. Some books and theoretical articles show the circuit a different way round using separate power supplies (these are necessary to ensure that the base is always positive with respect to the emitter). In practice only one power supply is normally available and this is why we have chosen to describe the circuit in the form shown in Fig. 4.1—this is the way you are most likely to come across it in constructional articles.

CIRCUIT DESIGN

Emitter current is approximately the same as collector current (actually it is equal to collector current plus base current but as the latter is comparatively small it can be ignored at this stage). In order to modulate the emitter current with a low voltage signal, the signal must come from a source of reasonably low resistance (impedance) because emitter current can be quite high (in this case consider it to be about 0.2mA).



To get maximum voltage amplification at the collector the emitter current must be used to generate a collector current that will give the largest voltage variations across a collector load resistor. To get maximum voltage swings across the load resistor for a given current variation the load resistance must be high.

Thus the grounded base stage must be driven from a low impedance source and the output impedance of the stage is usually quite high. To a first order approximation the voltage amplification is set by the ratio of collector load resistance to source impedance. If a 35 ohm loudspeaker is used as a microphone, the output is only in the order of one or two millivolts, for speech very close to the cone. Thus to be able

look! electronics really mastered

... practical
... visual
... exciting!

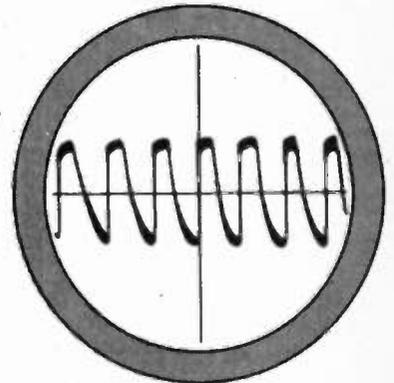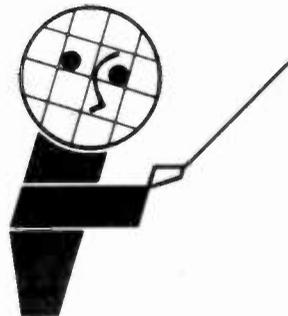no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

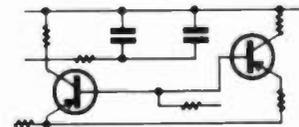2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EEL 33

special free gift also to all our students

HENRY'S - Your complete Semi-Conductor Store!

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. **BRANDED FROM TEXAS I.T.T. FAIRCHILD**



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
8N7400	0-20	0-18	0-16	8N7450	0-20	0-18	0-16	8N74145	1-50	1-40	1-30
8N7401	0-20	0-18	0-16	8N7451	0-20	0-18	0-16	8N74150	1-50	1-40	1-30
8N7402	0-20	0-18	0-16	8N7453	0-20	0-18	0-16	8N74151	1-10	0-08	0-00
8N7403	0-20	0-18	0-16	8N7454	0-20	0-18	0-16	8N74153	1-35	1-27	1-20
8N7404	0-20	0-18	0-16	8N7460	0-20	0-18	0-16	8N74154	2-00	1-75	1-55
8N7405	0-20	0-18	0-16	8N7470	0-30	0-27	0-25	8N74155	1-55	1-47	1-35
8N7406	0-30	0-27	0-25	8N7472	0-30	0-27	0-25	8N74156	1-55	1-47	1-35
8N7407	0-30	0-27	0-25	8N7473	0-40	0-37	0-35	8N74157	1-80	1-70	1-50
8N7408	0-20	0-18	0-16	8N7475	0-40	0-37	0-35	8N74160	2-60	2-40	2-25
8N7409	0-45	0-42	0-35	8N7475	0-55	0-52	0-50	8N74161	2-60	2-40	2-25
8N7410	0-20	0-18	0-16	8N7476	0-45	0-42	0-39	8N74162	3-40	3-25	3-20
8N7411	0-23	0-22	0-20	8N7480	0-80	0-75	0-67	8N74163	3-40	3-25	3-20
8N7412	0-42	0-40	0-35	8N7481	1-25	1-15	1-10	8N74164	2-75	2-30	2-10
8N7413	0-30	0-27	0-25	8N7482	0-87	0-80	0-70	8N74165	4-00	3-60	3-00
8N7416	0-30	0-27	0-25	8N7483	1-00	0-90	0-85	8N74166	4-00	3-60	3-00
8N7417	0-30	0-27	0-25	8N7484	0-80	0-75	0-70	8N74167	6-35	6-00	5-15
8N7418	0-20	0-18	0-16	8N7485	0-45	0-43	0-38	8N74170	4-10	3-55	3-05
8N7422	0-48	0-44	0-40	8N7490	0-75	0-70	0-65	8N74174	2-00	1-75	1-30
8N7423	0-48	0-44	0-40	8N7491AN	1-00	0-95	0-90	8N74175	1-35	1-27	1-15
8N7425	0-48	0-40	0-35	8N7492	0-75	0-70	0-65	8N74176	1-60	1-35	1-20
8N7427	0-42	0-39	0-35	8N7493	0-76	0-70	0-65	8N74177	1-60	1-35	1-20
8N7428	0-50	0-45	0-42	8N7494	0-80	0-75	0-70	8N74180	1-55	1-30	1-20
8N7430	0-20	0-18	0-16	8N7495	0-80	0-75	0-70	8N74181	1-55	1-30	1-20
8N7432	0-45	0-42	0-38	8N7496	1-00	0-97	0-95	8N74182	2-00	1-80	1-40
8N7433	0-70	0-61	0-44	8N7497	6-25	5-50	5-00	8N74184	2-40	2-00	1-80
8N7437	0-65	0-60	0-50	8N74100	2-50	2-30	2-00	8N74185A	2-40	2-00	1-80
8N7438	0-65	0-60	0-50	8N74104	1-45	1-35	1-20	8N74190	1-95	1-85	1-75
8N7440	0-20	0-18	0-16	8N74105	1-45	1-35	1-20	8N74191	1-95	1-85	1-75
8N7441AN	0-75	0-72	0-70	8N74107	0-50	0-45	0-40	8N74192	2-00	1-80	1-80
8N7442	0-75	0-72	0-70	8N74110	0-80	0-70	0-60	8N74193	2-30	2-00	1-10
8N7443	1-00	0-95	0-90	8N74111	1-00	0-95	0-90	8N74194	2-50	2-25	1-90
8N7445	2-00	1-75	1-60	8N74119	1-90	1-78	1-65	8N74195	1-85	1-70	1-60
8N7446	2-00	1-75	1-60	8N74121	0-60	0-55	0-50	8N74196	1-60	1-40	1-30
8N7447	1-75	1-60	1-45	8N74122	1-35	1-25	1-10	8N74197	1-50	1-40	1-30
8N7448	1-75	1-60	1-45	8N74123	2-70	2-55	2-47	8N74198	4-80	3-70	3-35
8N7449	1-75	1-60	1-45	8N74141	1-00	0-95	0-90	8N74199	4-80	3-70	3-35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
 LARGER QUANTITY PRICES PHONE (01) 402 4891
 TEXAS HANDBOOK NO. 2, I.C. 700 PAGES DATA 60p. POST 20p.
 HIGH POWER (SM 74 HCO) Now in stock—send
 LOW POWER (SM 74 LOO) for list No. 36

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA530 10p	BC147 12p	BU105 2.25	OC44 15p	T1843 35p	2N3055 55p
AA542 15p	BC169C 12p	BY100 15p	OC45 15p	V405A 25p	2N3440 75p
AAZ13 10p	BC182 10p	BY126 15p	OC57 15p	ZTX108 12p	2N3442 1.25
AC107 35p	BC214 15p	BY127 15p	OC71 50p	ZTX300 12p	2N3525 75p
AC126 25p	BCY32 75p	BY213 35p	OC72 25p	ZTX301 15p	2N3614 50p
AC127 25p	BCY33 15p	BY214 35p	OC73 25p	ZTX302 15p	2N3615 50p
AC128 25p	BCY39 1.80	GET111 55p	OC81 25p	ZTX341 20p	2N3702 1.00
AC176 25p	BCY42 30p	GET115 65p	OC83 25p	ZTX500 15p	2N3704 1.00
AC187 25p	BCY43 25p	GET880 45p	OC140 55p	ZTX503 17p	2N3705 10p
AC188 25p	BCY55 2.50	LM309K	OC170 25p	2G301 30p	2N3714 1.80
ACY17 30p	BCY70 1.5p	(T03) 1.87	OC171 30p	2N404 20p	2N3771 1.75
ACY29 20p	BCY71 20p	MA7121 25p	OC200 45p	2N527 35p	2N3773 2.00
ACY21 20p	BCY72 15p	MJ260 50p	OC205 75p	2N528 35p	2N3780 2.25
AD140 50p	BCY87 2.90	MJ3370 70p	OC202 80p	2N597 15p	2N3819 35p
AD149 50p	BCZ11 50p	MJE250 75p	OC203 50p	2N706 10p	2N3820 50p
AD161 35p	BD124 80p	MJE2955	OC271 1.25	2N930 20p	2N3866 85p
AD162 35p	BD131 75p	1.10	ORP12 50p	2N987 45p	2N3903 15p
AF117 20p	BD132 80p	MJE3055	ORP60 40p	2N1131 25p	2N3906 12p
AF118 50p	BF115 25p	75p	R346A 20p	2N1132 25p	2N4061 12p
AF124 25p	BF167 25p	MFP105 40p	RA6310AF	2N1302 15p	2N4062 12p
AF139 30p	BF173 25p	NKT214 20p	45p	2N1304 22p	2N4126 15p
AF186 40p	BF180 30p	NKT216 40p	RA5508AF	2N1305 22p	2N4871 35p
AF239 40p	BF194 15p	NKT403 70p	55p	2N1307 25p	2N5457 30p
AFY27 30p	BF195 15p	NKT404 50p	TAA263 75p	2N1308 25p	2N5777 55p
ABY28 25p	BP861 25p	OA5 50p	TIP209 35p	2N1613 20p	2N6011 1.00
BA102 30p	BP868 25p	OA10 35p	TIP28A 50p	2N1671 1.00	2B012 10.00
BA115 7p	BF113 25p	OA11 10p	TIP30A 60p	2N2147 75p	2B018 6.25
BA145 15p	BFX34 75p	OA91 7p	TIP31A 60p	2N2160 50p	2B026 8.95
BAX13 5p	BFX37 30p	OA200 7p	TIP33A 70p	2N2217 25p	2B301 50p
BAX16 7p	BFX88 20p	OA202 10p	TIP33A 70p	2N2221 20p	2B303 65p
BC107 10p	BFY50 20p	OC16 75p	TIP34A 1.00	2N2222A	2B324 95p
BC108 10p	BFY51 20p	OC20 85p	OC16 75p	2N2369A 25p	40250 50p
BC109 10p	BFY52 20p	OC23 85p	TIP35A 1.50	2N2906 15p	40361 40p
BC109C 12p	BFY59 20p	OC25 40p	TIP36A 3.00	2N2926 (all	40362 40p
BC113 15p	BFY36 8.00	OC35 60p	TIP41A 75p	cols) 10p	40408 75p
BC117 20p	BSX20 15p	OC36 65p	TIP42A 85p	2N3053 20p	40636 1.10
BC143 35p	BSY27 15p	OC42 40p		2N3054 50p	40430 1.00

INTEGRATED CIRCUIT SOCKETS
 LOW PROFILE PLATED PINS

(16 Lead D.I.L.) 17p
 (14 Lead D.I.L.) 15p
 (8 Lead D.I.L.) 15p

QUANTITY DISCOUNTS

20% 12+ ; 15% 25+ ; ANY ONE TYPE
 10% 100+ ; 25% 250+

From above sections except Integrated Circuits and Special Offers where discounts are included.
 Minimum order value \$1 please.
 Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90 59p	2N2926 10p
1000 MC/S	All Colours
25 + 20p	25 + 9p
100 + 17p	100 + 8p
500 + 15p	500 + 6p
	1000 + 5p
AF117 Mullard 25p	2N3819 Texas 35p
25 + 17p	25 + 30p
100 + 15p	100 + 25p
500 + 12p	500 + 20p
	1000 + 15p
OC170 Mullard 25p	BC107, BC108, BC109 10p each
25 + 20p	All Makes
100 + 18p	25 + 8p
500 + 15p	100 + 7p
1000 + 13p	500 + 6p
	1000 + 5p
BY127 Mullard 15p	ADI61, ADI62 35p each
25 + 12p	25 + 32p
100 + 10p	100 + 28p
500 + 9p	500 + 25p
1000 + 8p	1000 + 22p
OA202 10p	2N3053 20p
25 + 8p	25 + 18p
100 + 7p	100 + 15p
500 + 6p	500 + 12p
1000 + 5p	1000 + 10p
OC35 Mullard 50p	2N3055 55p
25 + 45p	25 + 50p
100 + 40p	100 + 45p
500 + 35p	500 + 38p
1000 + 30p	1000 + 33p

PLESSEY INTEGRATED CIRCUIT
 3 Watt Amplifier SL403D
 Complete with 8-page booklet, circuits and data

£1.50 each

TRIACS
STUD WITH ACCESSORIES

Type	Volts	Price
P.I.V. 1-11		
3 AMP RANGE		
8C35A	100	75p
8C35B	200	79p
8C35D	400	80p
6 AMP RANGE (T048)		
8C40A	100	85p
8C40B	200	90p
8C40D	400	£1.00
8C40E	500	£1.20
10 AMP RANGE (T048)		
8C45A	100	95p
8C45B	200	£1.00
8C45D	400	£1.25
8C45E	500	£1.45
15 AMP RANGE (T048)		
8C50A	100	£1.25
8C50B	200	£1.35
8C50D	400	£1.65
8C50E	500	£1.85
DIAC D32	25p	

TRIACS—Additional Types

40430	(T068)	85p
40689	(Plastic)	£1.00
		£1.00
40486	(T05)	80p

3 Amp T048
15 Amp T048

NEW BRIDGE RECTIFIERS

SMALL SIZE AND LOW COST

Type	Volts	Price
P.I.V. 1-11		
HALF AMP		
BO5/05	50	20p
BO5/10	100	25p
ONE AMP \times I H TUBULAR		
B1/05	50	25p
B1/10	100	25p
B1/20	200	30p
B1/60	600	35p
ONE AMP (G.I.) TUBULAR		
WO05	50	30p
WO1	100	35p
WO2	200	40p
WO6	600	45p
TWO AMPS \times I H \times L TUBULAR		
B2/05	50	35p
B2/100	100	

to measure the output a high degree of voltage amplification must be introduced. By making R1 22 kilohm the simple rule for amplification gives a factor:

$$\begin{aligned} \text{Voltage amplification} &= (\text{approx}) \frac{Z_{out}}{Z_{in}} \\ &= \frac{22,000}{35} \\ &= 630 \end{aligned}$$

Therefore if the circuit works the output voltage should swing by a volt or so resulting from the millivolt or two produced by the "microphone".

COMPONENT SELECTION

If R1 is to be 22 kilohm, the quiescent collector current (to give a mid-rail output of 4.5V) will be

$$\frac{4.5}{22} \text{ mA,}$$

approximately 0.2mA. The quiescent potential at the emitter (point E) must be sufficiently positive so that the alternating voltage from the microphone does not drive it to zero. If we make the potential at point E, 0.2V, assuming the emitter current is approximately the same as collector current, R2 will be

$$\frac{0.2}{0.2} \text{ kilohm}$$

(1 kilohm).

Because a silicon transistor is being used, the potential at the base (point C) must be 0.6V more positive than the emitter. Assuming h_{FE} for the transistor to be 200, the base current required to set the quiescent levels chosen must be

$$\frac{I_c}{h_{FE}} = \frac{0.2}{200} \text{ mA} = 0.001 \text{ mA.}$$

If (say) 81 times I_b flows through R3, and 80 times I_b flows through R4 (this is much more standing current through the resistor chain than

is normally required for common emitter configuration but a high input impedance is not required. A high standing current through R3 and R4 also leads to improved stability and helps maintain the potential at C with very little variation when signal is applied); resistor R3 is therefore

$$\frac{9.0.8}{81 \times 0.001} \text{ kilohm} = \frac{8.2}{0.081} = \text{approx } 100 \text{ kilohm;}$$

$$R4 \text{ is } \frac{0.8}{80 \times 0.001} \text{ kilohm} = \frac{0.8}{0.08} = 10 \text{ kilohm.}$$

It is now obvious why the factors 81 and 80 were chosen. Capacitor C1 must present a low impedance to the lowest frequencies therefore 50μF will be suitable.

If the loudspeaker (microphone) is connected directly across emitter to ground, its low resistance will modify all the calculations, as it is only the a.c. signal from the coil that is used it can be capacitively coupled to the emitter by C2 (this will not affect our d.c. calculations). Again this capacitor must be of low impedance to the lowest frequencies so again 50μF can be used.

MONITORING CIRCUIT

Because of the high output impedance of the grounded base stage it is difficult to make a simple monitoring circuit that does not in one way or another affect the voltage amplification; however the simple expedient of TR2 in Fig. 4.2 works reasonably well.

Potentiometer VR2 (5 kilohm) should be adjusted so that TR2 is only just conducting (i.e. the meter is just starting to move above zero). Make this adjustment very slowly because the coupling capacitor C3 slows the reaction. Any positive going a.c. signals at the collector of TR1 will be coupled to the base of TR2 and drive it further into conduction showing a useful output on the meter.

Negative going excursions will switch the transistor off and then be shunted to ground

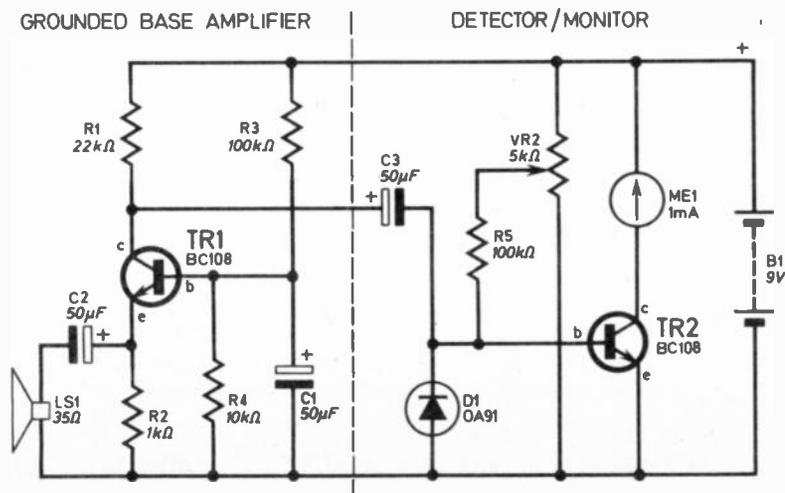


Fig. 4.2. "Working" circuit for the grounded base stage together with a simple monitoring stage.


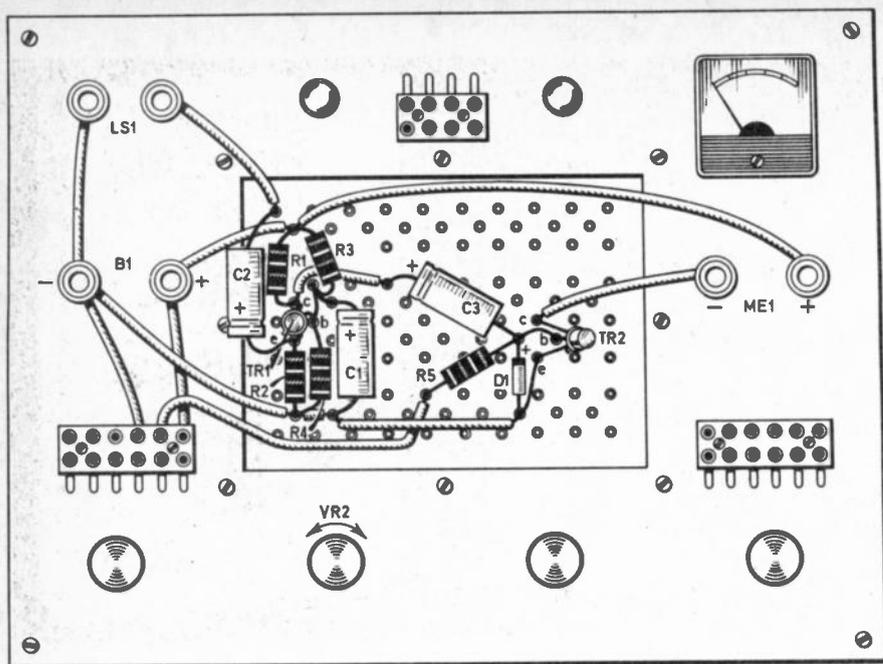


Fig. 4.3. The circuit of Fig. 4.2. Wired up on the Demo Deck. VR2 should be adjusted as mentioned in the text.

by D1. Transistor TR2 is "starvation" biased and acting as an audio detector with a useful amount of power gain that helps match the low impedance of the meter to the high output impedance of the grounded base stage.

Build the circuit of Fig. 4.2 on the Demo Deck as shown in Fig. 4.3 and speak close to the loudspeaker, full scale deflection should be obtained on the meter for loud passages. Strictly speaking the meter is not indicating the amplitude of voltage swings at the collector of TR1 but it can be seen that the amplitude—in parts—is certainly greater than 600mV by disconnecting the 100 kilohm resistor going to the wiper of VR2 (thus removing all bias). Again speak loudly into the loudspeaker, some indication will still be seen on ME1.

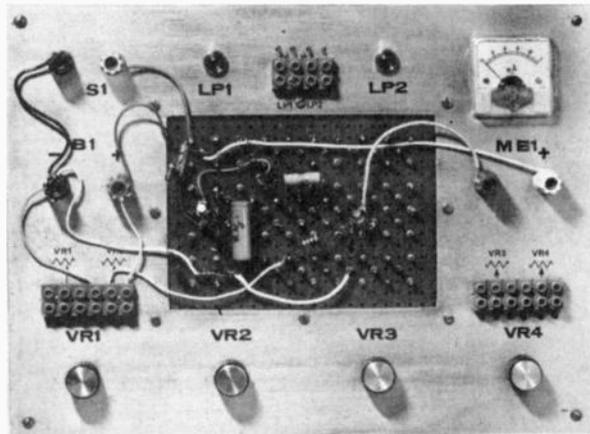Photograph of the construction shown in Fig. 4.3.



To get *any* indication on ME1 means that the voltage fed to the base of TR2 must be exceeding the 600mV base emitter forward voltage drop. When measured on proper test equipment the a.c. signal at the collector of TR1 is in the order of 1.5V,—thus bearing out that we are getting very high voltage amplification (between 600 and 700 as calculated).


USES

The grounded base stage is not the easiest amplifier to design or to use in equipment but nevertheless it has several useful features. It is very easy to design a circuit having a known voltage gain (by using the ratio of input and output impedances); adding a resistor in series with the signal source reduces the gain proportionately. Very frequently low voltage sources (that need voltage amplification) have very low impedance and therefore match the input of a grounded base stage e.g. moving coil microphones and the first stage of u.h.f. radio tuners.

The output signal is in phase with the input—unlike the common emitter stage where there is 180 degrees phase shift. When the input signal goes positive (Fig. 4.1) it opposes the emitter current, this opposes the collector current and the transistor conducts less; therefore the potential at the collector goes positive (in phase with the input). This is a very useful feature in some applications—particularly when dealing with non-symmetric waveforms as are encountered in television systems.

Next month: The Phase Shift Oscillator

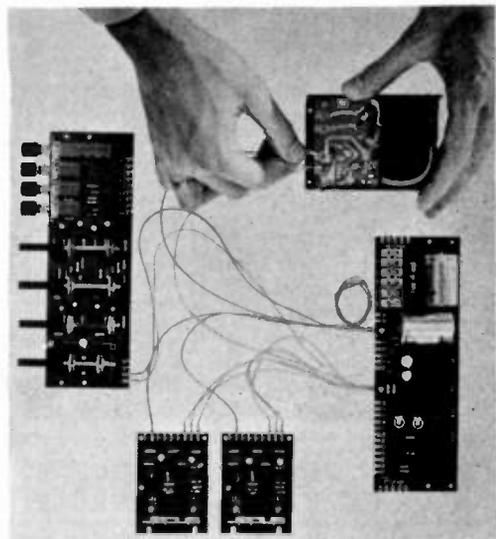Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same — there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative — Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one — Masterlink — which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together — the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

Guarantee

If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

sinclair

Sinclair Radionics Ltd., London Road.,
St. Ives, Huntingdonshire PE17 4HJ.
Telephone: St. Ives (04806) 4311

Everyday Electronics, March 1973

Specifications

Output — 30 watts music power (10 watts per channel R.M.S. into 3 Ω)

Inputs — Mag. P.U. — 3mV correct to R.I.A.A. curve 20—25,000 Hz ± 1dB. Ceramic pick-up — 50mV. Radio — 50 to 150mV. Aux. adjustable between 3mV. and 3V.

Signal to noise ratio — Better than 70dB.

Distortion — better than 0.2% under all conditions.

Controls — Press buttons for on-off, P.U., radio and aux. Treble +15 to —15 dB at 10 kHz. Bass +15 to —15 dB at 100 Hz. Volume. Stereo Balance.

Channel matching within 1dB.

Front panel — brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

£29.95

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE174HJ
Please send Project 605 post free Details and list of stockists

Name

Address

for which I enclose £29.95 cheque/money order/cash. EE2/73

SEW PANEL METERS

CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

- LOW COST
- QUICK DELIVERY
- OVER 200 RANGES IN STOCK
- OTHER RANGES TO ORDER

"SEW" BAKELITE PANEL METERS

Type SW.100 100 x 80 mm.

50μA	£3.90
50-500μA	£3.90
100μA	£3.90
100-1000μA	£3.70
500μA	£3.50
1mA	£3.40
20V. D.C.	£3.40
50V. D.C.	£3.40
300V. D.C.	£3.40
1 amp. D.C.	£3.40



5 amp. D.C. £3.40
300V. A.C. £3.40
VU Meter £4.15

Type MR.85P. 4 1/4 in. x 4 1/4 in. fronts

50mA	£3.10
100mA	£3.10
500mA	£3.10
1 amp.	£3.10
5 amp.	£3.10
15 amp.	£3.10
30 amp.	£3.20
20V. D.C.	£3.10
50V. D.C.	£3.10
150V. D.C.	£3.10
300V. D.C.	£3.10
1000μA	£3.40
100-1000μA	£3.30
200μA	£3.30
300μA	£3.30
500-5000μA	£3.10
1mA	£3.10
1-10mA	£3.10
5mA	£3.10
10mA	£3.10

Type MR.38P. 1 21/32 in. square fronts

200mA	£1.75
300mA	£1.75
500mA	£1.75
750mA	£1.75
1 amp.	£1.75
2 amp.	£1.75
5 amp.	£1.75
10 amp.	£1.75
10V. D.C.	£1.75
15V. D.C.	£1.75
20V. D.C.	£1.75
50V. D.C.	£1.75
100V. D.C.	£1.75
150V. D.C.	£1.75
300V. D.C.	£1.75
500μA	£1.96
100-1000μA	£1.96
200μA	£1.96
300μA	£1.96
500-5000μA	£1.75
1mA	£1.75
1-10mA	£1.75
5mA	£1.75
10mA	£1.75
20mA	£1.75
50mA	£1.75
100mA	£1.75
150mA	£1.75

Type MR.65. 3 1/4 in. square fronts

1 amp.	£2.15
5 amp.	£2.15
15 amp.	£2.15
50 amp.	£2.15
5V. D.C.	£2.15
10V. D.C.	£2.15
20V. D.C.	£2.15
50V. D.C.	£2.15
150V. D.C.	£2.15
300V. D.C.	£2.15
500V. D.C.	£2.40
1000V. D.C.	£2.40
30V. A.C.*	£2.20
50V. A.C.*	£2.20
150V. A.C.*	£2.20
300V. A.C.*	£2.20
500mA A.C.*	£2.15
1 amp. A.C.*	£2.15
5 amp. A.C.*	£2.15
10 amp. A.C.*	£2.15
20 amp. A.C.*	£2.15
30 amp. A.C.*	£2.15
50 amp. A.C.*	£2.15
VU Meter	£3.40



Type SD.830 82.5mm x 110mm Fronts

10mA	£2.50
50mA	£2.50
100mA	£2.50
500mA	£2.50
300V. D.C.	£2.50
5 amp.	£2.50
10 amp.	£2.50
5V. D.C.	£2.50
10V. D.C.	£2.50
20V. D.C.	£2.50
50V. D.C.	£2.50
300V. D.C.	£2.50
15V. A.C.	£2.75
300V. A.C.	£2.75
5mA	£2.50
VU Meter	£3.90



Type MR.52P. 2 1/4 in. square fronts

50μA	£3.40
50-500μA	£3.35
100μA	£3.40
100-1000μA	£3.25
200μA	£3.25
300μA	£3.25
500-5000μA	£3.10
1mA	£3.10
1-10mA	£3.10
5mA	£3.10
10mA	£3.10

Type MR.45P. 2 in. square fronts

50μA	£3.40
50-500μA	£3.30
100μA	£3.30
100-1000μA	£3.15
200μA	£3.15
300μA	£3.15
500-5000μA	£2.90
1mA	£2.90
1-10mA	£2.90
5mA	£2.90
10mA	£2.90
20mA	£2.90
50mA	£2.90
100mA	£2.90
150mA	£2.90

Type S-80 80 mm. square fronts

50μA	£3.50
50-500μA	£3.40
100μA	£3.40
100-1000μA	£3.20
200μA	£3.20
300μA	£3.20
500-5000μA	£2.95
1mA	£2.95
1-10mA	£2.95
5mA	£2.95
10mA	£2.95
20mA	£2.95
50mA	£2.95
100mA	£2.95
150mA	£2.95



Type SD.640 63.5mm x 85mm Fronts

50μA	£3.90
50-500μA	£3.85
100μA	£3.85
100-1000μA	£3.65
200μA	£3.65
300μA	£3.65
500-5000μA	£3.50
1mA	£3.50
1-10mA	£3.50
5mA	£3.50
10mA	£3.50
20mA	£3.50
50mA	£3.50
100mA	£3.50

Type MR.65P. 3 1/4 in. x 3 1/4 in. fronts

50μA	£3.70
50-500μA	£3.60
100μA	£3.60
100-1000μA	£3.40
200μA	£3.40
300μA	£3.40
500-5000μA	£3.25
1mA	£3.25
1-10mA	£3.25
5mA	£3.25
10mA	£3.25
20mA	£3.25
50mA	£3.25
100mA	£3.25
150mA	£3.25

Type MR.45P. 2 in. square fronts

50μA	£3.40
50-500μA	£3.30
100μA	£3.30
100-1000μA	£3.15
200μA	£3.15
300μA	£3.15
500-5000μA	£2.90
1mA	£2.90
1-10mA	£2.90
5mA	£2.90
10mA	£2.90
20mA	£2.90
50mA	£2.90
100mA	£2.90
150mA	£2.90

Type S-80 80 mm. square fronts

50μA	£3.50
50-500μA	£3.40
100μA	£3.40
100-1000μA	£3.20
200μA	£3.20
300μA	£3.20
500-5000μA	£2.95
1mA	£2.95
1-10mA	£2.95
5mA	£2.95
10mA	£2.95
20mA	£2.95
50mA	£2.95
100mA	£2.95
150mA	£2.95

Type SD.460 46mm x 59.5mm Fronts

50μA	£3.40
50-500μA	£3.35
100μA	£3.35
100-1000μA	£3.15
200μA	£3.15
300μA	£3.15
500-5000μA	£2.95
1mA	£2.95
1-10mA	£2.95
5mA	£2.95
10mA	£2.95
20mA	£2.95
50mA	£2.95
100mA	£2.95
150mA	£2.95

Type MR.65P. 3 1/4 in. x 3 1/4 in. fronts

50μA	£3.70
50-500μA	£3.60
100μA	£3.60
100-1000μA	£3.40
200μA	£3.40
300μA	£3.40
500-5000μA	£3.25
1mA	£3.25
1-10mA	£3.25
5mA	£3.25
10mA	£3.25
20mA	£3.25
50mA	£3.25
100mA	£3.25
150mA	£3.25

"SEW" EDGWISE METERS

Type PE.70. 3 17/32 in. x 1 15/32 in. x 2 1/2 in. deep

50μA	£3.40
50-500μA	£3.30
100μA	£3.30
100-1000μA	£3.15
200μA	£3.15
300μA	£3.15
500-5000μA	£2.90
1mA	£2.90
1-10mA	£2.90
5mA	£2.90
10mA	£2.90
20mA	£2.90
50mA	£2.90
100mA	£2.90
150mA	£2.90

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 100mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	£3.50
100μA	£3.10
1mA	£4.35
50-500μA	£3.10
1-10mA	£4.35
1A d.c.	£4.35
5A d.c.	£4.35
10V d.c.	£4.35
20V. d.c.	£4.35
50V. d.c.	£4.35
300V. d.c.	£4.35
Dual range	£4.35
500mA/5A d.c.	£3.10
5V/50V d.c.	£3.10



***MOVING IRON— ALL OTHERS MOVING COIL**
Please add postage

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. 1/2 in. dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, 90p. P. & P. 10p.
10 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.15 P. & P. 10p.
100 WATT. 1/10/25/50/100/250/500/1000 or 2500 ohms. £1.25 P. & P. 15p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality · Low price · Immediate delivery

S-300 General Purpose Bench Mounting

1 Amp	£7.00
2.5 Amp	£8.05
5 Amp	£11.75
8 Amp	£15.90
10 Amp	£23.80
12 Amp	£23.90
20 Amp	£49.00
25 Amp	£58.00
40 Amp	£83.50



S-300E Panel Mounting

1 Amp	£7.00
2.5 Amp	£8.05

Please add postage
ALL MODELS
INPUT 230 V 50/60 CYCLES
OUTPUT VARIABLE 0-250
Special discounts for quantity



AUTO TRANSFORMERS
0/115/250V. Step up or step down. Fully shrouded.

50 W	£2.10	P. & P. 15p
150 W	£2.70	P. & P. 15p
300 W	£3.00	P. & P. 23p
500 W	£3.25	P. & P. 33p
1000 W	£7.50	P. & P. 33p
1500 W	£10.50	P. & P. 43p
2250 W	£17.25	P. & P. 53p
5000 W	£35.00	P. & P. 61



MCA.220 AUTOMATIC VOLTAGE STABILISER

Input 55 125 VAC or 175 250VAC. Output 120V AC. or 240 VAC. 300 VA rating. £11.97, carr. 50p.



230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 8 amp rating. 50p each. P. & P. 10p (100 lots 240). Quantities available.



BM.001 HEAD SET AND BOOM MICROPHONE

Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 300 ohms. £4.98. P. & P. 15p.



240° Wide Angle 1mA Meters

MW 1-5 60mm square £3.97
MW 1-8 80mm square £4.97
P. & P. extra




RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V AC. Size 185 x 85 x 100mm. £8.97 P. & P. 25p.



PS.200 REGULATED P.S.U.

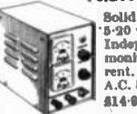Solid state. Variable output 0-20 volt DC up to 2 amp. Independent meters to monitor voltage and current. Output 220/240 V. A.C. Size 7 1/2" x 5 1/2" x 3 1/2". £14.97. P. & P. 25p.



PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V AC. Size 4" x 3 1/2" x 6 1/2". £11.97. P. & P. 25p.



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with all instructions, etc. £4.50. P. & P. 30 p.



LB3 TRANSISTOR TESTER

Tests 100 and B. PNP/NPN. Operates from 9V battery. Complete with all instructions, etc. £3.95. P. & P. 20p.



HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station, £3.97, 3 Station £3.95, P. & P. 15p.
4 Station £6.98, P. & P. 17p.



SEND SAE FOR LIST OF SEMI CONDUCTORS & VALVES

G. W. SMITH & CO. (RADIO) LTD.
Also see next three pages

MULTIMETERS for EVERY purpose!



TS60 POCKET MULTIMETER
High-precision at low-cost. Ranges: D.C. 15V, 150V, 1,000V (10,000 ohms), A.C. 15V, 150V, 100V (1,000 ohms). D.C. Current 100mA. Resistance 100k ohms. \$1.85. Post 15p.

MODEL 1092 TESTMETER
5,000 O.P.V.
0/3/15/100/300/1200 V.
D.C. 0/6/30/300/600 V.
A.C. 0/300mA/300 MA
0/10K/1 meg Ω
Decibels -10 to +16db
\$2.75 each +15p P. & P.



HIKOKI MODEL 720X
20,000 O.P.V.
Overload protection
5/25/100/500/1000 V.M.
10/50/250/1000 VAC.
50 μ A/250mA. 20K/2 meg
ohm. 5 to +62dB.
\$4.97. P. & P. 15p.

HIKOKI MODEL 730X
30,000 O.P.V. Overload
protection. 6/30/60/300/
600/1200 VDC. 12/60/120/
600/1200 VAC. 60 μ A/30
mA/300 mA. 2K/2000K/2
megohm. -10 to +63db.
\$6.50. P. & P. 15p.

MODEL TE-12
20,000 O.P.V. 0/0-6/30/120/
600/1200/3000/6000. D.C.
0/6/30/120/600/1200V. A.C.
0/60 μ A/6/60/600mA. 0/6K/
600K/6Meg. 60 Meg. Ω 50pF
0-2mFd. \$5.97. P. & P. 17p.

MODEL TE-200
20,000 O.P.V. Mirror scale,
overload protection. 0/5/25/120/
1000V. D.C. 0/10/50/250/
1000V. A.C. 0/50 μ A/250 mA
0/60K/6 meg Ω . -20 to +62db.
\$3.95. P. & P. 15p.

MODEL 500
30,000 O.P.V. with over-
load protection mirror scale
0/5/2-5/10/25/100/250/500/
1000V. D.C. 0/1/5/10/20/
100/250/500/1000V. A.C.
0/50 μ A/5/50/500mA. 12
amp. D.C. 0/60K/6 Meg. Ω
40 Meg Ω .
\$3.87. Post paid.

HIKOKI MODEL 750X
50,000 o.p.v. 43 ranges 0-0.3
to 1,200V D.C. 0-3 to 1,200V
A.C. 0-30mA/300mA. 0-3K/30
meg ohms. -10 to +17dB.
\$3.97. Post 20p.

HT100B4 MULTI-METER
Features A.C. current ranges.
100,000 o.p.v. Mirror Scale.
Overload protection.
D.C. 0/5/2-5/10/50/250/500/1000 V
D.C.
0/2-5/10/50/250/1000 V. A.C.
0/10/250 μ A/2-5/25/250 MA/
10 Amp. D.C.
10 Amp. A.C. 0/20K/200K/
2 MEG/20 MEG. -20 to +62db.
\$12.50. P. & P. 25p.

370 WTR MULTI-METER
Features A.C. current ranges.
20,000 o.p.v. 0/5/2-5/10/50/
250/500 1000 V. D.C.
0/2-5/10/50/250/500/1000V A.C.
0/50 μ A/1/10/100mA/1/10 Amp
D.C.
0/100mA/1/10 Amp A.C.
0/5K/50K/500K/5 MEG/ 50
MEG.
-20 +62db.
\$15. P. & P. 25p.

RUSSIAN 22 RANGE MULTIMETER
Model U437 10,000 o.p.v.
A first class versatile in-
strument manufactured in
U.S.S.R. to the highest
standards. Ranges: 2-5/10/
50/250/500/1000V D.C. 2-5/
10/50/250/500/1000V A.C.
DC Current 100mA/1/10/
100mA/1A. Resistance
300 ohms/3/30/300K/3m Ω .
Complete with batteries,
test leads, instructions and
sturdy metal carrying case.
OUB PRICE \$5.97. P. & P. 25p.

ROUND SCALE TYPE PENCIL TESTER
MODEL T.S.68
Completely portable, simple
to use pocket sized tester.
Ranges 0/3/30/300V AC
and DC to 2,000 o.p.v.
Resistance 0-20K ohms.
ONLY \$1.97 P. & P. 15p.

LT601 MULTIMETER
New style 20,000
o.p.v. pocket multi-
meter. 5/25/50/250/
500 / 2500 V. D.C.
10 / 50 / 100 / 500 / 1000V.
A.C. 50 μ A / 250mA. 6K / 6
meg ohms. -20 to +22 dB.
\$3.75. Post 20p.

MODEL TH-12
20,000 o.p.v. Overload pro-
tection. Slide switch selector
0 / 25 / 2.5 / 10 / 50 / 250 /
1000V. D.C. 0 / 10 / 50 / 250 /
1000V. A.C. 0 / 50 μ A / 25 /
250mA. D.C. 0 / 3K / 30K /
300K / 3 Meg -20 to +50dB
\$4.97. Post 15p.

MODEL TE-300
30,000 O.P.V. Mirror scale
overload protection 0/5/15/50/
300/1200V. D.C. 0/6/30/120/600/
1200V. A.C. 0/30 μ A/6mA/
60mA/300mA/600mA. 0/8K/
80K/800K/8 meg. ohm -20 to
+63 db. \$5.97. P. & P. 15p.

MODEL TE-300
30,000 O.P.V. Mirror scale
overload protection 0/5/15/50/
300/1200V. D.C. 0/6/30/120/600/
1200V. A.C. 0/30 μ A/6mA/
60mA/300mA/600mA. 0/8K/
80K/800K/8 meg. ohm -20 to
+63 db. \$5.97. P. & P. 15p.

MODEL PL436
20K Ω /Volt. D.C. 6k Ω /
Volt AC. Mirror scale.
6/3/12/30/120/600 V
D.C. 3/30/120/600 V
A.C. 50/600 μ A/60/600
mA. 10/100K/1 Meg/10
Meg Ω -20 to +46db.
\$6.97. P. & P. 12p.

MODEL TW-50K
48 ranges, mirror scale,
50K/Vol. D.C. 5K/Volt A.C.
D.C.: Volts -125, -25, 1/25,
2-5, 5, 10, 25, 50, 125, 250,
500, 1000V. A.C. Volts: 1-5,
3, 5, 10, 25, 50, 125, 250, 500,
1000V. D.C. Current: 25,
50 μ A, 2-5, 5, 25, 50, 250,
500mA, 5, 10 amp. Resistance:
10K, 100K, 1 MEG, 10 MEG
 Ω . Decibels: -20 to +81.5db
\$8.50. P. & P. 17p.

MODEL K228A
Taut band
suspension.
Overload
protection.
Polarity
reversing
switch. 30,000 o.p.v.
0 / 5 / 2-5 / 15 / 50 / 250 /
500 / 1000 / 2500V. D.C. 0 / 15 / 50 / 150 /
500 / 1000V. A.C. 0 / 50 μ A / 5 / 50 / 150 /
500mA / 5A. D.C. 0 / 3K / 300K / 3 meg.
\$8.95. Post 20p.

HIKOKI MODEL 700X
100,000 O.P.V. Overload
protection. Mirror scale.
-3/6/1-2/1-5/3/6/12/30/60/
120/300/600/1200V DC
1-5/3/6/12/30/60/150/300/600/
1200 V. A.C.
15/50 μ A/3/6/30/60/150/300mA
6/12 AMP. D.C. 1K/200K/2
Meg/20 Meg ohm -20 to
+63dB. \$13.50. P. & P. 20p.

MODEL C-7080 EN
Giant 6" mirror scale.
20,000 o.p.v. 0-25 / 1 /
2-5 / 10 / 50 / 250 / 1000 /
5000V. D.C. 0 / 2-5 / 10 /
50 / 250 / 1000 / 5000V.
A.C. 0 / 50 μ A / 1 / 10 / 100 /
500mA / 10 amp. D.C.
0 / 2K / 200K / 20 meg
ohm to 50 dB.
\$13.90. Post 35p.

U4312 MULTIMETER
Extremely sturdy instrument for general
electrical use. 667 o.p.v.
0/3/15/7-5/30/60/150/300/
600/900 VDC and 75mV.
0/3/15/7-5/30/60/150/300/
600/900 VAC.
0/300 μ A/1-5/6/15/60/150/300/
600mA/1-5/6 AMP. D.C.
0/1-5/6/15/60/150/600mA/
1-5/6 AMP. A.C.
0/200/2/5K/30K Ω .
Accuracy DC 1%. AC 1-5%.
Knife edge pointer, mirror scale. Complete
with sturdy metal carrying case, leads and
instructions. \$9.50 plus P. & P. 25p.

Selected TEST EQUIPMENT

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring
A, B and ICO, NPN or PNP.
Equally adaptable for check-
ing diodes. Supplied complete
with instructions, battery and
leads.
\$7.50. Post 20p.



TE-16A TRANSISTORISED SIGNAL GENERATOR

5 ranges 400KHz-30mHz.
An inexpensive instru-
ment for the handyman.
Operates on 9V battery.
Wide easy to read scale.
800KHz modulation.
5 1/2 x 5 1/2 x 3 1/2 in.
Complete with instruc-
tions and leads. \$7.97. Post 25p.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable
bridge offering ex-
cellent range and
accuracy at low
cost. Ranges: R.
1 Ω to 111 meg Ω
6 Ranges \pm 1%
L.L. μ H - 111
HENRY86 Range \pm 2% C.10pF \pm 110mPd
6 Ranges \pm 2%. TURNS RATIO 1:1/1000-
1:1/100. 6 Ranges \pm 1%. Bridge voltage at
1,000 cps. Operated from 9 volts, 100 μ A.
Meter indication. Attractive 2 tone metal
case. Size 7 1/2 x 2 1/2. \$20. P. & P. 25p.

MODEL TE.15 GRID DIP METER

Transistorised. Operates as
Grid Dip, Oscillator, Absorp-
tion Wave Meter and Oscil-
lating Detector. Frequency
range 440Kc/ps-280Mc/ps in
6 cells. 600 μ A Meter. 9V
battery operation. Size 180 x
80 x 40mm.
\$12.50. Post 20p.

BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18 x 200,000 Hz: Square 18 x 50,000 Hz.
Output max.
+10 dB.
(10 K ohms)
Operation in-
ternal batteries
Attractive 2-
tone case 7 1/2
x 5 x 2".
Price \$17.50.
Carr. 17 1/2p.

MODEL MG-100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19-220,000Hz
Sine Wave 19-100,000
Hz Square Wave.
Output Sine or Square
wave 10v. P. to P.
Size 180 x 90 x 90mm.
Operation 220/240v. A.C.
\$17.50. Post 37p.

MODEL AT201 DECADE ATTENUATOR

Frequency range 0-
200KHz. V. RMS/30 amp.
0-111db. 0-1db step.
Impedance 600 ohms.
Max. input power
30dbm. Size 180 x 90 x 55mm.
\$12.50. Post 37p.

TE-65 VALVE VOLTMETER

28 ranges. D.C. volts
1-5-1,500V. A.C. volts
1-5-1,500V. Resistance up
to 1,000 megohms. 200/
240V. A.C. operation
Complete with probe and
instructions.
\$17.50. P. & P. 30p.
Additional probes avail-
able: R.F. \$2-12; H.V.
\$2-50.

MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMPMETER

Sensitivity 330 ohms/Volt
AC and DC. Accuracy
5% D.C. 1% AC. Scale
length 165mm. 0/300/500 μ A/
1-5 / 3 / 7-5 / 15 / 30 / 75 /
150 / 300 / 750mA / 1-5 / 3 /
7-5 AMP DC / 0 / 3 / 7-5 / 15 /
300 / 750 V / 1-5 / 3 / 7-5 /
150 / 300 / 750V DC
0/750mV/1-5 / 3 / 7-5 / 15 / 30 / 75 / 150 / 300 / 750V AC
Automatic cut out. Supplied com-
plete with test leads, manual and test certifi-
cates. \$49.00. Post 50p.

Model S-100TR MULTIMETER TRANSISTOR TESTER

100,000 o.p.v. mirror scale/
overload protection. 0/12/
6/3/12/30/120/600 V DC.
0/6/30/120/600. V AC. 0/12/
600 μ A / 12/300mA/12 AMP
DC. 0/10 K / 1 MEG/100MEG.
-20 to +50db. 0-01-2 MFD.
Transistor tester measures
Alpha, beta and Ico. Complete
with batteries, instructions
and leads. \$13.50. P/P 25p.



MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C.
beta in/out. Checks
Icbo. Checks diodes
in/out. Checks
SCR, etc. Beta
HI 10 500,
LO 2-50. Icbo 0-3000 μ A. 220/240 V. A.C.
operation
\$17.50. Post 25p.

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal
generator covering
120 Kc/ps 500 Mc/ps on
6 bands. Directly cali-
brated Variable R.F. at-
tenuator, audio output.
Xtal socket for calibration.
220/240V. A.C.
Brand new with instruc-
tions \$15. C. Carr. 37p.
Size 140 x 215 x 170 mm.

MODEL L-55 FET V.O.M.

Input impedance 10 meg
ohms. 0 / 3 / 1-2 / 6 / 30 /
120 / 600V. D.C. 0 / 3 /
12 / 60 / 120 / 600V. A.C.
0 / 120 μ A / 120mA D.C.
0 / 1K / 100K / 10 meg
/ 100 meg ohms
\$15.97. Post 15p.



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and
periodic waveforms in
electronic circuits.
VERT. AMP. Band-
width 10MHz. Sensi-
tivity at 100KHz VRMS/
mm. 1-25; HOR. AMP. Bandwidth 500KHz.
Sensitivity at 100KHz, V RMS/mm. -3-25;
Preset triggered sweep 1-3,000cps.
Free running 20-200,000Hz in nine ranges.
Calibrator pipe. 220 x 360 x 430mm.
115-230V. AC. operation.
\$39.00. Carr. paid.

TO-3 PORTABLE OSCILLOSCOPE

3in. tube. Y amp. Sensitivity
0-1v p-p/CM. Bandwidth
1-5 cps-1.5 MHz. Input imp.
2 meg Ω 25pF X amp.
sensitivity 0.9v. p-p/CM.
Bandwidth 1-5cps-600KHz.
Input imp. 2 meg Ω 20pF.
5 ranges 10 cps
300 kHz. Synchronization.
Internal/external. Illuminated
scale 140 x 216 x 330 mm. Weight 15 1/2 lb.
220/240V. A.C. Supplied brand new with
handbook. \$40.00. Carr. 50p.

RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE



5 mc/ps Pass Band. Separate
Y1 and Y2 amplifiers.
Rectangular 5in. x 4in.
C.R.T. Calibrated trig-
gered sweep from .2 usec.
to 100 milli-sec. per cm.
Free running time base 50 cps/1 mc/ps. Built-
in time base calibrator and amplitude
calibrator. Supplied complete with all
accessories and instruction manual
\$87. Carr. Paid.



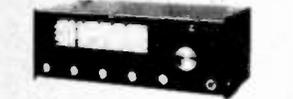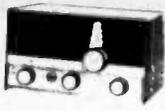G. W. SMITH
& CO (RADIO) LTD.
Also see opposite page
and next two pages

UNR-30 RECEIVER

4 Bands covering 550Kc/s - 30Mc/s. B.F.O. Built-in Speaker 220/240v A.C. Brand new with instructions. £18-75. Carr. 37p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550Kc/s - 30Mc/s. FET 8 Meter. Variable BFO for 88B. Built-in Speaker, Bandspread, Sensitivity Control. 220/240v. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.

SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 KHz and 55 to 30 MHz. Illuminated slide rule dial. Bandspread. Aerial tuning BFO. AVC, ANL, '8' meter. AM/CW/88B. Integrated speaker and phone socket. Operation 220/240v AC or 12v DC. Size 326 x 266 x 150 mm. Complete with instructions and circuit. £28-50. Carr. 50p.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400Kc/s. 550 Kc/s - 30Mc/s. FET front end. 2 mech. product detector, variable B.F.O., noise limiter. 8 Meter. Bandspread, R.C. Gain. 18" x 9 1/2" x 6 1/2". 18 in 220/240v. A.C. or 12v. D.C. Brand new with instructions. £40. Carr. 50p.



TRIO 9R59DS COMMUNICATION RECEIVER

4 band covering 550Kc/s. to 30 Mc/s. continuous. 4/8 ohm output and phone jack. 88B-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. IF frequency 455 Kc/s. audio output 1.5w. Variable RF and AF gain controls. 115/250v. A.C. Size: 7" x 13" x 10". with instruction manual. £49-50. Carr. Paid.

EMI LOUSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7-25 each P. & P. 37p.
Model 450. 13" x 6" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £8-82 each. P. & P. 25p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt. current and ohms with optional plug in camera. Specifications: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100v. D.C. Input: Fully floating (3 poles). Input power: 110-230v. A.C. 50/60 cycles. Overall size: 8 1/2 in. x 2 1/2 in. x 8 3/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED. £36-80. Carr. 50p.



SINCLAIR IC-12

List Price £2-98
OUR PRICE £1-80
P. & P. 10p

SINCLAIR EQUIPMENT

Project 60 Package offers:
2 x 230 amplifier, stereo 60 pre-amp, P25 power supply. £16-95 Carr. 37p. Or with P26 power supply £18-00 Carr. 37p. 2 x 250 amplifier, stereo 60 pre-amp, P28 power supply. £20-25 Carr. 37p.
Transformer for P28. £2-97 extra.
Add to any of the above £4-45 for active filter unit and £18-00 for pair of Q16 speakers. All other Sinclair products in stock.
2000 Amp £21-95 Carr. 37p.; 3000 Amp £28-50 Carr. 37p.; Neoteric Amp £43-95. Carr. 37p. IC12 £1-80 p. & p. 10p.
NEW PROJECT 605 — £20-97. Carr. 37p.

SPECIAL OFFER! GOODMAN AXIOM 301

Hi Fi 12" 20 watt twin cone full range speaker. 30-16,000 Hz. 16,500 gauss. 8 ohm impedance. Brand new and boxed.
(List price £21.72) **OUR PRICE £12-50** each. Carr. 50p.

EA-41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2 x 3 1/4 in. £5-97. P. & P. 15p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2" x 9" x 7 1/2". 8 ohms. 8 watt RMS. 16 watt peak. Complete with DIN lead. £12-95 pr. Carr. 50p.

HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 50mV/100mV. Output 50mW. £5-97. P. & P. 15p.

SPECIAL PURCHASE! NEAT G30J STATIC BALANCE PICK-UP ARMS

Identical specification to NEAT G30J in arm but with two-tone chrome and black finish. Complete with head shell, pick up rest and plug in phono leads.

BRAND NEW— FULLY GUARANTEED ONLY £8-95. P. & P. 25p.

ARF-300 AF/RF Signal Generator

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine square 10v. P-P. RF 100KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. AC. Complete with instructions and leads. £29-95. Post 50p.

AKAI BARGAINS

SUPER MONEY SAVING OFFERS— BUY NOW WHILE STOCKS LAST!

BRAND NEW AND FULLY GUARANTEED

1721 Tape Rec. £73-95
X5000 Tape Rec. £99-95
GX370 Tape Deck £259-95
4000D8 Tape Deck £73-95
4000D8 Dust Cover £4-75
X200 Tape Deck £99-95
X201D Tape Deck £132-95
X221D Tape Deck £169-95
GX220D Tape Deck £148-50
GX280D Tape Deck £240-40
X1810D Tape/8 Track Deck £169-95
GX1900D Tape/Cass Deck £177-95
X2000SD Tape/Cass/8 Track Rec. £232-50
CR81 8 track Rec. £50-95
CR81D 8 track Rec. £65-95
CR81T 8 track/Receiver £118-90
CR80D88 8-track £22-50
CR8088 8 track system £145-00


GXC40 Cassette Rec. £82-25
GXC40D Cassette Deck £66-95
GXC40T Cassette/Receiver £123-95
GXC45D Cassette Deck £89-95
GXC46D Cassette Deck £103-50
GXC46 Cassette Recorder £115-95
GXC60D Cassette Deck £111-25
GX C65D Cassette Deck £110-25
CS35D Cassette Deck £59-50
AA6300 Receiver £82-50
AA8030 Receiver £111-50
AA8090 Receiver £144-95
AA8500 Receiver £175-00
ADM11 Microphones (Pair) £7-50

Carriage 50p extra. (Recorders & Decks 75p)

DOLBY SYSTEM NOISE REDUCTION UNIT



Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 18kHz ± 1dB 19kHz — 35dB. Size 16 1/2" x 9" x 3 1/2". AC 200/250V. **OUR PRICE £32-50** Carr. 50p.

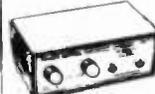

1021 STEREO LISTENING STATION
For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/4". £22-25. P. & P. 15p.



MP7 MIXER PREAMPLIFIER
5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3" Inputs Mics 3 x 3mV 50K: 2 x 3mV 600 ohm. Phono mag. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8-97. P. & P. 20p.



TE-1035 STEREO HEADPHONES
Low cost high performance stereo headphones. Foam rubber ear cups Adjustable head-band. 8 ohm impedance 25-18,000 Hz. With lead and stereo jack plug. **ONLY £1-97. P. & P. 12p.**

NEW GARRARD MODULES



Popular range of Garrard decks with Shure cartridge fitted in deluxe plinth with hinged lid.
SP25 III Module/M75-6 £23-50
A776 Module/M75-6 £33-80
A796 Module/M75-6 £38-75
Zero 1008 Module/M93E £62-60
Carr. 50p extra any item.

HOSIDEN DM-085 DE-LUXE STEREO HEADPHONES
Features unique mechanical 2 way unit and fitted adjustable lever, controls 8 ohm impedance 20-20,000cps. Complete with spring lead & stereo jack plug £7-97. P. & P. 12p.

GENUINE BARGAIN!

KOSS SP.3XC STEREO HEADPHONES
Response 10-15,000Hz. Impedance 4-6 ohms. Brand new. Boxed & fully guaranteed. (List £9.50). **OUR PRICE £8-50.** P. & P. 25p.

HOSIDEN DH-025 STEREO HEADPHONES
Wonderful value and excellent performance combined. Adjustable head-band. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug. **ONLY £2-37. P. & P. 12p.**

TAPE CASSETTES
Top quality Hi-Fi Low Noise in Library cases.
C80 3 for 75p. 10 for £2-35
C90 3 for £1-05. 10 for £3-30
C120 3 for £1-35. 10 for £4-20
Tape Head Cleaner 30p each. P. & P. 10p extra.

SPECIAL OFFER! ROTEL RM700 STEREO HEADPHONES
20-20,000Hz. 8-16 ohm. (List £9-95). **OUR PRICE £6-75. P. & P. 25p.**

TRANSISTORISED FM TUNER
6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2 in. 3 L.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £8-37p. P. & P. 12p. Stereo multiplex adaptors £4-97.


TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET
Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1-97. P. & P. 15p.

HAND HELD 2-WAY WALKIE TALKIES
Industrial quality in robust metal cases. Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases.
2 channel £52-50 Pair. Post 50p.
3 channel £79-50 Pair. Post 50p.
2 watt.

G. W. SMITH & CO (RADIO) LTD.
Also see previous pages and opposite page

FANTASTIC OFFER!

NIKKO TRM 50 STEREO AMPLIFIER

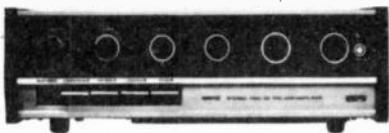

17 + 17 watts rms stereo amplifier with inputs for Magnetic and Crystal phono, Tuner, Tape, Aux and Tape Monitor. Outputs for two pairs of stereo speakers and Tape. Stereo headphone socket. Full range of controls including loudness control, scratch filter, etc. Size 13" x 9 1/2" x 3 1/2". Unrepeatable offer—limited stocks!

List price £59.50
OUR PRICE
£39.95
Carriage 50p

HI-FI EQUIPMENT SAVE UP TO 33 1/3% OR MORE

SEND S.A.E. FOR
FULL DISCOUNT
PRICE LISTS AND
PACKAGE OFFERS!



NIKKO TRM.50 SYSTEM



NIKKO TRM50 17 + 17 watt rms. stereo amplifier, BSR MP60, plinth & cover. Goldring G800 cartridge, pair of Linton 2 speakers and all leads.

OUR PRICE **£104.90** Carr. and Ins. £1.50

WHARFEDALE LINTON SYSTEM



Wharfedale Linton Amplifier, Linton Turntable, pair of Linton 2 speakers and all leads.

OUR PRICE **£104.00** Carr. and Ins. £1.25
LINTON RECEIVER SYSTEM **£155.00**. Carr. & Ins. £1.25.

SAVE £££'s PHILIPS GA308 TRANSCRIPTION TURNTABLE

2 speeds 33 $\frac{1}{3}$ and 45 rpm. Lightweight tubular counterbalanced arm. Belt driven low speed synchronous motor. Viscous damped pick up lift/lower device. Complete with teak plinth and hinged cover. GA308 less cartridge (List £58.55).
OUR PRICE **£34.50**. P. & P. 50p.
LIMITED NUMBER ONLY!



RECORD DECKS (P. & P. 50p)

B.S.R. McDONALD	
C114 Mini	£4.97
C129 Mono	£9.50
C137	£8.25
MP60	£9.50
610	£13.95
810	£21.25
210/TPD3	£3.75
MP60/G800	£12.95
MP60/TPD1	£12.95
MP60/TPD1/G800	£17.95
MP60/TPD2	£14.25
610/TPD1	£12.95
810/TPD1	£17.95
HT70	£18.95
HT70/G800	£17.95
HT70/TPD1	£20.25
HT70/TPD1/G800	£23.90
810 Plinth/Cover	£9.25



GOLDRING	
GL49/2	£18.50
GL73	£30.95
GL72/P	£27.50
Plinth 49/72	£7.95
LID 72	£2.25
GL75	£26.95
GL75P	£28.25
Plinth 75	£7.25
LID 75	£2.00
G99	£19.25
GL85P/C	£26.95
G101P/C	£26.50

HACKER
GPA45/30 **£49.50**
T45 Table **£4.95**

LEAK
Delta Turntable **£53.50**

MICRO-SIKI
MR111 **£29.50**
MR111 Plinth & Cover **£9.50**

PHILIPS
GA105 **£16.95**
GA160 **£27.00**
GA308 Teak **£24.50**
GA212 **£56.75**

PIONEER
PL12D **£24.50**
PL16C **£41.25**
PLA35 **£26.95**
PL50 **£111.25**
PLA1D **£112.50**
PL61 **£119.95**

THORENS
TD125 II **£96.50**
TD125AB II **£96.95**
TX25 **£6.95**
TD160C **£56.95**
TD150A II **£35.95**
TD150AB II **£39.95**

WHARFEDALE
Linton Turntable **£26.95**

PLINTHS & COVERS (P. & P. 50p)

Budget 8P25, etc.	£3.50
Budget AP76/Zero 1008	£4.50
Budget B.S.R.	£3.95
SME 2000 System	£34.50

RECORD DECK PACKAGES (P. & P. 50p)


Decks supplied with stereo cartridge ready wired in plinth with cover.



GARRARD	
2025TC/9TAHCD	£19.75
8P25 III/G800	£18.50
8P25 III/M75-6	£18.50
8P25 III/M44-7	£18.75
8P25 III/M44-E	£20.95
8P25 III/M55E	£22.40
AP76/G800	£27.95
AP76/M75-6	£30.25
AP76/M55E	£30.50
AP76/M75EJ	£32.50
AP76/G800E	£30.75
AP76/M44E	£30.95
AP76/M75ED	£33.95

B.S.R. McDONALD	
MP60/G800	£17.50
MP60/M44-7	£19.95
MP60/M44-E	£19.95
GOLDRING	
GL75/G800	£29.50
GL75/G800E	£42.50

LEAK DELTA 30 SYSTEM

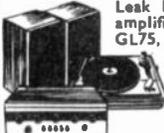

Leak Delta 30 stereo amplifier, Goldring GL75, plinth, cover and G800 cartridge. Pair of Leak 150 speakers and all leads.

OUR PRICE **£123.50** Carr. and Ins. £1.50

AMSTRAD 8000 II SYSTEM


Amstrad 8000 II 7 + 7 watt amplifier. BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.



OUR PRICE **£48.25** Carr. £1.00
Amplifier only, £16.95. Carr. 50p.

LEAK BARGAINS!

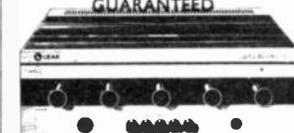LIMITED OFFER!
ALL STOCKS BRAND NEW AND GUARANTEED



Delta 30	£46.95
Delta 70	£57.95
Delta FM	£55.95
SP25 III	£10.25
SP25 III/M75-6	£15.95
8P25 III Module/ M75-6	£23.50
GL66B	£13.75
AP76	£17.95
AP76 Module/ M75-6	£23.00
GL72B	£21.95
GL95B	£22.25
401	£25.95
ZERO 100A	£28.95
ZERO 1008	£36.95
ZERO 1008 Mod/ M55-E	£38.90
AP96 Module/ M75-6	£33.75

ROTEL BARGAINS!

All brand new and guaranteed



RA210 Amp	£22.50
RA310 Amp	£34.95
RA610 Amp	£48.25
RX150 Receiver	£45.95
RX200 Receiver	£57.50
RX400 Receiver	£70.95

TELETON SAQ206B SYSTEM



Teleton SAQ206B B + B watt Amplifier, BSR MP60, plinth & cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE **£54.40** Carr. £1.50
Amplifier only, £22.95. Carr. 50p.

AUDIOTRONIC ACR.3500 MW/LW CAR RADIO



Fully transistorised, dual waveband. Size 6 1/2" x 4 1/2" x 2". 12v. D.C. Neg. or Pos. earth. Complete with fixing kit, speaker and leads. ONLY £7.95. Post 20p.

SUPER BARGAIN! AUDIOTRONIC ACP.8 8-TRACK CAR STEREO TAPE PLAYER



Tone, volume and balance controls. Track selector. Complete with matched pair of stereo speakers, connections and fittings. ONLY £15.95. Post 30p. (Illus is example only).

BH.001 HEAD SET AND BOOM MICROPHONE



Moving Coil. Ideal for language teaching, communications. Headphone imp. 15 ohms. Microphone imp. 200 ohms. £4.95. P. & P. 15p.

SPECIAL PURCHASE!

FERGUSON 3414 STEREO TUNER AMPLIFIER TURNTABLE UNIT



10 + 10 watts rms. Five push buttons with separate scales for pre-tuning to desired FM station. Housed in a handsome walnut finished cabinet with BSR PL128/MP60 record deck with Goldring G800H stereo magnetic cartridge. Offered complete with cover and a pair of matching Medway Speakers, size 18" x 11" x 8". TODAY'S VALUE AT LEAST £125!

OUR PRICE **£75.00** Carr. & Ins. £1.50.

WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5" dia. Impedance 4/8 ohms. High flux ceramic magnet, 20 watts rms. Brand new £1.80. Carr. 37p.



HOMER INTERCOMS

Ideal for home office, stores, factories, etc. Supplied complete with batteries, cable and tree instructions.

2 Station, £8.97, 3 Station £5.95, P. & P. 15p
4 Station £6.85, P. & P. 17p.

CREDIT TERMS AVAILABLE FOR CALLERS AND MAIL ORDER CUSTOMERS ON PURCHASES OF £100 AND OVER.
ACCESS & BARCLAYCARD WELCOME

G.W. SMITH & CO (Radio) LTD
Personal Callers Welcome - All Branches Open 9-6 Mon. to Sat.

10 TOTTENHAM CT. RD. LONDON, W.1
27 TOTTENHAM CT. RD. LONDON, W.1
257/258 TOTTENHAM CT. RD. LONDON, W.1
3 LISLE STREET, LONDON, W.C.2
34 LISLE STREET, LONDON, W.C.2
311 EDGWARE ROAD, LONDON, W.2

Tel: 01-637 2232
Tel: 01-636 2715
Tel: 01-630 0670
Tel: 01-437 8204
Tel: 01-437 9155
Tel: 01-262 0387

All Mail Orders to 11-12, Paddington Green, London, W.2
Tel: 01-262 6642

DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE
IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY
DEFECTIVE WE WILL REPLACE THE SAID GOODS
WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE
COVERED BY MANUFACTURERS 12 MONTHS
GUARANTEE

GARRARD SP25 Mk. III

Special Purchase. Limited number available

Garrard SP25 Mk. III £17.45
Goldring G800
Teak plinth and tinted cover
All leads supplied.
Please add £1.25 P. & P. & Ins.

TURNTABLES

Please add 75p P. & P. & Ins.

Connoisseur BDI Chassis £12.75
Garrard SP25 Mk. III £9.90
Garrard AP76 £17.20
Garrard SL65B £13.95
Garrard 401 £28.75
Garrard Zero 100 (Auto) £36.90
Garrard Zero 100 (Single) £35.90
BSR MP60 £9.40
Goldring GL72 £20.90
Goldring GL72/P £27.45
Goldring GL75 £26.85
Goldring GL75/P £34.95
Goldring 101/P.C. £20.00
Wharfedale Linton + cart. £25.90
Thorens TD125AB Mk. II. £91.45
Thorens TD150 Mk. II £27.95
Thorens TD160 AB & C £53.95

TUNERS

Please add 85p P. & P. & Ins.

Amstrad Multiplex 3000 £27.25
Armstrong 523 £39.50
Armstrong 524 £31.45
Rogers R/brook FET4 (Chassis) £35.75
Rogers R/brook FET4 (Cased) £38.95
Rogers R/bourne FET4 (Chassis) £45.00
Rogers R/bourne FET4 (Cased) £49.50
Sinclair PR060 (Module) £16.95
Sinclair 2000/3000 Tuner £29.90
Leak Delta FM (Cased) £53.60
Leak Delta AM/FM (Cased) £63.75
Alpha Highgate FT150 £37.95
Metrosound FMS20 £38.65
Philips RM690 £33.00

TUNER/AMPLIFIERS

Please add £1 P. & P. & Ins.

Alpha Highgate 150 £49.75
Armstrong 525 (Teak cased) £69.45
Armstrong 526 AM/FM (Teak cased) £77.25
Leak Delta 75 £119.00
Teleton 2100 £32.50
Goodmans One Ten £98.90
Goodmans MOD90 £85.50
Rotal 150 £49.50
Rotal 400 £75.50
Rogers Ravensbrook (Teak cased) £77.00
Rogers R/brook (Chassis) £72.00
Alpha FR 3000, New product £72.00

All prices correct at time of press E. & O. E. and are subject to alterations.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept (EE3) 174 Pentonville Road, London, N1. Telephone 01-278 1768

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

AMPLIFIERS

Please add 85p P. & P. & Ins.

Amstrad 8000 Mk. II £14.95
Amstrad IC2000 £27.50
Amstrad Integra 4000 £23.50
Armstrong 521 (Teak cased) £43.90
Alpha Highgate 212 £24.85
Alpha Highgate FA300 £32.25
Alpha Highgate FA400 £35.65
Leak Delta 30 £44.85
Leak Delta 70 £54.90
Metrosound ST20E £24.20
Metrosound ST60 £45.95
Pioneer SA600 & 610 £57.25
Pioneer SA500A £31.95
Pioneer SA1000 £96.95
Rogers R/brook (Chassis) £37.95
Rogers R/brook (Cased) £41.50
Rogers R/bourne (Chassis) £49.95
Rogers R/bourne (Cased) £52.75
Sinclair PR060 2 X Z30/PZ5 £14.70
Sinclair PR060 2 X Z30/PZ6 £16.70
Sinclair PR060 2 X Z50/PZ8 £22.95
Tran's Sinclair AFU (Filter Unit) £4.20
Sinclair 605 £17.95
Sinclair 2000 Mk. II £21.50
Sinclair 3000 Mk. II £28.00
Wharfedale Linton £39.70
Teleton SAQ 307 £22.95
Rotal RA310 £34.95
Rotal RA610 £52.95

SPEAKERS

Please add £1.50 per pair P. & P. & Ins.

Amstrad 138 £13.90
Wharfedale Denton 2 £28.40
Wharfedale Linton 2 £35.40
Wharfedale Milton 2 £45.90
Wharfedale Dovedale 3 £59.80
Celestion Ditton 120 £38.40
Celestion Ditton 15 £51.00
Celestion Ditton 25 £84.50
Celestion County (new prod.) £34.50
Goodmans Double Maxim £47.40
Goodmans Mezzo 3 £45.90
Goodmans Magister £82.95

Special bulk purchase

£2.90*

Plus 65p P. & P. & Ins.
Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25; 2025TC; 3000; AT76; 2000; 2500; 3500; 5100; 1025; SL65B; Also for McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B*. £3.90 + 65p. P. & P. & Ins.

Also finished in walnut to match Japanese equipment—at no extra.

CARTRIDGES

Please add 10p P. & P. & Ins.
Goldring G850 £3.35
Goldring G800 £4.70
Goldring G800E £7.50
Goldring G800 Super E £14.15
Shure M3D £3.70
Shure M44E £4.75
Shure M55E £5.55
Ortofon SL15 £15.85
Sonotone 9TANC £1.35

HOW TO MAKE THE DIGITRONIC SOLID-STATE DIGITAL CLOCK USING JUST 30 BITS

Full instructions in this month's issue for versions with either four or six figures

PLUS A

FREE 6" x 5" TRANSFER SHEET OF LABELS FOR AUDIO EQUIPMENT

Easy to apply and ideal for an impressively professional finish

And many other constructional features, including directions for making an *electronic maze* that will keep everyone amused for hours. Its cost? Around £2.

All in the March issue on sale now 20p

PRACTICAL WIRELESS



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

EEB. 33

BLOCK CAPS please

**FOR
RAPID
SERVICE**

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

TRANSFORMERS

all with 0-250 Volt primaries
Miniature
 MM6 6V, 500mA + 6V, 500mA
 MM12 12V, 250mA + 12V, 250mA
 MM20 20V, 150mA + 20V, 150mA
 £1.29 plus 13p p. & p.
L.T.
 LT1 6 3V, 1.5A—75p plus 18p p. & p.
 LT2 6 3V, 3A—87p plus 26p p. & p.
 LT3 12V, 1.5A—87p plus 26p p. & p.
 LT4 12V, 3A—£1.32 plus 30p p. & p.
LT5 9.0-9V, 0.5A—75p plus 21p p. & p.
 LT6 12.0-12V, 1A—95p plus 26p p. & p.

Multi-tapped
 MT30/2 0-12-15-20-24-30V, 2A—
 £1.95 plus 30p p. & p.
 MT60/1 0-5-20-30-40-60V, 1A—
 £2.10 plus 30p p. & p.
 MT60/2 0-5-20-30-40-60V, 2A—
 £2.95 plus 34p p. & p.

Charger
 CT/01 1A—£1.05 plus 26p p. & p.
 CT/02 2A—£1.30 plus 30p p. & p.
 CT/03 4A—£1.60 plus 30p p. & p.
 Secondaries—0-5-11-17V.

Speaker Matching 3 B-16 Ω
 Example: 16 Ω speaker to 8 Ω
 amplifier. 90p plus 20p p. & p.

SEMICONDUCTORS, etc.

Zeners—400mW, 15p; 1.5V, 22p
 L.D.R.—ORP12, 56p
 S.C.R.—400 P.I.V., 3.0A, 57p
 Bridge rectifier—40 P.I.V., 1.5A,
 50p
 Bridge rectifier—200 P.I.V., 2.0A,
 50p
 Transistor sockets—7p
 D.I.L. I.C. sockets—14 pin, 20p;
 16 pin, 20p
 IN4001—50 P.I.V., 1.0A, 6p
 IN4002—100 P.I.V., 1.0A, 7p
 IN4003—200 P.I.V., 1.0A, 8p
 IN4004—400 P.I.V., 1.0A, 9p
 IN4005—600 P.I.V., 1.0A, 12p

ALUMINIUM BOXES

with lids and screws

Type	L.	W.	O.	Price p. & p.
GB7	5 1/2	2 1/2	1 1/2	38p 15p
GB8	4 1/2	4 1/2	1 1/2	38p 15p
GB9	4 1/2	2 1/2	1 1/2	38p 13p
GB10*	5 1/2	4 1/2	1 1/2	44p 18p
GB11	4 1/2	2 1/2	2 1/2	38p 13p
GB12	3 1/2	2 1/2	1 1/2	33p 13p
GB13	6 1/2	4 1/2	2 1/2	52p 18p
GB14	7 1/2	5 1/2	2 1/2	63p 18p
GB15	8 1/2	6 1/2	3 1/2	81p 26p
GB16	10 1/2	7 1/2	3 1/2	92p 26p

* These sizes fit standard veroboards

EQUIPMENT CASES

in plain aluminium with sloping front panel.
Type H. W. O. Price p. & p.
 SF1 2in 5 1/2in 2 1/2in 45p 12p
 SF2 2in 7 1/2in 3 1/2in 60p 16p
 SF3 2in 9 1/2in 4 1/2in 75p 19p
 Stove-enamelled silver-grey hammer finished, 25p extra.

CONSOLE CASES

in plain aluminium, ideal for mixers, instruments, etc.
Type W. A B C O Price p. & p.
 GB20 8 9 3 1/2 3 £1.42 30p
 GB21 10 9 3 1/2 3 £1.58 30p
 GB22 12 9 3 1/2 3 £1.72 30p



VEROBOARD

Size	0.1 matrix	0.15 matrix
2 1/2in x 3 1/2in	22p	16p
2 1/2in x 5in	24p	25p
3 1/2in x 3 1/2in	24p	25p
3 1/2in x 5in	27p	29p
1 7/8in x 2 1/2in	75p	37p
1 7/8in x 3 1/2in	£1	75p

Pins—either size, packet of 36, 18p

ELECTROLYTICS

1µF 450V	10p	1,000µF 25V	27p
2µF 450V	20p	1,000µF 50V	42p
4µF 350V	14p	2,000µF 25V	39p
8µF 450V	17p	2,000µF 50V	53p
16µF 450V	18p	2,500µF 25V	45p
25µF 25V	7p	2,500µF 50V	60p
25µF 50V	10p	3,000µF 25V	48p
32µF 450V	27p	5,000µF 25V	£1.10
50µF 50V	10p	5,000µF 50V	£1.10
100µF 25V	10p	8-16µF 450V	18p
100µF 50V	11p	8-16µF 450V	20p
250µF 25V	14p	16-32µF 450V	27p
250µF 50V	17p	16-32µF 450V	63p
500µF 25V	18p	32-32µF 450V	49p
500µF 50V	25p	50-50µF 350V	38p

MINIATURE ELECTROLYTICS

1µF 63V	6p	47µF 16V	7p
2µF 63V	6p	47µF 25V	6p
3µF 63V	6p	68µF 16V	6p
47µF 63V	6p	100µF 10V	6p
8µF 40V	7p	220µF 16V	7p
10µF 25V	6p	330µF 16V	11p
10µF 64V	7p	470µF 10V	11p
16µF 40V	7p	1,000µF 16V	19p
33µF 16V	6p	1,500µF 16V	23p

CASSETTE OWNERS!

For Philips and similar cassette recorders.
 PU12 Power unit for connection to 12V + or - E car electrical systems, giving 7 1/2V, stabilised output. **£3.25**

PU14 As above but switched for 6V, 7 1/2V or 9V output. **£5.10**

PP75 Main power supply, output 7 1/2V d.c. **£1.95**

All units are complete with cable and plug.

CASSETTES

Top quality British made, low noise, complete with transparent library cases—
 C60—40p; C90—55p; C120—70p

BATTERY ELIMINATORS

suitable for transistor radios and similar light current equipment
 PP8 Input 240V a.c. Output 6V d.c.
 PP9 Input 240V a.c. Output 9V d.c.
 Price £1.50 plus 12p p. & p.

ILLUSTRATED CATALOGUE

Post Free **15p**

CONTROLS, Log. or Lin.

Single, less switch, 15p
 Single, D.P. switch, 24p
 Tandem, less switch, 40p
 5k Ω, 10k Ω, 25k Ω, 50k Ω, 100k Ω, 250k Ω, 500k Ω, 1M Ω, 2M Ω

RESISTORS

Carbon
 All 5%, high-stability, E12 values. 1W, 1p; 1W, 1p; 1W, 4p; 2W, 6p
 Wire-wound
 5W, 10p; 10W, 12p

SWITCHES

Toggle switches, standard size.
 SW20—S.P.S.T. 18p; SW21—D.P.D.T. 23p.
 Push Button, miniature, SW1—13p.
 Wafer switches (rotary)—24p each.
 SW4—1 pole, 12 way. SW5—2 pole, 6 way.
 SW6—3 pole, 4 way. SW7—4 pole, 2 way.
 SW8—4 pole, 3 way.

BONDED ACRYLIC FIBRE

B.A.F. wadding, 18in wide, 1in thick. The ideal lining for speaker enclosures. 30p per yard. p. & p. one yard 12p; each extra yard 4p.

TYGAN top quality loudspeaker covering material. Please send 6p for samples, sizes and prices.


MAGNETIC COUNTERS

Brand new, neat, 48 volt, 5 digit counters. 60p



PLUGS

Car aerial 14p
 Co-axial 9p
 D.I.N. 2 pin (speaker) 10p
 D.I.N. 3 pin 13p
 D.I.N. 4 pin 14p
 D.I.N. 5 pin, 180 13p
 D.I.N. 5 pin, 240 15p
 D.I.N. 6 pin 15p
 Jack, 2 1/2mm unscreened 10p
 Jack, 2 1/2mm screened 8p
 Jack, 3 1/2mm screened 12p
 Jack, 1/2in unscreened 12p
 Jack, 1/2in screened 20p
 Jack, stereo, unscreened 20p
 Jack, stereo, screened 35p
 Photo, plastic top 12p
 Photo, plated metal 10p
 Wander, red or black 3p
 Banana 4mm, red or black 6p

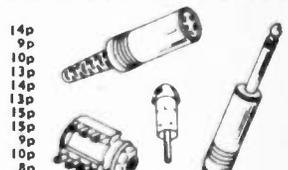

SOCKETS

Car aerial 8p
 Co-axial, surface 8p
 Co-axial, flush 9p
 D.I.N. 2 pin (speaker) 10p
 D.I.N. 3 pin 9p
 D.I.N. 5 pin, 180 9p
 D.I.N. 5 pin, 240 9p
 Jack, 2 1/2mm 10p
 Jack, 3 1/2mm 10p
 Jack, 1/2in unscreened 15p
 Jack, 1/2in switched 17p
 Jack, stereo, switched 24p
 D.I.N. 3 pin 3p
 Photo, single 7p
 Photo, 2 on a strip 7p
 Photo, 3 on a strip 7p
 Photo, 4 on a strip 10p
 Wander, single, red or black 5p
 Wander, twin strip 7p
 Banana 4mm red, or black 6p

CAPACITORS

2 2pF	500V	5/M	7p	0.0027µF	500V	5/M	15p
3 3pF	500V	5/M	7p	0.003µF	500V	Cer.	5p
5pF	500V	5/M	7p	0.0033µF	1,000V	MDC	6p
10pF	125V	P.S.	5p	0.0036µF	500V	5/M	15p
10pF	500V	5/M	7p	0.0047µF	125V	P.S.	5p
15pF	125V	P.S.	5p	0.0047µF	500V	Poly.	6p
15pF	500V	Cer.	4p	0.0047µF	500V	5/M	20p
18pF	500V	5/M	7p	0.0047µF	1,000V	MDC	6p
22pF	125V	P.S.	5p	0.005µF	100V	Mylar	3p
22pF	500V	5/M	7p	0.005µF	500V	Cer.	3p
25pF	500V	5/M	7p	0.0068µF	125V	P.S.	5p
27pF	500V	Cer.	4p	0.0068µF	500V	5/M	30p
33pF	125V	P.S.	5p	0.0068µF	500V	Poly.	6p
33pF	500V	5/M	7p	0.0082µF	125V	P.S.	10p
39pF	500V	5/M	7p	0.0082µF	500V	5/M	30p
47pF	125V	P.S.	5p	0.01µF	18V	Disc	4p
47pF	500V	Cer.	4p	0.01µF	125V	P.S.	10p
50pF	500V	5/M	7p	0.01µF	160V	Poly.	4p
56pF	500V	5/M	7p	0.01µF	250V	M.F.	3p
68pF	125V	P.S.	5p	0.01µF	400V	Poly.	3p
68pF	500V	5/M	7p	0.01µF	500V	Cer.	5p
75pF	500V	5/M	7p	0.01µF	500V	5/M	30p
82pF	500V	5/M	7p	0.01µF	600V	MDC	7p
100pF	125V	P.S.	5p	0.01µF	1,000V	MDC	9p
100pF	500V	Cer.	3p	0.015µF	400V	Poly.	3p
100pF	500V	5/M	7p	0.02µF	100V	Mylar	3p
120pF	125V	P.S.	5p	0.022µF	18V	Disc	3p
150pF	500V	5/M	7p	0.022µF	250V	M.F.	3p
150pF	500V	Cer.	3p	0.022µF	400V	Poly.	3p
180pF	500V	5/M	7p	0.022µF	600V	MDC	7p
200pF	500V	5/M	7p	0.022µF	1,000V	MDC	10p
220pF	125V	P.S.	5p	0.033µF	250V	M.F.	4p
220pF	500V	Cer.	3p	0.033µF	400V	Poly.	4p
250pF	500V	5/M	7p	0.047µF	12V	Disc	6p
270pF	500V	Cer.	3p	0.047µF	160V	Poly.	3p
300pF	500V	5/M	7p	0.047µF	250V	M.F.	3p
330pF	125V	P.S.	5p	0.047µF	400V	Poly.	4p
390pF	500V	5/M	7p	0.047µF	600V	MDC	8p
470pF	125V	P.S.	5p	0.047µF	1,000V	MDC	10p
470pF	750V	Disc	3p	0.1µF	30V	Disc	6p
500pF	500V	5/M	7p	0.1µF	250V	M.F.	4p
560pF	500V	5/M	7p	0.1µF	400V	Poly.	3p
680pF	125V	P.S.	5p	0.1µF	600V	M.F.	4p
680pF	500V	5/M	7p	0.15µF	1,000V	MDC	14p
820pF	500V	5/M	7p	0.15µF	250V	M.F.	5p
0.001µF	100V	Mylar	3p	0.22µF	160V	Poly.	6p
0.001µF	125V	P.S.	5p	0.22µF	250V	M.F.	5p
0.001µF	400V	Poly.	3p	0.22µF	400V	Foil	10p
0.001µF	500V	5/M	7p	0.22µF	1,000V	MDC	15p
0.001µF	500V	Cer.	3p	0.33µF	250V	M.F.	8p
0.001µF	1,000V	MDC	6p	0.47µF	400V	Foil	15p
0.0015µF	400V	Poly.	3p	0.47µF	1,000V	MDC	25p
0.0015µF	500V	5/M	7p	1.0µF	250V	M.F.	15p
0.0015µF	500V	Cer.	3p				
0.0018µF	500V	5/M	10p				
0.002µF	100V	Mylar	3p				
0.002µF	500V	Cer.	3p				
0.0022µF	125V	P.S.	5p				
0.0022µF	500V	5/M	10p				
0.0022µF	1,000V	MDC	6p				

Note: — silver mica 1% tol.
 5/M = polystyrene 2% tol.
 MDC—a.c. rating = 300V.
 M.F.—Mullard min. foil.
 Cer.—ceramic.


MAIL ORDERS. Some items have a post and packing charge shown against them. Where p. & p. is not shown the charge is 12p for any selection. When both classes of goods are ordered the charge is 12p plus any p. & p. charges shown. (Overseas extra.) Telephone 01-692 4412

Everyday Electronics Classified Advertisements

SOUND SUPPLIES

(Electronics) Co. Ltd.
P.A. EQUIPMENT, Marshall amps, instruments and guitars, etc. TOA and Eagle amps and accessories. Reslo mics, etc.
COMPONENTS. Resistors, capacitors, plugs, sockets, cables, audio leads, semiconductors, valves, vero board, etc., for the constructor. Power packs and car droppers for the cassette recorder or radio.
S.A.E. for list and enquiries. P.A. list 15p.
12 Smarts Lane, Loughton, Essex
Tel. 01-508 2715 Closed all day Thursday

INTER-LOCKING PLASTIC STORAGE DRAWERS

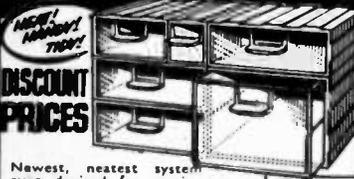

NEWEST, NEATEST SYSTEM EVER DEvised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.
SINGLE UNITS (5" 2 1/2") £1.35 Dozen
DOUBLE UNITS £2.25 Dozen
TREBLE (3D) £1.35 for 8
DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.65 for 8 extra large size (6D1) £3.30 for 8

PLUS QUANTITY DISCOUNTS! Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £. Pack/Post./Carr.: Add 35p to all orders under £5. Orders over £5 P/P/C free.

(Dept. EE1), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2
Tel: 01-450 4844

EX COMPUTER PRINTED CIRCUIT PANELS

2 x 4 in. packed with semi-conductors and top quality resistors, capacitors, diodes etc. Our price 10 boards 50p (8p). With a guaranteed min. of 35 transistors—data included.

SPECIAL BARGAIN PACK

25 boards for £1 (25p).
ELECTROLYTICS
10,000µ 75v, 33,000µ 40v, 4 1/2 x 2 1/2 in. dia., 25,000µ 25v, 20,000µ 30v, 8,000µ 55v, 4 1/2 x 3 in. dia. 50p (12p), 15,000µ 15v, 4 1/2 x 2 in. dia. 20p (10p), 2,000µ 25v wire ended, 3 x 1 in. dia. 15p (5p) or 12 for £1.50 (15p).

250 MIXED CAPACITORS 60p (8p)
250 MIXED RESISTORS 60p (8p)
3A STUD RECTIFIERS, 100 p.i.v.

4 for 50p (5p)
ASSORTED RELAYS 8 for £1 (25p)
SUB MIN. CO-AX PLUGS & SKTS. 4 pairs 50p (5p)

MINIATURE GLASS NEONS 12 for 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES, MIXED 8 for 50p (8p)

PAPST EXTRACTOR/BLOWER FANS 100 cfm 4 1/2 x 4 1/2 £3.50 (28p)

QUARTZ HALOGEN BULBS 12v 55w 50p (5p)

Postage and package for each item shown in brackets.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8.

01-478 8499

MINI MAINS PACK KIT. Safe double wound mini transformer, silicon rects., 1,000µF smoothing. Delivers 9V d.c., 120 mA. Components with data sheet; pack buildable to size of PP6, etc., battery. £0.90 + U.K. post 5p. By mail only from **AMATRONIX LTD.**, 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

FOR ALL YOUR Electronic Component requirements. Send for free list to **B.C. Electronic Supplies**, 7 Regent Road, Huddersfield HD1 4NR.

COMPUTER PANELS 5-BC108, Diodes, 4—50p (10p). Large panels 9" x 7 1/2". Long lead trans. and Comps. £4. 10 Trans 25p (10p) £45. 16 Trans. 40p (10p). Wire ended neon 10—45p (8p), 20—75p (8p). Silicon diodes 650V 1 1/2 amp. on tag boards 10—30p (5p). 22 way mains stepping switch with reset 80p (15p).

7lb assorted components £1.50
2lb assorted computer panels £1.50

J. W. B. RADIO,
75 HAYFIELD ROAD, SALFORD 6, LANCs.
Postage in brackets. MAIL ORDER ONLY

Versatile

10 in ONE



MINI-LAB Comprising

- AC & DC Voltmeter ● Audio Generator
- Ohm Meter ● Resistance Substitution
- Capacitance Substitution ● DC Ammeter
- Battery Supply ● RF Signal Generator ● RF Field Strength Indicator

This new, unique instrument combines all you need for testing. Guaranteed, money back if not satisfied.

£11.25

+25p. p&p

Cash with order or send s.a.e. for illustrated data sheet to:

J. H. ASSOCIATES LTD. (Dept. EE)
Cricklefield Lane, Bishop's Stortford, Herts.

EXPRESS COMPONENTS

17 Albert Sq. London E15 1HJ.

BETA

FUZZ-TREBLE

Ready built and tested
COMPONENT BOARD
for this E.E. project.

£3.25

£1.50 (Less T1)

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide, S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

EDUCATIONAL

FREE



TO ENGINEERS

Whatever your age or experience you must read **New Opportunities**. It describes the easiest way to pass A.M.S.E., A.M.I.M.I., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering: Mechanical, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book.

Send for your copy today—FREE!
B.I.E.T. BEE2, (CX), Aldermaston Court,
Reading, RG7 4PF

Accredited by the Council for the
Accreditation of Correspondence Colleges

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

TECHNICAL TRAINING in Radio, TV & Electronics thro' world-famous ICS. For details of proven home-study courses write: ICS (Dept. 731E1), Intertext House, London SW8.

SITUATIONS VACANT

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators
Training Centre
P11/Oxford House
9-15, Oxford Street, W.1.
Telephone: 01-734 2874
127, The Piazza, Dept.
Piccadilly Plaza, Manchester 1.
Telephone: 061-236 2935

MISCELLANEOUS

WORLD RADIO TV HANDBOOK 1973, £2.80. Fortnightly World Radio Bulletin, £3.13 (ask for sample copy). How to Listen to the World, £1.90. Confidential Frequency List; stations' QSL policies, etc., £1.70. P&P 10p per book; deliveries first class. David McGarva, Box 114N, Edinburgh EH1 1HP. Giro account 17 412 0001.

SINCLAIR AMPLIFIERS. (p & p 75p) Project 60: S60+Z30's+PZ5 £14.20; S60+Z30's+PZ6 £16.20; S60+Z50's+PZ8+Trans, £20.50; Tuner £15.50; AFU £4.10; 605 £17.50; SAE for separate module list. 2000 £20.25; 3000 £28; 2/3000 tuner £28.80; IC-12 £1.85 (p/p free); Neoteric £43; Executive calculator £55. Mail order or callers, Econsales, 9 Sherborne Road, Peterborough. (0733-60238).

RADIO & TELEVISION AERIAL BOOSTERS £2.95p, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50, carr. £1.50p. S.A.E. for 3 leaflets. **VELCO ELECTRONICS**, Bridge Street, Ramsbottom, Bury, Lancs.

PSYCHEDELIC MINI-STROBE

A very POWERFUL, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/receptor unit, printed-circuit-board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours. A veritable FLICKERING FASCINATOR! Adjustable flash-rate.

GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!

SEND £1.95 for YOUR MINI-STROBE.

To: Boffin Projects, 4 Cunliffe Road, Stoneleigh, Ewell, Surrey.

MUSICAL MIRACLES

KITS to build quality accessories:—

WAA-WA A all parts, electronic & mech. £2.95
FUZZORAMA quality fuzz box £4.75 P&P 20p.
BASS PEDAL 16' and 8' tones £35

BUILD A SYNTHESIZER OR AUTO RHYTHM from Dewtron professional modules

Cat. 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AR

KITS BUILT

Radio, Hi-Fi, Test Gear, etc.

Also equipment built to published designs or your specification.

A. Woodrow, 31 Crowland Walk, Morden, Surrey.

AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS

because this Ministry Approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW
S.A.E. for details

To: BOFFIN PROJECTS, DEPT. KEE, 4 CUNLIFFE ROAD, STONELEIGH, EWELL, SURREY.

YATES ELECTRONICS (FLITWICK) LTD

DEPT. E.E., ELSTOW STORAGE DEPT.
KEMPSTON HARDWICK, BEDFORD.

C.W.O. PLEASE. POST AND PACKING, PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request 10p stamp appreciated.

OPEN ALL DAY SATURDAYS

RESISTORS

½W Iskra high stability carbon film—very low noise—capless construction.
½W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. ½W 2% Electroil TR5.

Power watts	Tolerance	Range	Values available	Price	100+
½	5%	4.7Ω-2.2MΩ	E24	1.0p	0.8p
½	10%	3.3MΩ-10MΩ	E12	1.0p	0.8p
½	2%	10Ω-1M	E24	3.5p	3.0p
½	10%	1Ω-3.9Ω	E12	1.0p	0.8p
½	5%	4.7Ω-1MΩ	E12	1.0p	0.8p
4	10%	1Ω-10Ω	E12	6p	5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ½W, lin ½W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELTON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

TRANSISTORS

AC107	15p	AF124	22p	BD131	75p	OC26	45p	2N3702	13p
AC126	12p	AF125	20p	BD132	75p	OC28	50p	2N3703	12p
AC127	12p	AF126	20p	BD133	75p	OC35	50p	2N3704	13p
AC128	12p	AF127	20p	BF115	25p	OC42	12p	2N3705	12p
AC131	12p	AF139	32p	BF173	20p	OC44	12p	2N3706	11p
AC132	12p	AF178	32p	BF177	28p	OC45	12p	2N3707	12p
AC176	12p	AF180	40p	BF178	32p	OC70	12p	2N3708	10p
AC187	22p	AF181	40p	BF179	32p	OC71	12p	2N3709	11p
AC188	22p	BC107	9p	BF180	32p	OC72	12p	2N3710	11p
AD140	50p	BC108	9p	BF181	32p	OC81	12p	2N3711	11p
AD149	45p	BC109	9p	BF194	15p	OC82D	12p	2N4062	12p
AD161	33p	BC147	13p	BF195	15p	2N2904	20p	40360	35p
AD162	36p	BC148	13p	BF197	15p	2N2926G	9p	40361	35p
AF114	20p	BC149	13p	BF200	32p	2N2926P	9p	40362	40p
AF115	20p	BC157	14p	BFY50	20p	2N2926Y	9p	40408	40p
AF116	20p	BC158	14p	BFY51	20p	2N2926G	10p	ZTX302	15p
AF117	20p	BC159	14p	BFY52	20p	2N3054	58p	ZTX500	15p
AF117	38p	BC187	22p	BU105	225p	2N3055	60p	ZTX502	20p

ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

LINEAR IC's (DIL)

747 85p
741 28p

DIL SOCKET

14 and 16 pin
16p

DIODES RECTIFIER

BY127	1250V	1A	12p	OA85	7p
BZY10	800V	6A	25p	OA90	5p
BZY13	200V	6A	20p	OA91	5p
IN4001	50V	1A	7p	OA202	7p
IN4004	400V	1A	8p	IN4148	5p
IN4007	1000V	1A	12p	BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in=25p; 12in x 2½in=10p; 9in x 2in=7p.

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log, or lin, 40p.
DUAL GANG, 10K + 10K etc. log, or lin, 60p.
KNOB FOR ABOVE 12p.
FRONT PANEL 65p
18 Gauge panel 12" x 4" with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA10555	15p
VA10665	15p
VA1077	15p
VA1005	15p
VA1026	15p
VA1033	15p
R53	£1.35

COMPACT CASSETTES

C90 65p C120 85p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2½p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3p, 0.047µF, 0.068µF, 0.1µF, 4p, 0.15µF, 6p, 0.22µF, 7½p, 0.33µF, 11p, 0.47µF, 13p.
160V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 3p, 0.1µF 3½p, 0.15µF, 4p, 0.22µF, 5p, 0.33µF, 6p, 0.47µF, 7½p, 0.68µF, 11p, 1.0µF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 3p, 0.033µF, 0.047µF, 0.068µF 3½p, 0.1µF, 4p, 0.15µF, 0.22µF, 5p, 0.33µF, 6½p, 0.47µF, 8½p, 0.68µF, 11p, 1.0µF, 13p. 1.5µF, 20p, 2.2µF, 24p.

MYLAR FILM CAPACITORS 100V,

0.001µF, 0.002µF, 0.005µF, 0.01µF, 0.02µF

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD 015/6/7 RANGE

REPLACES C426, C487 RANGES

(µF/V): 1.0/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/40, 47/4, 47/10, 47/25, 47/40, 47/63, 68/6.3, 68/16, 100/4, 100/10, 100/25, 100/40, 150/6.3, 150/16, 150/25, 220/4, 220/16, 330/4, 330/10, 470/6.3, 5p each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/6.3, 1000/4, 9p, 100/63, 150/63, 220/40, 470/25, 680/16, 1000/10, 1500/6.3 12p, 220/63, 470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 15p. 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 18p.

SOLID TANTALUM BEAD CAPACITORS

0.1µF 35V	2.2µF 35V	22µF 16V	12p
0.22µF 35V	4.7µF 35V	33µF 10V	
0.47µF 35V	6.8µF 25V	47µF 6.3V	
1.0µF 35V	10µF 25V	100µF 3V	

ELECTROLYTIC CAPACITORS Miniature P.C. mounting 5p each
(µF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

VEROBOARD

0-1

0-15

2½ x 3½

2½ x 5

3½ x 3½

3½ x 5

17 x 24

17 x 34

17 x 5 (plain)

17 x 34 (plain)

24 x 5 (plain)

24 x 34 (plain)

Pin insertion tool 52p

Spot face cutter 42p

Pkt. 50 pins 20p

JACK PLUGS AND SOCKETS

Standard screened 18p 2.5mm insulated 8p

Standard insulated 12p 3.5mm insulated 8p

Stereo screened 35p 3.5mm screened 13p

Standard socket 15p 2.5mm socket 8p

Stereo socket 18p 3.5mm socket 8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin

Plug 12p. Socket 8p.

4 way screened cable 15p/metre

6 way screened cable 22p/metre

BATTERY ELIMINATOR £1.50

9V mains power supply. Same size as PP9 battery

LARGE (CAN) ELECTROLYTICS

1600µF 64V	74p	3200µF 16V	50p
2500µF 40V	74p	4500µF 16V	50p
2500µF 50V	58p	4500µF 25V	£1.68
2500µF 64V	80p	5000µF 50V	£1.10
2800µF 100V	£2.60		

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01µF	10p	0.047µF	13p	0.22µF	20p
0.022µF	12p	0.1µF	16p	0.47µF	22p

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI £2.00

The GDI is the World's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as industrial containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.


POLYSTYRENE CAPACITORS

160V 2½p to 1,000pF E12 Series values. 4p each

PRINTED BOARD MARKER 97p

Draw the planned circuit on to a copper laminate board with the P.C. Pen, allow to dry and immerse the board in the etchant. On removal the circuit remains in high relief.

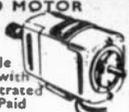PARVALUX TYPE SD2. 200/250 VOLT A.C. D.C. HIGH SPEED MOTOR
Speed 9,000 r.p.m.
approx. or 3,200 r.p.m. if used with built in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE: £3.99 Post Paid
Other models available on request.



600 WATT DIMMER SWITCH



Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3 inc. P. & P.

REVERSIBLE SPLIT PHASE MOTOR
250 r.p.m. 100-115/210-240V AC. 2in. x lin. Ideal for rim-drive motors, display etc. Extremely powerful for size. 75p. post paid. (Including small capacitor.)

METER BARGAINS

Balance/level meter
Size 1 1/2" x 1 1/2" x 1/2" deep 75p post paid.

AMMETERS NEW!

DC amps 1, 5, 15, 20. AC Amps 1, 5, 10, 15, 20. £1.75 incl. P. & P.
0-300V a.c. £1.90 incl. P. & P.



50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £8.05 post paid.

CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instruction. £1.75 inc. post.

VENNER Electric Time Switch
200/250V E.P.C. Tested. Manually set 2 on, 2 off every 24h. Overridable switch: 15A £3.45, 20A £3.95, 30A £4.15. post paid. Also available with solar dial ON dusk, OFF dawn. Price as above.



RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Light or Super Hy-Light Strobes in either 1, 2, 3, 4 sequence; 2+2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18.75 post paid. Send S.A.E. for details.

BIG BLACK LIGHT

450 Watt. Mercury vapour ultra violet lamp. Outer bulb designed to absorb visible light and to transmit u.v. rays. Extremely compact and powerful source of u.v. innumerable industrial applications, also ideal for stages, discos, etc. P.F. Ballast is essential with the bulbs. Price of matched ballast & bulb £16.30 post paid. Spare bulb £7.30 post paid.



BLACK LIGHT FLUORESCENT U.V. TUBES £1.45
4 ft. 40 watt. Price £5.80 incl. P. & P. (For use in standard bi-pin fluorescent fittings). MINI 9 inch 6 watt black light U.V. tube.

COLOUR WHEEL PROJECTOR

Complete with oil filled colour wheel, 100 watt lamp, 200/240 V A.C. Features extremely efficient optical system. £18.85 post paid



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/140V a.c. 50/60 OUTPUT VARIABLE 0.260V from 1/2 to 50 amp stock. SHROUDED TYPE

1 amp, £7.00 2-5 amp, £8.05
5 amp, £11.75
10 amp, £23.50 20 amp, £49.00
15 amp, £28.90 25 amp, £58.00
37 amp, £82.00 50 amp, £98.00



Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 3 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 250 mA; 1.5 kΩ, 230mA; 2-5 kΩ, 2-5 kΩ, 1.65mA 5 kΩ, 140mA. Diameter 33in Shaft length 3in, dia. 1/4in. All at £1.73 post paid.
50 WATT. 1/5/10/25/50/100/250/500/1k/1.5k/2-5k/5kΩ. All at £1.23 post paid.
25 WATT. 10/25/50/100/250/300/500/1k/1.5k/2-5k/3-5kΩ. All at 98p post paid.

RELAYS New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

1	2	3	4	1	2	3	4
52	3-6	2 c/o	63p	700	12-24	2 c/o	63p
52	4-6	4 c/o	78p	700	6-12	1 c/o HD	50p
52	4-6	6M	63p	700	22-30	6 c/o	75p
150	4-6	2 c/o	63p	700	18-35	2 c/o HD	75p
185	8-12	6M	63p	700	16-24	6M	65p
230	6-12	2 c/o	63p	1,250	24-36	4 c/o	63p
280	9-12	2 c/o	73p	2,500	36-45	6M	63p
410	10-18	4 c/o	73p	2,400	30-48	4 c/o	50p
600	9-18	2 c/o	63p	9,000	40-70	2 c/o	50p
700	10-18	4M 2B	63p	15k	85-110	6M	50p
700	16-24	4 c/o	78p				

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. *Including Base.
12 VOLT D.C. RELAY 140 OHM COIL
Type 1: 3 sets c/o contacts 5 amp. 78p incl. P & P (similar to illustration below).
Type 2: 1 set of c/o contacts 60p incl. P & P.
*DIAMOND H' 230 VOLT A.C. RELAYS
Three sets c/o contacts rated at 5 amps.
Price: 60p post paid (100 lots £40.00 incl. P & P.) (UNUSED)

HONEYWELL PROGRAMME TIMERS

240V A.C. 5 r.p.m. motor. Each cam operating a c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation etc. Also in the field of entertainment, for lights, animated displays, etc.
15 cam motor £6.00 post paid
£5.00 post paid
" " with 15 r.p.m. motor £2.00 post paid
SIMPLE 12 CAM PROGRAMMER with 4 adjustable cams and 8 that may be profiled to individual requirements. Available with 15 or 13 r.p.m. motor £3.75 post paid.



STROBE! STROBE! STROBE!


Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.
EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.35 post paid.
NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. approx. 1/2 the output of Hy-Light. Price £11.00 post paid.
HY-LIGHT STROBE MK III
Designed and produced for use in large halls and utilises a silica tube printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 joule) strobes. £12.90 post paid.
SPECIALLY DESIGNED, FULLY VENTILATED METAL CASE. Including reflector. £4.45 post paid

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe. Incorporating:
● Variable speed from 1-13 flash per sec.
● Reactor control circuit producing an intense white light. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20.75 post paid.
ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Light Kit including reflector £7.45 post paid.
7 inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 66p post paid or post paid with kits.
6 IN COLOUR WHEEL as used for disco lighting effects etc. £5.75 incl. P. & P.

SINCLAIR EQUIPMENT

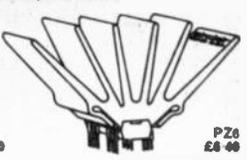IC12 £2.80
Z50 £4.25
PZ5 £3.87
Z30 £3.98
Project 60 tuner £16.80
AFU £4.50
Stereo 80 £7.80



PZ6 £2.40

KITS OF PARTS FOR THE IC12
Includes all parts for the printed circuit and volume bass and treble controls needed to complete the mono version £1.30. Stereo version with balance control £3.00.

POWER UNITS FOR THE IC12
A set of components to construct a 30V, 0.5 Amp power supply £2.27. Also suitable Sinclair PZ5 fully constructed £3.87.


PROJECT 60 KIT £2.50
Our extremely popular kit contains the extra capacitors. DIN plugs and sockets, cables and fuse holder needed to complete Project 60.

S-DECS AND T-DECS

S-DECS £1.44
T-DECS £2.88
M-DEC A £3.00
16 di IC carriers £1.25



SINCLAIR EXECUTIVE CALCULATOR

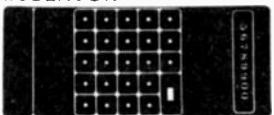

OUR PRICE ONLY £69 (List Price £79).

SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent
Mail order only. Postage 10p per item.
Lists 10p. Official credit orders welcome.

B.H. COMPONENT FACTORS LIMITED

SPECIAL RESISTOR KITS. (1/2W or 1/4W 5% Carbon Film) 10E12KIT, 10 each E12 value, 10ohms-1M. A total of 610. £8.80 net
25E12KIT, 25 each E12 value, 10ohms-1M. A total of 1525. 98-50 net
MULLARD POLYESTER C280 250V. (μF) 0-01, 0-015, 0-022, 0-033, 0-047, 5p, 0-068, 0-1, 0-15, 4p, 0-22, 5p, 0-33, 7p, 0-47, 5p, 0-68, 10p, 1-0, 15p, 1-5, 30p, 2-2, 33p.
MULLARD POLYESTER C280: 100V. (μF) 0-01, 0-015, 0-022, 5p, 0-047, 0-068, 5p, 0-15, 0-22, 4p, 0-33, 5p, 0-47, 5p, 0-68, 1-0, 10p, 400V: (μF) 0-001, 0-0015, 0-0025, 0-0033, 0-01, 5p, 0-015, 0-033, 5p, 0-64/64, 1-6/25, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/64, 125/16, 125/10.
LARGE ELECTROLYTIC: 500/25, 10p, 500/50, 15p, 1000/12, 10p, 1000/25, 2000/12, 2500/12, 15p, 1000/50, 25p, 2000/25, 5p, 2500/25, 5p, 3000/50, 5p, 5000/50, 5p, 2500/50, 5p, 1000/10, 6p.
CERAMIC PLATE, 50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8 (μF) 0-01, 0-015, 0-022, 0-033, 5p, 0-047, 30V, 5p, 0-1, 30V, 4p.
CARBON FILM RESISTORS. 1/2W, 1/4W, 5% 10ohms-2.2M; 1/2W 5% 22Ω-1M, 1p each or 100 for 65p.
METAL FILM RESISTORS. 1W 5% 27Ω-10M 11p each or 100 for 51.
HY-VOLT ELECTROLYTIC: 8/250, 15p, 16/250, 17p, 32/250, 25p, 50/250, 15p, 32/250, 25p, 100/500, 30p.
VEROBOARD 0-1 0-15 CARBON POTS
24" x 5" 25p 85p 5K-2M Log and Lin
24" x 3" 25p 17p single 15p, single
31" x 5" 25p 30p with SW, 84p, dual
31" x 3" 25p 25p 45p
Fin. Plat. 25 5p
2 Pin DIN Plug 15p, 8kt. 10p
3 Pin DIN Plug 15p, 8kt. 10p
5 Pin DIN Plug 180° 15p, 8kt. 15p
Red Panel Neon 240V. 16p
Preset Skeleton Pots 1K-1M 5 for 8p
Neon Bulb 90V, wire ended 5 for 50p
1N4001, 5p, 1N4002, 7p, 1N4008, 5p, 1N4004, 5p, 1N914, 5p, 7400N, 15p, 7401-7410-7430, 15p, 2N706, 10p, 2N514, 8p, BC108, 11p, BPS1, 20p, CWO, pp 10p. Discount £10-10%. The above items are only a few taken from our catalogue which is available free. Money back refund.
Dept. EE, 61 CHEDDINGTON RD., PITSTONE, LIGHTON BUZZARD, BEDS., LU7 9AQ.
Tel.: Cheddington 688446 (STD Code 0296)

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. E.E. 57 Bridgman Road, Chiswick, London, W4 5BB
Phone 01-995 1560 SHOWROOM NOW OPEN MON-FRI.
Personal callers only. Open Sat.
9 LITTLE NEWPORT ST.
LONDON WC2H 7JJ 01-437 0576

Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)



ROAMER EIGHT Mk I


NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost **£6-98** P. P. & Ins. 45p. (Overseas P. & P. £1)


ROAMER SEVEN MK IV

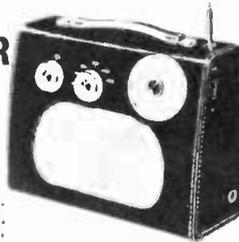

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£5-98** P. P. & Ins. 45p. (Overseas P. & P. £1)


ROAMER SIX

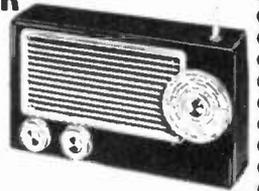

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 25p (FREE with parts).

Total building costs **£3-98** P. P. & Ins. 30p. (Overseas P. & P. £1)


POCKET FIVE

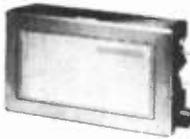

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-29** P. P. & Ins. 23p. (Overseas P. & P. 63p)

TRANSONA FIVE

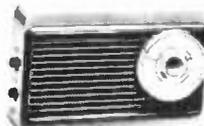


5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—6 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-50** P. P. & Ins. 24p. (Overseas P. & P. 63p)

TRANS EIGHT

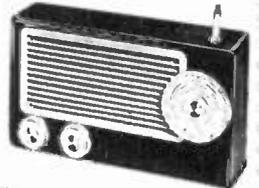

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£4-48** P. P. & Ins. 32p. (Overseas P. & P. £1)

NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

All parts including Case and Plans **£5-50** P. P. & Ins. 32p



(Overseas P. & P. £1)

FULL AFTER SALES SERVICE

- Callers side entrance "Lavelle's" Shop
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367

I enclose £..... please send items marked.

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Parts price list and plans for

Name

Address

(Dept. E.E.17.)

U.K.'s LARGEST ELECTRONICS CENTRES!

HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381
 354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736
 309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963
 303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1BW
ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

BUILD THE TEXAN

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

★ **FREE TEAK CABINET** with complete kits!

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.
HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.
FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).
 Constructional details Ref. No. 21 30p



(As featured in "Practical Wireless" May to August 1972)

SPECIAL KIT PRICE
£28.50 P & P 45p

★ **SLIM DESIGN WITH SILVER TRIM**
 Overall chassis size 14 1/2" x 6" x 2" high

COMPLETE WITH FREE TEAK CABINET
 Designer approved kits distributed by Henry's!

RECORD DECKS

CHASSIS (POST 50p)	
SP25/3 £10.25 HT70	£14.50
MP60 £9.95 MP610	£12.95
AP76 £17.95 GL75	£28.30

PLINTH/COVERS
 (State Model)
 SP25/MP60/610 £3.30 post 40p
 AP76 £4.50 post 40p
CART/PLINTH/COVER
 (Post 70p)
 (HL) MP60/G800H/PC £18.50
 MP610/SCSMD/TPD2/PC £19.95
 AP76/M756SM/PC £32.50
 AP96/M756SM/PC £29.95
 (HL) AP76/G800/PC £28.95
 (HL) SP25/G800H/PC £18.95
 HT70/G800/TPD1/PC £24.50
 (HL) 2025/97AHCD/PC £13.95
 MP60/SCSMD/PC £17.25
 (HL) GL75/G800/PC £29.95
 (HL) GL75/G800/PC £38.95

ULTRASONIC TRANSDUCERS
 Operate at 40Kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.
 £5.90 per pair. Post 10p

HARRIOT TAPE HEADS
4 TRACK MONO OR 2 TRACK STEREO

17" Med. Impedance	£2.00
18" Med. Impedance	£2.00
36" Med.-Low Imp.	£3.50

Erase Heads for above 75p
 '63' 2 track mono—Hi Imp. £1.75
 '43' Erase Head for above 75p

POWER INTEGRATED CIRCUITS
 Plessey SL403D—3 watt with 8-page data, layouts and circuits £1.50 P.C. Board 60p. Heat Sink 14p.
 Sinclair IC12—6 watt with data and circuits £1.80.
 TH9013P—20 watt Power Amp Module £4.57.
 TH9014P—IC Preamp £1.50.
 Data/Circuits for above No. 42 10p

7 SEG & NIXIE TUBES
 (Post 15p per 1 to 6)
 XN3, XN13, GNG 0-9 side view with data, 83p.
 GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
 3015F 7 seg £2 each. £7 per 4 with data.
 12 and 24 hour clock circuits Ref. No. 31 15p.

Miniature Amplifier
 S transistor. 300mW o/p. Fixed volume and sensitivity control, 9 volt operated. £1.75 each P/P 15p.


Quality Slider Controls
 60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K.
 1 meg, Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged, 60p each.

Hi-Fi & Tape Equipment
 Acknowledged as U.K.'s Largest Stockists with Lowest Prices Plus 12 months Guarantee. Write or call for FREE 16 page list (Ref. N. 17)

Transistors - IC's - SCR'S - Rectifiers - Triacs, etc. LATEST BROCHURE Ref. No. 36 on request, or see our earlier page

LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150 TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7.70. Post 28p.
POLISHED CABINETS 150, 150TC 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 ohms) SERIES 6 (Assembled 150 T/C) per pair £16.50. Post 70p
 SERIES 8 (Assembled 450) per pair £18.95. Post 70p

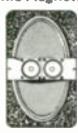

TEST EQUIPMENT

Just a selection!
 SE250B Pocket Pencil Signal Injector £1.90
 SE500 Pocket Pencil Signal Tracer £1.50
 TH133D Robust 2K/Volt £4.55 with case £4.95
 TE15 Grid Dip Meter 440 KHz-280 MHz £13.45
 500 30 K/V Multimeter £9.25
 With leather case £10.50
 200H 20K/V Multimeter £4.20. With case £4.95
 AF105 50K/V Multimeter £8.50. With case £9.50
 U4341 AC/DC Multimeter with transistor tester with steel case £10.50
 TE20D RF Generator 120KHz-500MHz £15.95. Carr. 35p
 TE22D Audio Generator 20Hz-200KHz £17.50. Carr. 35p
 Cl-5 3" Pulse Scope 10Hz-10MHz £39.00. Carr. 50p
 TE65 Valve Voltmeter 28 ranges £17.50. Carr. 40p
ALL NOMBEX MODELS IN STOCK



ML-3 MW/LW TUNER to BUILD

Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". **TOTAL COST TO BUILD £4.85, Post 15p.** All parts sold separately. Leaflet No. 6




"BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning. 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. **TOTAL COST TO BUILD £7.98, p.p. 32p.** (Battery 22p). All parts sold separately—Leaflet No. 2



PA-Disco-Lighting


UK's Largest Range—Write phone or call in. Details and demonstrations on request.
 DJ30L 3 Channel sound to light unit, 3KW. £29.75
 DJ40L 3 channel Mic (built-in) to light, 3kW. £38.75
 DJ705 70 watt Disco amp/mixer. £49.95
 DISCOAMP 100 watt amp/mixer, £66.50
 DJ1055 30 watt Disco amp/mixer, £32.75
 Anti-Feedback Quality Mic., £11.50
 DJ500 50 watt PA Amplifier £44.00
GROUP 300 150 watt rm "Group" Valve Amplifier £86.00
FIBRE OPTICS LIGHTING. — MICS. EFFECTS. PROJECTORS. SPOTS. DIMMERS — STANDS. MIXERS. SPEAKERS.
 Everything for PA — Disco — Lighting.
FREE Stock List Ref. No. 18
 ● PORTABLE DISCOS — DETAILS ON REQUEST
 ● CREDIT TERMS FOR CALLERS

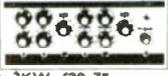

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed. **55p Post Paid (40p FOR CALLERS)**
PLUS! FIVE 10p VOUCHERS

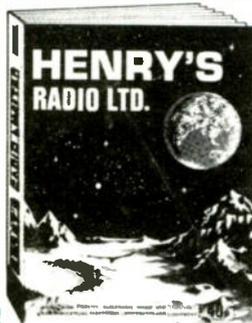Send to this address—HENRY'S RADIO LTD. (Dept. E.E.) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to '303' see above.



BUILD THIS VHF FM TUNER

S TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO
 A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. **TOTAL £6.97, p.p. 20p.** Decoder Kit £5.97.
 Mains unit (optional) Model P5900 £2.47. Post 20p
 Mains unit for Tuner and Decoder P56/12 £3.25. Post 20p



SINCLAIR PROJECT 60 MODULES —SAVE MONEY!

Z30 £3.57; Z50 £4.37
 STEREO 60 PZS £3.97
 £7.97; PZ8 £4.77
 PZ6 £6.37;



PACKAGE DEALS

Post 25p
 2xZ30, Stereo 60, PZS £15.95
 2xZ30, Stereo 60, PZ6 £18.00
 2xZ50, Stereo 60, PZ8 £20.25
 Transformer for PZ8 £2.95
PROJECT 60S KIT £19.95

MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S
 All the parts you need plus Data and Circuits — Get a Catalogue — it's all in there!
 Prices subject to change without notice E. & O.E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H