

An exciting hobby.... for everyone

JUNE 73
15p

everyday electronics

MINI ORGAN




SEMICONDUCTORS...



FREE

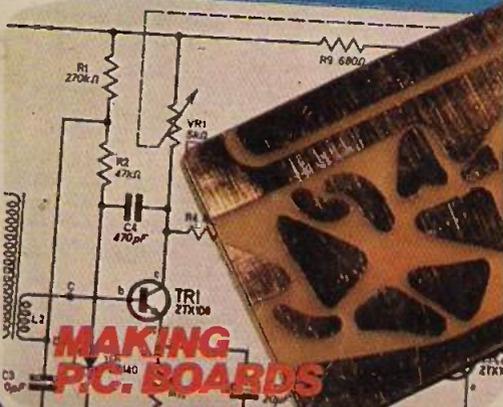ENTRY COMPETITION...
HI-FI SYSTEM AND OVER 100
OTHER PRIZES TO BE WON!!



Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VEF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 86p (FREE with parts). Earpiece with plug and switched socket for private listening 85p extra.

Total building cost

£9.35

P. P. & Ins. 52p

(Overseas P. & P. £1.05)

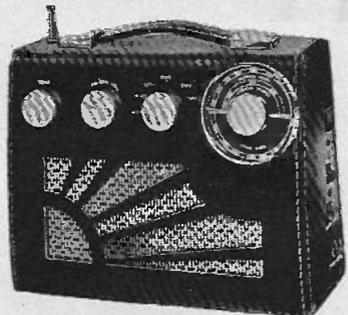

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 85p extra.

Total building cost **£7.68** P. P. & (Overseas P. & P. £1.05) Ins. 47p.


ROAMER SEVEN MK IV



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes. fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 85p extra.

Total building costs **£6.58** P. P. & (Overseas P. & P. £1.05) Ins. 47p.


ROAMER SIX

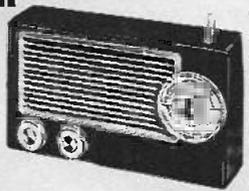

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—5 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 3 1/2in. approx. Easy build plans and parts price list 25p (FREE with parts).

Total building costs **£4.38** P. P. & (Overseas P. & P. £1.05) Ins. 31p

POCKET FIVE

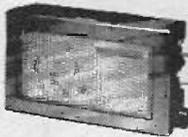

8 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc.

7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 6 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2.50** P. P. & (Overseas P. & P. 65p) Ins. 24p

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2.75** P. P. & (Overseas P. & P. 65p) Ins. 25p

TRANS EIGHT

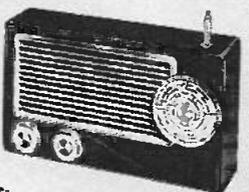

6 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 6 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£4.95** P. P. & (Overseas P. & P. £1.05) Ins. 39p

NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Pins and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

All parts including **£6.05** P. P. & Case and Plans Ins. 33p

(Overseas P. & P. £1.03)

FULL AFTER SALES SERVICE

Callers side entrance "Lavelle's" Shop
Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.
PLEASE NOTE: ALL PRICES NOW INCLUDE VAT

RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367
Reg. no. 788372

I enclose £..... please send items marked.

ROAMER TEN ROAMER SEVEN
ROAMER EIGHT TRANS EIGHT
TRANSONA FIVE ROAMER SIX
POCKET FIVE EDU-KIT

Parts price list and plans for.....

Name.....

Address.....

(Dept. E.E.20.)

* In addition to telling you about our Catalogue each month we would like to bring to your notice one or two items which we believe are **UNIQUE TO HOME RADIO (Components) LTD.**

To start off here is the

'ERSA' SPRINT IRON


We carry complete spares, right down to the last nut and bolt, even spare mains leads. Our price for this desirable object is **only £3-98 plus 18 pence p & p.** Essentially this is a tool for the field service engineer or the handyman and experimenter wishing to make a few quick joints. A constructor building something with a large number of joints might find a conventional iron quicker.

To our knowledge this remarkable iron has been in use on the Continent for over ten years. It has several unusual features:

- 1 Heats up in 10 seconds!
- 2 Weighs only 5 ounces.
- 3 Parts can be changed in seconds.
- 4 Can be used on anything from a transistor upwards.

(A friend of ours used one to repair his water tank. We think this is asking too much!)

The "ERSA" SPRINT IRON is just one of the many exciting things to be found in the famous 250-page Home Radio Components Catalogue. No less than 6,785 electronic components are listed and indexed, and 1,750 items are illustrated. A free bookmark with a useful list of technical abbreviations is included. The catalogue costs 55p plus 22p post and packing. Every copy contains 10 vouchers each worth 5 pence when used as directed. Regularly updated price lists are supplied to you free.

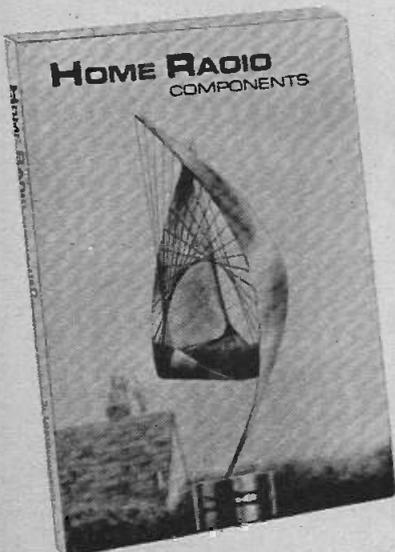

* Send now for catalogue

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....



POST THIS COUPON
with cheque or P.O. for 77p.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses


HOME RADIO (Components) LTD.
Dept. EE 234-240 London Road, Mitcham CR4 3HD

Regd. No.
912966
London

TERMS Retail mail order subject to £1.00 minimum order. Cash with order only.
Trade and educational establishments M/AC on application (minimum £5.00).
Postage 10p inland. 25p. Europe.
GUARANTEE: All goods carry full manufacturer's warranty. Get in touch
today for a complete run-down of devices available from SCS (include SAE).
S.C.S. Components Ltd., P.O. Box No. 26, Wembley, Middlesex HA0 1YY
Registered in London No. 888454




Device of the Month NE540L

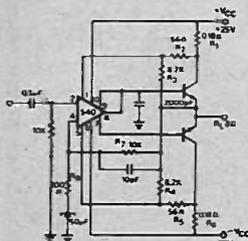

35Watt Amplifier

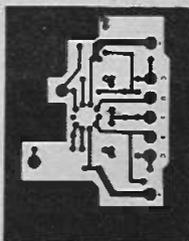The Signetics 540 is a monolithic, class AB power audio amplifier designed specifically to drive a pair of complementary output transistors.



This device features: internal current limiting; low standby current; high output current capability; wide power bandwidth; low distortion - features which make this device ideal for use as an audio power amplifier.

Signetics power driver NE540L
Yours for just

£1.20
+
VAT

including application notes.

Compatible device MCI339P



From Motorola, a monolithic dual stereo preamplifier for low noise

preamplification of stereo audio signals. Just look at some of these features:

- * Low audio noise
- * High channel separation
- * Single power supply
- * High input impedance
- * Built-in power supply filter
- * Emitter follower output

Motorola monolithic dual stereo preamplifier

only
£1.20
+
VAT

including application notes.

A DEXTER DIMMASWITCH

ALLOWS COMPLETE

LIGHTING CONTROL



The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42

All plus 12p post and packing

Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY

5 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO H.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

EX COMPUTER PC PANELS

2 x 4 in. packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (8p).

SPECIAL BARGAIN PACK

25 boards £1 (25p).
Panels with 4 Power transistors sim. OC28 50p (9p)

ELECTROLYTICS

10,000µ 75v, 68,000µ 16v, 4½ x 2 in. dia., 25,000µ 25v, 20,000µ 30v, 5,000µ 90v, 35,000µ 15v, 8,000µ 55v, 4½ x 5.3 in. dia., 50p (12p). 15,000µ 15v, 10,000µ 35v, 4½ x 2 in. dia., 30p (10p). 2,000µ 25v wire ends 15p (5p). 12 for £1.50 (15p).

8 BLACK TOGGLES dpst 50p (8p)
250 MIXED CAPACITORS 60p (8p)
250 MIXED RESISTORS 60p (8p)
150 HI-STAB RESISTORS 60p (8p)
200 Si PLANAR DIODES 50p (5p)

Sub min co-ax plugs & skts 4 prs 50p (5p)

REED RELAYS MIXED 10 for 50p (5p)

MICROS MIXED 8 for 50p (8p)

ASSORTED RELAYS 8 for £1 (12p)

MIN GLASS NEONS 12 for 50p (5p)

10 WAY TERMINAL BLOCKS 10 for 55p (5p)

G-H BULBS 12V 55W 50p (5p)

Postage and packing shown in brackets.

Please add 10% V.A.T. to prices.

(Mail Order only)

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8.
01-478 8499

INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.85 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC.. UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.85 post paid.

MAIL ORDER ONLY.

S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

98a, LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"!! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"!! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £18.50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! * Send quickly, after receiving goods, test 7 days, refund if not delighted. Elegant black & chrome finish, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer and sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques, in the field of space communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover sound's corners of the earth during 24 hours a day including all normal transmissions. V.H.F. FM/USW, AM: LW, MW, SW, gets, locally, local and new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!) Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. SIZE 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities and spares available for years and years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions and circuit diagram. PLUS ultra sensitive earphone for personal listening. **ONLY £18.50** (with mains/battery eliminator £2.00 ext.). **BOX, POST, ETC. 45p—NO MORE TO PAY. *BUT WAIT, for only 75p extra you get the sensational "COMPUTERISED" WORLD TUNING GUIDE** (it enables you to tune, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know what time into the U.K. when broadcast. **NO GUESSING! NO MESSING!**) PLUS Standard "longlife" batteries (Sorry—We cannot change these).

THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?

**THIS FANTASTIC
EARTH SHRINKER**



**YES, 24,901 miles
SHRUNK TO ONLY 14 x 10 1/2 x 4 1/2
inches approx?**

**28 TRANSISTORS
AND DIODES!
WAVEBANDS:**
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW,
LW, USW.)

BATTERY MODEL £19.47 **BOX POST ETC. 55p**
MAINS/BATTERY ELIMINATOR £1.62 extra

BRAND NEW FABULOUS ASTRAD 17
PORTABLE RADIO & COMMUNICATIONS RECEIVER

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS FROM THE FOUR CORNERS OF THE EARTH



"MAGIC EYE" tuning level indicator

*** MUST YOU PAY UP TO £80?**

FIRST TIME EVER!
*NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE! NO MORE GUESSWORK!
INSTANT DATA at your fingertips—enables you to TUNE IN A FLASH to transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £21.60 NOW!**

Fabulous BRAND NEW **SOLID STATE** This equipment's got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



RECOMMENDED RETAIL PRICE £44

OUR PRICE £22.40 **CARR ETC 39p**

WITH REMOTE CONTROL MICROPHONE

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards). We've snapped up 500 magnificent machines. Latest sensation in the world of sound: First-class makers! Fabulous V.H.F. AM/FM Radio AND Cassette Tape Recorder/Players combined and it also runs off standard batteries or mains. (Simply plug in the 220/240V. AC line cord.) Record and play back anything, anywhere! **RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: * Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL * "MAGIC EYE" Visual Battery check/Recording level indicator or built-in automatic Leveler! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in. approx.). Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. **AND** the amazing built-in full circuit V.H.F. AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, city and regional stations in every part of the country, plus B.B.C. National, V.H.F. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £4.5 more for a Car Radio or Car Cassette player ALONE! **OUR FANTASTIC PRICE ONLY £22.40, carr. etc. 39p. NO MORE TO PAY!** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, after receiving goods—test 7 days—refund if not delighted. **BONUS:** Batteries and Cassette Tape 28p extra if req.

SHOPERTUNITIES LTD.

Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7) BOTH OPEN MON. TO SAT. 9 until 6.

FIRST TIME EVER! SAVE £15.21!

BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER



With remote control microphone.

FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26.97!

OUR PRICE £11.76 **POST ETC. 34p**

(*All prices include V.A.T.)

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £11.76!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND **AUTOMATIC LEVEL CONTROL.** No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere). **Amazing performance ensures perfect tapings and superb reproduction!** Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on standard batteries AND 220/240V. AC mains. Separate jacks for remote control microphone, etc. Size 9 1/2in. x 5in. x 2 1/2in. approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Recommended selling price £26.97!) **OUR PRICE ONLY £11.76, post etc. 34p—NO MORE TO PAY!** *Send quickly, after receiving goods test 7 days—refund if not delighted. **BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries. AND microphone stand all for 55p extra, if req.

COMMERCIAL TRAVELLERS Please note: Merchandising office at our Holborn Store. (PERSONAL SHOPPERS WELCOME AT BOTH STORES).

Dept. EE/20, 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Late night shopping Fri. 7).

THE MONEY SAVING CATALOGUE

No. 6
4th printing



96 pages (8½ x 5½) packed with bargains in famous name transistors, resistors, capacitors, pots + I.C. circuits and diagrams; components, accessories, etc + valuable technical data, illustrations, etc. Everything is brand new, to makers' spec.—It's all in our fascinatingly informative catalogue. Yours for 25p. post free (U.K. only) and the voucher included allows you 25p. off when your order is for £5 or more.
SEND FOR YOUR COPY TO-DAY!

WITH **25p**
REFUND VOUCHER

- **DISCOUNTS**
10% on orders £5 or more.
15% on orders £15 or more.
except certain items charged nett
- **POST/PACKING**
Free in U.K. on orders above £2.
10p surcharge on orders under £2.

If you already have No. 6 Catalogue send S.A.E. for latest prices and information list.

ELECTROVALUE

ELECTROVALUE LTD. Reg. No. 1047769 R.O. as below

(Ev. 4) 28 ST. JUDES Rd., ENGLEFIELD Grn., EGHAM, SURREY, TW20 0HB
Hours: 9—5.30: Sat. 1 p.m. Tel: Egham 3603 Telex 264475

Make use of this vital passport to every worthwhile career.

Guaranteed ICS coaching brings you expert home tuition.

All books supplied.


Write for free prospectus to

ICS (Dept. 231M), Intertext House, London SW8

Scorpio Electronic Ignition


Complete kit with comprehensive construction and fault finding data. £10-95 inclusive of postage and VAT. Data 10p. Itemised prices. S.A.E. please.

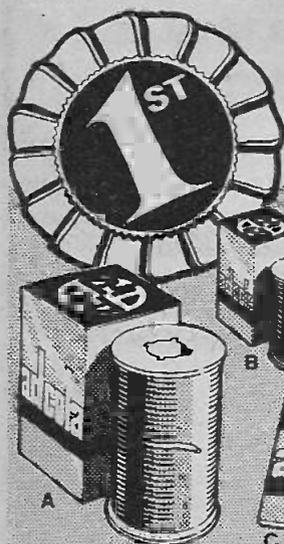AMCEL MAIL ORDER
160 DRAKE ST., ROCHDALE. Tel. 0708 46234



ADCOLA

the champions of soldering equipment

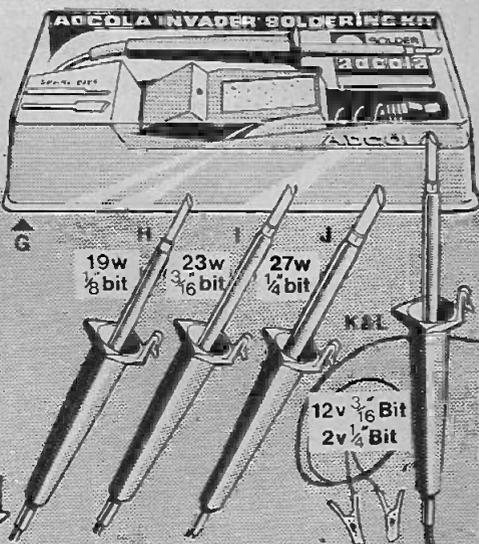

Please send me the following items

PRINT NAME
PRINT ADDRESS

A SOLDER REEL ½ KILO	£1.28	<input type="checkbox"/>
B SOLDER REEL 3 OZ	£0.45	<input type="checkbox"/>
C SOLDER PACK	£0.06½	<input type="checkbox"/>
D DE-SOLDERING BRAID	£0.66	<input type="checkbox"/>
E L686 SOLDERING STATION	£1.88	<input type="checkbox"/>
F L700 STAND	£2.26	<input type="checkbox"/>
G INVADER SOLDERING KIT	£4.39	<input type="checkbox"/>
H L706 INVADER	£2.15	<input type="checkbox"/>
I L646 INVADER	£2.33	<input type="checkbox"/>
J L1076 INVADER	£2.40	<input type="checkbox"/>
K BL646 BATTERY MODEL	£2.99	<input type="checkbox"/>
L BL1076 BATTERY MODEL	£3.12	<input type="checkbox"/>
New Catalogue		<input type="checkbox"/>



ADCOLA PRODUCTS LTD. ADCOLA HOUSE GAUDEN ROAD, LONDON, SW4 6LH
V.A.T. REGD. No. 235 6153 72 REGD. No. 442762

All prices include 10% V.A.T. Please tick items required.

SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES
FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A
'Plastic Power' Driver
Transistors Now Available



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2.95 carr. free

25 WATTS RMS. 7 transistors 7 diodes

SA35 £4.45 carr. free

35 WATTS RMS. 7 transistors 7 diodes

SA100 £10.90 carr. free

100 WATTS RMS. 11 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response 15-40,000 Hz \pm 1dB
Distortion 0.2% at 1 kHz
Loads 4 to 16 ohms
Quiescent current 15 mA
Noise Better than -75 dB
Supply voltage 25-45 volts SA25/35
40-70 volts SA100
Size 4 1/2" x 4" x 1" (SA100)
4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45 Unstabilized supply for 2 SA25/35 £4.90
PU70 Unstabilized supply for one or two SA100 £7.75 carr. 40p
PS45 Stabilized module for 2 SA25's or two SA35's £3.50 carr. free
MT45 Transformer for above, heavy duty £2.85 carr. 20p
MT30 Transformer for unstabilized supply complete with rectifier diodes mounted £3.50 carr. 20p
PS70 Stabilized supply module for one or two SA100's £4.90 carr. free
MT70 Transformer for PS70 £4.90 carr. 40p

ALL MODULES ARE BUILT ON
GLASS FIBRE P.C. BOARD
AND ARE SUPPLIED FULLY TESTED

Mail Orders to Dept. P.E.7.

SAXON ENTERTAINMENTS LTD., 327-331 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.
Telephone 01-684 6385

Hours of Business 9.30 a.m.-5.30 p.m.

TERMS OF BUSINESS—C.W.D.: C.O.D. 35p extra: Cash by registered post, please.

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE £13.90 + 20p carr. or with supply
£18.95 + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

SPECIFICATION

Power output 120 watts into 8 ohms
Freq. response 20-20,000 Hz \pm 2dB
Input sensitivity 200 mV Into 10k
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)
Low distortion parallel push-pull output stage.




NEW 160 watt version £27.90
4 supply

SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

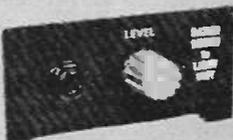Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



£8.90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in Tough Steel case for free mounting or panel fixing. Fully guaranteed.

£19.75 carr. 30p

MONO VERSION £6.50 carr. 20p (As illustrated, S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



£15.80 carr. 30p


SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black face. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE. (N.B.—Stereo only has mic input)

COMPLETE AMPLIFIERS

The CSE 100. £34.90 carr. free

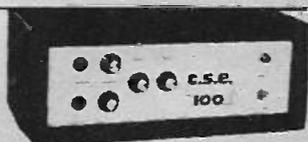This versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.



The SAXON 100 £48.50 carr. free

With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.



LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5.95 carr. 30p. 15" 50W, 8/15 ohm £14.50 carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.

600 Watt 3 colour Light Boxes Smart Resine finish £15 carr free.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use.
D11 DHL IDEAL DISCO MIKE ONLY £9.45 (rrp £11.00).

All prices subject to VAT at standard rate

SEND SAE FOR OUR A.K.G. PRICE LIST. DISCOUNTS ON ALL MICS.

TRADE & EXPORT
ENQUIRIES INVITED

I CHIP RADIO

Ferranti's latest device ZN414-gives results better than superhet. Supplied complete with technical notes and circuits. £1.35 each. 10 for £12.

Hi-Q TUNER COMPONENTS

For experimenting with the ZN414.
KIT NO. 1. Plessey Miniature Tuning Condenser with built in LW switch and 3" ferrit slab and litz wound MW coil. 72p.
KIT NO. 2. Air spaced tuning condenser 6" ferrit rod litz wound MW and LW coils. 94p.
KIT NO. 3. Air spaced TV with slow motion drive 6" ferrit rod, with litz wound LW and MW coils. £1.10.
KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coils. 50p.



12 VOLT 1 1/2 AMP POWER PACK
This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/50 smoothing. Price £2.20 + p. & p. 20p.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 16amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on lead silicon rectifiers and smoothing by 3,000mF. Price £8.33 plus 65p post.

BALANCED ARMATURE UNIT

500 ohm. operates as speaker or microphone, so useful in intercom or similar circuits. 37p each.

MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely 72p each or 5 for £2.50. Send for list of titles. We can't repeat when sold out.

FIRE ALARM BELL

Mains operated. Really loud ring 8" gong. Size approx. 12" x 6" x 4". Suitable outside or inside. Heavy cast case with 1" conduit entry. Made by A.F.A. Operates on 230/240V AC. £4.13 plus 60p.

5 AMP CHANGE OVER CONTACTS 9p each. 15 amp. On/Off 10p each. 15 amp. change over 15p each. **ULTRA sensitive 5 amp. change over 30p each.** 10% off if 10 of a type ordered.

FLEX CABLE SNIP

3 core heavy circular T.R.S. waterproof flex. Ideal for running in the garden to pool or shed. 1.5mm cores (5 amp) 100 yard coils £4.78 plus carriage 75p up to 200 miles. £1—300 miles £1.50—500 miles.

20 WATT INVERTER

Smart and Brown—For van lighting or camping etc. Will light a 2ft. 30 watt standard fluorescent tube from a 12V car battery, current approx. 2A. Very well made unit using die cast chassis. Size 11 1/2" x 2" x 1 1/2". Price £7.15 complete with lamp holders and tube clips.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V. A.C. Good British Make. Unused. Size approx. 1 1/2" x 1". Open construction. Single pole 28p each 10 for £2.50. Treble pole 38p each 10 for £3.47

QUICK CUPPA

Mini Immersion Heater. 350V. 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 20p. 12V car model also available. Same price. Jug heater also available £1.50 plus P. & P. 20p.

DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master inter-com. Simply plug-together. Originally sold at £10. Special snip price £2.85 plus 20p postage.

DIGITAL DISPLAY

Panel mounting unit measuring approx. 3 1/2in. x 1in. x 1 1/2in. deep. Size of the display aperture is approx. 1 1/2in. x 1in. Light up to 0-9. Ext. equipment but unused and in perfect order. Price £1.10 each.

10 AMP DIMMER CONTROLLER. For the control of lighting on stage or in studio or for the control of portable equipment in workshops etc. This has two 15 amp. socket outlets. Each is controlled by a 5 amp. solid state regulator. The overall length is 17", width 2 1/2" and depth 1 1/2". In the end is fitted a master on/off switch indicator, lamp and fuse. Price £3.25.

ZPM—MODULATION MOTOR

Could also be used to open ventilators, doors, valve, damper etc., particularly suitable for remote control. Made by Satchwell. Essentially a reversible geared motor fitted with internal limit switches to stop it at the end of its travel. Size approx. 6" x 6" x 5 1/2" and weighing approx. 10 lbs. This is extremely powerful and would lift a heavy door or open a long line of ventilators. To operate this motor you put the 30 cycle supply through a change over switch. For instance a thermostat with change-over contacts could automatically regulate the temperature in a growing house, chicken hatchery etc. An indicator on the motor graduated wires from this to a volt meter would give a remote indication of the open or close position. A very expensive motor if both direct from Satchwell, our price complete with step down Transformer is £16-15.

0-10 shows the state of open or close. Also internally fitted is a variable resistor, wires from this to a volt meter would give a remote indication of the open or close position. A very expensive motor if both direct from Satchwell, our price complete with step down Transformer is £16-15.

CENTRIFUGAL FAN

Mains operated turbo blower type. Pressed steel housing contains motor and aluminium impeller. Motor is 1/10th h.p. giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2in. wide x 12ins. dia. outlet in trunking 10 1/2" x 4 1/2in. £6.50 plus £1 post and insurance.



FORTYLITE

Fluorescent lighting units with polycater choke and finished white enamel. 40 lms model, ideal kitchen, bedroom, hallway, porch, loft etc. With tube assembled ready to install. £2.20.




PROCESS TIME CONTROLLER

Made by Smiths. Motorised and mains driven in metal case with glass front and chrome surround. Covers a period of 18 hours. During this 18 hours the controlled device can be made to switch on for a period of 15 minutes to 3 hours. Probable cost from Smiths over £6. Special snip price £1.76 plus 20p post and insurance.

THIS MONTH'S SNIP

KETTLE ELEMENTS

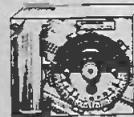Made by the famous A.E.I. Co. Complete with washers and combined firing ring and plug around. Normal 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1 1/2in. (approx.) suitable for G.E.C., Hotpoint, etc. All quick boil 2 1/2 K.W. elements at 240V. Price £1.33p.




24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods for 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. £2.75. post and ins. 23p. Additional time contacts 50p pair.


PAPST MOTORS

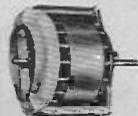Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. £1.68 each. Postage one 23p, two 33p. 230v model £3.20.



RADIO STETHOSCOPE

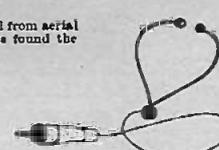Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transformers and all parts including probe tube and crystal earpiece. £2.20—twin stethoscope instead of earpiece 83p extra—post and ins. 20p.



MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500m watt power output 83p. Model 1172 750m watt power output 84p. Model EP9009 4 watt power output 21p. EP9001 Stereo preamp 22. 10% discount if 10 per type or more ordered.

1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a large clear dial, size 4 1/2in. x 3 1/2in., which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch. £1-2 8

DIGITAL COUNTER TIMER

Very stable and reliable crystal controlled circuit. Capable of work in excess of 15 MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case £43.50 or construction data and price list 50p.




TIME SWITCH

Smiths mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars keep pets warm, halve your heating bill, etc. £2.20.



PRESSURE SWITCH

Containing a 15 amp. change over switch operated by a diaphragm which in turn is operated by air pressure through a small metal tube. The operating pressure is adjustable but is set to operate in approx. 10 in. of water. These are quite low pressure devices and can in fact be operated simply by blowing into the inlet tube. Originally designed for washing machines to turn off water when tub has reached correct level but no doubt has many other applications £1.38, each.

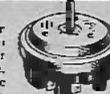

5 PUSH BUTTON SWITCHES

Mains, suitable for audio or R.F. Each switch rated at 250V. 15 amps. 1st (black push button) closes 2 circuits, 2nd (white push button) operates one change-over, 3rd (white push button) operates one change-over, 4th (white push button) opens one circuit. Note: depressed buttons remain down until cleared by the 5th (red button). Further note: It is a relatively easy job to alter the position of the tags thus making the switches suit your circuit. Fitted with 3 white, 1 red and 1 black button. 33p each or 10 for £2.97.

5A 3-PIN SWITCHED SOCKETS

An excellent opportunity to make that bench d/s board you have needed or to stock up for future jobs. This month we offer 6 British made (Herafit) bakelite flush mounting shut tered switch sockets for only 65p plus 20p post and insurance. (20 boxes post free.)



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method of making a quick connection into the car electrical system. 42p each or 10 for £3.75.

EXIT SIGNS

One of our customers has pointed out how easily our box signs can be converted to exit signs. These are illuminated, having a 20W fluorescent lamp with associated control gear. The front is clear plastic. Directly on to this you can stick down the letters available at most stationers. There is room inside the box for a battery and low volt lamp in the case of power failure. Size of sign is 2ft. high x 14in. wide x 5in. deep. Solidly made from sheet steel and hammer finished in enamel. Price £2.85 plus 50p carriage per 200 miles.



SPRING COIL LEADS

As fitted to telephones, 4 core 17p each, 10 for £1.53. 3 core 11p each, 10 for £1.

LARGE PANEL MOUNTING MOVING COIL METERS

Size 5in. x 4in. Centre zero 200-0-200 micro amp. Made by Sangamo Weston. Regular price probably £8. Our price £3.85.

A.C. AMMETER

0-5 amps. flush mounting—moving iron. Ex. equipment but guaranteed perfect £1.65.

CIRCUIT BOARDS

Heavy copper on 3/32 paxolin sheet, ideal for making power packs etc. as sheet is very strong and thick enough to allow copper to be cut away with hacksaw blade. 5in. x 6in. 9p each. 15in. x 9in. 26p.

PHOTO-MULTIPLIER TUBE

Hakuto Co. Ltd., Ref. No. R.450. The regular price is understood to be between £14 and £16 each. We offer these brand new and perfect for £4.50 each.

RESISTANCE WIRE

Kanthal, Nichrome etc. Approx. 2 tons of this coming in—many sizes and grades. If you are a user of this you can save yourself half the cost. Send now for our list. Sorry, not available on small size reels.

PP3 BATTERY CHARGER

Almost 3 times the life can be obtained from PP3 battery if you re-charge it from the mains —this ready to use charger with instructions only 55p.

SUB-MINIATURE MOVING COIL MICROPHONE

as used in behind the ear deaf aids. Acts also as earphone, size only 1in. x 1in. x 1in. Regular price probably £3 or more. Our price £1-10. Note these are ex equipment but if not in perfect working order they will be exchanged.

PROTECT VALUABLE DEVICES FROM THERMAL RUNAWAY OR OVER-HEATING

Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motor and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg.F. or with the dial removed range setting is between 80 to 800deg.F. Price 83p.



KITS FOR PREVIOUS PROJECTS

Unless otherwise stated, kits contain electronic parts only. The case and special items can be obtained locally. Also batteries are not included. Kits may be returned for refund if construction has not been started. We reserve the right to substitute components should deliveries be protracted so as to avoid undue delay.
If reprint of data is required add 10p.

HOME SENTINEL

"Ward off the unwanted intruder"—No elaborate setting up or wiring required. Kit of parts £4.35.

"SNAP" INDICATOR

Press your button first and your opponent is blocked also suitable for Quiz games and reaction testing. Kit of parts £1.10

RECORD PLAYER

Good quality at a reasonable price—good enough for classical records and pop. Kit of parts £6.10.

WINDSCREEN WIPER CONTROL

Wet dirty road—Drizzle—Fog—Smear screen—Scraping wipers—combat these with add-on wiper control. Kit of parts £2.50.

FUZZ BOX

Add weird and interesting effects to guitar playing with this solid state Fuzz box. Kit of parts £2.50.

PHOTOGRAPHIC COLOUR TEMPERATURE METER

Must for colour photographer get the colours right gives quick indication of filters necessary for correction in any light. Can be used with natural or Studio lighting. Kit of parts £3.85.

ASTRON M.W. RADIO

A simple M.W. reflex circuit receiver—easy to build. £2.80.

REMOTE TEMPERATURE COMPARATOR

Measures small temperature changes in liquids or gases—data bank, photographic solution—thermostatically controlled rooms etc. Kit £5.25.

RAIN WARNING ALARM

Keep your washing dry with this automatic alarm device. Kit £2.20.

WAA WAA PEDAL

Add excitement and sound vibration to your music. Kit £3.50.

ELECTROLAUGH

Laughter simulator also useful electronic alarm. Kits of part £2.20.

SOIL MOISTURE METER

Many plants are killed through over-watering—this meter measures soil moisture at root depth—probes can be left permanently beside the plant—indicator remotely housed could monitor several plants. Kit £3.90.

SIGNAL INJECTOR

A useful pocket instrument for fault finding in radios and amplifiers. Kit £1.10.

BABY ALARM

Keep a check on the kids—this device will give you peace of mind as you watch T.V. Kit £4.40.

SIMPLE CALCULATOR

Teaching aid for multiplication—can be used for quick checks. Kit £3.10.

POWER SUPPLY UNIT

Just right for testing low voltage circuits—a simple stabilised supply providing 0-16 volts D.C. continuously variable. Kit £5.20.

METAL LOCATOR

A simple easy to construct self-contained metal locator giving a meter indication of buried metal. Kit £5.00.

AUDIO TONE GENERATOR

Makes electronic music—covers range from 50—2000 Hz. Specifically designed for use with tape recorder. Kit £3.25.

LIGHT TO SOUND CONVERTER

Produces an audio tone—the frequency of which is dependent on the light level. Kit £2.15.

SHAVES INVERTER

Provides 240v 50Hz from 12 volt car battery—gives approx 10 watts which is enough for most shavers. Kit £4.35.

ELECTRONOME

Electronic Metronome with pulse frequency continuously variable from 40—225 beats per minute. Kit £2.15.

THROUGH LENS LIGHT METER

A simple light meter for use with single lens reflex camera. Kit £4.35.

MEDIUM AND LONG WAVE RADIO TUNER

A simple radio tuner for use with almost any amplifier. Kit £3.25.

INFRA RED BURGLAR ALARM

Uses an invisible, reflected beam to detect intruders when beam is intercepted—a power output is switched on for up to one minute. Kit £4.35.

TERMS—10% discount if ten of an item ordered, send postage where quoted—other terms, post free if order for these, over £6.00 otherwise add 20p.

MINI-ORGAN RAIN ALARM

To receive parts for these and other projects featured in this issue send quoted approximate amount any cash adjustment can be made later.


THYRISTOR LIGHT DIMMER

Domestic model for any lamp up to 250 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price £2.85. Industrial model 5 amp module with control knob £3.30.



DISTRIBUTION PANELS

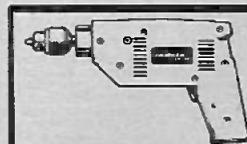Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.50 plus 25p P. & I



PORTABLE ELECTRIC DRILL

Very superior quality made by a famous Dutch toolmaker. Model No. ASM 830. 300w—2 speed 2200/3000. With 1" chuck and chuck key, also separate side handle and hammer facility for dealing with concrete, etc. An equivalent British made drill would cost £15.00.


£10.90—similar model but without the hammer attachment £7.95. Have either model on approval for 7 days.

HORTSMAN 24 HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:-

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice daily	Off
2	All day	Off
3	Twice daily	Twice daily
4	All day	All day
5	Continuously	Continuously

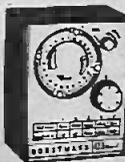Suitable of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling of taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated—Size 3" x 3" x 2" deep as illustrated but less cost. Price £3.30 each.




CD CAR IGNITION

This system which has proved to be amazingly efficient. We offer kit of parts as P.W. Circuit £8.55 plus 20p p. & p. Deluxe model with prepared circuit board £7.95. When ordering please state whether for positive or negative systems.



CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing fux smoke when soldering etc. A real bargain at £2.05.

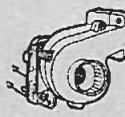

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 6 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices £5p upwards with circuits and technical data of each. Complete parcel only £1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.

GOOD COMPANION

We can now offer these again in L.L. version using Ferranti ZN414 and Mullard AP Modules 1172. Excellent tone wood cabinet. Cabinet size approx. 11in wide x 8in. high x 3in. deep. Complete assembly instructions £5.75 plus 25p post and ins.



MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January 73. All electronic parts £2.20 post paid.



DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.65 plus 13p post and insurance. Made up model also available. £2.50 plus 13p post & p.

KITS FOR PREVIOUS PROJECTS CONT. FROM LEFT HAND COL.

CASSETTE TAPE POWER SUPPLIES

Two units to power a cassette tape player or recorder one from the mains Price £2.50. Two from the car battery—price £1.40.

REACTOMATO

A reaction testing game that can also be a quiz answering indicator. Kit £3.30.

ELECTRONIC MOUSE TRAP

A humane mouse trap—catches them alive so that you can release them in the park. Kit £3.25.

TRANSISTOR TESTER

A rapid tester for checking most transistors—tests transistors in an oscillator circuit and gives audible indication of goodness. Kit £2.15.

RADIO CONTROL TRANSMITTER

A simple single channel transmitter for the radio control of boats, aeroplanes and other models. Kit £6.15.

RADIO CONTROL RECEIVER

A simple channel super regenerative receiver to work in with above transmitter. Kit £3.30.

BIT SAVER

Prolongs life of soldering iron bit—prevents pitting. Kit £1.95.

ICE WARNING DEVICE

A device that can be set to indicate 'ice' conditions or similar temperature levels. Kit £1.55.

AUDIO COLOUR UNIT

Add a colour dimension to your audio equipment. This unit will modulate three lamps in accord with Base—middle and treble notes of any music. Kit of parts £7.20.

U.H.F. T.V. AERIAL

A simple aerial for U.H.F. to reception on your band could improve your reception immensely. Kit £1.65.

DAMP LOCATOR

Easily carried in your pocket this little unit gives visible indication of damp. Kit £1.25.

ENLARGER & EXPOSURE METER

For D.L.Y. photographer £5.00.

EGG TIMER

Simple timer with audible warning. £4.15

WROX NOVELTY

Interesting modern ornamental device £1.65.

CONNECTING WIRE

500m. coils—7 stranded flex copper P.V.C. covered. Available in popular colours—£2.20 per coil, plus 40p post.

5" x 5" P.M. SPEAKER

15 ohm—£1.50. This is a good quality speaker by a famous maker. High flux ideal for use with our Mullard 4 watt amplifier.

3 GANG TUNING CONDENSERS.

500pf each section ideal for transmitter or communications receivers. 81p.

RECTIFIER PANELS

Contain 4 of EN40 (00v) wire ended rectifiers. A glass enclosed fuse, fusing current not known but believed low. Also 4 small wattage resistors at only 18p each, which is less than many shops charge for one of the rectifiers.

16 TRACK TAPE HEAD

For 1" or 1 1/2" tape. This is a brass encased tape head and measures approx. 1 1/2" x 1 1/2" x 1". Resistance is approx. 20-20 ohms. These heads are beautifully made but we have no technical data. Also have only a limited quantity. Price £5.50 each or 10 for £50.

RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are—
2 track record playback heads 57p each.
4 track record playback heads 72p each.
Erase heads are also available separately—
2 track 17p—4 track 28p.

AC CONDENSERS

In addition to the normal uses as motor starters, power factor correction etc. These make very good voltage droppers for working low voltage appliances from mains. The voltage working quoted is AO and condensers are usually suitable for working on DC at 2 1/2 times the quoted AC voltage.

1-5 mfd 400v 28p	5 mfd 570v 86p	12 mfd 250v 77p
2 mfd 440v 23p	6-25 mfd 280v	15 mfd 230v 88p
3-4 mfd 440v 44p		55p
3-5 mfd 250v 33p	8 mfd 250v 55p	20 mfd 275v 99p
		8 mfd 440v 83p

TINIEST AUDIO UNIT

Although only the same size as an Oxo cube these are completely self contained and comprise microphone, 3 transistor amplifier with volume control and battery compartment and finally a dynamic earpiece. All in a plastic case. Made by Arlent (Sold, we believe at over £50 each). These are really hearing aids complete except for the ear tube but we are not selling these as hearing aids only for the micro midget parts they contain. Believed to be in perfect working order but not tested. Price £8.80 each.

J. BULL (ELECTRICAL) LTD.


(Dept. E.E.), 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON.

QUALITY STEREO AT BUDGET PRICES!

The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.6 cm. This compact unit comes complete with on/off switch, volume control, balance, bass and treble controls. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak Input 1 (Cer.) 300mV into 1M Freq. res. 25Hz-25kHz Input 2(Aux.) 4mV into 30K Harmonic distortion Bass control $\pm 12\text{dB}$ at 60Hz typically 0.25% at 1 watt Treble con. $\pm 14\text{dB}$ at 14 kHz

£13.48 free p. & p.

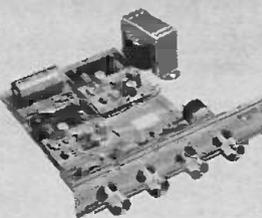

STABILISED POWER

MODULE SPM80

£3.25

AP80 especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. Embodies latest circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, will provide outputs of up to 1.5 amps at 35 volts. Size: 63 mm x 105 mm x 20 mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Ideal for many other applications including—Disco Systems, Public Address, Intercom Units, etc. Handbook available. 10p.

TRANSFORMER BMT80 £2.15 p. & p. 27p.

AL50 HI-FI AUDIO AMP 50W pk 25 (RMS)

0.1% DISTORTION

- Frequency Response 15Hz to 100,000—1dB.
- Load—3, 4, 8 or 16 ohms.
- Supply voltage 10–35 Volts.
- Distortion—better than 0.1% at 1kHz
- Signal to noise ratio 80dB.
- Overall size 63 mm x 105 mm x 13 mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry the AL50 was conceived to fill the need for all your A.F. amplification needs.

FULLY BUILT—TESTED—GUARANTEED.

BRITISH MADE only £3.58 each

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise PNP devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION:

Frequency response
Harmonic distortion
Inputs: 1. Tape head
2. Radio, Tuner
3. Magnetic P.U.

20Hz—20kHz $\pm 1\text{dB}$
better than 0.1%
1.25mV into 50k Ω
35mV into 50k Ω
1.5mV into 50k Ω

Bass control
Treble control
Filters: Rumble (high pass)
Scratch (low pass)

All input voltages are for an output of 250mV.
Tape and P.U. inputs equalised to RIAA curve within $\pm 1\text{dB}$ from 20Hz to 20kHz.

Signal/noise ratio
Input overload
Supply
Dimensions

$\pm 15\text{dB}$ at 20Hz
 $\pm 15\text{dB}$ at 20kHz
100Hz

8kHz
better than +65dB
+26dB
+35 volts at 20mA
292 x 82 x 35 mm.

SPECIAL COMPLETE KIT COMPRISING 2 AL50's,
1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

only £13.15

BI-KITS

Please send all orders direct to warehouse and despatch department Giro No. 388-7006

BI-PAK, P.O. BOX 6, WARE, HERTS

Guaranteed Satisfaction or Money Back



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

EEL 54
BLOCK CAPS please

ELECTROKIT

DRILL SPEED CONTROLLER (E.E. Aug. 1972)
Complete kit includes MK box, plate and socket £2.30

BIT SAVER (E.E. Dec. 1972)
Kit includes all the parts less the Microswitch lever £1.70

MIGHTY MIDGET (P.W. Jan. 1973)
Kit includes all parts less the Battery, the Box or Knob £2.25

"SCORPIO" CAPACITOR DISCHARGE

IGNITION SYSTEM (P.E. Nov. 1971)
Complete kit with construction data £9.50

LIGHT DIMMER:
Complete kit including MK plate and full construction data £2.10

Prices shown do not allow for V.A.T.
PLEASE ADD 10% TO ORDER.

We are offering various other kits published in most other popular Electronics magazines and will be pleased to forward details on receipt of a stamped addressed envelope.

FREE POST AND PACKING WITHIN U.K.

ELECTROKIT

12 Lauderdale Road, London, W.9
Telephone 01-286 0011

MON.-FRI. 9.30-5.30

THURS. 9.30-6.30


MAIL ORDERS: Some items have a postage and handling charge shown against them. Where p. & p. is not shown the charge is 13p for any selection. When both classes of goods are ordered the charge is 13p plus any p. & p. charges shown. (Overseas extra). Telephone 01-692 4412.

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

SWITCHES

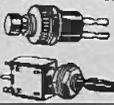Standard toggle switches: SW20—S.P.S.T. 20p; SW21—D.P.D.T. 25p.
Miniature toggle switches: SW18—S.P.S.T. 51p; SW19—D.P.D.T. 64p.
Slider switches, SW3—D.P.D.T. 15p.
Wafer switches (roll) —26p each
SW4—1 pole, 12 way.
SW5—2 pole, 6 way.
SW6—3 pole, 4 way.
SW7—4 pole, 2 way.
SW8—4 pole, 3 way.



PLINTH

to suit Garrard 2025, SP25 etc. Teak finish, complete with Perspex cover. Very attractive appearance. £3-95 plus 55p p. & p.




J-BEAM FM4S AERIAL

4 element, all channel aerial for stereo radio. £6-10 plus 50p p. & p.



PLASTIC BOXES

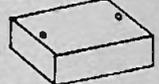for constructional projects. White, with lid and screws. EP1 4½ins x 3ins x 1½ins—37p.
EP2 6ins x 4ins x 2½ins—37p.



BATTERY HOLDERS

for 4 x HF7. Long or short—22p.
Press studs, ready wired PP3 size 10p; PP9 size—13p.



EQUIPMENT CASES

in plain aluminium with sloping front panel.

Type	H.	W.	D.	Price p. & p.
SF1	2in	5½in	2½in	50p 13p
SF2	2in	7½in	3½in	66p 17p
SF3	2in	9½in	4½in	83p 20p



MINIATURE SPEAKERS

2½in 8Ω
2½in 8Ω
2½in 80Ω
All at 68p each.



V.A.T.

PRICES IN THIS ADVERTISEMENT INCLUDE V.A.T.

GROOV-KLEEN

de luxe model 42. £1-83.



STEREO HEADPHONES

Eagle SES. 8Ω
40-16,000Hz.
Complete with cable and stereo jack plug. £3-43 Plus 24p p. & p.



10 WATT AMPLIFIER module

Input: 30mV into 10kΩ for 10W.
40-16,000 Hz.
Output: 3-8-16Ω
Power Supply 12V
£4.70 plus 24p p. and p.



CONSOLE CASES

in plain aluminium, ideal for mixers, instruments, etc.

Type	W.	A	B	C	D	Price p. & p.
GB20	8	9	3½	2	3	£1-56 33p
GB21	10	9	3½	2	3	£1-74 33p
GB22	12	9	3½	2	3	£1-89 33p



ALUMINIUM BOXES

with lids and screws

Type	W.	D.	Price p. & p.
GB8	4in	2½in	42p 16p
GB8*	4in	4in	42p 16p
GB9*	4in	2½in	42p 14p
GB10*	5½in	4in	49p 19p
GB11	4in	2½in	42p 14p
GB12	3in	2in	36p 15p
GB13	6in	4in	57p 20p
GB14	7in	5in	69p 21p
GB15	8in	6in	89p 29p
GB16	10in	7in	£1-00 29p



* These sizes fit standard veroboards

DYNAMIC MICROPHONE UD130HL

This sensitive, quality microphone is uni-directional and is complete with mute switch and 20 feet of cable and plug. 100-12,000Hz. Dual impedance 600Ω and 50kΩ.


£6-60 plus 24p p. & p.

MICROPHONE HOLDER

with swivel (as supplied with the mic. above). Fits most tubular mics. and stands. 57p.

MICROPHONE FLOOR STAND

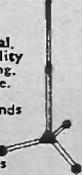Professional, heavy quality with folding, tripod base. Telescopic stem extends to 59ins. Chrome finish. £6-20 plus 45p p. & p.



TAPE ERASER

erases a whole reel of tape in seconds. 240V. A.C. Full instructions. £2-20 plus 22p p. & p.




SCREENED CABLES

Single for mics, audio leads, etc. 5½p yd.
Twin, as above, common screen 10p yd.
Stereo, two cores, individually screened 11p yd.
Four core with common screen 23p yd.
Four core, individually screened 30p yd.
Coiled screened leads, 20 feet long £1-05 each.

PLUGS

Car aerial	15p
Co-axial	10p
D.I.N. 2 pin (speaker)	11p
D.I.N. 3 pin	15p
D.I.N. 4 pin	15p
D.I.N. 5 pin, 180°	16p
D.I.N. 5 pin, 240°	16p
D.I.N. 6 pin	16p
Jack, 2½mm unscreened	10p
Jack, 2½mm screened	11p
Jack, 3½mm unscreened	9p
Jack, 3½mm screened	13p
Jack, ½in unscreened	13p
Jack, ½in screened	22p
Jack, stereo, unscreened	22p
Jack, stereo, screened	38p
Phono, plastic top	5p
Phono, plated metal	13p
Wander, red or black	3½p
Banana 4mm, red or black	6½p

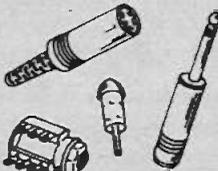

SOCKETS

Car aerial	9p
Co-axial, surface	10p
Co-axial, flush	10p
D.I.N. 2 pin (speaker)	11p
D.I.N. 3 pin	10p
D.I.N. 5 pin, 180°	10p
D.I.N. 5 pin, 240°	10p
Jack, 2½mm	11p
Jack, 3½mm	11p
Jack, ½in unscreened	16½p
Jack, ½in screened	18½p
Jack, stereo, switched	26p
Phono, single	5p
Phono, 2 on a strip	7p
Phono, 3 on a strip	7p
Phono, 4 on a strip	11p
Wander, single, red or black	3½p
Wander, twin strip	7p
Banana 4mm, red or black	6½p

LINE SOCKETS

Car aerial	15p
Co-axial	10p
D.I.N. 2 pin (speaker)	11p
D.I.N. 3 pin	15p
D.I.N. 5 pin, 180°	17p
D.I.N. 5 pin, 240°	17p
Jack, 2½mm	16p
Jack, 3½mm	16p
Jack, ½in screened	54p
Jack, stereo, screened	37p
Phono, plated metal	13p

MINIATURE ELECTROLYTICS

1-0µF 63V 7p	150µF 25V 8p
1-5µF 63V 7p	150µF 40V 13p
2-2µF 63V 7p	150µF 63V 15p
3-3µF 63V 7p	220µF 4V 7p
4-7µF 63V 7p	220µF 10V 7p
6-8µF 40V 7p	220µF 16V 8p
6-8µF 63V 7p	220µF 25V 13p
10µF 25V 7p	220µF 40V 15p
10µF 63V 7p	220µF 63V 22p
15µF 16V 7p	330µF 4V 7p
15µF 40V 7p	330µF 10V 8p
15µF 63V 7p	330µF 16V 13p
22µF 10V 7p	330µF 63V 26p
22µF 25V 7p	470µF 6-3V 8p
22µF 63V 7p	470µF 10V 13p
33µF 6-3V 7p	470µF 25V 15p
33µF 16V 7p	470µF 40V 22p
33µF 40V 7p	680µF 6-3V 13p
47µF 4V 7p	680µF 16V 15p
47µF 10V 7p	680µF 25V 22p
47µF 25V 7p	680µF 40V 26p
47µF 40V 7p	1000µF 4V 13p
47µF 63V 7p	1000µF 10V 15p
68µF 6-3V 7p	1000µF 16V 22p
68µF 16V 7p	1000µF 25V 26p
68µF 63V 13p	1500µF 6-3V 15p
100µF 4V 7p	1500µF 10V 22p
100µF 10V 7p	1500µF 16V 26p
100µF 25V 7p	2200µF 6-3V 22p
100µF 40V 8p	2200µF 10V 26p
100µF 63V 15p	3300µF 6-3V 26p
150µF 6-3V 7p	4700µF 4V 26p
150µF 16V 7p	

TRANSFORMERS

all with 0-250 Volt primaries.

Miniature
MM6 6V, 500mA 4-6V, 500mA.
MM12 12V, 250mA +12V, 250mA.
MM20 20V, 150mA +20V, 150mA.
£1-42 plus 14p p. & p.

LT.
LT1 6-3V, 1-5A—82p plus 20p p. & p.
LT2 6-3V, 3A—96p plus 28p p. & p.
LT3 12V, 1-5A—96p plus 28p p. & p.
LT4 2V, 3A—£1-43 plus 33p p. & p.
LT5 9-0-9V, 0-5A—83p plus 23p p. & p.
LT6 12-0-12V, 1A—£1-04 plus 29p p. & p.

Multi-tapped
MT30/2 0-12-15-20-24-30V, 2A—£2-18 plus 33p p. & p.
MT60/1 0-5-20-30-40-60V, 1A—£2-31 plus 33p p. & p.
MT60/2 0-5-20-30-40-60V, 2A—£2-25 plus 37p p. & p.

Charger
CT101 1A—£1-16 plus 28p p. & p.
CT102 2A—£1-43 plus 33p p. & p.
CT103 4A—£1-76 plus 33p p. & p.
Secondaries 0-5-1-17V.
Speaker Matching 3-8-16Ω
Example: 16Ω speaker to 8Ω amplifier.
99p plus 22p p. & p.

VEROBOARD

Size	0-1 Matrix	0-15 Matrix
2½in x 3½in	25p	18½p
2½in x 5in	28p	28p
3½in x 3½in	28p	28p
3½in x 5in	32p	35p
7in x 2½in	87p	66p
17in x 3½in	£1-18	94p

Spot face cutter—44p
Pins, either size, pack of 36—21p
Edge connectors:
24 way, 0-1—37½p 36 way, 0-1—48½p
24 way, 0-15—37½p 16 way, 0-15—25p

BONDED ACRYLIC FIBRE

B.A.F. wadding. 18in wide, 1in thick. The ideal lining for speaker enclosures. 33p per yard. P. & p. 1yd 14p; each extra yard 4p.

CONTROLS

Log. or Lin.
Single, less switch, 15p
Single, D.P. switch, 26p
Tandem, less switch, 44p
5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ.
1MΩ, 2MΩ

BATTERY ELIMINATORS

suitable for transistor radios and similar light current equipment. Input 240V. A.C.
Output: PP6—6V D.C.; PP9—9V D.C.
Price £1-65 plus 15p p. & p.

CASSETTE OWNERS!

For Philips and similar cassette recorders.
PU12 power unit for connection to 12V + or - E cars, giving 7½V stabilised output—£3-55 + 16p p. & p.
PP75 mains power supply, output 7½V D.C.—£2-15 + 16p p. & p.
Both units are complete with cables and 5 pin D.I.N. plug.

CASSETTE MICROPHONE

Low impedance dynamic with remote control switch. Fitted 2½mm and 3½mm plugs. £2-20 plus 15p p. & p.



ELECTROLYTICS

1µF 450V 21p	1000µF 50V 46p
2µF 450V 22p	2000µF 25V 43p
4µF 350V 15p	2000µF 50V 58p
8µF 450V 18p	2500µF 25V 50p
16µF 450V 20p	2500µF 50V 66p
25µF 25V 71p	3000µF 25V 53p
25µF 50V 11p	5000µF 25V 66p
32µF 450V 30p	5000µF 50V £1-21
50µF 50V 11p	8-µF 450V 20p
100µF 50V 12p	8-16µF 450V 20p
250µF 25V 15p	16-16µF 450V 22p
250µF 50V 19p	16-32µF 450V 69p
500µF 25V 20p	32-32µF 450V 54p
500µF 50V 27p	50-50µF 350V 42p
1000µF 25V 30p	

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N-9 803 1685

7" x 4" LOUDSPEAKER
A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7 1/2" x 4". Impedance: 8 ohms. Flux: 38,000. Max. Freq range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1-80. Free postage on this item.

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL

5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
complete with Fixing Bracket and £6-75 plus 25p P. & F.

S. G. BROWN "DIPLOMAT" MONO/STEREO HEADSET
Finest quality British made Lightweight Headphones. Incorporate ceramic piezo electric transducers.
Specification—Frequency—20-17,600 CPS.
Impedance—Predominantly capacitive, at 001MPFD per earpiece can be regarded as 160K at 1Kcs.
Weight—3.5oz. (98 grams).
Please include 10p per set P.P. A Bargain at £1-50 each set

LOW VOLTAGE AMPLIFIER

Few only at plus 13p P. & F. £1-75
5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.
With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.

"CRESCENT" DIGITAL CLOCK KIT

24 Hour Bixie Digital Clock Kit We Supply:
★ A complete set of components
★ A complete set of easy to follow instructions
★ Printed circuits made to make construction as simple as possible
★ A cabinet and front panel to give a professional finish.
All for the price of the components £22-50 + 50p. P. & F. Please send S.A.E. for more information.

MINIATURE RELAY

6 volt 70 ohm.
Single Pole Changeover.
Approx. size — 1 1/4" x 1" x 1/2".
40p plus 5p P. & F.

LOUDSPEAKER BARGAINS

E.M.I. 460 set 3.8. 15 ohm £3-75 plus 38p. P. & F.
E.M.I. set 8 ohm.
£7-00 plus 38p. P. & F.
MINI LOUDSPEAKERS
2 1/2" (57mm) 8ohm — 50p each
2 1/2" (57mm) 4ohm — 50p each
2 1/2" (57mm) 8ohm — 50p each
Please include 5p. P. & F. up to 3 Mini-Loudspeakers

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your transistor radio, amplifier, or cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug you can select the voltage you require — 6v, 7 1/2v or 9 volts. This means all your transistor power pack applications can be handled by this one unit.
Approx. size: 2 1/2" x 2 1/2" x 3 1/2". OUR PRICE — £2-75p + 10p. P. & F. Same model suitably wired for the Philips Cassette — £3-00 + 10p. P. & F.

ALUMINIUM CHASSIS

Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.
6 x 2 — 41p 12 x 3 — 53p 14 x 9 — 94p
6 x 4 — 46p 12 x 6 — 81p 16 x 6 — 86p
8 x 6 — 53p 12 x 8 — 59p 16 x 10 — 1-08p
10 x 7 — 63p 14 x 3 — 60p
Please send 10p per chassis P. & F.

V.A.T.

From the 1st April 1973 will you please include, on your total amount (Goods, plus Carriage) Value Added Tax at the Standard Rated Rate

INTEGRATED CIRCUIT SOCKETS

A must for the experimenter interested in I.C.s, 14 pin, 16p each. 16 pin, 16p each. Please include 5p P. & F. per 3 sockets.

AL20 5 WATT AUDIO AMPLIFIER

A low cost high quality 5 watt amplifier designed for use in stereo systems, record players and other audio equipment.
Supply Voltage — 9 to 30 volts.
Frequency — 50 to 25 kHz.
Overall Size — 5" x 2 1/2" x 1" approx.
Full technical data and diagrams with each module.
All guaranteed and a bargain at £2-63p plus 5p P. & F.

TRI-VOLT CAR CONVERTER

Enables you to work your Transistor Radio, Amplifier or Cassette etc. from the 12 volt car supply positive or negative earth.
This converter supplies 6, 7 1/2 or 9 volts and is transistor regulated. Approx. size 2 1/2" x 3 1/2" x 2"
Very easy to fit and a real money saving device for £2-50 + 10p. P. & F.

WAFER SWITCHES

1 pole 12 way
2 pole 2 way
2 pole 3 way
2 pole 4 way
2 pole 6 way
3 pole 4 way
4 pole 3 way
18p each. Please inc. 5p P. & F. Up to 3 switches.

POTENTIOMETERS

All types 1" and less diameter.
SINGLES DUAL
5K Log or 5K
10K Lin Less 10K
25K Switch 25K Less Switch
100K 12p ea, 100K 40p.
250K Double 250K
500K Pole 500K each
1M Switch 1M
2M 24p ea, 2M

MINIATURE RELAYS

Brand new range of British made Relays.
Size—1 1/4" x 1" x 1"
All two changeovers with 250V, 1.5A contacts and suitable for fitting on 1m Veroboard.
Type Volts Current Ohms
37/A 12v 17M/A 700 Ω
21/A 12v 28M/A 430 Ω
13/A 6v 33M/A 186 Ω
80p each.
Please include 5p P. & F. up to 3 Relays.

The Pictorial Method

BASIC ELECTRICITY (5vols) ELECTRONICS (6vols) TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

WHAT READERS SAY

I am now an Electrical Inspector with an Electronics firm and I owe my success to your excellent manuals. P.S. Mill Hill

Your simplified technique is really a stepping stone learning for the technician. P.A. Hoddesden

I am well pleased with Basic Electronics which are a great help in my appreciation of circuit functions. T.L. Southampton

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £4-50

BASIC ELECTRONICS 6 parts £5-40

BASIC TELEVISION 3 parts £3-60

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME

BLOCK LETTERS

FULL POSTAL

ADDRESS

POST NOW FOR THIS OFFER!

everyday electronics

PROJECTS...
THEORY.....

PRINTED CIRCUITS

The so-called "printed" circuit board has for long been the standard method of assembly used in industry for large quantity production of electronic equipments. Each printed circuit board is unique, for it comprises a wiring pattern created exclusively for one particular circuit design. Once the master has been proved and tested, mass production is an easy process without any possibility of errors creeping into individual boards. Thus the chance of sub-standard products emerging from a production line is reduced to the very minimum.

Ideal for mass production, yes. But does the printed circuit technique have any special advantages to offer to the private constructor? On the face of it it might well seem that the initial preparatory work is hardly warranted in the case of one single item of equipment, and the average constructor is normally concerned with building just "one off". A high productivity rate is certainly not one of the needs that have to be met.

Yet many private constructors do use this technique on occasions in preference to a standard breadboard or wiring board.

PRACTICAL—AND ATTRACTIVE

Without a doubt the p.c.b. has an increasing value as the size and complexity of the circuitry increases. The danger of wiring errors is considerably reduced, and components are more readily mounted in position since their individual locations are precise and are easily recognised.

Our July Issue will be published on Friday, June 15

Yet there are also other considerations. The finished p.c.b. has a stamp of individuality about it and an appearance which is usually more pleasing to the eye than the regimented pattern of a general purpose wiring board. Though just how important such aesthetic effects are is, of course, a matter for each individual to decide.


One undeniable fact is that a knowledge of the printed circuit technique and some practice in its application are useful and valuable acquisitions for any constructor.

REAL AND IMAGINARY

From an essentially practical matter to something more "in the mind". When one tries to envisage electrons—to say nothing of "holes"—the imagination is indeed put to quite a severe test.

It is not at all essential to understand the principles underlying the operation of a transistor or other semiconductor device in order to use it in an applied circuit. But as likely as not, the newcomer to electronics will eventually find his curiosity getting the better of him, and will begin wondering what makes these tiny devices tick.

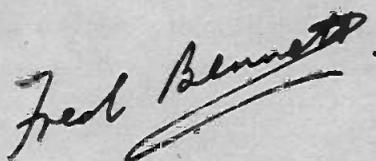Well it is not an easy subject, certainly not at the first encounter. But we feel the series commencing this month will provide a good basic insight into the semiconduction phenomenon—the mechanism which is the real hidden "works" of solid state electronics.



EDITOR F. E. Bennett ● ASSISTANT EDITOR M. Kenward ● B. W. Terrell B.Sc.

ART EDITOR J. D. Pountney ● P. A. Loates ● S. W. R. Lloyd

ADVERTISEMENT MANAGER D. W. B. Tilleard


© IPC Magazines Limited 1973. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Subscription Rates including postage for one year, to any part of the world, £2-35.

Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.

EASY TO CONSTRUCT SIMPLY EXPLAINED

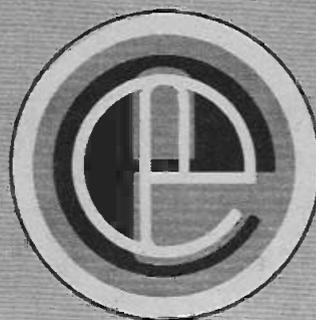

VOL. 2 NO. 6

JUNE 1973

CONSTRUCTIONAL PROJECTS

- | | |
|---|-----|
| MINI ORGAN <i>A portable musical instrument for the family</i> by D. B. Stiles | 294 |
| RAIN ALARM <i>An invaluable aid for the busy housewife</i> by C. Embleton | 310 |
| CASSETTE AMPLIFIER <i>A booster for your cassette tape recorder</i> by R. A. Penfold | 314 |

GENERAL FEATURES

- | | |
|---|-----|
| EDITORIAL | 292 |
| BRIGHT IDEAS <i>Readers construction hints</i> | 299 |
| MAKING P.C. BOARDS <i>Step by step instructions</i> by J. A. Nekrews | 300 |
| COMPETITION <i>Your chance to win a hi fi system</i> | 304 |
| SEMICONDUCTORS <i>Part I—Semiconductor Materials</i> by J. B. Dance | 306 |
| WHAT DO YOU KNOW? RESISTORS <i>Test your knowledge</i> | 313 |
| DEMO CIRCUITS <i>6 The Differential Amplifier</i> by Mike Hughes | 321 |
| READERS LETTERS <i>Your news and views</i> | 325 |
| RUMINATIONS <i>by Sensor</i> | 325 |
| SHOP TALK <i>Component buying and new products</i> by Mike Kenward | 326 |

DO YOU GET THE POINT

See page 304 for full details





mini ORGAN

A three octave "probe" operated portable instrument by D. B. Stiles

"I WANT an electric organ" said my six-year-old daughter. Visions of Wurlitzer and Hammond consoles crossed my sight.

"Would you like to play a guitar?" I asked, thinking of two old guitars in the attic.

"Aunty has an electric organ" she said accusingly.

In conversation with a friend it transpired that his son also aspired to ownership of an "electric organ". The result of these desires is contained in this article in the hope that it may save someone from having to purchase an expensive organ.

BASIC OSCILLATOR

The basis of the Mini Organ, it was decided, should be as simple as possible. One of the simplest oscillators can be made using a unijunction transistor; it has the attraction that the frequency can be altered over a fairly wide range merely by varying the value of one resistor.

The basic oscillator and its waveforms are shown in Figs. 1 and 2. An extensive coverage of the unijunction transistor is not within the scope

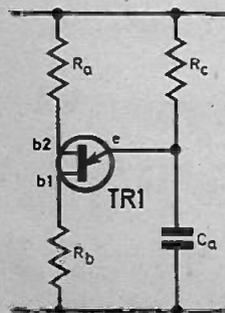



Fig. 1. (left) The basic unijunction oscillator circuit.

Fig. 2 (right) Waveforms associated with the oscillator.

Approximate cost of components including V.A.T.
£4.75 plus case and battery

of this article; suffice it to say that a capacitor charges via R_c until the "pinch" voltage is reached. At this point the capacitor discharges rapidly through the emitter/base 1 junction of the device. The rising edge of the emitter sawtooth waveform (a) is determined by the value of R_c and C_a and the trailing edge is dependent upon the value of C_a and the emitter/base 1 resistance.

Short pulses are produced at b1(b) and b2(c) when the capacitor voltage rises to the value of the "pinch" voltage. It was decided not to use

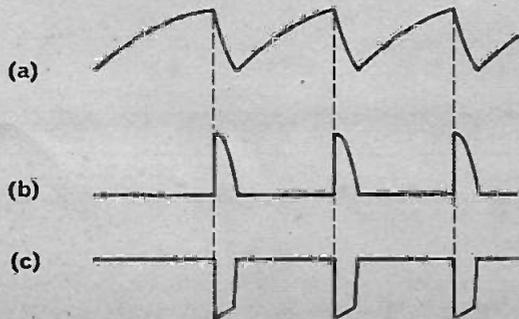

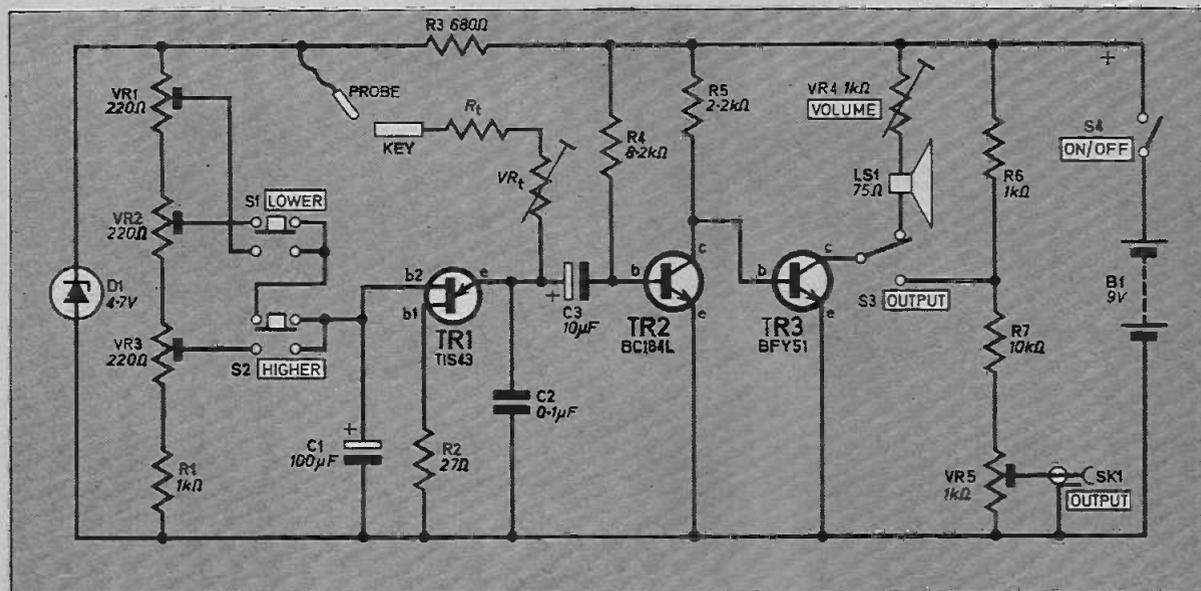


Fig. 3. Circuit diagram of the Mini Organ. Various values for R_t and VR_t for corresponding notes are given in Table 1.

these outputs as the sound was thought to be too staccato due to the short duration of the pulses. The emitter waveform seemed to be more promising, but for reasons explained later it was desirable to have a "square" waveshape rather than a sawtooth: TR2 (Fig. 3) accomplishes this.

FREQUENCY

The frequency of a unijunction oscillator is almost a linear function of the CR product. From the formula for the inter-semitone step for the standardised "concert pitch", the value of timing resistors for the circuit were calculated. A value of 15 kilohms was used as a starting point for the higher end of the scale.

As is probably known, the frequency of a note doubles for a complete octave step; thus it was to be expected that the value of timing resistor would halve, since the product of CR gives a time, and time is the inverse of frequency. This is shown in the formulae:

$$f = \frac{1}{t} \quad t = C \times R \times K$$

where f is the frequency, t is time, C and R are the timing elements, and K is the constant for the oscillator under given conditions.

The results of the calculations are shown in Table 1. In practice it is easier to "tune" an oscillator using trimmer resistors rather than with fixed resistors due to the large tolerances involved. It is not sufficient to say that a 5 per cent error in the pitch would not be noticed by the average child or, indeed, adult.

The values obtained for Table 1 were used to determine the values of fixed and variable resistors shown. The instrument may be tuned "by ear" against any convenient piano, guitar, etc. simply by adjusting the trimmers, starting with VR_B and working down the scale.

A rather more accurate method of tuning the organ is the method I chose; being rather tone deaf, and with a fairly large stock of resistors to hand I fed the output of the organ into a convenient frequency counter and replaced the trimmers with fixed resistors until the counter read the correct frequency. For those with access to a frequency counter I can recommend this method of calibration, particularly if you, too, are tone deaf.


MULTI-OCTAVE VERSION

It is possible, by altering the value of base 2 voltage to the unijunction transistor whilst keep-

Table 1: Resistor Values For Various Notes


Note	C	C#	D	D#	E	F	F#	G	G#	A	A#	B	C
Frequency	261.6	277.2	293.7	311.2	329.7	349.2	370.0	392.0	415.4	440.0	466.2	493.9	523.3
Resistance Value (kΩ)	30.0	28.3	26.8	25.2	23.8	22.5	21.2	20.0	18.9	17.8	16.8	15.9	15.0
Fixed Resistor (kΩ)	27	27	24	24	22	20	20	18	18	16	16	15	15
Trimmer (kΩ)	4.7	4.7	4.7	4.7	4.7	4.7	4.7	4.7	2.2	2.2	2.2	2.2	—

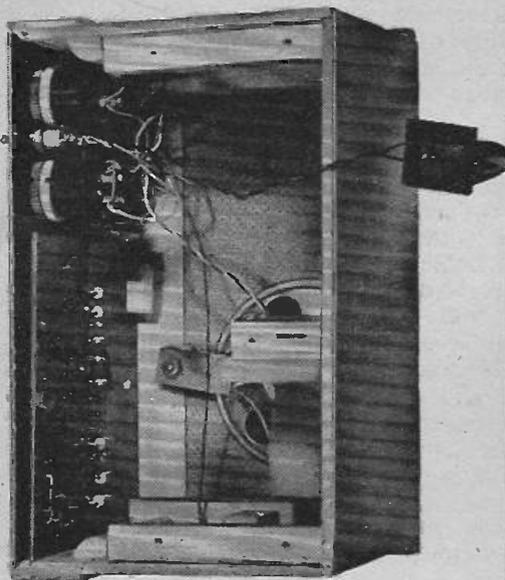The resistor and trimmer associated with each note take their designations from that note, e.g. fixed resistor for D is 24kΩ and its designation is R_D , similarly the trimmer will be 4.7kΩ and VR_D .



Photograph of the prototype Mini Organ.

Fig. 4 (right) The layout of the printed circuit panel underside, shown full size.

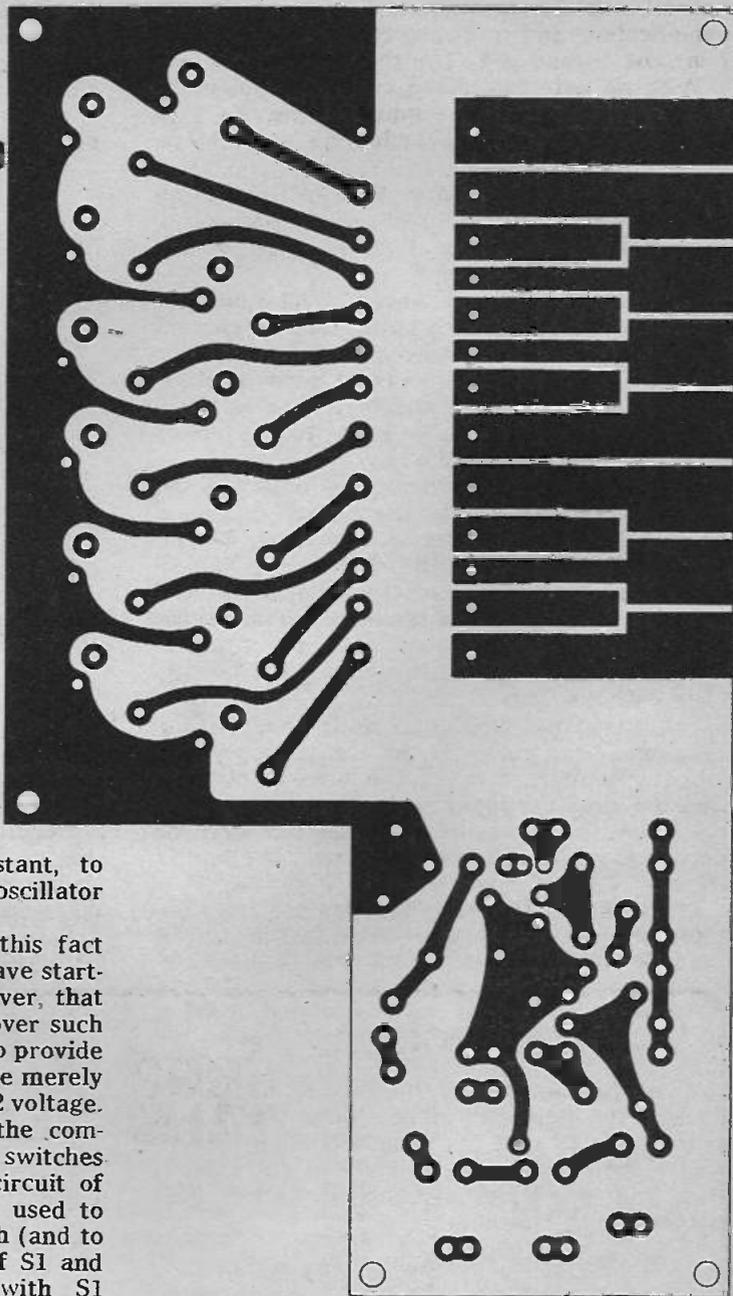

ing the emitter supply voltage constant, to change the basic frequency of the oscillator shown in Fig. 1.

Initially it was proposed to utilise this fact to tune the one-octave organ to the octave starting at "middle C". It was found, however, that it was possible to alter the frequency over such a wide range that it would be feasible to provide a full octave above and below this range merely by switching in different values of base 2 voltage.

To provide the full three octaves the components VR1, VR2, VR3, R1, and the switches S1, and S2 were added to the basic circuit of Fig. 1 (see Fig. 3). The trimmers are used to tune the three octaves to standard pitch (and to each other). In the normal positions of S1 and S2 the centre range is selected; with S1 depressed a lower octave is selected and with S2 depressed a higher one. Depression of both switches simultaneously results in the higher octave being selected.

KEYBOARD

As was stated at the beginning, the original design concept of the organ was that it should be both simple and inexpensive. A full set of keys, it was found, would be too expensive for such a simple design; making the keys was too complex.

A simple solution to the problem was to etch the key-pattern onto the printed circuit component board. The resulting layout is shown in

Fig. 4; if necessary the keyboard and oscillator/amplifier sections may be transferred to different relative positions or divorced from each other completely. The probe used on the keys can be of any suitable insulated metal object from a wander plug to a piece of brass rod in an old ball-pen case.

OUTPUT AMPLIFIER

Transistor TR2 (Fig. 3) is an overdriven amplifier, and is used to convert the sawtooth wave-shape from the emitter of TR1 to a reasonable facsimile of a square wave. It was decided that

normal amplifier techniques were unnecessarily complicated, and a direct coupling was made from the output of TR2 to the base of TR3.

With no note keyed the current supplied by R4 holds TR2 "on", or conducting heavily. This in turn holds TR3 non-conducting, so that no current flows through the speaker coil. This serves two purposes, first that of conserving power from the battery, and second, preventing the possible overheating of the speaker coil due to a continual power supply to it.

When the oscillator is "keyed", TR2 is momentarily turned off by each pulse, causing current to be supplied to the base of TR3 by R5. This turns TR3 on, allowing a current pulse of about 120 milliamps to flow through the speaker coil. This causes the speaker to emit strange noises which children appear to enjoy.

Adults, on the other hand, may object to the weird noises produced by the device, and shout phrases like "Turn it down!" or worse. To this end a volume control (VR4) has been provided.

The pulse amplitude at the collector of TR3 does not diminish, but the power available to the speaker coil does. In fact, the output power diminishes to somewhat less than 30 milliwatts r.m.s with adjustment of VR4.

For masochists who enjoy noisy children provision has been made for the unit to be plugged into the family hi-fi via SK1. It must be stressed that the amplifier input "low" terminal must be connected to the amplifier chassis, and that the chassis must be connected to earth, because of the open keyboard and probe used.

The collector of TR3 is disconnected from the speaker system by S3 and reconnected to the network of R6, R7 and VR5. Resistor R6 provides

the collector load, whilst R7 and VR5 drop the voltage output to about 0 to 0.5 volt r.m.s. If this output is too high to be easily adjusted by VR5 then R7 may be increased.

POWER SUPPLY

Because of the low quiescent current of the organ it is eminently suitable for battery operation. Due to the open contact type of keyboard it is inadvisable to operate the instrument from a mains derived source! Under no circumstances can the unit be operated from a "battery eliminator" type of device, since most of these are not isolated from the mains supply in any way, and a fatal shock could result.

The frequency of the oscillator is somewhat voltage-sensitive. To ensure that the basic note does not alter too much with battery voltage changes, the oscillator supply voltage is stabilised by means of a Zener diode D1.

The 120mA current pulses when the oscillator is keyed originally caused the battery voltage to drop by about 700 millivolts. Despite the Zener stabilizer this change was acting on the oscillator to cause false operation. To overcome this the value of C1 was increased to its present value, but it should be noted that only the larger battery types should be used.

CONSTRUCTION

Commence construction of the unit by cutting and making the printed circuit board to the design shown in Fig. 4. This should be carried out with reference to the *Making P.C. Boards* article in this issue (page 300).

Having completed the board, checked it and

Components

SEE
**SHOP
TALK**

Resistors

R1	1k Ω	R _D	24k Ω
R2	27 Ω	R _E	22k Ω
R3	680 Ω	R _F	20k Ω
R4	8.2k Ω	R _F	20k Ω
R5	2.2k Ω	R _G	18k Ω
R6	1k Ω	R _G	18k Ω
R7	10k Ω	R _A	16k Ω
R _{C1}	27k Ω	R _A	16k Ω
R _{C1}	27k Ω	R _B	15k Ω
R _D	24k Ω	R _C	15k Ω

Capacitors

C1	100 μ F elect. 12V
C2	0.1 μ F
C3	10 μ F elect. 12V

Variable Resistors

VR1	220 Ω	VR _D	4.7k Ω
VR2	220 Ω	VR _D	4.7k Ω
VR3	220 Ω	VR _E	4.7k Ω
VR4	1k Ω TV type preset	VR _F	4.7k Ω
VR5	1k Ω	VR _F	4.7k Ω
VR _{C1}	4.7k Ω	VR _G	4.7k Ω
VR _{C1}	4.7k Ω	VR _G	2.2k Ω

VR _A	2.2k Ω	VR _B	2.2k Ω
VR _A	2.2k Ω		

All horizontal p.c. mounting, miniature skeleton presets, except where stated.

Switches

- S1, S2 d.p.d.t. pushbuttons (Radiospares miniature type or similar—2 off)
- S3 s.p.d.t. toggle switch.
- S4 s.p.s.t. toggle switch.

Semiconductors

- D1 4.7V 400mW Zener diode
- TR1 TIS43 unijunction transistor
- TR2 BC184L silicon *n*p*n*
- TR3 BFY51 silicon *n*p*n*

Miscellaneous

- LS1 75 Ω or 80 Ω , approximately 300mW miniature loudspeaker
- B1 9V battery—see text
- SK1 coaxial socket and plug to suit Single sided copper clad paxolin or fibreglass panel 6 $\frac{1}{2}$ inches by 3 $\frac{1}{2}$ inches. Materials for case (see text) 6BA fixings, wire, connectors for B1, banana plug or similar for probe.

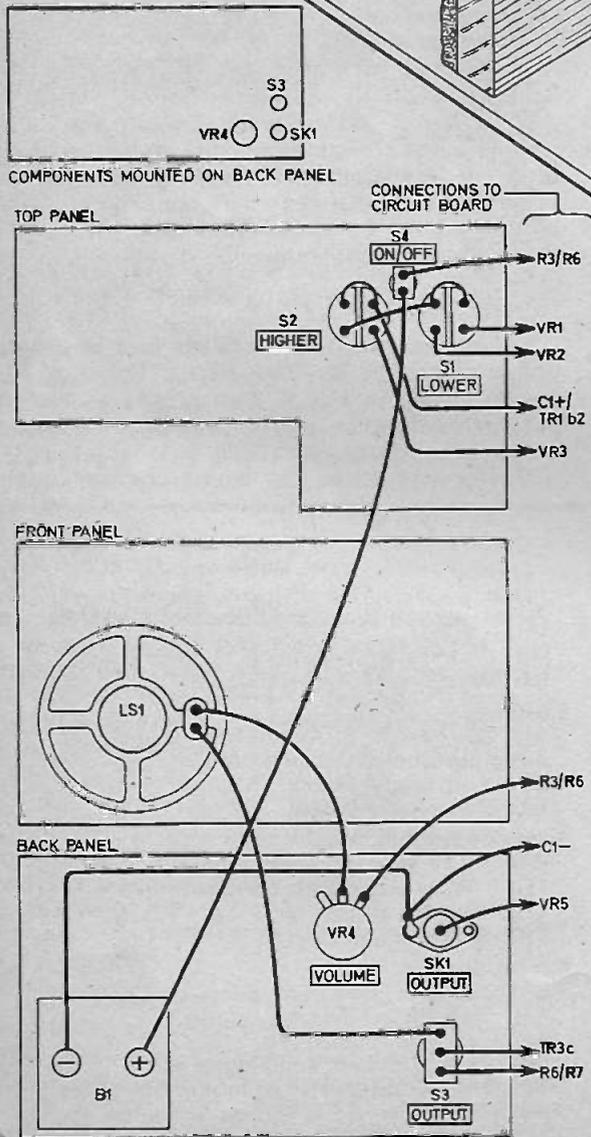


Fig. 7. (above) Layout and basic construction of the case. The size of the top is determined by the circuit board and thickness of the wood. The case is four inches high.

Fig. 6. (left) Wiring of the components mounted in the case and connections to the circuit board.

mini ORGAN

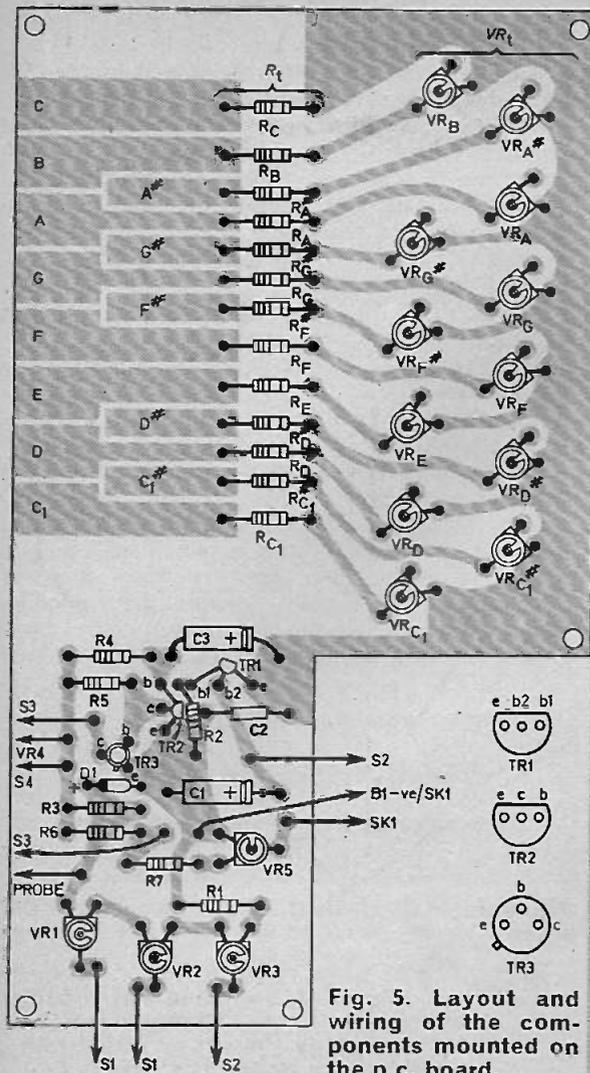


Fig. 5. Layout and wiring of the components mounted on the p.c. board.

drilled the holes, the components and flying leads can be attached as shown in Fig. 5. Note that the copper areas on the back of the board are shown tinted (as if looking through the board) in Fig. 5. Solder the transistors in after all other connections have been made, using a heat shunt on each lead as it is soldered.

Check the board and components against Fig. 5 paying particular attention to the transistor lead connections, diode polarity and capacitor polarities as shown. This is easily done by holding the board in front of a light so that the components can be checked and the image of the copper can be seen through the board. Finally wire up the complete unit as shown in Fig. 6 construct the case (Fig. 7) and install the electronics.

To test the unit switch on and place the probe on one of the key positions, check that all the notes are operable—including the upper and lower octaves and finally tune the organ by adjustment of the presets as mentioned earlier.



When drilling the component locating holes in a small, home made printed circuit, secure the board to the smooth side of a larger piece of hardboard using double-sided Sellotape.

The hardboard will support the brittle Paxolin and you can drill quickly and smoothly through it into the hardboard, making clean holes with less risk of breaking the fragile twist drill. Afterwards prise the circuit board and hardboard apart with a thin blade or a tab of tape left projecting from the "sandwich". Double-sided tape proves useful in many situations and a reel of 1 inch width is a handy addition to the hobbyist's toolkit.

E. Mullis
Dunmow, Essex.

The problem of overheating, oxidising, and eroding of soldering iron bits has always caused me concern, and annoyance. After trying various methods, including switched reduced voltage, I eventually devised a simple, long lasting, and foolproof method which kept the iron hot, but not too hot, and served the additional purpose of an iron bench stand and heat shunt.

Manufacture and construction; a length of heavy duty conduit is sawn to the desired length, and compressed near one end in the vice to produce a constriction in which the iron bit will rest. Secure the tube to the bench in a convenient place by means of two conduit clamps (the stand off type) and you have an almost everlasting, convenient iron stand and shunt; I used the same one for 30 years.

Incidentally I regularly notice in "radio books" different methods of heat shunts when soldering transistors, no doubt all the methods have some merit, but the one I use is to hold the transistor wire with a pair of small medical forceps of the self locking type, with these you can safely wave the transistor around and then present it accurately to any pinpoint, the forceps can usually be obtained as "throw outs" once personal contact has been established.

J. Hardman
Thornton-Cleveleys,
Lancashire.

Instead of using long nosed pliers as a heat shunt use a hair grip "the type with a spring in". This gives a free hand for holding the solder.

P. Ransey
Berks.



Easy step by step instructions.

by J. A. Nekrews

THE printed or etched circuit is used in virtually every piece of commercial electronic equipment produced these days. In fact projects detailed in this and other technical journals sometimes provide a ready designed layout to assist the amateur constructor in the production of his own printed circuit board.

Not all constructors are familiar with the techniques involved, especially the relative newcomer to solid-state circuitry, so if you are one of the many constructors who would like to attempt this most satisfying branch of our hobby, but you are not too sure where to start, read on.

REQUIREMENTS

The complete newcomer to this field may be well advised to start with one of the proprietary "printed circuit kits" currently available from suppliers who advertise in the technical journals from time to time.


These kits usually provide everything necessary to complete an etched circuit, including an instruction leaflet detailing the use of the etchant supplied.

However, all the "ingredients" are available separately and you will need;

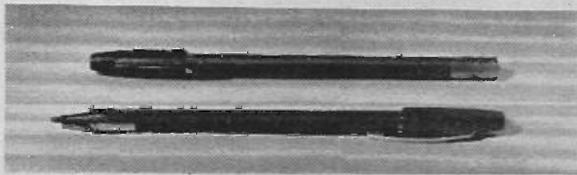- (a) copper clad s.r.b.p. or fibreglass board
- (b) resist
- (c) solvent
- (d) etchant

The copper clad board is available from the larger component retailers as well as several smaller firms who specialize in printed circuits. The board is generally sold in "stock size" pieces.

For the resist there are two main choices: small jars or tins of plastic enamel paint used by model makers or the special printed circuit pens available such as the Dalo Marker and the G.S.P.K. P.C. pen.



Photograph of the Dalo Marker pen used in this article.

Turpentine or white spirit makes an excellent solvent for removal of the paint and this also is readily available. Special solutions are available to remove the pen type resist or alternatively a light abrasive paste can be used such as Solvol Autosol—sold in garages.

There are several chemical agents used as etchants for printed circuits, one of the most common being ferric chloride.

The author has found this etchant to be reliable and efficient as well as relatively easy to obtain. Your local chemist should be able to supply this, if not then you must resort once more to mail order component suppliers.

Ferric chloride is normally supplied in powder or crystalline form for dissolution in water. A suitable etching solution for a board size 3in. by 2½in. can be made by adding about four heaped teaspoonfuls of ferric chloride powder to a quarter pint of luke warm water. For these conditions the etching time will be about 45 minutes.

A point worth mentioning here is to always add the chemical to the water, never add the water to the chemical.

Ferric chloride should be treated with some care as it will burn the skin and clothing if contact is prolonged. When using ferric chloride

make sure that it does not come in contact with the eyes. If some is spilt on clothing or comes in contact with the skin it should be washed off under running cold water as quickly as possible.

LAYOUT DESIGN

It is preferable, in fact almost a necessity to have all the components on hand and to design your circuit to suit the components, rather than have to shop around to find components to suit your design.

The author's experience has proved standard 0.1 inch graph paper to be an ideal medium on which to formulate a design.

Now to get to the actual design, the method is best described using a simple example such as the circuit of the Beta Fuzz as described in E.E. January 1973, see Fig. 1.

First of all decide on an approximate size for the completed board, and here you must be realistic; if you are striving for microminiaturization with discrete components then this system is not for you.

Getting back to the drawing board, first of all draw the outline of the board on the graph paper leaving the right-hand side blank just in case it is not possible to fit the complete circuit on the size of board originally desired. Conversely it may be found that the board could be made smaller if required.

Next, working from left to right on the circuit diagram and using the actual components as templates, mark the positions of all the components and connections using pencil until a satisfactory layout is produced.

Then, using coloured crayon or better still a felt-tip pen, shade in the interconnections to form a pattern similar to that shown in Fig. 2. It is common practice to have the "live" supply line along the top and an earth or zero volt line at the bottom just as in conventional circuit diagrams, see Fig. 2.

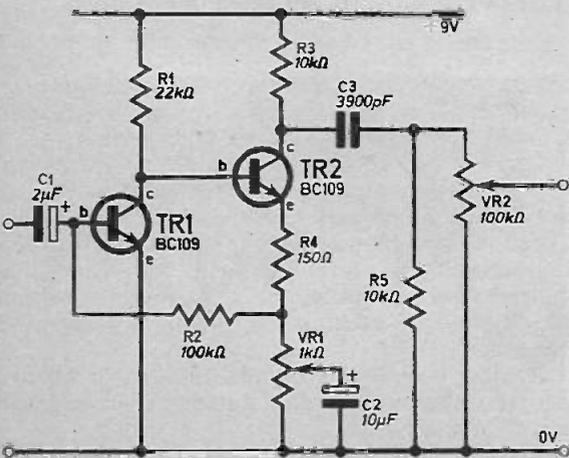


Fig. 1. The circuit diagram of the Beta Fuzz to be put on to the printed circuit board.

Everyday Electronics, June 1973

Remember that you are working from the top-side i.e. the unclad side of the board, therefore all components and connections are to be viewed from the topside. This is of particular importance with transistors and integrated circuits.

The resulting drawing should look something like Fig. 2. In this case, space was of no importance so a neat functional layout was obtained.

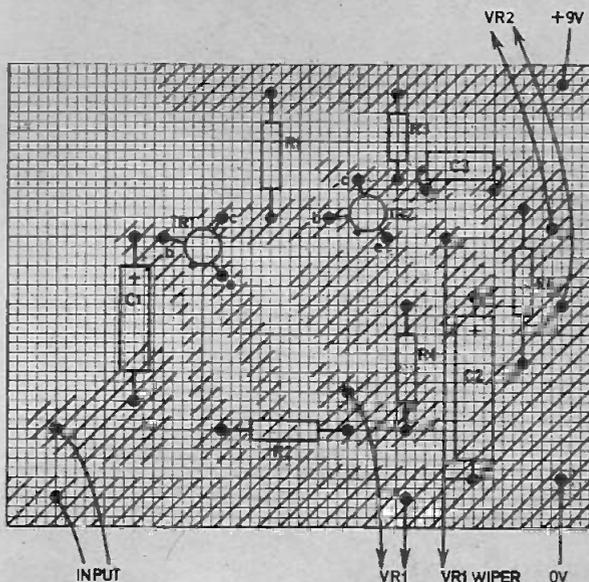


Fig. 2. The final design of printed circuit layout on graph paper.


CLEAN BOARD

A piece of copper clad board should now be cut to the required size, a fretsaw or hacksaw is very handy for this, and the edges carefully filed smooth. The board should then be thoroughly and scrupulously cleaned. Ordinary household scouring powder such as Vim or Ajax makes an excellent job of this, after which be careful not to touch the copper surface as fingerprints leave greasy marks which could impair the etching action.


TRANSFER

Using the pattern of Fig. 2 we shall make the master drawing of the printed circuit—this is the pattern given with most printed circuit articles and which is usually full sized so that a direct transfer can be made to the board. The areas shown in black are the areas of copper strip to remain on after the etching process.

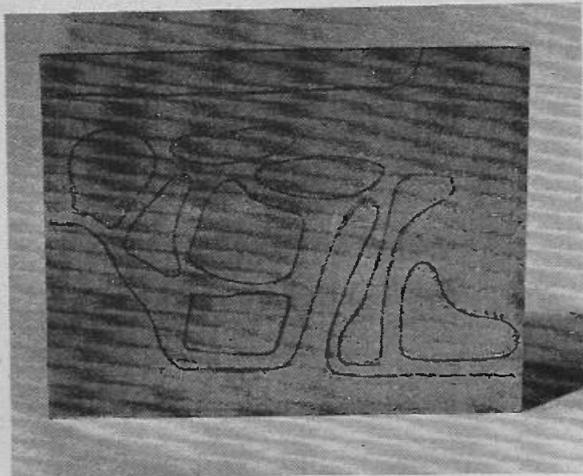
Place a piece of carbon paper (face side up) on the bench and then place your pattern of Fig. 2 on top of it. Run a soft pencil over the outline of the pattern so that a mirror image of the latter is produced on the reverse side. This "mirror image" is the master drawing. Shade in the areas of copper to be left on after etching, this will be helpful later. See Fig. 3.



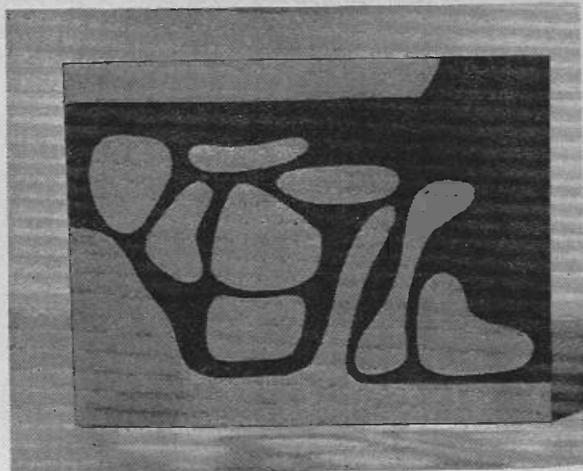
A. The carbon paper tracing from the master drawing on the copper side of the board.



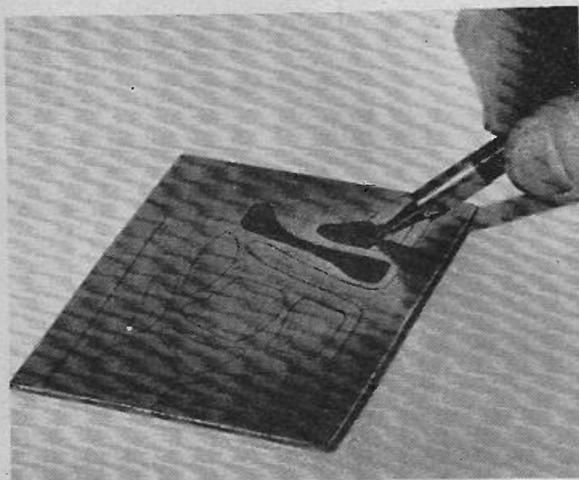D. The board after etching with resist cleaned off.



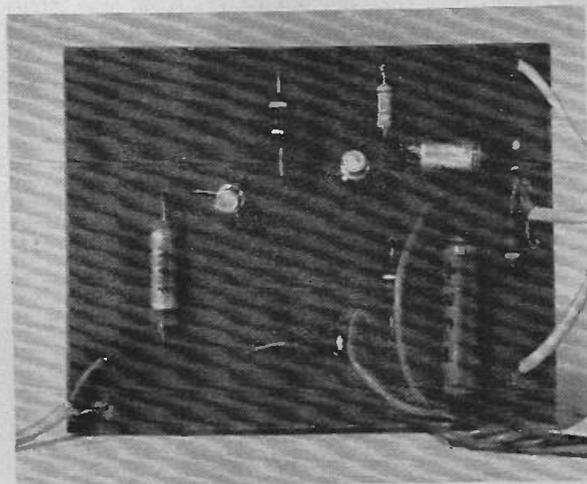
B. Using a printed circuit marker pen to fill in the areas of copper to remain after etching.



E. The components mounted in position.



C. The board dry and ready for etching.

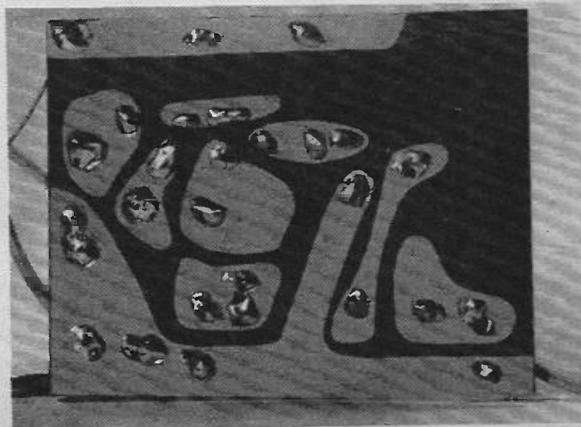

F. The underside of the completed board.



Fig. 3. The master drawing of the printed circuit board (full size).

Now place the carbon paper face side down on the copper clad side of the board (cut to size) and then place the master on top of this and align correctly with the board. Secure this in position with paper clips or Sellotape and then run a pencil over the outline of the master to produce the same on the copper. The result of this is shown in photograph A.

If using paint, such as Airfix or Humbrol (as used for painting models), paint in the areas of copper to remain (with reference to the master drawing) with a fine artists brush and leave to dry. Make sure there are no uncovered spots or "pin pricks", if there are, cover in.

If using one of the printed circuit pens, fill in the appropriate areas of the board according to the master drawing using the nib of the pen as shown in photograph B.

In both cases, ensure the edges of the resist are sharp and clean otherwise a ragged and diffuse type edge will result which looks unprofessional; allow the paint or pen resist to dry completely; photograph C shows the board ready for etching.

ETCHING

The following method of etching was selected for its simplicity and reliability. A Pyrex or photographic developing dish, large enough to allow the board to lie flat inside, is filled approximately half an inch deep with the ferric chloride solution, and the board is placed copper side upwards in the solution. This must then be constantly agitated. The etching process is complete after about 45 minutes.

The need for constant agitation cannot be overstressed as failure to do this results in the ferric chloride molecules combining with the copper forming an inactive coating on the surface of the board and halting the etching action.

If the board is left in the solution too long the etchant may start to undercut the painted areas, so be warned.

Once the etching process is finished, the board should be removed from the solution, well rinsed in fresh water and dried. The resist can now be removed using the solvent or light abrasive, leaving a neat and professional looking printed circuit board (see photograph D).

DRILLING AND COATING

Once the board is etched there remains the job of drilling the holes. This process needs to be carried out with care, otherwise the copper may be lifted from the board and then a new board has to be made.

With reference to the master drawing, mark the positions of all holes to be drilled on to the copper clad side of the board, and then carefully drill these with a 1/32in. diameter drill.

Drill slowly and apply minimum pressure to ensure that the drill breaks through the board cleanly; this will help to give the board a professional appearance; don't forget to drill the mounting holes before component assembly.

At this stage, if desired, the remaining copper on the board, thoroughly cleaned, can be coated with a thin layer of solder to protect the copper from oxidation. This also gives a neater appearance to the back of the board.

As an alternative to this, a coating of varnish may be applied to the back of the board after the components are soldered in position.

MOUNTING COMPONENTS

All component wires should be bent at right angles to the component body so that their bent leads exactly span the distance between the holes that have been allocated them. They should then be inserted in these holes such that the body of the component clears the board by about 1/16in. and then the leads cut off so they protrude only about 1/16in. beyond the copper. They should then be soldered in this position. See photographs E and F.

It is important to carry out the soldering of each component swiftly, as prolonged heat on the board (from the soldering iron) may cause the copper lamination to come adrift.

Transistors and other semiconductors should, as usual, be left until last, and when being soldered in position a heat shunt should be used.

CONCLUSION

In cases where several boards of the same design are required, special light-sensitive laquer is available. This process requires the design to be painted on a piece of thin acetate sheet. With this method an unlimited number of boards of the same design may be produced. □

FREE! COMPETITION

**... Win this VISCOUNT Audio System!
100 other prizes for Runners-up**

This fantastic Viscount Audio System can be yours—free! It's the first prize in this exciting competition, open only to EVERYDAY ELECTRONICS readers. The system comprises the new RTVC Viscount III P102 stereo amplifier, two duo type III speakers and a Garrard SP25 Mk III turntable mounted on a perspex covered plinth. It's selling for around £70!

The competition is all about soldering and so, appropriately, are the rest of our prizes. Just take a look at this list of soldering goods making up the 100 runner-up awards:

From Adcola Products Ltd. Soldering kits, soldering irons and iron stands.
From Antex (Electronics) Ltd. Soldering kits and soldering irons.
From Multicore Solders Ltd. Soldering handbooks, wire strippers and solder dispensers.

HOW TO ENTER

Listed below are eight points which make for successful and efficient soldering. All you have to do is place them in what you consider to be their order of importance in contributing to a perfect soldered connection. For example, if you consider that "Use non-corrosive flux cored solder" is most important of all, write C in the box marked 1st on your entry coupon. The key letter of your second choice goes into the box marked 2nd, and so on for all eight.

Complete the coupon, all in ink or ball-point, with your full name and address, then post it in a sealed envelope to:

EVERYDAY ELECTRONICS SOLDERING COMPETITION,
16 GARRICK STREET,
LONDON, WC2E 9PR.

IMPORTANT


Another free entry coupon for this competition will appear in the July EVERYDAY ELECTRONICS.

The closing date for entries—Friday, July 27th, 1973—gives you ample time to wait for our next issue and then post two different attempts together in one envelope.


- A** Parts to be soldered should be cleaned and tinned.
- B** Use soldering iron of correct size and weight.
- C** Use non-corrosive flux cored solder.
- D** Use soldering iron with tip of correct size.
- E** Maintain heat on joint until solder flows evenly over it entirely.
- J** Keep tip of iron "wet" with solder.
- K** Use soldering iron of correct temperature and wattage.
- L** Make good mechanical contact prior to soldering.



The Viscount Audio System

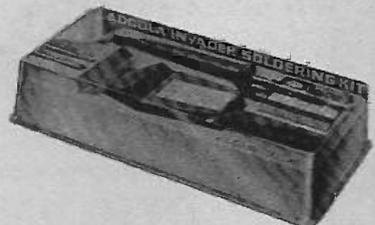

An Adcola soldering kit

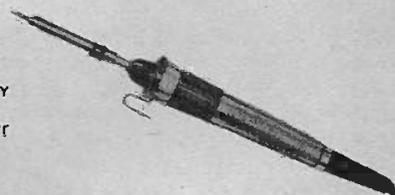

An Antex thermostatically controlled soldering iron

COMPETITION RULES

There is no entry fee, but each attempt must be fully completed in ink on the proper printed coupon cut from Everyday Electronics, and bear the entrant's own full name and address.

Every accepted entry will be examined and the first prize, as described, will be awarded to the entrant who, in the opinion of an expert panel of judges, and in any one attempt, has shown the most skill and judgement in listing the eight features in order of importance. The other prizes will be awarded to the senders of the 100 next best attempts in order of merit. No entrant may win more than one prize.

In the event of a tie or ties for any of the prizes, a further eliminating contest will be conducted by post between the tying competitors to determine such winner/s or winning order.

Any entry which does not comply with the printed instructions or is received after the closing date will be disqualified, as will any received mutilated or illegible, incomplete, bearing alterations, or with more than one key letter in each space. No responsibility will be accepted for entries lost or delayed in the post or otherwise.

The judges' decision, and that of the Editor of Everyday Electronics in all other matters affecting the competition, is final and legally binding. No correspondence can be entered into.

The competition is open to all readers in Great Britain, Northern Ireland, and the Channel Isles except employees (and their families) of IPC Magazines, the printers of Everyday Electronics or any company associated with the prizes.

The winners will be notified, and the result announced in the earliest possible issue of this magazine.

FREE ENTRY COUPON

Please post to:
EVERYDAY ELECTRONICS
SOLDERING COMPETITION,
16 GARRICK STREET, LONDON WC2E 9PR

1

My order of importance for the eight features is listed on the right. In entering the competition, I agree to the rules as final and legally binding.

NAME	1st
(Mr./Mrs./Miss)	2nd
ADDRESS	3rd
(Block letters)	4th
.....	5th
.....	6th
.....	7th
.....	8th

Closing date for entries: Friday, July 27, 1973

CUT ALONG THIS LINE



NEXT MONTH FOR THOSE WHO DO!

**CONSTRUCT-
IONAL
ARTICLES**

AUDIO MIXER

For use with a tape recorder or for p.a. systems

AUTOFAN

A thermostatic control for an electric, engine cooling fan

REPLICA CRYSTAL SET

Span the ages with this replica of an original, complete with "crystal" and "cats whisker"

AND THOSE WHO MAY

**FEATURES
AND
ADVICE**

AUTOMATION

A look at electronics at work

SEMICONDUCTORS

Second part of our new series introduces the diode



Our experts offer straightforward answers to technical problems

PLUS Second and final chance to enter the EE soldering competition

DON'T BE DISAPPOINTED Your newsagent will be pleased to take your order

**everyday
electronics**
July issue on sale Friday June 15

SEMICONDUCTORS

ONE

INTRODUCTION

J.B. DANCE M.Sc.

This series has been written to provide a very simple explanation of how common semiconductor devices function. No knowledge of mathematics or of the details of chemical bonding will be required in order to understand any part of the series. It is only necessary to know that, when a voltage is applied across a material, the electrons in the material are attracted towards the positive electrode and the positive charges towards the negative electrode.

This first part of the series introduces the basic principles of the semiconductor and semiconductor materials but later in the series it will be orientated more towards understanding the functioning of the various devices.

Simple ways of testing the various devices will be described in later articles, partly because the carrying out of such tests is very instructive for the beginner. The only equipment which will be required for the tests is a suitable meter, a battery and a few resistors.

CONDUCTION

All materials contain negative charges—electrons—and an approximately equal number of positive charges. The number of these charges in a small amount of matter is enormous (about one million million million $[10^{21}]$ in one gram of a substance).

A material will conduct electricity if it contains electric charges which are *free to move* under the influence of an applied voltage. The moving charges “carry” the current, since an electric current is merely a movement of electric charge.

Current flow in a material may consist entirely of electrons moving towards the positive electrode (anode) of the applied voltage and in some cases it consists only of positive charges moving towards the negative electrode (cathode) of the applied voltage, whilst in other circumstances both the electrons move to the cathode and the positive charges move to the anode at the same time. Any charges which are free to move will do so.

Metals are very good conductors of electricity because they contain very large numbers of *free* electrons, the word “free” implying that the

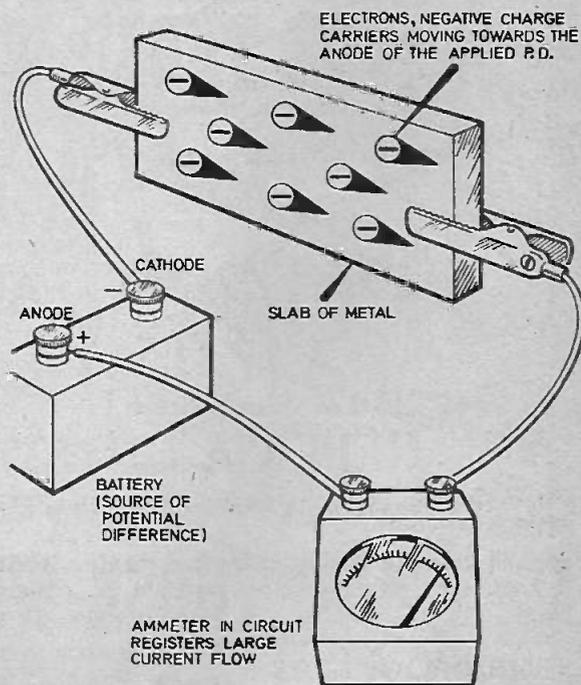


Fig. 1.1a. Schematic of conduction in a metal, movement of electrons.

electrons are able to move. Conduction in a metal is illustrated in Fig. 1.1a.

Solutions of acids, alkalies and salts are also good conductors of electricity, since they contain very large numbers of positive and negative charged particles (or ions as they are called) which are free to move. Conduction in such a solution is depicted in Fig. 1.1b.

A similar type of conduction occurs in the familiar yellow street lamps where an electric current passes through a gas which contains large numbers of electrons and positively charged sodium ions.

Insulators, such as glass, Perspex, air, etc., contain electrons and positive charges, but virtually all of these charges are firmly bonded to the atoms of the material and are not free to move when a voltage is applied across the substance. Insulators will not therefore conduct electricity unless an extremely high voltage is

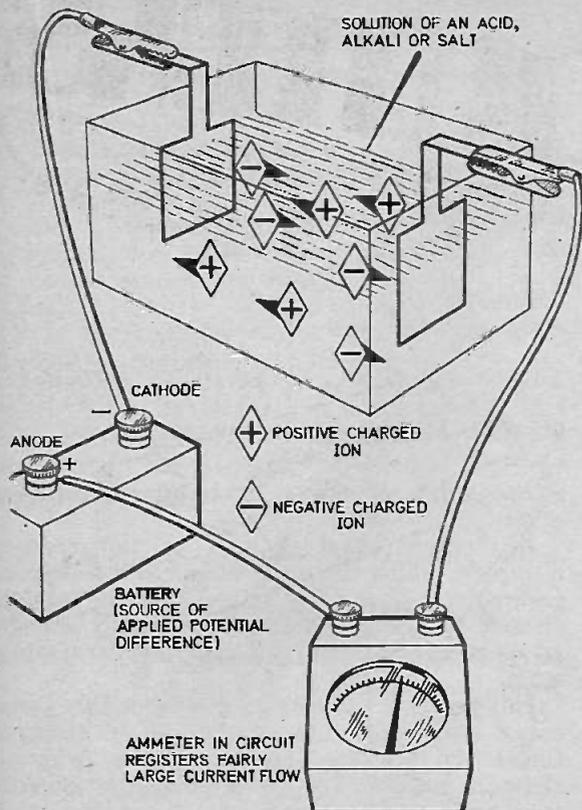


Fig. 1.1b. Electrical conduction in a solution, ionic movement.

applied across a very thin layer of the material so that some electrons are wrenched from their bonds.

SEMICONDUCTORS

Semiconductors form a class of substances intermediate between metals and insulators. The best known semiconductor materials are the hard grey brittle elements, germanium and silicon.

Such materials contain some electrons which are free to move, but the number of these mobile electrons is far far less than in a metal. Semiconductor materials will therefore pass a *small* current when a potential difference is applied across them, as depicted in Fig. 1.1c.

For example, metallic copper conducts about a million times better than germanium and about a thousand million times better than silicon.

The number of free electrons in a pure semiconductor material increases very rapidly as the temperature rises. At higher temperatures there is more energy in the material and this enables more electrons to break away from the bonds which secure them to a particular atom. As a "rule of thumb", it can be stated that the number of free electrons in a pure semiconductor material is doubled for each 10 degree

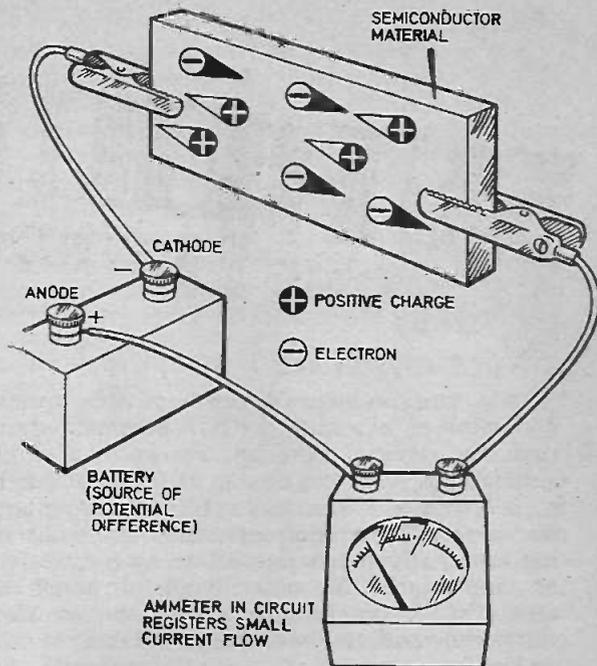


Fig. 1.1c. Schematic of electrical conduction in a semiconductor.

centigrade rise in temperature.

Electrons which are at some time free, become bonded to atoms, and other electrons break their bonds and become free so that the total number of free electrons in a piece of material remains fairly constant with time.

Pure germanium contains many more free electrons per unit volume than pure silicon at the same temperature. In general germanium devices cannot operate at temperatures much above 90 degrees centigrade, since at higher temperatures the number of electrons in the material becomes so great that the current cannot be controlled.

Silicon devices can operate at temperatures up to about 180 degrees centigrade. Some semiconductor materials, such as gallium arsenide, contain fewer free electrons than silicon at a given temperature and can therefore be used at even higher temperatures.

Conduction in a *pure* semiconductor material is known as **intrinsic conduction**, the word intrinsic merely showing that the conduction is taking place in the pure material itself.

IMPURITIES

Most *chemicals* are regarded as being pure if the total impurity content is less than one part in a thousand or even one part in a hundred.

However, the material used in semiconductor devices must contain a far smaller impurity concentration than this. Typically, the pure germanium and silicon used for manufacturing semiconductor devices contains less than one part of impurity in ten thousand million parts

of the material.

The preparation of materials in such extreme degrees of purity cannot be achieved by normal chemical methods, special techniques have been perfected to enable the required materials to be prepared at a suitable level of purity.

It is useless preparing such a pure material unless it is kept pure throughout the life of the device. Semiconductor devices are therefore sealed in metal (with insulated leads), glass or a suitable plastic material so that no impurities can reach the semiconductor material itself.

SINGLE CRYSTALS

Most semiconductor devices not only require materials of extreme purity, but also require that the material shall be present as a single crystal. A crystal contains an orderly pattern of atoms in three dimensions extending throughout its volume, whilst non-crystalline materials do not have such an orderly pattern extending over an appreciable distance. Impurity atoms or atoms which are in such a position that they spoil the pattern, constitute defects in the crystal.

N-TYPE MATERIAL

A semiconductor material contains few free electrons. If certain impurities (such as arsenic or antimony) are introduced into the crystal in extremely minute concentrations (typically one impurity atom in many millions of atoms of the semiconductor material), the number of free electrons (and hence the conductivity) is greatly increased.

Each atom of the impurity material can release an electron relatively easily. At normal temperatures almost all of these electrons are free to move in the crystal.

Semiconductor materials containing such impurity atoms are known as n-type or negative carrier materials, since conduction takes place by means of negative charge carriers, that is, electrons.

The atoms of arsenic, antimony or a similar element which donate the electrons are known as donor atoms.

P-TYPE

Certain other types of impurity atom such as aluminium, indium and phosphorous, also have a profound effect on the conductivity of a semiconductor material when they are added to it in minute amounts. These atoms are known as acceptor atoms, since each atom of such an element can readily accept one electron from a neighbouring atom of the semiconductor material.

HOLES

Let us consider how conduction takes place in a material containing acceptor atoms. In Fig. 1.2

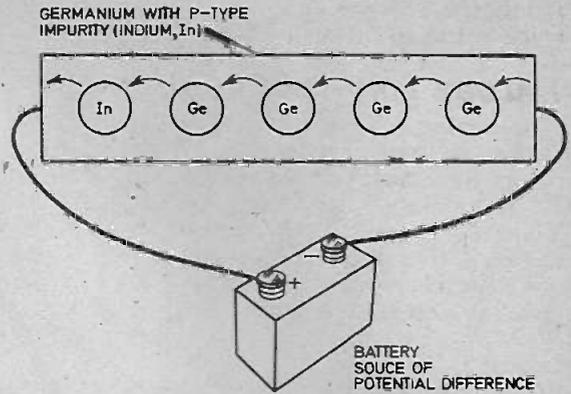


Fig. 1.2. Conduction in p-type germanium.

a single row of atoms is considered for simplicity.

An indium atom is next to the positive electrode, whilst the other atoms in the row are germanium. Under the influence of the applied electric field, the indium atom readily accepts an electron from the neighbouring germanium atom.

This leaves a vacancy or a hole in this germanium atom which can be filled by an electron. Under the influence of the electric field, an electron moves from the adjacent germanium atom to fill the vacancy as shown by the arrow. Similarly the new hole thus formed is in turn filled by an electron from the next atom.

Finally, an electron moves from the negative plate to fill the hole formed in the last germanium atom, and the electron which first moved into the indium atom now moves into the positive electrode. This whole process can be repeated indefinitely.

HOLE CONDUCTION

We have seen that conduction in a semiconductor material containing acceptor atoms actually consists of a movement of electrons from the cathode to the anode.

However, it is often easier to consider that one hole is moving from the anode to the cathode rather than to consider that the process consists of the movement of a large number of electrons in the opposite direction. This type of conduction is therefore known as hole conduction.

Holes behave as if they are positive charges. In Fig. 1.2 the holes move to the right, that is from the anode to the cathode, in the same direction as a positive charge would move.

Materials containing acceptor atoms are therefore called p-type materials, since conduction occurs by a movement of the hypothetical positive charge carriers known as holes.

In case any reader is in doubt about the matter, perhaps it should be made quite clear

that the hole is *not* equivalent to the positron (which is the antiparticle of the electron).

ANALOGY FOR HOLE CONDUCTION


The analogy shown in Fig. 1.3 may make the process of hole conduction clearer. Let us imagine a bookshelf containing five books, ABCD and E.

Book A is removed (by an external force) for reference, thus leaving an empty space or hole at the left hand end of the shelf.

Book B is moved into this space, and then the rest of the books, one at a time, are moved to the left.

Although each of the books have been moved, the net effect is the same as if a hole (that is, a book space) had moved from the left hand side to the right hand side in the opposite direction to the movement of the books.

Fig. 1.3. An analogy showing movement of a hole,

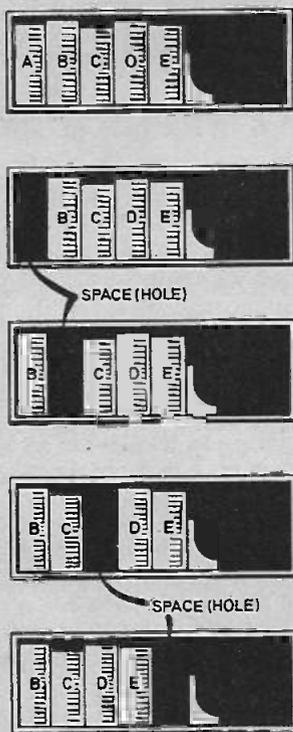

DOPING

The addition of donor or acceptor impurities to a semiconductor material is known as **doping**. A material is said to be **lightly doped** if it contains few impurity atoms per unit volume and **heavily doped** if it contains a relatively large number of impurity atoms.

BOTH TYPES OF IMPURITY

If a semiconductor material contains both donor and acceptor atoms, electrons from the

donor atoms will fill holes in the acceptor atoms. If the donor atoms are more numerous than the acceptor atoms, there will be more electrons than there are holes to be filled. The material will therefore be *n*-type.

Similarly, if there are more acceptor than donor atoms, there will not be enough electrons to fill all of the holes. The material will therefore be *p*-type.

As electrons tend to fill any holes they may meet as they pass through the semiconductor crystal, the number of holes in an *n*-type material will be less than the number of holes in the same volume of the pure semiconductor material.

Similarly, the number of electrons in a *p*-type material is less than in the pure semiconductor material, since the electrons keep tumbling into the more numerous holes where they are no longer free to move.

SUMMARY

As shown in Fig. 1.4, an *n*-type material contains mobile electrons. As the material is normally electrically neutral, there must be an equal number of positive charges to balance the charges of the electrons. However, these positive charges are fixed in position, as indicated by the broken circles around them.

In the case of *p*-type material, the positive holes are free to move, whilst the negative charges are fixed in position.

The very small number of holes in an *n*-type material and the free electrons in a *p*-type material are not shown in Fig. 1.4 since their numbers are so small. These charges are known as **minority carriers** because their numbers are far smaller than that of the carriers of opposite charge.

Thus the electrons in *n*-type material and the holes in *p*-type material may be referred to as **majority carriers**.

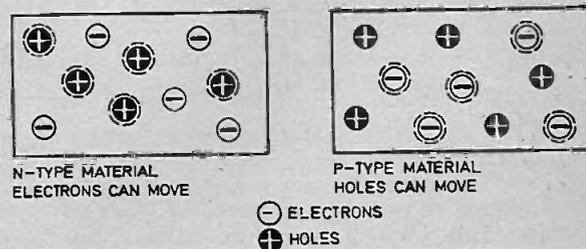


Fig. 1.4. *N* and *p*-type semiconductor materials. The broken circles show "fixed" charges.

The vast numbers of neutral atoms in any crystal are not shown in Fig. 1.4 since they play no part in the conduction process.

Suitably doped semiconductor materials employed in carefully designed devices have made modern miniature electronics possible.

Next month: Semiconductor diodes.



...time you made me

RAIN ALARM

A very useful device for the busy housewife.

by C. Embleton

GR^{EAT} BRITAIN is well known for its bad weather, and when the busy housewife hangs out her washing to dry, she often has to dash out and bring her washing in again as the rain starts to fall.

Sometimes she is busy in another part of the house, and by the time she realises that it is raining, the washing is quite wet again.

One answer to this problem is to install an electronic device which attracts the attention of the housewife before it is too late.

The Rain Alarm described here sounds an audible alarm as soon as the first few drops fall.

THE CIRCUIT

The complete circuit diagram of the Rain Alarm is shown in Fig. 1.

The circuit consists of a Veroboard sensor, a trigger circuit loaded with a relay, and a two transistor oscillator.

When rain falls on the sensor, the rain drop in effect connects the free end of R1 to the positive supply rail which causes a positive potential to be applied to the gate of the thyristor CSR1.

This immediately turns on the thyristor and causes current to flow through the relay RLA and the latter is energised. The thyristor does not turn off, this can only be done in this circuit by switching off the supply.

When the relay is activated, its contacts cause the oscillator circuit to be "made" and hence the audible alarm is heard through the loudspeaker.

The oscillator, which is of the relaxation type, functions in the following way: when the relay contacts close and make the circuit, a positive

bias is applied to the base of TR1 and to the emitter of TR2.

This positive bias switches on TR1 via R2 and this conducts a negative voltage to the base of TR2.

Because TR2 is a *pn*p transistor, this negative voltage switches on TR2. When TR2 conducts, it causes current to flow through the loudspeaker.

This positive signal is then passed back to the base of TR1 via C1 and the whole process is repeated producing a continuous tone for the whole time the relay contacts are closed. The pitch of the tone can be altered by changing the value of capacitor C1; increase C1 to decrease the pitch and vice versa.

The light dependent resistor PCC1 in series with the Veroboard sensor is included so that the alarm will not sound if it happens to rain during the night and the unit is switched on.

When the l.d.r. is subjected to dark conditions, its resistance is very high, in the order of megohms, and this prevents the gate of the thyristor receiving enough current for it to "fire."



Approximate cost
of components
including V.A.T.

£3.00

Components

Resistors

- R1 330 Ω
- R2 10k Ω
- $\frac{1}{4}$ watt \pm 10% carbon

Capacitors

- C1 0.1 μ F

Semiconductors

- TR1 2N3704 silicon *n*p*n*
- TR2 OC72 germanium *p*n*p*
- CSR1 CRS1/25-600 or any similar 1A device
- PCC1 ORP12 or similar

Relay

- RLA Post Office type 3000 with 400 Ω coil or similar (see text)

Miscellaneous

- S1 On/off toggle or slide
- LS1 3 ohm to 20 ohm loudspeaker
- B1 9V battery PP7
- Vero-board: 0.1in. matrix 5in. x 2 $\frac{1}{2}$ in., 0.15in. matrix 8 x 7 holes; battery connectors; 4-way terminal block; 4BA nuts, bolts and spacer; $\frac{3}{8}$ in. diameter dowel; length of two core cable; suitable case.

SEE
**SHOP
TALK**

In daylight conditions, the resistance of the l.d.r. is very low, and does not prevent the thyristor from firing.

RELAY AND LOUDSPEAKER

The relay used in the prototype was a Post Office type 3000 with a coil resistance of 400 ohms. It is not essential to use this exact type as any 9V relay with a coil resistance of 100 to 400 ohms will suffice.

If desired, the relay can be used to switch heavier loads, i.e. a power alarm, the limit of power being determined by the rating of the

relay contacts.

The loudspeaker used in the prototype had an impedance of 3 ohm, but this is not critical as any speaker up to 20 ohms will do.


CONSTRUCTION

Begin construction by cutting to size the Vero-board, 8 x 7 holes x 0.15in. matrix and making the necessary cut-outs on the reverse side, see Fig. 2.

Next, mount all the components as detailed in Fig. 2 leaving the transistors until last. Use a heat shunt on the legs of the transistors when soldering them in position.

Obtain a suitable case—the prototype used an old sandwich tin with lid—and fix the components RLA, LS1, S1, and the two-way terminal block in position. The layout shown in Fig. 3 is not critical and may be changed to suit individual requirements.

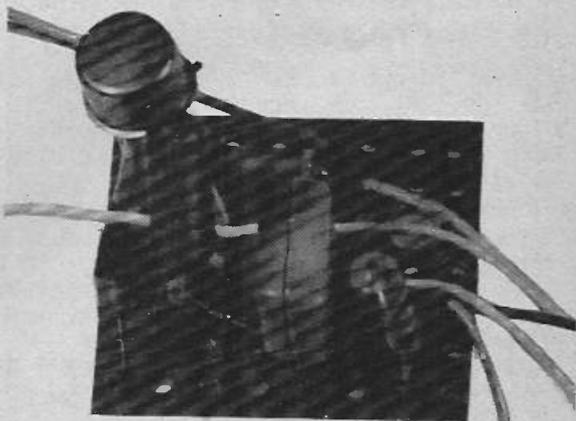With these components firmly fixed in position, wire up to the Veroboard as shown in Fig. 3 and then fix the board to the case using a 4BA nut, bolt and insulated spacer.



Photograph of the completed component board

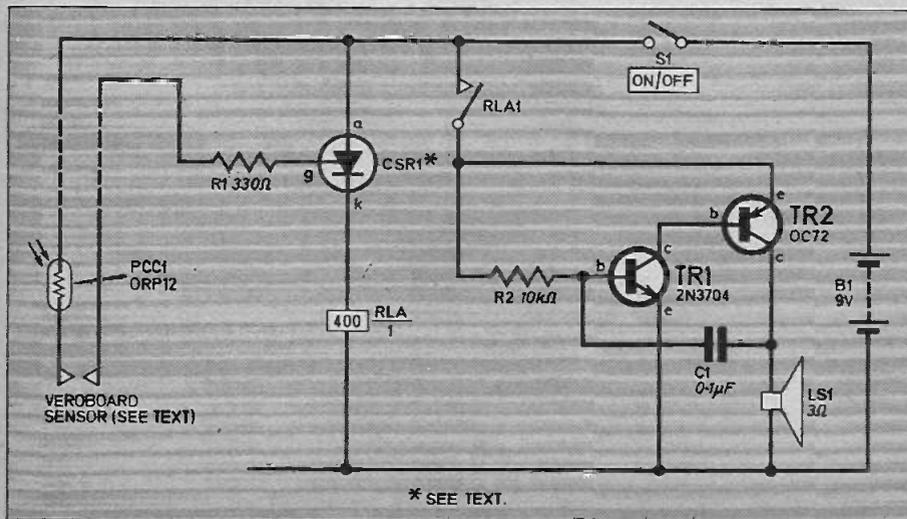


Fig. 1. The complete circuit diagram of the Rain Alarm. The l.d.r. prevents the alarm from sounding in dark conditions, i.e. at night.

RAIN ALARM

Fig. 2 (below). The layout of the components of the Veroboard.

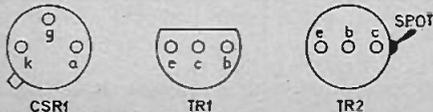
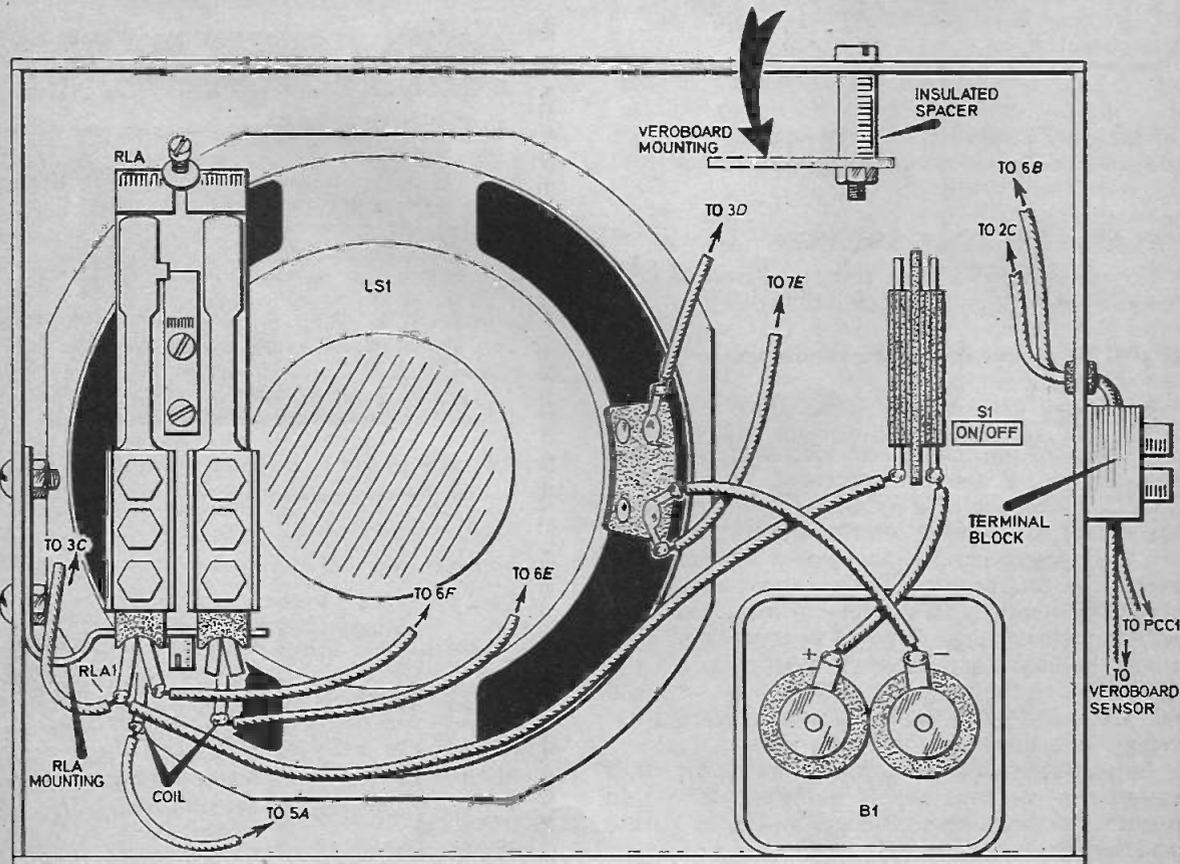
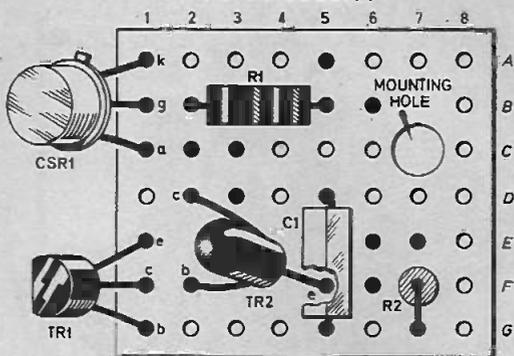
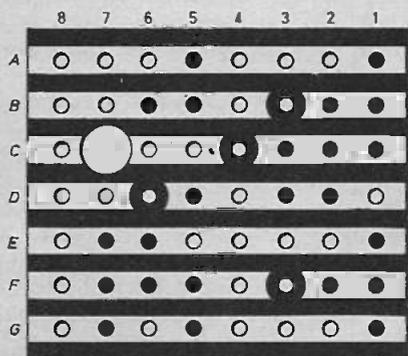


Fig. 3. (above). The complete wiring diagram of the Rain Alarm. Shown left are the thyristor and transistor lead outs viewed from the underside.

SENSOR

The sensor of the Rain Alarm should be made from a piece of 0.1-in. matrix Veroboard. The size used in the prototype was 5in. x 2½in.

The sensor is shown in Fig. 4 and the Veroboard has alternate strips joined at each end forming an interlocking finger pattern.

It is necessary to use 0.1-in. board to obtain the required sensitivity.

Wire up the l.d.r. to the Veroboard and the two-way terminal block and then glue to a piece of ¾in. diameter dowel. Araldite is a suitable adhesive.

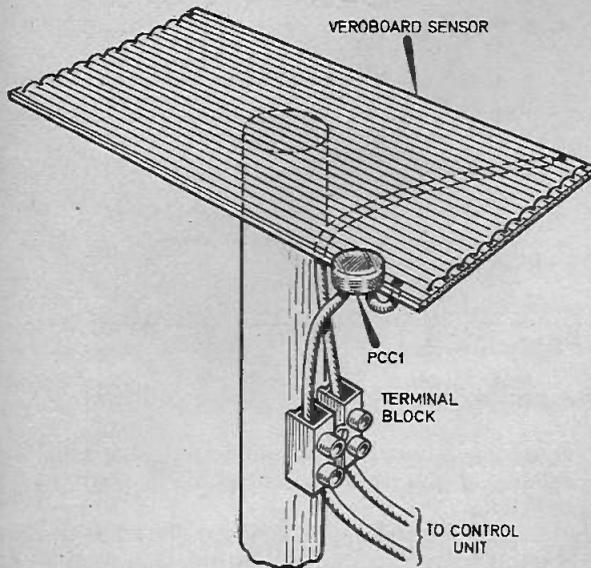


Fig. 4. Details of the Veroboard sensor.

TESTING

Before testing, check all wiring in the main control case. If satisfied, proceed.

Join, by means of a length of two-core cable, the sensor to the main unit and switch on.

Under bright conditions, place a wetted finger across the copper strips of the sensor and a tone should be heard from the loudspeaker; this tone will persist when the finger is removed and even when the board is completely dried.

To remove the tone, the unit must be switched off. Immediately switching on again should not trigger the alarm if the board is dry.

Repeat the above test procedure under dark conditions—no tone should be heard. If you do not obtain these results, check out your wiring and rectify.

MOUNTING AND USE

The sensor should be mounted somewhere in the garden such that it will not be sheltered from rain or daylight. It is recommended that the sensor should be mounted at an angle so that

the rain will run off; the photocell must be uppermost.

The control unit is mounted in the house so that its tone can be heard anywhere in the house when it is raining. Join the two parts by means of a suitable length of two core cable.

The unit is switched on when the laundry is hung out to dry and the alarm will sound when the first few drops of rain fall.

To reset the alarm, the unit is switched off by switch S1 and, assuming it has stopped raining, the switch can be switched on again after the sensor has become dry. If the sensor is not dry the alarm will continue.


The Rain Alarm can be left on permanently, hence the purpose of PCC1, since the current drain with no rain is minute, the battery should last for a couple of months or more.

Finally the sensor board should be cleaned every couple of months to ensure maximum sensitivity. □

What do you know?


RESISTORS

- 1 What are the missing numbers in this series, and what is the series called?
1.0, 1.2, 1.5, ? 2.2, ?
- 2 What is the overall tolerance of two ± 5 per cent tolerance resistors wired in series?
- 3 What does the pink band on some carbon resistors mean?
- 4 What are the following resistor values?
(a) 4K7; (b) 1R0; (c) red, red, red; (d) yellow, mauve, gold; (e) 4M7K
- 5 What do the following symbols represent?

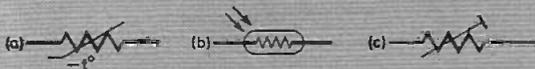

ANSWERS

- 1 1.8 and 2.7. They are preferred resistance values in the series designated E12. The series contains 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades e.g. 47K Ω .
- 2 ± 5 per cent—addition of the tolerance does not occur, e.g. a 100 Ω 5% resistor having a true value of 105 Ω , plus another similar resistor, equals 210 Ω which is still within 5% of the new total.
- 3 The pink band signifies a high stability resistor. (The last letter, represents the tolerance e.g. M = $\pm 20\%$, K = 10%, J = $\pm 5\%$, H = $\pm 2.5\%$, G = $\pm 2\%$, F = $\pm 1\%$.)
- 4 (a) 4.7k Ω (b) 1 Ω (c) 2.2k Ω (d) 4.7 Ω (e) 4.7M Ω
- 5 (a) A thermistor (temperature dependent resistor) (b) A light dependent resistor (or photoconductive cell) (c) A variable preset resistor.

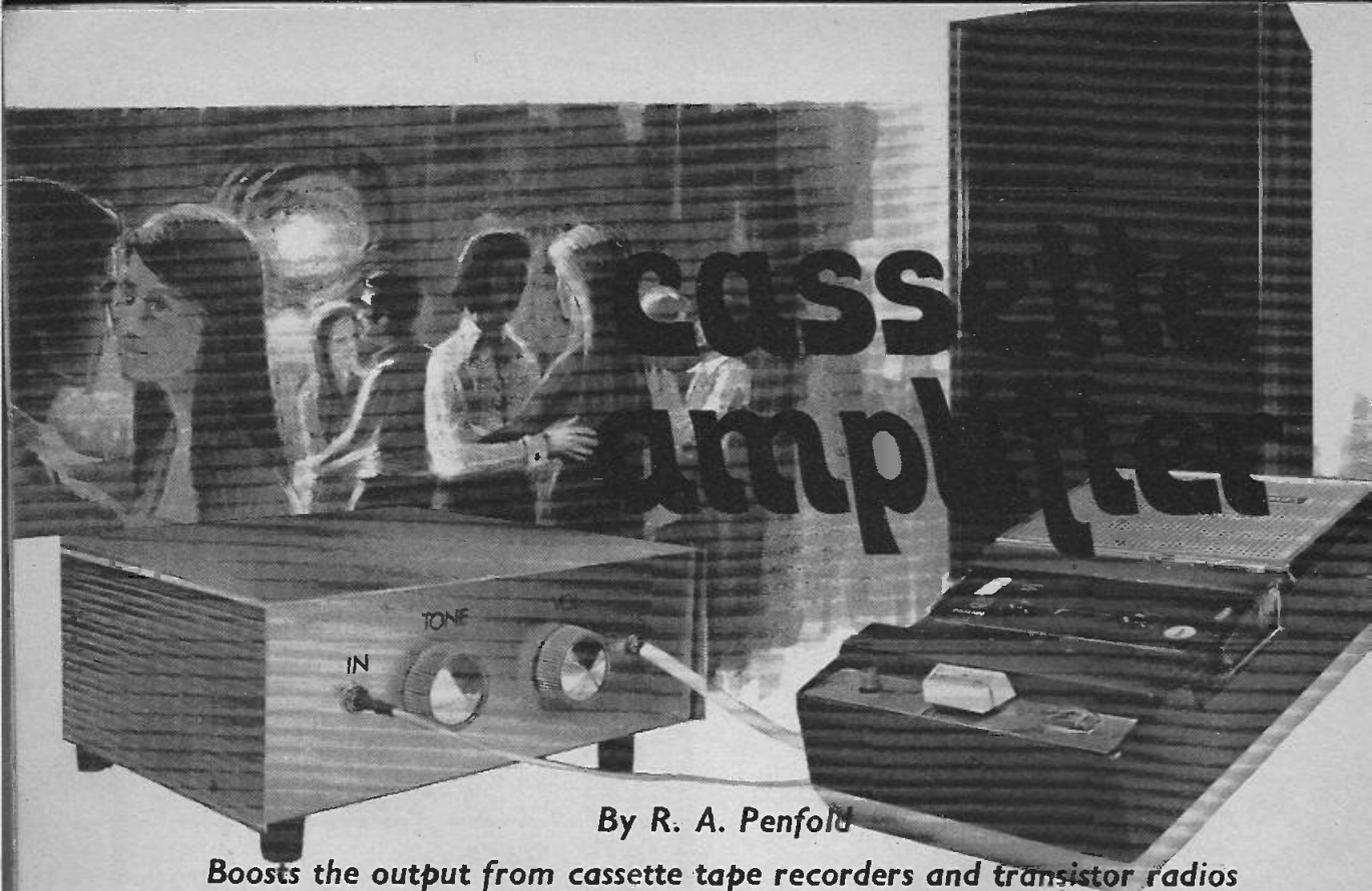

By R. A. Penfold

Boosts the output from cassette tape recorders and transistor radios

DUE to their small size, low cost, and portability, cassette tape recorders have become extremely popular. These do, however, usually suffer from having a rather limited output power (typically 500 milliwatts), and only a small internal speaker. The quality of the output is not therefore all one would desire.

It was therefore decided to construct an amplifier which would boost the output of the recorder to two or three watts, which is sufficient for most domestic requirements.

While it was originally intended to modify the recorder to take the output from its volume control circuit, so as to obtain a virtually noise, and distortion free signal, this was not found necessary, and perfectly satisfactory results were obtained by taking the output from the earphone socket.

The amplifier can be used in the same way with small pocket radio receivers.

CIRCUIT THEORY

A circuit diagram of the cassette recorder amplifier is shown in Fig. 1, VR1 is the volume control, which consists of a variable voltage divider. The full input signal voltage will be present across VR1; the slider can tap all, or part of this voltage.

Capacitor C1 is a d.c. blocking capacitor which feeds the alternating input to the base of TR1. The voltage set at the base of TR1 by the biasing

resistors, R1 and R2 would be altered with the setting of the volume control if C1 were to be omitted.

Transistors, TR1 and TR2 are wired as a Darlington pair. The Darlington pair is a method of connecting two transistors together in such a way that they in effect form a single transistor with a gain equal to that of the product of the gains of the two transistors—approximately 20,000 in this case.

OUTPUT STAGE

Resistors R1 and R2 bias the Darlington pair so that about half the supply voltage appears at TR2 collector.

Transistors TR3 and TR4 form the complementary class B output stage.

The output transistors are used in the common collector (also known as the emitter follower)



**Approximate cost
of components
including V.A.T.
£4.50 plus case**

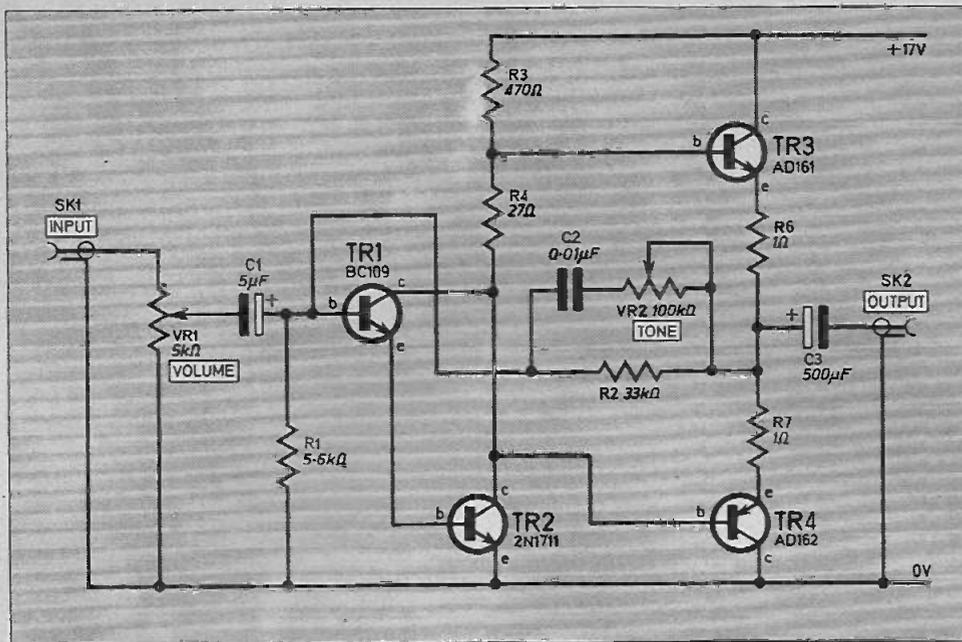


Fig. 1. Circuit diagram of the Cassette Amplifier.

configuration. An emitter follower has almost exactly unity voltage gain, but has considerably more current available at the output (the emitter) than is put in at the base. It has a very low output impedance compared to the input impedance. The output transistors are thus able to match the 500 ohms output of TR2 to the 8 ohms impedance of the speaker.

OUTPUT STAGE OPERATION

It will be easier to understand the operation of the output stage if reference is made to the skeleton circuit diagram, Fig. 2.

With no input signal applied to the amplifier, the voltage at TR3 and TR4 emitters will be the same as that at their bases (approximately half the supply voltage). The transistors are in effect working from two separate 8.5 volt supplies. As the output transistors stand, only leakage currents will flow, as their bases are in effect earthed.


If we now consider a positive pulse applied

at TR1 base, this will cause TR2 to conduct more heavily, the voltage at TR3 and TR4 bases falling in consequence. This will cause the voltage at TR3 base to in effect fall below "earth", and TR3 will remain cut off. However, the base of TR4 will now in effect be above "earth", and it will conduct heavily. The voltage at its emitter will drop for the duration of the pulse, and then return to normal.

If a negative pulse is now applied at the input, TR2 will conduct less heavily, causing the voltage at TR3 and TR4 bases to increase. Now TR4 will be cut off, while TR3 conducts for the duration of the pulse, causing the voltage at the output to swing to a high level, and then back to normal. Thus TR4 amplifies positive input half cycles, while TR3 amplifies negative input half cycles.

The capacitor between the output, and the loudspeaker LS1 is required to block direct currents from entering the speaker.

Fig. 2. Basic amplifier diagram.

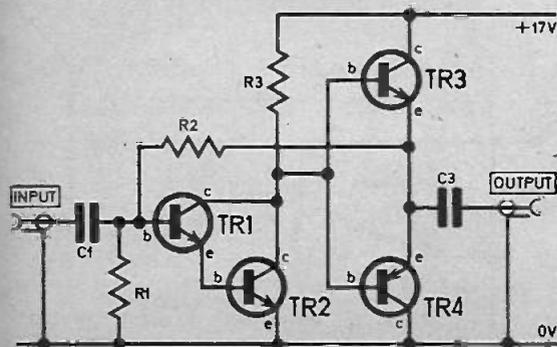

EXTRA COMPONENTS

Comparing the circuit of Fig. 1 with the skeleton circuit of Fig. 2, it will be noticed that in Fig. 2, R4, R6 and R7 are omitted.

Resistor R4 is required in order to minimise cross-over distortion.

This distortion is due to the fact that a germanium transistor (which the output transistors are) will not begin to conduct between its collector, and emitter terminals until about 0.2 volts is present at its base. When it is just turning on it has rather a non-linear characteristic; R4 is used to give a small biasing voltage to the output transistors, and so overcome cross-over

distortion, reducing it to an unnoticeable level.

Resistors R6 and R7 are current limiting resistors, which are required as a precaution against damage to the output transistors due to what is termed "thermal runaway".

NEGATIVE FEEDBACK

The biasing resistors for the Darlington pair obtain their biasing current from the output, and the biasing will alter as the output voltage fluctuates. This is in order to give negative feedback to the circuit. Negative feedback is required in order to reduce distortion. It also greatly reduces the gain of the circuit, but the distortion is reduced by a greater amount than the required signal.

Providing the amplifier is perfectly linear, the feedback will be linear also, and its only effect will be to reduce the gain of the amplifier.

No amplifier yet designed is completely linear, and thus the feedback will not be linear either. As the feedback is negative, however, this non-linearity will be in opposition to the non-linearity of the amplifier, and will tend to cancel out the distortion.

TONE CONTROL

In the output from the tape recorder there will be a certain amount of high frequency noise, known as tape hiss. Potentiometer VR2, and capacitor C2 form a simple tone control which can greatly reduce the high frequency response of the amplifier, and consequently this noise.

POWER SUPPLY

A stabilised mains power supply giving about 17V at up to 500 mA is incorporated in the amplifier. A circuit diagram of this is shown in Fig. 3. Switch S1 is the on-off switch which is ganged with the volume control, VR1. The mains transformer, T1, reduces the mains supply of 240V down to 12-15V. This refers to the r.m.s. value, and the peak value will be a little over 1.4 times this.

The bridge rectifier D1-D4 converts the alter-

nating currents from the mains transformer to a pulsating direct current.

Transistor TR5 is connected as an emitter follower. Resistor R5 and D1, the Zener diode, are used to hold the base of TR5 at 18V. In an emitter follower circuit using a silicon transistor, (such as TR5) the emitter voltage will be the same as base voltage, minus about 0.5 to 1 volt. The voltage at the output is thus stabilised at about 17 to 17.5 volts. Capacitor C5 smooths the output in the same way as C4, giving an almost ripple free output.

CONSTRUCTION

The unit is housed in a home made aluminium case measuring approximately 7 by 6 by 2 $\frac{1}{2}$ inches. This is made in two sections, one forming the base, front, and rear, and the second forming the sides and top. The two are fastened together by four self tapping screws. Details of the case are given in Fig. 4. It is made from 18 or 22 s.w.g. aluminium sheet.


The three power transistors, TR3, TR4, and TR5 are mounted on the rear of the case. TR3, and TR5 must be insulated from the case using the insulating mica washers and plastic bushes supplied with the AD161/162 matched pair. The AD162 (TR4) case, which is the connection to its collector, is connected to the negative supply, which is in turn connected to the case. There is therefore little point in insulating this transistor from the case. The spare insulating set should be used for the BD124 transistor, TR5.

No dimensions are given for the positioning of the mounting holes for the power transistors, in Fig. 4, as these are best found by using a mica insulating washer as a template—taking care not to damage the washer.

No exact dimensions are given for the mounting of T1, the 8-way tag strip, or the bridge rectifier, only their approximate positions being given. This is because the mountings for these components can vary tremendously. Usually the components themselves can be used as templates.

As well as details of the case, Fig. 4 also gives constructional details of the mounting bracket

Fig. 3. The stabilized power supply for the amplifier.

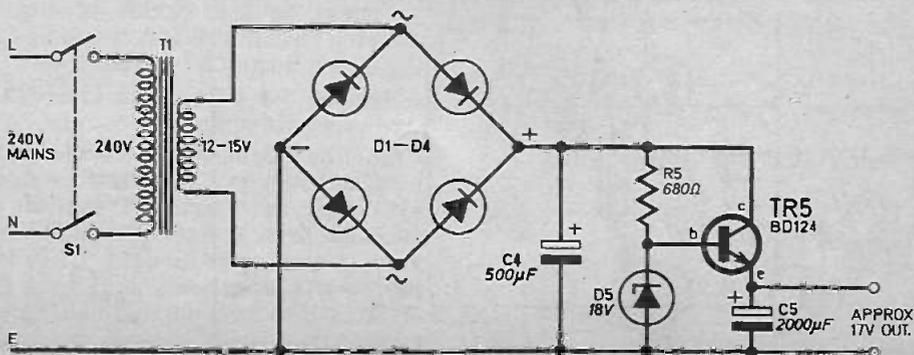

cassette amplifier

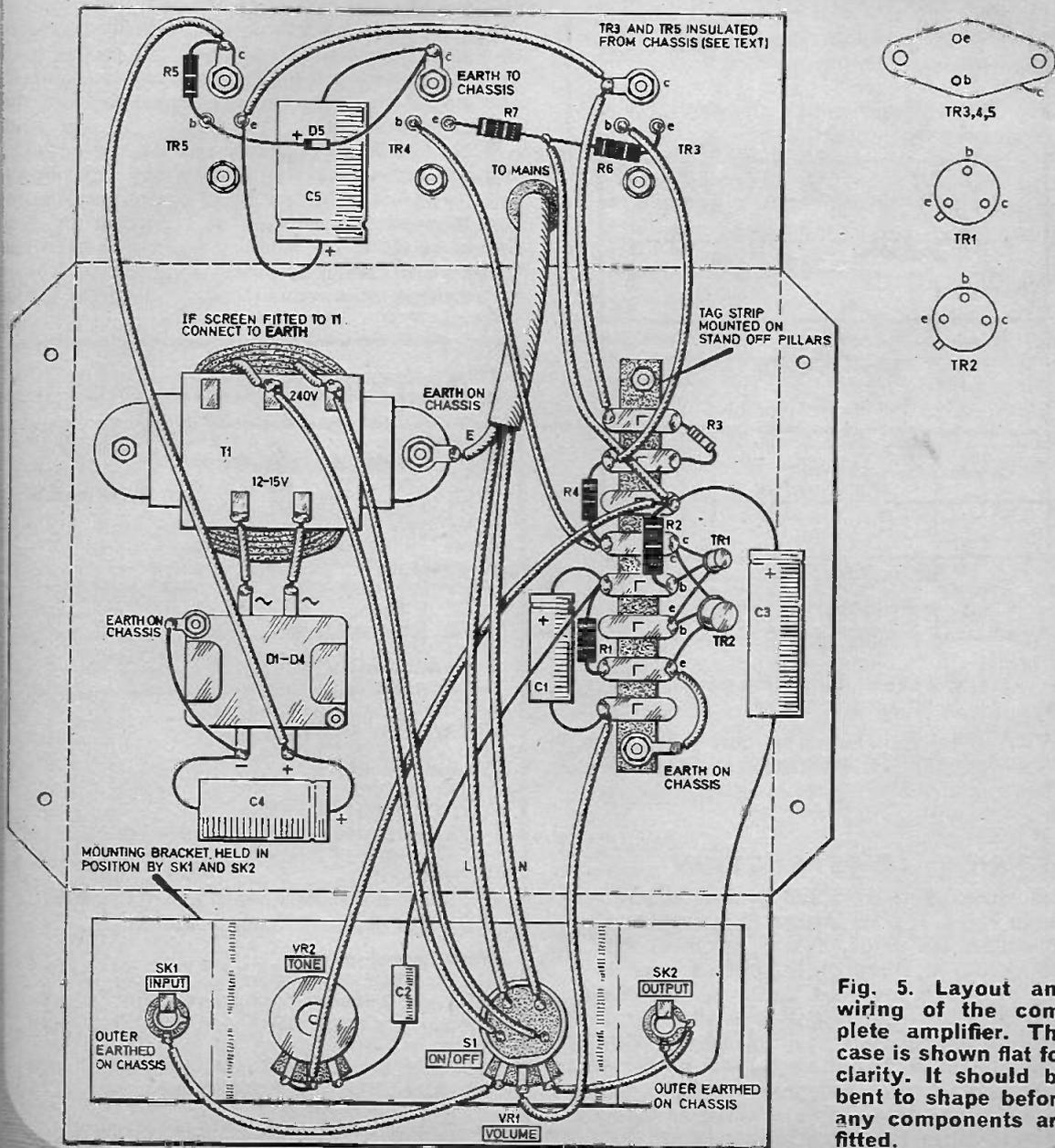
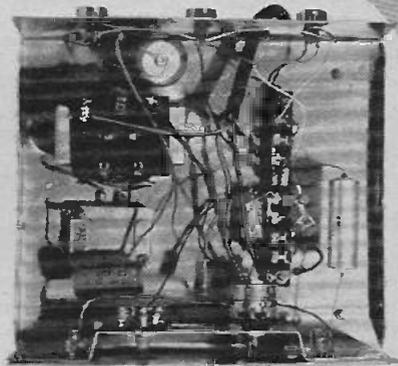


Fig. 5. Layout and wiring of the complete amplifier. The case is shown flat for clarity. It should be bent to shape before any components are fitted.

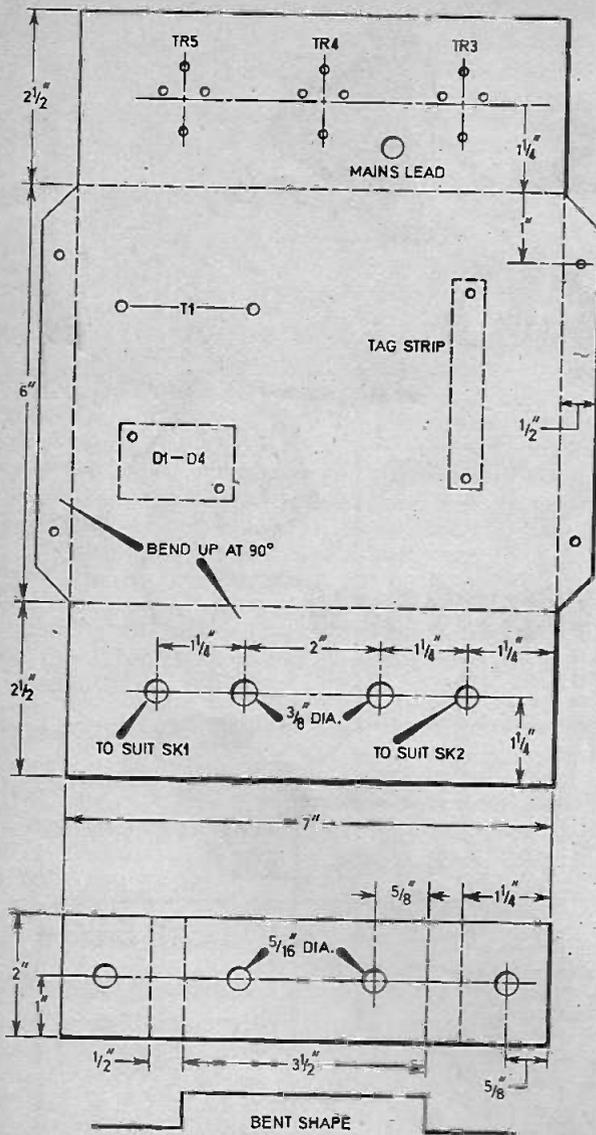


Fig. 4. Case construction details.

for VR1, and VR2. Details of how this is fixed are shown in Fig. 5. This bracket is to enable the control knobs to fit flush against the front panel.

ELECTRICAL CONSTRUCTION

Full wiring details of the complete unit are given in Fig. 5. It is important to make sure that no mistakes are made, as any incorrect wiring could result in ruining components, and as a mains supply is involved, could be dangerous.

The wiring up of the tag strip should be undertaken first and is quite easy, providing each of the component leads, and each tag is tinned with solder, before wiring is commenced. The connection to the negative supply is made to a solder tag on one of the tag strip mounting bolts.

The tag strip must be mounted on stand off insulators, so as to prevent the connections underneath the strip from being short circuited through the metal case. Use a heat shunt when soldering in the transistors and finally wire up the remaining circuitry.

The amplifier should be connected to the mains supply by way of a three core mains lead and a three pin plug fused at 1 amp. Check the wiring carefully before switching on.

USING THE AMPLIFIER

An external loudspeaker is required, and this should have an impedance of 8 ohms, and be capable of handling at least three watts. This is plugged into the output socket.

To connect the amplifier, and the cassette recorder, a screened lead about 18 inches long with a 3.5 mm. jack plug at each end is required. The output from the recorder is taken from the earphone socket.

Best results will probably be obtained with the volume control on the recorder set fairly high, so as to obtain a low degree of background noise. If a tone control is fitted on the recorder, this should be set to the midway point, and then the tone control on the amplifier is set for the lowest background noise, consistent with a good treble response.

Components....

SEE
**SHOP
TALK**

Resistors

R1 5.6k Ω	R5 680 Ω
R2 33k Ω	R6 1 Ω
R3 470 Ω	R7 1 Ω
R4 27 Ω	All $\frac{1}{4}$ W \pm 10%

Capacitors

C1 5 μ F elect. 25V	C4 500 μ F elect. 25V
C2 0.01 μ F	C5 2,000 μ F elect. 25V
C3 500 μ F elect. 25V	

Potentiometers

VR1 5k Ω log. carbon with d.p.d.t. ganged mains switch (S1)
VR2 100k Ω lin. carbon

Semiconductors

TR1 BC109
TR2 2N1711
TR3 AD161
TR4 AD162
TR5 BD124
D1-D4 24V, 500mA metal bridge rectifier
D5 18V, 400 mW Zener diode

Miscellaneous

T1 12-15V, 500mA mains transformer
SK1, 2 3.5mm jack sockets (2 off)
8-way tag strip, mains lead and fused 3-pin plug, 1A fuse, stand off mounting pillars, control knobs (2 off), aluminium for case (see text), connecting wire, earth tags, 4BA fixings, rubber feet.

The X25

Why two shafts?

220-240 Volts or 100-120 Volts.

Model X25

The leakage current of the X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".

Tested at 1500v A.C. 25 watt. Fitted long-life iron-coated bit 1/8"

2 other bits available 3/32" and 3/16"


Price: £1.75 (rec. retail) P & P 8p

"elementary"

One ceramic shaft to give you near-perfect insulation and negligible leakage current (only 3-5 microamps) so that you can safely solder delicate and expensive integrated circuits and transistors, even when "live"

Another shaft, of stainless steel, to give you the strength required of an everyday robust general purpose iron.

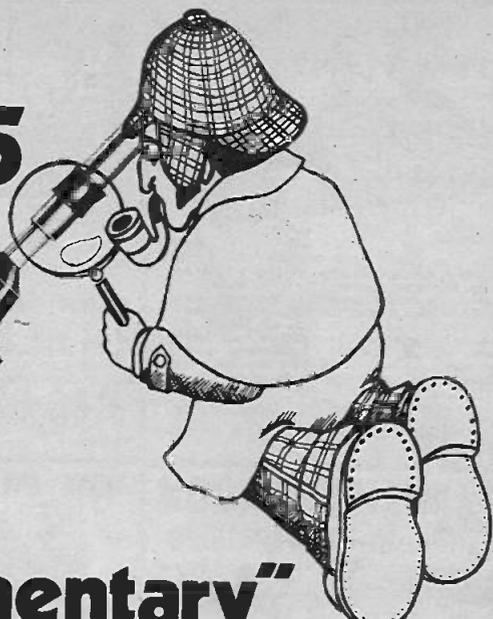Plus large volume long-life bits to store the enormous heat-capacity of the 25 watt element. Bits that do not stick (no screws or pins) and bits that slide over the element shaft to give you efficient heat transfer and a capacity equivalent to irons of 2-3 times the wattage.



MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage.

Test voltage 4000v A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".

PRICE: £1.80 (rec. retail) OR Fitted with triple-coated, iron nickel and Chromium bit 1/8". PRICE: £1.95 (rec. retail). P&P5p

MODEL G

18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.

PRICE: £1.83 (rec. retail). P&P5p



All prices mentioned are exclusive of V.A.T.

MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24. PRICE: £1.70 (rec. retail). P&P5p

MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.

PRICE: £1.70 (rec. retail). P&P5p

MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16"

bit, 2 spare bits 5/32" and 3/32", heat sink, solder, and "How to Solder" booklet.

PRICE: £2.40 (rec. retail). P&P8p

MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with book-


let "How to Solder"

PRICE: £1.95 (rec. retail). P&P12p

MODEL SK.1-KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: £2.75 (rec. retail). P&P12p

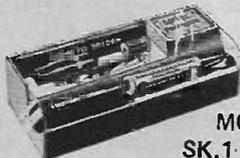

From radio or electrical dealers, car accessory shops or in case of difficulty direct from: ANTEX LTD. FREEPOST (no stamp required) PLYMOUTH PL1 1BR. Tel: 0752 67377.

- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000) Reg. No: 393594

NAME

ADDRESS

EE6

PREMIER 800 STEREO AMPLIFIER



(As used in
SYSTEM '800')

A truly high quality stereo amplifier—compare the specification, compare the price. Output: 6 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 160mV. Tape 100mV. Tape out 160mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch, Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 8½" x 2½".

ONLY £16.50 Carr. 50p.

Mk. 11 Version available with Teak Finish Cabinet. £17.87. Carr. 50p.


PREMIER HI-FI STEREO SYSTEMS

SYSTEM "800"

Consists of the Premier 800 Mk II all transistor stereo amplifier (described left) Garrard auto/manual record player unit fitted stereo/mono cartridge with diamond stylus and mounted in teak finish plinth with cover and two cloth front loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 800 Mk II amplifier has an output of 6 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch, Headphone socket. Power on/off. Teak finish cabinet with aluminium front panel. Size: 12½in x 6½in x 2½in.

£36.50

Carr. £1.75

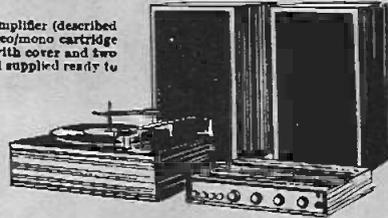

SYSTEM "TWO"

as above but with slotted front teak finish loudspeakers, Garrard SP25 Mk. III and magnetic cartridge.

£46.50

Carr. £1.75

SYSTEM "THREE"

This consists of KLINGER K4903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and Ceramic pick-up, tuner, tape in and out. Stereo headphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone STAROD diamond stereo cartridge. A pair of EMI Speakers size 16½" x 10½" x 10½" Carr. x 9" fitted EMI units complete £60.00 £1.75 the matching system.

FREE
LEADS
AND PLUGS
SUPPLIED
WITH ALL
SYSTEMS

PREMIER PARAGON STEREO HI-FI AMPLIFIER



Gives the best possible reproduction of records, radio and tape at a reasonable price. Fitted with all the controls and facilities you're ever likely to want, the Paragon gives you a degree of

sophistication that is usually only found with amplifiers costing twice its price. It has bass and treble slide controls, volume and balance knobs, and eight push-buttons. There's also a standard stereo jack socket on the front panel, plus a ceramic/magnetic cartridge switch and a mains outlet socket on the back panel.

Specifications 10 + 10 watts into 8 ohms. Power/frequency response: 0dB 10 watts into 8 ohms -3dB 20Hz - 25KHz. Distortion typically less than 0.25%. Inputs for Magnetic phono (4mV) Ceramic phono (66mV) Radio/Tape (100mV). High and low filters. Teak finish cabinet. Size: 12½" x 6½" x 10½".

£27.00 P. & P. 50p.

PREMIER STEREO SYSTEM '64'

Consists of the Premier Paragon Stereo Amplifier, Garrard SP25 III in teak finish plinth with cover and fitted Goldring G800 stereo magnetic cartridge plus a pair of Marsden Hall Annex 100 Loudspeaker Systems. Complete with Freecads and plugs. £64 Carr. & Insurance £1.75

VERITAS STEREO/MONO SOUND MIXER

Battery operated audio mixer. Size 6 x 3 x 2in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono/plugs output. Attractive teak wood grain finish case.



PREMIER PRICE £3.80

P. & P. 15p



E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2½in tweeters and crossover network. Impedance 8 or 16 ohm. Handling capacity 10W. Brand new.

£3.80 P. & P. 50p

NEW PREMIER COMPACT STEREO SYSTEM



All transistor stereo amplifier mounted into teak finish plinth with cover and Garrard 2025 T/C autochanger and a pair of matching teak finish cloth front speaker systems.

- ★ Output 4 watts rms per channel.
- ★ Separate volume, bass, treble and balance controls.
- ★ Stereo/Mono ceramic cartridge.
- ★ Tape/Tuner input and Tape output sockets.
- ★ Complete with all leads ready to use.

PREMIER PRICE ONLY £31.00 Carr. & Ins. £1.50



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE. COMPLETE IN TEAK PLINTH WITH COVER.

PREMIER PRICE £16.86

P. & P. £1

METER BARGAIN

MODEL LT 102 MULTIMETER
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 15, 150, 600 (1,000 opV). AC Voltage: 15, 150, 600 (1,000 opV). DC Current: 150mA. Resistance: A-100K ohms. (centre 2.5K ohms) £2.71 P. & P. 25p complete with test leads and battery



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in. speaker units with volt padded car muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug. £2.47 P. & P. 25p.



ROGERS RAVENSBROOK SEMI-PROFESSIONAL MODEL (as illustrated). (List £18.60).

OUR PRICE £12.10
AKAI A588 £6.00
SENNHEISER HD414 £9.90 P. & P. 25p each



E.M.I.

LOW NOISE CASSETTES in library cases

C60 48p
C90 70p
C120 92p
P. & P. 10p



LOW-NOISE COMPACT CASSETTES

Screw fixing—fully guaranteed. In Library cases.

	EACH	3 for	6 for	10 for
C60	31p	89p	£1.71	£2.75
C90	44p	£1.22	£2.38	£3.85
C120	57p	£1.54	£3.04	£4.95

P. & P. 10p each (3 and over 15p)

QUALITY RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

TT3 3' 450' POLYESTER 40p	DT6 6' 51" 1800' POLYESTER £1.23
DT3 3' 600' POLYESTER 62p	TT6 6' 2400' POLYESTER £2.06
SP5 5' 600' P.V.C. 48p	EP7 7' 1800' P.V.C. 68p
LP5 5' 900' ACETATE 55p	LP7 7' 1800' ACETATE 62p
DT6 6' 1200' POLYESTER 82p	DT7 7' 2400' POLYESTER £1.57
LP6 6' 1200' ACETATE 88p	TT7 7' 3600' POLYESTER £2.76

TAPE SPOOLS 3" 5p, 5" 5½", 7" 9p.
Post and Packing 3" 5p, 5" 5½", 7" 10p (3 reels and over Post Free).

"Litesold" Soldering Iron. Lightweight ½" pencil bit. Ideal for regular beach use and around the home. 25 watts. 240 volt A.C. £1.85 P. & P. 16p.

ALL PRICES INCLUDE VAT

NEW BRANCH NOW OPEN

56 GEORGE STREET, LONDON W1H 5RF

Tel: 01-935 7197

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



DEMO CIRCUITS

7

By MIKE HUGHES

The Differential Amplifier

As its name implies the differential amplifier operates by amplifying differences between two input signals. This operation is frequently required to show very small variations in quite large levels of electronic signal between that produced by a standard—or reference—and a variable. Imagine an application where you want to measure minute differences in lighting level that can be detected by a couple of photoelectric cells, one of which is illuminated by a standard level.


SIMPLE DIFFERENTIAL AMPLIFIER

The simplest form of differential amplifier is shown in general form in Fig. 7.1. Sometimes this circuit is called a long tailed pair—those who can remember valves will no doubt recall the term—because the emitters of both transistors terminate in a single emitter resistor (R4); this resistor forming the “tail” to the pair.

Imagine that the circuit in Fig. 7.1 is broken at the point C. Transistor TR1 becomes a straightforward common emitter amplifier biased into a quiescent operating condition by the potential divide effect of R1 and R2. If the transistors are silicon types the potential at point B will be 600mV less than the potential set at A and the current that flows between collector and emitter will produce a voltage drop across R3 giving a quiescent potential at the collector of TR1.

If we now reverse the operation and imagine that the circuit is broken at point B, TR2 is

Fig. 7.1. Circuit of the simple differential amplifier.

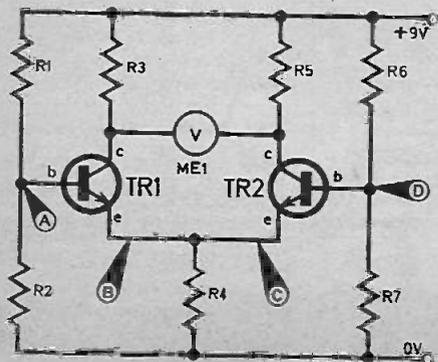

biased in exactly the same way as TR1 and if h_{FE} and the forward base/emitter drop are the same in both cases and identical biasing resistors are used, the quiescent potential at TR2's collector will be the same as at TR1 collector. Assuming both transistors are operating independently with separate emitter resistors a voltmeter (ME1) connected between the collectors would show a voltage difference of zero.

Imagine what would happen if a single emitter resistor is shared by the two transistors as shown in Fig. 7.1. The resistor (R4) having a value exactly half that of the imaginary independent resistors. Assuming both transistors are absolutely identical in every parameter and that all equivalent resistors have the same value, the circuit would act in the same way as before; the potential at B would equal that at C. A would equal D and the quiescent collector potentials would be the same.

Each transistor would be able to draw the same emitter current as before because we have halved the value of the emitter resistor and it will have twice the current flowing through it.

If we now reduced the value of R6 the potential at D will increase and more base current will flow in TR2. Several things now happen simultaneously, the potential at C will rise to become 600mV less than D and the potential at TR2's collector will fall because we are passing more base current; however that is not all! Because C and B are the same point (electrically) the potential at B will also rise; there will be less current drawn into the base/emitter circuit of TR1 and TR1 will conduct less between collector and emitter and thus its collector potential will rise.

Notice that there is a “see-saw” action; TR2's collector voltage falls and TR1's rises. Increasing the value of R6 to a value greater than R1 would produce the opposite effect. If R1 and R6 were photo conductive cells and R1 was illuminated by a standard source you can see that, provided both cells have identical photo-resistive characteristics, our circuit would show up differences in lighting levels falling on the two cells. The difference would be seen both in magnitude and direction if a centre zero meter was used as the voltmeter (ME1).

PRACTICAL CIRCUIT

We have, of course, assumed ideal characteristics so far and unfortunately it is impossible to get perfectly matched transistors—or for that matter resistors. Our practical circuit takes this into account and we compensate for slight differences in emitter current drawn by the two transistors with VR1 in Fig. 7.2.


As there is no centre zero meter on the Demo Deck a diode bridge is used to feed ME1; the diodes ensure that current always flows the same way through the meter, irrespective of whether TR1's collector is more positive than TR2's or vice versa. We therefore will not be able to see the direction of difference signals.

Wire up the circuit of Fig. 7.2 on the Demo Deck (Fig. 7.3) but initially make sure the circuit is broken at point X and temporarily connect a shorting link between both transistor bases (this is for setting up purposes to ensure that both transistors have identical bias conditions while we compensate for variations in their parameters). Set VR2 to the top of its track so that plenty of bias current is available; if you have a multimeter measure the collector potentials and see if you can tell whether both

transistors are passing identical current—one will almost certainly be conducting more than the other.

Imbalance will be shown on ME1 but the direction of imbalance will not be obvious. The difference in collector currents is caused by slight differences between the transistors' base/emitter voltage drops and can be compensated for by adjustment of VR1. The latter should be set so that ME1 reads zero and it should then stay at zero irrespective of what bias current is then applied to both transistors from VR2.

Remove the shorting link and connect up the photo conductive cell (PCC1) together with R6 and R7. The bias on TR2 will now be dependent on the amount of light falling on PCC1 and this—almost certainly—will be different from the last bias setting we had on TR1 from VR2; as a result ME1 will show a large deflection. Carefully re-adjust VR2 until ME1 again reads zero; thus restoring identical bias currents on both sides. Any small variations in lighting level on PCC1 will now show a positive indication on ME1 and the reading can be made extremely sensitive by shorting out the voltmeter series resistor R3.

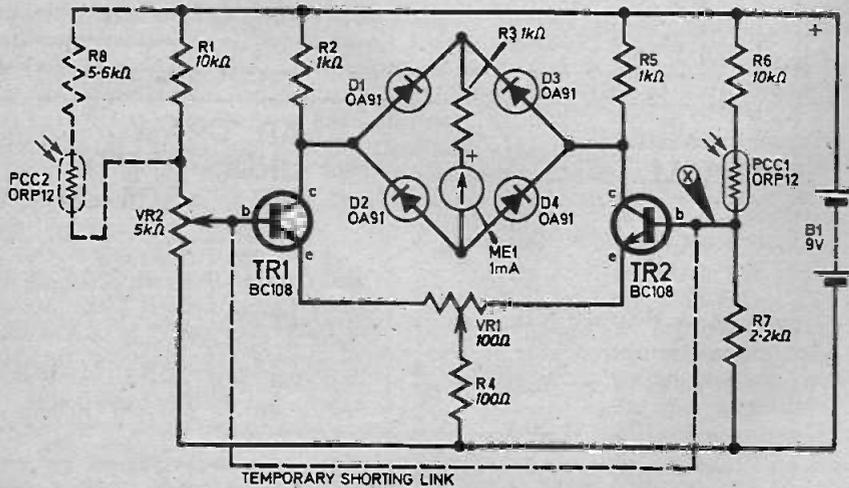


PHOTOMETER

If you have another ORP12, try experimenting with a simple photometer by discarding R1 and re-connecting R8, PCC2 and VR2 as shown in Fig. 7.2. When identical illumination falls on PCC1 and PCC2 adjust VR2 so ME1 reads zero; from then on any differences in light level on the two cells will show as an indication on ME1.

Fig. 7.2. (above) The practical differential amplifier circuit.


Fig. 7.3. (right) Layout and wiring of Fig. 7.2 on the Demo Deck.

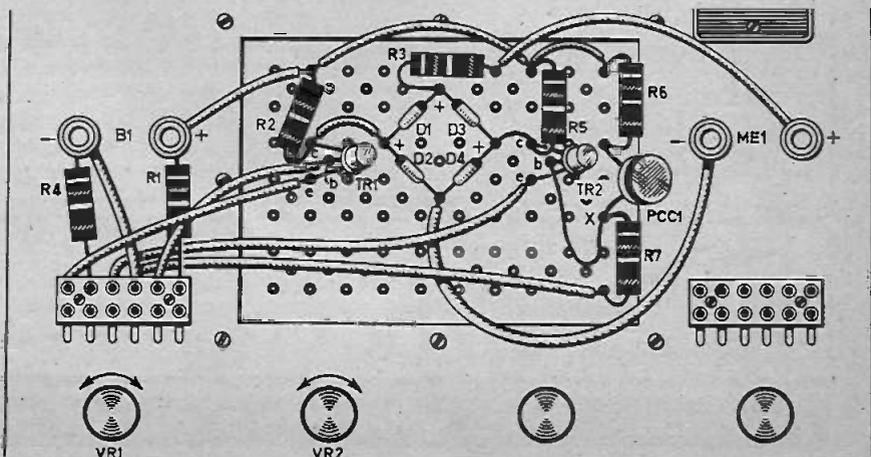

look! electronics really mastered

... practical
... visual
... exciting!

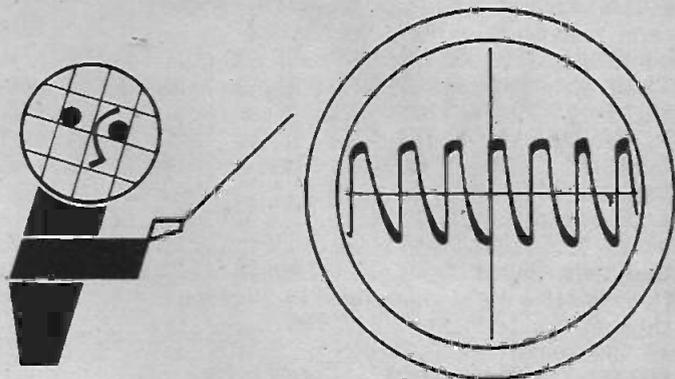no previous knowledge
no unnecessary theory
no "maths"




RAPY

BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

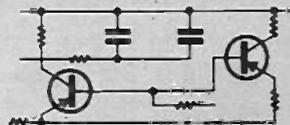2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EEB 54


special free gift also to all our students

TRANNIES

£19.50 ELECTRONIC DIGITAL CLOCK
(For complete kit of parts including case.)

1 DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX
Phone Harlow 37739

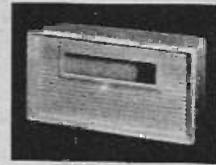P/P 10p. Price list S.A.E. (Saturday callers welcome)
ALL PRICES INCLUDE VAT



This 4 digit 24 hour clock is available to readers at this special price for 1 month only. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

74 Series TTL

1		25		1		25		1		25	
SN7400	16p	15p	SN7423	56p	50p	SN7450	16p	15p	SN7489	6-80p	5-85p
SN7401	16p	15p	SN7425	56p	50p	SN7451	16p	15p	SN7490	74p	72p
SN7402	16p	15p	SN7427	48p	48p	SN7453	16p	15p	SN7491	1-10p	1-04p
SN7403	16p	15p	SN7428	77p	72p	SN7454	16p	15p	SN7492	74p	72p
SN7404	16p	15p	SN7430	16p	15p	SN7460	16p	15p	SN7493	74p	72p
SN7405	16p	15p	SN7432	94p	48p	SN7470	38p	28p	SN7494	85p	72p
SN7406	88p	85p	SN7433	94p	82p	SN7472	38p	28p	SN7495	85p	72p
SN7407	88p	85p	SN7437	72p	89p	SN7473	41p	39p	SN7496	95p	82p
SN7408	20p	18p	SN7438	72p	89p	SN7474	41p	39p	SN74100	1-80p	1-75p
SN7409	20p	18p	SN7440	16p	15p	SN7475	50p	47p	SN74104	1-09p	1-06p
SN7410	17p	15p	SN7441	74p	70p	SN7476	44p	43p	SN74105	1-08p	1-06p
SN7411	27p	25p	SN7442	74p	70p	SN7480	73p	70p	SN74107	44p	42p
SN7412	38p	35p	SN7443	1-48p	1-37p	SN7481	1-28p	1-28p	SN74110	61p	58p
SN7413	38p	35p	SN7444	1-48p	1-37p	SN7482	97p	85p	SN74111	1-37p	1-27p
SN7416	47p	45p	SN7445	8-00p	1-28p	SN7483	1-20p	1-15p	SN74118	1-10p	1-05p
SN7417	47p	45p	SN7446	1-07p	1-02p	SN7484	1-10p	1-05p	SN74119	1-47p	1-37p
SN7420	16p	15p	SN7447	1-10p	1-03p	SN7485	3-96p	3-85p	SN74121	44p	41p
SN7422	55p	50p	SN7448	1-10p	1-03p	SN7486	38p	35p	SN74122	1-54p	1-43p

* Devices may be mixed to qualify for Price Breaks
* 100 Plus less 10% off 25 plus break

Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	6½p	15µF	6½p	47µF	6½p
100µF	6½p	33µF	6½p	100µF	9p
220µF	6½p	68µF	6½p	150µF	10p
330µF	6½p	150µF	8p	220µF	11p
1000µF	13p	220µF	9p	470µF	19p
4700µF	29p	680µF	17p	680µF	25p
		1000µF	17p	1000µF	25p
		1500µF	25p	2200µF	44p
		2000µF	43p		

6-3 VOLT		25 VOLT	
33µF	6½p	10µF	6½p
68µF	6½p	22µF	6½p
150µF	6½p	47µF	6½p
470µF	11p	100µF	8p
680µF	13p	150µF	8p
1500µF	18p	220µF	10p
2200µF	18p	470µF	13p
3300µF	26p	680µF	20p
		1000µF	22p
		5000µF	68p

10 VOLT		40 VOLT	
22µF	6½p	6-8µF	6½p
47µF	6½p	15µF	6½p
100µF	6½p	33µF	6½p
220µF	8p	1000µF	44p
330µF	10p		
470µF	10p		
1000µF	11p		
1500µF	20p		
2200µF	24p		

BARGAIN PACKS

- Unmarked Packs
- Pack of 25 IN4148 55p
- Pack of 10 BC108 55p
- BC107 (Plastic can)
- Pack of 10 Plastic BC109 55p
- Pack of 10 BC169 55p
- 2N2646 (unmarked) but tested 38p each
- 2N2646 (unmarked) 38p each
- Pack of 10 2N2926G 55p
- unbranded but tested
- Unmarked but fully tested 2N3055 33p
- 1-9 10 plus 27p

Linear Integrated Circuits

301 DIL	50p	723c DIL	99p
301 TO99	55p	723c TO99	85p
301 8 PIN DIL	48p	741c 8 PIN DIL	38p
301A DIL	69p	741c 14 PIN DIL	38p
301A TO99	69p	741c TO99	41p
301A 8 PIN DIL	68p	747c DIL	46p
307 DIL	69p	748c DIL	39p
307 TO99	69p	748c TO99	41p
307 8 PIN DIL	66p	748c TO99	41p
308 TO99	6-45p	1437 DIL	1-27p
308A TO99	6-40p	1458 TO99	1-27p
709c DIL	35p	3048 DIL	84p
709c TO99	81p	7503 DIL	1-27p

Transistors

AC107 16p	BC138 38p	BF260 28p	OC44 14p
AC126 14p	BC142 35p	DF329 18p	OC45 14p
AC127 18p	BC143 35p	BF813 18p	OC79 23p
AC128 13p	BC144 30p	BF830 37p	OC71 14p
AC1242K 22p	BC145 28p	BF834 28p	OC72 14p
AC141K 20p	BC147 8p	BFX35 35p	OC81 14p
AC176 15p	BC148 9p	BFX86 28p	OC83 24p
AC187 18p	BC149 9p	BFX87 28p	OC84 28p
AC187K 20p	BC153 18p	BFX88 28p	TIP29A 58p
AC198 13p	BC154 17p	BFY60 21p	TIP30A 64p
AC188K 20p	BC157 13p	BFY51 17p	TIP31A 64p
ACV17 24p	BC158 12p	BFY52 17p	TIP32A 78p
ACV18 21p	BC159 14p	BFY64 38p	TIP33A 41-55
ACV19 28p	BC167 13p	BFY90 72p	TIP34A 41-55
ACV20 22p	BC168 11p	BS210 18p	1N4007 22p
ACV21 23p	BC169 11p	C407 22p	1S113 17p
ACV22 18p	BC177 15p	C426 38p	1S117 17p
ACV30 68p	BC179 15p	C428 31p	1S121 15p
AD140 40p	BC182L 9p	C450 17p	1S130 9p
AD142 44p	BC183L 9p	MF8111 38p	1S131 11p
AD143 39p	BC184L 9p	MF8112 42p	1S132 13p
AD149 38p	BC186 35p	MF8113 35p	1S139 22p
AD150 60p	BC212L 11p	MF8121 35p	1S139 22p
AD161 28p	BC213L 11p	MF8122 44p	1S139 22p
AD162 28p	BC214L 11p	MF8123 50p	1S139 22p
AD MP 50p	BC258 9p	NKT211 28p	1S139 22p
AF114 14p	BC269 9p	NKT212 28p	1S139 22p
AF115 14p	BC267 14p	NKT214 25p	2N2904 40p
AF116 14p	BC268 15p	NKT217 55p	2N2904A 40p
AF117 14p	BC300 40p	NKT261 28p	2N2904A 40p
AF118 92p	BC301 32p	NKT271 20p	2N2905 44p
AF124 27p	BC302 30p	NKT274 20p	2N2905 44p
AF139 38p	BC303 30p	NKT275 25p	2N2906 44p
AF229 41p	BC304 40p	NKT403 71p	2N2907 44p
AL100 77p	BC370 17p	NKT405 83p	2N3054 55p
AL102 88p	BC371 8p	NKY603F 17p	2N3055 55p
AL103 56p	BC372 17p		2N3405 44p
ASV26 31p	BD123 88p	NKT0130 8p	2N3863 57p
ASV27 40p	BD130 50p		2N3702 9p
AU103 99p	BD131 68p	NKT674 26p	2N3703 9p
AU110 81-10	BD132 90p	NKT677G 18p	2N3704 9p
BC101 77p	BD135 42p		2N3705 9p
BC107 9p	BD136 50p	NKT713 32p	2N3706 9p
BC108 9p	BD141 81-87	NKT773 27p	2N3707 9p
BC113 151p	BF159 35p	OC19 55p	2N3708 9p
BC116 18p	BF173 29p	OC20 55p	2N3709 9p
BC125 16p	BF177 28p	OC25 28p	2N3710 9p
BC126 25p	BF178 29p	OC28 33p	2N3711 9p
BC132 18p	BF194 15p	OC32 33p	2N3719 17p
BC134 18p	BF195 17p	OC36 38p	2N3819 28p
BC135 16p	BF244 27p	OC38 38p	40661 50p
BC137 16p		OC41 14p	40636 50p
		OC41 14p	40636 50p

MULLARD POLYESTER'S

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 0-068µF, 0-1µF, 0-15µF, 0-22µF, 0-33µF, 0-47µF, 0-68µF, 1µF, 1-5µF, 2-2µF, 3-3µF, 4-7µF, 6-8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 10000µF, 15000µF, 22000µF, 33000µF, 47000µF, 68000µF, 100000µF, 150000µF, 220000µF, 330000µF, 470000µF, 680000µF, 1000000µF, 1500000µF, 2200000µF, 3300000µF, 4700000µF, 6800000µF, 10000000µF, 15000000µF, 22000000µF, 33000000µF, 47000000µF, 68000000µF, 100000000µF, 150000000µF, 220000000µF, 330000000µF, 470000000µF, 680000000µF, 1000000000µF, 1500000000µF, 2200000000µF, 3300000000µF, 4700000000µF, 6800000000µF, 10000000000µF, 15000000000µF, 22000000000µF, 33000000000µF, 47000000000µF, 68000000000µF, 100000000000µF, 150000000000µF, 220000000000µF, 330000000000µF, 470000000000µF, 680000000000µF, 1000000000000µF, 1500000000000µF, 2200000000000µF, 3300000000000µF, 4700000000000µF, 6800000000000µF, 10000000000000µF, 15000000000000µF, 22000000000000µF, 33000000000000µF, 47000000000000µF, 68000000000000µF, 100000000000000µF, 150000000000000µF, 220000000000000µF, 330000000000000µF, 470000000000000µF, 680000000000000µF, 1000000000000000µF, 1500000000000000µF, 2200000000000000µF, 3300000000000000µF, 4700000000000000µF, 6800000000000000µF, 10000000000000000µF, 15000000000000000µF, 22000000000000000µF, 33000000000000000µF, 47000000000000000µF, 68000000000000000µF, 100000000000000000µF, 150000000000000000µF, 220000000000000000µF, 330000000000000000µF, 470000000000000000µF, 680000000000000000µF, 1000000000000000000µF, 1500000000000000000µF, 2200000000000000000µF, 3300000000000000000µF, 4700000000000000000µF, 6800000000000000000µF, 10000000000000000000µF, 15000000000000000000µF, 22000000000000000000µF, 33000000000000000000µF, 47000000000000000000µF, 68000000000000000000µF, 100000000000000000000µF, 150000000000000000000µF, 220000000000000000000µF, 330000000000000000000µF, 470000000000000000000µF, 680000000000000000000µF, 1000000000000000000000µF, 1500000000000000000000µF, 2200000000000000000000µF, 3300000000000000000000µF, 4700000000000000000000µF, 6800000000000000000000µF, 10000000000000000000000µF, 15000000000000000000000µF, 22000000000000000000000µF, 33000000000000000000000µF, 47000000000000000000000µF, 68000000000000000000000µF, 100000000000000000000000µF, 150000000000000000000000µF, 220000000000000000000000µF, 330000000000000000000000µF, 470000000000000000000000µF, 680000000000000000000000µF, 1000000000000000000000000µF, 1500000000000000000000000µF, 2200000000000000000000000µF, 3300000000000000000000000µF, 4700000000000000000000000µF, 6800000000000000000000000µF, 10000000000000000000000000µF, 15000000000000000000000000µF, 22000000000000000000000000µF, 33000000000000000000000000µF, 47000000000000000000000000µF, 68000000000000000000000000µF, 100000000000000000000000000µF, 150000000000000000000000000µF, 220000000000000000000000000µF, 330000000000000000000000000µF, 470000000000000000000000000µF, 680000000000000000000000000µF, 1000000000000000000000000000µF, 1500000000000000000000000000µF, 2200000000000000000000000000µF, 3300000000000000000000000000µF, 4700000000000000000000000000µF, 6800000000000000000000000000µF, 10000000000000000000000000000µ

REMEMBER
TO USE THE
POSTCODE



Readers Letters

Transistor Point

As a complete beginner to electronics at the time of buying the first issue of EVERYDAY ELECTRONICS, I found great difficulty in differentiating between transistors of types *pnp* and *npn* as shown on circuit diagrams.

I therefore devised a method of remembrance by saying that *pnp* = point in plate.

The "point" and "plate" referred to of course, being the "emitter" and "base" respectively of the standard transistor configurations. Knowing this, it follows, that if the "point" is away from the "plate" then the transistor is of type *npn*.

Possibly this sounds rather elementary, but I find it useful even now and hope other readers may also.

C. C. Cullen,
Theford.

Volume

I have completed the *Audible Indicator Warning* unit and am very pleased with the result, but it seems to be too loud. Would it be possible to install a volume control?

J. Welch,
Shoreditch.

The volume may be reduced by putting a low value resistor in series with LS1—try 100 ohms.

Guitar Impedance

Ref. your *General Purpose Amplifier*. I note you refer to guitars as being in the 200 ohms (impedance?) category. Well this just 'aint so. With one exception, every guitar I have ever owned, used, or experimented with has

had a d.c. resistance of between 10 kilohms and 50 kilohms. So the nominal impedance must be at least that high. The exception has a measured resistance of 10 megohms. No, I don't understand it either, but it works well into a high impedance valve (EF 86) amplifier.

This fallacy about guitars is repeated regularly in your family of magazines and just does not have any factual basis, except perhaps for the home-made pick-ups featured at various times. I would suggest you check this with any reputable guitar manufacturers, and stop this rather silly "old wives tale."

If you treat a guitar as a rather inefficient ceramic cartridge you won't go far wrong. (Still a good mag. though.)

A. Gamble,
Ormskirk.

We have unfortunately, misled some readers. The text stated "Two inputs are provided one being rated at 5mV which is suitable for low level signal sources such as 200 ohm microphones or guitars." By this we did not mean 200 ohm guitars but simply that a guitar could be inputted into the low level socket. Most guitar pick-ups are around 50 kilohms impedance.

Ruminations By Sensor

The I.C. and the Haggis

I wrote recently in "Ruminations" (April 1973) drawing some comparisons between an integrated circuit and a haggis. I concluded the piece by observing that I had yet to hear an address to the I.C!

A reader in Hull has written one for me, based somewhat irreverently, on the Lord's Prayer. With apologies to anyone who may be offended, I offer a "Creed for Semiconductor Men."

"I believe in epitaxial growth, in the planar technology, and the diffusion of silicon."

Are You Receiving Me?

When reading of the increase

Everyday Electronics, Ju. e 1973

in telephone tapping, room "bugging" and other forms of snooping taking place these days, I began to wonder if it will ever be possible to "listen in" to an animal's mind. The thought was prompted by watching the dog, asleep in front of the fire, her paws twitching, nose wrinkling, ears moving, as she presumably, dreamed of a great chase.

It is easy enough to detect brain waves by means of an electronic encephalograph, but what a fascinating world might be opened to us if we could share the visual, olfactory, and other sensations experienced by the animals, birds and insects which share our planet.

Some very complex equipment would be needed to translate, for our appreciation, the pleasurable sensations of the dog on finding a putrefying old bone.

The possibilities are almost limitless. I can visualise the family sitting gathered around the equipment in the evenings (the television ignored) and ex-

periencing, say—"The life of the honeybee—from brood chamber to outcast, edited and condensed on tape to a two hour, never to be forgotten, experience."

Or, if you want thrills, what about "Be the horse that won the Grand National—jump Bechers Brook, feel the bit in your mouth as you clear Valentine's."

I would like to experience the soaring flight of an eagle, or the across the globe flight of the arctic tern, to join in the migration of the wild geese, or go with the salmon, down to the sea.

Impossible, do you say? I don't think so, much stranger things have happened. Perhaps, in the next ten years, we shall see suitable circuits and constructional details in EVERYDAY ELECTRONICS! There are snags of course, I would not wish my own "brain waves" to become available without my consent. And there would be many organisations that would attempt to obtain information of this kind—for our own good, of course!

MANY readers may be surprised to find that they can make their own printed circuit panels and, provided you follow our instructions, the result is well worth a little time and care.

There are one or two firms selling p.c. board "construction kits" and these are generally excellent to start off with. The alternative—which will probably be cheaper if a number of boards are likely to be made—is to buy the board, resist and etchant individually in reasonable quantities.



There seems to be something of a shortage of single sided copper clad paxolin or fibreglass board at the moment, but the larger suppliers should be able to help if your local dealer cannot. Incidentally, the fibreglass board is more expensive but should preferably be used where heat or moisture are present, e.g., for car gadgets that are fitted under the bonnet.

The resist can be either paint (Humbrol model type) available from model shops, or you can use one of the p.c. resist pens. A recently announced pen is now available from G.S.P.K. (Sales) Ltd., Hookstone Park, Harrogate, HG2 7BU, Yorkshire. The pen is priced at 60p and postage and packing are 10p. The ease with which such a pen can be used probably makes it worth the extra cost.

Having talked about the p.c. board we can now look at this month's projects and first at the one that uses a p.c. board both for component mounting and to form a "keyboard!"

Mini Organ

There should be little trouble with component buying for the *Mini Organ*—the p.c. board may be difficult to get but this has been mentioned above. Other problems should be limited to some resistors—try Electrovalue of 28 St. Jude's Way, Englefield Green, Egham, Surrey, for these—and the two push-button type switches. One of the larger suppliers should be able to help with the push-buttons although they may not be exactly the same style as those shown in the photographs.

Small 75 ohm speakers are generally available for about 50p.

Cassette Tape Amplifier

Looking through the ad's in a recent issue we were amazed at the price differences for a matched pair of AD161/162's as used in the *Cassette Tape Amplifier*. Although these are not that expensive, the prices vary by relatively large amounts; it just shows that it can be worth looking around even for transistors!

Aside from the above note there are no particularly helpful hints we can give for buying. The bridge rectifier can be almost any type of adequate ratings—there are a number of different types available from advertisers.

Incidentally, the current quoted for both the transformer and the rectifier are the minimum ratings—if the one you get is quoted as having a higher current rating, this is suitable.

Rain Alarm

If we keep publishing straightforward designs like the *Rain Alarm* the need for this page may disappear since we find it difficult to give advice on buying components that are all readily available. A case for this unit can be any suitable box or can be made up from an aluminium chassis and a wood or perspex front panel.

New Products

Not a completely new product but an improved version of a well-known existing amplifier; the Radio and TV Components, Viscount III. This amplifier has been uprated from 14 to 20 watts

r.m.s. per channel with no price increase (except for V.A.T. of course).

However, if a complete Viscount audio system is purchased, the V.A.T. increase is not passed on to the customer.

The latest amplifier, designated the R102, has a frequency response of 40Hz to 40kHz \pm 3dB and incorporates f.e.t. input stages, the price of the amplifier is £24.20.


Readers of E.E. have a chance to win one of these amplifiers, together with a record deck and speakers, in this month's competition—see page 304 for details.

Kabi (Electrical & Plastics) Limited of Cranborne Road, Potters Bar, Herts., have introduced a new series of compartment trays which have a wide range of uses. The range comprises four sizes. $5\frac{1}{4} \times 7 \times 1\frac{1}{2}$ inches, $6 \times 10\frac{5}{8} \times 1\frac{1}{2}$ inches, $6 \times 10\frac{3}{4} \times 1\frac{1}{2}$ inches and $6\frac{1}{4} \times 12 \times 2$ inches.


All models except the last quoted have fixed compartments of various sizes and all are formed in strong plastic which will give long service in normal usage (see photograph).

The largest model has moveable compartment modules, each module being capable of subdivision, so that compartments of virtually any size up to the total dimensions of the tray can be formed.

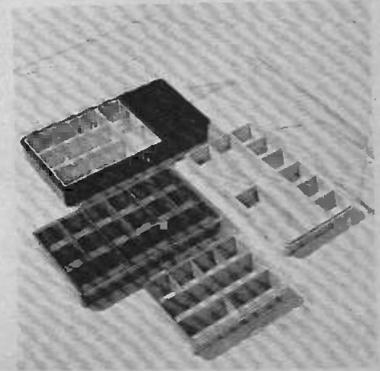The trays are ideal storage units for electronic components—and, in fact, anywhere where small parts have to be stored. Most are available in a range of colours at prices ranging from 45p to £1.50 each according to size. The trays are complete with clear plastic lids, having a hinge and snap fixing, and could accommodate small tools as well as components.



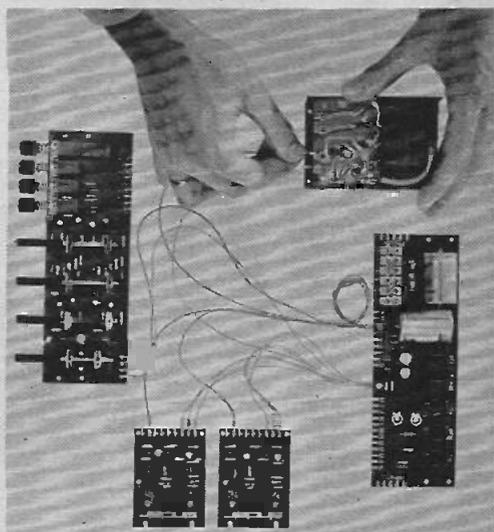Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same — there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative — Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one — Masterlink — which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together — the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

Guarantee If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air mail charged at cost.

Sinclair Radionics Ltd., London Road,
St. Ives, Huntingdonshire PE17 4HJ.
Telephone: St. Ives (04806) 4311

Reg. No. 393594

sinclair

Specifications

Output — 30 watts music power (10 watts per channel R.M.S. into 3Ω).

Inputs — Mag. P.U. — 3mV correct to R.I.A.A. curve 20–25,000 Hz ± 1dB. Ceramic pick-up — 50mV. Radio — 50 to 150mV. Aux. adjustable between 3mV and 3V.

Signal to noise ratio — Better than 70dB.

Distortion — better than 0.2% under all conditions.

Controls — Press buttons for on-off, P.U., radio and aux. Treble +15 to -15 dB at 10 kHz. Bass +15 to -15 dB at 100 Hz. Volume. Stereo Balance.

Channel matching within 1dB.

Front panel — brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

£29.95

Plus 10% V.A.T.

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ


Please send Project 605 post free Details and list of stockists

Name

Address

for which I enclose £29.95 cheque/money order/cash. EE6/73

SINCLAIR IC12 £2.00

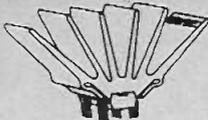

Max supply Volts 28. Power 6 Watts rms. Complete with free printed circuit board and 44 page instruction booklet.

SWANLEY IC TOMORROW £2.50

The World's most powerful IC amplifier. Similar to the above but operates at 35 Volts max supply and gives 12 Watts rms output. Manufactured for us by a leading semiconductor company. Supplied with our Instructions and a 6 month guarantee, but no printed circuit.

SINCLAIR EQUIPMENT



Z30	£3.50	Z50	£4.25
P25	£3.97	P26	£6.40
P28	£6.60	Transformer	
AFU	£4.50	for P28	£2.95
Stereo 60	£7.80	Project 60 tuner	£16.80

EXECUTIVE CALCULATOR £55

PROJECT 60 KIT £2.50
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cables and fuseholder needed to complete Project 60.

SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent BR8 8EZ

Postage 10p per item. Please add 10% extra to total cost of order for VAT. Official credit orders from schools etc. welcome. Full lists 10p post free. Send S.A.E. for free 8 page book on IC TOMORROW, IC12 kits and TBA651.

KITS FOR IC12 AND IC TOMORROW

Except for the power kits and speakers all items suit both integrated circuits

DELUXE KIT

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.45. Stereo version with balance control £3.30.

POWER KIT FOR IC12

A set of components to construct a 28V 0.5 Amp power supply £2.27. Also suitable Sinclair P25 £3.97.

POWER KIT FOR IC TOMORROW

A set of components to construct a 35V 1 Amp power supply £2.97.

LOUDSPEAKERS FOR THE IC12

8 ohm types. 5" £1.00. 5" x 8" £1.45.

PREAMPLIFIER KITS

Type 1 for magnetic pickups, mics and tuners with 3 position equalization switch. Mono model £1.20. Stereo model £2.20. Type 2 for ceramic or crystal pickups. Mono 60p. Stereo £1.20.

SEND S.A.E. FOR FREE LEAFLET ON KITS AND TBA651.

S-DECS AND T-DECS

S-Decs	£1.44
T-Decs	£2.88
µ-Decs A	£3.00
16 ill IC carriers	£1.20



IC RADIO CHIP

TBA651 £2.10

The World's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10. Send S.A.E. for free leaflet on chip and kit.

QUALITY COMPONENTS - BUDGET PRICES

PSYCHEDELIC LIGHTING UNIT IN KIT FORM

Make this fascinating three-channel unit from a kit which contains all components needed to produce a reliable and entertaining display. Takes its drive from the speaker terminals of a record player, tape recorder or portable radio. Will provide a brilliant 2Kw of light, using normal 240 volt coloured lamps. Price per kit .. £10.40

HALF PRICE CABINET OFFER

As a special introductory offer, one of the metal cabinets described below will be supplied with each kit at the additional price of only 79p. At this fantastic give-away price, stocks of cabinets are certain to disappear fast, so send your order today to avoid being disappointed. Please note that this special offer is not available separately.



METAL CABINETS

These attractive steel cabinets are PVC covered in a range of colours, and offer a really economically-priced unit for the home constructor. The chassis, which has a white PVC finish, provides an easily accessible building area, with an integral fascia panel. The cabinet is supplied complete with rubber feet. Colours available include Green, Grey, Black, White, Blue and Brown. Every effort will be made to supply a selected colour, but please give alternatives if possible.

Approximate size in inches	Price
8 w 6 d	£1.45
11 w 6 d	£1.85

Other sizes to special order. Please send S.A.E. for quotation.

FIXED VOLTAGE REGULATORS

T03 case. Gives stabilised supply. MVR 5 volt, MVR 12 volt, MVR 15 volt. All priced at .. £1.65

CONTACT FLUID PEN

Contains a special oil which cleans and lubricates contacts and bearings. Helps to eliminate arcing. Supplied in a snorkel dispenser with pocket clip. Price each .. 60p

Our CATALOGUE, priced at 25p post free, shows the majority of the R.S. range of professional components. Most of these are available by return of post.

All orders over 50p POST FREE. S.A.E. with all queries please.

CELETRON-E
P.O. Box No. 1, Llantwit Major, Glamorgan, Wales, CF6 9YN

B.H. COMPONENT FACTORS LIMITED

SPECIAL RESISTOR KITS (1/4W 5% or 1/2W 5% CARBON FILM)
10E12 Kit: 10 of each E12 value, 10 ohms—1M, a total of 610, £2.80 net
25E12 Kit: 25 of each E12 value, 10 ohms—1M, a total of 1,525, £6.50 net

POLYESTER CAPACITORS MULLARD C280 250V

µF: 0.01, 0.015, 0.022, 0.033, 0.047, 3p each; 0.068, 0.1, 0.15, 4p each; 0.22, 5p; 0.33, 7p; 0.47, 8p; 0.68, 10p; 1.0, 13p; 1.5, 20p; 2.2, 23p.

MULLARD POLYESTER CAPACITORS C296 SERIES

160V: (µF) 0.01, 0.015, 0.022, 2p; 0.047, 0.068, 3p; 0.15, 0.22, 4p; 0.33, 5p; 0.47, 6p; 0.68, 1.0, 10p.

400V: (µF) 0.001, 0.0015, 0.0022, 0.0033, 0.01, 2p; 0.015, 0.033, 3p; 0.068, 4p.

MINIATURE ELECTROLYTIC MULLARD C426 SERIES (5p each)
(µF/V) 1/63, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/6.4, 125/16, 200/6.4, 200/10, 320/6.4, 125/10.

MULLARD C437: (µF/V) 64/64, 9p; 160/25, 9p; 160/40, 11p; 640/6.4, 9p; 1600/6.4, 14p.

ELECTROLYTIC CAPACITORS. Tubular and large can

(µF/V) 2.5/50, 3p; 4/10, 10/25, 16/15, 20/25, 25/15, 25/25, 40/6, 64/10, 200/6, 250/10, 4p; 10/16, 10/50, 25/50, 32/50, 50/10, 64/25, 100/25, 5p; 50/50, 64/40, 250/15, 1,000/3, 6p; 100/50, 250/25, 400/10, 500/10, 500/12, 640/10, 1,000/6, 8p; 500/25, 10p; 500/50, 12p; 1,000/12, 10p; 1,000/25, 2,000/12, 2,500/12, 15p; 1,000/50, 35p; 2,000/25, 25p; 2,500/25, 30p; 2,500/50, 55p; 3,000/50, 65p; 5,000/50, 85p; 1,000/100, 60p; 8,350, 12p; 16,350, 17p; 32,350, 22p.

MINIATURE CERAMIC PLATE CAPACITORS

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 2p, 0.047, 30V, 3p, 0.1, 30V, 4p, 0.1, 100V, 5p.

CARBON FILM RESISTORS 1/4W 5%, 10 ohms—2.2M, 1/2W 5%, 10 ohms—1M, 1p each or 100 for 55p, 1,000 for £4.

METAL FILM RESISTORS 1/4W 5% 10 ohms—10M, 1p each or 100 for £1.

Veroboard	0.1	0.15	IN4001	6p
21 x 5in	25p	25p	IN4002	7p
21 x 3 1/2in	23p	17p	IN4003	8p
3 1/2 x 5in	29p	30p	IN4004	9p
3 1/2 x 3 1/2in	25p	25p	IN914	6p
21 x 1in	2 for 12p	12p	µI914	30p
21 x 5in (plain)	—	12p	OC71	12p
21 x 3 1/2in (plain)	—	11p	OC75	15p
5 x 3 1/2in (plain)	—	20p	OC83	18p
Insertion tool	54p	54p		
Track cutter	40p	40p		
Pins, pkt. 25	8p	8p		

2 pin DIN Plug, 12p; 5kt., 10p; 3 pin DIN Plug, 13p; 5kt., 10p; 5 pin DIN Plug, 180°, 15p; 5kt., 12p. Transistor Equiv. Book, 40p. Carbon pots 5K—2M log. & lin, single 15p, single with switch 24p, dual 42p.

Dept. E.E. 61, CHEDDINGTON ROAD, PITSTONE
Near LEIGHTON BUZZARD, BEDS. LU7 9AQ

Tel: Cheddington 668446 STD. (0296) Giro No. 331 705r
Inquiries—S.A.E. Catalogue FREE Callers please phone first

build an electronic nose . . .

A battery operated instrument which responds to certain gases, vapours, and smoke particles.

Applications include breathalyzer, fuel vapour and firedamp detector, air pollution meter, paint dryness indicator, and gas leak locator.

Get the full easy-to-follow details in PRACTICAL ELECTRONICS out Friday, June 8th.

PRACTICAL ELECTRONICS

QUANTITY DISCOUNT
SPECIAL BULK BUY PRICES ARE AVAILABLE BY QUOTATION FOR LARGE PROJECTS AND TRADE.

VAT 10% must be added to the total order value inc. P. & P.

Screened wire, yd.	5p
Twin screened wire, yd.	9p
Stereo s.c. wire, yd.	9p
Quad screened wire, yd.	19p
3 core circ. mains cable White, 3 yds.	24p
Neon bulb 90V wire ended	5 for 20p
Pre-set skeleton pots 1K—1M	5p

C.W.O. only. P. & P. 10p on orders below £5. Discount: £10—10%, £10—15%, Export Order enquiries welcome (VAT free)

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 25p

POST & PACKING 15p

TESTED AND GUARANTEED PAKS

B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H9	2	OC7P1 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	50p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 41V.	50p
H35	100	Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short Lead Transistors, NPN Silicon Planar types.	50p
H39	10	Integrated Circuits, 5 Gates BMC 962, 4 Flip Flops BMC 945	50p
H40	20	BFY507, 2N696, 2N1613 NPN Silicon uncoded TO-5	50p
H41	2	Sil Power transistors comp pair BD131/132	50p

UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA302	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H46	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This
encapsulated block will turn any
0-1mA meter into a linear and
accurate rev. counter for any
car with normal coil ignition
system.

£1 each



OVER
TRANSISTORS
IN STOCK **1,000,000**

We hold a very large range of fully marked,
tested and guaranteed transistors, power
transistors, diodes and rectifiers at very
competitive prices. Please send for free
catalogue.

600,000 Silicon planar plastic transistors.
Unmarked, untested,
factory clearance. A random
sampling showed these to be of remarkably
high quality.

Audio PNP, similar to ZTX500, 2N3702/3,
BCY70 etc.

Audio NPN, similar to ZTX300, 2N3708/9,
BC107/8/9, BC168/9 etc.

Please state Audio NPN or Audio PNP when
ordering.

ALL AT 500 for £3, 1,000 for £5, 10,000 for £40
P. & P. 10p/1,000.

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN silicon similar ZTX 300 range
TYPE "H" PNP silicon similar ZTX 500 range

**8 RELAYS FOR
VARIOUS TYPES £1**
P & P 25p

VALUE ON ORDERS OF
ADDED £4 OR OVER
TO YOU SEE BELOW

Please read very carefully:
We will give a discount to customers who send
in an order for £4 or over. This discount will
be equal to the V.A.T. rate current at this
time. If your order does amount to £4 or
over, all you need to send is the total
cost of goods and postage as stated
in this advertisement. No addition
for V.A.T. is needed.

V.A.T. for orders under £4:
If the total cost of goods plus
postage and packing is less
than £4, kindly add 10%
(10p in the £) to your
remittance. Incorrect
amounts will delay
your order.

A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including
Printed Circuit Board. A four position switch
gives X-hatch, Dots, Vertical or Horizontal
lines. Integrated Circuit design for easy
construction and reliability. This is a project
in the September edition of Television.

This complete kit of parts costs £3.50,
post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still
leading in value for money.

Full of Short Lead Semiconductors & Elec-
tronic Components, approx. 170. We
guarantee at least 30 really high quality
factory marked Transistors PNP & NPN, and
a host of Diodes & Rectifiers mounted on
Printed Circuit Panels. Identification Chart
supplied to give some information on the
Transistors.

Please ask for Pak P.1. Only 50p.
10p P & P on this Pak.

FREE CATALOGUE
FOR



TRANSISTORS,
RECTIFIERS,
DIODES,
INTEGRATED
CIRCUITS,
FULL PRE-PAK
LISTS

100,000 Plastic Power Transistors
in stock, more on way!

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power
Transistors of the very latest design, available in
NPN or PNP at the most shattering low prices of
all time. We have been selling these successfully in
quantity to all parts of the world and we are proud
to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.
40 Watt 1-12 13-25 26-50
90 Watt 20p 18p 16p
24p 22p 20p

Range 2. VCE. Min 40. HFE Min 40.
40 Watt 1-12 13-25 26-50
90 Watt 30p 28p 26p
35p 33p 30p

Complementary pairs matched for gain at 3 amps.
10p extra per pair. Please state NPN or PNP on
order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive
prices (from 10p each). These are all listed in our
FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator
carries thousands of classified references between
metric and British (and U.S.A.) measurements of
length, area, volume, liquid measure, weights etc.
Pocket Size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile
16 pin type at 16p each } type

BOOKS

We have a large selection of Reference and
Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and
Substitutes; 40p

This includes many thousands of British
U.S.A., European and C.V. equivalents.

The Iliffe Radio Valve & Transistor
Data Book 9th Edition; 75p

Characteristics of 3,000 valves and tubes,
4,500 Transistors, Diodes, Rectifiers and
Integrated Circuits.

Postage and Packing 21p.

Send for lists of publications.

M.B. Books are void of V.A.T.

Please send me the FREE BI-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 10p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. E, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX. SS0 9DF
TELEPHONE: SOUTHEND (0702) 46344 Reg. No. 820919

SEW PANEL METERS

CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK
 • OTHER RANGES TO ORDER

Type SW.100 100 x 80 mm.

50μA	\$2.90
50-0-50μA	\$3.80
100μA	\$3.80
100-0-100μA	\$3.70
500μA	\$3.50
1mA	\$3.40
20V. D.C.	\$3.40
50V. D.C.	\$3.40
300V. D.C.	\$3.40
1 amp. D.C.	\$3.40



5 amp. D.C. \$3.40
 300V. A.C. \$3.40
 VU Meter \$2.15

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts

50mA	\$3.10
100mA	\$3.10
500mA	\$3.10
1 amp.	\$3.10
5 amp.	\$3.10
15 amp.	\$3.10
30 amp.	\$3.20
20V. D.C.	\$3.20
50V. D.C.	\$3.10
150V. D.C.	\$3.10
300V. D.C.	\$3.10
15V. A.C.	\$3.10
300V. A.C.	\$3.10
100-0-100μA	\$3.80
200μA	\$3.30
500μA	\$3.20
500-0-500μA	\$3.10
1mA	\$3.10
1-0-1mA	\$3.10
1mA	\$3.10
10mA	\$3.10

Type MR.38P. 1 21/32 in. square fronts

200mA	\$1.75
300mA	\$1.75
500mA	\$1.75
750mA	\$1.75
2 amp.	\$1.75
5 amp.	\$1.75
10 amp.	\$1.75
3V. D.C.	\$1.75
10V. D.C.	\$1.75
15V. D.C.	\$1.75
50V. D.C.	\$1.75
100V. D.C.	\$1.75
150V. D.C.	\$1.75
300V. D.C.	\$1.75
100-0-100μA	\$1.85
200μA	\$1.85
500μA	\$1.85
500-0-500μA	\$1.75
1mA	\$1.75
1-0-1mA	\$1.75
1mA	\$1.75
10mA	\$1.75
20mA	\$1.75
50mA	\$1.75
100mA	\$1.75
150mA	\$1.75

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts

1 amp.	\$2.15
5 amp.	\$2.15
15 amp.	\$2.15
30 amp.	\$2.15
50 amp.	\$2.15
5V. D.C.	\$2.15
20V. D.C.	\$2.15
50V. D.C.	\$2.15
150V. D.C.	\$2.15
300V. D.C.	\$2.15
500V. D.C.	\$2.40
1000V. D.C.	\$2.40
10V. A.C.	\$2.15
50V. A.C.	\$2.20
150V. A.C.	\$2.20
300V. A.C.	\$2.20
500μA	\$2.15
1mA	\$2.15
1-0-1mA	\$2.15
10mA	\$2.15
50mA	\$2.15
100mA	\$2.15
500μA	\$2.15

Type SD.830 82.5mm x 110mm Fronts

10mA	\$2.50
50mA	\$2.50
100mA	\$2.50
500mA	\$2.50
1 amp.	\$2.50
5 amp.	\$2.50
10 amp.	\$2.50
5V. D.C.	\$2.50
10V. D.C.	\$2.50
20V. D.C.	\$2.50
50V. D.C.	\$2.50
100V. D.C.	\$2.50
15V. A.C.	\$2.75
300V. A.C.	\$2.75
VU Meter	\$3.00

Type MR.52P. 2 1/2 in. square fronts

50μA	\$2.40
50-0-50μA	\$2.35
100μA	\$2.35
100-0-100μA	\$2.75
500μA	\$2.55
1mA	\$2.20
5mA	\$2.20
10mA	\$2.20
50mA	\$2.20
100mA	\$2.20
500μA	\$2.20
1 amp.	\$2.20
5 amp.	\$2.20
10 amp.	\$2.20
20 amp.	\$2.20
30 amp.	\$2.20
10V. D.C.	\$2.20
20V. D.C.	\$2.20
50V. D.C.	\$2.20
300V. D.C.	\$2.20
15V. A.C.	\$2.20
300V. A.C.	\$2.20
8 Meter 1mA	\$2.30
VU Meter	\$2.50
1 amp. A.C.	\$2.20
5 amp. A.C.	\$2.20
10 amp. A.C.	\$2.20
20 amp. A.C.	\$2.20
30 amp. A.C.	\$2.20

Type MR.45P. 2 in. square fronts

50μA	\$2.50
50-0-50μA	\$2.30
100μA	\$2.30
100-0-100μA	\$2.05
200μA	\$2.05
500μA	\$1.95
500-0-500μA	\$1.85
1mA	\$1.85
5mA	\$1.85
10mA	\$1.85
50mA	\$1.85
100mA	\$1.85
500μA	\$1.85
1 amp.	\$1.85
5 amp.	\$1.85
10 amp.	\$1.85
20 amp.	\$1.85
30 amp.	\$1.85
10V. D.C.	\$1.85
20V. D.C.	\$1.85
50V. D.C.	\$1.85
300V. D.C.	\$1.85
15V. A.C.	\$1.85
300V. A.C.	\$1.85
8 Meter 1mA	\$2.00
VU Meter	\$2.20
1 amp. A.C.	\$1.85
5 amp. A.C.	\$1.85
10 amp. A.C.	\$1.85
20 amp. A.C.	\$1.85
30 amp. A.C.	\$1.85

Type S-80 80 mm. square fronts

50μA	\$3.50
50-0-50μA	\$3.40
100μA	\$3.40
100-0-100μA	\$3.80
500μA	\$3.05
1mA	\$2.85
20V. D.C.	\$2.85
50V. D.C.	\$2.85
300V. D.C.	\$2.85
1 amp. D.C.	\$2.85
5 amp. D.C.	\$2.85
10 amp. D.C.	\$2.85
20 amp. D.C.	\$2.85
30 amp. D.C.	\$2.85
15V. A.C.	\$2.85
300V. A.C.	\$2.85
VU Meter	\$3.70

Type SD.640 63.5mm x 85mm Fronts

50μA	\$2.60
50-0-50μA	\$2.55
100μA	\$2.55
100-0-100μA	\$2.55
500μA	\$2.55
1mA	\$2.55
5mA	\$2.55
10mA	\$2.55
50mA	\$2.55
100mA	\$2.55
500μA	\$2.55
1 amp.	\$2.55
5 amp.	\$2.55
10 amp.	\$2.55
5V. D.C.	\$2.55
10V. D.C.	\$2.55
20V. D.C.	\$2.55
50V. D.C.	\$2.55
300V. D.C.	\$2.55
15V. A.C.	\$2.40
300V. A.C.	\$2.40
VU Meter	\$2.70

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts

50μA	\$3.70
50-0-50μA	\$3.00
100μA	\$3.00
100-0-100μA	\$2.60
200μA	\$2.90
500μA	\$2.65
500-0-500μA	\$2.40
1mA	\$2.40
5mA	\$2.40
10mA	\$2.40
50mA	\$2.40
100mA	\$2.40
500μA	\$2.40
1 amp.	\$2.40
5 amp.	\$2.40
10 amp.	\$2.40
15 amp.	\$2.40
20 amp.	\$2.40
30 amp.	\$2.40
50 amp.	\$2.40
5V. D.C.	\$2.40
10V. D.C.	\$2.40
20V. D.C.	\$2.40
50V. D.C.	\$2.40
150V. D.C.	\$2.40
300V. A.C.	\$2.55
500V. A.C.	\$2.55
300V. A.C.	\$2.60
500V. A.C.	\$2.60
VU Meter	\$3.70
50mA A.C.	\$2.40
100mA A.C.	\$2.40
200mA A.C.	\$2.40
500mA A.C.	\$2.40
1 amp. A.C.	\$2.40
5 amp. A.C.	\$2.40
10 amp. A.C.	\$2.40
20 amp. A.C.	\$2.40
30 amp. A.C.	\$2.40



"SEW" EDGWISE METERS

Type PE.70. 3 17/32 in. x 1 15/32 in. x 2 1/2 in. deep

50μA	\$3.40
50-0-50μA	\$3.30
100μA	\$3.30
100-0-100μA	\$3.20
200μA	\$3.20
500μA	\$3.05
1mA	\$2.70
5mA	\$2.70
10mA	\$2.70
50mA	\$2.70
100mA	\$2.70
500μA	\$2.70
1 amp.	\$2.70

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	\$5.50	20V. d.c.	\$4.85
100μA	\$5.10	50V. d.c.	\$4.85
500μA	\$4.85	300V. d.c.	\$4.85
50-0-50μA	\$5.10		
1-0-1mA	\$4.85	Dual range	
1A d.c.	\$4.85	500mA/5A d.c.	\$5.10
5A d.c.	\$4.85	5V/50V d.c.	\$5.10
10V d.c.	\$4.85		

***MOVING IRON— ALL OTHERS MOVING COIL**
 Please add postage

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. 4in. dia. shafts. Best quantities available. 25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 9p. P. & P. 10p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. \$1.15 P. & P. 10p. 100 WATT. 15/10/25/50/100/250/500/1000 or 2500 ohms. \$1.65 P. & P. 15p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

S-260 General Purpose Bench Mounting

1 Amp	\$7.00
2.5 Amp	\$8.05
5 Amp	\$11.75
8 Amp	\$15.90
10 Amp	\$22.50
12 Amp	\$23.80
20 Amp	\$49.00
25 Amp	\$58.00
40 Amp	\$82.50

S-260B Panel Mounting

1 Amp	\$7.00
2.5 Amp	\$8.05

Please add postage
 ALL MODELS
 INPUT 230 V. 50/60 CYCLES
 OUTPUT VARIABLE 0-260 VOLTS
 Special discounts for quantity

AUTO TRANSFORMERS
 0/115/230V. Step up or step down. Fully shrouded.

80 W	\$2.10	P. & P. 18p
150 W	\$2.70	P. & P. 18p
300 W	\$3.60	P. & P. 23p
500 W	\$5.25	P. & P. 33p
1000 W	\$7.50	P. & P. 38p
1500 W	\$10.20	P. & P. 43p
2250 W	\$17.25	P. & P. 50p
5000 W	\$35.00	P. & P. 61p

MCA.220 AUTOMATIC STABILISER

Input 89 125 VAC or 175 250VAC. Output 120V AC. or 240 VAC. 200 VA rating. \$11.97. carr. 80p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots 240). Quantities available.

BH.001 HEAD SET AND BOOM MICROPHONE

Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. \$4.62. P. & P. 18p.

240° Wide Angle 1mA Meters

MW 1-6 60mm square	\$3.97
MW 1-8 80mm square	\$4.97

P. & P. extra

RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V AC. Size 185 x 85 x 105mm. \$29.97 P. & P. 25p.

PS.200 REGULATED P.S.U.

Solid state. Variable output 6-20 volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240 V. A.C. Size 7 1/2" x 5 1/2" x 3 1/2". \$19.95. P. & P. 25p.

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V AC. Size 4" x 3 1/2" x 6 1/2". \$11.97. P. & P. 25p.

230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 BRH CW; 50p each Post 12p.

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with all instructions, etc. \$4.50. P. & P. 20 p.

LB3 TRANSISTOR TESTER

Tests 100 and B. PNP/NPN. Operates from 9v battery. Complete with all instructions, etc. \$3.95. P. & P. 20p.

HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station, \$2.97, 3 Station \$5.25, P. & P. 15p.
 4 Station \$6.62. P. & P. 17p.

SEND SAE FOR LIST OF SEMI CONDUCTORS & VALVES

G. W. SMITH & CO. (RADIO) LTD.
 Also see next three pages

MULTIMETERS for EVERY purpose!




TS60 POCKET MULTIMETER
 High-precision at low-cost. Ranges: D.C. 15V, 150V, 1,000V (10,000 ohms). A.C. 15V, 150V, 100V (1,000 ohms). D.C. Current 150mA. Resistance 100K ohms. \$1.85. Post 15p.

MODEL 1092 TESTMETER
 5,000 O.P.V. 0/3/15/150/300/1200 V. D.C. 0/8/30/300/600 V. A.C. 0/300mA/300 MA 0/10K/1 meg Ω
 Decibels -10 to +16db \$2.75 each +16p P. & P.



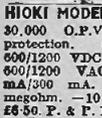HIOKI MODEL 720X
 20,000 O.P.V. Overload protection 5/25/100/500/1000 VDC. 10/50/250/1000 VAC. 50μA/250mA. 20K/2 meg ohms. -10 to +63db. \$4.97. P. & P. 15p.



HIOKI MODEL 730X
 30,000 O.P.V. Overload protection. 6/30/60/300/600/1200 VDC. 12/60/120/600/1200 VAC. 50μA/120 mA/300 mA. 2K/200K/2 megohm. -10 to +63db. \$6.50. P. & P. 15p.

KAMODEN 72.200 MULTITESTER


High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0.6/1/2/3/20/120/600/1200V. D.C. 0/3/12/60/300/11,200V. A.C. 0/6μA/1.2mA/120mA/600mA/12A. D.C. 0/12A. A.C. -20 to +63db. 0/2K/200K/2 meg/200 meg ohms. \$18.95. Post 30p




MODEL TE-200
 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V. D.C. 0/10/50/250/1,000V. A.C. 0/50/125/250 mA. 0/50K/1 meg Ω -20 to +63db. \$3.95. P. & P. 15p.



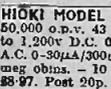
MODEL 500
 30,000 O.P.V. with overload protection mirror scale 0/5/2.5/10/25/100/250/500/1,000V. D.C. 0/2.5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/50K/1 meg Ω. 60 Meg Ω. \$8.87. Post paid.



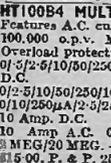
HIOKI MODEL 750X
 50,000 o.p.v. 43 ranges 0-0.2 to 1,200V D.C. 0-3 to 1,200V. A.C. 0-300mA/300mA/300 meg ohms. -10 to +17dB. \$3.97. Post 20p.



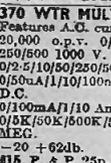HT10084 MULTI-METER
 Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection. 0/5/2.5/10/50/250/500/1000 V. D.C. 0/2.5/10/50/250/1000 V. A.C. 0/10/250μA/2.5/25/250 MA/10 Amp. D.C. 10 Amp. A.C. 0/20K/200K/2 MEG/20 MEG. -20 +62db. \$15.00. P. & P. 25p.



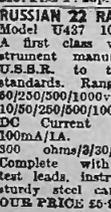370 WTR MULTI-METER
 Features A.C. current ranges. 20,000 o.p.v. 0/5/2.5/10/50/250/500/1000 V. D.C. 0/2.5/10/50/250/500/1000V. A.C. 0/50μA/1/10/100mA/1/10 Amp. D.C. 0/100mA/1/10 Amp. A.C. 0/5K/50K/500K/5 MEG/50 MEG. -20 +62db. \$15. P. & P. 25p.



RUSSIAN 22 RANGE MULTIMETER
 Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V. D.C. 2.5/10/50/250/500/1000V. A.C. DC Current 100mA/1/10/300mA/1A. Resistance 500 ohms/3/30/300K/1M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUB PRICE \$6.97. P. & P. 25p

ROUND SCALE TYPE PENCIL TESTER
 MODEL T.S.68
 Completely portable. simple to use pocket sized tester. Ranges 0/3/30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY \$1.97 P. & P. 15p.



LT601 MULTIMETER
 New style 20,000 o.p.v. pocket multi-meter. 5/25/50/250/500/2500 V. D.C. 10/50/100/500/1000V. A.C. 50μA/250mA. 6K/6 meg ohms. -20 to +22 db. \$3.75. Post 20p.




MODEL TH-12
 20,000 o.p.v. Overload protection. Slide switch selector 0/25/2.5/10/50/250/1000V. D.C. 0/10/50/250/1000V. A.C. 0/10μA/1/25/250mA. D.C. 0/1K/30K/300K/3 meg -20 to +50db \$4.97. Post 15p.


MODEL TE-300
 30,000 O.P.V. Mirror scale, overload protection 0/5/3/15/30/300/1200V. D.C. 0/6/30/120/600/1200V. A.C. 0/30μA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm -20 to +63 db. \$5.97. P. & P. 15p.



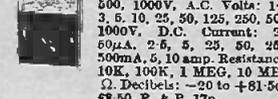MODEL PL434
 20k Ω/Volt D.C. 8k Ω/Volt A.C. Mirror scale. -5/3/12/30/120/600 V. D.C. 3/30/120/600 V. A.C. 50/600μA/60/600 mA. 10/100K/1 Meg/10 Meg Ω. -20 to +45db. \$8.97. P. & P. 12p.



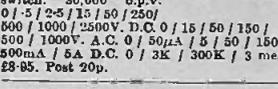TMK MODEL TW-50K
 48 ranges, mirror scale, 50K/Volt. D.C. 5K/Volt A.C. D.C.: Volts 125, 25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.25, 3.5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 60μA, 2.5, 5, 25, 50, 250, 500mA. 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +81.5db \$8.50. P. & P. 17p.



MODEL K228A
 Test band suspension. Overload protection. Polarity reversing switch. 30,000 o.p.v. 0/5/2.5/10/50/250/500/1000/2500V. D.C. 0/15/50/130/500/1000V. A.C. 0/50μA/1/50/150/500mA/5A. D.C. 0/3K/300K/3 meg. \$8.95. Post 20p.



HIOKO MODEL 700X
 100,000 O.P.V. Overload protection. Mirror scale. -3/6/12/3/5/30/60/120/300/600/1200V. D.C. 1.5/3/6/12/30/60/150/300/600/1200 V. A.C. 15/30μA/3/6/30/60/150/300mA 6/12 AMP. DC. 2K/200K/2 Meg/20 Meg ohm -20 to +63db. \$13.50. P. & P. 20p.

MODEL C-7080 EN
 Giant 6" mirror scale. 20,000 o.p.v. 0/25/1/2.5/10/50/250/1000 V. D.C. 0/2.5/10/50/250/1000 V. A.C. 0/50μA/1/10/100/500mA/10 amp. D.C. 0/2K/200K/20 meg -20 to +50 db. \$18.95. Post 35p.

U4312 MULTIMETER
 Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/3/1.5/3/30/60/150/300/600/300 VDC and 75mV. 0/3/1.5/7.5/50/80/150/300/600/300 VAC. 0/300μA/1.5/6/15/60/150/600mA/1.5/6 AMP. D.C. 0/1.5/6/15/60/150/600mA/1.5/6 AMP. A.C. 0/200Ω/3K/30K Ω. Accuracy DC 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. \$9.50 plus P. & P. 25p.

Selected TEST EQUIPMENT

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and ICO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$7.50. Post 20p.




TE-16A TRANSISTORISED SIGNAL GENERATOR

5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. \$7.97. Post 25p.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

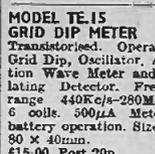A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 meg Ω. 6 Ranges ±1% L1 ±1% H - 111 HENRY S 6 Ranges 2-5% C10PF ±110mF 6 Ranges ±2% TURN RATIO 1:1/1000-1:1/100. 6 Ranges ±1% Bridge Voltage 0-1,000 cps. Operated from 9 volts. 100μA Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 1/2 in. \$20. P. & P. 25p.



MODEL TE.15 GRID DIP METER
 Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillation Detector. Frequency range 400KHz-280Mcs in 6 coils. 500μA Meter. 9V battery operation. Size 180 x 80 x 40mm. \$15.00. Post 20p.

Model S-100TR MULTIMETER/TRANSISTOR TESTER

100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V DC/0/6/30/120/600V. V. AC. 0/12/600μA/12/300mA/12 AMP. DC. 0/10 K/1 MEG/100MEG. -20 to +50db. 0-01-2 MPD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. \$13.50. P/P 25p.




MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta in/out. Checks Icbco. Checks diodes in/out. Checks SCR, etc. Beta HI 10 - 500. LO 2 - 50. Icbco 0-5000μA. 220/240 V A.C. operation \$17.50. Post 25p.



KAMODEN HM 720B F.E.T. V.O.M.

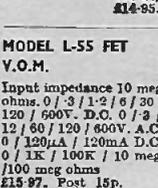Input impedance 10 meg ohms. Ranges: 0/25/1/2.5/10/50/250/1000V. D.C. 0/2.5/10/50/250/1000V. A.C. 0/25μA/10/25/250 MA D.C. -20 to +62db. 0/5K/50K/500K/5meg/500meg ohms. \$14.95. Post 30p




MODEL L-55 FET V.O.M.

Input impedance 10 meg ohms. 0/3/1.5/6/30/120/600V. D.C. 0/3/12/60/120/600V. A.C. 0/120μA/120mA. D.C. 0/1K/100K/10 meg/100 meg ohms \$13.97. Post 15p.




CI-5 PULSE OSCILLOSCOPE

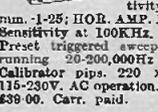For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz VRMS/mm. -1.25; HOI. AMP. Bandwidth 500KHz. Sensitivity at 100KHz. V RMS/mm. -3-25. Preset triggered sweep 1-5, 0.000sec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V. AC operation. \$39.00. Carr. paid.



TO-3 PORTABLE OSCILLOSCOPE

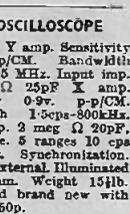3in. tube. V amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1-3cps-800KHz. Input imp. 2 meg Ω 20pF. Time base 5 ranges 10 cps-300 KHz. Synchronization. Internal/external illuminated scale 140 x 215 x 330 mm. Weight 15 1/2lb. 220/240V. AC. Supplied brand new with handbook. \$47.50. Carr. 50p.



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in. x 4in. C.R.T. Calibrated triggered sweep from -2 μsec. to 100 mill-sec. per cm. Free running time base 50 o/s-1 mc/s. Amplitude in time base calibrator and built-in calibrator. Supplied complete with all accessories and instruction manual \$87. Carr. Paid.



BELCO AF-5A SOLID STATE SINE SINE WAVE C.R. OSCILLATOR

Size 18x200,000 Hz; Square 150,000 Hz Output max. +10 dB. (10 K ohms) Operation internal batteries Attractive 7 1/2 x 5 x 2". Price \$17.50. Carr. 17p.



MODEL MG-100 SINE SQUARE WAVE AUDIO GENERATOR
 Range 19-220,000Hz Sine Wave 10-100,000 Hz Square Wave. Output Sine or Square wave 10v. F. to F. Size 180 x 30 x 90mm. Operation 220/240V. A.C. \$17.50 Post 37p.



MODEL AT201 DECADE ATTENUATOR
 Frequency range 0-200KHz. Attenuator 0-111db, 0-1db step. Impedance 600 ohms. Max. input power 30dbm. Size 180x90x55mm. \$12.50- Post 37p.



TE-65 VALVE VOLTMETER

28 ranges. D.C. volts 1.8-1,500v. A.C. volts 1.5-1,500v. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. \$17.50. P. & P. 30p. Additional probes available: R.F. \$2.12; H.V. \$2.50.



MODEL U4311 SUB-STANDARD RANGE VOLT AMMETER

Sensitivity 230 ohms/Volt AC Accuracy 5% D.C. 1% AC. Scale length 165mm. 0/300/750μA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out. Supplied complete with test leads, manual and test certificates. \$49.00. Post 50p.



G. W. SMITH & CO (RADIO) LTD. Also see opposite page and next two pages

KAMODEN HM.350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and DC current. Amplification factor of NPN, PNP, transistors, diodes, SCR's etc. 4" x 4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12.50. Post 30p.




KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1000 Meg-ohms. 500 Volt. Battery operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. £19.95. Post 30p.



ARF-300 AF/RF SIGNAL GENERATOR

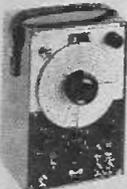

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine square 10V. P-P. RF 100 KHz to 200 MHz. Output 1r. maximum. Operation 220/240v. A.C. Complete with instructions and leads. £29.85. Post 50p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basis meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt. current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2. ±1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overflow digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100v. D.C. Input: Fully floating (3 poles). Input power: 110-230v. A.C. 50/60 cycles. Overall size: 5 1/2" x 2 1/2" x 1 1/2". AVAILABLE BRAND NEW AND FULLY GUARANTEED. £85.50 Carr. 80p.



HAND HELD 2-WAY WALKIE TALKIES

Industrial quality in robust metal cases. Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases.

2 channel	£52.50	Pair.
300 mW		Post 50p.
3 channel	£79.50	Pair.
2 watt.		Post 50p.

License required for operation in U.K.

EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7.25 each P. & P. 37p.

Model 450. 13" x 8" with twin tweeter/crossover. 55-19,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3.82 each P. & P. 25p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Date clock veneered finish. Size 14 1/2" x 8" x 7 1/2". 8 ohms. 8 watt RMS. 18 watt peak. Complete with DIN lead. £12.95 pr. Carr. 50p.

EA.41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2" x 8 1/2" x 4 1/2". £5.97. P. & P. 15p.



UNR-30 RECEIVER

4 Bands covering 550Kc/s-30Mc/s. B.F.O. Built-in speaker 220/240v. A.C. Brand new with instructions. £15.75. Carr. 37p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550Kc/s-30Mc/s. FET 8 Meter. Variable BFO for 88.5. Built-in 8 speaker. Bandspread, Sensitivity Control. 220/240v. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7 1/2". Brand new with instructions. £25. Carr. 37p.

SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 KHz and 55 to 30 MHz. Illuminated slide rule dial. Bandspread. Aerial tuning BFO, AVC, ANL, 'S' meter. AM/CW/SSB. Integrated speaker and phone socket. Operation 220/240v. A.C. or 12v DC. Size 325 x 265 x 150 mm. Complete with instructions and circuit. £29.50 Carr. 50p.

LAFAYETTE HA-600 SOLID STATE RECEIVER



General coverage 150-400Kc/s. 550 Kc/s-30Mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter. S. Meter, Bandspread, RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £50. Carr. 50p.

TRIO 9R59DS COMMUNICATION RECEIVER



4 band covering 880Kc/s to 30 Mc/s. continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. 1V frequency 465 Kc/s. audio output 1.5v. Variable BF and AF gain controls 118/250v. A.C. Size: 7" x 13" x 10" with instruction manual. £49.50. Carr. Paid.



HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 6M/100M. Output 50mW. £5.97. P. & P. 15p.



1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2.25. P. & P. 18p.




MP7 MIXER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3" inputs Mics: 3 x 3mV 50K : 2 x 3mV 600 ohm. Phone neg. 4mV 80K. Phone ceramic 100mV 1 meg. Output 250mV 100K. £3.97. P. & P. 20p.

HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE

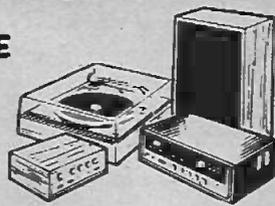SEND S.A.E. FOR FULL DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



FANTASTIC OFFER!

NIKKO TRM 50 STEREO AMPLIFIER



17 + 17 watts rms stereo amplifier with inputs for Magnetic and Crystal phono, Tuner, Tape, Aux and Tape Monitor. Outputs for two pairs of stereo speakers and Tape. Stereo headphone socket. Full range of controls including loudness control, scratch filter, etc. Size 13" x 9 1/2" x 3 1/2". Unrepeatable offer—limited stocks!

List price £59.50
OUR PRICE
£39.95
Carriage 50p



AA6300 AM/FM STEREO TUNER AMPLIFIER

20 + 20 watts rms. Magnetic, ceramic and tape inputs. FM 88-108 MHz. AM 535-1605 kHz. Dual stereo speaker outputs. Headphone socket. (Rec. List Price £117.46)

OUR PRICE **£61.95** P & P 75p

AKAI AA6300 SYSTEM

20 + 20 watt AM/FM stereo tuner amplifier. Garrard AP76. plinth and cover. G800 cartridge, pair of Mezzo III speakers.

OUR PRICE **£131.95** Carriage & Pack. £2.00

WHARFEDALE LINTON SYSTEM

Wharfedale Linton Amplifier, Linton Turntable, pair of Linton 2 speakers and all leads.

OUR PRICE **£95.95** Carr. and Ins. £1.25

LINTON RECEIVER SYSTEM £126.00. Carr. & Ins. £1.25.

AMSTRAD 8000 II SYSTEM

Amstrad 8000 II 7 + 7 watt amplifier. BSR MP60, plinth and cover. Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE **£43.50** Carr. £1.00

NIKKO TRM.50 SYSTEM

NIKKO TRM50 17 + 17 watt rms. stereo amplifier. Garrard AP76. plinth & cover. Goldring G800E cartridge, pair of Linton 2 speakers and all leads.

OUR PRICE **£93.95** Carr. and Ins. £1.50

LEAK DELTA 30 SYSTEM

Leak Delta 30 stereo amplifier. Goldring GL75, plinth, cover and G800 cartridge. Pair of Leak 150 speakers and all leads.

OUR PRICE **£110.50** Carr. and Ins. £1.50

TELETON SAQ206B SYSTEM

Teleton SAQ206B 8 + 8 watt Amplifier, BSR MP60, plinth & cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE **£50.95** Carr. £1.50

B.S.R. TD8S 8-TRACK STEREO TAPE PLAYER DECK

Integrated preamps (output 125 mV) to feed into any stereo amplifier. Automatic and manual programme selector. 4 pole synchronous motor. 210/240 V.

OUR PRICE **£12.75** Post 50p

G. W. SMITH & CO (RADIO) LTD.
Also see previous pages and opposite page

SINCLAIR IC-12

List Price £2.93
OUR PRICE £1.80
 P. & P. 10p

SINCLAIR PROJECT 60 PACKAGE DEALS

2x230/Stereo 60/PZ5. £16.95. P. & P. 37p.
 2x230/Stereo 60/PZ8. £18.00. P. & P. 37p.
 2x250/Stereo 60/PZ2. £20.25. P. & P. 37p.
 Transformer for PZ3 £3.65 extra.
 Active Filter Unit. £4.45 extra.
 Pair of Q16 Speakers. £20.70 extra.
 Sinclair Project 605. £20.97. P. & P. 37p.
 All other Sinclair Products in stock.

TRANSISTORISED FM TUNER



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 1.8x4x2 1/4in. 3 I.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 82-108Mc/s. Ready built ready for use. Fantastic value for money. £5.95. P. & P. 12p. Stereo multiplex adaptors £4.97.

AUDIOTRONIC ACR. 3500 CAR RADIO



Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker, mounting brackets and instructions.
OUR PRICE £6.50 P. & P. 50p

AUDIOTRONIC ACP-B 8 TRACK CAR PLAYER



Attractive black and silver finish. 12v neg. earth. Slider controls for volume, tone and balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.
ONLY £12.50 P. & P. 40p



TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET
 Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms.
£1.97. P. & P. 15p.



HOSIDEN DH-08S DE-LUXE STEREO HEADPHONES
 Features unique mechanical 12 way units and fitted adjustable level controls. 8 ohm impedance 20-20,000cps. Complete with spring lead & stereo jack plug.
£7.97. P. & P. 12p.



TE-1035 STEREO HEADPHONES
 Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable headband. 8 ohm impedance 20-18,000 Hz. With lead and stereo jack plug.
ONLY £1.97. P. & P. 12p.

ROTEL BARGAINS!

All brand new and guaranteed



RA310 Amp £34.95
 RA610 Amp £51.95
 RX150 Receiver £36.95
 RX200 Receiver £46.50
 RX400 Receiver £57.50
 P. & P. 50p extra any item.

ROTEL RA210 SYSTEM



OUR PRICE £54.50 Carr. & Ins. £1.25

4+8 watt amplifier, BSR MP60, plinth and cover, G800 cartridge, pair of Melway T188 speakers and all leads.

ROTEL RX150 SYSTEM



OUR PRICE £75.95 Carr. & Ins. £1.25

AM/FM 7 1/2 + 7 1/2 watt stereo tuner amplifier, BSR MP 60, plinth and cover, 11800, pair of Denton 2 speakers and all leads.

MONATONE 6750 SYSTEM



OUR PRICE £30.50 Carr. £1.00

AM/FM 4 + 4 watt stereo tuner amplifier, Garrard 2025 T/C, plinth and cover, stereo cartridge, pair of matching speakers and all leads.



SPECIAL OFFER! ROTEL RH700 STEREO HEADPHONES
 20-20,000Hz. 8-16 ohm. (List £9.95). **OUR PRICE £6.75. P. & P. 25p.**



KOSS SP.3XC STEREO HEADPHONES
 Response 10-15,000Hz. Impedance 4-6 ohms. Brand new, boxed & fully guaranteed. (List £9.50). **OUR PRICE £6.50. P. & P. 25p.**



HOSIDEN DH-02S STEREO HEADPHONES
 Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug. **ONLY £2.87. P. & P. 12p.**



CASSETTE (P. & P. 50p)

CS35D Deck	£44.95
CS35 Recorder	£57.75
CS36/CSS Speakers	£87.95
GXC40D Deck	£57.75
GXC40 Recorder	£87.95
GXC40T Deck/Receiver	£101.25
GXC45 Deck	£78.25
GXC46D Dolby Deck	£84.30
GXC46 Recorder	£90.75
GXC60D Deck	£87.65
GXC65D Dolby Deck	£98.40

CARTRIDGE (P. & P. 50p)

CR81 Deck with amps.	£86.90
CR51D Deck	£25.10
CR81T Recorder/Receiver	£93.70
CR80S8 4 channel Recorder	£114.25
CR80S8 4 channel Recorder	£94.95

TAPE (P. & P. 75p)

4000DS Deck	£59.95
4000DS Dust Cover	£3.95
172L Recorder	£80.85
X5000 Recorder	£82.50
X201D Deck	£108.20
GX220D Deck	£128.95
GX221D Deck	£138.40
GX280D	£196.50
GX370 Deck	£211.60

TAPE/CASSETTE (P. & P. 75p)

GX1900D Deck	£144.50
--------------	---------

TAPE/CARTRIDGE (P. & P. 75p)

172L Recorder	£138.40
---------------	---------

TAPE/CASSETTE/CARTRIDGE (P. & P. 75p)

X2000S Recorder	£180.75
-----------------	---------

MICROPHONES (P. & P. 60p)

ADM. II Dynamic (pair)	£7.50
------------------------	-------

RECEIVERS (P. & P. 75p)

AA8300 20 + 20 watt	£81.95
AA8000 25 + 25 watt	£92.50
AA8080 40 + 40 watt	£117.60
AA8500 65 + 65 watt	£150.50

TAPE/CASSETTE (P. & P. 75p)

GX1900D Deck	£144.50
--------------	---------

TAPE/CARTRIDGE (P. & P. 75p)

172L Recorder	£138.40
---------------	---------

TAPE/CASSETTE/CARTRIDGE (P. & P. 75p)

X2000S Recorder	£180.75
-----------------	---------

MICROPHONES (P. & P. 60p)

ADM. II Dynamic (pair)	£7.50
------------------------	-------

RECEIVERS (P. & P. 75p)

AA8300 20 + 20 watt	£81.95
AA8000 25 + 25 watt	£92.50
AA8080 40 + 40 watt	£117.60
AA8500 65 + 65 watt	£150.50

AUDIOTRONIC PROCESS 2 DOLBY SYSTEM NOISE REDUCTION UNIT



Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 15kHz ± 1dB 19kHz -35dB. Size 161" x 9" x 3 1/2". AC 200/250V.
OUR PRICE £32.50 Carr. 50p.

LOW NOISE TAPE CASSETTES



Top quality in library cases

C60	10	25	
C90	£1.29	£2.53	£5.99
C120	£1.85	£3.62	£8.59
	£2.29	£4.48	£10.63
	P. & P.	Post Free	

TAPE HEAD CLEANER 30p each.

VAT

All prices are subject to 10% VAT (10p in the £)

Order with confidence by post - but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY.

RECORD DECKS Carriage and Packing 50p

B.S.E. McDONALD	
C114 Mini	£34.95
C129 Mono	£8.50
C137	£7.00
610/TPD1	£13.85
610	£9.90
610/TPD1	£14.85
710	£19.20
810	£24.50
710/810 Plinth and Cover	£7.85
MP60	£7.65
MP60/G800	£10.25
MP60/TPD1	£12.60
MP60/TPD2	£11.25
HT70	£10.97
HT70/G800	£13.80
HT70/TPD1	£15.95
CONNOISSEUR	
BD1 Kit	£9.10
BD1 Chassis	£11.35
BD1/SAU2/Plinth/Cover	£27.60
RD2/SAU2/Chassis	£29.35
BD2/SAU2/Plinth/Cover	£28.20



GARRARD	
1025T Stereo	£4.95
2025 T/C Stereo	£6.40
SP25 III	£8.50
SP25 III/ACOM	
GP104 Ceramic	£8.50
SP25/M75-6	£13.90

PLINTHS & COVERS Carriage & Packing 50p

Budget SP25 etc.	£2.96
Budget AP76/Zero 100S	£3.95
Budget B.S.S.	£2.95
SME 2000 System	£36.40

RECORD DECK PACKAGES Carriage & Packing 75p

Complete units with stereo cartridge ready wired in plinth with cover.	
TD125/II	£52.15
TD126AB/III	£55.85
TX35	£39.25
TD160A/III	£59.25
TD160C	£43.95

GARRARD

2025 TC/PTA/ACD	£10.65
SP25 III/G800	£15.90
SP25 III/M44-2	£16.45
SP25 III/M44-7	£16.10
SP25 III/M55E	£16.90
SP25 III Module/M75-6	£18.99
AP76/G800	£23.50
AP76/M44E	£25.65
AP76/M55E	£24.95
AP76/M75ED	£31.70
AP76/M75EJ	£27.85
AP76 Module/M78-6	£28.98
AP76 Module/M75-6	£30.40
ZERO 100S Module/M85F	£41.55

B.S.E. McDONALD

210/SC7M	£6.85
MP60/G800	£15.00
MP60/TPD1/G800	£15.20
MP60/M44-7	£16.78
HT70/TPD1/G800	£18.90

GOLDRING

GL75/G800	£22.25
GL75/G800R	£24.95

GOODMANS

TD100/G800 Teak	£42.95
TD100/G800 White	£44.75

LEAF

Delta/M75-6	£43.95
-------------	--------

PHILIPS

GA105/GP200	£18.80
GA160/GP200 Teak	£20.00
GA219/GP400	£45.25

PIONEER

PL12D (Less cartridge)	£21.75
PL15C (Less cartridge)	£44.25
PL14D (Less cartridge)	£104.75
PL50 (Less cartridge)	£58.90
PL61	£110.00
PL65	£61.55

WHARFEDALE

Linton/M44-7	£23.70
--------------	--------

SPECIAL OFFER OF NEAT EQUIPMENT (Buy now while stocks last)

Neat G30J Arm	£7.50. P. & P. 25p.
Neat G30B Arm	£6.50. P. & P. 25p.
Neat V70 Cartridge (Original Pack)	£2.15
Neat V70 Cartridge (Bulk Pack)	£1.50
Neat V70F Cartridge	£3.25
Neat V60MH Cartridge	£2.15 P. & P. 12p extra.

CREDIT TERMS FOR CALLERS ON PURCHASES OF £50 AND OVER. ACCESS & BARCLAYCARD WELCOME

All prices correct at time of press. F. & O. E.

G.W. SMITH & CO (Radio) LTD

Personal Callers Welcome - All Branches Open 9-6 Mon. to Sat.

10 TOTTENHAM CT RD. LONDON, W.1
 27 TOTTENHAM CT RD. LONDON, W.1
 257/258 TOTTENHAM CT. RD. LONDON, W.1
 3 LISLE STREET, LONDON, W.C.2
 34 LISLE STREET, LONDON, W.C.2
 31 EDGWARE ROAD, LONDON, W.2

Tel: 01-637 2232
 Tel: 01-632 3715
 Tel: 01-580 0670
 Tel: 01-437 8204
 Tel: 01-437 9155
 Tel: 01 262 0387

All Mail Orders to: 11-12, Paddington Green, London, W.2
 Tel: 01-262 6562

Everyday Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p. extra. Semi-display—£6.00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisements Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House Farringdon Street, London EC4A 4AD.

RECEIVERS and COMPONENTS

Computer Panels, 5 BC108, Diodes, 4-55p (10p). Large Panels 9" x 7 1/2". Long lead trans. and comps. £4. 10 Trans 28p (10p). £45. 16 Trans. 44p (10p). Wire Ended Neons 10-50p (8p). 20-82p (8p). Silicon Diodes 650v 1 1/4A. 10-33p (5p) on tag board. 5ame with short leads 10-22p (5p).
71b. Assorted Components £1.60. p.p.
71c. Assorted Computer Panels £1.60. p.p.

J.W.B. RADIO,
75 HAYFIELD RD., SALFORD 6, LANCs.
Postage in brackets. Mail Order only.
Prices include V.A.T.

TRANSISTORS: mint, branded top grade AD161/162 c.p.r., 60p; BC107B, 12p; BC169C, 10p; 2N2926G, 12p; 2N3702, 10p; 2N3704, 10p. Diodes: OA90, 6p; IN4002, 5p. Mail order only, UK postage 5p. AMATRONIX LTD., 396 Selsdon Rd., South Croydon, Surrey, CR2 0DE.

BEDFORD ELECTRONICS

2 Grove Place, Bedford,
Bedford 51961

YOUR LOCAL
COMPONENTS SUPPLIER

Free catalogue on request

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus one used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 plus 10p p. & p. C.W.O. to CALEDONIAN COMPONENTS, Foster-ton Firs, Strathmore Road, Thornton, Fife.

TUNBRIDGE WELLS, components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 51805

Express Components

E.E. PROJECTS!

General Purpose Amp £4.50

20W Shaver Inverter £4.00

Beta Component Board

(Kit only) £1.30

Beta Transformer M218 £1.85

PLUS

Bass Booster Kit £2.00

(Supplied with full assembly details)

FREE POSTAGE (U.K. only)

17 Albert Sq. London, E15 1HJ

FOR SALE

ALL ISSUES OF E.E. Jan. '72 to Jan. '73. £8. GERAGHTY, 210 Camberwell New Road, London SE5.

EXPERIMENTERS! Hundreds of unusual items cheap. 1973 catalogue 5p. GRIMSBY ELECTRONICS, 64 Tennyson Road, Cleethorpes, Lincs. (Mail Order only).

FOR SALE. E.E. Volume 1, Nos. 1-14. Vol. 2, Nos. 1-4. Offers for complete set. Box 6.

HOLIDAYS

HOLIDAY FOR BOYS 14/16 years, Summer 1973. Tuition and practical work in electronics (and tape recording), engineering (Karting), and photography; 11 days in Norfolk—£17.50. Write for free brochure: Inter-School Christian Fellowship, c/o 1 Hubbard Road, London, SE27 9PJ.

EDUCATIONAL

FREE

TO ENGINEERS

Whatever your age or experience you must read *New Opportunities*. It describes the easiest way to pass A.M.S.E., A.M.I.M.E., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering: Mechanical, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book.

Send for your copy today—FREE!
B.I.E.T. BEE 05, (CX), Aldermaston Court, Reading, RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

TECHNICAL TRAINING in Radio, TV & Electronics thro' world-famous ICS. For details of proven home-study courses write: ICS (Dept. 751M2), Intertext House, London SW8.

DIGITAL COMPUTER Logic and Electronics. Four volume self-instructional course. £2.95 including p. and p. Money back assurance. CAMBRIDGE LEARNING (EE) 8a, Rose Crescent, Cambridge.

MISCELLANEOUS

PSYCHEDELIC MINI-STROBE

A very POWERFUL, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/ reflector unit, printed-circuit-board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours. A veritable FLICKERING FASCINATOR! Adjustable flash-rate.

GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!

SEND £2.10 (inc. VAT) for YOUR MINI-STROBE.
To: Boffin Projects, 4 Cuncliffe Road, Stoneleigh, Ewell, Surrey.
MAIL ORDER ONLY

RADIO & TELEVISION AERIAL BOOSTERS £2.95p, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50, carr. £1.50p. S.A.E. for 3 leaflets. ELECTRONIC MAIL ORDER (BURY) LTD., Bridge Street, Ramsbottom, Bury, Lancs.

AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS

because this Ministry Approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.80 (inc. VAT) NOW
S.A.E. for details

To: BOFFIN PROJECTS, DEPT. KEE,
4 CUNLIFFE ROAD, STONELEIGH, EWELL,
SURREY. MAIL ORDER ONLY

BUILD THE

TREASURE TRACER MK III Metal Locator



- Vario-cap tuning
- Excellent sensitivity and stability
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 1 1/2in.
- Prebuilt search coil assembly
- Ministry approved design
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- Completely new design

Send S.A.E. for leaflet

Complete kit

£8.90

Post 30p

Built, tested and guaranteed

£12.50

Post 30p

MINIKITS ELECTRONICS 35b LANGLEY DRIVE, WARESTEAD, LONDON E11 3LN. (Mail order only)

DIMMIT

range of light dimmers

- ★ attractive standard wall mounting models for home and office, etc.
- ★ commercial modules for studio, stage, disco and clubs, etc.
- ★ professional modules for industrial use on heaters, lamps, motors, etc.

Rotary and slider control versions. Ratings available: 400W, 1KW, 2KW. Send 10p for complete catalogue and price list. Discount for quantities. To dept. 22. Tel. 01-267-0201

YOUNG ELECTRONICS

54 Lawford Road, London, N.W.5 2LN

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide, S.A.E. orders/enquiries. Catalogue 15p. Hamilton Road, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

Everyday Electronics, June 1973

AMPLIFIERS

71b BARGAIN PARCELS
Contain many hundreds of new components—resistors, capacitors, pots, switches, crystals, etc., also computer panels. Amazing value at £1.65 (35p).

CASD AMPLIFIERS

2xECC83, EL84, EZ80 valves on 12x5x3in. chassis with tone and volume controls. 2W output to 7x4in. 3 speaker. Contained in a polished wood cabinet 14x13x9in. with a non-standard tape deck using single AC motor. Mains operation, tested in good used condition. £3 (£1 up to 300 miles, £1.25 over). Suitable cassettes £1 (25p). Spare record/replay heads 40p (3p).

GREENWELD (EE2)

24 Goodhart Way, W. Wickham, Kent. Shop at 21 Deptford Broadway, SE8, at which callers are most welcome. Carr. in brackets; SAE List; VAT EXCLUDED.

TOOLS

MICROJET WELDER
A TINY FLAME UP TO 5000°F!
WELDS, SWEATS, SOLDERS



£12.65
INC FLAME TIPS

A precision tool using a combination of butane and compressed oxygen or micro-mix. Gives a flame of pinpoint lead thickness. Adjustable temperatures up to 5,000°F. Lights instantly, no priming. Cuts metals, welds, brazes and solders, etc., gold and silver. Ideal for electrical work, jewellers, clockmakers, silversmiths. Up to 40 minutes' operation using fuel supplied. Replacement set of 2 micronoz and 1 butane cylinders £1.45 inc. post. Complete with instructions.
Our price £12.65 - 35p p. & p. Send £13.00.

JOHN DUDLEY & CO. LTD. (Dept EE4), 301 Cricklewood Lane, London, NW2.
Tel.: 01-458 5917. Callers Welcome. Open Saturdays

BINOCULAR MAGNIFIER
FOR PRECISION CLOSE-UP WORK—LEAVES BOTH HANDS FREE



6.30

See close-up work with less eye strain & fatigue. Lightweight adjustable headband. Powerfully optically ground lenses from Continental glass-works. Can be worn over normal glasses. An essential aid in electronics, home and workshop, industry, modelling. Stamp collecting. Jewellers, watchmakers and any fine work 2½ magnification £6.30 + 40p p. & p. 3 x model 60p extra. State model.

YATES ELECTRONICS (FLITWICK) LTD

DEPT. E.E., ELSTOW STORAGE DEPT.
KEMPSTON HARDWICK,
BEDFORD.

C.W.O. PLEASE. POST AND PACKING.
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request 10p stamp appreciated.

OPEN ALL DAY SATURDAYS

Please add 10% VAT

RESISTORS

1W Iskra high stability carbon film—very low noise—cleans construction.
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 1W 2% Electrovol TR5.

Power watts	Tolerance	Range	Values available	Price
1	5%	4.7k-2.2MΩ	E24	1-99 100+
1	10%	3.3MΩ-10MΩ	E12	1-0p 0-8p
1	2%	10Ω-1M	E24	1-0p 0-8p
1	10%	1Ω-3.9Ω	E12	1-0p 0-8p
1	5%	4.7Ω-1MΩ	E12	1-0p 0-8p
1	10%	1Ω-10Ω	E12	6p 5-5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix).
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 6p each.

TRANSISTORS

AC107	15p	AF124	22p	BD131	75p	OC26	45p	2N3702	13p
AC126	12p	AF125	20p	BD132	75p	OC28	50p	2N3703	12p
AC127	12p	AF126	20p	BD133	75p	OC35	50p	2N3704	13p
AC128	12p	AF127	20p	BF115	25p	OC42	12p	2N3705	11p
AC131	12p	AF139	22p	BF173	20p	OC44	12p	2N3706	11p
AC132	12p	AF178	32p	BF177	28p	OC45	12p	2N3707	12p
AC176	12p	AF180	40p	BF178	32p	OC70	12p	2N3708	10p
AC187	22p	AF181	40p	BF179	32p	OC71	12p	2N3709	11p
AC188	22p	AF182	40p	BF180	32p	OC72	12p	2N3710	11p
AD140	50p	BC108	9p	BF181	32p	OC81	12p	2N3711	11p
AD149	45p	BC109	9p	BF194	15p	OC82D	12p	2N4062	12p
AD161	35p	BC147	13p	BF195	15p	2N2904	20p	40360	35p
AD162	36p	BC148	13p	BF197	15p	2N2926R	9p	40361	35p
AF114	20p	BC149	13p	BF200	32p	2N2960	9p	40362	40p
AF115	20p	BC157	14p	BFY50	20p	2N2926G	9p	40408	40p
AF116	20p	BC158	14p	BFY51	20p	2N2926G	10p	ZTX302	15p
AF117	20p	BC159	14p	BFY52	20p	2N3054	58p	ZTX500	15p
AF117	38p	BC187	22p	BU105	225p	2N3055	60p	ZTX502	20p

ZENER DIODES

400mW 5% 3-3V to 30V, 12p. WIRE WOUND POTS, 3W, 10, 25, 50 Ω and decades to 100k Ω, 35p.

DIODES

DIODES RECTIFIER	1250V	1A	12p	SIGNAL		7p
BY127	800V	6A	25p	OA85		5p
BZ110	200V	6A	20p	OA90		5p
BZ113	50V	1A	7p	OA91		5p
IN4001	400V	1A	8p	OA202		5p
IN4004	1000V	1A	12p	IN4148		8p
IN4007				BA114		5p

BRUSHED ALUMINIUM PANELS

12in x 6in—25p; 12in x 2½in—10p; 9in x 2in—7p.

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log, or lin. 40p.
DUAL GANG, 10K + 10K etc. log, or lin. 60p.
KNOB FOR ABOVE 12p.
FRONT PANEL 65p
18 Gauge panel 12" x 4" with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA1055	15p
VA1065	15p
VA1077	15p
R53	£1.35

THYRISTORS

2N5060	50V	0-8A	30p
2N5064	200V	0-8A	47p
CR1140	400V	1A	25p
106F	50V	4A	106D
400V	4A	55p	

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 2½p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3p, 0-047µF, 0-068µF, 0-1µF, 4p, 0-15µF, 6p, 0-22µF, 7½p, 0-33µF, 11p, 0-47µF, 13p.
160V: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 0-068µF, 3p, 0-1µF 3½p, 0-15µF 4½p, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 7½p, 0-68µF, 11p, 1-0µF, 13p.
MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 0-068µF, 3½p, 0-1µF, 4p, 0-15µF, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 8½p, 0-68µF, 11p, 1-0µF, 13p
15µF, 20p, 2-2µF, 24p.

MYLAR FILM CAPACITORS 100V

0-001µF, 0-002µF, 0-005µF, 0-01µF, 0-02µF, 2½p, 0-04µF, 0-05µF, 0-068µF, 0-1µF, 3½p.

CERAMIC DISC CAPACITORS

100pF to 10,000µF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD 015/6/7 RANGE

REPLACES C426, C487 RANGES
(µF/V) 1-0/63, 1-5/63, 2-2/63, 3-3/63, 4-7/63, 6-8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6-3, 33/40, 47/4, 47/10, 47/25, 47/40, 47/63, 68/6-3, 68/16, 100/4, 100/10, 100/25, 100/40, 150/6-3, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10, 470/6-3, 5p each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/6-3, 1000/4 9p, 100/63, 150/63, 220/40, 470/25, 680/16, 1000/10, 1500/6-3 12p, 220/63, 470/40, 680/25, 1000/16, 1500/10, 2200/6-3, 15p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6-3, 4700/4, 18p.

SOLID TANTALUM BEAD CAPACITORS

0-1µF 35V	2-2µF 35V	22µF 16V	12p
0-22µF 35V	4-7µF 35V	33µF 10V	
0-47µF 35V	6-8µF 35V	47µF 6.3V	
1-0µF 35V	10µF 25V	100µF 3V	

VEROBOARD

0-1	0-15
2½ x 3½	22p
2½ x 5	24p
2½ x 7	24p
3½ x 3½	24p
3½ x 5	28p
3½ x 7	28p
17 x 2½	75p
17 x 3½	100p
17 x 5 (plain)	82p
17 x 7 (plain)	60p
17 x 2½ (plain)	42p
2½ x 5 (plain)	12p
2½ x 3½ (plain)	11p
Pin insertion tool	52p
Spot face cutter	42p
7kV 50 pins	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2-5mm insulated	8p
Standard insulated	12p	3-5mm insulated	8p
Stereo screened	35p	3-5mm screened	13p
Standard socket	15p	2-5mm socket	8p
Stereo socket	18p	3-5mm socket	8p
D.I.N. PLUGS AND SOCKETS			
2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin			
Plug 12p. Socket 8p.			
4 way screened cable 15p/metre			
6 way screened cable 22p/metre			

BATTERY ELIMINATOR

41-50 9V mains power supply. Same size as PP9 battery

LARGE (CAN) ELECTROLYTICS

1600µF	64V	74p	3200µF	16V	50p
2500µF	40V	74p	4500µF	16V	50p
2500µF	50V	85p	25V	25V	41-50
2500µF	64V	80p	5000µF	50V	£1-10
2800µF	100V	£2.60			

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0-01µF	10p	0-047µF	13p	0-22µF	20p
0-022µF	12p	0-1µF	16p	0-47µF	22p

POLYSTYRENE CAPACITORS 160V 2½p

10pF to 1,000pF E12 Series Values 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the World's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs; oxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £3.20. 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

97p Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIRCHILD



Type	1/11 12/24 25/99	Type	1/11 12/24 25/99	Type	1/11 12/24 25/99
SN7400	0-20 0-18 0-16	SN7450	0-20 0-18 0-16	SN74145	1-50 1-40 1-30
SN7401	0-20 0-18 0-16	SN7451	0-20 0-18 0-16	SN74150	2-35 2-25 2-15
SN7402	0-20 0-18 0-16	SN7453	0-20 0-18 0-16	SN74151	1-10 0-95 0-90
SN7403	0-20 0-18 0-16	SN7454	0-20 0-18 0-16	SN74153	1-35 1-27 1-20
SN7404	0-20 0-18 0-16	SN7460	0-20 0-18 0-16	SN74154	2-00 1-75 1-55
SN7405	0-20 0-18 0-16	SN7470	0-20 0-27 0-25	SN74155	1-55 1-47 1-35
SN7406	0-20 0-27 0-25	SN7472	0-20 0-27 0-25	SN74156	1-55 1-47 1-35
SN7407	0-20 0-27 0-25	SN7473	0-40 0-37 0-35	SN74157	1-50 1-70 1-50
SN7408	0-20 0-19 0-18	SN7474	0-40 0-37 0-35	SN74160	2-50 2-40 2-35
SN7409	0-45 0-42 0-35	SN7475	0-55 0-52 0-50	SN74161	2-60 2-40 2-25
SN7410	0-20 0-18 0-16	SN7476	0-45 0-42 0-35	SN74162	2-40 2-25 2-70
SN7411	0-25 0-22 0-20	SN7477	0-80 0-75 0-67	SN74163	2-30 2-25 2-70
SN7412	0-45 0-40 0-35	SN7481	1-25 1-18 1-10	SN74164	2-75 2-80 2-10
SN7413	0-20 0-18 0-16	SN7482	1-45 1-35 1-20	SN74165	4-00 3-50 3-10
SN7414	0-20 0-27 0-25	SN7483	1-00 0-90 0-85	SN74166	4-00 3-50 3-10
SN7417	0-20 0-27 0-25	SN7484	0-90 0-85 0-80	SN74167	6-25 6-00 5-10
SN7420	0-20 0-18 0-16	SN7486	0-45 0-41 0-38	SN74170	1-10 0-55 0-50
SN7422	0-48 0-44 0-40	SN7490	0-75 0-70 0-65	SN74174	3-00 1-75 1-80
SN7423	0-48 0-44 0-40	SN7491	1-00 0-85 0-90	SN74175	1-35 2-17 1-15
SN7425	0-48 0-40 0-35	SN7492	0-75 0-70 0-65	SN74176	1-60 1-35 1-20
SN7427	0-48 0-45 0-42	SN7493	0-75 0-70 0-65	SN74177	1-60 1-35 1-20
SN7428	0-48 0-45 0-42	SN7494	0-80 0-75 0-70	SN74178	1-55 1-30 1-20
SN7430	0-20 0-18 0-16	SN7496	0-80 0-75 0-70	SN74181	7-00 6-00 5-50
SN7432	0-42 0-39 0-35	SN7498	1-00 0-97 0-95	SN74182	3-00 1-80 1-60
SN7433	0-70 0-61 0-44	SN7497	6-25 5-50 5-00	SN74184	2-40 2-00 1-80
SN7437	0-65 0-60 0-50	SN74100	2-50 2-30 2-00	SN74185A	2-40 2-00 1-80
SN7439	0-65 0-60 0-50	SN74104	1-45 1-35 1-20	SN74190	1-85 1-85 1-75
SN7440	0-20 0-18 0-16	SN74105	1-45 1-35 1-20	SN74191	1-55 1-40 1-30
SN7441	0-75 0-78 0-70	SN74107	0-50 0-45 0-40	SN74192	2-00 1-90 1-80
SN7442	0-75 0-78 0-70	SN74110	0-80 0-70 0-60	SN74193	3-00 1-90 1-80
SN7443	1-00 0-95 0-90	SN74118	1-00 0-95 0-90	SN74194	3-50 2-25 2-10
SN7445	2-00 1-75 1-80	SN74119	1-90 1-75 1-85	SN74195	1-85 1-70 1-60
SN7446	2-00 1-75 1-80	SN74121	0-80 0-85 0-80	SN74197	1-55 1-40 1-30
SN7447	1-75 1-60 1-45	SN74123	2-70 2-55 2-47	SN74198	4-60 3-70 3-35
SN7448	1-75 1-60 1-45	SN74141	1-00 0-96 0-90	SN74199	4-60 3-70 3-35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SN 74 HOO } Now in stock - send for list No. 36
LOW POWER SM 74 LOO }

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA780 10p	BC147 15p	BU105 2.25	OC44 15p	T1R43 25p	2N3055 55p
AA742 15p	BC169C 15p	BY100 15p	OC45 15p	V405A 25p	2N3440 75p
AAZ13 10p	BC182 10p	BY126 15p	OC57 50p	ZTX108 15p	2N8442 1.25
AC107 25p	BC214 15p	BY127 15p	OC71 15p	ZTX200 15p	2N8525 75p
AC126 25p	BCY33 75p	BYZ13 25p	OC72 25p	ZTX301 15p	2N3614 50p
AC127 25p	BCY34 85p	CI06D 85p	OC77 45p	ZTX302 15p	2N3815 75p
AC128 25p	BCY39 1.00	CI08D 85p	OC81 25p	ZTX341 90p	2N3709 10p
AC129 25p	BCY42 80p	CI11L 55p	OC83 25p	ZTX500 15p	2N3704 10p
AC167 85p	BCY43 25p	CI11S 85p	OC85 25p	ZTX503 17p	2N3705 10p
AC168 25p	BCY65 2.50	LM309K	OC170 25p	2G301 80p	2N3714 1.50
ACY17 80p	BCY70 1.50	(T03) 1.87	OC171 30p	2N404 20p	2N3771 1.50
ACY20 20p	BCY71 90p	MAT121 25p	OC200 45p	2N457 25p	2N3773 2.50
ACT21 20p	BCY72 15p	MJE340 80p	OC201 75p	2N496 15p	2N3790 2.25
ACT38 55p	BCY87 2.90	MJE370 75p	OC292 80p	2N497 15p	2N3819 85p
AD140 50p	BCZ11 50p	MJE520 75p	OC203 50p	2N706 10p	2N3820 50p
AD149 50p	BD124 80p	MJE3955	OCY71 1.25	2N890 90p	2N3846 85p
AD161 25p	BD181 75p	1-10	ORP11 50p	2N987 45p	2N3903 1.5p
AD162 85p	BD182 80p	MJE3065	ORP60 40p	2N1181 25p	2N3906 1.5p
AF117 20p	BF167 85p	MFF105 75p	P346A 25p	2N1182 25p	2N4061 1.5p
AF118 50p	BF167 85p	MFF105 40p	RAS10A 7p	2N1205 15p	2N4062 1.5p
AF124 25p	BF173 25p	NKT214 20p	NKT304 25p	2N1204 15p	2N4125 1.5p
AF139 80p	BF179 80p	NKT216 40p	RAS508A 55p	2N1205 25p	2N4871 85p
AF236 40p	BF180 80p	NKT217 40p	TAA263 75p	2N1207 25p	2N6457 25p
AF239 40p	BF194 15p	NKT403 70p	TIL209 35p	2N1818 30p	2N6001 1.00
ASV27 30p	BFY57 25p	OA5 50p	TIP28A 50p	2N1974 1.90	2B012 10.00
ASV28 25p	BFY58 25p	OA5 50p	TIP30A 50p	2N1975 1.90	2B018 8.25
BA102 30p	BFY59 25p	OA10 25p	TIP32A 50p	2N2160 50p	2B028 3.00
BA115 7p	BFY60 25p	OA81 10p	TIP33A 70p	2N2217 25p	2B301 50p
BA146 15p	BFY61 25p	OA91 7p	TIP34A 1.00	2N2221 20p	2B303 65p
BA153 5p	BFY62 25p	OA200 7p	TIP35A 1.50	2N2222A	2B324 95p
BA156 7p	BFY63 25p	OA201 10p	TIP36A 1.00	2N2222B	40250 25p
BA157 7p	BFY64 30p	OC16 75p	TIP37A 1.50	2N2369A	40360 40p
BC107 10p	BFY65 30p	OC20 85p	TIP38A 2.50	2N2906 20p	40362 50p
BC109 10p	BFY66 30p	OC23 85p	TIP39A 2.50	2N2926 (all coils)	40408 50p
BC190 15p	BFY67 30p	OC25 40p	TIP39A 2.50	2N2926 (all coils)	40488 75p
BC118 15p	BFY68 30p	OC28 65p	TIP41A 75p	2N3053 20p	40638 1.10
BC119 15p	BFY69 30p	OC35 65p	TIP42A 85p	2N3054 50p	40430 1.00
BC127 10p	BFY70 30p	OC38 65p			
BC143 25p	BFY71 30p	OC42 40p			

VAT Prices DO NOT include Value Added Tax. From 1st April, 1973 10% must be added and shown separately to your total order (incl. cart/packing). Help us to help you receive your order without delay. E. & O. E.

QUANTITY DISCOUNTS

10% 1st + 15% 2nd + 20% 100+; 25% 250+ ANY ONE TYPE
From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value £1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	59p	2N2926	10p
1000 MC/S		All Colours	
25 + 50p		25 + 9p	
100 + 45p		100 + 8p	
500 + 40p		500 + 6p	
		1000 + 5p	

AF117 Mullard	25p
25 + 17p	
100 + 15p	
500 + 12p	

2N3819 Texas	35p
25 + 30p	
100 + 25p	
500 + 20p	
1000 + 15p	

OC170 Mullard	25p
25 + 20p	
100 + 18p	
500 + 15p	
1000 + 13p	

BC107, BC108, BC109	10p each
All Makes	
25 + 8p	
100 + 7p	
500 + 6p	
1000 + 5p	

BY127 Mullard	15p
25 + 12p	
100 + 10p	
500 + 9p	
1000 + 8p	

AD161, AD162	35p each
25 + 32p	
100 + 28p	
500 + 25p	
1000 + 22p	

OA202	10p
25 + 8p	
100 + 7p	
500 + 6p	
1000 + 5p	

2N3053	20p
25 + 18p	
100 + 15p	
500 + 12p	
1000 + 10p	

OC35 Mullard	50p
25 + 45p	
100 + 40p	
500 + 35p	
1000 + 30p	

2N3055	55p
25 + 50p	
100 + 45p	
500 + 38p	
1000 + 33p	

ZENER DIODES

400 M/W 5% Miniature
BZT 85 Range
All voltages
3-3 - 23 Volt
10p each.

25 +	8p
100 +	9p
500 +	8.5p
1000 +	5p

Any one type.

1 1/2 Watt 5% Wire Ends Metal Case
All voltages
6.8 - 100 Volts
20p each.

25 +	18p
100 +	16p
500 +	15p
1000 +	10p

Any one type.

3 Watt Plastic Wire Ends 5% SEZ Range
All voltages
6.8 - 100 Volts
30p each.

SILICON RECTIFIERS WIRE ENDED PLASTIC

Type	P.I.V. 1-11
1 amp miniature	
IN4001	50 6
IN4002	100 7
IN4003	200 8
IN4004	400 10
IN4005	800 12
IN4006	1000 15
1.5 amp miniature	
PL4001	50 8
PL4002	100 9
PL4003	200 10
PL4004	400 12
PL4005	600 12
PL4006	800 15
PL4007	1000 18

LINEAR (O/P AMPS)

709C	T08	75p
709C	T099	25p
728C	D.I.L.	25p
728C	T099	1.00
728C	D.I.L.	25p
728C	T099	1.00
741C	T099	55p
741C	D.I.L.	55p
747C	T099	1.10
747C	D.I.L.	1.10

72741P D.I.L. 60p
72748P D.I.L. 60p
SINGLAIR IC12 1.30

TOSHIBA T1901AF
TOSHIBA T1901AF
20 WATT AMP
84-47 PORT PAID
6.8 - 100 Volts
TE901AF Pre Amp
1.50

DATA AND CIRCUITS REF. 42 10p

FREE WITH PURCHASES

TRANSISTORS, IC's, TRIACS, BRIDGES, SCR's, LDR's



NEW FREE BOOKLET (No. 36) OVER 1500 TYPES - Send for yours today!

FREE!

Over 150 ways to engineer a better future



HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.R., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BEE17, Aldermaston Court, Reading RG7 4PF.

Published approximately the third Friday of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London. E.C.4A 4AD. Printed in England by Index Printers Ltd., Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/S) Ltd. South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingstons Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.95. Everyday Electronics is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.** Everything you need to know

about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

MECHANICAL	<input type="checkbox"/> Man. Prod.—cont.	<input type="checkbox"/> Constructional-cont.
<input type="checkbox"/> A.M.S.E. (Mech.)	<input type="checkbox"/> Quality Control	<input type="checkbox"/> Building Drawing
<input type="checkbox"/> Boiler Inspect. & Operation	<input type="checkbox"/> Salesmanship	<input type="checkbox"/> Build. Foreman
<input type="checkbox"/> C & G Eng. Crafts	<input type="checkbox"/> Storekeeping	<input type="checkbox"/> Carpentry & Join.
<input type="checkbox"/> C & G Fabricat.	<input type="checkbox"/> Work Study	<input type="checkbox"/> Civil & Municipal
<input type="checkbox"/> Diesel Eng.	<input type="checkbox"/> Management	<input type="checkbox"/> Engineering
<input type="checkbox"/> Eng. Inspection	<input type="checkbox"/> DRAUGHTSMANSHIP	<input type="checkbox"/> Constructional
<input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> A.M.I.E.D.	<input type="checkbox"/> Engineering
<input type="checkbox"/> Inst. Eng. & Tech.	<input type="checkbox"/> Design of Elec. Machines	<input type="checkbox"/> Construction
<input type="checkbox"/> Inst. Motor Ind.	<input type="checkbox"/> Die & Press Tool Design	<input type="checkbox"/> Surveyors
<input type="checkbox"/> Maint. Eng.	<input type="checkbox"/> Electrical	<input type="checkbox"/> Institute
<input type="checkbox"/> Mechanical Eng.	<input type="checkbox"/> Draughtsman-ship	<input type="checkbox"/> Clerk of Works
<input type="checkbox"/> Sheet Metal Work	<input type="checkbox"/> Gen. Draughts-ship	<input type="checkbox"/> Council Eng.
<input type="checkbox"/> Welding	<input type="checkbox"/> Jig & Tool Des.	<input type="checkbox"/> Geology
ELECTRICAL & ELECTRONIC	<input type="checkbox"/> Tech. Drawing	<input type="checkbox"/> Health Eng.
<input type="checkbox"/> A.M.S.E. (Elec.)	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS	<input type="checkbox"/> Hydraulics
<input type="checkbox"/> C & G Elec. Eng.	<input type="checkbox"/> Colour TV	<input type="checkbox"/> Inst. of Builders
<input type="checkbox"/> C & G Elec. Inst.	<input type="checkbox"/> C & G Radio/TV/ Electronics	<input type="checkbox"/> Inst. Works & Highway Sup.
<input type="checkbox"/> C & G Elec. Tech.	<input type="checkbox"/> C & G Telecom. Tech.	<input type="checkbox"/> Painting & Dec.
<input type="checkbox"/> Computer Elect.	<input type="checkbox"/> Frac. Rad. Elec. (with kit)	<input type="checkbox"/> Public Hygiene
<input type="checkbox"/> Elec. Maths	<input type="checkbox"/> Radio Amateurs Exam.	<input type="checkbox"/> Road Engineer.
<input type="checkbox"/> Elec. Science	<input type="checkbox"/> Radio Servicing & Repairs	<input type="checkbox"/> Structural Eng.
<input type="checkbox"/> Electronic Eng.	<input type="checkbox"/> Radio & TV Engr. Trans. Course	<input type="checkbox"/> Surveying
<input type="checkbox"/> Electrical Eng.	<input type="checkbox"/> TV Main. & Serv.	GENERAL
<input type="checkbox"/> Install. & Wiring	<input type="checkbox"/> AUTO & AERO	<input type="checkbox"/> Agricultural Eng.
<input type="checkbox"/> Motors & Measuring Instruments	<input type="checkbox"/> Aero Eng.	<input type="checkbox"/> Council of Eng. Inst.
MANAGEMENT & PRODUCTION	<input type="checkbox"/> A.M.I.M.I.	<input type="checkbox"/> Farm Science
<input type="checkbox"/> Auto Control	<input type="checkbox"/> A.E.C. Cert.	<input type="checkbox"/> General Educat.
<input type="checkbox"/> Computer Prog.	<input type="checkbox"/> Auto Engineer.	<input type="checkbox"/> Gen. Plastics
<input type="checkbox"/> Electronic Data Processing	<input type="checkbox"/> Auto Repair	<input type="checkbox"/> Pract. Maths
<input type="checkbox"/> Estimating	<input type="checkbox"/> C & G Auto. Eng. Garage	<input type="checkbox"/> Pract. Slide Rule
<input type="checkbox"/> Foremanship	<input type="checkbox"/> Management	<input type="checkbox"/> Pure & Applied Maths
<input type="checkbox"/> Inst. Cost & Man. Accountants	<input type="checkbox"/> MAA/IMI Dipl.	<input type="checkbox"/> Refrigeration
<input type="checkbox"/> Inst. Marketing	<input type="checkbox"/> Motor Vehicle Mechanics	<input type="checkbox"/> Rubber Tech.
<input type="checkbox"/> Management	<input type="checkbox"/> CONSTRUCTIONAL	<input type="checkbox"/> Sales Engineers
<input type="checkbox"/> Metrication	<input type="checkbox"/> A.M.S.E. (Civil)	<input type="checkbox"/> Tech. Report Writing
<input type="checkbox"/> Motor Trade Man. Network Plan.	<input type="checkbox"/> Architecture	<input type="checkbox"/> Timber Trade
<input type="checkbox"/> Numerical Cont.		<input type="checkbox"/> University Ent.
<input type="checkbox"/> Operational		
<input type="checkbox"/> Research		
<input type="checkbox"/> Personnel Man. Planning Eng.		
<input type="checkbox"/> Production Eng.		

Coaching for many major exams including ONC, C & G, etc.

G.C.E.

58 'O' & 'A' LEVELS SUBJECTS

Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BEE17 ON BEE17,
Aldermaston Court, Reading RG7 4PF

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

BUILD THE TEXAN

★ FREE TEAK CABINET with complete kits!

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector; Mag. P.U Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).
Constructional details Ref. No. 21 30p

SPECIAL KIT PRICE

£28.50

P & P 45p
COMPLETE WITH FREE TEAK CABINET
Designer approved kits distributed by Henry's!

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



P.W. Tricolor, as per April/May, June 1973. Parts list on request (52A).

★ SLIM DESIGN WITH SILVER TRIM
Overall chassis size 14 1/2" x 6" x 2" high

LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2" Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150 TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.50. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.50. Post 28p.



POLISHED CABINETS 150, 150TC 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 ohms)
SERIES 6 (Assembled 150 TC) per pair £16.50. Post 70p
SERIES 8 (Assembled 450) per pair £18.95. Post 70p

TEST EQUIPMENT

- SE250B Pocket Pencil Signal Injector £1.90
 - SE500 Pocket Pencil Signal Tracer £1.50
 - THL33D Robust 2K/Volt £4.55 with case £4.95
 - TE15 Grid Dip Meter 440 KHz-280 mHz £13.45
 - 500 K/V Multimeter £9.25
 - 200H 20K/V Multimeter £4.20. With case £4.95
 - AF105 50K/V Multimeter £8.50. With case £9.50
 - U4341 AC/DC Multimeter with transistor tester with steel case £10.50
 - TE30D RF Generator 120KHz-500MHz £16.50. Carr. 35p
 - TE22D Audio Generator 20Hz-200KHz £17.50. Carr. 35p
 - CI-5 3" Pulse Scope 10Hz-10mHz £39.00. Carr. 50p
 - TE65 Valve Voltmeter 28 ranges £17.50. Carr. 40p
- ALL NOMBREG MODELS IN STOCK



ML3 MW/LW TUNER TO BUILD



Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4.85, Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave Bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.
TOTAL COST TO BUILD £7.98
p.p. 32p. (Battery 22p).

PA-Disco-Lighting

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

- DJ30L 3 Channel sound to light unit, 3kW. £29.50
- DJ40L 3 channel Mic (built-in) to light, 3kW. £38.75
- DJ70S 70 watt Disco amp/mixer. £49.75
- DISCO AMP 100 watt amp/mixer. £68.85
- DJ105S 30 watt Disco amp/mixer. £32.25
- Anti-Feedback Quality Mic. £11.50
- DJ500 50 watt PA Amplifier £43.95
- DJ700 70 watt £52.75

GROUP 300 150 watt rms "Group" Valve Amplifier £86.00
FIBRE OPTICS LIGHTING. — MICS. EFFECTS. PROJECTORS.
SPOTS. DIMMERS — STANDS. MIXERS. SPEAKERS.
Everything for PA — Disco — Lighting.
FREE Stock List Ref. No. 18

- PORTABLE DISCOS — DETAILS ON REQUEST
- CREDIT TERMS FOR CALLERS




BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO

A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.

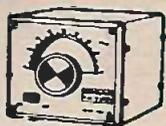TOTAL £6.97, p.p. 20p. Mk. I Decoder Kit £5.97.
Built IC Decoder £6.50. Tuning meter unit £1.75.
Mains unit for Tuner and/or Decoder P56/12 £3.25. Post 20p



SINCLAIR PROJECT 60 MODULES — SAVE POUNDS!

- Z30 £3.57; Z50 £4.37
- STEREO 60 PZ5 £3.97
- £7.97; PZ8 £4.77
- PZ6 £6.37;




PACKAGE DEALS
Post 25p
2xZ30, Stereo 60, PZ5 £15.95
2xZ30, Stereo 60, PZ6 £18.00
2xZ50, Stereo 60, PZ8 £20.25
Transformer for PZ8 £2.95
PROJECT 605 KIT £19.95

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS

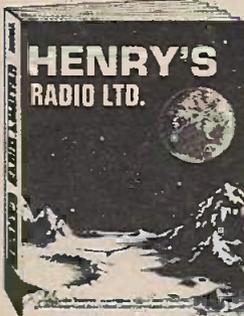Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1— for catalogue by post only. All other mail and callers to "303" see above.



VAT

All prices are exclusive of 10% VAT which must be added to all orders inc. carr/packing. (Note: Catalogue is not subject to VAT).

See earlier page of this magazine for transistors, I.C.'s and Semi Conductor prices—latest list Ref. no. 36 on request. E. & O.E.

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January 1973 Article Reprint Ref. No. 19 10p. Price £1.20.

BATTERY TAPE DECK

Garrard 9 volt Tape Deck with heads, etc. As previously advertised. Limited quantity. £9.50, post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish Italian. £1.36 per course. £5.00 per set of four.

DISCO SPOTBANK

3 channel Disco Spotbank for use with any psychedelic lighting display. £12.75, p. & p. 35p.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES. FREE—24 page detailed brochure (Ref. No. 17). You can see the savings!

HIGH QUALITY CASSETTES

The best UK low noise tapes but at a special price. 'Living Sound' cassettes meet the highest international standard (IEC 94A). Fantastic price savings.

	3 for	6 for	10 for
C60	1.00	1.80	2.80
C90	1.25	2.40	3.20
CI20	1.63	3.15	4.00

Full guarantee. Post paid. Made by EM especially for Henry's.

ULTRASONIC TRANSDUCERS

yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits. £5.90 per pair. Post 10p.

MARRIOTT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO
'17' High Impedance £2.00
'18' Med. Impedance £2.00
'36' Med.-Low Imp. £3.50
Erase Heads for above 75p
'63' 2 track mono—£1.75
Hi Imp.
'43' Erase Head for above 75p

7 SEG & NIXIE TUBES

(post 10p per 1 to 10)
XN3, XN13, GN6 0-9 side view with data, 85p.
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
3015F 7 seg £2 each. £7 per 4 with data.
12 and 24 hour clock circuits Ref. No. 31 15p.

Miniature Amplifier

5 transistor, 300mW o/p. Fitted volume and sensitivity control, 9v. Log and Lin. 40p. £1.75 each P/P 15p.

Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K, 1 meg, Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged, 60p each.

Henry's RADIO LIMITED
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open—9 am-6 pm
6 days a week
(309 closed Thursday)
All stores open all day Saturday