

An exciting hobby.... for everyone


everyday electronics

NOV. 73
15 p.



EXPLORE THE AIR WAVES!

4 Band T.R.F.
Receiver

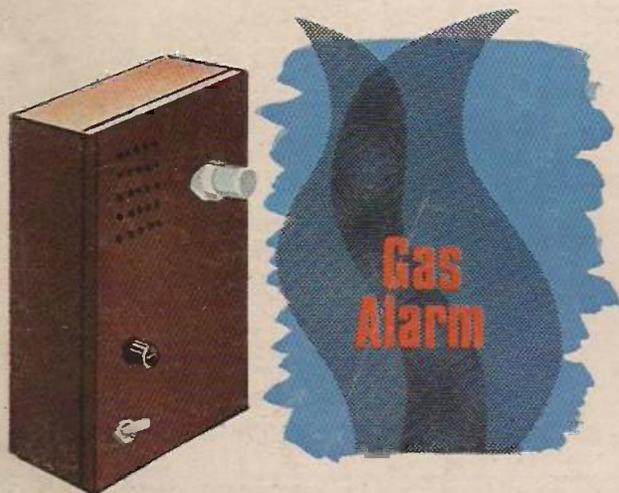

Gas
Alarm

3x3
Game



EXTRA **INSIDE**

8


PAGE SUPPLEMENT

ON CONSTRUCTIONAL METHODS

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS
ELECTRONIC CONSTRUCTION KIT.

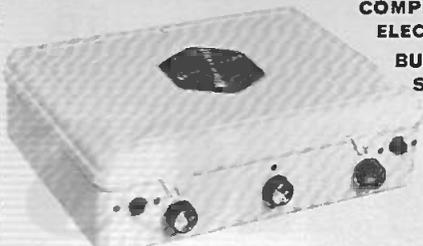BUILD THESE PROJECTS WITHOUT
SOLDERING IRON OR SOLDER.




Total Building Costs
£7-23 P P & Ins. 44p.
(Overseas P & P £1-85p.)
(+ 10% VAT 72p)

- ★ 4 Transistor Earpiece Radio
- ★ Signal Tracer
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator.
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.

- ★ 2 Transistor Regenerative Radio.
 - ★ 3 Transistor Regenerative Radio.
 - ★ Audible Continuity Tester.
 - ★ Sensitive Pre-Amplifier.
- Complete with parts price list & plans.

ROAMER TEN

with VHF including aircraft. 10 Transistors. 9 Tunable Wavebands. MW1, MW2, LW, SW1, SW2, SW3. Trawler Band, VHF and Local Stations also Aircraft Band. Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600 mw Transistors. Car Aerial and Tape Recording Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

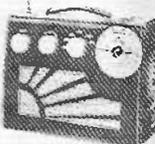

Total Building Costs **£8-50** P P & Ins. 52p
(Overseas P & P £1-85) (+ 10% VAT 85p)

NEW EVERYDAY SERIES

Build this exciting New series of designs

E.V. 5 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 6½" x 2½" approx.

Parts price list and Plans 15p. Free with parts.
Total Building Costs **£2-73** P P & Ins. 30p
(Overseas P & P £1-20p) (+ 10% VAT 27p)

E.V. 6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, loudspeaker, etc. MW/LW coverage. Push Pull output. Parts price list and Plans 15p. Free with parts.

Total Building Costs **£3-60** P P & Ins. 30p
(Overseas P & P £1-20p) (+ 10% VAT 36p)

E.V. 7 Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW. Trawler Band. SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. Parts price list and easy build plans 20p. Free with parts.

Total Building Costs **£4-08** P P & Ins. 31p
(Overseas P & P £1-85) (+ 10% VAT 40p)

ROAMER EIGHT Mk 1

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

Total Building Costs **£6-98** P P & Ins. 47p
(Overseas P & P £1-85) (+ 10% VAT 69p)



NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors, 9 Tunable wavebands as Roamer Ten, built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mw transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange. Attractive all white case with red grille and carrying strap. Size 9½" x 7" x 2½" approx. Parts Price list and Plans 30p (FREE with parts)

Total Building Costs **£6-95** P P & Ins. 44p.
(Overseas P & P £1-85p) (+ 10% VAT 69p)

POCKET FIVE

3 Tunable wavebands. M.W./L.W. and Trawler Band. 7 stages, 5 transistors and 2 diodes, superconductive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5½" x 1½" x 3½" approx. Plans and parts price list 15p. (Free with parts).



Total Building Costs **£2-28** P P & Ins. 24p
(Overseas P & P £1-25p) (+ 10% VAT 22p)

TRANSONA FIVE


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (Free with parts).

Total Building Costs **£2-50** P P & Ins. 25p
(Overseas P & P £1-25p) (+ 10% VAT 25p)

TRANS EIGHT

8 TRANSISTORS and 3 DIODES


6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8in. Speaker. 6 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

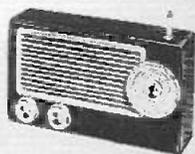

Total Building Costs **£4-48** P P & Ins. 33p
(Overseas P & P £1-25) (+ 10% V.A.T. 44p)

Please add 10% for VAT INC. P&P

"EDU-KIT"

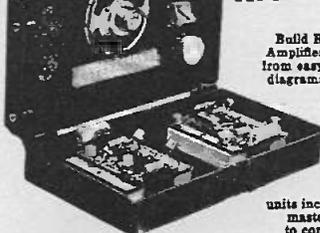

Build Radios, Amplifiers, etc. from easy stage diagrams. Five

units including master unit to construct

Components include: 2 Volume Controls; 2 Slider Switches; Fine Tone Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; 2 Plugs and Sockets; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

Parts price list and plans 25p (FREE with parts).
Total Building Costs **£5-50** P P & Ins. 33p
(Overseas P & P £1-85) (+ 10% VAT 55p)

ROAMER SIX

Case and looks as Trans-Eight

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3, Trawler band plus an Extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Plans and parts price list 25p (FREE with parts).

Total Building Costs **£3-98** P P & Ins. 31p
(Overseas P & P £1-85) (+ 10% VAT 39p)

RADIO EXCHANGE CO

61a HIGH STREET, BEDFORD, MK40 1SA

Tel. 0234 52367

Reg. no. 788372

I enclose £..... for.....

Name.....

Address.....

• Callers side entrance "Lavelis" Shop

• Open 10-1, 2.30-4.30 Mon. Fri. 9-12 Sat.

(Dept. E.E.24)

Among the 240 pages of the famous HOME RADIO COMPONENTS Catalogue, are seven pages listing Resistors . . .

Here is a page showing 2 of our unique money saving RESISTOR PACKS

HOME RADIO (COMPONENTS) LTD.

RESISTORS—Continued

These resistors are miniature carbon film components offering high stability characteristics, with a very low noise factor.

Car. No. SP22A smaller version of the SP21 pack. Containing 10 each of the popular values and 5 each of the less popular values of 1-watt resistors. Making a total of approximately 450 but quantities may be altered slightly at any time to avoid delay.

General Technical Data
 Resistance Range: 4.7Ω—10MΩ (see below)
 Tolerance: 4.7Ω—1MΩ ±5%
 1.2MΩ—10MΩ ±10%
 Wattage Rating: 25W at 40°C.

Ohmic values

4E7	330E	22K	1M5
5E6	390E	27K	1M8
6E8	470E	33K	2M2
8E2	560E	39K	2M7
10E	680E	47K	3M3
12E	820E	56K	3M9
15E	1K	68K	4M7
18E	1K2	82K	5M6
22E	1K5	100K	6M8
27E	1K8	120K	8M2
33E	2K2	150K	10M
39E	2K7	180K	
47E	3K3	220K	
56E	3K9	270K	
68E	4K7	330K	
82E	5K6	390K	
100E	6K8	470K	
120E	8K2	560K	
150E	10K	680K	
180E	12K	820K	
220E	15K	1M	
270E	18K	1M2	


Pack price . . . £5.50
 plus 24p standard p & p all parcels.



Car. No. SP23

Our famous bargain resistor pack. Containing 50 resistors (at least 25 different values).

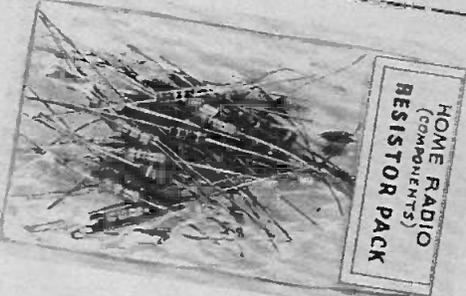Pack price 27p
 plus 24p standard p & p all parcels.



*The Famous Home Radio Components Catalogue lists 6,800 items — 1,770 of them illustrated

The Catalogue costs 55p plus 22p post and packing. Every copy contains ten vouchers each worth 5 pence when used as directed. Regularly up-dated price lists are supplied to you free

* Send now for catalogue

POST THIS COUPON
 with cheque or P.O. for 77p.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD.
 Dept. EE 234-240 London Road, Mitcham CR4 3HD

Regd. No. 912966
 London

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

10% VAT TO BE ADDED TO ALL GOODS & CARRIAGE PRICES

7" x 4" LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in. x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unstable. Price: £1.00. Free postage on this item.

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL

5 Section Extended Length 100cm Length under Fender 40cm Cable Length 120cm complete with Firing Bracket and Control Switch **£6.75** plus 25p P. & P.

STEREO / MONO HEADPHONE VOLUME CONTROL BOX
Plug Stereo phones into this control box and you then incorporate a right and left hand volume control and a stereo/mono switch. Complete with stereo jack plug and 2 m cable. A Bargain at £1. Plus 10p P. & P.

LOW VOLTAGE AMPLIFIER Few only at 5 transistor amplifier complete with volume control. Is suitable for 9V d.c. and a.c. supply. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.



"CRESCENT" DIGITAL CLOCK KIT

24 Hour Nixie Digital Clock Kit We Supply:
★ A complete set of components
★ A complete set of easy to follow instructions
★ Printed circuits made to make construction as simple as possible
★ A cabinet and front panel to give a professional finish.
All for the price of the components. £22.50 + 50p. P. & P. Please send S.A.E. for more information.

MINIATURE RELAY

6 volt 70 ohm. Single Pole Changeover. Approx. size - 1 1/2" x 1 1/2" **40p** plus 6p P. & P.

TWO WAY STEREO ADAPTOR

Stereo jack plug to two stereo line sockets complete with 110 mm of cable. For plugging two stereo inputs into one. A Bargain at 85p plus 5p P & P.

LOUDSPEAKER BARGAINS

E.M.I. 450 set 3. 8. 15 ohm £3.75 plus 38p. P. & P.
E.M.I. 350 set 8 ohm. £7.00 plus 38p. P. & P.

MINI LOUDSPEAKERS

7 1/2" (57mm) 40ohm — 50p each
2 1/2" (57mm) 80ohm — 50p each
Please include 5p. P. & P. up to 3 Mini-Loudspeakers.

MAIL ORDER DEPT. No. 11 MAYES RD. LONDON N22 6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR
OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685



TRI-VOLT BATTERY ELIMINATOR

Enables you to work your transistor radio, amplifier, or cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug you can select the voltage you require — 5V, 7 1/2V or 9 volts. This means all your transistor power pack applications can be handled by this one unit. Approx. size: 2 1/2" x 2 1/2" x 3 1/2". OUR PRICE — £2.75 + 10p. P. & P. Same model suitably wired for the Philips Cassette — £3.00 + 10p. P. & P.

"CRESCENT" 100 WATT E.M.S. ALL PURPOSE AMPLIFIER U. BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE IP 100W**
120W. r.m.s. sq. wave 200W instantaneous peak into 8 ohm (80W into 16 ohm). £14.28. carr. 45p.

★ **THE PRE-AMP MODULE**
Four control, pre-amp. Vol. Bass, Treble, Midtreble controls. Designed to drive most amplifiers using F.R.T. first stage. £3.96 carr. 25p.

★ **THE POWER SUPPLY MODULE P310**
Is supplied complete with the mains transformer. £9.96. carr. 50p. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. If you purchase all three modules. £25. carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers

TRI-VOLT CAR CONVERTER

Enables you to work your Transistor Radio, Amplifier or Cassette etc. from the 12 volt car supply positive or neg. earth. This converter supplies 5, 7 1/2 or 9 volts and is transistor regulated. Approx. size 2 1/2" x 3 1/2" x 2". Very easy to fit and a real money saving device for £2.50 + 10p. P. & P.

WAFER SWITCHES

1 pole 12 way
2 pole 2 way
2 pole 3 way
2 pole 4 way
2 pole 6 way
3 pole 4 way
4 pole 3 way
18p each. Please Inc. 5p. P. & P. Up to 3 switches.



200/250V MAINS RELAY

Heavy duty contacts. 2,500Ω coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.



"CRESCENT" BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT

This fantastic little box approx. 4" x 3" x 2 1/2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and can not harm your amplifier. A Bargain at £7.50 plus 10p P. & P.

MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 50mA. 6.3V @ 1A. This transformer is made to a very high standard and is a small size: 2 1/2" x 2 1/2" x 2 1/2". 63p plus 15p P. & P.

POTENTIOMETERS

All types 1" and less diameter. SINGLES DUAL.
5K Log or 5K
10K Lin Less 10K
25K Switch 25K Less
50K 50K Switch
100K 12pes, 100K 40p.
250K Double 250K
500K Pole 500K each
1M Switch 1M
2M 2M
24p ea.
Up to 3 Pots. Please add 5p. P. & P.

MINIATURE RELAYS

Brand new range of British made Relays. Size—1 1/2" x 1" x 1". All two changeovers with 250V. 1.5A contacts and suitable for fitting on 1mm Veroboard.
Type Volts Current Ohms.
37/A 12v 17M/A 700Ω
21/A 12v 28M/A 430Ω
12/A 5v 33M/A 185Ω
80p each.
Please include 6p P & P up to 3 Relays.

A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.
600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42

All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY
5 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED TO H.M. GOVERNMENT DEPARTMENTS, HOSPITALS, LOCAL AUTHORITIES, ETC.

INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.98 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC.. UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.98 post paid.


MAIL ORDER ONLY.
S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

88a, LICHFIELD STREET, WALSALL, STAFFS. WS1 1UZ

VEROSTRIP

LENGTH 8.5"

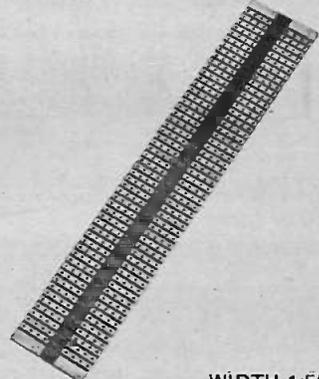

WIDTH 1.5"

Available from your Local Retailer

0.1 and 0.15 pitch Vero Strip is suitable for all applications where Tag Boards can be used.




VERO ELECTRONICS LTD. INDUSTRIAL ESTATE CHANDLERS FORD HANTS.


now...

Project 80

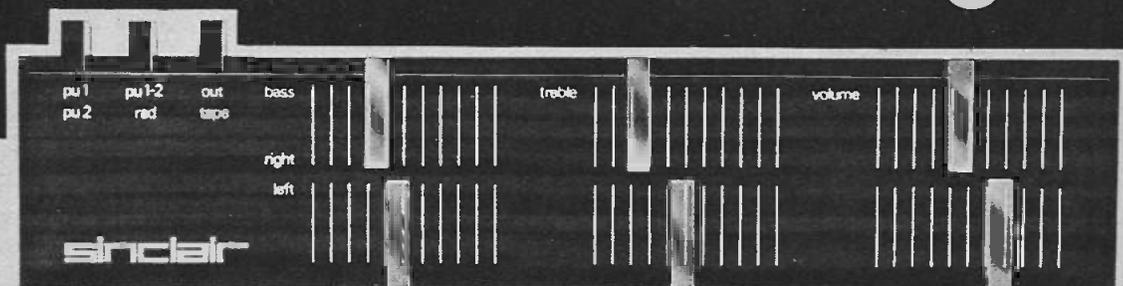...exciting new thinking
in modular hi-fi design



Stereo 80 pre-amplifier/control unit

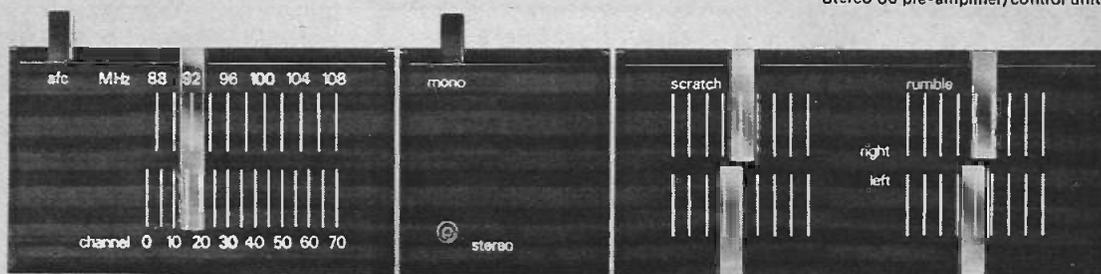

Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

the slimmest, most elegant hi-fi modules ever made



Living with hi-fi takes on new meaning now that Project 80 is here. These amazing new modules mark a brilliant technical advance all round; their size and presentation bring exciting new opportunities to install systems in ways hitherto only dreamed about but never before made practical. You can build a Project 80 system virtually anywhere and it is unbelievably simple to install and connect up. Everything that could possibly be wanted in a top quality do-it-yourself domestic hi-fi system will be found in Project 80 - compactness, elegantly ultra-modern styling, ease of fixing and operation, new control methods, and above all superb performance. New as well as popular established ideas on installation are featured on page four of this announcement to provide just a few examples of the system's fantastic versatility.

sinclair

INTERNATIONAL AUDIO FAIR STAND C 8


Project 80 new modules

Stereo 80 pre-amplifier and control unit

As with other Project 80 units, the Stereo 80 is mounted by means of two bolts fixed at the rear which pass through holes drilled in the wood or plastic on which modules are to be mounted. *All the electronics are contained within the $\frac{1}{2}$ " deep front panel!* Connecting leads are taken away similarly out of sight. Each channel in the Stereo 80 has its own independent tone and volume controls operated by sliders. This enables exceptionally good environmental matching to be obtained. Provision is made for magnetic and ceramic pick-ups, radio and tape in and out. A virtual earth input stage forms part of the up-dated circuitry of the Stereo 80 to ensure the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS


Size—260x50x20mm (10 $\frac{1}{2}$ x2x $\frac{3}{8}$ ins)
 Finish—Black, with white markings
 Inputs—Mag. P.U. 3mV RIAA corrected; Ceramic P.U. 300 mV
 Radio 300mV; Tape 30 mV
 S/N ratio—60db
 Frequency range—20Hz to 15KHz \pm 1dB; 10Hz to 25KHz \pm 3dB
 Power requirements—20 to 35 volts
 Outputs—100mV—AB monitoring for tape
 Controls—Press button for tape, radio and P.U. selection Volume, Bass—12dB to—14dB at 100Hz; Treble+11dB to—12dB at 10KHz

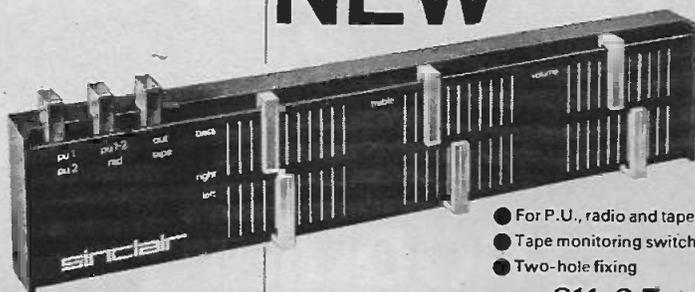

NEW

- For P.U., radio and tape
- Tape monitoring switch
- Two-hole fixing

R.R.P. £11.95 + £1.19 V.A.T.

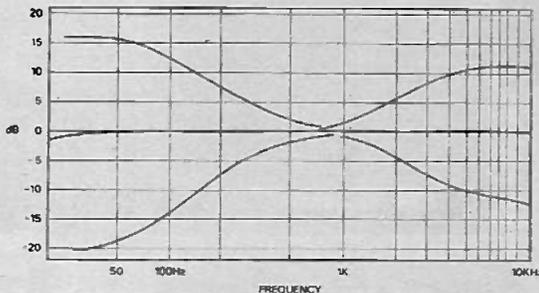

Project 80 FM tuner smaller, more efficient

A truly remarkable tuner in every way—its unbelievably compact size—its original circuitry—its dependable performance—all this in a boldly designed modern case measuring 85x50x20mm (3 $\frac{1}{2}$ x2x $\frac{3}{8}$ ins). Greater adaptability (and possibly financial convenience) results from the tuner and stereo decoder section being made available separately.

TECHNICAL SPECIFICATIONS

Size—85x50x20mm (approx. 3 $\frac{1}{2}$ x2x $\frac{3}{8}$ ins)
 Tuning range—87 to 108 MHz
 Detector—I.C. balanced coincidence, for good A.M. rejection
 AFC—Switchable, with thermistor control to prevent from drift
 One 26 transistor I.C.
 Twin dual varicap tuning
 Distortion—0.3% at 1KHz for 75KHz deviation
 Ceramic filter in I.F. section
 Aerial impedance—75 Ω or 240-300 Ω
 Sensitivity—4 microvolts for 30dB quieting
 Power requirements—12 to 45 volts



NEW

- AFC switch
- Twin dual varicap tuning
- 4-hole ceramic filter
- Slider tuning

R.R.P. £11.95 + £1.19 V.A.T.

Project 80 stereo decoder

Making the Project 80 decoder separate from the F.M. tuner gives the constructor a wider choice of systems as well as saving money in cases where stereo reception may not be required. This unit gives a 40dB channel separation with an output of 150mV per channel. The gallium arsenide light emitting beacon automatically lights up to show when a stereo transmission is tuned in. Designed essentially as an integral part of Project 80 systems, this multiplex stereo demodulator may be used in many cases with existing single channel frequency modulated tuners to provide stereo reception.
 Size—47x50x20mm (1 $\frac{1}{2}$ x2x $\frac{3}{8}$ ins)
 One 19 transistor I.C.



NEW

- Solid-state stereo indicating beacon
- Readily adaptable for use with other tuners

R.R.P. £7.45 + 0.74p V.A.T.

new constructional techniques

...and again Sinclair leads the world

- 1962 Micro-miniature power amp small enough to stand on a 10p. piece. Slimline pocket receiver smaller than a 20 cigarette pack
- 1963 Micro-6 receiver, smaller than a matchbox
- 1964 Pocket F.M. receiver; PWM amp.
- 1965 Z.12 power amplifier module; PZ.3 power supply
- 1966 Stereo 25 pre-amp/control unit
- 1967 Micromatic; Q.14 loudspeaker; the first Neoteric
- 1968 IC.10, the first ever integrated circuit for constructors use
- 1969 Q.16—improved version of Q.14; Systems 2000 and 3000: Project 60 launched
- 1970 IC.12 Project 60S
- 1971 Project 60 stereo FM tuner. Z.50 PZ.8
- 1972 Improvements to Project 60 with Z.50 MK.2 and PZ.8 Mk.3 The Executive Calculator: Digital multi-meter Q.30 speaker
- 1973 Cambridge Calculator

PROJECT 80 LAUNCHED
...and next?

Project 80 active filter unit

This efficiently designed unit makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls are applied to each channel thereby making it easier to obtain ideal stereo balance in any kind of indoor environment.

TECHNICAL SPECIFICATIONS

Size—108×50×20mm (4¼×2×¾ins)
Voltage gain—minus 0.2dB
Frequency response—36Hz to 22KHz, controls minimum
Distortion—at 1KHz—0.03% using 30V supply
HF cut off (scratch)—22KHz to 5.5KHz, 12dB/oct. slope
L.F. cut off (rumble)—28dB at 20Hz, 9dB/oct. slope

Z.40 & Z.60 power amplifiers totally short-circuit proof


Either of these entirely new power amplifiers is intended for use in Project 80 installations although, of course, they are readily adaptable to an even wider range of applications. Both Z.40 and Z.60 incorporate built-in protection against shortcircuiting and risk of damage arising from mis-use is greatly reduced. Comprehensive instructions are supplied with each of the modules.

Z.40 Technical Specifications

Size—55×80×20mm
(2½×3¼×¾ins) 9 transistors
Input sensitivity—100mV
Output—15 watts RMS continuous into 8 Ω (35V), 30 watts music power into 4 Ω (30V)
Frequency response—10Hz—100KHz±1dB
Signal to noise ratio—64dB
Distortion—at 10 watts into 8 Ω less than 0.1%
Power requirements—12-35 volts

Z.60 Technical Specifications

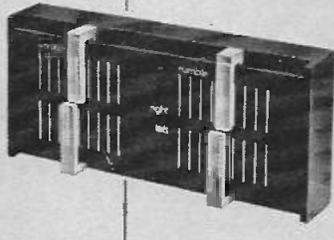
Size—55×98×20mm
(2½×3¾×¾ins) 12 transistors
Input sensitivity—100-250mV
Output—25 watts RMS into 8 Ω (45V), 50 watts music power into 4 Ω (50V)
Distortion—typically 0.03%
Frequency response—10Hz to more than 200KHz±1dB
Signal to noise ratio—better than 70dB
Built-in protection against transient overload and short circuit
Load impedance—4Ωmin; max. safe on open circuit



NEW

- For scratch and rumble control
- Transistorised active circuitry

R.R.P. **£6.95** + 0.69p V.A.T.

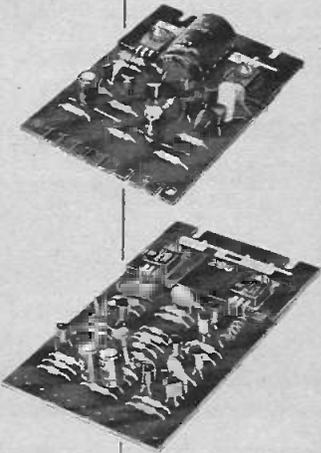

NEW

Z.40
R.R.P. **£5.45** + 0.54p V.A.T.


Z.60
R.R.P. **£6.95** + 0.69p V.A.T.

Sinclair power supply units PZ.8

the worlds most advanced unit in its class

Stabilised power supply unit. Resonant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V.

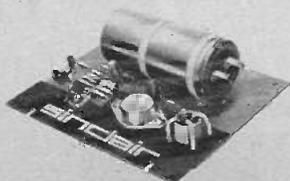R.R.P. £7.98+0.79p V.A.T.
Without mains transformer
PZ.5 30V un stabilised
R.R.P. £4.98+0.49p V.A.T.
PZ.6 35V stabilised
R.R.P. £7.98+0.79p V.A.T.




sinclair

Recommended Project 80 applications


System	The Units to use	Units cost
Simple battery record player	Z.40	£5.45 +54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10.43 +£1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	2× Z.40s, Stereo 80; PZ.6	£30.83 +£3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amplifier	2× Z.60s, Stereo 80; PZ.8	£33.83 +£3.38 V.A.T.
Indoor P.A.	Z.60, PZ.8	£14.93 +£1.49 V.A.T.
Car Radio	F.M. tuner, Z.40	£16.40 +£1.64 V.A.T.

From Sinclair the worlds most advanced hi-fi modules

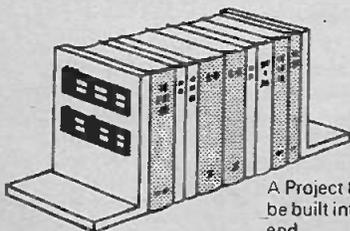
Sinclair Project 80 the ultra-modern non-obtrusive hi-fi



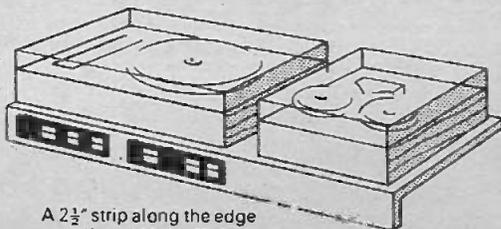
A Project 80 system could be built into a book-shelf end



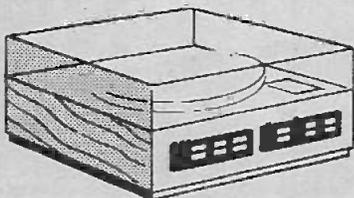
A 2 1/2" strip along the edge a shelf could be sufficient to contain a complete system



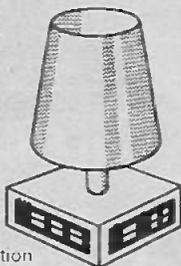
The modules mount very easily onto a playing plinth



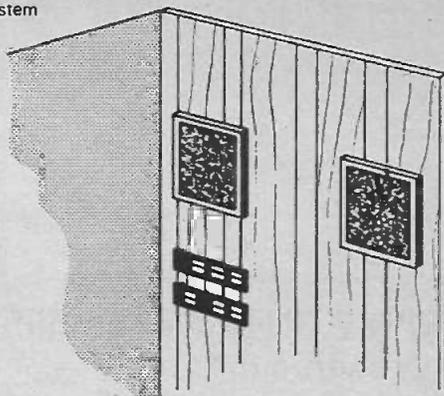
A novel application would be to build around the base of a lampshade



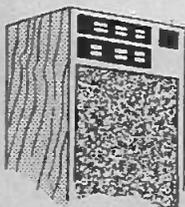Two Sinclair Q.16 loudspeakers suitably positioned together with Project 80 could be mounted on to a false wall.



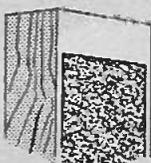Project 80 could be easily mounted onto a loudspeaker cabinet



When you have seen for yourself how fantastically slim and cleverly designed these modules are, further ways will suggest themselves in which they can become a pleasing part of your particular domestic environment.

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

EE11

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a small charge (typically £1.00) will be made.

sinclair

Sinclair Radionics Ltd.
London Road, St. Ives,
Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64311

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced there—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set". Complete with optional battery eliminator for both battery and mains use! You're almost giving them away at only £18.50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! ★ Send quickly, from receipt of goods test on mail order 7 days approval, refund if not delighted, Or call. Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques: in the field of spaceship and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions, VHF, FM/USW, AM-LW, MW, SW, gets, locally, local & new stations, not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s)! Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for ultra perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 in approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. SIZE 13in x 10in x 4in overall approx. Magnificently designed, in highly polished cases. Made to give years of perfect service. Pure & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary). With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **PLUS** ultra sensitive earphone for personal listening. **ONLY £18.50** (with mains/battery eliminator £2.25 extra). **BOX, POST, ETC. 45p, NO MORE TO PAY!** ★ **BUT WAIT**, for only 75p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to zone & time in a flash for transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard "longlife" batteries and Converter Plug. (Sorry—We cannot change these new radios for any earlier model purchased.) Send quickly to Uxbridge Road address, or call at either Store. But **HURRY!** **SHOPERTUNITIES SAVE YOU £££'s.**

THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! COMPUTERISED?



YES, 24,901 miles
SHRUNK TO ONLY 13' x 10' x 4 1/2
inches approx?

28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

BATTERY MODEL £18.50 **BOX POST ETC. 45p**
MAINS/BATTERY ELIMINATOR £2.25 extra

BRAND NEW FABULOUS **ASTRAD 17** PORTABLE RADIO & COMMUNICATIONS RECEIVER



***MUST YOU PAY UP TO £80?**

FIRST TIME EVER!
★ NOW AVAILABLE WITH **FABULOUS COMPUTERISED WORLD TUNING GUIDE!**
NO MORE GUESSWORK.
INSTANT DATA at your finger tips—enables you to **ZONE & TIME IN A FLASH** for transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £23.03 NOW!**
Fabulous BRAND NEW **SOLID STATE** This equipment got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

RECOMMENDED RETAIL PRICE £44
OUR PRICE £20.97 **CARR. ETC. 50p**

WITH REMOTE CONTROL MICROPHONE

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards)! We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First class makers. Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play back anything, anywhere! **IMPORTERS RECOMMENDED RETAIL PRICE £44! WE OFFER AT UNDER HALF PRICE** Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveler! ★ Separate ON/OFF and HI-LO volume controls! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker sockets! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. AND the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets locally, local city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player ALONE! £20.97, carr. etc., 50p—**NO MORE TO PAY!** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE**. Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 28p extra if required. Callers: ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES.

SHOPERTUNITIES LTD.

FIRST TIME EVER! SAVE £16.02!
BRAND NEW AC/DC BATTERY/MAINS

Cassette

TAPE RECORDER & PLAYER **FIRST CLASS MAKERS**

With remote control microphone.

WE COULD CHARGE UP TO £26.97!
OUR PRICE £10.95 **POST ETC. 50p**

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb deluxe portable BATTERY/MAINS tape recorder and player—and incredible Shopertunities bring it to you for ONLY £10.95. Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest BEST! Expensive "MASTER SWITCH" control) AND **AUTOMATIC LEVEL CONTROL**. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60 or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote-control microphone, etc. Size 9 1/2in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Importers recommended selling price £26.97!) **OUR PRICE ONLY £10.95, post, etc. 50p. NO MORE TO PAY!** ★ Send quickly, test on mail order 7 days approval from receipt of goods—refund if not delighted. **BONUS OFFER—Cassette tape, Standard batteries AND microphone stand 55p extra, if required.**

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores. (COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn Store.)

Dept. EE/NC/23, 164 UXBIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AG. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.). BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

FREE BOOKLET

All types of
TRANSISTORS — RECTIFIERS
BRIDGES — SCR'S — TRIACS
INTEGRATED CIRCUITS
F.E.T. — LIGHT DEVICES

OVER 1500 DIFFERENT DEVICES
 ENTIRELY NEW 1973 EDITION
SEND FOR YOUR FREE COPY TODAY

INTEGRATED CIRCUITS VERY IMPORTANT. ONLY branded I.C.'s
 are the FULL manufacturers specifications.
 ALL others are not. Henry's sell only branded Integrated Circuits... FROM TEXAS
 ... I.T.T. ... FAIRCHILD ... SIGNETICS. So why buy alternatives or under
 spec. devices when you can purchase the genuine article from us — ex stock...
 need we say more!



More Devices
 New Ranges
 This is a must for all

TBA800 5 WATT I.C.
 Suitable alternative to
 SL403D, 5.30 watt operat-
 ed, 8716 ohm 5 watt
 output.
 With circuits and
 data £1.50



Sinclair IC12
 with circuits and data.
 6 watt IC with printed
 circuit board
 28 volt output £1.80




ZN414 IC
 Integrated circuit radio as
 featured by many magazines
 (PW Jan. 73 Reprint
 Ref. No. 19 for 10p) £1.20




**Toshiba Power and
 Pre-amplifier modules**
TM9013P 20 watt
 Power amplifier 22-0-22
 or single 45 volts
 operated £4.57
TG9014P Stereo on
 two channel preamplifier. £1.50
 (circuit book No. 42 price 10p)



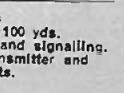Ultrasonic Transducers
 Operate at 40KHz up to 100 yds.
 Ideal remote switching and signalling.
 Complete with data transmitter and
 receiver new I.C. circuits.
 Per pair £5.50



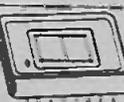3015F 7 SEG.
 I.C. size complete with
 data price £2 each or
 4 for £7
 (digital clock circuits
 ref. No. 31, 15p)



TRANSISTORS SPECIAL OFFER

2N3055	AF117
25 47p ea	25 15p ea
100 42p	100 12p
500 39p	500 13p
1000 34p	1000 10p

BY127
 25 12p ea
 100 10p
 500 9p
 1000 8p

OC35
 25 46p ea
 100 42p
 500 38p
 1000 34p

ZENER DIODES
 400 m/w BZY88/
 BZX83. From 3.3
 volt - 33 volts 10p
 each

LINEAR I.C.
 702C (T05) 75p
 709C (T05) 39p
 709C (D.I.L.) 39p
 723C (T099) 90p
 723C (D.I.L.) 90p
 728C (D.I.L.) 45p
 728C (T099) 45p
 741C (T05) 50p
 741C (D.I.L.) 50p
 747C (T099) £1.00
 748C (D.I.L.) 61p

**1.3 watts 5% Mini-
 tubulars**
 IN4700-series
 From 3.3 volt - 33
 volt 18p each.

4 AMPS P.I.V.
 B4/100 100v 55p
 B4/200 200v 55p
 B4/400 400v 65p
 B4/600 600v 75p
 B4/800 800v £1.60
 1H x 1L x 7/8" dia.

**10 watts. Std
 Mounting. 2S
 series 6-8 volts -
 100 volts 5% 40p
 each.**

6 AMPS P.I.V.
 B6/05 50v 85p
 B6/10 100v 70p
 B6/20 200v 80p
 B6/40 400v 90p
 B6/60 600v £1.00
 1H x 1L x 7/8" dia.

**SILICON
 RECTIFIERS**
 1 amp series
 IN4001 to IN4007
 From 6p ea
 1.5 amp
 PL4001 to PL4007
 From 8p ea
 3 amp
 PL7001 to IN5400
 From 14p ea
 Send for full list 36

**SEMI-
 CONDUCTOR
 QUANTITY
 DISCOUNTS**
 10% 12% - 15%
 25% + 20% 100+
 Any one type
 except where
 quantity
 discounts shown.
 Min. order £20.00
 please.

**MORE OF
 EVERYTHING
 AT
 HENRY'S**
 See pages 499-501,
 and Back Cover of
 this magazine.
BEST VALUE

**TRIACS - Std. mounting with
 accessories**
3 AMP RANGE
 Type P.I.V. Price ea.
 SC35A 100v 80p
 SC35B 200v 85p
 SC35D 400v 90p
 SC35E 500v £1.20

6 AMP RANGE
 SC40A 100v 90p
 SC40B 200v 95p
 SC40D 400v £1.20
 SC40E 500v £1.50

10 AMP RANGE
 SC45A 100v £1.05
 SC45B 200v £1.15
 SC45D 400v £1.45
 SC45E 500v £1.85

15 AMP RANGE
 SC50A 100v £1.45
 SC50B 200v £1.65
 SC50D 400v £1.95
 SC50E 500v £2.25

TRIACS - Additional Types
 40430 TRIAC (T065) 85p
 40689 TRIAC (Plastic) 90p
 40486 TRIAC (T05) 75p

**NEW RANGES
 BRIDGE RECTIFIERS
 FEATURES SMALL SIZE AND
 LOW COST. Sizes are approx.**
250MA QUARTER AMP
 B02/05 50 PIV 16p
 B02/10 100 PIV 18p
 1/2" x 1/2" dia.

1 AMP P.I.V.
 B1/05 50v 25p
 B1/10 100v 25p
 B1/20 200v 28p
 B1/60 600v 38p
 1H x 1L x 7/8" dia.

2 AMPS P.I.V.
 B2/05 50v 35p
 B2/10 100v 40p
 B2/20 200v 45p
 B2/60 600v 50p
 B2/100 1000v 55p
 1H x 1L x 7/8" dia.

4 AMPS P.I.V.
 B4/100 100v 55p
 B4/200 200v 55p
 B4/400 400v 65p
 B4/600 600v 75p
 B4/800 800v £1.60
 1H x 1L x 7/8" dia.

6 AMPS P.I.V.
 B6/05 50v 85p
 B6/10 100v 70p
 B6/20 200v 80p
 B6/40 400v 90p
 B6/60 600v £1.00
 1H x 1L x 7/8" dia.

**SILICON CONTROLLED
 RECTIFIERS**
 Type
ONE AMP (T03) P.I.V.
 CRS 1/05AF 50v 30p
 CRS 1/10AF 100v 30p
 CRS 1/20AF 200v 35p
 CRS 1/40AF 400v 45p
 CRS 1/60AF 600v 55p

THREE AMP (T048)
 CRS 3/05AF 50v 40p
 CRS 3/10AF 100v 40p
 CRS 3/20AF 200v 45p
 CRS 3/40AF 400v 55p
 CRS 3/60AF 600v 65p

FIVE AMP
 CRS 5/400 400v 60p
SEVEN AMP (T048)
 CRS 7/100 100v 80p
 CRS 7/200 200v 85p
 CRS 7/400 400v 95p
 CRS 7/600 600v 95p

Type	1/11	12/29	30/50	Type	1/11	12/29	30/50
	2p	5p	8p		2p	5p	8p
8N7400N	0.20	0.18	0.16	8N7448N	1.60	1.27	1.13
8N7401N	0.20	0.18	0.16	8N7450N	0.20	0.18	0.16
8N7402N	0.20	0.18	0.16	8N7451N	0.20	0.18	0.16
8N7403N	0.20	0.18	0.16	8N7452N	0.20	0.18	0.16
8N7404N	0.20	0.18	0.16	8N7453N	0.20	0.18	0.16
8N7405N	0.20	0.18	0.16	8N7454N	0.20	0.18	0.16
8N7406N	0.20	0.18	0.16	8N7455N	0.20	0.18	0.16
8N7407N	0.20	0.18	0.16	8N7456N	0.20	0.18	0.16
8N7408N	0.20	0.18	0.16	8N7457N	0.20	0.18	0.16
8N7409N	0.20	0.18	0.16	8N7458N	0.20	0.18	0.16
8N7410N	0.20	0.18	0.16	8N7459N	0.20	0.18	0.16
8N7411N	0.20	0.18	0.16	8N7460N	0.20	0.18	0.16
8N7412N	0.20	0.18	0.16	8N7461N	0.20	0.18	0.16
8N7413N	0.20	0.18	0.16	8N7462N	0.20	0.18	0.16
8N7414N	0.20	0.18	0.16	8N7463N	0.20	0.18	0.16
8N7415N	0.20	0.18	0.16	8N7464N	0.20	0.18	0.16
8N7416N	0.20	0.18	0.16	8N7465N	0.20	0.18	0.16
8N7417N	0.20	0.18	0.16	8N7466N	0.20	0.18	0.16
8N7418N	0.20	0.18	0.16	8N7467N	0.20	0.18	0.16
8N7419N	0.20	0.18	0.16	8N7468N	0.20	0.18	0.16
8N7420N	0.20	0.18	0.16	8N7469N	0.20	0.18	0.16
8N7421N	0.20	0.18	0.16	8N7470N	0.20	0.18	0.16
8N7422N	0.20	0.18	0.16	8N7471N	0.20	0.18	0.16
8N7423N	0.20	0.18	0.16	8N7472N	0.20	0.18	0.16
8N7424N	0.20	0.18	0.16	8N7473N	0.20	0.18	0.16
8N7425N	0.20	0.18	0.16	8N7474N	0.20	0.18	0.16
8N7426N	0.20	0.18	0.16	8N7475N	0.20	0.18	0.16
8N7427N	0.20	0.18	0.16	8N7476N	0.20	0.18	0.16
8N7428N	0.20	0.18	0.16	8N7477N	0.20	0.18	0.16
8N7429N	0.20	0.18	0.16	8N7478N	0.20	0.18	0.16
8N7430N	0.20	0.18	0.16	8N7479N	0.20	0.18	0.16
8N7431N	0.20	0.18	0.16	8N7480N	0.20	0.18	0.16
8N7432N	0.20	0.18	0.16	8N7481N	0.20	0.18	0.16
8N7433N	0.20	0.18	0.16	8N7482N	0.20	0.18	0.16
8N7434N	0.20	0.18	0.16	8N7483N	0.20	0.18	0.16
8N7435N	0.20	0.18	0.16	8N7484N	0.20	0.18	0.16
8N7436N	0.20	0.18	0.16	8N7485N	0.20	0.18	0.16
8N7437N	0.20	0.18	0.16	8N7486N	0.20	0.18	0.16
8N7438N	0.20	0.18	0.16	8N7487N	0.20	0.18	0.16
8N7439N	0.20	0.18	0.16	8N7488N	0.20	0.18	0.16
8N7440N	0.20	0.18	0.16	8N7489N	0.20	0.18	0.16
8N7441N	0.20	0.18	0.16	8N7490N	0.20	0.18	0.16
8N7442N	0.20	0.18	0.16	8N7491N	0.20	0.18	0.16
8N7443N	0.20	0.18	0.16	8N7492N	0.20	0.18	0.16
8N7444N	0.20	0.18	0.16	8N7493N	0.20	0.18	0.16
8N7445N	0.20	0.18	0.16	8N7494N	0.20	0.18	0.16
8N7446N	0.20	0.18	0.16	8N7495N	0.20	0.18	0.16
8N7447N	0.20	0.18	0.16	8N7496N	0.20	0.18	0.16
8N7448N	0.20	0.18	0.16	8N7497N	0.20	0.18	0.16
8N7449N	0.20	0.18	0.16	8N7498N	0.20	0.18	0.16
8N7450N	0.20	0.18	0.16	8N7499N	0.20	0.18	0.16
8N7451N	0.20	0.18	0.16	8N7500N	0.20	0.18	0.16


**LARGER QUANTITY AND O.E.M. PRICES PHONE (01) 723 3666. PRICING OF
 SNT400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED
 REGARDLESS OF MIX. SNT4 - HIGH POWER... SNT4 - LOW POWER
 SERIES IN STOCK. SEND FOR LIST 36, FREE ON REQUEST. LOW POWER
 SOCKETS 14 PIN... 15p 16 PIN... 17p. 8 PIN... 14p**

TRANSISTORS A SELECTION FOR FULL LIST SEND FOR BOOKLET 36 TODAY

AAZ13 10p	BC182 12p	BYZ13 35p	OC36 85p	ZTX108 10p	2N3714 1.70
AC107 35p	BCY32 85p	CO16 50p	OC44 18p	ZTX300 14p	2N3771 1.80
AC128 20p	BCY39 1.00	GET111 55p	OC45 18p	ZTX302 18p	2N3775 2.25
AC187 20p	BCY56 2.50		OC71 15p	ZTX500 15p	2N3790 2.25
AC177 35p	BCY70 1.50	GET115 55p	OC72 25p	2G301 40p	2N3816 2.5p
ACY39 85p	BCY71 20p	GET880 55p	OC77 55p	2N697 55p	2N3819 35p
AD149 50p	BCY72 13p	LM309K 1.87	OC81 28p	2N706 10p	2N3903 15p
AD161 30p	BD134 80p		OC83 25p	2N930 20p	2N4002 14p
AD162 30p	BD131 85p	MAT121 28p	OC140 65p	2N987 45p	2N4126 15p
AP117 20p	BF115 22p	MJE33 50p	OC120 25p	2N1132 25p	2N4871 35p
AP118 50p	BF180 33p	MJE520 85p	OC205 90p	2N1204 25p	2N4857 38p
AP139 35p	BF194 13p	MJE3055 75p	OC202 80p	2N1613 20p	2N5008 30p
AP186 40p	BFX13 25p	MPP105 46p	OCPT1 1.00	2N1671 1.00	2N5028 8.90
AP239 45p	BFX33 55p	MPT214 28p	OCPT2 55p	2N2147 75p	2N5033 7.90
ASX27 30p	BFY28 20p	NK7140 80p	ORP60 45p	2N2160 85p	40250 45p
BA113 10p	BFY50 20p	OAG 80p	P346A 20p	2N2926 10p	40261 45p
BA115 5p	BFY51 20p	OA2 10p	PC120 25p	2N3053 20p	40262 40p
BC107 12p	BFY64 45p	OA81 10p	TIP29A 58p	2N3064 45p	40108 50p
BC108 12p	BFY90 75p	OA200 10p	TIP30A 58p	2N3055 45p	40486 75p
BC109 14p	BLY36 6.25	OA200 10p	TIP31A 61p	2N3440 50p	40636 1.00
BC113 16p	BLX20 15p	OC16 85p	TIP41A 74p	2N3442 1.10	40430 85p
BC147 12p	BY100 15p	OC20 85p	TIP42A 80p	2N3525 80p	
BC169C 14p					

Henry's

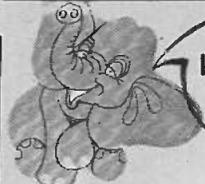PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS
 IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS
 You need a catalogue! 55p post paid complete with Discount Vouchers



UK's
**LARGEST RANGE
 OF KITS &
 GADGETS**

TEST EQUIPMENT

MULTIMETERS

- (carr. etc. 30p)
- 200H (M210) 20K/Volt Siimline with case 4-95
 - TLH33D 2K/Volt Robust with case 4-95
 - U437 10K/Volt Steel case, AC up to 40 KHz 4-95
 - U432A 20K/Volt with AC current ranges 8-00
 - AF105 50K/Volt with Leather case 9-50
 - U431S 20K/Volt AC current, Steel case 10-50
 - U4341 Plus Built In transistor tester 10-50
 - Model 500 30K/Volt 9-95



OTHER EQUIPMENT

- SE250B Pocket Signal Injector 1-90 carr. 15p
- SE300 Pocket Signal Tracer 1-50 carr. 15p
- TE15 Grid Dip meter 440KHz-280MHz 13-45 carr. 30p
- TE40 AC Millivoltmeter 1-2mHz 18-75 carr. 35p
- TE65 28 Range valve voltmeter 19-25 carr. 40p
- TE20D 120kHz-500MHz RF Generator 16-95 carr. 40p
- TE22D 20Hz-200kHz Audio Generator 18-75 carr. 40p
- SE350A Deluxe Signal Tracer 9-95 carr. 20p
- SE400 Volts/ohms/R-C sub./RF field/RF gen. 11-25 carr. 20p

A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester 5-50 p & p 15p
- E1300 Mono mag. cart. preamp. 1-95 p & p 15p
- E1310 Stereo mag. cart. preamp. 4-95 p & p 25p
- Easiophone telephone amplifier 6-15 p & p 25p
- D1203 Teleamp. with PU coil 3-60 p & p 20p
- LL1 Door Intercom. and chime 11-95 p & p 25p
- Chattalite (lights as you talk) 13-90 p & p 20p
- 1 Kw Dimmer/controller 3-00 p & p 10p
- 3rd Twin spring unit For 2-75 p & p 15p
- 16" Twin spring unit Reverbs 8-50 p & p 25p
- Car Tachometer Electronic 7-50 p & p 15p
- VHF 205 Merline band converter 3-95 p & p 15p
- B2005 4 Ch. mic. mixer 2-95 p & p 15p
- B2004 2 ch. Stereo mixer 4-75 p & p 15p



BUILD THIS TUNER

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 22" x 3 1/2". All parts £4-85, carr. 15p.

EXCLUSIVE: SPECIAL OFFERS

- MW/LW CAR RADIO AKAI GXC40 Stereo cassette recorder, and fixings. £6-50 carr. £59-95 carr/pack. 50p.
- 8 TRACK CAR STEREO (- Earth) with speakers in Pods & fixings. £12-50 carr/pack. 40p.
- HANIMAX HC1000 Battery cassette recorder. £10-50 carr/pack. 25p.
- HANIMAX HC2000 Battery/Main cassette recorder. £13-50 carr/pack. 30p.
- AKAI ADM microphones. £5-95 carr/pack. 20p.
- 5 WAVEBAND PORTABLE TWIN SPEAKER RADIO. FM/MW/SW/AIRCRAFT—PUBLIC SERVICES. £10-45 carr/pack. 30p.
- PORTABLE CASSETTE TAPE PLAYER—for car or carry around. £7-25 carr/pack. 20p.
- HANIMAX POCKET CALCULATOR WITH % KEY. £33-50.


SPECIAL PURCHASES

- AVOMETER MOVEMENTS AVO 8 or 9 50mA MOVEMENTS. Ex. Brand New AVO's £3-50 Post 20p.
- UHF TV TUNERS CHANNELS 21 TO 64 Brand new transistorised geared tuners for £25 Line Receiver IF output. £2-50. Post 20p.

EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

- | Model No. | Description | Price |
|-----------|--|-------|
| 310 | Radio control receiver | 3-00 |
| 300 | 4-channel R/C transmitter | 5-75 |
| 345 | Superhet R/C receiver | 5-00 |
| 495 | TV sweep generator | 10-24 |
| 435 | AM signal generator | 9-25 |
| 460 | FM signal generator | 9-91 |
| 65 | Simple transistor tester | 1-18 |
| 115 | 8 watt Amplifier | 2-87 |
| 120 | 12 watt amplifier | 3-88 |
| 125 | Stereo control unit | 4-20 |
| 130 | Mono control unit | 3-55 |
| 605 | Power supply for 115 | 3-88 |
| 610 | Power supply for 120 | 4-08 |
| 615 | Power supply for 2 x 120 | 4-85 |
| 230 | AM/FM aerial amplifier | 2-79 |
| 240 | Auto packing light | 5-18 |
| 275 | Mic. preamplifier | 5-83 |
| 460 | Electronic voltmeter | 17-51 |
| 485 | 0-12v 300mA STAB. supply | 9-68 |
| 570 | LF generator 10Hz-1mHz | 12-60 |
| 575 | Sq. wave generator 20Hz-20KHz | 12-87 |
| 590 | SWR meter | 10-24 |
| 620 | Hi-CAD Charger 1-2-12v | 7-47 |
| 630 | STAB Power supply 6-12v 0-25-0-1A | 7-65 |
| 690 | DC motor speed Gov. | 2-83 |
| 700 | Electronic Chaffinch | 5-96 |
| 705 | Windscreens wiper timer | 5-56 |
| 760 | Acoustic switch | 6-87 |
| 780 | Metal Detector (electronics only) | 7-27 |
| 790 | Capacitive Burglar alarm | 6-16 |
| 810 | Dynamic Compressor | 6-79 |
| 835 | Guitar preamp. | 3-75 |
| 840 | Delay car alarm | 5-20 |
| 875 | CAP. Discharge Ignition for car engine (-Ve Earth) | 10-68 |
| 80 | Scope Calibrator | 1-98 |
| 255 | Level Indicator | 5-50 |
| 430 | 3mHz Millivoltmeter | 18-23 |
| 525 | 120-160mHz VHF timer | 9-33 |
| 715 | Photo cell switch | 6-83 |
| 795 | Electronic continuity tester | 9-88 |
| 860 | Photo timer | 12-04 |
| 871 | Slide projector auto feed control | 8-72 |
| 235 | Acoustic Alarm for driver | 6-96 |
| 465 | Quartz XTAL checker | 7-89 |

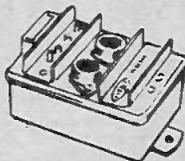ALL KITS OFFERED
 SUBJECT TO
 STOCK
 AVAILABILITY



BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7-88 (battery 22p), carr. etc. 32p.



MULTI-USE & RADIONIC KITS

- | | | |
|-------|------------------------|-------|
| 10-1 | 10 Projects | 3-60 |
| 50-1 | 10 Projects | 8-00 |
| 150-1 | 150 Projects | 13-20 |
| | Telephone Communicator | 7-20 |
| X20 | 20 (Elec.) Projects | 4-95 |
| X40 | 40 (radio) Projects | 9-45 |

All transistor circuits with hand books

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/Erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9-50 carr. 30p

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

- Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.
- ANGED Log and Lin 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.

Complete with knobs.

MARIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO '17' High Impedance £2-00

- '18' Med. Impedance £2-00
- R730/ET3 2 track mono Record/Erase low Imp. 75p pair.
- Erase Heads for '17' and '18' 75p
- '63' 2 track mono, Hi Imp. £1-75
- '43' Erase Head for '63' 75p

(Post, etc. 15p any quantity).

SINCLAIR & MINIATURE AMPLIFIERS

AMPLIFIERS (carr. etc. 20p)

- 4-300, 0-3 watt 9 volt 1-75
- 104, 1 watt 9 volt 2-20
- 304, 3 watt 9 volt 2-50
- 555, 3 watt 12 volt 2-85
- E1208, 5 watt 12 volt 4-50
- 608, 10 watt 24 volt 4-10
- 410, 10 watt 28 volt 4-95
- 230, 15 watt 30 volt 3-57
- E1206, 30 watt 45 volt 9-75


- Z50, 30 watt 50 volt 4-37
- E1210, 2 1/2 + 2 1/2 watts 12 volt 5-25
- RE500, 5 watt IC mains operated Amplifier with controls £8-30
- SAC14, 7 + 7 watt Stereo with controls £8-00
- SAC13, 15 + 15 watt Stereo with controls £11-00

SINCLAIR UNITS

- (carr. 20p) Z30 S-57 Z50 S-4-37 Stereo 60 Preamplifier 1-97
- PZ5 £3-97, PZ6 £5-37
- PZ8 (for Z50) £4-77 (TRANS £2-95)
- AFU £4-45

SINCLAIR PACKAGE DEALS

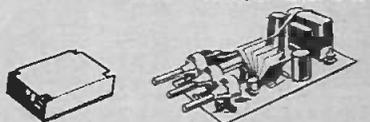- Post 25p
- 2 x Z30, Stereo 60, PZ5 15-95
- 2 x Z30, Stereo 60, PZ6 18-00
- 2 x Z50, Stereo 60, PZ8 20-25
- Transformer for PZ8 2-95
- PROJECT 605 KIT 19-95



POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
- 470C 67 1/2 volt 300 MA (includes Multi-Adaptor for Tape Recorders, etc.) 6-95 post 20p
 - Car Lighter Voltage Adaptors 2.0-1A (State voltage 6v, 7 1/2v, 9v) 1-95 ea. post 25p
 - SC202 3/6/7 1/2 volt 400mA 3-25 carr. 30p
 - HC244R Stabilised version 4-25 carr. 30p
 - P500 9 volt 500mA 2-50 post 20p
 - P11 24 volt 500mA (chassis) 2-50 post 20p
 - P15 26/28 volt 1 amp (chassis) 2-79 post 20p
 - P1080 12v 1 amp (chassis) 3-25 post 20p
 - P1081 45v 0-9 amp (chassis) 4-40 post 20p
 - P12 44-42 volt 0-4-1 amp 6-75 post 30p
 - SE101A 3/6/9/12 volt 1 amp (Stab.) 9-15 post 25p
 - RP164 6/7 1/2/9/12 1 amp (Stab.) 9-95 post 30p



FIBRE OPTICS

- 0-01 Diam. Mono Filament £1-50 per 25 metre reel
- 0-13 Diam. 64 Fibres Sheathed. £1-00 per metre
- SPRAY'S 15mm Diam. Marcs Tails £9-50.




Henry's RADIO LIMITED SEE FACING PAGE FOR ADDRESSES
 EDGWARE ROAD, W2

Henry's

DISCOUNT HI-FI, TV, TAPE AND CAR ENTERTAINMENT

Low prices means less VAT - Henry's give full guarantees and demonstrations for callers. Plus big savings. Also at Modern Electrics (Retail) Ltd., 120 Shaftesbury Avenue, W.1. Your Sony dealer.

**BEST VALUE
IN U.K.**

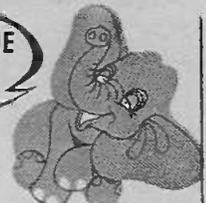

STEREO AMPLIFIERS

(carr./packing 50p)		
AKAI	AA5200	61-70
	AA5500	78-50
	AA5800	117-50
AMSTRAD	1C2000 Mk. II	29-50
	4000	23-10
EAGLE	TSA149	25-10
	TSA151	34-85
	AA2	30-80
	AA4	42-45
	AA5	55-95
	DA1000	22-45
HOWLAND WEST	Kit	28-50
HENELEC TEXAN	Built	35-00
HENELEC TEXAN	TRM300	25-95
NIKKO	TRM400	32-50
	SA500A	34-25
PIONEER	RA 211	32-65
ROTEL	RA31	41-15
	RA611	60-80
	RA810	75-75
	RA1210	92-50
SINCLAIR	3000	22-95
	3000	22-95
TANDBERG	TA300	66-10
TELETON	SAQ206B	22-50
	SAQ307	22-50
	GA202	28-50

STEREO RADIO TUNERS

(carr./packing 50p)		
AKAI	AT550	80-50
	AT580	94-50
AMSTRAD	3000	23-55
EAGLE	AA8	40-50
	TS152	29-45
HENELEC Stereo Kit		21-00
HENELEC Stereo Built		24-95
HOWLAND WEST	DA1000T	25-35
PIONEER	TX500A	48-75
ROTEL	R1222	32-65
	RT322	43-75
	RT622	65-40
SINCLAIR	2000	26-95
	3000	26-95
TELETON	GT202	30-50

DECODERS / SYNTHESIZERS

(carr. etc. 30p)		
DYNACO QUADRATOR		18-90
EAGLE	AA10	12-00
	AA26	18-35
TATE 1	Chassis	7-95
TATE 3		15-75
TATE 4		19-95
TATE 7	Boxed	25-95

MATCHED SPEAKER SYSTEMS

Recommended pairs 8 ohms (Carr. / Packing £1-50 pair)		
RANK DOMUS		
150	25-95 pr	
175	33-75 pr	
250	53-75 pr	
MARSDEN HALL		
110	22-50 pr	
150	27-50 pr	
200	24-50 pr	
DYNACO		
A10	43-00 pr.	
A25	69-00 pr.	
A35	79-00 pr.	
WHARFEDALE		
Denton 2	18 watt	27-20 pr.
Linton 2	20 watt	32-15 pr.
Melton II	25 watts	51-80 pr.
Triton	25 watt	40-80 pr.
LEAK		
150	18 watt	32-65 pr.
250	18 watt	44-30 pr.
CELESTION		
120	20 watt	37-80 pr.
COUNTY		
15	25 watt	33-60 pr.
15	30 watt	50-40 pr.
44	44 watt	81-20 pr.

UK's largest stockists for KEF Acoustic Research, Mordaunt Short & Cambridge Audio speakers. In stock and on demonstration. Phone for keenest price.

BATTERY CASSETTE RECORDERS

(carr. etc. 30p)		
Amerex	100	11-00
Wien	ET1008	11-00
Philips	EL3302	14-40
	N2203	16-60
	N2211	19-85
	M1101	13-90
Sonyo	M1102	12-95

STEREO MAGNETIC CARTRIDGES

(carr. etc. 15p)			
SHURE	M44G	4-20	
M3DM	M75/6/11B	6-75	
M44.7	M75 EDII	8-50	
M44E	M75 EJII	7-95	
M55E	M75GII	7-25	
GOLDRING			
G50	G800SE	10-00	
G800	G820	6-70	
G800H	G820E	10-00	
G800E	G820SE	13-35	
ADC			
Q36	10-70	Q30	5-90
Q32	8-70		
GRADO			
FTR	5-25	FTE	8-25
F3E	11-25	F2	18-75
EMPIRE		999TEX	14-95
		999REX	3-70
		999LUX	4-80
		999EXE	8-50
RONNETTE		SM500/J	4-60
		SM500/S	4-60
		SM500/E	6-95

STEREO COMPACTS

Complete with Speakers (c.p. £1-25)		
Fidelity	UA3	39-90
Sonyo	G2601KL	125-50
Sonyo	G2615N	71-50
Sonyo	GXT450KL	103-50
Sonyo	GXT4730KL	97-50
Philips	GF908	99-65
Philips	RH802	159-95
Philips	RF836	57-20
Philips	GF826	41-75
Philips	RH11/RH421	84-95
Philips	RF839	55-95
Philips	GF829	39-95
Philips	GF815	47-75
Philips	GF808	65-75
Philips	RH614/RH411	83-50
Philips	GF603	19-95

8 TRACK STEREO HOME UNITS

(with MW/FM stereo radio) 48-00

PORTABLE TV

BATTERY/MAINS (c.p. £1-00)

Elizabeth T9	9"	43-50
Crown 9TV	9"	46-50
Elizabethan T12	12"	43-95
Teleton TW12	12"	46-95
Sonyo 10T150	12"	49-95

CASSETTE PLAYER

FOR CAR - HOME AND AROUND

Actually the price far below the quality of the superb player. It is of beautiful quality both in sound and looks. Features wind, rewind, volume and tone controls. Speaker is very good indeed. Comes complete with earphone, batteries. Full guarantee. Optional adaptor to run off car or mains.

OUR PRICE
£7.25

CAR CIGAR LIGHTER
PLUG-IN ADAPTOR £1.95
MAINS ADAPTOR £1.95

MAINS ADAPTOR £1.95

DOLBY / NRU (carr./packing 30p)

Teleton	SNR100D	29-50
Philips	NE720	15-00
Teac	AN60/AN80/AN180	15-00

RECORD DECK PACKAGES

(carr./packing 75p) 1-lass cart. - rest with (HL)	SP25 III/800 or H	15-95
(M)	SP25 III/M756S	19-45
(HL)	AP16/G800	25-55
(M)	AP16/M756S	29-10
(HL)	GL75 P/C	33-50
(HL)	GL75 P/C G800	36-65
(HL)	GL75 P/C G800E	39-15
(HL)	MP60 (TRD1) G900	15-80
(HL)	HT70 (TPD1) G800	19-50
	*Pioneer PL12D	31-75
	*Thorens TD165	43-80
	Thorens TD16C	50-80
	BD200	43-60
RANK DOMUS	BA400	53-95

BATTERY / MAINS CASSETTE (carr. etc. 35p)

Wien	RT452	13-85
Amerex	AC101	12-00
Elizabethan	LZ315	12-25
Amerex	AC104	16-00
Philips	N2204	20-75
	N2205	29-50
PYE	9118	27-75
	9118	21-20
Hitachi	TRQ291	27-50
Sonyo	M2000G	23-25
	MR4010	28-95
	M4000G	49-90
BASF	CC9201	37-25
Hitachi	TRQ335	49-50

BATTERY / MAINS RADIO CASSETTE RECORDERS

(carr. etc. 30p)		
Amerex	ACR200	22-00
	ACR201	30-00
Elizabethan	LZ416	27-25
	LZ516	29-10
BASF	CC9301	50-75
Philips	RR322	28-75
	RR413	33-90
	RR712	48-30
Sonyo	M4141	39-50
	M2400W	31-50
	M2400FG	31-50
	M4400FC	62-50
	C850	47-95
Grundig	TR1940E	29-50
Hitachi	TRS1161	35-00
	KCT1210L	33-50

STEREO RECORDER DECKS

(carr./packing 50p)		
Cassette		
Philips	N2506	44-50
	N2510	£87-10
Pye	9145	44-50
Tandberg	TC300	112-00
Akai	CS30D	50-65
	CS38D Dolby	62-50
	GXC38D	65-15
	GXC40D	57-40
	GXC38D Dolby	81-45
	GXC46D Dolby	83-55
	GXC45D	92-85
TEAC	A250/A350-A450	62-50
Reel to Reel		
Akai	4000DS	62-50
Tandberg	3201X/341X	167-70
Large range Akai/Tandberg/Revox/Teac stocked.		

STEREO PHONES

(carr./packing 20p)			
AKAI			
ASE11	4-75	LOW COST	
ASE20	7-30	MD802	1-95
ASE22	8-25	MD806	3-75
DULCI		PIONEER	
SH650D	2-25	SE20A	5-90
SH850GX	3-95	SE30A	9-45
SH1200VS	5-25	SE50	6-25
AKG		SEL20	7-90
K60	8-25	SEL25	11-15
		SEL40	12-99
ROTEL		ACCESSORIES	
RH630	4-85	H1012/3B3	1-40
RH700	5-75	Junction Box	1-40
SENHEISER		JB3DE Din	
HD414	11-25	Junction Box	1-60
DD1	8-85	JB11D De Luxe	
ISODYN	15-00	Control Box	1-95
KOSS		0250 Phone	
K6	9-95	Switch	4-75
K6/LC	11-25	CONTROL BOXES	
K711	7-95	G1301	
KRD711	7-95	G1301	
HV1	17-50	(two phones)	2-62
K072B	12-45	G1305	
K0747	15-95	Controller	2-15
PR04AA	21-95	FF17 2-pairs	
PRO5LC	23-95	(Sliders)	6-25
HOWLAND WEST		Koss TA4	4-20
CIS200	2-75	TA5A	4-95
CIS250	5-25	T10AA	8-50
CIS1000	15-25	HW Mk.III	
CIS2000	15-25	Controller	6-90

YOU CAN PAY BY BARCLAYCARD OR ACCESS

For callers of by phone 01-402 4738

Easy credit terms for callers to 309 and 354-356

ALSO STOCKED AND DEMONSTRATED

Armstrong - Acoustic Research Cambridge Audio Leak - Lux Marantz - Quad - Revox - Sansul Tandberg - Sugen - Wharfedale Goodmans - Celestion - Grundig Kei - Teac - Bose - Sherwood Call or phone 01-402 4738 for best prices.

10% VAT to be added to all orders. Prices & description correct at time of press & O.E. All goods offered subject to stock availability.

Henry's

RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:-
9 am - 6 pm
6 days a week
All stores
open all day
Saturday

YATES ELECTRONICS (FLITWICK) LTD

DEPT. E.E., ELSTOW STORAGE DEPT.
KEMPSTON HARDWICK,
BEDFORD.

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m. 5 p.m.

PLEASE ADD 10% VAT

RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.
1W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7Ω-2.2MΩ	E24	1p-0.8p
1/2	10%	3.3MΩ-10MΩ	E12	1p-0.8p
1	2%	10Ω-1MΩ	E24	3.5p-3p
2	10%	1Ω-3.9Ω	E12	1p-0.8p
5	5%	4.7Ω-1MΩ	E12	1p-0.8p
10	10%	1Ω-10Ω	E12	6p-5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40, E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0-1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107	15p	AF126	20p	BF115	25p	OC42	12p	2N3707	12p
AC126	12p	AF139	32p	BF173	20p	OC44	12p	2N3708	10p
AC127	15p	AF178	32p	BF177	28p	OC45	12p	2N3709	11p
AC128	15p	AF180	40p	BF178	32p	OC70	12p	2N3710	11p
AC131	12p	AF181	40p	BF179	32p	OC71	12p	2N3711	11p
AC132	12p	BC107	12p	BF180	32p	OC72	12p	2N3819	32p
AC176	15p	BC108	12p	BF181	32p	OC21	12p	2N4062	12p
AC187	22p	BC109	12p	BF194	14p	OC82D	12p	2N4286	20p
AC188	22p	BC147	12p	BF195	14p	2N2646	60p	2N4289	20p
AD140	50p	BC148	12p	BF197	15p	2N2904	20p	40360	35p
AD149	45p	BC149	12p	BF200	32p	2N2926	10p	40361	35p
AD161	33p	BC157	14p	BFY50	20p	2N3054	58p	40362	40p
AD162	36p	BC158	14p	BFY51	20p	2N3055	60p	40408	40p
AF114	20p	BC159	14p	BFY52	20p	2N3702	13p	ZTX108	15p
AF115	20p	BC187	22p	BUY105	22p	2N3703	12p	ZTX300	15p
AF116	20p	BD131	75p	OC26	45p	2N3704	13p	ZTX302	20p
AF117	20p	BD132	75p	OC28	50p	2N3705	12p	ZTX500	15p
AF118	38p	BD133	75p	OC35	50p	2N3706	11p	ZXT503	20p

ZENER DIODES

400mW 5% 3.3V to 30V, 12p. WIRE WOUND POTS, 3W, 10, 25, 50Ω and decades to 100kΩ, 35p.

DIODES

RECTIFIER	1250V	1A	12p	SIGNAL	7p
BY127	1250V	1A	12p	OA85	7p
IN4001	50V	1A	7p	OA90	5p
IN4002	100V	1A	8p	OA91	5p
IN4004	400V	1A	8p	OA202	7p
IN4006	600V	1A	10p	IN4148	8p
IN4007	1000V	1A	10p	BA114	5p

BRUSHED ALUMINIUM PANELS

12in x 6in, 25p; 12in x 2 1/2in, 10p; 9in x 2in, 7p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K log, or lin. 40p.

DUAL GANG, 10K + 10K etc. log, or lin. 60p.

KNOB FOR ABOVE, 12p.

FRONT PANEL, 65p.

18 Gauge panel 12in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA10555 15p

VA10665 15p

VA1077 15p

RS3 41.35

THYRISTORS

2N5060 50V 0.8A 30p

2N5064 200V 0.8A 47p

106F 50V 4A 40p

106D 400V 4A 55p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V, 0.001μF, 0.015μF, 0.0022μF, 0.0033μF, 0.0047μF, 21p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7p, 0.33μF, 11p, 0.47μF, 13p.

160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 3p, 0.15μF, 4p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 2p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS

(μF/V) 1/63, 1-5/63, 2-2/63, 3-3/63, 4-7/63, 6-8/40, 6-8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6-3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6-3, 68/16, 100/4, 100/10, 100/25, 150/6-3, 150/16, 220/4, 220/6-3, 220/16, 330/4, 6p, 47/63, 100/40, 150/25, 220/25, 330/10, 470/6-3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4, 10p, 470/10, 680/6-3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16, 1500/6-3, 13p, 470/40, 680/25, 1000/16, 150/10, 220/6-3, 18p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300-6-3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF	35V	2.2μF	35V	22μF	16V	12p
0.22μF	35V	4.7μF	35V	33μF	10V	
0.47μF	35V	6.8μF	25V	47μF	6.3V	
1.0μF	35V	10μF	25V	100μF	3V	

VEROBOARD

2 1/2 x 3 1/2	0.1	0.15
2 1/2 x 5	22p	16p
2 1/2 x 5	24p	24p
3 1/2 x 3 1/2	24p	24p
3 1/2 x 5	27p	27p
17 x 2 1/2	75p	57p
17 x 3 1/2	100p	78p
17 x 5 (plain)	—	82p
17 x 3 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	42p
2 1/2 x 5 (plain)	—	12p
2 1/2 x 3 1/2 (plain)	—	11p
1in insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin 11g 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable, 22p/metre.

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF	64V	74p	2500μF	64V	80p	4500μF	16V	50p
2500μF	40V	74p	2800μF	100V	£2.60	4500μF	25V	£1.68
2500μF	50V	58p	3200μF	16V	50p	5000μF	50V	£1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	10p	0.047μF	13p	0.22μF	20p
0.022μF	12p	0.1μF	13p	0.47μF	22p

POLYSTYRENE CAPACITORS 150V 2 1/2p

10pF to 1,000pF E12 Series Values, 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs oxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £5.20. 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7400	18	16	14	13	7450	18	16	14	74121	43	40	38	36
7401	18	16	14	13	7451	18	16	14	74141	100	95	90	85
7402	18	16	14	13	7453	18	16	14	74150	140	140	135	130
7403	18	16	14	13	7454	18	16	14	74150	330	280	250	220
7404	20	18	16	14	7460	18	16	14	74151	110	100	95	89
7405	20	18	16	14	7470	30	28	25	74153	120	110	105	95
7406	50	45	40	35	7472	30	28	27	74154	200	180	170	160
7407	56	50	44	38	7473	40	38	36	74155	150	120	100	86
7408	36	30	27	23	7474	40	36	32	74156	130	120	100	96
7409	36	30	27	23	7475	55	52	50	74190	155	136	112	105
7410	18	16	14	13	7476	40	36	32	74190	195	190	185	180
7411	23	21	20	18	7480	100	95	90	74191	195	190	185	180
7412	36	30	27	23	7481	125	115	110	74192	200	190	180	164
7413	34	28	26	22	7482	100	96	90	74193	200	180	170	150
7416	45	43	39	34	7483	100	97	92	74196	200	190	180	170
7420	18	16	14	13	7484	120	115	110	74197	200	195	180	170
7421	36	30	27	23	7485	250	245	240					
7426	32	29	23	20	7486	45	42	37					
7430	20	18	16	14	7490	75	67	60					
7432	40	36	32	28	7491A	100	92	85					
7440	20	18	16	14	7492	75	70	65					
7441	80	75	70	65	7493	95	90	85					
7442	80	75	70	65	7494	95	90	85					
7443	125	120	115	115	7495	105	100	95					
7447	175	165	150	120	7496	100	95	90					
					74100	250	240	235					

LINEAR IC's

709	14 pin DIL	40p
741	8 pin DIL	38p
741	14 pin DIL	95p
723	14 pin DIL	85p
747	14 pin DIL	85p
748	8 pin DIL	45p
	DIL sockets	14 pin and 16 pin 16p

SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS.
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A 'Plastic Power' Driver Transistors Now Available. To meet demand, we have included a more powerful module in our well-established and proven range. These power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



SA35 35 watts RMS. Uses 7 transistors and 7 diodes Carr. paid. **£4-45**

A NEW ADDITION IS THE SA50 at £5-65

Carr. paid. A rugged, well built unit, capable of 50 watts R.M.S. out, with all the advantages of Saxon Amplifier design and quality. A guaranteed Saxon product.

SA100 makes an ideal unit in disco assemblies. A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10-90**

BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA 100.

Freq. response 15-40,000 Hz \pm 1dB
Distortion 0-2% at 1 kHz
Loads 4 to 16 ohms
Quiescent current 15 mA
Noise Better than -75 dB
Supply voltage SA35 25-45 volts
SA50/SA100 40-70 volts
Size 4 1/2" x 4" x 1" (SA100)
4" x 3" x 1" (SA35/SA50)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES

FOR THE SA 35, SA 50 & SA100 MODULES

PU45 Unstabilized supply for 2 SA35s £4-90
PU70 Unstabilized supply for one or two SA50 or SA100 power amps £7-75 carr. 40p
PS45 Stabilized module for two SA35's £3-50 carr. free
MT45 Transformer for above, heavy duty £2-85 carr. 20p
MT30 Transformer for unstabilized supply complete with rectifier diodes mounted £3-50 carr. 20p
PS70 Stabilized supply module for one or two SA50's or SA100's £4-90 carr. free
MT70 Transformer for PS70 £4-90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

Orders and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CRO 2HS.


Telephone 01-684 6385

Hours 9.30 a.m.-5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED

SAXON PA/MIXER CONTROL UNITS

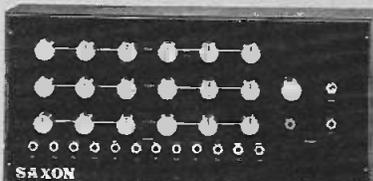Using grouped pairs of inputs and outputs (high low Z inputs) with bass, treble and volume on each pair, plus master control. These low-noise units will feed all makes of amplifiers. Ideal for clubs, discos, etc. Standard jack sockets. Compact design, strong metal cases. Guaranteed 3 years.



●M.4H

4 high Z, 4 low Z inputs, 4 sets of controls. Case 14" x 8" x 2 1/2" Carr. pd. **£18-50** V.A.T.

●M.6HL Case 18" x 8" x 2 1/2" 12 inputs (6 high Z, 6 low Z). Carr. pd. **£27-50** V.A.T.

Channel section module. Gain—16 x (24dB) Tone controls—18dB swing. Carr. pd. **£3-50** + V.A.T.

SAXON CONTROL UNITS

Mono (as shown)

For 9 volt battery operation. Spec. as for stereo, but less mic. input.

£6-50

Carr. 20p.

Stereo. Carr. 30p.

£15-80



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black face. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume. Microphone volume, bass, treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic input.)

120 WATT HEAVY DUTY MODULE



Rugged class A driver stage, this module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors. These are the modules where extra power is demanded.

Power output 120 watts into 8 ohms
Freq. response 20-20,000 Hz \pm 2dB
Input sensitivity 200 mV into 10K
Construction Fibreglass board
With supply 8" x 4" x 5"

Module & power supply **£18-95**
(Carr. 40p)

Low distortion parallel push-pull output stage.

160 watt version with power supply **£27-90**
(Carr. 50p)

SOUND AND LIGHT UNITS



Our popular 3 channel model handles up to 3KW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.

3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3KW lighting load. Smartly finished steel case. Carr. 30p.

£19-75

SINGLE CHANNEL UNIT


Operates from 5 to 100 watt amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p.

Carr. pd. **£8-90**

COMPLETE AMPLIFIERS

CSE 100. £34-90 carr. free

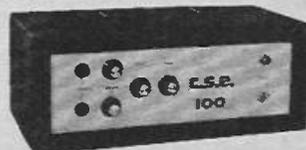This versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls.



SAXON 100 £48-50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5-95 carr. 30p. 15" 50 watt 8/15 ohm £14-50 carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11-50 carr. 40p.

500 Watt 3 colour Light Boxes Smart Rexine finish £15 carr. free.

A.K.G. MICROPHONES

D11 DHL IDEAL DISCO MIKE ONLY £9-45 (rtp £11-00).

Prices quoted do NOT include V.A.T. 10% must be added on to total value inc. carriage of order for V.A.T.

S.A.E. for special price list.

TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by regd. letter, please

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit - £24.95! (PLUS VAT)

The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 - so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

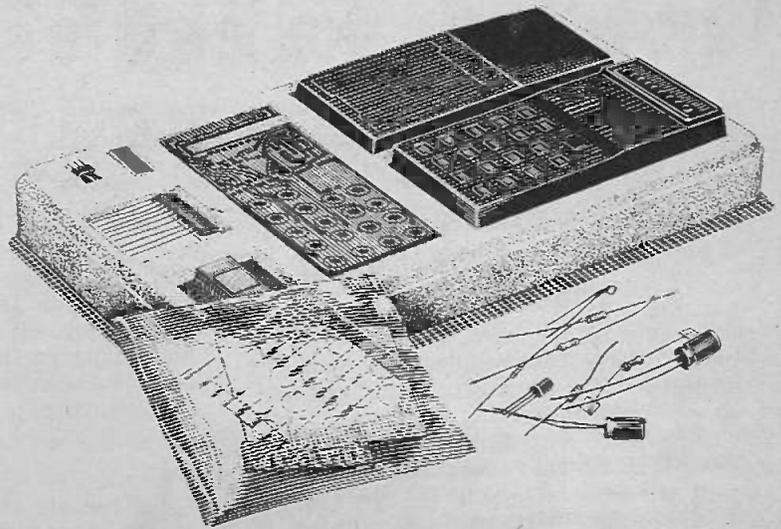1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book — free!

If you just use your Sinclair Cambridge for routine arithmetic — for shopping, conversions, percentages, accounting, tallying, and so on — then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

Logs Sines Cosines
Tangents Reciprocals nth roots
Currency Compound
conversion interest
and many others...

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Everyday Electronics, November 1973

Why only Sinclair can make you this offer

The reason's simple: only Sinclair — Europe's largest electronic calculator manufacturer — have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive — the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them — the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch — and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)

Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

EE 11.73

Please send me

Name

a Sinclair Cambridge calculator kit at
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready
built at £29.95 + £3.00 VAT
(Total: £32.95)

Address

*I enclose cheque for £ _____, made
out to Sinclair Radionics Ltd, and
crossed.

*Please debit my *Barclaycard/Access
account. Account number

*Delete as required.

PLEASE PRINT

everyday electronics

PROJECTS.
THEORY,...

WIRE-LESS

In the good old days when radio was known as wireless, it was commonplace to hear the question posed: why do they call it "wireless" when, as everyone knows, the set simply teems inside with wires? The knowledgeable would immediately explain that "wireless" was a contraction of wireless telephony (or telegraphy), and the significant thing was the absence of any interconnecting wires between the broadcasting station and the receiving set.

Wireless nowadays has a rather ancient ring about it and is seldom used in reference to radio. Yet strangely enough, there is every good reason for taking this word out of storage, dusting it down a bit and reintroducing it into the modern world of electronics. For it aptly describes some of the techniques now used in assembly work.

Yes, indeed, a perfectly accurate description of today's most popular methods for building electronic circuits would be "wireless construction." Wire has not, of course, been banished altogether as yet and interconnecting wires do still exist, often in great profusion. But most components in modern equipment are assembled on laminate plastics boards which embody either copper strips or patterns that serve the function of circuit wiring.

These wire-less constructional methods are described in this month's special supplement, as are certain other building techniques that do

depend upon the use of conventional wiring throughout. All these methods are suitable for home construction purposes, and beginners are recommended to try their hand at all in turn as the opportunity arises.

TUNE IN


Talking of radio, there can be few who have not at some time or another felt the urge to explore the short wave bands and to seek out broadcast and amateur stations operating in the four corners of the earth. This ethereal globe trotting becomes an even greater thrill when the vehicle used is a radio receiver built by one's own hands.

This need be no great or difficult task, even for the relatively inexperienced, as the constructional article in this issue will make quite clear.

ON THE SCENT

From a traditional field to one of the very latest developments in electronics. The Gas Alarm design is based upon a solid state sensor which represents an important breakthrough in technology.

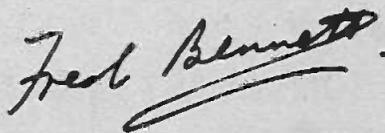Just another example of how EVERYDAY ELECTRONICS keeps the home constructor right up to date.



Our December issue will be published on Friday, November 16


EDITOR F. E. Bennett ● ASSISTANT EDITOR M. Kenward ● B. W. Terrell B.Sc.

ART EDITOR J. D. Pountney ● P. A. Loates ● K. A. Woodruff

ADVERTISEMENT MANAGER D. W. B. Tilleard

© IPC Magazines Limited 1973. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

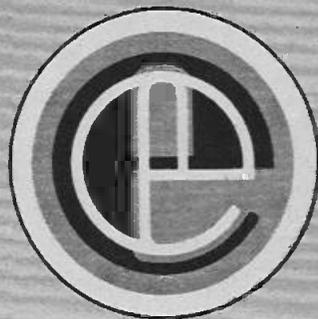All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



EASY TO CONSTRUCT SIMPLY EXPLAINED

VOL. 2 NO. 11

NOVEMBER 1973

CONSTRUCTIONAL PROJECTS

- 4 BAND T.R.F. RECEIVER** · Three short wavebands plus medium wave by F. G. Rayer 594
GAS ALARM Audible warning of concentrations of gas by M. Keene 610
THREE BY THREE GAME Simple game for two players by George Francis 616

GENERAL FEATURES

- EDITORIAL** 592
BRIGHT IDEAS Constructional hints from you 600
COMPETITION RESULTS 601
TEACH-IN '74 Lesson 2: Current flow, resistance and the diode by Phil Allcock 602
WHAT DO YOU KNOW? Current 606
SEMICONDUCTORS Six—Transistor Testing by J. B. Dance 607
HELP! Some of your question's answered 609
COUNTER INTELLIGENCE A retailer comments by Paul Young 614
DOWN TO EARTH Meter Sensitivity by George Hylton 615
PLEASE TAKE NOTE 621
TOOL KIT OFFER 622
RUMINATIONS by Sensor 625
SHOP TALK Buying components for projects by Mike Kenward 625
READERS LETTERS Your news and views 626

SPECIAL SUPPLEMENT YOUR GUIDE TO CONSTRUCTIONAL METHODS

Publisher's Annual Subscription Rate, including postage to any part of the world, £2.35. International Giro facilities Account No. 5122007. State reason for payment "message to payee". Address to Everyday Electronics, Subscription Department, Carlton House, Great Queen Street, London, WC2E 9PR. Binders for volumes 1 and 2 (state which) and indexes for volume 1 available for 97p and 11p respectively, including postage, from Binding Department, at the above address.

We are unable to supply back copies of *Everyday Electronics* or reprints of articles and cannot undertake to answer readers' letters requesting designs, modifications or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, both at the address shown opposite.



Special tool kit offer—see page 622.

EXPLORE THE AIR WAVES!

4 BAND T.R.F. RECEIVER



BY E.G. RAYER

For reception of "amateur" short wave transmissions as well as the normal medium wave

WHEN correctly used, a t.r.f. (tuned radio frequency) receiver is highly sensitive and is capable of long-distance reception. Its great advantage lies in its relative simplicity of construction, since there are no tuned circuits which have to be aligned, as with a "superhet" receiver. All tuning takes place at the radio frequency at which reception is wanted—it is in fact this which distinguishes any t.r.f. receiver from a superhet, as the latter has oscillator and intermediate frequency circuits which must be tuned to different frequencies.

Thus in its simplest form the t.r.f. receiver needs one tuning coil only for each waveband. This circuit employs Denco miniature plug-in coils, which fit a B9A holder.

The receiver to be described is primarily intended for short wave reception, but operates well over medium waves also. Any one of four coils may be inserted, giving the wave bands shown in Table 1.

The four coils will thus give continuous coverage from 550kHz to 38MHz.

CIRCUIT

The complete circuit diagram is shown in Fig. 1, and a few notes on this will help make clear the function of the various items.

Coil L1 is one of the four tuning coils, placed in the holder mentioned. Capacitor C3 is the

tuning capacitor, operated by a dual-speed ball drive, and frequencies can be marked directly on the scales. Components C2 and VR2 control regeneration in the f.e.t. detector TR1.

In use, VR2 is set to give a suitable drain potential, and regeneration is controlled mainly by C2. When regeneration is adjusted so that TR1 is nearly oscillating, the detector is highly sensitive to weak signals (more about this later).

Loading effects of the aerial influence regeneration and selectivity, especially on the higher frequencies, so it is worth while having optional aerial sockets—SK1 gives a direct connection to the aerial coupling winding of L1, while plugging the aerial into socket SK2 introduces the pre-set capacitor C1.

Audio signals are developed across the potentiometer VR1, which acts as volume control. The required audio level is taken off by VR1 slider, and reaches the pre-amplifier TR2. This stage is directly coupled to the integrated circuit audio amplifier which can provide 250mW power output. This arrangement has enough gain and output for loudspeaker reception of many stations. For weak short wave (s.w.) signals, or personal listening, headphones may be plugged into SK3. Resistors R7, R8 and R9

Table 1: Wavebands obtainable

Coil	Waveband	Frequency
2	Medium wave	550-1500kHz
3	Amateur and shipping	1.5-5.5kHz
4	Generally used short wave	5.0-20MHz
5	High frequency short wave	10-38MHz

Approximate cost
of components
including V.A.T.

£8:00 plus case

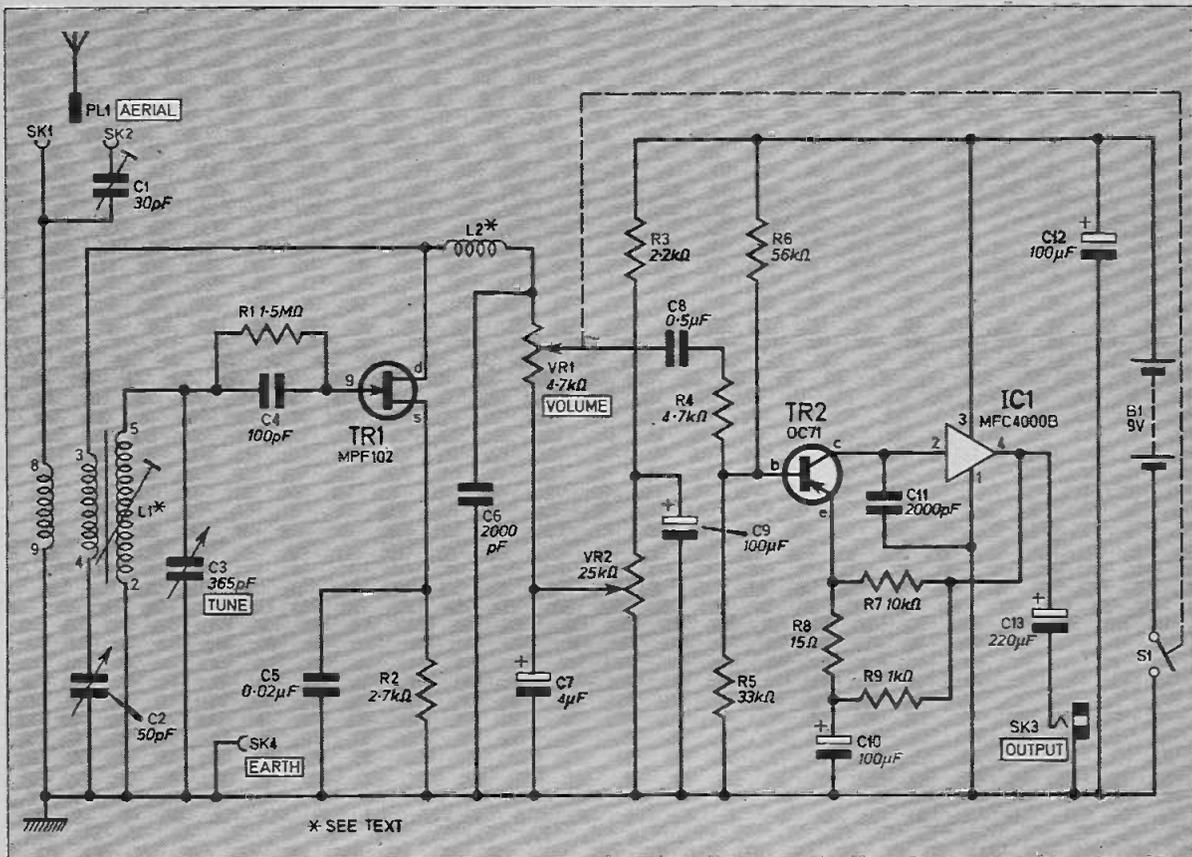


Fig. 1 Complete circuit diagram of the Four Band T.R.F. Receiver.

are feedback components which stabilise the whole audio section, including TR2.


Construction is in three main sections—the r.f. (radio frequency) circuit board containing the detector stage, the a.f. (audio frequency) board which consists of the audio amplifier, and the chassis and panel for the controls.

R. F. CIRCUIT

The board on which the r.f. section is mounted measures 75mm by 50mm, and is 0.15 inch plain matrix Veroboard. The components should be mounted exactly as in Fig. 2. First drill the holes for the 6BA bolts. Place the board in the chassis in the position shown in Fig. 4 and drill matching holes in the chassis. Fit two 12mm long bolts, with soldering tags locked on the underside of the board by means of nuts. Put an extra nut on each bolt. When the board is wired these bolts pass through the matching holes in the chassis, and further nuts on top of the chassis secure the board, and provide the electrical chassis return.

Mount the r.f. choke (L2), R1, C4, R2, C5 and C6 as in Fig. 2. Turn the board over, and

Fig. 2 (right). Layout and wiring of components mounted on the r.f. circuit board.

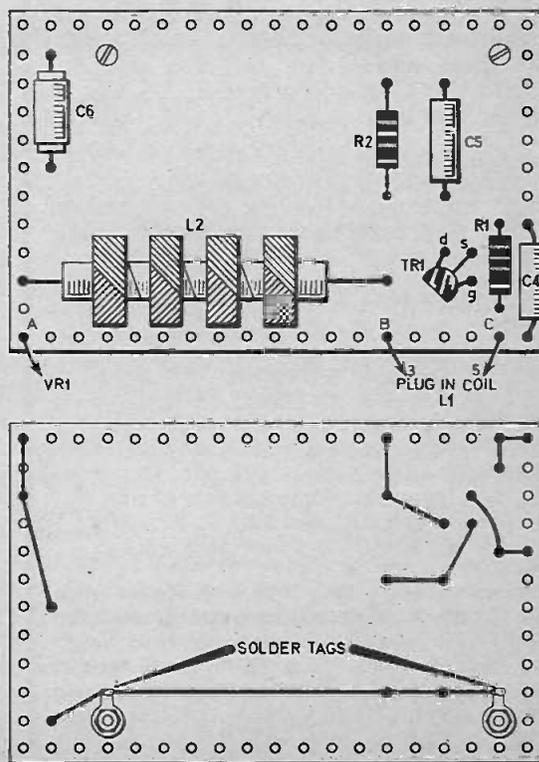

connect as shown for the underside wiring. A 20 s.w.g. tinned copper or similar wire is soldered between the tags for the metal chassis return points. In other places, the wire ends of the components are bent over and soldered as shown, and excess wire is then snipped off.

Later, connections will pass from the board to tags 3 and 5 of the coil holder, and to VR1 as indicated. This can be arranged by fitting three Veropins, or by leaving short projecting wires to which longer leads can be soldered.

Components

Resistors	R5	33k Ω	
R1	1.5M Ω	R6	56k Ω
R2	2.7k Ω	R7	10k Ω
R3	2.2k Ω	R8	15 Ω
R4	4.7k Ω	R9	1k Ω
All $\pm 5\%$ $\frac{1}{4}$ W carbon			

Capacitors	
C1	30pF beehive trimmer
C2	50pF variable, Jackson C804
C3	365pF variable, Jackson 00, single gang
C4	100pF
C5	0.02 μ F
C6	2000pF
C7	4 μ F elect. 9V
C8	0.5 μ F
C9	100 μ F elect. 10V
C10	100 μ F elect. 10V
C11	2000pF
C12	100 μ F elect. 10V
C13	220 μ F elect. 10V

SEE
**SHOP
TALK**

Potentiometers	
VR1	4.7k Ω log, with switch
VR2	25k Ω lin

Semiconductors	
TR1	MPF 102 <i>n</i> channel f.e.t.
TR2	OC71 germanium <i>p.n.p.</i>
IC1	MFC 4000B audio amplifier

Inductors	
L1	Denco "Green" miniature plug-in coils: Range 2 550-1500kHz Range 3 1.5-5.5MHz Range 4 5.0-20MHz Range 5 10-38MHz
L2	Denco RFC5 radio frequency choke

Miscellaneous
SK1, 2, 4 insulated single sockets (3 off)
PL1 plug to suit SK1 and SK2
B1 9V PP9 battery and connecting clips
SK3 Jack socket
Veroboard 78 x 51mm, 0.15 inch matrix plain type (2 off), insulated mounting tag, Jackson type 6/36 No. 4103/A drive and dial, H. L. Smith type W case (203 x 152 x 152mm) and type K chassis (178 x 146 x 146mm). Universal chassis flanged runner 76mm x 51mm, control knobs (3 off), earth tags, wire, 4BA fixings, etc.

The field effect transistor TR1 has drain, source and gate leads. If the transistor is placed as shown for the top of the board in Fig. 2, the wires can be brought out at the positions d, s and g, as marked for the underside of the board. As these wires are short, provide connections from R1, C5 and L2 for them, as in Fig. 2.


In the actual receiver, a "three lead" transistor holder was used but this was mainly so that alternative transistors could be tried easily. If a holder is fitted, connect its tags correctly, and afterwards insert the correct wires of TR1 into the sockets. If a holder is not used, solder these points directly to the leads using a heat shunt, but do not keep the iron in contact with the joint for more than a second or two, to avoid overheating.


AUDIO BOARD

The board housing the "audio" components is shown in Fig. 3. Wiring of this board is along similar lines to that already described. The electrolytic capacitors C9, C10, C12 and C13 have positive and negative ends, and must be fitted in the polarity shown.

Underneath, keep all connections close against the board, and put insulated sleeving on any leads which run near or cross other leads.

Fig. 3 Audio board layout and wiring.

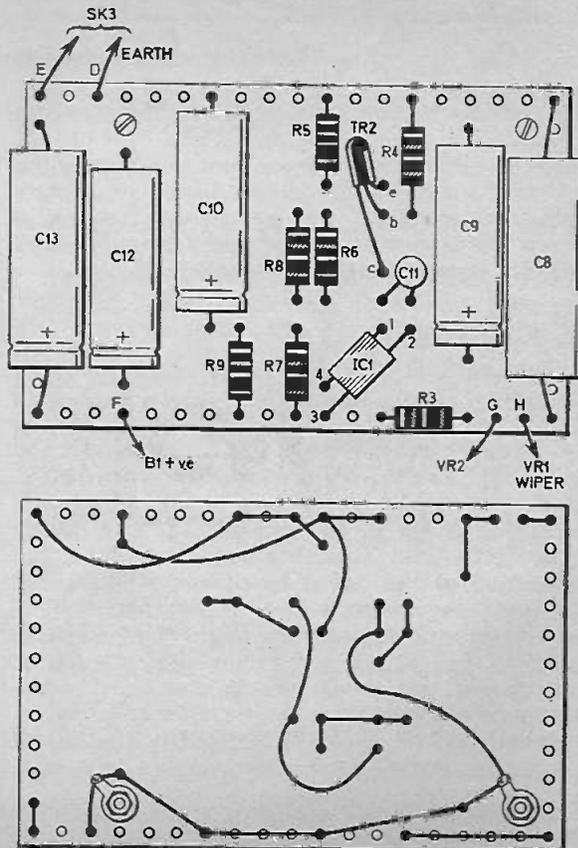

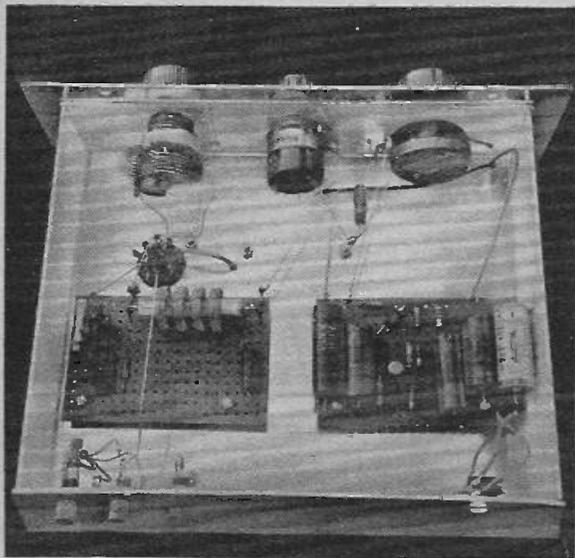

When fitting TR2, place emitter, base and collector leads in the positions e, b and c. The collector is marked by a spot on the case. The audio integrated circuit IC1 has two long and two short tags, and fits as in Fig. 3. These joints should be soldered without prolonged heating and preferably a heat shunt should be clipped on the leads while soldering.

Fit Veropins or projecting wires for the connections to VR1, VR2, B1 positive, and SK3, as before.

CHASSIS PREPARATION

Drill or punch holes for VR1, VR2 and C2 in the chassis, as in Fig. 4. Place the front panel and chassis together, marking through these holes so that the front panel can be drilled to match. Note that with the cabinet listed the panel must project 13mm lower than the bottom edge of the chassis. Also drill holes for the output jack (SK3), etc.

The coil holder is bolted as in Fig. 5, with its sockets located as in Fig. 4.

Capacitor C3 is mounted on a bracket, so that the ball-drive can be accommodated behind the panel. (This bracket can be cut from a 75mm x 50mm flanged "universal chassis" member.) The capacitor spindle passes through a clearance hole, and the capacitor is secured with three 4BA bolts. These bolts must be short, or washers must be put under their heads, so that they do not project more than the thickness of the capacitor frame. If they are longer than this, they may short-circuit or damage the capacitor.

The panel is fixed by VR1, VR2 and C2. Capacitor C3 is then temporarily moved forwards and the drilling position for its spindle marked on the panel. Drill through from behind, then use a punch or hole-cutter to obtain a 19mm

diameter hole. The slow-motion drive is fitted with the countersunk bolts provided with it. A template is also provided, and this is located on the panel, and the four corner holes for the dial are marked and drilled.

Check that the capacitor and drive line up correctly before tightening the bolts. Adjustment should not be necessary, but if it is, the holes in the capacitor mounting bracket can be enlarged or elongated with a small file, to permit horizontal and vertical adjustment of the capacitor, to match the drive.

The drive automatically provides two ratios. Some users may prefer the higher ratio to operate continuously. If so, place the control knob spindle in a vice, and cut off the small projecting stop which will be seen.

BOARD MOUNTING

If leads are kept near the boards, there should be no chance of shorts to the metal chassis, as the boards stand a little clear of this. If such shorts appear possible, due to large joints, the mounting bolts can be made longer, to give more clearance, or pieces of card can be cut to fit between the boards and chassis.

One top nut of the r.f. board also secures an insulated tag, Fig. 5. The centre pin of C1 is soldered to this, and insulated wires pass down to sockets SK1 and SK2. Socket SK4 (earth) is connected to the metal chassis, but C1 must of course be completely insulated from the metal.

OTHER WIRING

Complete the wiring as in Fig. 4. Leads from the r.f. board go to tags 3 and 5 of the coil holder, tags 2 and 9 are earthed to the chassis, tag 4 goes to the fixed plates of C2, and tag 8 to SK1. An insulated lead from tag 5 passes through the chassis to C3, Fig. 5.

Earth C7 negative at a bolt as shown in Fig. 4. Connect VR1 and VR2 as shown. Run a thin black flexile lead from S1 through the chassis, and solder on a negative battery clip. A red lead runs from B1 positive on the a.f. board, to a positive clip.

If the output jack is insulated, it does not matter which tags are used for the two leads. But if it provides a metal contact between chassis and plug sleeve, this lead must be that running to the earth line on the circuit board, Fig. 3, or the output will be shorted.

CABINET

The metal case measures 203 x 152 x 152mm (8 x 6 x 6 inches) and for easy coil changing it is necessary to arrange for an opening top. This can be done by marking a section 152 x 102mm in the case top, which is then cut out. A saw can be started by drilling a row of small holes (not larger than 2mm) close together. A file is used to smooth the cut edges afterwards.

4 BAND T.R.F. RECEIVER

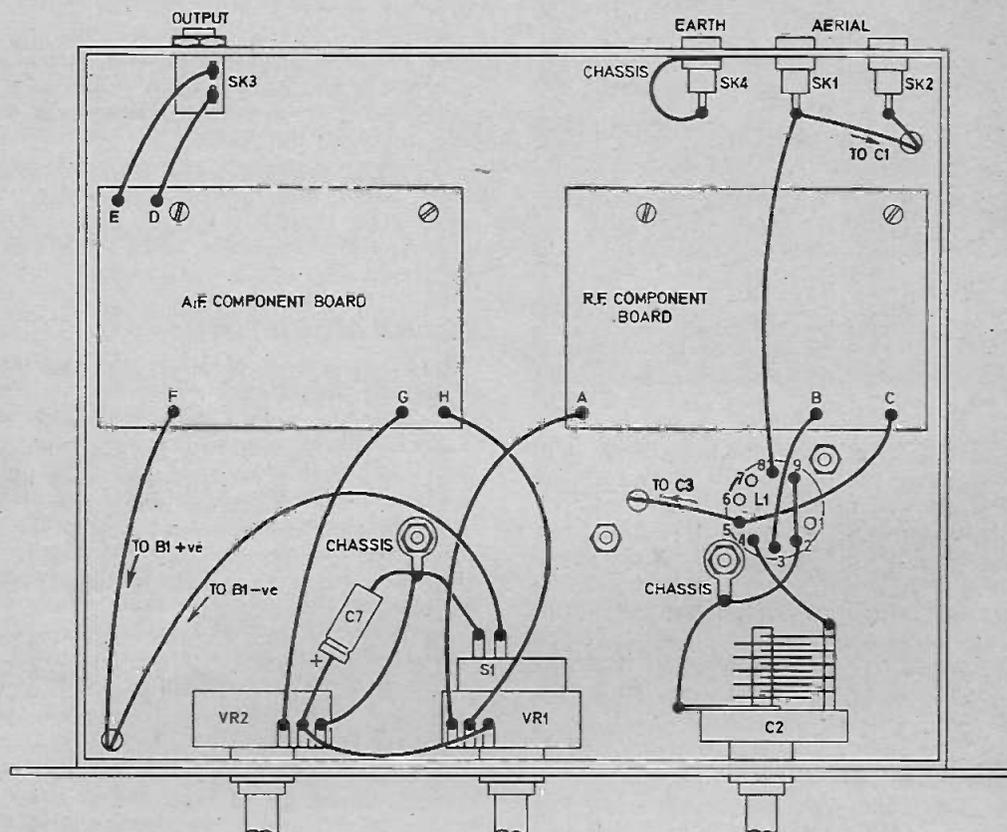


Fig. 4. Layout and wiring of parts mounted on the underside of the chassis.

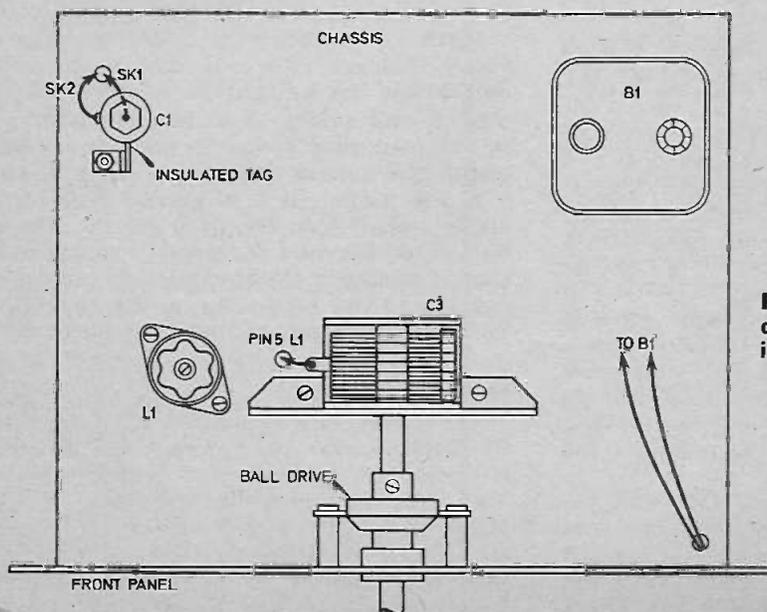


Fig. 5. Showing the positioning of the components and mounting for C3 on top of the chassis.

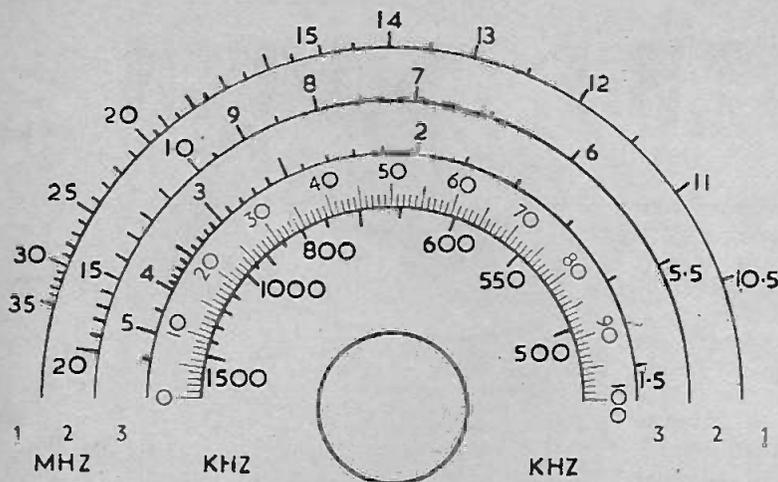


Fig. 6 Markings for the various ranges on the tuning dial this is shown full size and may be transferred directly to the scale.

The cut-out piece is hinged by a 152mm cabinet hinge at the back, or by cutting 152mm from a long plastic or metal hinge of this type available at carpentry equipment shops. A strip of aluminium about 180mm long and 25mm wide is bolted inside the top, at the front, for the lid to rest on when shut. A small terminal head was fitted to the lid here to enable it to be raised.

An alternative, with the case listed, is to drill out the six aluminium rivets which hold the top. This part can then be hinged on two 6BA bolts, passed through the rivet holes each side near the back. Another possibility would be to cut about 150x100mm from the cabinet back, so that the coils can be inserted from here.

A 25mm diameter hole was punched opposite the output jack. Two similar holes were punched near the earth and aerial socket position, and the metal between them cut away, so that aerial and earth plugs can be inserted.

A PP9 9 volt battery stands on the chassis to the right of C3.

LOUDSPEAKER/PHONES

A 16 ohm speaker is most suitable, but a 25 ohm unit can be employed with almost similar results. For best volume, a 90mm (3½ inch) or larger diameter speaker is recommended. It should be fitted in a cabinet or attached to a baffle.

When using headphones, maximum output is not required, and it is in order to have a headset of over 16 ohms impedance. Phones of 50 ohms or 100 ohms will work well, and phones of up to 500 ohms are satisfactory, though with these, and higher impedances up to 2,000 ohms, there is naturally a loss of volume.

TUNING DIAL

The drive has a scale marked 0-100, and three blank scales. These can be marked for ranges 1, 2 and 3, as shown. If range 4 (medium waves)

is also wanted, this is best marked on the inside of the 0-100 scale (Fig. 6).

Place the cursor line at 100 with C3 fully closed, and lock it here. The actual band coverage obtained with any coil depends on the position of the coil core. If agreement with the scales shown is to be obtained, it is necessary to adjust each core at some known frequency, preferably fairly near the low frequency end of the band.

As examples, adjust range 3 core for reception of a broadcast near 1.5MHz (1500kHz) while the cursor is set for this reading, and Range 2 core for reception of 7MHz amateurs while the cursor is at 7.0 to 7.1MHz.

The scales are given for guidance, and there is no need that these exact ranges are obtained. No loss of efficiency arises from having the cores in different positions, and stations can be logged against the 0-100 scale, if required. Subsequently, each core is locked with a 6BA nut, to maintain readings.

AERIAL AND EARTH

Many signals can be expected even with a short indoor aerial, but an outdoor aerial will give better volume and longer range. Even with a highly expensive commercial receiver, long distance short wave reception requires the use of a good aerial, and a short wave listener will give some attention to this item.

Some 8 to 18 metres or so of wire, supported by insulators, and as high and clear of walls and earthed objects as possible, can be expected to give good results. For particular purposes, such as long distance reception of weak 1.8MHz amateurs, a greater length would be put up, if circumstances allowed.

Again, many signals can be received at adequate speaker volume with no earth. But an earth connection, to a metal spike or other earthed object, can give a considerable increase in signal strength, and this may be very noticeable with frequencies from about 1.5 to 4MHz.

USING THE RECEIVER

For maximum sensitivity and selectivity (the ability to receive very weak signals, and choose one transmission from others on nearby frequencies) regeneration must be correctly adjusted. Results then compare with those obtained with a superhet.

With VR1 set at about half way (or as volume requires) close C2 slightly and slowly rotate VR2 until whistles are heard when tuning through signals, C2 should then be backed off very slightly so that oscillation almost rises.

To receive the usual a.m. broadcasts on medium or short waves, TR1 is kept just below the oscillation point, in this way. For the reception of c.w. morse, it is necessary to advance regeneration a little, so that an audible heterodyne note is produced, the pitch being adjusted by tuning.


The circuit will also receive single sideband, suppressed carrier (s.s.b.) signals, as largely used by amateurs. To do this, it is necessary to advance regeneration until oscillation provides the local carrier (removed at transmission) and to carefully adjust tuning until the speech is resolved. As strong c.w. or s.s.b. will tend to block the receiver, it may be necessary to transfer the aerial to SK2, or to open C1 if SK2 is in use, to weaken signals.

If VR2 is in the wrong position, the control of regeneration by C2 will be erratic and abrupt, and a smooth build-up of sensitivity will be impossible. So experiment with the setting of VR2, if necessary.

Abrupt loss of regeneration on some frequencies may be caused by resonant or loading effects from the aerial, and are avoided by plugging into SK2. Generally, SK1 is suitable for a short aerial, and SK2 for a long aerial.

Regeneration depends somewhat on the positions of the coil cores, as will be found if these are moved away from normal settings.

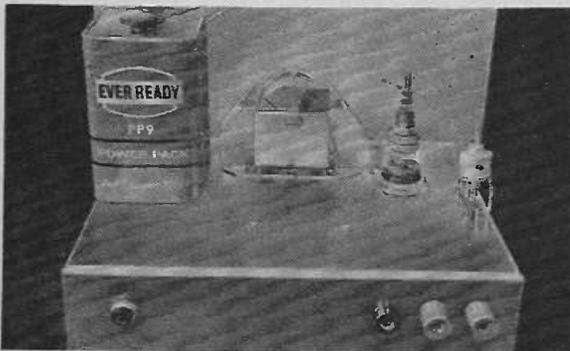From these details it should not be expected that using the receiver will be exceptionally tricky. However, the results which are obtained with any t.r.f. circuit depend so greatly on regeneration that it must be understood that the adjustment of C2 and VR2 is very important.



BRIGHT IDEAS

Readers' Bright Ideas; any idea that is published will be awarded payment according to its merit. The ideas have not been proved by us.

I would like to submit, for possible publication in your Bright Ideas column a cheap way of mounting l.d.r.s, such as the ORP12, when used remote from a unit. First, obtain a DIN in-line plug (or socket) and remove the metal plug section. Leads are then soldered to the l.d.r. which is pushed into the DIN plastic case until it is flush with the outside of the case. To avoid a possible short circuit within the case it is a good idea to cover the bare connections with suitable sleeving.

J. R. Seymour,
London.

I have found a good method of fitting small to medium size speakers on projects without glueing, so that they may be removed later if necessary. Blu-Tack, a putty-like adhesive sold in small slabs by Bostik is used. A small piece is worked into a thin "cord" by rolling and stretching, this is lightly placed around the edge (not on the cone) of the speaker, on the front where the glue would normally go. The speaker is placed on the desired spot and pressed down hard around the edges. This method provides quite a firm fix, especially if the speaker is fitted to Perspex or a smooth surface.

Blu-Tack can also be used to fix Veroboard into cases, provided the surface it is fixed onto is plastic, as metal is likely to short-circuit the connections underneath the board. This is easier than using screws as no fixing holes are drilled in the board.

M. Batter,
Shoreham-by-Sea.

If, like mine, other readers' hands shake when trying to paint straight, clean printed circuit outlines with enamel and a moulting brush or even the special, expensive pens, they might like to try covering the p.c. board, after polishing, with white p.v.c. tape, ensuring no trapped air, and transferring the pattern to tape through carbon paper as usual.

Then, with a sharp pointed craft knife, cut around the outline using a straight edge if needed. With point of knife, remove the tape from copper areas to be dissolved and agitate the board in ferric chloride. Rinse and peel off the remaining tape. The white adhesive tape takes and displays the transferred outline more clearly than copper and excludes the etchant perfectly. Also, there is no waiting for paint to dry or risk of blots, smudges, missed areas, loose bristles, etc.

M. E. Mullis,
Dunmow.


SOLDERING COMPETITION...




RESULTS



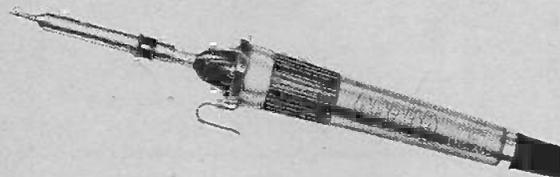The first prize—a complete Viscount Audio System from RTVC.



Runner-Up prizes from Antex and Adcola

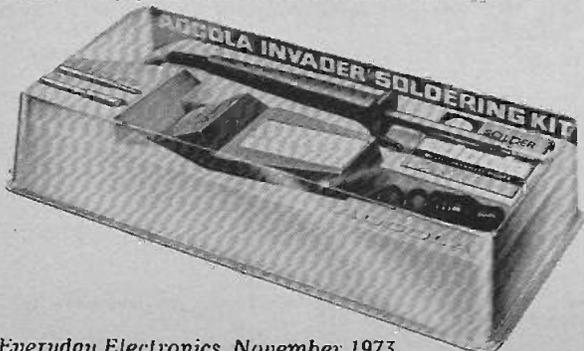

In our June issue, we offered a whole host of prizes for a competition based on soldering; readers were invited to place eight factors into the order of importance they contributed to the perfect soldered joint. Having considered all the entries, the judges decided that the best received were a small number which gave the following order: 1st-A; 2nd-C; 3rd-E; 4th-J; 5th-K; 6th-L; 7th-D; 8th-B.

In accordance with the rules, these tying competitors took part in a postal eliminating contest, from which **Mr. David Riley** of Orpington, Kent emerged as the first prize-winner. His award is that super **Viscount Audio System**, donated by Radio and TV components (Acton) Ltd.


These are the names of the 100 runners-up, who have won items of soldering equipment donated by Adcola Products Ltd, Antex (Electronics) Ltd and Multicore Solders Ltd.

100 Runner-Up Prize Winners Everyday Electronics Soldering Competition

L. Addison, London N.22; Peter Alexander, Swansea; A. C. Archard, Chippenham; R. Arendse, Harrow; M. J. Avery, Horsforth; Paul Beeson, Radlett; J. W. Berry, Bury St. Edmunds; M. J. Berry, Newmarket; T. Blackwell, Kenilworth; Richard Bowen, Shipley; R. C. Brackin, West Wickham; P. L. Bryan, Coventry; C. H. Burford, Eastbourne; John Carrington, Kirkby; C. M. Christison, Whauphill; Martin Cook, Dorchester; Martin Cooper, Teesside; Dave Copestake, Walsall; Gordon Coppock, Cranleigh; G. Crook, Bristol; W. J. Cuthbert, Hastings; R. B. Dale, Thirsk; R. S. Dewar, Keighley; Paul Dootson, Bolton; M. Dorsett, Bangor; Jeffrey Dunstone, Weston-Super-Mare; J. S. Ewins, London W.3; T. J. Felmingham, Wantage; R. Fletcher, London N.3; D. S. Franklin, High Wycombe; B. Fraser, Barrow-in-Furness; A. W. French, Brigg; W. R. Fulton, Middlesbrough; Jim Fulton, Dromore; K. Garten, London N.21; M. Georgiou, London N.22; M. Greest, Thornton Heath; David Hamilton, Slough; F. Higginson, Belfast; W. Hitchon, Blackpool; Anthony Hodkin, Sheffield; D. G. Hughes, Clayton-le-Moors; A. Humpston, Derby; Kevin King, Tadcaster; Peter Lamswood, Luton; G. Luckhurst, Erith; G. N. McCorkell, Londonderry; Gordon McKay, Eccles; William McLachlan, Greenock; Kevin Maddy, Halifax; I. Marsh, Maidstone; K. Martin, Luton; L. B. Mayger, Maidstone; H. Miles, Houghton-le-Spring; E. Milton, Aberdeenshire; W. Moran, Londonderry; L. R. Parker, Upton-by-Chester; C. Payne, Peterborough; N. H. Peebles, Haydock; Vercel Pinnock, Huddersfield; K. G. Prince, Bolton; Kevin Richards, Rainham; D. H. Robinson, Fiskerton; William Roots, Gillingham; B. P. Rumble, Bristol; Andrew Sasse, Leigh; C. Self, North Walsham; David Silvester, Dartford; Derek Smart, Motherwell; E. Smith, Poole; John Smith, Sheffield, P. A. Stonebanks, Newcastle upon Tyne; J. R. Stone, Buxton; A. Strickland, Ruislip; J. Sundberg, London E.6; P. R. Taylor, Benfleet; Kevin Terry, Scarborough; Ian Thomas, Theydon Bois; P. Thompson, Haywards Heath; D. A. Thornley, Dukinfield; Philip Thursfield, Newport; Ian Tindale, St. Albans; R. P. Tingle, Kettering; M. Turner, Lakenheath; John Tyler, Malvern; A. Vivian, Bournemouth; C. Wade, Leeds; G. Walker, Glasgow; K. Walker, Runcorn; Glyn Wall, Lydney; Geoffrey E. Walsh, Reading; Robert Wardle, Coalville; Cliff Watson, London S.W.1; Keith White, Birmingham; Ian Wilkie, Edinburgh; D. Wilkinson, Redditch; Jonathan Williams, Ruislip; N. E. Williams, Llandudno Junction; C. Willis, Benfleet; R. Brendon-Wynne, Birmingham.

TEACH-IN '74

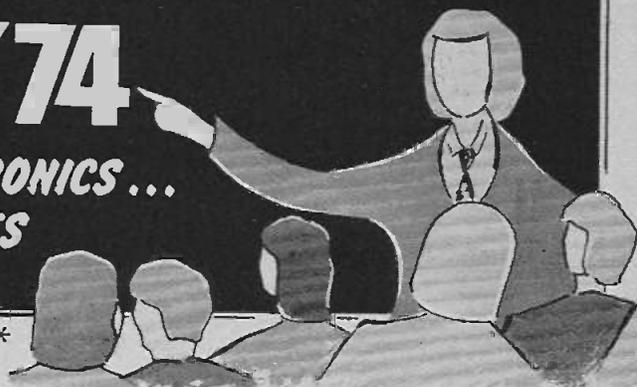FOR BEGINNERS IN ELECTRONICS...
THEORY AND EXPERIMENTS



TUTOR: PHIL ALLCOCK*

LESSON 2 Current Flow, Resistance and the Diode

LAST month, in the first lesson of this series, some basic ideas about current flow and series circuits were covered. Current is known to be simply a movement of electrons and each electron conveys a fixed amount of charge wherever it goes. This charge "on the move" is a very important concept which we shall refer to later on in the series but at this point it is necessary to mention a slight anomaly relating to current.

CONVENTIONAL CURRENT

Early scientists assumed that electrical current flow was from the positive (+) terminal of the battery, through the circuit components and then back to the negative (-) terminal of the same battery. This concept remains with us today. It is used in the majority of modern textbooks relating to the theory of circuits and has come to be known as conventional current.

The actual physical process is however a movement of electrons through the circuit in the opposite direction to the conventional current flow as shown in Fig. 2.1. The fact that the wrong direction was assumed by these early scientists need not cause any trouble. The electronic charge is negative and the movement of this charge, in one direction, is equivalent to the movement of a similar amount of positive charge in the opposite direction.

Hence our so called conventional current is simply a representation of the circuit behaviour using positive charge, and since like charges repel, this positive charge tends to move away from the positive battery terminal and proceed towards the negative terminal just like the assumed conventional current flow. When it is necessary to distinguish between conventional and electron flow the text will be specific, otherwise conventional flow should be assumed.

VOLTAGE DIFFERENCE

It is usually convenient to refer to the voltage difference between two points in a circuit, as this can be readily measured, rather than refer to the absolute voltage at a particular point. Such voltage differences can be positive, negative or zero and their measurement is similar to that normally used for specifying the heights of particular points on the surface of the earth. Sea level is usually taken as the arbitrary reference and is given a height of zero. Consequently the mountain in Figure 2.2 has a height of +3,000 feet whereas the sea bed has a height of -1,000 feet. The negative sign simply means that the sea bed is below the reference point.

Using the same ideas, in Fig. 2.1 the voltage of any point can be measured with respect to

Fig. 2.1. Conventional current and electron flow.


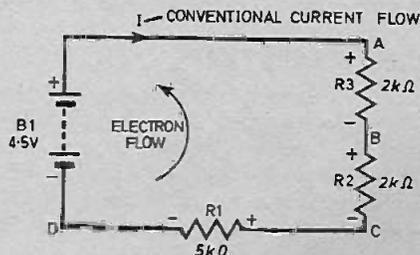


Fig. 2.2. Height with respect to the sea level reference.

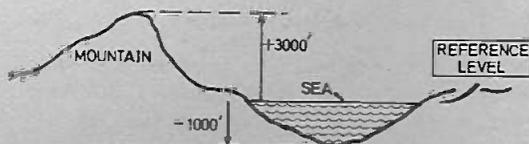

* North Staffordshire Polytechnic (Any communications arising from the Teach-In '74 series must be addressed to Everyday Electronics, Fleetway House, Farringdon Street, London E.C.4)

any other chosen reference point. If we choose point *D* as the reference and measure the voltage at points *A*, *B* and *C* the results will all be positive values.

REFERENCE

It is sometimes necessary to indicate the reference point in symbolic form and this can be done by writing, say, V_{AD} which means the voltage at point *A* with respect to *D*. Similarly V_{BC} is the voltage of point *B* with respect to *C*. The use of subscripts is very common in electronics, particularly when dealing with the voltages and currents in semiconducting devices such as transistors. Recalling what has been said above the reader should note that $V_{AB} = -V_{BA}$ and $V_{AC} = V_{AB} + V_{BC}$, etc. An example using Fig. 2.1 should make this all quite clear.

The total series resistance is $R_T = 2k\Omega + 2k\Omega + 5k\Omega = 9k\Omega$.

$$\text{Hence the current } I = \frac{4.5}{9.0} = 0.5 \text{ mA.} \left(\begin{array}{l} \text{volts} \\ \text{kilohms} \end{array} \right) \text{ milliamps}$$

$$\text{Thus } V_{AB} = 2 \times 0.5 = 1 \text{ volt (volts = kilohms} \times \text{milliamps)}$$

$$V_{BC} = 2 \times 0.5 = 1 \text{ volt}$$

$$V_{CD} = 5 \times 0.5 = 2.5 \text{ volts}$$

$$V_{DB} = -(7 \times 0.5) = -3.5 \text{ volts}$$

$$\text{and } V_{AB} + V_{BC} + V_{CD} = V_{AD} = \text{battery voltage} = 4.5\text{V.}$$

Notice that for resistors, the terminal at which a positive value of conventional current enters always has a positive voltage with respect to the other terminal, whereas for the battery the reverse is true. In the case of the battery conventional current leaves the battery at the positive terminal and returns via the negative terminal.

PARALLEL RESISTORS

Sometimes it is necessary to use resistors in parallel as shown in Fig. 2.3. The parallel connection differs from the series arrangement in that each component may now carry a different current. Since the current flowing into point *A*, must at all times be equal to the current flowing away, we can write $I_{\text{total}} = I_1 + I_2$.

Since the voltage across each resistor is the same, namely $V_{AB} = 9$ volts, the total current is given by

$$I_{\text{total}} = \frac{9}{6.0} + \frac{9}{3.0} \text{ mA} = (1.5 + 3.0) \text{ mA} = 4.5 \text{ mA.}$$

As far as the battery is concerned the parallel combination of these two resistors behaves as though it was a single resistor of effective value given by

$$R_{\text{effective}} = \frac{9.0 \text{ (V)}}{I_{\text{total}}} = \frac{9.0 \text{ (V)}}{4.5 \text{ (mA)}} = 2k\Omega.$$

In general the effective value of two parallel resistors R_1 , R_2 is given by

$$R_{\text{effective}} = \frac{R_1 \times R_2}{R_1 + R_2}$$

If more than two resistors are connected in parallel the effective value can be calculated from the formula

$$R_{\text{effective}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

MIXED SERIES/PARALLEL

To cover all possibilities it is necessary to study the circuit shown in Fig. 2.4 in which three resistors are arranged in a mixed series-parallel arrangement. Resistors R_2 and R_3 are in parallel with each other whilst the combination is in series with R_1 and the battery. If we replace R_2 and R_3 by their effective parallel resistance value the circuit becomes a simple "two-resistor" series circuit as indicated in Fig. 2.4. If the currents in the three original resistors are called I_1 , I_2 and I_3 it is possible to write the following equations using the ideas already covered:—

$$I_{\text{total}} = I_1 = I_2 + I_3$$

$$V_{AB} = I_1 R_1$$

$$V_{BC} = I_2 R_2 = I_3 R_3 = I_1 R_{\text{effective}}$$

$$V_{AB} + V_{BC} = 4.5 \text{ volts.}$$

It is not necessary to learn these particular equations by heart. What is important however is to follow the basic principles used in their derivation so that each circuit encountered can be studied and calculations made where this is necessary.

Series or parallel arrangements of resistors can be used to give a particular resistance value that is not otherwise hand, or to give a higher effective power rating. This is covered later.

Fig. 2.3. Resistors wired in parallel.


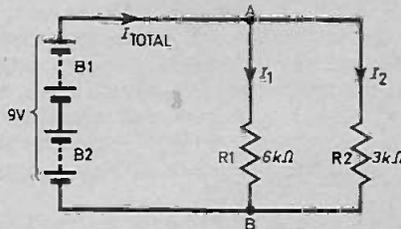


Fig. 2.4. A series parallel combination of resistors.

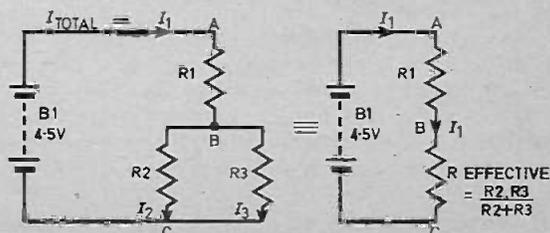

VARIABLE RESISTORS AND POTENTIOMETERS

Use has already been made of the 100 ohm and 5 kilohm potentiometers on the Tutor Board and most readers will have realised, from last month's experiments, that such a component is simply a resistance element with a moveable tapping point. The resistance between the outer tags is that of the whole element whilst the resistance between the sliding contact and either end varies with the slider position.

In the Tutor Board system the potentiometers are operated by rotating a spindle which moves the sliding contact over approximately $\frac{3}{4}$ of a complete turn. When connected so that only the slider and one end are in use the device is simply a variable resistor, covering the resistance range from zero to a maximum equal to the potentiometer value, say 5 kilohms.

In later experiments these components will be used as potentiometers for deriving a (variable) fraction of a given voltage applied across the whole resistance element. This is illustrated in Fig. 2.5 where the control varies the output voltage difference from zero to 4.5V if negligible current is taken from the output terminals.

POWER, ENERGY AND HEAT

When current flows in a resistor energy is dissipated. A similar situation occurs when someone pushes a load up an incline. The source of the electrical energy is the battery and the energy lost is expended as heat, produced in the resistor. The situation is most easily explained by referring to Fig. 2.6.

The flow of current I in resistor R_1 involves the expenditure of energy at a rate of $V_1 \times I$

Fig. 2.5. A potentiometer used for deriving a fraction of a given voltage.


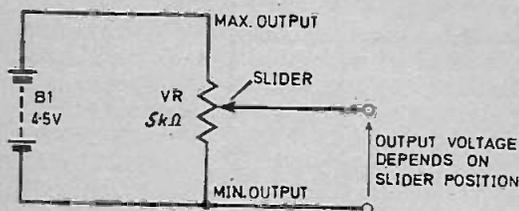


Fig. 2.6. Energy dissipation in a circuit.

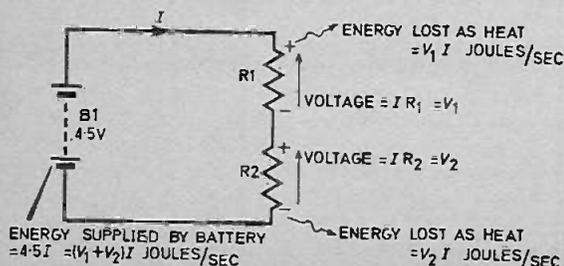

joules per second. A rate of one joule per second is known as a power of one watt. Thus power, which is a measure of the rate of doing work or the rate of using up energy is given by

$$\text{power in } R_1 = V_1 I \text{ watts}$$

but $V_1 = I R_1$ by applying Ohm's law.

$$\text{Hence, power in } R_1 = I R_1 \times I = I^2 R_1$$

An alternative expression can be obtained by substituting V_1/R_1 for I ,

$$\text{i.e., Power in } R_1 = V_1^2/R_1$$

The power dissipated in R_2 is obtained in a similar way by replacing R_1 by R_2 in the above equations.

Every resistor can dissipate a certain amount of power without suffering damage or excessive rise in temperature. If the power dissipation rating of a component is insufficient one can put resistors in series or parallel, as mentioned earlier to get a higher total dissipation. For example, two one watt-rating, 1 kilohm resistors give the equivalent of a two watt 2 kilohm resistor, when in series, or a 500 ohm two watt resistor, when in parallel.

In the Tutor Board experiments it is unlikely that any heat dissipation problems will arise due to the relatively low voltages in use. It is however necessary to be aware of the possibility of overheating in such circuits as power supplies, power amplifiers and similar equipment.

The resistance element of an electric fire is specially made to withstand high power dissipation even when the wire is glowing red. In general high dissipation resistors are large and sometimes have a vitreous coating to protect the wire.

SEMICONDUCTOR DIODES

The components used so far will all allow current to flow in either direction. Reversing the connections of say resistor R_1 in Fig. 2.4 does not affect the current in any way. Similarly if we change over the battery connections the currents flow in the opposite direction to before but the magnitude of these currents is unchanged.

The voltage differences are also the same magnitude as before, although opposite in polarity due to the reversed currents. The battery polarity is the important factor in determining the current direction and when it is delivering energy to the circuit the current always flows out of the positive terminal.

Unlike the resistor, the semiconductor diode will only pass current in one direction. For this so-called forward bias direction the diode offers very little resistance to current flow whereas for the opposite direction, known as reverse bias, the resistance is very high and the current flow is virtually cut off. The action is that of a one-way valve, just like the valves in our own blood circulation system, Fig. 2.7.

The easy direction or "forward bias" flow of conventional current is from anode to cathode and since the cathode is usually marked with

a band this is the lead from which current leaves the diode. If the diode is connected in a circuit so that current tries to flow into the cathode lead the diode turns off and the current is virtually zero.

The diode differs from the simple resistor in other ways. With a resistor the voltage difference is proportional to the current flow. As the current increases so does the voltage. However the current-voltage variation for the diode does not follow Ohm's law and the characteristic of a typical diode is shown in Fig. 2.8.

For appreciable forward current the voltage across a silicon diode must be about 0.6V. At this voltage the diode readily conducts and the current flow is then mainly determined by the conditions in the rest of the circuit. The voltage V_{AC} across the diode rises only slightly even though the current may increase from say 1mA to 100mA. A similar change of current in a resistor would involve a hundred-fold increase in the voltage.

If the diode or battery connections are changed over, current virtually ceases and the diode remains non conducting until the breakdown voltage is reached at point X. For the silicon 1N4001 diode this breakdown voltage is at least 50 volts. The maximum forward current

must be restricted to 1 ampere due to power dissipation requirements.

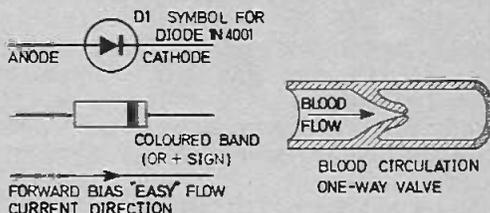


Fig. 2.7. The Diode and representation of its action.

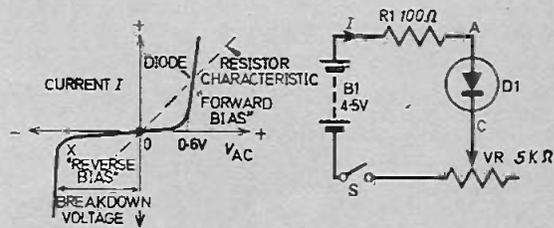


Fig. 2.8. Diode characteristics and test circuit.


Next month: another new component known as a capacitor is introduced and its behaviour is examined in theory and practice.

TUTOR BOARD EXPERIMENTS

Test No. 4

Build the series circuit shown in Fig. 2.9 together with the 0-10V voltmeter circuit. Remember to remove the shorting lead. Initially make $R1=R2=1$ kilohm and with the switch set to on, measure the voltages between points A and B, B and C, and A and C. Allowing for experimental error check these readings which should satisfy the relationship $V_{AC}=V_{AB}+V_{BC}$.

Fig. 2.9. Circuit and voltmeter circuit for use with test 4.

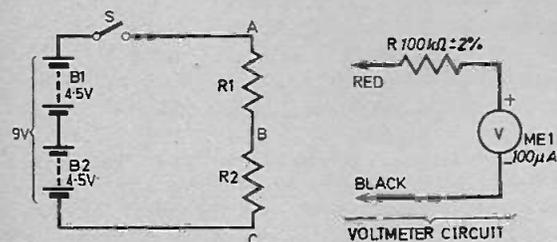

The red voltmeter lead should always be connected to the point at which current enters the component, otherwise the meter pointer will try to turn backwards. Repeat the test with $R1=R2=10$ kilohms and then with $R1=R2=100$ kilohms. In this last case the readings for V_{AB} and V_{BC} will both be lower than before at about 3.0 volts, whereas V_{AC} will still be approximately 9.0 volts. By reviewing Fig. 2.4 try to explain these results

which are due to the loading of the circuit by the resistance of the voltmeter. Dismantle the circuit, except for the voltmeter, and record your observations for future reference.

Test No. 6

In this test the circuit of Fig. 2.8 is used to measure the forward characteristic of the 1N4001 diode. The 5 kilohm potentiometer is used as a variable resistor to alter the circuit current over a range of about 4 to 40mA. The current, I , can be estimated by using the voltmeter to measure the voltage difference across the fixed 100 ohm resistor. By Ohm's law this voltage will be:—

$$V_R \text{ across } 100\Omega = \frac{I(\text{mA}) \times 100(\Omega)}{1000} \text{ volts}$$

Hence $I=(10 V_R)$ mA where V_R is the voltmeter reading in volts.

The diode voltage V_{AC} for any level of current

Table 2.1; Diode Characteristics

V_R (Volts)	0	1.0	2.0	3.0	4.0
$I=10V_R$ (mA)	0	10	20	30	40
V_{AC} (Volts)	0				

V_R READINGS CAN BE SET BY 5k Ω POTENTIOMETER

DIODE VOLTAGE DIFFERENCE FOR EACH LEVEL OF CURRENT

can also be recorded by using the voltmeter across points A and C. The corresponding results should be recorded in a table as shown (Table 2.1).

Notice that when the voltmeter is connected across the 100 ohm resistor the combination behaves in the same way as a 0-100mA milliammeter. Draw a schematic for this part of the circuit and try to explain how this behaviour arises.

Dismantle the test circuit and replace the shorting lead across the meter terminals for protection.

LAST MONTH'S TESTS

Last month the first two tests introduced a simple series circuit and the idea of a voltmeter. The series arrangement, Test No. 1, illustrates the existence of current flow when the switch is closed by virtue of the light output from the 6 volt bulb. Altering the total circuit resistance by means of the 100 ohm variable potentiometer changes the current flow and the light output varies.

The resistance of the lamp is not constant and actually rises as the element heats up. The bulb rating refers to operation at 6 volts and the nominal current of 60mA implies a resistance of 100 ohms at this voltage. When the element is cold the resistance will be less than 100 ohms.

The second test introduces the concept of a voltmeter. An ideal voltmeter would not require any current to operate it but this cannot be

achieved with the simple arrangement used. Since the meter requires current to make the pointer move, this current must be taken from the circuit being measured and will disturb the circuit conditions. This is often called "circuit loading". The extent of this loading effect depends on the circuit under consideration and the resistance of the voltmeter circuit.

The Tutor Board system uses a 100 μ A meter and this represents the maximum current necessary to give a full scale deflection. The loading effect can be considered by thinking of the voltmeter as a 100 kilohm resistor and comparing this with the effective resistance at the measuring point in the circuit. As a general guide the best results are obtained when the effective circuit resistance is much less than the voltmeter resistance.

The third test illustrates some of the ways in which voltage measurements can be taken. With the potentiometer set at maximum resistance, 5 kilohms, the circuit current is 1.5mA, assuming the batteries each provide 4.5 volts. Consequently the voltage across the 1 kilohm resistor must be 1.5 volts and that across the 5 kilohm potentiometer $(9 - 1.5) = 7.5$ volts. These values correspond to a difference of 3.0 volts between the points originally specified.

The potentiometer must be set to introduce a voltage difference of 4.5 volts, for the zero reading condition, and this corresponds to a value of 1 kilohm and a circuit current of 4.5mA. The resistance values are sufficiently low in this test that voltmeter loading errors are negligible.

What do you know?

CURRENT

- 1 Say which way conventional current flows and state the difference between this and electron flow.
- 2 An alternating current is applied to a circuit via a single diode, show the waveform of the voltage across the circuit.
- 3 The waveform above is applied to a large value electrolytic capacitor, show what effect this has on the waveform and say why this is advantageous in audio circuits.
- 4 What refinement can be made to the circuit of (3) to improve it further for supplying audio equipment, and what is the advantage.



ANSWERS

1 Conventional current flows from positive to negative, electrons flow in the opposite direction.

4 A full wave or bridge rectifier could be used. This would invert the "lost" half cycles of the original circuit and provide a much smoother waveform, thus reducing hum further e.g.

3 The electrolytic capacitor will tend to smooth in audio circuits because it helps to reduce the hum created by the pulsating supply; on load the waveform should appear thus:

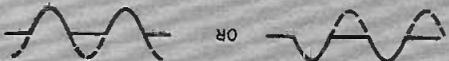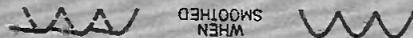2 The waveform will be a sine wave cut in half, it could be either positive or negative going, depending on the connection of the diode e.g.



SEMICONDUCTORS

SIX

TRANSISTOR TESTING

J.B. DANCE M.Sc.

IN this, the final part of the Semiconductors series, we deal with simple testing of *npn* and *pnp* transistors.

TESTING TRANSISTORS

Most of the simple transistor testers measure the leakage current and the common emitter current gain.

The circuits of Figs. 6.1 and 6.2 (for *npn* and *pnp* transistors respectively) are the simplest form of circuit for measuring the leakage current and checking that the transistor has a reasonably high current gain. These circuits can be assembled in a few moments by the amateur experimenter and crocodile clips may be used for connecting the leads to the emitter and collector of the transistor.

The circuits are intended mainly for the testing of small signal transistors; modifications to the resistor values and meter range may be desirable when testing power transistors.

However, the fact that the testing is carried out at small values of collector current prevents any possibility of the transistor being damaged. The 820 ohm series resistor limits the current which can flow to about 7.3mA when a 6V battery is employed.

TESTING PROCEDURE

Leakage current

In order to check that the transistor does not pass excessive leakage current, it should be connected in the circuit as shown, but no connection should be made to the base.

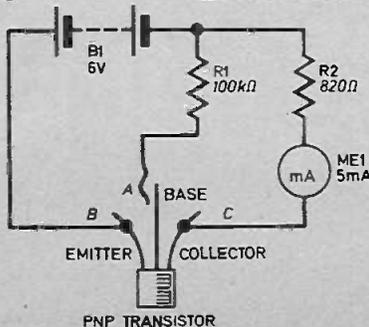
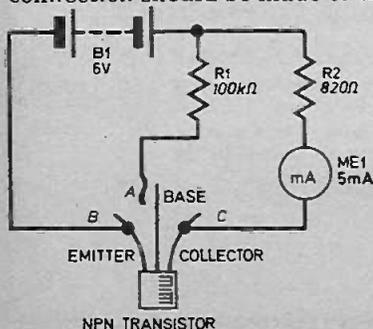


Fig. 6.1 (left). Circuit for the basic tests on an *npn* transistor.

Fig. 6.2. Circuit for the basic tests on a *pnp* transistor.

If the transistor is a silicon one, no detectable meter deflection should be observed. Small germanium transistors will pass a leakage current which is normally less than 0.2mA.

If the meter reads above 1mA when a small signal transistor is being tested, the leakage is excessive and the transistor is defective. Germanium power transistors may pass a higher current, but this leakage should not normally exceed about 3mA.

Current Gain

To test the current gain the lead marked A in Figs. 6.1 and 6.2 should be touched onto the base of the transistor. If the component is functioning satisfactorily, the collector current will rise and, in the case of a high gain transistor, the meter will show a full scale deflection.

If no appreciable deflection occurs when the lead A is connected to the base lead of the transistor, the device is almost certainly defective.

It should be mentioned, however, that there are a few types of switching transistor (such as the 2N711) which have a very low current gain at low collector currents. If such types are being tested, it is worth while checking that no appreciable collector current increase occurs when the 100 kilohm resistor is replaced by a 22 kilohm resistor before the transistor is discarded. However, it has been found that, even in the case of the 2N711, virtually all of the specimens tested gave a satisfactory reading even when the 100 kilohm resistor was used in the base circuit.

The current which flows in the base circuit when the lead A touches the base lead is given by Ohm's law, $I=V/R$ and is approximately $6/100,000 \text{ amps}=60\mu\text{A}$.

If the common emitter current gain (h_{ie}) of the transistor is 10, then $600\mu\text{A}$ will therefore flow in the collector circuit.

If the transistor gain is 500, one might expect that a collector current of $(60 \times 500) \mu\text{A}=30\text{mA}$ would flow. In this case, however, the collector current flowing through the 820 ohm series resistor limits this current to about 7mA. With a very high gain transistor, one may obtain a deflection which is a little over full scale.

Although it is possible to use this simple type of circuit to estimate the current gain of a transistor, the circuit is really intended to show only whether the transistor is functioning satisfactorily.

TESTING UNKNOWN TYPES

The circuits of Figs. 6.1 and 6.2 can be used for the testing of unknown transistors and for identifying the electrodes if the connections to the transistor are unknown.

A pair of the unknown transistor leads are connected between B and C of either circuit, first in one direction and then in the other. This is repeated with other pairs of the transistor leads (if necessary) until a pair is found which pass little current in either direction.

These two leads are the emitter and collector, since if the base were taken with either the emitter or collector, the base/emitter junction or the base/collector junction would conduct in one direction.

If no two leads can be found which show a high resistance in *both* directions, the device is almost certainly useless.

Before the device is discarded, it may be worth while checking that no two leads can be found which pass little current in either direction when the battery voltage is reduced to 1.5 volts.

The reason for using this lower voltage is that some transistors (especially modern silicon planar types) have an emitter/base breakdown voltage which is smaller than 6V.

We now know which electrode is the base, but we have not yet distinguished between the collector and emitter. If the base and either of the other electrodes is connected between B and C of either of the test circuits, an appreciable current will flow if the base is *positive* in an *npn* transistor or *negative* in a *pnp* type. Thus this test shows whether the device is *npn* or *pnp*.

Finally, the transistor is connected in the Fig. 6.1 circuit if it is an *npn* type or in the Fig. 6.2 circuit if it is *pnp*.

The deflection of the meter is noted when A touches the base lead, first with the other two transistor leads connected in one way to B and C and then with these two connections reversed.

The orientation which gives the greatest meter deflection is the one in which the collector is connected to the meter.

Although one can obtain a current gain in some transistors when the emitter and collector leads are interchanged, one normally obtains a much higher current gain when the connections are made in the correct way. This applies more to modern silicon transistors than to the older germanium types.

Indeed, a few germanium types have been made in the past which are known as "symmetrical transistors" because the emitter and collector are completely interchangeable and a similar gain is obtained with both connections.

FOUR LEADS

Devices which have four leads may cause problems when the device type is unknown and one wishes to test it. It may be that the device is not a simple transistor at all, but it is worth while ascertaining whether one of the leads is connected to the metal case. If so, one carries out the above tests using the other three leads.

□

CONSTRUCTORS TAKE YOUR PICK . . .

- WAA WAA EFFECTS UNIT
- SIMPLE TOUCH SWITCH
- DIODE THERMOMETER
- LIGHT OPERATED SWITCH

. . . THE CHOICE IS YOURS!

Build one of four special simple projects, described in an 8-page supplement, on the **FREE VERSATILE PRINTED WIRING BOARD** included in the **NOVEMBER** issue of **PRACTICAL ELECTRONICS**

THE GOOD COMPANIONS



Two magazines designed to complement each other in every way—together satisfying the needs of everyone involved in electronics.

PE

PRACTICAL ELECTRONICS

November issue on sale now

YOUR GUIDE TO -

Constructional Methods

- **Printed Circuit Board**
- **Copper Clad Veroboard**
- **Plain Matrix Board**
- **Stick-on Wiring**
- **Tag Board & Tag Strip**

EVERYDAY ELECTRONICS
NOVEMBER 1973

SPECIAL SUPPLEMENT



Not going back too far into the history of electrical and electronic circuits, the latter were built up in quite a different fashion from that employed today; the system used was called point-to-point wiring or the wired circuit, and this was the major (if not the only) method open to the amateur constructor at the time.

DAYS GONE BY

In these days gone by, the larger components (valves, large capacitors etc) were mechanically secured in position on the chassis or component board and were linked together and to the other components using the latter and many lengths of wire; it was quite common to find several components and wires all joined at a common point. Solder tags and tag strips were used extensively.

The general appearance of the finished product was, if special care was not taken, a mass of wire and a maze of components, not the ideal situation for the beginner or the constructor of limited experience. Also, this method was especially susceptible to omitted wire links and fault finding was tedious and difficult to carry out.

For today's amateur constructor of electronic projects there are several forms of construction open, namely (a) printed circuit board (b) Vero-board, copper clad and unclad (c) stick-on wiring, Q-strip (d) tag board and tag strip.

Each have their own advantages (and disadvantages) for a particular project but some methods will be found more suited to the project than others.

CONSIDERATIONS

Some factors to take into consideration when selecting a particular form of construction are:

- (1) maximum current flow in the circuit, especially in the cases of (a) (b) and (c) above;
- (2) the required completed size and geometry of the board;
- (3) high frequency signals where the inductance of a copper strip becomes evident as does the capacitance between neighbouring copper strips;
- (4) mounting the finished form to case or other components;
- (5) the component layout should be kept as simple as possible so that the circuit can be easily traced in the event of a failure.

PRINTED CIRCUIT BOARD

The printed circuit board, as its name implies, has the circuit of the project printed on the board. This is in the form of a copper laminate bonded, in general, to one side of an s.r.b.p. (synthetic resin bonded paper) or fibreglass board; the "pattern" of copper is designed to

link all the components, as required by the circuit diagram, see Fig. 1.

Components are connected to the copper circuit by drilling holes in the board and copper and inserting the appropriate component leads into these holes and soldering to the copper. Care must be taken not to leave the soldering iron on the joint too long because the copper may be lifted from the board.

Thus the printed copper takes the place of the linking wires mentioned earlier and gives a much neater and compact finished product.

The printed circuit is very versatile and is perhaps the neatest and most reliable of all electronic constructional methods.

Although it is easy to construct a printed circuit board, it takes time and patience, and is probably more suitable for large quantity production than for the amateur constructor requiring "one-off" quantities. It is found to be slightly more expensive than other methods but points in its favour lay in the fact that the finished product has a professional appearance and fault tracing is relatively simple.

The raw board comes in the form of a thin sheet of copper bonded to one side of an s.r.b.p. or fibreglass board; the copper pattern is made by dissolving, with a suitable solution, certain areas of the copper; this is known as etching. A common etchant is a solution of ferric chloride ($FeCl_2$).

In EVERYDAY ELECTRONICS and other journals, projects to be built on p.c. board show what is known as the "master-drawing", showing the copper pattern (full size) required to be formed on the board. The deep-black areas are the required areas of copper (referred to as "lands") to remain after etching, see Figs. 2 and 3.

Component layout diagrams in EVERYDAY ELECTRONICS show the components mounted in position on the top (plain) side of the board over a tinted area; this area is the copper pattern that would be seen when the board is held up to a strong light—plain side towards you—or what you would see if constructing with the aid of the P.C. Viewer (E. E. July 1973).

This tinted overlay helps to ensure that the component locating holes are found with minimum trouble and error, see Fig. 4.

When mounting components, the component leads should be bent neatly so that they are parallel and exactly span the holes allocated to them refer to Fig. 5.

The protruding leads should be cut so that only about 1 or 2 mm extends below the copper and then the lead is soldered to the copper. If desired a semi-mechanical joint can be made by bending the component leads parallel to the board prior to cutting and soldering. This way several components can be fixed in position and

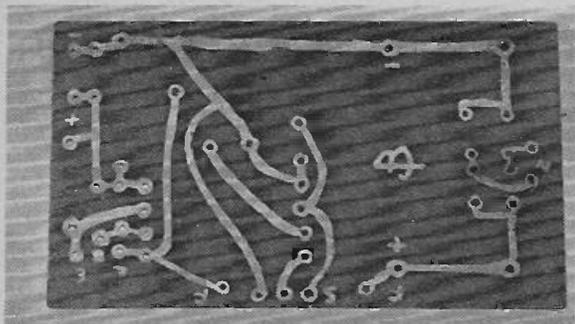


Fig. 1. The copper laminate pattern that replaces discrete wiring between components.

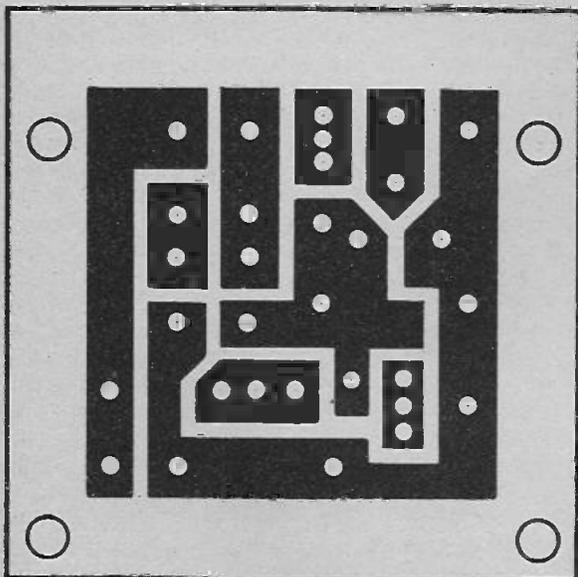


Fig. 2. The master drawing of the printed circuit.

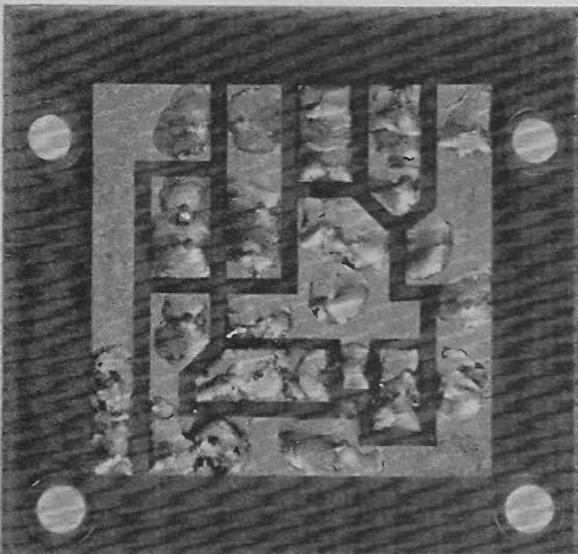


Fig. 3. The completed printed circuit board of Fig. 2 with components soldered.


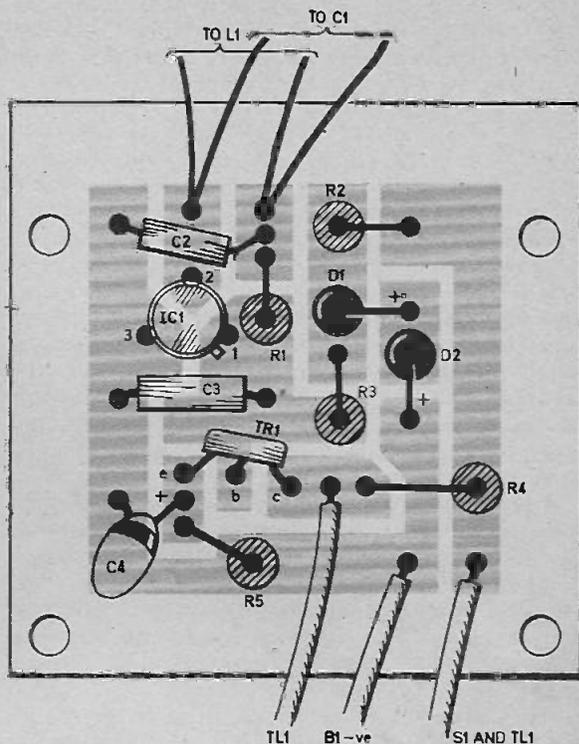


Fig. 4. Topside of printed circuit board showing component positions relative to copper pattern on underside (shown tinted).

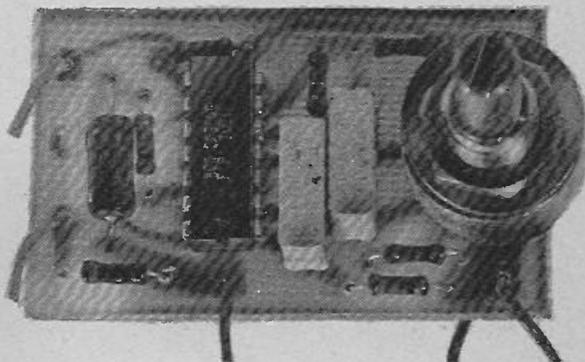

Photograph of a completed component board using the p.c. board method, illuminated from the rear.

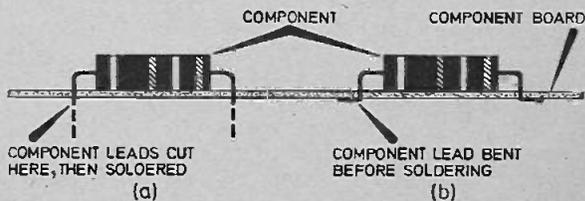


Fig. 5. Method of securing components to the component board.

then all is turned over. It is inadvisable to cut the component leads after soldering has been carried out since this can result in damage to the soldered joints.

In places where the copper is narrow, especially, do not apply the soldering iron for too long, otherwise the printed circuit will come away from the board and possibly be severed.

Connection of other components not mounted on the component board calls for the use of flying leads. These can be directly soldered into appropriate holes on the p.c. board—from the plain side through the board to the copper—and then soldered, or Veropins can be inserted and soldered in the holes and the wires connected to these. This method of using Veropins enables more than one flying lead connection to a single point if desired or required.

Flying leads from the board to remote components can be eliminated if desired, by the use of an edge connector. When using the latter, the printed circuit is designed so that all the required external connection points are brought out to one edge of the board, and the board is then plugged into the appropriately wired connector.

Mounting of the board in its case is accomplished by drilling suitable sized holes in a region on the board devoid of copper and then using a 4 or 6 BA nut, bolt and spacer.

Sometimes, when the p.c. board is small and light and when, say, a printed circuit type potentiometer has been used, the board need not be mounted in the above way, since the potentiometer when bolted in position, on say, the front panel of a case, eliminates the need for other fixings.

Full details of making printed circuit boards—from personal designs or those given in journals can be found in the June 1973 issue of **EVERYDAY ELECTRONICS**.

VEROBOARD

This is probably the most used type of general purpose construction board and is featured regularly in **EVERYDAY ELECTRONICS** constructional projects. The copper clad variety, as will be seen, is a special type of p.c. board.

Veroboard is available in two main sizes referred to as 0.15in. and 0.1in. types. This coding refers to the matrix of drilled holes i.e. the perpendicular distance between neighbouring rows and columns of holes.

The board is generally made of Paxolin (a brown plastic type insulator) but can be obtained in fibreglass. The two matrix sizes mentioned above are available in three versions: (a) with parallel strips of copper bonded to one side of the board along the rows of holes (b) with both sides clad in the above fashion (c) unclad board,

referred to normally as plain perforated or matrix board. Type (b) is hardly ever used in the amateur field and so will not be discussed further.

COPPER CLAD

The copper strips on the Veroboard are utilised as circuit interconnections, and the strips are linked or cut as required to produce the "physical" of the theoretical circuit diagram.

Usually in constructional projects, two views of the board are shown, one from the unclad side of the board, on which side the components are mounted—and the underside showing the copper strips with breaks and join along them where necessary, see Fig. 6. The holes in which component leads and flying leads emerge to be soldered to the strips, are shown as black dots, see Fig. 6.

For easy reference, all the holes on the board are labelled by use of co-ordinates from the top side; the rows are labelled A, B, C, D, E . . . etc and the columns, 1, 2, 3, 4 . . . e.g. location D6 is the intersection of row D with column 6, Fig. 7.


Components can be mounted in two ways, these being either with the component body parallel to the board or perpendicular to it, the latter method usually being employed when the completed size of the component board is to be kept minimal, see Fig. 8.

When mounting components (with the exception of transistors) the leads should be bent as indicated in Fig. 5 so that they exactly span the holes allocated to them. This can be done with either a pair of tapered nose pliers or the bending tool featured in *Bright Ideas* March 1973.

Once the leads have been bent, they should be inserted in place on the board and the leads cut so that only about 1 to 2mm projects below the board. The components can then be soldered directly by applying heat and solder to the component lead and copper around it, Fig. 5a; another method often employed is to bend the leads as shown in Fig. 5b to form a semi-mechanical joint before soldering. It should be pointed out that if this method is used component removal at a later stage, if necessary, can be a little difficult.

The main advantage of copper clad Veroboard is that the "wiring" is permanently bonded to the board (the copper strips) and this affords a rigid anchor point for the component when soldered.

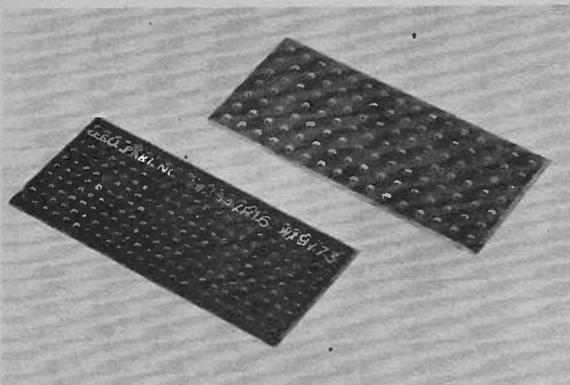A useful accessory (more used with the unclad board though) is the Veropin. This is a tinned brass pin manufactured so that it can be pushed into the holes of the matrix where desired, and holds firm. The pin should then be soldered to the copper strip at the point of entry.



Photograph, above and below, of the two most commonly used types of Veroboard referred to in the text.

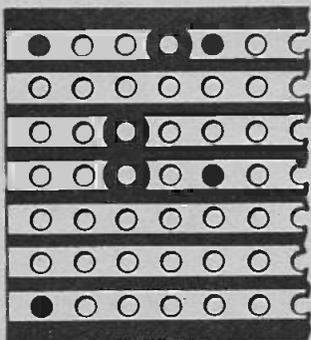
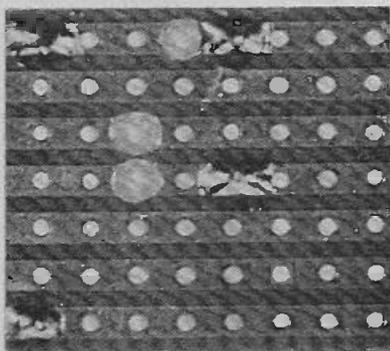
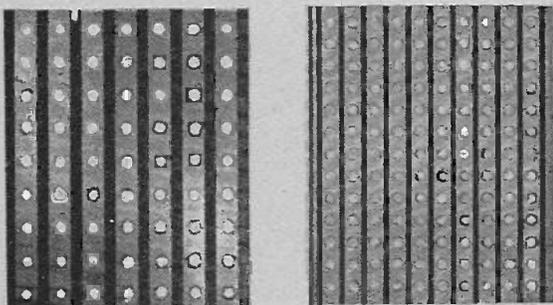


Fig. 6. Photograph and drawing of the underside of the same component board showing breaks and soldered connections.

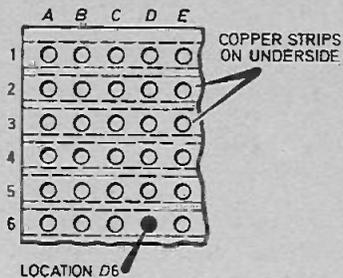


Fig. 7. Hole location using system of co-ordinates.



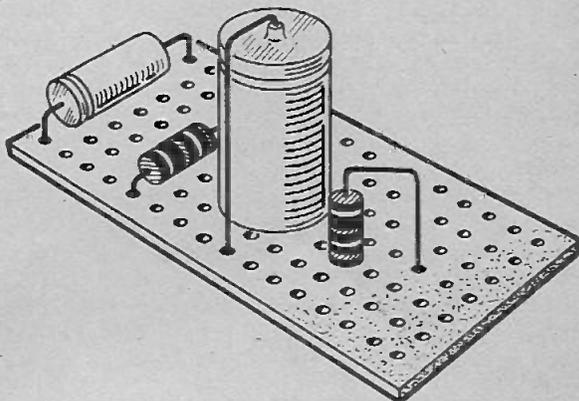


Fig. 8. Details of the two methods, horizontal and vertical, of mounting components on the component board.

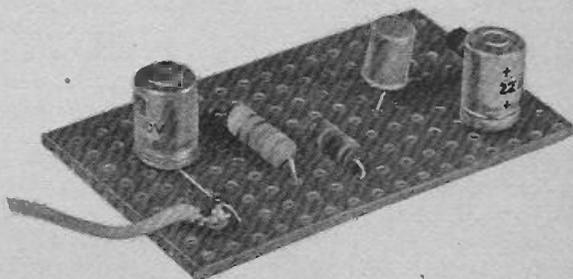

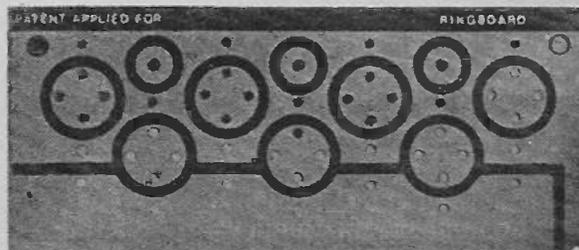Photograph of a simple project built on copper clad Veroboard.



Photograph of another general purpose wiring board (Ringboard).

UNCLAD VEROBOARD

Unclad Veroboard is also known as plain perforated board or matrix board.

Components are mounted in a similar fashion to that on the copper clad version i.e. component leads pushed through holes in the board, but here the components have to be linked using the component lead out wires and/or stout tinned copper wire, say 18 to 22 s.w.g. Single stranded p.v.c. covered connecting wire is also used.

A very useful accessory for plain matrix board is the Veropin discussed earlier. These afford rigid anchorage points for large components and flying leads to other components such as switches, potentiometers, lamps etc; they are also extremely useful when it is necessary to make multiple connections at a single point.

Both sides of the board are used and constructional projects in EVERYDAY ELECTRONICS show both sides of the board. On one side, called the topside, the component positions (layout) are shown; the reverse side shows all the interconnections required to link the board components as per circuit diagram, see Fig. 9.

When one wire (or more) is soldered to another on the underside, this is signified in the conventional way by a solder blob at the point of connection; emerging component leads are shown as black dots.

Flying leads to other circuit components usually are double labelled—at the end of the flying lead e.g. to VR1, and at its origination from the board by letters A, B, C, D, etc. The advantage of the latter labelling is evident when referring to the complete wiring diagram.

Mounting of the board is carried out in a similar manner to the clad Veroboard using 6BA or 4BA nuts, bolts, and spacers.

When mounting perpendicular to a chassis or front panel, right angled brackets can be used.

This form of construction has proved very popular with the amateur and has been successfully proven over and over again. However, its main drawback is that for complicated circuits, the number of linking wires on the underside tends to look "messy" and fault finding and circuit tracing can then be difficult.

STICK-ON WIRING

Stick-on wiring, available under the brand name of Q-strip, is another useful means of circuit construction and will be seen to be yet another form of printed circuit.

Basically, Q-strip consists of a narrow length of high-purity copper with a self-adhesive on one side. The self-adhesive carries a paper backing to protect its adhesive properties; Q-strip is available in widths of $\frac{1}{8}$ in. and $\frac{1}{16}$ in. and is

sold in reels.

The use of stick-on wiring enables the "physical" circuit layout to be made as per the theoretical circuit diagram. This is a very useful property for the beginner because he is readily able to see the component interconnections and compare them with the circuit diagram.

The idea behind Q-strip is that it is stuck down on to the component board and used as the connecting links between the components in just the same way as the strips on copper clad Veroboard or printed circuit board form connections between the components.

Q-strip can be stuck on almost any type of insulating board, the most favoured ones being Paxolin board, plain matrix Veroboard and Perspex.

First of all the layout is designed (if not given) on say a piece of graph paper—this is very useful for designing all types of layout. If using Paxolin or Perspex, it will then be necessary to drill all the component locating holes with reference to the graph paper layout. If using matrix board this is obviously not necessary.

The strip is applied to the board in much the same way as Sellotape is used; the strip is cut to the required length and offered up to check; the paper backing is then removed and the strip is carefully placed in the correct position and pressed down firmly. Run a finger or side of a pencil along the strip to remove any kinks that there may be. It is essential that the adhesive backing is not touched during this process, as this will impair its effectiveness. If the strip is found to be incorrectly positioned it can be carefully removed and replaced.

There are two modes of laying the stick-on wiring with reference to the component holes. One way is to cut the required length and stick the wiring to the board so that it covers all the component holes it is to link. Then using a pointed tool such as a sharp nail or scribe, the copper strip is pierced at the hole positions. Component leads can then be pushed through these holes from the unclad side and soldered in a similar way to when using Veroboard, Fig. 10a.

The second way is to stick the copper strip alongside the holes that are to take the components, and then when the component leads are pushed through, to bend the latter over so that they are in contact with the strip and then soldered in position, Fig. 10b.

When two pieces of Q-strip are to be joined this can be done quite easily by merely butting the two strips and then applying a blob of solder at the butt.

It will sometimes be found necessary to have one strip crossing another, but with no electrical contact. This is done by sticking a small piece of insulating tape over the lower strip and then passing the other strip over the top.



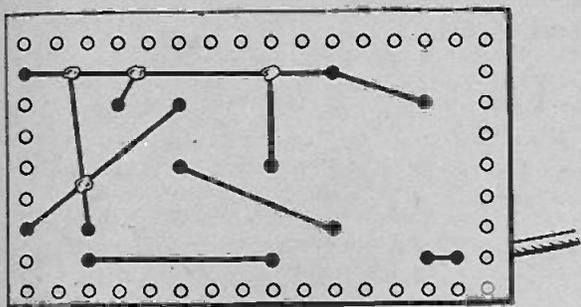


Fig. 9. Schematic of underside of component board using unclad Veroboard.

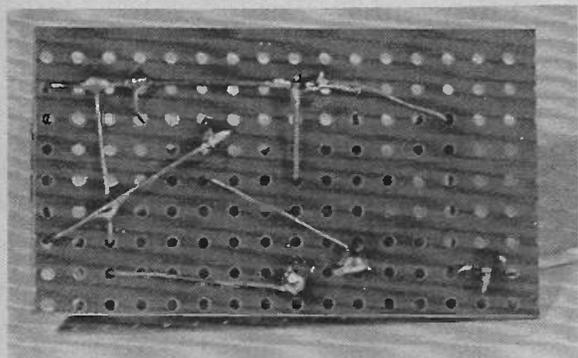


Photograph of Fig. 9.

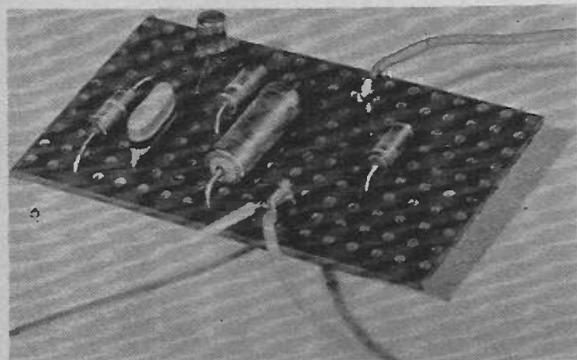


Photograph of simple project built on unclad Veroboard.

Difficulty will arise if the Q-strip is bent to form a curve of small radius since kinking will occur and the strip will not be adequately secured to the board. This should be avoided wherever possible and short-lengthed butting employed as mentioned above.

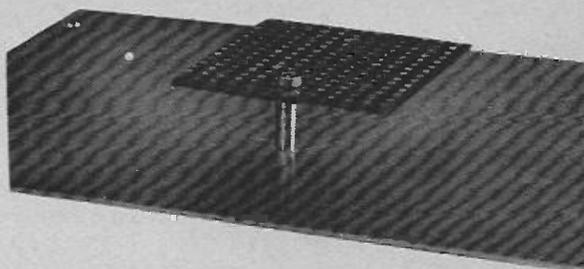
When Q-strip is being soldered the adhesive backing tends to melt, especially if the soldering iron is held on the strip for too long a period, and the strip is inclined to shift particularly in the case of short lengths. No permanent damage is incurred due to adhesive melt, since its property is restored on cooling off. After soldering it is advisable to press the strip firmly home



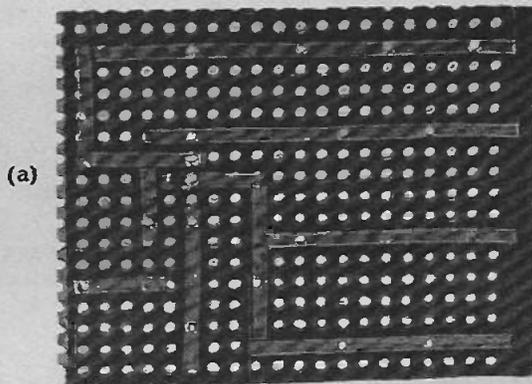Method of mounting component board; applicable to all types of construction discussed here.



(a)

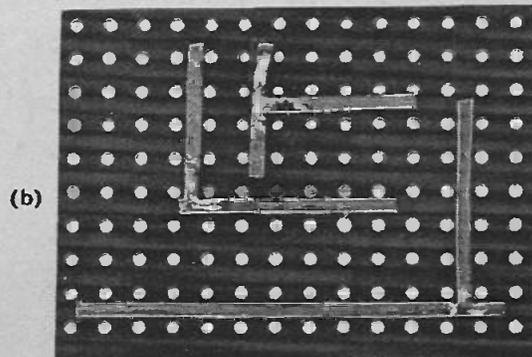

(b)

Fig. 10. Methods of placing stick-on wiring with reference to component holes.

again (and re-position if called for); long soldering periods should, of course, in any form of construction, be avoided.

Appearance-wise, the finished Q-strip board is like the printed circuit board; the difference is that no chemicals have been used by the constructor to produce it.

If required a double sided board can be made using this method.

Veropins will be found very useful with this method of construction for flying leads, large components, multiple connections at one point etc. and should be used as described in the previous methods.

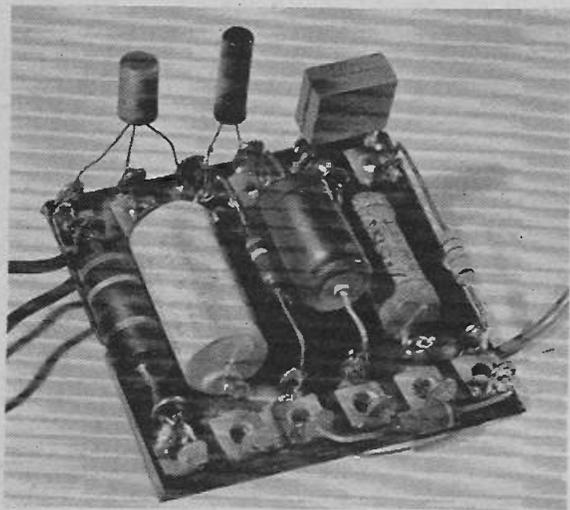


Fig. 11. A simple project wired up on a piece of standard tag board.


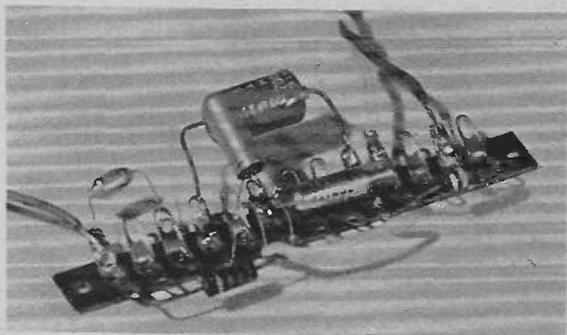


Fig. 12. Method of wiring up components on a piece of tag strip.

Fig. 13 (right). Photograph of alternative type tag strip and miniature tag board.

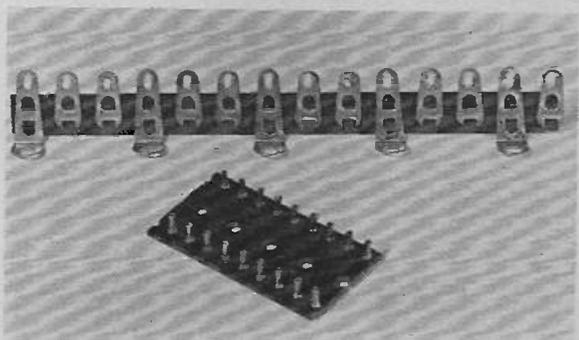

TAG BOARD

Tag board, also known as group board, is available in two sizes, standard and miniature, these sizes referring to size of the tags.

It consists of a Paxolin base panel with two rows of double tags directly opposite each other along the sides of the panel. The tags are held in position by means of small rivets or bent clips, these can be seen on the underside and are a possible means of connection.

The standard board is available in 8- and 16-way versions and the miniature in 10- and 20-way. This refers to the number of tags along each side, but these boards can be cut to suit individual requirements.

This means of construction is generally only suitable for projects containing only a small component count.

Components can be mounted and soldered across opposite tags or across tags on the same side, Fig. 11; wiring linkages between the various components can be carried out by using the tag fixings on the underside of the panel.

There is a series of holes along the centre of the tag boards and these afford a means of mounting the completed board; 6BA or 4BA nuts, bolts and spacers should be used.

TAG STRIP

There are some several forms of tag strip available in various lengths and tag size. The two most commonly encountered types are shown in Figs. 12 and 13.

One version consists of a thin strip of Paxolin with double sided tags riveted perpendicular to the length. Fixing holes for mounting are provided at both ends.

The second version is basically the same except that the tags are only single sided and every fourth tag affords a means of mounting to a base board or chassis.

Component mounting is carried out by soldering the component leads to the tags and then linking up the component with p.v.c. covered wire.

For the tag board and the double sided tag strip, tag push-on connectors are available for connecting, via a flying lead, to components remote from the board/strip. These push-on connectors are advantageous when the tag board/strip needs to be removed—desoldering is not then necessary.

Tag strip is secured to a base board or chassis by using 6 BA or 4 BA nuts, bolts and stand-off spacers through its fixing holes.



Feedback

You often say that there is negative feedback from the emitter of a transistor and yet, more often than not, there is no obvious wired connection from the emitter back to the input; how, then, can any feedback occur?

This is a very common problem for beginners because it is difficult to see how you can get feedback without wiring. The answer lies in the action of the transistor. When we say there is feedback from the emitter you will always find a resistor going between emitter and ground—there might be a capacitor associated with it. You must understand that to make a transistor conduct we must pass base current and this in turn is controlled by the potential difference between the base circuit and the emitter potential of the transistor.

The driving potentials in the base circuit are usually set relative to ground and in the absence of any resistor in the emitter circuit of the transistor you could say that base current is directly proportional to the voltages in the base circuit. However as soon as you introduce even a small value resistor in the emitter circuit base current will cause current to flow between collector and emitter of the transistor. This causes a potential difference between the ends of the emitter resistor and you can say that the emitter potential starts to rise—relative to ground.

This rise in the emitter's poten-

tial reduces the potential difference between the base circuit and the emitter and hence effectively reduces the amount of base current that can flow. It counteracts the input signal and hence is a form of negative feedback.

Bridge

What is the advantage of a bridge rectifier over a single diode in a power supply?

A single diode removes one half of the 50Hz a.c. current so you end up with a waveform that looks like half a sine wave (say just the positive going parts). This represents a voltage that rises and falls back to zero sinusoidally but then stays at zero for the period of the negative going half of the cycle. The power is rectified because all the voltages produced are either at zero or are all on the same side of zero; however you have a very intermittent signal. This has to be smoothed with capacitors to give an even d.c. level.

A bridge rectifier not only allows through the positive going parts of the cycle but also turns the negative going halves upside down and fills in gaps between the separated positive going "humps" you would have had with a single diode. The signal is still of an intermittent d.c. but is much easier to smooth because you do not have the gaps you had before.

In many simple power supply situations you could substitute a single diode for a bridge but you would have to increase the value of the smoothing capacitor to get rid of residual hum—particularly when high currents are being drawn (see *What Do You Know*).

Pots

Would it be possible, in experimental circuits, to use cheap skeleton potentiometers instead of the expensive types with shafts and knobs whenever the latter are specified?

This is certainly possible but you should remember that preset potentiometers are usually linear law—although for experimental work this does not matter very much. More important is that you should check the power dissipation of the circuit in which you intend to use the substitute devices. The larger shaft type pots

usually have a rating of around 500mW while many of the sub miniature presets are less than 100mW.

As a general guide you can do the substitution where small signals (e.g. audio signals) are concerned in applications like volume controls and tone controls, but you should be wary when dealing with power stages—e.g. the control potentiometers of a variable power supply.

Soldering

Having just started in electronics I am not very good at soldering but I have followed your various instructions to the letter. However when I use Veroboard I can never get the solder to wet the copper strip and flow on to it nicely—I always end up with a blob on the end of the lead. Is there any special trick?

The first thing to ensure is that the Veroboard is clean. Often—if it has been in store for a long time—the copper strips can tarnish slightly and this might not be very obvious to the naked eye. We suggest you try lightly polishing the copper side of the board before you start construction—use a household scouring powder and water but remember to wash off all the particles of the powder and dry the board properly before you begin.

When doing the soldering remember that you must make the iron touch the copper strip at the same time as it is touching the component lead and allow 2 or 3 seconds for it to take up the heat of the iron before you apply the solder.

INTERCOM SYSTEMS



"This one has a warning system—a red light flashes whenever your wife enters the office building."

GAS ALARM

By M.H. KEENE

Detects the presence of smoke and combustible gases and vapours

THIS article describes an alarm suitable for the detection of combustible gases, vapours and smoke which is ideal for domestic use. The main sensing element is a variable conductivity device whose resistance changes quite markedly in the presence of a combustible gas.

The device is suitable for n-butane, propane, ethane, methane, town gas, hydrogen, carbon monoxide and smoke, and will detect these gases in concentrations of 0.2 per cent which is well below the explosive limit of these gases, see Table 1. The device is also useful as a smoke or fire alarm as combustible gases are present as a result of fire. The level at which the alarm actuates may be varied using the described circuitry.

Table 1: Explosive limits

Gas	Lower Explosive Limit*
Butane	1.8
Propane	2.12
Ethane	3.0
Methane	5.0
Hydrogen	4.0
Carbon monoxide	12.55

*Expressed as percentage by volume in air at room temperature.

SENSOR

The sensing element is an *n*-type semiconductor. The doping is such that when the sensor material is heated in air it reacts with oxygen causing a decrease in conductivity. This can be seen when the sensor is first turned on, as it will conduct quite heavily and then slowly, the resistance will increase in time in the warming up period as there are less free electrons available. This condition then changes when a de-oxidising i.e. combustible gas or vapour, is present when there are free electrons available thus increasing the sensor's conductivity.

CIRCUIT

The complete circuit of the Gas Alarm is shown in Fig. 1 and can be seen to consist of four distinct sections: the power supply, level switch, output amplifier and audible alarm.

Now the sensor heater can run off a.c. or d.c. It has been decided to use an a.c. supply, the voltage and current required being 1 volt at 500mA.

The mains transformer used in the prototype is a readily available one with two 6V secondary windings. One is used for the heater of the sensor in series with R1, a voltage dropper resistor, while the voltage from the other winding is half-wave rectified by D1 and then smoothed by capacitor C1. This gives about 8V d.c. to supply the rest of the circuitry.

Resistor R2 is included to limit the current flow through the detection part of the sensor.

The level switch part of the circuit uses an integrated circuit IC1, known as an operational amplifier, and this enables an alarm level to be set, below which, there will be no signal to the load circuit. Unlike in normal use, no feedback resistor is used and full open loop gain is utilised.

One input is used as a reference set by a potentiometer VR1 and the other is fed from the output of the sensor via current limiting resistor R3.

When the voltage level of the output falls below that set by the potentiometer, the output





**Approximate cost
of components
including V.A.T.
£6.30 plus case**

Everyday Electronics, November 1973

of IC1 will switch from the zero volts to that of the full positive supply. The reverse will occur when the output rises above that set by the potentiometer

The capacitor C2 on the inverting input of IC1 provides additional smoothing to the signal which prevents chattering of the output at the switching point.

The output circuit can be of many types depending on which form of alarm indication is required. In its simplest form the output of IC1 can switch on a low power bulb or l.e.d. If using an l.e.d. a current limiting resistor must be placed in series with l.e.d. When *only* this type of alarm is required TR1, RLA and the audible alarm are omitted.

For those output circuits which require more current than the output of IC1 can supply, some current amplification is required. This can easily be achieved by a single transistor, TR1.

The load for TR1 may be bulb, or a relay coil as in the prototype. Resistor R4 is used to limit the base current of TR1. Reversed biased diode D2 across the coil protects the transistor from any back e.m.f. spikes caused when the relay is released. The contacts of the relay specified may be used to switch up to mains voltages.

One pair of contacts are used on the prototype to switch on the power to the audible alarm, a simple astable multivibrator, which gives a continuous tone at the alarm condition, through loudspeaker LS1. Other alarms, in-built or remote from the unit can be obtained by using any additional relay contacts, the power of the alarm depending on contact rating.

Components

Resistors

R1	12 Ω	5W
R2	2.2k Ω	} $\frac{1}{2}$ watt carbon $\pm 10\%$
R3	1k Ω	
R4	1k Ω	
R5	1k Ω	
R6	10k Ω	
R7	10k Ω	
R8	1k Ω	

Potentiometer

VR1 10k Ω carbon linear

SEE
**SHOP
TALK**

Capacitors

C1 1000 μ F 9V elect.
C2 100 μ F 9V elect.
C3, C4, C5 0.1 μ F


Semiconductors

TR1 ZT80 or 2N3704 silicon *n*p*n*
TR2 ZTX300 silicon *n*p*n*
TR3 ZTX300 silicon *n*p*n*
D1 ZS178 or IN4001
D2 ZS178 or IN4001
IC1 741 operational amplifier and holder
SGS1 Semiconductor gas sensor

Miscellaneous

S1 Mains on/off switch
T1 Mains transformer, secondary 6V-6V 500mA
RLA Type PC2, 185 Ω or similar with at least one set of normally open contacts
LS1 Miniature loudspeaker 35 Ω impedance; base holder type B7G; metal case; Veroboard 0.1in. matrix 24 x 22 holes; nuts and bolts, 4BA and 6BA; length of three core mains lead.

Fig. 1. The complete circuit diagram of the Gas Alarm.

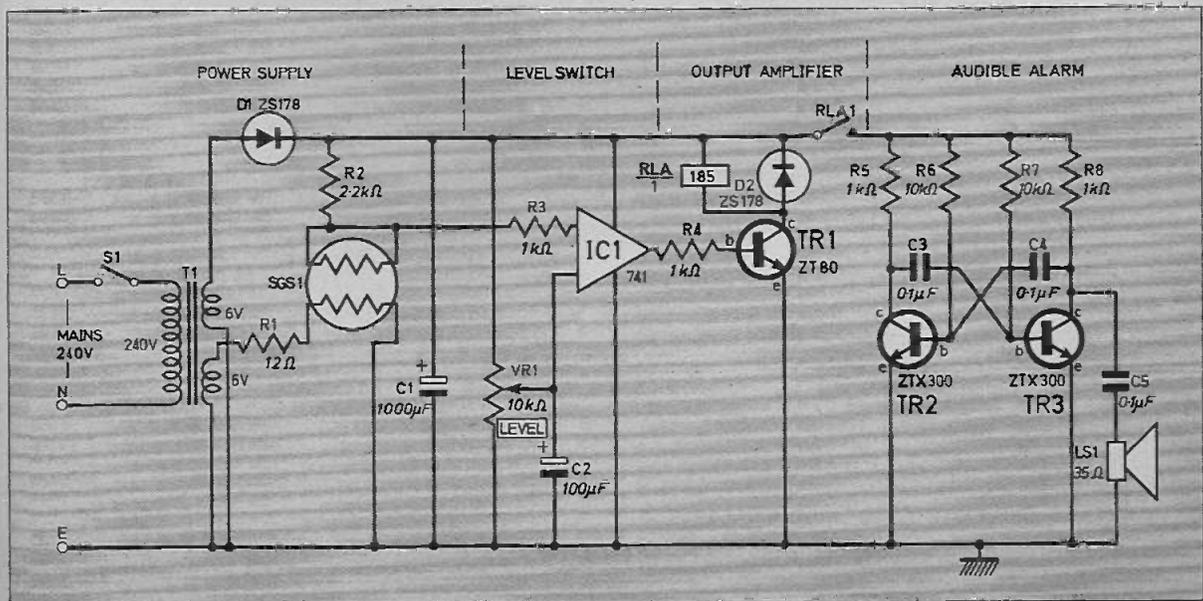


CONSTRUCTION

The components are mounted on a piece of 0.1in matrix Veroboard size 24 x 22 holes. The layout of these components is shown in Fig. 2.

Begin construction by drilling the two mounting holes and making the cut-outs along the copper strips as detailed in Fig. 2. Next mount and solder the resistors, capacitors, i.c. holder, link wires and flying leads as shown.

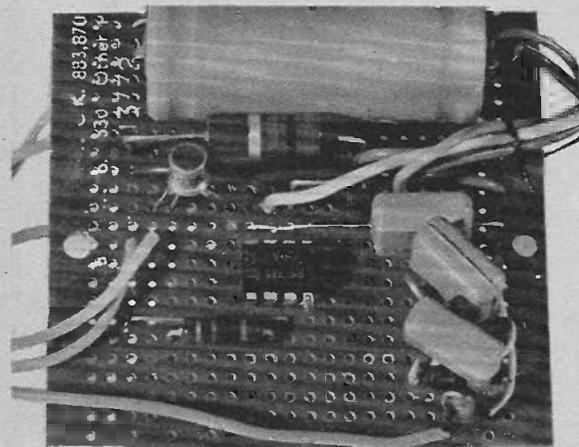When this has been done, the transistors should be soldered in position, remembering to use a heatshunt when doing so. Failure to do this may result in permanent damage to the transistors.



Photograph of the completed component board of prototype.

The prototype Gas Alarm was housed in a metal instrument box, approximate dimensions 170 x 120 x 50mm, with cut-outs as indicated in Fig. 3. A metal box is recommended since dropper resistor R1 dissipates some heat. The metal box must be earthed as a matter of safe practice.

Arrange the components, transformer, mains switch, loudspeaker, circuit board and relay in the box as shown in Fig. 3 so that none are physically too close to each other, especially the mains transformer. Remember also to check the position so that there is no physical interference when the lid is on.

When this has been achieved make the cut-out in lid and then mount the transformer, sensor base holder, loudspeaker and switch in their respective positions. Wiring up the components should now be carried out as shown in Fig. 3.

The sensor can be mounted on the outside of the instrument box via the B7G holder as in the prototype or if a hand held probe is required for gas leak detection in confined areas, the B7G base can be mounted on a piece of wood with a handle. A wander lead will then connect this to the instrument box.

The voltage dropping resistor R1 is mounted on a piece of Veroboard on stand-off legs and then spaced from the instrument case. It is advisable to keep this well away from the rest of the electronics to minimise any thermal effects.

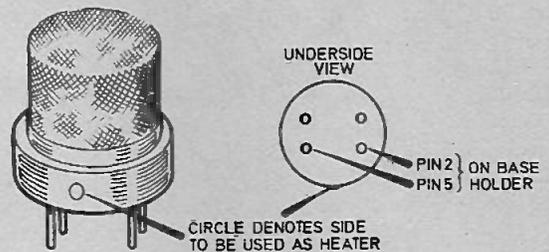



Fig. 4. Details of the sensor.

TESTING AND OPERATION

Before plugging into the mains for testing, check that the wiring is correct. If satisfied insert the sensor in the B7G valve base remembering that the heater side of the sensor is marked with a circle on the outside metal edge, see Fig. 4. Switch on the mains and check the voltage across the sensor heater and d.c. rail is correct, 1V and 8V respectively.

The circuit will go into the alarm condition for some several minutes as the sensor warms up. After a time, the alarm will come off, and the sensor will reach equilibrium.

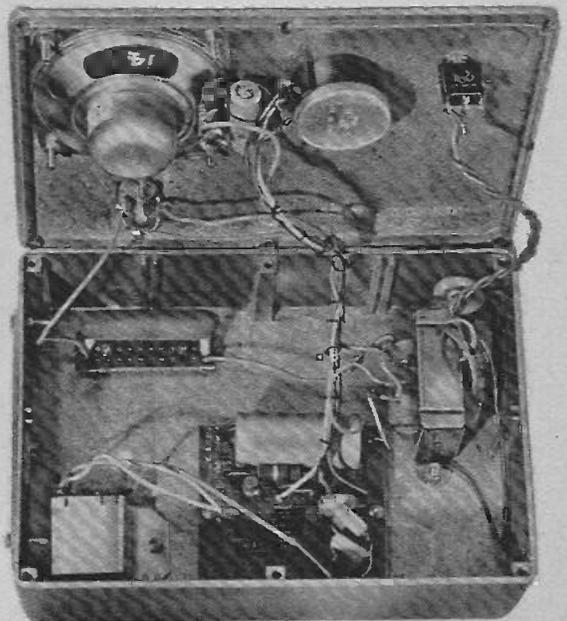Rotate the set level potentiometer VR1 until the alarm just comes off. This point is the position of maximum sensitivity and will easily de-



Photograph of the completed prototype with lid removed.

fect most combustible gases at a concentration of 0.2 per cent in air at this point.

One of the benefits of half-wave rectification for the illustrated circuit is that the voltage supply is load dependent to a small extent. This means that at the switching point of IC1, the 8 volt d.c rail voltage drops due to the increased current through the relay. This occurs when the gas concentration is sufficient to produce a voltage from the sensor which just drops below that set by potentiometer VR1, thus actuating IC1. The increase in load current causes a decrease in rail voltage which will give a voltage from the sensor above the voltage set by VR1, thus switching IC1 output to the earth rail. This is because of the unequal resistor ratios to earth at the inputs inside IC1 and the charging rate of C2.

The result is that a gas concentration which causes IC1 just to switch, will give a pulsed tone alarm on the loudspeaker. At concentrations above this the output will be a continuous tone.

The pulsed output occurs when the set level voltage on VR1 is up to one volt above the sensor output voltage and the output from the sensor changes to just below this. This means in practice, that two alarm conditions occur:

- (1) Pulsed tone when the gas concentration is approximately equal to that set by the potentiometer VR1.
- (2) Continuous tone when the gas concentration is well passed this point.

The uses of the Gas Alarm are only limited by imagination or the requirements of the user, but applications such as gas pilot light failure alarm, carbon monoxide levels in garages, leak testing on domestic, camping and boating equipment, fire alarms and smoke detectors spring to mind. Some care should be taken on the installation of the alarm to give the maximum benefit. If denser gases than air are being monitored, the sensor should be placed below the possible leak source, for less dense gases, it should be placed above. □



...Counter Intelligence

BY PAUL YOUNG

A retailer discusses component supply matters.

LAST month I had few words to say regarding ordering components by mail. It may be useful for newcomers to recap as follows:

- (1) Put on your order only the items your dealer lists.
- (2) If your dealer is out of stock of an item he lists, ask him for his forecast of delivery (and please bear in mind he can only pass on the information given to him, which is often inaccurate) and don't re-order until you have made sure (by phone or letter) that the item is now in stock.
- (3) Remember, with the best will in the world it may take 10-14 days to get your parcel. A letter can take four days, a parcel (2nd class) five days. So if you allow your dealer a two day turn round (quite fast) there will be at least one intervening weekend, and there are 13 days gone!

I would certainly advise you to plan your wants ahead. Difficult I know, but if you start ordering the parts for your next project while you are still working on

your current one, with any luck you will have everything to hand for your next piece of construction, by the time the present one is finished!

Stock

Naturally, if you are starting from scratch, you will have no stock of anything, but you will undoubtedly build it up as you go along.

One item that you will certainly be using all the time, is the ordinary $\frac{1}{4}$ watt ± 5 per cent or ± 10 per cent resistor. Every constructional article usually lists several of them. Some firms offer handy packs, giving a useful range with 5 or 10 of each value, and showing a substantial saving in price.

I think the same idea could be adopted for capacitors, of all types: ceramic, silver mica, paper, polyester and electrolytics, especially as so many projects are transistorised, and this usually means that a capacitor of 35 volts working is more than adequate. However, I don't wish to mislead you, because except for bargain parcels (where you take pot luck on the contents)

I don't think anything like this at present is available.

Bargain Packs

By the way, don't think I am knocking bargain packs. They are often excellent value, and even if there are only two or three capacitors you require you will more than re-coup your outlay. I will tell you an amusing instance of this.

A small shop had a mixed lot of widely assorted capacitors, so they made them up in plastic bags and offered them at 25p a bag. The sales were steady but not exciting. Then one day customers flocked in from far and wide, some even buying 12 bags at a time until the stock was all sold.

I heard the explanation from an "amateur" friend of mine. It appears a "Ham" went into the shop one day, and bought a pack. Among the contents he found a small ceramic capacitor, several kilovolts working which normally would have cost him £3! In the mysterious way these chaps work, he managed to pass the glad news (over the air I presume) to all and sundry, without breaking the Law.

Reverting to my original topic of stock you can hold, this about covers it. Except for the usual hardware ((nuts and bolts) most other requirements are so individual that they must be bought with a project in mind.

DOWN TO EARTH

By GEORGE HYLTON

"What is the significance of 'ohms per volt' as applied to voltmeters?"

One of the aims of this column is to keep out the demon mathematics, as far as possible. If I have to let him in, it's usually towards the end of an article, and in as painless a form as possible. But in the present case, simple mathematics (Ohm's law style) plus a little low cunning cracks the problem wide open. So let's take the bull by the horns and get it over with.

DIVISION

"Ohms per volt." What does the "per" mean? When I was at school, the more long-suffering of my maths teachers used to explain that words can sometimes be translated into instructions. Thus "of" can mean "multiply", "and" can mean "add", and "per" can mean "divide by". So "ohms per volt" might mean "ohms divided by volts".

In the case of a voltmeter, "ohms" refers to the resistance of the meter, on a particular range, and "volts" to the full-scale voltage on that range.

Do I hear cries of objection? You can't divide ohms by volts, because they are two different things. ("Divide a loaf by a knife!" said the White Queen.) Rubbish! We think nothing of dividing volts by ohms, to get current ($I=V/R$), so why not ohms by volts? In engineering, you can divide anything by anything, if it suits your purpose. The only snag, in the present case, is that the result doesn't seem to mean anything.

We all know that when you divide volts by ohms the answer comes out in amps. But ohms by volts...? There ain't no such animal. At this point, while we're thinking it over, we'll do our bit of mathematics. It's straightforward. Take our mysterious quantity R/V and substitute for R its Ohm's law equivalent, V/I .

You then find that "ohms per volt", or R/V , is the same as $1/I$. Worse and worse, you say, R/V was bad enough, but what on earth is this strange, nameless quantity, $1/I$?

THE SMITH

Let's give it a name, then we'll feel better. Let $1/I$ be measured and counted in named units from this time forward. Any name will do, but since electrical units are named after famous physicists and suchlike people we'll call this one the smith. (With a small 's', of course, because this is what you do to the people when you turn them into units. Since they are invariably dead long before it happens they can't offer any objections to this indignity.)

Why "smith"? Well, there must have been some electrical pioneer called Smith at some time or other.

So, $S=1/I$. Much tidier. But what, after all this, does the smith actually measure? A fair question. Whatever it is, you can see, by putting in some real values of I , that as the full-scale current of the voltmeter increases the number of S 's decreases. If meter A is 1 milliamp full-scale and meter B 10 milliamp, then meter A has 10 times the S value of B.

I suspect that for some readers the penny will now have dropped, so I'll put the rest out of their misery by suggesting that the smaller the current drawn by a meter from the circuit under test, for equal deflections of the pointer, of course, the greater the sensitivity of the meter; S is the unit of sensitivity. (By a fortunate coincidence, as you'll have noticed, "smith" and "sensitivity" begin with the same letter!)

WHY?

Why use this curious "ohms per

volt" quantity instead of simply quoting the current required to deflect the pointer to full scale? You may well ask. Just tradition, perhaps. There is one possible reason, though. "Ohms per volt" tells you fairly directly what the resistance of a voltmeter is on any particular range, and this is often what you need to know when making measurements with it.

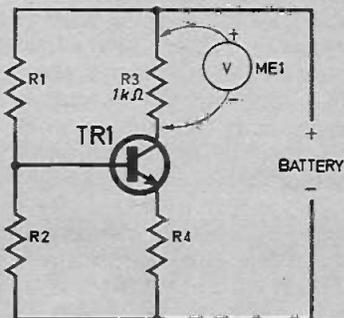


Fig. 1. Connecting ME1 as shown diverts current through R3.

Suppose you need to measure the drop across the 1 kilohm resistance in the circuit of Fig. 1. The voltmeter diverts some of the current which would normally flow through the resistor and so gives a false reading. How false? Well, obviously, the more current diverted by the meter the less accurate the readings.

To divert only a little current, the meter should have a resistance much greater than the resistance across which it's connected. Let's put some numbers in. Suppose the voltage in question is expected to be 1V. If the meter has a sensitivity of 1 kilohm per volt then in this case half the current is diverted through the meter and it reads 50 per cent low.

If you are stuck with $1k\Omega/V$, the best thing to do is to switch to the 10V range. The pointer won't be deflected very far (only one-tenth scale) but the meter cannot now divert more than 10 per cent of the current (actually not more than 9 per cent, if you work it out carefully) so the voltage indication is much more accurate, though harder to read because of the smaller deflection.

Armed with the "ohms per volt" figure for your meter, a quick bit of mental arithmetic tells you whether you are likely to be able to get a meaningful indication of voltage in a particular circuit.



THREE BY THREE GAME

BY GEORGE FRANCIS

A simple game for two players or a special "dice" for other games

THIS is a battery operated board game for two players, which can be used as a dice with other games or for several different games of skill. As well as trying to control the game for his own immediate and obvious advantage, the player needs to try to anticipate his opponent's probable play, as in certain Chinese games.

CIRCUIT

The complete circuit is shown in Fig. 1. The game board itself has nine small lamps, LP1 to LP9. One player has the three control push switches S1, S2 and S3, while the other player operates the push switches S4, S5 and S6. Each control switch assembly is attached to a flexible multi-way cord, and is held on the knees or under the table so that the opponent cannot see which push switch is operated.


CIRCUIT OPERATION

If player X pressed switch S1, he selects the row of lamps LP1, LP2 and LP3. Should he press switch S2, the selection is for lamps LP4, LP5 and LP6, while S3 similarly selects LP7, LP8 and LP9.

Player Y can choose the row of lamps LP1, LP4 and LP7 by pressing S4, or the row LP2, LP5 and LP8 by S5, or the lamps LP3, LP6 and LP9 by pressing switch S6.

Though each player has to make his selection, no lamps light until *both* players have pressed one switch, and it is then too late to change or retract this "move." While deciding on each move, each player thus has to decide on the probability of securing an advantage from his own selection, however it may be modified by the selection of the other player, who will in the same way be trying to secure his own advantage.

Fig. 1. Circuit diagram of the Three By Three Game.

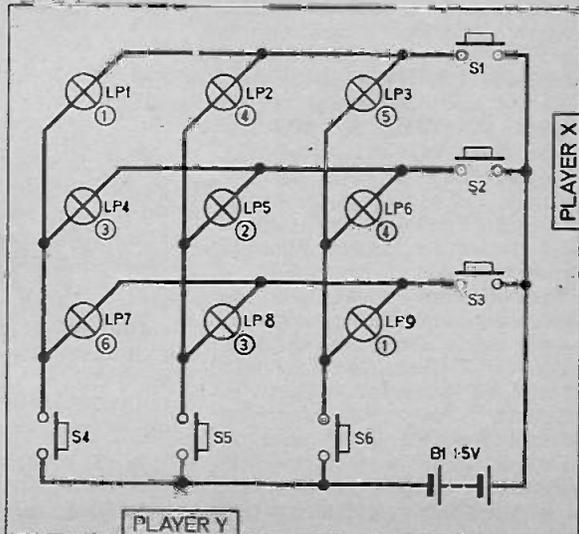



**Approximate cost
of components
including V.A.T.
£2.10 plus case**

Components

SEE
**SHOP
TALK**

Lamps

LP1-9 2.5V 0.3A m.e.s. (9 off)

Switches

S1-6 s.p.s.t. push to make, release to break small push buttons (6 off)

Miscellaneous

B1 1.5V HP2 or similar battery, metal clip and angle bracket for battery fixing, batten mounting lamp holders for LP1-9 (9 off), screws for fixing holders, connecting wire, materials for game board and two switch mounting boxes (see text).

The same board can be used for several games, and suggested rules for these are given later.

From Fig. 1 it will be seen that the full battery voltage is applied to only one lamp, according to the selection made. As an example, if S1 and S5 are closed, LP2 lights, while should S3 and S4 be closed, LP7 lights. At the same time, it is possible to trace out other circuit paths when player X and player Y have each closed a switch. However, these other paths through the lamps result in various series and parallel combinations, so that no lamp except the one actually chosen lights properly.

Provided all the bulbs are of the same type—2.5V 0.3A torch bulbs are suitable—only one lamp will light correctly, while others are so dim that there is never any doubt as to the indication which is to be followed.

GAME BOARD

The board was made approximately 280mm square to leave plenty of room for games. Batten mounting lamp holders are used for the lamps, these are mounted on the bottom panel which is about 45mm below the top. Nine 12mm diameter holes are made in the top panel to enable the bulbs to be seen. This allows each bulb to be fitted as in Fig. 2.

The base board is wired up as shown in Fig. 2. A hole is drilled at the centre of two adjacent sides, for the flexible leads to the switches.

SWITCH ASSEMBLIES

The switches are of an inexpensive type which make contact only when held down. Each board is about 90×45×13mm thick, and is recessed 75×25×8mm to take the switches, Fig. 2.

Each lead is made from four lengths of thin flex, about one metre long. Connect the wires as in Fig. 2. It is helpful to use a different colour to identify the common battery lead to all three switches. The other leads could be of

different colours, but it easy to identify these by temporarily connecting a bulb and battery. Take the leads to the board, and connect them correctly, so that the relative positions of switches and the circuits they complete are the same as in Fig. 1.

A 1.5 volt battery was found most suitable with 2.5V bulbs, and as current is only drawn for short periods a reasonably large cell will last a long time.

The top of the board is divided into nine squares, either by drawing lines, or by drawing on a sheet of reasonably thin paper and placing this on the board. Perspex or other transparent material can be put on top, for protection.

Alternative means of construction would give the same results. This includes mounting the switches in shallow metal or plastic boxes or cases.


GAMES

For each "move" of any game, both players must press one button. Moves or scores are taken alternately. Each player tries to make his own turns convey the best advantage to himself, but tries to make his opponent's turns unsuccessful, or to provide the least favourable probabilities.

The board can be added to some existing games, or can be used in conjunction with the counters or pieces of other games. With existing games, the rules can be taken from them. The following will help indicate typical methods of play.

DICE

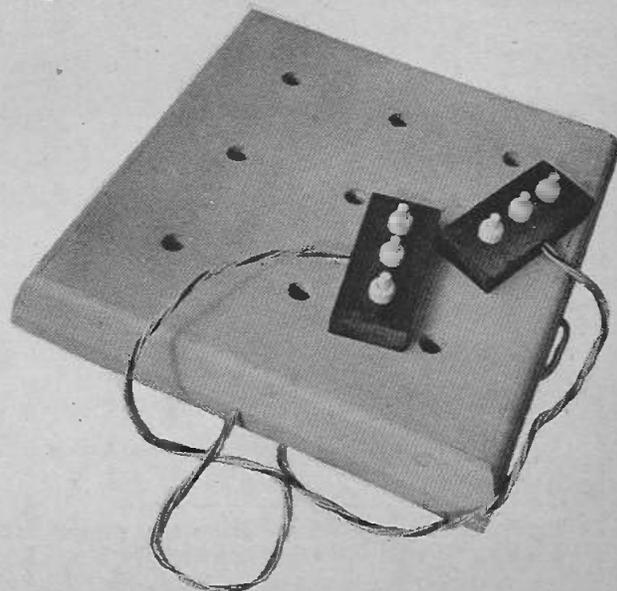If the board is used to replace a dice, introducing an extra element of skill. Mark the board as shown or put numbered counters in the positions as indicated by the numbers in circles in Figs. 1 and 2. Players read a number alter-



THREE BY THREE GAME

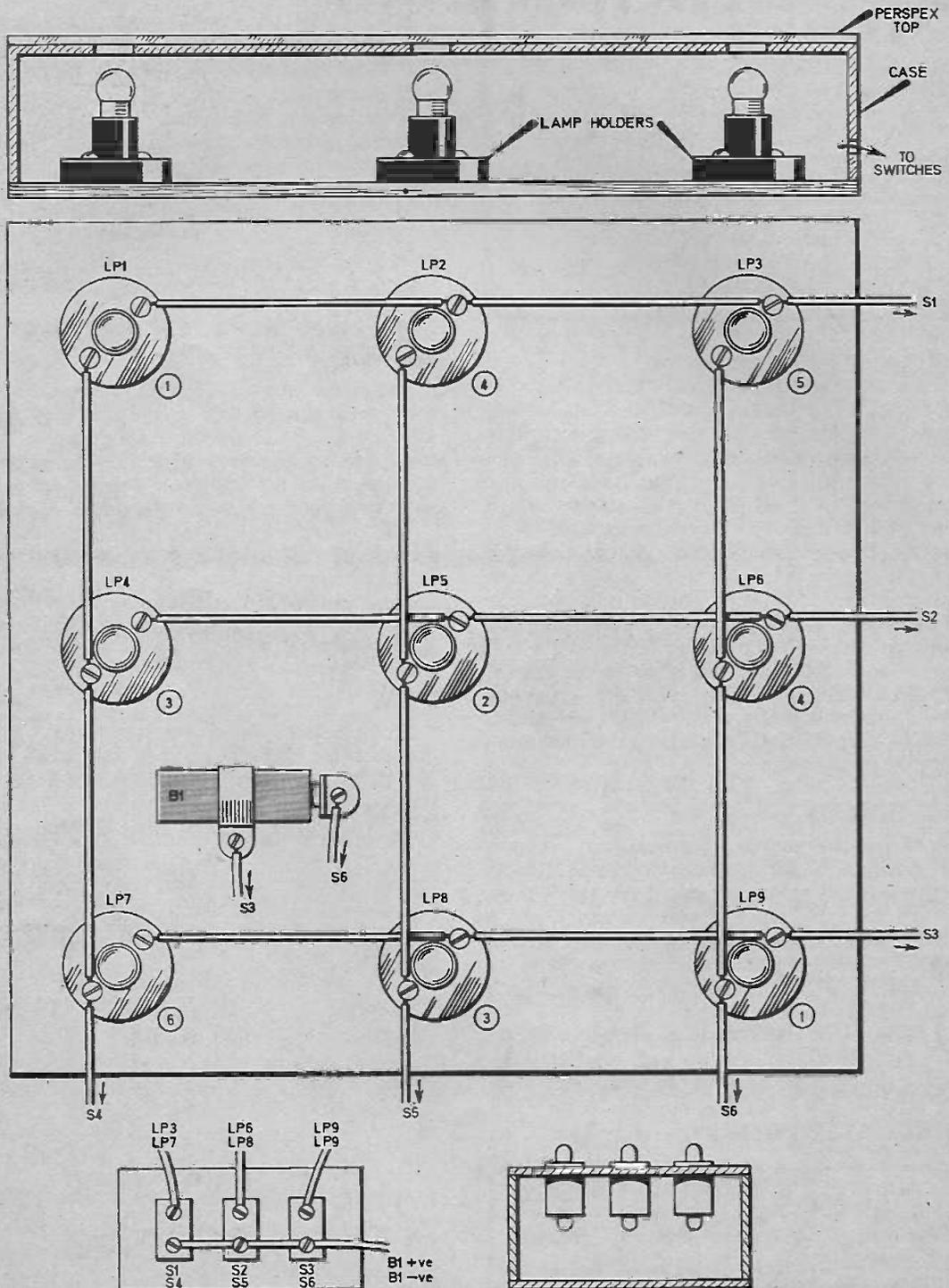


Fig. 2. Wiring of the base board and switch boxes. Two switch boxes are required, one housing S1, 2 and 3 with the other housing S4, 5 and 6.

VISCOUNT III— a boost in the output

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as value for money! And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! And the teak finish will harmonise and enhance virtually any style of interior decor! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back.

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have never experienced before! Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!


SPEAKERS: Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair + £2.20 p. & p. Duo Type III Size approx. 23½in x 11½in x 9½in. Drive unit approx. 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM 1
Viscount III R102 amplifier £24.20 + £1 p & p
2 Duo Type II speakers £14.00 + £2.20 p & p
Garrard SP25 Mk III with MAG. cartridge /plinth & cover £18.00 + £1.75 p & p
Total £56.20

Available complete for only **£49.00** + £3.50 p & p

PRICES: SYSTEM 2
Viscount R102 amplifier £24.20 + £1 p & p
2 Duo Type III speakers £32.00 + £3.30 p & p
Garrard SP25 Mk III with MAG. cartridge /plinth & cover £18.00 + £1.75 p & p
Total £74.20

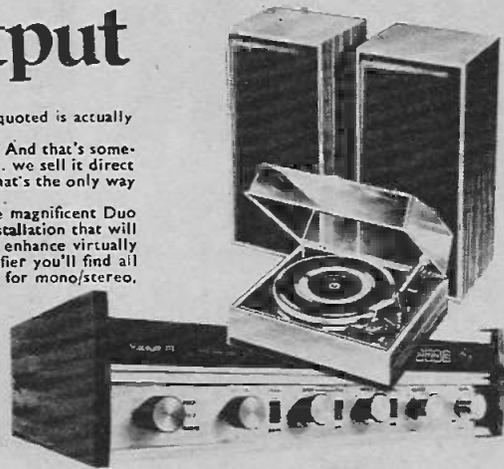Available complete for **£65.00** + £4 p & p



STILL ONLY £49 COMPLETE

THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms. Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire. The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep. Circuit diagram and comprehensive instructions 55p free with parts. Fully retractable and lockable car aerial £1.37 post paid.

CAR RADIO KIT £6.60 p. and p. 55p. Speaker with baffle and fixing strips £1.65, + 23p p. & p. post free if bought with the kit. Send stamped addressed envelope for leaflet.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

PE TAPE LINK CONSTRUCTORS




Suitable 3 speed tape deck, less heads. Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty.

£1 p. & p. **£4.00**



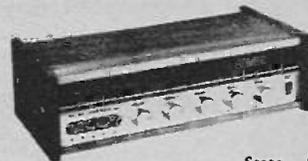RADIO AND TV COMPONENTS (ACTON) LTD. Dept. E 21 HIGH STREET, ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2



RELIANT Mk IV MONO AMPLIFIER


- *5 Electrically Mixed inputs.
- *3 Individual Mixing controls.
- *Separate bass and treble controls common to all 5 inputs.
- *Mixer employing F.E.T. (Field Effect Transistors).
- *Solid State Circuitry.
- *Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 1250mV sensitivity. Output 20 watts into 8 Ω (suitable for 15 Ω.) Size approx. 12½ x 6 x 3½ ins. **£13.50** p. & p. 60p

UNISOUND MODULES

ONLY £7.64 + 55p. p & p

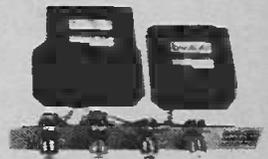For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. The Viscount III, the



fabulous Stereo 21 and the Unisound Modules **£10.60** + 80p. p. & p. will accept this unit, simply connect up.



Just write your order giving your Credit Card Number. Do not send your card.




Edgware: 9 a.m. to 5.30 p.m., half day Thurs.
Acton: 9.30 a.m. to 5 p.m. Closed all day Wed.

Mail order to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope
Goods not despatched outside U.K.

look! electronics really mastered

... practical
... visual
... exciting!

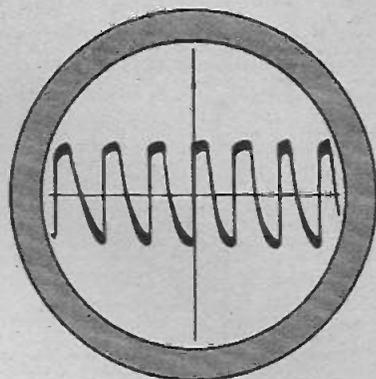no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

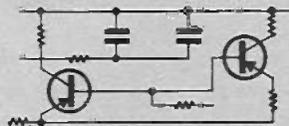2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments, amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EEL 11 3

special free gift also to all our students

nately, and for themselves select a row giving most favourable chance, while an opponent tries to make the indication least favourable. This can introduce the need for forethought, even with simple games such as snakes and ladders.

OTHER GAMES

It will be found that other games can be devised without too much difficulty. When doing so, check that one player cannot halt further play by always choosing a particular row. In some games this can be arranged by having a penalty for choosing such a row.

The following are among those which can be tried:

- (1) **Required:** Two sets of counters or flags numbered 1-20.

Each player places any 9 counters, one on a square, where he wishes. Each takes opponents alternately. A counter is put on to replace each taken. When none are in hand, the higher score taken wins.

- (2) **Required:** Two sets of small scale soldiers of different colour, or cowboys and indians, 15 for each player.

All the "men" placed on the board. Each player takes an outnumbered opponent on a lit square, and can move one piece to an adjacent square between operation of switches. Not more than four "men" may occupy any one square.

- (3) **Required:** As for (2) but of varying potential: e.g. foot soldiers; machine gunners, small scale vehicles, etc.

Play as before but more powerful piece takes opponent's smaller piece. ■

PLEASE TAKE NOTE

In Table I of the *Tutor Board* article, page 533 the wire lengths should be in cm *not* mm.

It should be noted that not all switches have the same operating position as that described in *Teach-In '74* page 538 last month. Some types, particularly miniature ones operate in the reverse direction.

Under the heading *What Do You Know?*, the formula for calculating the total resistance of resistors in parallel should have been

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \dots$$

we apologise for this fundamental error.

NEXT MONTH

BABY SNATCH ALARM



Unfortunately, the instances of babies being taken from prams or push chairs left outside shops are all too common these days. Next month we publish a circuit and constructional information for an alarm to prevent this unhappy occurrence.

The alarm is basically simple, easy to use, quite cheap to build and can be quickly fitted to almost any pram or push chair without any contact to the baby.

AUTO-WATER FOR PLANTS

Make sure your plants do not die of thirst when left unattended.

TREMOLO UNIT

For the "modern" guitarist or organist.

All in the December

**everyday
electronics**

On Sale Friday, November 16

..SPECIAL OFFER! A HIGH QUALITY TOOL KIT AT A SPECIAL PRICE

£2.99

The tools in the roll are as follows:

- 1 pair 5½ inch "telephone" pliers
- 1 pair 4 inch side cutters
- 1 4-inch insulated screw driver
- 1 2-inch mains tester (100 to 500 V) screw-driver

Please complete both parts of the coupon below
Allow 28 days for delivery



To: EVERYDAY ELECTRONICS
DEPT. E.E.1. ROCHESTER X
KENT, ME99 1AA

Please send me the Tool Kit(s) as indicated at
£2.99 per kit.

I enclose cheque/P.O. No.
Value

No. OF KITS REQUIRED

NAME
ADDRESS

Tel. No.

No. OF KITS REQUIRED

NAME
ADDRESS

From: EVERYDAY ELECTRONICS
DEPT. E.E.1., ROCHESTER X, KENT
ME99 1AA

(Please cut around dotted line)

To help new readers and established constructors, the staff of E.E. in conjunction with a leading supplier of tools, have put together four tools of high quality that form the basis of any constructor's tool kit. The tools are not cheap but, together with a strong, woven, greaseproof nylon "roll" are offered to readers at a saving of approximately 80p on the recommended retail price.

The kit would make an excellent Christmas present for anyone just starting electronic construction—but be sure to order in time to avoid disappointment.

Remittance must be by cheque or postal order (name and address on back of cheques please), crossed and made payable to IPC Magazines Ltd. This offer is open to readers in Northern Ireland, England, Scotland, Wales and Channel Islands only. It is not available in Eire or overseas.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY £1.05

POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 27½p

POST & PACKING 16p

TESTED AND GUARANTEED PAKS

B79	4	1N4007 Sil. Rec. diodes.	55p
		1,000 PIV lamp plastic	
B81	10	Reed Switches, 1" long, 1" dia. High Speed P.O. type	55p
B89	200	Mixed Capacitors. Approx. quantity, counted by weight	55p
		P & P 15p	
H46	250	Mixed Resistors. Approx. quantity counted by weight	55p
		P & P 15p	
H7	40	Wirewound Resistors. Mixed types and values	55p
H9	2	OCPT1 Light Sensitive Photo Transistor	55p
H38	20	OC2001/1/213 PNP Silicon uncoated TO-5 can	55p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8-43V.	55p
H33	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors. NPN Silicon Planar types	55p
H39	6	Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945	55p
H40	20	BFY50/2, 2N696, 2N1613 NPN Silicon uncoated TO-5	55p
H41	2	Sil Power transistors comp pair BD131/132	55p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	55p
H13	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each



OVER
1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Silicon planar plastic transistors. Unmarked, untested factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44 P. & P. 11p/1,000.

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" NPN Silicon alloy, TO-5 can.

TYPE "B" PNP Silicon, plastic encapsulation.

TYPE "E" NPN Germanium AF or RF.

TYPE "F" NPN Silicon plastic encapsulation.

TYPE "G" NPN Silicon similar ZTX 300 range

TYPE "H" PNP Silicon similar ZTX 500 range

8 RELAYS FOR VARIOUS TYPES £1.10

P & P 27½

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors. Please ask for Pak P.1. Only 55p. 11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television.

This complete kit of parts costs £3.85, post paid.

A MUST for Colour T.V. Alignment.

ELECTRONIC TRANSISTOR IGNITION

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features:-

Transistor and conventional switchability, burglar proof lock up and automatic alarm, negative and positive compatibility. This project is a "star" feature in the September edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine.

Complete kit including p & p £7.92

Ready built and tested unit £3.02 extra.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

PLASTIC POWER TRANSISTORS

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE, Min 15. HFE Min 15.

40 Watt 1-12 13-25 26-50

90 Watt 26p 24p 23p

Range 2. VCE, Min 40. HFE Min 40.

40 Watt 1-12 13-25 26-50

90 Watt 33p 31p 29p

Complementary pairs matched for gain at 3 amps.

11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of i.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16p each } Now new low profile
16 pin type at 18p each } type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I Transistor Equivalents and Substitutes; 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.

The Iliffe Radio Valve & Transistor Data Book 9th Edition; p. & p. 23p. 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications
N.B. Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue

NAME.....

ADDRESS.....

ALL PRICES INCLUDE 10% VAT
MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE Add 11p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE
BUY THESE GOODS WITH ACCESS.

BI-PRE-PAK LTD
CO. REG. No. 820919

DEPT. B, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF
TELEPHONE: SOUTHEND (0702) 46344

TRANNIES

1 Dockyard, Station Rd.,
Old Harlow, Essex.

Telephone: 37739
(Saturday callers welcome)
Add 10p PIP Catalogue 10p.

74 Series TTL (National Semiconductors and I.T.T.) LOW PRICES, HIGH QUALITY

7400	17p	25	7450	17p	15p	74141	71p	68p
7401	17p	15p	7451	17p	15p	74145	£1.30	£1.40
7402	17p	15p	7453	17p	15p	74150	£3.00	£2.69
7403	17p	15p	7454	17p	15p	74151	£1.00	97p
7404	17p	15p	7460	17p	15p	74153	£1.20	£1.12
7405	17p	15p	7470	29p	26p	74154	£1.80	£1.71
7406	38p	32p	7472	29p	26p	74155	£1.40	£1.30
7407	38p	32p	7473	38p	35p	74156	£1.40	£1.30
7408	18p	17p	7474	38p	35p	74157	£1.00	£1.81
7409	18p	17p	7475	46p	45p	74160	£1.80	£1.71
7410	18p	14p	7476	46p	39p	74162	£4.00	£3.76
7411	24p	19p	7480	88p	83p	74163	£4.00	£3.76
7412	30p	25p	7481	£1.20	£1.15	74164	£2.20	£2.16
7413	28p	27p	7482	88p	87p	74166	£2.28	£2.22
7416	44p	40p	7483	£1.11	£1.07	74175	£1.88	£1.55
7417	44p	40p	7484	£1.01	96p	74176	£2.55	£2.44
7420	16p	14p	7485	32p	31p	74177	£2.55	£2.44
7423	50p	48p	7486	£4.49	£4.24	74180	£2.05	£1.66
7425	50p	48p	7489	58p	45p	74181	£5.55	£5.10
7426	46p	42p	7490	58p	45p	74182	£2.05	£1.83
7427	46p	42p	7491	58p	45p	74184	£3.55	£3.23
7428	70p	65p	7492	68p	65p	74190	£2.00	£1.84
7430	18p	14p	7493	68p	65p	74191	£1.92	£1.87
7432	41p	42p	7494	78p	75p	74192	£2.00	£1.84
7433	80p	76p	7495	78p	75p	74193	£2.77	£2.66
7437	68p	62p	7496	88p	85p	74195	£2.05	£1.66
7438	68p	62p	74100	£1.65	£1.60	74196	£1.88	£1.75
7440	18p	14p	74101	97p	85p	74197	£1.88	£1.75
7441	68p	62p	74107	41p	39p	74198	£1.53	£1.50
7442	68p	62p	74108	41p	39p	74199	£5.55	£5.10
7443	£1.30	£1.25	74110	56p	54p			
7444	£1.30	£1.25	74111	£1.25	£1.18			
7445	£1.80	£1.76	74112	£1.00	95p			
7446	97p	94p	74113	£1.40	£1.30			
7447	97p	84p	74114	£1.40	£1.30			
7448	£1.00	97p	74123	£2.78	£2.67			

All Prices
FULLY
INCLUSIVE
of VAT

AMTRON KITS

We have been appointed stockists of
Amtron high quality Construction Kits.
(20p P.P. on all kits).

- Other Kits include:
- UK05 Transistor tester £2.50
 - UK10 Stereo Amplifier 5 + 5w £11.07
 - UK120 Hi-Fi Amplifier 12w £5.20
 - UK220 Signal Injector £2.57
 - UK235 Acoustic Alarm for Absent minded drivers £8.39
 - UK300 Four channel radio control transmitter £6.55
 - UK310 Radio control Receiver £3.28
 - UK325 'GCX2' channel splitting unit 1000 and 2000 Hz £7.88
 - UK330 'GCX2' channel splitting unit 1500 and 2500 Hz £7.88
 - UK345 Superhetrodyne radio control receiver £7.58
 - UK515 mW Radio Receiver £7.88
 - UK525 VHF Tuner 120 to 160 MHz £12.44
 - UK705 Windscreen Wiper timer £7.48
 - UK715 Photoelectric cell switch £8.49
 - UK760 Acoustic switch £11.85
 - UK875 Capacitive Discharge Electronic Ignition for internal combustion engines £14.51
 - TR100 24 hour Electronic Digital Clock £22.50

Many other kits available. Send for the Amtron Catalogue.

*THESE KIT PRICES INCLUDE V.A.T.

VEROBOARD		0-1	0-15
2 1/2 x 3 1/2		24p	19p
3 1/2 x 5		27p	23p
3 1/2 x 3 1/2		27p	23p
3 1/2 x 5		31p	23p
17 x 1 1/2		32p	23p
17 x 5 (Plain)		£1.10	87p
Pin insertion tool		57p	90p
Spot face cutter		46p	67p
Pk 36 Pins		20p	20p

Silicon Rectifiers lamp miniature

Type	PIV	1-99
IN4001	50	50p
IN4002	100	50p
IN4003	40p	6p
IN4004	400	61p
IN4005	600	74p
IN4006	800	10p
IN4007	1000	10p

MINITRON DIGITAL INDICATOR TYPE 3015F

Read 0-9 and decimal. ONLY £1.65

400mW ZENER DIODES

BZY88 Series 3-3 volt to 33 volt.

1-99	100 plus
7p	6p

Transistors/ Diodes	BC109	9p	BC805	50p	MP8121	33p	TIP81A	64p	Diodes & Rectifiers
AC107	16p	BC113	15p	MP8122	44p	TIP32A	78p	1N914	8p
AC126	14p	BC116	16p	MP8123	50p	TIP33	£1.05	1N916	8p
AC127	13p	BC125	16p	NK7211	28p	TIP34A	£1.54	1N4148	8p
AC128	13p	BC126	25p	NK7212	25p	TIP35A	£2.58	1S44	10p
AC142K	20p	BC134	18p	NK7215	25p	TIP36A	£3.19	1N4007	22p
AC141K	20p	BC135	16p	NK7216	25p	TIP41A	79p	BA192	25p
AC176	16p	BC137	16p	NK7217	25p	TIP42A	81p	BA121	11p
AC187	18p	BC138	36p	NK7218	25p	TIP43A	81p	AA123	11p
AC187K	18p	BC142	36p	NK7219	25p	TIP44A	81p	AA125	14p
AC198	18p	BC144	30p	NK7220	25p	TIP45A	81p	AA127	14p
AC198K	20p	BC145	26p	NK7221	25p	TIP46A	81p	AA129	14p
AC171	24p	BC147	9p	NK7222	25p	TIP47A	81p	AA130	14p
AC178	21p	BC148	9p	NK7223	25p	TIP48A	81p	AA131	14p
AC179	25p	BC149	9p	NK7224	25p	TIP49A	81p	AA132	14p
AC179K	25p	BC153	16p	NK7225	25p	TIP50A	81p	AA133	14p
AC172	23p	BC154	17p	NK7226	25p	TIP51A	81p	AA134	14p
AC172K	23p	BC157	18p	NK7227	25p	TIP52A	81p	AA135	14p
AC139	68p	BC158	12p	NK7228	25p	TIP53A	81p	AA136	14p
AD140	40p	BC169	14p	NK7229	25p	TIP54A	81p	AA137	14p
AD142	44p	BC167	13p	NK7230	25p	TIP55A	81p	AA138	14p
AD145	39p	BC168	11p	NK7231	25p	TIP56A	81p	AA139	14p
AD146	39p	BC169	8p	NK7232	25p	TIP57A	81p	AA140	14p
AD150	60p	BC177	15p	NK7233	25p	TIP58A	81p	AA141	14p
AD161	29p	BC179	15p	NK7234	25p	TIP59A	81p	AA142	14p
AD162	29p	BC182L	11p	NK7235	25p	TIP60A	81p	AA143	14p
AF114	18p	BC183L	11p	NK7236	25p	TIP61A	81p	AA144	14p
AF116	18p	BC184L	11p	NK7237	25p	TIP62A	81p	AA145	14p
AF117	18p	BC185	8p	NK7238	25p	TIP63A	81p	AA146	14p
AF117	18p	BC212L	11p	NK7239	25p	TIP64A	81p	AA147	14p
AF118	92p	BC213L	11p	NK7240	25p	TIP65A	81p	AA148	14p
AF124	27p	BC214L	11p	NK7241	25p	TIP66A	81p	AA149	14p
AF129	39p	BC258	9p	NK7242	25p	TIP67A	81p	AA150	14p
AL102	77p	BC257	14p	NK7243	25p	TIP68A	81p	AA151	14p
AL103	55p	BC268	15p	NK7244	25p	TIP69A	81p	AA152	14p
BC107	9p	BC265	15p	NK7245	25p	TIP70A	81p	AA153	14p
BC108	9p	BC269	9p	NK7246	25p	TIP71A	81p	AA154	14p
		BC270	8p	NK7247	25p	TIP72A	81p	AA155	14p
		BC271	8p	NK7248	25p	TIP73A	81p	AA156	14p
		BC272	14p	NK7249	25p	TIP74A	81p	AA157	14p
		BC273	14p	NK7250	25p	TIP75A	81p	AA158	14p
		BC274	14p	NK7251	25p	TIP76A	81p	AA159	14p
		BC275	14p	NK7252	25p	TIP77A	81p	AA160	14p
		BC276	14p	NK7253	25p	TIP78A	81p	AA161	14p
		BC277	14p	NK7254	25p	TIP79A	81p	AA162	14p
		BC278	14p	NK7255	25p	TIP80A	81p	AA163	14p
		BC279	14p	NK7256	25p	TIP81A	81p	AA164	14p
		BC280	14p	NK7257	25p	TIP82A	81p	AA165	14p
		BC281	14p	NK7258	25p	TIP83A	81p	AA166	14p
		BC282	14p	NK7259	25p	TIP84A	81p	AA167	14p
		BC283	14p	NK7260	25p	TIP85A	81p	AA168	14p
		BC284	14p	NK7261	25p	TIP86A	81p	AA169	14p
		BC285	14p	NK7262	25p	TIP87A	81p	AA170	14p
		BC286	14p	NK7263	25p	TIP88A	81p	AA171	14p
		BC287	14p	NK7264	25p	TIP89A	81p	AA172	14p
		BC288	14p	NK7265	25p	TIP90A	81p	AA173	14p
		BC289	14p	NK7266	25p	TIP91A	81p	AA174	14p
		BC290	14p	NK7267	25p	TIP92A	81p	AA175	14p
		BC291	14p	NK7268	25p	TIP93A	81p	AA176	14p
		BC292	14p	NK7269	25p	TIP94A	81p	AA177	14p
		BC293	14p	NK7270	25p	TIP95A	81p	AA178	14p
		BC294	14p	NK7271	25p	TIP96A	81p	AA179	14p
		BC295	14p	NK7272	25p	TIP97A	81p	AA180	14p
		BC296	14p	NK7273	25p	TIP98A	81p	AA181	14p
		BC297	14p	NK7274	25p	TIP99A	81p	AA182	14p
		BC298	14p	NK7275	25p	TIP100A	81p	AA183	14p
		BC299	14p	NK7276	25p	TIP101A	81p	AA184	14p
		BC300	14p	NK7277	25p	TIP102A	81p	AA185	14p
		BC301	14p	NK7278	25p	TIP103A	81p	AA186	14p
		BC302	14p	NK7279	25p	TIP104A	81p	AA187	14p
		BC303	14p	NK7280	25p	TIP105A	81p	AA188	14p
		BC304	14p	NK7281	25p	TIP106A	81p	AA189	14p
		BC305	14p	NK7282	25p	TIP107A	81p		

Ruminations

By Sensor

Picking Over

A reader in Norfolk wrote in to E.E. with a query about possible radiation hazards from imploded cathode ray tubes. As far as I know there are no such dangers since radiation cannot be stored by the tube materials and no radiation-emitting substances are used in the construction. When tubes are working at high voltages X rays can be produced but these only present a danger when the tube is actually operating; even then, the shielding provided by the manufacturer of the television set is adequate to protect the viewer.

I know of a number of people who have picked up quite useful television and radio sets from the

local rubbish tip but before you all rush off to the dump a few words of warning. Probably the best times for hunting are Saturday evenings and Sunday afternoons when the local populace are home from work and are busy clearing out their rubbish. You will have to be prepared to dig amongst the grass cuttings, hedge trimmings, builders rubble and old mattresses.

The equipment that you may find might be quite useless depending upon how long it has been lying there as well as its condition when it was dumped. Avid collectors seem to acquire a nose for the art and talk like anglers of the one that got away, i.e. of the beautiful walnut console with doors that was taken by the council man in charge of the tip.

On official tips some councils do not permit items to be removed and it is worth finding out if this is the case in your area as this can save a good deal of embarrassment. One should of course be very careful to wash thoroughly after delving in to the tip because poisonous substances

are often disposed of in this way. So good hunting!

One Man's Meat

In one large engineering factory, I knew an old fitter who gave a lot of help to laboratory staff by building up prototypes and models for development projects. In his greasy cap and bib and brace overalls he regularly visited the factory scrap bins and carefully collected together any material that might be useful. His bench, being also his material store, occupied the working space of eight men and with his free access to all parts of the factory he was able to obtain almost anything without a stores requisition form.

From the vaguest of instructions he would manufacture quite complex pieces of equipment in a very short time. He was not a tidy worker but he had proved his worth many times over and was therefore permitted to have a quiet corner where he could get on with the job in his own individual fashion.



SHOP TALK

By Mike Kenward

It was very interesting to look through last month's adverts and see the various prices asked for the Tutor Board kit. We did not quote the firms an approximate cost—they simply advertised their own price. Luckily the prices quoted bore out our approximate cost in all but one case; the difference between the highest and lowest prices reinforces what we have always said

about shopping around for components before buying.

The prices quoted are of course for all the electronic parts for the first six months. There are a couple of components which are proving troublesome to supply—the MR45P meter and the precision wirewound pots, so if you receive substitutes for these don't be surprised.

Those of you who are now building or have built the Tutor Board should make sure all the components left over are carefully stored so that when they are required in the *Teach-In '74* series they are to hand and in good condition.

These components will also provide a useful stock when *Teach-In '74* comes to an end—in about 12 months. No soldering is used in the series and hence all the components will still be useful for other projects.

T.R.F. Receiver

There are one or two rather special components required for the *T.R.F. Receiver*; basically these components are all available from the larger stores but things like the Denco coils may be diffi-

cult to find in some areas.

The coils used in the receiver are available from some component shops or direct from Denco. They cost 48p each and 6p should be sent with each order to cover post and packing. Make sure you state clearly which coils are required when ordering. Incidentally, if demand is heavy there may be some delay in the supply of coils due to the shortage of polystyrene used for the formers. Write to Denco (Clacton) Ltd., 355/7/9 Old Road, Clacton on Sea, Essex CO15.

Make sure you get the plug-in types that can fit the B9A holder (this is a valve holder—valves are those glass things that light up in the backs of televisions!)

The MFC 4000B amplifier is available for 67p including VAT from Arrow Electronics Ltd., 7 Coptfold Road, Brentwood, Essex, postage is free.

The case used to house the prototype is available from H. L. Smith & Co. Ltd., 287-289 Edgware Road, London, W.2. (Note this is not G. W. Smiths). The Universal Chassis part, used to mount the dial, comes from Home Radio.

Gas Alarm

Yet another valve (see above) holder is used in the *Gas Alarm* this time a BTG type—it just goes to show that there was something good about valves! The gas sensor although quite a new device is now available from at least one advertiser in the issue.

The 741 IC is generally available in two types of case—the construction is designed around the 8 pin, dual in line type and construction will therefore be easier to follow if this type is purchased. The case for the pro-

totype was a die cast box, when painted these boxes make very tough, long lasting cases that are not unattractive.

Three By Three Game

An unusual, simple but quite interesting item, the *Three By Three Game* uses relatively few types of component, almost all of them being available from a local hardware store. The push buttons can be any cheap type and most shops keep some for less than 15p. Construction of the

case is not critical and plastic boxes could easily be used.

Cases

We are often asked where small plastic cases can be purchased and we have recently noticed that Home Radio can supply a range (5 sizes) which are very strong, "showerproof" and quite cheap—starting at 24p for size 82mm x 82mm x 35mm and rising to £1.03 for size 219mm x 168mm x 79mm.

ture dropped considerably before the owner realised what was happening.

I know cost is the prime importance, but why not wire in series with the heater a milliamp meter—suitably shunted to read heater current.

Mr. L. H. Cox,
Pevensey, Sussex.

As you say the cost of such a meter is quite high compared with the cost of the unit, and you would have to look at the monitor to know that the heater had failed, a thermometer in the tank would serve the same purpose.

Etching


Many thanks for a very interesting magazine.

I wish to construct the *Mini Organ* in the June 1973 issue. I have read the article on *Making P. C. Boards*, and found it very helpful, but have two questions I would like answered. Firstly, the quantity of ferric chloride solution quoted is for a board 3 inches x 2½ inches, as the copper clad board of the *Mini Organ* is considerably larger, is it correct to assume I increase the quantity of ferric chloride in direct proportion to the increase in size?

Secondly, after etching has been completed does the solution have to be thrown away or can it be used again?

Mr. A. Ellis,
Brighton, Sussex.

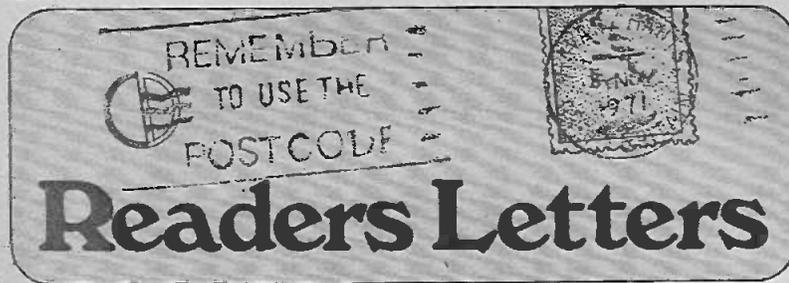The amount of solution required is only a rough estimate—it would be correct to increase the amount in proportion to the size of board. The solution may be used more than once but as it becomes saturated with copper the etching will take longer.



Storage

On the cover and on page 234 of your May 1973 issue, you show a photograph of a set of interlocking plastic drawers, with transparent trays.

Please would you tell me by whom these are manufactured, and their address; as I wish to purchase some, but cannot, as no shops around here seem to sell them.

Mr. J. C. Ohlsen,
Glenfield, Leicester.

The storage drawers you require are available from Ivoryet Ltd, Dept EE, 124 Cricklewood Broadway, London N.W.2. They are also available from R. S. Components and can be obtained from them, via your local radio and TV shop.

Crystal Set

The article in the July issue of *EVERYDAY ELECTRONICS* on a *Replica Crystal Set* brought back nostalgic memories of my first efforts of building such a set as a schoolboy. Money was of prime importance and with the exception of the headphones virtually everything else in the set was made using odds and ends from the garage.

With a little ingenuity the set you describe could be made in the same way except for the tuning

coil, since the sliding contact mechanism could prove difficult to improvise. I used two "spider web" coils mounted one above the other about ½ inch apart. Tuning was achieved by moving one coil across the top of the other. To the best of my recollection this device, which was quite common in the early days of radio was called a variometer.

Manufacture is easy. Cardboard discs with slots cut out can be used as the former and about 50 turns per coil of 28 s.w.g. wire should enable the medium wave to be covered, although a little experimentation with both the number of turns per coil and the gap between them may be required for best results in individual cases.

F. C. Boucher,
Chelmsford, Essex.

Thermostat Monitor

In the September issue of *EVERYDAY ELECTRONICS*, appeared an article entitled *Aquarium Thermostat*.

On the mains side of the circuit on page 475, the diagram shows a neon indicator in parallel with the heater. This method only indicates when the supply is on, when relay contacts RLA1 are closed. The heater could become open circuit, so that the tempera-

PLUGS

Pack 107 5 pin Din	22p
Pack 108 3 pin Din	20p
Pack 135 1/2" Jack	27p
Pack 130 1/2" Jack Stereo	50p
Pack 103 Loudspeaker Plug	17p
Pack 100 Phono Plug	7p
Pack 230 3 pin Socket	25p
Pack 236 5 Pin Socket	33p
Pack 234 L/speaker Socket	33p

READY MADE LEADS

3 pin to 3 pin Din	70p
3 pin to open end	55p
5 pin to 5 pin Din	90p
5 pin to open end	70p
5 pin to 4 phono plugs	£1
Speaker lead Din to spade	40p
12ft.	
Extension lead Din plug to	40p
socket 12ft.	70p

All leads approx. 6ft. in length.

DIAMOND STYL!

8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GCB
All at 80p each.
Double Diamond £1.25.
Diamond suitable for Orbit
NM22; G800; M3D £2.25 each.

HEADPHONES

Sennheiser HD414	£10-60
AKG K50	£6-50
Beyer DT48S	£35-00

RECORD CARE

Cecil Watts Dust Bug	£1-20
Parastatic Disc Preener	45p
Antistatic Fluid	20p
Dust Bug Spares	
(Brush & Roller)	15p

Prices inc VAT and Post.

J. J. Francis (WOOD GREEN) Ltd.

MANWOOD HOUSE, MATCHING GREEN,
HARLOW, ESSEX CM17 0RS Tel: Matching 476

CASSETTE TAPES

Audio-Magnetics C60	
3 6 10 20	
£1-00 £1-90 £3-20 £6-30	
Cassette Caddy £1-20	
Cassette Head Cleaner 35p	

ZONAL ILFORD TAPE

5" Standard 600ft	25p
5 1/2" Standard 900ft	50p
7" (Plain boxed) 1200ft	60p
7" (Westminster Boxed) 1800ft.	£1-25
7" Reel of Leader Tape (Blue or green)	75p

MICROPHONES

AKG D109	£11-50
AKG D202E1	£39-50
AKG D190C	£17-00
AKG D190E	£18-20
AKG D224	£50-00
Sennheiser MD211N	£45-00
Sennheiser MD413N	£27-00
Sony ECM50	£85-00
Audio RMS7F Radio Mike	£210-00


SPEAKERS

E.M.I. 350 Kit 8 ohms	£8-20
E.M.I. 450 Kit 8 ohms	£4-50

CARTRIDGES

Goldring G800	£6-00
Orbit NM22	£4-00
Shure 75/6	£6-00
Sonotone 9TAHC (Dia)	£2-00
Sonotone 8T4A (Dia)	£1-50
Ronnette 105 (Dia)	£1-25

DABAR MN3 MIXER KIT

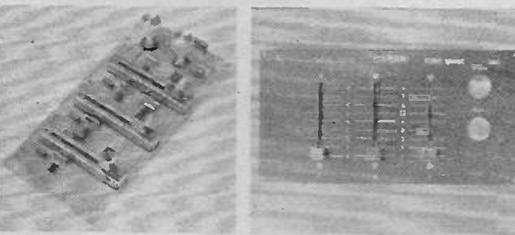

INTRODUCING THE NEW DABAR MINI THREE CHANNEL MIXER KIT WITH THE FOLLOWING FEATURES:

- ★ Three inputs easily adjustable to suit users input requirements, e.g. Mic., Tape, Disc., etc.
- ★ Uses advanced design with five integrated circuits.
- ★ Slider fader volume controls mount directly on P.C. board.
- ★ Full range bass and treble controls.
- ★ Guaranteed top grade components with fibreglass printed circuit board, ready-drilled and tinned.
- ★ Battery operated (2 x PP3) not supplied with kit.
- ★ Easy to follow assembly instructions (available separately 25p).
- ★ Attractive ready punched fascia plate, available at extra cost, gives that professional finish to the unit.
- ★ Size: 9.5" x 4.3" x 2".

PRICE: KIT ONLY £11.00
FACIA PLATE £1.50
MANUAL AND ASSEMBLY INSTRUCTIONS 25p
AVAILABLE READY BUILT WITH FACIA £15.00

ALL PRICES INCLUDE V.A.T. & POSTAGE IN U.K.
S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

98, LICHFIELD STREET, WALSALL, STAFFS, WS1 1UZ.

DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 1 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE

ALL PRICES ARE INCLUSIVE OF V.A.T.

FANTASTIC OFFER

GARRARD SP25 Mk III
Goldring G800, Teak finish, plinth and fitted cover with mains lead and DIN plug and screened lead.
All fully wired.
Please add £1-75 for P. & P. & Ins.

£14-75

TURNTABLES

Please add 95p P. & P. & Ins	
BSR MP60	£9-15
Garrard SP25 Mk III	£9-95
Garrard SL65B	£12-75
Garrard AP76	£16-75
Garrard 401	£27-75
Garrard Zero 100 (sgle)	£33-95
Garrard Zero 100 (Auto)	£37-45
Goldring GL85/P P&C	£39-30
Goldring G101/P P&C	£19-35
Goldring GL72	£21-90
Goldring GL72/P	£28-50
Goldring GL75	£27-35
Goldring GL75/P	£31-90
Goldring GL75 Lid	£3-55
Goodmans TD100 P&C G800 Cart.	£47-15
Thorens TD125	£59-95
Thorens TD125 AB Mk II	£92-50
Thorens TD160 AB & C	£51-26
Thorens TD165 AB & C	£44-15
Wharfedale Linton with cart.	£25-50

TUNERS

Please add 95p P. & P. & Ins.	
Alpha Highgate FT150	£32-95
Amstrad Multiplex 3000	£24-50
Lowther FM Mk 8 N/P	£42-75
Lowther FM Mk 9 N/P	£72-50
Metrosound FMS 20 Mk II	£36-95
Rogers R/brook FET 4 (Cha.)	£32-95
Rogers R/brook FET 4 (cased)	£36-50
Sinclair PRO60 Mod.	£14-90
Sinclair cased tuner	£25-30

TUNER/AMPLIFIERS

Please add £1-10 P. & P. & Ins.	
Alpha FR 3000	£61-35
Goodmans Module 80	£59-90
Goodmans Mod. 80 Com.	£106-50
Goodmans Mod. 90	£74-75
Goodmans One-Ten	£86-50
Rogers R/brook (Cha.)	£61-95
Rotel 150A	£45-25
Rotel 200A	£57-95
Wharfedale WE 40 Receiver	£69-95

AMPLIFIERS

Please add 95p P. & P. & Ins.	
Amstrad 8000 Mk II	£15-95
Amstrad IC2000 Mk II	£34-95
Amstrad Integra 4000	£22-95
Alpha Highgate FA400	£39-05
Global 10-10	£19-75
Global 20+20	£25-95
Keletron 700	£18-25

Prices correct at time of going to press (E. & O. E.) and are subject to alterations



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (EE1), 174 Pentonville Road, London N.1. Tel. 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel. 01-550 1886

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card)

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country



HIGH QUALITY CONSTRUCTION KITS
Approved models at all branches
Complete with components, easy to follow instructions, and convenient full warranty.
Post and packing 15p per kit

- AF20 Mono transistor amplifier £4.80
- AF30 Mono transistor amplifier £2.61
- AF310 Mono transistor (size two for stereo) £5.91
- ATS Automatic light control £2.58
- AT30 Photo cell switching unit £5.70
- AT50 420W Trac light dimmer/phase control £3.90
- AT55 1.200W Trac light dimmer/phase control £5.70
- AT60 2.200W Trac light dimmer/phase control £6.30
- AT65 Psychronic light control, 3 channel £7.80
- AT66 Psychronic light control, 3 channel £14.98
- HF15 Medium wave transistor radio £13.33
- HF75 FM transistor receiver £2.88
- HF210 FM tuner unit £15.81
- HF225 Deluxe FM tuner unit £26.42
- MF130 Stereo decoder for MF130HF325 £2.98
- HF395 Audio amplifier for AM/FM bands 1, 11 £11.77
- GP110 Stereo pre-amplifier for use with 2x AF310 £21.97
- GL130 Transistor unit for guitar etc. £6.15
- NT10 Power supply 300 ma 9V stab. 12V unstab. £12.51
- NT300 Professional substitute power supply 2x 30 Volt, 2.2 amp. £4.90
- NT305 Transistor converter 12/15V AC/DC to 8V, 7.5V or 9V DC £4.90
- NT310 Power supply 240V AC to 2x 18V DC at 2 Amps £4.80
- NT315 Power supply 240V AC to 4x 15V DC 500 ma £5.57



PS.200 REGULATED P.S.U.
Solid state. Variable output 5-20 volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240 V. A.C. Size 7" x 5" x 3". £19.95. P. & P. 25p.



PS.1000B REGULATED POWER SUPPLY
Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240 V. A.C. Size 4" x 3" x 2". £11.97. P. & P. 25p.



MCA.820 AUTOMATIC VOLTAGE STABILISER
Input 88/125 VAO or 176, 250VAC. Output 120VAC or 240VAC. 200VA rating. £11.97. Carr. 60p.



POWER RHEOSTATS
High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. In dia. shafts. Bulk quantities available.

- 25 WATT. 10/25/50/100/250/500/1000 ohms. 95p. P. & P. 10p.
- 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.35. P. & P. 10p.
- 100 WATT. 15/10/25/50/100/250/500/1000 or 2500 ohms. £1.85. P. & P. 15p.



230V 240V SMITHS SYNCHRONOUS GEARED MOTORS
Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CCW; 20 RPH CW; 2 RPH CCW; 30 RPH CW.
56p each Post 12p.



REFLEX HORN SPEAKER RUM.6
Built in driver unit. Impedance 16 ohm. Power rating 10 WATT. Response 350-1000Hz. Approx. size 6" x 8". Weatherproof and shock proof.
OUR PRICE £4.97 P. & P. 30p.



BVD.5 VERNIER TUNING DIAL
Approx. 7-1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scale 1 to 5. Scale width 4 1/2". Dial size 5" x 9". Overall size 7 1/2" x 4 1/2" x 1 1/2" deep including knob and coupling. 1/2" dia. shaft.
OUR PRICE £1.62 P. & P. 15p.



1021 STEREO LISTENING STATION
For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2".
Our Price £2.25 P. & P. 15p



CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

Type SW.100 100 x 80 mm

50µA	£4.15
50-0-50µA	£3.90
100µA	£3.95
100-0-100µA	£3.90
500µA	£3.70
1mA	£3.60
20V. D.C.	£3.60
50V. D.C.	£3.60
500V. A.C.	£3.70
1 amp. D.C.	£3.60



Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts

50µA	£3.90
100µA	£3.90
500µA	£3.90
1 amp.	£3.90
5 amp.	£3.90
15 amp.	£3.90
30 amp.	£3.95
20V. D.C.	£3.90
50V. D.C.	£3.90
150V. D.C.	£3.90
300V. D.C.	£3.90
15V. A.C.	£3.95
30V. A.C.	£3.95
300µA	£4.05
5 Meter 1mA	£3.90
VU Meter	£4.55
1 amp. A.C.*	£3.90
5 amp. A.C.*	£3.90
10 amp. A.C.*	£3.90
20 amp. A.C.*	£3.90
30 amp. A.C.*	£3.90



Type MR.38P. 1 1/2 3 1/2 in. square fronts

200µA	£2.25
300µA	£2.25
500µA	£2.25
750µA	£2.25
1 amp.	£2.25
5 amp.	£2.25
10 amp.	£2.25
3V. D.C.	£2.25
10V. D.C.	£2.25
15V. D.C.	£2.25
20V. D.C.	£2.25
50V. D.C.	£2.25
100V. D.C.	£2.25
100-0-100µA	£2.40
200µA	£2.25
100V. D.C.	£2.25
150V. D.C.	£2.25
300V. D.C.	£2.25
600V. D.C.	£2.25
750V. D.C.	£2.25
15V. A.C.	£2.25
50V. A.C.	£2.30
300V. A.C.	£2.30
5 Meter 1mA	£2.30
VU Meter	£2.65




Type SD.830 82.5mm x 110mm Fronts

10mA	£3.10
50mA	£3.10
100mA	£3.10
500mA	£3.10
1 amp.	£3.10
5 amp.	£3.10
10 amp.	£3.10
5V. D.C.	£3.10
10V. D.C.	£3.10
20V. D.C.	£3.10
40V. D.C.	£3.10
300V. D.C.	£3.10
18V. A.C.	£3.30
300V. A.C.	£3.30
VU Meter	£3.50




Type MR.52P. 2 1/2 in. square fronts

50µA	£2.50
50-0-50µA	£2.50
100µA	£2.50
100-0-100µA	£2.50
500µA	£2.50
1mA	£2.50
5mA	£2.50
10mA	£2.50
50mA	£2.50
100mA	£2.50
5 amp. A.C.*	£2.50
10 amp. A.C.*	£2.50
20 amp. A.C.*	£2.50
30 amp. A.C.*	£2.50

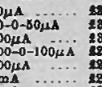


Type MR.45P. 2 in. square fronts

50µA	£2.70
50-0-50µA	£2.65
100µA	£2.60
100-0-100µA	£2.60
200µA	£2.60
500µA	£2.45
600-0-500µA	£2.45
1mA	£2.40
5mA	£2.40
10mA	£2.40
50mA	£2.40
100mA	£2.40
1 amp.	£2.40
5 amp.	£2.40
10V. D.C.	£2.40
20V. D.C.	£2.40
50V. D.C.	£2.40
15V. A.C.	£2.60
30V. A.C.	£2.60
8 Meter 1mA	£2.60
VU Meter	£2.60
1 amp. A.C.*	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60

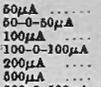


Type SD.640 63.5mm x 85mm Fronts

50µA	£2.05
50-0-50µA	£2.05
100µA	£2.00
100-0-100µA	£2.00
200µA	£2.00
500µA	£2.05
1mA	£2.00
5mA	£2.00
10mA	£2.00
50mA	£2.00
100mA	£2.00
1 amp.	£2.00
5 amp.	£2.00
10 amp.	£2.00
5V. D.C.	£2.00
10V. D.C.	£2.00
20V. D.C.	£2.00
300V. D.C.	£2.00
18V. A.C.	£2.00
300V. A.C.	£2.00
VU Meter	£2.15

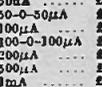

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts

50µA	£2.70
50-0-50µA	£2.65
100µA	£2.65
100-0-100µA	£2.65
200µA	£2.65
500µA	£2.75
600-0-500µA	£2.60
1mA	£2.60
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
5V. D.C.	£2.60
10V. D.C.	£2.60
20V. D.C.	£2.60
50V. D.C.	£2.60
150V. D.C.	£2.60
300V. D.C.	£2.60
15V. A.C.	£2.80
30V. A.C.	£2.80
8 Meter 1mA	£2.80
VU Meter	£2.80
1 amp. A.C.*	£2.80
5 amp. A.C.*	£2.80
10 amp. A.C.*	£2.80
20 amp. A.C.*	£2.80
30 amp. A.C.*	£2.80

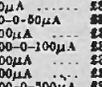

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts

1 amp.	£2.60
5 amp.	£2.60
15 amp.	£2.60
30 amp.	£2.60
60 amp.	£2.60
5V. D.C.	£2.60
10V. D.C.	£2.60
20V. D.C.	£2.60
30V. D.C.	£2.60
150V. D.C.	£2.60
300V. D.C.	£2.60
500V. D.C.	£2.60
1000V. D.C.	£2.60
30V. A.C.*	£2.65
60V. A.C.*	£2.65
150V. A.C.*	£2.65
300V. A.C.*	£2.65
150V. A.C.*	£2.65
300V. A.C.*	£2.65
600µA A.C.*	£2.60
1 amp. A.C.*	£2.60
5 amp. A.C.*	£2.60
10 amp. A.C.*	£2.60
20 amp. A.C.*	£2.60
30 amp. A.C.*	£2.60
50 amp. A.C.*	£2.60
VU Meter	£3.65



Type SD.460 46mm x 59.5mm Fronts

50µA	£2.80
50-0-50µA	£2.80
100µA	£2.75
100-0-100µA	£2.75
200µA	£2.70
500µA	£2.55
1mA	£2.60
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60
1 amp.	£2.60
5 amp.	£2.60
10 amp.	£2.60
5V. D.C.	£2.60
10V. D.C.	£2.60
20V. D.C.	£2.60
50V. D.C.	£2.60
300V. D.C.	£2.60
18V. A.C.	£2.70
300V. A.C.	£2.70
VU Meter	£2.80



"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm



A new range of high quality moving coil instruments ideal for school experiments and other bench applications. The 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50µA	£3.90
100µA	£3.40
50-0-50µA	£3.40
1mA	£3.95
1-0-1mA	£3.95
1A d.c.	£3.95
10V d.c.	£3.95
20V d.c.	£3.95
50V d.c.	£3.95
300V d.c.	£3.95
Dual range	£3.90
500mA/5A d.c.	£7.00
5V/50V d.c.	£7.00

"SEW" EDGWISE METERS

Type PE.70. 3 1/2 3 1/2 in. x 1 1/2 3 1/2 in. x 2 1/2 in. deep

50µA	£3.75
50-0-50µA	£3.60
100µA	£3.60
100-0-100µA	£3.60
200µA	£3.60
500µA	£3.60
1mA	£3.60
500V. A.C.	£3.25
VU Meter	£3.85

*MOVING IRON—

ALL OTHERS MOVING COIL

Please add postage

1021 STEREO LISTENING STATION




For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2".
Our Price £2.25 P. & P. 15p

AUDIOTRONIC AHA-101 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery.
INPUTS: 6mV/100mV.
OUTPUT: 50mV per channel.
Our Price £7.50 P. & P. 15p

EA.41 REVERBERATION AMPLIFIER

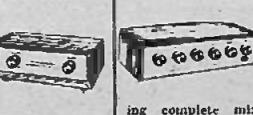

Self contained transistorised, battery operated. Simply plug in microphone, and output into your guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2" x 3" x 4 1/2".
Our Price £7.50 P. & P. 15p

MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mics: 3x 3mV 50K; 2x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.
Our Price £8.97 P. & P. 20p

SEND SAE FOR NEW 8 PAGE SEMI CONDUCTORS & VALVES LIST

ALL PRICES ARE SUBJECT TO 10% VAT



ALSO SEE FOLLOWING PAGES

G.W. SMITH & CO (RADIO) LTD

TRIO JR599 RECEIVER



9 wavebands covering 1.8-29.7MHz 144-146MHz and 10.00MHz WWV. SSB, CW, AM and FM. AF output more than 1 watt. 8 Meter. Squelch control. BFO. Variable RF and AF controls. 4-16 ohm output and phone jack. Power requirements 100/240v. AC. 12-14v. DC.

Our Price **£155.00** Carr. Paid

TRIO TR2000 TRANSCEIVER

Fully transistorized portable VHF transceiver. Will transmit and receive on 6 channels between 144-146MHz. 1 watt transmitter. 12v DC internal or external supply. Built in charger for nickel-cadmium. Power/volume switch, squelch control, channel selector, mike socket, earphone/external speaker socket. Complete with microphone. 144.48, 144.72 and 145.32 crystals. Size 134 x 58 x 180mm.

Our Price **£79.50** Carr. Paid

TRIO TS515/PS515 TRANSCEIVER



High quality TS515 SSB/CW amateur band receiver covering 80, 40, 20, 15 and 10 metre bands with PS515 power supply and speaker unit. Transmit/receive frequency 3.5-29.7MHz. Output 1.5 watts. Power requirements 110-240/220-240v. AC.

Our Price **£210.00** Carr. Paid

BELTEK W5400 CAR TRANSCEIVER



Solid state mobile transceiver for 12v DC neg. use. Transmits and Receives on any 12 of 28 channels between 144 and 146MHz. Power output 10w and 1w switchable. Internal 3" speaker. Complete with dynamic mike, PTT switch, three sets of crystals for 144-48MHz, 144-80MHz, 145-00MHz. mounting bracket and instructions. Size approx. 150 x 60 x 220mm.

Our Price **£75.00** P & P 50p

TRIO JR310 SSB RECEIVER



Covers 3.5, 7, 14, 21, 28, 28.5 and 29.1 MHz bands and WWV 15MHz. SSB, AM and CW. AF output more than 1 watt. Circuitry controlled BFO for SSB. 8 meter. ANL etc. AC 110/120-220/240v.

Our Price **£75.00** Carr. Paid

UNR 30 RECEIVER



4 Bands covering 550 Kc/s-30 Mc/s. B.F.O. Built-in Speaker 220/240 v. A.C. Brand new with instructions.

Our Price **£15.75** Carr. 37p

UR-1A RECEIVER



4 Bands covering 550 Kc/s-30 Mc/s. FET. 8 Meter. Variable BFO for 88B. Built-in Speaker, Bandspread, Sensitivity Control. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price **£25.00** Carr. 37p

LAFAYETTE HA-600 RECEIVER



General coverage 150-400 Kc/s. 550 Kc/s-30 Mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter Bandspread. RF Gain. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price **£50.00** Carr. 50p

TRIO 9R59DS RECEIVER



4 bands covering 550 Kc/s to 30 Mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW, ANL. Variable BFO. 8 meter. Sep. bandspread dial. 1F frequency 445 Kc/s, audio output 1.5w. Variable RF and AF gain controls 115/250 v. A.C. with instruction manual.

Our Price **£49.50** Carr. Paid

HAND-HELD

2-WAY

WALKIE-TALKIES

P. & P. 50p.

3-STATION INTERCOM KE.630

SKYFON -100MW. 224.95 pair.

P302-2 CHANNEL 300MW. £52.50 pair.

P1003-3 CHANNEL 1 Watt £71.25 pair.

LICENSE REQUIRED FOR OPERATION IN U.K.

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

AUDIOTRONIC

RANGE OF HIGH QUALITY EQUIPMENT

Audiometric Products are manufactured exclusively for the Audiometric Group of Companies and as a member of the group we are pleased to offer you this fabulous range of high quality equipment. Made to our own specifications each item provides outstanding performance and reliability at a value for money price!

ACD.660 Stereo Cassette Deck



A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, notch/echo/tone tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/DIN line input sockets, 3.5mm mike input sockets etc. etc. Frequency response 100-8KHz (100-12KHz Cr02) 8V-45dB. Crosstalk 45dB. Separation-55dB. Noise limiter-6dB at 10KHz. Complete with phone connecting leads. Carr. & Ins. 50p

AHP-8D 8 Track Stereo Tape Deck

Can be used with most hi fi amplifiers. Push button track selector and illuminated track indicators.

Attractive cabinet with black and silver trim. Output level 760mV. AC 220/240v. Carr. & Ins. 50p

AHP-8A 8 Track Stereo Tape Player



Incorporates built in amplifiers giving 21 x 21 watts rms output. Push button track selector, illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output level 760mV. AC 220/240v. Carr. & Ins. 50p

Stereo Headphones

LSH.20 Individual volume controls Stereo mono switch. 8 ohms. 40 19,000 Hz. £3.50 P & P 30p

LSH.30 Open back type. Individual tone and volume controls. 8 ohms. 30-20,000 Hz. £5.50 P & P 30p

LSH.40 Two way speaker system. Individual volume controls. 8 ohms. 20-20,000 Hz. £6.95 P & P 30p

LSH.60 3" speaker units. 8 ohms. 20,000 Hz. Complete with zippered carrying case. £8.50 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4.32 ohms. 20,000 Hz. £8.95 P & P. 30p

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 24dB at 600Hz, 6dB at 3200Hz and 10dB for all frequencies above 3000Hz. Size 16" x 4" x 3". AC 200/250v



PROCESS FOUR For use with semi-professional tape recorders. Freq. res. 30Hz-20KHz ± 2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

Our Price **£50.00** P & P 50p

PROCESS TWO For use with cassette and tape recorders. Freq. res. 30Hz-20KHz ± 2dB. OQ tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

Our Price **£34.50** P & P 50p

ACR.14 Battery Mains Cassette Recorder

Portable twin track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. AC 220/240v or 6v DC operation. Complete with remote control microphone, mains lead, earpiece and batteries.

Our Price **£10.50** P & P 50p

ACR 3500 CAR RADIO



Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker. Mounting brackets and instructions.

Our Price **£6.50** P & P 50p

ACP.8 8 TRACK CAR PLAYER



12v neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp, with speakers, mounting brackets and instructions.

Our Price **£12.50** P & P 40p

LOW NOISE CASSETTES

Top Hi-Fi quality in library cases

TYPE	5	10	25
C60	£1.29	£2.35	£3.99
C90	£1.85	£2.42	£3.99
C120	£2.29	£4.48	£10.68

P. & P. 15p. Cassette Tape Head Cleaner 80p

AMR-900 GLOBAL RADIO AM/FM PORTABLE RADIO



10 wavebands covering AM: 335-1605 KHz LW: 150-360 KHz MW: 1.6-4.0 MHz SW: 4.0-30 MHz SW3: 8.0-16.0 MHz SW3: 16-24 MHz, PSB1: 30-50 MHz, PSB2: 148-174 MHz, FM: 88-108 MHz, AIR: 108-136 MHz. Features: time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. APC or FM. 6" x 4" speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm. Our Price **£36.00** P & P. 50p.

AR.1000 SPORTSMAN AM/FM PORTABLE RADIO



5 wavebands covering AM 535-1605KHz and FM 88-108MHz. AIR 108-136MHz. PB 147-174MHz. WB 162-5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for FM and built in ferrite bar for AM. AFC. 3in. speaker. Earpiece socket. Size 152 x 79 x 218mm. Battery/mains operation. Our Price **£11.50** P & P. 35p.

AUDIOTRONIC AMB.500 MULTIBAND RADIO



5 wavebands covering MW 535-1605KHz and FM 88-176MHz. AU transistor. Battery or mains operation. Built in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece. Our Price **£6.95** P & P 35p

AM/FM Portable Radio AR3000



4 wavebands covering MW 87-108 MHz, MW510 - 1605 KHz, LW 145 - 285 KHz, SW 5.8 - 12.5 MHz. Push button wave change plus AFC and on/off. Thumbwheel tuning. Slider volume and tone controls. Earphone socket. Built in and telescopic aerials. Car aerial socket. Battery/Mains operation. Our Price **£14.95** P & P. 50p

DIGITAL CLOCK RADIO ADC.1



Covers AM 540 - 1600 KHz. FM 88 - 108 MHz with AFC. Illuminated dial. 24 hour alarm setting. Wake up to the sound of music or loud buzzer. Sleep switch will automatically turn off radio etc. Internal speaker plus socket for earpiece or pillow speaker. AC 240v. Size 95 x 91 x 178mm. Complete with earpiece. FM aerial and operating instructions. Our Price **£12.50** P & P. 50p.



ALSO SEE PREVIOUS PAGES

SAVE UP TO 33 1/3% OR MORE! GWS

SH626 STEREO HEADPHONES



Outstanding value. Soft ear-pads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

Our Price £1-87 P. & P. 30p

LH025 STEREO HEADPHONES



Lightweight headpiece with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft. cord and plug.

Our Price £1-97 P. & P. 30p

TEI018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (i.e., 600 ohms). Frequency response 200-4,000 Hz.

Our Price £2-25 P. & P. 30p

BH001 HEAD SET AND BOOM MICROPHONE



Moving Coil. Ideal for language teaching, communications, etc. Imp. 16 ohms. Microphone imp. 200 ohms.

Our Price £4-95 P. & P. 30p

DH025 STEREO HEADPHONES



Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug.

Our Price £2-25 P & P 30p




SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe leak vented drivers. Size 14 1/2" x 8 1/2" x 7 1/2" 8 ohms. 8 watt RMS. 16 watt peak. Complete with DIN lead.

Our Price £12-95 Carr. 50p

SUPER AKAI HiFi BARGAINS

CS35 Stereo Cassette Recorder

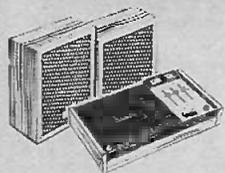

For conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-16kHz (using CR02 tape), distortion better than 2%, wow and flutter better than 0.2% RMS. Complete with pair of matching Akai CS35 speakers.

Rec. Price £96-10 £56-50 P.&P. OUR PRICE 50p

CS35D STEREO DECK

4 track record/playback deck. Accepts chrome/regular tape cassettes.

Rec. Price £68-30 £44-45 P.&P. GWS PRICE 50p

MICROPHONES (P. & P. 60p)
ADM Dynamic (pair) £7-50

FERGUSON EXPORT MODELS



FERGUSON 3408 STEREO TUNER AMPLIFIER

Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape etc. Separate bass treble, balance and volume controls.

Our Price £31-50 P. & P. 50p



3416 STEREO TAPE DECK

4 track. 7 1/2, 3 1/2, 1 1/2 i.p.s. Stereo/mono record/play. 7" reels. Inputs for dynamic mikes, radio, gram. Complete with cover.

Our Price £41-95 P. & P. 75p



EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 16 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 27p.

Model 450. 13" x 5" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 16 ohms. £3-92 each. P. & P. 25p.

RECORD DECK PACKAGES

Carriage and Packing 76p. Complete units with Stereo cartridge ready wired in plinth cover.

GARRARD	
2025 TC/STACD	£11-85
SP25 111/G800	£16-60
SP25 111/M44E	£17-95
SP25 111/M4-7	£17-50
SP25 111/M55E	£18-50
SP25 111 Module/M75-6	£19-45
SP25 IV Module/M75-68M	£21-15
AP76/G800	£28-45
AP76/G800E	£28-65
AP76/M44E	£27-70
AP76/M44-7	£27-20
AP76/M55E	£28-30
AP76/M75EJ	£24-90
AP76 Module M75-6	£29-10
366B Module/M75-68M	£22-30
AP96 Module M75-6	£28-20
ZERO 1008 Module/M93E	£44-15
ZERO 1008B Module/M75-68M	£44-20

B.S.E. McDONALD	£7-40
G129/GC7M	£7-40
MP60/G800	£16-50
MP60/TPD1/G800	£15-80
MP60/M44-7	£17-50
H770/TPD1/G800	£19-20

GOLDRING	£24-20
GL72/G800	£21-55
GL76/G800	£30-10
GL78/G800F	£41-55
GL78/G800	£45-15
GL78/G800E	£47-80

RECORD DECKS

Carriage and Packing 50p

B.S.E. McDONALD	£3-95
C114 Mini	£5-50
C129 Mono	£5-50
C137	£7-00
810/TPD1	£13-95
810	£13-20
810/TPD1	£15-45
710	£21-15
810	£28-30
MP60	£8-25
MP60/G800	£10-80
MP60/TPD1	£13-20
MP60/TPD2	£11-25
H770	£11-60
H770/G800	£14-25
H770/TPD1	£16-55

CONNOISSEUR	£9-10
B01 Chassis	£11-35
B02/SAU2/Chassis	£22-70
B02/SAU2/Plinth/Cover	£28-20

GARRARD	£6-35
2025 TC/KS40A	£6-85
SP25 III	£9-25
SP25 III Acos GP104C	£8-50
SP25111/G800	£10-95
SP25/M76-6	£18-80
SP25 TV	£19-25
AP77	£18-00
868B	£18-50
8L65B	£11-15
8L72B	£17-75
8L95B	£31-15
401	£28-35
ZERO 100A	£24-10
ZERO 100S	£21-40
ZERO 100 B	£27-00

GOLDRING	£29-50
G101P/C	£22-50
GL69/JC	£16-70
GL72	£26-45
GL72/P	£33-75
GL75	£32-20
GL76E	£41-85
GL78/JC	£55-25
GL85E/C	£72-00

BSR 8 TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model TD68 complete with silver and black excitecon ready to fit into cabinet. Output 125mV. AC 240V. Overall size approx. 185 x 215 x 80mm.

OUR PRICE £8-95 P. & P. 50p.

PORTABLE CASSETTE RECORDER

Instant recording and playing. Piano key controls. Automatic level control. Built in speaker. Complete with remote control microphone, carrying case and shoulder strap.

OUR PRICE £8-50 P. & P. 50p.

NEW! SINCLAIR CAMBRIDGE CALCULATOR

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator.

OUR PRICE £24-95 P. & P. 50p.

(Also available ready built (Rec. Price £29-95))

OUR PRICE £27-20 P. & P. 25p

MINUTEMAN MM3 POCKET CALCULATOR

Size only 4 1/2" x 3" x 1 1/2". 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.

OUR PRICE £23-95 P. & P. 25p

MINUTEMAN MM3

as above with addition of memory key, per cent key and a fixed or floating decimal. Complete with rechargeable batteries, AC adaptor, instructions and case.

OUR PRICE £28-50 P. & P. 25p

BINATONE D5100 DIGITAL CLOCK

240r. mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Approx. size 6 1/2" x 3" x 3 1/4".

OUR PRICE £4-50 P. & P. 30p.

SINCLAIR PROJECT 60 PACKAGE DEALS



2 x Z30 Stereo 60/PZ5 £15-95. P. & P. 37p.

2 x Z30/Stereo 60/PZ6 £18-00. P. & P. 37p.

2 x Z50/Stereo 60/PZ8 £20-25. P. & P. 37p.

Transformer for PZ3 £3-85.

Active Filter Unit £4-45.

Pair of Q16 Speakers £10-70.

Sinclair Project 605 £20-87. P. & P. 37p.

All other Sinclair Products in stock

2000 Amplifier £22-95

3000 Amplifier £28-85

2000/3000 Tuner £28-20

Q830 Speakers £29-85 pair

P. & P. 50p each of above items.

FM TUNER CHASSIS



6 TRANSISTOR HIGH FIDELITY TUNER. 6 I Z K ONLY.

6 x 6" x 2 1/2". 3 I.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money.

Our Price £5-95 P. & P. 20p

Stereo multiplex adaptor £4-97.

A1018 FM TUNER



Specification as above chassis but complete in cabinet with on/off switch. Size 7 1/2" x 3 1/2" x 6".

Our Price £9-65 P & P 30p

Stereo multiplex adaptor £4-97.

DIGITAL CLOCK MECHANISM DT.55B



Features 24-hour alarm setting with built-in buzzer. On/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off TV, radio, light, etc. and with auto setting will switch on again when required. AC 240v. operation. Switch rating 250v. 3A.

OUR PRICE £5-95 P. & P. 30p.

LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY -



Prices on request or send S.A.E. for full Discount List

ALL EQUIPMENT IS FULLY GUARANTEED AND COVERED BY 12 MONTHS FREE SERVICE!

G.W.SMITH & CO (RADIO) LTD

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON	Tel: 01-580 0670	211, Edgware Road, W.2.	Tel: 01-262 0387
257/8, Tottenham Court Rd, W.1.	Tel: 01-637 2232	382, Edgware Road, W.2.	Tel: 01-723 4194
10, Tottenham Court Rd, W.1.	Tel: 01-636 3715	152/3, Fleet Street, E.C.4.	Tel: 01-353 2833
27, Tottenham Court Rd, W.1.	Tel: 01-580 3739	378, Harrow Road, W.9.	Tel: 01-286 9530
87, Tottenham Court Rd, W.1.	Tel: 01-437 2169	555EX	
21, Old Compton Street, W.1	Tel: 01-437 8204	86, South Street, Romford.	Tel: Romford 20218
2, Little Street, W.C.2.	Tel: 01-437 9155	1048, Whitgift Centre, Croydon.	Tel: 01-681 3027
34, Little Street, W.C.2.	Tel: 01-723 9789	27, Eden Street, Kingston.	Tel: 01-548 7845
118, Edgware Road, W.2.	Tel: 01-723 6211	32, Hill Street, Richmond.	Tel: 01-948 1441
192, Edgware Road, W.2.			

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

HEAD OFFICE AND MAIL ORDER DEPARTMENT
UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JW
TELEPHONE 01-205 3735

PRICES SUBJECT TO 10% VAT


Order with confidence by Post—but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.



TELEPHONED ORDERS ACCEPTED FROM ACCESS and BARCLAYCARD HOLDERS

CREDIT TERMS FOR PERSONAL CALLERS (on terms of £50 and over).

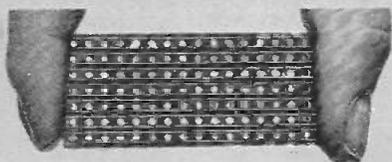All prices correct at 3-10-73 but subject to change without notice. G.W.S.




FREE VEROBOARD IN OCTOBER ISSUE

VEROBOARD PROJECTS

ONE


A.F. OSCILLATOR

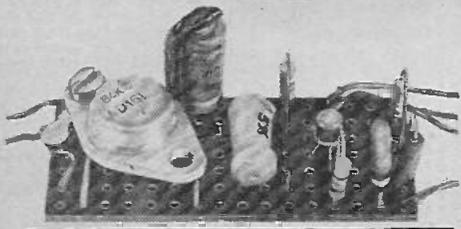

RADIO & ELECTRONICS CONSTRUCTOR

TWO

GRAM AMPLIFIER

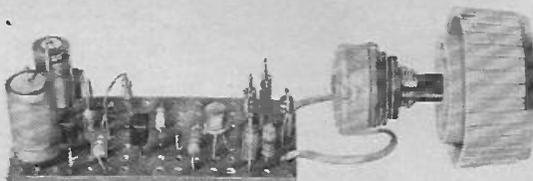

Plus many more
constructional features

*Buy NOW and be sure
of your copy - PRICE 20p*



become a RADIO-AMATEUR!

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

**BRITISH NATIONAL RADIO &
ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

EEB 11 3
BLOCK CAPS please

"P.E" F.M. Varicap Stereo Tuner

THE STEREO F.M. TUNER

YOU CAN BUILD



Approx. Size 8½" x 2½" x 6½"

Features include push button "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses NEW pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated Circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator. TOTAL KIT price only £28.50 including V.A.T. and postage. With Fibre Glass P.C. Board, neat slimline teak veneered cabinet with brushed aluminium front panels, push buttons etc. All parts available separately.

IDEAL FOR USE WITH THE "TEXAN", "GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER. Please send large S.A.E. for full details.
228, ECCLESALL ROAD, SHEFFIELD S11 8PE
Telephone No. (0742) 668888
THE COMPONENT CENTRE OF THE NORTH

ELECTRO SPARES

es

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p	BCY58	18p	CA3035	£1.37	NKT406	62p	1N4004	7p	2N6027(D13T1)	45p
AA120	50p	BCY70	15p	CA3043	£1.57	NKT713	29p	1N4005	7p		£1.39
AC126	29p	BCY71	26p	CA3044	£1.28	NKT773	25p	1N4006	8p	3N384	10p
AC127	25p	BCY72	14p	CA3046	70p	NKT781	29p	1N4007	9p	3N128	73p
AC128	24p	BD124	75p	CA3048	£2.11	NTGD10	40p	1N4148	4p	3N140	92p
AC128/AC176	44p	BD131	40p	CA3052	£1.82	OA10	40p	1N5400	14p	3N152	92p
		BD132	40p	CA3065	£1.28	OA47	3p	1N5404	18p	3015F	£1.50
AC151	20p	BD131/132	80p	CA3088E	£1.24	OA79	8p	1N5408	25p	3015G	£2.00
AC152	25p	RDY20	91p	CA3089E	£1.96	OA90	5p	1S44	4p	7400	20p
AC153	26p	BF115	23p	CA3090Q	£4.23	OA91	5p	1S920	7p	7401	20p
AC176	20p	BF163	35p	CD4001AE	55p	OA95	5p	1S940	5p	7402	20p
AC153/176K	52p	BF167	25p	CD4009AE	£1.16	OA200	8p	2N404	23p	7403	20p
AC187K	17p	BF173	29p	CD4011AE	55p	OA202	7p	2N696	15p	7404	20p
AC188K	23p	BF177	25p	CD4012AE	55p	OC25	45p	2N697	17p	7405	25p
AC187/188K	40p	BF178	31p	CD4813AE	£1.17	OC28	78p	2N698	39p	7408	25p
ACY17	27p	BF180	35p	CD4015AE	£2.92	OC29	79p	2N706	10p	7409	25p
ACY18	20p	BF194	15p	CD4017AE	£2.92	OC35	66p	2N706A	12p	7410	20p
ACY19	20p	BF195	15p	CD4018AE	£2.92	OC36	69p	2N708	18p	7413	30p
ACY20	20p	BF196	15p	CD4020AE	£2.92	OC41	40p	2N911	50p	7420	20p
ACY21	19p	BF200	35p	CD4024AE	£2.99	OC42	40p	2N914	20p	7425	30p
ACY22	10p	BF254	14p	CR11051C	54p	OC44	20p	2N916	42p	7430	20p
AD140	60p	BF255	15p	CR11401C	71p	OC45	20p	2N929	25p	7440	24p
AD149	60p	BFX13	25p	CRS3/05AF		OC71	20p	2N930	28p	7442	£1.16
AD161	44p	BFX23	32p	CRS3/40AF		OC72	20p	2N1131	24p	7443	£1.45
AD162	44p	BFX24	25p	CRS3/40AF		OC75	25p	2N1132	24p	7444	£1.45
AD161/162	88p	BFX85	34p	CZ8	£1.53	OC76	25p	2N1302	17p	7445	£1.45
AF106	32p	BFX86	25p	D10 (NTGD10)		OC77	40p	2N1303	17p	7446	£1.45
AF114	27p	BFX87	30p			OC78	20p	2N1304	17p	7447	£1.25
AF115	27p	BFX88	24p			OC81D	20p	2N1305	24p	7450	20p
AF116	25p	BFY50	22p	IRT84	£2.90	OC83	23p	2N1306	30p	7451	20p
AF117	25p	BFY51	19p	IR2100	£5.90	OC84	25p	2N1307	30p	7453	20p
AF118	44p	BFY52	20p	IRC20	42p	OC139	25p	2N1308	34p	7454	20p
AF124	25p	BFY53	17p	JA424	£2.89	OC170	25p	2N1309	34p	7450	20p
AF125	24p	BFY90	£1.50	LIC709C/5	42p	OC171	30p	2N1538 (CRI)	45p	7450	45p
AF126	24p	BP101	£1.40	LIC709C/8	42p	ORP12	42p	50P2N1613	71p	7472	32p
AF139	47p	BPX66	£1.40	LIC723C/5	£1.02	ORP12	50p	2N1613	15p	7473	45p
AF186	40p	BRY39	45p	LIC723C/14	£1.02	ORP60	50p	2N1711	15p	7474	48p
AF239	52p	BSX19	18p	LIC741C/5	45p	ORP61	50p	2N1893	54p	7475	45p
AF279	88p	BSX20	18p	LIC741C/8	34p	ORP69	50p	2N2218	33p	7476	45p
ASV26	25p	BSX21	20p	MC1303L	£1.75	PN70	10p	2N2218A	44p	7480	87p
ASV27	30p	BSY27	20p	MC1305P	£2.80	PN71	10p	2N2219	44p	7484	87p
ASV28	22p	BSY29	25p	MC1307P	£1.68	PN107	8p	2N2219A	53p	7483	£1.32
ASV29	30p	BSY95A	12p	MC1310P	£2.93	PN108	8p	2N2368	17p	7488	33p
BA138	15p	BY100	20p	MC1330P	£2.00	PN109	8p	2N2369	17p	7490	70p
BB103	20p	BTY127	22p	MC1352P	£2.00	PN3819(2N3819)	2N2369A	17p	7491A	£1.28	
BB104	34p	BTY19/400R	£1.80	MC1468L	£4.20		20p	2N2484	42p	7492	85p
BB105	28p		£1.20	MFC4000B	15p	SL146D	£2.90	2N2645	45p	7493	75p
BC107	13p	BT106	£1.20	MFC4002A	£2.20	SL103A	50p	2N2904A	49p	7485	£1.13
BC107/BC177	33p	BZY88C/3V	10p	MC4044P	£2.20	SL403A (Rec)	2N2905	85p	7496	£1.48	
BC108	12p	BZY88C/9V	10p	MFC6030	£1.83		60p	2N2905A	75p	74100	£1.84
BC108/BC178	28p	BZY88C/4V7	10p	MFC6040	£1.15	SL803A	80p	2N2924	18p	74107	52p
BC109	13p	BZY88C/5V1	10p	MFC6010	£1.99	TAA263	£1.12	2N2925	29p	74121	43p
BC109/BC179	33p	BZY88C/6V2	10p	MFC6020	£1.24	TAA293	87p	2N2926	10p	74141	£1.00
BC109C	44p	BZY88C/8V8	10p	MJE371	68p	TAA320	£1.25	2N3053	54p	74150	£3.35
BC117	15p	BZY88C/7V5	10p	MJE520	85p	TAA861	45p	2N3055	65p	74151	£1.10
BC140	30p	BZY88C/2V	10p	MJE521	82p	TAD100	£1.97	2N3055	65p	74153	£1.35
BC147	12p	BZY88C/9V1	10p	MJE2985	£1.96	TAD110	£1.97	2N3228	£1.10	74154	£2.00
BC148	11p	BZY88C/10V	10p	MJE3055	88p	TIL112	£2.00	2N3228	£1.04	74156	£1.55
BC149	12p	BZY88C/11V	10p	MJ481	97p	TLP209	35p	2N3202	14p	74150	£1.10
BC157	13p	BZY88C/12V	10p	MJ481	£1.25	TIP31A	50p	2N3703	12p	74191	£1.10
BC158	15p	BZY88C/13V	10p	MJ491	£1.38	TIP32A	78p	2N3704	12p	74192	£1.74
BC159	13p	BZY88C/15V	10p	MJ802	£4.12	TIP41A	85p	2N3705	12p	74193	£1.74
BC147/157	25p	BZY88C/16V	10p	MJ802/MJ4502	£1.90	TIP42A	£1.00	2N3706	12p	74198	£1.50
BC148/158	25p	BZY88C/18V	10p	MJ900	£3.50	TIS43	38p	2N3707	12p	74197	£1.50
BC149/159	25p	BZY88C/20V	10p	MJ1000	£1.80	VA10688	15p	2N3708	12p	40350	68p
BC167	11p	BZY88C/22V	10p	MJ4502	£4.44	VA1040	15p	2N3709	12p	40306	40p
BC168	10p	BZY88C/25V	10p	MPF102	37p	VA1977	15p	2N3711	12p	40311	42p
BC169C	12p	BZY88C/30V	10p	MPF103(2N5457)	W005		30p	2N3773	£2.50	40312	62p
BC177	20p	BZX61C/7V5	28p		48p	W01	31p	2N3819	28p	40320	42p
BC178	18p	BZX61C/8V2	28p	MPF104(2N5458)	W02		32p	2N3820	60p	40380	56p
BC179	20p	BZX61C/9V1	28p		49p	W04	33p	2N3822E	20p	40361	45p
BC182	14p	BZX61C/10V	28p	MPF105(2N5459)	W05		35p	2N3826	30p	40382	45p
BC182L	14p	BZX61C/11V	28p		46p	W08	44p	2N3886	£1.10	40406	52p
BC183	13p	BZX61C/12V	28p	NKT0033	95p	ZTX107	11p	2N3904	28p	40407	48p
BC183L	14p	BZX61C/13V	28p	NKT121	26p	ZTX108	12p	2N3906	28p	40408	54p
BC184	17p	BZX61C/15V	28p	NKT122	25p	ZTX300	13p	2N4058	15p	40408	62p
BC184L	16p	BZX61C/16V	28p	NKT123	48p	ZTX302	18p	2N4059	15p	40410	62p
BC212	16p	BZX61C/18V	28p	NKT124	28p	ZTX303	15p	2N4061	15p	40430	62p
BC212L	16p	BZX61C/20V	28p	NKT125	50p	ZTX304	23p	2N4062	13p	40468A	44p
BC238	10p	BZX61C/22V	28p	NKT126	25p	ZTX314	11p	2N4441	70p	40511	£1.92
BC238/308	10p	BZX61C/24V	28p	NKT127	27p	ZTX320	30p	2N4444	£2.20	40575	£1.54
BC257	11p	BZX61C/27V	28p	NKT128	20p	ZTX330	11p	2N4871	44p	40576	£1.48
BC258	10p	BZX61C/30V	28p	NKT129	18p	ZTX500	14p	2N4890	66p	40600	70p
BC259	12p	CA3004	£2.03	NKT130	15p	ZTX502	15p	2N4991	46p	40601	70p
BC307	12p	CA3005	£1.35	NKT131	29p	ZTX503	15p	2N5245	45p	40602	70p
BC308	10p	CA3011	83p	NKT132	29p	ZTX503	15p	2N5457(MPF103)	40p	40603	70p
BCY30	25p	CA3013	£1.17	NKT135	75p	ZTX504	17p	2N5458(MPF104)	40p	40669	£1.00
BCY31	48p	CA3014	£1.37	NKT140	71p	1N814	4p	2N5459(MPF105)	49p	40739	£1.50
BCY32	56p	CA3018	72p	NKT402	77p	1N3754	20p				
BCY33	20p	CA3018A	83p	NKT403	65p	1N4001	4p				
BCY34	25p	CA3020	£1.39	NKT404	49p	1N4002	4p				
BCY38	30p	CA3028A	79p	NKT405	79p	1N4003	5p				

CAPACITORS ELECTROLYTIC AXIAL LEADS

Mfd.	Working Voltage	Price	Mid.	Working Voltage	Price
1.0	40v	10p	100	16v	9p
1-0	100v	8p	100	25v	9p
2-2	25v	10p	100	40v	10p
2-2	63v	8p	100	50v	13p
4-7	40v	8p	220	25v	11p
£2.00	10	25v	8p	220	40v
	20p	10	25v	220	14p
	20p	22	25v	1000	21p
	20p	22	40v	2200	39p
	20p	47	25v	4700	15v
	47	40v	9p	25v	45p

CAPACITORS—METALLISED POLYESTER

Stock values: MFD Price each

0.01, 0.015, 0.022, 0.033	4p
0.047, 0.068, 0.1	5p
0.150, 0.220	6p
0.33	8p
0.47	9p
2.0	12p
10	15p
1.5	22p
2.2	26p

Order as "Polyesters" + Capacitance.

CAPACITORS—POLYSTYRENE

Axial leads. Clear encapsulation, 5% Tolerance. 160 volt working. Stock values: Price each

10pF, 15pF, 22pF, 33pF, 47pF, 68pF, 100pF, 150pF, 220pF, 330pF, 470pF, 560pF, 680pF, 820pF, 1000pF, 1500pF, 2200pF, 3300pF, 4700pF, 5600pF, 6800pF	4p
--	----

Order as: "Polystyrene" + Capacitance.

NEW LOW PROFILE IC HOLDERS

14 pin DII 18p, 16 pin DII 25p, 8 pin DII 18p.

NYLON NUTS AND BOLTS

Chesse head screw bolts. Nuts with Integral washer. Moulded in high density nylon. Ideal for mounting "live" assemblies, power transistors, etc.</

LARGE STOCKS ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new & to makers specs.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power 80p
AC153K npn germanium low power 32p
AC176K npn germanium low power 32p
AD161 npn germanium medium power 42p
AD162 npn germanium medium power 40p
AF139 npn germanium UHF 48p
BC107 18p; BC109 12p; BC109 13p; } npn
BC167 11p; BC168 10p; BC169 11p; }
BC177 21p; BC178 19p; BC179 21p; } npn
BC257 12p; BC258 11p; BC259 18p; }
Standard groupings available.
BD135 npn med power 87p
BD136 npn med power 35p
DIODES
OA90, OA91, OA95 each 6p
OA200 9p; OA202 10p
Other semiconductor
AC128 17p; AF117 32p
BFY51 18p

Full lists and technical data will be found in Catalogue No. 6. See also amendments list.


SIEMENS THYRISTORS

0-8A 400V 56p, 600V 70p
3A 400V 80p, 600V 88p

ZENER DIODES full range E24 values: 400mW: 0.7V to 36V, 14p each; 1W: 0.8V to 83V, 21p each; 1.5W: 4.7V to 75V, 45p each. Clip to increase 1.5W rating to 3 watts (type 286F) 4p.

DIN PLUGS & SOCKETS

by Hirschmann, 4A rating

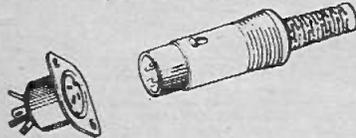

2 way LS—socket 10p; plug 12p. 3 way scr. socket 10p; plug 12p. 5 way scr. socket 13p; plug 15p.


TRANSISTOR ACCESSORIES

To3 cover 7p
Heat sinks 1°C/w, type 6W1, undrilled 60p Drilled 78p.

SWITCHES

TOGGLE SWITCHES

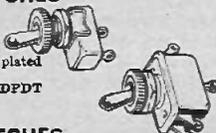101IC SPST toggle 20p;
409 DPDT toggle 29p. (These are chrome plated 2.5A rating);
7201 Sub-miniature DPDT 250V ac/2A 48p



ROTARY SWITCHES

Radiospares Miniature Make-switch (in assembly kit form) Shaft 6p;
Waters, MBB-2P5W, 1P11W; BBM-1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each 6p.

WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, each 24p



ELECTROLYTIC CAPACITORS

AXIAL LEAD Prices subject to amendment by the manufacturer.

Rated voltage: 3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity μ F							
0.47						10p	7p
1.0						7p	7p
2.2						7p	8p
4.7				10p		7p	7p
10				7p		7p	7p
22				7p		7p	8p
47	7p	7p	7p	7p	7p	7p	8p
100	8p	7p	7p	7p	7p	7p	11p
220	7p	8p	8p	8p	8p	10p	17p
470	8p	8p	9p	10p	12p	17p	24p
1000	10p	12p	12p	17p	20p	24p	40p
2200	14p	17p	22p	25p	35p	40p	
4700	25p	29p	37p	41p	54p		
10,000	40p	43p					

Polycarbonate —5% Tolerance

250V up to 0.1 μ F; 100V/0.1 μ F and above.
0-01; 0-012; 0-015; 0-018; 0-022;
0-027; 0-033; 0-047; 0-056; each 3p.
0-068; 0-082; 0-1; 0-12; each 4p
0-15 each 5p. 0-18; 0-22; each 6p.
0-27; 8p. 0-33; 8p. 0-39 8p. 0-47 8p.
0-56 12p. 0-68 13p. 1 μ F 14p.
Prices subject to amendment by the manufacturer.

SILVERED MICA non-polarised capacitors in 34 values from 2.2 pF to 680 pF, each 6p

RESISTORS 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 μ p
C	1/20W	5%	82 Ω —220K Ω	E12	9	8	7.5
C	1/8W	5%	4.7 Ω —470K Ω	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 Ω —10M Ω	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 Ω —10M Ω	E24	1.2	1	0.81 nett
C	1W	5%	4.7 Ω —10M Ω	E12	2.5	2	1.6 nett
MO	1/2W	2%	10 Ω —1M Ω	E24	4	3	2.3 nett
WW	1W	10% \pm 120 Ω	0.22 Ω —3.9 Ω	E12	9	5	7.5
WW	3W	5%	1 Ω —10K Ω	E12	7	6	6
WW	7W	5%	1 Ω —10K Ω	E12	9	8	7.5

Codes: C—carbon film, high stability, low noise.
MO—metal oxide, Electroval TR5, ultra low noise.
WW—wire wound, Pleesey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.


Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order).

* Please remember to add V.A.T. to your order.

If you have already got your No. 6 catalogue and want to know latest additional items and price amendments, send S.A.R. for special supplementary list.

KNOBS

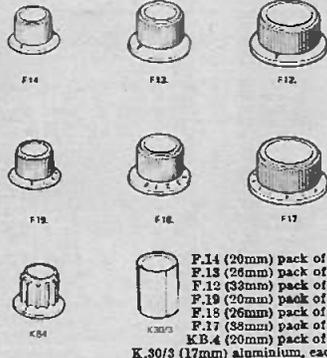All grub screw fitting for 1" shafts. Black. For other types—see Catalogue No. 6, P.54



F.14 (20mm) pack of 2 32p
F.15 (26mm) pack of 2 38p
F.12 (32mm) pack of 2 40p
F.19 (20mm) pack of 2 32p
F.18 (26mm) pack of 2 38p
F.17 (32mm) pack of 2 40p
K.B.4 (20mm) pack of 4 40p
K.30/3 (17mm) aluminium, each 24p

BAXANDALL SPEAKER KIT

Designed by P. J. Baxandall, of tone control circuit fame, and as described originally in *Wireless World*, this brilliantly designed economy speaker is simple to assemble and provides genuine hi-fi reproduction. Handles 10 watt and provides genuine hi-fi reproduction. Complete kit including pack-flat cabinet 18" x 12" x 10" £14.90, plus 60p part cost of carr. Equaliser assembly £2.00. Loudspeaker Unit 59ERM109 £2.45. Cabinet (to Baxandall design) £10.45

POTENTIOMETERS

Rotary carbon track, double wiper SINGLE P20 lin 100 Ω to 2.2M Ω 12p, P20 log 4.7K Ω to 2.2 meg, 12p
Dual gang lin 4.7K Ω to 2.2m Ω 42p
Dual log, 4.7K Ω to 2.2m Ω 42p; Log/antilog, 10K, 22K, 47K, 1M Ω only 42p; Dual anti-log, 10K only, 42p. Any of above types with 2A D.F. mains switch, 12p extra.
Only decades of 10, 22 & 47 available in ranges quoted.

DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.

SLIDER
Lin or log, 10K to 1meg, in all popular values, each 28p.
Escutcheons—White, grey, black, 10p each.
Control knobs: blk/white/red/yel/gr./blue/dk. grey/lt. grey, each 5p.

CARBON SKELETON PRE-SETS
Small high quality, PR lin: 100 Ω 220 Ω , 470 Ω , 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω . Vertical or horizontal mounting, 6p each.

All items offered for sale in accordance with our stated terms of business, copy of which available on request. Prices quoted DO NOT include V.A.T.
Orders from U.K. customers must be accompanied by an additional 10% of nett value for V.A.T.

DISCOUNTS Not allowed on nett price items. 10% on orders for 25 or more, 15% on orders for 115 or more. Prices subject to alteration without prior notice. PLEASE SEE LATEST AMENDMENT LIST. SEND S.A.E.

POSTAGE AND PACKING FREE
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.


U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. BOX 27, Swarthmore PA19081.

ELECTROVALUE

(Dept. E.E. 9) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 3603 Telex 264475

ENG. REG. NO. 104768. R.O. 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB

PREMIER 800 STEREO AMPLIFIER

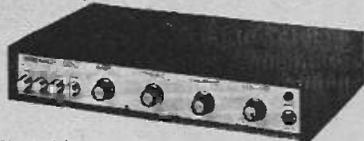

(As used in
SYSTEM '800')

A truly high quality stereo amplifier compares the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz — 2 db. Distortion: 1% Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch, Stereo headphone socket. Attractive slim line design teak cabinet with aluminium front panel. Size 12 1/2" x 6 1/2" x 2 1/2"

ONLY £17.85 Carr. 50p.

PREMIER PARAGON STEREO HI-FI AMPLIFIER



Gives the best possible reproduction of records, radio and tape at a reasonable price.

Fitted with all the controls and facilities you're ever likely to want, the Paragon gives you a degree of

sophistication that is usually only found with amplifiers costing twice its price. It has bass and treble slide controls, volume and balance knobs, and eight push-buttons. There's also a standard stereo jack socket on the front panel, plus a ceramic/magnetic cartridge switch and a mains outlet socket on the back panel. Specification: 10+10 watts into 8 ohms. Power/Frequency response: 0dB 10 watts into 8 ohms -3dB 20Hz -25KHz. Distortion typically less than 0.25%. Input for Magnetic phono (4mV) Ceramic phono (66mV) Radio/Tape (100mV). High and low filters. Teak finish cabinet. Size: 12 1/2" x 5 3/4" x 10 1/2".

£27.50 P. & P. 50p.

PREMIER STEREO SYSTEM '84'

Consists of the Premier Paragon Stereo Amplifier, Garrard SP25 III in teak finish plinth with cover and fitted Goldring G800 stereo magnetic cartridge plus a pair of Mareden Hall Annex 100 Loudspeaker Systems. Complete with Free leads and plugs. £64 Carr. & Insurance £1.75

SELMAR



STEREO CAR CASSETTE PLAYER WITH MW/LW RADIO

- ★ 7 watts per channel output
 - ★ 12V DC negative earth
 - ★ Speaker impedance 4 ohms. x 160mm. W. x 50mm. H.
- OUR PRICE
£41.00 P. & P. 50p
- ★ Measures 170mm. D.

MONATONE CAR STEREO CASSETTE PLAYER

- ★ Fast forward
- ★ Eject
- ★ 3 watts per channel output
- ★ 12V DC negative earth
- ★ Speaker impedance 8 ohms
- ★ Measures 175mm. D. x 152mm. W. x 50mm. H.
- ★ Matching pair of wedge-shaped speakers.




ONLY
£19.95 P. & P. 50p.

PREMIER HI-FI STEREO SYSTEMS

SYSTEM 'ONE'

Consists of the Premier 800 Mk II all transistor stereo amplifier (described left) Garrard auto/manual record player unit fitted stereo/mono cartridge with diamond stylus and mounted in teak finish plinth with cover and two cloth front loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 800 Mk II amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Mono/Stereo switch. Headphone socket. Power on/off. Teak finish cabinet with aluminium front panel. Size: 12 1/2" x 6 1/2" x 2 1/2".

£43.00
Carr. £1.75

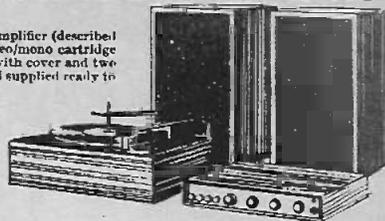

SYSTEM 'TWO'

As above but with slotted front teak finish loudspeakers. Garrard SP25 Mk III and magnetic cartridge.

£49.50
Carr. £1.75

FREE

STEREO HEADPHONES AND ALL LEADS AND PLUGS WITH ABOVE SYSTEMS

NEW PREMIER COMPACT STEREO SYSTEM




All transistor stereo amplifier mounted into teak finish plinth with cover and Garrard 2025 T/C autochanger and a pair of matching teak finish cloth front speaker systems.

- ★ Output 4 watts rms per channel.
 - ★ Separate volume, bass, treble and balance controls.
 - ★ Stereo/Mono ceramic cartridge.
 - ★ Tape/Tuner input and Tape output sockets.
 - ★ Complete with all leads ready to use.
- £31.00 Carr. & Ins. £1.50

STEREO HEADPHONE EXTENSION LEAD

15 foot curly cord. £1.50. P. & P. 10p.

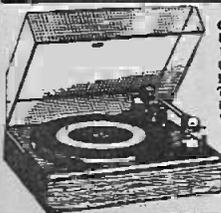

GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE. COMPLETE IN TEAK PLINTH WITH COVER.

PREMIER PRICE
£16.50
P. & P. £1



ONLY
£11.95 P. & P. 50p.

★ Tape eject button
★ Complete with microphone, batteries and handle



MODEL CT-330 MULTITESTER

The Model CT-330 Multitester is a de-luxe, accurate and high sensitivity instrument having many features which are desirable and required in testing modern electronic equipment. The Model CT-330 is very compact and of sturdy construction. Only the finest parts are used — 1% resistors, low-resistance selector switch, clear scales and rugged meter movement. Ranges: DC Voltages: 0, 0.6, 6, 30, 120, 600, 1,200, 3,000, 6,000V (20,000ohms/V). AC Voltages: 0, 6, 30, 120, 600, 1,200V (10,000 ohms/V). DC Current: 0, 0.6, 6, 60, 600mA. Resistance: 0, 6k, 60k, 6M, 60M (30, 3k, 30k, 300k ohms at centre scale). Capacity: 0-0.0005-0-0.1µF. 0-0.01-0-2µF. Decibels: —20 to +63dB.

£8.25
P. & P. 25p



MODEL 630 MULTITESTER

Ranges: DC Voltages: 0, 3, 15, 60, 300, 600, 1,200V (30,000 ohms/V). AC Voltages: 0, 6, 30, 120, 600, 1,200V (15,000 ohms/V). DC Current: 0, 0.03, 3, 30, 300mA. Resistance: 0, 16k, 160k, 1.6M, 16M ohms (10, 100, 10k, 100k ohms at centre scale). Decibels: —20 to +63dB.

£8.50 P. & P. 25p



MULTIMETER 20,000 O.P.V.

Compares with meters costing double its price. Features large easy-to-read meter, unusually high sensitivity—wide choice of ranges. With test leads, batteries and manual. Size: 4 1/2" x 3 1/2" x 1". Ranges: DC Voltages: 5, 25, 50, 500, 2,000V. (20,000 O.P.V.). AC Voltages: 10, 50, 100, 500, 1,000V (10,000 O.P.V.). DC Current: 50µA. 2.5, 250mA. Resistance: 6k, 6M ohms. Decibels: —20 to +22 db. Capacitance: 10µF to 0-100µF, 0-100µF to 0-1µF. Optional leather case. £5.90 P. & P. 25p

HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.



£2.25
P. & P. 25p.

COMPACT CASSETTES LOW-NOISE

Screw Fixing. Fully Guaranteed. In Library Cases.

	EACH	3 for	6 for	10 for
C80	31p	89p	£1.72	£2.76
C90	44p	£1.23	£2.38	£3.85
C120	57p	£1.54	£3.04	£4.85

P. & P. 10p each (3 and over 15p)

EMI LOW NOISE CASSETTES

Brand New in Library Cases

	C80 (List 71p) 48p	C90 (List 98p) 70p	C120 (List £1.48) 92p

P. & P. 15p

PREMIER RADIO

56 GEORGE STREET, LONDON W1H 5RH. TEL: 01-935 7917

ALL PRICES INCLUDE VAT

Also at:
23 Tottenham Court Road,
London W1P 9RA
Tel: 01-636 3451

- the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS

Code and Guaranteed	Pak No.	EQVT
T1 8 2G3713 OC71		
T2 8 2D1374 OC78		
T3 8 2D1216 OC81D		
T4 8 2G381T OC81		
T5 8 2G382T OC82		
T6 8 2G344B OC44		
T7 8 2G345B OC45		
T8 8 2G378 OC78		
T9 8 2G399A 2N1302		
T10 8 2G417 AP117		

All 55¢ each pak

HD 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for	20 For	55
BSX 21, C 407, 2N 1893	50 For	1.10
120vch.	100 For	1.82
	500 For	8.25
	1000 For	14.30

Sil. trans. suitable for P.C. Organ. Pkt. 10-18 Eqvt. ZTX300 6p each. Any Qty.

GP 100 TO3 METAL CASE SILICON

Vebo=10V, Vcco=50V. I.C.=10 amps. Ptot.=1.0w. hfe=30-170. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0.48	0.44	0.40

GP 300 TO3 METAL CASE SILICON

Vebo=100V, Vcco=60V P.C.=15 amps. Ptot.=1.1W. hfe=20, 100T.-1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1	25	100+
0.55	0.53	0.51

NEW 7th EDITION TRANSISTOR EQUIVALENTS BOOK

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. 90p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK.

SEND FOR FREE LIST.

UT 46 UNIJUNCTION TRANSISTORS

Direct replacement for T18 4trans. BEN 3000 also electrically equivalent to 2N2646

1	25	100+
0.30	0.28	0.22

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N706/8, BSY-2708/9SA. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Form. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

SIL. G.P. DIODES 5p

300mV	30.0	65
40V(Min.)	100.0	1.55
Sub-Min.	500.0	8.80
Fully Tested 1,000.0	9.90	

Ideal for Organ Builders.

R 3400 TO3 NPN SILICON HIGH VOLTAGE

Vebo=250V, Vcco=100V. I.C.=6 amps. Ptot.=20W. hfe=typ. 20 FT=5MHz.

1	25	100+
0.55	0.50	0.44

ADI61/162

M/P COMP GERM TRANS. OUR LOWEST PRICE OF 61p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS

in PRACTICAL ELECTRONICS RADIO CONSTRUCTOR

SILICON PHOTO TRANSISTOR TO-18 Lens and NPN Sim. to BPX25 and P21. BRAND NEW. Full data available. Fully guaranteed.

Qty. 1-24 25-99 100 up
Price. ea. 69p 44p 35p

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about IC's and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UK000	-12 x 7400	0.55	UIC46	-5 x 7446	0.55	UIC90	-5 x 7490	0.55
UK001	-12 x 7401	0.55	UIC45	-5 x 7445	0.55	UIC91	-5 x 7491	0.55
UK002	-12 x 7402	0.55	UIC50	-12 x 7450	0.65	UIC92	-5 x 7492	0.55
UK003	-12 x 7403	0.65	UIC31	-12 x 7451	0.65	UIC93	-5 x 7493	0.55
UK004	-12 x 7404	0.65	UIC53	-12 x 7453	0.65	UIC94	-5 x 7494	0.55
UK005	-12 x 7405	0.65	UIC34	-12 x 7454	0.65	UIC95	-5 x 7495	0.55
UK006	-8 x 7406	0.55	UIC80	-12 x 7460	0.55	UIC96	-5 x 7496	0.55
UK007	-8 x 7407	0.55	UIC70	-8 x 7470	0.55	UIC100	-5 x 74100	0.55
UK010	-12 x 7410	0.65	UIC72	-8 x 7472	0.55	UIC121	-5 x 74121	0.55
UK020	-12 x 7420	0.55	UIC73	-8 x 7473	0.55	UIC141	-5 x 74141	0.55
UK030	-12 x 7430	0.55	UIC74	-8 x 7474	0.55	UIC151	-5 x 74151	0.55
UK040	-12 x 7440	0.55	UIC76	-8 x 7476	0.55	UIC154	-5 x 74154	0.55
UIC41	-5 x 7441	0.65	UIC80	-6 x 7480	0.55	UIC193	-5 x 74193	0.55
UIC42	-5 x 7442	0.65	UIC81	-5 x 7481	0.55	UIC195	-5 x 74195	0.55
UIC43	-5 x 7443	0.65	UIC82	-5 x 7482	0.55	UIC21	-5 Assorted	74's 1-65
UIC44	-5 x 7444	0.65	UIC83	-5 x 7483	0.55			
UIC45	-5 x 7445	0.65	UIC86	-5 x 7486	0.55			

Packs cannot be split, but 25 assorted pieces (four mix) is available as PAK UIC N1.

2 Amp. BRIDGE RECTS.

50 v RMS	25p each
100 v RMS	40p ..
400 v RMS	50p ..
Size 16 mm x 16 mm.	

D1899 NPN SILICON DUAL TRANSISTOR

(Similar to 2N2060)	1	25	100+
	0.28	0.25	0.23

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 5p
Q1	20 Red spot transistors PNP	0.55
Q2	16 White spot R.F. transistors PNP	0.55
Q3	4 OC 77 type transistors	0.55
Q4	6 Matched transistors OC44/45/81/81D	0.55
Q5	4 OC 75 transistors	0.55
Q6	5 OC 72 transistors	0.55
Q7	4 AC 128 transistors PNP high gain.	0.55
Q8	4 AC 126 transistors PNP	0.55
Q9	7 OC 81 type transistors	0.55
Q10	7 OC 71 type transistors	0.55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0.55
Q12	3 OC 71 type transistors	0.55
Q13	3 AF 117 type transistors	0.55
Q14	3 OC 111 H.F. type transistors	0.55
Q15	7 2N2926 SIL. Epoxy transistors mixed colours	0.55
Q16	2 GPT980 low noise Germanium transistors	0.55
Q17	5 NPN 2 x ST.141 & 3 x BT.140.	0.55
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0.55
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0.55
Q20	4 OC 44 Germanium transistors A.F.	0.55
Q21	4 AC 127 NPN Germanium transistors	0.55
Q22	20 NKT transistors A.F. R.P. coded.	0.55
Q23	10 OA 202 Silicon diodes sub-min.	0.55
Q24	8 OA 81 diodes	0.66
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.55
Q26	8 OA85 Germanium diodes sub-min	0.55
Q27	2 10A PIV Silicon rectifiers 184.2SR.	0.55
Q28	2 Silicon power rectifiers BYZ 13.	0.55
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.55
Q30	7 Silicon switch transistors 2N706	0.55
Q31	6 Silicon switch transistors 2N708 NPN	0.55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.55
Q33	3 Silicon NPN transistors 2N1711, 0.55	
Q34	7 Silicon NPN transistors 2N2369, 500MHz. (code P397)	0.55
Q35	3 Silicon PNP TO-3, 2 x 2N2904 & 1 x 2N2905	0.55
Q36	7 2N3846 TO-18 plastic 800 MHz NPN	0.55
Q37	3 2N3053 NPN Silicon transistors	0.55
Q38	7 NPN transistors 4 x 2N3703, 0.55	
	2N5702	0.55

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:- Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and 'e' Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 22 cm x 4cm. Complete with case and instructions. Price each: 55-69

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-22V. 400mV (DO-7 Case) 15p ea. 1 1/2 (Top Hat) 20p ea. 10W (50-10 Stud) 55p ea.

NEW LOW PRICED TESTED S.C.R.'s

PIV 1A	3A	5A	5A	7A	10A	16A	30A
TO5	TO6T	TO6T	TO6T	TO4S	TO4S	TO4S	TO4S
50	0-28	0-28	0-32	0-32	0-65	0-59	1-27
100	0-28	0-37	0-52	0-52	0-64	0-70	1-54
200	0-39	0-41	0-54	0-54	0-63	0-67	0-83
400	0-48	0-52	0-62	0-62	0-74	0-83	1-03
800	0-59	0-63	0-75	0-75	0-85	1-07	1-38
800	0-70	0-77	0-88	0-88	0-99	1-32	1-65

F.E.T.'S

POST OFFICE TELEPHONE	2N3810 31p	2N5459 85p
DIALS 60p each.	2N3820 55p	2N5469 44p
	2N3821 30p	BFW10 66p
	2N3822 31p	MPP105 41p

CADMIUM CELLS

ORP12 48p
ORP60, ORP61 44p each

FREE

One 55p Pak of your own choice free with orders valued £5 or over

2N3055

115 WATT SIL POWER NPN 55p EACH

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price 5p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.55
U 2	60 Mixed Germanium Transistors AF/RP	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.55
U 4	40 Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 SIL Planar Trans. NPN, like BSY95A, 2N706	0.55
U 7	16 SIL Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0.55
U 8	50 SIL Planar Diodes TO-7 Glass 250mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.65
U10	20 BAY50 charge storage Diodes DO-7 Glass	0.55
U11	25 PNP SIL Planar Trans. TO-5 like 2N1132, 2N2904	0.55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0.55
U13	30 PNP-NPN SIL Transistors OC200 & 2N 104	0.55
U14	150 Mixed Silicon and Germanium Diodes	0.55
U15	25 NPN SIL Planar Trans. TO-5 like BFY61, 2N697	0.55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.55
U17	30 Germanium PNP AF Transistors TO-3 like AC127	0.55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.65
U19	25 Silicon NPN Transistors like BC108	0.55
U20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U21	30 AF. Germanium Alloy Transistors 26300 Series & OC71	0.55
U22	30 MADT'S like MHz Series PNP Transistors	0.55
U23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.55
U24	25 300 MHz NPN Silicon Transistors 2N708, BSF27	0.55
U25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U26	12 NPN Germanium AF Transistors TO-3 like AC127	0.55
U29	10 1 Amp SCR's TO-6 can, up to 600 PIV CR91/25-600	1-10
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0.55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0.55
U32	25 Zener Diodes 400mW DO-7 case 3-16 volts mixed	0.55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.55
U34	30 Silicon PNP Alloy Trans. TO-6 BCY26 28302/4	0.55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.55
U36	25 Silicon Planar NPN Transistors TO-3 BFY50/51/52	0.55
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0.55
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.55
U39	30 RF. Germ. PNP Transistors 2N1303/5 TO-3	0.55
U40	10 Dual Transistors 6 lead TO-5 2N2060	0.55
U41	25 RF Germanium Transistors TO-1, OC45, NKT72	0.55
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0.55
U43	25 SIL Trans. Plastic TO-18 A.F. BC119/114	0.55
U44	20 SIL Trans. Plastic TO-6 BC115/116	0.55
U45	7 SA SCR. TO66 up to 500PIV	1-10

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SIL. RECTS. TESTED

PIV 300mA	750mA	1A	1.5A	3A	10A	30A
50	0-04	0-06	0-06	0-08	0-16	0-23
100	0-04	0-07	0-06	0-15	0-18	0-26
200	0-06	0-10	0-07	0-16	0-22	0-27
400	0-07	0-15	0-09	0-22	0-30	0-41
600	0-08	0-18	0-11	0-26	0-35	0-50
800	0-11	0-19	0-12	0-28	0-41	0-61
1000	0-12	0-28	0-16	0-33	0-51	0-70
1200		0-37		0-42	0-63	0-83

DIACS TRIACS

FOR USE WITH TRIACS.	VBOM 2A	6A	10A
BR100 (D32) 41p each	100	33	55
	20		

Everyday Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p. extra. Semi-display—£6.00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisements Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

RECEIVERS and COMPONENTS

TUNBRIDGE WELLS, components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes Resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p. and p. c.w.o. to CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

MUST GO! Electronic components. Pots, resistors, capacitors, etc. Send large stamped, addressed envelope for list. P. FASOLI, 28 Middleham Street, Manchester M14 7NG.

CHRIS SMITH COMPONENTS. Veroboard holder 10 inches long 5p (as in E.E.). C60 Cassettes 26p. 2 station intercom £3 (Kit £2.50). DPDT slide-switches 10p. 5p for lists. Post 10p C.S.C. 31 Priory, Neston, Cheshire.

Computer Panels, 5-BC108, Diodes, 4-35p (10p)
Wire Ended Neons—10—50p (8p). Silicon Diodes 850V 1½A, 10-35p. (5p). 3 Ass. M.C. Meters 2"-3" £1-15 (25p). 100 Mixed Polystyrene/S. Mica caps 50pp Tagboards 20 way, 1½" between pins 15pp. Similar 12 way 13pp. Copper C. Paz Panels 5½" x 5½" 6-45 p.c.p. 7½" x 9½" 25 p.c.p. 6-£1.20c.p.
7lb Assorted components £1-60pp.
2lb Assorted computer panels £1-60pp.
J. W. B. RADIO
75 Hayfield Road, Salford 6 Lancs
Postage in brackets. Mail order only

SPECIAL resistor kit. ¼W Carbon Film 10 each £12 value. 22Ω to 2.2M. Total 610 for £3 p&p. 20p. NEK Electronics (E2), 28 Carnegie Road, St Albans, Herts.

Express Components

E.E. PROJECTS!

General Purpose Amp £4.50

20W Shaver Inverter £4.00

Beta Component Board
(Kit only) £1.30

Beta Transformer M218 £1.85

WAA-WAA

SEND AMOUNT SHOWN IN COST BOX TO RECEIVE KIT.

FREE POSTAGE (U.K. only)

17 Albert Sq. London, E15 1JH

BOOKS

WORLD RADIO TV HANDBOOK 1974 (published December), £3.15! Delivered direct from Denmark if ordered now! How to Listen to the World (late October), £2! Postage and VAT included! Every order acknowledged immediately! David McGarva, PO Box 114, Edinburgh EH1 1HP.

RADIO BOOK SERVICE

Handbk of Transistor Equip & Substitutes..... 45p
Boys Bk of Crystal Sets and Simple Circuits..... 23p
How to make FM & TV Aerials, Bands 1,2,3..... 23p
Radio Servicing for Amateurs..... 25p
Transistor Test Equip & Servicing Manual..... 30p
Transit Circuits for Radio Controlled Models..... 45p
Modern Transistor Circuits for Beginners..... 45p
Practical Transistor Novelty Circuits..... 45p
Manual of Electronic Circuits for the Home..... 55p
All prices include postage & packing

Dept E. 40 Elwill Way, Beckenham BR3 2RZ

EDUCATIONAL

TECHNICAL TRAINING in Radio, TV & Electronics thro' world-famous ICS. For details of proven home-study courses write ICS (Dept. 731X), Intertext House, London SW8.

FOR SALE

TIMBER Plywood cut to your requirements. **GENERAL WOODWORK SUPPLIES**, 76-80, Stoke Newington High Street, N16 5BR.

ALL BACK COPIES of Everyday Electronics offers. 12 Birch Drive, Billingham, Sussex. Phone 2248.

EXPERIMENTERS! Hundreds of unusual items cheap. Catalogue 5½p. Grimsby Electronics, 64 Tennyson Road, Cleethorpes, Lincs. (Mail Order Only).

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide, S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

MISCELLANEOUS

OMNI-DETECTORS

(Featured ★ TV ★ Radio ★ Nat. Press)
Ancient art of Dowsing in Modern Guise. Thrill to new discovery in this over-looked aspect of the Electro-Magnetic Spectrum. A LABORATORY IN A SINGLE PACK. Treasure Hunter! Use Omni-Detectors to—
• Locate ANY buried substance, ANY depth.
• Save hours of fruitless searching—MAP-DOWSING pinpoint search area before you leave home.
• Limitless other uses.
Dowsing used in World War 2 and by USA troops in Vietnam to locate underground springs, tunnels, mines.
Send only £2.40 + 15p p. & p. for unique pack of 4 dowsing instruments (non-electronic) and explicit 40-page manual to sole suppliers—Omni-Detector Co., (Dept. EE), 27, Latham Road, Twickenham, Middx. TW1 1BN.

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warks.

BATTERY ELIMINATOR KITS. Our well-known Mini Mains Pack Kits now complete with drilled insulated base 32 x 55mm. Fits into space of most large transistor batteries. Easy wiring instructions. Safe, silent mains transformer, silicon rects, smoothing capacitor, all top grade. For any ONE of these voltages (state which): 3V, 300mA max.; 6V, 180mA; 9V, 120mA; 18V, 60mA. £1.50 VAT included. By mail only, UK post 5p. Amatronics Ltd., 396 Selsdon Rd., South Croydon, Surrey CR2 0DE.

RADIO & TELEVISION AERIAL BOOSTERS £2.95p, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. **UHF-VHF** televisions £7.50, carr. £1.50. S.A.E. for 3 leaflets. **ELECTRONIC MAIL ORDER (BURY) LTD.**, Bridge Street, Ramsbottom, Bury, Lancs.

BEGINNERS, we exist for you. Instruction, components, construction kits. Send S.A.E. to Electrolern, Lyburn Lodge, Normansland, Wiltshire.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ **Pocket-sized MAXI-VOLT** Big ¼ inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (85g.) send £1.35 for your Maxi-Volt now!

★ **Unique TRANSMITTER/RECEIVER Kit**. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5.90 for yours now!

★ **Psychedelic MINI-STROBE Kit**. Take a pocket-sized lightning storm to Disco's and parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £2.20 now!

(All prices include V.A.T., packing, and postage.)

Send reference to:

BOFFIN PROJECTS,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY
(Mail order only)

Or for more details, send 15p for lists, plus free design project sheet.

LOW-COST I.C. MOUNTING. I.C. socket pins in lengths of 100 pins for 60p (p & p 5p). S.A.E. details and sample. Gaskell, Oak Lodge, Tansley, Derbyshire.

P.E. SYNTHESISER KNOB KIT

Complete kit as Feb. issue £3.91 post free
43 knobs, 7 calibrated discs.
DE LUXE KIT as above but £5.89 post free
calibrated for programming

Inclusive postage and V.A.T.

RE-AN PRODUCTS LTD.
Burnham Road, Dartford, Kent
Tel.: Dartford 20705

ELECTRONI-KIT

EDUCATIONAL FUN FOR ALL AGES 7 to 70

Click together electronic kit makes THIRTY different working projects—Transistor RADIOS, microphones, amplifiers, alarms, Morse code, etc.

COMPLETELY SAFE, INSTRUCTIVE & FASCINATING


Beautifully produced electronic transistors and components encapsulated in transparent plastic block form plus all accessories. NO SOLDERING, wiring or screwing.

HIGHLY INSTRUCTIVE 90 PAGE CIRCUIT & DATA MANUAL INCLUDED

£6.95 per complete Kit inc. Battery, p & p.
Other Kits too — 16 Projects £4.95; 100 — £14.50 etc.

Satisfaction guaranteed. Special quotations for Educational Authorities on request.

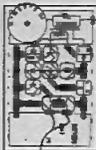Cheque or P.O. (or SAE for catalogue) to: **ELECTRONI-KIT**, 34, Brookfield, West Hill, Highgate, London, N.6. Mail order only.



COMPUTER PANELS

Type E: 4 OC29, 4 ACY19, 8 other transistors 35 diodes etc £1(10p); Type H; 12 ASZ20 + 176 other components 66p(10p); Type M: 17 silicon transistors, 2 trim pots, etc 50p (8p). 12 High quality panels including IC's, trim pots, power transistors etc £2(25p); 3lbs lower quality £1(25p); 7lbs £2(40p); 5lbs £12(6p). **COMPUTER TAPE**: 7" x 1200" on 7" NAB spool 68p (25p). 2" x 1800" on 10 1/2" NAB spool in case 68p (40p).

71b BARGAIN PARCELS

Hundreds of NEW resistors, capacitors, pots, switches, crystals, PC boards etc. loads of odds & ends. Only £1-65(37p).

CASED AMPLIFIERS

4 valve amplifier with tone and volume controls giving 3 watts output into the 7x4" 3 speaker. Oak-faced cabinet 14 x 13 x 9" also contains non-standard tape deck. Mains operated, tested in good working condition. Only £3 (£1 up to 200 miles, £1-20 over). Suitable cassettes £1(25p); spares heads 40p, ICT 1500 computer. All parts available. Decks from £15.

NEW COMPONENTS: 741C 32p, BC107 8p; 2N3055 35p; OC140 25p; OC170 15p; BCY72 8p. **VAT NOT INCLUDED—ADD 10% TO TOTAL.** Carriage in brackets, small parts 4p. SAE list, enquiries.

GREENWELD ELECTRONICS [EE7]

24 Goodhart Way, West Wickham, Kent
Shop at 21 Deptford Broadway, SE8
Tel: 01-692 2099 and 38 Lower Addiscombe Rd., Croydon. Callers most welcome.

BUILD THE

TREASURE TRACER MK III Metal Locator



- Variable tuning
 - Excellent sensitivity and stability
 - Weighs only 22oz.
 - Speaker and earphone operation
 - Knocks down to only 17in.
 - Prebuilt search coil assembly
 - Ministry approved design
 - Thoroughly professional finish
 - You only need soldering iron, screwdriver, pliers and snips
 - Completely new design
- Send s.a.e. for leaflet

Complete £9-80
Post 35p

Built, tested and guaranteed £13-75
Post 35p

MINIKITS ELECTRONICS, 35a LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN. (Mail order only)

PLEASE BE SURE
TO
MENTION

EVERYDAY ELECTRONICS

when replying to
advertisements

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEARLY
HUMANLY
TIGHT!
DISCOUNT
PRICES



Newest, neatest system ever devised for storing small parts and components; resistors, capacitors, diodes, transistors, etc.

Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots; 1D 2D have removable Space divider. Build up any size cabinet for wall, bench or table top. **SINGLE UNITS** (5" x 2 3/4" x 2 1/2") £1.25 Dozen. **DOUBLE UNITS** £2.10 Dozen. **TREBLE** (3D) £2.20 for 8. **DOUBLE TREBLE** 2 drawers in one outer case (6D) £3.25 for 8. **EXTRA LARGE SIZE** (6D1) £3.10 for 8.

PLUS QUANTITY DISCOUNTS! Order £6 and over Deduct 5% in the £. Order £10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £. Pack./Post Carr.: Add 35p to all orders under £10. Orders over £10 P.P.C. free.

PLEASE ADD 10% VAT TO TOTAL REMITTANCE

(Dept EE11), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844.

IVORYET LIMITED

SINCLAIR EQUIPMENT



Project 60 FM Tuner £15.95 (£1-85)
2 Z30/Stereo 60/PZ5 £16.75 (£2-05)
2 Z30/Stereo 60/PZ6 £18.85 (£2-25)
2 Z50/Stereo 60/PZ8/Trans £23.20 (£2-70)
Z50 £3-50 (55p) Stereo 60 £7-80 (98p)
Z50 £4-30 (63p) Trans for PZ8 £2-95 (50p)
PZ5 £3-47 (57p) 2000 Amp £22-00 (£2-70)
PZ6 £8-30 (83p) 3000 Amp £31-50 (£3-35)
AFU £4-40 (64p) 2000 Tuner £27-00 (£2-90)
PZ8 £8-40 (84p) 3000 Tuner £27-00 (£2-90)
Q16 £5-90 (79p) Project 60S £20-98 (£2-40)

PROJECT 60 KIT £2-70 (49p)
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuse-holder needed to complete Project 60.

BATTERY ELIMINATOR BARGAIN £3-60 (58p)
Introducing the most versatile battery

eliminator ever offered, with a high current output that makes it suitable for operating most battery tape recorders, record players, cassette recorders and shavers. Input 200/240V. Output voltage selected by front panel switch may be set to 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500mA.



IC RADIO CHIP TBA651 £2-10 (32p)
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2-10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1-75 (29p).


S-DECS AND T-DECS

S-DECS £1-44 (25p)

T-DECS £2-88 (40p)


µ-DEC A £3-18 (43p)

16 dll IC carriers £1-20 (17p)

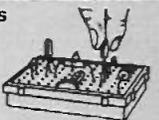

SINCLAIR SUPER IC12 £2-10 (43p)

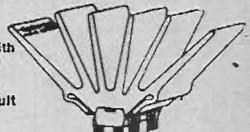Supplied complete with free 44 page instruction booklet and printed circuit



DELUXE KIT
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-85 (28p). Stereo model with balance control £3-56 (46p).

BASIC KIT FOR THE IC12
Contains components for P.C. board and volume and simple tone controls. Mono version £1-25 (24p). Stereo model with balance control £2-90 (40p).

IC12 POWER KIT
A set of components to construct a 28V 0.5 Amp power supply £2-47 (50p).

LOUDSPEAKERS FOR THE IC12
5" 8 ohm £1-10 (27p). 5" x 8" 8 ohm £1-55 (37p). 10" x 6" 15 ohm £2-20 (44p).

PREAMPLIFIER KITS FOR THE IC12
Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1-30 (24p). Stereo model £2-30 (24p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1-20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

SINCLAIR EXECUTIVE CALCULATOR



NOW ONLY £38 00 (£4 00).

SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Mail order only. No callers, please.

BRAND NEW SEMICONDUCTORS AND COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS		TTL LOGIC I.C.'s	
2N301	0.15 2N3405 0.27	80381	0.43 BC125 0.11
2N302	0.15 2N3414 0.10	80382	0.43 BC136 0.15
2N303	0.25 2N3415 0.10	80383	0.61 BC137 0.15
2N306	0.25 2N3416 0.11	80384	0.58 BC140 0.24
2N309	0.30 2N3417 0.23	80385	0.65 BC141 0.39
2N343B	0.25 2N3570 1.25	80386	0.44 BC142 0.24
2G247	0.15 2N3571 1.12	80387	0.33 BC143 0.21
2G274	0.15 2N3572 0.97	80388	0.50 BC144 0.24
2N374	1.45 2N3703 0.13	80389	0.27 BC145 0.21
2N404	0.43 2N3703 0.11	80390	0.27 BC147 0.12
2N456	0.75 2N3704 0.14	80391	2.00 BC148 0.12
2N456A	0.75 2N3705 0.10	80392	0.18 BC149 0.18
2N467A	0.80 2N3706 0.09	80393	0.18 BC153 0.18
2N491	3.25 2N3707 0.13	80394	0.44 BC154 0.18
2N495	0.15 2N3709 0.07	80395	0.89 BC157 0.14
2N498	0.15 2N3710 0.12	80396	0.18 BC158 0.18
2N499	0.29 2N3711 0.08	80397	0.46 BC159 0.14
2N706	0.10 2N3712 0.06	80398	0.58 BC160 0.37
2N706A	0.12 2N3713 1.08	80399	0.56 BC167A 0.11
2N708	0.13 2N3714 1.15	80400	0.11 BC168B 0.13
2N709	0.28 2N3715 0.12	80401	0.25 BC169C 0.11
2N711	0.80 2N3716 1.00	80402	0.16 BC170 0.11
2N718	0.21 2N3718 3.00	80403	0.20 BC171 0.18
2N719A	0.30 2N3719 3.15	80404	0.13 BC172 0.11
2N720	0.60 2N3790 2.20	80405	0.10 BC173 0.15
2N721	0.55 2N3791 2.08	80406	0.20 BC174 0.11
2N742	0.22 2N3793 2.05	80407	0.20 BC175 0.11
2N816	0.17 2N3792 2.20	80408	0.09 BC182 0.09
2N818	0.30 2N3794 0.10	80409	0.00 BC183L 0.00
2N829	0.14 2N3819 0.32	80410	0.25 BC184 0.11
2N830	0.14 2N3820 0.47	80411	0.11 BC184L 0.11
2N1099	0.28 2N3823 0.97	80412	0.25 BC185 0.25
2N1091	0.28 2N3824 0.75	80413	0.25 BC186 0.25
2N1131	0.20 2N3825 0.23	80414	0.20 BC187 0.12
2N1132	0.20 2N3826 0.16	80415	0.18 BC188 0.18
2N1302	0.16 2N3825A 0.16	80416	0.20 BC189 0.20
2N1303	0.16 2N3825B 0.16	80417	0.20 BC190 0.20
2N1304	0.20 2N3826A 0.16	80418	0.18 BC191 0.18
2N1305	0.20 2N3826B 0.16	80419	0.18 BC192 0.18
2N1306	0.22 2N3827 0.16	80420	0.18 BC193 0.18
2N1307	0.22 2N3828 0.16	80421	0.18 BC194 0.18
2N1308	0.25 2N3829 0.16	80422	0.18 BC195 0.18
2N1309	0.25 2N3830 0.16	80423	0.18 BC196 0.18
2N1383	0.80 2N3831 0.18	80424	0.18 BC197 0.18
2N1507	0.18 2N3860 0.18	80425	0.18 BC198 0.18
2N1613	0.20 2N3866 0.20	80426	0.18 BC199 0.18
2N1631	0.38 2N3877 0.26	80427	0.18 BC200 0.18
2N1637	0.38 2N3877A 0.26	80428	0.18 BC201 0.18
2N1639	0.32 2N3900 0.20	80429	0.18 BC202 0.18
2N1701	1.10 2N3906A 0.21	80430	0.18 BC203 0.18
2N1792	2.15 2N3901 0.32	80431	0.18 BC204 0.18
2N1711	0.40 2N3902 0.24	80432	0.18 BC205 0.18
2N1893	0.34 2N3904 0.17	80433	0.18 BC206 0.18
2N2102	0.30 2N3905 0.21	80434	0.18 BC207 0.18
2N2147	0.70 2N3906 0.22	80435	0.18 BC208 0.18
2N2148	0.94 2N4036 0.46	80436	0.18 BC209 0.18
2N2122	0.40 2N4037 0.42	80437	0.18 BC210 0.18
2N2123	0.40 2N4038 0.42	80438	0.18 BC211 0.18
2N2193	0.61 2N4060 0.11	80439	0.18 BC212 0.18
2N2194	0.27 2N4061 0.11	80440	0.18 BC213 0.18
2N2195A	0.30 2N4062 0.11	80441	0.18 BC214 0.18
2N2195B	0.37 2N4063 0.25	80442	0.18 BC215 0.18
2N2195C	0.40 2N4064 0.15	80443	0.18 BC216 0.18
2N2196A	0.37 2N4065 0.17	80444	0.18 BC217 0.18
2N2196B	0.37 2N4066 0.17	80445	0.18 BC218 0.18
2N2196C	0.37 2N4067 0.17	80446	0.18 BC219 0.18
2N2196D	0.37 2N4068 0.17	80447	0.18 BC220 0.18
2N2196E	0.37 2N4069 0.17	80448	0.18 BC221 0.18
2N2196F	0.37 2N4070 0.17	80449	0.18 BC222 0.18
2N2196G	0.37 2N4071 0.17	80450	0.18 BC223 0.18
2N2196H	0.37 2N4072 0.17	80451	0.18 BC224 0.18
2N2196I	0.37 2N4073 0.17	80452	0.18 BC225 0.18
2N2196J	0.37 2N4074 0.17	80453	0.18 BC226 0.18
2N2196K	0.37 2N4075 0.17	80454	0.18 BC227 0.18
2N2196L	0.37 2N4076 0.17	80455	0.18 BC228 0.18
2N2196M	0.37 2N4077 0.17	80456	0.18 BC229 0.18
2N2196N	0.37 2N4078 0.17	80457	0.18 BC230 0.18
2N2196O	0.37 2N4079 0.17	80458	0.18 BC231 0.18
2N2196P	0.37 2N4080 0.17	80459	0.18 BC232 0.18
2N2196Q	0.37 2N4081 0.17	80460	0.18 BC233 0.18
2N2196R	0.37 2N4082 0.17	80461	0.18 BC234 0.18
2N2196S	0.37 2N4083 0.17	80462	0.18 BC235 0.18
2N2196T	0.37 2N4084 0.17	80463	0.18 BC236 0.18
2N2196U	0.37 2N4085 0.17	80464	0.18 BC237 0.18
2N2196V	0.37 2N4086 0.17	80465	0.18 BC238 0.18
2N2196W	0.37 2N4087 0.17	80466	0.18 BC239 0.18
2N2196X	0.37 2N4088 0.17	80467	0.18 BC240 0.18
2N2196Y	0.37 2N4089 0.17	80468	0.18 BC241 0.18
2N2196Z	0.37 2N4090 0.17	80469	0.18 BC242 0.18
2N2197	0.37 2N4091 0.17	80470	0.18 BC243 0.18
2N2198	0.37 2N4092 0.17	80471	0.18 BC244 0.18
2N2199	0.37 2N4093 0.17	80472	0.18 BC245 0.18
2N2283	0.37 2N4177 0.17	80556	0.18 BC329 0.18

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course" - Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects" - Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold" - Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T., Dept. BEE22, Aldermaston Court, Reading RG7 4PF.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

CUT OUT THIS COUPON
Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL A.M.S.E. (Mech.) Boiler Inspect. & Operation C & G Eng. Crafts C & G Fabricat. Diesel Eng. Eng. Inspection Eng. Metallurgy Inst. Eng. & Tech. Inst. Motor Ind. Mainten. Eng. Mechanical Eng. Sheet Metal Work Welding	<input type="checkbox"/> Man. Prod. -cont. Quality Control Salesmanship Storekeeping Work Study Works Management	<input type="checkbox"/> Draughtsmanship A.M.I.E.D. Design of Elec. Machines Die & Press Tool Design Electrical Draughtsmanship Gen. Draughtsmanship Jig & Tool Des. Tech. Drawing	<input type="checkbox"/> Construction-cont. Building Building Drawing Build. Foreman Carpentry & Join. Civil & Municipal Engineering Construction Engineering Construction Surveyors Institute Clerk of Works Council Eng. Geology Hydraulics Inst. of Builders Inst. Works & Highway Sup. Painting & Dec. Public Hygiene Road Engineer. Structural Eng. Surveying
<input type="checkbox"/> ELECTRICAL & ELECTRONIC A.M.S.E. (Elec.) C & G Elec. Eng. C & G Elec. Inst. C & G Elec. Tech. Computer Elect. Elec. Maths Elec. Science Electronic Eng. Electrical Eng. Install. & Wiring Meters & Measuring Instruments	<input type="checkbox"/> RADIO & TELECOMMUNICATIONS Colour TV C & G Radio/TV/Electronics C & G Telecomm. Tech. Frac. Rad. Elec. (with kit) Radio Amateurs Exam. Radio Servicing & Repairs Radio & TV Eng. Trans. Course TV Main. & Serv.	<input type="checkbox"/> RADIO & TELECOMMUNICATIONS Colour TV C & G Radio/TV/Electronics C & G Telecomm. Tech. Frac. Rad. Elec. (with kit) Radio Amateurs Exam. Radio Servicing & Repairs Radio & TV Eng. Trans. Course TV Main. & Serv.	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Inst. Farm Science General Educat. Gen. Plastics Pract. Maths Pract. Slide Rule Pure & Applied Maths Refrigeration Rubber Tech. Sales Engineers Tech. Report Writing Timber Trade University Ent.
<input type="checkbox"/> MANAGEMENT & PRODUCTION Auto. Control Computer Prog. Electronic Data Processing Estimating Foremanship Inst. Cost & Man. Accountants Inst. Marketing Management Metrication Motor Trade Man. Network Plan. Motor Vehicle Operatiional Cont. Operational Research Personnel Man. Planning Eng. Production Eng.	<input type="checkbox"/> AUTO & AERO Aero Eng. A.M.I.M.I. A.E.C. Cert. Auto Engineer. Auto Repair C & G Auto. Eng. Garage Management M.A.A./M.I. Dipl. Motor Vehicle Mechanics	<input type="checkbox"/> CONSTRUCTIONAL A.M.S.E. (Civil) Architecture	<input type="checkbox"/> G.C.E. 58 'O' & 'A' LEVELS SUBJECTS Over 10,000 group passes

Coaching for many major exams, including C & G and assistance in ONC/HNC.

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BEE22 Aldermaston Court, Reading RG7 4PF

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Mrs P. Pitt

Henry's

DONT RELY ON YOUR MEMORY BUY NOW AT BARGAIN PRICES
Order your latest Henry's Catalogue Price 55p post paid complete with Discount Vouchers



You pay less VAT with Henry's Low Prices

BUILD THE TEXAN

20 + 20 WATT IC STEREO AMPLIFIER
As featured by Practical Wireless 1972



Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6-IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES, On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector, Mag. P.U., Radio Tuner, Aux.** Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21 30p. Distributed by Henry's throughout UK. FREE—Teak cabinet with complete kit.

Kit price **£28.50** (+VAT +50p carr/packing) or built and tested **£35.00** (+VAT +50p carr/packing) as illustrated.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe.



KIT PRICE **£21.00** (+ VAT) or built and tested **£24.95** (+ VAT)

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN 1/4 REC. PRICES

	3 for	6 for	10 for	25 for
C 60	£1.00	£1.80	£2.80	£6.75
C 90	£1.33	£2.57	£4.20	£10.25
C 120	£1.62	£3.15	£5.00	£12.25

Quantity and trade enquiries, invited




LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian £1.36 per course. £5 for any 4.

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98.50**
- 100 watt amplifier for above **£38.75**
- SL100 100 watt mixer/amplifier with slider controls **£69.00**
- R50 50 watt mixer/amplifier **£49.50**
- DISCO AMP 100 watt mixer/amplifier chassis unit. **£65.85**
- DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers)
- SDL1 (rotary controls) **£49.50**
- SDL11 (slider controls) **£58.50**
- DISCO VOX (slider controls) the complete disco unit **£69.50**
- DJ100 100 watt power amplifier for above **£38.75**
- DJ30L 3 channel 3kw sound to light **£29.50**
- DJ40L as 30L plus built in microphone **£38.75**
- DIMANATIC 1 kW adjustable speed auto dimmer **£25.00**
- SCENE STROBE **£19.00**. ROAD STROBE **£25.00**
- DISCO anti-feedback microphone **£11.95**
- Colt 150 watt liquid wheel projector **£22.50**
- 150 watt Q1 liquid wheel projector **£50.00**
- 150 watt Q1 cassette wheel projector **£30.00**
- Spare Effects cassettes large range of patterns **£8.00**
- Mini spot bank fitted 3 lamps **£11.00**
- Auto Trillite (mini with flashers) **£17.00**
- Mixers/Mics/Speakers/Lighting UK'S LARGEST RANGE.

FREE stock list ref. No. 18 on request.

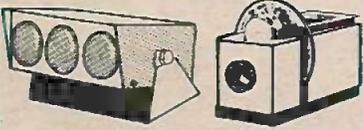

TEXAN STEREO SYSTEM PLUS PRICE SAVINGS



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems size 21" x 12" x 10" and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

System 25 (list approx. £109) **£79.50**
System 76 (list approx. £117) **£89.50**
(plus 10% VAT and plus £1.45 carr/packing)

Barclaycard/Access, call, write or phone, your order 01 402 4736 EASY TERMS FOR CALLERS

- KITS—TEST GEAR—AMPLIFIERS—SPEAKERS—DECKS—POWER SUPPLIES—TRANSISTORS—IC'S

See pages 584—586 of this magazine

LOW COST HI-FI SPEAKERS

SPECIAL OFFERS

- EMI 13" x 8" full range speakers (post 20p each or 30p pair)
- *150TC—8 ohms Twin Cone 10 watt £2.20 each or £4.00 pair.
- *450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms £3.50 each or £6.90 pair.
- EW 15 watt 8 ohms C/o Tweeter £4.30 each or £7.90 pair.
- 350 20 watt C/o Tweeters 8 or 15 ohms £7.50 each or £14.20 pair.
- * Polished wood cabinet £4.60 post 35p.



8 ohms full range (post 20p)			
FR4	5 watt		£4.00
FR5	10 watt		£5.50
FR8	15 watt		£7.60
FR23	15 watt		£6.00
BASS & MID RANGE—8 ohms (post 20p)			
AA12	5" 15 watt		£3.20
B110	5 1/2" 15 watt		£5.60
B200	8" 15 watt		£6.45
B139/2	13" x 8" 30 watt LF		£10.25
TWEETERS AND CROSSOVERS (post 20p)			
K2006	10 watt	8 or 15 ohms	£1.90
PH16	15 watt	8 ohms	£3.20
K2011	30 watt	8 ohms	£3.75
T27	KEF		£4.25
Accent 100	30 watt	8 ohms	£4.90
K4009	1kHz/5kHz C/o		£2.00
SN75	3kHz var. C/o		£1.75
SPEAKER KITS (carr. etc. 35p)			
20-2	8" 30 watt		£10.00 each
20-3	4" 40 watt		£15.00 each
LINTON 2	8" 20 watt		£15.95 pair
GLENDALE 3	30 watt		£28.95 pair
DOVEDALE 3	50 watt		£42.00 pair
KEF KK2			£70.40 each
KEF KK3			£32.00 each

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/4" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines etc.



£24.95 Also available assembled ready to use. **£27.22** + VAT. + VAT.

All prices carr. paid (UK) (VAT EXTRA)
Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

10% VAT to be added to all orders. Prices and descriptions correct at time of press. E & OE.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open: 9 am-6 pm
6 days a week
All stores open all day Saturday