

An exciting hobby.... for everyone

PAGE 11

JULY 74

20p

# everyday electronics

## TELEPHONE CALL CHARGE CALCULATOR

Australia 40c  
New Zealand 45c  
South Africa 40c  
Malaysia \$1.80  
Sweden Kr.3.50  
MkTB 22cs



ALL  
INEXPENSIVE  
AND EASY TO  
BUILD

## AUTOMATIC LIGHT LEVEL CONTROLLER



**FREE** ENTRY  
**COMPETITION**

*Your last chance  
to win a...*

**Multimeter**


**GENERAL PURPOSE  
5WATT AMPLIFIER**


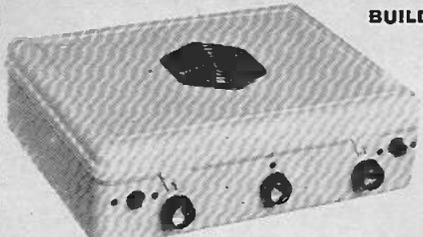
# NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT.

BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER.




- ★ 4 Transistor Earpiece Radio ★ Signal Tracer ★ Signal Injector ★ Transistor Tester NPN-PNP ★ 4 Transistor Push Pull Amplifier ★ 5 Transistor Loudspeaker Radio MW/LW ★ 7 Transistor Loudspeaker Radio MW/LW ★ 5 Transistor Short Wave Radio ★ Electronic Metronome ★ Electronic Noise Generator ★ Batteryless Crystal Radio ★ One Transistor Radio ★ 2 Transistor Regenerative Radio ★ 3 Transistor Regenerative Radio ★ Audible Continuity Tester ★ Sensitive Pre-Amplifier.

Total Building Costs

**£7.23** P.P. & Ins. 44p.  
(Overseas P & P  
£1-85p.)  
(+ 10% VAT 72p)

- ★ 24 Resistors ★ 21 Capacitors ★ 10 Transistor★ 21 loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12-way connectors ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs ★ Ready Wound Coils ★ Ferrite Rod ★ 6½ yards of wire ★ 1 yard of sleeving, etc. ★ Parts price list and plans 50p (FREE with parts).

## NEW ROAMER NINE

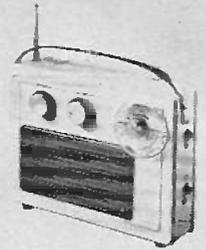


WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten, built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for V.H.F. and SW. Push Pull output using 600 mw transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange control. Attractive all white case with red grille and carrying strap. Size 9½" x 7" x 2½" approx. Parts Price list and Plans 50p (FREE with parts)

Total Building Costs **£6.95** P.P. & Ins. 44p.  
(Overseas P & P £1-85p.)  
(+ 10% VAT 69p)
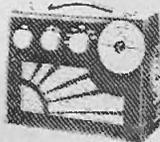
## ROAMER TEN

with VHF including aircraft, 10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers, 9 Tunable Wavebands, MWL, MWE, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band, Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600 mw Transistors. Car Aerial and Tape Recording Sockets. 10 Transistors plus 3 Diodes. Gauged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off, Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts). Total building costs **£8.50** P.P. & Ins. 52p.  
(Overseas P & P. £1-85) (+ 10% VAT 85p)



## NEW EVERYDAY SERIES

Build this exciting New series of designs  
E.V. 5 6 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5½" x 2½" approx. Parts price list and Plans 15p. Free with parts.  
Total Building Costs **£2.95** P.P. & Ins. 30p.  
(Overseas P & P £1-25p.)  
(+ 10% VAT 29p)



E.V. 6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts price list and Plans 15p. Free with parts.  
Total Building Costs **£3.60** P.P. & Ins. 30p.  
(Overseas P & P £1-25p.)  
(+ 10% VAT 36p)

E.V. 7 Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" loudspeaker. Parts price list and easy build plans 20p. Free with parts.  
Total Building Costs **£4.08** P.P. & Ins. 31p.  
(Overseas P & P £1-85) (+ 10% VAT 40p)

## ROAMER EIGHT Mk 1 NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet Loudspeakers. Air spaced gauged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).  
Total Building Costs **£6.98** P.P. & Ins. 47p.  
(Overseas P. & P. £1-85) (+ 10% VAT 69p)



## "EDU-KIT"



Build Radios, Amplifiers, etc from easy stage diagrams, Five

units including master unit to construct

Components include:  
Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine 5" Tone Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three ½" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).


Total Building Costs **£5.50** P.P. & Ins. 35p.  
(Overseas P & P £1-85) (+ 10% VAT 65p)

## ROAMER SIX Case and looks as Trans-Eight

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3, Trawler band plus an Extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. Six Speaker, 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6½ x 2½in. approx. Plans and parts price list 25p (FREE with parts).  
Total Building Costs **£3.98** P.P. & Ins. 31p.  
(Overseas P. & P. £1-85) (+ 10% VAT 39p)
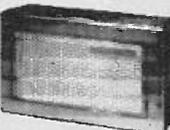
## POCKET FIVE

3 Tunable waveband. M.W./L.W. and Trawler Band. 7 stages, 5 transistors and 4 diodes, super-sensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5½" x 1½" x 3½" approx. Plans and parts price list 15p. (Free with parts).  
Total Building Costs **£2.50** P.P. & Ins. 26p.  
(Overseas P & P 1-25p) (+ 10% VAT 25p)



## TRANSONA FIVE


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (Free with parts).  
Total Building Costs **£2.75** P.P. & Ins. 26p.  
(Overseas P & P 1-25p) (+ 10% VAT 27p)


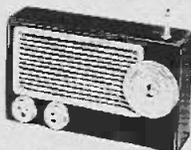
## TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands; MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker, 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 26p (FREE with parts).



Total Building Costs **£4.48** P.P. & Ins. 33p.  
(Overseas P & P £1-25) (+ 10% V.A.T. 44p)

- Callers side entrance "Lavells" Shop
- Open 10-1, 2.30-4.30 Mon.-Fri.—9-12 Sat.

## RADIO EXCHANGE CO

61a HIGH STREET, BEDFORD, MK40 1SA Tel. 0234 52387

Reg. no. 788372


I enclose £..... for

Name.....

Address.....

(Dept. E.E.7.)

# The Catalogue you **MUST** have!

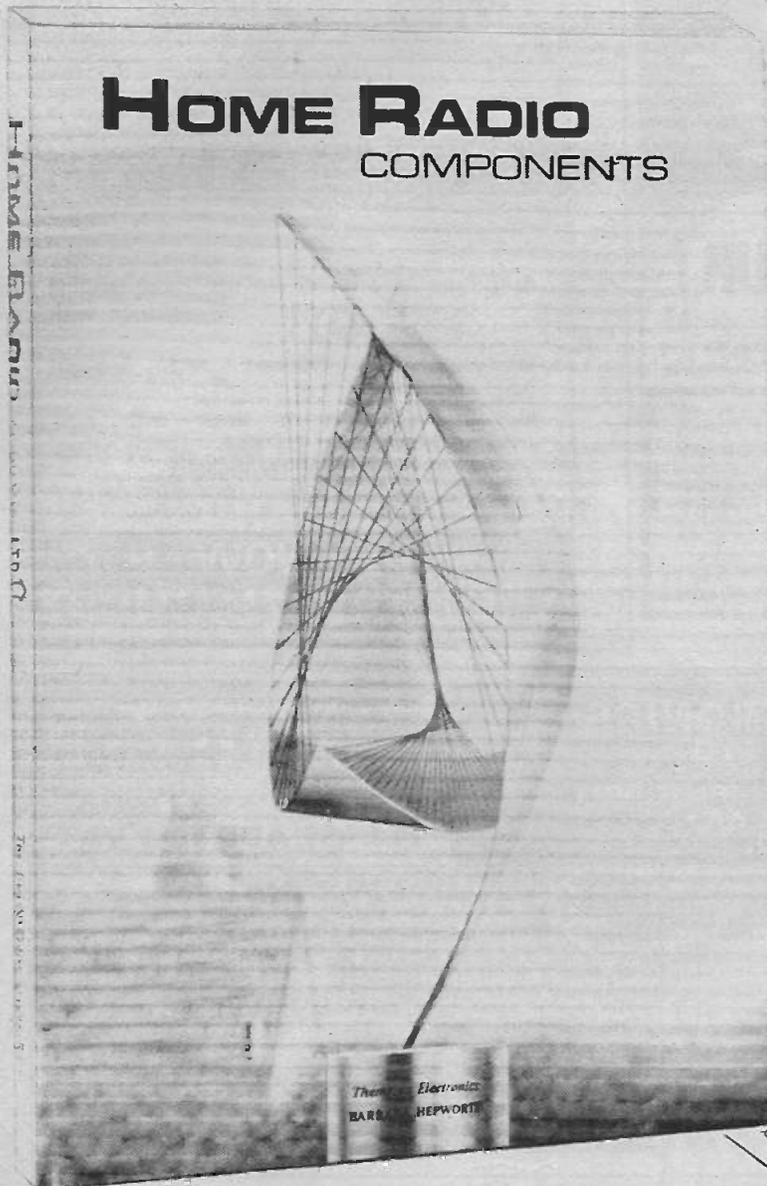

250 pages 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ "

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

*Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.*

**Only 55p.** plus 22p POST AND PACKING

**POST THIS COUPON**  
with cheque or P.O. for 77p.

The price of 77p applies only to customers in the U.K. and to BFPO addresses

Name \_\_\_\_\_

Address \_\_\_\_\_



HOME RADIO (Components) LTD. (Regn. No. London 912966)  
Dept. EE, 234-240 London Road, Mitcham CR4 3HD



# become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!** Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

EEB 74  
BLOCK CAPS please



## Beginner's Guide To Electronics

3rd Edition

T.L. Squires and C.M. Deason



This book describes as simply as possible the basic concepts in electronic engineering and the various components used in electronic equipment so that the reader gains an understanding of the terms used and the practical side of the subject. Prominence throughout has been given to the transistor and the integrated circuit.

- Provides a 'short cut' for those wishing to obtain a quick acquaintance with modern electronics
  - Completely revised and brought up-to-date
  - Each section is dealt with non-mathematically and explanatory diagrams are used throughout
- 240 pages 191 x 128mm. ISBN 0 408 00126 7  
Cased £1.90

**BUY NOW**



**Newnes-Butterworths**

Borough Green, Sevenoaks, Kent

## YATES ELECTRONICS (FLITWICK) LTD

DEPT. E.E., ELSTOW STORAGE DEPT.  
KEMPSTON HARDWICK,  
BEDFORD.

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m.-5 p.m.

**PLEASE ADD 10% VAT**

### RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.  
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.

### 1W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	1-99	Price	100+
1	5%	4-7Ω-2.2MΩ	E24	1-3p	1-1p	1-1p
	10%	3-3MΩ-10MΩ	E12	1-3p	1-1p	1-1p
1/2	2%	10Ω-1MΩ	E24	3-5p	3p	3p
	10%	1Ω-3-9Ω	E12	1-3p	1-1p	1-1p
1/4	5%	4-7Ω-1MΩ	E12	1-3p	1-1p	1-1p
	10%	1Ω-10Ω	E12	8p	7p	7p

Quantity price applies for any selection. Ignore fractions on total order.

### DEVELOPMENT PACK

0-5 watt 3% Iskra resistors 5 off each value 4-7Ω to 1MΩ.  
E12 pack 325 resistors £2-40. E24 pack 650 resistors £4-70.

### POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1W, 1in 1/2W).  
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch 28p.

### SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix).  
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 7p each.

### SMOKE AND COMBUSTIBLE GAS DETECTOR—GD1

The GD1 is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector. Detector GD1 £2. Kit of parts for mains operated detector, including GD1 but excluding case £5-60. Suitable case £1-50. Kit of parts for 12 or 24V battery operation, including GD1 and P.C. Board £7-70. As above for PPG battery £8-90. Note: the battery operated kits incorporate our patented circuit to minimise battery drain—typically 90mA for 24V.

### PRINTED BOARD MARKER

97p  
Draw the planned circuit onto a copper laminate board with the P.C. Pen allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

### MULLARD POLYESTER CAPACITORS C296 SERIES

160V: 0-01μF, 0-015μF, 0-022μF, 0-033μF, 0-047μF, 0-068μF, 3p, 0-1μF, 3p, 0-15μF, 4p, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 7p, 0-68μF, 11p, 1-0μF, 13p.

### MULLARD POLYESTER CAPACITORS C290 SERIES

250V P.C. mounting: 0-01μF, 0-015μF, 0-022μF, 3p, 0-033μF, 0-047μF, 0-068μF, 3p, 0-1μF, 4p, 0-15μF, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 8p, 0-68μF, 11p, 1-0μF, 13p, 1-5μF, 20p, 2-2μF, 24p.

### MYLAR FILM CAPACITORS 100V: 0-001μF, 0-002μF, 0-005μF, 0-01μF, 0-02μF, 3p, 0-04μF, 100μF to 10,000μF, 2p each.

0-05μF, 0-023μF, 0-1μF, 4p.

### ELECTROLYTIC CAPACITORS

(μFv) 1-63, 1-5/63, 2-2/63, 3-3/63, 4-7/63, 6-8/40, 6-8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33-6-3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6-3, 68/16, 100/4, 100/10, 100/25, 150/6-3, 150/16, 220/4, 220/6-3, 220/16, 330/4, 5p, 47/63, 100/40, 150/25, 220/25, 330/10, 470/6-3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4, 1p, 470/10, 680/6-3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16, 1500/6-3, 13p, 470/40, 680/25, 1000/16, 1500/10, 2200/6-3, 18p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6-3, 4700/44, 21p.

### SOLID TANTALUM BEAD CAPACITORS

0-1μF	35V	2-2F	35μV	22μF	16V
0-22μF	35V	4-7F	35μV	33μF	10V
0-47μF	35V	8-8F	25μV	47μF	6-3V
1-0μF	35V	10F	25μV	100μF	3V

### VEROBOARD

2 1/2 x 3 1/2	0-1	0-15
2 1/2 x 5	24p	20p
2 1/2 x 8	28p	28p
3 1/2 x 3 1/2	28p	28p
3 1/2 x 5	32p	32p
1 7/8 x 2 1/2	85p	67p
1 7/8 x 3 1/2	120p	108p
1 7/8 x 3 1/2 (plain)	76p	52p
1 7/8 x 2 1/2 (plain)	—	41p
2 1/2 x 3 (plain)	—	12p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	62p	62p
Spot face cutter	52p	52p
Pkt. 50 pins	20p	20p

### JACK PLUGS AND SOCKETS


Standard screened	28p	2-5mm insulated	12p
Standard insulated	18p	3-5mm insulated	12p
Stereo screened	40p	3-5mm screened	18p
Standard socket	20p	2-5mm socket	11p
Stereo socket	30p	3-5mm socket	11p

### D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 1800, 5 pin 2400, 6 pin, 7 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 25p/metre.  
6 way screened cable, 30p/metre.
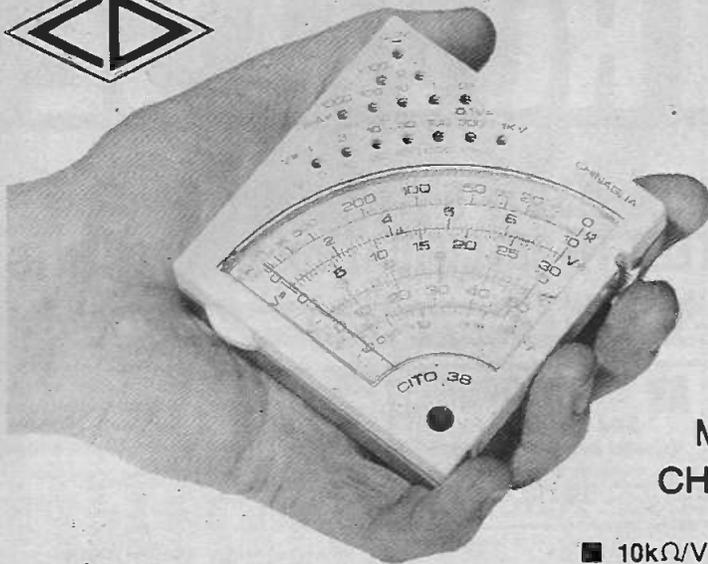
### BATTERY ELIMINATOR

8V mains power supply. Same size as PP9 battery. £1-70



A CITO IN  
THE HAND

IS

WORTH **£10.10**

INC. V.A.T.

THE TRULY POCKET  
MULTIMETER FROM  
CHINAGLIA OF ITALY

- 0.1V to 1kV f.s.d. d.c.; 5V to 1.5kV f.s.d. a.c.
- 100µA to 1A f.s.d. d.c.; 5mA to 0.5A f.s.d. a.c.


- 10kΩ/V d.c. sensitivity with 2.5% accuracy.
- Resistance 0-10kΩ and 0-1MΩ.
- Power - 10 to +65dB in 6 ranges.

For further information on the "CITO" or other instruments from the exciting Chinaglia range write or telephone:

**CHINAGLIA (U.K.) LTD.**

19 Mulberry Walk, London S.W.3 Tel. 01-352 1897  
Trade enquiries welcomed
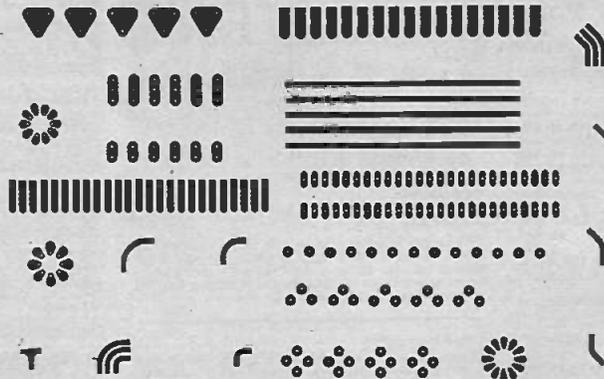
## PRINTED CIRCUIT BOARD TRANSFER SYSTEMS



Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes—i.e. edge connectors, lines, pads, dual in line I.C.'s, 8-10-12, T.O.5 Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry. A full money back guarantee is sent with each order, trade prices on application.

### List of Prices

Complete system including post and VAT .....	£2.00
Individual sheets .....	22p
Sample sheet .....	22p
Copper laminate (boards) size 6" x 4½" 6 sheets.....	50p
(with six months guarantee)	

Printed circuit board PCB transfer systems patent applied for.

**E. R. NICHOLLS, 46 LOWFIELD ROAD, STOCKPORT, CHESHIRE**

TELEPHONE NUMBER : 061-480-2179

# ELECTROVALUE

Present

## THIS MONTH'S SELECTION OF GUARANTEED-TO-SPECIFICATION COMPONENTS

Everything Brand New ★ Attractive Discounts ★ Free Postage (U.K.)  
Build that EE Design with EV components

### TRANSISTORS

and semi-conductors of many types from simple diodes to ICS photo-sensitive devices, threshold switches, etc. etc.  
**MINITRON DIGITAL INDICATORS**  
3415F Seven segment filament, compatible with standard logic modules, 0-9 and decimal point; 9mm characters in 16 lead DIL (some alphabetical symbols available) £1-20  
Suitable BCD decoder driver 7447 £1-15  
3015G showing + or - & 1 & dec. pt. £1-29

### CAPACITORS

**DALY ELECTROLYTIC**  
In cans, plastic sleeved  
1000µF/25V 28p 1000/50 41p  
5000/100 £2-91 2000/50 57p  
5000/25V 62p 5000/50 £1-18  
2200/100 £1-56

### POLYESTER TYPE C-220

Radial leads for P.C.B. mounting. Working voltage 250V d.c.  
0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p  
0-068, 0-1, 0-15 ea. 4p  
0-22, 5p; 0-21 7p; 0-47 8p; 0-68 11p; 1-0 14p;  
1-5 21p; 2-2 24p.

### SILVERED MICA

Working voltage 500V d.c.  
Values in pFs—2-2 to 820 in 32 stages ea. 6p  
1000, 1500 7p; 1800 8p; 2200 10p; 2700, 3600 12p;  
4700, 5000 15p; 6800 20p; 8200, 10,000 25p

### TANTALUM BEAD

0-1, 0-22, 0-47, 1-0 MFF 35V. ea. 14p  
2-2/16V, 2-2/35V, 4-7/16V, 10/6-3V ea. 14p  
4-7/35V, 10/16V, 22/6-3V ea. 18p  
10/25V, 22/16V, 47/6-3V 100/3V ea. 20p

### POLYCARBONATE

Type B42540 Working Voltage—250V  
Values in mF:  
0-0047; 0-0068; 0-0082; 0-01; 0-012; 0-015 ea. 3p  
0-018; 0-022; 0-027; 0-033; 0-039; 0-047; 0-056  
0-068; 0-082; 0-1 ea. 4p

### CERAMIC PLATE

Working voltage 50V. d.c.  
In 26 values from 22pf to 6800pF, each, 2p

### POTENTIOMETERS

**ROTARY CARBON TRACK.** Double wipers for good contact and long working life.  
P-20 SINGLE linear 100ohms to 4-7megohms, ea. 14p  
P-20 SINGLE log. 4-7Kohms to 2-2megohms, ea. 14p

JP-20 DUAL GANG lin. 4-7Kohms to 2-2megohms, ea. 48p  
JP-20 DUAL GANG log. 4-7Kohms to 2-2megohms, ea. 48p

JP-20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only ea. 48p

JP-20 DUAL GANG antilog 10K only 48p

2A DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets Type PR, horizontal or vertical 6p each.

### SLIDER

Linear or log. 4-7K to 1 meg. in all popular values ea. 36p

Ecutcheon plates, black, white or light grey, ea. 10p

Control knobs, blk/wh/red/yel/grn/blue/dk. grey/lt. grey ea. 7p

### JACKS AND PLUGS

Sockets  
2-circuit unswitched S1/SS 12p

2-circuit 1/2 break contacts S1/BB 15p

3-circuit unswitched (Not GPO) S3SSS 17p

3-circuit with 3 break contacts S3/BBB 20p

2-circuit with chrome nut and black/white/red/grey or grey unswitched S3/SS 16p

with 2 break contacts S5/BB 20p

Miniature 3.5mm 2-circuit, (black) 2 br. cont S6/BB 9p

### PLUGS

2 circuit screened top entry P1 24p

side entry SEP1 36p

Line socket mono 231 40p

Line socket stereo 244 45p

3 circuit unscreened, bl/grey/wh. P4 48p

2 circuit, unscreened, bl/wh/red/bl/grn/gy P2 18p

3 circuit screen top entry P3 53p

side entry SEP3 55p

Miniature 3-5mm 2-circuit screened P5 13p

Min. 3-5mm 2-circ. unscrnd. various colours P6 10p

## EV CATALOGUE

### 2nd printing

(Green and buff cover)

112 pages, thousands of items; illustrations; diagrams; much useful technical information. The 2nd printing of this catalogue has been updated as much as possible on prices. It costs only 25p, post free and includes a refund voucher for 25p for spending when ordering goods list value £5 or more.

### INSULATED SCREW TERMINALS

In moulded polypropylene, with nickel plate on brass. With insulating set, washers, lag & nuts. 15A/250V in blk/brown/red/yel/grn/bl/gy/wh. Type TP.1, ea. 14p  
Suitable plugs Type TP4, 4mm each 7p  
Type TP2, 2mm each 4p

### ZENER DIODES

Full range E24 values: 400mW: 2-7V to 33V, 14p each; 1W: 5-8V to 32V, 28p each; 1-5W: 4-7V to 75V, 48p each, 20V: 7-5V to 75V, 69p each. Clip to increase 1-5W rating to 3 watts (type 266F), 5p.

### RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/3	4-7-470K	1-3	1-1	0-9 nett
C	1/2	4-7-10M	1-1	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-97 nett
C	1	4-7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-3-9	9	9	8
WW	3	1-10K	7	7	6
WW	7	1-10K	9	9	8

Codes:  
C — carbon film, high stability, low noise.  
MO — metal oxide, Electrofit TR5, ultra low noise.  
WW — wire wound, Plessey.  
Values: All E12 except C 1/3, C 1/2, and MO 1/2.  
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:  
5% except WW 10% ±0-05Ω under 10Ω and MO 1/2 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only.

### VEROBOARD

Copper clad 0-1 matrix—2-5 x 3-75 ins. 30p; 3-75 x 3-75 ins.—30p; 2-5 x 5 ins.—30p; 3-75 x 5 ins.—33p.  
Copper clad 0-15 lin. matrix 2-5 x 3-75 ins.—20p; 3-75 x 3-75 ins.—30p; 2-5 x 5 ins.—30p; 3-75 x 5 ins.—36p.  
Vero spot face cutter (any matrix) 48p.  
0-040 pins (for 0-1 matrix) per 100—38p.  
0-052 pins (for 0-15 matrix) per 100—36p.

### APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

## ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.  
NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA  
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily: Sat 9-1 p.m.  
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

### ELECTROLYTICS

Axial Lead	µF	3V	6-3V	10V	16V	25V	40V	63V	100V
0-47	—	—	—	—	—	—	11p	11p	8p
1-0	—	—	—	—	—	—	—	—	8p
2-2	—	—	—	—	—	11p	—	—	8p
4-7	—	—	—	—	—	—	8p	8p	8p
10	—	—	—	—	—	—	8p	8p	8p
22	—	—	—	—	—	—	8p	8p	10p
47	8p	—	—	—	—	—	8p	8p	10p
100	9p	8p	—	—	—	—	8p	10p	12p
220	8p	8p	9p	10p	10p	11p	17p	24p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p	—
1,000	11p	13p	13p	17p	20p	25p	41p	—	—
2,200	15p	18p	23p	26p	37p	41p	—	—	—
4,700	26p	30p	39p	44p	58p	—	—	—	—
10,000	42p	46p	—	—	—	—	—	—	—

### KNObS

In a great variety of modern types, for 1/4" shaft, from plastic to solid aluminium as well as pointer and numbered types.

### CONNECTORS

DIN from two way to 7 way plugs and sockets, phono types mains connections, etc. etc. Page 88 in Catalogue 7

### BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-90.  
The size and weight of this product obliges us to charge 70p part cost of cart. In U.K.  
Equaliser Assembly, £2-30  
Loudspeaker Unit 59RM109, £2-45  
Cabinet Kit (to Baxandall design), £10-45.  
Cross-over choke for additional woofer to above £1-30

## This is EV Service

### DISCOUNTS

Available on all items except those shown with NETT PRICES, 10% on orders from £5 to £14-99, 15% on orders £15 and over.

### PACKING AND POSTAGE FREE

In U.K. for pre-paid mail orders, except Baxandall. For order list value £2 and under there is an additional handling charge of 10p.

### GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale.

### GIRO ACCOUNT—No. 38/671/4002

Prices quoted do not include V.A.T., for which 10% must be added to total net value of order. Every effort is made to ensure correctness of information and prices at time of going to press. Prices subject to alteration without notice.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. EE7. S.A.E. with enquiries requiring answers.



### SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52. Indicator 100uA DC. Full scale 5 section colorable antenna. Size 145 x 50 x 60mm.

**OUR PRICE £4.25** P&P 25p

### AT201 Decade ATTENUATOR

Frequency range 0-200kHz. Attenuator. 0-1110dB, 0.1dB steps. Impedance 600 ohms. Input power maximum 300mW. Size: 130 x 90 x 66mm.

**OUR PRICE £12.50** P&P 37p

### TRANSISTORISED I.C.R. A.C. BR/8 MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm ± 1% Inductance: 1 microhenry-111 henries ± 2% Capacity: 6 ranges: 10pf-1110 mfd ± 2% Turns Ratio: 6 ranges: 1:1/1000-1:11100 ± 1% Bridge Voltage at 1,000cps. Operating from 9-volt battery. 100 microamp meter indication. Size 7 1/2" x 6" x 2"

**OUR PRICE £25.00** P&P 25p

### TE16A TRANSISTORISED SIGNAL GENERATOR

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 148 x 148 x 92mm. Complete with instructions and leads.

**OUR PRICE £8.97** P&P 25p

### MODEL TE20 RF SIGNAL GENERATOR

Six bands. 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 6V. Power requirements: 106-120V, 220-240V A.C. Size: 193 x 295 x 150mm. Complete with test leads etc.

**OUR PRICE £17.50** P&P 40p

### TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-800 MHz x 6 bands. Directly calibrated. Variable R.F. transmitter audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.

**OUR PRICE £17.50** P&P 30p

### TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to 200kHz on 4 bands. Square 20 cps to 20 kHz. Output impedance 500 Ohms. 200/250V A.C. operation. Supplied brand new guaranteed, with instruction manual and leads.

**OUR PRICE £24.95** P&P 37p

### ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P.F. 100kHz to 200kHz. Output 1V maximum. 220/240V A.C. operation. Complete with instructions and leads.

**OUR PRICE £37.50** P&P 60p

### KE630 3 Station INTERCOM

Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries.

**OUR PRICE £5.25** P&P 50p

### MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19-220,000Hz Sine Wave 19-100,000 Hz Square Wave. Output Sine or Square wave 10V. P. to P. Size 180 x 90 x 90mm Operation 220/240V. A.C.

**OUR PRICE £19.95** P&P 37p

### PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V A.C. Size: 190 x 136 x 98mm.

**OUR PRICE £19.95** P&P 25p

### POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range of sizes. Single hole fitting. 3/4" diameter shafts. Bulk quantities available.

1W 10/50/100/250/500/1000 Ohms **£1.15** P&P 10p

50 Watt 10/25/50/250/500/1000/2500/5000 Ohms. **£1.62** P&P 10p

100 Watt 1/10/25/50/100/250/500/1000/2500 Ohms **£2.34** P&P 15p

### YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V. MODEL S260 BEACH MOUNTING

1A £10.50 30p

2.5A £12.00 35p

5A £17.50 27p

8A £30.35 30p

10A £33.75 75p

12A £29.50 75p

20A £85.00 125p

25A £95.00 130p

40A £120.00 150p

MODEL S260B PANEL MOUNTING

1A £10.00 30p

2.5A £12.00 35p

### BV05 Vernier TUNING OIAL

App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 28 x 76mm. Overall size 190 x 117 x 41mm. Deep including knob and coupling. 3/4" diam. shaft

**OUR PRICE £1.62** P&P 15p

### 240° Wide Angle 1mA METERS

MW 1-6 60x60mm **£6.50** P&P 15p

MW 1-8 80x80mm **£6.90** P&P 15p

### CP110 CHASSIS PUNCH SET

Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.

**OUR PRICE £3.00** P&P 40p

### HITACHI FLUORESCENT LANTERN L1901

A portable battery operated lantern ideal for home, motoring, camping etc. Approx. 10" tall. Provides brilliant light from 9 1.5V batteries (not supplied).

**OUR PRICE £7.19** P&P 25p

### EM1 LOUDSPEAKERS

Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.

**OUR PRICE £7.50** each P&P 37p

Model 450 13 x 8" with two tweeter/crossover. 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms

**OUR PRICE £3.62** each P&P 25p

### SPECIAL PURCHASE LIMITED QUANTITY!

Tannoy 12" DR/8 Bass Speakers

8 ohms 30" watt. Heavy duty, ideal for Hi-Fi P.A. Group.

**OUR PRICE £12.50** P&P 60p.

### WALKIE TALKIES

SKYFON 100mW **OUR PRICE £24.95** per pair  
P302 Two Channel 300mW **OUR PRICE £82.50** per pair  
P1003 Three Channel 1 Watt **OUR PRICE £71.25** per pair  
P&P 50p per pair  
N.B. Unavailable in U.K.

### OT55G DIGITAL CLOCK MECHANISM

Features: 24 hour alarm setting, on/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, light etc. and with auto-switching will turn on again when required. 240V A.C. operation. Switch rating 250V-3 Amp.

**OUR PRICE £5.95** P&P 30p

### SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER

complete with printed circuit mounting board. **OUR PRICE £2.35** P & P 15p

### LH02S STEREO HEADPHONES

Light weight head-phones with padded ear pieces. 4-15 ohms 20-20,000Hz. Complete with 6' lead and plug.

**OUR PRICE £1.97** P&P 30p

### TE1018 Deluxe Mono High Impedance Headset.

Sensitive magnetic headset with soft ear pads. Impedance 2,600 ohms (600 ohms DC). Frequency response: 200-4,000Hz.

**OUR PRICE £2.25** P&P 30p

### TE1035 Stereo HEADPHONES

Low cost with excellent response. Foam rubber cups. Adjustable headband. 8 ohms impedance. Frequency response 20Hz-18kHz. Complete with cable and stereo jack plug.

**OUR PRICE £2.60** P&P 30p

### SH8DV MONO/STEREO HEADPHONES

Volume control for each channel. 4-15 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.

**OUR PRICE £4.97** P&P 30p

### 8H001 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.

**OUR PRICE £5.95** P&P 30p

### EMI LOUDSPEAKERS

Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.

**OUR PRICE £7.50** each P&P 37p

Model 450 13 x 8" with two tweeter/crossover. 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms

**OUR PRICE £3.62** each P&P 25p

### SPECIAL PURCHASE LIMITED QUANTITY!

Tannoy 12" DR/8 Bass Speakers

8 ohms 30" watt. Heavy duty, ideal for Hi-Fi P.A. Group.

**OUR PRICE £12.50** P&P 60p.

### SPECIAL BARGAIN! FERUGSON 3406 HI-FI SPEAKERS

High quality 2 way speaker systems. 25 Watts. 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 255mm approx. Wood grain finish with black fronts. **OUR PRICE £26.95** P&P £1

### SPECIAL BARGAIN !! STEREO SOUND SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size: 358 x 228 x 130mm. 8 ohms. 8 watts RMS. 16 watts peak. Complete with Din lead.

**OUR PRICE £12.95** P&P 50p

### FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.

**OUR PRICE £8.95** P&P 20p

### Model A1018 FM TUNER

6 transistor high quality unit - 3 IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery. **OUR PRICE £13.50** P&P 30p

Stereo multiplex adapter **£5.95** extra.

### SINCLAIR "SCIENTIFIC" CALCULATOR

8 digit display. Four functions plus logarithms to base 10, arith, sine, cosine, tangent, arcSine, arcCosine and arcTangent. Complete with instructions, case and batteries. Rec. Price **£49.00**

**OUR PRICE £44.50** P & P 25p plus VAT

### SINCLAIR SYSTEM 2000 STEREO AMPLIFIER AND TUNER

Amplifier output 8 watts per channel RMS. Distortion less than 0.06%. Silicon transistors. Two pick-up plus radio and tape inputs. tape output and scratch filter. Excellent Value. **OUR PRICE £28.50** P & P 60p.

### FM TUNER

Excellent selectivity and sensitivity. Twin dual-varicap tuning. 4 pole ceramic filter. 18 transistor stereo demodulator giving 40 db separation. Distortion 0.2% output. Fantastic Value. **OUR PRICE £28.50** P & P 60p.

### SINCLAIR Project 80 Modules

240 Power Amplifier **£5.45**  
250 Power Amplifier **£6.95**  
Stereo 80 Pre-Amplifier **£11.95**  
Active Filter Unit **£6.95**  
Project 80S **£28.95**  
P25 Power Supply **£4.98**  
P28 Power Supply **£7.98**  
P28 Power Supply **£7.98**  
Transformer for P28 **£4.05**

### SINCLAIR Project 80 Packages

2 x 240/Stereo 80/P25 **£25.00**  
2 x 240/Stereo 80/P28 **£27.75**  
2 x 250/Stereo 80/P28 **£30.45**  
POST & PACKING 35p each.

### MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mic, 3 x 2mV 50k; 2 x 3mV 600 ohms. Phono, Mag. 400V 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k. **OUR PRICE £8.97** P&P 20p

### HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.

Post and Packing 15p per kit.

AF20 Mono amplifier	£4.80
AF30 Mixer	£3.60
AF30 Mono pre-amplifier	£2.81
AF35 Driver amplifier	£2.27
AF80 0.5W mic. amplifier	£4.22
AF305 Intercom	£8.52
AF310 Mono amplifier	£5.91
AT5 Automatic light control	£2.58
AT25 Window wiper robot	£5.82
AT30 Photo cell switch unit	£5.70
AT50 400V triac light dimmer/speed control	£4.80
AT56 2,200W triac light dimmer/speed control	£6.80
AT60 1 channel light control	£7.80
AT65 3 channel light control	£14.55
GP304 Circuit board	£4.94
GP310 Stereo pre-amplifier for use with a FM tuner	£21.27
GP312 Circuit board	£11.45
GU330 Tremolo unit	£7.50
HF61 Diode detector	£3.32
HF65 FM transmitter	£2.87
HF75 FM receiver	£2.70
HF310 FM tuner	£15.81
HF305 Deluxe FM tuner	£24.12
HF330 Decoder (HF310/325)	£9.96
HF380 lw/hf aerial amplifier	£4.94
HF395 broadband serial amp.	£1.77
HF390 Quadraphonic device	£11.36
M160 Multi-vibrator	£1.71
M191 VU Meter	£4.55
M192 Stereo balance meter	£6.97
M1302 Transistor tester	£8.45
NT10 Stabilised power supply 100mA, 9V	£6.15
NT300 Stabilised 2 x AF310	£9.61
NT305 Voltage converter	£4.50
NT315 Power supply 240V AC to 4, 5, 15V DC, 500mA	£9.57

Amateur Electronics by Josty-Kit, the professional book for the amateur - covers the subject from basic principles to advanced electronic technique. Complete with circuit board for AE1 to AE10 listed below.

**OUR PRICE £3.30 (No VAT)** P&P 25p plus VAT

AE1 100mW output stage	£1.50
AE2 Pre-amplifier	£1.15
AE3 Diode receiver	£1.82
AE4 Flasher	99p
AE5 100Hz oscillator	98p
AE6 Monostable multi-vibrator	93p
AE7 RC generator	97p
AE8 Bass filter	90p
AE9 Treble filter	93p
AE10 CCR filter	90p

### 1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. Two gain controls, speakers on-off slide switch, stereo headphone socket.

**OUR PRICE £2.25** P&P 15p

### AUDIOTRONIC LOW NOISE CASSETTES

TYPE	10	25
CR9	£1.87	£3.00
CR9	£2.24	£4.25
CR10	£2.73	£5.17

### AUDIOTRONIC CR02 CASSETTES

TYPE	5	10	25
CR90	£1.32	£2.72	£10.12
CR90	£5.32	£10.46	£22.22

### AUDIOTRONIC 8 TRACK CARTRIDGES

TYPE	Each	5	10
40M	85p	£4.00	£7.50
80M	£1.15	£5.40	£10.25

P&P Casettes 3p, Cartridges 5p each

OVER 10 of either. POST FREE!

### AUDIOTRONIC AHA101 Stereo Headphone Amplifier

All silicon, transistor amplifier operating from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. I.N.P.T.S. 50mV and 100mV. Output: 50mV per channel.

**OUR PRICE £8.50** P&P 20p

### EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverb on control. Walnut cabinet. 184 x 77 x 108mm.

**OUR PRICE £7.50** P&P 20p

### ALL PRICES EXCLUDE VAT

# SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

## CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3.80
100uA	£3.85
200uA	£3.70
500uA	£3.65
50-0-500uA	£3.75
100-0-1000uA	£3.70
1mA	£3.65
5mA	£3.65
10mA	£3.65
50mA	£3.65
100mA	£3.85
500mA	£3.65
1A DC	£3.65
5A DC	£3.65
10A DC	£3.65
5V DC	£3.65



10V DC	£3.65
20V DC	£3.65
50V DC	£3.65
15V AC	£3.65
30V AC	£3.75
VU Meter	£3.90

## CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.80
100uA	£4.80
500uA	£4.30
50-0-500uA	£4.50
100-0-1000uA	£4.45
1mA	£4.30
1A DC	£4.30
5A DC	£4.30
20V DC	£4.30
50V DC	£4.30
300V DC	£4.30



150V AC	£4.45
300V AC	£4.45
VU Meter	£4.90

## EDGWIS MODEL PE70

Size: 90 x 34mm

50uA	£4.15
100uA	£4.10
200uA	£4.05
500uA	£3.90
50-0-500uA	£4.10
100-0-1000uA	£4.05
1mA	£3.85
300V AC	£3.85
VU Meter	£4.30



## MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



50uA	£8.50
100uA	£7.90
50-0-500uA	£7.90
1mA	£7.60
1-0-1mA	£7.60
1A DC	£7.60
5A DC	£7.60
10V DC	£7.60
15V DC	£7.60

20V DC	£7.60
50V DC	£7.60
300V DC	£7.60
500mA/5A DC	£8.60
5V/50V DC	£8.60
5V DC	£8.60
10V DC	£8.60
15V DC	£8.60
1/5A DC	£8.60
1A/15A DC	£8.60

## CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5.45
100uA	£5.40
200uA	£5.35
500uA	£5.25
50-0-500uA	£5.40
100-0-1000uA	£5.35
1mA	£5.20
1-0-1mA	£5.20
5mA	£5.20
10mA	£5.20
50mA	£5.20
100mA	£5.20
500mA	£5.20
1A DC	£5.20
5A DC	£5.20
15A DC	£5.20
30A DC	£5.40
10V DC	£5.20
20V DC	£5.20
50V DC	£5.20
150V DC	£5.20



300V DC	£5.20
15V AC	£5.30
30V AC	£5.30
5A AC	£5.20
15A AC	£5.20
30A AC	£5.20
1A DC	£5.20
5A DC	£5.20
10A DC	£5.20
20A AC	£5.20
30A AC	£5.20

\*Items with asterisk are Moving Iron type, all others are Moving Coil

## CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4.30
100uA	£4.25
200uA	£4.20
500uA	£4.15
50-0-500uA	£4.25
100-0-1000uA	£4.20
1mA	£4.10
5mA	£4.10
10mA	£4.10
50mA	£4.10
100mA	£4.10
500mA	£4.10
1A DC	£4.10
5A DC	£4.10
10A DC	£4.10
5V DC	£4.10



10V DC	£4.10
20V DC	£4.10
50V DC	£4.10
15V AC	£4.10
30V AC	£4.20
VU Meter	£4.40

## CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.05
50-0-500uA	£3.15
100-0-1000uA	£3.10
1mA	£2.95
5mA	£2.95
10mA	£2.95
20mA	£2.95
50mA	£2.95
100mA	£2.95
500mA	£2.95
1A DC	£2.95
5A DC	£2.95
10V DC	£2.95
20V DC	£2.95
50V DC	£2.95
300V DC	£2.95
15V AC	£3.05
30V AC	£2.95
50A AC	£2.95
100A AC	£2.95
200A AC	£2.95
300A AC	£2.95



## CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.10
100uA	£3.05
200uA	£3.00
500uA	£2.85
50-0-500uA	£3.05
100-0-1000uA	£2.90
1mA	£2.80
1-0-1mA	£2.80
2mA	£2.80
5mA	£2.80
10mA	£2.80
20mA	£2.80
50mA	£2.80
100mA	£2.80
150mA	£2.80
200mA	£2.80
300mA	£2.80
500mA	£2.80
750mA	£2.80
1A DC	£2.80
2A DC	£2.80
5A DC	£2.80
10A DC	£2.80
3V DC	£2.80
10V DC	£2.80
15V DC	£2.80



20V DC	£2.80
50V DC	£2.80
150V DC	£2.80
300V DC	£2.85
500V DC	£2.85
750V DC	£2.90
15V AC	£2.90
30V AC	£2.90
50V AC	£2.90
150V AC	£2.90
300V AC	£3.00
S Meter 1mA	£2.80
VU Meter	£3.20

## CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.80
100uA	£3.45
200uA	£3.40
500uA	£3.35
50-0-500uA	£3.45
100-0-1000uA	£3.40
1mA	£3.30
5mA	£3.30
10mA	£3.30
50mA	£3.30
100mA	£3.30
500mA	£3.30
1A DC	£3.30
5A DC	£3.30
10A DC	£3.30
5V DC	£3.30



10V DC	£3.30
20V DC	£3.30
50V DC	£3.30
15V AC	£3.45
30V AC	£3.45
50V AC	£3.45
VU Meter	£3.65

## CLEAR PLASTIC MODEL MR 65P

Size: 85 x 78mm

50uA	£3.95
100uA	£3.85
200uA	£3.80
500uA	£3.75
50-0-500uA	£3.85
100-0-1000uA	£3.80
1mA	£3.70
1-0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
20A DC	£3.70
30A DC	£3.85
50A DC	£4.05
50V DC	£3.70
10V DC	£3.70
15V DC	£3.70
20V DC	£3.70
50V DC	£3.70
150V DC	£3.70



300V DC	£3.70
15V AC	£3.80
30V AC	£3.80
150V AC	£3.80
300V AC	£3.90
500V AC	£3.80
S Meter 1mA	£4.10
VU Meter	£3.70
1A AC	£3.70
5A AC	£3.70
10A AC	£3.70
20A AC	£3.70
30A AC	£3.70
50A AC	£3.70
100A AC	£3.70
200A AC	£3.70
500A AC	£3.70

## BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.50
100uA	£4.45
500uA	£4.20
50-0-500uA	£4.45
100-0-1000uA	£4.40
1mA	£4.20
1A DC	£4.20
5A DC	£4.20
20V DC	£4.20
50V DC	£4.20
15V AC	£4.40
30V AC	£4.20
300V AC	£4.30
VU Meter	£4.70



## CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.70
100uA	£3.50
200uA	£3.45
500uA	£3.40
50-0-500uA	£3.50
100-0-1000uA	£3.45
1mA	£3.30
5mA	£3.30
10mA	£3.30
50mA	£3.30
100mA	£3.30
500mA	£3.30
1A DC	£3.30
5A DC	£3.30
10V DC	£3.30
20V DC	£3.30
50V DC	£3.30
300V DC	£3.30
15V AC	£3.40
30V AC	£3.40
50A AC	£3.30
S Meter 1mA	£3.30
VU Meter	£3.80



## BAKELITE MODEL MR 65 Size: 80 x 80mm

25uA	£5.25
50uA	£4.00
100uA	£3.95
500uA	£3.65
50-0-500uA	£3.95
100-0-1000uA	£3.90
1mA	£3.60
1-0-1mA	£3.60
5mA	£3.60
10mA	£3.60
50mA	£3.60
100mA	£3.60
500mA	£3.60
1A DC	£3.60
2A DC	£3.60
5A DC	£3.60
10A DC	£3.60
15A DC	£3.60
30A DC	£3.60
50A DC	£3.80
5V DC	£3.60
10V DC	£3.60
15V DC	£3.60
20V DC	£3.60
50V DC	£3.60
150V DC	£3.60



300V DC	£3.60
30V AC	£3.60
50V AC	£3.60
150V AC	£3.60
300V AC	£3.60
500V AC	£3.60
VU Meter	£4.10
1A AC	£3.60
5A AC	£3.60
10A AC	£3.60
20A AC	£3.60
30A AC	£3.60
50A AC	£3.60
100A AC	£3.60
200A AC	£3.60
500A AC	£3.60

CALL INTO YOUR NEAREST LASKYS BRANCH OR ORDER WITH CONFIDENCE BY MAIL ORDER

CENTRAL LONDON	
481 OXFORD ST.	01-493 8641
10 TOTENHAM CT. RD.	01-637 2232
27 TOTENHAM CT. RD.	01-636 3715
33 TOTENHAM CT. RD.	01-636 2605
42/45 TOTENHAM CT. RD.	01-636 0845
87 TOTENHAM CT. RD.	01-580 3739
257/8 TOTENHAM CT. RD.	01-580 0670
3 LISLE ST. WC2	01-437 8204
34 LISLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-353 5812
152/3 FLEET ST. EC4	01-353 2833

## ESSEX

86 SOUTH ST. ROMFORD 70-20218

## KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS 0892-23242

## LEICESTERSHIRE

45 MARKET PLACE, LEICESTER 0533-537678

## SURREY

1046 WHITGIFT CENTRE, CROYDON 01-481 3027

27 EDEN ST. KINGSTON 01-546 7845

32 HILL ST. RICHMOND 01-948 1441

# The largest selection

## EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50. 3 for ONLY 55p + p & p 30

**SPECIAL ONE.** As above PLUS Power Transistors ONLY 45p each + p & p 15p

**STABILISED POWER MODULES**  
Complete with circuit diagrams, etc. 59p each + p & p 15p

**PAKOLITE BOARDS** 7 1/2" x 9" approx. 4 for 80p + p & p 20p.

## FIBRE-GLASS PRINTED CIRCUIT BOARDS

16 1/2 x 4" approx. 2 for 65p

## DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen 90p each

## VEROBOARDS

Packs containing approx. 50± ins. various sizes, all 1-matrix 65p

## REPANCO CHOKES & COILS

RF Chokes  
CH1. 2.5mH 25p CH2. 5.0mH 25p  
CH3. 7.5mH 25p CH4. 10mH 25p  
CH5. 1.5mH 25p

## COILS

DRX1 Crystal set 81p DRB2 Dual range 45p

## COIL FORMERS & CORES

NORMAN 1/2" Cores & Formers 7p  
1" Cores & Formers 8p

## SWITCHES

DP/DT Toggle 25p SP/ST Toggle 18p

## FUSES

1 1/2" and 20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A  
QUICK-BLOW 4p ea. ANTI-SURGE 5p ea.

## EARPHONES

Crystal 2.5mm plug 33p  
Crystal 3.5mm plug 33p  
8 ohms 2.5mm plug 22p  
8 ohms 3.5mm plug 22p

## DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.60

## 3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

## 2-WAY CROSSOVER NETWORK

K4007. 60 ohms Imp. Insertion loss 3dB £1.21

## CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

## BI-PAK

CATALOGUE AND LISTS  
Send S.A.E. and 10p.

## INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	4"	2"	90p
BV2	11"	6"	3"	£1.20

## ALUMINIUM BOXES

BA1	5 1/2"	4"	1 1/2"	42p
BA2	4"	4"	1 1/2"	41p
BA3	4"	2 1/2"	1 1/2"	41p
BA4	5 1/2"	4"	1 1/2"	47p
BA5	4"	2 1/2"	2"	41p
BA6	3"	2 1/2"	1 1/2"	34p
BA7	7"	5"	2 1/2"	68p
BA8	8"	6"	3"	84p
BA9	6"	4"	2"	54p

## VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9-5.30 p.m. Tel. 61592

## BIB HI-FI ACCESSORIES

### De Luxe Groov-Kleen

Model 42 £1.84

Chrome Finish Model 60 £1.50



Ref. 36A. Record/Styleus Cleaning Kit 28p

Ref. 43. Record Care Kit £2.35

Ref. 31. Cassette Head Cleaner 64p

Ref. 32. Tape editing Kit £1.54

Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 81p

Ref. 32A. Styleus Balance £1.38

Ref. J. Tape Head Cleaning Kit 61p

Ref. 34. Cassette Case £1.27

Ref. 55. Hi-Fi Stereo Hints & Tips 32p

## ANTEX SOLDERING IRONS

X25. 25 watt £1.93

OCN 240. 15 watt £2.15

Model G. 18 watt £2.15

8K2. Soldering Kit £2.88

STANDS: ST1 £1.21. ST2 77p

SOLDEE: 18SWG Multicores 7oz 82p

22SWG 7oz 82p. 18SWG 22ft 25p

22SWG Tube 22p

## ANTEX BITS and ELEMENTS

Bits No.

102 For model CN240 3/32" 38p

104 For model CN240 3/16" 38p

1100 For model CCN240 3/32" 38p

1101 For model CCN240 3/8" 38p

1102 For model CCN240 1/2" 38p

1020 For model G240 3/32" 38p

1021 For model G240 1/8" 38p

1022 For model G240 3/16" 38p

50 For model X25 3/32" 38p

51 For model X25 1/8" 38p

52 For model X25 3/16" 38p

## ELEMENTS

ECN 240 £1.16 EOCN 240 £1.33

EG 240 £1.16 EX 25 £1.16

## ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

## NEW COMPONENT PAK BARGAINS

Pack No. Qty. Description Price

C1 250 Resistors mixed values approx. count by weight 0.55

C2 200 Capacitors mixed values approx. count by weight 0.55

C3 50 Precision Resistors 1%, 2% mixed values 0.66

C4 75 1/4 W Resistors mixed preferred values 0.55

C5 5 Pieces assorted Ferrite Rods 0.65

C6 2 Tuning Gangs, MW/LW VHF 0.55

C7 1 Pack Wire 60 metres assorted colours 0.55

C 8 10 Reed Switches 0.55

C 9 3 Micro Switches 0.55

C10 15 Assorted Pots & Pre-Sets 0.55

C11 5 Jack Sockets 3 x 3.5m 2 x Standard Switch Type 0.55

C12 40 Paper Condensers preferred types mixed values 0.55

C13 20 Electrolytics Trans. types 0.55

C14 1 Pack assorted Hardware—Nuts/Bolts, Grommets etc. 0.55

G15 4 Mains Slide Switches 0.55

C16 20 Assorted Tag strips & Panels 0.55

C17 10 Assorted Control Knobs 0.55

C18 4 Rotary Wave Change Switches 0.55

C19 3 Relays 4-24V Operating 0.55

C20 4 Sheets Copper Laminate approx. 10" x 7" 0.55

## PLUGS AND SOCKETS

SOCKETS

PS 35 DIN 2 Pin (Speaker) 0.06

PS 36 DIN 3 Pin 0.10

PS 37 DIN 5 Pin 180° 0.10

PS 38 DIN 5 Pin 240° 0.10

PS 39 Jack 2.5mm Switched 0.09

PS 40 Jack 3.5mm Switched 0.10

PS 41 Jack 1/2" Switched 0.17

PS 42 Jack Stereo Switched 0.96

PS 43 Phono Single 0.06

PS 44 Phono Double 0.06

PS 45 Car Aerial 0.10

PS 46 Co-Axial Surface 0.09

PS 47 Co-Axial Flush 0.14

## INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0.13

PS 22 D.I.N. 3 Pin 0.17

PS 23 D.I.N. 5 Pin 180° 0.17

PS 24 D.I.N. 5 Pin 240° 0.17

PS 25 Jack 2.5mm Plastic 0.10

PS 26 Jack 3.5mm Plastic 0.12

PS 27 Jack 1/2" Plastic 0.24

PS 28 Jack 1/2" Screened 0.28

PS 29 Jack Stereo Plastic 0.28

PS 30 Jack Stereo Screened 0.82

PS 31 Phono Screened 0.14

PS 32 Car Aerial 0.15

PS 33 Co-Axial 0.17

## PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0.11

PS 2 D.I.N. 3 Pin 0.12

PS 3 D.I.N. 4 Pin 0.15

PS 4 D.I.N. 5 Pin 180° 0.14

PS 5 D.I.N. 5 Pin 240° 0.15

PS 6 D.I.N. 6 Pin 0.15

PS 7 S.I.N. 7 Pin 0.15

PS 8 Jack 2.5mm Screened 0.10

PS 9 Jack 2.5mm Plastic 0.09

PS 10 Jack 3.5mm Screened 0.12

PS 11 Jack 1/2" Plastic 0.13

PS 12 Jack 1/2" Screened 0.18

PS 13 Jack Stereo Screened 0.99

PS 14 Phono 0.06

PS 15 Car Aerial 0.15

PS 16 Co-Axial 0.10

## CABLES

CP 1 Single Lapped Screen 0.06

CP 2 Twin Common Screen 0.06

CP 3 Stereo Screened 0.06

CP 4 Four Core Common Screen 0.23

CP 5 Four Core Individually Screened 0.30

CP 6 Microphone Fully Braided Cable 0.10

CP 7 Three Core Mains Cable 0.07

CP 8 Twin Oval Mains Cable 0.06

CP 9 Speaker Cable 0.04

CP 10 Low Loss Co-Axial 0.10

## CARBON POTENTIOMETERS

Log and Lin

4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M

VC 1 Single Less Switch 0.14

VC 2 Single D.P. Switch 0.28

VC 3 Tandem Less Switch 0.44

VC 4 1K Lin Less Switch 0.14

VC 5 100K Log anti-Log 0.44

## HORIZONTAL CARBON PRESETS

0.1 watt 0.06 each

100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

## WORLD SCOOP

### JUMBO SEMICONDUCTOR PACK

Transistors - Germ. and Silicon Rectifiers - Diodes - Triacs - Thyristors - I.C.s and Zeners ALL NEW AND CODRED.

### APPROX 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

## EX-COMPUTER BOARDS BY THE BOXFULL!!

20 Boards packed with Semiconductors and other Electronic Components. Each board approx. size 8" x 7". All known type no's and easily recognizable.

FANTASTIC VALUE AT £2.20 per BOX p. & p. 52p

## SPECIAL PURCHASE

2N3045. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one abel 115w. T03. Metal Case.

OUB SPECIAL PRICE £1

## LOW COST CAPACITORS

0.01UF 400V. 5p. each  
500UF 50V. Elect. 10p each

## RECORD STORAGE/CARRY CASES

7 1/2" EP. 18 1/2" x 7" x 7" (50 records) £2.10  
12" LP. 13 1/2" x 7 1/2" x 12 1/2" (50 records) £2.95

## CASSETTE CASES

Holds 12. 10" x 3 1/2" x 5". Lock & Handle. £1.30

## 8-TRACK CARTRIDGE CASES

Holds 14. 13" x 5" x 6". Lock & Handle. £1.95  
Holds 24. 13 1/2" x 8" x 5 1/2". Lock & Handle. £2.70  
COLOURS: Red, Black and Tan—Please state preference.

## REPANCO TRANSFORMERS

240v. Primary. Secondary voltages available from selected tappings 4v, 7v, 8v, 10v, 14v, 15v, 17v, 19v, 21v, 26v, 31v, 33v, 40, 50 and 25v-0-25v.

Type	Amps.	Price	P & P
MT50/1	1	£1.93	30p
MT50/1	1	£2.42	35p
MT50/2	2	£3.30	40p

## CARTRIDGES

ACOS GP91-18C. 200mV at 1.2cm/sec £1.18  
ACOS GP92-1. 280mV at 1cm/sec £1.65  
ACOS GP96-1. 100mV at 1cm/sec £2.65  
TTC J-2005. Crystal/Hi Output 95p  
TTC J-20 10C Crystal/Hi Output Compatible £1.30  
TTC J-206 CS Stereo/Hi Output £1.60  
TTC J-2105 Ceramic/Med. Output £1.84

## CARBON FILM RESISTORS

The E13 Range of Carbon Film Resistors. 1/8th watt available in PAKS of 50 pieces, assorted into the following groups—

R1	50 Mixed 100 ohms-820 ohms	40p
R2	50 Mixed 1K ohms-8.2K ohms	40p
R3	50 Mixed 10K ohms-82K ohms	40p
R4	50 Mixed 100K ohms-1 Meg. ohms	40p

THESE ARE UNBEATABLE PRICES—LESS THAN 1p EACH INCL. V.A.T.


## BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C60. 32p C90. 41p C120. 52p

# -the lowest prices!

## BI-PAK QUALITY COMES TO AUDIO!
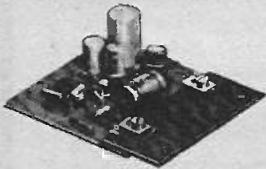
### AL10/AL20/AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	$P_o = 3 \text{ WATTS } f = 1\text{KHz}$	0.25%
LOAD IMPEDANCE	—	8 - 16 $\Omega$
INPUT IMPEDANCE	$f = 1\text{KHz}$	100 k $\Omega$
FREQUENCY RESPONSE @ 3dB	$P_o = 2 \text{ WATTS}$	50 Hz - 25KHz
SENSITIVITY FOR RATED O/P	$V_s = 25\text{V. } R_L = 8 \Omega f = 1\text{KHz}$	76mV. RMS
DIMENSIONS	—	3" x 2 1/4" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. ( $R_L = 8 \Omega f = 1 \text{ KHz}$ )	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

#### AUDIO AMPLIFIER MODULES

AL 10. 3 watts RMS £2.10  
AL 20. 5 watts RMS £2.59  
AL 30. 10 watts RMS £3.01

#### POWER SUPPLIES

P8 12. (Use with AL10 & AL20) 83p  
SPM 80. (Use with also AL30 & AL50) £3.25  
FRONT PANELS SP 12 with Knobs £1.10

#### PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20) £4.35  
PA 100. (Use with AL30 & AL50) £13.15

#### TRANSFORMERS

T461 (Use with AL10) £1.38 P & P 15p  
T538 (Use with AL20) £1.93 P & P 15p  
BMT80 (Use with AL30 & AL50) £2.15 P & P 25p

#### PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.


Frequency response—  
20Hz - 20KHz (-3dB)  
Bass control—  
 $\pm 12\text{dB at } 60\text{Hz}$   
Treble control—  
 $\pm 14\text{dB at } 14\text{KHz}$   
\*Input 1. Impedance  
1 Meg. ohm  
Sensitivity 300mV  
†Input 2. Impedance  
30 K ohms  
Sensitivity 4mV

Look for our  
SEMICONDUCTOR ADVERTISEMENTS in  
Practical Wireless  
Wireless World  
Radio Constructor

ALL PRICES INCLUDE V.A.T.

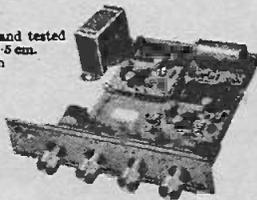
### The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power caps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power: 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 20Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control  $\pm 12\text{dB at } 60\text{Hz}$  typically 0.25% at 1 watt. Treble con.  $\pm 14\text{dB at } 14\text{KHz}$ .



£14.45
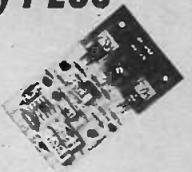
### NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £3.95



- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- 0.1% Distortion
- Distortion better than 1% at 1KHz
- Supply voltage 10-35 volts
- Thermal Feedback
- Latest Design Improvements
- Load—3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

### STABILISED POWER MODULE SPM80



SP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disco Systems, Public Address Intercom Units, etc. Handbook available 10p PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p

### STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



**SPECIFICATION**  
Frequency Response 20Hz - 20KHz  $\pm 1\text{dB}$   
Harmonic Distortion better than 0.1%  
Inputs: 1. Tape Head 1.25 mV into 60K  $\Omega$   
2. Radio Tuner 35 mV into 50K  $\Omega$   
3. Magnetic P.U. 1-5 mV into 50K  $\Omega$   
All input voltages are for an output of 250mV. Tape and P.U. input equalised to RIAA curve within  $\pm 1\text{dB}$ . from 20Hz to 20KHz.  
Bass Control  $\pm 15\text{dB at } 20\text{Hz}$   
Treble Control  $\pm 15\text{dB at } 20 \text{ KHz}$   
Filters: Rumble (High Pass) 100Hz  
Scratch (Low Pass) 8KHz  
Signal/Noise Ratio better than -65dB  
Input overload  $\pm 25\text{dB}$   
Supply  $\pm 35 \text{ volts at } 20\text{mA}$   
Dimensions 292mm x 82mm x 35mm

ONLY £13.15  
SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

Giro No. 388-7005

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS  
Postage and packing add 11p. Overseas add extra for airmail.  
Minimum order 55p. Cash with order please.  
Guaranteed Satisfaction or Money Back

# Save a massive £10 on the popular Sinclair Cambridge kit...

## now only £14.95!

(PLUS VAT)

### An advanced 4-function calculator in kit form

The Cambridge kit is the world's largest-selling calculator kit.

It's not surprising – no other calculator matches the Sinclair Cambridge in functional value for money; and buying in kit form, you make a substantial saving.

Now, simplified manufacture and continuing demand mean we can reduce even the kit price by a handsome £10. For under £15 (plus VAT), you get the power to handle complex calculations in a compact, reliable package – plus the interest and entertainment of building it yourself!

### Truly pocket-sized

With all its calculating capability, the Cambridge still measures just  $4\frac{1}{8}'' \times 2'' \times \frac{11}{16}''$ . That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of normal use before replacement.

### Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

### Total cost? Just £16.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £27.45 – so you're saving £11! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.

### Features of the Sinclair Cambridge

- \* Uniquely handy package.  $4\frac{1}{8}'' \times 2'' \times \frac{11}{16}''$ , weight  $3\frac{1}{2}$  oz.
- \* Standard keyboard. All you need for complex calculations.
- \* Clear-last-entry feature.
- \* Fully-floating decimal point.
- \* Algebraic logic.
- \* Four operators (+, -, x, ÷), with constant on all four.
- \* Constant acts as last entry in a calculation.
- \* Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £17.
- \* Calculates to 8 significant digits.
- \* Clear, bright 8-digit display.
- \* Operates for weeks on four U16-type batteries.




# A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

## Contents:

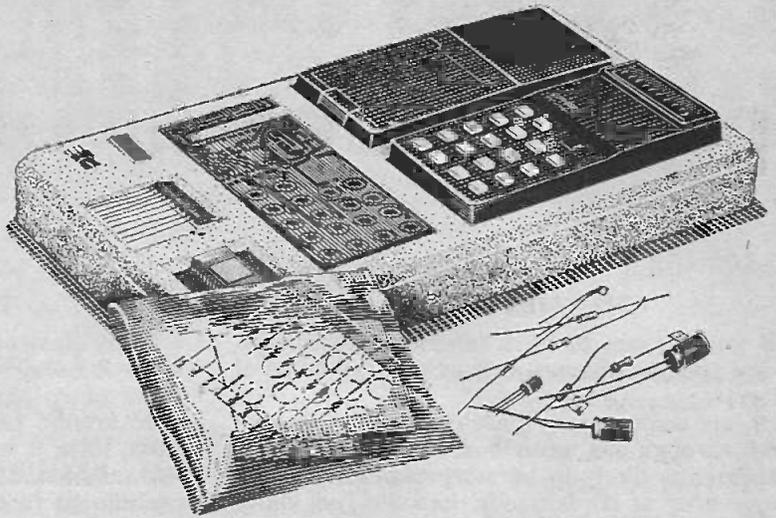1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



## This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

# sinclair

Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire  
Reg. no: 699483 England  
VAT Reg. no: 213 8170 88

Everyday Electronics, July 1974

## Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 80 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

## Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

**Price in kit form: £14.95 + £1.50 VAT. (Total: £16.45)**

**Price fully built: £24.95 + £2.50 VAT. (Total: £27.45)**

EE 7 74	
To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdonshire, PE17 4HJ	
Please send me	Name _____
<input type="checkbox"/> a Sinclair Cambridge Calculator kit at £14.95 + £1.50 VAT (Total: £16.45)	_____
<input type="checkbox"/> a Sinclair Cambridge calculator ready built at £24.95 + £2.50 VAT (Total: £27.45)	Address _____
*I enclose cheque for £ _____, made out to Sinclair Radionics Ltd, and crossed.	_____
*Please debit my *Barclaycard/Access account. Account number _____	_____
*Delete as required.	_____
PLEASE PRINT	

# everyday electronics

PROJECTS...  
THEORY.....

## ON THE PHONE

If you happen to be a telephone subscriber, one of this month's projects cannot fail to be of interest.

Of all those many unwelcome missiles that shoot through the letter box at quarterly intervals none is likely to be more unpredictable in the severity of its demands than the Post Office bill for telephone service.

"Surely we can't have made all those calls?" are the first words to be gasped by the unbelieving recipient following examination of the account. The customary dire warnings to all members of the household to moderate their conversations in future are then made—but have little lasting effect, as the next bill will undoubtedly show.

Strange how those minutes tick away. And at today's rates the charges rapidly mount up. What is required is some means to monitor the total call charge ticking up as one speaks. This, we are happy to say, is now possible with the *Telephone Call Charge Calculator* described in this issue.


A useful aid to have beside the 'phone, an ever-present reminder of the accumulated call charges and (let's hope) a deterrent or moderating influence for the more loquacious members of the family.

## TRY IT AND SEE

Many devices essential in electronics as we know it today were not in existence a mere 20 years or so ago. The magnet, in contrast, has been around rather longer: in its natural lode-stone form it was in use about 4,000 years ago. An understanding of magnetism is an essential prelude to further study into electronics principles. So this venerable yet humble and commonplace device receives top billing in the opening articles of our new series *Physics Is Fun!*

These articles, specially prepared for beginners, are intended to amuse and instruct by means of simple experiments anyone can carry out at home. The expense involved will be nil, or very nearly so. For this is one special and exceptional occasion when we advocate the seeking out an use of "junk" material.

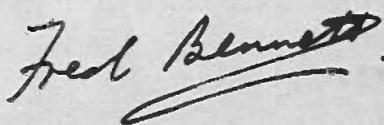Just try the experiments and you'll quickly discover that the title of this series is perfectly true.




Our August issue will be published on Friday, July 19

EDITOR F. E. Bennett ● ASSISTANT EDITOR M. Kenward ● B. W. Terrell B.Sc.  
ART EDITOR J. D. Pountney ● P. A. Loates ● K. A. Woodruff  
ADVERTISEMENT MANAGER D. W. B. Tilleard

© IPC Magazines Limited 1974. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

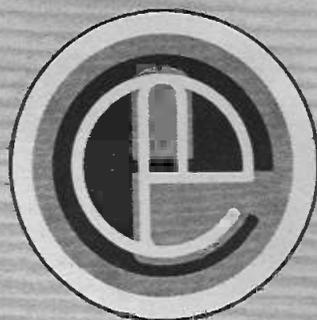All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Everyday Electronics Fleetway House, Farringdon Street, London. E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



# EASY TO CONSTRUCT SIMPLY EXPLAINED

VOL. 3 NO. 7

JULY 1974

## CONSTRUCTIONAL PROJECTS

### TELEPHONE CALL CHARGE CALCULATOR

*A watchful eye for the mounting 'phone bill* by B. W. Terrell B.Sc. 366

**AUTOMATIC LIGHT LEVEL CONTROLLER** *For constant intensity lighting* by M. Dvorak 384

**GENERAL PURPOSE 5W AMPLIFIER** *Useful in the home and workshop* by Tom Mason 390

## GENERAL FEATURES

### EDITORIAL

364

**TEACH-IN '74** *Lesson 10: Transformer, reed relay, loudspeaker and Unijunction* by Phil Allcock 372

**FOR YOUR ENTERTAINMENT** *Going abroad* by Adrian Hope 378

**RADIO ASTRONOMY AT JODRELL BANK** by S. McClelland 379

**HELP!** *Your problems answered* 382

**SEMICONDUCTOR PRIMER** *Facts and figures* by A. P. Stephenson 383

**PHYSICS IS FUN** *Magnetism* by Derrick Daines 389

**BRIGHT IDEAS** *Readers' constructional hints* 396

**COMPETITION** *Last chance to win a multimeter!* 398

**SHOP TALK** *Component buying problems* by Mike Kenward 401

**READERS' LETTERS** *Your news and views* 402

**JACK PLUG AND FAMILY** *Cartoon* 402

**KNOW YOUR COMPONENTS** *The resistor* by Ron Adams 405

**DOWN TO EARTH** *Unwanted radio reception* by George Hylton 406

Publisher's Annual Subscription Rate, including postage to any part of the world, £2-95. International Giro facilities Account No. 5122007. State reason for payment "message to payee". Address to Everyday Electronics, Subscription Department, Carlton House, Great Queen Street, London, WC2E 9PR. Binders for volumes 1 to 3 (state which) and indexes for volume 1 and 2 available for £1.25 and 11p respectively, including postage, from Binding Department, at the above address.



We are unable to supply back copies of Everyday Electronics or reprints of articles and cannot undertake to answer readers' letters requesting designs, modifications or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, both at the address shown opposite.



**BE WISE!**  
ENSURE YOUR COPY OF  
**everyday  
electronics**

Place a regular order with your newsagent

# Telephone call charge calculator

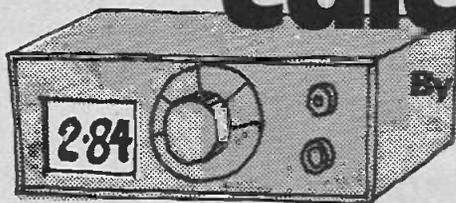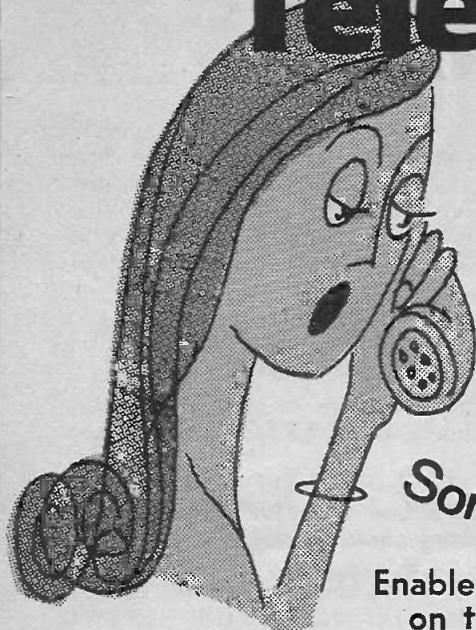

By **BRIAN W. TERRELL** B.Sc.

Sorry - can't afford another second....

Enables you to keep a watchful eye on the mounting telephone bill.

WITH the ever-increasing cost of living, it is the wise person who keeps a controlling eye on his (or her) bills as they are mounting up and puts funds aside regularly to meet the bills, so that when they do arrive he is adequately prepared for the amount demanded.

As far as electricity and gas bills are concerned, these can be easily estimated since there are dials and meters that the consumer can read and note. With the telephone bill it is not so easy since there are no dials to be read by the user and the cost of a telephone call depends on three factors:

1. Time spent on the telephone
2. Time of day the call is made
3. The distance of the call

With all these factors to take into consideration, the calculation of the costing of calls becomes complex and tedious.

The Telephone Call Charge Calculator does all the calculating for you electronically, and automatically gives you a running total of all calls placed, thus enabling the cost of all self-dialled calls over any period to be noted and allowed for.

## CHARGES

The relation between the three factors mentioned above and the cost of a call is summarised in Table 1 which is reproduced from the latest Post Office leaflet entitled "New Charges for Telecommunications Services".

It is seen from Table 1 that times for all calls are normalised to a unit of one penny (1p)—see later; that is to say, depending on the call made, one penny buys a fixed amount of time and this is charged whether the whole time is used or

Table 1: Time bought for 1p for trunk and local dialled telephone calls from STD exchanges.

Peak Mon-Fri 9am-noon	Standard Mon-Fri 8am-9am noon-6pm	Cheap Every night 6pm-8am and all day Sat and Sun	Code
24	40	90	a
8	10	40	c
(seconds)			
<b>Local calls</b>	Mon-Fri 8am-6pm All other times	3min 12min	1 2

not. For example, if a "c" call is made during the "peak" period, and the call lasts for 18 seconds, the cost is three pence.

## THEORY


The block diagram of the unit is shown in Fig. 1. It consists of a pulse generator whose

**FOR GUIDANCE ONLY**

**ESTIMATED COST\* OF COMPONENTS including V.A.T.**

**£4.50**  
**excluding case**

\*Based on prices prevailing at time of going to press

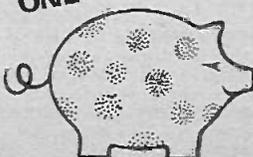

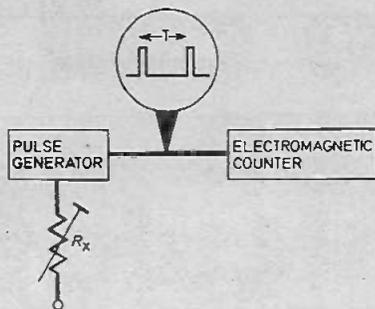


Fig. 1. Block diagram of the unit.

periodic time ( $T$ ) can be controlled by selecting value of  $R_x$  these values being trimmed so that the periodic times of the pulses are made equal to the fixed times depicted in Table 1.

The pulses are then fed to an electromagnetic counter which causes its readout to advance by one unit for each pulse received.

### INTEGRATED CIRCUIT

The heart of the unit is the versatile timer i.c. known as the "555". It is used in the astable multivibrator mode, see Fig. 2, and thus forms the pulse generator.

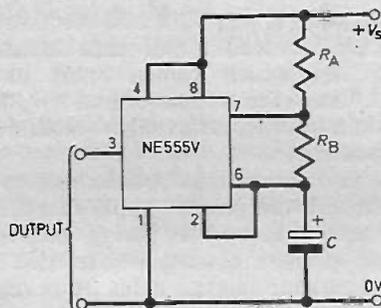


Fig. 2. The 555 timer i.c. wired as an astable multivibrator.

On connecting the positive supply voltage, the capacitor begins to charge up through the series combination  $R_A + R_B$ . When the potential at pin 6 reaches two-thirds the supply voltage, the internal circuitry of the i.c. switches and the capacitor begins to discharge through resistor  $R_B$ . When the potential at pin 6 drops to one-third the supply voltage, the internal circuitry resets and re-charging starts immediately. This action is repeated for as long as the supply is connected.

The output is at pin 3 and the voltage here can have only two values, these being either equal to the positive supply voltage or zero. While the capacitor is charging the output is equal to the supply voltage, when the capacitor is discharging the output is zero. This action is shown graphically in Fig. 3.

The reasons for using the 555 i.c. are two-fold; firstly construction is made very simple and secondly the most important, the frequency

( $1/T$ ) of the multivibrator is virtually independent of the supply voltage which can range from 5 to 15V. Also, the frequency is virtually unaffected by temperature over its range of 0 to 70 degrees centigrade. The choice of operating voltage depends on the type of electromagnetic counter used; the type used in the prototype had a coil impedance of 500 ohms and operates from a voltage in the range 12 to 24 volts. With the transformer specified, an output of 15V is available which satisfies both counter and i.c.

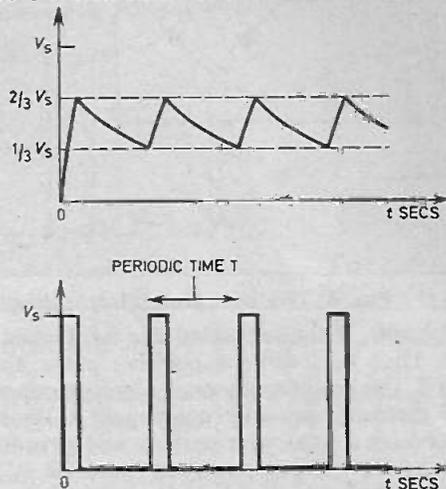


Fig. 3. (top) Charging and discharging of the timing capacitor as a function of time and (bottom) the corresponding output at pin 3.

### CIRCUIT DESCRIPTION

The complete circuit diagram of the Telephone Call Charge Calculator is shown in Fig. 4. It can be either mains or battery operated depending on the choice of the constructor. If battery operated, components T1, D1-D4, C1 and LP1 should be omitted. A suitable battery supply is three bell batteries type 126 wired in series.

The power supply consists of a readily available Friedland bell transformer and uses the 8V tappings. On full wave rectification by the diode bridge D1-D4 and smoothing by capacitor C1, a 15V d.c. supply is available.

The pulse generator has been described earlier (Fig. 2); the basic difference between the two circuits is the addition of the steering diodes D6 and D7. With these diodes, the charging time of the capacitor C2 is proportional to  $R_{10}$  and the discharge time proportional to the series combination of  $(R_1 + VR_1)$ ,  $(R_2 + VR_2)$  etc, depending on the position of S2.

This arrangement is necessary so that the charging time can be made rapid (in the order of 120 milliseconds) and the first pulse must be produced and operate the counter at the instant of switch on.

The electromagnetic counter is connected directly across pin 3 and ground, and D5 prevents the back e.m.f. produced when the counter

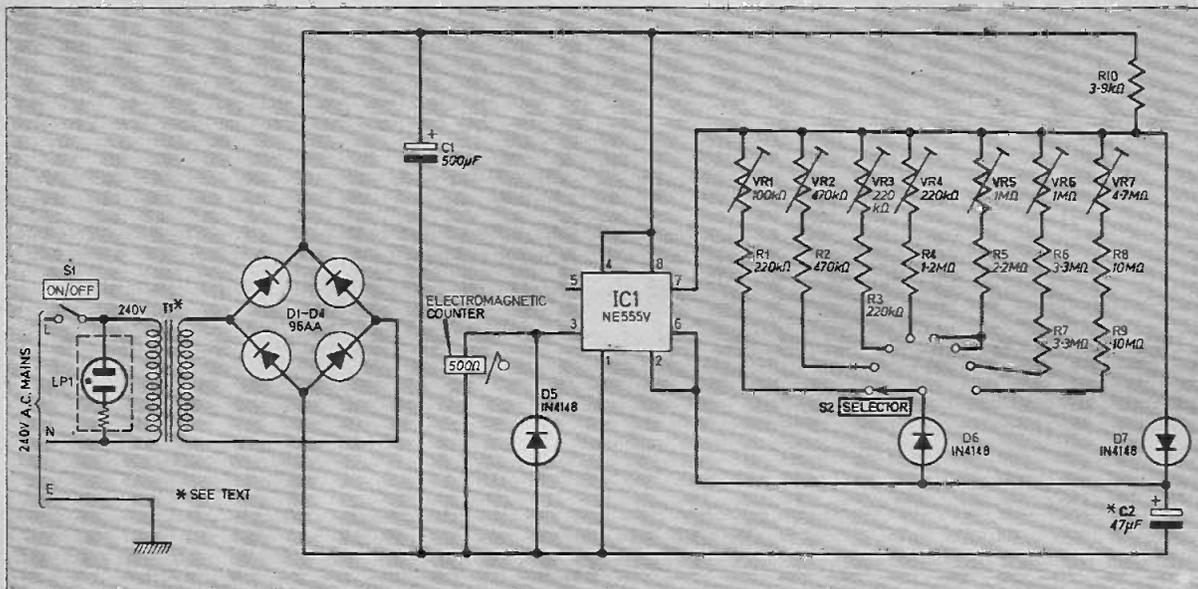


Fig. 4. The complete circuit diagram of the Telephone Call Charge Calculator.

switches off, from damaging the i.c. output transistor. Thus each time a positive pulse appears at pin 3, the counter advances by one count.

The discharge resistor (previously  $R_B$ ) has been replaced by a bank of resistors and presets, R1-R9 and VR1-VR7 respectively, and S2 is incorporated so that a fixed discharge time can be readily selected. The seven discharge paths are calculated so that the discharge times are in accordance with Table 1.

The charge ( $t_c$ ) and discharge ( $t_d$ ) times can be calculated from the following formulae:


$$t_c = 0.7 \times R_{10} \times C_2 \text{ and this has been fixed at approx. } 0.7 \text{ sec.}$$

$$t_d = 0.7 \times R_x \times C_2 \text{ where } R_x \text{ can be } (R_1 + VR_1), (R_2 + VR_2) \text{ etc.}$$
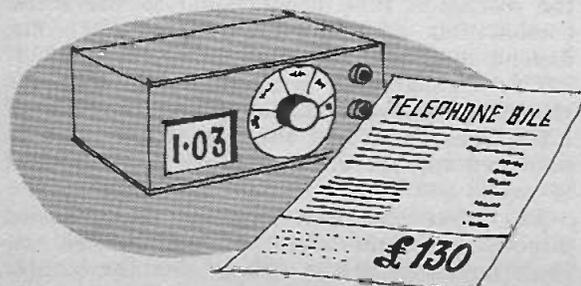
### TIMING CAPACITOR

For accurate long time delays, capacitor C2 ideally needs to be a low leakage type with low tolerance such as 20 per cent or better. Values for the discharge resistors were calculated based on a 20 per cent capacitor. Normal electrolytic capacitors may be used but may need a higher value preset than that detailed, depending on the leakage factor.

The capacitor used in the prototype was obtained from a surplus computer panel and was a tantalum type.



A 25V working electrolytic chosen at random functioned satisfactorily.

### CONSTRUCTION DETAILS

The prototype unit was built in a commercially available p.v.c. covered metal case measuring 150×130×75mm which comes apart as two "U-sections". This case size should be considered as the minimum to comfortably accommodate all the components.

There are two component boards, one to take the timing circuit and power supply components (board A), and a second to carry the timing resistors and presets (board B). In this way, should the telephone charge rates be revised in the future, it will only be necessary to remove board B to update the device.

Begin construction by drilling the fixing holes in the boards and then making the breaks along the copper tracks as detailed in Figs. 5 and 6. Now assemble and solder the components in positions indicated paying attention to diode and capacitor polarities. Veropins are used on board B.

An 8 pin d.i.l. socket should be used for IC1 as this facilitates easy removal and replacement should this be necessary. Also, using a socket eliminates possible damage from the heat of the soldering iron. When complete, recheck for possible errors and insert the i.c. in its holder, paying attention to polarity indicated by a notch at one end. Do not attach the flying leads.

Next, with reference to Fig. 7 the case should be prepared to accept the counter, S2, S1 and LPI, all of which are mounted on the front face. The case should then be drilled to accept all the other component fixings, and a hole made in the rear face to suit a grommet through which the mains cable is passed.

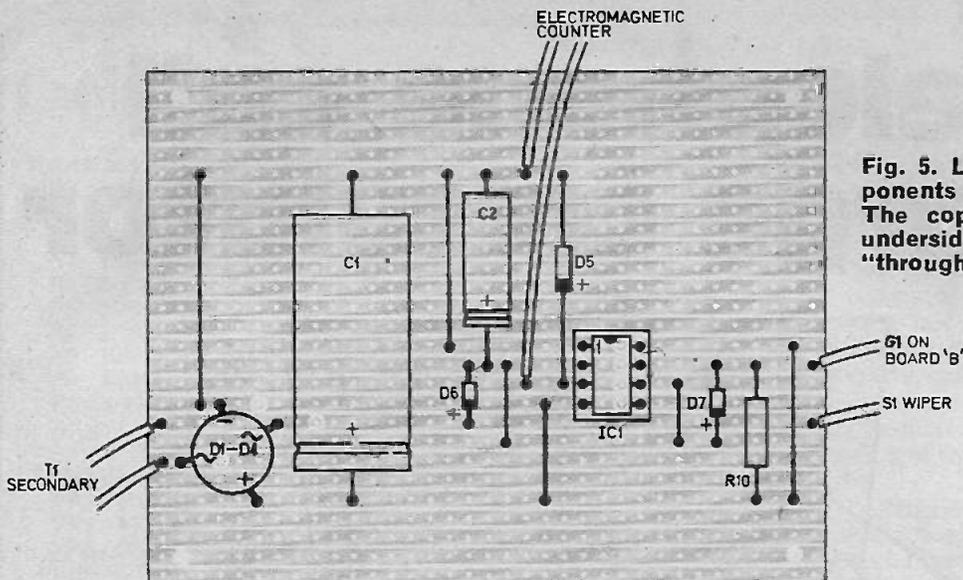


Fig. 5. Layout of the components on the main board. The copper strips on the underside are shown tinted "through" the board.

Two small aluminium brackets are required, one to hold board B in position and the other to secure the counter to the case.

With the exception of board B, secure all the components and board A in place as indicated in the photograph and wire up as shown in Fig. 7. Thoroughly check all the wiring and when fully satisfied, secure board A in place using 4BA nuts, bolts and spacers. A piece of stiff cardboard interposed between the case and each board will eliminate possible shorting against the case.

Three-core mains cable should be used and led out at the rear of the case via a rubber grommet. The mains lead should be fitted with a fused plug. A suitable earthing point is board B fixing bracket via a solder tag.


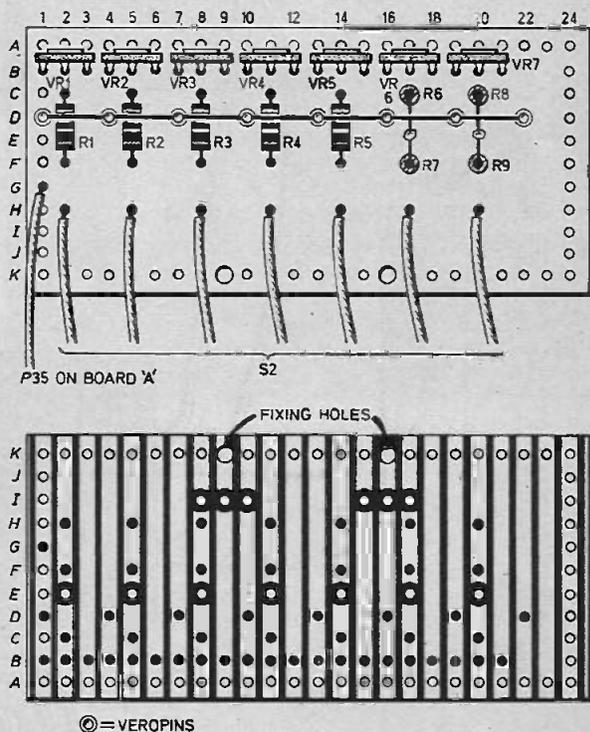


Fig. 6. Layout of the components on board B. Note the use of Veropins.

knob fitted. The pointer should be made to read "peak c" with S2 set so that (R1+VR1) are in circuit. Set all the potentiometers at their mid-way positions and plug into the mains.

Switch on at S1; the neon should illuminate and the counter should click and its readout advance by one. If this does not happen switch off immediately and check the circuit wiring etc.

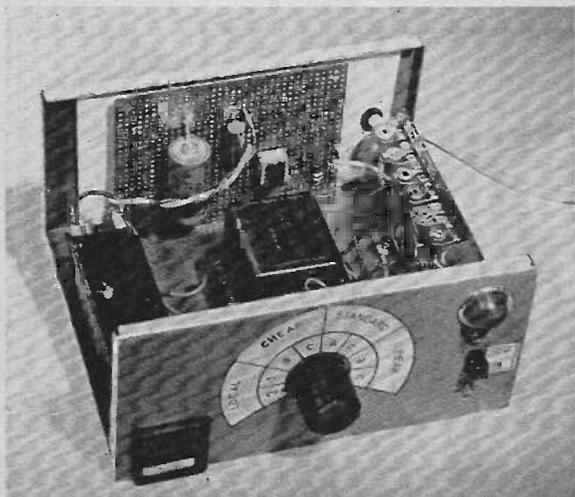Assuming all is well, switch off; obtain a timing device such as a stop watch or clock with



Photograph of the finished unit with lid removed.

## CALIBRATION

A dial should now be drawn up and glued around S2 as shown in photograph and a pointer

# Telephone call charge calculator

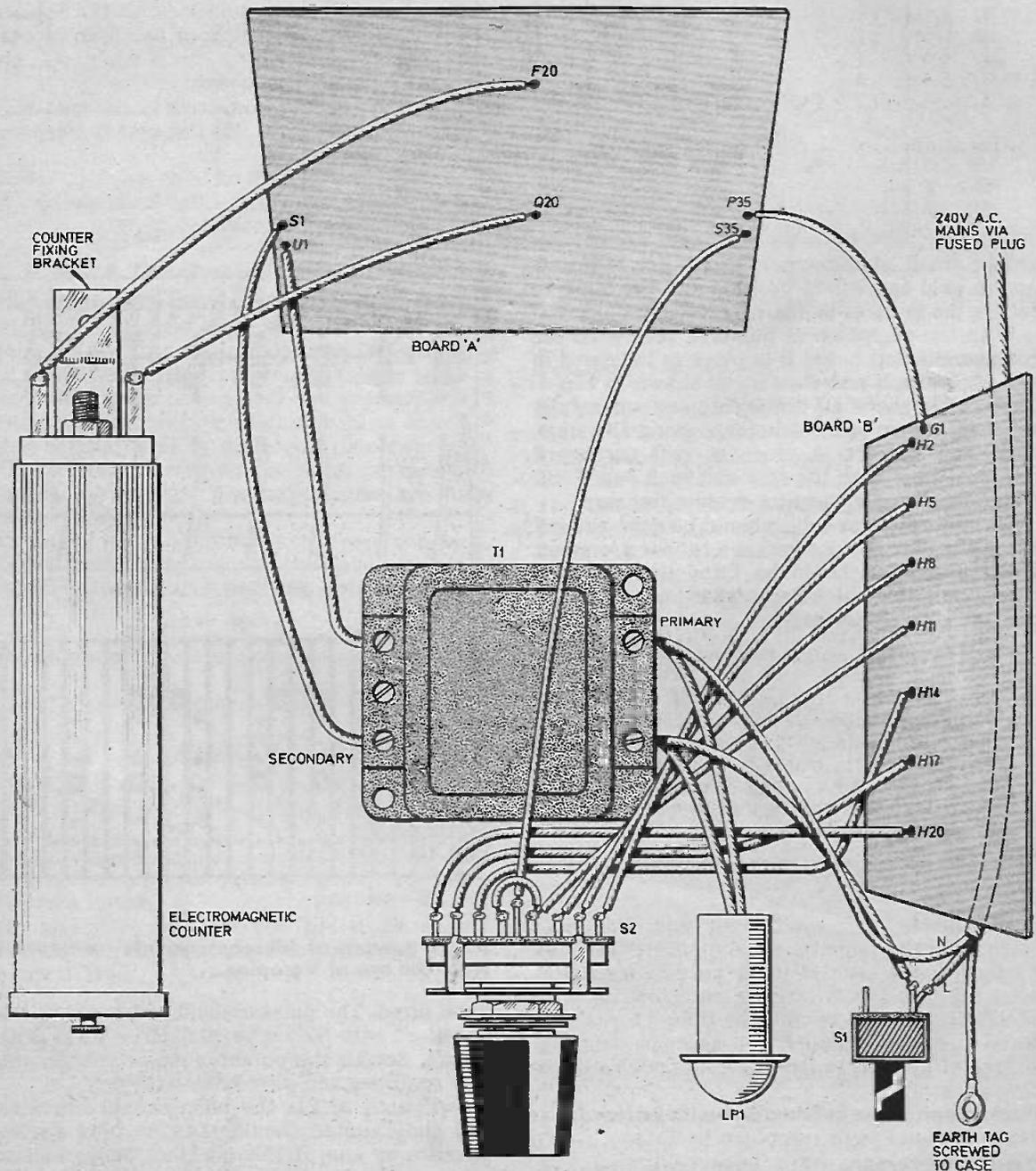


Fig. 7. The complete wiring up details of the unit.

## Components . . . .

### Resistors

- R1 220k $\Omega$
- R2 470k $\Omega$
- R3 220k $\Omega$
- R4 1.2M $\Omega$
- R5 2.2M $\Omega$
- R6 3.3M $\Omega$
- R7 3.3M $\Omega$
- R8 10M $\Omega$
- R9 10M $\Omega$
- R10 3.9k $\Omega$

All  $\frac{1}{4}$ W carbon  $\pm$  5% tolerance

### Potentiometers

- VR1 100k $\Omega$
- VR2 470k $\Omega$
- VR3 220k $\Omega$
- VR4 220k $\Omega$
- VR5 1M $\Omega$
- VR6 1M $\Omega$
- VR7 4.7M $\Omega$

All miniature carbon vertical skeleton types

### Capacitors

- C1 500 $\mu$ F 16V elect.
- C2 47 $\mu$ F 10V elect.—see text

### Semiconductors

- D1-D4 96AA  $\frac{1}{2}$ A 50 p.i.v. bridge rectifier or similar
- D5, 6, 7 1N4148 (3 off)
- IC1 NE555V timer i.c. 8-pin d.i.l.

### Miscellaneous

- S1 mains on/off slide or toggle
- S2 1-pole 8-way wafer
- LP1 mains neon with built-in resistor
- T1 Friedland mains bell transformer—see text

Electromagnetic counter type 14A or similar having a minimum coil resistance of 200 ohms that will operate at 15V; 8-pin d.i.l. socket; Veroboard: 0.1in. matrix 35 holes by 27 strips; 0.15in matrix 11 holes by 24 strips; Veropins; solder tag; length of three-core mains cable; 4BA fixings; knob; case.

SEE  
**SHOP  
TALK**

second hand, and switch both unit and stop watch on at the same time and measure the time it takes for the counter to advance by a further count after its initial turn on count. Preset VR1 should be adjusted so that the time interval between successive counts is 8 seconds. Turning the preset in a clockwise direction decreases the timing period.

All other settings should be adjusted in a similar manner with reference to Table 1.

When all ranges have been calibrated and checked, a dab of glue or nail varnish should be applied to each preset to prevent the latter being disturbed from their set positions.


## USING THE UNIT

The unit should be situated within easy reach of the telephone when in use. When wishing to cost a call, the call code should first be determined from the Dialling Instructions booklet as an "a", "c" or local call; switch S2 is then set to this code according to rate for the time of day i.e. cheap, standard, peak, 1 or 2 (see Table 1).

The call should then be dialled and the unit switched on at the instant of "getting through"; the unit should be switched off as the receiver is replaced. The difference in the counter readings before and after the call is made, will give the cost of the call in pence.

Alternatively, the counter can be read regularly, say once a week and the weekly telephone bill determined.

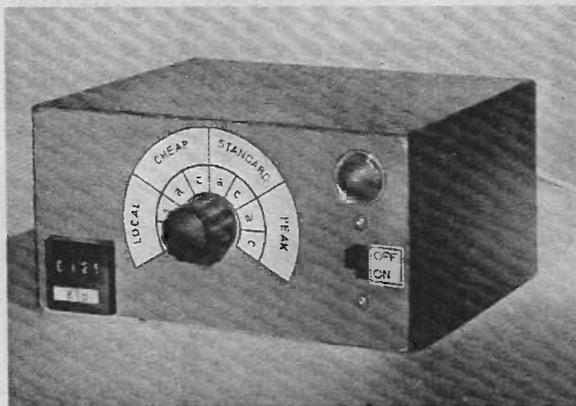In the Dialling Instructions booklet (issued pre-Oct 1973) there are some calls coded "b", these should now be changed to "c".



Photograph of completed unit.

## REVISION OF CHARGES

Since the charges at present are normalised to a 1p unit, the counter display can be read directly in pounds and pence. If in the future the basic unit changes from 1p the readout will give the number of units used.


Also, if the rates are later revised, the timing resistors will need replacing, values being calculated using the formula given above.



# TEACH-IN '74

FOR BEGINNERS IN ELECTRONICS ...  
THEORY AND EXPERIMENTS

TUTOR: PHIL ALLCOCK\*

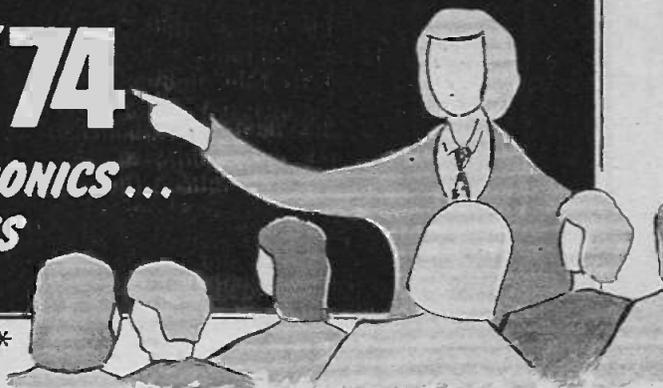

## LESSON 10 Transformer, Reed Relay, Loudspeaker and Unijunction

THE ratio of the numbers of turns on the coils is an important quantity since it can be used to measure the amount by which the input voltage or current is transformed (i.e. stepped up or down).

### RATIO

The Friedland transformer, which is used later in the Tutor Board experiments, is designed to be connected to the normal mains supply on the primary side and to supply 3, 5 or 8 volts from the secondary side.

The mains supply provides the current to magnetise the core and since the supply is a.c. the resulting magnetic flux is continuously varying. The varying flux links equally with the primary and secondary coils and each coil will have a voltage induced in it, just as in the case of the alternator coil.

Since the changing flux is common to all coils the rate of change of flux linkage will only depend on the number of turns on each coil. The situation is illustrated in Fig. 10.1 and if we assume that  $N_1=3000$  and  $N_2=100$  the primary flux linkage will be  $3000\Phi$  whereas the secondary flux linkage will be  $100\Phi$ . ( $\Phi$  represents the rate of change of magnetic flux.)

We know that voltage is proportional to the rate of change of flux linkage so we can write:—  
(primary current)  $\times$  (primary turns) =  
(secondary current)  $\times$  (secondary turns)

The first equation tells us that  $\Phi = \frac{240}{3000}$  and substituting this in the second equation we get—

$$\text{Secondary voltage} = \left(\frac{100}{3000}\right) 240 = 8 \text{ volts.}$$

The ratio 100:3000 is the "step down" turns ratio going from the primary coil to the secondary coil. Note that the coil with least turns also has the least voltage. The turns ratio thus determines the output voltage for a given mains supply voltage at the primary (input) coil. If this same transformer was connected to a mains supply of say 210 volts the output voltage would be reduced:

$$\text{Output voltage} = \left(\frac{100}{3000}\right) 210 = 7 \text{ volts.}$$

### TRANSFORMER ON LOAD

If a resistor or some other form of load is connected to the secondary a secondary current must flow due to the existing secondary voltage.

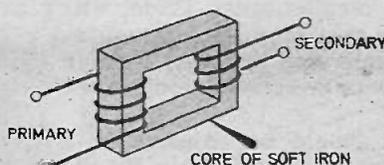
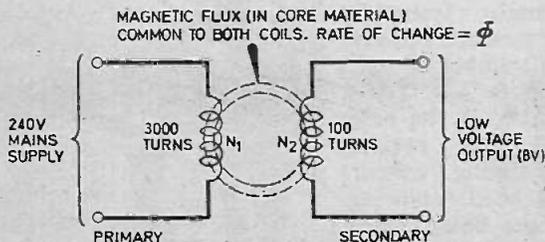


Fig. 10.1. Flux linkage in a simple transformer, and illustration of a simple transformer system.

\* North Staffordshire Polytechnic (Any communications arising from the Teach-In '74 series must be addressed to Everyday Electronics, Fleetway House, Farringdon Street, London E.C.4).

To keep the magnetisation of the core at its correct level, so that the primary induced voltage is equal to the mains supply voltage, extra current must be taken from the mains supply to compensate for the flow of secondary current.

Since the magnetic effect of each current depends on the product of the current magnitude and the number of turns through which it flows, the transformer flux "constancy" requires that:

$$(\text{primary current}) \times (\text{primary turns}) = (\text{secondary current}) \times (\text{secondary turns}).$$

Thus the current ratio also depends on the turns ratio but this time the least turns is associated with the greatest current. If our load is 100 ohms an 8 volt output would give a secondary

current of  $\left(\frac{8}{100}\right)A = 80\text{mA}$ . The corresponding

primary current would be  $\left(\frac{100}{3000}\right)80\text{mA} = 2\frac{2}{3}\text{mA}$ .

If these are the r.m.s. values, the power dissipation in the load will be 0.64 watts and a similar power is taken at the primary side since

$$240\text{V} \times \frac{8}{3}\text{mA} = 640\text{mW}.$$

Our transformer is 100 per cent efficient simply because we have not allowed for any of the losses that occur in practice due to coil resistances, core heating and magnetisation. For our purposes we can neglect these losses and use the following simple relationship for all our calculations:

$$\left(\frac{\text{primary turns}}{\text{secondary turns}}\right) = \left(\frac{\text{primary voltage}}{\text{secondary voltage}}\right) = \left(\frac{\text{secondary current}}{\text{primary current}}\right)$$

## REED RELAY

Another component that uses the magnetic effect of a current is the reed relay. The reed switch is usually encapsulated in a thin glass tube and consists of two (or sometimes three) blades made of magnetic material. The tips of the blades are usually gold plated to form a low resistance contact.

If the reed switch is exposed to a suitable magnetic field from a current-carrying coil or a permanent magnet the blades become magnetised and the contacts attract each other. If the magnetic field is sufficiently strong the contacts will close whilst the field is present. The reed switch with outer coil is known as a reed relay, and a wide variety of different types are now available.

Some switches have three blades to form a "change-over" contact. One of the characteristics of these switches is that the contacts can "bounce" when the relay is operated. This means that the contacts do not settle down to their

operated positions immediately but undergo a series of momentary closures before final closure. The effect is due to the bouncing of contacts and can depend on the strength of the magnetic field used.

In some systems this "bounce" cannot be tolerated and precautions must then be taken to minimise its effects. In the experiments this month a simple "make" contact switch is used to demonstrate the action of the reed relay using an easily wound relay coil.

## RELAY TRANSIENTS

If an inductor, reed relay coil or transformer winding carries a steady current (d.c.) the resulting magnetic field will be constant. When the current is switched off the magnetic flux must fall to zero and must therefore generate an induced voltage in the coil due to the changing flux linkage. Since the rate of change can be very high, large induced voltages can be produced which might cause damage to semiconductor devices if not protected.

A typical situation in which a reed relay coil is connected in the collector circuit of a transistor is shown in Fig. 10.2. If the transistor is saturated when on, the collector current will be limited by the resistance of the reed relay coil which in this case is one kilohm. When the transistor is switched off the collapsing magnetic flux, linked with the coil turns, produces an induced voltage that makes the collector end of the coil positive with respect to the other end.

By connecting a suitable diode D1 across the coil, as shown dotted, this voltage spike can be limited so that excessive voltage does not appear at the transistor collector. The diode provides a current path whilst the field collapses and the energy previously stored in the magnetic field is lost by power dissipation in the coil.

In some circuits, resistance is included in series with the diode to limit the current flow. The waveforms in Fig. 10.2 show the effect of the diode. Note that the induced voltage is established in a direction that tries to maintain the relay current in its original direction.

By using similar reasoning it can be seen that if we switch a current on and off and the current flow is via, say, a transformer winding, then a large voltage can be produced at a second winding if a suitable turns ratio is employed. This is of course the same principle as that used in the well established method of generating the high voltage pulses for the spark plugs of a car-engine.

## LOUDSPEAKER

One further component using magnetic effects is the moving coil loudspeaker. Just as the coil of a moving coil meter is made to turn by the interaction of a permanent magnet field and the field of the current-carrying coil, so the cone of


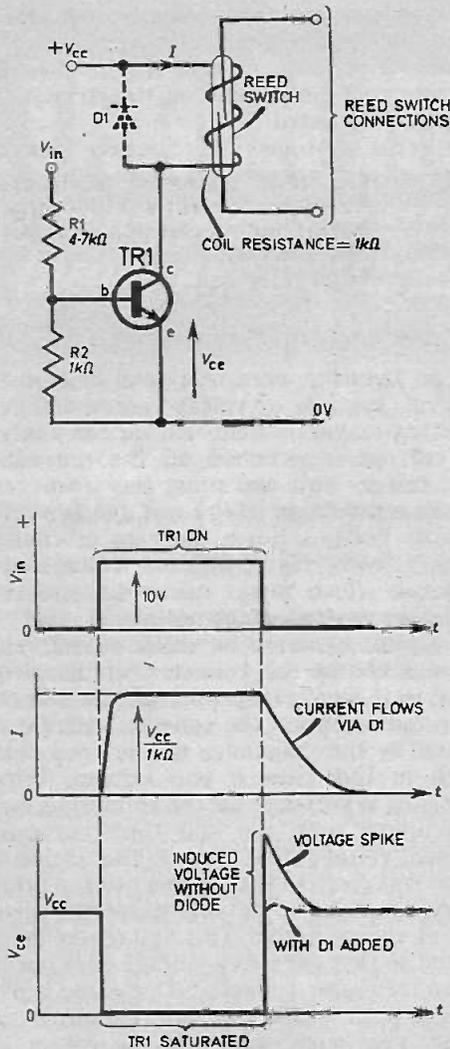


Fig. 10.2. Transistor operated reed relay with associated waveforms.

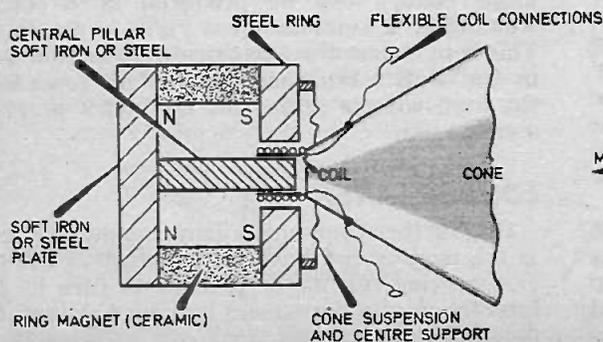a loudspeaker is displaced by a similar interaction. In this case the moving coil is attached to the base of the cone and the cone movement generates variations in air pressure which we observe as sound, see Fig. 10.3.



It is apparent from what we have said so far that devices employing magnetic effects are very common in electrical and electronic engineering. Some of these devices are specialised and need not concern us now. However the main features of the electromagnetic effects have been illustrated and it is usually a straightforward matter to apply the basic ideas to other devices such as buzzers, horns and motors.

## OTHER SEMICONDUCTOR DEVICES

In addition to the diode and bipolar transistor, covered in earlier lessons, a wide variety of semiconductor devices exist and some of these will be used in the experimental circuits that have been planned for the remaining parts of the Teach-In series. The first of these devices is the so called unijunction transistor which was originally known as a double-base diode.

Like the bipolar transistor it has three connections but there the resemblance ends. The device we have selected is the TIS43 and we shall deal specifically with this type, but other types of similar ratings are available and may be tried if these are available.

## UNIUNCTION OPERATION

The unijunction behaves in some respects like a voltage-sensitive switch. The device connections are known as emitter (e), base No. 1 (b1) and base No. 2 (b2) and these are illustrated together with the circuit symbol in Fig. 10.4. Notice that the arrow head on the emitter symbol points towards the connection known as base No. 1 (b1).

As far as the b1, b2 connections are concerned the device behaves just like a resistor made of lightly doped n-type silicon material. The use of light doping means that the resistance of the device between the points b1 and b2 is relatively high, typically 10 kilohms, due to the restricted number of free electrons available.

The connections to the silicon at b1 and b2 are "non rectifying" i.e. they do not behave like a diode, but the emitter connection which is formed part way along the silicon material is in

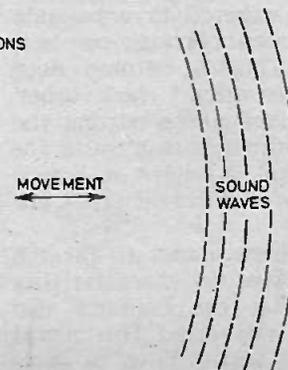


Fig. 10.3. Construction of a loudspeaker using the moving coil principle.

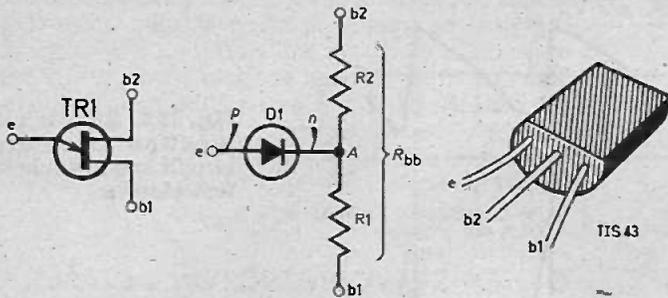


Fig. 10.4. Detail of the unijunction transistor, circuit symbol, equivalent circuit and mechanical details.

fact a normal *pn* junction and so the equivalent circuit for the unijunction is as shown in Fig. 10.4.

Point A represents the region at which the emitter junction is formed and R1, R2 represent the resistance of the material between this point and the base connections b1, b2. In use, a voltage  $V_{bb}$  is developed across the effective potential divider formed by R1 and R2 as shown in Fig. 10.5 and this makes point A positive with respect to b1. If the total resistance is  $R_{bb} = (R1 + R2)$  then we can define our first useful parameter as

$$\eta(\text{eta}) = \frac{R1}{R_{bb}} = \text{intrinsic stand-off ratio.}$$

This rather fancy title need not frighten anyone—it is simply the ratio of the resistance R1 to the total resistance  $R_{bb}$  and is particularly useful since the voltage at A is given by  $\eta V_{bb}$ . Since the voltage level at A is important to the subsequent mode of operation it is useful to realise that  $\eta$  must always be less than unity and is typically about 0.6 for the TIS43 transistor.

Thus if  $V_{bb}$  was set to +10 volts the voltage at point A would be +6 volts (measured with respect to the b1 terminal). Let us now consider the test circuit of Fig. 10.5 in which the emitter is connected to a variable voltage supply via a current limiting resistor  $R_e$ .

If we had suitable instruments available we could measure the current  $I_e$  and the voltage  $V_{eb1}$  for various settings of the variable voltage supply  $V_{ee}$ . With  $V_{bb}$  connected and  $V_{ee}$  set at zero a small leakage current would flow via the diode because of the positive voltage at point A. As we increase  $V_{ee}$  this leakage current would reduce until at point Z, on the characteristic shown in Fig. 10.5, the current would be zero.

For this zero current condition the emitter-base voltage  $V_{eb1}$  must be equal to the voltage at point A so that the voltage across the diode

is zero. Thus the voltage at point Z is

$$V_{eb1} = \eta V_{bb} = \text{voltage across R1,}$$

and  $I_e = 0$ . If we increase  $V_{ee}$  further the voltage  $V_{eb1}$  will continue to rise until the diode starts to conduct. This is a critical point on the characteristic (X) and is known as the **peak point**.

As the diode starts to conduct the number of current carriers in the R1 section of the device increases and this has the effect of increasing the conductivity of the silicon in this region. The resistance R1 thus tends to fall and this causes a further increase in diode current.

The resulting characteristic is shown by the curve between X and point Y, and this latter point is usually known as the **valley point**. Once the peak point is reached the transition from X to Y is very rapid and does not require any change in  $V_{ee}$ . The increased emitter current is limited by the external emitter resistor  $R_e$  and if the transistor reaches the region to the right of the valley point the circuit will remain in this new condition until the  $V_{ee}$  supply is disconnected or reduced to a much lower value.

If  $R_e$  is made sufficiently large the current  $I_e$  will not reach the valley current and the circuit can then be made to oscillate by adding a single capacitor to the emitter circuit.

## OSCILLATOR

The complete oscillator is shown in Fig. 10.6 where it can be seen that the same battery is used for the two supply voltages i.e.  $V_{bb} = V_{ee}$ . The resistance in the emitter is made variable, by VR3, and has a minimum value determined by R1. A second variable resistor VR1 is used as a potentiometer in the b1 lead to derive an output voltage waveform.

The capacitor C1 charges via the resistances and VR3 and the capacitor voltage ( $V_c$ ) rises exponentially as described in earlier lesson material. When the critical peak voltage ( $V_p$ ) is

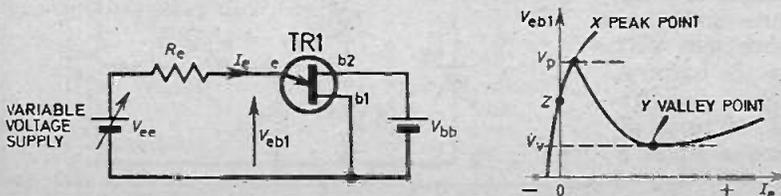


Fig. 10.5. Unijunction operating characteristics.

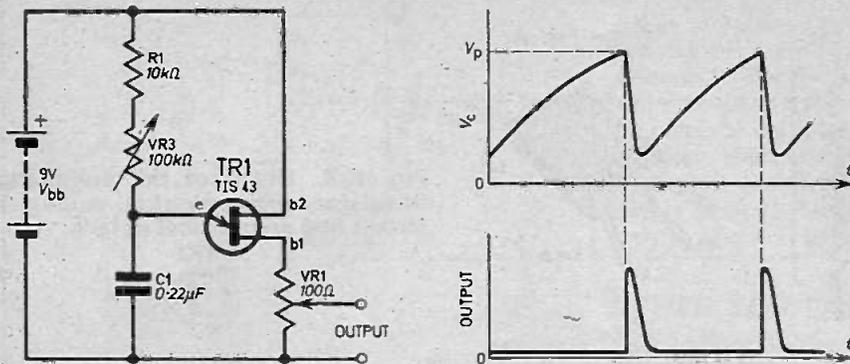


Fig. 10.6. Simple uni-junction oscillator circuit and associated waveforms.

reached the transistor switching action is initiated and  $V_c$  falls rapidly. If the total emitter resistance is large enough the final emitter current will be limited to less than the valley point current and the capacitor will start to recharge again.

Every time the capacitor discharge occurs a pulse of current flows via VR1 and this produces a series of voltage pulses at the output. Since the charging of C1 depends on the time constant C1 (R1+VR3) the frequency of the pulses can be controlled by VR3. The waveforms shown in Fig. 10.6 illustrate the circuit behaviour. Note that the voltage  $V_p$  is given by

$$V_p \approx 0.5 + \eta V_{bb}$$

where the forward voltage of the emitter diode has been taken as 0.5 volts. Since  $V_p$  depends on both  $\eta$  and  $V_{bb}$  the frequency will also depend on these two quantities.

Next month we shall investigate some of the features of field effect transistors.

## TUTOR BOARD EXPERIMENTS

### Test No. 20

Remove the cotton from the plastic spool (as listed in the May 1974 issue) by winding it onto a piece of cardboard so that it is not wasted. Carefully wind the enamelled wire onto the spool until it is full. The start end can be fixed with sticky tape, to stop it slipping, and it will help if someone can support the bobbin of wire on a knitting needle whilst the coil winding is in progress. Fasten the end of the wire with tape to complete your relay coil.


Use the circuit of Fig. 10.7 to check that your reed switch operates. The potentiometer VR1 can be used to vary the coil current—note that your coil will have a low resistance and VR1 helps to limit the current taken from the battery. The prototype coil used a plastic spool approximately 1½ inches long and a coil of 400 turns of 30 s.w.g. wire. The coil resistance was about 3 ohms.

The 6-RSR-A reed switch requires 20 to 40 ampere-turns to give reliable operation and with 400 turns this means a current of 50 to 100mA. By noting the position of the potentiometer VR1 at which the relay operates it may be possible to estimate the operating current for your coil. Once operated the current must be reduced to about half the operating value to ensure that the relay contact opens again.

If the range of adjustment is insufficient using the 100 ohm potentiometer an additional resistor of 100 ohms, 1W, can be used to reduce the coil current using the circuit modification shown in Fig. 10.7. With this arrangement the maximum current is limited to about 45mA but the current can be reduced to zero.

If a larger number of turns is used the operating and release currents will be correspondingly reduced. A coil of at least 400 turns is recommended. An accurate measurement of operating and release current can be made by measuring the voltage drop across the 100 ohm fixed resistor but because of the limited maximum current not all coils can be tested this way.

Fig. 10.7. Reed relay test circuit and modification.

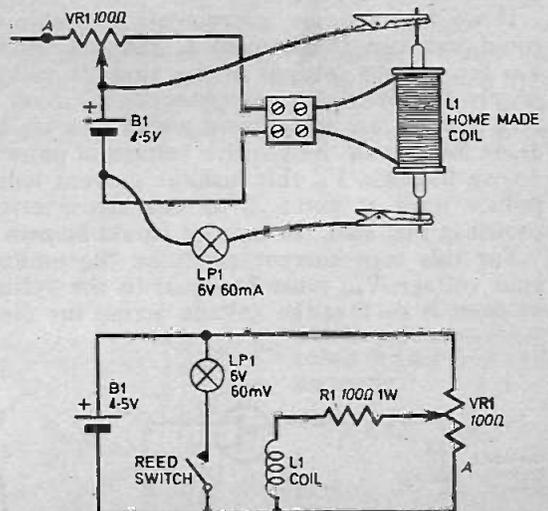



# For your Entertainment...

By Adrian Hope

ONLY a few years ago the only electronics used for entertainment in most homes was a radio set, a simple black and white TV set running on an indoor aerial, and a mono record player. Now many people are almost literally ankle deep in exotic electronic gear. And daily they are subjected to the temptation of buying yet more.

Matching one piece of new equipment with another so that both work properly is no mean feat and I'll bet that all over the country, or the world for that matter, there are expensive electronic arrangements producing such bad results that the owner would have been far better off with what he had before.

Some times the fault is with the equipment, some times with the setting up and some times local conditions are responsible for poor results. Whatever the cause the effect is little or no entertainment for anyone. The idea of this column is to offer a few practical suggestions on buying and using equipment which really is primarily *For Your Entertainment*.

## CONTINENTAL ENTERTAINMENT

Cheap holidays in Spain and the Balearic Islands beckon all the year round. So a few thoughts on the electrical facts in Spanish life should not come amiss. Also many people, myself included, like the idea of a little music or world news being available on tap in the privacy of our hotel room.

Palma, Majorca has a local f.m. studio which broadcasts in the English language every evening and into the night on 96.6MHz. The programming is mostly good popular music, for instance in the Sinatra bracket, and reception is fine in the coastal area around

Palma. But because the station is low strength (1 kilowatt transmitter power) and the island very mountainous, you will be hard pressed to receive it in any other part of Majorca.

This radio station is, incidentally commercial and one of the few in the world that you can visit any time you like. This is because the "studio" is a Palma bar called "My Own Place" run by American expatriate Riki Lazaar. Buy the local English language newspaper (The Majorca Bulletin) for further information.

Elsewhere in Spain there is little, if any, English language f.m. radio so you will need to rely on the medium and long wave bands for your listening. And this is where the plot starts to thicken. Although Radio Algeria should come in loud and clear on the long wave band with some light music every night, it is in many concrete hotels likely to be a weak signal and drowned out by local interference. The prime source of this interference is hard to tie down but may well be thyristor-controlled circuitry for dimming lights or controlling heaters or drive motors for lifts and airfans.

## INTERFERENCE

The interference problem is bad enough in England, but in Spain it is even worse and reception of m.w. and l.w. may be impossible. This is probably because even new modern hotels being built there are electrically wired with little or no earthing. This is not only potentially dangerous, but it also means that any interference which is created for instance by a motor, a thermostat or a thyristor control will have the best possible chance of pervading the hotel wiring system, which then acts as one glorious aerial.

I have stripped down several

hotel wall sockets and switches in Spain and never yet found any earthing, even in stone-floored bathrooms where unshielded two-pin sockets are provided with astonishing lack of common safety sense. Shocks received from lift switch panels also suggest that their high-power drive motors may be unearthed. And even the toilets in some new Spanish hotels are flushed by heavy duty electric solenoids. Small wonder that a.m. radio reception is so poor!

Of course f.m. radio is largely immune to interference of this type, but as we have already seen, there is relatively little f.m. to be received. So anyone going on holiday to Spain and wanting to be sure of some music in their hotel room, will need to take not only an f.m./a.m. radio, but also a cassette player with some pre-recorded cassettes. That way if there is no local f.m. station and local interference blots out everything on the a.m. bands, taped music can come to the rescue.


## VOLTAGE

Incidentally, the mains supply voltage in Spain is now a nominal 220 volts a.c., with the plug sockets of standard continental two-pin type. The pins of the plugs to fit these sockets are smaller than those on British two-pin plugs and are spaced apart by 2cm.

Although adapters to convert British plugs to continental size are cheap in most Spanish shops, the hotels often charge an exorbitant price so it may be worth buying one in England. And don't be too bothered if you run equipment such as a shaver, hair dryer or radio off the mains and find its performance erratic.

Although mains voltage is nominally 220 volts it fluctuates like mad, often down to around 190 volts. In this country a 6 per cent change only is allowed by law i.e. 15 volts either way. All over Spain there is a roaring trade in voltage stabilisers for use with television sets. So if you see a television in a bar and it has a mysterious white boxed gadget standing on top, the chances are that it's a stabiliser. This keeps the voltage to the set steady and prevents the picture size from shrinking.

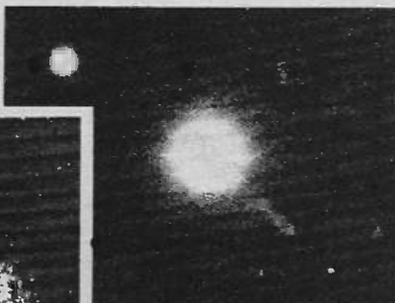In fact a few days with Spanish electricians makes the British system a joy to live with.



*The Andromeda Galaxy  
The Crab Nebula  
The Quasar 3c 273*

*(United States Information Service)*

# RADIO ASTRONOMY AT JODRELL BANK

BY S. McCLELLAND

EVERY second of the day and night, many types of electromagnetic radiation impinge on the earth from outer space. Although we can see some of this—the starlight—most is invisible and it was totally unknown until the advent of radio astronomy.

This fascinating science probes every secret of our amazing universe through this newly-discovered “window”. To do this, it uses highly-complex instruments such as the radio telescopes at Jodrell Bank, Cheshire where Manchester University’s Nuffield Radio Astronomy Laboratories are based. This article will briefly look at these telescopes and the purpose for which they were built.

## A NEW WINDOW ON THE SKY

The science of radio astronomy is young even compared to the relatively brief life of radio communication. Indeed, it was not until 1931 that Karl G. Jansky, an American engineer working on the problems of radio interference, discovered a background static in his equipment and deduced from its nature that it must originate in space. Although he published the results of his important work little notice was taken of it.


In fact, only an American radio amateur named Grote Reber followed up Jansky’s discoveries by building a small parabolic dish aerial in his garden. He used it to discover that areas of our galaxy were strong radio sources. However it became apparent that, contrary to expectations, only our sun, among all the normal stars in the sky, had a definite radio output

associated with it. This is because of its proximity.

The second world war provided an impetus to radio astronomy and the subject was re-examined. Among the post-war researchers in England was a physics lecturer at Manchester University named Bernard Lovell.

Interested in the detection of the cosmic rays and meteors which continually bombard our planet, he was allowed to set up his equipment on a site free from man-made electrical interference at the botanical department of the University—a place called Jodrell Bank.

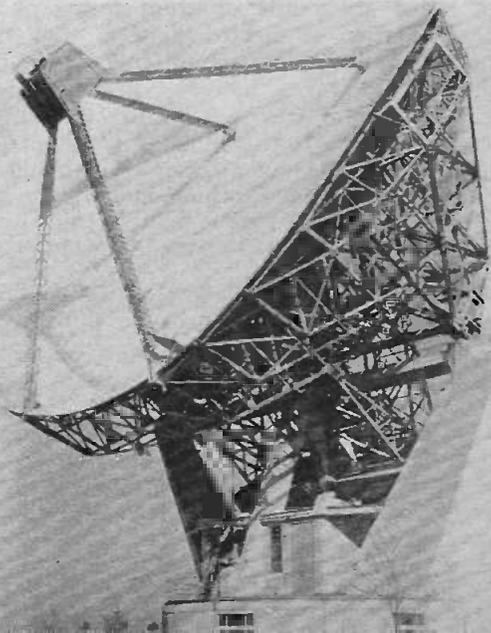Jodrell Bank mark II radio telescope. (Jodrell Bank)



## THE GROWTH OF JODRELL BANK

The work of Bernard Lovell with fairly elementary equipment was so successful that he was allowed to build larger and more efficient radio telescopes. Eventually he realised that to make further progress a giant, fully-steerable radio telescope with a parabolic dish 250 feet in diameter, was required.

The magnificent design of, and supervision work on, the telescope was carried out by H. C. Husband and Co., of Sheffield.

Construction of the telescope commenced in 1952, and it was finished in the International Geophysical Year of 1957. About half of the £700,000 cost was borne by the Department of Scientific and Industrial Research (now the Science Research Council), the bulk of the remainder being very generously met by Lord Nuffield and the Nuffield Foundation.


Any existing doubts about the value of the telescope were disposed of in an immediate and spectacular way, when the instrument showed its great versatility by being the first Western device to detect and track the carrier rocket of the first space satellite—the Russian Sputnik I. Great successes, also in the field of tracking, continued to be achieved at Jodrell Bank, notably with the American Pioneer space probes, and the first man-made object to hit the moon—the Russian Lunik II.

Today, Jodrell Bank has become world famous through these events, but it still remains primarily a radio astronomical station with a very small percentage of its research time being devoted to tracking. In the past decade, it has been greatly involved with the discoveries of the so-called “new” astronomy—especially the fantastic quasars and pulsars.
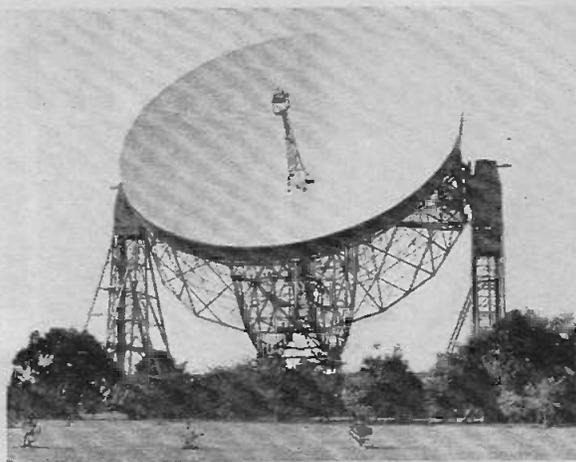
## THE RADIO TELESCOPE

The light and radio waves which originate from space are really different forms of the same radiation — electromagnetic radiation. Some methods of receiving them are thus similar. Radio waves, however, are very much longer than light waves—typically ten million times, and those from about one centimetre to many metres in wavelength can easily penetrate the earth's atmosphere which hinders the passage of light waves. This means that radio astronomical observations can be made through cloud and mist, etc.

However, because of the dissimilarity in wavelengths, radio telescopes have to be much larger in order to achieve the resolving power—or distinguishing power—of a comparable optical telescope. Hence the collecting area, the parabolic dish, of the big telescope (called the mark IA) at Jodrell Bank is 250 ft. in diameter. This steel bowl weighs over 1,000 tons, and the giant mass of steel which supports it weighs roughly twice as much.



This photograph gives some idea of the size of the Jodrell Bank Mark IA telescope. (Jodrell Bank)

Modifications recently carried out on the telescope have resulted in a lower working wavelength, namely 11 centimetres. The instrument has a large working range and is thus very versatile in operation. Indeed, it is this versatility which has contributed to the great success of the telescope. It is also fully steerable, still one of the largest of this kind in the world, and it can be pointed to any area of the sky.


This is achieved by using computer-controlled electric motors to drive the complete telescope in azimuth (i.e. to the various points of the compass) and the bowl alone in elevation (i.e. tilt) through two huge racks that were salvaged from the gunnery equipment of the *Royal Sovereign* battleship. These are housed at the top of the two bowl support towers, 180 feet above the ground.

Radio waves which are collected by the bowl are focused on to the aerial at the dish's centre. Here, a very sensitive receiver amplifies the weak signals and they are passed to the control building and converted to binary form for analysis by a computer. This can print out its results on punched tape for further reference or make pen-recordings of signal intensity in the area of sky studied.

This is the nearest the radio astronomer can get to having a “picture” of the source, but his observations are usually combined with those made by an optical telescope in the same area to build up a complete knowledge about it.
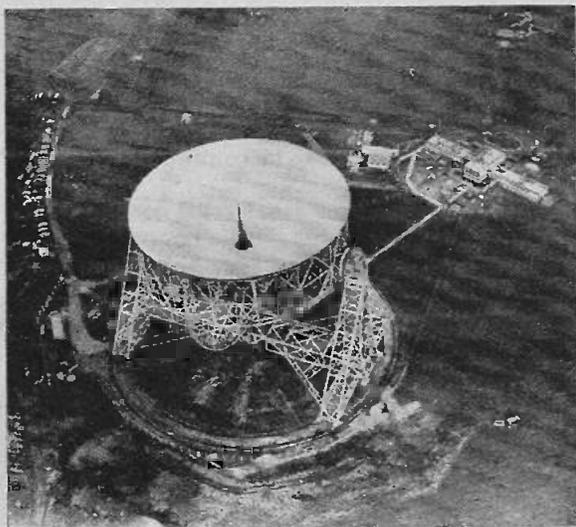
## OTHER TELESCOPES

Besides the mark IA, Jodrell Bank also has a mark II instrument. This is a smaller and more recent instrument with an unusual dish shape (see photograph) and it is used for lower wavelength work.



**Aerial view of the Jodrell Bank telescope.**

A similar telescope, the mark III, has a mesh dish and is stationed near Nantwich.

These instruments, besides being independent, can be used together, the output from each telescope being combined in a special way to effectively produce a very large radio telescope. The complete arrangement is known as an interferometer. Interferometers have been constructed between a Jodrell Bank telescope and instruments at places as far ranging as Malvern in Worcester, to Onsala, Sweden and Arecibo, Puerto Rico.

The remaining instruments at Jodrell Bank include a 50 foot telescope for lunar radar and miscellaneous work and another 50 foot "az-el" telescope for tracking space probes.

## **THE NEW TELESCOPE**

In December 1972, it was announced that the University of Manchester is to build another radio telescope on a site near Welshpool, in Wales. The diameter of its dish will be 375 feet, making it the largest of its type in the world. It also means that the telescope's resolving power will be considerably greater than that of the present mark IA.

## **THE RADIO SKY**

There are several varieties of radio sources in the sky, and Jodrell Bank has been concerned with almost every type, ranging from the radio "noise" areas of the sun and the planet Jupiter to the incredibly distant objects in the farthest reaches of the universe.

A great feat of radio astronomy has been the mapping of our galaxy. This is because the internal structure of the atoms of hydrogen gas of which the galaxy is largely composed can undergo a slight energy change. This change

gives rise to a radio signal on a unique wavelength of 21cm, which can be detected by radio telescopes such as those at Jodrell Bank, so the distribution of hydrogen in our galaxy can be mapped. Also, the fact that the hydrogen line, as it is called, is sometimes slightly shifted in frequency due to the Doppler effect, means that the hydrogen gas and, therefore the galaxy, is in motion.

Such investigations have helped to build up a picture of our galaxy as being a gigantic, slowly rotating disc with spiral arms. It is indeed huge—about 100,000 light years across (a light year is the distance light travels in one year: it is about six million million miles)—and probably contains in the region of 100,000,000,000 stars.

Our sun, one of that number, is insignificantly placed away from the centre. The whole galaxy is probably quite similar to the Andromeda galaxy—also a nearby radio source, but still over two million light years away.

Other very interesting and mysterious radio sources exist in the sky which emit radio signals by different methods. These include the radio galaxies and the intriguing quasars and pulsars.

Quasi-stellar objects or quasars for short are certain, very small, star-like objects which emit incredible amounts of radio and optical energy. Evidence from the latter tends to suggest that they are enormously distant, but until the true distance is actually ascertained, quasars will continue to be a central problem in astronomy. The radio telescope at Jodrell Bank has played an important part in the discovery of the quasars.

Another of the amazing phenomena that have been discovered by the science of radio astronomy in the past ten years are the pulsating radio sources or pulsars. As their name suggests they emit bursts of radio and sometimes, light-energy. Perhaps the most famous example of a pulsar is that in the Crab Nebula.

This is a glowing cloud of gas which is thought to contain an incredibly dense neutron star. The latter could give rise to the radio pulses as a consequence of its spin. Although its origination is unclear, astrophysicists believe that the Nebula and the neutron star are remnants of a star which just blew itself up in a gigantic explosion or supernova which was observed by Chinese astronomers in 1004 A.D.

In this field, too, Jodrell Bank has made a very significant contribution by discovering many new pulsars.

## **RADIO ASTRONOMY AND OUR UNIVERSE**

The aim of radio astronomy is to discover by its singular techniques more about the universe—its formation, evolution and end, if any, and its true nature. These are some of the most

important questions of all. A great advantage with observational astronomy in general is that not only vast gulfs of space but also of time, can be surpassed.

This is because even light and radio waves, the messengers of the events which we observe in the sky, can take an enormous time to cross the distances involved. Thus, the farther we can probe into space, the farther we also probe back in time, perhaps even towards the possible creation of the universe. This is why the nature of distant galaxies and quasars is of great importance to the astronomer.

Radio astronomy is helping scientists to decide between the various theories of the creation of the universe. These include the widely held

"big bang theory" that suggests that at one time in the distant past all the matter in the universe was concentrated at one point before being scattered by a colossal explosion. Another theory, that of the "steady state" considers the matter in the universe to be continuously created as the universe expands.

In radio astronomy's brief life of 40 years almost paralleled by the development of Jodrell Bank, many questions have been answered, but many more have been unearthed. However, in the future, as in the past, we can be sure that Jodrell Bank will number among those prominent establishments providing the knowledge so necessary to mankind's understanding of the universe. □



### Circuit Supply

Please would you tell me how it is possible to vary the current of a circuit whilst keeping the supply voltage constant?

For a fixed supply voltage circuit current is set by the total circuit resistance. In the simplest case this would comprise a set of resistors in series. The only way of altering the current is to alter the value of one or more of the resistors. In a more complicated case the current in question might be the collector or emitter current of a transistor and in this instance the circuit current can be controlled via the transistor's base current.

### Loudspeaker Connection

Could you tell me how to connect two 60 watt loudspeakers together to give a total power rating that will handle 100 watts.

This is simply done by putting the two loudspeakers either in series or parallel but remember that you must match the output impedance of your amplifier. If your loudspeakers are twice the impedance of your amplifier then connect them in parallel; if they are each half its impedance put them in series. If each of your loudspeakers has the same impedance as your amplifier then you cannot use this simple technique because it is impossible to produce a good match without the use of a transformer.

Remember to keep the phasing correct; when connecting the speakers in parallel connect like terminals together. For series connection, unlike terminals should be linked.

### Preferred Values

Some of your advertisers show resistors categorised as E12 and E24 series. I would be pleased if you could explain what this means.

As you must be aware, resistors are supplied with preferred values. There are 12 different values within a decade of  $\pm 10$  per cent tolerance resistors. These

are 1.0, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and multiples of ten on these values. The values have been carefully selected so that the upper 10 per cent tolerance of the lower value approximately equals the lower 10 per cent tolerance of the next higher value—this is how the rather strange selection of values comes about. This is called the E12 series of values.

There is a similar series for  $\pm 5$  per cent tolerance devices—called E24—and there are twenty-four different values within a decade as follows: 1.0, 1.1, 1.2, 1.3, 1.5, 1.6, 1.8, 2.0, 2.2, 2.4, 2.7, 3.0, 3.3, 3.6, 3.9, 4.3, 4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1. Note that the same tolerance law applies except that now it is  $\pm 5$  per cent.

## PRACTICAL ELECTRONICS

Take the Broad View,

Read PRACTICAL ELECTRONICS

High-Power Amplifiers, a Random Light Display, a Car System Monitor, and the start of the Rondo System F.M. Tuner—All there in the July Practical Electronics. On Sale Now.

Look forward to—

A High Impedance Voltmeter with lots of Scientific applications, an Underwater Colour Temperature Meter for the photographer, amplifier Power Modules for up to 100W for the Audiophile, and the final steps in The Rondo F.M. Tuner—In the August issue, On Sale July 12.

# SEMICONDUCTOR PRIMER

By A. P. STEPHENSON

## 16 ■ TESTING TRANSISTORS

The instruments available for testing transistors, and how an AVO can be used both for testing and sorting out *pnp* from *npn* types.

Various transistor-test sets are manufactured, some quite simple, others bristling with knobs, dials and switches and capable of measurements on almost any transistor.

For transistor manufacturers they are no doubt very useful for testing  $h_{fe}$ ,  $h_{oe}$ ,  $h_{re}$ ,  $h_{ie}$ , noise,  $f_T$  etc. For the small workshop, the capital investment in one of these spectacular instruments is seldom justified.

By the time the voluminous instruction manuals are studied, the various knobs twiddled, the dial readings laboriously checked, the poor technician is mentally exhausted and too weak to insert the transistor.

In most cases, it is only required to find out if a suspect transistor is working at all, or definitely unserviceable. An AVO meter (on resistance range) is quite adequate. Three tests are required.

(a) Resistance between base and emitter

should be *LOW* with leads one way round but *HIGH* the other way. The difference should be at least 10:1.

(b) As (a) above but between base and collector.

(c) A test across emitter and collector should be *HIGH* either way round. The actual reading in ohms will vary widely between serviceable transistors even of the same type and there is little point in attempting figures—it is only the *ratio* which is important. (Note: it is unwise to use the very high ohms range in case the highest battery voltage causes damage).

Unknown transistors can be sorted into *pnp* or *npn* by this method.

Put RED lead of AVO to base and BLACK lead to emitter. If reading is low ohms, the transistor is *pnp*. (This appears to contradict normal *pn* junction theory until it is remembered that an AVO on ohms range is delivering a small *negative* voltage from its RED lead and a *positive* voltage from its BLACK lead).

## 17 ■ VARIOUS BIASING METHODS

The simple diagrams of Fig. 17.1 (a-e) illustrate the various methods of setting the d.c. bias conditions in a class A amplifier operating in the common-emitter mode.

- Simple, economical on current, but gain sensitive to  $h_{FE}$  production spreads, temperature and supply voltage, seldom used.
- The inclusion of the emitter resistor  $R_E$  helps to reduce the sensitivity of the stage to temperature, supply voltage and  $h_{FE}$  spreads. Also, the input impedance is higher due to the series negative feedback across  $R_E$ . Unfortunately, the gain is lowered as well as the output swing.
- Instead of an emitter resistor a direct voltage negative feedback action is provided by  $R_F$ . Has a similar effect on reducing sensitivity as well as the gain. Also the amount of feedback is fixed by the bias required on base. Output swing not affected.
- Has all the advantages of (b) but the potential divider  $R_1, R_2$  provides a much steadier base bias. Unfortunately the extra resistor  $R_2$  provides an additional load across the signal. However, this circuit is the most widely used in general amplifier design.
- Similar to (d) but the emitter as well as the base, is fed by a potential divider. The extra stability of this circuit must be paid for in extra current drain through  $R_3, R_4$ .

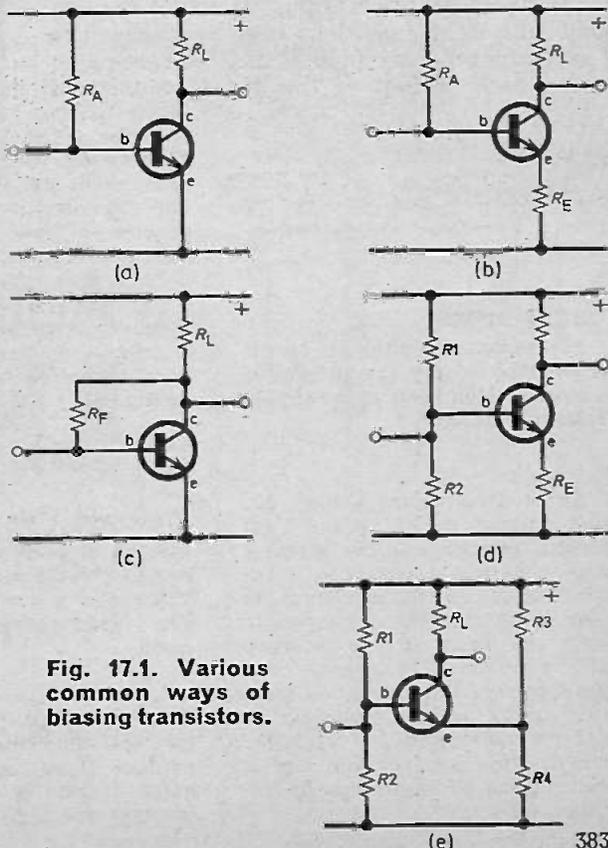


Fig. 17.1. Various common ways of biasing transistors.

**T**HANKS to the selection of semiconductors, such as relatively cheap triacs and high-tension transistors which are at present on the market, it is possible to design a simple device to automatically control light level in household or similar uses.

With regard to the fact that there are a large number of non-fluorescent light sources in use, this light controlled device was designed to control a luminous intensity over a very wide range and at the same time automatically hold a pre-set light level.

### DESIGN CONSIDERATIONS

As the only practical solution, without visible flickering effect, a phase shift system was chosen although this system is known to have some disadvantages, such as the necessity for interference suppression circuitry and the deformation of the supply waveform. These disadvantages are caused by the fast triac switching.

The circuit described is not expected to be connected to the mains in large quantities where consumption exceeds 200 watts. Due to the large number of light dimmer units using the same principle and working satisfactorily it was not necessary to develop a new control principle.

Light dimmers at present on the market are characterized by manual adjustment of required light level only. These dimmers are without any automatic readjustment of luminous intensity of the light source according to actual requirement (the light conditions may be changed in a very short period such as in the evening or during dark periods of the day in connection

with weather changes). In such cases normal circuits require readjustment of light level or the user must be satisfied with an unsuitable light level.

In some cases it would be desirable to switch some of the lights in the house on whilst the house is unoccupied. To fulfil this condition the light must be switched on when leaving the house. In the case of the controller to be described a constant level of light will be automatically kept.

### ADJUSTMENT


In manually controlled dimmers the adjustment of a very low light level becomes critical and from a certain point practically impossible due to instability of the mains voltage and the inaccuracy of triac switching circuits.

Another disadvantage of manually controlled dimmers is the use of potentiometers for control of the phase-switching triac circuit. These potentiometers, which are in some designs loaded with high currents, are the reason for many faults and instability after a certain time of use.

To avoid the disadvantages of presently manufactured dimmers the described device was designed, this unit solves these problems for an

FOR  
GUIDANCE  
ONLY

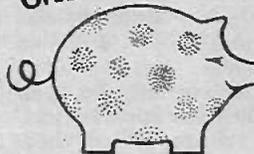**ESTIMATED COST\***  
OF COMPONENTS  
including V.A.T.



**£4.00**

**excluding case**

\*Based on prices prevailing at  
time of going to press

# Automatic Light Level Controller

By M. DVORAK

**A dimmer unit with the ability to automatically keep a pre-set light level.**



In some cases after a sudden change of light level a sort of damped oscillation can be observed on the luminous intensity of the controlled light source. This effect is caused by the imperfection of the low frequency filter and lasts about one second. It does not visibly affect normal conditions of the dimmer unit in use.

The 25 $\mu$ F capacitor C4 is across a low voltage and a 12V type is quite sufficient for this purpose. Resistor R2 (9.1 megohm) is not always available and it may be necessary to use two resistors of 4.7 megohms connected in series. The transistors TR1 and TR2 should be 300V types of low collector dissipation, the most suitable transistor is the D40N3 designed for power line connection. If this is not available a BF259 can be used.

### REFERENCE LIGHT SOURCE

The light level is controlled by an iris in front of the photocell a substitute light source (neon LP2) in front of the photoresistor is necessary because with the iris fully open it would not be possible to set a completely dark level. The internal light source serves as a commanding light during the period in which the main light is turned fully off.

Without the use of this arrangement it is not possible to set up an extremely low light level which could be dependent on the sensitivity of the unit and its distance from the light. So that this arrangement cannot reduce the light sensitivity of the unit, by adding a constant light level, the signal lamp must be placed in such a way that it will not effect the photoresistor until the iris is almost fully opened and the controlled light is dimmed.

This neon is connected across the d.c. side of the bridge-rectifier; if the lamp is fully dimmed the voltage across the neon is high and the neon lights to its maximum. If the lamp is half on the neon lamp is automatically turned off in consequence of a high voltage drop across the dimmer. This function fully corresponds to the requirements of the light reference.

It is necessary to position the signal neon with regard to the photoresistor and iris in such a way that the unit suits all requirements of light regulation and at the same time would allow the unit to switch off the light source by means of the iris.

### R.F. FILTER

Interference caused by the unit appears mostly on wireless frequencies because of switching of high current by the triac in the controlled light circuit. To suppress this interference the unit employs an r.f. filter, formed by L1, L2, C1 and R1.

In the prototype unit the suppression coils used (L1, L2) were readily available ready-wound TV type chokes capable of passing two amperes. The capacitor C1, 0.1 $\mu$ F must be 400V

a.c. working and resistor R1 (22 ohms) is used to limit the voltage peaks due to discharging of the capacitor when the triac switches, at the same time it suppresses any oscillation in the filter circuit.

The filter, made as described was used and tested on the prototype and interference frequencies higher than 100kHz were reliably suppressed. On medium and short wave radio bands virtually no interference appeared. The disadvantage of this filter is a low load capacity but a lamp load of up to 200W may be applied—more than adequate for most situations.

### CONSTRUCTION

The complete unit can be housed inside any suitable case—it is a good idea to use a plastic case to provide good insulation but a metal case can be used provided the case is connected to the mains earth via three-core lead and plug fused at one amp.

Commence construction by cutting a length of tagboard to size and wiring up the components as shown in Fig. 4. The wires to LP2 should be about 150mm long so that LP2 can be positioned correctly as described earlier, LP2 is glued to the lid of the unit when finally positioned.

When mounting PCC1 it must be positioned slightly above all the other components on the board with its front on the same plane as the tagboard.

The wiring to the mains should be normal twin flex or—if a metal case is used—three-core wire.

## Components . . . .

### Resistors

R1 22 $\Omega$	R4 200k $\Omega$
R2 33k $\Omega$	R5 1.5k $\Omega$
R3 9.1M $\Omega$	R6 1.5M $\Omega$
All $\pm 5\%$ $\frac{1}{4}$ W carbon	

SEE

**SHOP  
TALK**

### Capacitors

C1 0.1 $\mu$ F 400V a.c. metalized paper
C2 0.01 $\mu$ F 250V metalized paper
C3 0.01 $\mu$ F 250V metalized paper
C4 25 $\mu$ F elect. 12V

### Semiconductors

D1-D4 400V 0.5A bridge rectifier
CSR1 40486 triac or any 400V 2A triac
TR1 D40N3 or BF259 silicon npn
TR2 D40N3 or BF259 silicon npn

### Miscellaneous

LP1,2 neon lamps 80V type—no series resistor (2 off)
L1,2 2 amp chokes type TV2 (2 off)
PCC1 ORP12 light dependent resistor.
11 way double sided tagboard, stand off spacers, 4BA fixings, wide based insulated knob, 6mm diameter bolt with nut, aluminium for iris, felt to shade PCC1, case (size depends on tagboard used), wire.



Having completed the tagboard it should be placed in the case and mounted so that it is insulated, using stand off spacers and nylon bolts. With the board mounted the position of PCC1 should be marked on the lid and a hole cut as shown in Fig. 5.

## IRIS

The iris is constructed from 22 s.w.g. aluminium with two bends, as shown in Fig. 5, so that the neon LP1 is covered by one side of it. It is important that the leads to the neon are completely insulated so that they cannot touch the iris or case (if metal) and also that the control knob used is an insulated type with a sunken grub screw attachment.

The iris must be made the correct width so that it covers the whole of the aperture plus LP2 and also touches the side of the case nearest PCC1. This prevents the iris from twisting around since it is only fixed to the lid by the slider control, fixed to the spindle passing through the slot cut in the lid.

Actual dimensions of the iris and cutouts in the lid will depend on the case used and the position of PCC1 inside the case. The aperture hole must be covered with cellophane or a piece of Perspex can be glued into it. Finally a piece of felt or other thick material should be glued around the outside of PCC1 to provide shading when the iris is closed.

## INSTALLATION

The unit can replace the light switch for a single room but its fixing position will not necessarily be where the light switch was previously situated. It is essential to take into account some principles which result from the function of devices of this sort. The following analysis shows which principles are to be dealt with.

(1) Placing the dimmer unit very close to the light source a very strong negative feedback will come into effect, the iris will be usually fully closed and the whole device will become insensitive to other sources of lighting, such as the daylight and its changes. In this case it is easy to adjust a very low level of light, in consequence of the optical feedback which operates as a stabilizing factor.

(2) Another extreme will come into effect when the dimmer unit is placed in a position where it is strongly influenced by other light sources. In this case any insignificant change of the outside light will cause a strong alteration in the controlled light source. During dark periods the dimmer unit will try to work to its full capacity and it will be much more difficult to adjust a low level of light because the stabilizing effect of the feedback will not operate sufficiently.

It is not practical to install the dimmer unit in a place where the photoresistor could be shaded

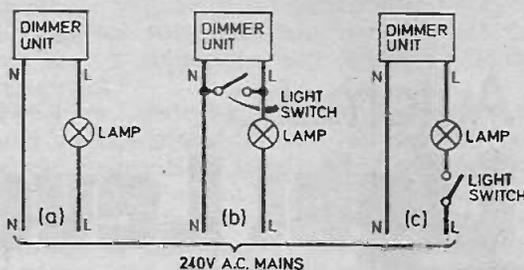


Fig. 6. Methods of connecting the unit to the supply and load (a) no mains switch (b) in parallel with switch (c) in series with switch.

by any movement in the room. Because PCC1 is very sensitive it would be affected by such changes and the intensity of operated light source would change as a result. A similar effect will take place where the dimmer unit is used for operating the light level in shop windows, when the unit is facing outside light. In this case for instance cars passing-by would cause a change of the light intensity if their lights were directed onto the shop window.

The dimmer is very useful for operating the light intensity level when table lamps are used. In this case the unit automatically levels the light during dark periods of the day. It is not suitable for use with fluorescent lights.


## CONNECTION

The unit can be connected to the light source in one of three different ways, in Fig. 6a the unit is connected without a mains switch, the light source is operated by the dimmer iris only, this includes switching fully on and fully off.

It is possible to leave the automatic regulation to the dimmer, and in case of immediate necessity to switch the light fully on the light switch can be wired in parallel with the unit (Fig. 6b). In this case a constant light level can be set up by the iris and the lamp can be turned fully on if required by the switch.

In Fig. 6c the dimmer unit is connected in series with the mains switch this results in complete disconnecting of the light source by the switch with automatic regulation of the light level being controlled by the dimmer unit. It is also possible to achieve a complete switching off by means of adjusting the iris to its end position.

The functional model was tested in various conditions for 7 months without any faults whatsoever and no interference of radio reception was noticed. As no potentiometer is used in the dimmer unit, a longer life is expected in comparison with the dimmers which are at present on the market. The neon LP2 can provide a small amount of external light, so that the knob can easily be found in the dark (this will not be the case if the circuit of Fig. 6c is used and the switch used to turn off the lamp). □

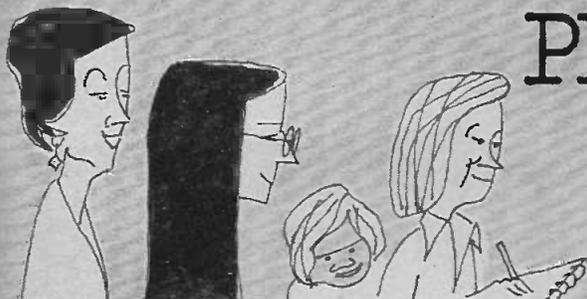

# Physics is FUN!

By Derrick DAINES



**T**HIS is the series for you—and you—and YOU. No matter if you are the most complete beginner or if you already know quite a lot, you will get something out of this series.

We are going to describe simple and practical experiments in a language that all can understand. These experiments will enable you to discover for yourself the fundamental laws of physics that govern our hobby and give rise to the often bewildering tricks that we get up to in designing circuits. This is in fact the BASIC basic series!

If we are ever to get a start in electronics, we must accept, various laws, but later we run into difficulties because we do not fully understand the reason for those laws. However, here we present you with a series of experiments designed especially to give you the most basic understanding possible; an understanding that will stand you in good stead in future years.

Please do carry out the experiments. Seeing and doing will fix facts in your mind far more effectively than just reading. Besides, it is more fun, and these experiments should give you plenty of that.

Finally, keep a little notebook. It doesn't matter what sort, nor how you keep it—what IS important is that after you have finished experimenting and just before you turn to something else, you jot down in your own words what the experiment has taught you. Again, this will help to fix it in your mind and later, when you browse through your notebook, the experiments will come alive again.

## THE MAGNETIC FIELD

Take a magnet—any magnet; bar, horseshoe, pot, anything. (Many fine magnets are to be had for the asking from car-breakers' yards or out of old TV sets). Sprinkle a few pins on the table and slowly lower the magnet towards them. Notice that the magnet does not have to actually touch the pins, but that when the magnet is some distance away, the pins leap up to cling to the magnet. "So what?" you say. So this—we are so familiar with this extraordinary event that we don't stop to think about it.

**Magnetism stretches out  
into space**

Silently, invisibly, magnetism reaches out to grab the pins. Isn't it odd that little old ladies who are uneasy at the very idea of silent, invisible electricity, will use a magnet to pick up pins?

If magnetism stretches out into space, there ought to be a way in which we can map it—find out what shape it is and how far it goes. Well, there is a way. Put your magnet firmly on the table and place a sheet of cartridge paper over the top. Now you need some iron-filings. You can buy these, but it's cheaper to drag your magnet round underneath a bench. Or why not actually file a piece of iron?!!

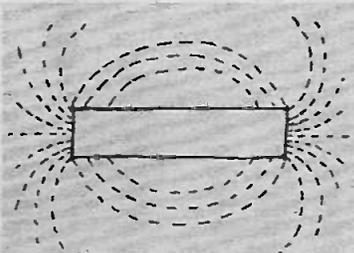


Fig. 1: Iron filing pattern obtained with a bar magnet.

Sprinkle the filings evenly over the paper and tap the paper very gently. The filings will arrange themselves into a pattern conforming to the shape of the magnet field. The actual shape of this pattern will depend upon what sort of a magnet you have. If it is a bar magnet, the shape will be as in Fig. 1. If a horseshoe, as in Fig. 2. (Pot magnets and ring magnets are not really suit-

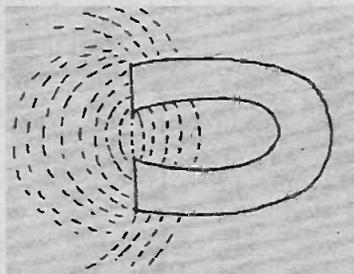


Fig. 2. A Horseshoe magnet will produce this filing arrangement.

able for this experiment.) If you tap too hard or too long, the filings will travel across the paper to cluster over two areas of the magnet—but only two.

**The centre of the magnet  
does not attract the filings**

We say that the magnetic field (and the magnet) is polarised—that is, they have a North pole and a South pole. Strictly speaking, we should call them North-seeking and South-seeking, as the next experiment shows.

If you have a bar-magnet, hang it up by a fine thread. After swinging about for some time, the magnet will eventually settle down in a North/South orientation. Mark one end with a piece of chalk and swing the magnet again. However many times you do it, the marked end will always finish up pointing in the same direction. This of course is what a compass does. Again—so what?

Well, ask yourself this question—you know that the compass points North/South, but is this because the Earth is attracting the compass, or because the compass is attracting the Earth? In other words, in the compass/Earth relationship, is one of the pair active and the other passive? If so, which?

**Answer next month.**

# General Purpose 5 Watt AMPLIFIER

By Tom Mason

For use with electric musical instruments, record player, radio and tape deck.



**A**N AMPLIFIER is probably one of the most popular projects for the amateur electronics constructor for it can find many applications both in the home and as a test amplifier on the work bench.

The General Purpose 5 Watt Amplifier described here can be used to amplify the signals from record players fitted with ceramic or crystal cartridges, radio tuners, tape decks, musical instruments such as electric guitar and organ, microphones, and in the workshop for testing prototypes requiring an amplification stage.

The quality is not claimed to be up to hi fi standard, but nevertheless is good enough to be acceptable to most listeners; maximum available output power is 5W r.m.s.

## SEPARATE UNITS

The complete amplifier as shown in Fig. 2 uses three integrated circuits, IC1, IC2 and IC3 and can be split into two distinct sections: (1) the battery powered preamplifier and tone controls, consisting of operational amplifiers IC1, IC2 and local components, and (2) the mains powered power amplifier IC3.

If desired, the two sections can be built and used independently of each other; some constructors may not wish to include the tone control and preamplifier stages into their amplifier in which case these should be omitted and input fed directly to capacitor C5.

The sensitivity of the main amplifier is 80mV for full output into a 16 ohm load, and this is suitable for most of the audio devices listed above, but for those with a lower signal output, down to 5mV, maximum output will only be obtained with a suitable preamplifier stage.

## OPERATIONAL AMPLIFIERS

The preamplifier and tone control stages each use differential operational amplifiers type 741;


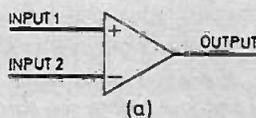
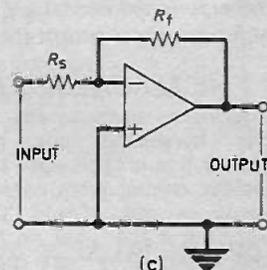


Fig. 1. Feedback arrangements for differential operational amplifiers.

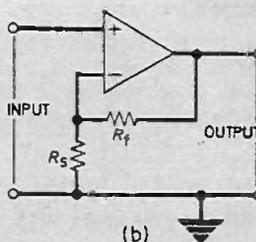


these are two-input devices, one inverting (-) and one non-inverting (+) and are symbolised as shown in Fig. 1a. The output voltage of these devices is proportional to the difference in voltage between the two inputs.

In audio work they can be used in two basic modes as shown in Figs. 1b and c. The gain of the system is controlled by the choice of feedback resistor  $R_f$  and source resistor  $R_s$ , both external components, and it can be shown that for Fig. 1b.

$$\text{gain} = \frac{\text{output voltage}}{\text{input voltage}} = \frac{R_f + R_s}{R_s}$$

$$\text{and Fig. 1c, gain} = \frac{R_f}{R_s}$$

FOR  
GUIDANCE  
ONLY

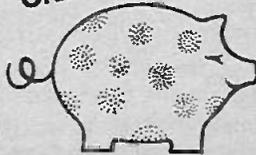

**ESTIMATED COST\***  
OF COMPONENTS  
including V.A.T.

**£8.00**  
excluding case  
and loudspeaker

\*Based on prices prevailing at  
time of going to press

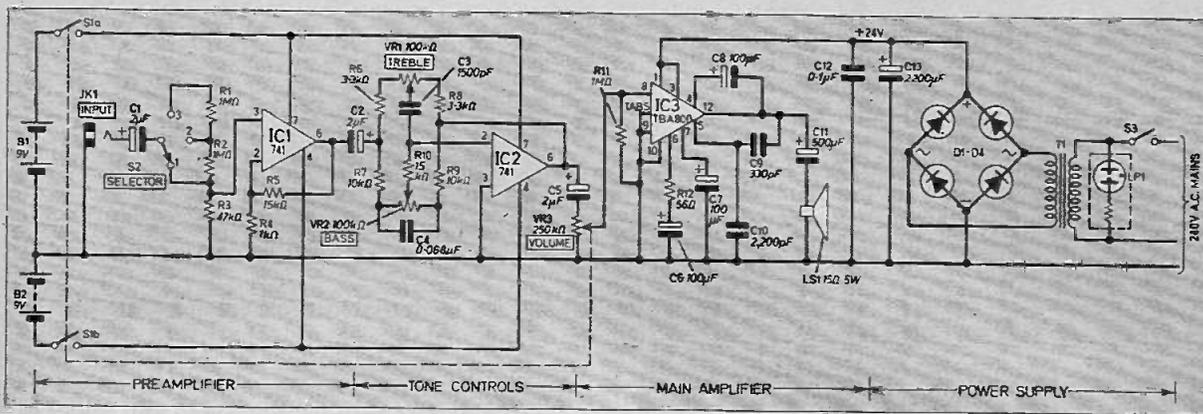


Fig. 2. The complete circuit diagram of the General Purpose 5W Amplifier.

### CIRCUIT DESCRIPTION

The complete circuit diagram of the General Purpose 5 Watt Amplifier is shown in Fig. 2. The main amplifier i.c. TBA800 can be powered by a supply in the range 5 to 30 volts (depending on load) and can be terminated in an 8 to 16 ohm loudspeaker to give output powers up to 5W r.m.s. (with suitable heatsink).

It was decided to use a 15 ohm loudspeaker (since this is more readily available than a 16 ohm one) to obtain 5 watts. This necessitates a 24 volt supply, which in the prototype is mains derived via T1 which steps down the mains voltage to approximately 17V; diode bridge D1-D4 gives full-wave rectification and the output from the bridge is smoothed by capacitor C13 to give a 24V (approx.) supply to pins 1 and 3 of IC3.

The prototype used a mains transformer with a secondary rated at 16V 1A. Any similarly rated transformer will do; current consumption at maximum output is about 600mA.

Input to IC3 is at pin 8 from the wiper of potentiometer VR3 (volume control) which is connected across the output of IC2. The output is a.c. coupled to the loudspeaker by capacitor C11.

Other circuit components around IC3 should be evident to readers from the pin identification drawing of Fig. 3.

### PREAMPLIFIER

Input to the preamplifier is via d.c. blocking capacitor C1 and selector switch S2, the position

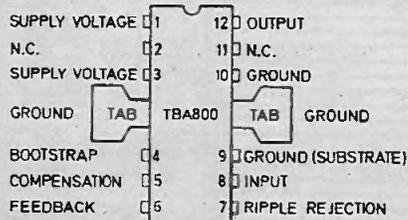


Fig. 3. Pin identification for the TBA800.

of the latter being chosen to suit the amplitude of the input signal.

The resistor chain, R1, R2 and R3 form an attenuator network, the voltage appearing across R3 being applied to IC1 input (pin 3). The value of these resistors has been calculated such that (1) 5mV at position 1 (2) 100mV at position 2 (3) 200mV at position 3 causes 5mV to be present at the input to IC1 which is connected in the mode of Fig. 1b. Thus the gain of the first stage is approximately 16.

### TONE CONTROLS

Output from IC1 is fed to the tone control circuitry, IC2 and local components, via C2.

The tone control employed is a Baxandall-type network that gives both boost and cut of treble and bass. Inspection of Fig. 2 will show that IC2 is connected in the mode of Fig. 1c, but since capacitors are now in circuit, the "resistances" equivalent to  $R_t$  and  $R_b$  are now frequency

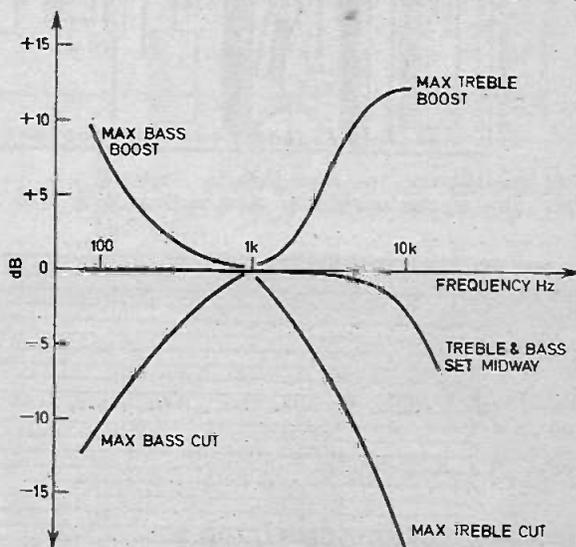


Fig. 4. Performance graphs for the tone control stage.

dependent i.e. they are impedances.


When VR1 and VR2 are set to their midway positions, the gain of this stage is unity for all frequencies; also, the gain for a frequency of 1kHz is unity for all settings of the tone controls (within component tolerances). All other frequencies are boosted or cut as the controls are rotated. This is standard practice. The performance of the tone controls is shown graphically in Fig. 4.

### MAIN AMPLIFIER BOARD

The main amplifier is constructed on a piece of 0.1in. matrix Veroboard size 58 holes by 24 strips. The layout of the components on the top side of the board and the breaks along the copper strips on the underside are shown in Fig. 5.

Begin by making all the cut-outs and drilling the fixing holes and then with the exception of IC3, position and solder the components and link wires to the board as shown in Fig. 5.

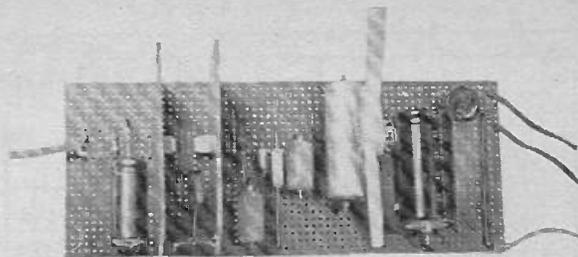The heatsinks for IC3 are made from two pieces of copper clad board size 65mm x 50mm




Completed main amplifier board.

which are soldered to the heatsink tabs on the i.c. These tabs should be very carefully straightened using a pair of pliers and then about 4mm of each end bent up vertically.

The i.c. should then be positioned and soldered to the board paying attention to polarity (pin 1 is marked on the body of the i.c.). The two heatsink boards should now be soldered to the tabs so that they rest on the component board and stand vertical. Now connect the link wire between ground and heatsink.

The flying leads to the loudspeaker should now be soldered in position. In the prototype, 200mm of twin-cored mains cable was used.

Fig. 5. Layout details for the main amplifier board.

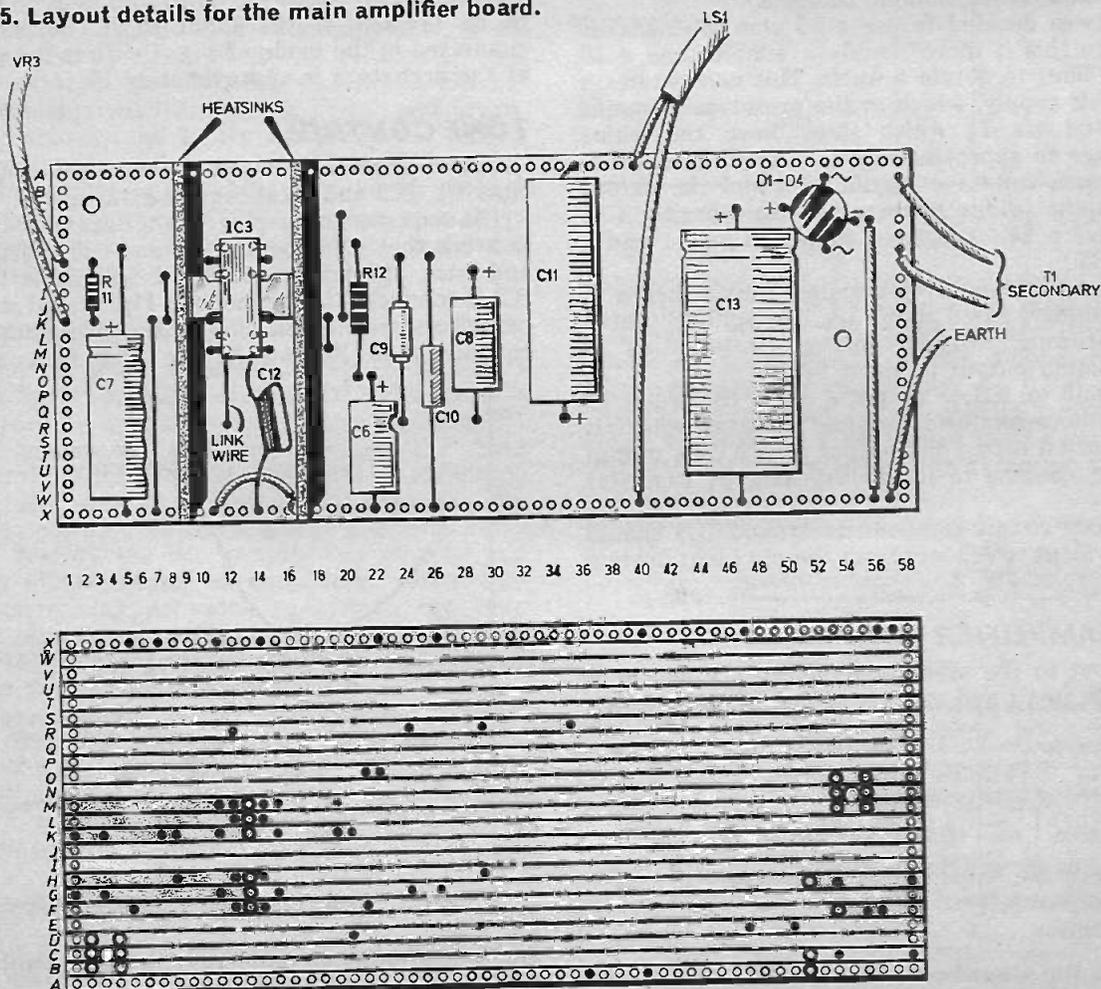


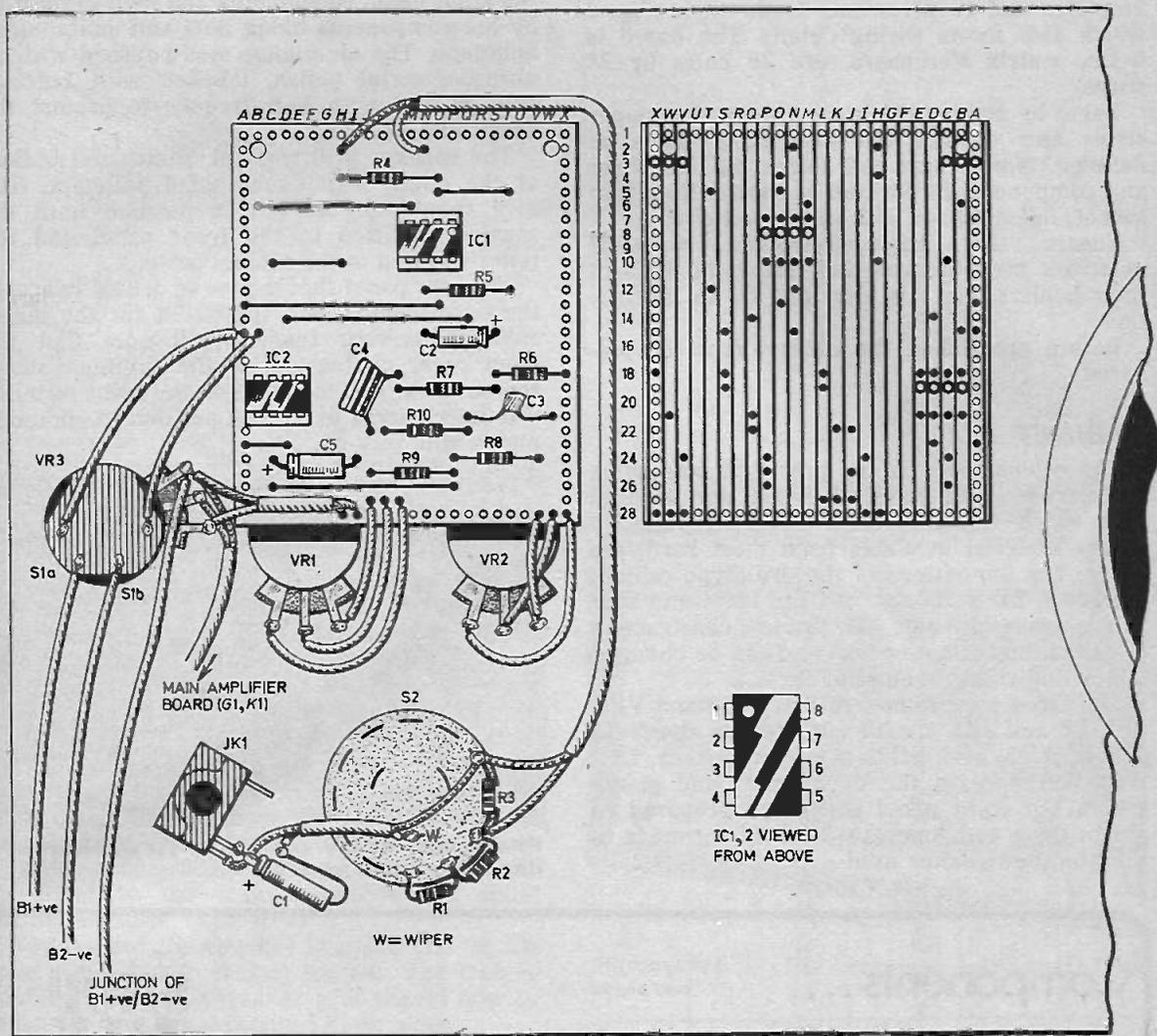


Fig. 6. The layout of the components on the preamplifier board and wiring up details.

Below: photograph of completed unit showing new position of mains neon indicator.

# General Purpose 5 Watt AMPLIFIER

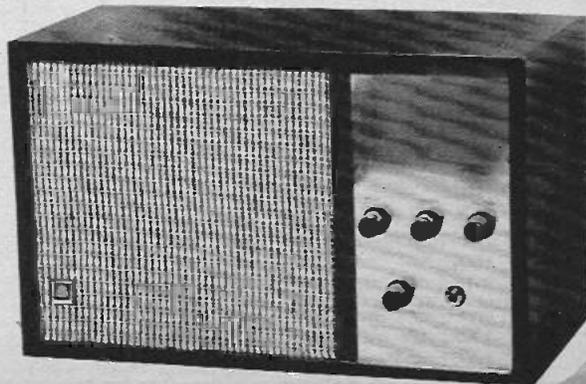

## PREAMPLIFIER BOARD

The layout of the components for the pre-amplifier and tone controls is shown in Fig. 6 which also shows wiring details. The board is 0.1in. matrix Veroboard size 28 holes by 24 strips.

Begin by making the breaks along the copper strips and drilling the two fixing holes as detailed. Next insert and solder all link wires and components in position as shown. Note that sockets are used for both integrated circuits.

Ensure that the electrolytic capacitor polarities are observed and insert the i.c.'s in their holders, pin 1 is identified by an indentation.

Before proceeding the cabinet must be prepared.

## CABINET


The cabinet used in the prototype was home made from 12mm thick chipboard and covered with black Contact which is a self-adhesive plastic material available from most hardware shops. The dimensions of the prototype cabinet are 380 x 230 x 200mm and the front and rear panels are removeable. The size and construction of the cabinet is not critical and can be changed to suit individual requirements.

The three potentiometers VR1, VR2 and VR3, LP1, S2 and JK1 are all mounted on the front panel which also holds the loudspeaker LS1. With reference to the illustrations and photograph, the front panel should be prepared to accept these components with a cut-out made to suit the loudspeaker used.

In the prototype a fascia was made from a thin sheet of aluminium which is drilled to suit the front panel components and held in position by the components fixing nuts and double-sided Sellotape. The aluminium was polished with an abrasive metal polish, labelled with Letraset and sprayed with hair lacquer to protect the sheen and lettering.

The speaker grill was cut to size and backed at the edges with double-sided Sellotape. The grill should not be put in position until the speaker is fitted to the front panel and the latter screwed to the cabinet battens.

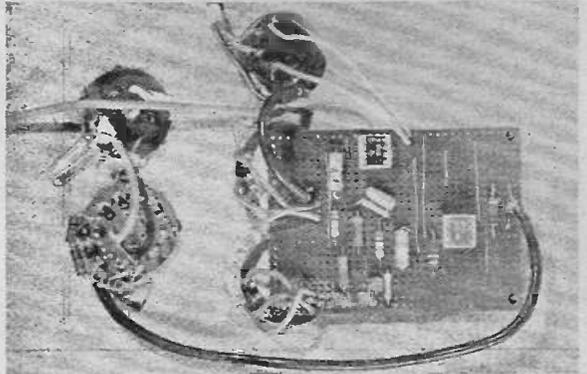The rear panel should now be drilled to accept the on/off switch and the outlet for the mains cable. Observant readers will note that the front cover photograph of the amplifier shows the on/off switch mounted on the front panel. It was later moved to its new position to eliminate mains hum pick-up.



Photograph of the completed preamplifier section mounted in position.

## Components . . . .

### Resistors

R1 1M $\Omega$	R5 15k $\Omega$	R9 10k $\Omega$
R2 1M $\Omega$	R6 3-3k $\Omega$	R10 15k $\Omega$
R3 47k $\Omega$	R7 10k $\Omega$	R11 1M $\Omega$
R4 1k $\Omega$	R8 3-3k $\Omega$	R12 56 $\Omega$

All  $\frac{1}{4}$ W  $\pm$  10% carbon

### Potentiometers

VR1 100k $\Omega$ lin. carbon
VR2 100k $\Omega$ lin. carbon
VR3 250k $\Omega$ log. carbon with ganged d.p.d.t. switch

### Capacitors

C1 2 $\mu$ F 10V elect.	C8 100 $\mu$ F 15V elect.
C2 2 $\mu$ F 10V elect.	C9 330pF
C3 1500pF	C10 2200pF
C4 0.068 $\mu$ F	C11 500 $\mu$ F 15V elect.
C5 2 $\mu$ F 10V elect.	C12 0.1 $\mu$ F
C6 100 $\mu$ F 6V elect.	C13 2200 $\mu$ F 25V elect.
C7 100 $\mu$ F 25V elect.	

### Integrated Circuits

IC1, 2	741 differential operational amplifier, 8-pin d.i.l. (2 off)
IC3	TBA800 5W audio amplifier

### Miscellaneous

D1-D4	$\frac{1}{2}$ A 50 p.i.v. type 96AA or similar
S1	d.p.d.t.—see VR3
S2	1-pole 3-way wafer
S3	mains on/off toggle
LP1	mains neon with built-in resistor
JK1	standard jack socket
T1	mains/17V 1A secondary—see text
LS1	15 $\Omega$ 5 watts
B1, B2	9V PP3 (2 off)
0.1in. matrix Veroboard:	58 x 24 strips (main amplifier), 28 holes x 24 strips (preamplifier); 8-pin d.i.l. sockets (2 off); copper clad board—p.c.b.—for heatsinks; screened lead; knobs (4 off); small wood screws for fixing boards; length of three-core mains lead; materials for cabinet.

SEE  
**SHOP  
TALK**

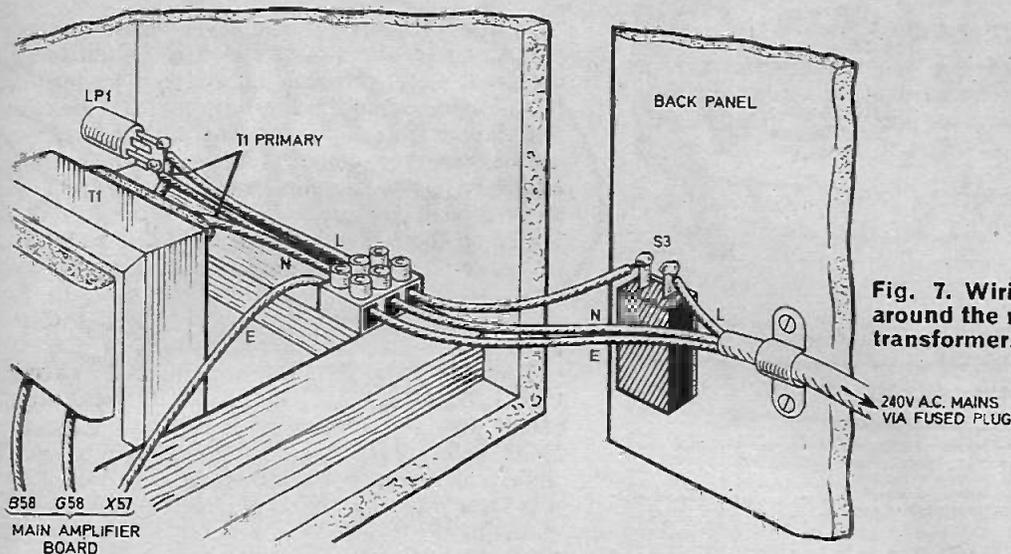


Fig. 7. Wiring up details around the mains transformer.

## ASSEMBLY

Place all the front panel components in position and wire up to the preamplifier board as shown in Fig. 6; using small wood screws secure the board to a short length of batten on the front panel. Ensure that the board does not touch VR1 and VR2. Screened lead must be used where shown.

Two PP3 9V batteries were found suitable to power the preamplifier and these should be wired up to the switch on VR3 and fixed to the side of the cabinet with a suitable bracket.

Solder about 200mm of screened lead to VR3 for input to the main amplifier and about 150mm of mains cable to LP1.


Now secure the speaker in place and fix the front panel to the cabinet battens. The treated labelled fascia and speaker grill should now be attached. Insert and secure LP1 in place.

Use two woodscrews to hold T1 firmly to the cabinet base and then wire up the primary to S3, LP1 and terminal block as shown in Fig. 7. Connect T1 secondary, the earth lead and screened input lead to the main amplifier board. All that remains is to solder the lead to the speaker and secure the board to the base. Screw on the back cover and the unit is complete.

Connection to the mains should be via a fused plug containing a 500mA fuse.
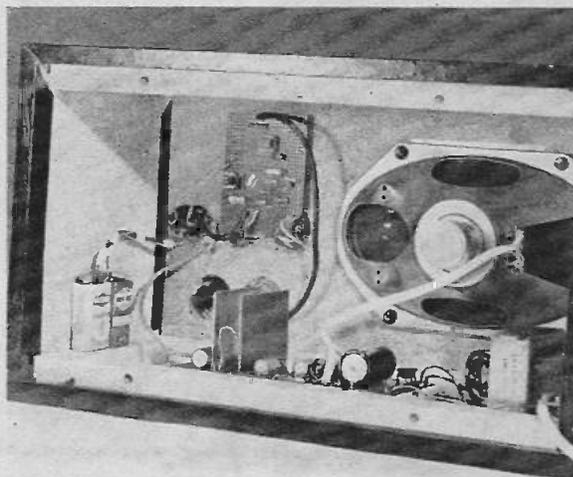
## IN USE

The main amplifier is switched on at S3 located on the rear panel (indicated by the illumination of LP1) and the preamplifier at S1 ganged to VR3 (volume). Input is via a jack socket—which may be changed to suit existing plugs—and should be via screened lead for best results.



Photograph of the prototype with rear panel removed.

## SPECIFICATION

OUTPUT	5 watts r.m.s. into 15 ohms
SENSITIVITY	1. 5mV r.m.s. into 47 kilohms
	2. 100mV r.m.s. into 1 megohm
	3. 200mV r.m.s. into 2 megohms
TONE	Boost Cut
	Bass +9dB -11dB at 100Hz Treble +12dB -20dB at 10kHz
FREQUENCY RESPONSE	Within $\pm 3$ dB from 20Hz to 13kHz

If in doubt as to the amplitude of the input signal set S2 to least sensitive position, (3), and adjust so that volume control gives widest range. For input signals greater than 200mV, the attenuator should be modified to suit. □

The new Oryx 50 is temperature controlled, light, small, easy to handle, rapid heating and high performance. It has a temperature control within  $-2^{\circ}\text{C}$  and adjusted in seconds whilst running to any value between  $200^{\circ}\text{C}$  and  $400^{\circ}\text{C}$ . Long life iron coated tip as standard (11 sizes available).

Oryx De-Soldering Irons—small model SR3A instantly removes solder from printed circuits, etc. accurate, reliable, simple. PTFE nozzle. Larger instrument SR2 gives more suck, less recoil as only piston moves.



De-Soldering Tools  
SR3A £5.06  
SR2 £6.65  
Oryx 50 Iron  
1 at £6.60

Lower prices for quantities



Safety Stand £2.44

Prices Correct May 1974  
Prices include P & P and 10% VAT



Readers' Bright Ideas; any idea that is published will be awarded payment according to its merit. The ideas have not been proved by us.

Since cabinets for loudspeakers on the infinite baffle system must have two main features, i.e. they must be perfectly air tight and they must be made of something which prevents the passage of sound, then I suggest that when cabinets have been made from wood, a coat of rubberised underseal for cars would be a good idea as it would seal any small holes and even the pores of the wood and, as it says on the container, it is a very good sound insulator.

J. Beever,  
Chippenham, Wilts.

I wish to submit, for possible publication in the Bright Ideas column, a design for a simple and inexpensive cordless electric soldering iron.

A miniature insulated three-pin mains plug is fitted to the soldering iron lead, the lead is cut about 2cm away from the point where it leaves the iron, it is then fitted into the plug which is Araldited to the iron, a matching socket is fitted to the bench and connected to the mains. This system relies on the fact that when the iron is hot it will remain hot for a long enough time for one or more joints to be completed.

M. Renshaw,  
Sheffield, Yorks.

An idea which may be of interest to readers concerns the use of nails when trying small circuits: Instead of drilling elaborate boards or using turret board, both of which due to the time and trouble in their making, not to mention the cost, have to be cleaned afterwards for re-use, simply mark the circuit diagram on to a piece of scrap wood, and then tap 10mm long brass brads in at all the junctions and solder the components and wires on to these. I make less mistakes this way, when I'm in a hurry. With the parts removed the board can become firewood once again, or in the case of rough projects for the garage etc. can be made into the back of the box quite easily.

P. Stokes,  
Lowestoft, Suffolk.



### WH-MK spacemiser storage system

Cabinets have stove enamelled steel frames in three heights all of equal width and depth. The frames are strong and rigid, fitted with top and bottom locating pegs and rear slots making stacking, wall or frame mounting positive and simple.

	1 off	4 off
121, 122, 123, 124	£4.07	£3.70
251, 252, 253	£6.16	£5.50
501, 502, 503	£10.67	£9.68
254, 257, 258	£5.83	£5.30
504, 507, 508	£10.01	£9.08

Less for quantities

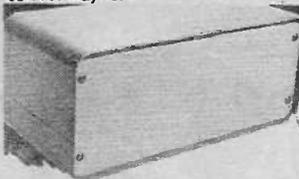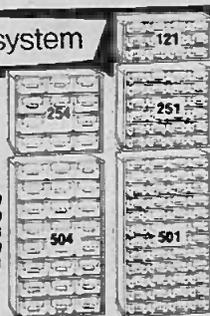All prices include P. & P. and 10% VAT. Prices correct May 1974.



### CONTIL MOD-3

Contil Mod-3 cases are in six sizes and offer the manufacturer of small instruments an attractive low cost case available ex stock. Made in blue PVC coated steel and complete with front and rear panels and chassis. They are light strong and rigid. PCE and PSU mounting systems available.

	Width	Height	Depth
Mod-301	£4.82	7"	3"
Mod-302	£4.22	7"	4 1/2"
Mod-303	£4.78	7"	6"
Mod-304	£4.78	11"	3"
Mod-305	£5.69	11"	4 1/2"
Mod-306	£6.58	11"	6"

Less for quantities. Prices correct May 31. Prices include P & P. 10% VAT feet and screws.




### BRADRAD DRILLING AND DEBURRING TOOL

BRADRAD DRILLING AND DEBURRING TOOL equals eleven drills. One cut drills and deburs the normal run of steels, aluminium, brass, copper and all types of plastics, perspex, fibre glass, etc., and hardboard should the need arise. It is designed to overcome all the problems associated with drilling thin materials—it drills interlocking holes for instance.

$\frac{1}{8}$ "- $\frac{1}{2}$ " in  $\frac{1}{16}$ " steps or 6-36mm in 3mm steps. Both with  $\frac{1}{8}$ " shanks. £10.75. Also  $\frac{1}{4}$ "- $\frac{1}{2}$ " and 36-60 mm. £27.88.

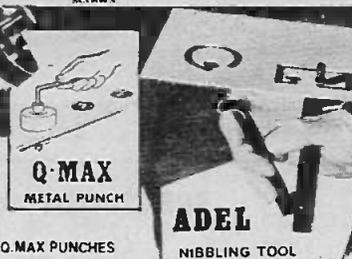All prices include P & P. and 10% VAT. Prices correct May 31.



### Q-MAX METAL PUNCH

### Q-MAX PUNCHES

$\frac{1}{8}$ "	£1.18
$\frac{1}{4}$ "	£1.38
$\frac{3}{8}$ "	£1.47
$\frac{1}{2}$ "	£1.88
$\frac{3}{4}$ "	£2.22

### ADEL NIBBLING TOOL

ADEL The Adels cuts holes of virtually any shape and size starting from a  $\frac{1}{16}$ " hole, cutting cleanly like a punch and die. Ideal for notching clearances on flanges of cabinets or chassis. £8.76.

Available in a range of six sizes in 21 gauge Zintec with blue Acrylic texture. Front panels white Zintec steel or PVC Aluminium

### CONTIL TEXTURED CASES


Width	Depth	Height	No.	Case cost	Extra for alu panel
7"	5"	5"	755	£5.64	24p
8"	6"	7"	867	£6.64	35p
9"	7"	5"	975	£8.64	35p
12"	7"	7"	1277	£7.42	26p
12"	7"	7"	1277	£8.11	—
16"	12"	7"	16127	£10.52	58p
19"	10"	10"	191010	£14.48	unpainted

Less for quantities. Prices include steel panel with feet and screws. P & P. and 10% VAT. Prices correct May 31.

## WEST HYDE

WEST HYDE DEVELOPMENTS LTD, Ryefield Cres. Northwood Hills, Northwood, Middx HA6 1NN. Tel. Northwood 24941/26732. Telex: 923231  
Write or phone for new free catalogue. Prices correct May 31

# NEXT MONTH...

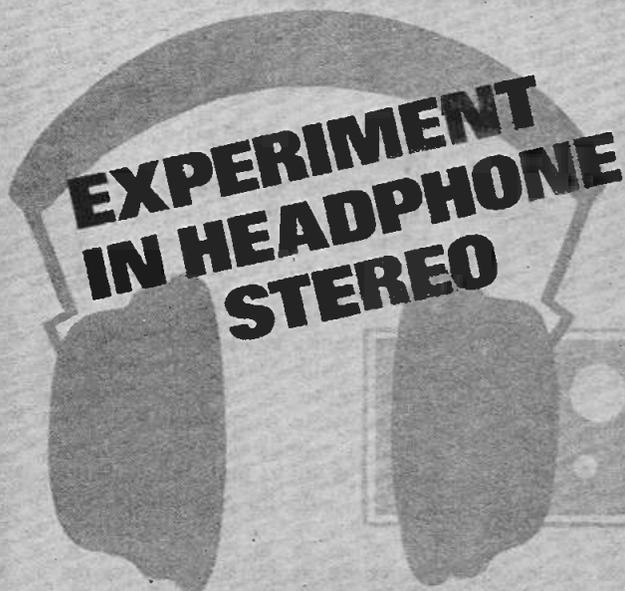

When listening to stereo material through headphones one tends not to get the impression of a continuous sound stage in front of you. This simple experimental circuit sets out to try and overcome this problem, it also provides alternation to give a comparable speaker to phones level, and a balance control.

## RADIATION MONITOR

Consisting of a very simple circuit powered by a small battery, this monitor is portable and can be used for field work or demonstration purposes. Despite the simple circuit the unit is as commercial units using six tubes.

## HEADS OR TAILS

An electronic version of "heads and tails". The unit is inexpensive and employs an integrated circuit for ease of con-




ever  
elect

# FREE ENTRY


# COMPETITION
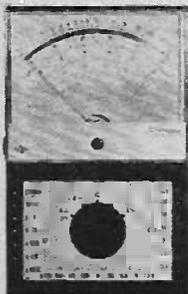
## ... WIN A CHINAGLIA MULTIMETER!

Here is your second and last chance to try for one of these high quality multimeters. Thirteen meters are being presented as prizes in this exciting free competition, open only to Everyday Electronics readers.



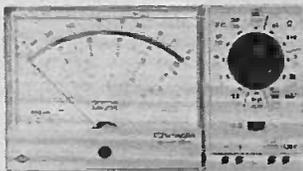First prize, a Chinaglia Dino electronic multimeter which utilises f.e.t.s. to provide a d.c. input impedance of 200k $\Omega$ /V and an a.c. impedance of 20k $\Omega$ /V. This instrument has 33 ranges, all with high accuracy and costs over £28.



Second and third prize, a Chinaglia Minor multimeter with a sensitivity of 20k $\Omega$ /V on d.c. and 4k $\Omega$ /V on a.c. ranges. This instrument is a versatile pocket-sized instrument, having 25 ranges all with high accuracy. It sells for over £13.



Ten runner-up prizes, a Chinaglia Cito pocket multimeter designed specifically to provide a low cost instrument for everyday use. Sensitivity 20k $\Omega$ /V on d.c. ranges and 2k $\Omega$ /V on a.c. ranges. With 24 high accuracy ranges the Cito sells for over £10.

### HOW TO ENTER

Place the eight multimeter features, given below, in what you consider to be their order of importance to the average reader working on typical Everyday Electronics constructional projects.

For example, if you consider that "A.C. current ranges" is the most important of them all, write "C" in the box marked 1st on your entry coupon; the key letter of your choice goes into the second box and so on for all eight.

### IMPORTANT

All entries must be with us by Monday 22nd July 1974—the closing date. Regular readers submitting last month's entry coupon as well, may send both in the same envelope.

- A Anti-parallax mirrored scale.
- B Degree of accuracy.
- C A.C. current ranges.
- D Resistance ranges beyond 1M $\Omega$ .
- E Clearly marked, well arranged controls.
- J High sensitivity (ohms/volt).
- K Large, easy to read scale.
- L Overload Protection.

### COMPETITION RULES

There is no entry fee, but each attempt must be fully completed in ink on the proper printed coupon cut from Everyday Electronics, and bear the entrant's own full name and address.

Every accepted entry will be examined and the first prize, as described, will be awarded to the entrant who, in the opinion of an expert panel of judges, and in any one attempt, has shown the most skill and judgement in listing the eight features in order of importance. The other prizes will be awarded to the senders of the 12 next best attempts in order of merit. No entrant may win more than one prize.

In the event of a tie or ties for any of the prizes, a further eliminating contest will be conducted by post between the tying competitors to determine such winners or winning order.

Any entry which does not comply with the printed instructions or is received after the closing date will be disqualified, as will any received mutilated or illegible, incomplete, bearing alterations, or with more than one key letter in each space. No responsibility will be accepted for entries lost or delayed in the post or otherwise.

The judges' decision, and that of the Editor of Everyday Electronics in all other matters affecting the competition, is final and legally binding. No correspondence can be entered into.

The competition is open to all readers in Great Britain, Northern Ireland, and the Channel Isles except employees (and their families) of IPC Magazines, the printers of Everyday Electronics or of Chinaglia (U.K.) Ltd.

The winners will be notified, and the result announced in the earliest possible issue of this magazine.

Mulberry Walk, London, S.W.3

Everyday Electronics, July 1974

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



## Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1.05p** P & P 45p each

## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order

Only **27 1/2p** POST & PACKING 16p

## Tested and Guaranteed Paks



- |     |     |   |     |
|-----|-----|---|-----|
| B79 | 4   | IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic             | 55p |
| B81 | 10  | Reed Switches, 1" long. 3/4" dia. High Speed P.O. type      | 55p |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.  | 55p |
| H38 | 30  | Short lead Transistors. NPN Silicon Planar types            | 55p |
| H39 | 6   | Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945  | 55p |
| H41 | 2   | Sil Power transistors comp pair BD131/132                   | 55p |
| H63 | 4   | 2N3055 type NPN Sil. power transistors. Below spec. devices | 55p |
| H64 | 4   | 3819 N Channel FETs 2N3819 in plastic case                  | 55p |



## Unmarked Untested Paks

- |     |     |   |     |
|-----|-----|---|-----|
| B1  | 50  | Germanium Transistors PNP, AF and RF                        | 55p |
| B66 | 150 | Germanium Diodes Min. glass type                            | 55p |
| B83 | 200 | Transistors, manufacturers rejects, AF, RF, Sil. and Germs. | 55p |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202            | 55p |
| B86 | 100 | Sil. Diodes sub. mln. IN814 and IN816 types                 | 55p |
| H34 | 15  | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.         | 55p |
| H67 | 10  | 3819N Channel FETs plastic case type                        | 55p |

## Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1.10p** each

## Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

**£2.75 p.p. 38 1/2p** Per Instrument

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73p.

Extension Telephones. 71p each. p.p 27 1/2p. £1 37 1/2 for 2. P.&P. 55p.

These phones are extensions and do not contain bells.

## Electronic Transistor Ignition £6.60

Complete kit incl. V.A.T. p. & p. 11p. Ready built & tested unit £9.90 inc. V.A.T. Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

## New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available

Essential for alignment of colour guns on all T.V. receivers.

Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3" x 5 1/2" x 3". We have already received a large order from a major T.V. Rental company.

Ready built unit only **£10.92** Complete kit **£8.72** (Includes V.A.T. and p. & p. but no batteries)

## Over 1,000,000 Transistors in stock

We hold a very large range of fully marked tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular, 4p transistors

TYPE "A" PNP Silicon alloy. TO-5 can  
TYPE "B" PNP Silicon, plastic encapsulation  
TYPE "C" PNP Germanium AF or RF  
TYPE "E" NPN Silicon plastic encapsulation  
TYPE "G" NPN Silicon similar ZTX 500 range  
TYPE "H" PNP Silicon similar ZTX 500 range

**8 RELAYS FOR VARIOUS TYPES P & P 27p £1.10p**


## High Speed Magnetic Counter

4 digit (non-reset) 24v or 48v (state which) 4 x 1 x 1 in. 33p, p.p 5p.



## Plastic Power Transistors

NOW IN TWO RANGES

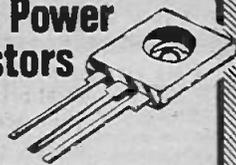

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.  
40 Watt 1-12 13-25 26-50  
22p 26p 18p  
90 Watt 26p 24p 22p

Range 2. VCE. Min. 40. HFE Min 40  
40 Watt 1-12 13-25 26-50  
33p 31p 29p  
90 Watt 38p 36p 33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in Practical Wireless December issue complete with application data £1.10

## INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

## METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 15p Wall Chart 18p  
LOW COST DUAL IN LINE I.C. SOCKETS 14 pin type at 16p each } Now new low profile 16 pin type at 18p each }

## BOOKS

We have a large selection of Reference and Technical Books in stock.

Send for lists of publications

## Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 20 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak

Please ask for Pak P.1. only **55p**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME .....  
ADDRESS .....

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co Reg No B20919

Dept. E. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.

# JOSTY KITS FROM ELECTRO SPARES

The Josty appointed stockists

**\* ALL KITS POST FREE! \* ALL PRICES INCLUDE VAT!**

It makes practical sense to invest in Josty Kits. They come complete with everything you need — all the components ready to use, including even the solder. Plus easy-to-understand, fully comprehensive instructions, and a cast-iron guarantee. Just look at the list of Josty Kits available now from Electro Spares. Remember, every price includes VAT, and every Kit is *post free*.

Model No.	Josty Kit Retail Price List	Total RRP inc. VAT		
AF20	Mono Transistor Amplifier	5-28	AT30	Photo Cell Switching Unit 6-27
AF25	Mixer	3-96	AT50	400w Triac Light Dimmer Speed Control 5-28
AF30	Mono Transistor Pre-Amplifier	2-87	AT56	2,200w Triac Light Dimmer Speed Control 7-59
AF35	Emitter Amplifier	2-50	AT6	Automatic Light Control 2-84
AF80	Small 0-5 W Amplifier for microphone	4-65	GU330	Tremelo Unit for guitars, etc. 8-25
AF305	Intercom	8-28	HF61	Diode Detector 3-66
AF316	Mono Amplifier (for Stereo use two)	6-50	HF65	Frequency modulated FM transmitter 2-97
M160	Multivibrator	1-88	HF75	FM Transistor Receiver 3-16
M1302	Transistor Tester	9-30	HF310	FM Tuner Unit 17-39
M191	Vu-Meter	5-01	HF325	De-Luxe FM Tuner Unit 26-53
M192	Stereo Balance Meter	5-47	HF330	Stereo Decoder for use with HF310 or HF325 10-95
LF380	Quadrophonic Device	12-50	GP310	Stereo Pre-Amp to use with 2, AF310 23-39
AT60	Psychedelic Light Control. Single Channel	8-58	GP312	Basis circuit board 12-60
AT65	Psychedelic Light Control, 3 Channel	16-00		Plus many others.
AT25	Window Wiper Robot	6-40		

## 'AMATEUR ELECTRONICS'

Specially produced by the makers of Josty Kits to give you a professional insight into the fascinating world of electronics. Written with the amateur in mind from start to finish, "Amateur

Electronics" is an ideal introduction to the whole subject — from first principles to advanced electronic techniques. The price includes a circuit board for making ten Josty Kit projects. Only £3.30 plus 20p p & p. No VAT. Send S.A.E. now for a free 8-page colour brochure all about Josty Kits and Amateur Electronics.

## COMPONENT LISTS FOR "EVERYDAY ELECTRONICS" PROJECTS

You only need to have constructed a few projects as published in "Everyday Electronics", to know what a problem it is to get every component just when you need it. Electro Spares have devised the complete solution. Now you can get lists of all the components required for any of the projects in this issue. Just send us a stamped addressed envelope, and tell us which project you are interested in. The list shows a separate price for each item, as well as a price for the complete kit. You can buy any one or more components to suit yourself.

### GUARANTEED COMPONENTS FROM ELECTRO SPARES

Every single component you buy from us is a new branded product from a reputable manufacturer. And it carries the manufacturer's full guarantee.

Save money — and time — buy all your components from one source

# ELECTRO SPARES



The Component Centre of the North  
288 ECCLESALL RD., SHEFFIELD S11 8PE (B)  
Tel: Sheffield (0742) 668888

## PLUGS

Pack 107 5 pin Din	25p
Pack 108 3 pin Din	20p
Pack 135 1/2" Jack	30p
Pack 130 1/2" Jack Stereo	50p
Pack 103 Loudspeaker Plug	20p
Pack 100 Phono Plug	10p
Pack 230 3 pin Socket	25p
Pack 236 5 pin Socket	35p
Pack 234 1/2" Speaker Socket	35p

## READY MADE LEADS

3 pin to 3 pin Din	70p
3 pin to open end	55p
5 pin to 5 pin Din	£1
5 pin to open end	70p
5 pin to 4 phono plugs	£1

All leads approx. 6ft. in length.

Speaker lead Din to spade 12ft.	50p
Extension lead Din plug to socket 12ft.	80p

## DIAMOND STYLI

8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8 All at 80p each.
Double Diamond £1-25.
Diamond suitable for Orbit NM22; G800; M3D £2-25 each.

## HEADPHONES

Sennheiser HD414	£12-50
AKG K50	£6-50
Beyer DT485	£35-00

## RECORD CARE

Cecil Watts Dust Bug	£1-20
Parastatic Disc Preener	45p
Anticstatic Fluid	20p
Dust Bug Spares (Brush & Roller)	15p

Prices inc VAT and Post.

Prices correct when going to press but subject to change without notice.

**J. J. Francis (WOOD GREEN) Ltd.**  
MANWOOD HOUSE, MATCHING GREEN,  
HARLOW, ESSEX CM17 0RS Tel: Matching 476

## CASSETTE TAPES

Audio-Magnetics C60	25p
3 6 10 20	
£1-00   £1-90   £3-20   £6-30	
Cassette Caddy £1-20	
Cassette Head Cleaner 35p	

## ZONAL ILFORD TAPE

5" Standard 600ft	25p
5 1/2" Standard 900ft	50p
7" (Plain boxed) 1200ft	60p
7" (Westminster Boxed) 1800ft.	£1-25
7" Reel of Leader Tape (Blue or green)	75p

## MICROPHONES

AKG D109	£12-65
AKG D202E1	£43-45
AKG D190C	£18-70
AKG D190E	£20-02
AKG D224	£55-00
Sennheiser MD211N	£49-50
Sennheiser MD413N	£29-70
Sony ECM50	£93-50
Audio RM57F Radio Mike	£231-00

## SPEAKERS

E.M.I. 350 Kit 8 ohms	£8-20
E.M.I. 450 Kit 8 ohms	£4-50

## CARTRIDGES

Goldring G800	£6-00
Orbit NM22	£4-00
Shure 75J6	£6-00
Sonotone 9TAHC (Dia)	£2-00
Sonotone 8T4A (Dia)	£1-50
Ronnette 105 (Dia)	£1-25

## SOLDERING GUN




£2-75

VAT PAID

P&P 33p

New surplus stock as illustrated. AC240 volts. Input power 100 VA. Instant heat at touch of trigger switch in handle. Constructed in robust plastic casing with work light in front and 4' x 3' core cable.

## PROGRAMME TIME SWITCHES

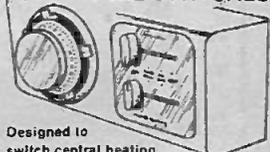

Designed to switch central heating and hot water on/off twice a day. Suitable for any electrical appliance up to 3 amps 240 volts A.C.

£5-50 P&P 28p  
VAT paid.

New surplus stock as illustrated. Size 7" x 4" x 3"

Smiths Time Switch with 24 hour dial which is simple to set to switch on/off twice per day at any times required. Also fitted with two lever switches which can be set to operate two circuits which can each be set to operate on Time Switch twice per day, all day, continuous, or off. Mounted in robust white plastic casing Drilled for fixing on back supplied with wiring instructions. Ideal for shop lighting and many other applications.

## SAE FOR CATALOGUE WITH MANY OTHER BARGAINS TO

C. W. WHEELHOUSE & SON,  
9/13 BELL ROAD,  
HOUNSLOW.  
PHONE 01-570-3501.

**New products and component buying for constructional projects**

# SHOP TALK

By Mike Kenward

WE often get letters from readers asking how to get started in constructional electronics and we usually reply by saying buy a kit for one of our more simple projects—some of the advertisers sell them—and build it to the details shown, this way we know the unit works and that the reader will be starting at a fairly elementary level. However there is another way of constructing items—a way which requires very little skill and no soldering, you can build things and learn something with no fears of damaging components and when you are proficient you can gradually change to normal construction methods. The new way—with an Electroni-Kit.

Some time ago we were supplied with a SR4A kit which we tried out (the electronic machine-gun is good but fortunately failed to injure anyone!) and eventually passed on to the son of a staff member for further "trials". The unit has proved to be quite good and has

**The Electroni-Kit ST100 kit—good value for value for money.**



provided hours of fun and entertainment as well as education.

The biggest advantage is that youngsters can build many projects without help and without the need for tools, cases or soldering irons. The kits are not cheap but are worthwhile and cost from £8.80 to £33.95 including V.A.T. They provide many designs to build and the components can be used over and over again. There is no reason why almost any design should not be constructed and tested once the user became able to lay out the design.

Details from Electroni-Kit Ltd., 408 St. John's St., London EC1.

## General Purpose Amplifier

The parts for the *General Purpose 5 Watt Amplifier* should all be readily available, only the speaker is likely to provide any difficulty and this is an R. S. Components type which can be ordered from them by almost any dealer. The speaker unit must be a 15 or 16 ohm type.

Some notes on one or two other parts will not be amiss, the 741 integrated circuit should be obtained in the eight-pin dual-in-line (d.i.l.) case—most of them are this type nowadays. The transformer used can be any type with a mains primary and secondary rated at about 17V at 1A, various types are available from suppliers and prices vary considerably.

In the prototype one of the tags on the input selector switch has been used for component mounting (earth), if your switch is a single pole three way type it will not have this extra tag and the connection will have to be self supporting—this will be quite satisfactory in this application.

## Telephone Call Charge Calculator

The most important part in the

*Telephone Call Charge Calculator* is probably the counter—the bit that actually shows what your wife has spent, provided you can convince her to use the unit! As far as we know this counter is only available from Henry's Radio. If you find one anywhere else make sure that it is a 12V to 24V type (the 24V only types will not work on the 15V supply) and the coil resistance is in excess of 200 ohms.

The 555 timer integrated circuit should be obtained in the eight pin d.i.l. case, once again most of them are these days anyway. We always advise readers to use sockets with integrated circuits since they can be damaged by soldering and are difficult to remove without special tools once they are soldered in.

## Light Level Controller

We recommend the use of a plastic case for the *Light Level Controller* and advise readers to take note of the points concerning insulation as mentioned in the text.

The triac listed is a 6A 400V device but is reasonably priced at about 90p and is more than adequate for the maximum permissible lamp load imposed by the suppression coils. Other types of triac can be used provided they are rated at least 400V at 2A (to avoid overheating—no heatsink is fitted), remember other types may have different cases and wire configurations.

The transistors are high voltage types and have few direct equivalents. A. Marshall (London) Ltd., 42 Cricklewood Broadway, London NW2 3ET can supply two BF259s for £1.35 including V.A.T and postage.

## Transistor Assisted Ignition

We have been informed by Marshall's that due to the very large number of orders they have received for the semiconductor for the Transistor Assisted Ignition they have run out of stock of the TIP49 transistor.

Unfortunately their suppliers have already put back the quoted delivery date (in April) by approximately three months and it could be quite a few weeks before Marshalls can supply the outstanding orders. Readers' money will be refunded on request or the orders will be held until a supply is available.



## Blow for Bagpipes

Just a few comments about the *Electronic Bagpipes* article of the May issue of *EVERYDAY ELECTRONICS*.

Firstly there appears to be an error in the second full paragraph of column 2 page 254 in that the references to positions 1 and 3 of the switch are interchanged. Position 1 gives vibrato, whilst position 3 gives "bagpipes", or so it seems to me from Fig. 1. Incidentally I do not think that the Scottish folk will like it one bit to read the part that says that "in position 3 it becomes a

pleasing sound not unlike an organ".

I suspect that the author is Tom Richardson of North Shields former fellow of the Electronic Organ Constructors Society, and next time I see him, I must pull his leg about this, should we say, "praising with feint damns", or left handed compliments.

However I do think that the article would have been improved by the inclusion of a few dimensions, and perhaps an extra elevation, in Fig 3. Also by the inclusion of a musical stave showing the exact compass to be aimed at (because the "spread" of unijunctions can alter the tuning), together with much more precise instructions for the tuning of the drones than is given in the closing paragraph.

James W. Robson  
Newcastle upon Tyne.

*We thank you for pointing out the error in our text namely that in the above mentioned paragraph, positions 1 and 3 should be transposed. We apologise to any Scottish readers who may have been offended.*

*As far as "more information" is concerned we think sufficient has been given to successfully construct the unit. We would be interested in readers' comments on this point.*

## Suppression

I feel that I must make a few comments on the reply given in your *Help* column of the May issue of *EVERYDAY ELECTRONICS*, concerning automobile interference.

If carbon leads are fitted (as the practice seems to be these days) the standard way of suppressing these leads is to replace the carbon h.t. lead between the coil and distributor with a length of copper h.t. lead, and insert a "cut-lead suppressor" 1½ inches from the coil end of the lead.

The h.t. coil is suppressed with a 1µF not 0.1µF capacitor as stated, and is fitted to the ignition, or SW side of the coil. The same value 1µF is fitted to the alternator, or dynamo. In either case it is advisable to disconnect the battery.

Hoping you will correct these errors made in a future issue of your otherwise excellent magazine.

A. N. Choat  
Medway Sound Service  
Rainham.


## Amateur Exhibition

I was very interested to see in the May issue of *EVERYDAY ELECTRONICS* the discussion by Mr. Paul Young on page 270 in *Counter Intelligence*. I am pleased to say that I can answer Mr. Young's plea as the British Amateur Electronics Club is holding a B.A.E.C. Amateur Electronics Exhibition at the Shelter, The Esplanade, Penarth, from July 20 to July 27 next.

I am expecting many exhibits from members in all parts of the country, so that there should be a very good cross-section of both original exhibits and designs taken from your excellent magazine. All readers are welcome.


Cyril Bogod  
B.A.E.C.

## JACK PLUG & FAMILY...

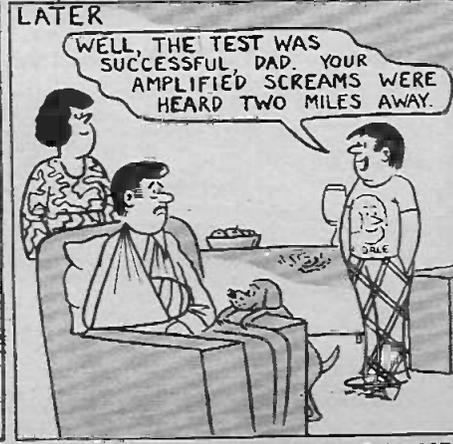
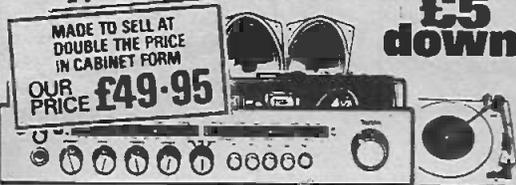
# QUALITY STEREO SOUND

ALMOST  $\frac{1}{2}$  PRICE OFFER! SOLENT AUDIO SYSTEM



MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM  
OUR PRICE **£49.95**

**£5 down**

\*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 $\frac{1}{4}$ " x 3 $\frac{1}{4}$ ". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £2.50. Send £7.50 today.

Chassis only available for cash at £35.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every order.



**LEWIS** radio


E.E. 7/74, 100 CHASE SIDE SOUTHGATE  
LONDON N14 5PL Telephones: 01-886 9666/3733

# CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL  
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.  
11 MAYES ROAD, LONDON N22 6TL  
Phone 888 3206 & (EDM). 803 1685

## PLASTIC BOXES

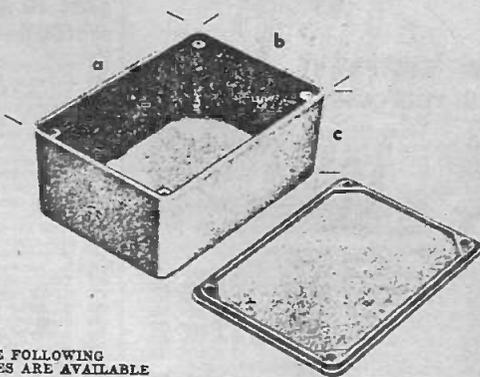

THE FOLLOWING SIZES ARE AVAILABLE

	a	b	c	
1005	10.5 cm	7.3 cm	4.7 cm	51p
1006	14.9 cm	7.3 cm	4.8 cm	66p
1007	18.2 cm	12.2 cm	6.4 cm	95p
1021	19.5 cm	7.4 cm	4.5 cm	50p

Post and Packing 10p.  
:- SLOPING FRONT 60DEG (Approx.)

### stabilised

#### POWER PACK CONVERTER

Switched 3, 6, 7, or 9 volts  
Up to 400mA Output



SA- Output Lead with 3.5mm plug plus P.R.E.T. multi plug and socket adaptor  
Metal Case  
Potentiometer  
Voltage Selector  
Power Output Transistor  
Mains Lead (over 4ft)  
Transistor and Transformer Stabiliser Circuit  
Even Indicator  
On/Off Switch  
Rubber Feet

£5.25 + VAT. 16p P. & P.

#### "CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

##### ★ THE POWER AMP MODULE

170W. r.m.s. eq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). £14.28, carr. 45p.

##### ★ THE PRE-AMP MODULE

Four control pre-amp, Vol. Bass. Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage. £8.96 carr. 25p.


##### ★ THE POWER SUPPLY

Is supplied complete with the mains transformer. £9.68, carr. 50p. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. If you purchase all three modules. £25, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

#### MAINS TRANSFORMER

200-240 P.R.I.  
180v. 50MA SEC.  
6.3v. 1 Amp Sec.

£1.00 + 10p P. & P. EACH

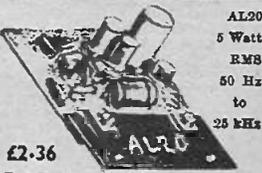

£2.36

P. & P. 10p.

#### ELAC HI-FI

10" Twin Cone

Speaker

7 Watts

Free Air

40 Hz 12000 Hz

£3.75 P. & P. 25p.



#### 3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)

£18.50 plus 38p P. & P.

#### CRESCENT CATALOGUE

If you construct you should own one. Send 20p inc. carriage.

#### VAT

Please include 10% VAT on goods plus carriage.

## ENGINEERS

# FREE

YOURSELF FOR A

# BETTER JOB WITH MORE PAY!



This 76 page  
FREE book  
shows how!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

POST NOW

CUT OUT THIS COUPON  
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- |   |                          |   |                          |  |                          |
|---|--------------------------|---|--------------------------|--|--------------------------|
| Practical Radio & Electronics (Technatron)    | <input type="checkbox"/> | Radio Amateurs Practical TV               | <input type="checkbox"/> | General Electrical Engineering         | <input type="checkbox"/> |
| Electronic Engineering                        | <input type="checkbox"/> | Colour Television                         | <input type="checkbox"/> | Society of Engineers (Electrical Eng.) | <input type="checkbox"/> |
| Television Maintenance & Servicing            | <input type="checkbox"/> | Computer Electronics                      | <input type="checkbox"/> | Electrical Installations and Wiring    | <input type="checkbox"/> |
| General Radio & TV Engineering                | <input type="checkbox"/> | C & G I.I. Radio TV Servicing Cert.       | <input type="checkbox"/> | C & G Electrical Technicians (Primary) | <input type="checkbox"/> |
| Radio Servicing, Maintenance and Repairs      | <input type="checkbox"/> | Post Master General 1st & 2nd class Certs | <input type="checkbox"/> | C & G Telecommunications               | <input type="checkbox"/> |
| City & Guilds Radio, TV Electronics Mechanics | <input type="checkbox"/> | C & G Electrical Engineering Practice     | <input type="checkbox"/> |  |                          |
|   |                          | C & G I.I. Installations and Wiring       | <input type="checkbox"/> |  |                          |

To B.I.E.T. BEE 05 Aldermaston Court, Reading RG7 4PF QK **BEE 05**

NAME (Block Capitals Please)

ADDRESS

Other subjects

Age

Accredited by C.A.O.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# Henry's

**DON'T RELY ON YOUR MEMORY  
BUY NOW AT BARGAIN PRICES**  
Hi Fi and Transistors - Up to date  
Brochures on request

**HENRY'S  
CATALOGUE**  
Due to rapid price changes,  
shortages of paper and raw  
materials, all prices in the  
existing catalogues no longer  
apply. Call or phone for latest  
prices. A new catalogue will  
be available for Aug/Sept. 1974.



**UK's  
LARGEST RANGE  
OF KITS &  
GADGETS**



## TEST EQUIPMENT

### MULTIMETERS

- (curr. etc. 30p)
- ITI-2 20K/Volt Slimline 5-95
  - M210 (Case £1-25) 20K/Volt Slimline de-luxe 6-75
  - TLH33D 2K/Volt Robust 7-00
  - UA323 (+H/BAF Osc) 12-50
  - AF105 (Case £2-25) 50K/Volt 10-50
  - UA313 20K/Volt AC current. Steel case 10-50
  - UA341 Plus Built in transistor tester 10-50
  - Model 500 (Case £2-25), 30K/Volt 11-75

### OTHER EQUIPMENT

- SE250B Pocket Signal Injector 2-25 carr. 15p
- TE15 Grid Dip meter 440KHz-280MHz 18-50 carr. 30p
- TE40 AC Millivoltmeter 1.2mHz 18-75 carr. 35p
- TE65 2S Range valve voltmeter 22-50 carr. 40p
- TE20D 120KHz-500MHz RF Generator 18-95 carr. 40p
- TE22D 20Hz-200KHz Audio Generator 19-95 carr. 40p
- SE350A Deluxe Signal Tracer 12-95 carr. 20p
- SE400 Volts/ohms/R-C sub./RF field gen. 15-50 carr. 20p

### New Revolutionary Supertester 680R

- 680R Multi-tester £18-50
- Accessories
  - Transistor tester 11-00
  - Electronic voltmeter 18-00
  - Amplamp 11-95
  - Temperature probe 11-95
  - Signal Injector 11-95
  - Guess meter 5-95
  - Phase Sequence 5-95
  - EHT Probe 5-95
  - Shunts 25/50/100A 4-50

### A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester 8-95 p & p 15p
- Q4002 Photoelectric System £13-70
- E1310 Stereo mag. cart. preamp. 4-80 p & p 25p
- E1310 Stereo mag. cart. preamp. 7-50 p & p 25p
- E1310 Stereo mag. cart. preamp. 4-95 p & p 20p
- D1203 Telemag. with PU coil 4-95 p & p 25p
- LL1 Door Intercomm. and chime 8-40 p & p 25p
- 9" Twin spring unit For 3-30 p & p 15p
- 18" Twin spring unit Reverbs 6-85 p & p 25p
- US50 Ultrasonic Switch Transmitter/Receiver £12-75
- C3041 1-250 MHz 24-25
- C3043 5CH 1-300 MHz £5-75
- VHF 105 Aircraft Band Converter 4-50 p & p 15p
- B2005 4 Ch. mic. mixer 4-20 p & p 15p
- B2004 2 ch. Stereo mixer 6-75 p & p 15p
- PK3 Kilg. Etch your own ptd. circuits £1-95 p & p 20p

### BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW-banded for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7-98 (battery 22p), carr. etc. 32p.




### EXCLUSIVE: SPECIAL OFFERS

- MW/LW CAR RADIO PORTABLE CASSETTE
- + or - Earth with speaker TAPE PLAYER for car or and fixings. £8-50 c.p. 30p. carry around. £7-25 c.p. 20p.
- 3 TRACK CAR STEREO HANIMAX BC908 POCKET (- Earth) with speakers in CALCULATOR WITH Pds & fxgs. £12-50 c.p. 43p. % KEY. £28-95
- Portable Battery Cassette HANIMAX BC811M Tape Player £7-25. MEMORY VERSION £33-75
- Car Lighter Plug and adaptor for all cassette and radio. BC807 % Key £22-95
- 67/7/9 volt output (state BC850 % Key + Memory £33-95 width) £1-95 each
- Rotel Stereophones £8-80 COMPACT RECORD HANIMAX H101 STEREO £10-25 PLAYER 2 x 7 watts. Complete with Speakers (Plus Weir W500 Battery/Mains £54-50) Price £39-95. Last free pair of stereo phones.
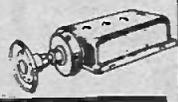
## SPECIAL PURCHASES

**UHF TV TUNERS CHANNELS 21 TO 4**  
Brand new transistorised geared tuners for 625 Line Receiver IF output. £2-50, Post 20p.



## EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

- Model No.
- 310 Radio control receiver 3-20
  - 300 4-channel R/C transmitter 6-61
  - 345 Superchet R/C receiver 6-61
  - 65 Simple transistor tester 6-61
  - 115 8 watt Amplifier 4-50
  - 120 12 watt amplifier 4-73
  - 125 Stereo control unit 6-61
  - 130 Mono control unit 5-31
  - 605 Power supply for 115 5-31
  - 610 Power supply for 120 5-31
  - 615 Power supply for 2 x 120 3-23
  - 230 AM/FM aerial amplifier 6-90
  - 240 Auto packing light 6-98
  - 275 Mic. preamplifier 21-45
  - 570S LF generator 10KHz-1MHz 19-77
  - 575S Sw. wave generator 20Hz-20KHz 9-47
  - 590 SWR meter 9-24
  - 630 STAB Power supply 0-12v 0-25-0-1A 3-31
  - 690 DC motor speed Gov. 7-92
  - 700 Electronic Chaffinch 12-57
  - 760 Acoustic switch 10-91
  - 780 Metal Detector (electronics only) 7-92
  - 790 Capacitive Burglar alarm 4-99
  - 835 Guitar preamp. 8-99
  - 840 Delay car alarm 13-99
  - 875 CAP. Discharge Ignition for car engine 6-98
  - 80 Scope Calibrator 11-31
  - 255 Level Indicator 8-97
  - 525 120-180MHz VHF timer 15-51
  - 715 Photo cell switch 8-61
  - 795 Electronic continuity tester 9-30
  - 880 Photo timer 9-30
  - 235 Acoustic Alarm for driver 8-61
  - 465 Quartz XTAL checker 19-30
  - 220 Signal Injector 6-55
  - 390 VOX 18-75
  - 432 Testkit 58-50
  - 670 Buffer Battery Charger
  - 850 Electronic Keyer
  - 820 Electronic Digital Clock

**ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY**  
Prices correct at time of preparation. Subject to change without notice.

### BUILD THIS TUNER ML3

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, h.c.a.s.d. in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £5-25, carr. 15p.

- Mullard FM Modules
- LP1185 Tuning Heart Module. £7-95.
- LP1185 IF Module. complete with data. Price £9-00 pair.
- FM Tuner Module
- FMS231 12v FM Tuner £7-95.
- SD4912 Stereo Decoder £7-95.
- SF82H 6v Stereo FM Tuner £14-95.

Sinclair Special Offer Stereo 60 Pre-amplifier - for use with most small amplifiers. Exclusive offer £6-75.

- TBA800 5 WATT I.C. Suitable alternative to EL400D 5/30 volt operated. 8/16 ohm 5 watt output. With circuits and data £1-95.
- Kit with printed circuit panel £2-70. All kits available from stock.
- STROBE TUBE ZFT4A. Suitable for December 73 Pract. Electronics £3-50.
- ST2 (D32) DIAC 25p CR51/40 SCR 45p.
- ZFT4 £3-50
- ZFT8 £4-00

## JUST A SELECTION

- TBA800 5 Watt IC £1-50
- Sinclair IC12 6 Watt IC £2-00
- ZM414 C Radio £1-20
- Ultrasonic Transducers £5-90 pr.
- 3015F 1550 Indicator £1-70
- 212 LED 24p each. 22p each per 10
- With circuits/data sheet
- OVER 1500 DIFFERENT SEMI-CONDUCTOR DEVICES IN STOCK
- Free stock list—latest edition (Ref. 36) on request. Includes radio valves, I.C.'s Rectifiers, Triacs, SCR's, LED's, etc. More types—better prices—discounts for quantity small or large.

## GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape deck. Fitted record/play and oscillator/Erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9-50 carr. 30p.

## TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any qty).

- Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.
- Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 50p each.
- Quantity discounts available
- Complete with knobs.

## MARIOT TAPE HEADS


4 TRACK MONO or 2 TRACK STEREO

- '17 High Impedance £2-50
- '18 Med. Impedance £3-50
- '36 Med. Impedance £5-00
- R730/R73 2 track mono Record/Eraser low Imp. 75p each.
- Erase Heads for '17, '18 and '36' £1-00
- '63' 2 track mono, Hi Imp. £1-75
- '43' Erase Head for '63' 75p

(Post, etc. 15p any qty.)
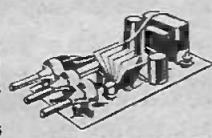
## SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

- AMPLIFIERS (carr., etc. 20p)
- 4-300, 0-3 watt 9 volt 1-75
  - 104, 1 watt 8 volt 3-10
  - 304, 3 watt 9 volt 3-95
  - 555, 3 watt 12 volt 4-10
  - E1208, 5 watt 12 volt 5-10
  - 608, 10 watt 24 volt 4-95
  - 410, 10 watt 28 volt 4-95
  - E1208, 30 watt 45 volt 9-85
  - E1210, 2 1/2 + 2 1/2 watts 8-25
- RE350, 5 watt IC mains operated Amplifier with controls 6-30
- SAC14, 7 + 7 watt Stereo with controls 11-75
- SAC13, 15 + 15 watt Stereo with controls 14-95
- SP40-5 2240/stereo 2-25 post 20p
  - 80/PZ5 25-00
  - SP40-6 2240/stereo 27-75
  - SP60 5280/stereo 30-45
  - 80/PZ8 30-45
  - Transformer PZ8 3-95



## POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)

470C 67/7/9 volt 300 mA (includes Multi-Adaptor for Tape Recorders, etc.)

Car Lighter Voltage Adaptors 300mA (State voltage 1-95 ea. post 25p)

- 4-25 carr. 30p
- 5-50 carr. 30p
- 2-28 post 20p
- 2-80 at 20p
- 2-80 post 20p
- 4-70 post 20p
- 7-80 post 20p
- 7-15 post 30p
- 12-75 post 25p
- 13-45 post 30p

## FIBRE OPTICS

0-01 Diam. Mono Filament £5-50

0-100 meter reel 0-13 Diam. 64 Fibres Sheathed. £1-00 per metre.

SPRAYS 15mm Diam. (Mares Tail Spray £10-50)

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT to be ADDED to ALL ORDERS. UK post etc. 15p per order unless stated.



**Henry's RADIO LIMITED**  
EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381  
309 PA - Disco - Lighting High Power Sound 01-723 6963  
303 Bargains Store (Callers only)  
Home and Car Entertainment Centres London and branches now open.  
120 Shaftesbury Avenue, London W1 01-437 9692  
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402  
130-134 Station Road, Harrow, Middlesex 01-663 7788/9  
354-356 Edgware Road, London W2 01-402 8854/4736


All mail to 303 Edgware Road, London W2 1BW  
All stores open 9 am to 6 pm six days a week  
Hi-Fi - Tape Equipment Discount Stock List Free at all stores

# KNOW YOUR COMPONENTS...
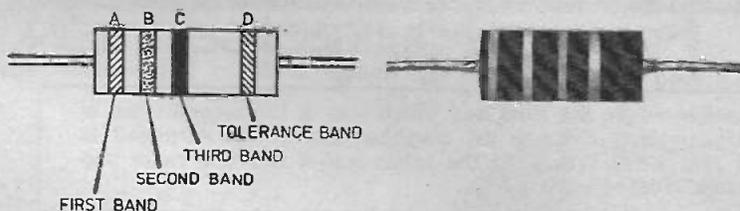
## Hints & Tips for the Novice Constructor

By Ron Adams

THE beginner in electronics often has difficulty in identifying components, component values (sometimes coded), polarities, etc. This "information page" has been formulated to help in this area and begins this month with the most common component—the resistor.



### The Resistor

The obviously important thing to watch on this device is the ohmic value, depicted by a colour code. At least all resistors—excepting some high stability types, which have the value printed on the body—have a colour coding of bands or dots, see Table 1.

If you don't know your colour code, then keep it written on a card next to you when constructing your projects. You will save yourself a lot of headaches and time by putting the right resistors in circuit. Not to mention the damage to components that can result.

The other thing to watch carefully is the current rating. Remember that you can put a half watt resistor in place of an eighth watt resistor, but not vice versa.

The wattage of the resistors can usually only be found from the size and type of resistor and various types and sizes with wattage ratings are also shown in full-sized silhouettes below.

Also, it is surprising how many people think that a resistor is polarised and has to be put in circuit one way only—it isn't and can be put in either way round.

### Colour Code Example

A resistor coded as A—red, B—violet, C—yellow, D—gold indicates a value of 470 kilohm  $\pm 5$  per cent.



Next part: capacitors.

Table 1: Resistor Colour Code

Colour	1st digit (A)	2nd digit (B)	Multiplier (C)	Tolerance $\pm$ per cent (D)
Black	—	0	1	—
Brown	1	1	10	1
Red	2	2	100	2
Orange	3	3	1,000	3
Yellow	4	4	10,000	4
Green	5	5	100,000	—
Blue	6	6	1,000,000	—
Violet	7	7	10,000,000	—
Grey	8	8	100,000,000	—
White	9	9	1,000,000,000	—
Gold	—	—	0.1	5
Silver	—	—	0.01	10

No fourth band indicates a  $\pm 20$  per cent tolerance.

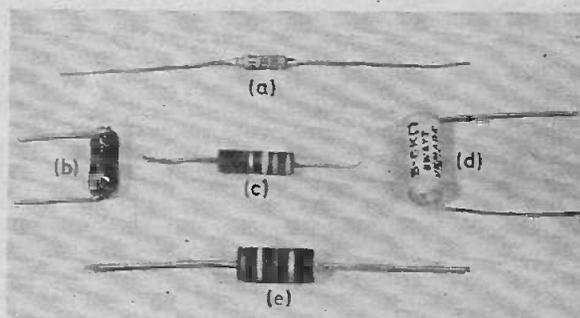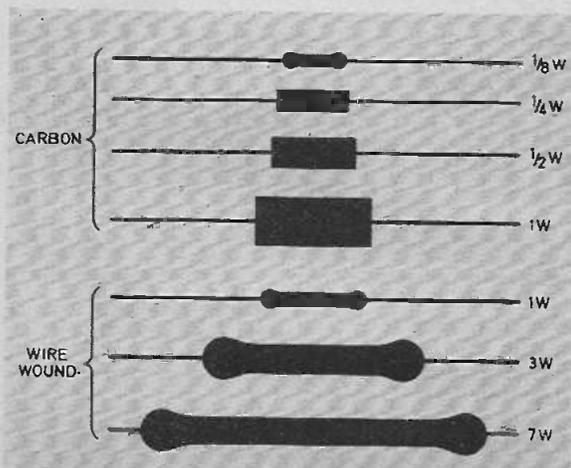A fifth band is sometimes used, colour salmon pink, to indicate high stability (hi-stab) resistors.



Above. A selection of resistors. (A) high stability (B) enamelled wirewound (C) and (E) carbon composition (D) high voltage wire wound. Left. Size and wattage of common types.

# DOWN TO EARTH

By GEORGE HYLTON

"I connected up the *Fuzz Box* which was in the second issue of *Everyday Electronics* to my amplifier and I was surprised to find that when I touched the input lead I heard a radio programme. Please explain."

This kind of experience isn't at all uncommon. It explains why audio pre-amplifiers have "unnecessary" capacitors in them which have no appreciable effect on their audio performance. They are there to prevent "break-through" of unwanted r.f. signals picked up by the input leads.

## HUMAN AERIAL

In the dear old days when even medium wave receivers had to have an aerial wire plugged in at the back, many of us found out that a finger touched on the aerial terminal was a useful temporary substitute. Not that anybody spent his evenings standing by a set with a finger poked into it, but it was a handy trick for testing purposes.

The human body may not be a very efficient aerial, but it does pick up strong radio signals. That explains how the radio-frequency signals got into the *Fuzz Box*. What it doesn't explain is how they were converted to audio, in other words how they were "detected."

## RECTIFICATION

Detection is rectification—the conversion of the r.f. carrier into d.c. Fluctuations in the r.f. strength appear as fluctuations in the d.c. output. The fluctuations are caused deliberately at the

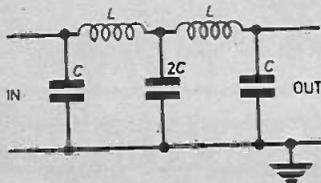


Fig. 1. A low-pass LC filter.

transmitter, by "modulating" the r.f. carrier with the audio programme, and rectification recovers the audio.

Now, rectification is normally carried out by diodes, and there are no diodes in the *Fuzz Box*. So how does it rectify?

## DISTORTION

Well, rectification is a form of distortion, in which the positive half-cycles, say, are allowed to pass and the negative ones are suppressed. Even if the process is incomplete, and the unwanted half-cycles are only partially suppressed some degree of rectification still takes place. In the *Fuzz Box* this kind of distortion is deliberately introduced to provide the "fuzz" effect, so it's not surprising that r.f. signals are detected by it.

The question is, how to eliminate the r.f. breakthrough, if it is bad, without at the same time eliminating the "fuzz" effect.

## LOW-PASS FILTER

The obvious method is to put a low-pass filter in the input circuit, so as to allow audio signals to pass but attenuate radio-frequency signals. In theory, an LC filter (Fig. 1) is most effective, but the chokes are apt to be bulky and expensive.

If the lowest radio frequency is far above the highest audio frequency the less efficient but cheaper RC filter is adequate.

In the U.K., the 200kHz long wave transmitter (Radio 2) is likely to be the lowest dangerous radio frequency (unless you live near one of the v.l.f. navigational aid transmitters). The highest audio frequency of interest is 10kHz, since "fuzz" in the form

of harmonics of higher frequencies is beyond the limit of human hearing, and anyway most of the "fuzz" tends to be at much lower frequencies than even 10kHz. So a filter which attenuates 10kHz slightly is the best bet, since it will attenuate 200kHz at least 20 times more.

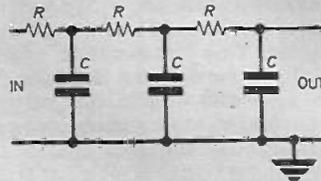


Fig. 2. A three-section low-pass RC filter.

The values of R and C and the number of filter sections needed are a matter for experiment, but a three-section filter as shown in Fig. 2, with R=10 kilohms and C=1,500picofarads should function satisfactorily. Neither value is critical, but ceramic or mica capacitors are better than paper or plastic types. The rated capacitor working voltage is not important here.

## SCREENING

The filter should, along with the rest of the *Fuzz Box* components, be enclosed in an earthed metal box for screening, and connected to the amplifier with a screened lead. Quite short lengths of unscreened lead can pick up enough r.f. to cause interference, particularly if the source is a short-wave one such as the local television transmitter.




"I wish you wouldn't make so many labour-saving gadgets—I get tired of going round switching them all on."

Everyday Electronics, July 1974
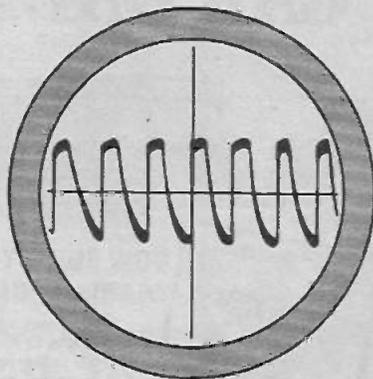
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
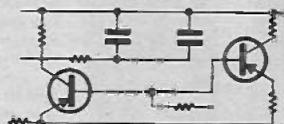
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**,  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
*we do not employ representatives*

NAME

**BLOCK CAPS**

ADDRESS

PLEASE EEL 7.4.

**special free gift also to all our students**

# R T V C

## FOR AUDIO ON A BUDGET

### PUSH BUTTON<sup>(\*)</sup> CAR RADIO KIT



*The first time Motor magazine have nominated a push button car radio for their Top Ten Accessory Awards*



#### NOW BUILD YOUR OWN AWARD WINNING PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
- 2.) Integrated circuit output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.  
Size Chassis 7 ins. wide, 2 ins. high and 4 1/8 ins. deep approx.

*NOTE:* The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p. free with kit.

#### Car Radio Kit

£6.60 + 55p. postage & packing.

Speaker including baffle and fixing strips  
£1.65 + 23p. postage & packing.

Recommended Car Aerial - fully retractable and locking.  
£1.35 post paid.

## STEREO 21



### QUALITY SOUND<sup>(\*)</sup> FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit. - no soldering required. Includes:-

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded:-

Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV. Power output 2.7 watts per channel; Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout.

Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions: Speakers approx.

15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6". Complete only £18.95

Extras if required. Optional Diamond Stylus £1.37 + £1.60 p & p.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. £3.85.



### DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).


Inputs \*5 Electrically Mixed Inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling.

#### INPUT SENSITIVITIES

1) Crystal Mic or Guitar 9mV. 2) Moving coil Mic or Guitar 8mV. 3), 4), 5) Medium output equipment (Gram, Tuner, Monitor, Organ, etc.) - all 250mV sensitivity.

AC Mains 240V. operation. Size approx. 12 1/2 ins x 6 ins x 3 1/2 ins  
£15.00 + 60p. postage & packing

## DISCO 50

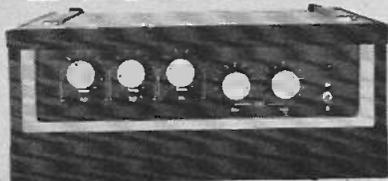

### 45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 1/2" x 10 1/2" x 8 ins. approx. Amplifier £27.50 + £1.50 p. & p

Special Offer: Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on opposite page). Complete £57.00 + £4.00 p&p.

# COMPLETE (\*) STEREO SYSTEM



**£51.00**

40 Watt Amplifier.  
Viscount III - R102 now 20 watts per channel.  
System I includes:  
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/ stereo on/off function and bass and treble filters. Plus headphone socket.  
Specification  
20 watts per channel into 8 ohms.  
Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within -1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power).  
Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics:* Bass: -12dB to -17dB @ 50Hz. Bass filter: 6dB per octave cut. Treble control: treble -12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.  
Crosstalk better than 35dB on all inputs.  
Overload characteristics better than 26dB on all inputs. Size approx. 13 3/4" x 9" x 3 1/2".  
Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.  
Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 1/2" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter (10 watt handling)

**Complete System £51.00**

**£69.00**

System II  
Viscount III amplifier (As System I)  
Garrard SP. 25 (As System I)  
Two Duo Type IIIA matched speakers - Enclosure size approx. 31" x 13" x 11 1/2". Finished in teak veneer. Drive units approx. 13 1/2" x 8 1/2" with 3 1/2" HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

**Complete System £69.00**

**PRICES: SYSTEM 1**  
Viscount III R 102 amplifier £24.20 + £1 p & p  
2 Duo Type II speakers £14.00 + £2.20 p & p  
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover £21.00 + £1.75 p & p.

total £59.20


Available complete for only **£51.00 + £3.50 p. & p.**

**PRICES: SYSTEM 2**  
Viscount R102 amplifier £24.20 + £1.00 p. & p.  
2 Duo Type IIIA speakers £39.00 + £4.00 p. & p.  
Garrard SP25 with MAG cartridge de luxe plinth £21.00 + £1.75 p. & p.  
and hinged cover total £84.20

Available complete for only **£69.00 + £4 p. & p.**
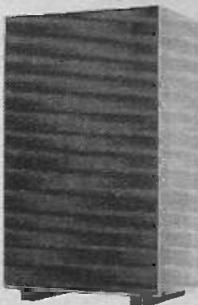
# EMI SPEAKERS AT FANTASTIC REDUCTIONS


**THE ULTIMATE COMPLETE SPEAKER SYSTEM**  
EMI LE 315 listed price £86.00



A professional standard five way speaker system with enclosure giving top quality performance.  
Enclosure Dimensions approx. (3ft. x 2ft. x 1ft.).  
Drive Units  
Hand built - 15" diameter bass with 3" voice coil. - two 5" diameter Mid Range units. - two 3 1/2" HF. units. plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.  
Power Handling  
Continuous rating 35 W rms. Peak power rating 70 W.  
Frequency Response  
20 Hz to 20,000 Hz. Imp. 8 ohms.

Our price **£45.00 - £3.50 p. & p.**

Recommended retail price **£86.00**

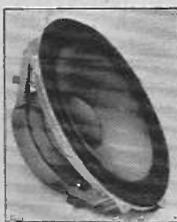

**15" 14A/780 BASS UNIT**

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price **£40.80.**

**OUR PRICE £18.70 + £1.50 p & p + £1.50 p & p Special Offer.**



**950 KIT**

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz. Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00. **OUR PRICE £19.50**



## BUILD YOUR OWN STEREO AMPLIFIER (\*)

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

**£7.64 + 55p. p & p**



## 8 TRACK CARTRIDGE PLAYER (\*)

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound model and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx.

**Yours for only £10.95 + 90p. p & p**



Just write your order giving your credit card number

**DO NOT SEND YOUR CARD**

● Mail orders to Acton. Terms C.W.O.  
All enquires Stamped Addressed Envelope.  
Goods not despatched outside U.K.

● Leaflets available for all items listed thus (\*)  
Send stamped addressed envelope.


**R T V C**

Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG /c  
323 Edgware Road, London W2

Personal Shoppers — Edgware Road: 9a.m.—5.30p.m. Half day Thurs.  
Acton: 9.30 a.m.—5 p.m. Closed all day Wed.

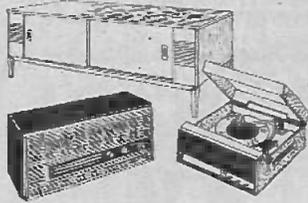The items below are from the March Supplement to our 1974 Catalogue. You can receive this Catalogue and the next 12 supplements by sending 66p.



Stereo Radiogram Cabinet. Long, Low and Modern. Peak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 41" x 15" x 18". Probably cost over £30 to make. Our Price £3-10 each. Carriage £2 per 200 miles. Bush Record Player. Bush Ref. No. SRP 64. Separate bass and treble controls help give this unusually good sound quality. A suitable amplifier/speaker unit converts this to full stereo. Cabinet size 17" x 16 1/2" x 18" deep. Finished in charcoal grey leather cloth. Fully transistorised with 8" x 7" speaker. Controls bass, on/off, treble and volume. Socket stereo. Makers recommended price £27-73. Our Price £17-72. A saving of over 08. Post and insurance £2.

Erres Table Radio. Dutch made. Three wavebands (L.M. & B.) Nice size (16 1/2" x 8 1/2" x 4 1/2") wooden cabinet with high gloss finish. 6" x 4" speaker gives better than average tone—these radios are very well made from good quality components and should not be confused with Hong Kong makes. They recently retailed at £18 each and were well worth it. The ones we have are brand new and working but have failed final inspection because either they will work only on mains or only on batteries. It is unlikely that the fault is very much however and we are arranging for a circuit diagram. Price £8-64 plus £1 post and insurance.

Electric Welder. Big transformer in metal case with carrying handle and control switch, output through very heavy duty terminals. Output volts 1.9-4.25 volts max. 117 amps. normal mains input socket for optional foot switch. £18-50 plus £2 carriage up to 200 miles. A further £1 for each 100 miles extra.

24V 3 amp Mains Transformer. Upright mounting with fixing clamps, standard primary 240/200V, 195/160—£2-50 plus 30p post and service.

Mains Transformer. (6.5v-0-6.5v at 500 mA and 1v at 1 amp). Normal tapped primary. Upright mounting with fixing lugs. £1-00.

Mains Transformer. (18v-37v-80v—41v at 2 amp or this would function at 18v-0-18v). Primary tapped 110, 115, 127, 200, 220 and 240v selected by labelled plug. Primary screen and multi-tapped. Upright mounting with fixing lugs. £2-95.

Midget Two Gangs. Tuning condensers as fitted in many Japanese and Hong Kong radios—probably 40p each section with 1/2" spindle with terminal-less trimmers. Price 35p. With trimmers 50p. Ferrite Rods for aerials, etc. The following type in stock Dia. 1/2", 4" long 15p. 5" long 18p. Dia. 3/16", 5" long 20p. 6" long 25p. 8" long 30p. Dia. 3/8", 4" long 20p. 5" long 25p. 6" long 30p. 7" long 40p. Dia. 1/2", 6" long 35p. Ferrite Stator long x 1/2" x 1/8" x 20p.

Photo Resistor. Mullard type. This drops its resistance from approx. 250 Kohms in dark to only approx. 200 ohms in bright light but it is only quite small, in fact less than 1/2" square with leads coming out of corners on one side. Price 22p. 0-8 Ammeter. 2" square, full vision face for bush mounting—moving iron. Ideal for charger 75p each.

I.F. Transformers. Tuneable around 465 KC. Japanese manufacture as fitted to many Japanese-made portable radios. Three sizes available—

Sub-miniature approx. 1 1/2" x 1 1/2" x 2" high—Miniature approx. 1 1/2" x 2" x 1 1/2" high—Small approx. 9/16" x 1/16" x 1 1/2" and Standard 9/10" x 9/10" x 1 1/2". All at 11p each.

"Smooth flow". Double wound mains transformer, full wave rectifier and overload protection. Completely enclosed in plastic case with output terminals and dex lead—ideal to operate models, drive motors, charge small batteries etc. Price £2-25.

Time Switch. Mains driven 24 hours clock—driving 4 pairs of on/off switches this switch sequence will repeat until re-programmed. Complete in pressed-steel case with glass window in front. Continental make. Price £3-50.

Relay. Clare Elliot. Sealed and wire coded. 675 ohm coil with two pairs change over contacts. Price £1-65.

TERMS:—Add 10% V.A.T.

Send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 20p.

**J. BULL (ELECTRICAL) LTD.**  
(Dept. E.E.)  
102/103 Tamworth Rd.,  
Croydon. CRO 1XX

## INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2-88 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2-88 post paid.

MAIL ORDER ONLY.  
S.A.E. ALL ENQUIRIES.

## DABAR ELECTRONIC PRODUCTS

88a, LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ

## ELECTRONI-KIT

Electronic fun for all ages

THE MOST VERSATILE ELECTRONICS KITS.

All components are beautifully encapsulated in unbreakable transparent plastic blocks. Perfect connections are made WITHOUT SOLDERING, SCREWING OR WIRING.

INCREDIBLE VALUE! Build, dismantle and rebuild projects any number of times and invent your own experiments too.

COMPLETELY SAFE. Instructive and FUN - all kits operate from 9v. battery only.

VALUABLE MANUALS included with every kit. No previous knowledge is required, even with the largest kits.

Kit 2A-30 projects £10.45  
Radios, amplifiers, alarms,  
microphones, etc.

Kit 3A-100 projects £20.45  
As 2A plus electronic  
birds, cat, sirens, organs,  
metronome, quartz light and  
sound, etc.

3ADX-105 projects £25.25  
As 3A plus solar cell  
experiments and complete  
sophisticated control


4ADX-150 projects £33.95  
As 3ADX plus Relay and  
Neter experiments: ion  
concentration, volume,  
output, field intensity,  
volt., resistance meters,  
snooper, illuminometer, etc.

ADD-ON parts and manuals  
available as required.

The three larger kits  
include Electrical  
experiments too.

All prices include Battery, VAT & p. & p.  
Cheque/P.O. (or 6p. for literature) to:

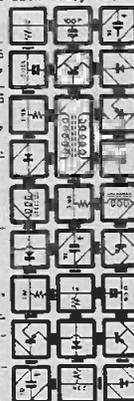Satisfaction guaranteed  
**ELECTRONI-KIT LTD, 408 St. John's Street,  
London, EC1. [01-278 4579]**



### SINCLAIR CALCULATORS

Cambridge Kit £19-95 (£2-25)  
Cambridge Assembled £21-95 (£2-50)  
Executive £27-95 (£3-05)  
Executive with Memory £34-95 (£3-75)  
New Sinclair Scientific £39-95 (£4-25)

### FERRANTI ZN414

IC radio chip with data £1-20 (23p). Also available kit of extra parts to complete a radio £2-39 (40p). Send SAE for free leaflet.

### SINCLAIR PROJECT 30

AFU £6-95 (69p)  
Z40 £5-45 (54p)  
Z60 £8-95 (59p)  
Q16 £7-70 (77p)  
P25 £4-88 (49p)  
P26 £7-98 (79p)  
P28 £7-98 (79p)  
Decoder £7-45 (74p). Trans. for P28 £3-35 (50p).  
Tuner £11-95 (£1-19). Stereo 80 £11-95 (£1-19).  
Project 805 £26-95 (£2-69)  
2 x Z40/Stereo 80/P25 £22-90 (£2-50)  
2 x Z40/Stereo 80/P26 £27-75 (£2-77)  
2 x Z80/Stereo 80/P28/Transformer £33-11 (£3-31)  
Write for our most competitive quotation.



### SINCLAIR GOES QUADRAPHONIC

Introducing the Naxoslex QA10 self-contained matrix quadraphonic synthesizer. Just feed the output of a Project 30 stereo system into it and hook on 4 speakers to obtain the latest experience in sound. Send for free leaflet. Only £9-95 (£1-30).



### SINCLAIR SUPER IC12

6W rms power. With 44 page booklet and printed circuit £2-10 (43p)



### SWANLEY IC TOMORROW £1-80 (40p)

The world's most powerful IC amplifier. Similar to IC12 but rated at 10W r.m.s. power. Supplied with data but no printed circuit. Write for leaflet

### DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-80 (27p). Stereo model with balance control £3-60 (48p)

### IC12 POWER KIT

Supplies 28V 0.5 Amps £2-67 (50p)

### LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1-10 (27p). 5" x 8" 8 ohm £1-53 (37p)

### PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners) Mono model £1-35 (25p). Stereo model £2-40 (35p). Type 2 for ceramic or crystal pickups. Mono 65p (18p). Stereo £1-30 (25p)

### SEND SAE FOR FREE LEAFLET ON KITS

### BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 800 mA £4-15 (70p)



### Other eliminators

stocked:—

50mA:—6V £1-83 (30p). 9V £1-80 (30p). 7 1/2V

cassette type £2-25 (30p). Double 6V + 6V

£2-50 (35p). 9V + 9V £2-50 (35p)

250mA:—3-way switched model giving 6, 7 1/2 and 9V £2-95 (60p).

### S-DECS AND T-DECS

S-DEC £1-98 (31p)

T-DEC £3-63 (47p)

µ-DEC A £3-99 (51p)

µ-DEC B £8-99 (81p)

IC carriers:—

16 dill:—plain 81p (15p). With socket £1-77 (25p)

10 TOB:—plain 78p (15p). With socket £1-68 (24p)

Experiment guides:—A £1-59 (35p). B £1-77 (29p). C 90p (15p). D £2-40 (35p). E £4-20 (53p)



### SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools, etc. welcome. No VAT charged on overseas orders.

# Trannies

4 Bush House,  
Bush Fair, Harlow,  
Essex.

- ★ PRICES INCLUSIVE OF V.A.T.
- ★ Retail Shop open 9 to 5.30 Mon. to Sat.
- ★ Post & Package 15p.

Semiconductors		2N2926	11p	IN4148	6p	200V	48p
AC126	14p	BC183	11p	2N3053	26p	IN5400	16p
AC127	18p	BC184	14p	2N3054	55p	IN5401	17p
AC128	15p	BC212	13p	2N3055	49p	IN5402	19p
AC141K	26p	BC213	13p	2N3702	14p	IN5404	24p
AC142K	26p	BC214	13p	2N3703	13p	IN5406	26p
AC176	18p	BD131	68p	2N3704	14p		
AC187	24p	BD132	90p	2N3705	13p		
AC188	24p	BF194	16p	2N3706	12p	BRIDGE	3 Amp
AC187K	28p	BF195	17p	2N3707	13p	RECTI-	100V
AC188K	28p	BF244	27p	2N3708	11p	FIERS	200V
AD149	49p	BFY50	18p	2N3709	12p	1 Amp	400V
AD161	38p	BFY51	18p	2N3710	12p	100V	22p
AD162	40p	BFY52	17p	2N3711	12p	200V	24p
AF114	20p	MP8111	36p	2N3819	35p	600V	27p
AF115	20p	OC28	50p	40361	55p	THRYIS-	400V
AF116	20p	OC36	50p	40362	55p	TORS	10 Amp
AF117	20p	OC44	16p	40363	69p	1 Amp	99p
BC107	13p	OC45	10p	IN914	8p	50V	29p
BC108	12p	OC71	11p	IN916	8p	100V	32p
BC109	13p	OC81	12p	IN4001	7p	200V	34p
BC147	13p	2N706	14p	IN4002	8p	400V	44p
BC148	13p	2N1131	24p	IN4003	10p	3 Amp	3 to 33
BC149	13p	2N1132	28p	IN4004	11p	50V	39p
BC182	13p	2N2904	20p	IN4006	15p	100V	44p

## Trannies Disco Unit



- Includes
- ★ DJ 100 watt discotheque amp with full mixing & PFL facilities £94.75
  - ★ Stereo headphone with boom microphone £9.90
  - ★ Trannies disco console with 2 Garrard SP25 Mk IV turntables £59.00
  - ★ Pair 50 watt speakers £47.00

Or complete system £189.97 carriage £5.00. Terms available no deposit £10.16 monthly for 24 months. We stock a full range of Disco Equipment send for list, or pay a visit.

## £1 BARGAIN PACKS

- £1 10 Silicon NPN Power transistor (like 2N3055) Below spec.
  - £1 30 Plastic FET's unmarked/untested similar to 2N3819 (random test showed good yield).
  - £1 20 TO5 transistors NPN or PNP State which 2 to 5 amp untested.
  - £1 20 TO18 transistors PNP like BC178, BC179 etc. untested.
  - £1 30 Plastic Power NPN transistor TO220 case like 2N3055 untested.
  - £1 10 General Purpose fully tested FET's.
  - £1 200 mixed capacitors.
  - £1 500 mixed resistors.
- any 5 packs £4.50

We stock a large range of electronic semi-conductors at competitive prices. Our new '74 catalogue is now available at 20p.

A small range from our catalogue.

## Resistors

- ½ watt 5% carbon..... 1p
- ½ watt 5% carbon..... 1p
- 1 watt 10% carbon..... 3p
- range 10 ohms to 4.7 meg-ohms.
- ½ watt m/o 2%..... 4p
- range 10 ohms to 1 megohm

## VEROBOARD

	0-1	0-15
2½ x 3½	24p	19p
2½ x 5	27p	23p
3½ x 3½	27p	23p
3½ x 5	31p	31p
17 x 2½	82p	63p
17 x 3½	£1-10	87p
17 x 5 (Plain)		90p

## Electrolytic Capacitors

6.3 VOLT	16 VOLT	40 VOLT
68µF 6p	220µF 9p	47µF 6p
150µF 6p	680µF 17p	100µF 9p
470µF 11p	1000µF 17p	68µF 10p
680µF 13p	1500µF 25p	220µF 11p
1500µF 18p	2000µF 35p	470µF 18p
2200µF 18p	5000µF 44p	680µF 25p
3300µF 26p		1000µF 25p
		2200µF 44p
10 VOLT		63 VOLT
47µF 6p	10µF 6p	1µF 6p
100µF 6p	22µF 6p	2.2µF 6p
220µF 8p	47µF 6p	4.7µF 6p
330µF 10p	100µF 8p	6.8µF 6p
470µF 10p	220µF 10p	10µF 6p
1000µF 11p	470µF 13p	2.2µF 6p
1500µF 20p	680µF 20p	10µF 6p
2200µF 24p	1000µF 22p	22µF 6p
	2200µF 39p	68µF 10p
	5000µF 68p	100µF 11p
16 VOLT	40 VOLT	150µF 13p
15µF 6p	220µF 19p	220µF 19p
33µF 6p	6.8µF 6p	330µF 22p
150µF 6p	15µF 6p	470µF 26p
150µF 8p	33µF 6p	1000µF 44p

## Mullard Polyester Capacitors

C280 SERIES  
250V P.C. mounting: 0-01µF, 0-015, 0-022 3p, 0-033, 0-047, 0-068 4p, 0-1 6p, 0-15, 0-22 5p, 0-33 7p, 0-47 9p, 0-68 12p, 1µF 14p, 1-5µF 22p, 2-2µF 27p.

C296 SERIES  
400V: 0-001µF, 0-0015, 0-0022, 0-0033, 0-0047 3p, 0-0068, 0-01, 0-015, 0-022, 0-033 3p, 0-047, 0-068, 0-1 4p, 0-15 6p, 0-22 8p, 0-33 12p, 0-47 14p.

# BI-PRE-PAK

## AUDIO BARGAINS STEREO DECODER




£4.95

incl. P. & P. and VAT

A ready built unit, ready for connection to the I.F. stages of existing F.M. Radio or Tuner. A tell tale light can be connected. The unit is a small printed circuit, no further alignment necessary. A L.E.D. is recommended as the indicating light, suitable device available from us at 36p. Instructions included

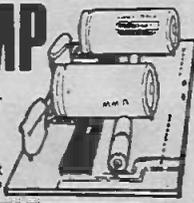
## 3 W.R.M.S. I.C. AMP

only £1.65 incl. P. & P. and VAT  
Order Code I.C.A. 1  
on P.C. Board with all components  
or 2 on one board for £2.85



Order Code I.C.A. 1/5  
These amps. are supplied with a free booklet on connecting up, specifications and easy to build projects using the I.C.A.1

## 5W & 10W AMPS

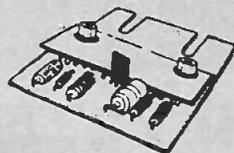

5W ONLY £1.98  
10W ONLY £2.49

incl. P. & P. and V.A.T  
These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2½" x 1½". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the UK. Built and tested.

## Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit .15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain crystal or ceramic pick-up cartridges. £1.21

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. £1.69

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. £1.21

Instruction leaflet supplied with all units. Post and packing and VAT included in prices.


I enclose £..... for..... Decoders/.....  
3W Amps/..... 5W Amps/..... 10W Amps/.....  
Stereo Pre-Amps 1..... Stereo Pre-Amps 2.....  
Stereo Tone Controls.....  
(Please insert quantities and delete those not applicable)  
Name.....  
Address.....

## BI-PRE-PAK

Dept. D, 222/224 West Road,  
Westcliff-on-Sea, Essex SS0 9DF  
Telephone: Southend (0702) 46344  
Ca. Regn. No. 820919

# Sinclair Project 80

exciting

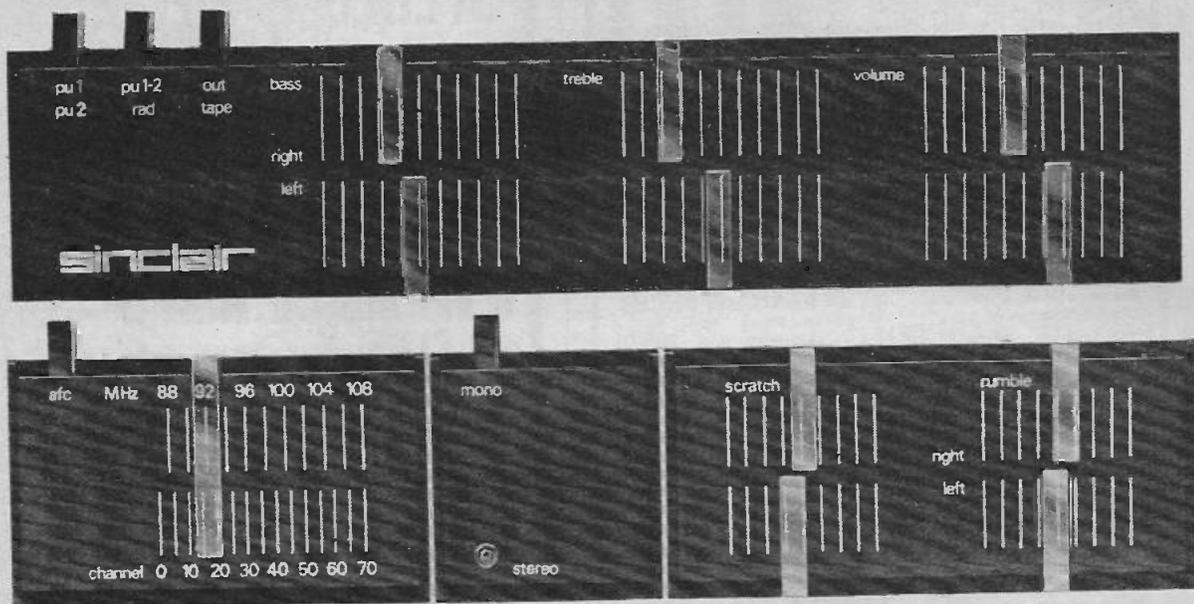


only  $\frac{3}{4}$ " deep x 2" high

Living with hi-fi takes on new meaning with Sinclair Project 80. The electronics of these revolutionary new modules are all contained within elegantly designed matching cases no more than three-quarters of an inch deep. They are designed for mounting on any appropriate flat surface by means of 6BA bolts extending from the rear of each module and which pass through suitably drilled holes. Connections are taken away out of sight in a similar manner. The possibilities opened up by Project 80 are endless – superb hi-fi systems can be installed in ways hitherto only dreamed about and never before made practical. No more cutting out and shaping to put modules in position. A few holes drilled with the aid of templates supplied and the job is done. Now you need never again be faced with problems of keeping the hi-fi from clashing with carefully thought-out furnishing schemes. (That will surely please wives!) Slider controls have been introduced in place of knobs and all modules in the range incorporate new up-dated circuitry with emphasis on performance standards and built-in protection against overload and shorting. The aim was to re-think modular construction completely – to make it infinitely more versatile, even simpler and more reliable – the result – Project 80 – another triumph for Sinclair, and the most exciting construction modules ever.

the slimmest, most elegant hi-fi modules ever made

## Typical Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	£5.45 +54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10.43 +£1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; PZ.6	£30.83 +£3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amp.	2 x Z.60s, Stereo 80; PZ.8	£33.83 +£3.38 V.A.T.
Indoor P.A.	Z.60, PZ.8	£14.93 +£1.49 V.A.T.

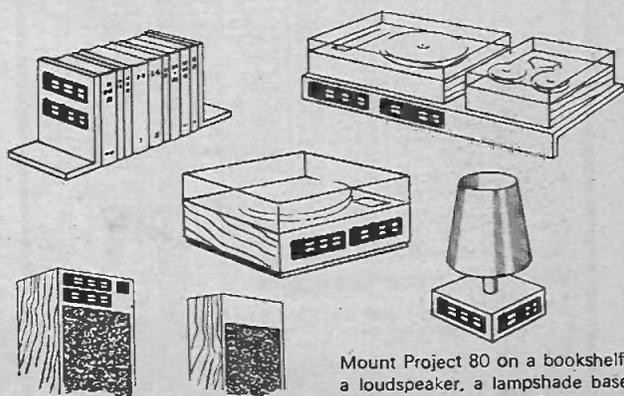


Mount Project 80 on a bookshelf, a loudspeaker, a lampshade base, a false wall with two Q.16 loudspeakers... almost anywhere.

Everyday Electronics, July 1974

Project 80 FM tuner, decoder, and A.F.U. may be added as required

# new thinking in modular hi-fi
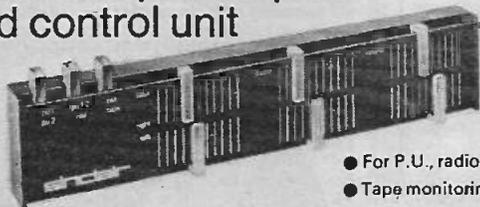
## Stereo 80 pre-amplifier and control unit



- For P.U., radio and tape
- Tape monitoring switch
- Simplest ever fixing


Each channel has its own separate tone and volume controls operated by sliders, enabling ideal environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry that ensures the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

### TECHNICAL SPECIFICATIONS

Size - 260 x 50 x 20mm (10 1/2 x 2 x 3/8 ins)  
 Finish - Black with white indicators and transparent sliders  
 Inputs - Magnetic pick-up 3mV RIAA corrected; Ceramic pick-up 300mV  
 Radio 300mV; Tape 30mV  
 Signal/noise ratio - 60dB  
 Frequency range - 20Hz to 15KHz ± 1dB; 10Hz to 25KHz ± 3dB  
 Power requirements - 20 to 35 volts  
 Outputs - 100mV + AB monitoring for tape  
 Controls - Press button for tape, radio and P.U. Sliders for volume, bass (+ 12dB to - 14dB at 100Hz) treble (+ 11dB to - 12dB at 10KHz)

R.R.P. £11.95 +£1.19 V.A.T.
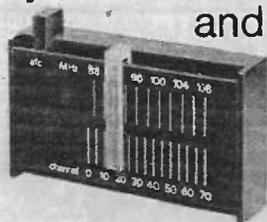
## Project 80 FM tuner and stereo decoder



- Twin dual varicap tuning: 4 pole ceramic filter; switchable A.F.C.
- On the decoder, solid state stereo indicating beacon.

Making the Project 80 F.M. tuner and decoder available separately gives a wider choice of systems and saves money where stereo reception may not be required. The tuner is a triumph of electronic design and assures excellent performance. The decoder gives a 40dB channel separation with 150mV output per channel. Both units may be used with other than Project 80 systems.

### TECHNICAL SPECIFICATIONS OF TUNER

Size - 85 x 50 x 20mm (3 1/2 x 2 x 3/8 ins)  
 Tuning range - 87.5 to 108 MHz  
 Detector - I.C. balanced coincidence for good A.M. rejection  
 One I.C. equal to 26 transistors  
 Distortion - 0.2% at 1KHz for 30% modulation  
 4 pole ceramic filter in I.F. section  
 Aerial impedance - 75 Ω or 240-300 Ω  
 Sensitivity - 4 microvolts for 30dB quieting  
 Output - 300 mV for 30% modulation  
 Power requirements - 23 to 33 volts

### DECODER

Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/8 ins)  
 One-19 transistor I.C.


R.R.P. £11.95 +£1.19 V.A.T.

R.R.P. £7.45 +0.74 V.A.T.

## Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge.
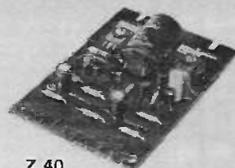
## Z.40 & Z.60 power amplifiers totally short-circuit proof



Z.40



Z.60

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.

### Z.40 TECHNICAL SPECIFICATIONS

Size - 55 x 80 x 20mm (2 1/4 x 3 1/8 x 3/8 ins) 9 transistors  
 Input sensitivity - 100mV  
 Output - 15 watts RMS continuous into 8 Ω (35v)  
 Frequency response - 10Hz - 100KHz ± 1dB  
 Signal/noise ratio - 64dB  
 Distortion - at 10 watts into 8 Ω less than 0.1%  
 Power requirements - 12 to 35 volts


### Z.60 TECHNICAL SPECIFICATIONS

Size - 55 x 98 x 15mm (2 1/4 x 3 7/8 x 3/8 ins) 12 transistors  
 Input sensitivity - 100-250mV  
 Output - 25 watts RMS continuous into 8 Ω (45V).  
 Distortion - typically 0.03%  
 Frequency response - 10Hz to more than 200KHz ± 1dB  
 Signal/noise ratio - better than 70dB  
 Built-in protection against transient overload and short circuiting  
 Load impedance - 4 Ω min; max. safe on open circuit

Z.40 R.R.P. £5.45 + 0.54 V.A.T.; Z.60 R.R.P. £6.95 + 0.69p V.A.T.
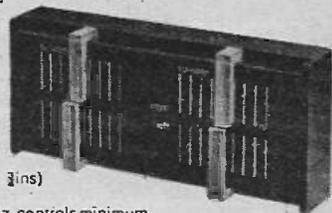
## Project 80 active filter unit

Makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls applied to each channel make it easier to obtain ideal stereo balance.



### TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/8 ins)  
 Voltage gain - minus 0.2dB  
 Frequency response - 36Hz to 22KHz controls minimum  
 Distortion - at 1KHz - 0.03% using 30V supply  
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct. slope  
 LF: cut off (rumble) - 28dB at 20Hz, 9dB/oct. slope

- For scratch and rumble control
- Transistorised active circuitry

R.R.P. £6.95 +0.69 V.A.T.

## Power supply units


### PZ.8

Stabilised. Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 45V.

R.R.P. £7.98 + 0.79p V.A.T.  
 Without mains transformer

PZ.5 30V unstabilised  
 R.R.P. £4.98 + 0.49p V.A.T.

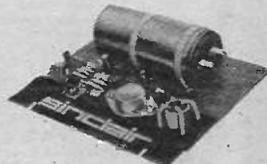PZ.6 35V, stabilised  
 R.R.P. £7.98 + 0.79p V.A.T.



# sinclair

Sinclair Radionics Ltd. London Road, St. Ives, Huntingdon PE17 4HJ  
 Telephone St. Ives (0480) 64646

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid

for which I enclose Cash/Cheque for £ \_\_\_\_\_ including V.A.T.

Name

Address

# Everyday Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p. extra. Semi-display—£6.00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

## EDUCATIONAL

### C AND G EXAM

Make sure you succeed with an ICS home study course for C and E Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecommunications Technicians and Radio Amateurs.

### COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

### TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

#### INTERNATIONAL

#### CORRESPONDENCE SCHOOLS,

Dept 731P, Intertext House, London SW6 4UJ.  
Or Phone 01-822 9911

## FOR SALE

FOR SALE E.E. volume 1, Nos 1-14, Bound volume 2, Nos 1-12. Offers for complete set. Box No. 2.

EVERYDAY ELECTRONICS No. 1 to December 1973: £6 including postage. Apply with stamped addressed envelope.—T. Darby, 85 Lakedale Road, Plumstead, London SE18 1PR.

E.E. from first copy to date in binders, mint condition. Offers, Skillbeck, 12 South Cliff Avenue, Eastbourne (STD 0323) 33280.

## MISCELLANEOUS

### DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ Pocket-sized **MAXI-VOLT** Big 4-inch Spark Generator (instant 15,000 volts). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (85g.) send £1.35 for your Maxi-Volt now!

★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £6.40 for yours now!

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's and parties. 'Brain-freeze' 'em with var-speed stop-motion flashes. Includes super case too. Send £2.40 now!  
(All prices include V.A.T., packing, and postage.)

Send remittance to:

**BOFFIN PROJECTS,**  
4 CUNLIFF ROAD,  
STONELEIGH, EWELL, SURREY  
(Mail order U.K. only)

Or for more details, send 20p for lists, plus free design project sheet.

**LOAD 6V SIRENS** for burglar alarms etc. (New and Boxed) £1.25p. Clockwork motors 16p, Reed switches 8p. Add 10p P.P. List 6p. Grimby Electronics, 64, Tennyson Road, Cleethorpes, Lincs.

**SUPERB INSTRUMENT** cases by Bazelli, manufactured from heavy duty PVC faced steel, choice of 70 types, send for free list: Bazelli Instrument Cases, Dept 24, St. Wilfrid's, Foundry Lane, Halton LA2 6LT, near Lancaster.

### A BONANZA FOR CONSTRUCTORS— B. B. SUPPLIES OFFER

CURLIES, 5ft., 3-core, 15p ea. 4-core, 20p ea. STRAIGHT Cords, 25ft., 4-core, 25p ea. DIODES, Silicon, CV7040 (OA 202), 3" leads 4 for 25p DIALS, (GPO Type), plastic face, metal mech. 30p ea. TRANSISTOR panels, type M4, comprising: 5 BCY34, 4 ACY17, diodes, resistors & capacitors (ex new equipment—rel. long leads) 50p ea. INTRODUCTION OFFER: 1 of each above plus surprise item for £1.25c (offer ends 31-7-74) MONEY back guarantee—prices inc. VAT and pp. ORDERS or SAE for complete list!

38, HEATHWOOD GARDENS SWANLEY  
KENT BR8 7HN

**CONSTRUCTION AIDS.** Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit board-masters, negatives and boards, one-off or small numbers. Send 6p for list. **RAMAR CONSTRUCTOR SERVICES,** 29 Shelbourne Road, Stratford-on-Avon Works.

**AMAZING OFFER!** **ELECTRIC SOLDERING GUN** WITH BUILT IN TRANSFORMER



This Soldering Gun is a MUST for D.I.Y. Men, Motorists, Mechanics, etc. A rugged, strong construction that will last a lifetime. Now you can do all those repairs that would normally cost you 4's at any electrical shop. Voltage 240 AC, 50c/s. LIMITED QUANTITY AVAILABLE. Similar product sells at £4.50. C.W.O. Immediate despatch. Refund if not delighted.

V.G.S. INTERNATIONAL (SGE10)  
Pickworth, Sleaford, Lincolnshire.

**BEGINNERS**, we exist for you. Instruction, components, constructional kits. Send S.A.E. to **Electrolern**, Lyburn Lodge, Nomanland, Wiltshire.

#### FERRIC CHLORIDE

Anhydrous technical quality in sealed bags 1lb 35p (20p), 5lb £1.32 (30p), 10lb £3.85 (60p).

#### COMPUTER PANELS

51ba asstd. panels £1-10 (30p), 71b £2-20 (40p), 561b £14 (£2), 12 high quality panels with trim pots, IC's, power transistors etc. £2-20 (30p), 100 panels £13 (£1). Pack of boards containing at least 500 components inc. at least 50 transistors 66p (20p).

#### DEKATRON UNITS

Contain 2x CV2271 dekatrons, 2 4-dig. resettable counters, 2 sealed relays, R's, c's etc. Only £1-70 (30p).

#### 3W TAPE AMPLIFIERS

2X ECC83, EL84, EZ80 on 12 x 5 x 3" chassis with tone and volume controls. 3 watts output to 7 x 4" 3 Ω speaker (provided) £2-59 (50p). Or in case 14 x 13 x 9" with non-standard tape deck £2-59 (£1). Suitable cassette £1-10, tape 75p, head 30p.

#### "HOT WHEELS" MODEL GARAGE

Contains 1-7V @ 1A transformer (can be modified to give up to 10V output) lamp, switch, jack plug etc. ONLY £1-65 (30p).

#### 71b BARGAIN PARCELS


Hundreds of new resistors, capacitors, pots, switches, + PC boards with transistors and diodes and loads of odds and ends. Still only £1-12 (40p). New 8 x 4" Q speakers £1-10 pr (20p). 500 asstd. resistors £1-10 (20p). 150 mica, ceramic, poly caps 66p (14p). All prices include V.A.T. SAE list, enquiries.

### GREENWELD ELECTRONICS [EE4]

51 Shirley Park Rd. SOUTHAMPTON,  
TEL 0703 72581. Callers only at 38 Lower Addiacombe Road, Croydon.

**RADIO & TELEVISION AERIAL BOOSTERS** £2.95p, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7-50, carr. £1-50p. S.A.E. for 3 leaflets. **ELECTRONIC MAIL ORDER (BURY) LTD.**, Bridge Street, Ramsbottom, Bury, Lancs.

## LOUDSPEAKERS

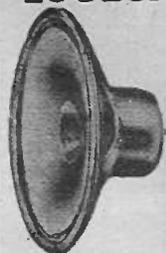

Speakers, kits and cabinets for D.I.Y., Hi Fi, P.A., Disco, etc. by EMI, Fane, Goodmans, Baker, Elac, Richard Allan, Wharfedale, etc. Send for free booklet "Choosing a speaker"

### WILMSLOW AUDIO

Dept. H, Swan Works, Bank Square,  
Wilmslow, Cheshire SK9 1HF  
Tel. Wilmslow 29599

## RECEIVERS and COMPONENTS

**KITS FOR THE Everyday Electronics Buzzer** £1. Balanced armature Earpieces 25p, MLK034CN/S Lever Keys £1-06. Chris Smith Components, 31 Priory, Neston, Wirral, Cheshire.

3 ASS. M.C. METERS 2-3" £1-15 (27p). WIRE ENDED NEONS 10-50p (10p). COPPER CLAD PAX. PANELS 6 1/2" x 5 1/2" 4-8p c.p. 7 1/2" x 9" 8-£1-25 c.p.

T.V. CONVERGENCE PANELS 2 x AC 128, 3 slugged coils, 3 slide switches, 11 w.w. pots, 3 carbon presets, 2 ferrite chokes etc. £1-10 c.p. VALUPAKS P9 100 p/mica caps 65p c.p. Send 10p for lists of others plus panels etc. Refund on purchase.

128 ASSORTED COMPONENTS £1-85 c.p.

31B ASSORTED PANELS £1-85 c.p.

J. W. B. RADIO  
2 Barnfield Crescent, Sale, Cheshire M33 1N L  
Postage in brackets Mail order only

**COMPONENTS GALORE.** Pack of 500 mixed components manufacturers surplus plus once used. Pack includes Resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p. and p. c.w.o. to **CALEDONIAN COMPONENTS**, Strathore Road, Thornton, Pife.

### ELECTRONIC COMPONENTS WATFORD

Visit our Warehouse for your requirements of Resistors, Capacitors, Transistors, SCR's, Speakers, Metal Boxes, Headphones, Intercoms, Meters, Audio Cables, Cartridges, Microphone, wide range of Plugs & Sockets etc., etc.

**HILLS COMPONENTS LTD.**  
Units 8, Melnita Industrial Estate,  
Brixton Road,  
Watford, Herts.

Telephone: Watford 27711

**SPECIAL PACK** of components, 25 resistors, 10 diodes, 20 capacitors, all tested and guaranteed. Also contains 20 transistors, untested manufacturers rejects. Send 50p to **Telelectronics**, 6 The Grassing, Carlisle.

### SERVICE SHEETS

**SERVICE SHEETS** for Televisions, Radios, Transistors, Record Players, Tape Recorders, etc., from 5p with free Fault-Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

# Marshall's

A. Marshall (London) Ltd.  
42 Cricklewood Broadway London NW2 3HD Telephone 01-452 0161/2 Telex 21492  
& 65 Bath Street Glasgow G2 2BX Telephone 041-332 4133

Everything you need is in our  
New Catalogue  
available now price 20p  
(100 pages of prices and data)  
Call in and see us 9-5.30 Mon-Fri  
9-5.00 Sat  
Trade and export enquiries welcome

## Popular Semiconductors

2N456	0-75	2N3711	0-11	AF116	0-25	BC338	0-13	BU104	1-42
2N456A	0-75	2N3712	0-96	AF117	0-20	BCY30	0-43	BU105	2-25
2N457A	1-35	2N3713	1-20	AF118	0-50	BCY31	0-52	C106A	0-46
2N490	3-16	2N3714	1-33	AF124	0-24	BCY32	1-15	C106B	0-55
2N491	3-58	2N3715	1-50	AF125	0-20	BCY33	0-34	C106D	0-63
2N492	3-99	2N3716	1-80	AF126	0-19	BCY34	0-37	C106E	0-43
2N493	4-20	2N3717	2-20	AF127	0-20	BCY38	0-53	CA3020A	1-80
2N696	0-15	2N3772	1-80	AF139	0-39	BCY39	1-05	CA3046	0-70
2N697	0-15	2N3773	2-65	AF170	0-25	BCY40	0-67	CA3048	2-11
2N698	0-25	2N3779	3-15	AF172	0-25	BCY42	0-15	CA3089E	1-96
2N699	0-29	2N3790	2-42	AF176	0-55	BCY58	0-23	CA3090Q	4-23
2N706	0-16	2N3791	2-35	AF179	0-45	BCY59	0-22	LM301A	0-48
2N706A	0-18	2N3792	2-69	AF180	0-50	BCY70	0-17	LM304A	2-03
2N708	0-14	2N3794	0-10	AF186	0-40	BCY71	0-22	LM309K	1-83
2N709	0-38	2N3819	0-37	AF200	0-35	BCY72	0-13	LM702C	0-75
2N711	0-30	2N3820	0-38	AF239	0-51	BCY87	3-54	LM709 T099	0-48
2N718	0-29	2N3832	1-42	AF240	0-72	BCY88	2-42		
2N718A	0-49	2N3900	0-21	AF279	0-54	BCY89	0-97	8D1L	0-38
2N720	0-50	2N3901	0-32	AF280	0-54	BD115	0-75	14D1L	0-33
2N721	0-55	2N3903	0-24	AL102	0-75	BD116	0-75	LM723C	0-75
2N914	0-22	2N3904	0-27	AL103	0-70	BD121	0-75	LM741 T099	0-48
2N915	0-741	2N3905	0-24	BC110	0-18	BD123	0-32		
2N918	0-47	2N3906	0-27	BC109	0-15	BD124	0-67	8D1L	0-46
2N923	0-30	2N4036	0-63	BC109	0-19	BD131	0-40	14D1L	0-38
2N1302	0-19	2N4037	0-42	BC113	0-13	BD132	0-50	LM747	1-00
2N1303	0-19	2N4058	0-16	BC115	0-15	BD135	0-43	LM7488DIL	
2N1304	0-24	2N4059	0-09	BC116	0-15	BD136	0-49		
2N1305	0-24	2N4060	-0-11	BC116A	-0-18	BD137	-0-35	14D1L	0-73
2N1306	0-33	2N4061	-0-11	BC117	-0-21	BD138	-0-43	MC1303P	1-26
2N1307	0-22	2N4062	-0-11	BC118	-0-18	BD139	-0-71	MC1310	1-26
2N1308	0-25	2N4126	0-20	BC119	0-29	BD140	0-81	MC1458CP1	
2N1309	0-36	2N4289	0-13	BC121	0-23	BDY20	1-05		
2N1671	1-44	2N4919	0-84	BC125	0-15	BF115	0-25	MJ480	0-70
2N1671A	1-54	2N4920	0-99	BC125	0-20	BF116	0-23	MJ481	1-14
2N1671B	1-72	2N4921	0-73	BC132	0-30	BF117	0-43	MJ490	0-98
2N1671C	4-32	2N4922	0-84	BC134	0-18	BF119	0-58	MJ491	1-38
2N1711	0-45	2N4923	0-83	BC135	-0-11	BF121	-0-25	MJE340	0-42
2N1907	5-50	2N5172	0-12	BC136	0-15	BF123	0-27	MJE2955	1-12
2N2102	0-50	2N5174	0-22	BC137	0-15	BF125	0-25	MJE3055	0-88
2N2147	0-70	2N5175	0-26	BC138	0-24	BF152	0-20	MP8111	0-32
2N2148	0-94	2N5176	0-32	BC140	0-34	BF153	0-32	MP8113	0-47
2N2160	0-60	2N5190	0-32	BC141	0-23	BF158	0-23	MP1102	0-40
2N2192	0-40	2N5191	0-95	BC142	0-23	BF158	0-23	MP1102	0-39
2N2192A	0-40	2N5192	1-24	BC143	0-21	BF159	0-27	MPSA05	0-25
2N2193	0-40	2N5195	1-46	BC145	0-21	BF160	0-23	MPSA06	0-26
2N2194	0-61	2N5245	0-43	BC147	0-12	BF161	0-42	MPSA55	0-26
2N2194A	0-73	2N5257	0-49	BC148	0-13	BF163	0-32	MPSA58	0-27
2N2194B	0-30	2N5458	0-43	BC149	0-42	BF165	0-30	NE555V	0-96
2N2194C	0-60	2N5459	0-49	BC153	0-10	BF167	0-21	NE560	4-48
2N2219	0-45	40361	0-48	BC154	0-18	BF173	0-24	NE561	4-48
2N2219A	0-60	40362	0-50	BC157	0-14	BF177	0-29	NE565A	4-48
2N2220	0-45	40363	0-61	BC158	0-13	BF178	0-35	OC23	2-56
2N2221	0-40	40334	0-49	BC159	0-14	BF179	0-43	OC28	0-78
2N2221A	0-40	40335	0-56	BC160	0-14	BF180	0-37	OC35	0-80
2N2222	0-50	40406	0-65	BC167B	0-13	BF181	0-34	OC42	0-35
2N2222A	0-50	40406	0-44	BC168B	0-13	BF182	0-40	OC45	0-32
2N2368	0-31	40407	0-33	BC168C	0-11	BF183	0-40	OC71	0-12
2N2369	0-37	40408	0-50	BC169B	0-13	BF184	0-30	OC72	0-13
2N2369A	0-41	40409	0-49	BC170	0-13	BF185	0-17	OC81	0-26
2N2646	0-77	40410	0-52	BC170	0-19	BF189	0-18	OC83	0-30
2N2647	1-12	40411	2-25	BC171	0-13	BF195	0-17	ORP12	0-50
2N2904	0-55	40414	3-55	BC172	0-11	BF196	0-15	SC35D	1-68
2N2904A	0-70	40430	0-85	BC182	0-12	BF197	0-15	SC36D	1-46
2N2905	0-45	40583	0-23	BC182L	0-12	BF198	0-18	SC40D	1-89
2N2905A	0-56	40601	0-67	BC183	0-09	BF199	0-18	SC41D	1-32
2N2906	0-31	40602	0-56	BC183L	0-09	BF200	0-40	SC45D	1-89
2N2906A	0-37	40603	0-53	BC184	0-11	BF225J	0-19	SC46D	1-98
2N2907	0-40	40604	0-56	BC184L	0-11	BF237	0-22	SC50D	2-30
2N2907A	0-45	40636	1-10	BC186	0-25	BF238	0-22	SC51D	2-69
2N2924	0-14	40669	1-90	BC187	0-27	BF244	0-16	SL414A	1-80
2N2925	0-11	40673	1-12	BC193	0-12	BF250	0-33	SL623	0-59
2N3053	0-32	AC1107	0-25	BC208	0-11	BF246	0-43	TA A263	0-10
2N3054	0-60	AC113	0-16	BC212K	0-10	BF247	0-23	TA A350	2-10
2N3055	0-75	AC117	0-20	BC212L	0-16	BF254	0-16	TA A621	2-03
2N31390	0-28	AC126	0-25	BC214L	0-21	BF255	0-17	TA A661B1	3-2
2N3391	0-23	AC127	0-25	BC237	0-09	BF257	0-46	TAD100	1-50
2N3391A	0-29	AC128	0-25	BC238	0-06	BF259	0-59	Filler	0-25
2N3392	0-13	AC151V	0-14	BC239	0-09	BF259	0-59	TA A271	0-64
2N3393	0-13	AC152V	0-17	BC281	0-20	BF251A	2-30	TBA641B	2-25
2N3394	0-13	AC153	0-25	BC252	0-18	BF258	0-92	TBA800	1-50
2N3402	0-18	AC153K	0-25	BC253	0-23	BF561	0-27	TBA810	1-50
2N3403	0-18	AC154	0-20	BC257	0-09	BF598	0-29	TIL209	0-35
2N3440	0-16	AC176	0-18	BC258	0-06	BF599	0-30	TIP29A	0-49
2N3441	0-97	AC176K	0-25	BC259	0-13	BF630	0-25	TIP30A	0-58
2N3442	1-69	AC187K	0-23	BC261	0-20	BF44X	2-33	TIP31A	0-82
2N3414	0-10	AC188K	0-34	BC262	0-18	BFX63	2-48	TIP32A	0-74
2N3415	0-10	AC189	0-24	BC263	0-23	BFX68	0-30	TIP33A	1-01
2N3416	0-16	AC191	0-27	BC300	0-12	BFX84	0-24	TIP34A	1-51
2N3417	0-21	AC192	0-32	BC301	0-34	BFY20	0-20	TIP34A	1-51
2N3638	0-15	AC192	0-26	BC302	0-29	BFX87	0-25	TIP35A	2-30
2N3638A	0-15	AC192	0-20	BC303	0-54	BFX88	0-25	TIP36A	3-70
2N3639	0-17	AC193	0-42	BC307	0-10	BFX89	0-45	TIP41A	0-79
2N3641	0-17	AD142	0-50	BC307A	0-10	BFY18	0-35	TIP42A	0-90
2N3702	0-11	AD143	0-45	BC308	0-09	BFY19	0-35	TIP295S	0-83
2N3703	0-12	AD189V	0-45	BC309A	0-10	BFY20	0-35	TIP305S	0-60
2N3704	0-14	AD150	0-53	BC308B	0-09	BFY29	0-29	TIP305S	0-60
2N3705	0-12	AD161	0-45	BC309	0-10	BFY50	0-23	TX300	0-12
2N3706	0-09	AD162	0-45	BC309A	0-10	BFY51	0-19	ZTX302	0-20
2N3707	0-13	AD161	pr	BC309B	0-10	BFY52	0-21	ZTX500	0-15
2N3708	0-17	AD162	1-05	BC237	0-21	BFY53	0-16	ZTX502	0-17
2N3709	0-11	AC109R	0-41	BC238	0-19	BFY90	0-60	ZTX502	0-17
2N3710	0-12	AF115	0-24	BC337	0-19	BFY93	0-40	ZTX530	0-21

**New from Siemens**  
7 segment 4 digit Decimal Display  
Liquid Crystal Type AN 413: Complete  
with data. From stock now. Price £13.00  
complete with holder. Ideal for battery  
operated Quartz clock using two of the  
latest CMOS ICs from Solid State  
Scientific. 15v battery operated, minimum  
of discrete components required.  
Send SAE for details.

**Seven Segment Read Out**  
Minitron 3015F £1-55  
DL707 Litronix £2-35  
All data in our new catalogue price 20p  
**Printed Circuit Marker Pen**  
DALO 33PC - complete with instructions.  
No masking! No mess! Red or blue  
Price 87p

**400mW Zeners 3.3v to 4.3v**  
New low price 1p each £8.20 for 100

A large selection of heatinks for all types  
of transistors from Redpoint, in stock now  
T05-6p T018-7p  
6W1-6" x 4" drilled £1.00  
4W1-4" x 4" drilled £0.80  
2W1-2" x 4" drilled £0.45

Resistor	W	Price	Tantalum	Capac	Price
1/8	5%	1p	Value	14p	
1/4	5%	1-5p	Value	14p	
1/2	5%	2p	22/35v	14p	
1	10%	2-5p	47/35v	14p	
2	10%	6p	1p/35v	14p	
2 1/2	5%	7p	2-2/35v	14p	
5	5%	9p	4-7/35v	18p	
10	5%	10p	2-2/16v	14p	

**Veroboard Largest stockist**

	Copper	Plain
-15	-1	-15
2-5x3%	20	28
2-5x5	30	30
3x3x3%	30	30
3x5x5	35	34
2x1x7	67	89
3x4x7	95	121
76	69	

trade or retail supplied

**Thermistors**  
Multard E2980D Series 12/p  
E2980E Series 10p  
Neg Temp Coef VA1000 Series 20p  
R53 £21-20  
Full details of ranges in our catalogue 20p

**Equivalents Books**  
Transistors 90p  
ICs 70p

**Veropins** -1 -15 Face Cutter 46p  
36pcs 24 24 Insertion Tools 64p  
200pcs 89 92

Full range of Carbon and  
Wirewound resistors avail-  
able.

## Integrated Circuits

TTL (SN 7400 Series)			
Type	Price	Type	Price
SN7400	20p	SN7432	45p



GIRO NO. 331 7056  
 C.W.O. only. P. & P. 10p on orders below £5  
 Discount: £10-10%, £20-15% (except net items)  
 Export Order enquiries welcome (VAT free)  
 Official Orders accepted from  
 Educational & Government Departments  
**ALL PRICES INCLUDE VAT**

**SPECIAL RESISTOR KITS** (Prices include post & packing)  
 10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 370 (CARBON FILM 5%), £3-65 net  
 10E12 4W KIT: 10 of each E12 value, 22 ohms—1M, a total of 370 (CARBON FILM 5%), £3-85 net  
 25E12 1W KITS: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8-35 net  
 25E12 4W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8-45 net  
 20E12 1W KIT: 20 of each E12 value, 22 ohms—2M2, a total of 1220 (METAL FILM 5%), £11-05 net  
 15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £13-35 net  
 10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £17-35 net

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
 250V P.C. Mounting: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 3p, 0-068µF, 0-1µF, 4p, 0-15µF, 6p, 0-22µF, 8p, 0-33µF, 12p, 0-47µF, 15p, 1-2µF, 23p, 2-2µF, 26p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
 400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 23p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3p, 0-047µF, 0-068µF, 0-1µF, 4p, 0-15µF, 6p, 0-22µF, 8p, 0-33µF, 12p, 0-47µF, 14p.  
 160V: 0-01µF, 0-015µF, 0-022µF, 3p, 0-047µF, 0-068µF, 3p, 0-1µF, 4p, 0-15µF, 5p, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 8p, 0-68µF, 12p, 1µF, 14p.

**MINIATURE CERAMIC PLATE CAPACITORS**  
 50V: (pP) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, 10µF 0-01, 0-015, 0-022, 0-033, 0-047, 23p, each, 0-1, 30p, 44p.

**POLYSTYRENE CAPACITORS 160V 5%**  
 (pP) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p, 6800, 10,000, 44p.

**RESISTORS**

W. Type	Range	1-99	100-499	500-999	1000+	Size mm
CF	22-1M	1	0-75	0-60	0-55	2-4x7-5
CF	22-1M	1	0-75	0-60	0-55	3-9x10-5
CF	22-1M	1	0-75	0-60	0-55	5-5x16
MF	10-2M7	2	1-54	1-32	1-1	3x7
MF	10-2M2	2	1-43	1-21	0-99	4-2x10-8
MF	10-10M	3	1-98	1-81	1-65	6-6x13
MF	10-10M	4-5	3-52	3-08	2-75	8x17-5

For value mixing prices, please refer to our catalogue. (price in pence each)  
**VALUES AVAILABLE—E12 Series only. (Net prices above 100.)**

**PRESET SKELETON POTENTIOMETERS**

MINIATURE 0-25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω.  
 SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 5p each

**B. H. COMPONENT FACTORS LTD.**

(E.E.) 61 CHEDDINGTON ROAD, PITSTONE,  
 NR. LEIGHTON BUZZARD, BEDS., LU7 9AQ  
 Tel.: Cheddington 688446 (Std. Code 0296)  
**PLEASE WRITE FOR FREE CATALOGUE**

**Miniature Mullard Electrolytics**

1-0µF 63V 64p	68µF 63V 12p
1-5µF 63V 64p	100µF 10V 64p
2-2µF 63V 64p	100µF 25V 64p
3-3µF 63V 64p	100µF 63V 14p
4-7µF 63V 64p	150µF 16V 64p
6-8µF 63V 64p	150µF 63V 15p
10µF 16V 64p	220µF 6-4V 64p
10µF 25V 64p	220µF 10V 64p
10µF 63V 64p	220µF 16V 8p
15µF 16V 64p	220µF 63V 21p
15µF 63V 64p	330µF 16V 12p
16µF 40V 64p	330µF 63V 25p
22µF 25V 64p	470µF 6-4V 9p
22µF 63V 64p	470µF 40V 20p
32µF 10V 64p	680µF 16V 15p
32µF 16V 64p	680µF 40V 25p
32µF 40V 64p	1000µF 16V 20p
32µF 63V 64p	1000µF 25V 25p
47µF 10V 64p	1500µF 6-4 13p
47µF 25V 64p	1500µF 16V 25p
47µF 63V 8p	2200µF 10V 25p
68µF 16V 64p	3300µF 6-4 26p

**VEROBOARD 0-1 0-15**

24 x 5"	28p 28p
24 x 3 1/2"	26p 19p
38 x 5"	32p 33p
38 x 3 1/2"	28p 28p
24 x 5" (Plain)	7p
24 x 3 1/2" (Plain)	14p
5 x 3 1/2" (Plain)	12p
Insertion tool	59p 59p
Tracer Cutter	44p 44p
Pins, Pkts. 25	10p 10p

**TRANSISTORS**

AC127 16p	BC112L 12p
AC128 22p	BC131L 12p
BC107 11p	BC214L 17p
BC108 12p	OC44 18p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	T1543 33p
BC183L 12p	2N2976 11p
BC184L 13p	2N3702 11p

**POTENTIOMETERS**

Carbon Track 5K Ω to 2M Ω, log or lin. Single, 16p Dual Gang 46p, Log Single with switch 26p  
 Slider Pots. 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 35p.

**DIODES**

IN4001 64p	DIN 2 Pin 12p
IN4002 71p	3 Pin 13p
IN4003 9p	5 Pin 180° 15p
IN4004 94p	Std. Jack 14p
IN4005 12p	2.5mm Jack 11p
IN4006 14p	Phone 51p
IN914 7p	
IN916 7p	
BA100 10p	
OA5 42p	
OA47 9p	
OA81 11p	
OA200 8p	

**SOCKETS**

DIN 2 Pin 10p
3 Pin 10p
5 Pin 180° 12p
Std. Jack 14p
2.5mm Jack 11p
Phone 51p

**ELECTROLYTIC CAPACITORS. Tubular & Large Cans**

(µF/V): 1/25, 2/25, 4/25, 4-7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 80p, 2000/25, 30p, 2000/100, 50p, 2500/25, 38p, 2500/50, 62p, 3000/50, 80p, 5000/25, 66p, 5000/50, £1-10.

**HI-VOLT: 4/450, 14p, 8/350, 19p, 8/450, 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/350, 60p.**

**METALLISED PAPER CAPACITORS**

250V: 0-05µF, 0-1µF, 6p, 0-25, 6p, 0-5µF, 7p, 1µF, 9p, 500V: 0-025, 0-05, 6p, 0-1, 6p, 0-25, 7p, 0-5, 9p, 1000V: 0-01, 11p, 0-022, 13p, 0-047, 0-1, 15p, 0-22, 23p, 0-47, 25p.

**NEW KIT**

SE12½W Metal Film 5% Ultra Low Noise New Resistors with full colour coding, 5 each E12 value 10ohm—1M total 305 £2-75 Net.

**A SPARK OF GENIUS**



**THE SPARKRITE MK2 ELECTRONIC IGNITION KIT**

WHEN COMPLETE THE SYSTEM CAN BE FITTED IN ONLY 15 MINUTES TO GIVE—

Instant all weather starting, up to 20% fuel saving, longer battery life, higher top speed, faster acceleration, spark plugs last about 5 times longer, misfire due to contact breaker bounce electronically eliminated, purer exhaust emission resulting in less air pollution, Contact breaker burn eliminated (suitable for petrol engined cars up to 8 cylinders).

**PRICE ONLY £11.62**

Ready built £14.85 (State + or - earth)


We can supply a Sparkrite Ignition (ready built) to fit all petrol engined vehicles (boats, motor cycles etc) with coil and contact breaker ignition prices on application.

**ORDER NOW FROM:**

SEND S.A.E. FOR FULL BROCHURE, OR CALL FOR DEMONSTRATION BETWEEN 9 AND 5.30 WEEKDAYS, AND 10-4 SATURDAY. TRADE ENQUIRIES WELCOME.

**ELECTRONICS DESIGN ASSOCIATES (DEPT E.E.7)**  
 82, BATH STREET  
 WALSALL WS1 3DE  
 Phone: WALSALL 33652

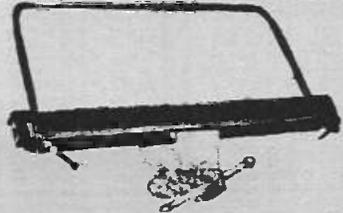**PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS**



With Bevelled Former Bars


No. 1. Capacity 18 gauge mild steel x 36in. wide ... £21-00 carr. free  
 No. 2. Capacity 18 gauge mild steel x 24in. wide ... £15-00 carr. free  
 No. 3. Capacity 16 gauge mild steel x 18in. wide ... £15-00 carr. free

Also new bench models. Capacities 36in. x 18 gauge £40-00 24 in. x 16 gauge £38-00. Carriage free. Add 10% VAT to total price of machine. End folding attachments for radio chassis, tray and box making. Steel angle 36" model, 40p per ft. Other models 30p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

**A. B. PARKER, Folding Machine Works,  
 Upper George St., Heckmondwike, Yorks. Heckmondwike 403997**

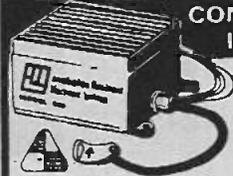**CONTACTLESS ELECTRONIC IGNITION BY MOBELEC**



We break the price barrier with this trouble-free inductive discharge contactless ignition which replaces contact points by a solid-state trigger-head giving high energy spark for excellent cold-weather starting and super-smooth tick-over. Designed for 4 or 6 cylinder neg. earth cars at a price you can afford. Easy to fit, clear illustrated instructions, free fitting kit. State model, make and year. Other Mobelec capacitive discharge E series models available. Mobelec E series for high performance engines. 4 & 6 cylinder NEG. AND POS. EARTH. £22.82. 8 cyl. £24.75. Post free.

**FROM ONLY £13.95 p&p 25p**

**SILHILL PRODUCTS**

Dept EE/6 226 Mary Street, Birmingham B12 9RJ. Tel: 021-440 3600.

# FREE!

## Over 150 ways to engineer a better future

**HIGHER PAY**      **A BETTER JOB**

**SECURITY**

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T., Dept. BEE1, Aldermaston Court, Reading RG7 4PF.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.** Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



**CUT OUT THIS COUPON**

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers—	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineers Designers (A.M.I.E.D.) General Draughtsmanship	<input type="checkbox"/> A.B.T. Clerk of Works Construction Surveyors Institute—I.C.S.I. CITY & GUILDS General Building (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities Estimates Hydraulics Structural Eng.
<input type="checkbox"/> A.M.S.E. (Mech.)	<input type="checkbox"/> Elec. Draughtsmanship	<input type="checkbox"/> Architectural Draughtsmanship
<input type="checkbox"/> Institute of Engineers & Technicians (A.M.E.)	<input type="checkbox"/> Drawing	<input type="checkbox"/> RADIO & TELECOMMUNICATIONS CITY & GUILDS. Radio, TV, Electronics
<input type="checkbox"/> CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding	<input type="checkbox"/> Gen. Diesel Eng. Sheet Metal Work Eng. Inspection Eng. Metallurgy	<input type="checkbox"/> CITY & GUILDS. Telecons. Gen. Radio & TV Eng. Radio Amateurs Exam Radio Servicing TV Servicing Colour TV
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers—	<input type="checkbox"/> A.M.S.E. (Elec.) CITY & GUILDS Gen. Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng. Practical Radio & Electronics (With kit)	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Acctnts. Computer Programming Works M'nt. Work Study Gen. Production Eng. Estimating & Planning Stockkeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I.I. MAA TMI CITY & GUILDS Auto Eng. Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage M'nt. A.R.S. Aero Engineering Certs. Gen. Aero Eng.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers—	<input type="checkbox"/> A.M.S.E. (Civ.) Institute of Building—L.I.O.B.	<input type="checkbox"/> G.C.E. — choose from 58 'O' & 'A' level subjects.

*Coaching for many exams, including C & C*

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BEE1      QN      BEE01  
Aldermaston Court, Reading RG7 4PF

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
OTHER SUBJECTS \_\_\_\_\_  
AGE \_\_\_\_\_

Accredited by C.A.C.C.      Member of A.B.C.C.  
**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Published approximately the third Friday of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 4AD. Printed in England by Index Printers Ltd., Donstable, Beds. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/Sia) Ltd. South Africa—Central News Agency Ltd. Publisher's Subscription Rate (including postage): For one year to any part of the world £2.95. Everyday Electronics is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade, at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# Henry's

DON'T RELY ON YOUR MEMORY  
BUY NOW AT BARGAIN PRICES  
Hi Fi and Transistors - Up to date  
Brochures on request

**HENRY'S CATALOGUE**  
Due to rapid price changes, shortages of paper and raw materials, all prices in the existing catalogue are no longer valid. Call or phone for latest prices. A new catalogue will be available for Aug/Sept. 1974.

## BUILD THE TEXAN

20 + 20 WATT IC STEREO AMPLIFIER

As featured by Practical Wireless 1972



You pay less VAT with Henry's Low Prices

Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6 IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as in kit form. HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE RELIABILITY AND EASE OF CONSTRUCTION FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner. Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21 30p. Distributed by Henry's throughout UK. FREE—Teak cabinet with complete kit.

Kit price **£28.50** (+VAT+50p carr./packing) or built and tested **£35.00** (+VAT + 50p carr./packing) as illustrated.

## BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise IF stages, LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe.



Kit price **£21.00** (+VAT) or built and tested **£24.95** (+VAT)

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S ALL POST PAID LESS THAN 1/4 REC. PRICES COMPLETE WITH LIBRARY CASES

3 for	6 for	10 for	25 for
C 60 £1.10	£1.98	£3.00	£7.40
C 90 £1.46	£2.80	£4.60	£11.25
C 120 £1.80	£3.45	£5.45	£13.45

Quantity and trade enquiries, invited  
LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian £1.36 per course. £5 for any 4.



## EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98.50**  
As above but with Slider Controls **£118.50**  
100 watt amplifier for above **£49.50**  
SDLS 100 watt mixer/amplifier with slider controls **£69.00**  
RS50 50 watt mixer/amplifier **£49.50**  
R100 100 watt mixer/amplifier **£57.50**  
DISCO AMP 100 watt mixer/amplifier Northcourt: **£73.00**  
400 40 watt mixer/amp **£37.50**  
800 80 watt mixer/amp **£45.00**  
DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers)  
SDLI (roary controls) **£49.50**  
SDLI (slider controls) **£58.50**  
DISCO VOX (slider controls) the complete disco preamp **£72.00**  
DJ100 100 watt power amplifier for above **£49.50**  
DJ30L Mk II 3 channel 3kw sound to light **£36.00**  
DJ30L Mk III slider controls **£45.50**  
DJ DISC LITE as 30L-2 plus variable speed flasher: **£54.00**  
Carlsboro Reverberation Unit **£44.00**  
Disco anti-feedback microphone **£11.95**  
Colt 150 watt liquid wheel projector **£23.50**  
150 watt QI liquid wheel projector **£50.00**  
Spare Effects and liquid cassettes large range of patterns **£6.00**  
6 inch Liquid wheels **£5.00**  
Various cassettes **£6.00**  
Mini spot bank fitted 3 lamps **£12.95**  
Auto Trilite (mini wheel flasher) **£17.00**  
Bubblemaker with light **£22.50**

Mixers/Mics/Spokers/Lighting U.K.'s largest range of Disco Lighting. FREE STOCK LIST REF. NO. 18 ON REQUEST.  
AKG / RESLO / DJ / CARLSBRO / EAGLE MICS, STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURN-TABLES, PUBLIC ADDRESS COMPONENTS.



All prices carr. paid (UK) (VAT EXTRA) Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

## EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter systems. 8" Bass/Midrange and Melinex Domed HF radiator plus crossover £12.50 per pair of systems (carr./packg. 40p) or built into veneered cabinets, size 18 x 12 x 6 1/2" £19.50 pair (carr. £1)

## HI-FI TAPE EQUIPMENT



U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17). Phone 01-402-4736 for Barclay/Access Card. Direct orders and latest prices.

## TRANSISTORS/SEMI-CONDUCTORS

U.K.'s largest range for every application. Small quantity discounts. Also Trade, Export and Industrial enquiries invited. Latest stock lists (Ref. No. 36) including valves on request.

## ELECTRONICS SUPPLIES

Specialists in electronics for more than 30 years. Trade and industry supplies—every type of component and equipment.



## NEW SINCLAIR PROJECT 80

Stereo PreAmplifier **£6.95**  
Audio Filter Unit **£5.45**  
Z40 15 Watt Amplifier **£6.95**  
Z60 25 Watt Amplifier **£6.95**  
PZ5 Mod. for 1 or 2 Z40 **£4.98**  
PZ6 Mod. (S Tab) 1 or 2 Z40 **£7.98**  
PZ8 Mod. (S Tab) 1 or 2 Z60 **£7.98**  
TRANSFORMER FOR PZ8 **£3.95**

NEW FM TUNER **£11.95**  
STEREO DECODER **£7.45**  
All items post paid.

## LOW COST HI-FI SPEAKERS

### SPECIAL OFFERS

EMI 13" x 8"—full range speakers (post 20p each or 30p pair)  
\*150TC—8 ohms 15" Twin Cone 10 watt £2.20 each or £4.00 pair.  
\*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms £3.85 each  
EW 15 watt 8 ohms C/o Tweeter £2.25 each or £7.40 per pair  
350 20 watt C/o Tweeters 8 or 15 ohms £7.80 each or £14.00 pair  
\* Polished wood cabinet £4.80 post 35p.



8 ohms full range (post 20p)	5 watt	£4.75
FR4	4"	£6.30
FR65	6 1/2"	£8.50
FR8	8"	£8.40
FR23	9 x 6"	£3.75
BASS & MID RANGE—8 ohms (post 20p)	15 watt	£7.20
AA12	5"	£8.50
B110	5 1/2"	£13.75
B200	8"	£2.10
B139/2	13" x 8"	£2.10
TWEETERS AND CROSSOVERS (post 20p)	8 or 15 ohms	£2.10
K2006	10 watt	£3.35
FHT6	15 watt	£4.80
K2011	30 watt	£5.50
T27	KEF	£5.52
Axcnt 100	30 watt 8 ohms	£2.70
K4009	1kHz/5kHz C/o	£3.10
SN75	3kHz var. C/o	
SPEAKER KITS (carr. etc. 35p)		
20.2	30 watt	£24.50 pair
20.3	40 watt	£35.95 pair
20.4	8"	£18.30 pair
LINTON 2	20 watt	£32.95 pair
GLENDALE 3	30 watt	£51.50 pair
DOVEDALE 3	50 watt	£55.00 pair
KEF KK2		£78.00 pair
KEF KK3		

## BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines etc.

SPECIAL OFFER **£13.60** Also available assembled ready to use. **£19.95** + VAT. + VAT.



10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E & O. ALWAYS BARGAINS FOR CALLERS.

# Henry's LIMITED

RADIO EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381  
309 PA - Disco - Lighting High Power Sound 01-723 6963  
303 Bargains Store (Callers only)  
Home and Car Entertainment Centres London and branches now open  
120 Shaftesbury Avenue, London W1 01-437 9692  
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402  
190-194 Station Road, Harrow, Middlesex 01 863 7788/9  
354-466 Edgware Road, London W2 01-402 5854/4736

See page 404 of this magazine  
All mail to 303 Edgware Road, London W2 1BW  
All stores open 9 am to 6 pm six days a week  
Hi-Fi - Tape Equipment Discount Stock List Free at all stores