

Practical projects to build at home

everyday electronics

MAY 75

25p


**SPECIAL 8 PAGE
SUPPLEMENT...**
**Using
Multimeters**

**ALL
INEXPENSIVE
AND EASY TO
BUILD**


The MINSTREL



WARNING WINKER

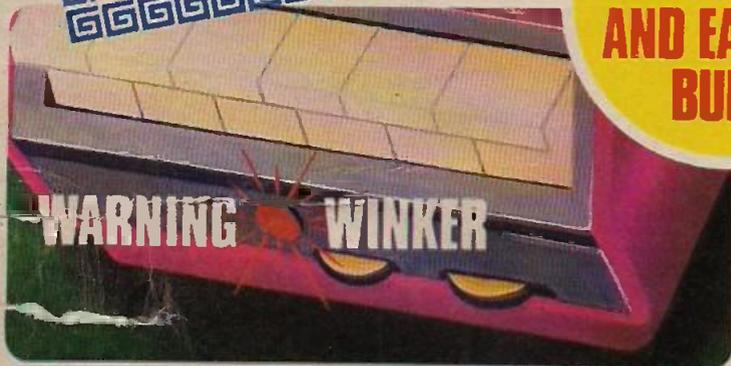

**ANTI-
THEFT
ALARM**

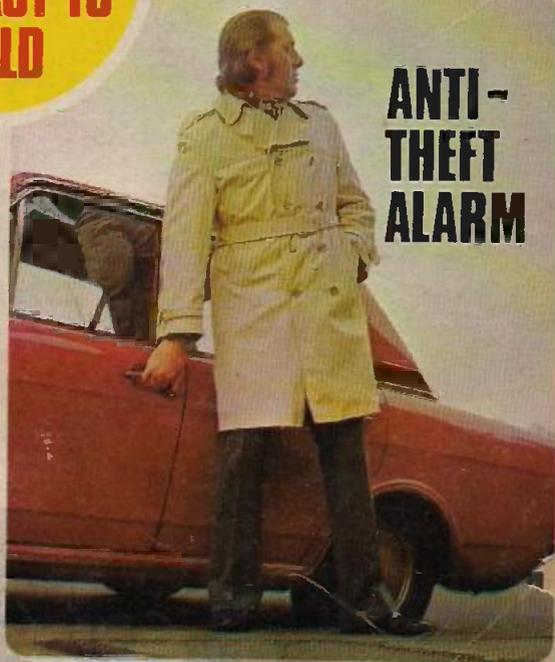

Plus
MW/LW TUNER
*and all the
regular features*

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteryless Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ One Transistor Radio.
- ★ Signal Injector.
- ★ 3 Transistor Loudspeaker Radio MW/LW.
- ★ 2 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP.
- ★ 5 Transistor Short Wave Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Neotome.
- ★ Audible Continuity Tester.
- ★ Electronic Noise Generator
- ★ Electronic Noise Generator
- ★ Sensitive Pre-Amplifier.

Total Building Costs
£7-23 P P & Ins. 44p
(Overseas Seamail P & P £2-35)
(+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans free with parts.

NEW ROAMER NINE


WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and warchange controls. Attractive all white case with red grille and carrying strap. Size 9" x 7" x 2 1/2" approx. Parts Price List and Plans free with parts.

Total Building Costs **£6-95** P P & Ins. 44p
(Overseas Seamail P & P £2-35)
(+ 8% VAT 55p)

NEW Everyday Series

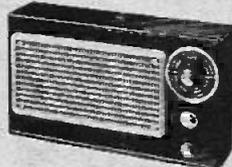

Build this exciting New series of designs

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 44 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans free with parts.

Total Building Costs **£2-95** P P & Ins. 36p
(Overseas Seamail P & P £1-70)
(+ 8% VAT 23p)

E.V.6. Case and looks as above. 5 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

Total Building Costs **£3-60** P P & Ins. 36p
(Overseas Seamail P & P £1-70)
(+ 8% VAT 29p)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Ferrite rod aerial. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans free with parts.

Total Building Costs **£4-08** P P & Ins. 36p
(Overseas Seamail P & P £2-00)
(+ 8% VAT 32p)

ROAMER TEN Mk 2

WITH VHF INCLUDING AIRCRAFT



Now with free earpiece and switched socket. 10 Transistors. Latest 2 watt Ferrite Magnet Loudspeaker. 9 Tunable Wavebands. MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blockings. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 60p free with parts.

Total building costs **£9-50** P P & Ins. 52p
(Overseas Seamail P & P £2-50)
(+ 8% VAT 76p)

POCKET FIVE

NOW WITH 3" LOUD-SPEAKER



3 Tunable wavebands, M.W., L.W. and Trawler Band, 2 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and red case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List free with parts.

Total Building Costs **£2-50** P P & Ins. 36p
(Overseas Seamail P & P £1-70)
(+ 8% VAT 20p)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4 1/2" approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

Total building costs **£6-98** P P & Ins. 47p
(Overseas Seamail P & P £2-50)
(+ 8% VAT 56p)

TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List free with parts.

Total Building Costs **£2-75** P P & Ins. 36p
(Overseas Seamail P & P £1-70)
(+ 8% VAT 21p)

TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for MW, and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Total building costs

£4-48 P P & Ins. 40p
(Overseas Seamail P & P £2-00)
(+ 8% VAT 36p)



Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed, can be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

Total building costs **£5-50** P P & Ins. 35p
(Overseas Seamail P & P £2-35)
(+ 8% VAT 44p)

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelis" shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel.: 0234 52367. Reg. No. 788372.

I enclose £..... for.....
Name.....
Address.....


(Dept. EE5.)

ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Total building costs

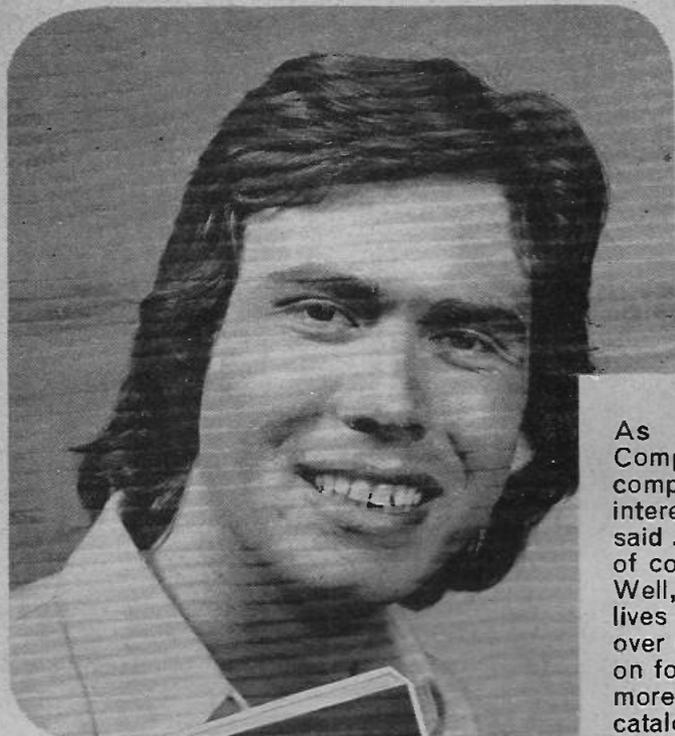£3-98 P P & Ins. 40p
(Overseas Seamail P & P £2-00)
(+ 8% VAT 32p)




kom-pre-hense-iv

As no doubt you've noticed, Home Radio Components Ltd. are always going on about how comprehensive their catalogue is! So out of interest I looked up the word in a dictionary. It said . . . "KOM-PRE-HENSE-IV, having the quality of comprising much; extensive; full."

Well, on that definition, the catalogue certainly lives up to their claim. In its 240 pages there are over 6,000 items listed and there must be getting on for a couple of thousand illustrations. What's more, to make it easy to find your way around, the catalogue is most carefully indexed, with cross references where necessary. Recently someone at Home Radio Components told me that they've sold over 150,000 copies of the catalogue. I'm not surprised! They also mentioned that many professional people in the world of radio and electronics regard it as a standard reference work. I don't know about the professionals, but I know lots of we amateur freaks would be quite lost without it.

But perhaps you have managed to struggle along so far without this invaluable catalogue. Why hamper yourself any longer? *Send off the coupon below with cheque or P.O. for 98 pence.* (65p plus 33p postage & packing). Every catalogue contains 14 vouchers each worth 5p when used as directed. This means that you can recover 70 pence, the whole cost of the catalogue plus 5p towards the postage. Needless to say, the catalogue is backed by a really good Mail Order Service.

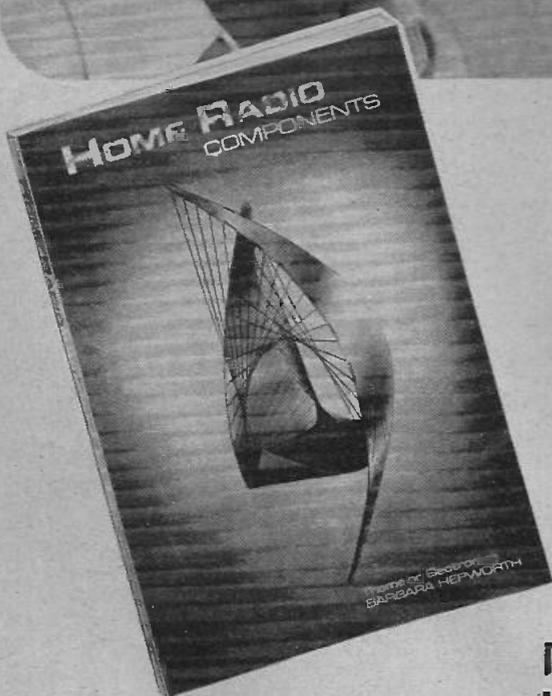

65p. plus 33p POST AND PACKING

Send off the coupon today. It's your first step to solving your component buying problems.

The price of 98p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME.....

ADDRESS

.....

.....



**HOME RADIO (Components) LTD., Dept. EE,
234-240 London Road, Mitcham, Surrey CR4 3HD**

(Regn. No.
London 912966)

HOME RADIO (Components) LTD, Dept. EE, 234-240 London Road, Mitcham, CR4 3HD. Phone 01-648 8422

The Largest Selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107 0.22	162(MP) 0.75	BC152 0.19	BD155 0.44	BF157 0.30	MJE2956 0.95	ZN414 41-20	2N2192 0.39	2N3391 0.16	2N4060 0.18
AC118 0.20	ADT140 0.55	BC153 0.41	BD156 0.44	BF158 0.24	MJE2955 0.62	29391 0.21	2N2193 0.39	2N3391A 0.18	2N4061 0.18
AC115 0.22	AF114 0.27	BC154 0.33	BD157 0.50	BF194 0.12	2C300 0.21	29392 0.21	2N2194 0.39	2N3392 0.16	2N4062 0.18
AO117K 0.32	AF115 0.27	BC155 0.20	BD158 0.56	BF195 0.13	MFF102 0.46	2G303 0.21	2N2217 0.24	2N3393 0.16	2N4284 0.18
AC122 0.18	AF116 0.27	BC156 0.18	BD159 0.48	BF196 0.16	MFF104 0.41	2G304 0.27	2N2218 0.22	2N3394 0.16	2N4285 0.19
AC123 0.19	AF117 0.27	BC157 0.33	BD160 0.50	BF197 0.16	MFF105 0.41	2C306 0.44	2N2219 0.22	2N3395 0.19	2N4286 0.19
AC126 0.19	AF118 0.30	BC158 0.18	BD161 0.56	BF200 0.50	OC19 0.42	2G311B 0.18	2N2220 0.24	2N3402 0.23	2N4287 0.19
AC127 0.20	AF124 0.33	BC159 0.18	BD162 0.56	BF202 0.50	OC20 0.50	2G317 0.18	2N2221 0.22	2N3403 0.23	2N4288 0.19
AC128 0.20	AF126 0.33	BC160 0.50	BD163 0.56	BF205 0.50	OC21 0.42	2G317B 0.18	2N2222 0.22	2N3404 0.31	2N4289 0.19
AC182 0.18	AF126 0.33	BC161 0.18	BD164 0.56	BF207 0.50	OC22 0.50	2G317 0.18	2N2223 0.22	2N3405 0.46	2N4290 0.19
AC134 0.16	AF127 0.31	BC162 0.18	BD165 0.56	BF208 0.50	OC23 0.54	2G317 0.18	2N2224 0.22	2N3414 0.17	2N4291 0.19
AC137 0.16	AF139 0.33	BC163 0.18	BD166 0.56	BF209 0.50	OC24 0.42	2G317 0.18	2N2225 0.22	2N3415 0.17	2N4292 0.19
AC141 0.20	AF178 0.55	BC164 0.18	BD167 0.78	BF258 0.56	OC25 0.48	2G317 0.18	2N2226 0.22	2N3416 0.31	2N4293 0.19
AC141K 0.28	AF179 0.55	BC165 0.18	BD168 0.78	BF259 0.56	OC26 0.48	2G317 0.18	2N2227 0.22	2N3417 0.31	2N4294 0.19
AC142 0.20	AF180 0.55	BC166 0.18	BD169 0.78	BF260 0.56	OC27 0.48	2G317 0.18	2N2228 0.22	2N3418 0.31	2N4295 0.19
AC142K 0.28	AF181 0.55	BC167 0.18	BD170 0.78	BF261 0.56	OC28 0.48	2G317 0.18	2N2229 0.22	2N3419 0.31	2N4296 0.19
AC151 0.17	AF186 0.55	BC168 0.18	BD171 0.78	BF262 0.56	OC29 0.48	2G317 0.18	2N2230 0.22	2N3420 0.31	2N4297 0.19
AC154 0.22	AF187 0.55	BC169 0.18	BD172 0.78	BF263 0.56	OC30 0.48	2G317 0.18	2N2231 0.22	2N3421 0.31	2N4298 0.19
AC155 0.22	AF188 0.55	BC170 0.18	BD173 0.78	BF264 0.56	OC31 0.48	2G317 0.18	2N2232 0.22	2N3422 0.31	2N4299 0.19
AC156 0.22	AF189 0.55	BC171 0.18	BD174 0.78	BF265 0.56	OC32 0.48	2G317 0.18	2N2233 0.22	2N3423 0.31	2N4300 0.19
AC157 0.27	AF190 0.55	BC172 0.18	BD175 0.78	BF266 0.56	OC33 0.48	2G317 0.18	2N2234 0.22	2N3424 0.31	2N4301 0.19
AC158 0.22	AF191 0.55	BC173 0.18	BD176 0.78	BF267 0.56	OC34 0.48	2G317 0.18	2N2235 0.22	2N3425 0.31	2N4302 0.19
AC159 0.22	AF192 0.55	BC174 0.18	BD177 0.78	BF268 0.56	OC35 0.48	2G317 0.18	2N2236 0.22	2N3426 0.31	2N4303 0.19
AC160 0.22	AF193 0.55	BC175 0.18	BD178 0.78	BF269 0.56	OC36 0.48	2G317 0.18	2N2237 0.22	2N3427 0.31	2N4304 0.19
AC161 0.22	AF194 0.55	BC176 0.18	BD179 0.78	BF270 0.56	OC37 0.48	2G317 0.18	2N2238 0.22	2N3428 0.31	2N4305 0.19
AC162 0.22	AF195 0.55	BC177 0.18	BD180 0.78	BF271 0.56	OC38 0.48	2G317 0.18	2N2239 0.22	2N3429 0.31	2N4306 0.19
AC163 0.22	AF196 0.55	BC178 0.18	BD181 0.78	BF272 0.56	OC39 0.48	2G317 0.18	2N2240 0.22	2N3430 0.31	2N4307 0.19
AC164 0.22	AF197 0.55	BC179 0.18	BD182 0.78	BF273 0.56	OC40 0.48	2G317 0.18	2N2241 0.22	2N3431 0.31	2N4308 0.19
AC165 0.22	AF198 0.55	BC180 0.18	BD183 0.78	BF274 0.56	OC41 0.48	2G317 0.18	2N2242 0.22	2N3432 0.31	2N4309 0.19
AC166 0.22	AF199 0.55	BC181 0.18	BD184 0.78	BF275 0.56	OC42 0.48	2G317 0.18	2N2243 0.22	2N3433 0.31	2N4310 0.19
AC167 0.22	AF200 0.55	BC182 0.18	BD185 0.78	BF276 0.56	OC43 0.48	2G317 0.18	2N2244 0.22	2N3434 0.31	2N4311 0.19
AC168 0.27	AF201 0.55	BC183 0.18	BD186 0.78	BF277 0.56	OC44 0.48	2G317 0.18	2N2245 0.22	2N3435 0.31	2N4312 0.19
AC169 0.16	AF202 0.55	BC184 0.18	BD187 0.78	BF278 0.56	OC45 0.48	2G317 0.18	2N2246 0.22	2N3436 0.31	2N4313 0.19
AC176 0.22	AF203 0.55	BC185 0.18	BD188 0.78	BF279 0.56	OC46 0.48	2G317 0.18	2N2247 0.22	2N3437 0.31	2N4314 0.19
AC177 0.27	AF204 0.55	BC186 0.18	BD189 0.78	BF280 0.56	OC47 0.48	2G317 0.18	2N2248 0.22	2N3438 0.31	2N4315 0.19
AC178 0.27	AF205 0.55	BC187 0.18	BD190 0.78	BF281 0.56	OC48 0.48	2G317 0.18	2N2249 0.22	2N3439 0.31	2N4316 0.19
AC179 0.27	AF206 0.55	BC188 0.18	BD191 0.78	BF282 0.56	OC49 0.48	2G317 0.18	2N2250 0.22	2N3440 0.31	2N4317 0.19
AC180 0.22	AF207 0.55	BC189 0.18	BD192 0.78	BF283 0.56	OC50 0.48	2G317 0.18	2N2251 0.22	2N3441 0.31	2N4318 0.19
AC180K 0.32	AF208 0.55	BC190 0.18	BD193 0.78	BF284 0.56	OC51 0.48	2G317 0.18	2N2252 0.22	2N3442 0.31	2N4319 0.19
AC181 0.22	AF209 0.55	BC191 0.18	BD194 0.78	BF285 0.56	OC52 0.48	2G317 0.18	2N2253 0.22	2N3443 0.31	2N4320 0.19
AC181K 0.32	AF210 0.55	BC192 0.18	BD195 0.78	BF286 0.56	OC53 0.48	2G317 0.18	2N2254 0.22	2N3444 0.31	2N4321 0.19
AC187 0.24	AF211 0.55	BC193 0.18	BD196 0.78	BF287 0.56	OC54 0.48	2G317 0.18	2N2255 0.22	2N3445 0.31	2N4322 0.19
AC187K 0.32	AF212 0.55	BC194 0.18	BD197 0.78	BF288 0.56	OC55 0.48	2G317 0.18	2N2256 0.22	2N3446 0.31	2N4323 0.19
AC188 0.24	AF213 0.55	BC195 0.18	BD198 0.78	BF289 0.56	OC56 0.48	2G317 0.18	2N2257 0.22	2N3447 0.31	2N4324 0.19
AC188K 0.32	AF214 0.55	BC196 0.18	BD199 0.78	BF290 0.56	OC57 0.48	2G317 0.18	2N2258 0.22	2N3448 0.31	2N4325 0.19
AC177 0.27	AF215 0.55	BC197 0.18	BD200 0.78	BF291 0.56	OC58 0.48	2G317 0.18	2N2259 0.22	2N3449 0.31	2N4326 0.19
AC178 0.27	AF216 0.55	BC198 0.18	BD201 0.78	BF292 0.56	OC59 0.48	2G317 0.18	2N2260 0.22	2N3450 0.31	2N4327 0.19
AC179 0.27	AF217 0.55	BC199 0.18	BD202 0.78	BF293 0.56	OC60 0.48	2G317 0.18	2N2261 0.22	2N3451 0.31	2N4328 0.19
AC180 0.22	AF218 0.55	BC200 0.18	BD203 0.78	BF294 0.56	OC61 0.48	2G317 0.18	2N2262 0.22	2N3452 0.31	2N4329 0.19
AC180K 0.32	AF219 0.55	BC201 0.18	BD204 0.78	BF295 0.56	OC62 0.48	2G317 0.18	2N2263 0.22	2N3453 0.31	2N4330 0.19
AC181 0.22	AF220 0.55	BC202 0.18	BD205 0.78	BF296 0.56	OC63 0.48	2G317 0.18	2N2264 0.22	2N3454 0.31	2N4331 0.19
AC181K 0.32	AF221 0.55	BC203 0.18	BD206 0.78	BF297 0.56	OC64 0.48	2G317 0.18	2N2265 0.22	2N3455 0.31	2N4332 0.19
AC187 0.24	AF222 0.55	BC204 0.18	BD207 0.78	BF298 0.56	OC65 0.48	2G317 0.18	2N2266 0.22	2N3456 0.31	2N4333 0.19
AC187K 0.32	AF223 0.55	BC205 0.18	BD208 0.78	BF299 0.56	OC66 0.48	2G317 0.18	2N2267 0.22	2N3457 0.31	2N4334 0.19
AC188 0.24	AF224 0.55	BC206 0.18	BD209 0.78	BF300 0.56	OC67 0.48	2G317 0.18	2N2268 0.22	2N3458 0.31	2N4335 0.19
AC188K 0.32	AF225 0.55	BC207 0.18	BD210 0.78	BF301 0.56	OC68 0.48	2G317 0.18	2N2269 0.22	2N3459 0.31	2N4336 0.19
AC176 0.22	AF226 0.55	BC208 0.18	BD211 0.78	BF302 0.56	OC69 0.48	2G317 0.18	2N2270 0.22	2N3460 0.31	2N4337 0.19
AC177 0.27	AF227 0.55	BC209 0.18	BD212 0.78	BF303 0.56	OC70 0.11	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC178 0.27	AF228 0.55	BC210 0.18	BD213 0.78	BF304 0.56	OC71 0.11	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC179 0.27	AF229 0.55	BC211 0.18	BD214 0.78	BF305 0.56	OC72 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC180 0.22	AF230 0.55	BC212 0.18	BD215 0.78	BF306 0.56	OC73 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC180K 0.32	AF231 0.55	BC213 0.18	BD216 0.78	BF307 0.56	OC74 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC181 0.22	AF232 0.55	BC214 0.18	BD217 0.78	BF308 0.56	OC75 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC181K 0.32	AF233 0.55	BC215 0.18	BD218 0.78	BF309 0.56	OC76 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC187 0.24	AF234 0.55	BC216 0.18	BD219 0.78	BF310 0.56	OC77 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC187K 0.32	AF235 0.55	BC217 0.18	BD220 0.78	BF311 0.56	OC78 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC188 0.24	AF236 0.55	BC218 0.18	BD221 0.78	BF312 0.56	OC79 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC188K 0.32	AF237 0.55	BC219 0.18	BD222 0.78	BF313 0.56	OC80 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC176 0.22	AF238 0.55	BC220 0.18	BD223 0.78	BF314 0.56	OC81 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC177 0.27	AF239 0.55	BC221 0.18	BD224 0.78	BF315 0.56	OC82 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC178 0.27	AF240 0.55	BC222 0.18	BD225 0.78	BF316 0.56	OC83 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC179 0.27	AF241 0.55	BC223 0.18	BD226 0.78	BF317 0.56	OC84 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC180 0.22	AF242 0.55	BC224 0.18	BD227 0.78	BF318 0.56	OC85 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC180K 0.32	AF243 0.55	BC225 0.18	BD228 0.78	BF319 0.56	OC86 0.16	2N2824 0.48	2N2905A 0.33	2N3704 0.14	2N3902 0.62
AC181 0.22	AF244 0.55	BC226 0.18	BD229 0.78	BF320 0.56	OC87 0.16	2N2824 0.48	2N2905A 0.33		

-the lowest prices!

BRAND NEW TEXAS SEMI TRANSISTORS

Coded and Guaranteed Pak No.	EQVT
11 5 2G3713	OC71
8 5 D1874	OC10
8 5 D1216	OC81D
8 5 2G3811	OC81
8 5 2G3827	OC82
8 5 2G3444	OC44
8 5 2G345B	OC45
8 5 2G378	OC78
8 5 2G399A	2N1309
10 2G417	AP117

AB 55p each pak

ED 120 MIXIE DRIVER TRANSISTOR

Suitable replacement for BX2 21, C 407, 2N 1893 120reb.

1	25	100+
0-19	0-17	0-16

SL trans. suitable for P.E. Organ Metal TO-18 Expt. 21X300 6p each. Any Qty.

GP 100 TO3 METAL CASE GERMANIUM

V_{ceo}=80V. V_{ceo}=80V. I_C=10 amp. P_{tot}=30W. h_{fe}=30-170. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-47	0-44	0-40

GP 300 TO3 METAL CASE SILICON

V_{ceo}=100V. V_{ceo}=80V. I_C=15 amp. P_{tot}=115W. h_{fe}=20, 100T-1.5MHZ. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1	25	100+
0-55	0-53	0-51

NEW 9th EDITION

over 300 pages TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. \$2.80 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EXISTOCK. SEND FOR FREE LIST.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	0-55
50	For	1-10
100	For	1-92
500	For	8-25
1000	For	14-30

SIL. G.P. DIODES 2p

300mV 30 0-55
40PIV (Min.) 100 1-65
Sub-Min. 500 5-50
Fully Tested 1,000 9-90
Ideal for Organ Builders.

AD161/162

MFP COMP. GERM. TRANS. OVER LOW EST. PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES

VOLTAGE	RANGE
2-33V	400mV (DO-7 Case) 9p ea. 13W
(Top-Hat) 18p ea. 10W	(80-10 Stud) 82p ea.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q 1	20 Red spot transistor PNP	0-54
Q 2	16 White spot R.F. transistors PNP	0-54
Q 3	4 OC77 type transistors	0-54
Q 4	6 Matched transistors OC44/45/81/81D	0-54
Q 5	4 OC76 transistors	0-54
Q 6	6 OC72 transistors	0-54
Q 7	4 AC128 transistors PNP high gain	0-54
Q 8	4 AC126 transistors PNP	0-54
Q 9	7 OC81 type transistors	0-54
Q 10	7 OC71 type transistors	0-54
Q 11	2 AC127/128 Complementary pairs PNP/NPN	0-54
Q 12	3 AP116 type transistors	0-54
Q 13	3 AP117 type transistors	0-54
Q 14	3 OC71 H.F. type transistors	0-54
Q 15	7 2N2926 Sil. Epoxy transistors mixed colours	0-54
Q 17	6 NPN 2xST.141 & 3xST.140	0-54
Q 18	4 MADT'S 2xMAT 100 & 2xMAT 120	0-54
Q 19	3 MADT'S 2xMAT 101 & 1xMAT 121	0-54
Q 20	4 OC44 Germanium transistors A.F.	0-54
Q 21	4 AC127 NPN Germanium transistors	0-54
Q 22	20 NKT transistors A.F. R.F. coded.	0-54
Q 23	10 OA292 Silicon diodes sub-min.	0-54
Q 24	5 OA31 diodes	0-54
Q 25	16 IN814 Silicon diodes 75PIV 75mA	0-54
Q 26	8 OA95 Germanium diodes sub-min IN69	0-54
Q 27	2 10A PIV Silicon rectifiers 18425R	0-54
Q 28	2 Silicon power rectifiers BY213	0-54
Q 29	4 Silicon transistors 2x2N2956, 1x2N697, 1x2N698	0-54
Q 30	7 Silicon switch transistors 8N706 NPN	0-54
Q 31	6 Silicon switch transistors 2N708, NPN	0-54
Q 32	3 PNP Silicon transistors 2x2N1151, 1x2N1152	0-54
Q 33	3 Silicon NPN transistors 2N1711	0-54
Q 34	7 Silicon NPN transistors 2N2869, 500MHz (code P397)	0-54
Q 35	3 Silicon PNP TO-5, 2x2N2904 & 1x2N2905	0-54
Q 37	2N3646 TO-18 plastic 300MHz NPN	0-54
Q 36	7 2N3023 NPN Silicon transistors	0-54
Q 38	7 PNP transistors 3 x 2N3703, 2x2N3702	0-54

555 I.C. 65p each

MAMMOTH I.C. PACK

APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS MANY CODED also some UNKNOWN TYPES - YOU TO IDENTIFY

PAK NO. M.I.C. 200

PRICE £1.25 per PAK including p & p & V.A.T.

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classified as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	-12x7400	0-54	UIC45	-5x7446	0-54	UIC90	-5x7490	0-54
UIC01	-12x7401	0-54	UIC46	-5x7448	0-54	UIC91	-5x7491	0-54
UIC02	-12x7402	0-54	UIC49	-12x7450	0-54	UIC92	-8x7492	0-54
UIC03	-12x7403	0-54	UIC54	-12x7453	0-54	UIC93	-5x7493	0-54
UIC04	-12x7405	0-54	UIC56	-12x7454	0-54	UIC94	-5x7494	0-54
UIC05	-12x7406	0-54	UIC60	-12x7460	0-54	UIC95	-5x7495	0-54
UIC06	-8x7408	0-54	UIC70	-8x7470	0-54	UIC96	-5x7496	0-54
UIC07	-8x7407	0-54	UIC72	-8x7472	0-54	UIC100	-5x74100	0-54
UIC10	-12x7410	0-54	UIC73	-8x7473	0-54	UIC121	-5x74121	0-54
UIC20	-12x7420	0-54	UIC74	-8x7474	0-54	UIC141	-5x74141	0-54
UIC30	-12x7430	0-54	UIC75	-8x7475	0-54	UIC151	-5x74151	0-54
UIC40	-12x7440	0-54	UIC76	-8x7476	0-54	UIC154	-5x74154	0-54
UIC41	-5x7441	0-54	UIC80	-5x7480	0-54	UIC193	-5x74193	0-54
UIC42	-5x7442	0-54	UIC81	-5x7481	0-54	UIC199	-5x74199	0-54
UIC43	-5x7443	0-54	UIC82	-5x7482	0-54			
UIC44	-5x7444	0-54	UIC83	-5x7483	0-54			
UIC45	-5x7445	0-54	UIC86	-5x7486	0-54			

Packs cannot be split, but 25 assorted pieces (four mix) is available as PAK UIC X1.

LINEAR INTEGRATED CIRCUIT PAKS
Manufacturers fall-outs

UIC700	10-200	0-54
UIC710	7-710	0-54
UIC741	7-741	0-54
UIC747	5-747	0-54
UIC748	7-748	0-54

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-54
U 2	50 Mixed Germanium Transistors AP/RF	0-54
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-54
U 4	30 Germanium Transistors like OC81, AC128	0-54
U 5	60 300mA Sub-Min. Silicon Diodes	0-54
U 6	30 80L Planar Trans. NPN like B8Y95A, 2N706	0-54
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGR up to 1000 54	0-54
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-54
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-54
U 10	20 BAY50 charge storage Diodes DO-7 Glass	0-54
U 11	20 PNP Sil. Planar Trans. TO-5 like 2N1152, 2N2904	0-54
U 12	30 PNP-NPN Sil. Transistors OC200 & 2B 104	0-54
U 14	180 Mixed Silicon and Germanium Diodes	0-54
U 15	20 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-54
U 16	10 5 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-54
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-54
U 18	8 6 Amp Silicon Rectifiers BY213 Type up to 600 PIV	0-54
U 19	20 Silicon NPN Transistors like BC108	0-54
U 20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-54
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-54
U 22	25 MADT's like MHz Series PNP Transistors	0-54
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 300PIV	0-54
U 25	25 300MHz NPN Silicon Transistors 2N708, B8Y27	0-54
U 26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-54
U 29	10 1 Amp SCR's TO-5 can. up to 800PIV CB81/25-600	1-08
U 32	25 Zener Diodes 400mV DO-7 case 8-33 volts mixed	0-54
U 33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-54
U 34	30 Silicon PNP Alloy Trans. TO-5 B0Y26 2B302/4	0-54
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-54
U 36	20 Silicon Germanium NPN Transistors TO-5 BFY50/51/52	0-54
U 37	30 Silicon Alloy Transistors BO-2 PNP OC200, 2B322	0-54
U 38	20 Fast Switching Silicon Trans. NPN 400MHz 2N2011	0-54
U 39	20 RE. Germ. PNP Transistors 2N1305/5T0-5	0-54
U 40	10 Dual Transistors 5 lead TO-5 2N2906	0-54
U 43	25 Sil. Trans. Plastic TO-18 A.F. BC133/114	0-54
U 44	20 Sil. Trans. Plastic TO-5 BC133/116	0-54
U 45	7 3A SCR. TO35 up to 600PIV	1-08
U 46	20 Unijunction transistors similar to T1849	0-54
U 47	10 TO220AB plastic triacs 50V 5A	1-08
U 48	9 NPN Sil. Power transistors like 2N3055	1-08
U 49	12 NPN Sil. plastic power trans. 60W like 2N2984/2996	1-08

Code No.'s mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE

One 55p Pak of your own choice free with orders valued 24 or over

CADMIUM CELLS

ORP12 48p

SIL. RECTS. TESTED

One 55p Pak of your own choice free with orders valued 24 or over	PIV 300mA 750mA 1A	1-5A 3A	10A 30A
50 0-05 0-06	IN4001 0-05	0-08 0-15 0-21 0-60	
100 0-05 0-07	IN4002 0-05	0-10 0-17 0-23 0-75	
200 0-06 0-10	IN4003 0-07	0-18 0-22 0-25 1-00	
400 0-08 0-15	IN4004 0-08	0-15 0-30 0-38 1-35	
600 0-09 0-17	IN4005 0-10	0-18 0-38 0-45 1-90	
800 0-12 0-19	IN4006 0-11	0-23 0-38 0-55 2-10	
1000 0-14 0-20	IN4007 0-12	0-25 0-48 0-85 2-50	
1200 - 0-35		0-30 0-58 0-75 3-00	

DIACS

FOR USE WITH TRIACS

3B100 (DS2) 25p each

10 amp POTTED BRIDGE RECTIFIER on heat sink.

100PIV. 99p each

TRIACS

VBOM 2A 6A 10A TO-5 TO-46 TO-48

D P 5p

100 33 55 83

200 55 66 99

400 77 88 1-21

Giro No. 388-7006
Please send all orders direct to warehouse and despatch department.

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 20p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

- * 6 OR 12 VOLT
- * + VE AND - VE GROUND

Here's the new, improved version of the original Scorpio Electronic Ignition System — with a big plus over all the other kits — the Electro Spares Kit is designed for *both* positive and negative ground automotive electrical systems. Not just +ve ground. Nor just —ve ground. But both! So if you change cars, you can be almost certain that you can change over your Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car or motor cycle.

When your Scorpio Mk. 2 is installed, you instantly benefit from all these Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only **£10.85** inc. VAT and p & p.
Ready Made Unit **£13.65** inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

PE FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics' Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components — pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results — or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only **£28.50** inc. VAT and p & p.

PE GEMINI STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is —3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from **£50** to **£60** inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 9p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE(B)
Tel: Sheffield (0742) 668888

BURNEZE

Cools
soothes
and heals
minor
burns

Burneze — unique aerosol first aid — cools instantly, contains a fast-acting local anaesthetic plus antihistamine to control swelling. It deals with the lingering pain of a minor burn or scald and reduces the chance of a blister.

From Boots and other chemists. S.A.E. to Potter & Clarke, Croydon CR9 3LP, for intriguing leaflet.

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today — both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fulllest details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept E.E.C. 55
P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME Block

ADDRESS Caps.

..... Please

**BRITISH NATIONAL RADIO
AND ELECTRONICS SCHOOL**

Marshall's

Everything you need is in our
New 1975 Catalogue
available now price 25p
(100 pages of prices and data)

A. Marshall (London) Ltd. Dept. EE
42 Cricklewood Broadway London NW2 3HD Telephone 01-452 0161/2 Telex 21492
& 65 West Regent Street Glasgow G2 2OD Telephone 041-332 4133

Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat
Trade and export enquiries welcome

Top 500 Semiconductors from the largest range in the UK

2N456 0-80	2N2924 0-20	2N5195 1-46	AF117 0-35	BC2144 0-18	BF178 0-35	8D1L 0-38	OC72 0-25
2N456A 0-80	2N2926 0-20	2N5245 0-47	AF119 0-35	BC237 0-16	BF179 0-43	14D1L 0-40	OC81 0-25
2N457A 1-20	2N3053 0-25	2N5294 0-48	AF124 0-30	BC238 0-15	BF180 0-35	LM710 0-47	OC83 0-24
2N490 3-16	2N3054 0-60	2N5295 0-48	AF125 0-30	BC239 0-15	BF181 0-36	LM3900 0-70	ORP12 0-53
2N491 4-38	2N3055 0-75	2N5296 0-48	AF126 0-28	BC251 0-25	BF182 0-35	LM723C 0-90	RS3 1-80
2N492 5-00	2N3390 0-45	2N5298 0-50	AF127 0-28	BC253 0-25	BF183 0-35	LM741T099	SL1414 1-80
2N493 5-20	2N3391 0-28	2N5457 0-49	AF137 0-65	BC257 0-16	BF184 0-30	8D1L 0-40	SL610C 1-70
2N696 0-22	2N3391A	2N5458 0-46	AF186 0-46	BC258 0-16	BF185 0-30	14D1L 0-73	SL611 0-70
2N697 0-16		2N5459 0-49	AF200 0-65	BC259 0-17	BF194 0-12	14D1L 0-38	SL612C 1-70
2N698 0-82	2N3392 0-15	2N5492 0-58	AF239 0-65	BC261 0-25	BF195 0-12	LM747 1-00	SL620C 2-60
2N699 0-59	2N3393 0-15	2N5494 0-58	AF240 0-90	BC262 0-25	BF196 0-13	LM7488D1L	SL621C 2-60
2N706 0-14	2N3394 0-15	2N5496 0-61	AF279 0-70	BC263 0-25	BF197 0-15	14D1L 0-60	SL623 4-59
2N706A 0-16	2N3402 0-18	2N5627 0-45	AF280 0-79	BC300 0-38	BF198 0-18	LM7805 2-00	SL640C 3-10
2N708 0-17	2N3403 0-19	2N5777 0-45	AL102 1-00	BC301 0-34	BF200 0-40	14D1L 0-73	SL641C 3-10
2N709 0-42	2N3440 0-59	3N1228 0-73	AL103 1-00	BC302 0-29	BF225J 0-23	LM7805 2-50	SN76003N
2N711 0-10	2N3441 0-97	3N1139 1-42	BC107 0-14	BC303 0-54	BF244 0-21	LM7812 2-50	SN76013N
2N718 0-23	2N3442 1-40	3N1140 1-00	BC108 0-14	BC307 0-17	BF245 0-15	LM7824 2-50	SN76023N
2N718A 0-28	2N3441A 0-10	3N1141 0-81	BC109 0-14	BC308A 0-15	BF246 0-38	MC1303 1-50	SN76033N
2N720 0-27	2N3445 0-10	3N2000 2-49	BC113 0-15	BC309C 0-17	BF247 0-65	MC1310 2-92	
2N914 0-59	2N3416 0-15	40361 0-40	BC115 0-17	BC322 0-27	BF247 0-65	MC1330P 0-90	
2N916 0-38	2N3417 0-21	40362 0-45	BC116 0-17	BC328 0-28	BF255 0-19	MC1351P 0-80	
2N918 0-32	2N3638 0-15	40363 0-88	BC116A 0-18	BC337 0-20	BF257 0-47	MC1352P 0-80	
2N929 0-37	2N3638A	40389 0-46	BC117 0-21	BC338 0-20	BF258 0-53	MC1465 3-50	
2N930 0-22		40394 0-15	BC118 0-14	BCY30 0-80	BF259 0-55	MC1469 2-75	
2N1302 0-19	2N3639 0-27	40395 0-65	BC119 0-20	BCY31 0-85	BF259 0-55	ME4002 0-20	
2N1303 0-19	2N3641 0-17	40406 0-35	BC122 0-35	BCY32 0-85	BF259 0-55	ME4004 0-13	
2N1304 0-26	2N3702 0-11	40407 0-35	BC125 0-16	BCY33 0-85	BF521A 2-30	ME4012 0-18	
2N1305 0-24	2N3703 0-12	40408 0-30	BC126 0-23	BCY34 0-79	BF528 0-92	ME4102 0-11	
2N1306 0-31	2N3704 0-15	40409 0-52	BC132 0-30	BCY38 1-00	BF561 0-27	ME4104 0-11	
2N1307 0-30	2N3705 0-15	40410 0-52	BC134 0-13	BCY39 1-00	BF598 0-25	MJ480 0-95	
2N1308 0-47	2N3706 0-15	40411 2-25	BC135 0-13	BCY40 0-97	BF598 0-25	MJ481 1-20	
2N1309 0-47	2N3706 0-15	40412 2-25	BC136 0-17	BCY42 0-97	BF598 0-25	MJ490 1-50	
2N1671 1-54	2N3708 0-14	40595 0-84	BC137 0-17	BCY43 0-97	BF598 0-25	MJ491 1-45	
	2N3709 0-15	40601 0-67	BC138 0-24	BCY59 0-32	BF598 0-25	MJ2955 1-00	
1-67	2N3710 0-15	40602 0-61	BC140 0-26	BCY70 0-17	BF598 0-25	MJ340 0-48	
2N1671B1 0-85	2N3711 0-15	40603 0-58	BC141 0-68	BCY71 0-22	BF598 0-25	MJ370 0-65	
2N1711 0-45	2N3712 1-20	40604 0-56	BC142 0-23	BCY72 0-15	BF598 0-25	MJ371 0-65	
2N1907 5-50	2N3713 0-20	40636 1-10	BC143 0-25	BD115 0-75	BF598 0-25	MJ372 0-65	
2N2102 0-60	2N3714 1-38	40669 1-00	BC145 0-21	BD116 0-75	BF598 0-25	MJ373 0-65	
2N2147 0-78	2N3715 1-50	40673 0-73	BC147 0-14	BD121 1-00	BF598 0-25	MJ374 0-65	
2N2148 0-94	2N3716 1-80	AC126 0-20	BC148 0-14	BD123 0-82	BF598 0-25	MJ375 0-65	
2N2160 0-90	2N3717 2-20	AC127 0-20	BC149 0-15	BD124 0-67	BF598 0-25	MJ376 0-65	
2N2181A	2N3722 1-80	AC128 0-20	BC153 0-18	BD131 0-40	BF598 0-25	MJ377 0-65	
2N2219 0-22	2N3723 2-65	AC151V 2-7	BC154 0-18	BD132 0-50	BSX20 0-21	MJ378 0-65	
2N2219A	2N3729 0-24	AC152V 0-49	BC157 0-16	BD133 0-43	BSX21 0-29	MJ379 0-65	
0-26	2N3729 0-24	AC153 0-35	BC158 0-16	BD134 0-43	BU104 2-00	MJ380 0-65	
2N2220 0-25	2N3791 2-35	AC153K 0-40	BC160 0-60	BD135 0-55	BU105 2-25	MJ381 0-65	
2N2221 0-18	2N3792 2-60	AC154 0-25	BC167B 0-15	BD138 0-63	CI06D 0-65	MJ382 0-65	
2N2221A	2N3797 0-10	AC176 0-30	BC168B 0-15	BD139 0-71	CA3180A	MJ383 0-65	
0-21	2N3810 0-37	AC176K 0-40	BC168C 0-15	BD140 0-87	CA3020A	MJ384 0-65	
2N2222 0-20	2N3823 1-42	AC187K 0-35	BC169B 0-15	BD529 0-80	MPSA25 0-25	MJ385 0-65	
2N2222A	2N3904 0-27	ACY18 0-24	BC169C 0-15	BD530 0-80	MPSA26 0-31	MJ386 0-65	
0-25	2N3906 0-27	ACY19 0-24	BC170 0-15	BF179 0-24	CA3028A	MPSA27 0-25	
2N2368 0-25	2N4036 0-67	ACY20 0-22	BC172 0-17	BDY20 1-05	CA3035 1-37	MPSA28 0-25	
2N2369 0-20	2N4037 0-42	ACY21 0-25	BC173 0-28	BF115 0-36	CA3052 1-62	MPSA29 0-25	
2N2369A	2N4038 0-18	ACY28 0-20	BC177 0-28	BF116 0-36	CA3052 1-62	MPSA30 0-25	
2N2646 0-95	2N4059 0-15	ADY30 0-58	BC178 0-27	BF117 0-55	CA3046 0-70	MPSA31 0-25	
2N2647 0-98	2N4060 0-15	AD142 0-57	BC179 0-30	BF121 0-35	CA3048 2-11	MPSA32 0-25	
2N2904 0-22	2N4061 0-15	AD143 0-68	BC182 0-12	BF122 0-35	CA3089E1-96	MPSA33 0-25	
2N2904A	2N4062 0-15	AD149V 0-20	BC183 0-12	BF123 0-35	CA3090Q	NE555V 0-70	
2N2905 0-24	2N4063 0-15	AD150 0-21	BC183 0-12	BF124 0-35	CA3090Q	NE555V 0-70	
2N2905A	2N4064 0-15	AD151 0-21	BC183 0-12	BF125 0-35	CA3090Q	NE555V 0-70	
0-26	2N4065 0-15	AD152 0-21	BC184 0-13	BF154 0-16	LM301A 0-48	NE560 4-48	
2N2906 0-19	2N4066 0-15	AD153 0-21	BC184 0-13	BF154 0-16	LM308 2-50	NE561 4-48	
2N2906A	2N4067 0-15	AD154 0-21	BC184 0-13	BF154 0-16	LM309K 1-88	NE565A 4-48	
0-21	2N4068 0-15	AD155 0-21	BC184 0-13	BF154 0-16	LM571 1-50	OC23 1-35	
2N2907 0-22	2N4069 0-15	AD156 0-21	BC184 0-13	BF154 0-16	LM572 1-50	OC23 1-35	
2N2907A	2N4070 0-15	AD157 0-21	BC184 0-13	BF154 0-16	LM573 1-50	OC23 1-35	
0-24	2N4071 0-15	AD158 0-21	BC184 0-13	BF154 0-16	LM574 1-50	OC23 1-35	
	2N4072 0-15	AD159 0-21	BC184 0-13	BF154 0-16	LM575 1-50	OC23 1-35	
	2N4073 0-15	AD160 0-21	BC184 0-13	BF154 0-16	LM576 1-50	OC23 1-35	
	2N4074 0-15	AD161 0-21	BC184 0-13	BF154 0-16	LM577 1-50	OC23 1-35	
	2N4075 0-15	AD162 0-21	BC184 0-13	BF154 0-16	LM578 1-50	OC23 1-35	
	2N4076 0-15	AD163 0-21	BC184 0-13	BF154 0-16	LM579 1-50	OC23 1-35	
	2N4077 0-15	AD164 0-21	BC184 0-13	BF154 0-16	LM580 1-50	OC23 1-35	
	2N4078 0-15	AD165 0-21	BC184 0-13	BF154 0-16	LM581 1-50	OC23 1-35	
	2N4079 0-15	AD166 0-21	BC184 0-13	BF154 0-16	LM582 1-50	OC23 1-35	
	2N4080 0-15	AD167 0-21	BC184 0-13	BF154 0-16	LM583 1-50	OC23 1-35	
	2N4081 0-15	AD168 0-21	BC184 0-13	BF154 0-16	LM584 1-50	OC23 1-35	
	2N4082 0-15	AD169 0-21	BC184 0-13	BF154 0-16	LM585 1-50	OC23 1-35	
	2N4083 0-15	AD170 0-21	BC184 0-13	BF154 0-16	LM586 1-50	OC23 1-35	
	2N4084 0-15	AD171 0-21	BC184 0-13	BF154 0-16	LM587 1-50	OC23 1-35	
	2N4085 0-15	AD172 0-21	BC184 0-13	BF154 0-16	LM588 1-50	OC23 1-35	
	2N4086 0-15	AD173 0-21	BC184 0-13	BF154 0-16	LM589 1-50	OC23 1-35	
	2N4087 0-15	AD174 0-21	BC184 0-13	BF154 0-16	LM590 1-50	OC23 1-35	
	2N4088 0-15	AD175 0-21	BC184 0-13	BF154 0-16	LM591 1-50	OC23 1-35	
	2N4089 0-15	AD176 0-21	BC184 0-13	BF154 0-16	LM592 1-50	OC23 1-35	
	2N4090 0-15	AD177 0-21	BC184 0-13	BF154 0-16	LM593 1-50	OC23 1-35	
	2N4091 0-15	AD178 0-21	BC184 0-13	BF154 0-16	LM594 1-50	OC23 1-35	
	2N4092 0-15	AD179 0-21	BC184 0-13	BF154 0-16	LM595 1-50	OC23 1-35	
	2N4093 0-15	AD180 0-21	BC184 0-13	BF154 0-16	LM596 1-50	OC23 1-35	
	2N4094 0-15	AD181 0-21	BC184 0-13	BF154 0-16	LM597 1-50	OC23 1-35	
	2N4095 0-15	AD182 0-21	BC184 0-13	BF154 0-16	LM598 1-50	OC23 1-35	
	2N4096 0-15	AD183 0-21	BC184 0-13	BF154 0-16	LM599 1-50	OC23 1-35	
	2N4097 0-15	AD184 0-21	BC184 0-13	BF154 0-16	LM600 1-50	OC23 1-35	
	2N4098 0-15	AD185 0-21	BC184 0-13	BF154 0-16	LM601 1-50	OC23 1-35	
	2N4099 0-15	AD186 0-21	BC184 0-13	BF154 0-16	LM602 1-50	OC23 1-35	
	2N4100 0-15	AD187 0-21	BC184 0-13	BF154 0-16	LM603 1-50	OC23 1-35	
	2N4101 0-15	AD188 0-21	BC184 0-13	BF154 0-16	LM604 1-50	OC23 1-35	
	2N4102 0-15	AD189 0-21	BC184 0-13	BF154 0-16	LM605 1-50	OC23 1-35	
	2N4103 0-15	AD190 0-21	BC184 0-13	BF154 0-16	LM606 1-50	OC23 1-35	
	2N4104 0-15	AD191 0-21	BC184 0-13	BF154 0-16			



GIRO NO. 331 7056 ACCESS ACCEPTED
C.V.V.O. only. P. & P. 15p on orders below £5
Discount: £10-10%, (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS (Prices include post & packing)
10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.95 net
25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
5 1/2W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £3.45 net
DUE TO CURRENT WORLD SHORTAGES, RESISTOR KITS MAY TEMPORARILY CONTAIN
WATTAGE OR VALUE SUBSTITUTIONS.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 3p, 0-068µF, 1p, 0-1µF, 4p, 0-15µF, 5p, 0-22µF, 6p, 0-33µF, 8p, 0-47µF, 10p, 0-68µF, 13p, 1µF, 15p, 1-5µF, 24p, 2-2µF, 27p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 3p, 0-068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3p, 0-047µF, 0-068µF, 0-1µF, 4p, 0-15µF, 7p, 0-22µF, 9p, 0-33µF, 13p, 0-47µF, 15p.
160V: 0-01µF, 0-015µF, 0-022µF, 3p, 0-047µF, 0-068µF, 4p, 0-1µF, 4p, 0-15µF, 5p, 0-22µF, 6p, 0-33µF, 7p, 0-47µF, 9p, 0-68µF, 13p, 1µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0-01, 0-015, 0-022, 0-033, 0-047, 24p, each. 0-1, 30V, 50p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 44p.

RESISTORS

W. Type Range	1-99	100-499	500-999	1000+	Size mm
CF 22-1M	1	0-80	0-65	0-60	2-4x7-5
CF 22-2M2	1	0-80	0-65	0-60	3-9x10-5
CF 22-1M	1	0-80	0-65	0-60	5-5x16
MF 10-2M7	2	1-7	1-4	1-2	3x7
MF 10-2M2	2	1-6	1-3	1-1	4-2x10-8
MF 10-10M	3	1-98	1-81	1-65	6-6x13
2 MF 10-10M	4-5	3-52	3-08	2-75	8x17-5

For value mixing prices, please refer to our catalogue. (price in pence each)
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0-25W Vertical or horizontal 7p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 7p each

(E.E.) 59, NORTH STREET,
LEIGHTON BUZZARD BEDS.
Tel. Leighton Buzzard 2316 (Std. Code 05253)
CATALOGUE No. 4-20p

B. H. COMPONENT FACTORS LTD.

Miniature Mullard Electrolytics		VEROBOARD 0-1 0-15		POTENTIOMETERS	
1-0µF 63V 7p	68µF 63V 14p	24 x 5"	36p 36p	Carbon Track 5K Ω to 2M Ω, log or lin. Single, 17p Dual Gang 43p. Log Single with switch 28p	Slider Pots. 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 35p.
1-5µF 63V 7p	100µF 10V 7p	24 x 3 1/2"	33p 25p	DIODES	
2-2µF 63V 7p	100µF 25V 7p	38 x 5"	42p 46p	IN4001 6p	DIN 2 Pin 12p
3-3µF 63V 7p	100µF 63V 17p	38 x 3 1/2"	36p 36p	IN4002 7p	3 Pin 12p
4-7µF 63V 7p	150µF 16V 7p	24 x 5"	10p 9p	IN4003 9p	5 Pin 180° 16p
6-8µF 63V 7p	150µF 63V 17p	24 x 5" (Plain)	— 19p	IN4004 9p	Std. Jack 20p
10µF 25V 7p	220µF 6-4V 7p	24 x 3 1/2" (Plain)	— 19p	IN4005 12p	2.5mm Jack 13p
10µF 63V 7p	220µF 10V 7p	5 x 3 1/2" (Plain)	— 29p	IN4006 14p	Phone 7p
15µF 63V 7p	220µF 16V 8p	Insertion tool	73p 73p	IN914 7p	SOCKETS
15µF 63V 7p	220µF 16V 8p	Track Cutter	56p 56p	IN916 7p	DIN 2 Pin 10p
16µF 40V 7p	220µF 63V 25p	Pins, Pkt. 50	22p 22p	BA100 10p	3 Pin 10p
22µF 25V 7p	330µF 16V 14p	TRANSISTORS		OA5 42p	5 Pin 180° 12p
22µF 63V 7p	330µF 63V 28p	AC127 21p	BC212L 13p	OA47 9p	Std. Jack 18p
32µF 10V 7p	470µF 6-4V 8p	AC128 22p	BC213L 13p	OA81 11p	2.5mm Jack 13p
33µF 16V 7p	470µF 40V 25p	BC107 12p	BC214L 18p	OA200 8p	Phone 7p
33µF 10V 7p	680µF 16V 17p	BC108 12p	OC44 19p	STOP PRESS	
37µF 40V 7p	680µF 40V 28p	BC109 13p	OC71 13p	Our Retail Shop	Screwed Wire, Metre 7p
47µF 25V 7p	1000µF 16V 25p	BC148 13p	OC81 17p	in now open	Twin Screwed Wire, Metre 13p
47µF 63V 8p	1000µF 6-4 17p	BC149 13p	OC170 29p	in North St.,	Stereo Screwed Wire, Metre 21p
68µF 16V 7p	1500µF 16V 28p	BC182L 13p	TI543 34p	Leighton Buzzard	Connecting Wire, All colours, Metre 21p
	2200µF 10V 28p	BC183L 13p	2N2926 13p		Neon Bulb, 90V Wire Ended 5 for 25p
	3300µF 6-4 28p	BC184L 14p	2N3702 14p		Panel Neon, 240V Red, Amber, Clear 21p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans		METALISED PAPER CAPACITORS	
(µF/V): 125, 2125, 425, 4-7/10, 525, 825, 10/10, 10/50, 16/25, 22/5, 22/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100 90p, 2000/25, 30p, 2000/100, 95p, 2500/25, 38p, 2500/50, 68p, 3000/50, 80p, 5000/25, 69p, 5000/50, £1-20.	HI-VOLT: 8/350, 23p, 16/350 35p, 32/350, 38p, 50/250, 27p, 100/100, 27p, 100/250, 40p, 32/500, 46p, 16-4-32 & 32/350, 65p.	METALISED PAPER CAPACITORS	
250V: 0-05µF, 0-1µF, 6p, 0-25, 6p, 0-5µF, 7p, 1µF, 9p, 500V: 0-025, 0-05, 6p, 0-1, 6p, 0-25, 7p, 0-5, 9p, 1000V: 0-01, 11p, 0-022, 13p, 0-047, 0-1, 19p, 0-22, 28p, 0-47, 36p.		5E12 1W METAL FILM. 5 each Value 10Ω-1M. Total of 305 £3.75. NET	

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

This 76 page FREE book shows how!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Electrical Engineering <input type="checkbox"/>	General Radio and TV Engineering <input type="checkbox"/>	CITY AND GUILDS Electrical Technicians <input type="checkbox"/>
Electrical Installations and Wiring <input type="checkbox"/>	Radio Servicing, Maintenance and Repairs <input type="checkbox"/>	CITY AND GUILDS Telecommunications <input type="checkbox"/>
Electrical Draughtsmanship <input type="checkbox"/>	Transistor Technology <input type="checkbox"/>	Radio Amateurs' Exam. etc. etc. <input type="checkbox"/>
Electrical Mathematics <input type="checkbox"/>	CITY AND GUILDS Installations and Wiring <input type="checkbox"/>	
Electronic Engineering <input type="checkbox"/>		
Computer Programming <input type="checkbox"/>		

ALDERMASTON COLLEGE
Dept EEV 05/Reading RG7 4PF

NAME (Block Capitals Please) _____

ADDRESS _____

POSTCODE _____

Other subjects _____ Age _____

Accredited by C.A.G.C. Member of A.B.O.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

QUALITY STEREO SOUND.

ALMOST 1/2 PRICE OFFER! SOLENT AUDIO SYSTEM

£5 down

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM

OUR PRICE £49-95

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49-95. Credit Sale £5-00 deposit 9 monthly payments of £5-75 (Total Credit price £56-75). P. & P. £3.00 Send £8.00 today.

Chassis only available for cash at £35-00.

Full 12 months Guarantee.

CALLERS WELCOME.


Stereo headphones supplied with every complete order.

LEWIS radio EE/5/75 100 CHASE SIDE SOUTHBATE LONDON N14 5PL Telephones: 01-882-1644





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

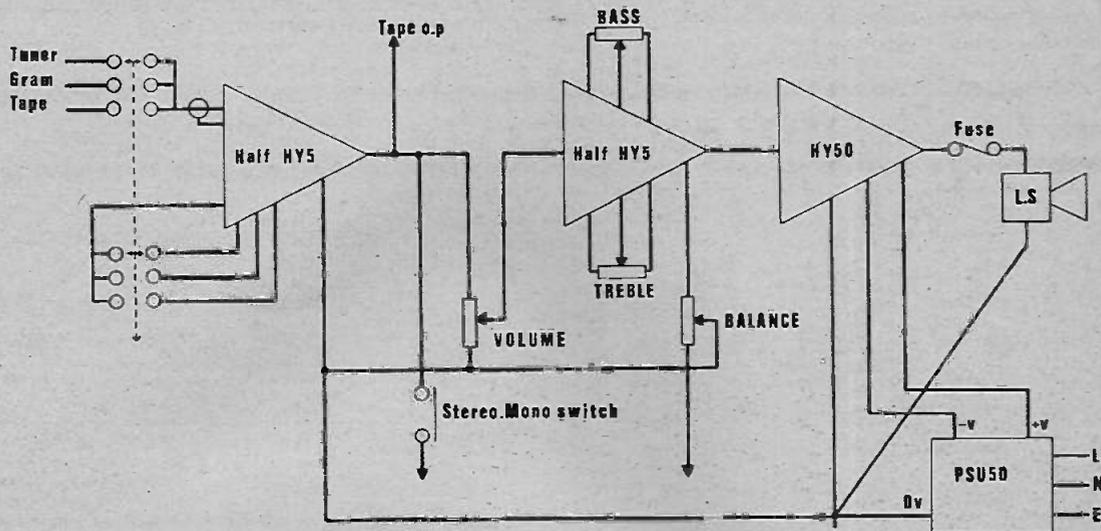

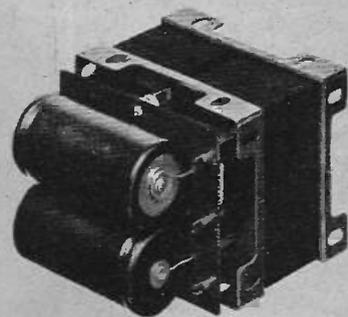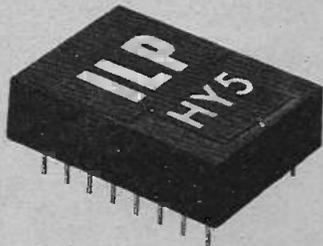MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN
POWER CONNECTIONS FROM PFU50 to HY5 NQT SHOWN FOR CLARITY OF DIAGRAM



The HY5 is a complete mono hybrid preamplifier. Ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up: 3mV RIAA; Ceramic Pick-up: 30mV; Microphone: 10mV; Tuner: 100mV; Auxiliary: 3-100mV; Input Impedance: 47kΩ at 1kHz. Outputs: Tape: 100mV; Main output: 0db (0.775V RMS). Active Tone Controls: Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 65db. Overload Capability: 40db on most sensitive input. Supply Voltage: ± 18-25V.

The HY50 is a complete solid state hybrid Hi-Fi amplifier. Incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8Ω. Load Impedance: 4-16Ω. Input Sensitivity: 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 x 50 x 25mm.

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: 50V (25-0-25V). Input Voltage: 210-240V. Size: L.70. D.90. H.60mm.

PRICE £4.50 + 36p VAT
P. & P. free

PRICE £5.98 + 48p VAT
P. & P. free

PRICE £6 + 48p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Registered Office
Tel (0227) 63218

Please supply,

Total Purchase price

I Enclose, Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account EE5

Account number

Name & Address

Signature

NEW LOW PRICES!

Sinclair Scientific kit

(Was £19.95 - save £5!)

£14.95
(INC. VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range - features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £21.55 (including VAT).

And as a kit it costs under £15!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle directly

- sin and arcsin,
- cos and arccos,
- tan and arctan,
- automatic squaring and doubling,
- log₁₀, antilog₁₀, giving quick access to x^Y (including square and other roots),
- plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer - they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

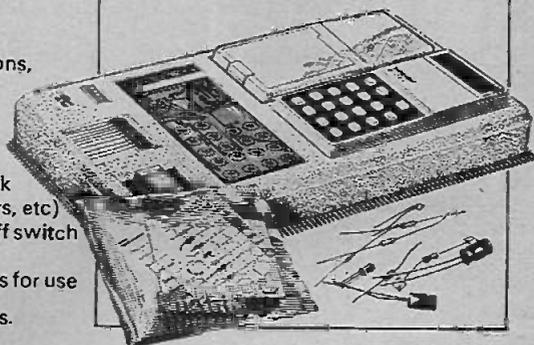

Features of the Sinclair Scientific



- 12 functions on simple keyboard
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.

- Scientific notation
Display shows 5-digit mantissa, 2-digit exponent, both signable.

- 200-decade range
10⁻⁹⁹ to 10⁺⁹⁹.

- Reverse Polish logic
Post-fixed operators allow chain calculations of unlimited length - eliminate need for an = button.

- 25-hour battery life
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.

- Genuinely pocketable
4 1/3" x 2" x 11/16".
Weight 4 oz. Attractively styled in grey, blue and white.

everyday electronics

PROJECTS..
THEORY....

WHAT EVERYONE NEEDS

It is small and portable, sometimes pocket size. Indispensable to the likes of readers of EVERYDAY ELECTRONICS, it is available in a great variety of forms, of varying specifications. It may cost anything from a fiver to twenty-five pounds (or more) and its country of origin might be Japan, Italy, Russia or Yugoslavia, or even the U.K. What is it? Well it is not a transistor radio nor is it a miniature calculator. What we have in mind at the moment is a multimeter.

Yes, a multimeter is an essential instrument for anyone who wishes to become involved practically in electronics. It is an initial purchase that should turn out to be a good investment. For if the choice is carefully made the instrument should give service for an indefinite number of years. Provided of course that it is at all times treated with respect, handled with care and used intelligently.

The number and variety of popular and inexpensive multimeters on the market is quite staggering. Selection can therefore be a problem, especially for the inexperienced. The purpose of our special supplement this month is to assist newcomers in this important matter. The information provided concerns not only the factors which should govern the buyers' choice, but also the everyday use of a multimeter. This is every bit as important. Remember the instrument's life will be literally in your hands!

MUTUAL AID

Rising costs of labour and materials hit the headlines every day. They also hit our pockets, as everyone is all too well aware. In the publishing business as elsewhere it is impossible to escape the consequences of these difficult economic times. The printing of issues of this magazine in excess of actual advance orders from the trade, for example, cannot be justified. Cost apart, paper is after all a valuable commodity which is in short supply throughout the world.

We would like our readers to understand this and see the advisability of giving a firm order to their newsagent. The local supplier will greatly appreciate this, and please do remember that he is in business to make a living and cannot take chances by buying copies of magazines from his wholesaler just on spec.

To ensure that you get your own copy of EE every month, please advise your newsagent—don't leave it to chance. We hate hearing of disappointed would-be readers. Do as we suggest and everyone involved in the production and distribution of this magazine will be happy. So will you.

Fred Bennett

Our June issue will be published on Friday, May 16

EDITOR F. E. Bennett • ASSISTANT EDITOR M. Kenward • TECHNICAL EDITOR B. W. Terrell B.Sc.
ART EDITOR J. D. Pountney • P. A. Loates • K. A. Woodruff
ADVERTISEMENT MANAGER D. W. B. Tilleard

© IPC Magazines Limited 1975. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Everyday Electronics Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.

EASY TO CONSTRUCT SIMPLY EXPLAINED



VOL. 4 NO. 5

MAY 1975

CONSTRUCTIONAL PROJECTS

THE MINSTREL A stylus operated miniature organ by P. Mills	244
WARNING WINKER Be a Battery EconoMISER by George Hylton	250
CAR ALARM Simple burglar alarm by D. T. Goodwin	260
M.W./L.W. TUNER A superhet. design for most amplifiers by R. A. Penfold	268

GENERAL FEATURES

EDITORIAL	242
RUMINATIONS by Sensor	249
WORKSHOP PRACTICE Part 2 Professional Finish by Mike Hughes	252
YOUR CAREER IN ELECTRONICS The Importance of Qualifications by Peter Verwig	256
BRIGHT IDEAS Readers' constructional hints	258
SHOP TALK Components for constructional projects by Mike Kenward	259
JACK PLUG AND FAMILY Cartoon	259
PLEASE TAKE NOTE	262
PHYSICS IS FUN More on Home-Made Capacitors by Derrick Daines	264
FOR YOUR ENTERTAINMENT Sensurround and "flat" batteries by Adrian Hope	265
COUNTER INTELLIGENCE A retailer comments by Paul Young	266
PROFESSOR ERNEST EVERSURE The Extraordinary Experiments of. by Anthony J. Bassett	275
DOWN TO EARTH Loop gain by George Hylton	280

Publisher's Annual Subscription Rate, including postage Inland £3.55, Overseas £3.60, USA/Canada \$10. International Giro facilities Account No. 5122007. State reason for payment "message to payee". Address to Everyday Electronics, Subscription Department, Carlton House, Great Queen Street, London, WC2E 9PR. Binders for volumes 1 to 4 (state which) and indexes for volume 1 and 2 available for £1.25 and 30p respectively, including postage, from Binding Department, at the above address.

We are unable to supply back copies of Everyday Electronics or reprints of articles and cannot undertake to answer readers' letters requesting designs, modifications or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, both at the address shown opposite.

An INDEX for Vol.3

**WILL BE INCLUDED WITH
NEXT MONTH'S
Everyday Electronics**

A portable electronic musical instrument

MODERN electronic organs are sophisticated pieces of equipment, but a lot of fun can be had with the simple one-octave organ described in this article.

The circuit can be split into two distinct parts, first the oscillator which uses a unijunction transistor, for simplicity, and secondly the audio amplifier, consisting of a driver stage and a complementary output stage.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Minstrel is shown in Fig. 2. Operation of the oscillator is easiest understood with reference to Fig. 1, a basic unijunction relaxation type oscillator.

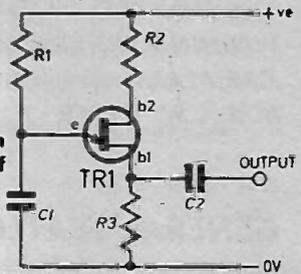


Fig. 1. A unijunction oscillator, the basis of the Minstrel.

When the supply is first connected, the capacitor $C1$ begins to charge up via $R1$ causing the emitter of $TR1$ to rise. At a certain voltage level, called the threshold voltage, the capacitor is able to almost instantaneously discharge through the unijunction from emitter to base 1 and via $R3$ to ground. This results in a positive pulse at base 1 developed across $R3$.

Serenade
your
Lady
with



the
Minstrel

By P. MILLS



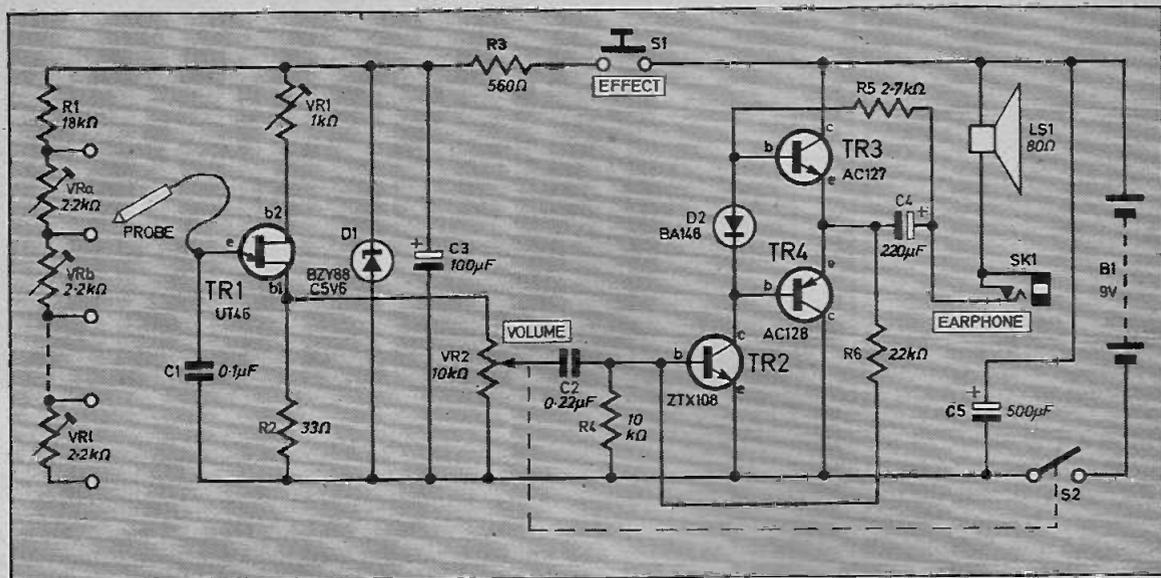


Fig. 2. The complete circuit diagram for the Minstrel.

When this has happened the capacitor begins to charge up again and the above process is repeated and continues for as long as the battery is connected, resulting in a train of pulses. The frequency of these pulses is proportional to the values of $C1$ and $R1$. Keeping $C1$ constant and varying $R1$ will change the pitch of the output tone.

In the circuit of Fig. 1 $R1$ has been replaced by a string of potentiometers, VR_a to VR_i , and by adjusting these values a set of frequencies can be generated (one at a time) to form a musical octave.


The frequency of the oscillator varies with the supply voltage; to help reduce this effect Zener diode $D1$ has been incorporated in parallel with reservoir capacitor $C3$. Potentiometer $VR2$, across $b1$ load resistor serves as a volume control and the output from the latter is coupled to the amplifier by d.c. blocking capacitor $C2$.

AUDIO AMPLIFIER

The audio amplifier is a conventional complementary output stage, $TR3$ and $TR4$ being fed from the driver transistor $TR2$. Diode $D2$ provides base bias for the output transistors and $R6$ provides some negative feedback. The cur-

FOR
GUIDANCE
ONLY

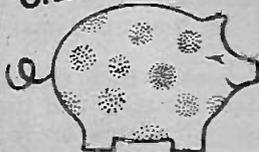ESTIMATED COST*
OF COMPONENTS
including V.A.T.



£4.50
excluding case

*Based on prices prevailing at time of going to press

Components

Resistors

R1	18kΩ
R2	33Ω
R3	560Ω
R4	10kΩ
R5	2.7kΩ
R6	22kΩ
All ½W ± 10% carbon	

SEE
**SHOP
TALK**

Potentiometers

VR1	1kΩ horizontal skeleton preset
VR2	10kΩ log. with s.p.s.t. switch
VR _a	VR _i 2.2kΩ horizontal skeleton presets (12 off)

Capacitors

C1	0.1µF
C2	0.22µF
C3	100µF elect. 10V
C4	220µF elect. 10V
C5	500µF elect. 10V

Semiconductors

TR1	T1S43 or UT46 unijunction
TR2	BC108 or ZTX108 silicon npn
TR3	AC127 germanium npn
TR4	AC128 germanium pnp
D1	BZY88C5V6 400mW Zener (5.6V)
D2	BA148 or any similar silicon diode

Miscellaneous

LS1	80 ohms 75mm diameter
SK1	3.5mm switched earphone socket
S1	push-to-break switch
B1	9V PP9
Veroboard: 0.1in. matrix 41 strips x 36 holes; printed circuit board size 94 x 45mm; battery clips; wander plug for probe; veropins; plastic case size 22 x 14 x 8cm (approx); multistrand flexible wire.	

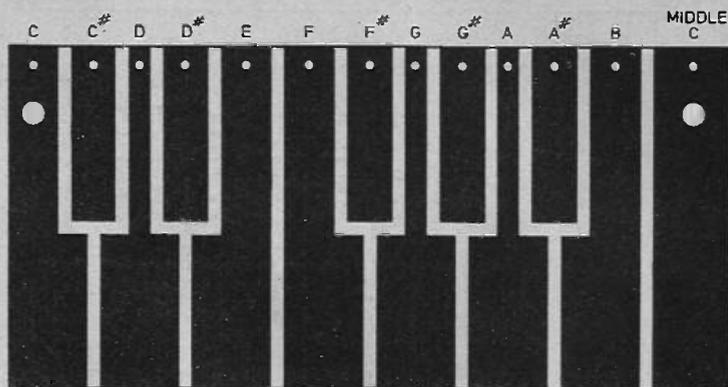


Fig. 3. The master drawing of the Minstrel Keyboard, shown full size. The black areas indicate the regions of copper to remain after etching.

rent drain is about 30 milliamps, so a PP9 battery should last for a long time.

An effect button has been incorporated that produces a tremolo-like effect if pressed rapidly whilst the unit is being played. When this is depressed the supply to the oscillator is cut off.


KEYBOARD

The keyboard was made from a piece of printed circuit board, dimensions 94 x 45mm. Shown in Fig. 3 is a master drawing of the keyboard (shown full size) where the black regions indicate the areas of copper to remain after etching.

With reference to Fig. 3 the black regions should be marked with an etchant resist, such as a Dalo pen, enamel paint or nail varnish, and allowed to dry. The board should then be placed in a dish of ferric chloride solution and left until all the unwanted copper has dissolved.

Etching time will depend on solution strength but can be accelerated by warming the solution and constant agitation.

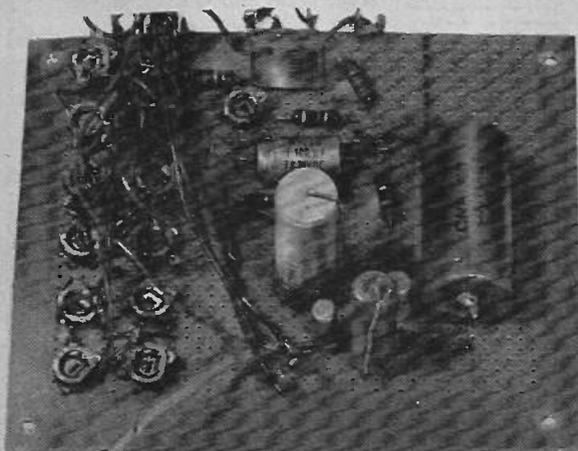When etching is complete, the board should be removed with a pair of tweezers and thoroughly washed under a running tap. Care should be taken not to get the ferric chloride



Photograph of the completed prototype component board.

solution on the body or clothing as it is a very corrosive chemical and poisonous. Always wash hands immediately after using this chemical.

Finally clean off the etchant resist with an abrasive powder and drill the fixing and wiring holes. Suitable lengths of wire should now be soldered to each of the copper areas via the holes; it is recommended that different wire colours be used so as to avoid confusion. If this is not available, each keyboard wire should be labelled by its note i.e. C, C#, D etc.

CONSTRUCTION


Most of the components are mounted on a piece of 0.1in. matrix Veroboard size 41 strips by 36 holes. Begin by drilling the fixing holes and making the breaks along the copper tracks on the underside as shown.



Photograph of the Minstrel completed, with lid removed.

Next insert the Veropins as indicated and position and solder the components as detailed in Fig. 4. The transistors should be soldered in last of all, observing their lead-out connections and a heatshunt used so as to avoid thermal damage by the soldering iron.

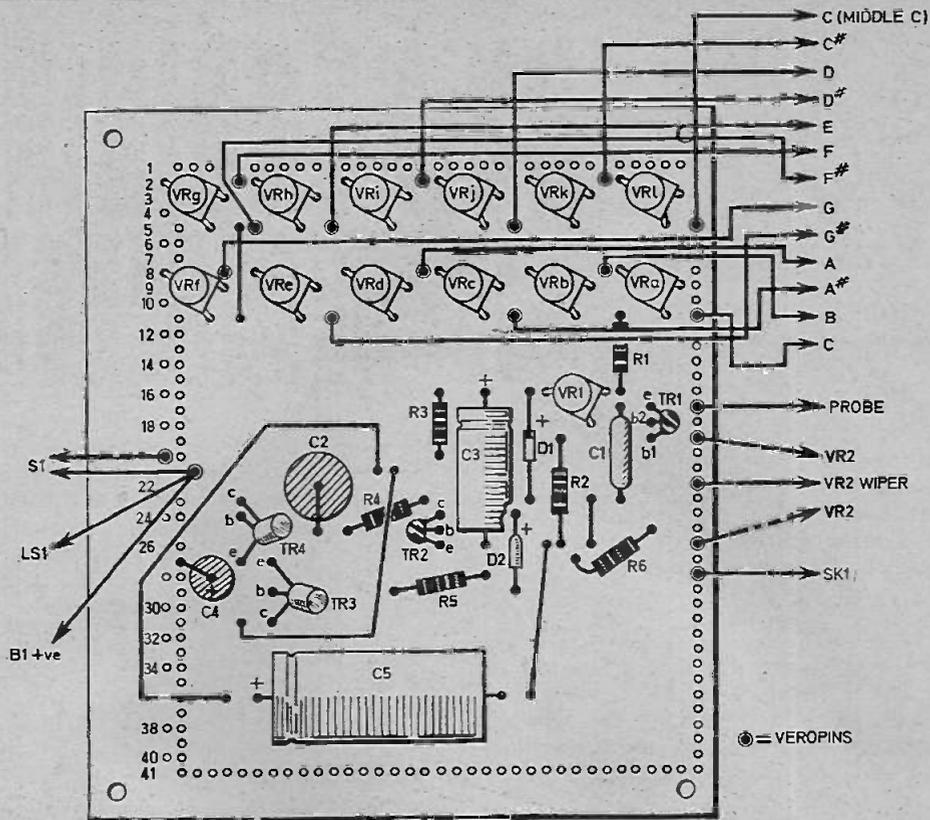The prototype unit was housed in a plastic case size 22 x 14 x 8cm approximately and the remainder of the components mounted on the removable lid, see Fig. 5.



ABCDEF GHI JKLMNOPQRST UVWXYZAA CC EE GG II

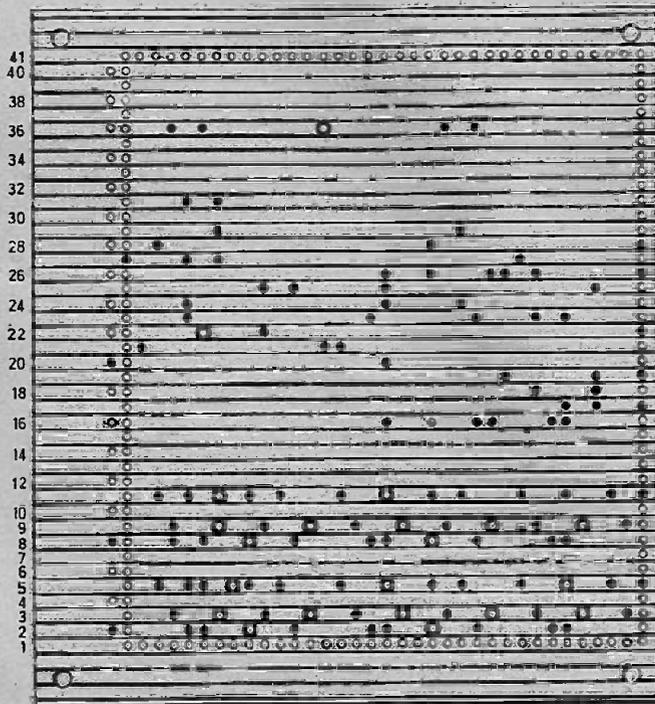


Fig. 4. The layout of the components on the Veroboard and the cut-outs to be made along the copper strips on the underside.



the minstrel

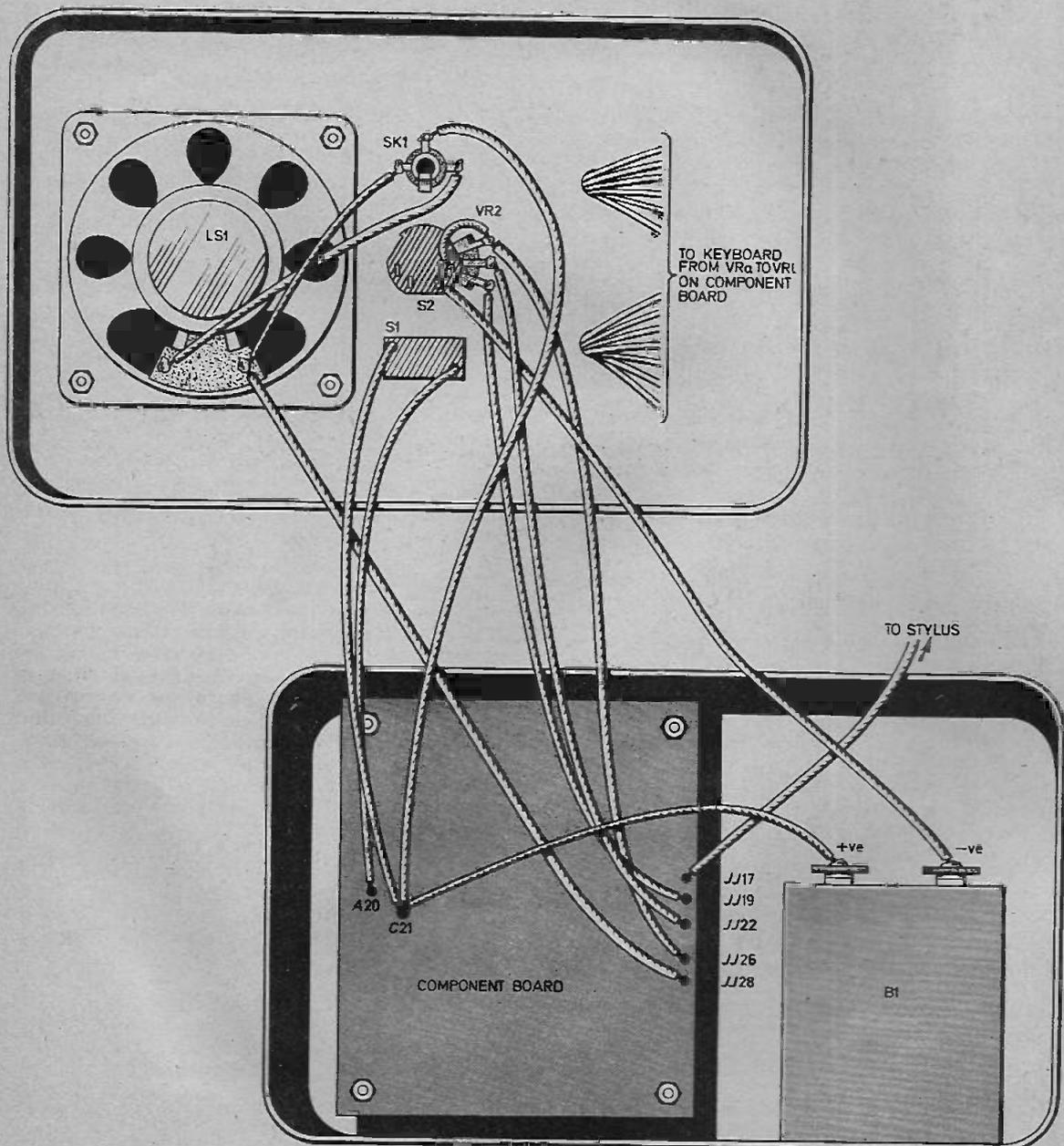


Fig. 5. Complete wiring up details and layout of the components.

Prepare the lid to accept components LS1, VR2 and S1. Drill two holes near to where the keyboard is to be cited and pass the keyboard wires through these holes in two convenient groups. Glue the keyboard to the outside lid and cover the wiring with a piece of moulded wood, see photograph below.

Now secure the lid components in position and wire up to the component board at the Veropin locations. Next connect the battery terminals and secure the board to the base of the case using four self-tapping screws. The flying lead from location JJ17 should now be passed out through a hole in the side of the case and terminated in a wander plug. This will be the probe or stylus.


Finally glue a piece of speaker covering over the speaker cut-out and the unit is ready for testing and setting up.

TESTING AND SETTING UP

First turn all the skeleton preset potentiometers VR_a to VR₁ (including VR1) so that they give minimum resistance and turn on at VR2. Place the probe in contact with the highest note on the keyboard, and with the aid of a piano, or other instrument set VR1 to give a middle C note. This will put the other notes, when adjusted, on the right part of the scale. Next place the probe in contact with the next key down, and adjust VR_a to give note B. The rest of

the notes are tuned in a similar fashion.

If the unit does not work, check that the components are soldered in the right positions, observing the polarities of electrolytic capacitors and diodes, and check the leadouts of the transistors. Also place a meter in one of the battery leads, this should read around 30mA. The voltage at the emitters of the output transistors to ground should be about 4.5 volts, and the voltage across the Zener diode D1 should be about equal to the nominal Zener voltage. □

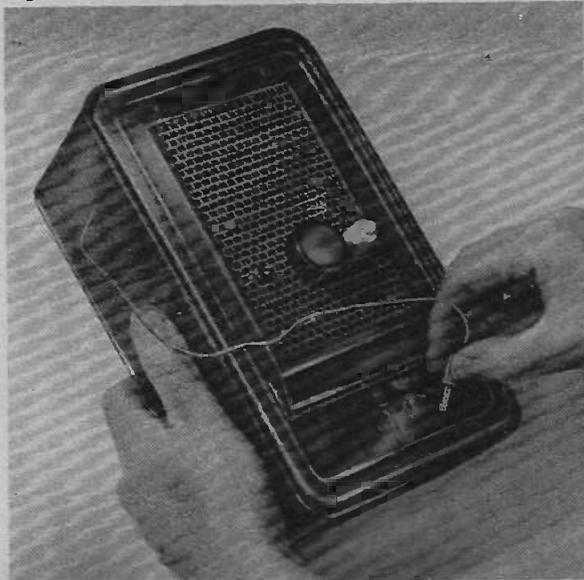

Ruminations

By Sensor

Smaller and Smaller

Larger scale integration, or l.s.i. is quietly creeping into all branches of electronics. Pocket calculators containing just one l.s.i. circuit are now common and the "one chip" radio has been with us for some time. Extremely complex circuits can now be manufactured by semiconductor techniques, all one has to do is to provide the input signal, the power, and the output equipment. By "output equipment" I mean the loudspeaker, cathode ray tube, numerical display or whatever is required to sense the output signals from the device. For without some means of "talking" to the circuit (the input signal) and some means of listening to the circuit (the output signal)

there is just no point in having the circuit at all!

Generally speaking, which is always a dangerous thing to do, it seems to me that as the "works" get smaller the output device gets bigger. We demand larger television screens, our search for high fidelity leads us to larger speakers and enclosures, calculators are required to have a bright, easily read display. And, yet the real "business" part continues to shrink. It would seem that we ought to be working to find a better way of receiving information into our minds.

Taking It In

Since all these circuits merely take in electrical impulses and operate upon them, albeit in complex fashion, and since our brains also function by sensing electrical impulses generated by external stimuli, then, it must be possible to bypass our senses, hearing and vision for example and stimulate our minds directly. I have read the neuro-surgeons have been able

to do this kind of thing activating certain areas of the brain by tiny impulses applied by probes. The patient has been made for example to experience the sensation of tasting onion by placing the probes in a particular position.

I don't know just how this "direct link" with our brains could be achieved, and I am certainly not suggesting that we should undergo major surgery in order to accomplish it, but there would seem to be a great potential field to explore in this direction. The electronics engineer would certainly have a part to play, but the neurologist, bio-chemist, and no doubt others would have a great deal of work to do before results could be expected.

Just think of the benefits, we could each "listen" to our own choice of programmes, "watch" our own television show without disturbing the rest of the family (or the neighbours), the bulky loudspeakers and cathode ray tubes would no longer be required—just one or two l.s.i. circuits!

be a battery econoMISER with the

WARNING WINKER...

By George Hylton



A visual indication that battery operated equipment is switched on

Now that light-emitting diodes are obtainable cheaply it is practicable to use them as pilot lights. Being small and of a distinctive colour (usually red) they are made for the job, except for one thing. That is their current consumption, which, though less than an average pilot bulb's, is still great enough to discourage their use in really low-consumption battery equipment.

The usual red l.e.d.s. begin to light up at 10 milliamps and are fairly bright at 20 milliamps. This is often greater than the standby consumption of the battery equipment itself. It is clearly very wasteful to use a l.e.d. just to remind you to switch the equipment off if the penalty is to double or treble the consumption when it is on.

CIRCUIT THEORY

A way out of the difficulty is to make the pilot lamp flash intermittently. Then, even if the peak current is high enough to produce a bright flash, the mean current can still be kept low.

One way to achieve intermittent flashing is to build the l.e.d. into a relaxation oscillator circuit. One such circuit is shown in Fig. 1 and uses one npn and one pnp transistor. This "complementary" circuit can be made to have long "off" periods and short "on" periods, and also, it needs only one capacitor.

When the circuit is on, both transistors conduct. The current through D1 is now the emitter current of TR2, and for safety this must be kept below the maximum d.c. current limit as specified by the manufacturer. For the specified Motorola MLED 500 used in this circuit this limit is 100 milliamps.

The emitter current of TR2 is of course the sum of the base current and the collector current. The base current is limited to a small value by R2. (Even if TR1 becomes a short-circuit not more than about 7 milliamps can flow through R2.)


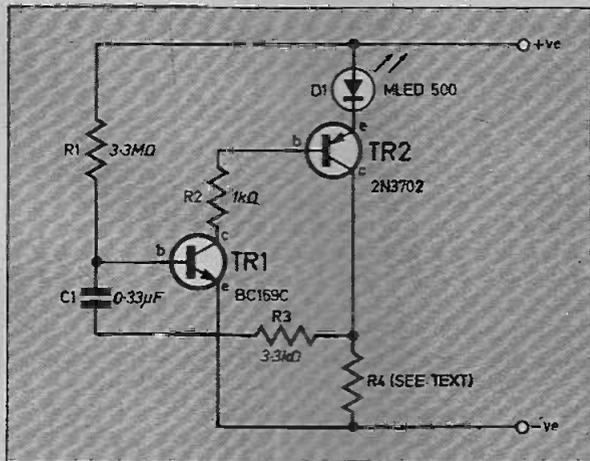


Fig. 1. The circuit diagram for the Warning Winker.

The collector current of TR2 depends on the sum of the voltage drops across D1 (about 1.6 volts), across TR2 (emitter to collector) and across R4. The voltage across TR2 is an uncertain quantity but it is not very large. To be on the safe side, R4 should be selected so that even if TR2 becomes a short circuit the current limit for the l.e.d. will still not be reached. Since the l.e.d. drops about 1.6 volts, this leaves, with a 9 volt supply, a maximum of about 7.4 volts across R4. If R4 is 100 ohms, as in Fig. 1, the current cannot exceed 74 milliamps, which

FOR GUIDANCE ONLY

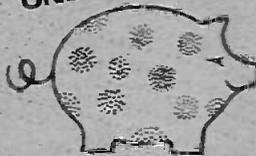ESTIMATED COST* OF COMPONENTS including V.A.T.



£0.65

*Based on prices prevailing at time of going to press

Components

Resistors

- R1 3.3M Ω
- R2 1k Ω
- R3 3.3k Ω
- R4 See text and Table 1
- All $\frac{1}{4}$ watt \pm 10% carbon

SEE
**SHOP
TALK**

Semiconductors

- TR1 BC169C silicon npn
- TR2 2N3702 silicon pnp
- D1 MLED light-emitting diode

Miscellaneous

- C1 0.33 μ F
- Plain matrix board, 0.15in. matrix 13 x 13 holes; Veropins; connecting wire.

allows a margin of safety for resistor tolerances and other circuit variables. (For other supply voltages, R4 needs to be altered. The appropriate value for the MLED 500 *only* is given in Table 1).

PULSE LENGTH

Although the circuit has been designed for safety in terms of the d.c. current limit for the l.e.d., in actual operation the current flows in pulses. It is important that each pulse should last long enough for the eye to see the flash of light clearly. If the flash is too short, it appears faint.

The duration of the on period of the oscillation is what governs the duration of the flash. During the on period, C1 charges up. With the standard form of complementary relaxation oscillator circuit, C1 charges much too rapidly. For this reason the circuit of Fig. 1 is not standard. It has been modified by putting resistor R3 in series with C1, to reduce the rate at which it charges and so prolong the flash.

Even with R3, the flash duration is quite short, so despite the fact that peak currents of up to 70 milliamps may flow, the mean current is only about 0.9 milliamps (see Table 1). In practice the peak amount is often a lot less than 70 milliamps, especially if the supply voltage is low.

The rate of flashing depends on the value of R1 x C1, and the higher this is the *slower* the flashing. A rate of roughly one flash per second is about right, and this is achieved when R1 (in

Table 1:
Circuit details for different supply voltages

Supply voltage (V)	R4 (Ω)	Mean current (mA)	Flashes per min.
8	47	0.8	90
9	100	0.85	86
12	150	0.9	83

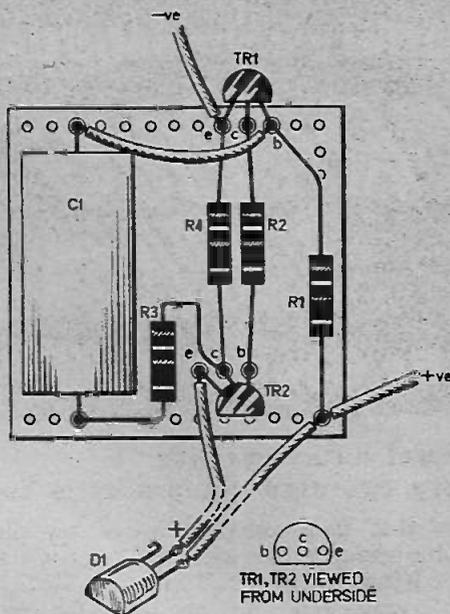


Fig. 2. The layout of the components on the matrix board and wiring up details.

megohms) times C1 (in microfarads) is equal to unity.

Since this calls for a high capacitance for C1, and since it must be a non-electrolytic capacitor, it is economic to keep R1 high in order to reduce the value of C1. This calls for a high-gain transistor for TR1, because a high R1 implies a low base current. The BC169C has a current amplification factor (h_{fe}) of 450 to 900.

CONSTRUCTION

The prototype unit was constructed on a small piece of 0.15in. plain matrix board size 13 x 13 holes. Veropins are used to anchor the component lead-out wires. The layout is shown in Fig. 2; this is not critical and may be changed to suit individual requirements. Fixing holes should be drilled where required.


Begin by inserting the Veropins and then soldering in position the capacitor, resistors flying leads and then the transistors and diode in this order. A heatshunt should be used when soldering the semiconductors so as to avoid damage to these devices.

The l.e.d. can be glued to the case of the unit to which it is to be fitted, and the connecting wires passed through a small hole drilled in the case. The l.e.d. should be glued on the flat face, since the light comes out of the curved side. The supply leads should be connected to the equipment on/off switch so that the Warning Winker is switched on with the equipment.

When operated from different voltages, R4 must be selected from Table 1 to suit the voltage. For intermediate voltages use the value for the next highest voltage; e.g. for 7.5 volts use the 9 volt value. □

Workshop Practice

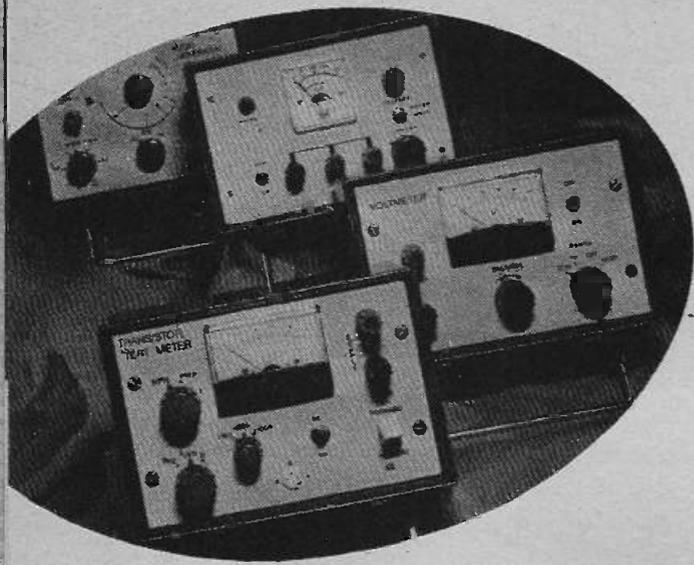By MIKE HUGHES M.I.E.R.E.
PART TWO
A Professional Finish



THIS part is really a follow-on from last month when we made a few suggestions as to how you might go about making cabinets for simple projects. Irrespective of how you go about making the cabinet or how good a craftsman you are, you can make or marr your project with the type of finish you give it. By and large we have to concern ourselves with the appearance of the cabinet and the design and lettering (if any) on the front panel. Let's deal with the cabinet first.

METAL CABINETS

These are usually made from bent aluminium or wood—plastic cabinets usually do not warrant special finishes as the material itself usually suffices. If you have used the cheaper type of aluminium box as an enclosure you will probably wonder what you can do about the unwelded corners. These always look unsightly and cannot be adequately covered or painted over. A simple solution is to fill the gaps with an epoxy resin glue (e.g. Araldite).

To do this economically and to get a good finish you should first stick a length of Sellotape down the *inside* of the corners in question and then run a thin fillet of the glue down the length of the gap on the outside, see Fig. 1. The fillet should be allowed to stand slightly proud of the gap so that it can be rubbed down when it has set.

If a bit more care is taken you can cover the outside of the fillet (while it is still fluid) with another piece of Sellotape making sure that you do not trap any air bubbles; when the glue is dry this can be stripped off to leave a nice shiny smooth curved surface.

If you have inadvertently drilled small holes in the wrong places you can use the same technique to fill the holes—provided you will be

covering the area later with paint or other material. If you use this suggestion make sure you stick a piece of Sellotape over the hole on the *outside* surface of the metal so that you end up with the epoxy resin exactly flush with the surface—a slight mound on the inside probably will not matter very much.

A cabinet is usually going to have to withstand a fair amount of handling, so it is essential that you finish off metal surfaces so that they are resilient enough to stand up to the odd knock or scrape.

Professional metal cases are usually finished off with a stove enamel, a crackle or hammer finish paint, anodising or cladding with a plastic laminate. All of these techniques tend to be outside the scope of the amateur because he does not have the necessary equipment nor the specialised materials.

The two most popular finishes to amateur grade metal cabinets are paint and self-adhesive plastic film. On the face of it there might seem little to advise one to do when using one of these methods but there are one or two little tricks which will help you obtain a good end product.

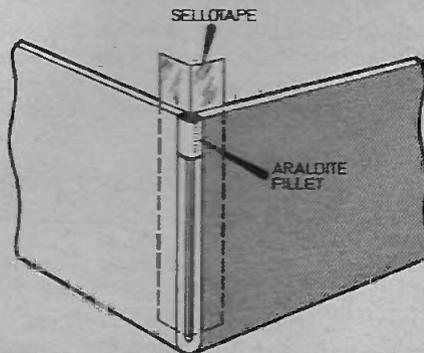


Fig. 4. Filling the gap along the edge of a bent aluminium case.

PAINING METAL CABINETS

There is no short cut to producing a good painted finish on metal. Never fall for the temptation of using an aerosol spray straight on to the unprepared metal surface—it might look nice initially but it only takes one small tap for the paint to start flaking off. The ideal method described below may sound a long winded process but can be guaranteed to give excellent long lasting results.

First, remove everything from the case, this goes for screws which pass through the sides of the case. You *must* start with a surface that is as free as possible from protrusions. Next make absolutely sure that all the cut edges of the case have been smoothed (and rounded if necessary). Use some very fine emery cloth (that used for rubbing down car cellulose is ideal) and gently abrade the surfaces of the case by rubbing with the emery cloth in small circles. Do not worry about the fine pattern of scratches produced, these are what we need to act as a key to the layers of paint.

When you are satisfied that the surface is evenly abraded and that there are no burrs sticking up at drilling holes, you should thoroughly wash the case in a strong solution of warm water and domestic detergent. This removes the fine particles of metal dust and at the same time removes any remaining grease or oil. Dry the case well, using paper tissues, and try to avoid handling the prepared surface as finger grease can still cause problems. You are now ready to start the painting sequence.

PRIMER

Always start with a coat of primer paint; the type you choose depends on whether you intend to use cellulose spray later or ordinary oil bound domestic paints. Do not apply too much primer—if you overdo the application you might get runs down the vertical sides of the case and it is almost impossible to remove these later. If you do get runs it is better to wipe the paint off while it is still wet and start again rather than let it dry and hope for the best!

If you have a box shaped cabinet try to avoid placing it so that all four rear edges are on a newspaper as there is always a tendency for the paint to run slightly and this builds up a thickening at the edges in contact with the protective paper. It is best to stand the back edges on four lengths of matchsticks while waiting for the paint to dry as shown in Fig. 2.

Provided you are careful in brushing on the primer and make sure that there are no loose hairs in the paint brush, it should not be necessary to do any rubbing down between coats when working on metal (this, however, is not the case with wood!) and when the primer coat is completely dry you should then apply a layer of undercoat.

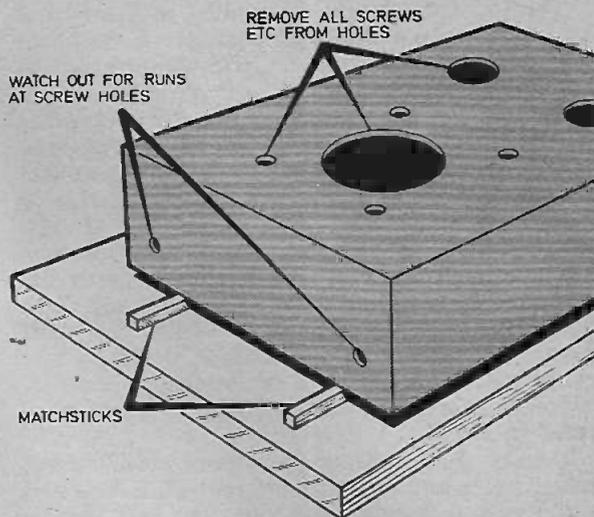


Fig. 2. When painting, stand the back of the box on match-sticks and try to keep the most important face horizontal.

Although it is a little old-fashioned, the author prefers normal oil bound household paints without any of the magical "non-drip" additives as they are usually easier to control and generally produce a better finish in the long run. Do not be tempted to use the so called, single coat "super cover" paints, as these crack and flake off easily. Likewise avoid the temptation of putting brush-on enamel paint straight on to the primer—a good oil bound undercoat will provide a better key, give resilience to knocks and produce a smoother finish when the final top coat is applied.

The undercoat, whether brushed on or sprayed on, should look as even and as free from brush marks as you would expect the top coat to be. Sometimes it might be worthwhile rubbing down gently with a *very fine* emery cloth and applying a second coat of undercoat to ensure a really high gloss finish; there is no point in doing this, however, unless you make certain that you keep your work free from dust. It is better to apply several coats of undercoat *thinly* (making sure that one is dry before applying the next) than a single thick one which might cause runs and is sure to show the brush marks.

TOP COAT

Provided you have carried out all the preparatory work as recommended, the final, and most important coat (top coat), as far as appearance is concerned, will be the easiest to apply. This can be brushed or sprayed and if you have used oil bound undercoat you can use almost any type of proprietary gloss paint for the top coat but you should *not* use spray on car cellulose unless you used a cellulose base primer and undercoat.

The top coat should be applied as thinly and as evenly as possible and probably a spray on polyurethane based paint will be easiest to handle.

Finally, before moving on to other finishing methods, a word about spraying. If ever you watch a professional sprayer at work you will see that he works in even sweeps from side to side but he stops the spray at the end of each sweep before starting on the return journey. There is a very good reason for this—it prevents a thicker build up of paint at the left and right hand edges of the job which would happen if he allowed the spray to continue while he was changing the direction of the sweep. It is worth following his example if you wish to avoid runs, refer to Fig. 3.

During the painting operations some of the screw holes and other apertures will have filled slightly; you should wait until the last coat is completely dry and then ease away the excess paint from these areas with a hand-held drilling bit or a knife. It is particularly important that you remove any paint which has dribbled round to the inside of such fixing holes as it might act as an insulator at earthing points.

SELF-ADHESIVE COVERINGS

Very attractive cabinets can be made by using self-adhesive plastic films to cover the basic

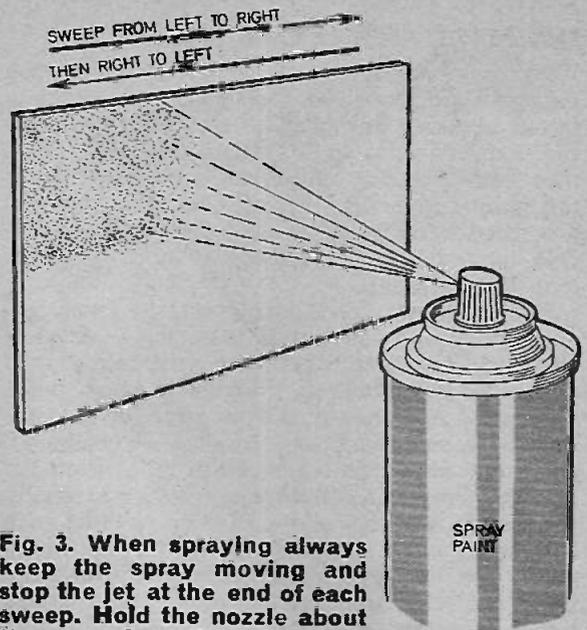


Fig. 3. When spraying always keep the spray moving and stop the jet at the end of each sweep. Hold the nozzle about 6in. away from the workpiece.

metal work. This material is known as Contact or Fablon and can be obtained in most decorating shops and Woolworths. There are some extremely attractive designs available and, in particular, you can get a very smart result by using the simulated wood grain finish.


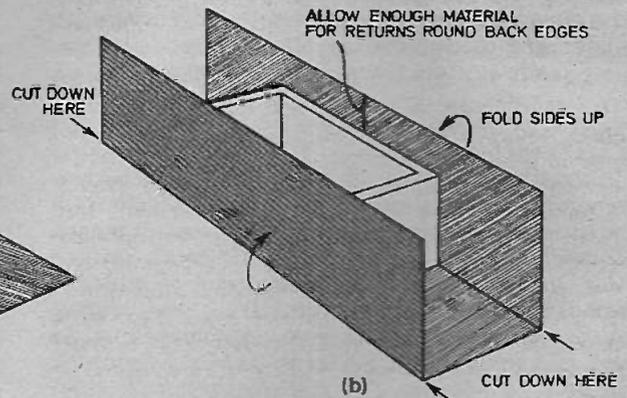
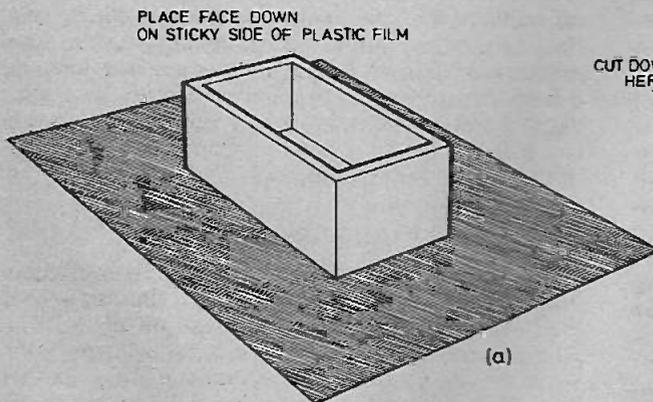
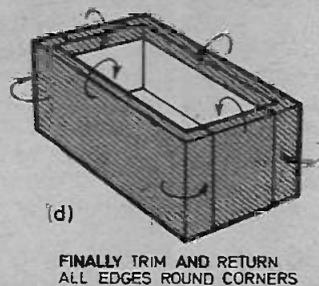


Fig. 4. Stages in covering a box with "Contact" or "Fablon".

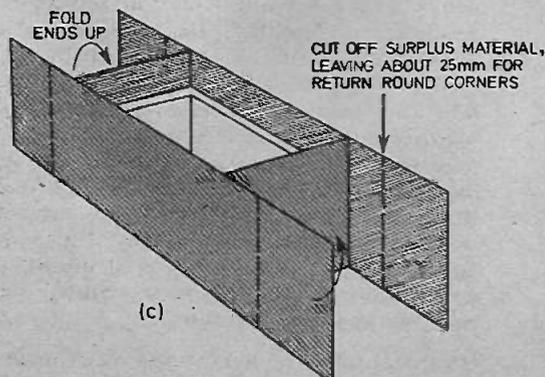

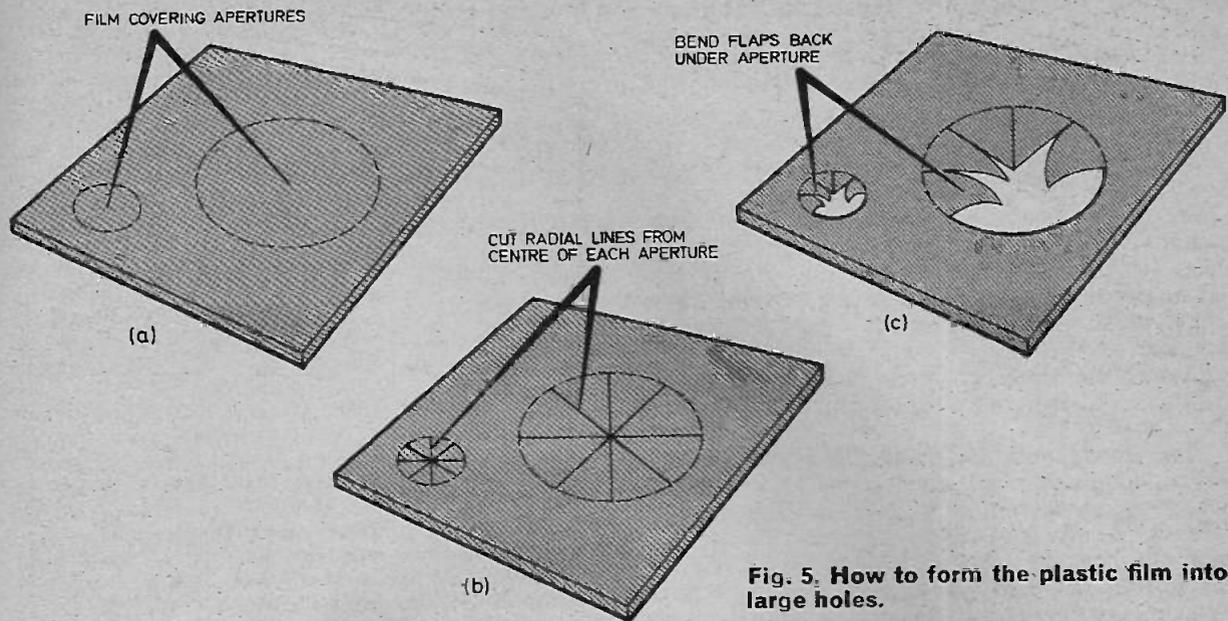


Fig. 5. How to form the plastic film into large holes.

Before deciding to use this material you should first ensure that the metal case you wish to clad will not get hot from the circuitry within it; a problem with this material is that the adhesive softens considerably at temperatures in excess of 35 to 40 degrees centigrade and at the same time it tends to shrink in its dimensions. This means that when applying it to a surface you must always return it round any edges to allow for shrinkage.

Where you have difficult corners to manage you may have to use several pieces; if so you must overlap the pieces by at least 5mm and not simply butt the edges together. Butt jointed edges will only pull apart as shrinkage occurs. Where you have such overlaps you will find, over a long period of time, that the adhesive tends to appear at the edge of the joint and this acts as a trap for dust and dirt therefore it is advisable to arrange for any such laps to be at the rear or underneath the box; Fig. 4 shows the stages in covering a box with Contact or Fablon.

As with painting you must ensure that there are no protrusions above the outside surface of the case otherwise you will deform the plastic film in trying to get it to stick. Therefore remove all nuts and bolts and any instruments which are let into the outside surface. Apart from ensuring that the surface of the metal is clean, free from grease or oil and dry, there is no need to do any other preparatory work. Before commencing to cut your material you should carefully plan where you will be returning the free edges and, in the case of wood grained plastic, you should decide whether the grain will follow the right directions when you have folded the material round corners.

At some corners you might have a problem with two butt edges meeting right on the corner;

there is very little you can do about this except to put a narrow strip of the same material over the corner so that the two free edges lap over this strip—thus hiding the gap which would otherwise ensue. Do as much of the cutting as you can with the protective backing paper in place and be very generous at the free edges.

When peeling off the backing paper try to avoid stretching the plastic film as this will only aggravate the shrinkage problem and in the worst case you might end up with creases. Having removed the backing it is not a bad idea to leave the pieces of adhesive plastic on a flat surface for a few minutes to allow any stretch to pull back before you start applying the material to the cabinet.

HOLES AND CUT-OUTS

Where you have screw holes just ignore them and stick the film straight over the top—you can carefully trim the material away with a sharp knife later. Where you have a large hole, such as an aperture for a loudspeaker, do the same but instead of trimming all the material away afterwards you should make a series of radial cuts from the centre of the aperture and push the triangular shaped flaps of material back through the hole to stick on to the reverse side of the box—the smaller the diameter of the hole the more radial cuts you will need to end up with a smooth circle see Fig. 5.

Where you have a hole for a meter it is probably best not to do this because you will reduce the internal dimension of the hole and the meter will no longer fit, and anyway, there will probably be no problem with a shrinking edge because the outside edge of the meter will return over the edge of the film.

Next month we continue on the same theme.

Your Career in **ELECTRONICS**

By Peter Verwig

A career in electronics is an exciting prospect! Month by month our contributor Peter Verwig will explain what working in electronics is all about, how to prepare yourself for a rewarding career, and the job opportunities available in the world's fastest growing industry.

THE IMPORTANCE OF QUALIFICATIONS

LAST month we gave a broad outline of the electronics industry and indicated just a few of the career opportunities open to those keen enough to graduate from just having an interest in electronics to becoming a real professional.

This month we turn our attention to the qualifications you will need to get ahead and which most employers will expect you to have, or to obtain later, before offering you a job. Don't be discouraged by the thought of having to struggle through more exams. If you have a genuine interest in electronics, the battle is more than half won. And unless you are genuinely interested then you would be better off trying something else that does interest you.

Some of your friends may scoff at your ambitions. The temptation to take the job that pays most money and has least demand on your time can be almost overpowering, especially when you are young. And it is by no means impossible to get a job in electronics without having paper qualifications. But what sort of job? And how far do you want to climb the promotional ladder?

QUALIFICATIONS

Qualifications, however modest, are always worth having. Moreover, in a world which tends towards categorisation, it is even conceivable that without adequate qualifications you will not be able to practice. This state of affairs is already with us in the medical profession. It could happen in electronics, but even if it doesn't the man or woman

who is on the register as a chartered engineer will clearly be in a far stronger position than one without such a qualification.

We shall be discussing the role of the professional institutions next month and it should be the aim of everyone to reach out for chartered status. This generally means that you will need to continue studying through to a pass degree, and also to demonstrate that you have spent some time in industry.


You will need to satisfy the examining bodies that your academic training is to an acceptable standard, that you have received professional engineering training and that you have had a period of responsible experience as an engineer.

Fortunately there are a number of routes which you can take to reach your goal and they can be taken in easy stages and very often with the active assistance of your employer. It is in his interest as well as yours that you should get ahead.

If you are still at school try to do well at your general academic work. The better you do the bigger the range of opportunities that will be available to you. If you haven't done too well it may be that you are a late developer and it is still possible to get into electronics through craft training. If you don't think you can get to degree standard you can still aim at chartered technician engineer status.

Your careers master will give you guidance. Those who have already left school can get advice through the local Further Education Centre.

An engineer engaged on thick film microcircuit technology research at Standard Telecommunication Laboratories, Harlow, Essex.

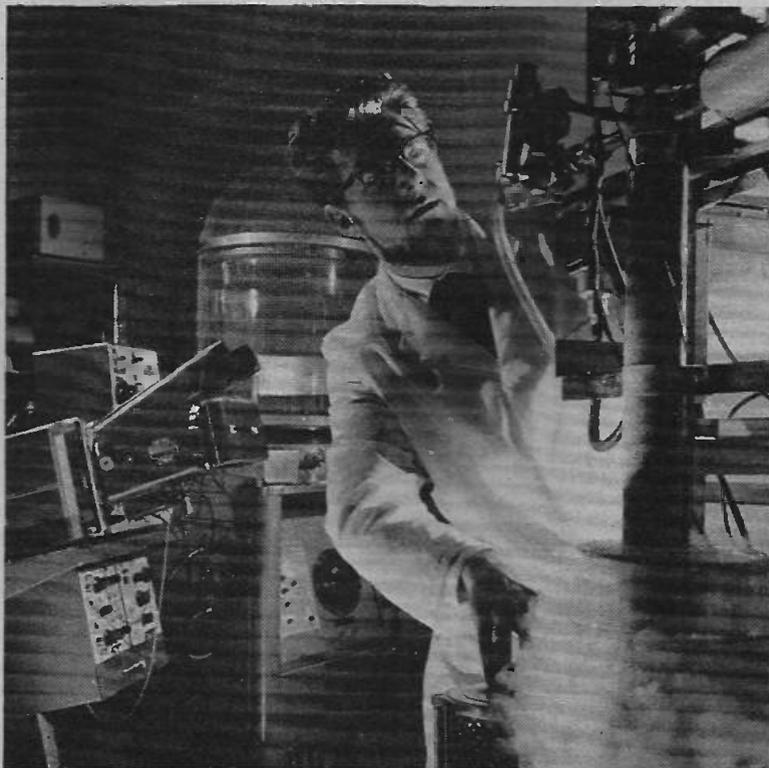

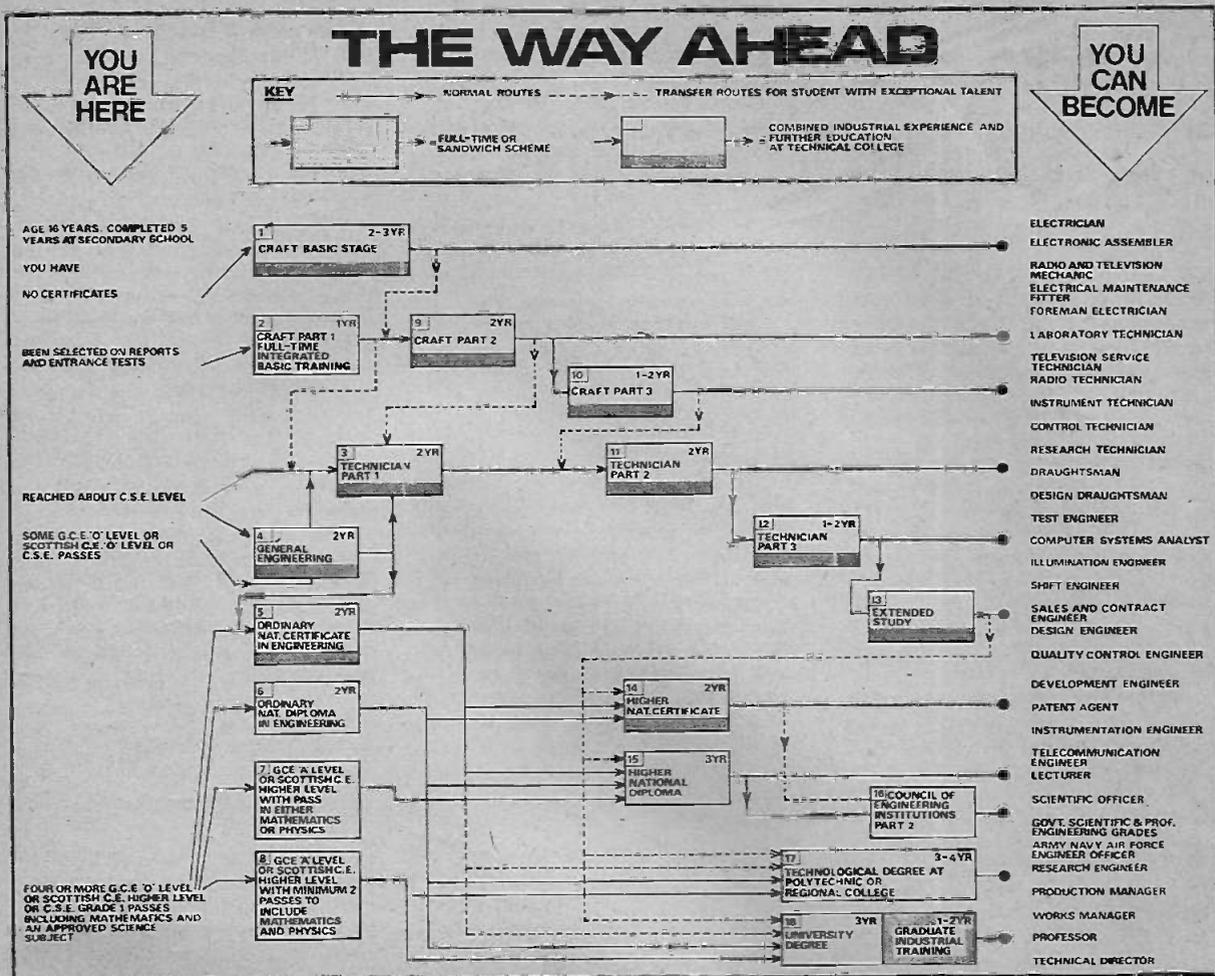


Fig. 1. The Way Ahead. As you move down the chart on the left hand side the entry qualifications become greater but the job opportunities on the right hand side become greater. But if you follow the dotted lines you will see that a craft apprentice with talent can still climb to the top grades in the industry. (Chart by courtesy of the Institution of Electrical Engineers).

EDUCATION AND TRAINING

Education and training will generally consist of education in the classroom and laboratory, and training at work. If you enter the profession with the intention of becoming a craftsman or technician then education and training is a combined operation where you do a lot of on-the-job training with part-time release to a technical college.

Normally you would join a firm straight from school and the part-time release is generally one day a week at college. An alternative is the block release when the firm releases you for several weeks of study at a time. The certificates

for which you will be studying are the part-time National Certificates or certain of the City and Guilds full technological certificates or full time National Diplomas.

If you aspire to full chartered engineer status the education and training are separate but they can be interleaved when you spend some of your time with the firm and some in education. This is known as the "Integrated Sandwich Course". But you can, for example, spend a year at work after leaving school, then do a spell at university, followed by a final period of training back at work. This is the "Thick Sandwich Scheme". Yet a third method is to go straight from school to uni-

versity and leave all your on-the-job training until you have obtained your degree.

DEGREE

Quite clearly to go on to university you will need to have good general academic qualifications to satisfy the university entry regulations. But the late developer can still climb the ladder. For example you may start in craft training and after a year or so start showing exceptional promise. In this case there is nothing to stop you transferring to a higher level of course with the intention of becoming a technician rather than a craftsman.

You may even climb eventually on to a degree course, depending on your progress. Satisfactory completion of an Ordinary National Certificate course will automatically open the door to the Higher National Certificate course. But a student who does exceptionally well in the ONC

may find the door open to a Degree or Higher National Diploma course. A good employer will encourage you in your ambition.

The length of your training will vary. Craft training extends over three years and sometimes longer. Three years or more will also be required for technician grades. A technological degree taken through a Polytechnic or Regional College will take three to four years.

A university degree coupled with sufficient graduate industrial training to satisfy the requirement for on-the-job experience will spread over five years. So whichever route you take, don't expect to become qualified overnight. It's much better to face up to the fact that it may take five years, perhaps even longer, before you are fully trained.

AFTER TRAINING

What sort of job can you

expect after your training? Craft grades will fit you for radio and TV servicing and for testing assemblies and systems and for installation work. Technician grades can expect to be laboratory assistants, could be engaged on quality control, or as draughtsment, sales engineers or, after suitable laboratory experience, could become development engineers.


Those technicians with the capability of expressing themselves could become technical authors. Those with aptitude for computer science could do a useful job as computer systems analysts.

The fully chartered engineer with requisite experience can really get ahead in the area of his choice. He can become a technical director, or works manager, a project leader with a team of development engineers working under his direction, a scientific officer in government research establishments or a technical

officer in the armed services. As a fully qualified person he may, after some years in industry, become a lecturer and help train a younger generation of entrants to the profession.

In future articles we shall discuss specific sectors of employment. But first you should think seriously about becoming qualified. The opportunities for doing so have never been greater or less costly. There are some 150 colleges in the UK with approved schemes leading to Higher National Certificates or Diplomas in Electrical and Electronic Engineering. Including the Polytechnics there are some 70 establishments where you can take a degree course.

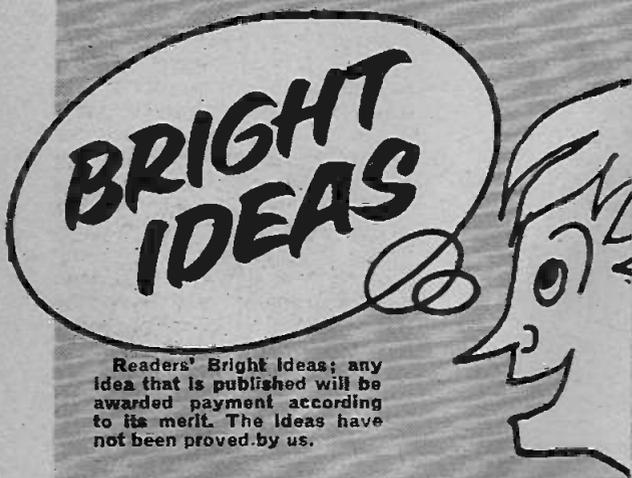And most of the larger commercial companies, public corporations and all the armed services run schemes to help you with qualifications. What could be better than to earn while you learn?



I find it hard to resist sending in a couple of ideas from this part of the world. I am an electronic hobbyist and I have found these ideas very handy and would like to share them with your readers.

Very often a service or instrument technician is faced with the difficulty of inserting a screw into a position inaccessible to a finger. By wrapping a suitable length of 18 s.w.g. solder wire around the shank, the screw can be located in position with the other hand free to screw it in. With a little effort the solder wire can be forced off the shank.

I was faced with the problem of assembling parts of instruments. Having screw locations accessible to only one finger and perpendicular to the force of gravity. I have overcome this problem by inserting a suitable length of 18 s.w.g. solder through the location, ringing the nut round the solder and while withdrawing the solder place

a finger on the nut. After the solder is fully withdrawn the nut is in position for the screw to be fitted.

A. Bertie,
Bombay.

When drilling holes in printed circuit boards to mount integrated circuits, the holes frequently show the amazing property of being able to transport themselves miraculously a millimeter or two to either side of the intended position. My method produces holes in perfect line by relying on the ability of 0.1-inch matrix Veroboard to take integrated circuits "straight off". The boards are aligned, taped down and the Veroboard holes used as guide holes for the drill. This works for 28, 14, 16 and 8 pin integrated circuits.

J. Savage,
Barnsley.

I have found a simple way of constructing cheap cases for projects.

It is possible to obtain from electrical wiring engineers heavy gauge plastic square section conduit. The sizes I have used are 50 x 50mm outside measurement and 75 x 75mm. The conduit is made in a pleasing grey colour, is extremely rigid and has a sliding panel along one side. This panel is a tight fit when pushed into place.

The advantages of this system are: the case may be any length (it is easily sawn with a wood saw or hacksaw), it is insulating, the walls are heavy enough to support switches and pots without bending and the sliding panel makes an ideal lid.

End caps are needed for the open ends and can easily be made from offcuts. They are extremely firm if glued in with polystyrene cement, but for extra strength, small self tapping screws may be used, as the wall thickness is about 3mm. The cost is between 15p and 30p per metre—a considerable saving over aluminium boxes.

R. M. Henderson, B.Sc.,
Newcastle upon Tyne.

New products and component buying for constructional projects

SHOP TALK

By Mike Kenward

A NEW range of educational "toys" has recently been introduced in this country by Patterson Edwards Ltd. The kits, designed for young people, will appeal to inquisitive minds of all ages and include optics, aeronautics, electrics and electronics, and range in price from approximately £4.95 to £17.95 including V.A.T. Each comes with its own comprehensive illustrated manual giving assembly instructions and details of the experiments which can be carried out.

The most expensive kit, is a miniature computer that can be assembled by a twelve-year-old and programmed to play games and solve simple problems. It comes complete with a 112-page assembly and programming manual. Apart from the fifty pro-

grammes illustrated, youngsters can make up their own programmes.

All kits should be available from toy shops, hobby shops or large department stores by the time you read this.

The Minstrel

Parts for *The Minstrel* should all be readily available—that printed circuit kit from Home Radio (mentioned last month) would also be useful for this project. One point to watch when buying components—the skeleton presets should be the very small type, otherwise you may have difficulty in fitting them all on the board. The case for the original unit was a plastic food box—the type sold in most hardware and general stores.

Warning Winker

Once again, no buying problems for the *Warning Winker*, in fact there are very few parts to buy anyway. Different l.e.d.s. can be used—red ones are the cheapest normally. Some types are available with a chrome mounting case and these would enhance the appearance of the unit to which they are fitted—they are, of course, more expensive.

Incidentally, the end of diodes marked with a plus sign is the cathode not the anode as some readers tend to think. The positive sign goes on the "arrow head" of the circuit symbol and this is the cathode.

Car Alarm

The *Car Alarm* components should not provide any undue

difficulty. The prototype unit shown in the photographs used an enclosed preset for one of its controls, but this is not essential and a skeleton type will do just as well.

A suitable heavy duty relay may require some looking for, but most of the larger suppliers should have something to suit with approximately the correct coil resistance. Suitable extra switches for bonnet and boot may be required and either micro-switches or normal courtesy light door switches can be employed. The latter should be available from a garage.

M. and L.W. Tuner

The special coils and transformers for the *M. and L.W. Tuner* are all available from Denco. A cheque or P.O. for £3.85 and an order for their parts as listed should bring results. A trimming tool type TT5 is available for an extra 22p if ordered with the other components—prices include V.A.T. and postage. Denco are at 357/9 Old Road, Clacton-on-Sea, Essex.

Incidentally, we should make it clear that it is simply not possible to build a superhet radio for less than the cost of an equivalent Japanese set. Thus we cannot say that you will be saving money by building this design, but we have been asked to publish one by many readers and hope that they will learn from the construction and have the satisfaction of completing a sensitive design that will make an excellent addition to any amplifier.

JACK PLUG & FAMILY...



A simple circuit for the protection of your car.

WITH the number of car thefts increasing daily a simple and effective car alarm is becoming a necessity for every car owner. This article describes just such an alarm. The circuit is extremely easy to construct and its time delays are adjustable for personal requirements. It is quite a small device and thus can easily be concealed under the dashboard.

CIRCUIT ACTION

The heart of the alarm circuit is simply a large capacitor C1 which controls the voltage at the base of TR1 (see Fig. 1) and thereby the state of the relay RLA. The alarm is triggered by any one of the door, bonnet or boot switches being made by the would-be thief entering the car. When a switch is made the capacitor begins to charge up through VR2 and D1, the rate of charge being set by VR2.

When the voltage across C1 reaches a certain level (the switching voltage of the relay (8V)) RLA1 switches on, activating the car horn. When the switch is opened again the horn will continue to sound, this is because the holding level (3V) of the relay is much less than the switching level (8V). When the door is closed the capacitor will begin to discharge through VR1, the rate being dependent on the setting of VR1, and when the voltage across C1 drops below the holding voltage the alarm will switch off.

The low resistance of the relay coil is isolated from the capacitor circuit by the super-alpha pair TR1 and TR2, this configuration having a high input impedance and thus drawing only a minute discharge current. Because of this the discharge time is virtually solely dependent on the value of VR1 and is adjustable from zero up to minutes depending on the value chosen. In this circuit the maximum VR1 setting is 10 kilohms and thus the maximum hold-on time is only about a minute, but with no resistor across the capacitor (i.e. only the super-alpha discharge path) the relay will stay latched for about ten minutes.

The purpose of the switch on delay introduced by VR2 is to enable the owner to open the car door and immotivate the alarm on entering

CAR ALARM

By D.T. GOODWIN

FOR
GUIDANCE
ONLY


ESTIMATED COST*
OF COMPONENTS
including V.A.T.



*Based on prices prevailing at time of going to press

SPECIAL SUPPLEMENT

Choosing and using MULTIMETERS

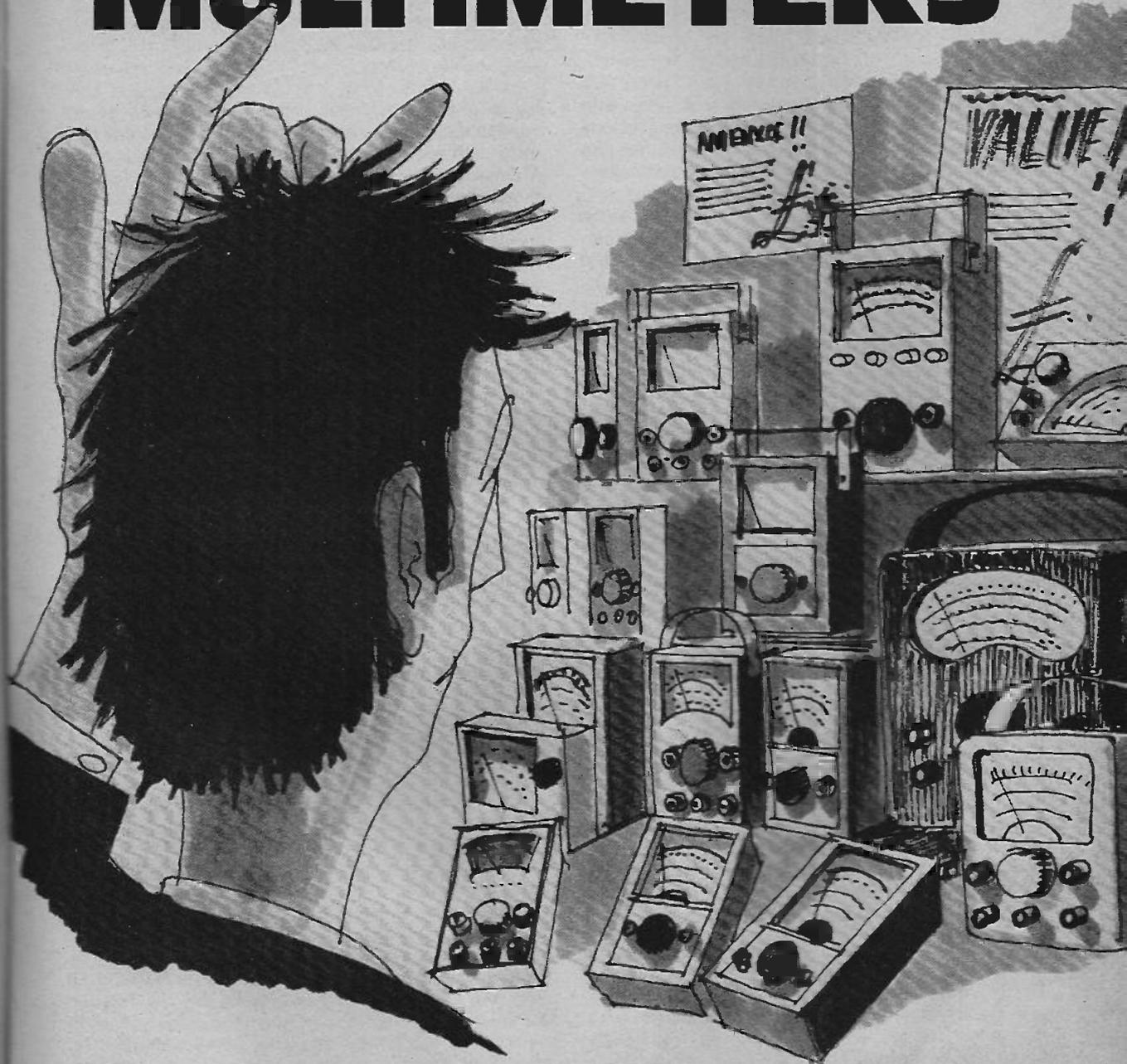

WHEN starting into the hobby of electronics there are comparatively few essential items to possess. Of course, a soldering iron, pliers and side cutters are taken for granted and nobody would deny that these are essential. Test instruments, on the other hand, are expensive and as far as possible

one has to do without unnecessary luxuries. We, however, feel that there is one instrument that no constructor should be without; it is the multimeter and should be considered as essential a part of the tool box as a pair of pliers.

Very few hobbyists are able to get away with

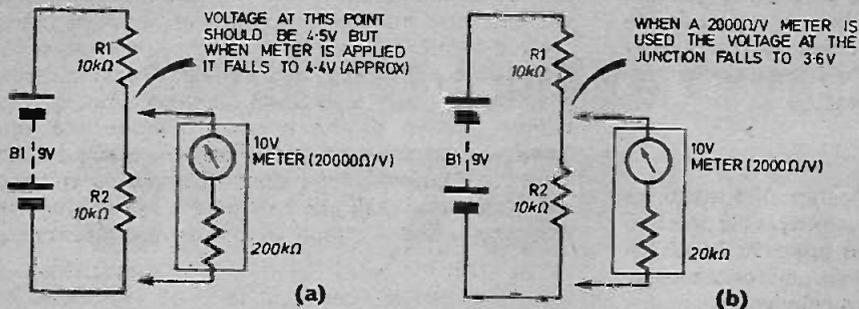


Fig. 1. The 20,000 Ω /V meter would read about 2 per cent low (a). Whereas the error would be over 15 per cent if a 2,000 Ω /V meter was used (b).

many projects working absolutely correctly first time—there are often dry joints to locate, connections left off, transistors put in the wrong way round and sometimes (we hope not often) some components have values other than their markings suggest.

Whether you are a newcomer to the business or an "old stager" there is only one instrument that can help you sort out problems like these; without the multimeter the only way to carry out "get-it-going" tests is by a process of guesswork, component substitution and luck.

Even with a test meter you need a good supply of the first and last of these commodities but the less unsoldering and re-soldering of alternative value components the better—it spoils the circuit, is time consuming and can be a very frustrating job.

TYPES

To follow up our statement that a multimeter is as essential as a pair of pliers or a soldering iron, have a brief look through the advertisements in our pages and, if you like, count up the number of different types of meters, pliers and soldering irons that are advertised and we bet you will find that the meters greatly outstrip the others—and they would not be advertised if the suppliers did not feel them to be essential!

The great proliferation of different types of meters presents the newcomer with a problem to decide which one to go for. Some are big, some small, some cheap, some expensive; some claim to have all sorts of fancy adjuncts while others look positively tame in comparison. We hope that the first portion of this supplement will throw a guiding light on what to look for when buying a meter and having invested your money in the ideal instrument the latter portion is designed to help you get the most out of it.

USER

Firstly we had better specify the type of person to whom we are aiming our recommendations because different meters are sometimes offered with totally different applications in mind. We shall assume he is the average reader who will be embarking on the types of projects we publish; that he is a newcomer but quite likely will progress on to more complicated projects in years to come.

He will probably want to use his meter for other applications—e.g. on the car or house electrics and

he is a practical fellow who would rather go for servicability, ruggedness and ease of use rather than ultra high precision accuracy.

One, very safe, way of ensuring one is getting the best instrument is to shop around and go for the highest price but, unfortunately, the sky tends to be the limit for this method. We must assume that the buyer is as much interested in getting value for money as any of the foregoing.

Advertisements for meters have, usually, to be brief specifications and consequently much of what we have to say may not easily be checked against such short details. By far the best method of buying is to go to a shop and have a good look at the product in real life—ask the shop assistant for sight of the full specifications of the instrument; if he is worth his salt he will realise that you need to know quite a bit more than simply the number of ranges available on the switch!

MOVEMENT

The heart of any meter is its movement. There are two types on the market; the most common one, thank goodness, is now the **moving coil** movement and this is the one to go for. We will mention the other (**moving iron**) to advise you against such an instrument.

Unfortunately moving iron types are seldom stated to be such but there are one or two distinguishing features which can be used to identify them. First and foremost they are very cheap and are usually quite small. Instead of having totally different switched positions for a.c. and d.c. voltage their inputs are often stated as "volts a.c./d.c." and they are equipped with two sets of markings on the scale for a.c. or d.c. measurements.

If you pick one up in a shop and carefully tilt it in different directions you will find that the needle will swing away from its zero position to quite some distance up the scale and stay there for as long as you hold the tilt. The reason why we say "avoid such an instrument" is that they are invariably low in sensitivity; the needle tends to swing around a lot before settling down to a true reading and they should only be operated when placed on a flat surface. They are admirable for some applications—but not ours!

It would be unfair to dismiss a meter as a moving iron type solely on its price because, fortunately for us, the cost of moving coil types has fallen dramatic-

ally in recent years. Even so we would suggest that meters costing in the range of two or three pounds are probably not very suitable for our type of work—and certainly would not prove a worthwhile investment to last you for years to come.

SENSITIVITY

Probably the most important feature of a meter for electronic applications is its sensitivity. This is specified by the unusual units of **ohms per volt**. Ohms per volt (Ω/V) represents the total internal resistance of the meter when switched to a particular voltage range. For example if you have a good meter having a sensitivity of 20,000 ohms per volt and switch it to a 10V full scale range then its internal resistance will be $10 \times 20,000$ or 200 kilohm.

If you then were to measure the voltage across the bottom resistor of a potential divider as shown in Fig. 1—the meter is, in effect, connected in parallel with the lower of the 10 kilohm resistors and thus modifies the resistance in the lower leg of the divider. As the meter's resistance is 200 kilohm there will be very little change to the effective resistance of the potential divider—the bottom leg becomes 9,525 ohms instead of its original value of 10 kilohm.


The voltage drop that you are measuring across the bottom resistor will therefore be slightly less than the 4.5V you would expect; nevertheless the dif-

ference is so small that it is negligible. If, however, you had used a meter having a lower value of ohms per volt (say 2,000) then its internal resistance, when switched to a 10V range, would be 20 kilohm and this would have a very significant shunting effect on the bottom portion of the potential divider and you would obtain a much lower voltage reading than expected. Obviously the higher the ohms per volt of a meter the less likely the instrument will modify the parameters of the circuit which you are measuring.

We used the word "sensitivity" to describe this parameter and at first sight this does not seem to accurately describe the effect. If you remember that a moving coil meter measures voltage by having a resistor in series with the basic movement then all should become clearer. The internal resistance is governed by the value of this series resistor—plus the relatively insignificant resistance of the movement's coil.

Obviously the higher the series resistor the better—as we have just seen—but with a very high value of resistance the amount of current flowing through the coil will be very small and this calls for an extremely sensitive basic meter movement (possibly responding to a small fraction of a milliamp). For a 20,000 ohm per volt meter the series resistance on the 10V range will be 200,000 ohms so to get a full scale deflection when measuring 10V the meter

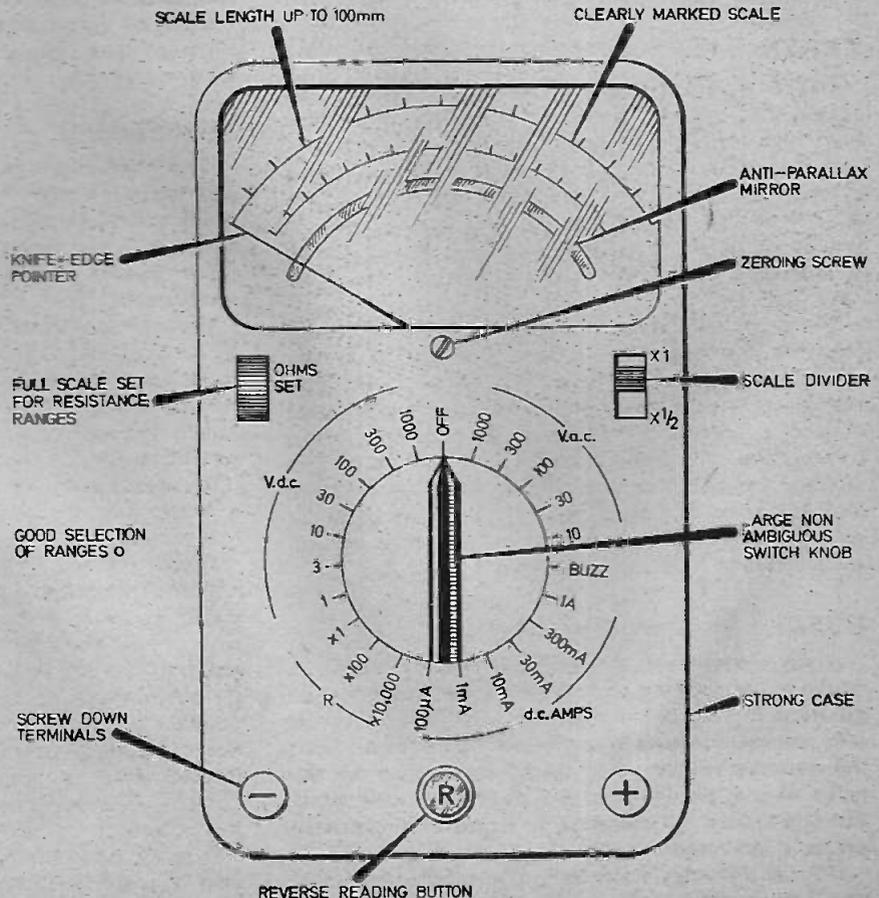The type of meter to aim for when buying. The availability of all the facilities shown may not be possible in low priced meters.



movement must have a full scale deflection of $50\mu\text{A}$.

Always buy a meter having at least 20,000 ohms per volt sensitivity (some go as high as 50,000 ohms per volt!). Most advertisements state this parameter but if it has been omitted you can check very quickly by looking for its highest sensitivity range on current. Many multimeters allow you access direct to the terminals of the movement when you switch to the most sensitive current range and if this is marked as $50\mu\text{A}$ then you have a high sensitivity instrument.

If the most sensitive current range is only 1mA it does not necessarily mean the meter has poor sensitivity but unless a high ohms per volt value is quoted you should be very suspicious.

ELECTRONIC TYPES

Some multimeters are quoted as having exceptionally high input resistance values—sometimes several megohms per volt. These are most likely electronic meters—comparable to the older valve voltmeters. The high input resistance is obtained by having an internal voltage amplifier.

While such instruments are very good indeed they are at the higher end of the cost spectrum and generally speaking offer more than the normal amateur wants—unless he intends to go very deeply into the subject.

ACCURACY

Some people wrongly expect a meter to be accurate to the ultimate degree. While it may be nice to think that the reading you get is accurate to a fraction of a per cent, what are you prepared to pay for it?

Normally we are only interested in using a meter to check approximate values of voltage in a circuit and seldom would one raise one's eyebrows if a correctly indicated voltage was off that specified by up to 10 per cent. We hasten to add that we are not advo-

cating 10 per cent accuracy meters but are trying to illustrate a point.

Further than this you must remember that with normal sized scales it is almost impossible to read a meter to better than plus or minus 2 per cent. A small pocket meter might have a scale length of 50mm—to read this to an accuracy of 2 per cent is equivalent to using a ruler and measuring a length to 1mm.

Obviously the longer the scale length the more accurate your reading will be. It is unusual for amateur grade meters to have their calibration accuracy quoted and you are in the hands of the manufacturers but generally speaking if you pay in excess of £7 you can expect better than 2 per cent and if the scale length is in the order of 50-100mm you can be assured that your reading accuracy approximately matches the latent accuracy of the meter.

There is no point in going to a larger scale length meter—at a much higher price—unless a calibration accuracy of better than 1 per cent is quoted.

RANGES

When looking at different types of meters one can easily be confused by the large proliferation of different switchable ranges but when you actually come to look at the differences you will probably not see much to choose from. Certainly you must have a reasonably good selection of ranges.


The meter should provide you with means of measuring with some confidence from about 1V full scale to about 1,000V full scale for d.c. voltages. This means ranges similar to: 1, 3, 10, 30, 100, 300, and 1,000V d.c. For alternating voltage you need not be quite so fussy because, on the whole, you will only want to be checking the outputs from transformers or mains voltages; 10V, 30V, 100V, 300V and 1,000V a.c. would suffice (in most cases the 1,000V ranges could be dispensed with for the sake of cost).

You do not often need to measure current but it is useful to have a few d.c. ranges available. You should have no difficulty finding a meter to give you ranges similar to: 3mA, 100mA and 300mA. Sometimes a range going up to 1A can be useful but this is not so common on lower priced instruments.

Three good resistance measuring scales are most valuable. These are usually calibrated to give you mid scale readings of about 100 ohms, 10,000 ohms, and 1,000,000 ohms. Because the ranges are cramped towards the left hand end of the scale it is always convenient to switch to a higher range to bring the needle more central on the scale.

Resistance ranges are a little misleading because they are quoted for what the manufacturer regards as the highest readable resistance value on each scale. It is better to look at the centre of the ohms scale, see what figure is quoted at that position and then see that when multiplied by the factor on the switch (usually $\times 1$, $\times 100$ and $\times 10,000$) you get something near the three figures mentioned above.

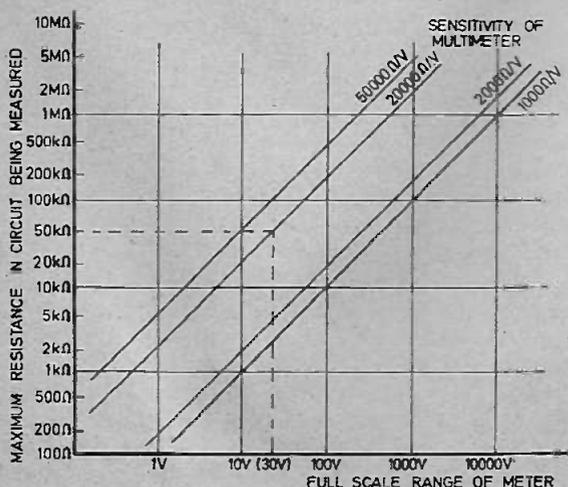If the meter has only two resistance ranges you should go for the lower two values of the above.



Graph showing maximum advisable resistor value across which you should measure. Example shown dotted—for a 20,000 Ω/V meter on 30V range maximum value is 50k Ω

EXTRAS

Although not essential we would suggest you give preference to a meter which has an "off" position on its range changing switch. By turning the knob to this position you will help protect the movement from mechanical damage because the switch applies a short circuit across the coil and thus damps down the needle's tendency to swing about when carried.

A "buzz test" facility is a useful little extra on some meters but is not really essential and certainly should not rate very highly on your selection list. On the other hand you should always try to buy a meter with some form of overload protection—most medium priced instruments have this embodied.

Some meters have a range "divide by two" switch which simply changes the scaling by a factor of two on all ranges. This is a useful feature and effectively doubles the number of ranges available—thus making it easier to get accurate readings around the centre of the meter's scale. This facility is worth while looking for but it is not worth paying more than a pound extra for it if a cheaper instrument has all the rest of the functions you desire.

The same can be said of a scale reversing switch—which enables you to reverse the connections to the meter without having to disconnect the leads.

SWITCHES OR SOCKETS

The tendency is for low priced meters to use sockets to connect the probe leads to the instrument. These certainly help keep the prices down but after a period of use can suffer from loose and dirty contacts which give rise to erratic indications. It is, perhaps, expecting a lot but we would ideally recommend screw down terminals for connecting leads to meters. These are found on the more expensive of the middle price range instruments.

There is, however, a point in favour of the socket input variety; they enable the manufacturer to give you a few extra facilities at virtually no extra cost e.g. a capacitively coupled input to measure low frequency a.c. signals superimposed on d.c. levels (useful for

checking r.m.s. signal levels of audio at loudspeaker)

They also allow extra high voltage inputs—up to several thousand volts. It is doubtful that you would wish to use these options very frequently so you ought to weigh up the pros and cons yourself.

If you get a chance to study the instrument in real life before you buy it make sure that it is mechanically robust. Lightweight plastic cases are very liable to break so if you feel that its enclosure it is a bit flimsy check to see if there are any leather cases designed to go with it—a carrying case is very useful because it enables you to keep the leads and any other accessories with the meter.

Have a close look at the calibration of the scale; it should be clear and legible and preferably different ranges should be printed in different colours to prevent ambiguities in reading. If you are interested in accuracy of reading make sure that the pointer is really thin like a knife edge and that there is an anti-parallax mirror running round the scale.

In conclusion we suggest you go for a straightforward meter that is robust and easy to use. Unless you are wealthy it is best to avoid too many gimmicks like transistor testing sockets, internal signal generators, buzz tests etc. To help a little, here is a check list with our opinion of the order of priorities you should put on the selection:

- 1) Must be moving coil movement
- 2) Sensitivity of 20,000 ohms per volt or greater
- 3) Should have good length scale (about 100mm)
- 4) Should be robust mechanically
- 5) Overload protection should be present
- 6) Should have switched ranges which overlap
- 7) D.C. voltage from 1V to 1,000V
- 8) Resistance measurement should be split over two or three ranges
- 9) A.C. voltage from about 10V to 1,000V
- 10) D.C. current from a milliamp to about 1A
- 11) An off position on the range switch is useful
- 12) A leather case should be available
- 13) Screw terminals are preferable to sockets
- 14) Extras like buzz testers, scale reversal switches and scale range dividers are useful

USING

WE'LL assume you have bought your "ideal" multimeter; the following paragraphs will give a few hints about how to get the best use from it.

Your meter is a delicate instrument and has probably cost a lot of money. It is probably your only way of checking what is going on inside an electronic circuit and should be regarded as an extension of one of your own senses so take very great care of it.

GENERAL CARE

Avoid subjecting the meter to knocks; if you do accidentally drop it always check that it is functioning correctly by measuring a known voltage or a known value of resistance—the chances are that the only damage sustained by a drop is to the movement and

provided it gives a correct reading on one range you can be fairly sure that all other ranges are working correctly. When carrying out this check make sure that the needle moves up the scale smoothly without any jerks and that the tip of the pointer has not been bent by the impact.

Keep the meter away from magnetic fields as these will tend to de-magnetise the movement's magnet and cause the calibration to change (the meter will start to read low). Avoid keeping it in dusty or damp conditions—if you do not have a leather case for it, keep it in a shoe box together with all its leads and probes and, in particular, keep it out of the hands of small children.

You should keep all the connecting terminals clean

and free from grease and dirt — this is particularly important if access to the meter is via sockets.

When putting your meter away after use always check that you have not left it switched to a resistance measuring range (otherwise you might run down the internal batteries if the leads were to short together). Preferably switch the meter to the off position if one is available. Failing that switch to the highest current measuring range (the internal shunt will provide a short across the movement). Do not transport the meter if it is switched to a sensitive current range.

Every month check the condition of the internal batteries and at the slightest indication of deterioration remove them. If you do not intend to use the meter for some length of time it is a wise move to take the batteries out. Leaking batteries can totally ruin a multimeter by corroding the switch contacts and leaking into the movement itself.

ZERO AND PARALLAX

Before and after each reading (whether on d.c. or any other range) always check that the needle comes to rest exactly on zero. If it does not, give the meter a gentle tap with the finger—some plastic meters can pick up a static charge and this sometimes causes the needle to be deflected slightly from its true position.

If a gentle tap does not correct the zero reading you should carefully adjust the zero setting screw on the front of the movement. When doing this make sure you are looking vertically down over the needle to avoid parallax errors. **Always** carry out zeroing when the meter is in its correct operating position (i.e. on its back or standing up vertically).

Parallax errors are caused by the slight gap between the needle and the scale and you can experience this by positioning your head so that your nose is vertically above the needle; shut one eye and then the other while keeping your head still and you will notice that the needle appears to show slightly different readings.

Better quality meters have an anti-parallax mirror which helps prevent the errors that arise from this problem. If you have such a mirror on your meter you should close one eye and then move your head until the needle and its reflection in the mirror are exactly coincident. When this happens you know that your eye is in an exactly vertical position over the needle and the reading obtained in this position is the correct one.

POLARITY

As well as making an estimate of the voltage range you select you should likewise try to ensure that you apply the probes with correct polarity. This is usually not a very difficult thing to do but you should not be casual with the leads. Always keep the red probe on the red lead and the black on the black lead. Keep the black lead connected to the negative or common terminal of the meter and only use the red lead in the alternative input sockets. Provided you do this the meter will always read "up-

scale" if the red lead is connected to the more positive voltage.

If you have a scale reversing switch this should, likewise, be kept in the "normal" position and only switched to "reverse" when needed. If you do not have a reversing switch but have made a mistake in your estimate of polarity it is better to reverse your connections at the probe ends of your leads rather than at the meter because you will only have to change the meter connections back afterwards.

Never try switching the meter to a current measuring range while your probes are connected to a piece of equipment because it is quite possible to overload the circuit with the internal meter shunt. For a similar reason **never** switch through the resistance measuring range while connected to a circuit—not only might you damage the circuit but you could damage the meter movement.


D.C. VOLTAGES

We shall go through the principles of using each of the main ranges one finds on general purpose multimeters — much is obvious but there are a few important points that are often overlooked and these can cause errors or damage to the instrument. D.C. voltages are probably the measurements most frequently required.

It may seem obvious to say that you should switch the meter to a d.c. range but many people have found that they get readings of d.c. voltages when their meter is switched to a.c. This is to be expected if you remember that all you are doing is applying the d.c. through a rectifier.

You will not, however, get a correct reading because the meter is calibrated to give an r.m.s. value of a.c. with a duty cycle that may be half wave or full wave. The rule is never use the a.c. range when measuring d.c. and always check that you have the selector switch set correctly.

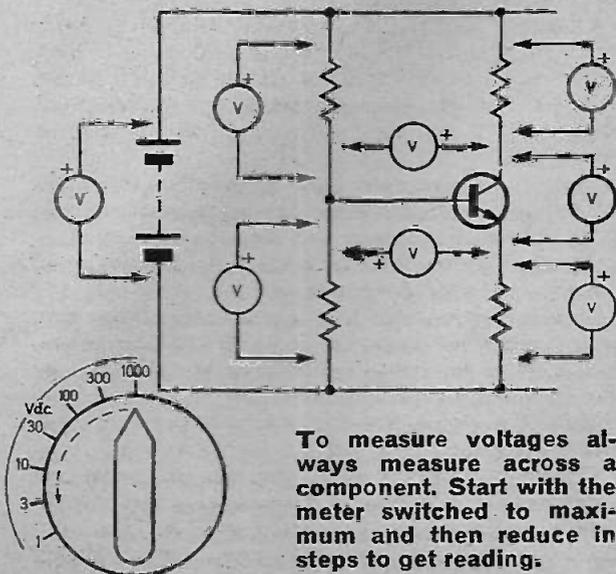When measuring voltage you are invariably measuring the **voltage drop** across a component and the



To measure voltages always measure across a component. Start with the meter switched to maximum and then reduce in steps to get reading.

internal resistance of the meter can shunt the component and give a lower than true reading. Before connecting the meter across a resistor check that the value of the resistor is—at most—a tenth of the resistance of the meter when switched to the range you desire.

For example if you are measuring with the 10V range of a 20,000 ohms per volt meter the meter's resistance is 200 kilohm so you should not expect accurate indications if you measure across resistors having values greater than 20 kilohms.

If it is essential to get some sort of reading across, say, 100 kilohms you should switch the meter to the 100V range and by doing this you will increase its internal resistance to 2 megohms but your reading will, of course, be very much down the scale to the left hand side! Your reading accuracy will therefore be impaired even though the meter is indicating a more correct value.

Always make a mental estimate of the voltage you expect to see and select a range that should put your expected reading in about the middle of the scale. If you are totally in the dark about the voltage you might expect it is wise to set the meter to its highest d.c. range and then switch down through the ranges until you get a measurable reading.

Never start with the meter set to a high sensitivity range and switch up or you will quite likely cause the needle to hit the end stop. If the meter has overload protection you will not burn the meter out but you might cause the needle to bend when it hits against the end of the scale at high speed!

A.C. VOLTAGES

The same rules apply to measuring a.c. voltages. You are most likely to be concerned with signals having frequencies of 50Hz—for example mains voltages and those from transformers. Polarity of lead connections is not important because, by definition the polarity of the signal you are measuring is changing continuously.

We must qualify this, however, because true a.c. alternates equally about zero and your meter is only calibrated with that type of signal in mind. If the voltage oscillates unevenly about zero (i.e. there is a d.c. shift to the a.c.) then your reading will be inaccurate.

You can check that such a condition exists by first trying to measure the a.c. signal on a suitably high d.c. range. A true a.c. signal will show zero volts when connected thus because the meter cannot respond to the high frequency.

When carrying out this test **do not under any circumstances** drop the range of the d.c. meter selection to get a reading because you will damage the overload protection circuitry. If you have a d.c. biased a.c. signal the d.c. bias will show up quite readily without doing this.

If such a condition exists you can still get a true value reading for the a.c. by switching back to the correct a.c. range and inserting a 0.22 μ F capacitor (with a working voltage higher than that which you are measuring) in series with one of the meter leads.

This capacitor will block the d.c. level but will pass the a.c. signal.

Some meters have this capacitive input option built in and if so you should simply transfer the red lead to the socket thus marked. Also some meters have this socket marked "output"—not because anything comes out of the socket but because the facility is usually required for making measurements across loudspeaker output terminals where a.c. audio signals are often superimposed on d.c. levels. This special capacitive input will only operate when the meter is switched to an a.c. range.

INSULATION

If ever you use your meter to measure mains voltage you must check that there is no possibility of you personally coming into contact with any of the terminals. This goes for the probes as well as the sockets or terminals on the meter. The probes **must** be fully insulated and tested to withstand voltages in excess of 1,000V. Unless your meter states this fact in its book of instructions do not attempt to use the probes across a mains socket!

For safety reasons **never** leave one probe of your meter connected to a source of high voltage and the other probe lying on the bench; if you accidentally touch the metal contact of the loose probe you could get a shock. If you, or a child, inadvertently switched the meter to a current measuring range while this state of affairs existed there would be virtually no limiting resistor in the meter to protect you from a lethal shock.

For convenience and, again, safety you should—as far as possible—always use long insulated probes with spring loaded hooks. Because they are insulated right down to the small hook there is very little chance of them shorting across parts of a circuit you do not wish to touch and at the same time they are very easy to apply to the ends of small components.



Crocodile clips ought to be avoided. Better quality meters are provided with probes such as the type we describe but if not they can be obtained from most electronic suppliers.

AUDIO MEASUREMENTS

Although most a.c. measurements are likely to be carried out on 50Hz signals you can usually get useful readings on the a.c. range of most meters up to a few kilohertz, hence they can be used to measure the a.c. audio signals feeding loudspeakers as we have just explained.

Do not expect precision readings and remember that you cannot hope to measure signal levels of less than about 0.25V on normal meters when operating in this mode. There is, of course, the same limitation on the maximum impedance of the voltage source—as for the maximum resistance in d.c. measurements.

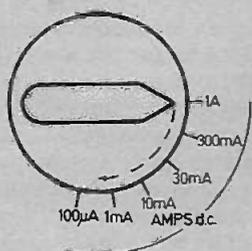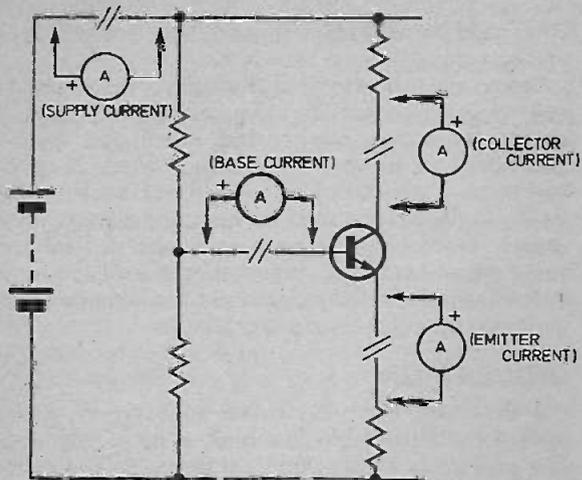Most meters have a lower "ohms per volt" when measuring on a.c. and this should be taken into account. Even though some crystal cartridges give outputs of up to 500mV you cannot expect to measure this on a multimeter because the source impedance



To measure current you must break the circuit and insert the meter across the break. Start with the highest range and reduce in steps to get a reading.

is far too high—you would need a valve voltmeter or a transistorised multimeter for this purpose.

CURRENT RANGES

When measuring d.c. current you have to break the circuit and insert the multimeter in series with the wire down which the current you wish to measure is flowing. The red lead of the meter should be connected to the positive source of the current and initially you should always set the meter to its maximum current range. While viewing the scale reading you should then increase the sensitivity of the meter in steps with the range switch until you get as near a mid scale reading as possible.

Remember that by putting a current measuring meter in series with the power supply rail of an amplifier you are, in effect, introducing a series resistor into the circuit you are measuring—in the case of amplifiers this can sometimes degrade the performance of the circuit and in the worst of cases can cause oscillations to start. To prevent this happening you must keep the meter set to the highest current range possible (commensurate with getting a useful reading) because that way you are operating with the lowest value shunt resistance in the series circuit.

Some of the more expensive meters are equipped with a.c. current ranges. These are not often required in electronics work (they are more suitable for electrical engineers) but they should be used in

exactly the same way as the d.c. ranges but the polarity of lead connection is unimportant.

RESISTANCE

Using the resistance measuring ranges is fairly straightforward. The main point to remember is that you must—before every measurement—short the probes together and adjust the resistance range control so that the needle points to zero ohms on the top end of the scale.

If you change ranges you must remember to re-adjust this control because its setting will vary from one range to another. Select a range that will keep your readings as near the top end of the scale as possible—this way you will obtain the highest accuracy.



When using the resistance range for continuity testing you should make sure that you select the lowest resistance setting of the switch—you are then more likely to see the resistance caused by dry joints and dirty contacts—which may only be a few ohms.

Apart from resistance and continuity tests you can use these ranges for a quick check on transistors, capacitors and diodes. (An article concerning checking of these devices will be published in a future issue of EVERYDAY ELECTRONICS).

You must remember that there is a battery inside your meter which comes into play when you switch to the resistance ranges. The polarity of this battery is such that its positive terminal is effectively applied to the black lead which comes out of the meter.

The simple rule is that "positive comes out of the black lead"!

When measuring resistance, lead polarity is not important. Select a range between the middle and top of the scale and multiply the reading by the factor on the switch.

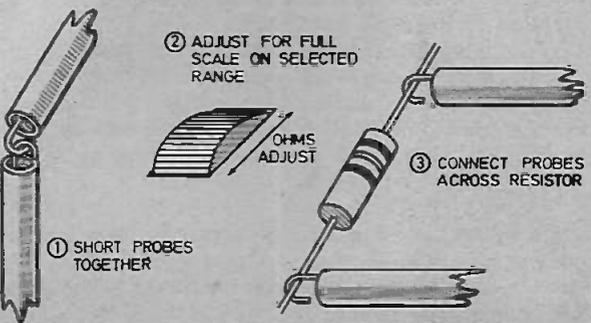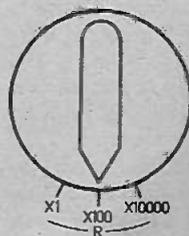

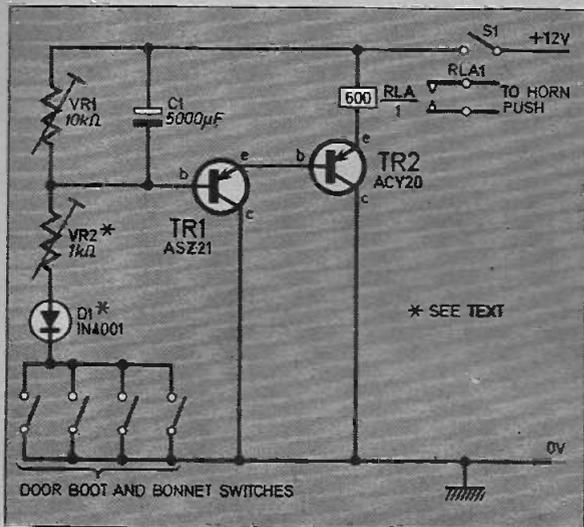


Fig. 1. The circuit diagram for the Car Alarm.

the car. This is made possible due to the fact that there is a considerable difference in the time taken to open the door and switch the alarm off and the time taken to open the door and get in; VR2 is set about mid-way between the two times.

An alternative to this is to use a locking switch mounted on the car exterior as the main on/off switch and replace VR2 with a low value resistor, say 100 ohms (necessary to protect the capacitor). The key-operated switches should be readily obtainable from most car spares dealers.

SWITCH WIRING

If the courtesy light switches are to be utilised for SW1 the wiring is extremely simple. However, the bulb presents a low resistance path across the capacitor which rapidly discharges it; to avoid this a diode (D1) is wired in series with VR2 as shown.

To connect the unit, a wire is run from the switch side of the bulb holder to the circuit board. The switch side can be found by looking at the switch in the light unit which will be in parallel with the door switches.

If however the existing switches are not going to be used or if the system is extended to cover the boot, and bonnet, etc., then simple push-to-break switches can be used. These can be mounted on a metal bracket screwed to the door frame such that when the door is closed it pushes the switch and opens the contacts. The switches are all wired in parallel, one side being taken to the car earth and the other being taken to the circuit board input. The mounting plates should be positioned so they do not obstruct normal use of the door.

CIRCUIT CONSTRUCTION

The whole circuit is constructed on a piece of 0.15 inch matrix Veroboard, 22 holes by 17 strips, and the layout is shown in Fig. 2. A connection block is glued to the board to make wiring the circuit in much simpler, all external wiring is then taken to this block. The circuit is held in the car with a circlip mounted around the capacitor.

Commence construction by cutting the board

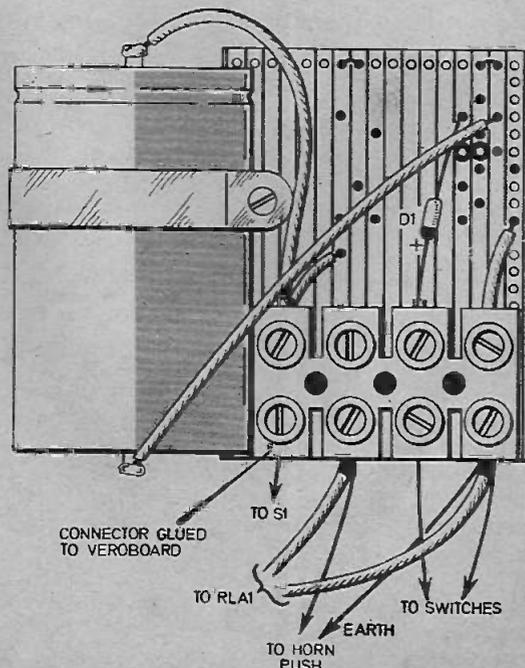
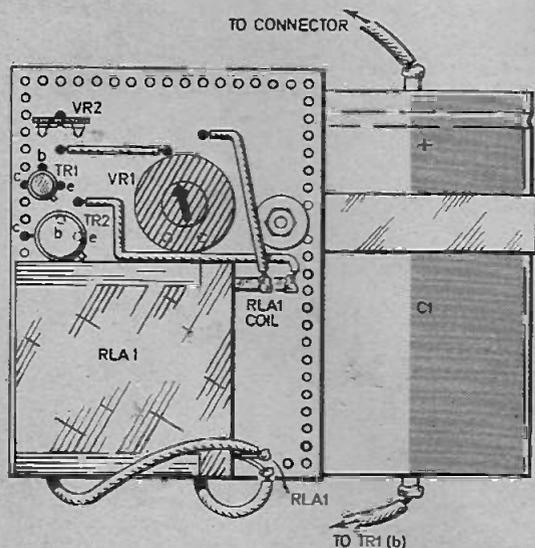


Fig. 2. The layout of the components on the Veroboard and complete wiring up details.

to size and making the necessary breaks in the copper strips, as shown in Fig. 2. Next mount C1 and the connection block and finally the remaining components and connection wires. Take care not to overheat the transistors when soldering.

If RLA1 is much larger than that in the prototype a bracket may be needed for its fixing. The circuit diagram (Fig. 1) is for negative earth systems. For positive earth cars simply change TR1 and TR2 to 2N2483 and 2N1306 respectively (*npn* types) and reverse the connections to C1 and D1, i.e., change positive to negative in Fig. 2 by placing the components the other way round.


EXTRA SECURITY

The positioning of the on/off switch is obviously most important, it can be either hidden or camouflaged. Personally I prefer camouflage; if the master switch is placed in a row of other switches and mounted such that when it is up it is on, and when it is down it is off, then it will be fairly well concealed once activated.

For extra security two more switches can be incorporated. One of these should be wired in parallel with the door switches so that anyone trying to fiddle with the switches will prolong the alarm or, if the timer has timed out, restart the alarm. The other is used to short out the contact breaker points and is wired the same way round as the on/off switch such that up is on. This is used as a last line of defence should the would-be thief get past the alarm.

SETTING UP

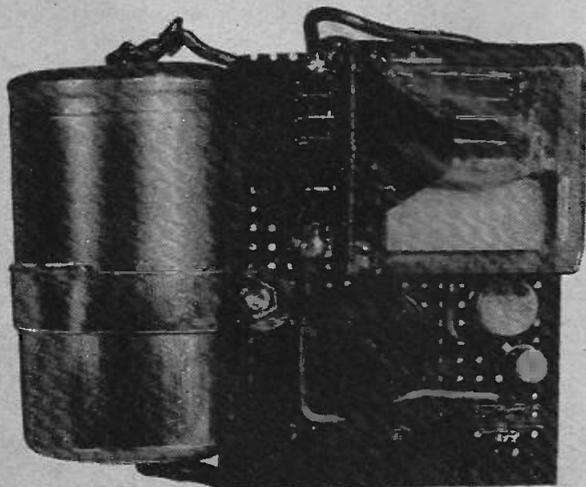When setting up the timing periods it is advisable not to have the horn connected. The switch-on time should be just enough for the driver to get to the master switch and turn it off



Photograph of the completed prototype Car Alarm.

Components . . .

Potentiometers

VR1 10k Ω miniature or skeleton preset
VR2 1k Ω miniature or skeleton preset

Capacitor

C1 5,000 μ F elect. 24V

Semiconductors

D1 1N4001 silicon diode
TR1 ASZ21 silicon *npn* (negative earth)
2N2483 silicon *npn* (positive earth)
TR2 ACY20 silicon *npn* (negative earth)
2N1306 silicon *npn* (positive earth)

Miscellaneous

RLA1 12V relay 600 Ω (approximately) coil with at least one set of normally open heavy duty contacts.
S1 s.p.s.t. toggle switch—dash type if required (see text).
Veroboard 22 holes by 17 strips by 0.15 inch matrix, 5A 4-way connection block, circlip for C1 and board mounting, connecting wire.

SEE
**SHOP
TALK**

before the alarm is triggered. The switch off time is up to the driver but it should not be too long or it may drain the battery.

A cautionary note about the values chosen for the preset potentiometers. As should be clear from the circuit diagram VR1 and VR2 form a potential divider thus limiting the voltage to which the capacitor is allowed to charge, therefore care must be taken to ensure that the VR1:VR2 relationship is greater than 3:1 otherwise the capacitor will never charge up to the switch on voltage of the relay.

The horn connection can be taken to the horn push button for ease of wiring.

Wiring from RLA1 to the horn should be of heavy duty wire e.g. 14 strand insulated. \square

PLEASE TAKE NOTE

The battery specified for the Quiz master (April '75 issue) should be a 6V type, not 9V as stated. This can be four U7 batteries (1.5V each) in a plastic holder connected by the PP3 clip.

Some recent issues of EE have been slightly oversize and may not fit in the binder, to overcome this, slightly trim the top of each issue near the spine.

In Part Two of the Modula 3 (EE March '75) Fig. 9 shows two C9's. The one on the right should be C10. In the text under Pre-amplifier Wiring, page 129, the tape input pins are incorrectly numbered 6 and 7, this should be 6 and 17.

All in **NEXT MONTH'S** *issue!*

WHITE LINE FOLLOWER

Not only an interesting and unusual exercise in electronic construction, but also an introduction to simple control systems.



MULTIMETER SENSITISER

A simple add-on unit that can increase meter sensitivity from 20,000 ohms/volt up to 10,000,000 ohms/volt. Provides three d.c. voltage ranges each with increased sensitivity.

It's not my fault!

Do some of your circuits not work first time? We show you how to fault find in easy stages.

FAULT FINDING FEATURE


THERMOSTAT

An integrated circuit design for use with heating or cooling systems. Provides temperature control in the range -50 to +120 deg. F.

... more Practical Projects to build at home

everyday electronics

JUNE ISSUE ON
SALE FRIDAY
MAY 16

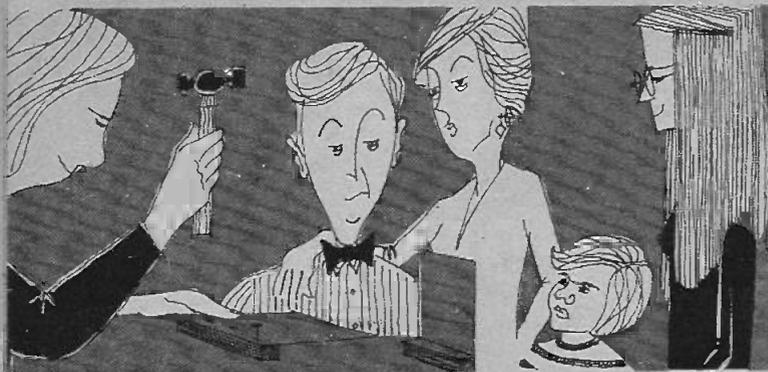

Physics is FUN!

By Derrick DAINES

MORE ON THE HOME-MADE CAPACITOR

Cut each of the two plates so as to make four equal-sized plates. We now have two complete, but smaller, capacitors. Now consider the following question—if we link the capacitors with wire as in Fig. 1, will the total charge that we can put on the combination be greater or less than on one capacitor alone?

The answer is obviously greater—twice as great, in fact. A few minutes experiment will convince you of this, if you cannot see it immediately.

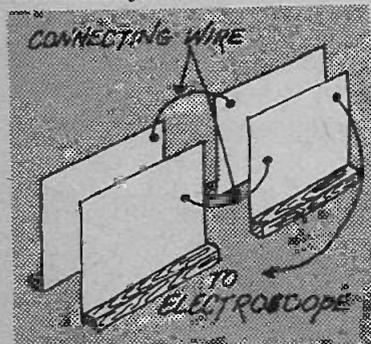


Fig. 1. Linking two home-made capacitors so they are in parallel.

If you now consider Fig. 2, you will see the similarity between this and Fig. 1; Fig. 2 uses the symbol that we use for a capacitor. You will see that there are two and that they are in parallel. From this we deduce the simple fact that:

Capacitors in parallel are added together

In formal terms, we may write $C_1 + C_2 = C_{\text{total}}$ and the same holds no matter how many capacitors we put in parallel. Therefore if we have a 100 microfarad capacitor and a 50 microfarad capacitor in parallel, the resultant value is 150 microfarads.

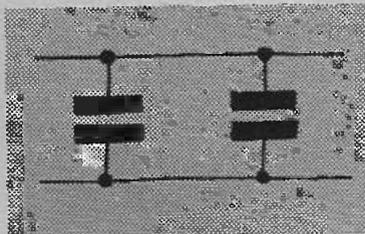


Fig. 2. How two capacitors in parallel are represented by circuit symbols. Compare this with Fig. 1.

Now consider Figure 3. Here the capacitors are no longer in parallel, but in series; what could their value be? If you duplicate the set-up with your four plates of the home-made capacitor, you will find to your surprise that the whole thing is more easily charged than with one pair of plates alone.

Conduct the experiment this way: have one plate connected to your electroscopes and another to earth. Between them put another pair back-to-back but electrically connected. Now charge a film by rubbing it with wool and bring it up to the electroscopes needle. Repeat as often as necessary until the leaves of the electroscopes fly apart and remain apart when the film is removed. The pair of capacitors are now charged.

Use an insulated rod to push the two centre plates out of the way and the earthed one near to

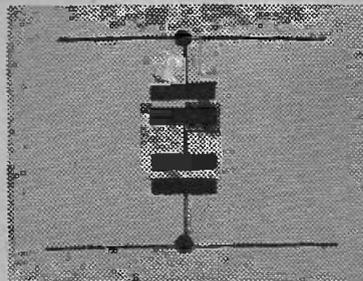


Fig. 3. Circuit symbol representation of two capacitors in series.

the one connected to the electroscopes. The leaves of the electroscopes will have collapsed and will remain collapsed.

It may be argued that we have removed some of the charge with the centre plates, so as an alternative, try counting the number of times a charge must be brought up to the electroscopes, both with the centre plates in and without.

With our limited means we cannot accurately determine the value of capacitors in series. Finer methods have, however, determined that the value is:

$$\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

So for 100 microfarad and a 50 microfarad capacitors in series, the result is 33.3 microfarads, which is smaller than either.

One interesting point arises when we stop to ask ourselves what exactly the electroscopes is showing. It cannot be the quantity of electricity because in many of our experiments the quantity held in charge remained constant but the electroscopes changed its indication. Clearly, what it shows is the pressure or potential charge. This is known as the voltage (after Volta) and can reach many hundreds of volts even with our simple equipment.

When we consider that the sometimes lethal household supply is normally 240 volts, the prospect of many hundreds of volts can be frightening. However, we have not had any more than a faint tingle from our equipment, so obviously the quantity of electricity is the vital factor.

We apologise for an error last month where it was said that all capacitors are electrolytic. It should have said all capacitors have a dielectric. An electrolytic capacitor is one in which "electrolysis" takes place when charge is stored.

for your
Entertainment...
By Adrian Hope

OUT of a combined sense of duty and pleasure I went along and saw the film *Earthquake* at the Empire Cinema, Leicester Square. Probably "subjected" myself to the film would be a better description.

By now everyone will know that this film is a feature film starring Iron Jaw Heston and the work of just about every special effects man in Hollywood. In remarkably convincing detail it pre-constructs what will happen to San Francisco when the inevitable earthquake finally comes.

Readers will also doubtless know that the events on screen are accompanied by off-screen noises as have never before been heard in the cinema. Three American inventors (W. O. Watson, Robert Leonard and Richard Stump) have devised for Universal Pictures a sound effects system that simulates the sound of an earthquake. Having, fortunately, never been in an earthquake, I have no idea whether the sound is authentic but it certainly is dramatic.

I took along a sound level meter and deliberately sat fairly near the front of the cinema, in between the two massive black boxes that stand one each side of the screen. Two more similar boxes lurk at the rear of the cinema, rather like the four speakers of a mammoth quadraphonic set-up.

SOUND LEVELS

During the earthquake sequences the Sensurround equipment (for that is what the system has been christened) generates low frequency rumbles which not only assault the audience's ears

but also physically shake their bodies and their seats. In fact when the Sensurround gear is running full blast the noise level in the cinema is quite staggering. The level of speech on the screen is automatically boosted by 6dB to make it audible over the earthquake rumble and all the ashtrays in the cinema rattle in high-pitched unison.

My sound level meter reads only up to 110dBA and the pointer wrapped itself round the dial stops, suggesting that the sound level towards the front of the cinema is probably around 120dBA or even more. As the A scale favours high frequencies a true reading would be even higher!

If you need some kind of guidance as to what this means in practice, the average dBA level in the cinema is somewhere in the dBA 70s, and only the very noisiest tube train blasting into a station notches up over 90dBA. Some pop groups produce sounds at the level of 100dBA, 110dBA or even 120dBA, but in Leeds the local authority has made it illegal to make musical sounds above 96dBA.

DANGER LEVEL

The Leeds legislation is intended to protect pop fans who regularly attend loud concerts from the hearing damage which could result from prolonged exposure to high level musical sounds. Although the Sensurround levels are very, very high it is unlikely that anyone will suffer any hearing damage because the exposure time is short. But I checked with the inventors in the USA on the frequencies

used, because both very high frequencies and very low frequencies can be a special danger to the human body.

For instance, high frequencies, as used in some intruder detection alarms, can cause fatigue and irritability, even though their high-pitched whistle cannot actually be heard by the human ear. Likewise low frequencies, as may be generated in trains and cars, can cause fatigue and possibly even symptoms resembling drunkenness.

INFRASOUND

Infrasound, as the low frequency noise is called, is in the audio range of 1 to 20 hertz. Few people are able to hear below around 20 hertz and above around 16 kilohertz.

I would like to think it is through good judgement rather than luck that the Sensurround inventors have produced a system which generates rumbles in the region of between 20 hertz and 125 hertz; in other words, outside the region of infra-sound.

Because most cinema sound systems cannot possibly cope with most of the low frequencies involved or with the high sound levels required, simple pulses are recorded on the sound tracks which trigger independent sound effects generators and amplifiers powering the speakers at the four corners of the cinema.

PATENTS

Because patents are pending on the system, the inventors will not say exactly how they work, but I would guess that fairly straightforward, positive feedback circuits and band-pass filters are used to produce low frequency oscillations. These oscillations are amplified by equipment rated at around 750 watts and reproduced by massive, low-frequency loud-speaker horns specially made by the audio firm Cerwin-Vega.

The system was first tried out in the States with a 1,000 watt amplifier powering a 32-foot spread of horns in front of the screen at the Chinese Theatre in Hollywood. But, not surprisingly, bearing in mind the way my meter reacted to the Empire Cinema presentation, this layout was found just too violent and

the horns were relegated to the corners of the cinema instead.

Everyone concerned seems quite confident that no physical damage to the audience or building can result and I hope they are right. In fact they will need to be right because there are plans to use the Sensurround system for future films, using the gear to reproduce other extra-high-level sounds. Like volcanos erupting, aircraft crashing or cinemas falling down under the effects of low-frequency sound waves, perhaps?

Finally, still on the subject of

safety, anyone receiving a suspicious package through the post should not be lulled into a false sense of security simply because it appears too flat to contain a bomb and battery.

Explosive can, of course, be flat sheets and the half-a-billion dollars invested by the Polaroid Company in the new SX70 instant picture system currently being advertised by Peter Ustinov in the UK and Sir Laurence Olivier in the USA, have answered the bombers' prayer for a flat battery.

The SX70 camera body con-

tains complicated electronics but not power source. Each film pack contains its own battery. These were developed by E.S.B. Inc. of Philadelphia, the company which makes Ray-O-Vac batteries. Nineteen cell-layers are compressed into a battery flat enough to fit unobtrusively into a film pack—or a flat letter.

This is obviously well known, now both to the terrorists and to the police. Thus to publicise the fact can only safeguard the public, by dispelling the illusion that only thick packages can contain letter bombs.



...Counter Intelligence

BY PAUL YOUNG

A retailer discusses component supply matters.

SUPPOSE everybody must have heard the old joke about the difference between a salesman and an engineer.

The salesman must have a very wide knowledge, so he learns less and less about more and more until he knows nothing about everything! An engineer on the other hand must specialise and therefore he learns more and more about less and less until in the end he knows everything about nothing! Exactly how the poor old component retailer (who is both) fits into all this I have not yet fathomed out, but it set me thinking about two big problems he has to wrestle with. Knowledge and stock.

RUNNING A BUSINESS

The average small retailer will most likely have only one technical person on the premises and that is himself. Unfortunately, he is the one who is least able to put his knowledge at the customers' disposal, because he is tied up with a hundred and one other things, that running a business entails, buying, banking, wages, V.A.T., income tax and the reams of paper work. I am fortunate in having two or three technically minded friends who help me out (or more accurately, help the customers out) on Saturdays. The rest of the week, we have to leave it to the customers, to find what they want in our catalogue, list it out, with

quantities and catalogue numbers, and then one of our good ladies will produce it for them.

Most of our customers are understanding and appreciate the problem, but occasionally I have the indignant one who says, "You really should have a technical assistant serving behind the counter". In extreme cases I explain that such a person's wages (even if I could find a suitable candidate) in the long run are paid by the customer, and I do not think our customers would stand for the increase in prices it would necessitate.

STOCKING

Another problem the retailer has, is trying to keep up with all the new devices that are arriving on the market. The poor man is usually so hard pressed that the best he can do is to skim through the magazines each month, and he probably only does that to see his advert has not been left out. In an ideal world he would have time to read of new inventions, and even time to experiment with a few of them himself, perhaps even time to wish his customers "Good day". Alas, that world does not exist.

But enough of dreaming, to come back to reality let us consider the question of stock. The small retailer, and even the large one, has only a certain amount of money he can invest in stock, and with electronic components proliferating at such a fast rate,

he has to make the invidious choice of stocking in width or depth. In other words if he decides to stock everything that comes along, he will have less and less of (quantity) more and more (variety) if he decides to keep narrowing his ranges he will have less and less (variety) of more and more (quantity).

I am fairly certain most of us steer a middle course; some veering slightly more one way, some the other.

SUMMING UP

What does all this add up to for you, the consumer? Simply this. You must reconcile yourself to the fact, that you are unlikely to be able to obtain all your requirements from one source of supply; and any firm that advertises that they can supply you with everything should be regarded as suspect! In my opinion you will need to deal with at least three or four and my suggestion would be this.

Select six or seven from the magazines and send each of them small trial orders (not too small). From the results, you will be able to judge their performance both as to prices and delivery.

Do of course make allowances for the fact that any of them might be unlucky with the post. If this does happen give them a second chance. Finally, I think you will be able to narrow your choice down to one main supplier for the "run of mill" components (resistors, capacitors, transformers) and two or three for specials such as for transistors, modules and i.c.s, etc.

Well, here's wishing you successful buying.

STARTING IN P.E. THIS MONTH...



The PE JOANNA

State-of-the-art piano design with additional choice of harpsichord or honky-tonk voicing. Keyboard is fully touch sensitive. Piano effect is further heightened with soft and sustain pedals. Other features include easy tuning, two speed vibrato and stool-integrated amplifier.

I.C. PULSE GENERATOR

A handy test instrument for analysing TTL circuits. Wide operating speeds covering 0.1Hz to 100kHz in six switched ranges. Pulse width is also variable from 1s to 1 μ s. An output reed relay enables it to be used with electromechanical systems.

ELECTRONIC DIRECTION INDICATOR

Electronic substitute for conventional thermal flasher. Advantages are: immediate indication when switched, long term reliability and an emergency flashing facility.

PRACTICAL ELECTRONICS

MAY 1975 ISSUE ON SALE NOW

THE MAGAZINE FOR IDEAS IN ELECTRONICS

MW / LW TUNER

By R. A. PENFOLD

A superhet. circuit to feed most amplifiers

THIS is a good quality tuner covering the m.w. and l.w. bands, and which will feed virtually any amplifier or tape recorder. The unit can also be used as a high quality personal receiver by plugging a crystal earpiece into the output socket.

A standard three transistor plus one diode superhetrodyne circuit is used, providing a very sensitive receiver. It is quite compact, measuring approximately 170 x 135 x 70mm, and is self-contained, using an internal ferrite aerial, and 9 volt battery supply. It is very economical to run, having a battery consumption of only about 2mA.

SUPERHETRODYNE CIRCUIT

In a superhet. circuit, the received signal is converted to an intermediate frequency (i.f.), where it is greatly amplified, and then passed to the detector, which produces the a.f. output from the i.f. signal. The stages of a basic superhet. circuit are shown in block form in Fig. 1.

The input tuned circuit is tuned to the frequency of the received signal, and in this design is the tuned circuit on the ferrite aerial. The signal is passed from here to a mixer, where it is combined with the output from an oscillator. Here the hetrodyne principle is used to convert the signal to the i.f., which is 470kHz in this circuit. The frequencies at the output of the mixer are equal to the two input frequencies, plus their sum and difference frequencies.

For instance, if the tuner is tuned to Radio 1 on 1214kHz, the oscillator will be on 1684kHz, producing frequencies of 470kHz ($1684 - 1214 = 470$) and 2898kHz ($1684 + 1214 = 2898$), plus the two input frequencies at the output. The i.f. amplifier will reject all but the 470kHz signal, which it will amplify. It is worth noting that the oscillating frequency could have been 744kHz ($1214 - 470 = 744$), but it is more convenient to have the oscillating frequency above the signal frequency in this instance. The oscillator is adjusted so that it is always 470kHz

above the frequency of the input tuned circuit, so as to always produce an i.f. of 470kHz.

Automatic gain control is incorporated in the circuit, and is described in more detail later.

To a beginner the superhet. may seem unnecessarily complicated, but this system is used in all good quality sets. By having the main amplification at a fixed frequency, it is possible to have the stages concerned adjusted for optimum performance, and a high degree of sensitivity and selectivity is obtained.

It would not be possible to obtain such a high performance if these amplifiers were at the signal frequency, having to operate over a wide range of frequencies. Also, although the circuit would be more simple, the physical layout and construction would be very critical. Thus most t.r.f. sets (ones which have the r.f. amplification at the signal frequency) usually have only one r.f. amp., and subsequently an inferior performance.


The superhet. does have disadvantages, the two main ones being its comparatively high cost, and that it is more difficult to adjust once built, as the oscillator and aerial circuits must be properly aligned over each band.

CIRCUIT

A circuit diagram of the tuner is shown in Fig. 2; TR1 performs the functions of both mixer and oscillator. Coils L1, L2, and L3 are wound on the ferrite aerial, L1 being the m.w. winding,

FOR
GUIDANCE
ONLY

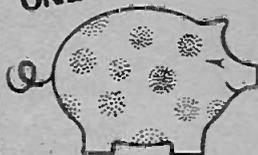ESTIMATED COST*
OF COMPONENTS
including V.A.T.



£8.50
excluding case

*Based on prices prevailing at time of going to press

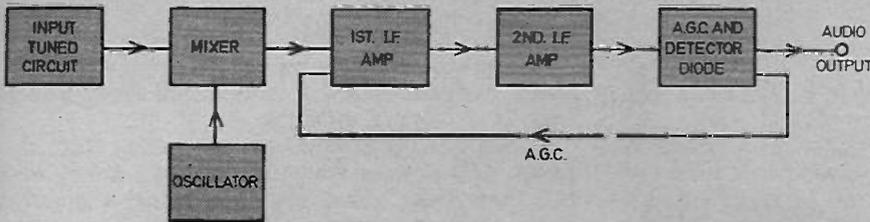


Fig. 1. Block diagram of a superhet. circuit.


and L1 and L2 in series forming the l.w. winding. Switch S1 is the wavechange switch, and this shorts out L2 in the m.w. position. These coils are coupled to the base of TR1 via the coupling coil, L3, on the m.w. band, and the tap on L2 plus L3 on the l.w. band.

The transformer formed by L4/5/6 is the oscillator transformer, and provides positive feedback between the collector and emitter of TR1, at a frequency determined by the tuned winding, L5. Capacitor C1 tunes the aerial tuned circuit, and C2 tunes L5 (C1 and C2 are ganged on a common shaft), C1a and C2a are alignment trimmers. With S1 in the l.w. position, C3 and C4 are shunted across L5, so as to reduce the oscillator frequency range to one which is suitable for l.w. coverage.

The output of TR1 is developed across the primary of IFT1, which is tuned to 470kHz. This couples the signal to the first i.f. amplifier, TR2. This has a similar transformer in its collector circuit, which couples the output of this stage to the second i.f. amplifier, TR3. From here the signal is coupled by a third transformer to the diode detector, D1. The volume control VR1 forms the load across which the audio frequency is developed. This is connected via C12 to the output socket.

The selectivity of tuner is largely determined by the three tuned circuits in the i.f. stages, and not by the selectivity of the ferrite aerial, as it would be in a simple t.r.f. design. This gives greatly superior selectivity.

Fig. 2. Complete circuit diagram of the MW/LW tuner.

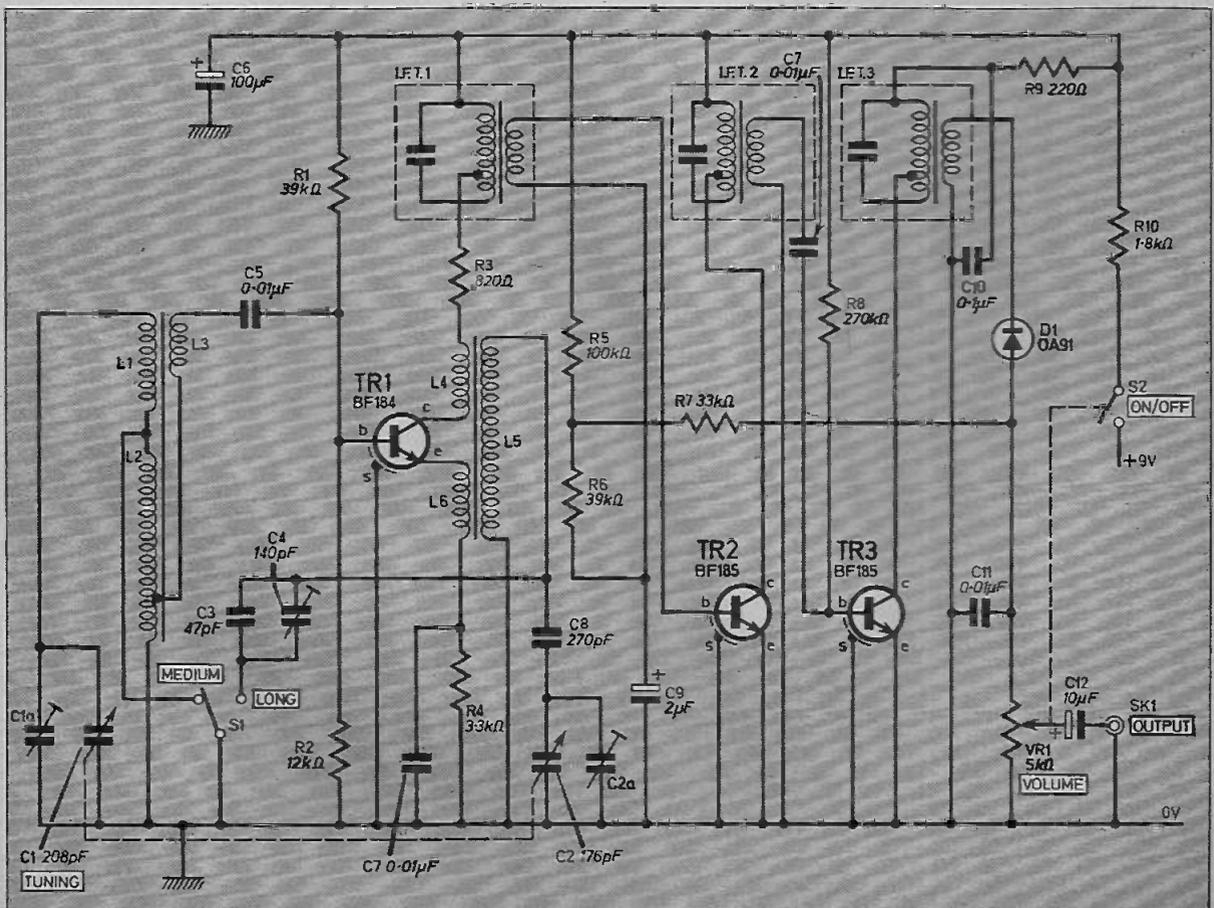

AUTOMATIC GAIN

Capacitor C11 smooths the r.f. half cycles that pass D1 to negative d.c. bias. This bias is fed via R7 to the biasing resistors of TR2, which are R5 and R6. On weak signals the bias voltage is small, and will have no significant effect on the circuit. On strong signals it will be large enough to cause the biasing voltage at TR1 base to fall noticeably, causing TR2 collector current to be reduced, this in consequence causing TR2 gain to be reduced.

The stronger the signal, the larger the a.g.c. bias voltage, and the resultant reduction in gain. This prevents the detector from being overloaded by strong signals, and also gives a fairly constant audio output level, even though the strength of received signals will vary considerably. It also minimises the effect of fading on stations prone to this form of interference.

Components....

Resistors

R1	39k Ω	R6	39k Ω
R2	12k Ω	R7	33k Ω
R3	820 Ω	R8	270k Ω
R4	3.3k Ω	R9	220 Ω
R5	100k Ω	R10	1.8k Ω

All $\frac{1}{2}$ W $\pm 10\%$ carbon

Capacitors

C1/C1a	208 + 176pF air spaced variable
C2/C2a	(Jackson 00 with trimmers)
C3	47pF silver mica
C4	40 to 140pF mica compression trimmer
C5	0.01 μ F disc ceramic
C6	100 μ F elect. 10V
C7	0.01 μ F disc ceramic
C8	270pF
C9	2 μ F elect. 10V
C10	0.1 μ F disc ceramic
C11	0.01 μ F disc ceramic
C12	10 μ F elect. 10V

SEE
**SHOP
TALK**

Inductors

L1/2/3	Denco MW/LW/5FR ferrite rod aerial (1 off)
L4/5/6	Denco TOC1 oscillator coil
IFT1/2	Denco IFT13 transformers (2 off)
IFT3	Denco IFT14 transformer

Semiconductors

TR1	BF184 silicon npn
TR2/3	BF185 silicon npn (2 off)
D1	OA91

Miscellaneous

VR1 5k Ω log. potentiometer with switch (S2).
S1 s.p.d.t. rotary switch.
SK1 phono socket.

Materials for case—see Fig. 3, control knobs (3 off), plain perforated board 33 by 24 holes 0.15 inch matrix, PP3 battery and connecting clip, 6BA and 4BA fixings, connecting wire.

CASE

The prototype case was made from 6mm plywood, with an 18 s.w.g. aluminium front panel. Details of this are shown in Fig. 3.

Commence construction by cutting out the parts to the sizes shown. The base, sides, and back are then glued together using a general purpose clear adhesive. Four corner pieces are used to strengthen the structure, and when these have been glued in position, the lid is glued in position also.

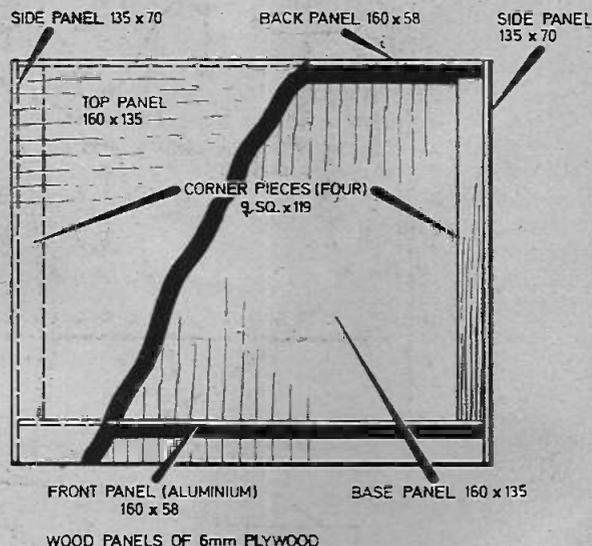


Fig. 3. Construction and dimensions of the prototype case for the tuner.

The front panel is drilled as shown in Fig. 4. A paper template can be made with the aid of C1/2 to enable the positions of the three small mounting holes for this component to be located.

Details of the mounting bracket for the component panel are also shown in Fig. 4. This is also made from 18 s.w.g. aluminium, drilled as shown in the diagram, and then bent at 90 degrees along the line indicated. The two 6BA clearance holes on the lower edge of the bracket are used to mount the component panel using two 6BA screws. The component panel is not mounted until it has been drilled, and then it is used as the template to locate the positions of the two mounting holes on the mounting bracket.

The bracket fits in place behind the front panel; C1/2, S1, VR1 and SK1 are mounted on the panel, so as to fasten the bracket to the front panel. Capacitor C1/2 is mounted by three 4BA 6mm countersunk screws. If the case is made accurately, the front panel assembly will be a snug push fit into the outer casing. The outer casing can be finished with a veneer of fablon, etc., or it can be painted or varnished, as preferred by the constructor.

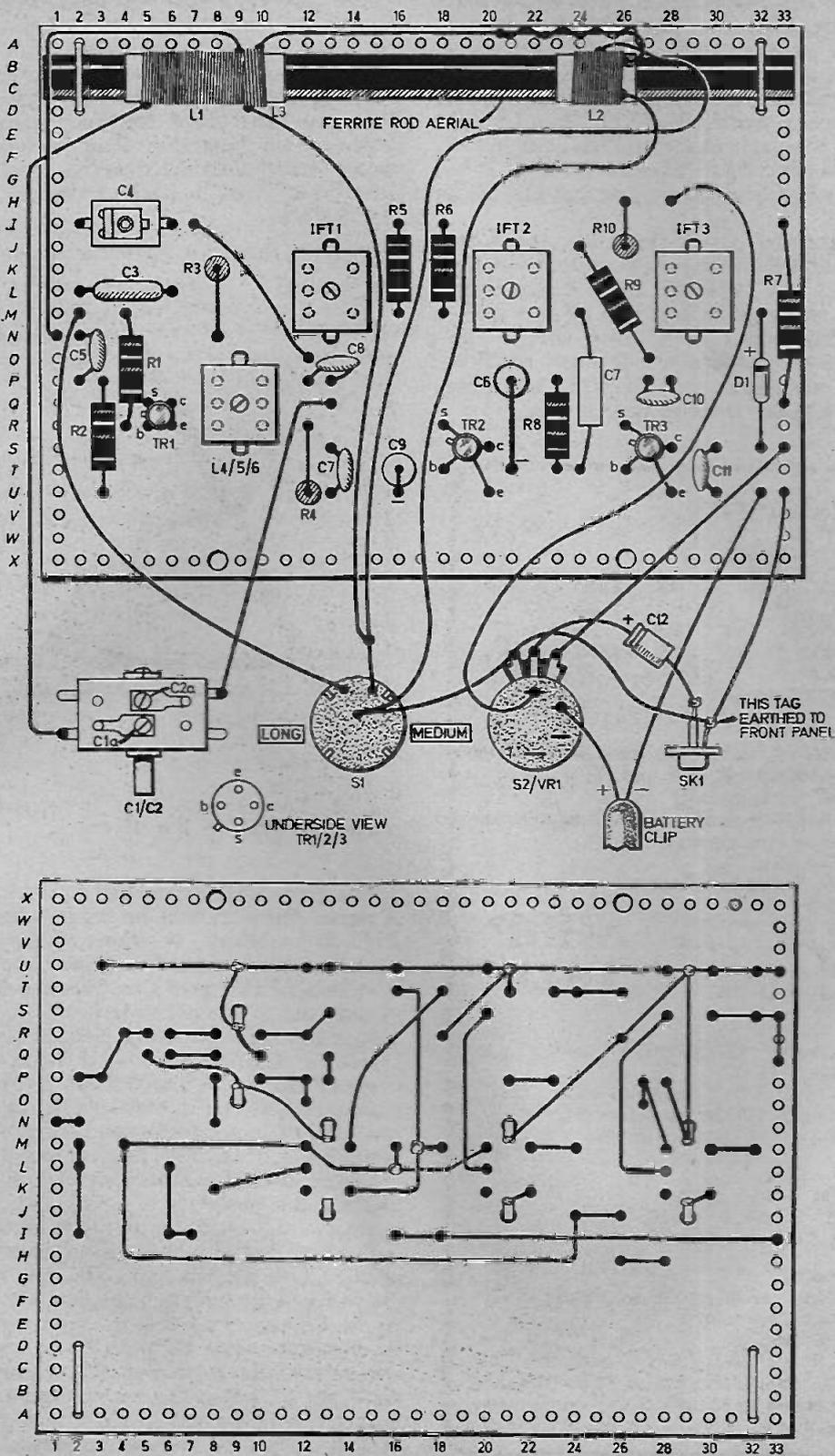


Fig. 5. Construction and wiring of the complete tuner.

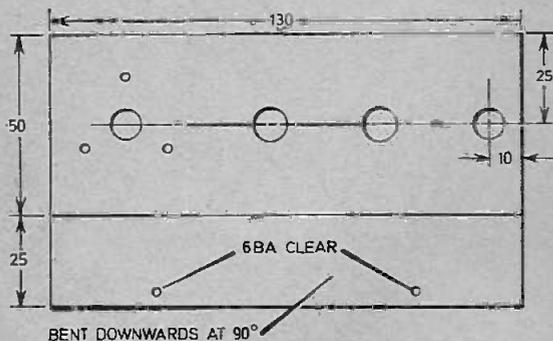
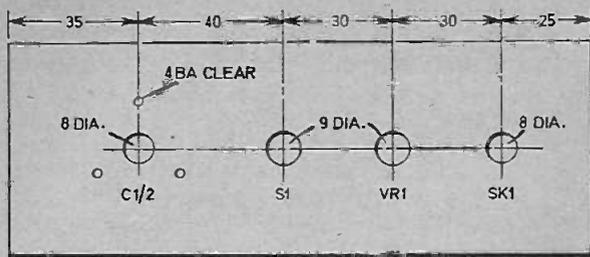


Fig. 4. Front panel and mounting bracket for component panel.

COMPONENT PANEL

Constructional details of the component panel are shown in Fig. 5, this diagram also shows all the other wiring of the tuner. The perforated board is a standard size.

Before the oscillator coil, C4, and the IFTs can be mounted, it is necessary to enlarge the holes for their pins and mounting lugs, using a No.31 twist drill. The ferrite rod is tied to the panel using two loops of thin p.v.c. sleeving, knotted on the underside of the panel.

Start the wiring by inserting all the components in the positions shown. The board is then turned over, and the negative supply lead is connected up, followed by all other wiring, until the board looks like Fig. 5. Wherever possible, use the component leads to do this wiring. Where these are too short, link wires made from about 18 to 22 s.w.g. tinned copper wire can be used. Where leads cross, or pass close to one another, they should be insulated using p.v.c. sleeving.

Note that connections are made to the mounting lugs of the IFTs and oscillator coil, as the screening cans are earthed.

The ends of the lead outs of the ferrite rod aerial coils have been prepared ready for soldering, and so should not be shortened. All other leads are kept short and direct, and are insulated.

ALIGNMENT

Before the tuner is ready for use, it is necessary to adjust the various tuned circuits for

maximum performance. With the unit connected to an amplifier or an earphone, it should be turned on, and switched to the m.w. band. Adjusting C1/2 should enable a few stations to be received. Tune accurately to one of these, choosing a weak one which will not operate the a.g.c.

Using a proper trimming tool (Denco TT5 or similar), give the core of IFT3 a slight adjustment in each direction, and leave it with the setting which gives the greatest volume. Repeat this with the core of IFT2, and then that of IFT1.

Note that the IFTs are prealigned, and any adjustment required will only be very small. Do not use a screwdriver to adjust the IFTs, as this could damage their cores.

R.F. ALIGNMENT

After dark the m.w. band is crowded from end to end. It will probably be found that the tuner covers slightly more than the m.w. band, and that there is an area at each end of the band where there are no stations. If the unit lacks sensitivity, this may be difficult to detect, but sliding L1/3 up and down the rod will permit sensitivity to be optimised at any setting of the tuning control.

Trimmer C2a is screwed down until the gap at the high frequency end of the band (C1/2 vanes unmeshed) disappears. Tune to the other end of the band and by slightly unscrewing the core of the oscillator coil, the gap should disappear here also, but will reappear at the h.f. end again. Repeat this process a few times, until, gradually, the correct coverage is obtained. Note that again, any adjustment required will not be large, especially that to the core of the oscillator coil.

Now tune to a weak station at the h.f. end of the band, and adjust C1a for maximum volume. Then tune to a weak station at the other end of the band, and slide L1/3 along the ferrite rod to find the setting which gives the best volume. Go back to the h.f. end of the band, and repeat this process a few times until no further improvement in sensitivity can be made. Carefully tape L1/3 to the ferrite rod, being careful not to alter their position (use insulation tape not Sellotape).


Turn to the l.w. band, and set C1/2 at about the central position. Then adjust the screw of C4 until Radio 2 is received. Slide L2 along the rod to obtain the best signal, and then tape it in this position. The chassis can then be placed in the outer casing, and the unit is ready for use. The battery fits between the two corner pieces on the right hand side of the case.

The lead connecting the tuner to the amplifier or tape recorder should be screened (the outer braiding going to the barrel of the jack plug). □

look! electronics really mastered

... practical
... visual
... exciting!

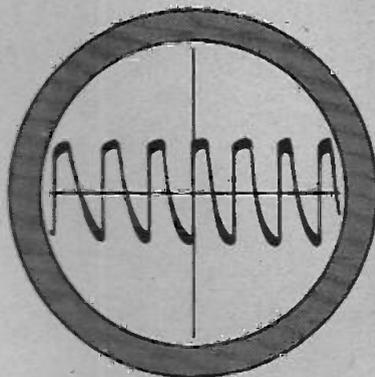no previous knowledge
no unnecessary theory
no "maths"




RAPY

BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

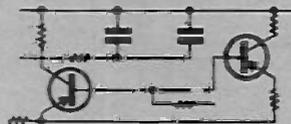2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**, Dept. EEL 55,
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE

special free gift also to all our students

CHROMASONIC electronics

Dept. 1
56, Fortis Green Road, London. N10 3HN.
telephone: 01-883 3705

INDUCTORS

Dence Maxi-Q Coils



Ferrite Rod Aerial:
FR1 Long & Medium Wave band (2000)
FR2 Long & Medium Wave band (5000)

Tuning Coils in two series:
Range

- 1 150 kHz to 400 kHz
- 2 515 kHz to 1.545 MHz
- 3 1.67 MHz to 5.3 MHz
- 4 5 MHz to 15 MHz
- 5 10.5 MHz to 31.5 MHz
- 6 30 MHz to 50 MHz
- 7 45 MHz to 78 MHz

* 50 pf tuning, all others based on 300 pf.

Series A Transistor-750 each

Only available in ranges 1 to 5 inc.
4 Coils complete each range:

- Blue - Aerial Coil
- Yellow - R.F. Interstage
- Red - Osc. Coil for 465 kHz I.F.
- White - Osc. Coil for 1.6 MHz I.F.

give range number, letter 'T' and colour.

Series B Dual Purpose Coils 650 each

For FET or Valve Circuits
All ranges available
5 Coils complete each range:

- Blue - Aerial
- Yellow - Interstage R.F.
- Green - R.F. plus reaction
- Red - Osc. Coil for 465 kHz I.F.
- White - Osc. Coil for 1.6 MHz I.F.

(Note use Red instead of White for ranges 6 & 7).



We stock from 1 μH to 19 mH
Check levels & prices when ordering


TUNING CONDENSERS



Tuned Block Filter incorporating a Ceramic element. Pre-tuned to 470 KHz. 3db bandwidth 5KHz. Zin 100K. Zout 100K.

LF-175 E1.45

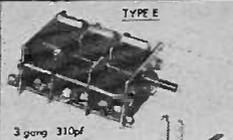- I.F. Transformers
- IFT 13 465 kHz 1st & 2nd of tuned 70p
 - IFT 14 465 kHz final single tuned 70p
 - IFT 15 10.7 MHz d/tuned 75p
 - IFT 16 1.6 MHz 1st & 2nd of tuned 65p
 - IFT 17 5.6 MHz Final d/tuned 85p
 - IFT 18 465 kHz or 1.6 MHz d/tuned 70p



3 gang 310pf
47-T



TYPE CB04
Slow Motion Drive
Ratio 6:1 Ref: 4511



TYPE O
365pf 2.5 x 365/1.58



TYPE OO
288-176pf with screen & trimmers 42-55



DILECON
100pf E1-25
500pf E2-11

VEROBOARD



	COPPERCLAD	PLAIN	EXTRA
0.1"	0.15"	0.15"	P&P
2 1/2" x 1"	7p	7p	-
2 1/2" x 3 1/2"	26p	21p	12p
2 1/2" x 5"	10p	25p	13p
3 1/2" x 3 1/2"	30p	25p	-
3 1/2" x 5"	34p	34p	25p
1 7/8" x 2 1/2"	90p	69p	45p
1 7/8" x 3 1/2"	E1.21	75p	57p
1 7/8" x 5"	-	99p	10p

D.I.P. Breadboard 4.15" x 6.15" E1.40
VEROSTRIP-Stack (1" or 1.5") 43p
Pin Impression Tool (Stack .1" or .15") 51p
Spot Face Cutter INVO14 8p
Terminal Pins in Pkts. of 50 (Stack .1" or .15") 22p

Details of I.C.'s, Rectifiers, Diodes, Bridges, Passive Components, LED's, Clocks, Triacs, etc. can be seen on other pages and/or issues of Wireless World; Practical Wireless, and Practical Electronics.

Electrolytics

UF	4V	6.3V	10V	16V	25V	40V	63V	100V	160V	450V
1.5							6p	8p	15p	
2.2							6p	8p		
3.3							6p			
4.7							6p		17p(4UF)	
6.8							6p	8p		
10							6p	8p		
15							6p	8p		
22							6p	11p		
33							6p		33p(32F)	
47							6p	8p	25p(50F)	
100							6p	8p	14p	25p
150							6p	8p	11p	14p
220							6p	8p	11p	14p
330							6p	8p	11p	14p
470							8p	11p	14p	20p
680							10p	14p	20p	25p
1000							13p	14p	20p	25p
1500							18p	19p	25p	
2200							18p	24p		
3300							26p			
4700									44p	68p
6800									79p	149p
10000										252p

DIODES

AA119	10p	8Y103	22p	0A91	8p
AA120	10p	8Y105	16.5p	0A200	11p
AA129	10p	8Y126	16p	0A202	12p
BA100	10p	8Y127	16.5p	Z5120	5p
BA102	22p	8Y133	22p	Z5140	25p
VA110	44p	8Y164	54p	Z5141	42.5p
BA115	17p	8Y176	E1.62	Z5142	32.5p
BA144	20p	8Y182	E1.62	Z5170	10p
BA145	22p	8Y250	25.5p	Z5270	11p
BA148	22p	8ZX70	Z7p	Z5271	16p
BA156	20p	Series		Z5278	36p
BA155	15.5p	8ZY88		INVO14	8p
BA156	16.5p			IN916	10p
BA116	10p	0A47	11p	IN4009	7p
8B104	45p	0A79	10p	IN4148	5p
8B108	41p	0A81	8p	IN4448	9p
8Y100	16.5p	0A85	10p	I25 Series	18p
		0A90	8p		

REGULATORS

100mA (TO-39)	500mA (TO-3)	500mA (SO1-32)	1A (TO-220)
3V	5V	5V	5V
7.5V	12V	15V	15V
10V	15V	20V	20V
15V	20V	25V	25V
20V	25V	30V	30V
490V	495V	500V	500V

DIGITAL SWITCH

ICD encoded digital switch
Reading 0 to 9. Suitable for
digital clock alarm setting
DVM input scaling etc.

1 to 9. E1.49 each.

ALUMINIUM BOXES

With Baseplate and screws.




REF	(No.)	(L)	(W)	(H)	PRICE	P&P
AB7	22"	51"	13"	4.5p	15p	
AB2	4"	4"	1.5"	4.5p	15p	
AB9	4"	2.5"	1.5"	4.5p	15p	
AB10	4"	5.5"	1.5"	5.1p	15p	
AB11	4"	2.5"	2"	4.5p	15p	
AB12	3"	2"	1"	3.6p	15p	
AB13	6"	4"	2"	6.1p	17p	
AB14	7"	5"	2.5"	7.3p	17p	
AB15	8"	6"	3"	9.2p	17p	
AB16	10"	7"	3"	E1.05	20p	
AB17	10"	4.5"	3"	9.2p	25p	
AB18	12"	5"	3"	E1.04	25p	
AB19	12"	8"	3"	E1.38	25p	

THYRISTORS SCR'S

V	800mA	4A	8A
30v	MC2102	32p	106y
50v			106f
60v	MC2103	44p	

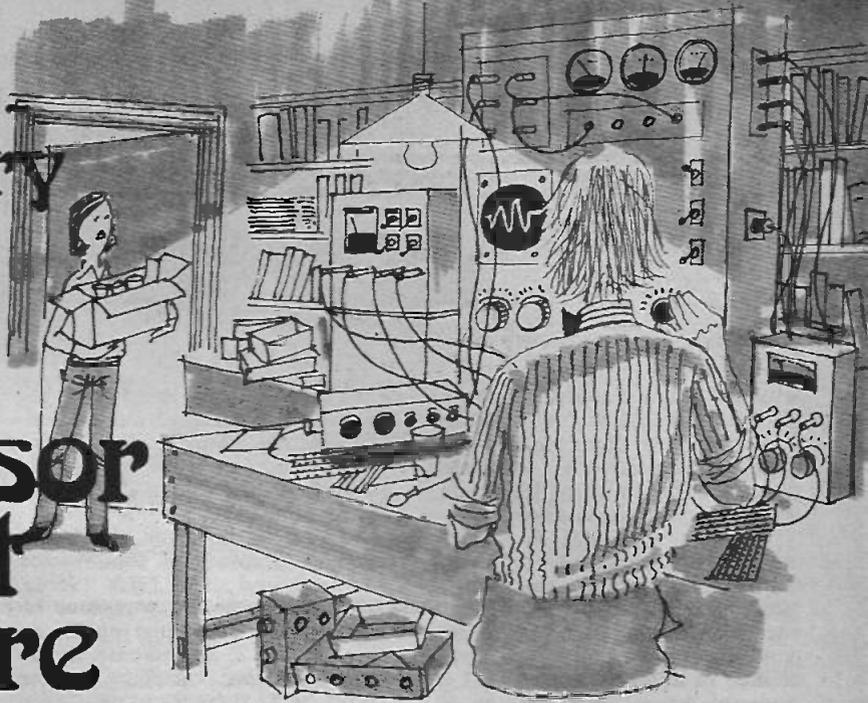The Extraordinary Experiments of Professor Ernest Eversure



by Anthony John Bassett

Professor Ernest Eversure, or the Prof. as his friends call him, has been experimenting in electronics for more years than anyone can remember and we thought that you might like to hear of, and perhaps repeat, some of his extraordinary experiments. Anthony J. Bassett recounts some of these experiments every month so why not follow the Prof's work and learn along with young Bob, his friend.

PAUL rushed across the laboratory and switched off the helmet. He removed it from the head of his sister Suzy, despite her protests.

"How did you manage to get this helmet?" he asked, "I only built one of them and that has been destroyed!"

"I found your plans in the workshop," Suzy replied, "and built a copy for myself. It's really fabulous!"

"We've had quite enough trouble with the one I built." Commented Paul. He handed the helmet to the Prof., who locked it safely away in a cupboard.

With the electronic kazoo and banjo in one hand, and his sister's hand in the other, Paul and Suzy bade farewell to Bob and the Prof.

Bob and the Prof. had both had enough, for the time being, of the mysterious helmets and their seemingly unpredictable properties, and began to discuss various theories of operation of transistors.

TRANSISTOR THEORY

"There are so many different explanations of how a transistor works," complained Bob, "That I wish someone would come up with one that is sufficiently simple for me to understand and use in a practical way, without need of huge mathematical formulae or complicated concepts."

"To find a simple but workable theory," replied the Prof., "We only need to go back to the history of the invention of the transistor, to find that a transistor can be regarded, for many purposes, simply as a variable resistor, whose resistance is controlled by base current. This can be seen by a simple experiment."

He sketched the circuits shown in Figs. 1a and b. As the variable resistor in Fig. 1a is altered in value, the apparent resistance of the transistor varies, and the meter needle moves across the scale.

If the transistor is a silicon *npn* type such as a BC109 (almost any *npn* silicon transistor will do), the apparent resistance

will vary from a very high value, usually over one megohm, down to a very low level (usually below one ohm). If an *npn* germanium transistor (such as type AC176) is used, the resistance shown is usually considerably lower than for silicon. This is due to differences between the properties of the silicon and germanium materials of which the transistors are constructed.

As indicated by the multimeter, the transistor appears like the variable resistor of Fig. 1b.

Bob quickly built the circuit of Fig. 1a. He soon found that, although the circuit behaved in the manner described by the Prof., the resistance values were different according to which way round the meter probes were connected!

The correct method of connecting the meter is such that the test voltage will bias the collector of an *npn* transistor positive with respect to the emitter. This can be confusing as on most meters, the positive wire is black and the negative wire is red! A simple test to find out which is which is to connect the meter leads to the base and collector of an *npn* transistor. When the lowest reading is obtained, the positive lead is on the base.

With the meter Bob was using, the black lead was positive with respect to the red lead. As he

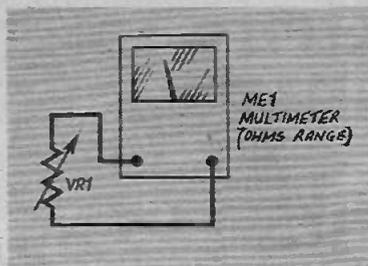
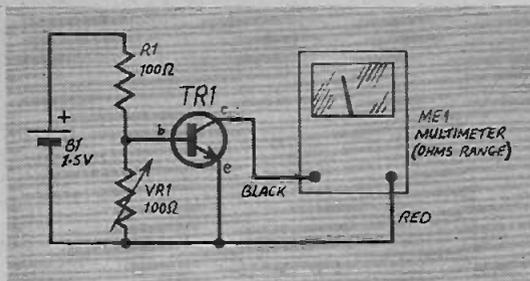


Fig. (1a left) Transistor action as a variable resistor. The transistor appears like the variable resistor of Fig. 1b (right).

adjusted the variable resistor VR1, Bob found that a variation of only a few ohms caused the apparent resistance of the transistor to alter by hundreds, or even thousands, of ohms.

"This is one way in which amplification can be demonstrated," remarked the Prof., "Isn't it marvellous how a small variation in one part of the circuit can produce such a large change in another; and if VR1 is replaced by a transistor as in Fig. 2., the variation in resistance seen by the meter will be even greater."

Bob built up the circuit of Fig. 2 and tested it. He found that only a small alteration of the variable resistor caused the meter needle to swing right across the scale! However, the direction of movement had reversed.

"You will notice that in Fig. 1b, as the resistor is varied and increased, the meter reads a higher value, and as the resistor is decreased the meter reads a lower value.

In Fig. 1a, however, the meter reading increases as the resistor is decreased and vice versa. Addition of another transistor inverts the action once again, so that in Fig. 2, an increase in the value of the variable resistor results in an increase in resistance reading on the meter."

Now Bob drew a diagram (Fig. 3).

SWITCHING ACTION

"It seems to me that almost any number of transistors could be connected in this way, Prof." he suggested, "And each one

would act as a variable resistor to control the resistance of the following transistor."

The Prof. agreed. "But you will find, that if you build that circuit and measure the voltage at the collector of each transistor whilst gradually varying VR1, there will be a big difference between the speeds at which the voltages vary. The voltage on the collector of TR1 will change much more slowly than the voltage on the collector of the next transistor, and so on.

After the first two or three transistor stages, the subsequent stages switch rapidly from high to low resistance even if VR1 is varied very slowly! This is called "transistor switching action" and the transistor which is acting like a switch goes quite rapidly from a high resistance state which "blocks" current flow, to a low resistance state like a closed switch."

"When the transistor is not acting as a switch, either fully conducting, or 'blocking' current, it may be in an intermediate condition where it is conducting but there is an appreciable resistance to the flow of current. This condition is the basis of operation of a 'class A' amplifier."

"I would like to experiment with class A amplifiers," remarked Bob, "and build some inexpensive and basic designs for general purpose use and for music. A small portable audio amplifier which I could take from one workbench to another, or carry about as I please could be very useful. Tell me, Prof., how were amplifiers built before the invention of the transistor?"

CARBON AMPLIFIER

"Before transistors came into extensive use, thermionic valves were relied upon for most amplifiers. But solid state audio amplifiers were in use even before the invention of the thermionic triode valve, and


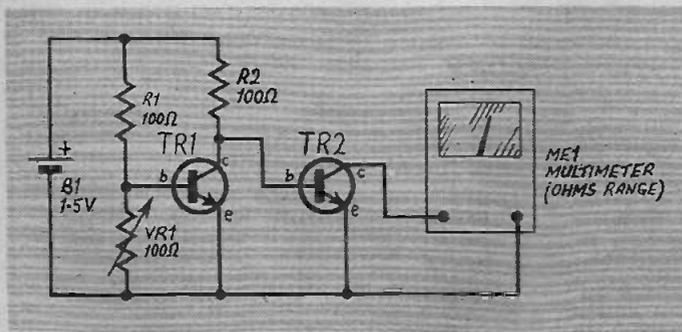


Fig. 2. One transistor is seen by the meter as a resistor whose resistance is varied by the other (TR1).

Fig. 3. Each transistor is controlled by the previous one.

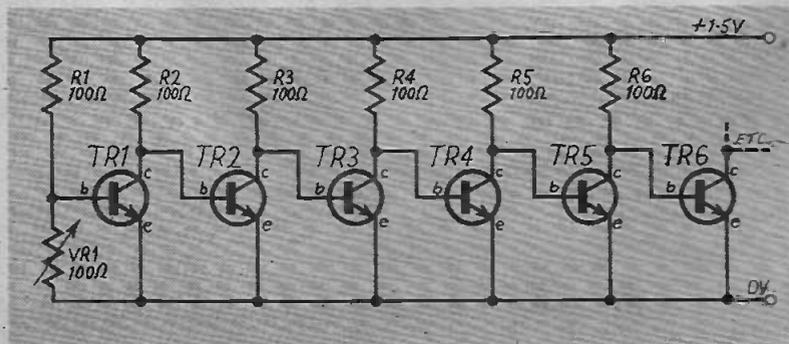

MAINS TRANSFORMERS

All models 230-250 volt primaries

1V	1 amp (special)	1.75
2-4v	5 amp	85
6-3v	2 amp	1.00
6-3v	3 amp	1.50
9v	1 amp	95
9v	3-5 amp	1.95
12v	1 amp	1.00
12v	2 amp	1.50
6-5v-0-6.5v	1 amp	1.35
18v	1 amp	1.25
20v	1 amp	1.00
24v	1 amp	1.50
24v	3 amp	3.50
12-0-12v	50mA	1.20
0-0-6v	50mA	1.20
8-0-8v	1/2 amp	1.25
18-0-18v	2 amp	3.50
25v	1/2 amp	1.95
30v 2 amp & 6-3v 1 amp		5.50
40v 5 amp & 5v 1 amp		7.50
37v	3/4 amp	4.50
30v	3/4 amp	22.00
80v tapped 70v & 70v	4 amp	5.50
230v-60mA & 60v	1.5 amp	1.75
275-0-275v at 33mA & 6-1v	3 amp	2.25

Charger Transformers

6v and 12v	2 amperes	1.25
6v and 12v	3 amperes	2.25
6v and 12v	5 amperes	3.50

RHT Transformer 0Kv at 23mA (intermittent) 5.50

NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XNII Price **99¢** each, 10 for **£9**

OIL PUMP

Driven by Redmond Motor of approx. 1/20th horse power, pump originally intended for oil-fired boilers etc. with normal inlet and outlet pipes and unions. **£2.15** plus 30p post and insurance.

LIGHT DIMMER KIT

For dimming up to 250w without heat sink or 750w with heat sink. This comprises quadrate variable control potentiometer, condenser, resistor, tag strip for mounting and data. Price **£1.50**.

RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable for closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. **33p** each.

AM/FM TUNER

Unit made by the American GEC company. 3 transistor, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tuner AM range 540 to 1620 KHz. FM range 88 to 108 MHz. Switches for on-off and AFC. Outputs for MXP or direct. Special snip price **£5** plus 30p post. Three or more post free.

7 WATT STEREO AMPLIFIER

Again by the American GEC company. This has exceptionally good tone quality. Is complete with pre-amp and treble base, volume and balance controls. Also has mains smoothing circuit and rectifier so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner, pick-up, mike, etc. Special snip price **£6** plus 30p post. Three or more post free.

WINDSCREEN WIPER CONTROL

Very speed of your wiper to suit conditions. All parts and instructions to make. **22.75**.



PORTABLE CABINET OFFER

A nicely made portable cabinet, soft padded black finish intended for portable stereo system. Dimensions as sketch. With motor board cut out for Garrard 8P 25. This was obviously a very costly cabinet originally made for deluxe record player. Offered at **£1.95** plus **£1** carriage free if bought with the Garrard or BSR record decks.



CAR CASSETTE POWER SUPPLY


To give stabilized output of 6 or 9v, complete kit contains 2 transistors—zener diode—zero board panel resistors and plastic case to house it with constructional data. **£2.50**.

PLAY YOUR 8-TRACK CASSETTE FROM MAINS

12v, 700mA unit all assembled and in neat plastic case with mains lead and terminals. Full wave rectifier and transformer has overload protection and is double insulated. One of today's best buys at **£2.95** + 35p V.A.T.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated to equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated, 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signa. Signalling, etc. Price from makers probably over **£20** each. Special snip price **£8.50** plus 25p post and insurance. Don't miss this terrific bargain.

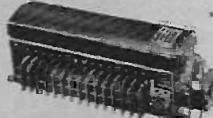

SWITCH TRIGGER MATS


So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc.

24in x 18in **£1.99**
13in x 9in **£1.50**

High compliance 8" round speakers suitable for 8-12 ohm outputs, these speakers have rubber mounted diaphragms and will handle up to 12.5 watts. Made originally for an expensive Decca hi-fi outfit, we offer at **£3.25** each or **£5.00** a pair plus 40p each postage.



THIS MONTH'S SNIP

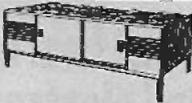

STEREO RADIO CABINET

Long, Low and Modern. Teak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 4ft 2in x 14in x 15in. Probably cost over **£20.00** to make. Our price **£3.10** each.

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable, of course, to programme other than central heating and hot water. For instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated. Size 3in x 3in x 2in deep. Price **£4.35** as illustrated but less case.



TAPE DECK

In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 31. Mains operated on metal platform with tape head and guide. Not new but in good order. Price **£1.95** plus **£1** post and insurance.

TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient and quiet running. Is set in Hoover and blower heaters costing **£15** and more. We have a few only. Comprises motor, impeller, with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. 2kW Model **£2.75**. Don't miss this. Control Switch **60p** plus V.A.T. P.&P. 60p.



SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25-31.39 metre bands—Kit contains chassis front panel and all the parts. **£1.25**—crystal earphone 50p.

SPIT MOTOR

200-250V Induction motor, driving a Carter gearbox with a 1 1/2" output drive shaft running at 5 revs p.m. Intended for roasting chickens, also for driving models—windmills, coloured disc lighting effects, etc. **£2.50** plus 20p post and ins.



INFRA-RED BINOCULARS

Made for military purposes during and immediately after last war to enable snipers, vehicle drivers, etc. to see in the dark. The binoculars have to be fed from a high voltage source (5KV approx.) and providing the objects are in the rays of an infra-red beam, then the binoculars will enable these objects to be seen. Each binocular eye tube contains a complete optical lens system as well as the infra-red cell, technical data on which is available. The binoculars are unused, believed to be in good working order. In fact they were never issued and are still in original cases, but since they were made a long time ago, they can hardly be called new. Sold without guarantee. Price **£15.50** per set + **£1** carriage.

BATTERY CHARGERS

Famous Atlas in metal case with meter, output leads for charging 6 or 12v charging simply by changing plug on front panel. Ready built new and still in maker's original packing. Two models: 1 1/2 amp **£1.99** and 3-4 amp **£2.95**. Please add 40p postage for one and 75p postage for two.

12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price **£2.50** plus 30p post & packing.

HEAVY DUTY MAINS POWER PACK
Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 18V. This really is a high power heavy duty unit with use. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price **£3.75** plus **£1.00** post.



NEW ITEMS THIS MONTH

The bargains in this column are just some of the items which appeared in the December supplement to our catalogue. You can receive this catalogue and the next 12 supplements by sending **£1**.

Laboratory volt meter, BS1. This is the conventional square case, size 7" x 7" x 3 1/2" with a rubber carrying handle and rubber feet for horizontal and vertical standing. The meter is intended for horizontal use on the bench and has a mirrored scale. Hefty terminals along the top select the 3 ranges 0-150v, 0-300v and 0-600v D.C. Price **£6** plus **£1** post and insurance.

Laboratory amp meter, companion instrument to the above, but to read 0-200 amps 50 cycles, **£5** plus **£1** post and insurance.

Soil heating transformer, 4v, 5v or 6v output, very heavy duty secondary rated at 250 amps, price **£20** plus carriage **£2** first 100 miles then **£1** per very heavy duty extra.

7 watt stereo/mono amplifier with usual switches and controls, in attractive teak style case, **£2** 3 core lead, 7" 6" long, ribbed, virtually non-kinkable 23/36 conductors, no OK for 8 amps. Price **10p** each.

0-1 mA meter 2 1/2" square, flush mounting, English make ex equipment but perfect. **£1.75**.

0-100 microamp meter, as the above, but **£2.25**. Solenoid 4-6v, size approx. 1" x 1" x 4" thick, twin coils give excellent pull. Mounted in frame box easily removable from this frame. Fitted with lever giving approx. 1/4" push or pull. Price **30p** each.


Gold cathode tube Swiss made "Eletata" type no. ER 12A. We have no technical information on this tube and if any reader has this we will be obliged for any information. Price of the tubes **30p** each.

AC mains operated relay with single changeover 10 amp contacts, open type single screw fixing through the base. **50p** each.

Push switch, metal body and metal push, normally on. These are replacements in many "break glass" fire alarms. Made by Arrow, contact rating 250v 5 amps. **30p** each.

MAINS TRANSISTOR POWER PACK

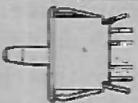Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPL, PPS, PPA, PPE, PPF, PPG and others. Kit comprises: main transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only **£1.50**.



plastic body, snap fitting into a hole size 1 1/4" x 1". Offered at only a fraction of its proper price namely **20p** each.

Dimo, but single pole changeover, fits into a hole size 1" x 1". Price **15p** each.

(Note: the two switches above do not require a knob as they have a polished and tapered plunger). Dimo, but double knob, 10p extra with knob.

Two new speakers, 5" round 8 ohm impedance 5 watt output, **£1.25** plus 20p post and 6" mid-range 12 watt speaker, **£4** plus 40p post. (This is a GOODMAN speaker don't miss it!).

AM/FM tuning condenser as fitted to many Japanese and Hong Kong portables, this has two main tuning sections and four trimmers, approx. size 1" x 1" x 1". **60p** each.

Battery charger kit comprising 2 amp transformer, 2 amp full wave rectifier and 2 amp motor suitable for charging 6v or 12v. Special bargain price **£1.50** the kit plus 30p post.

McDonald record auto-changer with cueing arm and ceramic stereo cartridge. This is a very superior auto changer and one we can thoroughly recommend. Limited quantity, special price **£7.35** plus **£1** post and insurance. Plinth and cover (the plinth has to be modified very slightly) available, price **£4.95** plus **£1** post, or if you buy both together you can get a discount of **21**.

Instrument case measures 18" x 12" x 12". This is a very well-made case built up on an angled framework specially designed for instruments which has rounded corners and edges. Into this framework fits the 6 panels. All panels are laser cut for ventilation.

side panels are also fitted with handles which drop down and in the down position are almost flush; the bottom panel has four rubber feet, the back panel has aperture for leads voltage adjustment panel and fuses, the front panel you provide yourself. These instrument cases would probably cost around **£15** each. We have approx. 100, not new but in very good condition and offer them at **£8** each plus carriage.

Battery condition testers. This is another item which has been set out of stock temporarily but we are pleased to say in stock again. Price now **£3.50**.

TERMS:—ADD 8% V.A.T.
Send postage where quoted—other items, post free if order for these items is **£6.00**, otherwise add 30p.

J. BULL (ELECTRICAL) LTD.
(Dept. E.E.), 102/103 TAMWORTH ROAD,
CROYDON CRO IXX

With a kit
as complete as this,
all you need add
is a little time.



You may have found, from past experience, that your definition of 'complete' is not quite the same as other people's. And your so called complete kit comes minus a cabinet, or knobs, or a multitude of other bits and pieces.



That won't happen with a Heathkit.

Take our very popular digital alarm clock kit. Every part you need will be there, right down to the solder. And you'll also receive a very easy to understand instruction manual that makes light work of assembly.

In fact all you need are a few basic tools and a few enjoyable hours of your time.

After which you may like to try your hand at our AR-1214 stereo receiver. Or even a TV.



And how about an ultrasonic burglar alarm disguised as a book?

Or, for a bookful of other ideas, just clip the coupon and we'll send you the Heathkit catalogue.

Otherwise call in and see us at the London Heathkit Centre, 233 Tottenham Court Road.

Or at our showroom in Bristol Road, Gloucester.

You'll find it well worth your time.

Heath (Gloucester) Limited, Dept. EE-55

Bristol Road, Gloucester, GL2 6EE.

Tel: Gloucester (0452) 29451.



To: Heath (Gloucester) Limited,
Dept. EE-55 Gloucester, GL2 6EE.

My free Heathkit catalogue, please.

Name _____

Address _____

Postcode _____

Remember easy terms are available
with the Heathkit Monthly Budget Plan.

HEATH
Schlumberger



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering - yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits—assemble components—build things—experiment. You enjoy every minute of it! You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. AT NO EXTRA CHARGE! And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire high-powered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book - see how easy it is - read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST
TODAY FOR
FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CEE 05
READING RG7 4PF

CEE 05

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME _____

ADDRESS _____

POSTCODE _____



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Everyday Electronics, May 1975

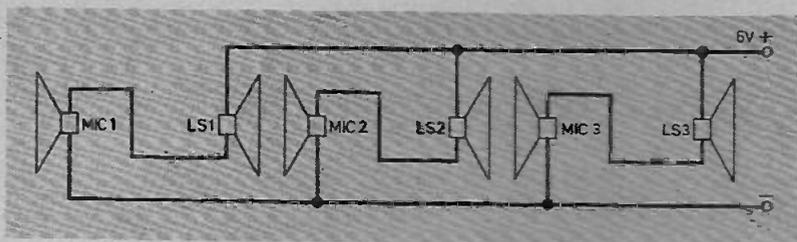


Fig. 4. The carbon granule amplifier.

these took advantage of the electrical properties of graphite in the form of carbon granules. Here is a diagram to illustrate the operation of this type of amplifier." (Fig. 4).

"Sound is picked up by a carbon granule microphone MIC1 which acts as a variable resistor modulating the current flow through a small loudspeaker or earpiece LS1. The sound output from LS1 brings about a sound level higher than the original signal, and this is picked up by MIC2. An even louder signal is produced at LS2. A further stage, MIC3, LS3 can be used to amplify the signal even further. But the greater the number of stages used, the greater the risk of acoustic feedback, high noise level, and extensive deterioration in signal quality."


"It would be very interesting to build one of these," remarked Bob, "and compare it with an amplifier built using transistors!"

From an obscure section of his enormous store of components the Prof. produced a number of carbon granule microphones, and also some high impedance moving reed headphone inserts.

"Fortunately I happen to have some suitable microphones and loudspeaker units here. These are ex-government and can be obtained from some government surplus stores."

"Why use moving-reed loudspeakers?" enquired Bob.

Fig. 5. A multiple stage class "A" amplifier can be regarded as a series of variable resistors each controlled by the signal from the previous stage.

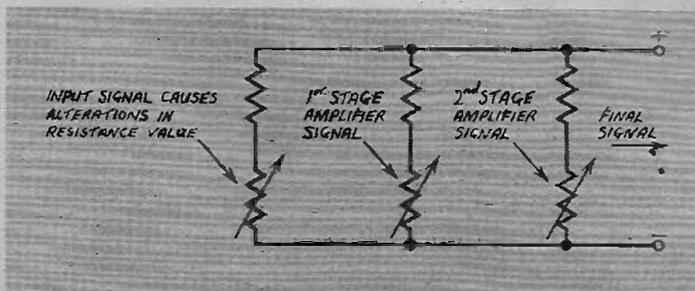

carbon granule amplifier inserted part way along the line would cause the speech to be more intelligible at the other end."

"In amplifiers built especially for this purpose, the carbon granules were in direct contact with the speaker diaphragm, and this improved quality and efficiency very considerably in comparison with use of a separate microphone!"

"It is interesting to experiment with methods of amplification which differ somewhat from the conventional valves and transistors, yet we may consider both the carbon granule amplifier, and the circuit of Fig. 3 to be a series of variable resistors each of which has an amplifying effect, and an effect upon the following stage. Compare this diagram (Fig. 5) with both of the other two (Figs. 3 and 4). The variable resistors represent transistors, carbon microphones or any other device whose resistance can be controlled by another similar device. You can easily see how a number of class A stages can be linked together so that each stage is controlled by the previous one."

Bob had been listening to the Prof. through the carbon granule amplifier. As the Prof stopped speaking, Bob suddenly listened more closely to the earpiece. Then he handed it to the Prof. "Do you hear what I hear Prof?" he asked, "A strange bubbling noise!"

The Prof. could hear it too, and it rapidly grew louder so that it could be heard easily without the aid of the amplifier.

The Prof's experimental robot appeared, covered in bubbles.

A foaming mass appeared to be pursuing the robot towards Bob and the Prof., and from this mass came uncanny squeaking, clicking, popping, bubbling and oozing sounds.

Continued next month.



DOWN TO EARTH

By GEORGE HYLTON

"What is the meaning of *loop* in expressions like *loop gain* which are found in literature concerning amplifiers?"

There are loops and loops. In electrical circuits, a loop is just any part of the circuit in which you can trace a path from a starting point through connecting leads and circuit elements and get back to where you started from without passing the same way twice. There are loops in all electrical and electronic circuits—often dozens of them.

In the present case "loop" has to do with feedback, probably negative feedback. In a negative feedback amplifier the significant loop is the one which connects the feedback from output to input. It ought to be called a feedback loop, of course, but electronic engineers, in their slipshod way, just refer to it as "the loop", in much the same way that astronomers talk of "the galaxy", meaning our own galaxy, and disregarding the fact that the universe is full of the damn things.

OPERATIONAL AMPLIFIER

The bare bones of a common type of negative feedback amplifier (most "operational amps" are like it) are shown in Fig. 1. Here A is an amplifier of unspecified type whose action is to increase the input voltage V_i by A times, A being the amplification, of

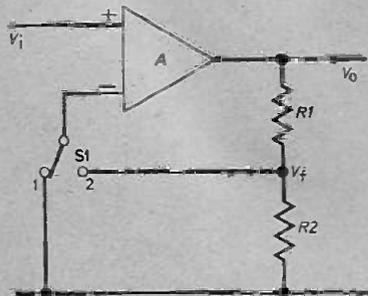


Fig. 1. An operational amplifier with negative feedback.

course. This gives an output voltage V_o , which of course is A times V_i . The polarity of V_o can be the same as that of V_i or it can be inverted, depending on the design.

The present amplifier has alternative input terminals. If the input voltage is applied to the one marked with a positive sign it gives rise to an amplified output which is in phase with the input. If V_i goes to the other terminal, marked with a negative sign, the output is in the opposite phase. The two inputs are called the non-inverting and the inverting input terminals respectively, at any rate in operational amplifier parlance.

The plus and minus signs have nothing to do with d.c. voltages, they are just a bit of designers' shorthand.

In the present case the input goes to the non-inverting terminal, so the output V_o is in phase with V_i . Being highly observant, you'll have noticed that a third voltage, V_f , is marked on the diagram. It's just a portion of V_o tapped off by the voltage divider (or potential divider—if you like) formed by $R1$ and $R2$.

At the moment, V_f isn't doing anything. But move $S1$ to position 2 and V_f is now connected to the inverting input. This means that a new output is produced, which is in opposite phase to the original V_o and so tends to cancel V_o . It can't cancel V_o completely, because if there's no V_o there can't be any V_f to do the canceling. This is a long-winded way of saying that with $S1$ in position 2, V_f becomes a negative feedback signal.

EFFECT OF NEGATIVE FEEDBACK

How does the negative feedback affect the gain and frequency response? This is shown

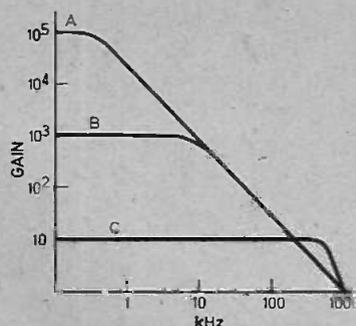


Fig. 2. The effect of negative feedback on gain and frequency response.

on the graph (Fig. 2). Naturally, it depends on how much of V_o is tapped off by the voltage divider and fed back. The graph shows the effect of tapping off various proportions, from none at all (curve A), which is the case with $S1$ at position 1, through B and C which correspond to $S1$ at position 2 and different values of $R1$ and $R2$. Curve B is for a moderate amount of feedback, curve C for rather a lot.

As you can see, when feedback—negative feedback, that is—is applied, gain is sacrificed but the frequency response is improved. That's not all. Distortion is reduced, too, and the effect on the gain, of changing the supply voltage, is reduced.

So where does "loop" come in? Well, with $S1$ at position 2, there is a negative feedback loop from the amplifier output back to the input and of course through the amplifier itself back to the output again. Putting $S1$ to position 1 breaks this feedback loop. For this reason the gain without feedback (curve A) is often called the "open-loop gain", that is the real gain of the amplifier inside the triangular "box".

Moving $S1$ so as to connect the feedback signal closes the feedback loop and we now have the "closed-loop gain", often called just the loop gain. It approximates to V_o/V_i , especially if a lot of feedback is applied. This means that the gain can be set by choosing the right values for $R1$ and $R2$. If $R1=9 \times R2$ the voltage is divided by 10, so $V_o=10V_i$ and the gain is 10, or very nearly so. To be able to set the gain to an accurate value by selecting $R1$ and $R2$ you should use an amplifier with a very high open-loop gain then apply a lot of feedback.

Sinclair Project 80



**For elegant, versatile, stereo hi-fi systems
designed and built by you!**

Until recently, if you wanted a first-class hi-fi system you had two ways to get it.

You could buy the individual electronic components and build a system from scratch. If you were an electronics genius – fine.

Or you had to buy ready-made units. Expensive – and dull. About the only creative pleasure you'd get would be matching your amp and your speakers, or making your speaker enclosures.

So what's new?

A comprehensive hi-fi system, combining the enjoyment and satisfaction of build-it-yourself (without too much struggle) ... a real value-for-money feeling ... and results of the highest quality.

It's the new Sinclair Project 80.

How does Sinclair Project 80 work?

Project 80 is a comprehensive set of hi-fi modules, or sub-assemblies. Amps ... pre-amps ... FM tuner ... stereo decoder ... control units ... everything you need to assemble hi-fi units. They're all designed to look alike and they're all completely compatible with each other. Simply decide on the specifications of the unit you want to build ... buy the necessary modules ... connect them ... and house them.

No need to buy everything at once for your eventual set-up. All the modules are designed so that you can add to them as your system grows – whether or not it's based on Project 80.

This applies to refinements, like filters ... to up-grading, adding a second set of amps, say, for greater output ... or to real innovation, like quad. (Add a Project 80 quad decoder, a power supply, a pair of amps, and a pair of speakers – and your stereo's gone quad.)

Is it difficult to build?

Not at all. The modules are complete in themselves. All you do is connect them to your turntable ... your speakers ... or to each other. It's absorbing, but if you can solder wires to a 5-pin DIN plug, you can build a complete system with Project 80.


And if you're not so hot with a soldering iron? Use Project 805. Project 805 uses Project 80 modules, but provides special clip-on tagged wire connections – absolutely *no* soldering required.

And, of course, both Project 80 and Project 805 come complete with instructions for easy, step-by-step assembly. But if you do run into problems, just call our Consumer Advisory Service who are always happy to help.

OK: Where do I go from here?

Over the page! There you'll see for yourself the exacting specifications to which Sinclair Project 80 modules are made, and you'll see some suggested systems.

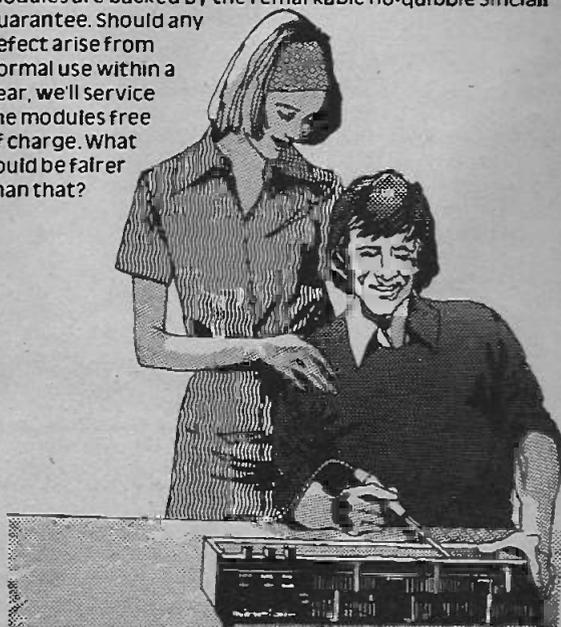As you skim the suggestions, remember all Project 80 modules are backed by the remarkable no-quibble Sinclair guarantee. Should any defect arise from normal use within a year, we'll service the modules free of charge. What could be fairer than that?



Choose the Project 80 modules that are right for you.



Project 80 pre-amp/control unit

The control centre of Project 80. With its distinctive white-on-matt-black styling and plastic control sliders, it's a pleasure to look at, as well as to use.

Specification

(9½ in x 2 in x ¾ in.) Separate slider controls on each channel for treble, bass and volume. Inputs: PU magnetic – 3 mV (RIAA corrected), ceramic – 350 mV;

Radio 100 mV; Tape 30 mV. S/N ratio: 60 dB. Frequency range: 20 Hz to 15 kHz ± 1 dB. Outputs: 100 mV and tape plus AB monitoring. Press buttons for PU, radio and tape. Operating voltage: 20 V – 35 V.

Price: £13.95 + VAT



Project 80 FM tuner

Excellent reception from a tuner only 3½ in long x ¾ in deep! Styled to match Project 80 control unit.

Specification

(3½ in x 2 in x ¾ in.) Tunes 87.5 MHz to 108 MHz. Detector: IC balanced

coincidence (IC equivalent to 26 transistors). Distortion: 0.3% at 1 kHz for 30% modulation. Sensitivity: 5 µV for 30 dB signal to noise. Output: 100 mV for 30% modulation. Aerial imp: 75 Ω or 240–300 Ω. Features: dual Varicap tuning, 4-pole ceramic filter, switchable AFC. Operating voltage: 23 V – 30 V.

Price: £13.95 + VAT



Project 80 stereo decoder

Designed for use with Project 80 FM tuner. Sold separately to

keep down the price of a mono FM system, but also to make the stereo decoder available for use with existing mono FM tuners.

Specification

(1¾ in x 2 in x ¾ in.) 1 IC equivalent to 19 transistors. LED stereo indicator glows red.

Price: £8.95 + VAT



Project 80 active filter unit

Eliminates scratch and rumble (high and low-frequency noise).

Specification

(4¼ in x 2 in x ¾ in.) Voltage gain: –0.2 dB. Frequency response: filter at zero: 36 Hz – 22 kHz; HF (scratch) out: variable 22 kHz to 5.5 kHz, 12 dB/octave slope; LF (rumble) out: –28 dB at 28 Hz, 9 dB/octave slope.

Price: £7.45 + VAT



Project 80 power amplifiers

Two different amplifiers, designed to be used separately or combined, with Project 80 modules or as add-ons to existing equipment. Protected against short circuits and damage from mis-use.

Z40 Specification

(2¼ in x 3 in x ¾ in.) 8 transistors. Input sensitivity: 100 mV. Output: 12 W RMS continuous into 8 Ω (35 V). Frequency response: 30 Hz – 100 kHz ± 3 dB. S/N ratio: 64 dB. Distortion: 0.1%


at 10 W into 8 Ω at 1 kHz. Voltage requirements: 12 V – 35 V. Load imp: 4 Ω – 15 Ω; safe on open circuit. Protected against short circuit.

Price: £5.95 + VAT

Z60 Specification

(2¼ in x 3¼ in x ¾ in.) 12 transistors. Input sensitivity: 100 mV – 250 mV. Output: 25 W RMS continuous into 8 Ω (50 V). Frequency response: 10 Hz to more than 200 kHz ± 3 dB. S/N ratio: better than 70 dB. Distortion: less than 0.1% at 12 W into 4 Ω at 1 kHz. Voltage requirements: 12 V – 50 V. Load imp: 4 Ω min; max safe on open circuit. Protected against short circuit.

Price: £7.45 + VAT

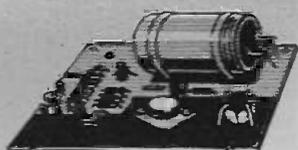

Power supply units

Range of power supply units to match desired specification of final system.

PZ5 Specification

Unstabilised. 30 V output. Including mains transformer:

Price: £5.95 + VAT

PZ6 Specification

Stabilised. 35 V output. Including mains transformer.

Price: £8.95 + VAT

PZ8 Specification

Stabilised. Output adjustable from 20 V to 60 V approx. Re-entrant current limiting makes damage from overload or even shorting virtually impossible. Without mains transformer.

Price: £8.45 + VAT



Project 80 SQ quadrasonic decoder

Combines with and exactly matches Project 80 control unit for true quadrasonics. This unit is based on the CBS SQ system and is a complete quadrasonic decoder, rear channel pre-amp and control unit.

Specification

(9½ in x 2 in x ¾ in.) Connects with tape socket on Project 80

control unit or similar facility on any stereo amplifier. Separate slider controls on each channel for treble, bass and volume.

Frequency response: 15 Hz to 25 kHz ± 3 dB. Distortion: 0.1%. S/N ratio: 58 dB. Rated output: 100 mV. Phase shift network: 90 ± 10° 100 Hz to 10 kHz. Operating voltage: 22 V – 35 V.

Price: £18.95 + VAT

Some system suggestions from Sinclair



Project 805 amplifier kit

Contains following Project 80 units:

Project 80 control unit
2 x Z40 power amplifier modules
1 x PZ5 power supply unit
Masterlink unit
On/off switch
plus pre-cut wiring loom with clip-on tagged wire connections, nuts and bolts, instruction manual.

Price: £39.95 + VAT




Project 8050 quadraphonic add-on kit

Converts your existing stereo hi-fi system to quad using solderless connections.

Contains following Project 80 units:

Project 80 50 quad decoder/rear channel pre-amp and control unit
2 x Z40 power amps
PZ5 power supply unit
Masterlink unit
On/off switch
plus pre-cut wiring loom with clip-on tagged wire connections, nuts and bolts, instruction manual.

Price: £44.95 + VAT

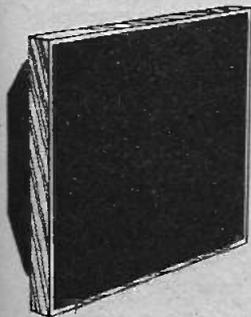

Sinclair Q16 speaker

Original and uniquely designed speaker of outstanding quality.

Specification

(10 1/8" in square x 4 1/4" in deep.)
Pedestal base. All-over black front. Teak surround. Balanced sealed sound chamber. Special driver assembly. Frequency response: 60 Hz to 16 kHz.

Power handling: up to 14 W RMS.
Impedance: 8 Ω.

Price: £8.95 + VAT

1. Quadraphonic system: 25 W per channel RMS
Pre-amp/control unit + quadraphonic decoder + 4 x Z60 amps + 2 x PZ8 mains power supplies + (2 x mains transformers) + (4 x equivalent speakers) + (turntable).
Total Project 80 cost: £79.60 + VAT.

2. Stereo amplifier: 12 W per channel RMS
Pre-amp/control unit + 2 x Z40 amps + PZ6 power supply + 2 x Q16 speakers. Total Project 80 cost: £52.70 + VAT.

3. Stereo tuner/amplifier: 12 W per channel RMS
Pre-amp/control unit + FM tuner + stereo decoder + 2 x Z40 amps + PZ6 power supply + 2 x Q16 speakers. Total Project 80 cost: £75.60 + VAT.

Other applications

4. PA system
(Mic) + pre-amp/control unit + Z40 amp + PZ6 power supply + 2 x Q16 speakers. Total Project 80 cost: £46.75 + VAT.

5. Convert existing mono record-player to stereo
Pre-amp/control unit + Z40 amp + Q16 speaker. Total Project 80 cost: £28.25 + VAT.

What more can we tell you?

The basic facts are covered on these two pages. And you'll find Project 80 at stores like Laskys and Henry's.

But before you look, why not get really detailed information? Clip the FREEPOST coupon for the fully-illustrated Project 80 folder - today!

Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.
Telephone: St Ives (0480) 64646.

sinclair

Sinclair Project 80
a new concept in
expandable hi-fi

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me, by return post, a copy of the fully-illustrated Project 80 folder.

Name _____

Address _____

Please print FREEPOST - no stamp needed.

EE/5/75

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

TRANSISTOR PACKS ALL AT 50p EACH TESTED & GUARANTEED

B79	4	IN4007 Sil. Rec. diodes. 1,000PIV 1 amp. plastic	H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC945 BD131/BD132
B81	10	Reed Switches, 1 long 2" dia. High-speed P.O. type	H41	2	Complementary Plastic Transistors
H35	100	Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked.	H65	4	40381 Type NPN Sil. Transistors TO-5 can comp. to H66
H38	30	Short lead, NPN Silicon Planar Ex Equipment.	H66	4	40382 Type PNP Sil. Transistors TO-5 can comp. to H65

UNMARKED & UNTESTED

B1	50	Germanium Transistors PNP, AF and RF	H6	40	25mW zener diodes. At least 20 good.
B46	150	Germanium Diodes Min. glass type	H15	30	Silicon rectifiers 750mA assorted. Top-hat type.
H68	10	Experimenter's pack of I.C.s, D.T.L. and TTL (some marked)	H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
B36	100	Sil. Diodes sub. min. IN914 and IN916 types	H67	10	3819N Channel FET's plastic case type

PLASTIC POWER TRANSISTORS

40 WATT SILICON

Type	Polarity	Gain	VCE	Price
40N1	NPN	15	15	26p
40N2	NPN	40	40	30p
40P1	PNP	15	15	26p
40P2	PNP	40	40	30p

50 WATT SILICON

Type	Polarity	Gain	VCE	Price
50N1	NPN	15	15	25p
50N2	NPN	40	40	35p
50P1	PNP	15	15	25p
50P2	PNP	40	40	35p

NEW X-HATCH GENERATOR Mk. 2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U.2 type batteries (extra).

P/P add 30p Complete kit **£7.93** Ready built unit only **£9.93**

TO CLEAR

Hundreds of various portable transistor radio chassis with FM & AM tuning. Ideal for experimenters. All in going order, but no instructions or tuning drives. A cheap way to make a portable. Each £1.

SUNDRY

Capacitor Discharge Ignition Kit £7.70. 8 assorted relays £1.00. Rev counter device (for cars) £1.90. U.H.F./TV Tuner Units £25 £2.90. L.M.390 Audio I.C. £1.00 and technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do NOT include V.A.T. Please add V.A.T. at current rate, to total value of your order including postage. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 20p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.



challenging values!



Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.

AMPLIFIER MODULES



Pre-amplifiers; tone control

SS.100	Active tone control unit to provide bass, treble, balance and volume controls	£1.60
SS.101	Pre-amp for ceramic cartridge, tape and radio	£1.60
SS.102	Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction ±1dB at 1K	£2.25

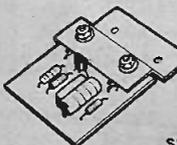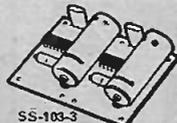



POWER AMPLIFIERS

SS.103	Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6 to 22. Size 2" x 2"	£1.75
SS.103-3	Stereo version of above using one I.C. on each channel	£3.25
SS.105	A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2 1/2" x 1 1/2"	£1.95
SS.110	Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26 to 32V.	£2.40
SS.140	Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0.15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms	£3.60

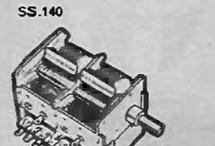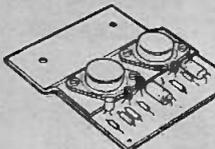

BUILD A STEREO FM TUNER!

SS.201	Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V	£6.25
SS.202	I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4.5 to 14V	£5.25
SS.203	Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c.	£5.62

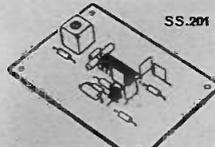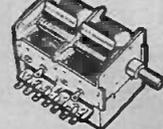


POWER SUPPLY STABILIZER

SS.300	Add this to an unregulated supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential on your audio and special systems. Money saving and very reliable	£3.25
--------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------

ALL MODULES TESTED AND GUARANTEED WITH INSTRUCTIONS

MAINS TRANSFORMERS FOR ABOVE

Add 35p per transformer for P/P	
Type A 18V/1A (Suit SS.103)	£1.50
Type B 25V/2A (Suit SS.110)	£2.00
Type C 30V/2A (Suit SS.140)	£3.25
Bridge Rectifiers—Type A 27p. Types B & C 38p	

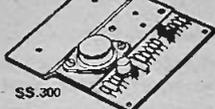

BI-PRE-PAK LTD

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.
TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send
for which I enclose Inc. V.A.T.
Name
Address

EE6

SPARKRITE MK 2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

"Sparkrite MK 2" is a high performance, high quality, capacitive discharge, electronic ignition system. Sparkrite completely eliminates problems of the contact breaker. Misfire due to contact breaker bounce is electronically eliminated, contact breaker burn is eliminated, the condition of the contacts is not relevant to the performance of the ignition, and the system is no longer dependant on the dwell period for recharging.

Sparkrite will give you: Up to 20% better fuel consumption, instant all weather starting, cleaner plugs, faster acceleration, higher top speed, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

The Kit comprises everything needed. Already drilled and guaranteed components and parts.

Prices: D.I.Y. assembly kit £10.93*. Ready built unit £13.86*. (Both to fit all vehicles with coil/distributor ignition up to 8 cylinders.) Switch for instant changeover from "Sparkrite" ignition to conventional ignition £2.79*. R.P.M. limiting control £2.42*. Details of more specialised units on request. CALL IN AND SEE US FOR A DEMONSTRATION.



ORDER NOW

TO Electronics Design Associates
Dept E.E. 5
82 Bath Street, Walsall, WS1 3DE.
Phone 33652.

FROM Name
Address

QTY Please Supply
SPARKRITE MK 2 DIY Assembly kits @ £10.93
SPARKRITE MK 2 Ready Built Negative earth @ £13.86
SPARKRITE MK 2 Ready Built Positive earth @ £13.86
Ignition changeover switches @ £2.79
R.P.M. Limit systems in the above units @ £2.42
Fluorescent light assembly kits @ £3.19
Fluorescent light built units @ £3.78
Diffusers for the above @ 59p of number alum. boxes @ of number alum. boxes @

I enclose cheque/P.O.s for £.....

Cheque No.
(Send SAE if brochure only required)

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

Prices include lids, screws and V.A.T. (@8%). Add 18p to the total order value for postage and packing.

No. 7	5 1/2"	2 1/2"	1 1/2"	high	47p
No. 8	4"	4"	1 1/2"	high	48p
No. 9	4"	2 1/2"	1 1/2"	high	46p
No. 10	5 1/2"	4"	1 1/2"	high	49p
No. 11	4"	2 1/2"	2"	high	46p
No. 12	3"	2 1/2"	1 1/2"	high	38p
No. 13	5"	4"	2"	high	58p
No. 14	7"	5 1/2"	2 1/2"	high	75p
No. 15	8"	6"	2 1/2"	high	95p
No. 16	10"	7"	3"	high	£1.14

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12v, 8w, fluorescent light. Everything needed is supplied: white enamelled ready drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, end caps, cable, the fluorescent tube, nuts bolts washers, and simple assembly and operating instructions. Prices: Assembly kit £3.46*. Ready built £4.10*. Diffuser 59p. *inc. V.A.T. p. and p.

CJL PRICES INCLUDE P&P AND V.A.T.

- AERIAL, telescopic, 15-120cm. £1.20
- AERIAL, telescopic, h and v swivel, 15-80cm. . . £1.78
- BIB HI-FI ACCESSORIES**
- CASSETTE TAPE RECORDER CARE KIT £1.95
- CASSETTE SPLICING AND EDITING KIT £1.50
- HI-FI STEREO TEST CASSETTE £2.10
- 1" TAPE EDITING KIT £1.35
- GROOV-KLEEN RECORD CLEANER £1.85
- EARPHONE, stethoscope style, 8 ohm dynamic . . £1.00
- HAND DRILL (Laytool), compact precision drill, 5/16" chuck. Gears totally enclosed. S/L bearings. . £2.99
- INTEGRATED CIRCUITS**
- AUDIO POWER AMPLIFIER (National) LM380 £1.00
- A.M. RADIO RECEIVER (RCA) CA3123E £1.40
- F.M. STEREO DECODER (Motorola) MC1310P £2.80
- TIMER (Signetics) NE555V £0.78
- VOLTAGE REGULATOR (Fairchild) UA7805 £1.70
- VOLTAGE REGULATOR (Signetics) NE550A £0.80
- D.I.L. SOCKETS (Pk of 3) 8 or 14 pin £0.50
- KEYNECTOR, rapid connect-to-mains-single/multiple leads. Built-in piano switches neon & 13A fuse . . £3.20
- LOCKFLEX RULE (Rabone Chasterton), 3m/10ft precision pocket rule. Easy to read, 13mm/1/2" wide steel tape. Blade length lockable-power return. A superb rule £0.93
- MICROPHONE, lightweight dynamic, remote start stop, 200 ohms, 100-10kHz, 6mV average output . . £1.80
- MULTIMETER, attractive design, Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA. R-150k . . £4.95
- SIGNAL INJECTOR, audio through video signals, excellent for servicing amplifiers, radio & tv . . £3.92
- SOLDERING IRON, 25 WATT (Antex), X25, 240V. Very low leakage, 1/8" long life bit (interchangeable) £2.05
- 3/32" bit £0.47 3/16" bit £0.47 Element £1.10
- STAND, ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits . . £1.00
- SPEAKER, miniature, 75mm dia, 8 ohms. £0.80



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept EEB 55 P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

BLOCK CAPS please

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

Everyday Electronics Classified Advertisements

RATES: 11p per word (minimum 12 words). Box No. 30p, extra. Semi-display—£7.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

The advertiser warrants that the advertisement does not contravene any of the provisions of the Trade Descriptions Act 1968. The Publishers reserve the right to refuse or withdraw any advertisement. Although every care is taken to avoid mistakes, the publishers cannot be liable for clerical or printer's errors or their consequences.

SITUATIONS VACANT

College of Further Education, Plymouth.

Electronics and Radio Communications

Full-time courses are offered by the Department of Electrical Engineering, for those seeking a career as

Marine Radio and Radar, Officers Radio, Television and Electronics Technicians
Radio, Television and Electronics Mechanics

Courses are also offered for those seeking Revalidation or Conversion of Radio Officer Certificates.

Further details from:

The Registrar, College of Further Education, Kings Road, Devonport, Plymouth, PL1 5QG.

EDUCATIONAL

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

INTERNATIONAL CORRESPONDENCE SCHOOLS, Dept 731, Intertext House, London SW8 4UJ. Or Phone 01-422 8911 (all hours)

FOR SALE

E.E. from first copy to date, good condition. Offers: Peter Mckay, Grimsby 58816.

MICROPHONES: AKG D109, £12-65; AKG D202E1 £43-45; AKG D190C, £18-70; AKG D190E, £20; AKG D224, £55; Sennheiser MD211N, £49-50; Sennheiser MD413N, £29-70. All brand new and boxed. Send CWO to J. J. Francis (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets, Manuals, Books on Radio's TVs etc. Service Sheets 40p plus SAE. Free book lists on request. Back issues of PW, PE, EE, TV available, cover price plus 9p post. SAE with enquiries. B.T.S. (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

RECEIVERS and COMPONENTS

COMPONENTS GALORE. Pack of 600 mixed components manufacturers surplus plus once used. Pack includes Resistors, carbon and W.W. capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p and p.c.v.o. to CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

3 ASSORTED M.C. METERS £1.30 (40p). LARGE COMPUTER PANELS 35-50 Transistors, Long Leads, 85p (40p). COPPER CLAD PAX PANELS 6 1/2" x 5 1/2", 6-85p c.p. FIBRE GLASS 8 1/2" x 7 1/2" each 60p c.p. T.V. CONVERGENCE PANELS 2x AC128, 3 Slugged Coils, 3 Slide Switches 11 w.w. Pots, 3 Carbon Presets, 2 Ferrite Chokes, etc. £1-20 c.p. VALU-PAKS P9, 100 5/16c Caps 67p c.p. P24, 100 Polyester Caps. Mullard C280 series, £1-12, c.p. Send 12p for lists. Refund on purchase. 71bs ASSORTED COMPONENTS £2, c.p.

J. W. B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL. Postage in Brackets. Mail Order Only

MISCELLANEOUS

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warks.

AERIAL BOOSTERS—£1.30

We make three types of aerial boosters B45-UHF-TV, B12-VHF-TV, B11-VHF-Radio.

VALVES BARGAINS

ANY 5-50p, 10-75p, 50-£3.30, ECC82, EF80, EF183, EF184, PCC189, PCF80, PCF80Z, PCL82, PCL84, PCL85/80S, PFL200, PL36, PL504, PY800, PY85.

COLOUR TV VALVES—PL508, PL509, PY500-25p each.

Prices includes VAT, P&P 10p, SAE—leaflet Electronic Mail Order Ltd, 62 Bridge Street, Rambsottom, Bury, Lancs. Tel RAMS 3036.

SUPERB instrument cases by Bazelli, manufactured from heavy duty P.V.C. faced steel. Hundreds of Radio, Electronic and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Largest choice at highly competitive prices, why pay more, prompt dispatch. Free literature (stamp would be appreciated). Bazelli, Department No. 24, St. Wilfrids, Foundry Lane, Halton, Lancaster, LA2 6LT.

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram, £3-66 plus VAT. "Jumbo" LED digits (16mm high), type DL-747, only £2-04 each plus VAT, post free. Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside L62 5AG.

GADGETS GALORE!!

★ READY BUILT + TESTED ★

Signal Injector £1-95 Signal Tracer £2-85
Logic Probe £4-45 Noise Generator £2-85
Metronome £3-50 Continuity Tester £3-95
Automatic Transistor Checker £15-25

Prices include U.K. Postage and Batteries—Mail Order Only—S.A.E. 11at to.

G.K. SERVICES, (G2)

83 Westdale Road, London SE16 3BQ

VALVES TRANSISTORS Valves 1930 to 1975 2,000 types in stock many types. Also transistors. Cox Radio We buy new and boxed valves all types. Also transistors. Cox Radio (Sussex) Ltd, The Parade, East Wittering, Sussex. West Wittering 2025.

LOUD 6 VOLT SIRENS

for BURGALAR ALARMS, etc. £1.20p + 15p pp. TELEPHONE PICKUP COILS 55p, MIKES 40p. 4V-12V MINIATURE BUZZERS 50p. 3" TAPE & SPOOL IDEAL MESSAGE TAPES 25p. LARGE RED L.E.D.S. 25p. FIBRE OPTICS 8p yd. WHITE ROCKER SWITCH, 250v A.C. 15A, 42p. ADD 10p post UNLESS STATED, LIST 8p. GRIMSBY ELECTRONICS 54 TENNYSON ROAD CLEETHORPE, SOUTH HUMBERSIDE (Callers to Lambert Road, Saturdays only)

LOWEST COST IC SOCKETS. Use Soldercon IC socket pins for 8 to 40 pin DIL's. 50p for strip of 100 pins, £1-50 for 3 strips of 100, £4 for 1000. 10p p&p for orders under £2. Add 8% VAT. Instructions supplied—send s&e for sample. SINTEL, 55e Aston Street, Oxford. Tel: 0865 43203.

MULTIMETER

Type U4324

20,000 Ω/V, Overload protected, Ranges: 0.1, 1.2, 3, 12, 30, 60, 120, 600, 1200V DC; 3, 6, 15, 60, 150, 300, 600, 900V AC; 0.06, 0.6, 6, 60, 600mA, 3A DC; 0.3, 3, 30, 300mA, 3A AC; 5 resistance ranges to 5M Ω, dBs, -10 to +12, Size 167 x 98 x 83mm. Supplied complete with test leads, clips spare diode and instructions.

ONLY £10.20.

PC ETCHING KIT

Contains 1lb Ferric chloride, DALO etch-resist pen, 100 sq ins copper clad board, etching dish, abrasive cleaner and instructions. £3-30

FERRIC CHLORIDE

Anhydrous to Mill-spec in double-sealed 1lb packs. 1lb 80p; 3lb £1-80; 10lb £4-78.

VEROBOARD

100 sq ins 0.1, 0.15 & 0.2" good, 41/2 size offcuts (About 8 pieces) £1-18.

TRANSFORMERS

Miniature type, mains primary, 100mA sec. 0-0.5V 80p; 0-0.9V 90p; 12-0.12V 95p.

COMPUTER PANELS

3lbs each £1-55; 7lb £2-80; 50lb £18; 12 high quality panels with trim pots, power transistors, IC's etc. £2.30. Pack of boards with 800 components inc. at least 50 transistors £1.


GREENWELD ELECTRONICS [EE5]

51 SHIRLEY PARK ROAD, SOUTHAMPTON SO1 4FX

Tel (0703) 772501. Also at 38 Lower Adlecombe Rd, Croydon & 21 Deptford Bdy SE8.

ALL PRICES INCLUDE P&P AND UK POSTAGE. SAE LIST, ENQUIRIES, CALLERS WELCOME.

LOUDSPEAKERS

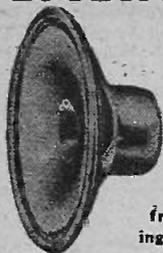

Speakers, kits and cabinets for D.I.Y., Hi Fi, P.A., Disco, etc. by EMI, Fane, Goodmans, Baker, Kaf, Elac, Richard Allan, Wharfedale, etc. Send stamp for free booklet "Choosing a speaker"

WILMSLOW AUDIO

Dept. EE, Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF
Tel. Wilmslow 29599

ELECTRONIC KIT

Electronic fun for all ages

The most versatile electronics kits. All components are beautifully encapsulated in unbreakable transparent plastic blocks. Perfect connections are made WITHOUT SOLDERING, SCREWING OR WIRING. INCREDIBLE VALUE. Build, dismantle and rebuild projects any number of times and invent your own experiments too. COMPLETELY SAFE. Instructive and FUN—all kits operate from 9v. battery only.

VALUABLE MANUALS included with every kit. No previous knowledge is required, even with the largest kits.

KIT 2A—30 projects £10-45. Radios, amplifiers, alarms, microphones, Morse, etc.
KIT 3A—100 projects £20-45. As 2A plus electronic birds, cats, sirens, organs, metronome, guns, light and sound, burglar alarms, etc.

3ADX—105 projects £25-25. As 3A plus solar cell experiments and complete sophisticated control panel, etc.

4ADX—150 projects £33-95. As 3ADX plus Relay and Meter experiments; ion concentration, volume, out-put, field intensity, volt, resistance meters, ammeter, illuminometer, etc. and many, many more.


ADD-ON parts and manuals available as required.

The three larger kits include Electrical experiments too.

All prices include Battery, Manual, VAT & p. & p.
Cheque/P.O. (or 6p for literature) to:

Satisfaction guaranteed
ELECTRONIC-KIT LTD, 408 St. John's Street, London, EC1. (01-278 4579)

verobox[®]

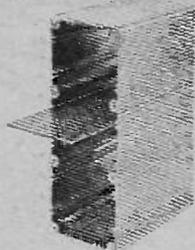

ALUMINIUM ENCLOSURES

- 6 standard sizes available from your local retailer.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.

Eastleigh, Hants SO5 3ZR
Tel: Chandler's Ford 2952 Telex: 47551

Subsidiaries and Agents throughout the World

BUILD THE **TREASURE TRACER MK III** Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete Kit £9.80 P & P 60p
Built, tested and guaranteed £13.75 P & P 60p, + £1.10 VAT

MINIKITS ELECTRONICS,
65 CLEVELAND ROAD,
LONDON. E18 2AN (Mail order only)

BINDERS FOR E.E.

Why not keep your copies of Everyday Electronics neatly on the bookshelf?

You can with an E.E. Binder. Finished in orange with title and volume on the spine these hardback binders protect your issues and, with a yearly index, provide a means of quick easy reference.

BINDERS FOR VOLUMES 1 to 4 (state which), £1.25 each.

INDEXES FOR VOLUMES 1 and 2 (state which) 30p each.

(Index for Volume 3 will be included in next months' issue)

Both prices include postage.

Send cheque or P.O. to Binding Department, Everyday Electronics, Carlton House, Great Queen Street, London, WC2E 9PR

everyday electronics

4 1/4 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £3-85. P. & P. 11p.

TAPE RECORDER LEVEL METER 500µA, 70p P. & P. 5p.

CARDIOID DYNAMIC MICROPHONE Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £6-55. P. & P. 11p.

42 x 42mm METERS 100µA, 500µA, 1mA, 500mA £2-76, 11p P. & P.

60 x 45mm METERS 50µA, 100µA, 500µA and 1mA VU METER £2-92, 11p P. & P.

EDGEWISE METERS, 90mm x 34mm, 1mA £3-40, 11p P. & P.

MULTI-METER Model MTI-2 20,000 ohm/volt, £6-90. P. & P. 15p.

3 WATT STEREO AMPLIFIER 1 1/2 W PER CHANNEL £4-30. P. & P. 10p.

All above prices include 8% V.A.T. LARGE S.A.E. for List No. 11. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

ELECTROVALUE

Present

**STABILIZED PRICE POLICY
QUALITY COMPONENTS, KEEN
PRICES AND DEPENDABLE SERVICE**

112 page catalogue · attractive discounts · free postage & packing (U.K.)

**A 100 OF THE BEST
out of our latest catalogue**

2N1307	47p	AF200U	40p	BD135	37p
2N2646	81p	AF239	80p	BD138	39p
2N3053	30p	B1906	36p	BDY20	83p
2N3054	69p	BA138	31p	BF184	15p
2N3055	70p	BB103	24p	BFR30	23p
2N3702	11p	BB104	48p	BFR78	23p
2N3703	10p	BB105	34p	BFX29	33p
2N3704	11p	BB107A	18p	BFX84	27p
2N3705	10p	BC107B	18p	BFY61	23p
2N3794	18p	BC108B	15p	BRV39	56p
2N3919	28p	BC108C	15p	BY164	51p
2N4062	11p	BC109B	15p	C10651	42p
2N4443	83p	BC109C	18p	C108D1	47p
2N5052	42p	BC147A	12p	C1405	78p
2N5163	20p	BC147B	18p	MJ481	£1-20
2N5459	35p	BC148B	12p	MJ491	£1-35
40381	48p	BC149C	14p	MJ2955	80p
40382	44p	BC158B	15p	MJ3371	89p
40602	46p	BC159A	15p	MJ5221	81p
40836	£1-36	BC167B	13p	MJE2955	£1-12
40859	£1-10	BC168B	12p	MJE3055	68p
AC128	17p	BC169B	12p	OA91	8p
AC151R	36p	BC159C	18p	SD4	8p
AC183	27p	BC179B	28p	TIP31A	70p
AC158K	37p	BC182L	12p	TIP32A	80p
AC176	24p	BC184L	10p	TIP41A	80p
AC178K	38p	BC212L	12p	TIP42A	£1-00
AC187K	31p	BC214L	14p	W02	30p
AC188K	39p	BC257A	14p	ZTX300	14p
AD133	£1-92	BC259B	14p	ZTX304	23p
AD136	£1-14	BCY58	30p	ZTX304	23p
AD149	52p	BD130	70p	ZTX500	14p
AD181	42p	BD131	48p	ZTX504	45p
AD182	40p	BD132	52p		

ELECTROLYTIC CAPACITORS

Axial Lead	3V	5-3V	10V	16V	25V	40V	63V	100V
0-47	—	—	—	—	—	11p	8p	8p
1-0	—	—	—	—	—	11p	8p	8p
2-2	—	—	—	—	—	11p	8p	8p
4-7	—	—	—	11p	—	8p	8p	8p
10	—	11	—	—	8p	8p	8p	8p
22	—	—	8p	—	8p	8p	8p	10p
47	8p	—	8p	8p	8p	8p	10p	13p
100	8p	8p	8p	8p	10p	10p	12p	19p
220	8p	8p	8p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	—	—	26p	37p	41p	—	—
4,700	—	—	38p	44p	58p	—	—	—
10,000	42p	48p	—	—	—	—	—	—

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99 100 up
(see note below)				
C	1/3	4-7-47K	1-3	1-1 0-9 nett
C	1/2	4-7-10M	1-3	1-1 0-9 nett
C	3/4	4-7-10M	1-3	1-2 0-97 nett
C	1	4-7-40M	3-2	2-5 1-82 nett
MO	1/2	10-1M	4	3-3 2-3 nett
WW	1	0-22-0-47 Ω	10	14 11 nett
WW	1	0-56-3-9 Ω	12	10 8 nett
WW	3	1-0K	9	8 6 nett
WW	7	1-10K	11	10 8 nett

Codes:
C=carbon film, high stability, low noise.
MO=metal oxide, Electroil TR5 ultra low noise.
WW=wire wound, Pleassey.
Values: All E12 except C 1/3, C 3/4 and MO 1/2.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 82, 88, 82, and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 52, 75, 91 and their decades.
Tolerances:
5% except WW 10% ±0-05Ω below 10Ω and 1/3W MO 2%
Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

**all in the E.V.
CATALOGUE 7
(issue 3)**

112 pages of up-dated information and prices. More valuable than ever now that our price stabilizing has been introduced. Includes a 25p refund voucher for spending on orders for £5 or more list value. So before you even look at a screwdriver, make sure you have your E.V. Catalogue No. 7 issue 3 to hand. Price, post paid **30p**

PRICE STABILIZATION

Instead of changing prices from day to day with all the difficulties that brings, EV prices are now held for 3 monthly periods (as from April 1st) and then reviewed to see if changes are necessary for the next 3 months following.

DISCOUNTS

apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

FREE POSTAGE & PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under, there is an additional handling charge of 10p.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to makers specifications. No rejects, seconds or sub-standard merchandise.

V.A.T. @ 8% must be added to total value of orders. Every effort is made to ensure correctness of information at time of preparing and putting this advertisement to press.

WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 6 way; 3 pole 4 way; 4 pole 3 way each 33p
TAG STRIP 28 way 11p

NUTS, SCREWS, etc.

In lots of 100 each
4BA NUTS 34p; 8BA NUTS 28p
1" 4BA Screws 36p; 1" 6BA Screws 24p
Threaded pillars 6BA, 1" hexagonal £1-40
Plain spacers 1" round £1-32
Other sizes available

CAPACITORS

DALY ELECTROLYTIC In cans, plastic sleeved
1000mF/25V 34p 2200/100 £3-91
5000/100 £3-56 1000/50 50p
5000/25V 75p 2000/50 70p
1000/100 £4-00 5000/50 £1-44

POLYESTER TYPE C.250. Radial leads for P.C.B. mounting. Working voltage 250V d.c.
0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p
0-068, 0-1, 0-15 ea. 4p
0-22 5p; 0-33 7p; 0-47 8p; 0-63 11p; 1-0 14p; 1-5 21p; 2-2 24p

SILVERED MICA. Working voltage 500V d.c. Tolerance 1% or 0-6pF
Values in PFs—2-2 to 250 in 28, stages ea. 6p
270-820 in 9 stages, ea. 7p
1000, 1500, 1800 9p; 2200 18p; 2703, 3600, 4700, 5000 16p; 6800, 8200, 10,000 25p

TANTALUM BEAD
0-1, 0-22, 0-47, 1-0 mF/35V, 1-5/20V, 3-5/16V ea. 16p
2-2/18V, 2-2/35V, 4-7/16V, 10/8-3V ea. 16p
4-7/35V, 10/16V, 22/8-3V ea. 21p
10/25V, 22/16V, 47/6-3V, 100/3V, 6-8/25V, 15/25V ea. 23p

POLYCARBONATE
Type B42540 Working Voltage—250V Values in mF:
0-0047; 0-0068; 0-01; 0-015; 0-022 ea. 4p
0-018; 0-027; 0-033; 0-038; 0-047; 0-068; 0-082; 0-1; 100v ea. 5p
0-18; 0-22 7p; 0-27 8p; 0-33 9p; 0-39, 0-47 11p; 0-56, 0-68 16p

CERAMIC PLATE
Working voltage 50V. d.c.
In 28 values from 22p1 to 6800pF, ea. 2p

POTENTIOMETERS

ROTARY CARBON TRACK.
Double wipers for good contact and long working life
P.20 SINGLE linear 100 ohms to 4-7 meg ohms, each 14p
P.20 SINGLE log. 4-7 Kohms to 2-2 megohms, each 14p
J.P.20 DUAL GANG lin. 4-7 Kohms to 2-2 megohms, each 48p
J.P.20 DUAL GANG log. 4-7 Kohms to 2-2 megohms, each 48p
J.P.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only, each 48p
J.P.20 DUAL GANG antilog 10K only 48p
2A DP mains switch for any of above 14p extra.
Decades of 10, 22 and 47 only available in ranges above.
Skeletal Carbon Presets, Type PR, horizontal or vertical 8p each.

SLIDER
Linear or log mono 4-7K to 1 meg. in all popular values each 30p
STEREO, matched tracks, lin. or log in all popular values from 4-7K to 1 meg. 65p
Escutcheon plates, mono, black or grey, each 10p
Control knobs, blk/wht/red/yel/gm/blue/dk.grey/lt.grey, each 7p

MINITRON DIGITAL INDICATORS
3615F Seven segment filament compatible with standard logic modules. 0-9 and decimal point: 9mm characters in 16 lead DIL
Suitable BCD decoder driver 7447 £1-15
3615G showing + or - & 1 & dec. pt. £1-20

LED'S (Light Emitting Diodes) 25p
Photo Cells, cadmium sulphide each 48p
ANTEX Soldering Irons
C240 £2-25 Spare bits 32p
CCN240 £2-65 Spare bits 42p

ELECTROVALUE LTD


28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.
NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-5.30 daily: Sat. 9-1 p.m.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

All postal communications, mail orders etc. to Head Office at Egham address, Section 4/5 S.A.E. with enquiries requiring answers.

Henry's

LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT.
LOW PRICES - MEAN LESS VAT.

VAT 8% EXTRA
ON ALL ITEMS

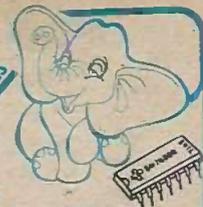

You can build the Texan and Stereo FM Tuner

TEXAN 20 - 20 WATT IC STEREO AMPLIFIER

Features glass fibre PC board, Gardners low field transformer. 5-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and, P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised Supply. Overall size 15 1/2" x 2 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit.



£31.00 (carriage 50p)

(also built and tested £37.50)



STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter. Indicators stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 2 1/2" x 6 1/2". Complete kit with teak sleeve

£21.00 (carriage 50p)

(also built and tested £24.95)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

TRANSISTORISED MODULES

Tuners - Power Supplies - Amplifiers

AMPLIFIERS (All single channel unless stated)

	£ p
4-300	1-75
2004	2-70
104	3-10
304	3-95
555	4-10
555ST	5-95
E1208	5-10
508	4-95
410	4-95
620	9-95
Z40	5-45
Z60	6-95
S A6817	10-20

	£ p
E1210	8-25
R500	6-30
SAC14	11-75
SAC30	14-95
CA038	6-95
CA088	10-50

	£ p
AM/FM Modules	
Mullard LP 1186 FM tuner (front end with data 10.7 MHz O/P)	4-85
LP1157 Am/Module	2-50
LP1171 Am/FM Module	4-50
LP1179 Am/FM Front End	4-85
Mullard LP 1185 10.7 MHz IF unit with data	4-50

	£ p
FM and AM Tuners and Decoders	
FM5231 (tu 2) 6 volt FM tuner	7-95
TU312 volt version (FM use with Decoder)	7-95
SD4912 Stereo Decoder for TU 3-12 volt	4-80
SP82H 6 volt stereo FM tuner	4-80
A1007 9 volt MW-AM	11-95
Sinclair 12/45 volt FM tuner stereo recorder for above	7-45
A1018 9 volt FM tuner in cabinet	13-95
A1005M (S) 9-12 volt Stereo decoder FM for above	7-50
106Z 12 volt Stereo decoder general purpose	6-50

	£ p
Preamplifiers	
Sinclair Stereo 60 Preamplifier	6-75
E1300	2-85
E1310	2-85
FF3	4-95
3042	5-95
EQ25	5-95

	£ p
Power Supplies Mains Input (chassis-rest cased)	
470C 6.7A/9V 300 MA with ad/rs	2-25
P500 9 volt 500 MA	3-20
HC244R 3.6/7A/9V. 400 MA stabilised	5-50
*P11 24v. 1 amp. 3-30	3-30
*P15 28V. 1 amp	3-30
*P1080 12V 1A 4-70	7-80
*P1081 45V 0.3A	7-80
P12 4-12V. 0.4-1 amp	7-15
SE101A 3.6/9/12V. 1 amp stabilised	12-75
PI076 3.4/4.6/7.9/12V. 1 amp	4-20
SE800A -1.5 VOLT 0.1A stabilised	17-50

EMI SPEAKERS SPECIAL

PURCHASE



13 in. x 8 in. chassis speakers (Carr./packing 30p each or 50p pr.)

*150 TC 10 watts £2-20
8 ohms twin cone

*450 15 watts 4, 8, 15 ohm with twin tweeters and crossover £3-85 each

EW 15 watt 8 ohms with tweeter £5-25
350 20 watt 8, 15 ohm with tweeter £7-80 each

*Polished wood cabinet £4-80 carr. etc. 35p each or 50p pair

UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation. Brand new. (Post/packing 25p. each).

TYPE C variable tuning £2-50

TYPE B 4-button push-button (adjustable) £3-50

PA-DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc.

FREE stock lists (Ref. No. 18) on request. CALL AT HENRY'S DISCO CENTRE, 309 EDGWARE ROAD. TEL. 01-723 6963

NOW OPEN SUPERMARKET

Come and browse round the new components supermarket at 404, Edgware Road, Bargins Galore. Goodie Bags. Components Etc.

EP27 Low Cost Seven Segment Led. Digit Height 1/3 inch £1.35 pp 15p.

L450 RECHARGEABLE BATTERY

2v 400mA/HR 50p p.p. 15p.

PHILIPS 12V FLUORESCENT INVERTOR

for 8w fluorescent tube. Supplied with instr. and tube £3.50 p.p. 30p

10.7 MHZ MINIATURE CERAMIC IF FILTER

40p per pair p p 15p

TEST EQUIPMENT

MULTIMETERS

Carr./packing	£ p
35p	
J4324 20kΩ/V	1-75
J45 20kΩ/V with steel case 8-75	
J4312 20kΩ/V with steel case 12-50	
J4317 20kΩ/V with case 16-50	
J4341 33kΩ/V plus trans. steel case 10-50	
U4323 20kΩ/V plus 1kHz OSC with case 7-70	
ITL-2 20kΩ/V slim type 5-95	
THL32D (L33DX) 2kΩ/V Robust 7-50	
TP55N 20kΩ/V (Case £2) 8-25	
TP10S 2kΩ/V 6-25	
TW20S 20kΩ/V 10-00	
TW50K 50kΩ/V 11-25	
EP10KN 10kΩ/V 9-95	
AF10S 50kΩ/V Deluxe 12-50	
S100TR 100kΩ/V plus transistor tester 22-50	



NEW REVOLUTIONARY SUPERTESTER 680R

£ p
680R Multi-tester 18-50
*TK40 ACMultivoltmeter 19-75
*TM15 Grid dip meter 19-50
*TH85 Range valve voltmeter 22-50
*TK20D RF Generator 120kHz-500MHz 18-95
*TK22D AF Generator 20Hz-200kHz 19-95
*H4320 in circuit transistor tester 19-50
*C302S Deluxe meter 1-300MHz 6-95
*TT145 Compact transistor tester 14-75
*C3-36 P/C osc. 20Hz-200kHz 19-75
*C304Z SWR meter 5-75
*SE350A De-luxe signal tracer 12-95
*SE400 Mini-lab all in one tester 15-50
CI-5 Series 500-1000kHz (carr. £1.00) 43-00
*C3043 5 CM FIA meter 1-300MHz 5-75
Resist. sub box Post 2-40
Capacitor etc 20p 2-10
2 amp variable transformers (carr. £1) 6-55
Radio activity counter 0-10r (carr. £1) 9-97
Mains unit for above (carr. 50p) 3-75

TAPE HEADS

Marrfot XRSP/17 1/2 Track High 3-50
Marrfot XRSP/18 1/2 Track Med. 2-50
Marrfot XRSP/36 1/2 Track Med. 5-00
Marrfot XRSP/83 1/2 Track High 1-75
Marrfot Erase Heads for XRSP/17/36 (XES11) 75p
Marrfot BXIZE 3431 track erase 75p
R/RP1 Record/Play 1 Track 45p
H/RP Single Track Rec/Play 35p
Bogen Type UL290 Erase Miniature Stereo Cassette Rec/Play 2-25

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max. DC operation, complete with data. Price £1-50 each or 2 for £2-85. Printed Circuit Panels. 50p.

CALCULATORS

Sinclair Cambridge Kit £13.50
Sinclair Cambridge (Built) £17.50
Sinclair Memory £22.50
Sinclair Scientific Kit £18.95

74 SERIES & LINEAR

EXTRA DISCOUNT

Semiconductors - Any one type or mixed SN74 Series IC's. 12-extra 10%; 25-extra 15%; 100-extra 20%.

£ p	£ p	£ p
SN7400N 0-16	SN7485N 1-63	SN74191N 2-00
SN7401N 0-16	SN7486N 0-47	SN74192N 2-00
SN7402N 0-16	SN7489N 3-87	SN74193N 2-00
SN7403N 0-16	SN7490N 1-70	SN74194N 1-30
SN7404N 0-16	SN7491N 1-00	SN74195N 1-10
SN7405N 0-16	SN7492N 0-70	SN74196N 1-20
SN7406N 0-42	SN7493N 0-70	SN74197N 1-20
SN7407N 0-42	SN7494N 0-80	SN74198N 2-77
SN7408N 0-28	SN7495N 0-90	SN74199N 2-52
SN7409N 0-28	SN7496N 0-95	
SN7410N 0-18	SN7497N 3-87	CA3012 1-32
SN7411N 0-20	SN74100N 1-89	CA3014 1-30
SN7412N 0-30	SN74104N 0-58	CA3018 1-02
SN7413N 0-36	SN74105N 0-53	CA3019 1-12
SN7414N 0-72	SN74107N 0-45	CA3020 1-80
SN7415N 0-36	SN74110N 0-50	CA3022 1-93
SN7416N 0-36	SN74111N 1-53	CA3028A 1-03
SN7417N 0-36	SN74116N 1-89	CA3036 1-08
SN7418N 0-18	SN74118N 0-90	CA3046 1-03
SN7421N 0-33	SN74119N 1-68	CA3048 2-76
SN7422N 0-25	SN74120N 0-95	CA3075 1-75
SN7423N 0-37	SN74122N 0-50	CA3081 1-50
SN7425N 0-37	SN74125N 1-00	CA3089E 2-94
SN7426N 0-32	SN74123N 1-00	CA3090 5-40
SN7427N 0-37	SN74125N 0-65	Signetics
SN7428N 0-40	SN74132N 0-72	NE555 0-85
SN7430N 0-16	SN74141N 0-90	NE560B 5-00
SN7432N 0-37	SN74145N 1-26	NE561B 5-00
SN7433N 0-37	SN74150N 1-75	NE567B 3-50
SN7437N 0-37	SN74151N 1-00	Motorola
SN7438N 0-37	SN74153N 0-95	MC1303L 1-42
SN7440N 0-22	SN74154N 2-00	MC1304P 1-79
SN7441AN 0-92	SN74155N 1-00	MC1305 2-91
SN7442N 0-79	SN74156N 1-00	MC1456CP 0-77
SN7443N 0-27	SN74157N 1-38	MC17100C 0-80
SN7444N 1-27	SN74158N 1-38	MFC4000P 0-45
SN7445N 1-60	SN74161N 1-38	MFC4010P 0-55
SN7446N 1-89	SN74162N 1-38	MFC6040P 1-00
SN7447AN 1-60	SN74163N 1-38	Others
SN7448N 1-27	SN74164N 1-76	TLA980 1-50
SN7450N 0-16	SN74165N 1-76	SN7600SN 1-50
SN7451N 0-16	SN74166N 1-76	SN74241P 0-60
SN7452N 0-16	SN74167N 3-00	SN74248P 0-81
SN7454N 0-16	SN74170N 2-52	709C 0-75
SN7456N 0-36	SN74173N 1-66	709C 0-39
SN7472N 0-38	SN74174N 1-57	709C 0-90
SN7473N 0-41	SN74175N 1-10	728C 0-50
SN7474N 0-42	SN74176N 2-26	728C 0-45
SN7475N 0-59	SN74177N 1-26	747C 1-00
SN7476N 0-45	SN74180N 1-26	747C 0-81
SN7480N 0-60	SN74181N 3-95	748C 0-61
SN7481N 1-10	SN74182N 1-26	LM309K 2-00
SN7482N 0-87	SN74184N 1-80	TLA980 1-75
SN7483N 1-10	SN74186N 1-10	Sinclair IC12, 6w amp 2-20
SN7484N 1-00	SN74190N 2-00	

Comos Integrated Circuits. Full Range

AZ13 0-12	BLV36 6-00	TIP24A 0-90
AC107 0-15	BSX20 0-13	TIS43 0-28
AC128 0-15	BUJ05 2-20	V405A 0-22
AC187 0-21	BY100 0-27	ZTX108 0-68
AC197 0-40	BY127 0-12	ZTX300 0-13
ACY39 0-78	BY213 0-62	ZTX302 0-18
AD149 0-50	CI060 0-34	ZTX500 0-13
AD161 0-44	GET111 0-72	ZN697 0-16
AD162 0-44	GET115 0-90	ZN705 0-62
AF117 0-24	GET880 0-60	ZN930 0-18
AF118 0-57	LM309K 2-00	ZN987 0-42
AF139 0-41	MA1121 0-25	ZN987 0-24
AF166 0-48	ME340 0-47	ZN1304 0-25
AF239 0-44	MJE520 0-63	ZN1613 0-21
AS27 0-33	MJE3055 0-77	ZN1671 1-20
BA115 0-10	MJE2955 1-27	ZN2147 0-78
BAX13 0-05	MPF105 0-36	ZN2160 0-78
BC107 0-14	NK7404 0-65	ZN2928 0-12
BC108 0-13	OAS 0-72	ZN3053 0-18
BC109 0-14	OAS1 0-35	ZN9654 0-68
BC109C 0-16	OA200 0-08	ZN3055 0-42
BC113 0-15	OA202 0-06	ZN3440 0-58
BC147 0-10	OC28 0-66	ZN3442 1-38
BC148 0-08	OC35 0-55	ZN3525 0-91
BC149 0-10	OC36 0-60	ZN3614 0-65
BC159C 0-15	OC44 0-20	ZN3702 1-01
BC182 0-12	OC45 0-20	ZN3714 1-41
BCY32 0-85	OC71 0-18	ZN3771 1-77
BCY39 1-50	OC72 0-28	ZN3773 2-48
BCY55 2-64	OC77 0-54	ZN3900 2-16
BCY70 0-18	OC81 0-29	ZN3919 0-38
BCY71 0-22	OC83 0-27	ZN3988 0-72
BCY72 0-12	OC140 1-14	ZN3983 0-15
BD124 0-65	OC170 0-30	ZN4002 0-14
BD131 0-42	OC200 0-54	ZN4126 0-15
BF115 0-20	OC202 0-90	ZN4871 0-34
BF180 0-36	OC271 0-50	ZN5457 0-30
BF184 0-10	ORP12 0-60	ZN5503 0-60
BFX13 0-26	ORP60 0-55	ZO550 0-54
BFX34 0-70	P346A 0-18	ZO631 0-45
BFX88 0-24	TIL209 0-29	ZO632 0-40
BFY50 0-21	TIP29A 0-45	ZO649E 0-85
BFY51 0-29	TIP30A 0-57	ZO648