

An exciting hobby.... for everyone


APRIL 77
35p

everyday electronics




SPECIAL
8 PAGE
SUPPLEMENT

..GUIDE to
COMPONENT
BUYING

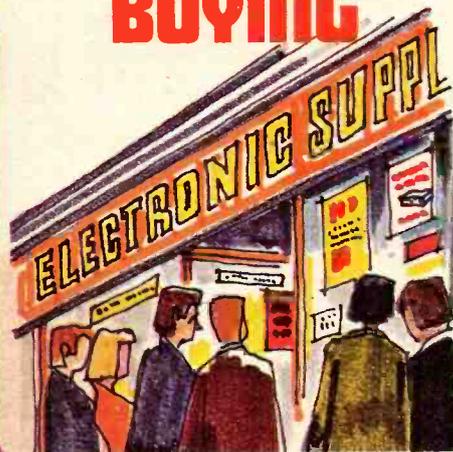

MODEL
RAILWAY
CONTROLLER

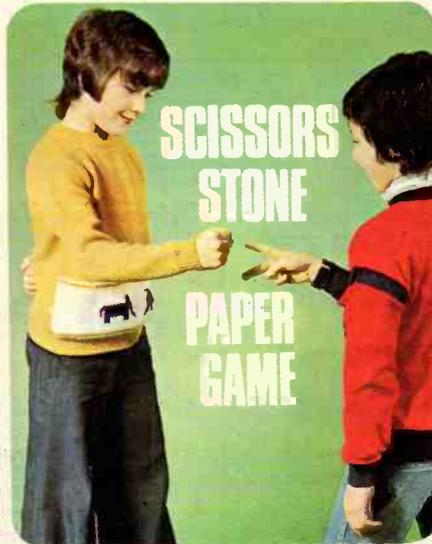

SCISSORS
STONE

PAPER
GAME

...Also

CAR
BURGLAR
ALARM

CONTINUITY
TESTER

Stirling Sound


Q.V. MODULES FOR COST CONSCIOUS CONSTRUCTORS

MADE IN OUR OWN U.K. FACTORY

NEW THIS MONTH!

UNIT TWO FOR LOW AND HIGH OUTPUT CARTRIDGES

Another real money saver from Stirling Sound! Wire this unit in and style it how you wish. Full instructions make this completely straight-forward. Use Stirling Sound power amps, for choice, but Unit Two will work superbly in any system. Active tone control circuits give bass and treble rise and cut of $\pm 15\text{dB}$ each; accepts inputs from 1 to 5 mV, RIAA corrected also adaptable for use with ceramics, etc. S/N ratio—60dB; channel separation typically 50dB; frequency range—30-20,000 Hz $\pm 1\text{dB}$. Tested ready built and guaranteed. For 10-20 V. operation.

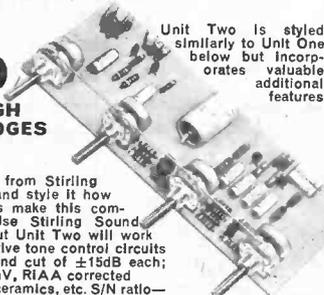


Unit Two is styled similarly to Unit One below but incorporates valuable additional features

£10.85

100 WATT R.M.S. POWER AMP AND MATCHING 70V. POWER SUPPLY

Your chance to save £1.95

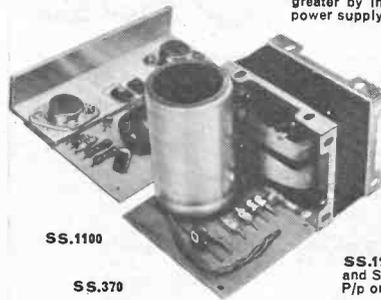


Today's best 100 watt value is now made even greater by including the Stirling Sound SS.370 power supply together at the sensational price of £21.00*. A ruggedly built and guaranteed assembly, ideal for disco, P.A., guitar use etc. Normal selling price for items bought separately is £22.95*—already superb value—so don't delay—order NOW!

SS.1100
100 watt power amp
with heatsink type
mounting flange **£9.45***
Full size heat sink **£1.00**

SS.370
70V/2A power supply
with low volt take-off **£12.50***

SS.1100H (with large heat sink)
and SS.370
P/p on item sinc. SS.370 £1.00 **£21.00***

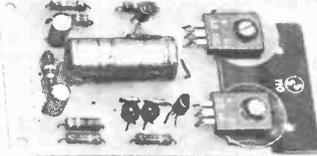MORE STIRLING SOUND Q.V. MODULES TO SAVE YOU MONEY



POWER AMPLIFIERS

3 TO 40 WATTS R.M.S.

SS.103 3 watt r.m.s. mono. I.C. **£1.75**

SS.103-3 Stereo version of above using two I.C.s **£3.25**

SS.105 5 watts r.m.s. into 3 ohms, using 12V **£2.25**

SS.110 10 watts r.m.s. using 24V and 4 ohm load **£2.75**

SS.120 20 watts r.m.s. into 4 ohms, using 34V **£3.25**

SS.140 Delivers 40 watts R.M.S. into 4 ohms using 45 volts supply unit such as SS.345. Ideal for small disco, P.A., etc. **£3.95***

If ordering Stirling Sound power supply units with Modules SS.103 to SS.120, V.A.T. becomes 12½%.

SS.103 to SS.120, V.A.T. becomes 12½%.

TONE CONTROLS/PRE-AMPS

SS.100 Active tone control, stereo. $\pm 15\text{dB}$ on bass and on treble **£1.60**

SS.101 Pre-amp for ceramic cartridges, etc. Stereo. Passive tone control details supplied. **£1.60**

SS.102 Stereo pre-amp for low output magnetic P.U.s. R.I.A.A. corrected. **£2.65**

UNIT ONE TONE CONTROL/PRE-AMP

A real money saver this. Compatible with all relevant Stirling Sound modules as well as other makes.

Combined pre-amp with active tone-control circuits. $\pm 15\text{dB}$ at 10KHz treble and 30Hz bass. Stereo. Vol./balance/treble/bass. 200mV out for 50mV in. Operates from 10 to 16V supply. **£7.80**

F.M. TUNING MODULES

SS.201 Front end tuner, slow geared drive, two gang. A.F.C. facility. Tunes 88-108 MHz. **£5.00**

SS.202 I.F. amplifier. Metering and A.F.C. facilities. **£2.65**

SS.203 Phase lock loop Stereo Decoder for use with the above or other FM mono tuners. A LED may be fitted. **£3.85**

SS.203-1 Coil-type stereo decoder for use with SS.201 and SS.202, recommended where economy is called for. Available in two forms:-

SS.203-1N with I.C. for neg. earth **£2.50**

SS.203-1P transistor type for pos. earth **£2.00**

SS.203-1P transistor type for pos. earth **£2.00**


WHAT QV MEANS TO YOU

It means Stirling Sound QUALITY and VALUE from modules made in our own Essex factory. They are all tested and guaranteed and offer unbeatable value. Designed by highly specialist electronic engineers with wide experience of constructors' and experimenters' needs. WATCH HOW THE STIRLING SOUND RANGE GROWS!

POWER SUPPLY UNITS

WITH 13-15V
TAKE-OFF
POINTS

Except
SS.312

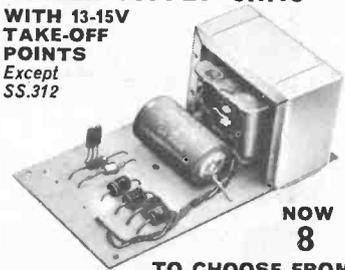

NOW
8

TO CHOOSE FROM

Complete with mains transformers and low volt take-off points (not SS.300). All at 8% V.A.T. rate.

Model	Output	Price	P/p
SS.312	12V/1A	£3.75*	50p
SS.318	18V/1A	£4.15*	50p
SS.324	24V/1A	£4.60*	50p
SS.334	34V/2A	£5.20*	50p
SS.345	45V/2A	£6.25*	50p
SS.350	50V/2A	£6.75*	50p
SS.370	70V/2A	£12.50*	£1

SS.310/50 Stabilised power supply with variable output from 10V to 50V/2A. Built-in protection against shorting **£11.95***

SS.300 Power stabilising unit 10-50V adjustable for adding to unstabilised supplies. Built in protection against shorting (p/p 35p) **£3.26***

LARGE S.A.E. BRINGS LATEST STIRLING SOUND 16 LARGE PAGE EQUIPMENT COMPONENTS PRICE LIST

WHEN ORDERING add 35p for p/p unless stated otherwise. V.A.T. add 12½% to total value of order unless price is shown* when the rate is 8%. Make cheques, etc. payable to Bi-Pre-Pak Ltd. Every effort is made to ensure correctness of information at time of going to press. Prices subject to alteration without notice.

Stirling Sound

A member of the Bi-Pre-Pak group (Westcliff on Sea)


Dept. PE/4, 220-224 West Road, Westcliff-on-Sea, Essex SS0 9DF
Tel: Southend (0702) 46344. Personal callers welcome.

DE-LUXE 25 WATT HI-FI AMP BARGAIN

Made to sell at £7.25
LIMITED NUMBER
AVAILABLE AT


£5.20

This is the Bi-Pre-Pak SS.125, designed and made for the connoisseur market of hi-fi and technical specialists. 25w r.m.s. into 8 ohms using 50V; 22 w.r.m.s. into 4 ohms. (35V). Input sensitivity—150 mV for full output; distortion less than 0.05% at all powers. Size 4½" x 3" x 3" (120 x 76 x 22mm). With full instructions. TESTED & GUARANTEED. LIMITED NUMBER ONLY AVAILABLE. Ideal with Unit Two described above and SS.310/50

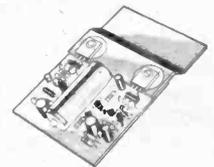

SS.125
DE-LUXE
POWER AMP

Bring 'scope' to your interest.



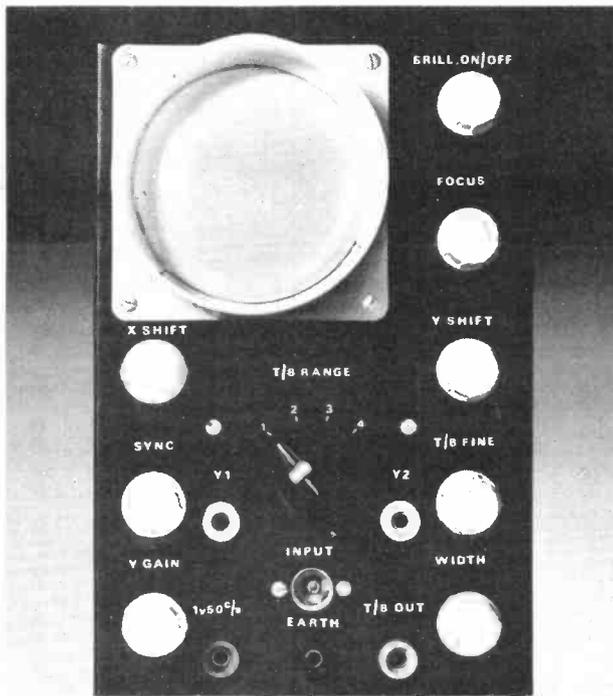


'There's only one way to master electronics... to see what is going on and learn by doing.'

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

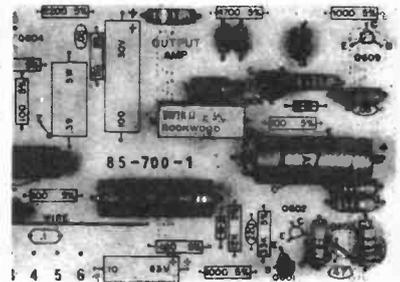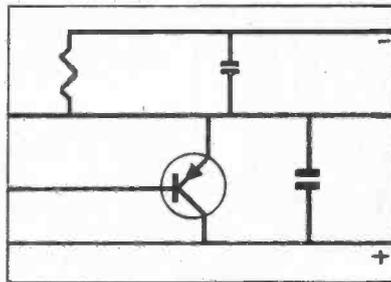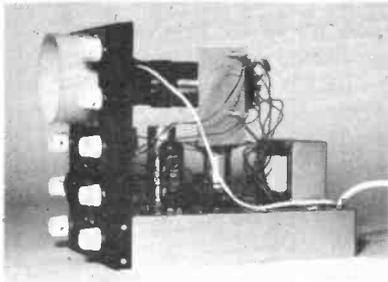All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

FREE GIFT

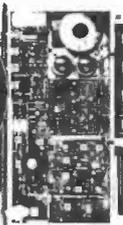

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronics School,
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

EEB 47

It's just like an electronic supermarket



Doram has everything for the home constructor available by speedy mail order service.

"We've built our name on quality and reliability —TRY US!"

DORAM ELECTRONICS LTD., PO BOX TR8, LEEDS LS12 2UF

I enclose..... EE4/77
 Please send me the DORAM Edition 3 Catalogue, price 60p
 the DORAM Kit Brochure, price 25p ..
 or the pair together for 70p ..

tick as appropriate

NAME.....

ADDRESS.....


(O'seas orders except for N. Ireland please add 30p p & p surface only).

AN ELECTROCOMPONENTS GROUP COMPANY

THESE



PLUS THIS

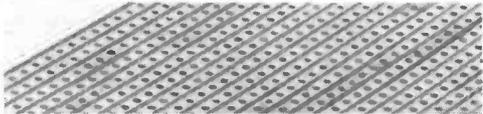

EQUALS

The easiest, fastest way of constructing your electronic circuits. 0.1" x 0.1" or 0.15" x 0.15" Matrix, 15 sizes.



VEROBOARD®

New catalogue available (price 10p + S.A.E. at least 7" x 9")
 Vero Electronics Limited, Retail Dept.,
 Industrial Estate, Chandler's Ford, Hants. SO5 3ZR
 Telephone: Chandler's Ford 2956 (STD 04215)

vero

GREENWELD

443 Millbrook Road Southampton
 SO1 0HX Tel:(0703) 772501

OPEN 6 DAYS A WEEK, 9 to 6.
 Callers Welcome
VAT INCLUSIVE PRICES—NO EXTRAS TO PAY, JUST ADD 20p POST.

RESISTORS
 Miniature 1/8 Watt Carbon Film Hi-stabs, 5% (Over 1M 10%). All values from 1 ohm to 10 Megohm, 1p each.
 1 Watt Metal Film 5%. All values from 27 ohms to 10 Megohms 2p each.
 2 1/2W Wirewound, All values from 0-22 ohms to 4-7k. 8p each.
 5W Wirewound, All values from 0-47 ohms to 47k. 16p each.
 15W Wirewound from 1ohm to 100k 15p each.
 Sub-min presets, all values from 22 ohms to 4-7 Megohms 7p each. Standard Pots 22p each.

TRANSFORMERS
 6-0-6V 100mA 90p; 9-0-9V 75mA 90p; 12-0-12V 50mA 90p; 12-0-12V 100mA £1; 6-0-6V 1 1/2A £2-70; 12-0-12V 1A £2-90; 6-3V 1 1/2A £2-30; Multitapped type 0-12-15-20-24-30V 1A £3-80; 2A £5-00; 20-0-20V 2A £4-20; 55-0-55V 5A £8-00.

TRANSISTORS AND IC's
 AC127 15p BC184 12p 2N2926G
 AC126 15p BC212 14p 12p
 AC176 18p BC213 14p 2N3053 18p
 AC187 18p BC214 14p 2N3054 45p
 AC188 18p BCY70 15p 2N3055 38p
 AD161 35p BCY71 15p 2N3440 54p
 AD162 35p BCY72 15p 2N3442
 BC107 16p BD131 38p £1-20
 BC108 10p BD132 40p 2N3702 10p
 BC109 10p BFY50 15p 2N3703 10p
 BC109C 15p BFY51 15p 2N3704 10p
 BC147 16p BFY52 15p 2N3705 10p
 BC148 10p TIP41A 80p 2N3708 10p
 BC149 10p TIP42A 75p 2N3819 22p
 BC157 16p TIP2955 96p 2N4059 10p
 BC158 10p TIP3055 42p 2N4418 10p
 BC159 10p TIP3055 42p 2N4418 10p
 BC161 18p 2N2219 28p 2N5295 30p
 BC182 12p 2N2369 22p 741 25p
 BC183 12p 2N2646 60p 555 40p

44 Page Illustrated Catalogue only 18p + large S.A.E. FREE with orders over £3.

DIODES & LEDS
 1N4001, 25p; 1N4003, 46p; 1N4005 7p; 1N4006 8p; 1N4007 9p; 1N4148 4p; OA81-91 etc. 5p; BY127 12p; 100V3A 12p; 400V 3A 15p; Bridges 400V 1A 30p; 300V 1A 40p; 250V 2 1/2A 40p; 200V 5A 70p; TIL209 Red LED 15p; 0-2" Red, green or yellow 24p.

VEROBOARD
 100sq Ins asstd. size offsets, in 4 diff. packs: Pack A: All 0-1" Pack B: All 0-15" Pack C: Mixed Pack D: All 0-1" plain. All packs £1-20 each. 17 x 3 1/2" boards 0-1" £1-80. 0-15" £1-60; Plain 0-1" £1-40.

DEVELOPMENT PACKS
 Save £££'s by buying a full range of components at one go! All full spec. marked devices, no rejects or old stock.

50V Ceramic plate Capacitors, 5%. 10 of each value from 22pF to 1000pF. Total 210 for £2-70. Save £1-50!
 Carbon Film Min. resistors, 1/8 watt 5%, 10 each value 10 ohms to 1 Megohm, total 610 for £6-00. Save £3-15!

Electrolytic, 10 each value 1, 2-2, 4-7, 10, 22, 47, 100uF. All 25V. Total 70 for £3-20. Save £1-10!

CAPACITORS
 Miniature ceramic plate from 22pF to 1000pF 5% 2p; 1500pF to 1000pF 4p. Mylar 1000pF to 8200pF 5p each. Polyester .01 to 0-1uF 4p; .15, .22 5p; .33 8p; .47 8p; .68 10p; 1uF 12p; 2-2 18p.

Electrolytic, 25V working: 1, 2-2, 4-7, 10, 22, 47uF All 6p; 100uF 7p; 220uF 9p; 470uF 16V 9p; 470uF 25V 11p; 470uF 63V 18p; 1000uF 15V 12p; 1000uF 25V 18p; 1000uF 50V 32p; 1000uF 63V 40p; 2200uF 16V 20p; 2200uF 25V 29p; 2200uF 40V 48p; 4700uF 16V 43p; 4700uF 25V 58p; All the above are wire ended. Tag ended 4700uF 40V 72p.

Get a great deal from

Marshall's

A. MARSHALL (LONDON) LTD. DEPT. E.E.
LONDON — 40-42 Cricklewood Way, NW2 3ET
Tel. 01-452 0161 Telex 21492

GLASGOW — 85 West Regent Street, G2 2QD
Tel. 041-332 4133

BRISTOL — 1 Straits Parade, Fishponds Rd. BS16 2LX
Tel. 0272 654201

NEW CATALOGUE 77

168 page catalogue with 500 new lines, 55p post paid (40p to callers)

2N696	0-35	2N3639	0-30	2N6101	0-65	BC142	0-30	BCY32	1-70	BF245	0-34	TIP32A	0-50	LM710N	0-60	TAD100	1-95
2N697	0-30	2N3641	0-20	2N6107	0-42	BC143	0-30	BCY33	1-00	BF246	0-75	TIP33A	0-80	LM723C	0-85	TBA120	0-65
2N698	0-62	2N3702	0-17	2N6109	0-42	BC147	0-12	BCY34	1-20	BF254	0-24	TIP34A	0-90	LM723N	0-75	TBA400	1-50
2N699	0-55	2N3703	0-15	2N6121	0-38	BC148	0-12	BCY38	2-00	BF255	0-24	TIP35A	2-50	LM741C	0-65	TBA500	2-21
2N706	0-24	2N3704	0-15	2N6122	0-41	BC149	0-13	BCY42	0-60	BF257	0-37	TIP36A	3-35	LM742N	0-50	TBA500Q	2-30
2N706A	0-12	2N3705	0-15	2N6123	0-43	BC153	0-27	BCY58	0-25	BF258	0-45	TIP41A	0-70	LM741-8	0-40	TBA510	2-21
2N708	0-21	2N3706	0-16	2N6126	0-45	BC154	0-27	BCY59	0-25	BF259	0-49	TIP42A	0-80	LM747N	0-90	TBA510 2	2-21
2N709	0-50	2N3707	0-18	40361	0-45	BC157	0-12	BCY70	0-25	BF459	0-45	TIP29C	0-60	LM748-8	0-50	TBA520	2-21
2N718	0-27	2N3708	0-16	40362	0-48	BC158	0-11	BCY71	0-25	BF459	0-45	TIP30C	0-65	LM748N	0-50	TBA520 2	2-21
2N718A	0-50	2N3709	0-18	40363	0-20	BC159	0-14	BCY72	0-24	BF521A	2-60	TIP31C	0-66	LM3301N	0-85	TBA520Q	2-21
2N720A	0-80	2N3710	0-16	40406	0-58	BC160	0-50	BD115	1-20	BF528	1-04	TIP32C	0-75	LM3302N1	4-0	TBA520Q	2-21
2N914	0-35	2N3711	0-18	40407	0-45	BC161	0-50	BD116	1-20	BF561	3-30	TIP33C	1-10	LM3401	0-70	TBA520Q	2-21
2N916	0-30	2N3712	1-20	40408	0-65	BC167	0-12	BD131	0-51	BF598	0-27	TIP34C	1-20	LM3900	0-75	TBA530	1-98
2N918	0-38	2N3713	0-20	40409	0-65	BC168	0-12	BD132	0-54	BFX29	0-38	TIP41C	0-85	LM3905	1-60	TBA530Q	2-07
2N929	0-25	2N3714	2-45	40410	0-65	BC169	0-12	BD135	0-37	BFX30	0-40	TIP42C	0-95	LM3909	0-68	TBA540	2-21
2N930	0-28	2N3715	2-55	40411	0-85	BC170	0-16	BD136	0-37	BFX84	0-40	TIP2955	0-65	MC1035	1-75	TBA540 2	2-21
2N1131	0-60	2N3716	2-80	40594	0-74	BC171	0-14	BD137	0-38	BFX85	0-41	TIP3055	0-55	MC1303	1-47	TBA540Q	2-21
2N1132	0-60	2N3717	1-85	40595	0-85	BC172	0-12	BD138	0-38	BFX87	0-40	TIS43	0-30	MC1304	1-85	TBA540Q	2-21
2N1613	0-35	2N3772	2-00	40673	0-73	BC177	0-20	BD139	0-40	BFX88	0-40	CA3020	1-78	MC1305	1-85	TBA550	3-13
2N1711	0-37	2N3773	2-90	AC126	0-37	BC178	0-20	BD140	0-40	BFX89	1-25	CA3020A	2-29	MC1306	1-00	TBA550Q	3-22
2N1893	0-38	2N3789	2-90	AC127	0-44	BC179	0-23	BD239	0-40	BFY50	0-34	CA3028A	1-01	MC1312	1-98	TBA560Q	3-22
2N2102	0-60	2N3790	1-10	AC128	0-37	BC182	0-11	BD240	0-45	BFY51	0-38	CA3028B	1-01	MC1327	1-54	TBA560Q	3-22
2N2218	0-33	2N3791	3-10	AC151V	0-35	BC182L	0-14	BD241	0-45	BFY52	0-36	CA3028B	1-01	MC1309	0-92	TBA570	1-29
2N2218A	0-37	2N3792	3-50	AC152V	0-50	BC183	0-11	BD242	0-47	BFY53	0-34	CA3028B	1-29	MC1350	0-75	TBA570Q	1-38
2N2219	0-30	2N3794	0-20	AC153	0-49	BC183L	0-14	BD243	0-60	BFY90	1-37	CA3030	1-24	MC1357	1-45	TBA641B	1-38
2N2219A	0-32	2N3819	0-36	AC153K	0-55	BC184	0-12	BD244	0-62	BRV39	0-50	CA3030A	1-89	MC1357	1-45	TBA641B	1-38
2N2220	0-35	2N3820	0-38	AC176	0-40	BC184L	0-14	BD245	0-65	BSX21	0-32	CA3045	1-40	MC1458	0-91	TBA651	1-80
2N2221	0-22	2N3823	0-75	AC176K	0-60	BC207	0-12	BD245	0-65	BU015	1-50	CA3046	0-89	NE555	0-53	TBA651	1-80
2N2221A	0-26	2N3904	0-21	AC187K	0-55	BC208	0-11	BD246	0-66	BU025	2-20	CA3048	2-23	NE556	1-05	TBA700Q	1-52
2N2222	0-25	2N3906	0-22	AC188K	0-55	BC212	0-14	BD250	0-42	ME0402	0-20	CA3049	1-66	NE565	1-20	TBA700Q	1-52
2N2222A	0-25	2N4036	0-67	AD161	0-85	BC212L	0-17	BD530	0-47	ME0412	0-20	CA3052	1-62	NE566	1-65	TBA720Q	2-30
2N2268	0-25	2N4037	0-55	AD162	0-85	BC213	0-14	BDY20	1-13	ME4102	0-10	CA3053	0-60	NE567	1-80	TBA750Q	2-30
2N2369	0-25	2N4058	0-20	AF109	0-75	BC214	0-16	BF115	0-70	ME4104	1-10	CA3080	0-88	SAS560	2-50	TBA750Q	2-30
2N2369A	0-25	2N4059	0-20	AF124	0-65	BC214L	0-17	BF121	0-55	MJ480	1-35	CA3080A	1-88	76003N	2-55	TBA750Q	2-30
2N2646	0-75	2N4060	0-20	AF125	0-65	BC237	0-14	BF123	0-55	MJ481	1-55	CA3088	0-51	76013N	1-70	TBA750Q	2-30
2N2647	1-40	2N4061	0-17	AF126	0-65	BC238	0-12	BF152	0-25	MJ490	1-35	CA3088	0-51	76013ND	1-57	TBA800	2-07
2N2904	0-36	2N4062	0-18	AF127	0-65	BC239	0-15	BF153	0-25	MJ491	1-85	CA3089	2-52	76013ND1	1-57	TBA810	1-16
2N2904A	0-37	2N4126	0-17	AF129	0-69	BC251	0-15	BF154	0-25	MJ2955	1-25	CA3090	3-60	76023ND	1-57	TBA820	0-13
2N2905	0-37	2N4289	0-20	AF186	0-50	BC253	0-22	BF159	0-35	MJE304	0-58	CA3090	3-60	76033ND	2-55	TBA820	0-13
2N2905A	0-38	2N4919	0-65	AF200	0-70	BC257A	0-17	BF160	0-30	MJE370	0-58	CA3130	0-94	76033N	2-55	TAA301A	1-50
2N2906	0-28	2N4920	0-70	AF239	0-74	BC258A	0-17	BF161	0-60	MJE371	0-60	LM301A	0-65	TAA301A	1-50	TBA920	0-79
2N2906A	0-25	2N4921	0-50	AF240	0-98	BC259B	0-18	BF161	0-60	MJE521	0-65	LM307N	0-65	TAA350A	1-15	TBA940	2-99
2N2907	0-21	2N4922	0-55	AF279	0-80	BC261A	0-21	BF166	0-40	MJE2955	1-40	LM308C	1-82	TAA350A	1-15	TCA160C	1-85
2N2907A	0-22	2N4923	0-70	AF280	0-85	BC262B	0-17	BF167	0-38	MJE3055	0-85	LM308N	1-17	TAA521	1-00	TCA160B	1-85
2N2924	0-15	2N5190	0-60	BC107	0-15	BC263C	0-24	BF173	0-38	MP8111	0-35	LM309N	2-10	TAA522	1-00	TCA160B	1-85
2N2926	0-13	2N5191	0-70	BC108	0-15	BC300	0-45	BF177	0-30	MP8121	0-40	LM317K	3-00	TAA550	0-50	TCA160B	1-85
2N3019	0-55	2N5192	0-75	BC109	0-15	BC301	0-45	BF178	0-35	MP8111	0-35	LM318N	2-25	TAA560	1-60	TCA160B	1-85
2N3053	0-30	2N5195	0-90	BC113	0-17	BC303	0-60	BF179	0-35	MP8112	0-40	LM323K	6-40	TAA560	1-60	TCA160B	1-85
2N3054	0-60	2N5245	0-35	BC115	0-19	BC307	0-20	BF180	0-40	MP8113	0-45	LM3319	1-75	TAA570	2-30	TCA290A	3-13
2N3055	0-70	2N5294	0-40	BC116	0-19	BC308	0-18	BF181	0-40	MP8102	0-30	LM3379N	3-50	TAA611B	1-85	TCA290A	3-13
2N3390	0-25	2N5295	0-40	BC116A	0-20	BC309C	0-25	BF182	0-45	MPSA050	2-3	LM3390	3-80	TAA621	2-15	TCA420A	3-13
2N3391	0-25	2N5296	0-40	BC117	0-22	BC312	0-14	BF183	0-45	MPSA060	2-3	LM3390N	0-98	TAA661A	1-84	TCA420A	3-13
2N3319A	0-25	2N5298	0-40	BC118	0-16	BC318	0-12	BF184	0-38	MPSA520	3-35	LM381A	2-45	TAA661B	1-32	TCA420A	3-13
2N3392	0-16	2N5447	0-15	BC119	0-30	BC327	0-20	BF185	0-35	MPSA550	2-4	LM381N	1-60	TAA661B	1-32	TCA420A	3-13
2N3393	0-15	2N5448	0-15	BC121	0-45	BC328	0-19	BF194	0-14	MPSU560	2-4	LM382N	1-25	TAA700	3-91	TCA760	1-38
2N3394	0-15	2N5449	0-19	BC132	0-40	BC337	0-19	BF195	0-13	MPSU560	2-4	LM389N	1-00	TAA700	3-91	TCA760	1-38
2N3439	0-88	2N5457	0-32	BC134	0-15	BC338	0-21	BF196	0-14	MPSU560	2-4	LM702C	0-75	TAA930A	1-00	TCA800	3-13
2N3440	0-64	2N5458	0-33	BC135	0-15	BC547	0-12	BF197	0-17	MPSU560	2-4	LM709C	0-65	TAA930B	1-00	UAA170	2-00
2N3441	0-85	2N5459	0-29	BC136	0-19	BC548	0-12	BF198	0-18	TIP29A	0-45	LM709N	0-65	TAA930B	1-00	UAA180	2-00
2N3442	1-35	2N5484	0-34	BC137	0-14	BC549	0-13	BF200	0-35	TIP30A	0-49	LM710C	0-60	TAA930B	1-05	UAA180	2-00
2N3638	0-16	2N5486	0-38	BC140	0-40	BCY30	1-03	BF225J	0-25	TIP30A	0-49	LM710C	0-60	TAA930B	1-05	UAA180	2-00
2N3638A	0-16	2N6027	0-53	BC141	0-45	BCY31	1-06	BF244	0-35	TIP31A	0-50	LM710C	0-60	TAA930B	1-05	UAA180	2-00

TRIACS Plastic pack 400V
4 amp 0-70 10 amp 0-90
6 amp 0-75 12 amp 1-10
8 amp 0-80 16 amp 1-60

DIACS
ST2 20p
BR100 48p

BRIDGES
Full range of Bridge Rectifiers and Diodes listed in New Catalogue

THYRISTORS Plastic C106 116
5 amp 100V 0-35 8 amp 100V 0-43
5 amp 200V 0-40 8 amp 200V 0-49
5 amp 400V 0-49 8 amp 400V 0-62

OPTO ELECTRONICS
Full range of Opto devices in our New Catalogue

LEDs
3mm Red 18p, Gr. 25p, Y. 25p
5mm Red 20p, Gr. 25p, Y. 25p
TIL209 24p, ORP12 80p.
BPX25 £1-65

DISPLAYS 7 Segment
Single Double Display
DL704 2-00 3-00 3" Red
DL707 2-00 3-00 3" Red
DL747 2-50 3-40 5" Red
DL750 2-50 3-40 5" Red

SEE MARSHALL'S FOR CMOS

CD4000	0-20	CD4018	1-01	CD4042	0-83
CD4001	0-20	CD4019	1-10	CD4043	1-00
CD4002	0-20	CD4020	1-12	CD4044	0-94
CD4					

An exciting NEW series from...

Newnes Technical Books

Each of the books in this series is written by an expert in his own particular field. The books are authoritative yet easily understood by those with no technical knowledge whatsoever, and the texts are supplemented by many highly informative illustrations.

MASTER ELECTRONICS IN MUSIC

T. D. Towers

Contents: Creating Musical Sounds by Electricity — Making Musical Instruments Louder — Musical Special Effects by Electronics — Electronic Keyboard Instruments — Electric Guitars — Magnetic Tape Music — The Robot Drummer — Music Synthesisers — Music by Computer — Index.

130 pages 0 408 00262 X £2.50

MASTER HI-FI INSTALLATION

Gordon J. King

Contents: How it Works — The Amplifier — Programme Signal Sources — Importance of a Good F.M. Signal — The Loudspeaker — Mono, Stereo and Quadrophonic Sound — Four-channel Techniques — Room Effects — Best Use of Controls — Terminology — Index.

150 pages 0 408 00237 9 £2.50

MASTER STEREO CASSETTE RECORDING

I. R. Sinclair

Contents: Stereo Systems — Signal Sources — Controls and Facilities — Making the Recording — Replaying and Monitoring — Essential Maintenance — Aids to Better Recording — Noise Reduction Systems — Cassette Recorder and Hi-Fi.

140 pages 0 408 00238 7 £2.50



NEWNES TECHNICAL BOOKS, Newnes-Butterworths, Borough Green, Sevenoaks, Kent

B. BAMBER ELECTRONICS

Dept. EE, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

SPECIAL OFFER...
STARPHONE HIGH BAND RF PCB BOARDS, with conversion data for making into a good 2M Converter. (All that is needed: 1 xtal, 7 caps, 2 resistors, and 9V DC). PCB contains 2 Dual gate Mos Fet RF stages (3N140). Diode ring mixer, 3 stage Osc/Multiplier. All on one PCB, approx. size 6" x 1 1/2", ext. connections, 9V DC supply, AGC (can be left fixed bias, or RF gain control) Ant. input, IF output (works from a few MHz to over 30MHz). All Brand New. £6.50 each, while stocks last.

TELEPHONE HANDSETS with "PRESS-TO-TALK" buttons, on curly lead, brand new, £3.50 (few only).

GARRARD 9V DC MINIATURE MOTORS, Type 31BM, 3200 RPM governed, size approx. 1 1/4 in. dia. x 1 1/4 in. high, with 2mm spindle. Brand New. 60p each or 2 for £1.

SILICON HIGH VOLTAGE RECTIFIER STICKS, BY185 (new) 35kV 2.5mA £1 each, BY140 (ex-equip) 12kV 2.5mA 45p each.

VARIABLE STABILISED POWER SUPPLY, mains input, 0-24V output, stabilised and current limiting at 500mA + 32V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 2 1/2 x 4 in. complete with external 5kΩ 3-turn pot for voltage control. Connection data supplied. £7.

14 DIL REED RELAYS, 5 to 12V DC, 450 ohm coil. Designed to work directly from TTL Logic. Simple Pole Change over. Contact ratings 28V 1/4A 3W, £1.75 each.

PLASTIC BOXES 3 1/2" square, 1 1/2" deep (wall-mounting type) with 5-pin din plug on front panel, 50p each.

2N3055 type Transistors. O.K., but unmarked, 5 for £1.

110V NEONS, SCREW-IN-TYPE, 4 for 50p.

PROGRAMMERS (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable. Ideal for switching disco lights, displays, etc., or industrial machine programming. (Need slow motion motor to drive cams, not supplied.) 3 switch version £1-50.

MAINS ISOLATION TRANSFORMERS. Tapped mains input. 240V at 3A + 12V at 500mA output. New. boxed, made by Gardners, £12.

4MHz XTAL PACKS (10 assorted xtals between 4MHz and 5MHz), our selection only. £1 Pack.

MINIATURE PLIERS. High quality "Crescent", made in USA. £4.35 + VAT (35p).

SIDE CUTTERS. High quality. £3.70 + VAT 30p.

SPERRY 7-SEGMENT P.G.D. DISPLAYS, digit height 0.3in. red, with decimal points, 150V to 200V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new. AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one mount) £1 each. (Sorry, no single digit available.) Data supplied.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY5 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type TOS Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
2N3819 Fet, 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAY31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 50p.
1N9314 Diodes, 10 for 25p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.), approx. 3/4 in. x 1 1/2 in., 3 for 50p.

PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/2 in. x 1 1/2 in., 2 for 35p.
Lead suppressors (10kohm) for mobile plug leads, 4 for 50p.

HEAVY DUTY RELAYS, 24V d.c. operated (will work on 18V) 3 heavy duty make contacts around 10A rating) + 4 change over contacts + 1 break contact. New, complete with mounting bracket. (Ideal for switching HT on Linears.) Many uses for this high quality unit. £1.50 each.

T03 transistor insulator sets, 10 for 50p.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

ALU-SOL ALUMINIUM SOLDER (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p pack. Large reel £2.75.

VARICAP TUNERS Mullard Type ELC1043/05. Brand New. £4.40 + 12 1/2% VAT.

I.C.'s some coded, 14 DIL type, untested, mixed, sorry sold out.

Mobile Converters, 24V DC input 13.8V at approx. 3.4A DC output, fully stabilised. £3-50 each (ideal for running 12V car radio from 24V lorry battery).

We now stock Spiralax Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

Miniature earphones with min. jack plug, 2 for 50p + 12 1/2% VAT.

TWIN I.F. CANS, approx. 1in. x 3/4 in. x 1in. high, around 3-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.

Duobiler Electrolytics, 50µF, 450V, 2 for 50p.
Duobiler Electrolytics, 100µF, 275V, 2 for 50p.
Plessey Electrolytics, 470µF, 63V, 3 for 50p.
TCC Electrolytics, 1000µF, 30V, 3 for 60p.
Plessey Electrolytics, 1000µF, 180V, 40p each (3 for £1).
Duobiler Electrolytics, 5000µF, 35V, 50p each.
Duobiler Electrolytics, 5000µF, 50V, 60p each.
ITT Electrolytics, 6800µF, 25V, high grade, screw terminals with mounting clips, 50p each.
Plessey Electrolytics, 10,000µF at 63V, 75p each.
Plessey Cathodray Capacitors, 0-0.4µF at 12.5kV DC. Screw terminals, £1-50 each.
PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS
TV Plugs (metal type), 5 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p.
Please add 12 1/2% VAT.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

PLUGS AND SOCKETS
N-Type Plugs 50 ohm, 60p each, 3 for £1-50.
PL259 Plugs (PTFE), brand new, packed with reducers, 65p or 5 for £3.
S0239 Sockets (PTFE), brand new (4-hole fixing type), 50p each or 5 for £2.25.

SOLDER SUCKERS (Plunger Type). Standard Model, £4-50. Skined Model, £4-95. Spare Nozzles 60p each.

WELLER SOLDERING IRONS
EXPERT. Built-in-spotlight illuminates work. Plating grip with fingertip trigger. High efficiency copper soldering tip.

EXPERT SOLDER GUN. £6-80 + VAT (54p).

EXPERT SOLDER GUN KIT (spare bits case, etc.), £9-80 + VAT (78p).

SPARE BITS, PAIR, 30p + VAT (2p).

MARKSMAN SOLDERING IRONS

SP15D 15W £3 + VAT (24p).

SP25D 25W £3 + VAT (24p).

SP25DK 25W + bits, etc. kit £3-85 + VAT (31p).

SP40D 40W £3.44 + VAT (28p).

BENCH STAND with spring Marksmen Irons, £2-22 + VAT (18p).

SPARE BITS

MT8 for 15W, 46p + VAT (4p).

MT4 for 25W, 38p + VAT (3p).

MT2 for 40W, 42p + VAT (3p).

TCPI TEMPERATURE CONTROLLED IRON. Temperature controlled iron and PSU. £20 + VAT (£1-60).

SPARE TIPS

Type CC single flat, Type K double flat fine tip, Type P, very fine tip. £1 each + VAT (8p).

MOST SPARES AVAILABLE.

MULTICORE SOLDER

Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).

Size C1SAV18 Savbit 18 s.w.g., 56p + VAT (4p).

Size 12 Savbit 18 s.w.g. on plastic reel £1-80 + VAT (15p).

1/2 Kg. (1-11b) 80 x 40, 20 s.w.g. on plastic reel £3.

LOW, LOW PRICES ON BRANDED COMPONENTS.

These are the same components we supply in millions to industrial users. That's your guarantee of quality and service. It's also how we can maintain these sensationally low prices.

- All 'big name' manufacturers
- Same day service
- Money back guarantee

CD4001AE 0.19	CD4053AE 0.86	CA3075 1.35	SN74113 0.87	2N3440 0.57
CD4001AE 0.19	CD4054AE 1.07	CA3080 0.54	SN7417 0.37	2N3442 1.54
CD4002AE 0.19	CD4055AE 1.21	CA3081 0.82	SN7120 0.29	2N3702 0.17
CD4002AE 0.19	CD4056AE 1.00	CA3082 0.84	SN7427 0.31	2N3703 0.17
CD4003AE 0.19	CD4057AE 1.03	CA3083 2.01	SN7430 0.23	2N3704 0.18
CD4004AE 0.19	CD4058AE 1.00	CA3090E 0.92	SN7432 0.23	2N3706 0.17
CD4006AE 0.88	CD4059AE 0.87	CA3097E 0.99	SN7437 0.35	2N3708 0.18
CD4006AE 0.88	CD4060AE 1.00	CA3097E 0.99	SN7442 0.90	2N3708 0.18
CD4010AE 0.52	CD4061AE 0.42	CA3127E 1.31	SN7441 0.80	2N3709 0.18
CD4010AE 0.52	CD4062AE 0.20	CA3600E 1.01	SN7445 1.51	2N3709 0.18
CD4011AE 0.19	CD4063AE 0.20	8 pin 0.16	SN7447 1.69	2N3709 0.18
CD4012AE 0.19	CD4064AE 0.20	16 pin 0.20	SN7448 1.51	2N3711 0.79
CD4013AE 0.52	CD4065AE 0.20	28 pin 0.33	SN7472 0.31	40360 0.24
CD4016AE 0.52	CD4066AE 0.20	28 pin 0.37	SN7473 0.46	40361 0.25
CD4017AE 0.52	CD4067AE 0.20	LM555CN 0.52	SN7474 0.38	40362 0.25
CD4018AE 0.52	CD4068AE 0.20	703CN 0.88	SN7475 0.60	40406 0.42
CD4019AE 0.52	CD4069AE 0.20	709CN 0.40	SN7476 0.49	40407 0.42
CD4020AE 1.01	CD4070AE 0.20	710CN 0.86	SN7482 0.90	40408 0.40
CD4021AE 0.52	CD4071AE 0.20	711CN 0.53	SN7489 2.91	40409 0.40
CD4022AE 0.52	CD4072AE 0.20	8 pin 7411CN 0.29	SN7489 2.91	40410 0.40
CD4023AE 0.52	CD4073AE 0.20	7470CN 1.07	SN7490 0.71	40411 0.40
CD4024AE 0.52	CD4074AE 0.20	748CN 0.49	SN7491 1.01	40495 0.20
CD4025AE 0.52	CD4075AE 0.20	395CN 0.75	SN7492 0.71	40564 0.69
CD4026AE 0.52	CD4076AE 0.20	301AN 0.98	SN7493 0.71	40656 1.08
CD4027AE 0.52	CD4077AE 0.20	DIODES	SN7495 0.81	40673 0.49
CD4028AE 0.83	CD4078AE 0.20	1N4001 0.41	SN7497 0.42	8C107 0.14
CD4029AE 0.83	CD4079AE 0.20	1N4002 0.04	SN7498 0.46	8C108 0.13
CD4030AE 0.83	CD4080AE 0.20	1N4003 0.13	SN7499 0.46	8C109 0.16
CD4031AE 0.83	CD4081AE 0.20	1N4004 0.05	SN7499 0.46	8C110 0.16
CD4032AE 0.83	CD4082AE 0.20	1N4005 0.06	SN7499 0.46	8C111 0.16
CD4033AE 0.83	CD4083AE 0.20	1N4006 0.05	SN7499 0.46	8C112 0.16
CD4034AE 0.83	CD4084AE 0.20	1N4007 0.05	SN7499 0.46	8C113 0.16
CD4035AE 0.83	CD4085AE 0.20	1N4008 0.05	SN7499 0.46	8C114 0.16
CD4137AE 0.83	CD4187AE 0.20	1N4110 0.05	SN7499 0.46	8C216 0.16
CD4138AE 0.83	CD4188AE 0.20			

YES SIR 1st class post TONIGHT!
We specialise in high spec components
with express service for phone customers



HIGH SPEC components FAST!

Agents for VERO - ANTEX -
BIB MULTICORE SOLDER

- OPEN 9am-5pm, 6 days—Phone orders 9am-4pm.
- S.A.E. for stock list including pots, presets, I.C.'s 7400 & CMOS.
- capacitors, plugs, sockets, switches, cable, etc.
- Post free envelope included for your next order.
- SUPER EXPRESS phone service—ask for details.
- Shop at keen prices 6 days per week. Late night—Fri. 7-10p.m.

Electrolytic MFD/V	TRANSISTORS + 200 OTHER TYPES IN STOCK	IC's TTL	C/MOS
1/25 10p*	AC128 20p 157B 12p* 90 7p 3053 25p	7400 10p 3055 60p	4000 18p
1/63 10p*	AD161 52p 178B 18p 200 10p 3702 11p*	4011 18p	4012 75p
1/75 10p*	162 52p 179B 19p OC44 45p 3703 43p	4012 18p*	4014 52p
2-2/25 10p*	MCH/PR 184B 12p* 184L 11p* DRP12 65p 3704 13p*	4013 18p*	4016 52p
2-2/63 10p*	AF117 28p 187 26p TIP29A 47p* 3707 12p*	4014 52p	4024 75p
2-5/64 10p*	BC107 11p 212A 13p 30A 56p	4015 18p*	
4-7/16 8p*	107A 12p 212L 15p* 31A 57p 3819E 25p*	4016 52p	
4-7/63 10p*	108 10p 213B 12p* 41A 67p		
5/10 10p*	CIL108 6p 214 15p* 42A 80p 7400 15p		
6-8/25 10p*	BC108B 11p 214L 17p* TIS43 35p 7401 20p		
6-8/40 10p*	108C 12p 282A 19p ZTX300 13p* 7473 38p		
8/70 8p*	109 12p 287 28p 302 18p* 7493 55p		
10/25 9p*	109B 13p 300 35p 500 15p*		
10/35 10p*	109C 13p 301 34p 502 18p*		
10/64 10p*	117 18p* 303 35p 1N91A 5p		
15/40 10p*	142 24p 338 16p* 1N4001 5p		
16/10 10p*	143 24p 557 15p* 4002 8p		
20/15 10p*	147A 9p BCY71 18p 4005 9p		
20/70 10p*	147B 10p 72 14p 4006 10p		
22/16 10p*	148 9p BFY50 25p 4148 5p		
22/6V3 10p*	148B 10p 51 25p 2N2219 30p LINEAR		
22/16 10p*	148B 10p 51 25p 2N2646 45p 741		
25/25 11p*	149B 11p* 52 25p 2N2666 45p 741		
33/50 12p*	149C 11p* MPF102 32p 2N2660 13p* NE555 60p		
47/6V3 10p*	BC154 18p* OA 47 14p 2N266G 15p* ZN414 1-60*		
47/16 10p*	330/16 15p*		
47/25 10p*	470/6V3 10p*		
50/10 10p*	470/10 12p*		
50/15 10p*	470/25 20p*		
100/18 6p*	470/25 25p*		
100/25 10p*	680/25 25p*		
100/50 15p*	1000/16 25p*		
150/35 15p*	1000/50 40p*		
220/18 15p*	1500/25 35p*		
220/25 18p*	2200/40 60p*		
220/63 25p*	2500/15 45p*		
250/12 12p*	5000/12 45p*		
250/64 20p*	3300/30 45p*		

Post & Packing 25p per order.

VAT please add to total * 12½%, rest 8%.

DISCOUNTS, ORDER VALUE OVER
£5=5% £10=7½% £15=10%

NEW - - - FROM OUR BOOKSHOP VAT - - FREE!!!

First book of Transistor Equivalents & Substitutes—40p. Handbook of Tested Transistor Circuits—40p. Handbook of Simple Transistor Circuits—35p. Radio & Electronic Colour Codes & Data Chart—15p. Modern Crystal & Transistor Set Circuits for Beginners—35p. Practical Transistor Novelty Circuits—40p. Electronic Novelties for the Motorist—50p. Second Book of Transistor Equivalents—95p. Constructors Manual of Electronic Circuits for the Home—50p. Handbook of Electronic Circuits for the Amateur Photographer—60p. Radio Receiver Construction Handbook using IC's & Transistors—60p. Boys & Beginners Book of Practical Radio & Electronics—60p. 79 Electronic Novelty Circuits—75p. First Book of Practical Electronic Projects—75p. 52 Projects using IC741 (or Equivalents)—75p. How to Build your Own Metal & Treasure Locators—85p. Handbook of IC Audio Preamp. & Power Amplifier Construction—95p. Boys Book of Crystal Sets—25p. Coil Design & Construction Manual—50p. Modern Transistor Circuits for Beginners—40p. Handbook of Practical Electronic Musical Novelties—50p. Practical Transistorised Novelties for Hi-Fi Enthusiasts—35p. Handbook of Integrated Circuits (IC's) Equivalents & Substitutes—75p. IC's and Transistor Gadgets Construction Handbook—60p. Practical Electronic Science Projects—75p. The Complete Car Radio Manual—75p. Electronic Circuits for Model Railways—85p. Audio Enthusiasts Handbook—85p. Electronic Gadgets & Games—85p. Solid State Power Supply Handbook—85p. Build your own Electronic Experimenters Laboratory—85p. Solid State Novelty Projects—85p. Build your own Solid State Hi-Fi & Audio Accessories—85p. 28 Tested Transistor Projects—95p. Solid State Short Wave Receivers for Beginners—95p. 50 Projects using IC CA3130—95p. 50 CMOS IC Projects—95p.

ORCHARD ELECTRONICS

FLINT HOUSE, HIGH STREET, WALLINGFORD, OXON, OX10 9DE
Telephone 0491 35529.

SOLDERLESS BREADBOARDING—DECS

The famous DEC System of Solderless Breadboarding is ideal for both the young and more mature students of Electronic Engineering as it enables circuits to be tried and tested without the use of soldering and because of the specially designed contacts allows components to be used over and over again. It is also extremely useful for the Circuit Designer who wishes to experiment with and perfect his circuit quickly yet economically.

S-DEC (Model PB11)

This, the most popular Board, is designed solely for the use of discrete components and is particularly useful for basic educational purposes.
(No. of Contacts: 70)

1 off £1.98
5 off £1.76

T-DEC (Model PB21)

This Board allows 2 TO5 or 1 DIL IC Station to be used and so is primarily intended for discrete work or for linear IC application where considerable numbers of discrete components may be required.
(No. of Contacts: 208)

1 off £3.62
5 off £3.21

μ-DEC 'A' (Model PB31)

The μ-DEC 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 TO5 stations to be used with all accommodate discrete components with equal facility.
(No. of Contacts: 208)

1 off £3.97
5 off £3.53

μ-DEC 'B' (Model PB41)

The μ-DEC 'B' is for similar uses as μ-DEC 'A', but has two 16 lead IC sockets as part of the Board.
(No. of Contacts: 208)

1 off £6.97
5 off £6.19

DEC ACCESSORIES

16 DIL adaptor (with socket) PB062	£1.92
10 TO5 adaptor (with socket) PB072	£1.80
Single ended leads (set of ten) PB101	£0.90
Double ended leads (set of ten) PB102	£0.99
1mm plugs (set of ten) PB103	£0.45

All prices include 8% VAT. P. & P. 25p.

Our retail counter is now open, stocking a large variety of audio and electronic parts and accessories, branded and surplus.

WE ARE SITUATED 2 MIN. WATFORD JUNCTION STATION

THE COMPONENTS CENTRE
7 Langley Road, Watford, Herts., WD1 3PS.
Tel.: Watford 45335

ELECTRONICS

54 Montagu Street Kettering
Northants Phone Kettering
43822

shop open Monday to
Saturday 9.00 to 6.00
early closing Thursday 1.00pm
closed daily for lunch 1-2 p.m.

T.T.L.	CRYSTALS & FILTERS
7400 16p 7445 100p	1-0 MHZ HC33/3
7401 16p 7446 100p	300p
7402 16p 7447 72p	3-2768 MHZ HC-33/10
7403 16p 7448 75p	300p
7404 16p 7450 16p	4-194304 MHZ HC-33/10
7405 16p 7451 16p	300p
7406 30p 7453 16p	4-7 MHZ HC33/10
7407 38p 7454 16p	300p
7408 18p 7460 56p	6-364068 MHZ HC-33/10
7409 22p 7470 30p	300p
7410 18p 7472 28p	37 MHZ HC25/10
7411 24p 7473 28p	300p
7412 26p 7474 28p	27 MHZ HC25/10
7413 30p 7475 47p	300p
7414 70p 7476 30p	39 MHZ HC25/10
7415 34p 7480 45p	215p
7416 32p 7481 100p	
7417 30p 7482 85p	
7420 16p 7483 100p	
7421 46p 7484 120p	
7422 20p 7485 120p	
7423 35p 7486 34p	
7424 30p 7489 240p	
7425 30p 7490 39p	
7426 24p 7491 70p	
7427 35p 7492 45p	
7428 40p 7493 45p	
7430 16p 7494 80p	
7432 27p 7495 70p	
7437 27p 7496 75p	
7438 27p 74100/10p	
7439 27p 74107 35p	
7440 16p 74109 65p	
7441 68p 74110 50p	
7442 68p 74118 85p	
7443 100p 74121 32p	
7444 100p 74123 70p	
C.M.O.S.	CD's
4000 21p	4011 21p
4001 21p	4012 21p
4002 23p	4013 60p
4007 21p	4015 93p
4008 95p	4016 63p
4009 70p	4017 93p
4010 66p	4018 120p

TRANSISTORS & I.C.'s

AA117 10p	BC557 15p*
AA119 18p	BD131 40p*
AC126 18p*	BD132 40p*
AC127 18p*	BD137 38p
AC176 19p*	BD138 40p
AC187 19p*	BD139 40p
AC188 19p*	BD140 42p*
AD149 50p*	BF194 10p*
AD161 45p*	BF195 10p*
AD182 45p*	BF199 15p
AF114 25p*	BT200 30p
AF115 25p*	BFY50 16p
BB103 45p*	BFY51 16p
BB104 60p*	BFY52 16p
BB105 37p*	BR101 30p
BB106 55p*	MJE2955
BC107 10p	140p
BC107B 13p	MJE3055
BC108 10p	110p
BC108B 13p	OC45 16p
BC109 10p	OC71 15p
BC109C 15p	TIP31 50p
BC147B13p	TIP32 50p
BC148 9p	TIS43 30p
BC149 10p*	2N2219 30p
BC157 10p*	2N2926 10p
BC158 10p*	2N3055 55p
BC159 30p	CA3080 90p
BC161 33p*	LM309L
BC177 15p	180p
BC178 15p	LM3800
BC179 15p	140p*
BC182L	LM3811
12p*	220p
BC184L	LM555 50p
12p*	LM709 50p
BC212L	LM723 75p
12p*	LM3900 90p
BC214L	MM5314
12p*	450p
BC516 60p	SN7601
BC517 65p	150p*
BC546 17p	SN76131N
BC547 9p*	195p*
BC547B	TBA800
14p*	205p*
BC549 12p*	32/10
BC549C	TBA810
15p*	200p*

BULK OFFERS

Red Leds 0.2 110/ 90

Clear Leds 0.2 110/ 10

741 Op Amp 8 DII 230/10

741 Op Amp 14 DII 190/10

IN4148 32/10

BC184L 90/10*

555 Timer 8 DII 180/10

Read Inerts 55/10

4 Amp Triax 400v

TO22D 420/10

022μf 250v polyester cap C280

25/10*

*High VAT.

ORDERING DETAILS

VAT at high rate to standard rate to others. Overseas please add freight costs and state surface or air.

Radiant Wall Heaters for bathrooms, workshops etc. advantage with this type of heater is that the benefit is felt immediately, there is virtually no warm up period. Due to a recent large purchase we can offer the Springfield 750w. This is a 750w heater 20" inches long. Quite nice design with highly polished reflector and chrome plated guard, wall mounting. Pull cord switch. Retail price originally intended to be £6.50/5p. We are able to see these at £3.95p+32p. Post 70p+6p. 4 Pole Motor. Carefully balanced spindle fitted with belt drive pulley for tape recorders etc. Normal mains working, speed 1250 rpm. Price £1.50p+19p. Post 30p+13p.

100watt Mains Transformer. 240v 50hz primary wound in separate halves, primary screen. This has three secondaries 24-0-24v, 0-49v and 0-88v tapped to 80v. Any one of these secondaries may be loaded up to the 100 watts or the load can of course be spread over to all the secondaries. Upright mounting, impregnated and varnished. Size 4" x 3 1/2" x 3". Price £3.50p+25p Post 80p+6p. Stereo Flex twin screen fig. 8 type. PVC insulated overall 10 metres for £1+8p.

Latching Relay by Guardian Electric, mains operated it is in fact two relays mounted on a metal base plate. The relays being mounted in such a way to ensure that when one closes the other opens and vice versa thus when closed, relay A would remain locked until manually released or electrically released by energising relay B. Each relay has 2 sets of 10 amp change-over contacts. Should be ideal for burglar alarms and similar applications. Price £1.95p+18p.

Connecting Wire. 7 stranded PVC insulated on 500 metre drums, 6 different colours available, price £4 per 500 metres + 32p. Post £1+8p. Please give alternative colours when ordering.

2 Track Stereo Cassette Deck. Complete mechanism with push button operated track selection. Tape head and pre-amp, Japanese made with front flap for cassette entry. Price £5.50p+62p. Post 40p+6p.

Mains Power Supply to suit deck £2+25p.

6 Track Stereo Cassette Player. 12 volt with polarity reversing switch. Speakers not included, these were sold under the trade name "Elpico" at just under £20 each. The ones we have were faulty on arrival from Japan but have been serviced. Price £9.50p+£1.99p. Post 50p+7p. We also have a few of our Elpico's in repair, but not complete and we believe quite repairable. Price £6.50p+82p. Post 50p+7p.

Shaver Light with isolated socket. As you know normal mains sockets must not be used in bathrooms on account of the danger of an accident through touching the socket when earthed through bath or sink etc. However, provided it is isolated from earth a shaver socket is allowable and the one we are offering complies with this requirement. It is also fitted with a pull cord switch and is ideal for use over the mirror in the bathroom. Price £3.50p+82p. Post £1.50p+12p.

Pressure Control Switch made by Allan Bradley of the U.S.A., their ref. no. 836. Completely adjustable from 30" of vacuum to zero then up to 75lbs per square inch of air pressure. This also has an adjustable differential which can be set to pressure tolerance of between 1.5 and 2.5 lbs. The switch operates changeover contacts which look capable of breaking up to 15 amps AC. Few only of these, price £15+£1.20p.

Air Flow Sensor, American made by the Foxborough Company. We have two different types. One bears ref. NFB-502A and the other NFB-502B. These are beautifully made precision units obviously intended for fitting into very high pressure air or gas lines. There is an inbuilt turbine and transducer/convertor with electrical contacts but other than this we have no information on the sensors, price in negatives.

Converter Amplifier again made by the Foxborough Company, their part no. N 137 CR. We believe these are for use with the above air flow sensors, price again negotiable.

Motor with Gear Box made by Klaxon, their type no. EK3Q J2-M21. This is a very popular type of motor, final speed is 10 rpm. Approximate size of the motor casing 0 7/8" long x 1 1/2" diameter. These are ex-equipment but guaranteed o.k. supplied complete with transformer for use on standard 230v 50hz mains. Price £4+32p. Post 80p+6p.

Main Table Radio, Japanese made. This is a medium wave valve receiver with built in aerial, plenty of volume and reasonable tone. Will receive all strong and medium powered stations on the wave bands—medium wave. This type of radio is coming back into popularity owing to the very high price of battery types. Price £4.95p+50p. Post £1.50p+19p.

Auto Transformer 200 watt 240 to 115 volt. This is the same as the transformer above as this has a centre tapped primary. Price £1.50p+19p.

Main Battery Japanese made. Enclosed in a plastic case with two prongs for shaver and adaptor. This has output of 4.5v at 100 mA and is, therefore, suitable to use in radios or similar equipment that use three 1.5 cells or by small internal alterations the voltage can be stepped up to 6 volts very easily or 9 and 12v. Price £2.00+25p. DITTO BUT 5V. Price £2.50p+30p.

Car Starter. Most drivers who use their car around town find that on a very cold morning they have difficulty in starting because the battery has not any charge left in it. This always seems to happen on the morning when you are in a particular hurry so a charger/starter is well worth having. Our kit for this comprises: a heavy duty 250w transformer and full wave rectifier which for short periods will deliver 20 amps. This is usually enough to get the car started, directly it has started of course it can be disconnected from the battery as the internal charger will take over. Special offer price of this is £8.60p including post and VAT.

MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Celestion speakers. This should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14 including VAT and postage.



PAPST MOTOR

West German make, these fine motors are noted for their performance and reliability. Special features are the rotating heavy outer which acts as a flywheel to eliminate wow and flutter and switchable reversing.

We have four types, in stock, all 1350 revs., including starting capacitor.

- (1) Reference No. KLZ 20.50-4, 230 volts 50HZ, price £5.50
- (2) Reference No. KLZ 32.50-4, 230 volts 50HZ, price £6.50
- (3) Reference same as above, 115 volts 50HZ, price £2.50
- (4) Reference same as above, 110 volts 60HZ, price £2.50

AEROSOL RELEASE LUBRICANT

Dry Film Lubricant. In aerosol can for easy application and for putting lubricant into places where the normal oil can cannot reach. Home and everyday uses. We have purchased a large quantity of these from the Liquidator and are able to offer them to you for about half of the original list price. 88p per 8oz can or 12 cans for £5 Post & VAT Paid. The lubricant is I.C.I. Fluon L169.



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heaters, etc. New and perfect. Snip at 95p+VAT & Postage 35p. 1" stackmotor £1.68+VAT & postage 35p. 1 1/2" stackmotor. £2+VAT and Postage 40p.

MULTI SPEED MOTORS

Six speeds are available 500, 850 and 1,100 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 1/4" in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor. Very powerful and useful motor size approx. 2 in. dia x 5 in. long. Price £2.00 including Post & VAT. Speed control switch £1+4p.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.75, VAT & postage 85p.

MOTORISED DISCO SWITCHES

With six 10 amp changeover switches. Multi adjustable switches are rated at 10 amp each so a total of 2000w's can be controlled and this would provide a magnificent display. For mains operation £4.25 post & VAT & Postage 35p. £4.95 Post & VAT Paid. DITTO BUT 15 SWITCH £5.75 POST & VAT PAID.



BATTERY CONDITION TESTER

Made by Malloy but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—lead—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prod. £4.50 post & VAT paid.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quick running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment, but to suck it out, mount from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying, cabinet or for removing fume smoke when soldering, etc. etc. A real bargain at £3.30 60p post & VAT.

BREAK-DOWN UNIT

Contains hundreds of useful parts some of which are as follows—56 silicon diodes equivalent to 0.049 18 resistors, mostly 1 watt 5% covering a wide range of values 4 x 1 mfd 400v mfd condensers, 15 x .01 mfd 100v condensers. 2 RF chokes 8 x B9 valve holders, 1 x 4H choke, 1 x 115v transformer, 1 boxed unit containing 4 delay lines also tag panels, trimmer condensers, suppressors, etc., on a useful chassis sized approx. 9" x 5" x 7". Only 75p (the 66 diodes would cost at least 10 times this amount). This is a snip not to be missed. Post and VAT 75p.

HONEYWELL PROGRAMMER

This is a drum timing device, the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control. Boiler firing. Dispensing and Vending machines. Display lighting animated and signs. Signaling, etc. Price from makers probably over £20 each. Special snip price £29.95. £1.00 Post and VAT. Don't miss this terrific bargain.

TERMS: Where order is under £6 please add 50p surcharge to offset packing expenses

J. BULL (ELECTRICAL) LTD.
(Dept. E.E.), 103 TAMWORTH ROAD,
CROYDON CR9 1SG.

ITS FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from a recent list.

Light for Growing. With the ever increasing price of oil, more and more growers are using insulated buildings without any daylight and are using electric lamps for light and heat. Various different types of lamps are recommended, amongst these are 8' fluorescent tubes, white with internal reflector. We recently acquired a quantity of them, with suitable control gear and can, therefore, make a special offer as follows: if you buy 100 sets each set comprising 8ft tube, instant start ballast, current regulating capacitor, two bi pin tube connectors and two terry clips for holding the tube. Price £3+24p per set. Collected from our depot in Sussex or delivered to you—delivery charge at cost. We have only 1000 of these sets so this offer should be taken up quickly.

Mains Volt Drop Compensation Transformer. Another irritating thing which happens in cold weather is that the voltage drops and this can often drop to such a low point as to make soldering irons unusable or very slow in operation and also upsets the working of other instruments. Even in normal weather if you put a long line through to a distant workshop you may find that the voltage is low, due to voltage drop along the line so the compensation transformer may be a cheap way of restoring voltage to normal. The other alternative is to install a much heavier cable. Our 500w Auto Transformer will give voltage increases of 10, 20, 30 or 50 volts depending on which tapping you use. Price £4.50p+36p. Post £1.00+8p.

Cable Bargains. We have now sold out of all the 7029 3 core and also all the 1-5mm 3 core. We are also rapidly going through our stocks of 7029 3 core and earth and 1-5, 3 core and earth. You will recall that we made this offer of these cables at £9.50p+76p and £5.50p+44p. So if you have installation work planned then we advise you to buy early to avoid disappointment. We have most other sizes of cable in stock but of course these are not so popular.

Variable Inductance Choke. In an unsaturated core state a choke will oppose the flow of AC very much more than when its core is saturated, therefore, if the choke is built with a separate coil to deliberately saturate the core, a very small current of variable dimension will act as a voltage regulator. Use this for power dimming and a multitude of other purposes. We offer with a choke of 8 amps AC rating requiring 75mA DC control current at bargain price of £22.50p+£1.88p. Carriage £5.00+40p. Weighs approx. 60lbs. Panel Meter 0-1mA. Japanese made full vision pointer front, flush size £2.00+16p. Constant Voltage Auto Transformer for operating 110v equipment off our standard 230/240v mains. Input voltage can be plus or minus 20% output voltage will be a steady 115 volts, beautifully made by an American Company. Two models available 500w £35+£2.50p. Post £2+16p. 750w model £50+£4. Carriage £2+24p.

Tangential Blower, paddle type metal impeller driven by a powerful but quiet mains operated induction motor. These give a real blow (or suck) with the minimum of noise. The air outlet is 9 1/2" x 1 1/2" approx. so they are ideal for fitting into a cooker heat duct heater etc. Price £3.00+24p. Post 80p+6p.

Tubular Heating Element. Spiral wire element, wound on a porcelain tube approx. 1 1/2" dia. and 3 1/2" long. 500w rating at 240 volts flat tag connectors. Internal diameter of the porcelain tube is 1 1/2" and it is completely free from obstructions and live parts so this can be slipped over a tube to heat the contents of the tube or the tube could simply be used to support the element, for instance if this was being mounted in front of the tangential blower mentioned above. Price 60p+4p.

Rectangular Hot Plate. Polished aluminium panel with ridged top and angles underneath to strengthen it. This is approx. 10" x 4 1/2" of flat plate. Beneath plate is 100w element and sensor switch which will maintain the surface of the plate just too hot to touch. With leads and tags. This is ideal if you are making up a fitted warmer or for an airing cupboard etc. Price 75p+6p. Post 20p+4p.

Miniature Mains Transformer, standard primary centre tap secondary giving 4.5v-0-4.5v 200 mA. Price £1.50p+12p.

Mains Transformer 200vlt ± amp. Upright mounting standard, primary centre tapped and 53ing feet. Price £1.50p+19p.

Humidity Switch, American made by Ranco, their type No. J 11. The action of this device depends upon the dampness causing a membrane to stretch and dryness causing it to contract. The stretching of the membrane through the dampness will trigger a sensitive microswitch. The actual point of switching is adjustable by a screw within the device. It is quite sensitive breathing on it for instance will switch it on. The rating of the micro-switch we understand is 3 amp 250v AC. Overall size of the device approx. 3 1/2" long 1" wide and 1 1/2" deep. Price 60p+5p.

Charge/Discharge indication meter. This is a heavy panel mounting instrument made originally for the G.P.O., rather old design but still we feel we fill an urgent need. Basically the operation of this depends upon a Mercury motor which revolves clockwise or anti clockwise depending upon whether the batteries are charging or discharging. A pointer shows the state of charge of the batteries at any time. Also fitted within the instrument are auxiliary contacts which could be used to operate alarm lamps etc. Price £4.50p+36p. Post £1.00+8p.

everyday electronics

PROJECTS.
THEORY...

IDEAS AROUND

Readers' suggestions for projects continue to arrive at our office in a steady flow. This is a good sign for it indicates a lively interest and frequently a very fertile imagination on the part of those who write.

All ideas are looked at carefully, and those judged to be viable are actively pursued. Our investigations do not always come up trumps, however. Some suggestions will not stand our three-part test which involves these considerations: (1) technical feasibility, (2) practicability and (3) cost to the builder.

Sometimes it happens that alternative approaches can be made to a problem. An example is given by the recent projects for use with tumble dryers. Last month's Tumble Dryer Alarm was a spin-off from an earlier design and had the advantage of being battery operated, simpler in design and less expensive to build. The original Tumble Dryer Controller (published in January) offered automatic control of the mains supply to the machine—a valuable facility but one that had to be paid for of course, both in cash and in the more demanding nature of the construction work because of the more complex design.

Some readers may feel that their particular suggestions take a long time to materialise. But never give up hope! For instance the Model Railway Controller is an answer to a model railway enthusiast whose comments appeared in EVERYDAY ELECTRONICS exactly a year ago. At that time we promised that some designs for

*Our May issue will be published on Friday, April 15
See page 177 for details.*

model railways would be forthcoming. In this case, the longer-than-normal delay in publishing was not due to design problems, but simply because of prior commitments in our available space.

We strive to give every specialist interest a fair crack of the whip. But because electronics is so universal in use, the range of possible applications is immense and it is inevitable that suggestions have to take their turn in the queue.

BUYING COMPONENTS

Isn't this remarkable? A vast number of electronics constructors will never have stepped across the threshold of an electronic component shop—and as likely as not they have never even seen such a shop. The answer of course is Mail Order. Without this service thousands of constructors would be deprived. Despite the odd stories one does hear from time to time, mail order works very well.

The *Guide To Component Buying* which comes as a special supplement in this issue, gives a listing of component retailers who advertise in EVERYDAY ELECTRONICS and indicates the kind of components they normally stock. A useful reference for all constructors, both those who order by post and those who can indulge in personal shopping. For the privileged latter—a reminder also of those shops that are in their own neighbourhood or within easy reach.



EDITOR F. E. Bennett ● ASSISTANT EDITOR M. Kenward ● TECHNICAL EDITOR B. W. Terrell B.Sc.
ART EDITOR J. D. Pountney ● P. A. Loates ● K. A. Woodruff
ADVERTISEMENT MANAGER D. W. B. Tilleard ● P. Mew

© IPC Magazines Limited 1977. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Editorial Department: Everyday Electronics, Fleetway House, Farringdon Street, London EC4 4AD. Phone 01-634 4452.

Advertisement Departments: Everyday Electronics Advertisements, Fleetway House, Farringdon Street, London EC4 4AD. Phone 01-634 4504. Everyday Electronics Classified Advertisements, Kings Reach Tower, Stamford St., London SE1 9LS.



...EASY TO CONSTRUCT
...SIMPLY EXPLAINED

VOL. 6 NO. 4

APRIL 1977

CONSTRUCTIONAL PROJECTS

MODEL RAILWAY CONTROLLER Provides realistic speed control by F. G. Rayer	162
CAR BURGLAR ALARM Protect your vehicle and equipment by A. D. Huff	165
CONTINUITY TESTER A versatile piece of test gear by A. Irwin	174
PAPER/SCISSORS/STONE GAME Modern version of an old game by A. W. Gibbs	183

GENERAL FEATURES

EDITORIAL	160
DOING IT DIGITALLY Part 7 Pulse generator, wired OR, Schmitt trigger, and card reader by O. N. Bishop	168
SHOP TALK Component buying and catalogues by Mike Kenward	173
COUNTER INTELLIGENCE A retailer's comments by Paul Young	175
FOR YOUR ENTERTAINMENT ILEA TV, VAT and Space Junk by Adrian Hope	176
YOUR CAREER IN ELECTRONICS Television Capital Equipment by Peter Verwig	178
JACK PLUG AND FAMILY Cartoon	181
PHYSICS IS FUN Sound by Derrick Daines	182
RAPIER MISSILE SYSTEM by G. A. G. Brooke	186
READERS' LETTERS	190
ABBREVIATIONS	191
PROFESSOR ERNEST EVERSURE The Extraordinary Experiments of. by Anthony J. Bassett	192
DOWN TO EARTH Noise by George Hylton	196
PLEASE TAKE NOTE	196

SPECIAL SUPPLEMENT

GUIDE TO COMPONENT BUYING

Between 176 and 177

BACK NUMBERS, LETTERS AND BINDERS

We are unable to supply back copies of Everyday Electronics or reprints of articles and cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, at the address shown opposite.

Binders for volumes 1 to 6 (state which) are available for £2.10, including postage, from Post Sales Department, Lavington House, 25 Lavington St., London SE1 0PF

FREE
NEXT MONTH
MATRIX MARKER

Don't miss your issue—see page 195!

control from a standstill to full speed.

CONSTRUCTION

The prototype case was made from 6mm plywood for the front, back and sides and 4mm plywood for the top and bottom such that the control panel was on top and sloping from the rear to the front. Any convenient metal or insulated box could be used.

It is a good idea to provide some ventilation holes in the case back and bottom, and stand the case on four small rubber feet.

The layout of the components within the case and complete wiring up details are shown in Fig. 2. The transformer is bolted to the back of the case. One side carries two output sockets, and a strap of metal formed so that it holds the lamp, which sits under a coloured lens in the control panel.

Anchor the mains lead at a tag strip as shown, taking the earth lead (yellow-green) to the d.c. negative line (which will include the metal box, if used).

Most items are supported by a tag-strip, which is bolted at X-X. Four 1N4001 diodes could be used instead of the full-wave bridge rectifier if these are more readily available. Diode D2 has a band at the positive end, and the larger diode D1 tapers to indicate positive.

The thyristor anode stud was fitted with a solder tag, and then soldered to the tagstrip as shown. No difficulty arises in fitting items here with the tagstrip already bolted to the side of the case. (Pinning for CSR1 is shown in Fig. 1.)

The transformer used was tapped for 2, 6 and 12 volts charging, at 1 ampere, and delivers approximately 17 volts peak. A 12 volt 12 watt lamp at LP1 will limit current to 1 ampere, if derailment or other circumstances result in a short circuit, which is indicated by the indicator lamp fitting above LP1 being illuminated.

Assuming that any such mishap will soon be cleared, a 21 watt lamp can be used here. Another alternative to the 12 watt lamp is a 10 watt festoon bulb, which does not of course cause any temporary overload. A lamp of unnecessarily low wattage should not be used.

There is some latitude in components, but it is wise to fit a thyristor and D1 rated at over 1A, even though this is the normal

maximum load for the controller.

Speed controller, VR1, should have a large control knob and it must not be overlooked that S2 needs a central off position which avoids any short-circuit of power.

RUNNING

It should be found that VR1 allows the train to be started and run at a very low speed if wished, and that tractive effort is good at low speed. The engine is less likely to stall, when running very slowly and encountering additional friction or load, than when a series resistance controller is used.

Track and wheels should be clean, as at low speed there is no momentum to carry the engine over any dirty spots where contact is poor. □

Components

Capacitors

- C1 25 μ F elect. 25V
- C2 12 μ F elect. 25V
- C3 470 μ F elect. 25V

Semiconductors

- D1 1N4001
- D2 1N5400
- D3-D6 2A 50V bridge rectifier
- CSR1 CRS3/05 or similar 3A 50V thyristor

Miscellaneous

- S1 mains on/off toggle
- S2 d.p.d.t. with centre off position
- T1 mains primary/12V 1A secondary transformer
- VR1 1k Ω 1 watt lin. potentiometer
- LP1 12V 12W lamp with coloured lens
- FS1 200mA fuse
- SK1, 2 insulated screw terminals 1 red, 1 black (2 off) Tagstrip: 10 way and 3 way; mains cable; BA fixings; connecting wire; fuseholder for FS1; case.




See
**Shop
Talk**

Railway Controller

A simple unit providing realistic speed control.
by F. G. Rayer

Model Railway Controller

Fig. 2. Construction and wiring of the Model Railway Controller.

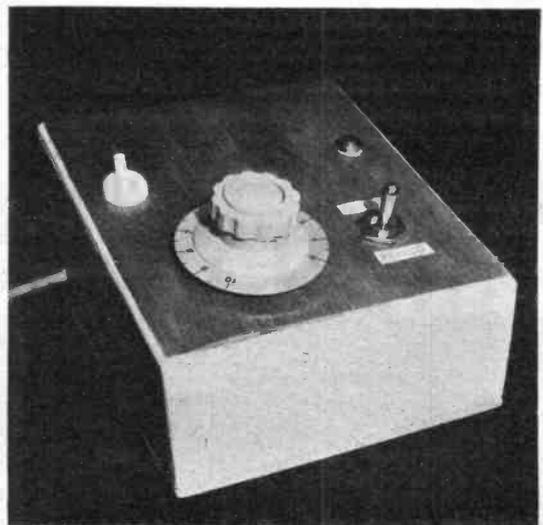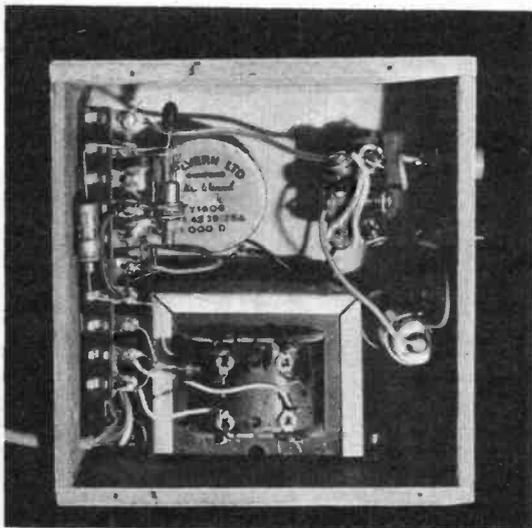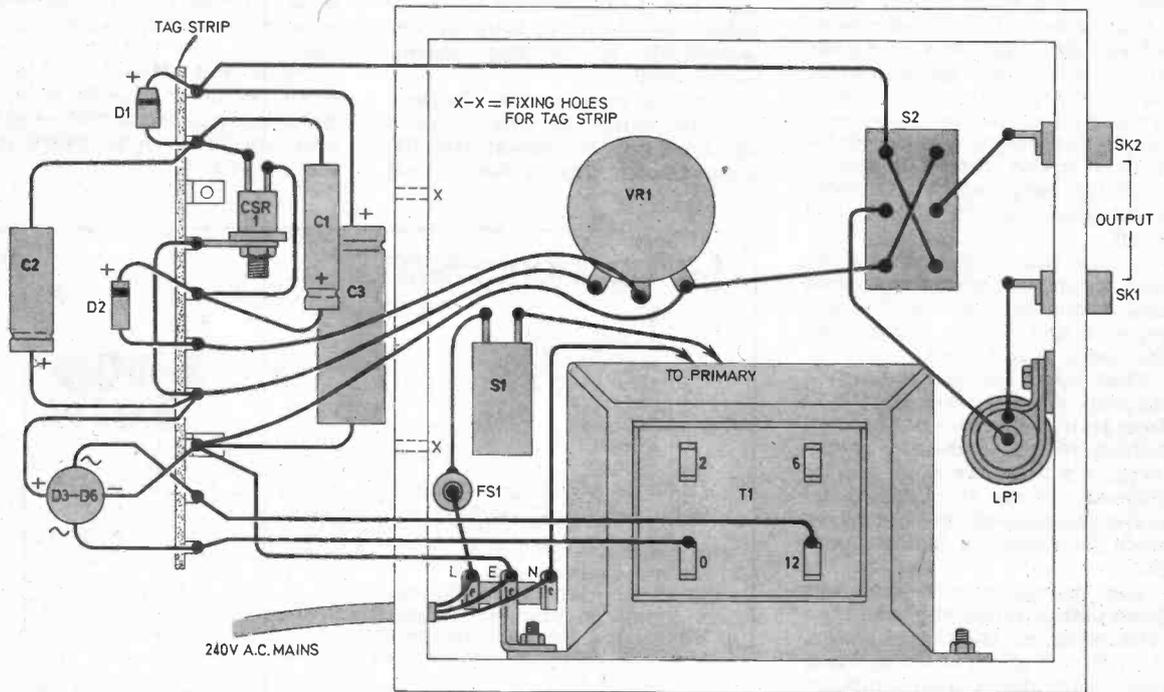

WITH crime on the increase, and the cost of cars and "in-car" stereo equipment, radios etc, also on the increase, a cheap effective car alarm is essential for the everyday motorist.

If a car is fitted with a trembler switch in the engine compartment and microswitches on the doors and boot, the following protection is afforded.

Anyone tampering with the wheels, spotlights and such will set off the alarm (car horn) due to the trembler switch. The alarm will sound off and reset itself.

If the thief opens the car door the horn will sound, two things may happen. If he runs away leaving the door open the horn will continue to sound until the battery is exhausted, the door is closed or the alarm switched off.

It was thought disadvantageous in the design to have the horn switch off automatically whilst the door is left open. If the would-be thief closes the door in an effort to stop the horn sounding, it will only switch off after the pre-set time has elapsed.

The time that the horn will sound has been designed to be between 5 and 25 seconds. In fact with one component change the range can be extended to be between 12 and 45 seconds. Longer times than these should not be required for a car alarm.

An automatic turn off saves having to switch the alarm off if it is accidentally triggered by children for example.

With this design the driver will not return to his car to find a flat battery if the alarm has been sounded in his absence.

CIRCUIT

The complete circuit diagram of the Car Burglar Alarm is shown in Fig. 1. It is simply a monostable feeding a relay driver. The monostable is composed of TR1 and TR2 and associated components. With the microswitches and trembler open circuit, and the unit turned on, TR1 is fully on and TR2 is fully off. There is no drive to TR3 hence the relay is not energised.

The circuit will remain in this state until a microswitch or the trembler is caused to short D1 cathode to ground. Transistor TR1 is then caused to switch off and TR2 on thereby supplying drive to TR3 and causing the relay to be energised; the relay contacts close and supply power to the horn. The horn will continue to sound even though the microswitch or trembler become open circuit and will remain in this state until capacitor C3 discharges through the resistance formed by (R3+VR1), so that the potential on the base of TR1 exceeds that on TR2 when the circuit will revert to its original state i.e. TR1 on TR2 off.

Thus the relay on time is controlled by the value of VR1 and C3. An approximate formula for the on time of the relay is $T=0.7 \times C3 \times (R3+VR1)$ seconds where C3 value is in microfarads and resistance is in ohms. It can be seen that doubling the value of C3 doubles the on time.

SOME ASPECTS OF THE CIRCUIT

Capacitor C2 is incorporated to prevent the ripple on the +ve supply line (caused by the horn operating), from prematurely resetting the monostable. The back e.m.f. from the horn is prevented from re-triggering the unit by the inclusion of D4.

Diode D3 is used to suppress the back e.m.f. developed across the relay coil when de-energised. Diode D2 is included to limit the reverse bias on the base/emitter junction of TR1 due to the large negative voltage present on C3.

If more than one horn is connected to the circuit the value of the 5 amp fuse will have to be increased. Also a relay with a higher contact current rating will have to be used. It is a good idea to check the current consumption of your horn circuit before building this unit and selecting the relay to suit if greater capacity than 5A is required.

CONSTRUCTION AND FITTING TO CAR

The prototype unit was constructed on a piece of 0.1 inch matrix stripboard measuring 19 strips by 39 holes. The layout of the components is shown in Fig.2 as are the breaks to be made on the underside of the board. The holes to take the relay tags should be enlarged to suit the size of the tags. There are two copper strips that need to be reinforced to carry the current to the horn. This is easiest done by soldering

car burglar alarm

By A. D. Huff



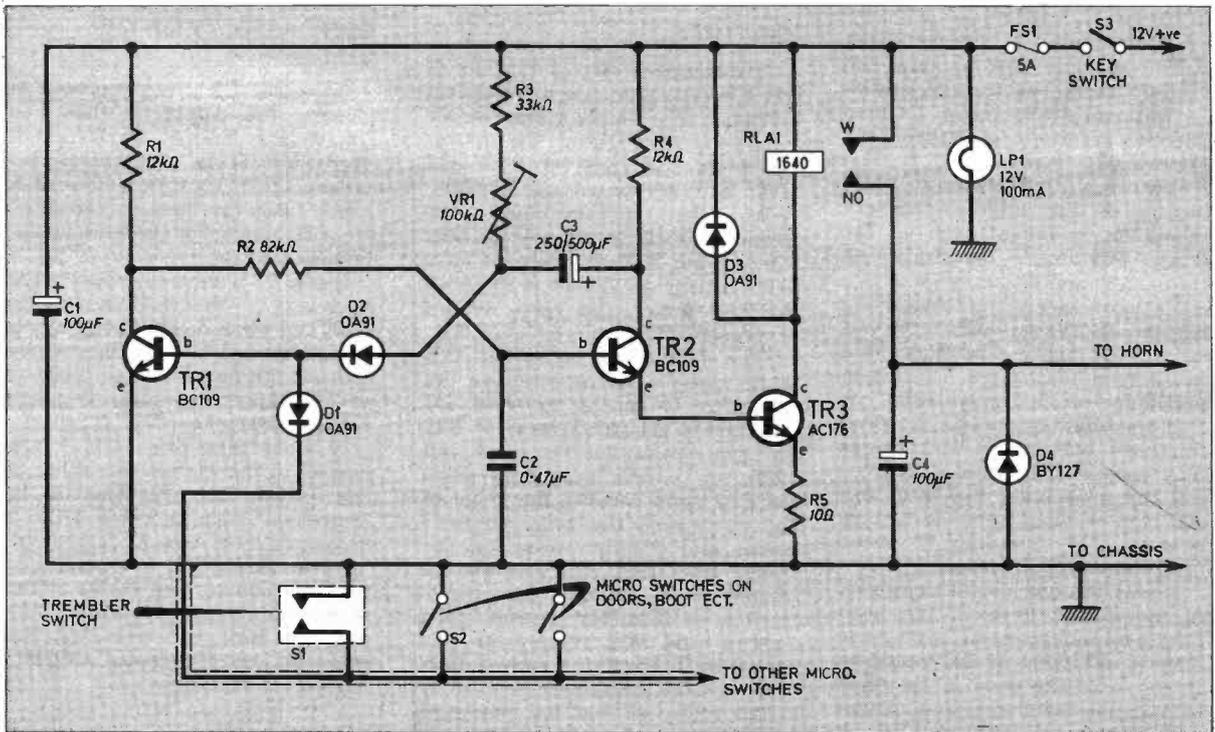


Fig. 1. The Complete circuit diagram of the Car Burglar Alarm.

Components

Resistors

R1 12k Ω
 R2 82k Ω
 R3 33k Ω
 R4 12k Ω
 R5 10 Ω

All $\frac{1}{4}$ W carbon $\pm 10\%$

Potentiometer

VR1 100k Ω horizontal preset

Capacitors

C1 100 μ F 25V elect.
 C2 0.47 μ F plastic or ceramic
 C3 250 μ F 25V elect.
 C4 100 μ F 25V elect.

Semiconductors

TR1 BC109 silicon npn
 TR2 BC109 silicon npn
 TR3 AC176 germanium npn
 D1 OA91
 D2 OA91
 D3 OA91
 D4 BY127

Miscellaneous

FS1 5A with in-line fuseholder
 RLA1 12V 1640 ohm coil with 5A normally open contacts (Doram 349-131)
 S1 Trembler type switch
 S2 Microswitches (number to suit)
 S3 Key operated switch
 LP1 12V 100mA m.e.s. with holder and lens to suit
 Stripboard: 0.1in. matrix 19 strips x 39 holes; robust case; screened lead; 5A connecting wire.

FOR
GUIDANCE
ONLY

ESTIMATED COST
OF COMPONENTS *
excluding V.A.T.

£4.80

excluding switches
and case

SEE
SHOP
TALK

short lengths of stout tinned copper wire to the tracks as indicated.

The usual practice should be observed in assembling the components, that is, resistors and capacitors, link wires, flying leads, followed by the semiconductors (use a heatshunt when soldering these in place).

Screened cable should be used for connecting the microswitches to the component board to reduce the possibility of the alarm being triggered by r.f. transmitted from the wiring of passing vehicles.

The placement of the completed unit within the car will be a personal choice, but the author recommends that for long time reliability the unit should be fitted inside the car and not in the engine compartment. It is also advisable to fit the completed component board inside a robust case such as an aluminium diecast box.

Obviously the key operated switch will have to be mounted on the car bodywork if you don't want the alarm to sound as you are getting back into the car so that it can be "de-activated" before getting into the car. For obvious reasons the wiring to the horn and battery from the unit should be well concealed. □

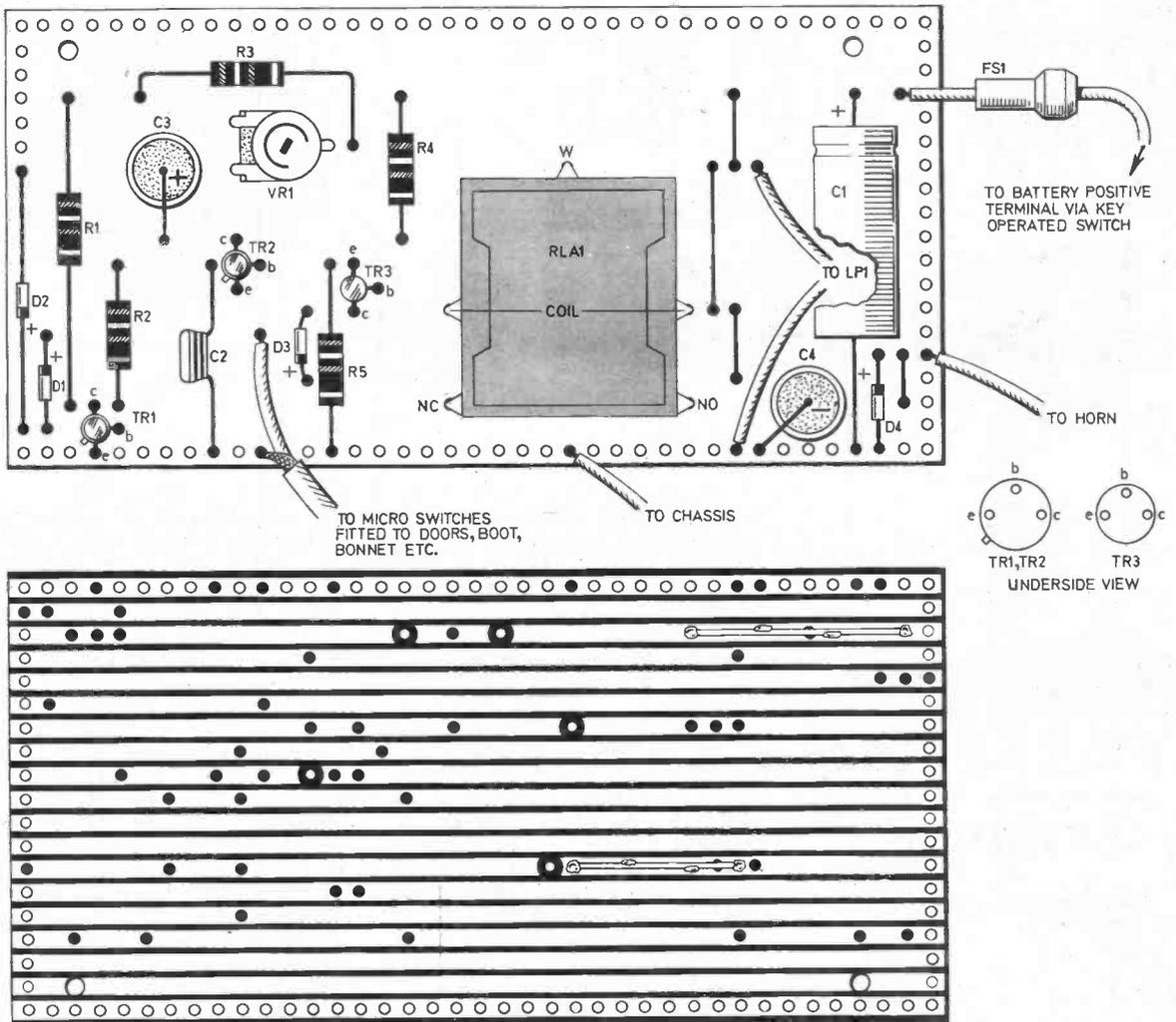


Fig. 2. The layout of the components on the topside of the stripboard and the cut-outs to be made on the underside and wiring details to the car. Note the stout copper wire soldered along the strips to enable high current flow.

EVERYDAY ELECTRONICS EASIBINDER

Create your own **EVERYDAY ELECTRONICS** Library. Bind your magazines in the **EASIBINDER**

Attractively bound in orange Balacron with the title blocked in black on the spine, the Easibinder is designed to hold 12 copies of **EVERYDAY ELECTRONICS**.

In addition to the title, the current (or last) Volume No. and date is blocked on the spine, but for any of the previous volumes a set of transfer figures is supplied.

When ordering please indicate which Volume is required.

Price £2.10 including postage and V.A.T.

Note the details on a sheet of paper if you do not wish to cut the magazine.

Send your order with remittance to:

To Post Sales Dept., I.P.C. Magazines Ltd., Lavington House, 25 Lavington St., London S.E.1 0PF
 I enclose p.o./cheque value..... for binders at £2.10 each for **EVERYDAY ELECTRONICS**.
 Vol. Nos
 Name
 Address
 Date

Doing it Digitally...

Part 7

By O. N. Bishop

THREE new circuits are discussed in this month's section: a single pulse generator; the WIRED-OR connection and the Schmitt trigger. We will also look at two useful input devices which can be made quite easily from a piece of stripboard some drawing pins and paper clips.

the heart of the circuit consists of two NOR gates. One of the gates is connected to form an INVERTER. Normally the input is low which causes the output of the INVERTER to be high and hence the output of the second gate to be low. In this state the voltage across the capacitor C1 will be zero.

A SINGLE PULSE GENERATOR

The single-pulse generator is a useful circuit which produces a short high pulse every time its input changes from low to high. A typical use for this circuit might be after a light operated switch whose output goes from low to high at dusk. The single pulse may then be used to clock a flip-flop or some other counting device.

The basic circuit is shown in Fig. 7.1a and it can be seen that

If the input is now taken high (Fig. 7.1b) the output of the INVERTER will immediately go low. The voltage across C1 will gradually rise towards the high input but for a certain time (determined by the values of C1 and R1 and the switching threshold of the gate) gate IC1b will see a low on both its inputs and so its output will be high.

Eventually C1 will charge to such a voltage that it presents a high input to gate IC1b (Fig. 7.1c) and the output will there-

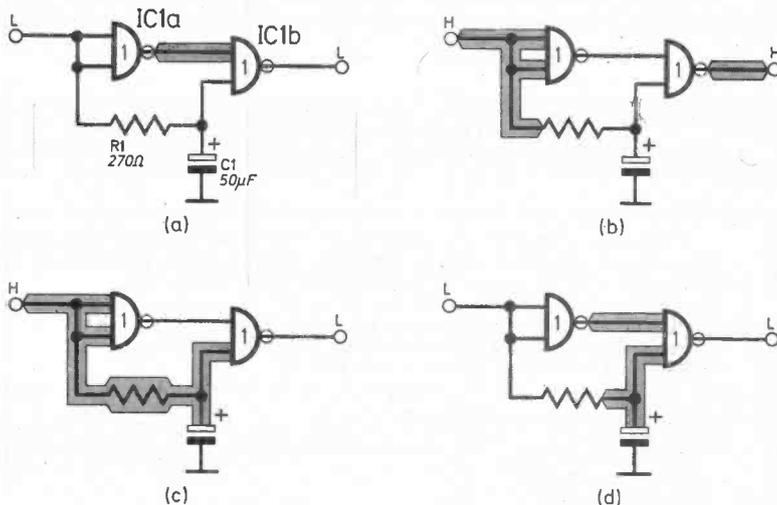


Fig. 7.1. Single pulse generator (a) shows the circuit before it is activated. The shaded areas indicate a high level. (b) shows the state of the circuit just after the input has gone high (c) shows the state after the capacitor has had time to charge and (d) shows the circuit when the input returns to low.

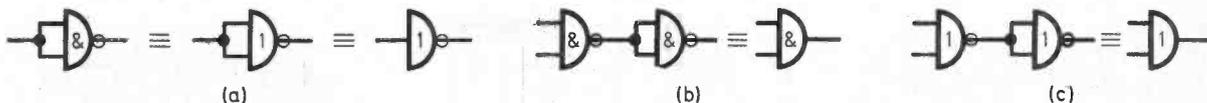


Fig. 7.2.(a) Using a NAND or NOR gate as an INVERTER (b) Combining two NAND gates to form an AND (c) Two NORs forming an OR

fore go low again.

If the input now goes low the output will be unaffected since the INVERTER will immediately present a high input to gate IC1b keeping its output low. Capacitor C1 will now discharge through R1 until its voltage falls to that equivalent to a low input and sufficient time must be allowed for this to happen before the generator is once again ready for action.

The length of the pulse can be varied by changing the value of C1. With the value shown the pulse length will be about five milliseconds.

WIRED-AND CONNECTION

On looking through the list of 7400 integrated circuits it will be found that there are many containing NAND gates and quite a few containing NOR gates. Most logic combinations can be formed with just these two types but sometimes other functions such as INVERT, AND and OR are required.

If only one of these gates is required it is easy to make them from NANDS and NORs and this saves the trouble of buying a package containing four gates.

In Fig. 7.2 various functions which can be obtained from combinations of NAND and NOR gates are illustrated. If several AND gates are required then it is wise to buy the 7408 i.c. which con-

tains four such gates and if several INVERTERS are needed then one would use the 7404 i.c. which contains six.

Rather than waste two NAND gates just to make a single AND gate, there is a way of using just a few discrete components to achieve the required result.

Remember that TTL (*transistor transistor logic*) gates work by drawing current from the following gate when the input is taken low. In other words we can say that if no current is being drawn from the input of a gate then that input must be high.

Referring to Fig. 7.3, input to gate D will be high if no current is drawn from the gate through any of the diodes D1 to D3. No current can be drawn from the gate through the resistor since it is connected to the positive supply—it is called a pull-up resistor as it “pulls up” the voltage on the input when no current flows through the diodes.

Now if the outputs of any of the gates A to C goes low (Fig. 7.3b) the respective diode will conduct and the voltage at the input to gate D will fall to a value equal to the forward voltage drop across a diode (about 0.6V) which is seen by the gate as a low input and hence current flows from the input. (This assumes that the voltage at the output of a gate when it is low is zero which is not exactly true,

there always being about 0.2V present.)

From this description it can be seen that the input to gate D will only be high if the outputs from gates A to C are all high (Fig. 7.3c)—hence D1 to D3 and R1 form an AND gate.

It is an unfortunate fact that diodes are as expensive as gates so it is not an economic proposition to use this method of making AND gates if many are needed. The use of 7408 i.c.s means that one is restricted to two-input gates. Happily there is a way of forming AND gates with as many inputs as required without using any gates!

Suppose one has a circuit with a number of outputs from NAND gates and one wishes to AND their outputs to give a single output which only goes high when all the outputs from the gates are high. The outputs could be combined with a diode gate as described above but if, instead of ordinary type 7400 NAND gates, one uses a special type of NAND gate then no diodes are required—the outputs are simply joined together with wire, the common connection being taken to the positive supply through a resistor.

This method of connecting the outputs of special gates with wire to form AND gates gives rise to the name “WIRED-AND”. The special i.c.s containing these gates

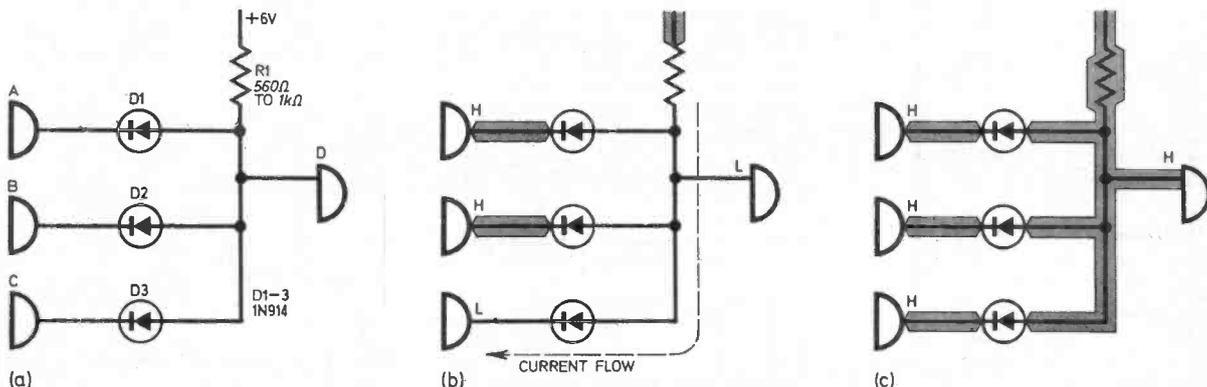


Fig. 7.3.(a) An AND gate using three diodes and a resistor connected to the output of three gates. Gates A, B, C and D can be any type of gate. (b) Current flow when the output of one of the gates is low (c) State of the circuit when the output from all gates are high.

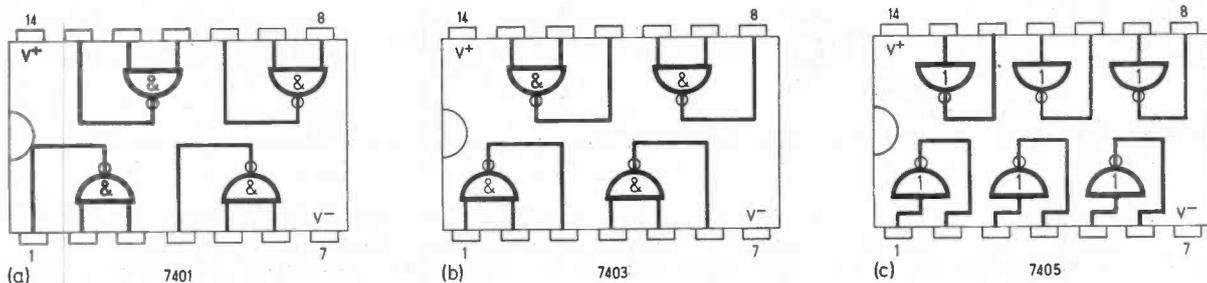


Fig. 7.4. Pin connections for three types of open collector i.c.s. (a) the 7401 quad two-input NAND gate (b) the 7403 quad two-input NAND gate and (c) the 7405 hex INVERTER.

are usually referred to by the manufacturers as "open collector" gates.

The internal connections of three i.c.s containing open collector gates are shown in Fig. 7.4. The 7401 is a quad two-input open collector NAND gate i.c. as is the 7403. The pin connections of the 7403 are identical to those of the 7400 but the 7401 is different. Also available is the 7405 which contains six INVERTERS with open collector outputs which can be WIRED-AND connected.

When wired together the outputs of the 7405 are ANDed but if the inputs of these gates are considered it will be seen that if any one or more of them is high its output is low and the ANDed output is therefore low. This takes us once more to NOR. Thus a NOR

gate with many inputs can be formed using the 7405 i.c. (see Fig. 7.5b).

This type of gate is sometimes seen referred to as a WIRED-NOR gate for obvious reasons. By placing an INVERTER after the WIRED-NOR gate, a WIRED-OR gate is obtained.

It can be seen that a gate is not always what it appears to be—a NAND gate may in fact be part of an INVERTER and an INVERTER may be part of an OR gate! When in doubt either build the circuit on the experimental board and test it or write the truth table for the gate.

It is permissible to WIRE-AND as many as eight outputs together using 7401 or 7403 or 7405 i.c.s and the ANDed output can be used to feed up to seven inputs.

One method of overcoming the problem is to use a circuit called a Schmitt trigger. An integrated circuit type 7413 is available which contains two four-input NAND gates with a rather special property. Its pin connections are shown in Fig. 7.6.

The Schmitt trigger NAND gates differ from the ordinary NAND gate in that the switching voltage differs depending on whether the input is going from high to low or low to high.

As the voltage rises from zero the gate will switch at about 1.7V, the output then going low. If the input voltage is now reduced nothing will happen when it passes through 1.7V. In fact the voltage has to fall below about 1V before the output of the gate will go high. The gate switches at 1.7V "on the way up" and 1V "on the way down."

A slowly changing input is shown in Fig. 7.7a with the output states of the gate. Even with slowly changing inputs the Schmitt trigger produces an out-

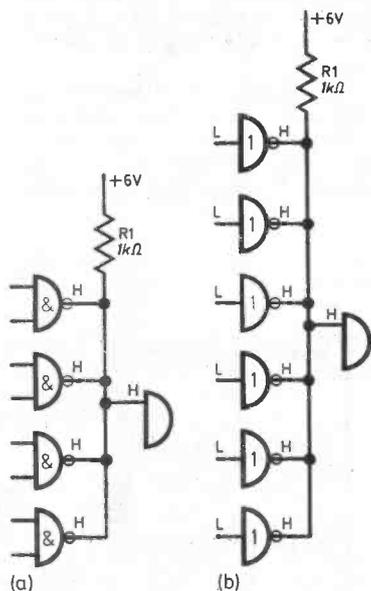


Fig. 7.5. (a) Type 7403 or 7401 i.c.s. wired together to form a WIRED-AND gate (b) Gates in a 7405 wired together form a WIRED-NOR gate.

THE SCHMITT TRIGGER

One of the problems of operating counters and flip-flops is that they require clock pulses with very short rise and fall times. This is because with a slowly changing clock pulse the input to a gate may be biased into a region of uncertainty where the gate changes from being an on/off switch into an amplifier with very high gain. This can in turn lead to oscillation which can cause serious malfunctioning of a system.

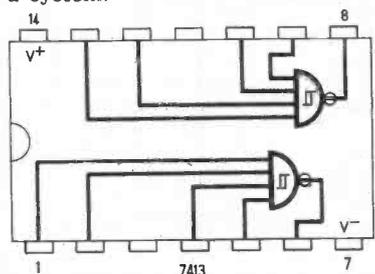


Fig. 7.6. Pin connections of the 7413 four-input Schmitt NAND.

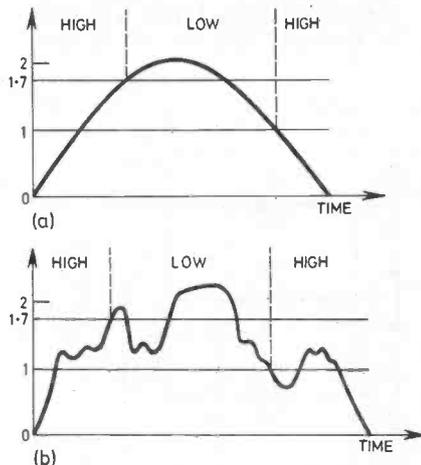


Fig. 7.7. (a) The output of the 7413 with a slowly changing input (b) the elimination of noise using the Schmitt.

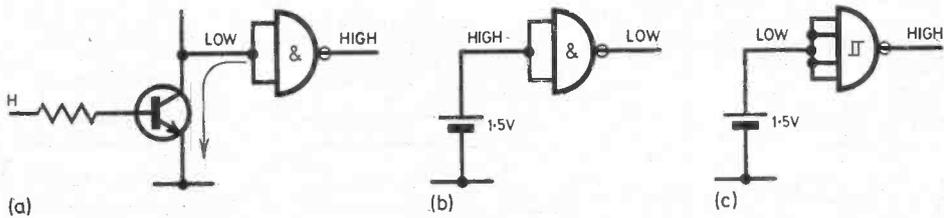


Fig. 7.8(a). A transistor connected to an ordinary gate provides a path for current to ground (b) A battery connected to an ordinary gate does not provide a current path to ground. (c) A 1.5V battery connected to a Schmitt gate acts as a low input

put with fast transitions.

The Schmitt trigger is also useful for removing "noise" from waveforms as illustrated in Fig. 7.7b. The input is a waveform which wanders up and down rather than switching from on to off directly. This "wandering" would cause many pulses to be generated by an ordinary gate but the Schmitt trigger only produces one transition.

There is another use for the 7413 because it depends only on its input voltage to make it change state. Other i.c.s need to have a certain type of input—one that will let current flow from the gate to ground. Even a slight voltage at the input will be equivalent to a high input, as shown in Fig. 7.8.

The Schmitt will treat any input voltage below 1V as low and "on the way up" and will treat any voltage below 1.7V as low. There is no need to provide a path to ground.

This means that the gate can be operated by devices other than transistors or other gates or direct connection to positive or ground.

For instance the input can be from a potentiometer connected across a 6V battery as shown in Fig. 7.9a. It is possible to connect the spindle of the pot to a working model using a pulley or gear-wheel so that as some part of the model moves it produces a

logic output.

Since the light operated switch shown in Fig. 7.10 using the ORP12 is really a potential divider the ORP12 can be connected directly to the 7413 Schmitt gate to give a clean changeover as the light increases or falls. Because the switching levels of the Schmitt vary according to whether the input is on the way up or down, the light level for "on" will be different to that for "off". This can be an advantage for example, if the device is being used to turn a radio on at sunrise a passing cloud will not turn it off again.

The Schmitt can also be used to detect when the voltage of a battery falls below a certain

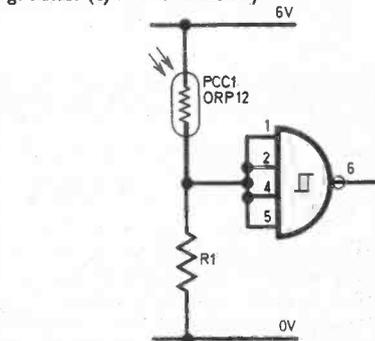


Fig. 7.10. The light operated switch described in an earlier part may be used to drive the Schmitt

level. Suppose the battery must not fall below 5.1V. The circuit is shown in Fig. 7.11a.

The Zener diode stops the voltage to the potential divider from

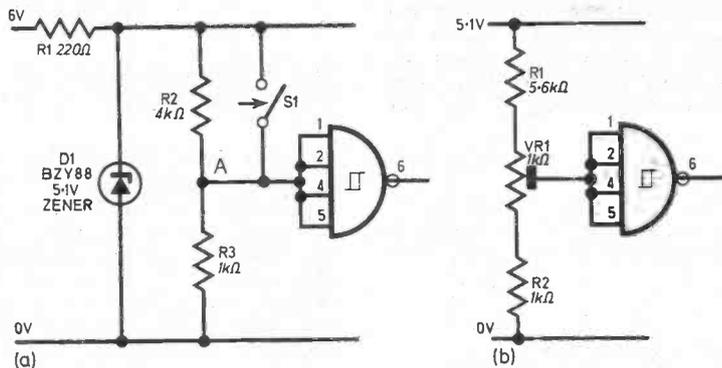


Fig. 7.11.(a) Circuit for a low battery indicator. The potential divider can be made from a preset and two resistors for setting the switching point, as at (b).


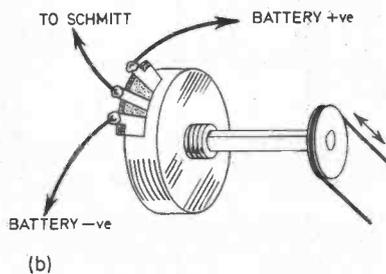


Fig. 7.9.(a) The input to the Schmitt can be from a potentiometer connected across a 6V battery. The potentiometer can be part of a working model as shown in (b).

rising above 5.1V but if the battery goes flat this voltage will fall below 5.1V. When the voltage is 5.1V the voltage at point A will be one fifth of this i.e. nearly 1V.

To activate the low battery indicator the switch S1 is closed which applies a high voltage to the Schmitt causing its output to go low. The switch is then released. Now if the voltage ever falls below 1V the output of the gate will go high indicating a low battery.

Components

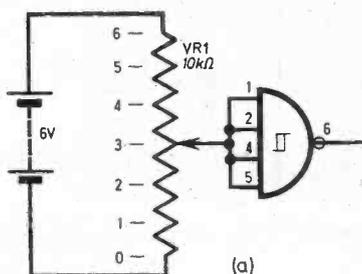

Single Pulse Generator

R1 270Ω ¼W
C1 50μF elect. 6V
IC1 7402

Wired—AND

R1 560Ω to 1kΩ ¼W
D1-D3 IN914 (3 off)
IC1 7403
IC2 7401
IC3 7405

Schmitt Trigger

R1 5.6kΩ
R2 1kΩ
VR1 10kΩ lin.
VR2 1kΩ preset
D1 5.1V 400mW Zener diode
IC1 7413

Keyboard/Card Reader

Stripboard: 0.15in. matrix 25 holes
x 16 strips; drawing pins (10 off);
large paper clips (10 off); terminal
pins (20 off).

The circuit of Fig. 7.11a shows two fixed resistors making up the potential divider. In practice it might be hard to find two resistors with a ratio of exactly four to one and this, together with the fact that the Schmitt may not trigger at exactly 1V makes the use of a preset potentiometer as shown in Fig. 7.11b more apt. The preset can then be adjusted so that the Schmitt triggers when the voltage of the battery falls below 5.1V.

This is just one example of the use of the Schmitt trigger. It has applications in many other circuits as a voltage level detector.

SIMPLE KEYBOARD

It is very useful to have a set of keys ready made especially when working with flip-flops. The set of keys to be described here is easy to construct and gives five switches very cheaply.

The keyboard is assembled on one half of a piece of 0.15in matrix stripboard as shown in Fig. 7.12. The card reader to be described next uses the other half of the board. If required the board could be sawn in half and the two units used separately.

The method of construction is similar to that used with the paper tape reader described last month. The drawing pins are soldered into the board as shown


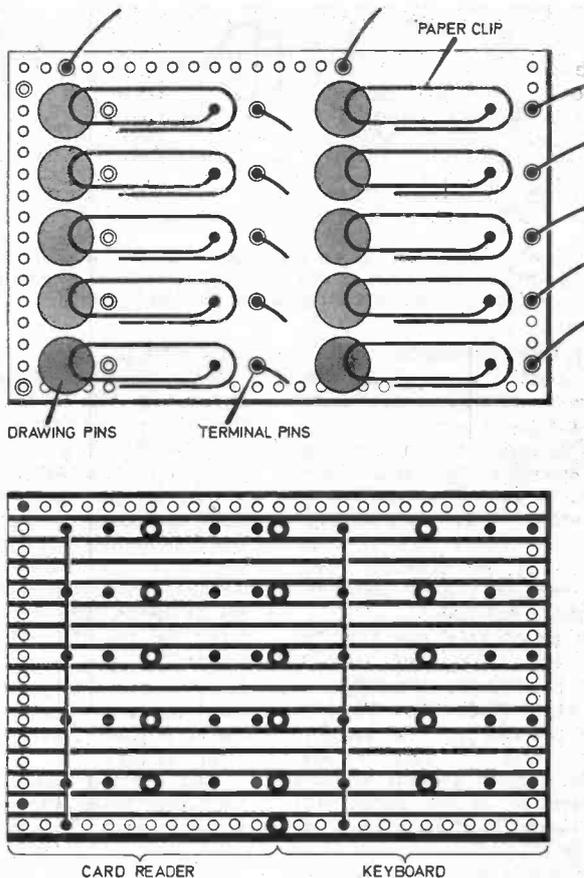


Fig. 7.12. Layout of the card reader (left) and keyboard (right) on the 0.15in matrix stripboard. Note the cuts in the strips under the board. The board can be sawn in half if the two units are to be used separately.

and their ends cut off. They are all joined together and the wire is taken to a terminal pin at the side of the board. The paper clips are then bent as shown and placed in position on the board. A piece of Blu-Tack or Plasticene is then used to hold the clip in position while it is soldered. The clip must

lie so that it is slightly above the drawing pin, only making contact when it is pressed.

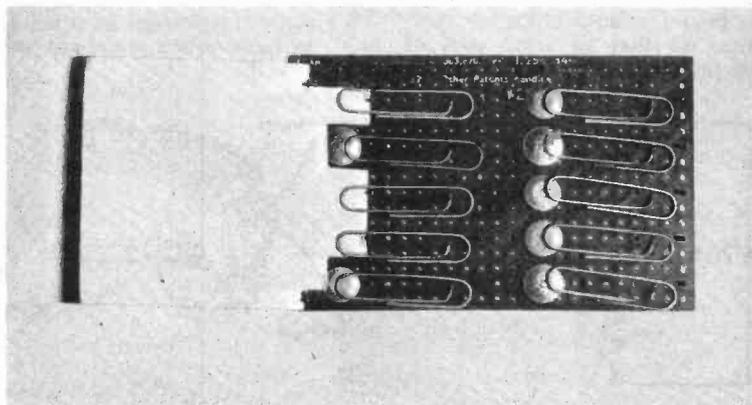Keys or switches made in this way are called "push to make" switches: when they are pressed they make contact; when pressure is released they open.




Photograph of the keyboard and card reader.

CARD READER

The card reader is similar to the keyboard except that the keys are normally touching the drawing pins. When a card is pushed between the keys and the drawing pins, some contacts (depending on how the card is cut) are broken (see Fig. 7.13). The method of construction is the same but when soldering in the paper clips hold them firmly in contact with the drawing pins.

Fig. 7.13. A card inserted into the card reader. It has been cut so as to produce a high on pins two, three and five.

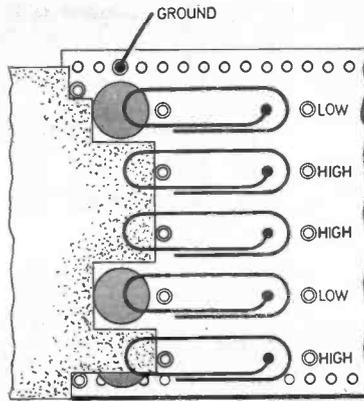


As with the keyboard, join the drawing pins together and to a terminal pin at the side. If the keyboard is on the same piece of board as the card reader, make sure the cuts in the copper strips are made as shown.

Some of the pins in the card reader are not for electrical connections but serve merely to guide the card in straight.

The card reader can serve as a keyboard if required since contact will be broken if the paper clips are pressed at the end farthest from the drawing pin.

To be continued

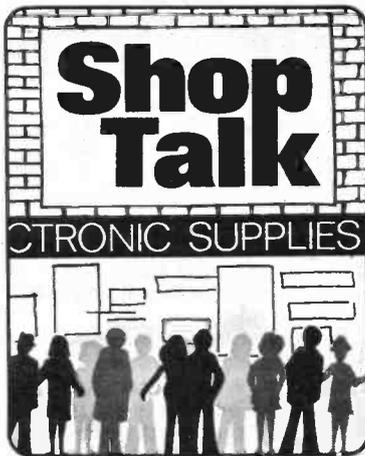

By Mike Kenward

New products and component buying for constructional projects.

FOR the first time in the history of Marshall's they have produced a second catalogue (now available) within 12 months. This has been necessary mainly due to the "unprecedented increase in component prices, stemming partly from the falling pound, but also from an all round rationalisation of prices and product ranges from our main suppliers," more about this aspect later. The new catalogue also includes an additional 500 lines which come mainly from National Semiconductors, these lines include various microprocessor items.

It was unfortunate that the very day we received the new catalogue we also received the sad news that Mr. Marshall had died a few days earlier. His firm have always been helpful and provided an excellent service which we are sure will be continued by his able staff.

Rationalising

Many of the larger semiconductor suppliers have recently been looking

Everyday Electronics, April 1977

closely at their range of products and have taken steps to rationalise the range. This has resulted in the axeing of some lines and also in large price increases in lines which are deemed to be "specialist". It can also mean lengthy delays in the supply of some of these specialist items because they are no longer manufactured continually and because the supplier might well be trying to discourage their use in order to delete them from the new streamlined range.

Fortunately this has not affected many of our projects since we tend to use the most common devices. However two transistors specified for our *Transistor Assisted Ignition*, published three years ago, now cost about £5 each and are not expected to be available again for a good few months. This obviously makes that particular circuit redundant since it would now be cheaper to buy a commercial unit, even if supplies of the transistors were readily available.

Continuity Tester

As is mentioned in the article none of the parts for the *Continuity Tester* are particularly critical and those constructors who have been around for some time will probably find they have something suitable for most of the parts at hand.

The case for this project can be any of suitable size and no doubt many constructors will build their own.

Car Burglar Alarm

Some items used in the *Car Burglar Alarm* require a special mention, they are the relay which is a Doram type available direct from them—see the buyers guide for details of how to order etc.—and the trembler switch. Although this switch is not essential it is a useful addition to the circuit, however we have not been able to locate a source of supply of new switches but we are informed that one can usually be purchased from a breakers yard. This should provide a suitable source for

most readers although we feel that it must be possible to buy such a switch on its own as a replacement unit.

A similar thing applies to the key switch—although some of the larger suppliers can provide suitable switches these are usually expensive and an old ignition switch would be a cheap alternative.

Train Controller

None of the components for the *Train Controller* should cause any buying problems but readers should make sure that they obtain the correct type of switch—a centre off type—for S2.

Paper/Scissors/Stone

A number of switches are employed in the *Paper/Scissors/Stone Game* and these are rather special in that they are double pole push buttons. Since there are six to buy it is important that they are reasonably priced—we suggest you contact Electrovalue who can supply Castelco switches cheaply; see the buyers guide for their details.

Catalogue

Just as we were about to submit the copy for this page a Maplin catalogue "landed" in the office. Having only had a brief chance to scan the pages we must say that it appears to have been well worth waiting for and is probably the most comprehensive catalogue we have ever come across. How they have managed to provide it and send it out for 50p is beyond us.

The range of available items is vast—covering components, kits, tools, instruments and books with many items of allied interest such as hi fi, disco and organ parts and equipment. We are sure they should be able to provide most constructors with all their requirements.

CONTINUITY TESTER

By A. Irwin



THE unit described is of triple purpose; it can be used as a morse code practice oscillator, as a continuity tester, or test oscillator.

A morse code practice oscillator is often required for the training of scouts, cadets and radio amateurs. This unit can be built up mostly from spare components as none of the values of capacitors or resistors are critical. It is desirable, however, to use a high-gain type of transistor and high-resistance phones.

CIRCUIT

The oscillator (Fig. 1) is a basic three section dipper type which relies on the phase shift created

by the network consisting of C1 to C3 and R1 to R3 to provide positive feedback and thus cause TR1 to oscillate. The transistor itself provides 180 degrees phase shift, which would give negative feedback if applied to the base but this signal is taken via the phase shift network, which provides a further 180 degrees shift, to the base of TR1.

Potentiometer VR1 alters the base bias on TR1 and thus provides some control of the tone, whilst the output is taken from VR2 which acts as a volume control.

CONSTRUCTION

Commence construction by


drilling a suitable panel to take the main components and tag board as shown in Fig. 2. Next mount the various components on the tag panel together with link and connecting wires. Fix the tag panel and other parts to the front panel and complete the wiring up of the unit.

The metal box is large enough to take any type of 4.5 volt battery. It is essential that red and black leads are used to connect the battery so that the transistor will not be harmed by incorrect connection.

USE

Used as a continuity tester when trying to trace faults, the unit has several advantages over an ordinary buzzer. It delivers a clear, audible note which can be adjusted to ones liking. It will stand a lot of knocking about and the note does not depend on a critical mechanical adjustment,

Fig. 1. The circuit diagram of the tester.

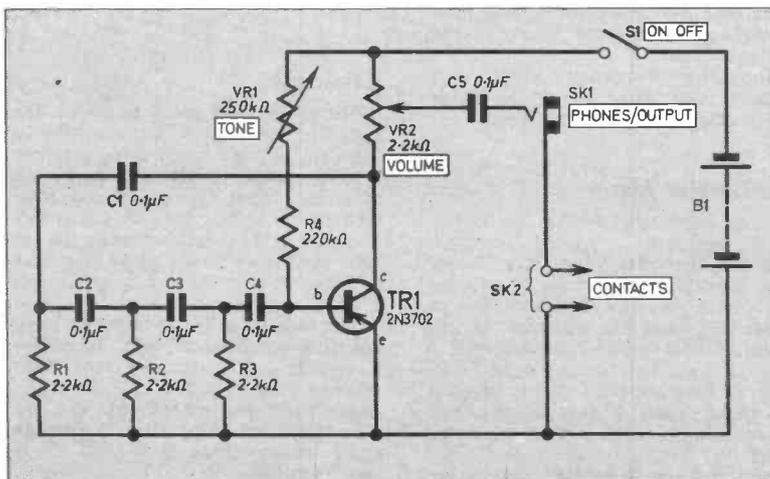

FOR
GUIDANCE
ONLY



ESTIMATED COST
OF COMPONENTS
excluding V.A.T.

£2.40
excluding case

like a buzzer, and will remain constant throughout tests. One other advantage, it is not necessary to look up from the work

to read a meter as when a visual type of indicator is used.

To use the unit as a test oscillator to feed an amplifier or

other audio equipment, simply short the two terminals of SK2 and take an output from SK1 to the unit being tested. ☐

Components

Resistors

R1	2.2k Ω
R2	2.2k Ω
R3	2.2k Ω
R4	220k Ω
All $\frac{1}{4}$ W $\pm 10\%$ carbon	

Potentiometers

VR1	250k Ω
VR2	2.2k Ω

Capacitors

C1	0.1 μ F
C2	0.1 μ F
C3	0.1 μ F
C4	0.1 μ F
C5	0.1 μ F
Any small types	

Transistor


TR1	2N3702 silicon pnp
-----	--------------------

Miscellaneous

S1	s.p.s.t. toggle switch
SK1	mono jack socket
SK2	single screw contacts (2 o \bar{r})
B1	4.5V battery
Six way double tag board; knobs for VR1 and VR2; case, approx 150 x 100 x 75mm; connecting wire; 4BA fixings etc.	

See
**Shop
Talk**

Fig. 2. Mechanical construction and wiring of the unit.

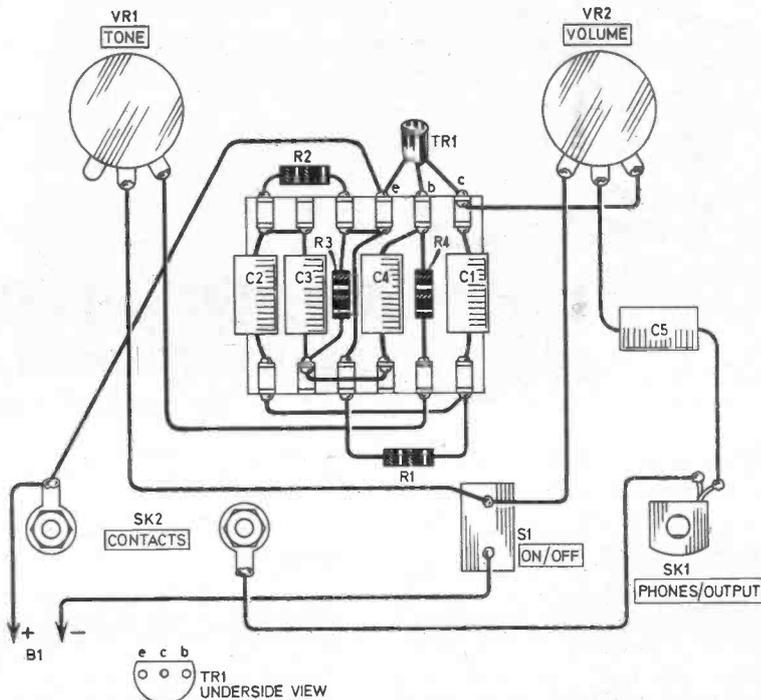

COUNTER INTELLIGENCE

By PAUL YOUNG

ONE big advantage you have dear reader, which I would like to stress, is that you are dealing almost exclusively with people who are enthusiasts. The staff of EVERYDAY ELECTRONICS are dedicated to giving you the best, and right the way down the chain to the humble retailer like myself, because we are extremely interested in our subject we want you to be also.

Obviously the most useful way we can do this is to give you good service. In case a cynically minded reader suggests we do it for money, I would assure him there are many easier ways available. In addition none of the firms you buy your supplies from are very big, which means that any grumble is dealt with at the top, as it should be.

In my own case I always insist on dealing with any dissatisfaction. I am pleased to report that not much of my time is taken up in this way. I even go further, I demand that all orders that are incomplete be brought to me. I then go through them to see if I can offer a reasonable substitute. There is usually plenty of scope here.

For example if we are out of a particular value of resistor in $\frac{1}{4}$ watt, one can send a $\frac{1}{2}$ watt, or if the customer wants a capacitor we may not have it in 10 volts but we have it in 16 volts. What is less obvious, is that a single pole double throw toggle switch could be replaced by a double pole, double throw. In fact you will probably have worked out for yourself that the latter could be used to replace all of them


except the centre off variety and the biased types.

If there are items on the order which are out of stock, we photostat the order and send them on later. If there is likely to be long delay, we return the money in the form of a credit note.

We may not please all the people all the time, but we do try, and believe me in this day and age this is really something. I am also very optimistic that in time we shall improve our performance and this will be done by narrowing down our selection. With a smaller range we can stock in greater depth and the chance of running out of stock will be much less.

It would be nice if all the component retailers got together and stated the items they were going to concentrate on. It would mean that you would have to purchase from more than one source but I have said previously that you may have to deal with about four suppliers to be completely covered.

I know in the past, we have erred in giving customers too large a choice. To quote, we were offering electrolytic capacitors in the following voltages: 2.5V 6.4V 10V 16V when obviously the 16V one would have covered the lot. I often wonder, is it correct to offer a choice of 10 different colours, when probably the customer would be just as happy if we repeated Henry Ford's dictum, "you can have any colour you like as long as it's black."

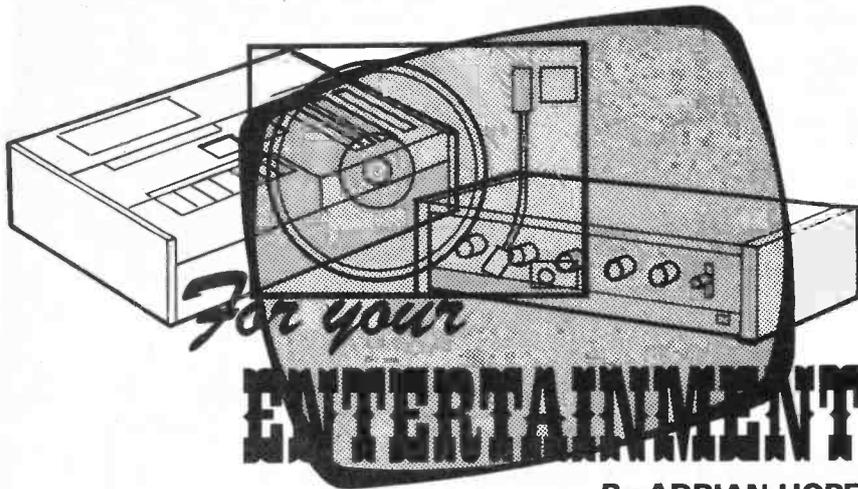

By ADRIAN HOPE

VAT Calculation

As we are still cursed with multi-rate VAT and some shops are still advertising exclusive prices, there is often a need to convert exclusive to inclusive, at one rate or another. How odd that no-one made any effort to tell the public that the original Budget reduction (25 per cent to $12\frac{1}{2}$ per cent) was actually an overall ten per cent cut on retail prices, and was thus a very easy calculation if you knew how.

In fact most exclusive-to-inclusive and vice versa calculations can be made with an equally simple single step, if you know how. To convert a VAT-exclusive price to a VAT-inclusive price, all you do is multiply the exclusive price by the VAT rate with the digit 1 ahead of the decimal point. It may sound complicated, but actually it's dead easy.

To get a price including 8 per cent VAT, you simply multiply the exclusive price by 1.08, and to get a price including $12\frac{1}{2}$ per cent you multiply by 1.125, and so on. Even more convenient, the formula works in reverse. So, to get an exclusive price you divide the inclusive price by 1.08, or 1.125 and so on. I find it somewhat odd that officialdom has never let the public into this simple secret—or wasn't I listening when they told us?

Space Junk

Here's a final unrelated thought for the month. It is topical and fashionable to bemoan the amount of valuable waste that we throw away, usually because it is too expensive to repair or reclaim. But the ultimate in waste must be the $1\frac{1}{2}$ million dollars' worth of electronic, mechanical and photographic hardware that I understand the USA left on the moon because it was cheaper to junk it than bring it back home again with the astronauts.



"Of course I can't cook like your mother used to—I haven't got the electronic devices her husband made for her!"

Everyday Electronics, April 1977

HAVE you ever wondered how it is that schools can receive television programmes without a roof aerial?

In the London area, 500 miles of coaxial cable were laid underground by the Post Office ten years ago. One object was to provide good TV reception for all ILEA schools without the need to erect aerials. Another was to enable those schools to receive closed circuit broadcasts originating from an educational TV studio at Battersea. This coaxial cable can carry nine separate TV channels (BBC1, BBC2, ITV and several special ILEA programmes) to every educational establishment in the London area, and the school sets each have a tuner with switching between nine channels.

Standard

The sets are unusual in that, although they operate on 625-line standard, they can accept only v.h.f. (rather than u.h.f.) signals. This is because it is easier to distribute television signals on v.h.f. frequencies rather than u.h.f., there being more loss of signal in a cable the higher the frequency it carries. Even so, the Post Office have to provide underground repeater amplifiers every mile along the main route and every half mile along the spur routes which use thinner cable. As the channel spacing on the educational distribution network differs from that adopted for normal broadcasting, the TV sets you find in schools are usable only in schools.

Although it comes as a surprise to some schools this is why an ordinary, off-the-shelf video recorder (videocassette or reel-to-reel) intended for domestic use will almost certainly not work if plugged straight into a school TV set.

Colour

Although all the ILEA distribution network to schools is colour-capable and the BBC and the ITV stations are piped down the line in colour, very few schools have colour sets. There was a plan a few years ago to start replacing old monochrome sets in London schools with colour sets, and the Post Office have been updating the distribution network with improved colour quality in mind. But with money for education so short, all hope of introducing colour sets to schools is now gone, at least for the foreseeable future.

There is even talk of axing the distribution network for London schools. This would surely be madness, because, apart from anything else, it would involve every school in the London area in the need to expensively erect an aerial to receive off-air signals in u.h.f. They would then have to convert the signals to v.h.f. for feeding to the school TV which, of course, can only work with v.h.f.

Let's hope that no decisions are taken over this by politicians who don't understand the technology involved and end up spending more money than axing the system saves!

Anyone using a London school TV set may wonder why and how educational TV programmes are sometimes interrupted by the sound of airline pilots talking to ground control. It's one of the disadvantages of using a v.h.f. distribution network. Some of the channels operate on exactly the same frequencies as the very powerful transmitters installed in modern airliners. If one is approaching London Airport only a thousand feet above a TV set tuned to the same frequency, breakthrough is virtually inevitable.

Free! - in next month's issue

MATRIX MARKIER


...another exclusive tool for **ee** readers

MULTI-BAND TUNER



This a.m. tuner is capable of receiving many stations on the short, medium and long wavebands.


REMOTE READING THERMOMETER

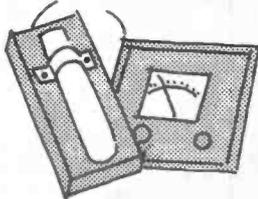

Designed for measuring temperatures outside the house, in the garage or greenhouse from inside the home.

METRONOME

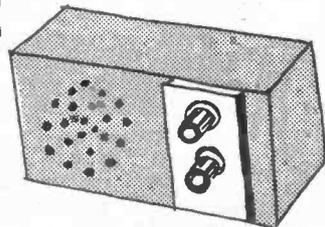An aid for the musician with a range from about 45 beats per minute to over 300 beats per minute.



everyday electronics

MAY ISSUE
ON SALE
FRIDAY
APRIL 15



Your Career in Electronics

by Peter Verwig

TV CAPITAL EQUIPMENT

TELEVISION today is so commonplace that we hardly give a thought to the fact that it is a comparatively recent invention, much newer, for example, than the automobile which equally had a profound effect on our life-style.

Of course imaginative people had dreamed about it long before it became a practical system. Transmitting still-pictures by electric telegraph was not too difficult. An elementary system was being worked on in France as early as the 1860s although the first practical system was not to be demonstrated before 1904.

The invention of the selenium cell in 1873 provided the means of defining light and shadow in terms of electrical current and the famous scanning disc invented by Paul Nipkow in 1884 provided the basic elements of a crude low-definition television system. But it was not until 1925 that the British pioneer John L. Baird made his first public demonstration in Britain and in the same year Charles Jenkins demonstrated a similar system in the USA.

EARLY SYSTEMS

Although the early systems using mechanical scanning with either the Nipkow disc or mirror-drums showed considerable ingenuity it soon became obvious that an all-electric system would be the ultimate solution. The theoreticians had already worked out that for reasonable picture

quality some 100,000 picture elements would need to be transmitted and, to obviate flicker, at a rate of more than 20 times a second. A mechanical system relying on spinning discs or drums would be expensive to build and extremely difficult to synchronize at such operating speeds.

The famous British experimenter A. A. Campbell-Swinton had foreseen all this and had suggested that electronic scanning tubes would be the answer as early as 1908 but it was not until Dr Vladimir Zworykin invented the iconoscope in 1928 that electronic scanning and the all-electric TV system became a practical possibility. From then on TV developed at remarkable speed.

The first public regular high-definition TV service in the world was transmitted by the BBC in 1936 from Alexandra Palace in North London. In the same year RCA in the United States started experimental transmissions from the Empire State Building in New York and television was here to stay. Except, that is, for the war-time years when all stations closed down because the TV transmitters might be used as "homing" beacons by enemy bombers.

FREQUENCY

It was not only the problem of the camera tube and the picture tube in receivers that delayed high-definition TV for so long. Because of the wide bandwidths required to carry all the picture



CCTV in action. Six camera channels monitor the road traffic through the Dartford Tunnel.



Mini-Mobile OB van introduced by Marconi last year. Note the cameraman with his hand-held portable camera protruding through the vehicle roof.



Marconi Telecine equipment nearing readiness for export

information plus the synchronizing signals, it was necessary to transmit and receive on v.h.f. and this part of the frequency spectrum had been virtually unexplored. So not only did electro-optics need developing but transmitting and receiving valves which would work at v.h.f. with acceptable efficiency. In fact the early TV work on developing v.h.f. and u.h.f. valves, circuits and antennas, enormously helped radar development, then in its experimental period, and a lot of the technological advances made in the crash research programmes on radar during the war were to enhance new TV developments when services resumed after the war.

An interesting point to note is whereas with radio the early development was for professional communications with broadcast entertainment only coming after some 30 years with the BBC, for example, not being formed until 1926, TV started life as a system for entertainment and only later found application in other areas.

The BBC re-started the TV service on June 7, 1946, using the pre-war equipment and a second station serving the Midlands started transmission on December 17, 1949. The North was next to be served by Holme Moss which came into service on October 12, 1951. Thereafter, the programme went smartly ahead to give complete coverage of the United Kingdom.

On June 6, 1954, international viewing became possible through the Eurovision network and a month later the Independent Television Authority was formed

to provide the viewer with alternative programmes and ITA's first transmissions were put out to London area in September 1955.

DEVELOPMENT

In the past 20 years TV development has been spectacular with nation-wide coverage now in colour, Eurovision supplemented by intercontinental broadcasts via earth satellites, and the imminence of new types of service via TV such as information on demand through CEEFAX and ORACLE. And TV is no longer confined to the technologically developed nations. You find it today in all the great subcontinents and even in the poorer areas of the world.

When I started preparing this report I thought of heading it Television Broadcasting. By this I meant not the receivers in your home which belong to that broad category of products we call consumer electronics, but the professional end meaning TV cameras, studio equipment, transmitters and antennas. But this sector is only half of the professional TV sector.

APPLICATIONS

TV may have started as an entertainment but its value has now been recognised in dozens of other ways. Most of us have seen closed-circuit television at main railway stations, at airports, on motorways and as security devices in shops.

Less well known are the remarkable developments in low-light TV as used in military

applications which enable bright pictures to be resolved with natural ambient lighting no brighter than starlight. Military aircraft are flying today armed with TV-equipped stand-off missiles and bombs. These are released in safety well away from the target area and are guided to their target by a built-in TV camera and transmitter in the nose, the aircraft crew observing the progress of the bomb on their airborne TV receiver.

The effect is just as if you, yourself, were in the bomb guiding it to its destination, the target approaching at what seems higher and higher speed and growing larger and larger until the moment of impact when the picture suddenly goes blank.

One such system is Martel, an Anglo-French development with the TV guidance and command system engineered by Marconi Elliott Avionic Systems. Performance figures are secret but informed guesses estimate the range of the Martel missile at about 40 miles although this would depend on the height of release from the parent aircraft. If this figure is anywhere near accurate it means that the missile can be released, say, 20 miles away from the target and be directed from the TV screen by the missile operator while the aircraft is already on its way home.

An American TV-guided missile, the Condor, made a direct hit on a ship target at a range of nearly 40 miles from the parent aircraft during trials in 1971. Both Martel and Condor are now deployed with the armed

services of their respective countries.

We might also mention in passing that TV is used in medicine, in all sorts of hostile environments such as atomic power stations and the bottom of the ocean, and in hundreds of industrial applications. This is why I broadened the title of the article to Television Capital Equipment.

COMPANIES

It can thus be seen that TV is today a lot more than Angela Rippon, or Poldark, Panorama or Kojak. It is true that today's professional TV engineer may have some connection with these programmes by working in the BBC engineering department or with the Independent channel equivalents by working for the IBA, but these jobs are only a fraction of the total. At the user end the TV engineer might equally work in a hospital or with an underwater salvage firm or with a security company.

At the manufacturing end the engineer is likely to be in the TV division of one of the major companies such as Pye TVT, Marconi, or EMI, all with considerable

business in TV equipment supply, or with a smaller specialist equipment company such as Crow of Reading or Prowest, or with Ampex who specialise in professional video recorders. Or as a TV specialist in a Ministry R & D establishment or in the Services.

SPECIALISING


TV engineering is a good career because it embraces so many different engineering disciplines. Once you have found employment and have some fundamental training behind you it is possible to specialise. I have met people who have spent upwards of 20 years solely on successive designs of TV cameras. Others might wish to specialise in other areas which interest them, perhaps TV transmitters or mixing consoles or telecine equipment.

Some super-specialists have even narrower interests, perhaps concentrating only on the all-important electro-optics or in such delicate subjects as video recording heads. The fact is that there is room for everybody who has his wits about him (or her) and who is willing to learn and to make a contribution. In the factory environment there is


nearly always a demand for test engineers and for those who like knocking around the world and seeing how the other half lives there are opportunities to travel as installation and commissioning engineers.

In fact a willingness to travel is almost a necessity nowadays. If you join a TV manufacturing company as an apprentice or trainee it is quite likely that at a late stage in your training programme you will do a stint on commissioning equipment on site. Even if you are eventually destined for the R and D laboratories such outside experience in the field is invaluable in revealing the real-life problems that need to be faced. What worked quite well in the temperate conditions in the UK may not do so well in the high temperatures and humidity of the tropics or survive the salt-spray of the marine environment. Of course all export equipment is built to withstand such hazards and are tested in environmental chambers at home, but it is hard to appreciate the working conditions, for example, an outside broadcast van and its equipment has to cope with until you've actually experienced it.

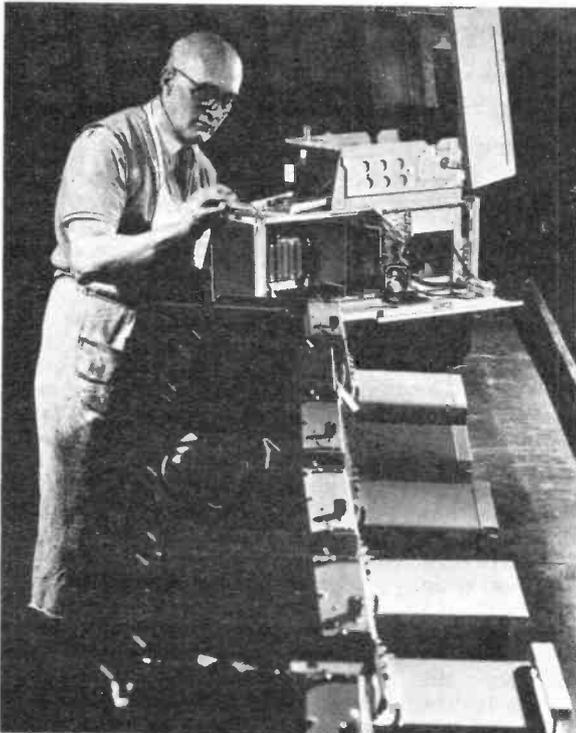Marconi Mark VIII colour cameras in final assembly at Chelmsford.



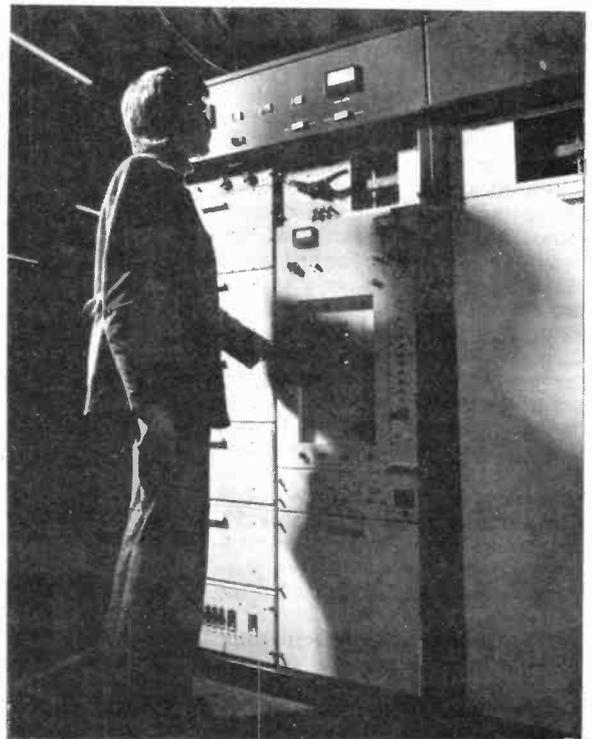Final check-out of a Marconi v.h.f. TV transmitter.



MARKET

First the bad news. The home market for TV broadcast equipment is stagnant. Very little business is being done because (a), the nation is virtually saturated with transmitters and studios. The great build-up is virtually over, including the transition to colour, which leaves only a replacement market and it's a fair bet that the manufacturers are wishing now that they hadn't built such long-lasting equipment. And (b), even if most of the equipment was falling to pieces (which happily it isn't) the BBC and IBA are not by any means flush with cash in these hard times.

Now for the good news. TV broadcast equipment exports are doing very nicely. Among the reasons for this is that no other country in the world has such long experience in the game as the British. The technical quality of British TV equipment is in the world leadership class. Those reared only on British TV should give themselves a treat and see what passes for TV in New York and here I'm talking of picture quality, not programme content although that's pretty awful there, too. In short, the British have a deservedly fine reputation for TV engineering and a present currency exchange rate which makes our exports attractive.

OVERSEAS

Another reason why we are

doing well overseas is because although we have reached saturation in the UK with 94 per cent of all households equipped with TV (each on average used 21 hours a week!) there are dozens of other countries who have hardly yet started on monochrome systems, let alone got around to colour. So there is still plenty of business about provided the British product remains competitive in the world market.

What's more, the larger British companies supply complete turnkey projects. This is virtually the complete package from surveying a country or territory to decide on location of transmitters and aerials, laying the first brick, equipping the studios and right through to getting the first programmes on the air. Such contracts go down to the last detail such as provisioning of spares and supplying emergency generator sets in case of power supply failure.

This is the sort of service that won Pye TVT an £8 million contract in the great complex of over 3,000 islands forming the Indonesian archipelago. Marconi was also in on the same deal with orders worth over £5 million for both sound radio and vision equipment.

Many countries are in the process of changing to colour equipment. Egypt's changeover to colour, for example, brought another £4 million worth of orders to Marconi as a follow on to other substantial orders from

Jordan and the Lebanon when they, too, made the change. More recently further TV contracts came from Nigeria and the equipment is to be air-freighted there later this year.

SUBSYSTEMS

As well as complete systems, British companies supply subsystems and individual pieces of equipment. Crow, for example, is doing very well with the Berkshire colour receiver/monitor now selling by the thousand at £850 each. You can see from the price that professional quality equipment is of a different standard to that found in the home.

Marconi enjoys a big export trade with telecine equipment and TV cameras, both monochrome and colour. The Marconi telecine won the Queen's Award for technology last year and orders are now well in excess of £5 million and the Mk VIII colour camera is used by broadcast authorities all round the world including China, the Soviet Union and the U.S.A. The new portable version for TV news action shots and interviews is another winner.

Thus, we see television engineering as still an expanding field of enterprise with a secure future. Those entering this exciting activity as young people today will see further startling developments. TV transmission through fibre-optics, domestic coverage by satellites, seven stereoscopic 3-D pictures, perhaps. ☐

JACK PLUG & FAMILY...

I'VE BEEN THINKING - MAYBE I ALLOWED JUST A LITTLE TOO LONG A DELAY BETWEEN WIPER SWEEPS WHEN I CONSTRUCTED...



Physics is FUN!

By DERRICK DAINES

A PUPIL was walking with his tutor in a garden. "What is happening, Grasshopper?" the old man asked.

"The temple bell is ringing, master," replied the young man.

The old man did his proverbial nut. "You are ignoring a long string of miracles" he shouted. Indeed he was, from the effect of gravity on the bell, kinetic energy, the impact of the clapper causing the bell to vibrate, and so on, all the way to the transmutation of tiny electrical signals to the brain into knowledge that it was the temple bell ringing and not some other bell. A great string of miracles; an exciting string of miracles, that it behoves us not to ignore.

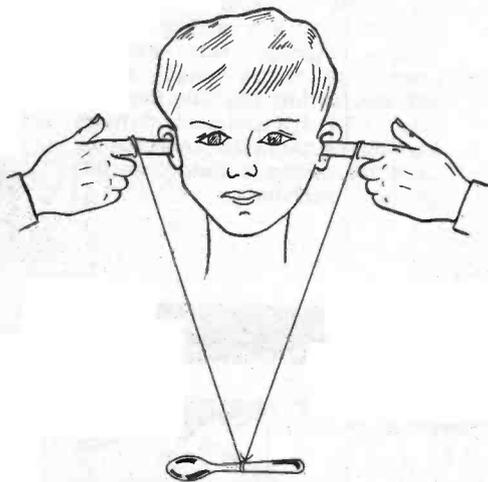


Fig. 1. Simple experiment with sound.

Sound is produced by vibrations, easily observable when a cymbal is struck. Even a pin firmly held in a piece of wood will give off a very high-pitched sound, while strips of tin or phosphor-bronze wire will sound louder. The vibrations of the metal cause the air around to vibrate thus being transmitted to the ear. Solids and liquids however will transmit sound far better than does air and we've all seen films in which

the cowboy puts his ear to the ground, thus hearing hooves sooner.

EXPERIMENTS

A fascinating series of simple experiments may be conducted as shown in Fig. 1. Take a piece of hard thin string about 2 or 3 feet long and tie the middle of it round a spoon. Wrap the ends once or twice round the forefingers and put the forefingers into the ears. Bend forwards so that the spoon swings freely and allow it to strike the table edge. The spoon will sound like a gong. Any number of other objects may be substituted for the spoon and you will soon get an instinct for the type of thing that will vibrate.

Similar but softer sensations can be heard with the string held in the teeth, while the sound can be heard very loudly if the vibrating object is held directly between the teeth. Some kinds of deafness can be by-passed in this way, giving rise to the science of dentophonics.

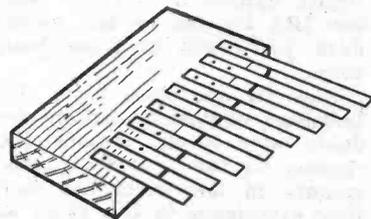


Fig. 2. The construction of a Kaffir Piano.

the chromatic scale—or any other arrangement desired. In use the wooden part is held between the teeth, leaving the fingers of both hands free to pluck the reeds. The writer has observed Africans playing such an instrument on numerous occasions and has no doubt that much pleasure is to be obtained from one.

The string telephone is another well-known instance of the transmission of sound along a solid object but I pose the question, is it capable of transmitting intelligible speech? (Fig. 3). I ask because although sounds

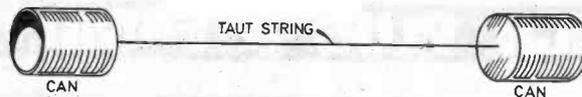


Fig. 3. Arrangement of a string telephone.

KAFFIR

A versatile and genuine musical instrument that used to be known as the Kaffir Piano is commonly seen in use in Africa, combining dentophonics and vibrating metal reeds. It is very easily made and has the overwhelming advantage that only the player can hear it! See Fig. 2.

The base is a piece of hard wood smoothed and polished and is of a size to fit easily and comfortably in the mouth. Strips of springy metal of various lengths are tacked to it and then trimmed with scissors to achieve

can certainly be transmitted and received, personally I have never been successful in understanding speech. I begin to suspect that there might be an element of the Indian rope trick about it, or that the speech heard has been transmitted through the air. Anyway, I would be interested to hear of successful experiments under test conditions.

The velocity of sound in air is easy to remember—333 metres per second, although barometric pressure has an effect.

THIS is based on an old game for two players which can be played with no preparation or equipment, but it allows the maximum of gamesmanship, "guessability" or E.S.P.

The basic idea is that PAPER wraps STONE, STONE blunts SCISSORS, and SCISSORS cuts PAPER; these are represented by both players simultaneously offering a hand as a clenched fist—STONE, or an open palm—PAPER, or with fingers in a V-sign—SCISSORS. One will win over the other, or it will be a draw.

Although there is some satisfaction in playing the game physically, it can be inconvenient or impossible to do so, and in any case it is essentially a contest of minds.

The device described here is the application of this old principle to circuitry so that, instead of making hand signs, each player presses one of three switches on his hand-held control. The result of the players "conflict" will be shown by a lit lamp on

one or both sides of a central box. This enables the game to be played at any time without the players having to stand and face each other, and to play it at a faster rate than is possible with the hands only.

CIRCUIT DESCRIPTION

The circuit diagram of the Scissors, Stone, Paper Game is shown in Fig. 1 and is seen to be a simple switching arrangement with diodes used to steer to produce the required results.

The wiring has been designed so that the indicator lamps will light on the winning players side according to the above statements. In the event of the same name button being pressed by each player, a lamp will light on each side of the display box (this is accomplished by the steering diodes).

CONSTRUCTION

The lid of the display box (of any convenient size and material) is first drilled or cut to take the six lampholders—three at each end. These can be of three colours, but it is not essential because the bulbs positions indicate what they represent. They should preferably be low voltage types.

Six-way miniature tag strip is fixed to the lid between them, and the connections are made as detailed in Fig. 2.

A neat job is possible when the wires are cut and bent at right

angles before soldering to fit snugly down the sides of the lamps and along the surface of the lid to go into the tag strips from the inside as indicated in Fig. 2. All the tag strips can then be soldered from the middle of the strips away from the wires.

The prototype used 6-core screened cable (about one metre or so) to connect the players boxes to the display box. The screening braid is used as the seventh conductor between the boxes. Begin by cutting the leads to their respective differing

**FOR
GUIDANCE
ONLY**



**ESTIMATED COST
OF COMPONENTS
excluding V.A.T.**

£6.60

SCISSORS. STONE·PAPER GAME

By A.W.GIBBS

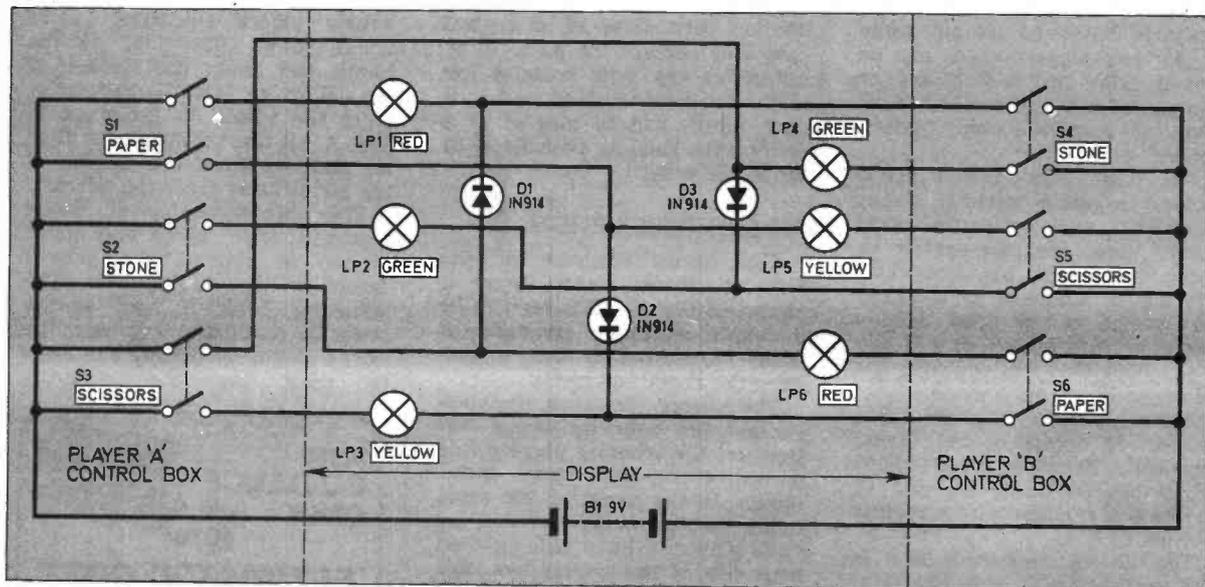


Fig. 1. The circuit diagram of the Scissors-Stone-Paper Game.

lengths so that they fit along the edge of the box. Attach the battery clip to the screening from each lead and cover the joint with insulating tape.

Next the diodes should be soldered as shown in Fig. 2—again these are best bent at right angles where necessary to fit before being soldered to the tags. In the prototype the diode leads were insulated.

The sides of the display box can then be cut at the top to allow the leads to pass under the lid when it is screwed down. There should be enough space in the box to comfortably accommodate the PP3 type battery.

The hand controls need be only as wide and deep sufficient to take three double pole switches. In this case the switches can be positioned in the box itself.

Where the material is thick it may be necessary to shave the edges of the holes to allow the cap to be screwed down far enough for the buttons to be depressed fully. This was found necessary on the prototype.

The double pole switches will have four lugs. (Where they are of a different type to that shown, the respective terminals can be found by using a loose battery and bulb).

A notch is cut at the edge of the box to allow the lead to be passed through the front of the box but held in place by the

Components

Diodes	
D1 to D3	IN914 or similar (3 off)
Lamps	
LP1 to LP6	12 volt 0.1 amp Lilliput screw types (6 off)
Switches	
S1 to S6	double pole push-to-make release-to-break (6 off)
Miscellaneous	
B1	9 volt type PP3
	Tagboard miniature 6-way; 6-core screened cable (about 2 metres); battery clip to suit; square head, indicator lamp-holders with coloured lenses (6 off); plastic cases size 110 × 60 × 30mm (3 off).

See
**Shop
Talk**

screwed down lid. (Alternatively, a hole can be drilled in the box and the wire pulled through before work is started—a grommet will keep the lead in place).

The switch buttons tops can be chosen to correspond with the lamp colours if required or the names of the switches can be printed/typed on. Wiring up details within the player boxes are given in Fig. 2.

PLAYING THE GAME

No lamp lights until two buttons are pressed, but if more than one button is pressed on one or both sides, then two lights will show on one side indicating a "cheat". The controls are held cupped in the hands so that both thumbs can be used and without the other seeing which button is pressed.

The game will suit all ages and moods. Children can simply press the buttons as quickly as they like without regard to their significance, and they can play the "best of five" or the first one to get, say, ten wins. Adults can play more slowly trying to anticipate the other's reaction. Usually, one player somehow obtains dominance over the other at different times. As well as the previous games, adults can see which player gains three consecutive wins. A game is drawn say after three consecutive draws.

Further rules can increase the sophistication, such as barring the use of the same button for more than twice consecutively, or awarding an extra point for a sequence such as the second PAPER (say red) light, on the opposite side. ☐

SCISSORS • STONE • PAPER GAME

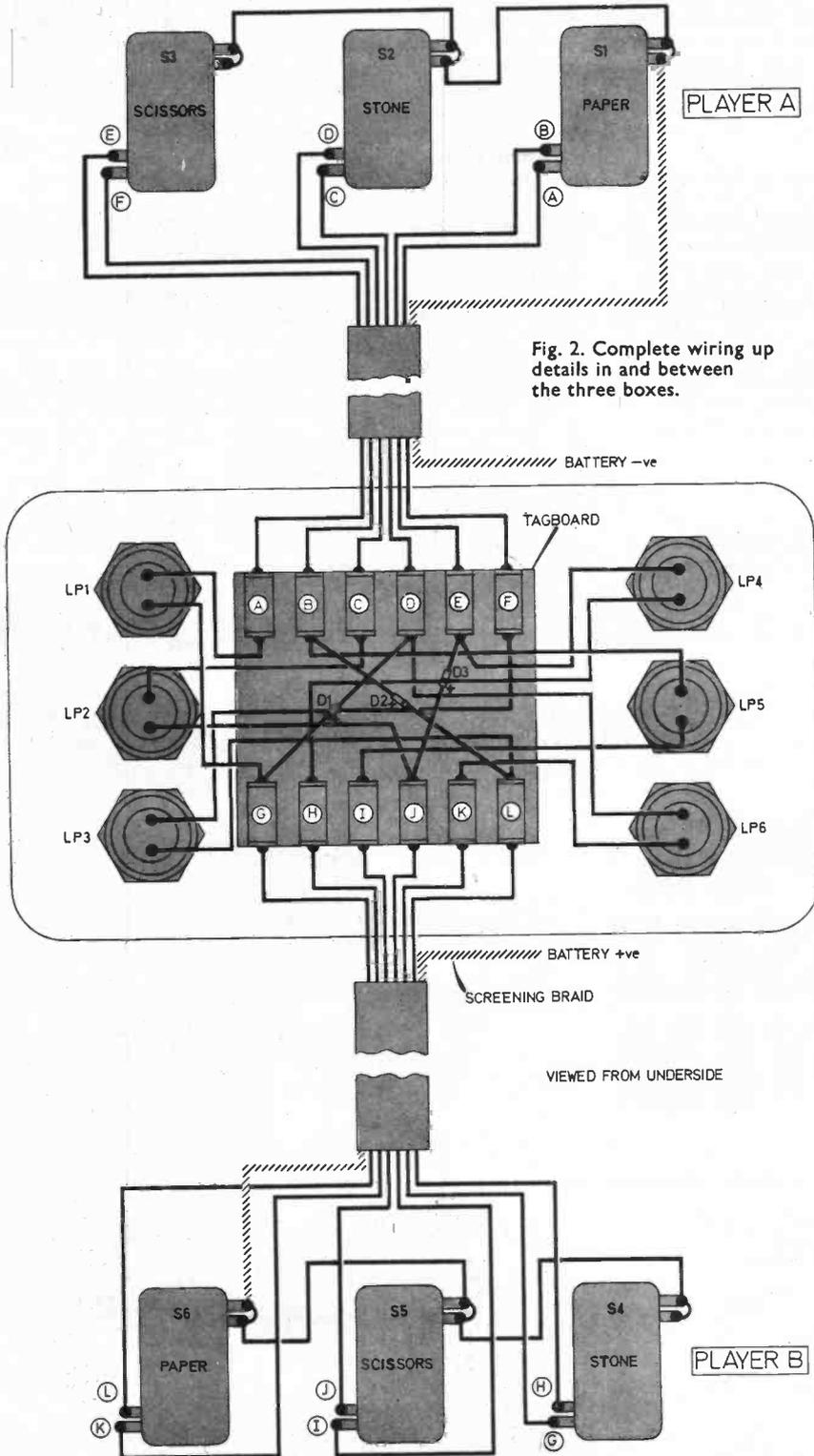


Fig. 2. Complete wiring up details in and between the three boxes.

VIED FROM UNDERSIDE

THE BAC "Rapier" low-level anti-aircraft missile system was in the news recently as having been re-ordered by Iran. In service with the British Army, the RAF and the forces of other countries it is the most successful weapon of its type. Unlike the Franco-German "Roland" which uses a proximity fuse, a Rapier missile is designed to score a direct hit.

When you think of the fleeting chance offered by a modern, small fighter-type aircraft crossing at the speed of sound about a mile away, the fact that Rapier constantly scores a very high percentage of hits, borders on the miraculous. Add that the operator is usually a young soldier of unflappable demeanour but no special qualifications and one is even more impressed. How does it work?

BASICS

Though the new order calls for a self-contained tracked vehicle

with which the two parts of the system are integrated, the standard Rapier consists of a Launcher (incorporating a generator) towed by a Land Rover, in which is carried the Tracker. To deploy the system the Launcher is detached from the Land Rover, which, after depositing the Tracker about 30 metres away, moves off to hide. Launcher, Tracker and generator are then connected by cabling. Four missiles are mounted on the Launcher in the top of which is a search radar aerial. There is also a computer and a missile control (command) radio transmitter with a dish aerial mounted in front. The Tracker consists of an optical sight, a TV camera and control facilities.

On being brought into action the radar carries out a normal 360 degree search. When a target is detected it is automatically interrogated by IFF (Identification Friend or Foe) and the radar ceases to respond to information from any other sector. If a

friendly reply is received full surveillance is resumed, but if not, an alarm is initiated. This alerts the operator and also slews the optical Tracker head onto the bearing indicated. The Tracker's bearing is transmitted to the Launcher turntable, on which the missiles and their command radio aerial are mounted, and the turntable follows this bearing.


The operator, whose optical sight will be already on the target for bearing searches for and locates it in elevation. He then switches to the "track" mode which stops the radar control of the Tracker bearing, leaving the optical tracking of the target under his full control. It also causes the missile launcher arms (hitherto immobile in elevation) to elevate as necessary,

While the operator keeps dead on target, the computer, which is being fed with information from both the radar and the Tracker's sight, assesses whether or not the target is engageable and informs

RAPIER MISSILE SYSTEM

From target search through to its destruction.

By G.A.G. Brooke

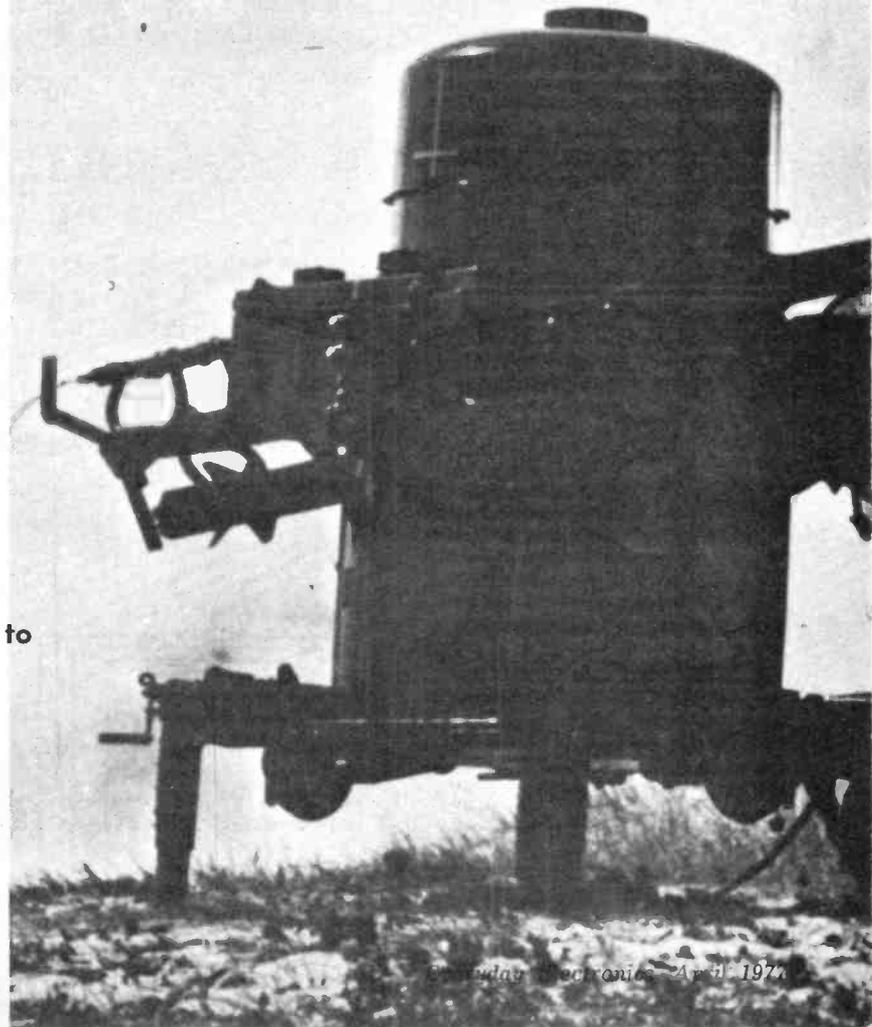

the operator. If the computer's answer is yes it lights an IN COVER indication lamp in the operator's field of view and he can then press the FIRE button when he wishes.

On being launched the missile receives an initial correction which directs it into the field of view of the Tracker's vidicon camera. Flares in the tail of the missile are picked up by the camera which is mounted as one with the optical sight. The camera then measures the amount by which the missile is off the line of sight (the error) and transmits this to the computer. The necessary corrections are formulated by the computer and transmitted by the command radio transmitter to a guidance receiver in the missile. Thus the missile is made to fly as near as possible along the operator's line of sight.

In this article we are particularly concerned with the surveillance radar and command transmitter elements (designed and manufactured by Decca Radar

Limited) and let us now go back over the sequence of events, with particular emphasis on these two aspects.

RADAR

The computer in the Launcher, in order to work out whether a detected target is (or will soon be) engageable by the missile system, needs more radar information than can be supplied by a standard pulse radar of the type described in the January 1975 issue (*How Radar Works*). In particular it needs the ability to detect moving low-level targets in heavy ground clutter. This requires a radar with the facility of extracting target velocity.

The Doppler principle is best explained by the train whistle analogy. When the train is approaching a stationary listener the note rises due to the fact that the distance between the sound source and the listener is decreasing and hence each successive sound wave has less distance to

returning from moving objects. When an aircraft is circling at constant range there will be no change of frequency (i.e. no Doppler shift) but as soon as it closes or retires a change occurs and can be translated into radial velocity by comparison with the outgoing frequency (crystal controlled to ensure consistency). Radial velocity of the target can be obtained from the amount of Doppler frequency shift, and the direction of travel (i.e. approaching or receding) from the polarity of the Doppler frequency shift.

In the Rapier radar a solid state drive unit is used to provide the transmitter drive, the first and second local oscillator signals and the clock pulse for r.f. generating range gates. As the transmitter drive and the first local oscillator signals are derived from the same crystal oscillator they are coherent (i.e. spaced apart by a constant frequency) any variation occurring equally to both. Any Doppler shift of frequency due to a moving target) can

travel than the preceding one. This causes each individual sound wave to arrive at the listener a little earlier than would have been the case if it has been emitted from a stationary source.

The shortened interval between the sound waves arriving at the listener results in the reception of a higher tone than that emitted. Conversely, when the train has passed, the increasing distance results in a lengthened interval between sound waves and the listener hears a lower tone than that emitted. Hence a prolonged whistle sounds like a wail that rises and then falls.

Precisely the same occurs with the radio frequency of echoes

vary about the i.f. centre frequency by up to a few thousand hertz.

RANGE

For the measurement of range there is a range gate generator in the receiver, producing a number of continuous range gate pulses (i.e. the end of the first pulse is synchronous with the start of the second and so on, all being completed well within the interval between transmitter pulses).

Considering the first range gate pulse, its timing and duration are such that echo signals returning from targets between about 1 km and 2 km distant are allowed through the first range channel,





Shows the Rapier System in operation: the Tracker is shown in the foreground and the Launcher in the background containing four missiles.



The end result of a successful missile launch—a direct hit.

that is, reach the rest of the receiver. Similarly, the next range gate pulse passes echoes from 2 to 3 km through the second range channel and so on.

The result is that an echo from a certain range channel generates a signal representing that range, the information being passed to the computer as target range. The measurement is imprecise but very accurate range is not required in the Rapier system.

RADIAL VELOCITY

Radial velocity is obtained by comparing the echo frequency with the emission frequency on the Doppler principle described. The Rapier operator is not interested in stationary targets (those without any change of frequency) and these are rejected by a clutter filter tuned to second i.f. centre frequency. Signals from moving targets, which pass through the filter in any range channel, are amplified and applied to a bank of ten frequency-conscious filters. Each one covers a band of frequencies corresponding to a 50 metre per second range of radial velocities.

The first velocity channel covers from about 37 microseconds to 87 microseconds, the next from 87 to 137 microseconds and so on, in much the same way as the range channels cover discrete sections of the total range coverage. The presence of an output from any particular velocity channel, in the relevant range channel, indicates target velocity and this information is fed to the computer.

In the context of velocity information, it should be mentioned that the presence of sidebands in the Doppler receiver results in an ambiguity which can cause a slow approaching target to appear as a fast receding one, and vice versa. This ambiguity is resolved in the computer.

BEARING MEASUREMENT

Bearing (or azimuth) measurement is a combined operation on the part of an azimuth pulse generator (situated in the radar head), the Doppler radar receiver and a digital counter and store in the Tracker. The aerial beamwidth is 8 degrees and it is necessary to ascertain the bearing of the aerial (relative to the fore and aft line of the Launcher) when the target is in the centre of the beam.

There is an optical system in the pulse generator comprising a lamp, lens, and a disc which revolves between these and photo electric cells. The disc has two concentric tracks, one of which is half clear and half blank, and the other divided into 2048 perforations. The disc is driven by the gearbox of the aerial which revolves at 60 r.p.m., and so it follows that the intermittent light falling on the photoelectric cells will be in square waveform of 1Hz and 2048Hz respectively.

Electrical signals of this nature are passed to the second element of the combination, a counter. This uses the 1Hz signal as an azimuth zero reference. As soon as the radar detects a moving target, a target width pulse is

generated in the Doppler receiver which causes the counter to stop counting and transfer its contents to the store. But the bearing at this moment is that of the leading edge of the beam, not its centre, and to obtain the latter it is necessary to add half the beamwidth.

This is done by feeding pulses at half azimuth pulse frequency (i.e. half-speed pulse) from the Doppler receiver into the Tracker store for the whole of the duration of the target width pulse. The resultant final count then equals aerial bearing at target start plus half the beamwidth, which is the same as when the target is at the centre of the beam.

So we now have the ability to assess a target's range, bearing and radial velocity. The bearing data is used (in the SEARCH mode) to turn the Tracker head and the Launcher onto the target bearing when a radar alarm is raised. The range and velocity data are used together with information from the Tracker, during coverage computation. This takes place between the time when the operator switches from SEARCH to TRACK and when he presses the FIRE button. When the missile is fired the role of the computer changes from coverage computation to guidance computation and the TV vidicon camera then comes into the story.

VIDICON CAMERA

As soon as the missile flare appears in the camera's field of vision, the latter informs the computer of the error between the

flare position and the centre of the camera's field of view. Though there is no c.r.t. involved as with normal TV the principle is similar but in reverse. Instead of a picture being built up by a scanning process, the bright light from the flare is recorded by what can be termed a reverse scanning process which transmits its findings to the computer.

To convert the vidicon output into flare-spot position information, it is first necessary to find the flare spot on the image plate. During the initial period of an engagement, the television is operating in the widefield flare acquisition mode and a systematic search is performed over an area of the image plate which is slightly larger than the area of the optical field of vision presented to it.

The search is made by a fine electron beam which scans the underside of the vidicon image plate, and an output from the vidicon occurs when the electron beam passes across the flare image. After flare acquisition the TV optics change to high magnification and narrow field.

In order to scan the designated area of the image plate, the beam makes 625 horizontal sweeps across the plate. These sweeps are said to cover a frame, and take 10mS to do so. At the end of each sweep the beam returns very quickly to a new starting point on the same side of the plate from which it started but slightly displaced perpendicularly from the last starting point. The displacement is brought about by the vertical sweep which takes place at the same time as the horizontal sweep.

In effect, when the beam ends its return journey it finds that it has been slightly deflected from its original starting point. As only one vertical sweep is required for the whole series (frame) of horizontal sweeps needed to scan the designated area of the image plate, the vertical sweep speed is much slower than the horizontal, and lasts for 10mS.

AZIMUTH AND ELEVATION

Now, the beam is caused to sweep across the image plate by supplying a current, increasing with time, to the vidicon control circuits required. For a particular current magnitude then, the beam is moved to a defined spot

on the image plate. Conversely, by measuring the current supplied, the position of the beam at any instant can be determined. This feature is made use of in the television system, for the length of the horizontal sweep is made to represent the full ambit of the TV system in azimuth, and the vertical sweep the ambit in elevation. It has been explained that when the electron beam passes the flare image, the vidicon tube produces an output.

Considering the azimuth alone, the vidicon output is used to switch a sample of the horizontal sweep current to the azimuth error channel. As explained, the magnitude of this current is indicative of the point reached by the beam during the horizontal sweep and is thus directly related to the azimuth of the flare image. For elevation, the vidicon output causes the vertical sweep current to be sampled and switched to the elevation error channel. The magnitude of this current is indicative of the distance of the path of the vertical sweep in progress, from the path of the first horizontal sweep in the frame, and is thus directly related to the elevation of the flare image.

The outputs to the error channels are processed within the TV system so that when the flare image is at a point on the image plate which is coincident with the TV optical axis, a zero output is given in each channel. If the image is offset from this position in a channel, an output is given with polarity dependant on the direction of offset.

The computer receives 'error' signals from the vidicon camera which are derived from the flare's position relative to the line of sight. Resolving these the computer produces pitch and yaw demands for the command transmitter to send to the missile.

TRANSMITTER AND MISSILE

The command radio transmitter changes the characteristics of the pulses so received in accordance with the code used by the particular Rapier in question. If this did not happen an adjacent Rapier might be affected by mistake. The specially coded pulses are applied to the modulator which fires the magnetron, which in turn changes them into r.f. pulses for beaming to the missile.

Two aerials are employed for this. The first is a flared horn type with wide beam for "gathering" the missile in its early stages. After allowing a short time for the latter to settle, an automatic waveguide change-over switch switches to the second aerial, a dish with narrow beam.

The command signals are received as pulses in the missile, detected, amplified and converted into voltage analogues of the original yaw and pitch demands, and passed eventually to the guidance assembly. This demands control solenoid valves regulating the flow of a hot gas to cylinder and piston actuators operating the four control surfaces near the tail of the missile. Manipulation of these is the last link in the chain of operations, the missile being brought onto the line of sight of the vidicon camera, and therefore of the operator.

The missile carries an impact fuse, and all the operator has to do, having pressed the FIRE button, is to keep his sight exactly on the target. This is done with a sensitive joy-stick control, simply a lever that can be pressed in any direction to transmit information in the two modes with an urgency varied by pressure on the stick. The effect of a hit is devastating, far more destructive than a proximity fuse. ☞





Comments about a Retailer

Having just read *Counter Intelligence* in my copy of February EVERYDAY ELECTRONICS, I would suggest that you inform Mr. Paul Young of the existence of Orchard Electronics in particular, and most component retailers in general (except, it seems, for the establishment he orders from) who have a remarkable service.

They remit your order within a few hours of receiving it, and the only reason for an order taking more than three days to return is either that a 6½p stamp was used or the terrible postal service has just put its third foot in the grave.

Orchard are so fast that inflation does not have a chance to act. Please ask Mr. Young to try their services or print a retraction.

S. Phillips,
Chislehurst, Kent

... and more

What on earth was the writer of *Counter Intelligence* (Feb. 1977) thinking of? Having read the article I half expected customers to crawl in on their hands and knees apologising for intruding and begging forgiveness for having the gaul to come in at all.

Is he trying to kill off the component business? He writes—"I am always baffled by the customer who phones to say their order was a fortnight in coming and they consider it disgraceful". The customer is the baffled one. The order comes in, is checked for accuracy, is packed and sent out. What is difficult about that?

Two weeks delay!! a month!! this guy says two months. Come off it. We advertise a by return post service and we mean it. If your goods fail to arrive in 7 days let us know. The inference that component suppliers are a lazy bunch of inefficient layabouts is just not on.

The magazine spends weeks preparing projects. The customer pays good money for the magazine. He is tempted to build a project and by the time he gets the bits two more issues of the publication are on his bookshelf. The writer of *Counter Intelligence* is baffled.

Dear reader, disassociate Orchard Electronics from such clap-trap. "By return post" means what it says.

Inflation is another matter, we are all suffering with that one. The clearly written and accurately calculated order is a joy to deal with. The only part of our service we cannot control is the postal system. According to our records about a dozen packages have failed to arrive. Not bad when one considers that at least half of these went up in smoke when some goon set fire to the local Post Office.

Finally we are proud to be part of the fastest developing industry in the world today. Proud to be British, the most advanced nation in electronics today.

So we suppliers may have problems, so what, that's what business is all about. If it were humanly possible we would deliver in two hours (in fact on more than one occasion we have even done that) but 2 months or 2 weeks—NO! Electronics should be a pleasure not a pain in the neck.

D. M. Trueman
(Orchard Electronics)

Thank you for your letter and constructive criticism. As you know I am as keen about the electronics industry as you. I think that I should perhaps have made it clearer in my article that two weeks is not the norm for the delivery of goods. We do manage an immediate turn round, or the same day where a customer has an account. No, this only occurs on out of stock items.

Where you have two unknown variables, (length of time for supply, and weekly demand) and where you are dealing with about 500 to 600 orders a week it is difficult not to be occasionally caught out.

The point that I was trying to make and failed, that compared to other hobbies our component retailers do superbly well. Anyway we can do with lots more enthusiasts like yourself in the business, so keep up the good work, even if it means criticising yours truly from time to time.

Paul Young,
Surrey

Appeal from abroad

I am writing on behalf of the International Voluntary Service in the Seychelles. We are part of the British Volunteer Programme which is a voluntary organisation with a view to training technicians etc in the developing countries.

At present the college in which I am teaching has a City and Guilds of London 235A and 235B Electricians Course. We are trying to start a Basic Electronics course, which is (in the "Electrical Industry") a vital part of training.

The Islands I should explain have just received independence, and of course

have a limited budget, therefore we have problems in supplying texts for our students, and components for building circuits. I would add that a lot of British Technology is exported to the Islands but only limited training is available.

Part of the plan is to expand on this training, so I would like to appeal to you and your readers, to help in as many ways as possible. One very practical way would be to receive unwanted back issues of your magazine which I feel would be a tremendous help in the work. Also old or used texts, would certainly be gratefully received, and, of course, what we in the trade call "junk" such as old p.c.b.s, resistors, diodes, transistors, capacitors etc.

The students are hard working and would be grateful for any help in developing the skills of our industry.

My colleagues and I, some of whom are directly employed by the Seychelles government all feel that the possibilities that exist are excellent. British people have given political independence to the Seychelles, we can give them economic independence by giving as generously as possible the technical training that they need.

If anyone would like further information on our school please write and I would be only too willing to forward it.

Gordon Catto,
Seychelles Technical School, Education Department, P.O. Box 48, Victoria Mahe, Seychelles.

Can anybody help?

Your readers will be interested to know that large sheets of fibreglass can be obtained extremely cheaply—sometimes even for nothing—from any car breaker who deals with lorries and vans, particularly ex-GPO vehicles. Many of these have fibreglass roofs, etc, which the average breaker has no use for and is glad to get rid of.

I have used this material very successfully for circuit boards, and with the aid of a glass-fibre and resin car repair kit very neat and professional looking boxes, housings and cabinets can be constructed with it.

In common with many other electronic enthusiasts, I have a large collection of integrated circuits etc, mainly removed from computer and surplus panels which I cannot identify as I do not know the makers and they bear totally unfamiliar type letters and numbers which I cannot find in any reference book. Consequently they are completely useless to me.

Does anyone know how or where I can obtain identification and data on these devices? After all, somebody somewhere must know what they are and what they do!

Possibly someone might be interested in starting a "Postal Identification and Data Service".

How about it, some of you boffins? Possibly some scheme where for a reasonable fee (say £1?) you undertake to attempt to identify and supply brief essential data on up to 10 different devices—preferably, of course, on a "no identification—no fee" basis!

Some such service would be a godsend to people like myself, and should show a good profit to anyone who cares to operate it.

J.M. Pascoe, B.H.S.P.I.,
Kent.

We shall be pleased to forward any correspondence to Mr. Pascoe concerning the points raised in his letter. Please ensure that the letter to be forwarded is accompanied by a stamped envelope.

What's watt

I have just started with electronics as a hobby and decided that the best way to enjoy my new hobby was to take a magazine regularly. Having purchased your magazine I was delighted to find that it contained projects to suit people

at different levels in electronics.

I was impressed with the *Brake Light Warning Device* (Jan. '77) and decided to build this as my first project. I have however experienced a little difficulty in buying some of the components, namely DI (TIL 209) and R1 (0.47 ohm $\frac{1}{2}$ W, 4 off).

I did manage to find a 0.56 ohm resistor but rated at 1 watt. Four of these resistors wired in parallel gives the exact value quoted in the text (0.14 ohm) but gives a wattage of 4 watts instead of 2 watts. Is this wattage acceptable in this project?

The difficulty with the diode (I.e.d.) was finding one of the correct voltage. Shops locally do not seem able to translate the reference you gave (TIL 209). Please could you tell me where this component can be purchased or possibly state an alternative.

B. F. Scott
Sittingbourne, Kent.

When a resistor wattage is specified, it is in most cases the minimum preferred rating for the job. In your case the four

0.56 ohm 1 watt resistors are o.k.—provided the physical size of the components is acceptable. We are surprised you have had difficulty in obtaining the general purpose light emitting diode TIL209. Voltage ratings are never quoted. Any small I.e.d. will be suitable.

Improvement

On the *Transistor Checker* in the February edition of *EVERYDAY ELECTRONICS*, because of the wiring of the switch S1, to put it in npn you have to take it through pnp before you can test npn transistors. If you rewire the switch so all the connections which go to tag 1, go to tag 2, and all the connections which go to tag 2, go to tag 1. Thus you do not have to put the switch to pnp before npn because off is in the middle. All the connections which go to tag 3 stay the same.


I read *Everyday Electronics* every month and enjoy it very much.

David Stratt (Age 10)
High Wycombe, Bucks.

...For Your Reference

a.c.	alternating current	oz	ounces (avoirdupois)
a.f.	audio frequency	p.i.v.	peak inverse voltage
a.f.c.	automatic frequency control	p.v.c.	polyvinyl chloride
a.g.c.	automatic gain control	r.f.	radio frequency
a.m.	amplitude modulation	r.m.s.	root mean square
BA	British Association (nut and bolt sizes)	s.p.s.t.	single-pole single-throw (switch)
cm	centimetre	s.r.b.p.	synthetic resin bonded paper
d.c.	direct current	s.w.g.	standard wire gauge
d.p.d.t.	double-pole double-throw	t.r.f.	tuned radio frequency
elect.	electrolytic	u.h.f.	ultra high frequency
e.h.t.	extra high tension	u.j.t.	unijunction transistor
e.m.f.	electromotive force	v.h.f.	very high frequency
f.e.t.	field effect transistor	%	per cent
f.s.d.	full scale deflection	X	reactance
f.m.	frequency modulation	Z	impedance
g.	gram	A	ampere (amp)
h.t.	high tension	dB	decibel
i.c.	integrated circuit	F	farad
I.e.d.	light emitting diode	H	henry
I.d.r.	light dependent resistor	Hz	hertz (cycles per second)
lin.	linear	Ω	ohm
log.	logarithmic	V	volt
m	metre (measurement of length)	W	watt
mm	millimetre	p	pico (\div 1,000,000,000,000)
m.w.	medium wave	μ	micro (\div 1,000,000)
npn } pnp }	transistor structure (two types)	m	milli (\div 1,000)
		k	kilo (\times 1,000)
		M	Mega (\times 1,000,000)

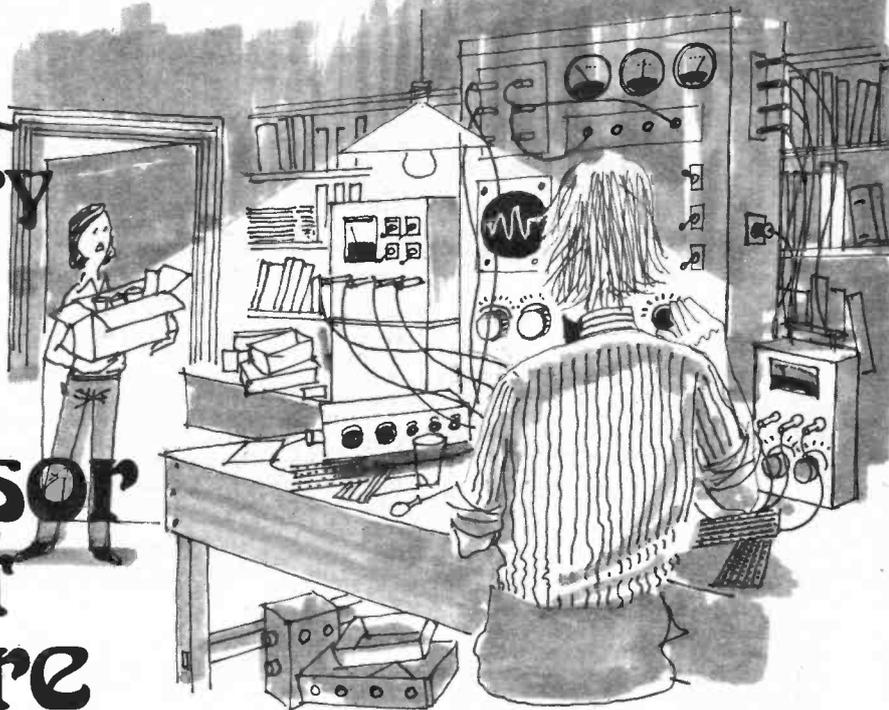The Extraordinary Experiments of Professor Ernest Eversure



by Anthony John Bassett

WE will not occupy the reader unnecessarily with any detailed description of the joyful departure of Tom and Maurice from the Professor's laboratory, carrying with them impedance converters which allow connection of extra loudspeakers to an amplifier without mismatch, and an Electronic Steady Hand Tester.

Tom and Maurice have been "roped in" to assist with voluntary charity work, and the interesting technical problems which crop up ensure that they will be regular visitors to the Professor's laboratory. One of the ideas they have left with the Prof. is for a simple coin-collecting mechanism which can be connected to a number of simple but fascinating electronic amusements.

Meanwhile the ever-enquiring mind of the Prof.'s young friend Bob had prompted him along another channel of thought.

PICK-UPS

"I have been wondering, Prof., why there are so many different kinds of pick-ups for hi-fi, and for musical instruments. I have come across crystal, ceramic and magnetic pickups and microphones, and it is quite a puzzle to me why there should be so many different kinds. For instance, what

are these mysterious crystals which are used in so many microphones and pick-ups?"

"These are crystals which, when a changing force is applied to them in certain directions, produce a changing output of electrical charges on the faces of the crystal. This electrical change can be picked up by an electrically conducting substance such as thin sheet metal, and taken by wires to the input of an amplifier.

A large number of chemical substances produce crystals which behave in this way, and are known as piezo-electric crystals. Each type of crystalline substance differs in its properties from the others, so that there is a large range of substances available for the purpose of experiments.

One which is very commonly used is known as Rochelle salt, and consists of sodium potassium tartrate. The particular properties which make it a favourite material for use in record-player pick-ups and crystal microphones are high sensitivity and large electrical output, low cost and ease of production. Also it is non-poisonous and is a safe chemical substance to experiment with. I have some in the laboratory stores".

The Prof. summoned his experimental robot and, using a strange code, quickly instructed

it to bring some Rochelle salt from the stores. A few minutes later, guided by its electronic brain, a masterpiece of experimental electronic wizardry which the professor has connected using microprocessors and other miniature and integrated-circuit type devices, the robot returned and carefully presented to the Prof. a jar labelled 'Sodium Potassium Tartrate (Rochelle Salt)' and containing a white powder. It also gave the Professor a small package, which he unwrapped, and inside, Bob could see two clear colourless crystals of Rochelle salt.

SLICING

"You could experiment with one of these crystals Bob, by slicing it up carefully into thin slices in various directions parallel to the crystal faces, and across them. But you must take considerable care, because three of the physical properties of Rochelle salt may cause difficulty; one is that the crystals are brittle and must not be subjected to heavy stress or shock. So the material must be handled gently to avoid breakage.

Another property of Rochelle salt is that it is soluble in water, and the crystals may easily be destroyed by water or damaged



The Home Radio Components catalogue has 200 pages filled with over 5,000 items, well over a thousand of them illustrated. With every catalogue comes a free bargain list showing many items at such give-away prices that the savings can pay for the catalogue several times over. The catalogue costs just £1 plus 40p for post and packing. Send for one today!

Please write your Name and Address in block capitals

NAME
ADDRESS

HOME RADIO (Components) LTD., Dept. EE,
234-240 London Road, Mitcham, Surrey CR4 3HD



POST THIS COUPON with cheque or p.o. for £1.40

(Regn. No. London 912966)

HOME RADIO (Components) LTD. Dept. EE., 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422



TRAMPUS ELECTRONICS LTD

58-60 GROVE RD.
WINDSOR, BERKS.
SL4 1HS.
TEL. 54525

ADD 8% VAT TO PRICES MARKED *
ADD 12% TO ALL OTHER PRICES,
OR AS CURRENT VAT LEGISLATION
SEND C.W.O. (EXCEPT GOVT DEPT)
POST & PACKING 20P FOR THE U.K.
BARCLAYCARD & ACCESS BY POST
OR £5 MIN ON TELEPHONE ORDERS.
NEW CATALOGUE LIST FREE S.A.E.
MONEY BACK IF NOT SATISFIED.

FAST SERVICE



ON EX STOCK ITEMS
NORMALLY 24 HOURS



SEVEN SEGMENT LED DISPLAYS
BRIGHT DL707 COM ANODE &
DL704 COM CATH. 0.3" £1*
DL747 0.6" JUMBO CA £1.25*

RED LEDS 10P.

RED LEDS 209 STYLE 0.125" OR 0.2" DIA. NO CLIP-10P*
TIL209 RED LED & CLIP 12P*
BIG 0.2" RED LED & " 14P*
GREEN OR ORANGE LEDS 29P*
ORP12 54P*2N5777/OCPT1 34P*

TRAMPUS THE GREAT BRITISH DISTRIBUTOR



INDUSTRIAL, EDUCATIONAL, TRADE & EXPORT SUPPLIED, SEND FOR OUR FREE CATALOGUE LIST SAE MANUFACTURERS EXCESS STOCKS PURCHASED. DISCOUNTS 10% OFF 100 up, 15% OFF 1000 up, ...

TOP DISCOUNTS.

INTEGRATED CIRCUITS

555 TIMER 34p*	LM380(60745) £1.11
555 2 x 555 90p*	LM331 Preamp £2
703 RP/IF AMP 29p	LM3900 4xOPA 53p*
709 T099 or DIL26p*	MC1303 2xPre £2
710 DIL14 35p*	MC1310 stereo£2
723 Regulator 44p*	MC1312P SQ £1.70
741 DIL 8pin 21p*	MC1330 75p
741 DIL 14pin 31p*	MC1339 Preamp£2
741 T099 33p*	MFC4000B 1W £2p
747 DUAL 741 69p*	MFC6030 7p
748 DIL 8 pin 32p*	NE536 PETOPA £2*
7805 5V1A+reg1.35*	NE540 or 550 £2*
7812 & 7815ea1.40*	NE555 TIMER 34p*
78013 6W AF £1.50	NE555 2x555 90p*
AY51224 CLOCK f4 *	NE560/1/2/5/6/7f3
CA3046 54p*	SN72741 aa 741
ICL8038 Sigen f4 *	SN76601 IF 74p
LM300H £1 *	SN76611 IF £1
LM301A D11 8 33p*	TBA800 5W AP 84p
LM309K 5W reg f2 *	TBA810 7W AF 94p
LM309H T05 can f1 *	ZN414 Radio f1.19
LM318 70VuoOPA f3*	NEW 1466/69 f4

CMOS TTL

4000 14p*	7400 12p*	7490 39p*
4001 15p*	7401 13p*	7491 75p*
4002 16p*	7402 15p*	7492/93 45p*
4003 16p*	7404 19p*	7495/96 72p*
4009 10p*	7408/10 18p*	74100 £1.25*
4011 16p*	7413 29p*	74107 32p*
4012 17p*	7440 16p*	74121 29p*
4049 50p*	7441 71p*	74123 69p*
4069 20p*	7442 72p*	74141 74p*
4501 26p*	7447 79p*	74145 65p*
4511 £1.65*	7470/72 27p*	74147 £2.50*
4528 11*	7475/74 31p*	74151 75p*
4543 £2*	7475/36 35p*	74154 £1.40*
4553 £5*	7486 35p*	74196 £1.50*

DIL SOCKETS PROFESSIONAL QUALITY
8pin, 14pin & 16pin ALL 12p ea *
SOLDERCONS 100 49p* 1000 £3.95*

NEW LOW PRICES.

TRANSISTORS AND DIODES

1N50 PNP 20p Fr* TIP31/32.50p*
AC127/B 178 15p* TIP131/32.69p*
AD161/162 ea36p* TIP41/42ea 66p*
BC107 8p* TIP2955 69p*
BC107B 13p* TIP3055 65p*
BC108 8p* T1S43 UJT 26p*
BC108B or C 13p* 1N914/4148 4p
BC109 9p* 1N4001/2 4p*
BC109B or C 12p* 1N4004 5p*
BC147/8/9 8p 1N4007 7p*
BC157/8/9 11p 2N706/8 14p*
BC167/8/9 12p 2N2646 UJT 40p*
BC177/8/9 16p 2N2904/5pmp29p*
BCR12/3/4a/110 2N2926 ory 7p*
BC212/3/4a/112p 2N3053 17p*
BCY70/1/2 15p* 2N3055 90W 33p*
BD131/132ea 36p* 2N3055 115W45p*
BFY50/51 15p* 2N3614 T03 31p*
BFY52/53 16p* 2N3702/3/4 10p*
BSX19/20/2119p* 2N3705/6/7 9p*
BZY88 ZENER 10p 2N3708/9 9p*
C106D SCR 54P* 2N3710/11 15p*
MJ2955 T03 99p* 2N3819 a23e17p
MJE2955 99p* 2N3820 PPR40p
MJE3055 65p* 2N3904/5/6 12p*
OAS1/9/1 5p 2N5457 PET 32p
TIP29 & 30 40p* BRIDGE1A50 20p*

BARGAIN PAKS FULL SPEC 11ea.

PAK A: 11 RED LEDS full spec f1*
PAK B: 5 741C 8 PIN OP AMP f1*
PAK C: 4 2N3055 f1* D 12 BC109 f1*
PAK E: 11 BC182 f1 P 11 2N3704 f1
PAK G: 7 BFT51 f1* R 8 2N3819 f1
PAK J: 6 2N3053 f1* K 40x1N914 f1
PAK L: 3 T099 3055 f1* N 25 OAS11
PAK P: 20 PLASTIC BC109 TYPENpnf1

10-365PF TUNER, SINGLE GANG FOR
MED/SHORT WAVE, XTAL SET etc f1*
SETS/IF CANS 455/470KHZ TOKO f1*

Full spec devices

DALO pen 75p

PCB ETCH KIT 3 ITEMS £2*
ETCH RESIST PEN 2TIPS 75p*
FPC ETCH PAK TUB 600gm f1*
6x4" SRBP 45p*NTLON F/Gf1*
SCR+AND TRIACS BR100 25p*
TAG 1A400V 50p*1A500V 65p*
1A50V 37p*, C106D 4A400 60p*
TRIACS:SC146D 10A400V f1*
DISCO TRIAC 15A400V £2*

AUDIBLE WARNING BLEEPER
12V35mA £1.20f10 off f1*
CAPACITORS 22pF01 5p
ELECTROLYTIC IN 10 & 25V
1/2/10/50/100 7p 50V 10p
200/500 10p. 1000/25 20p

vero

VERO 0.1" PITCH COPPERCLAD
24"x5" 40p* 31"x5" 45p*
24"x31"36p* 31"x31" 40p*
31"x17" £2 FACE CUTTER 65p*
DIL BREADBOARD 2"x4" f1 or
6"x4" £2, YERO PINS 36 30p*
BLACK PLASTIC CASES 42mmx.
80x60 50p*100x75 60p*89*
120 70p, DESOLDER BRAID 50p

Sparkrite mk2

Capacitive discharge
electronic ignition kit

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE
(Oct. '74)



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel-consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition and up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device. Includes switch connectors, mounting bracket and instructions. Cables excluded. Also available: RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service. - phone (0922) 33008

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

Note:- vehicles with current Impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT post & packing.

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, DEPT EE/4
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

Item	Price	Quantity	Notes
Mk. 2 DIY Ass. Kit	£11.80	<input type="text"/>	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth	£14.97	<input type="text"/>	
Mk. 2 Ready Built Positive Earth	£14.97	<input type="text"/>	Cheque No. <input type="text"/>
Ignition Changeover switches	£4.30	<input type="text"/>	Send SAE if brochure only required.
R.P.M. Limit systems in above units	£2.42	<input type="text"/>	

CRESCENT RADIO LTD.

164-166 HIGH ROAD LONDON N22 6EJ 888-3206
(also) 13 SOUTH MALL, Edmonton, N.9 803-1685
MAIL ORDER DEPT. 1 St Michaels Terrace Wood Green
London N22 4SJ Phone 888-4474

POWER PACKS
PP1 Switched 3, 4, 6, 7, 9 and 12 volt @ 500 m/a, with on/off switch and pilot light.
Size - 130 mm x 55 mm x 75 mm
ONLY - £5.50 + 8%

CASSETTE MICROPHONE
On/Off switch for Remote Control. Split Lead with 2.5mm and 3.5mm plugs. Standard Cassette Mics to suit all types. Complete with Desk Rest.
Please state which Impedance required 200ohm/50K.ohm.
PRICE £1.60 + 12 1/2% VAT.

P.O. ETCHING KIT
This kit contains all that the constructor will need to etch the circuits of his own design.
Contents—Plastic etching dish. Sample copper clad board. Laminate Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions.
Complete and Big Kit Value at £4.25p + 8% VAT.

FERRIC CHLORIDE
Anhydrous ferric chloride in double sealed one pound Poly packs.
OUR PRICE - 65p + PP + 8% per lb.

3 KW WATTS PSYCHEDELIC LIGHT CONTROL UNIT
Three Channel Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed).
£18.50 plus 75p P. & P. + 8%



ABS PLASTIC BOXES
Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.
1005 - 105mm x 73mm x 45mm = 60p
1006 - 150mm x 74mm x 47mm = 80p
1007 - 185mm x 124mm x 60mm = £1.80
1021 - 106mm x 74mm x 45mm = 57p (sloping front) Plus 8% VAT

"C100" 100 WATT AMPLIFIER
All built and tested, mounted on a plain aluminium chassis which measures 18" x 9 1/2" x 4" and which you can mount into a cabinet of your choice. Four Controlled Inputs, Master Volume, Treble, Middle and Bass Controls. S/C protected output. 100 watts Clean into 8ohm L/S. Ideal for Disco, Music Groups, PA and Clubs.
A Bargain at £48 + £1 carr. + 8% VAT.

TI MULTI-METER
Ideal tester for everybody interested in electronics. Weighing less than 100 grammes and only 60mm x 24mm x 90mm.
Ranges: AC volts: 0.10v, 50v, 250v, 1,000v. DC volts: 0.10v, 50v, 250v, 1,000v. DC current: 0.1m/a, 0.100m/a. Resistance: 0.150K ohm.
PRICE £5.50 + VAT 8%

MINI LOUDSPEAKERS
2 1/2" 80 ohm 90p + 12 1/2% VAT
2 1/2" 40 ohm 90p
2 1/2" 8 ohm 90p

BARGAIN PROJECT BOX
A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).
OUR PRICE 50p + 8%

U.K. CARR. All prices are excluding VAT. Please add to each item the VAT rate indicated to all orders.
ACCESS AND BARCLAYCARD ACCEPTED



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free! Brochure, without obligation to: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,** P.O. Box 156, Jersey, Channel Islands. **EEK47**

NAME

ADDRESS

(Block caps please)

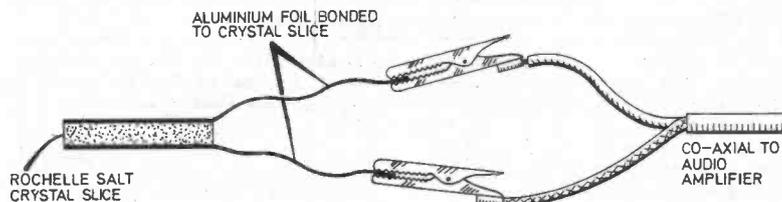


Fig. 1. The crystal pick-up constructed by Bob.

by perspiration during handling. So to avoid this, use a pair of plastic tweezers instead of picking the crystals up in your hands.

The third property is sensitivity to high temperatures. You must be careful not to overheat the material by rapid sawing, drilling or polishing as the crystal is likely to melt".

Now Bob, who had a few moments previously been full of enthusiasm, began to feel dubious.

"What if I damage one of those crystals, Prof., and make it unusable? Then there would only be another one left, and I would not be happy to break that as well".

"Don't worry about that, Bob. The Professor advised. "You can experiment all you like with these two, as we can easily grow some more from the Rochelle salt in the bottle. By referring to a suitable book on the subject of

physical chemistry you can easily find out how to grow the crystals from a saturated solution of water, using the same type of procedure as for say, copper sulphate crystals".

Bob was reassured, and began to very carefully cut one of the crystals into slices of about 1mm thick, rubbing the cut smooth with fine emery paper. Although he broke one or two of these delicate slices, he soon had a number of them ready.

CONTACTS

"Usually the metals used for the purpose of contacting the crystal surfaces are silver, or aluminium foil, Bob. Would you like to attach a piece of aluminium foil to each face of some of these slices of crystal, using quick set epoxy resin, whilst I try out some silver conductive paint

on the others?"

Bob cut some aluminium foil into narrow strips, and, using quick set epoxy resin, bonded some of the foil to each crystal slice as shown in Fig 1, leaving plenty of spare foil loose, for the purpose of making connections.

A few minutes later, when the epoxy resin was set, Bob, knowing that it would be difficult to attempt to solder the aluminium foil, and that this would almost certainly melt the crystal, prepared a length of thin screened wire with a pair of crocodile clips at one end. He connected the crocodile clips to the aluminium foil as in Fig. 1, plugged the other end of the screened wire into the input of an audio amplifier and carefully turned up the volume control. Now, by gently tapping the crystal, the tapping sound could be clearly heard through the loudspeaker and it was obvious to Bob that he had made a simple crystal pickup capable of converting sounds and vibrations into electrical signals suitable for amplification.

Meanwhile the Prof. had been doing some experiments with the other crystal slices, and was busily making another type of pick-up, which could be used as a contact microphone.

Continued next month.

Do you always get your copy? if not—fill in the coupon below without delay!



To	NAME
(Name of Newsagent)	ADDRESS.....
Please reserve/deliver the MAY issue of EVERYDAY
ELECTRONICS (35p) on sale APRIL 15th, and continue
every month until further notice.

GEORGE HYLTON brings it down

THE idea that a resistance, any resistance, just sitting by itself, minding its own business, should automatically generate a voltage seems at first sight to be very strange. Why should it? An electric cell, sitting alone, can generate an e.m.f., a voltage, because the chemicals inside it work that way. But a simple resistor, with no electro-chemical contents . . . surely not?

Yet the plain fact is that it happens. Resistors do generate voltages, and these voltages manifest themselves as electrical noise. How do they do it? Well, any source of electrical energy must have some sort of driving power. In the case of a cell, it's the chemicals. In a power station, it's the steam or water which turns the turbogenerators. In a cycle dynamo it's the muscle power of the cyclist, turning the wheel. In a resistor, it is *heat*.

Energy

Any piece of matter, solid liquid or gas, contains energy in the form of heat. If you cool it, you extract heat, which proves that the heat was there in the first place. If you could go on cooling it until *all* the heat was extracted it would have a temperature of about minus 273 degrees C, known as absolute zero (0 degrees K). But real-life resistors, even if they are at the South Pole, have temperatures far above absolute zero. So they all contain thermal energy.

This means that the atoms which they are made of are in a state of thermal agitation. The electrons which orbit the atomic nucleus can gain or lose energy from their neighbours. If they gain enough energy they may escape from their parent atom and skip to another. Since an electron is a charged particle, this movement is a tiny local *current* inside the resistor. (A current is just a movement of electrical charges.)

So, all the time, in the atoms and molecules which make up the resistor, there are tiny currents. They can flow in any direction and frequently they must happen to flow in opposite directions and cancel out. However, there's a definite chance that at any one instant enough charges will be moving in the same direction to set up an appreciable voltage across the resistor. This voltage changes constantly, both in size and polarity and is quite unpredictable.

Random a.c. voltages like this are called *noise voltages*. This thermal noise is an equal mixture of all frequencies. By analogy with white light, which is an equal mixture of all colours, this sort of noise is called *white noise*.

Power

If the resistor is large, there are more moving charges but also a greater chance that at any instant there will be opposite movements whose effects cancel one another. For this reason the amount of noise is the same for all shapes and sizes of resistor. Similarly it turns out that the noise power is the same for *all* values of resistance. In a low resistance the noise voltage is low but the current high. In a high resistance it's the other way round. But the power, which is current times voltage, is the same.

The noise power, in fact, depends on only two factors. One is the temperature: the hotter the noisier. The other is the range of frequency over which you measure the noise.

Since white noise is an equal mixture of all frequencies, the more frequencies you take into account the greater the noise. So the essential factor which controls noise power is temperature times bandwidth, or TB for short. To get the noise power in watts you have to multiply this by a fixed number, a constant. It's called Boltzmann's constant, after the physicist who first

computed it, and it's written *K* for short. So noise power in any resistance is *KTB* watts.

This may sound like a lot of noise power. In fact, *K* is a very small number indeed so the power (at ordinary temperatures) doesn't really come out in watts, or even microwatts. At room temperature (which is about 300 degrees on the absolute or Kelvin scale, which is the one to use here) the available noise power over the whole audio band up to 20kHz is only 80 $\mu\mu\text{W}$. The noise voltage depends on the resistance. For a resistance of 10 kilohms it is, over the entire audio band, 2 μV .

In most ordinary audio circuits this noise voltage is appreciably increased by noise generated by transistors in the amplifiers used. Also, carbon resistors themselves generate extra noise when d.c. flows in them. However, the thermal noise imposes an absolute limit on signal-to-noise ratio.

The Sky

In radar and radio astronomy there is another source of noise—the sky. For example, the sun, being a hot body, generates noise. Radar engineers often describe this noise in terms of a *temperature*. If the temperature of the aerial and receiver were raised, just as much noise would be generated as arrives from space. So you can say that a radar receiver pointed at the sun has a *noise temperature* of so many degrees.

It is impossible to escape entirely from noise from space. The whole of space generates a tiny amount of background noise, equivalent to a temperature of about 3 degrees above absolute zero. Astronomers who think that the universe began as a huge fireball which exploded and spread out regard this 3 degrees as the temperature to which the universe has now cooled since the original "Big Bang."

to earth

PLEASE TAKE NOTE

We apologise for a mistake in the *Quasi-Quad Adaptor*, March 1977. In Fig. 5 the signal wires of the screened leads to VRI should be transposed.

There is a link wire missing from the drawing shown in Fig. 2 in the *Multi-Tester*, January 1977. On switch S1c the link between positions 2 and 4 (Ω and mA) has been omitted.

Careers and Hobbies in Electronics.

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.



Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

FREE! Brochure without obligation to: EEL 47
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
 P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME _____
 ADDRESS _____

BLOCK CAPS PLEASE

THE OPEN DOOR TO QUALITY

THE COVER IS BLACK & WHITE



4th ISSUE INCLUDES NEW METERS

This 144 page catalogue—Electrovalue Catalogue No. 8 (Issue 4, up-dated) offers items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts continue on many purchases; Access and Barclaycard orders are accepted. **FREE POSTAGE** on all C.W.O. mail orders in U.K. over £2.00 list value (excluding V.A.T.) if under odd 15p handling charge.

BUILD WITH THE EVERYDAY ELECTRONICS TEACH-IN KIT nett **£15.75** inc. V.A.T.
from Electrovalue as described in this journal

144 Page

40p

inc. refund voucher worth 40p

ELECTROVALUE LTD

All communications to Dept. EE4.
 28 ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY TW20 0EB. Phone Egham 3603. Telex 284475.
 NORTHERN BRANCH: 660 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4345.
 Shop hours both addresses 9-5.30 p.m.; 1 pm Sats.

IT'S EASY WHEN YOU KNOW!

To avoid missing your copy of EVERYDAY ELECTRONICS—simply complete this order form and hand it to your newsagent.

ORDER FORM

To: (name of newsagent)

Address

Please reserve/deliver every month one copy of EVERYDAY ELECTRONICS until further notice.

My Name

Address

TECHNOMATIC LIMITED

54 Sandhurst Road, London NW9

DISTRIBUTORS OF SEMICONDUCTORS

Please see our advertisements in W.W., P.E., P.W., TV., E.T.I., & Elektor.

MAIL ORDER ONLY



RECEIVERS and COMPONENTS

BUILD 5 TRIED AND TESTED CIRCUITS. Digital precision timer (2-30 min.), Sensitive burglar alarm. Voltmeter/ammeter. A.F. Circuit Tracer Metal Detector. Diagrams 50p each + SAE (£2 for 5). Buildit, 100 Colstead, New Ash Green, Kent DA3 8LW.

P.C.Bs Paxolin, 5 1/2in x 5 1/2in, 6 for 85p, 12in x 9in 50p, 17 1/2in x 9 1/2in, 90p. Fibre Glass, 13in x 5 1/2in, 80p, 13in x 11in, £1.50. D.S. 7in x 8in, 70p. Neons, 20 for £1. 5 Floure Resettable Counter 18/22V works on 12V. £3. Assorted 74 Series I.Cs on panel(s), 10 for 90p. 3 Assorted Meters £2-10. 100 Assorted S/Mica Caps 75p. Silicon Diodes 650V 1 1/2, 10 for 60p. List 15p. Refund on purchase.

7lb Assorted Components, £2-75.

J. W. B. RADIO

2 Barnfield Crescent, Sale, Cheshire, M33 1NL
All items post paid. Mail order only.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £8.25 plus 20p P&P. 'Brain-Freeze' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £3.80 plus 20p P&P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5.00 each plus 20p P&P.

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey. (E.E.)

Loud Sirens for Burglar Alarms etc. 6 v. D.C. £1.25. Buzzer Alarms 65p. Reed Switch small 10p. Magnets 6p. Large Reed Switch 12p. Micro Switches 10p. Bulgin Key Switch 89p. Electrolytics 680uf 25v 10 for 57p. 8Ω Earphone & Plug 16p. 5 pin Din Plugs 15p. Component Panels 15p. Jap Radio Tuning Capacitors 30p. Knobs 5p. 90v Neons 8p. Resistors 1W 10Ω-10M 2p ea. PRICES INCLUDE VAT. ADD 15p POST.

GRIMSBY ELECTRONICS

64, Tennyson Rd., Cleethorpes, Humberside
Veroboard, Pots etc. at our Lambert Road Components Shop (open Saturdays), Bargains List 9p

SERVICE SHEETS

SERVICE SHEETS, Radio, TV etc., 50p and SAE. Catalogue 20p and SAE. Hamilton Road, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICE for service sheets of Radio, TV etc. 75p plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

SMALL ADS

The prepaid rate for classified advertisements is 14 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £9.00 per single column inch (2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower; Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

BOOKS and PUBLICATIONS

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4.50, request free circuit diagram Stamp brings details unique TV publications. Aussee, 76 Church Street, Larkhall, Lanarkshire.

Start your own business printing pound notes

Printing pound notes? Well not quite—but 'Start your own business rewinding electric motors' could easily be your licence to make money in 1977.

Levishly illustrated, this unique instruction manual shows step by step how to rewind motors, working part or full time, without experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc. etc.

A goldmine of information and knowledge. Only £3.90 plus 25p P & P from:

MAGNUM PUBLICATIONS, Dept EE5, Brinkway Trading Estate, Brinkway, Stockport SK3 6EZ.

FOR SALE

NEW ISSUES OF 'EVERYDAY ELECTRONICS' available from April 1974 up to date, cover price plus 15p postage per copy—BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

WANTED

WANTED EE MAY 1972 or Photocopy of half term test answers. 01-907 2096.

WANTED. Nov. 71, Dec 71, Jan. 72, March 72, March 73, April 73, May 73, E.E. Magazines. £1. each offered. PACKER, 21 Calder Close, Swindon, Wilts.

MISCELLANEOUS

RECHARGEABLE NICAD BATTERIES 'AA' (HP7)—£1.26. Sub 'C'—£1.29. 'C' (HP11)—£2.38. 'D' (HP2)—£2.92. PP3—£4.98. Matching chargers, respectively, £4.48, £4.48, £5.24, £5.24, £3.98. All prices include VAT add 10% Post & Package. SAE for full list, 1 plus, if wanted, 50p for 'Nickel Cadmium Power' Booklet. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands B73 6PP. Tel. 021-354 9764.

DIY BURGLAR ALARM EQUIPMENT

COMPLETE DIY INSTALLATION KITS Magnetic switches, Pressure Mats, Bells and Bell Housing, Junction Boxes, Control Panels, Foli, etc. . . .


Send s.a.e. for lists:

DACH ELECTRONICS, 13 Hamilton Square, Birkenhead, Merseyside, L41 6BP. Tel. 051 647 5030.

STYLI, CARTRIDGES & AUDIO LEADS ETC. For the best at keenest prices send SAE for free illustrated list to: **FELSTEAD ELECTRONICS,** (EE), Longley Lane, Gatley, Cheadle, Cheshire SK8 4EE.

NEW! From H.M. ELECTRONICS A BASIC D.I.Y. CASE

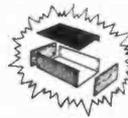- ★ One piece aluminium chassis.
- ★ Whitewood Ply end cheeks, that can be painted, stained, etc.
- ★ Simulated black leathergrain lid.



REAL VALUE FOR MONEY

GB1 14" x 6" x 2"	£2.65	Post and
GB1a 9" x 6" x 2"	£2.05	Packing
GB2 14" x 7" x 3"	£3.25	90p
GB3 14" x 9" x 4"	£3.95	Plus
Mini-Bec 7" x 5" x 3"	£1.75	V.A.T.

Other Types and Styles. Dry Transfer lettering. Send 15p for leaflets to:—
275a Fulwood Road, Broomhill, Sheffield, S10 3BD

BINOCULAR MAGNIFIER



FOR PRECISION CLOSE-UP WORK—LEAVES BOTH HANDS FREE
2, 2½ or 3x Model with Hinged Lens Mount

See close-up work with less eye strain. Lightweight adjustable headband. Powerful optically ground lenses. Can be worn over normal glasses. Essential Industry, Home Workshop, Collecting, Modelling, Jewellery, Watchmakers. Any fine work. DE LUXE model with superior quality lens. PLUS hinged lens mount. 2x model, £9.95 + 75p p. & p., 2½x model, £10.50 + 75p p. & p., 3x model, £10.95 + 75p p. & p. Also Headstrap Focussable Torch with pocket Battery Container. £8.70 post paid.



MICROJET WELDER

A TINY FLAME UP TO 5000°F!
WELDS—BRAZES—SOLDERS

£19.25

INC. FLAME TIPS

Precision tool using combination of butane and compressed oxygen or micronox. Pencil lead thin flame size. Adjustable to 5,000°F. Cuts metals welds, brazes and solders gold, silver. Ideal ELECTRICIANS model engineering, opticians, dentists, silver-smiths, jewellery, clockmakers, electronic and computer servicing. Up to 40 minutes' use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder. £1.98 extra including post. £19.25 + 95p p. & p. Send £20.20.

Access accepted. Send Name, Address & No. **JOHN DUDLEY & CO. LTD.,** Dept. EE12, 301 Cricklewood Lane, Finchley Rd., London, NW2. Tel. 01-458 5917. (Callers welcome).

GLASS FIBRE P.C.B.'s

From your own tape film or ink master. Send S.A.E. for quotation.

EVERYDAY ELECTRONICS P.C.B.'s In glass fibre tinned and drilled. Dec. '76. Mini organ £2.48.

PRACTICAL ELECTRONICS P.C.B.'s Send S.A.E. for list. C.W.O. please.

PROTODESIGN, 4 Highcliffe Way, Wickford, Essex SS11 1LA.

BARGAIN BOX FOR BEGINNERS containing 2 Transistor/component panels, 1 Relay, 1 Rectifier, 1 earphone insert, 1 mike insert, 2 diodes, 1 buzzer, 3 core cord, 1 salvaged tool—an ideal collection for experiments: £1.80 Inc. VAT & P.P. 5 digit counter, 10 digits/sec., 24-48v. non-reset, brand new GPO type 85p Inc. Also 3, 4, 5, 6 & 9 core cords many other telephone spares at give away prices!

Trade enquiries welcome. S.A.E. for lists or orders to:

B. B. SUPPLIES

141, Shalmsford St., Near Canterbury, Kent. CT4 7QZ.

I.C. EXPERIMENTER'S KITS

Learn about modern electronics with our new series of Kits on digital logic techniques. Each Kit contains specially selected I.C.s, Holders, Veroboard, LEDs and instructions.

Available £4.00 each (including P & P)

Kit One—Gates Kit Two—Flip-Flops

Kit Three—Shift Registers.


Kit Four—Counters Kit Five—Displays

S.A.E. for further details to:

AUTOMATED HOMES

69 High Street, Ryton, Coventry CV8 3JF (Mail order only)

LOUDSPEAKERS

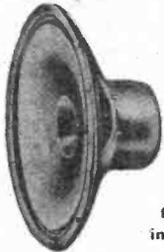

Speakers, kits and cabinets for D.I.Y.,

Hi Fi, P.A., Disco,

etc. by EMI, Fane,

Goodmans,

Baker, Kef, Elac,

Richard Allan,

Wharfedale, etc.

Send stamp for

freebooklet "Choosing a speaker."

WILMSLOW AUDIO

Dept. EE, Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Tel. Wilmslow 29599

ENAMELLED COPPER WIRE

SWG	1 lb	8oz	4oz	2oz
14-19	2.40	1.20	.60	.30
20-29	2.45	1.60	.82	.50
30-34	2.60	1.70	.89	.64
35-40	2.85	1.90	1.04	.75

Inclusive of p&p and VAT.

SAE brings Catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4 9BW

Reg: office 22, Coningsby Gardens.

BUILD THE

TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit; 4,000 sold
- Weighs only 22oz. Fitted with Faraday shield
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped addressed envelope for leaflet

Complete Kit £14.75 Built & tested £19.75
Post £1.00-£1.18 VAT (8%) Post £1.00-£1.38 VAT (8%)


MINIKITS ELECTRONICS

4b CLEVELAND ROAD, LONDON, E11 2AN (Mail order only)

DENCO (CLACTON) LIMITED

Dept. E.E.

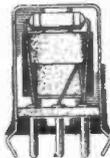357-8-9 OLD RD., CLACTON-ON-SEA ESSEX CO15 3RH



Our components are chosen by technical authors and constructors throughout the world for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment.

General Catalogue showing full product range 34p. Overseas Customers 70p, Air-Mail Post Paid.

U.K. & OVERSEAS MANUFACTURERS/STOCKISTS ENQUIRIES WELCOME

Australian Readers Please Note—Our Complete Range of Coils are available from Hobipak, Box 224, South Carlton, 3053, Victoria, Australia and Watkin Wynne Pty. Ltd., 32, Falcon Street, CROWS NEST, 2065, AUSTRALIA. P.O. Box 392.

4-STATION INTERCOM



£18.95

+ V.A.T. £1.62

Solve your communication problems with this 4-station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Completes with 3 connecting wires each 60ft. and other accessories. P. & P. 90p.

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £33.74 per pair P. & P. 90p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£13.95

VAT £1.12

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conferences" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch. Volume. Direct tape recording model at £16.95 + VAT £1.38 P. & P. 75p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (E.E.A)
169 KENSINGTON HIGH STREET, LONDON, W8

PRINTED CIRCUIT KIT £3-65

Make your own printed circuits. Contains etching dish, 100 sq ins of pc board, 1lb ferric chloride, etch resist pen, drill bit and instructions.

JC12 AMPLIFIER

6W IC audio amp

with free data and

printed circuit £1.95

DELUXE KIT FOR JC12

Contains extra parts except JC12 needed to complete the amp including balance, volume, bass and treble controls. Mono £2.09. Stereo £5.25

JC12 POWER KIT

Supplies 25V 1 Amp £3.65.

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono £1.50. Stereo £3.00. Type 2 for ceramic or crystal pickups. Mono 88p. Stereo £1.76.

SINCLAIR IC20

IC20 10W+10W stereo integrated circuit amplifier kit with free printed circuit and data £4.95.

P220 Power supply kit for above £3.65

VP20 Volume, tone-control and preamp kit £8.95.

JC46 AMPLIFIER

New integrated circuit 20W amplifier kit complete with chip, printed circuit and data £3.95.

FERRANTI ZM414

IC radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send sae for free data.

BATTERY ELIMINATORS

RADIO MODELS

50mA with press-stud battery connectors. 9V £3.45. 6V £3.45. 9V+9V £5.45. 6V+6V £5.45. 4½V+4½V £5.45.

CASSETTE MAINS UNITS

7½V with 5 pin din plug. 150mA £3.65.

3-WAY MODELS

With switched output and 4-way multi-jack connector. Type 1: 3/4/6V at 100mA £2.30. Type 2: 6/7/9V at 150mA £2.90.

FULLY STABILISED MODEL £5.45

Switched output of 3/6/7/9V stabilised at 400mA.

CAR CONVERTERS £5.10

Input 12V DC. Output 6/7/9V DC 1Amp stabilised

BATTERY ELIMINATOR KITS

Send sae for free leaflet on range.

100mA radio types with press-stud battery terminals. 4½V £2.10. 6V £2.10. 9V £2.10. 4½V+4½V £2.50. 6V+6V £2.50. 9V+9V £2.50.

100mA cassette type 7½V with 5 pin din plug £2.10.

Transistor stabilised 8-way type for low hum. 3/4/6/7/9/12/15/16V. 100mA. £3.20. 1 Amp £3.50.

Heavy duty 13-way types 4½/6/7/8/11/13/14/17/21/25/28/34/42V. 1 Amp model £4.95. 2 Amp model £7.95.

Car converter kit input 12V DC. Output 6/7/9V DC 1A transistor stabilised £1.95.

BATTERY ELIMINATOR BARGAINS

MILLENNIA KITS

5 Transistor highly stabilised power units. Switched 1 to 30V in 0.1V steps. Send sae for free leaflet. 1 Amp kit £12.45. 2 Amp kit £14.95. Case £2.95 extra.

MAINS TRANSFORMERS

6-0-6V 100mA 94p. 9-0-9V 75mA 94p. 18V 1A £1.95.

0/12/15/20/24/30V 1A £3.65. 12-0-12V 50mA 94p.

0/12/15/20/24/30V 2A £4.95. 20V 2½A £2.55.

6-0-6V 1½A £2.55. 9-0-9V 1A £2.19. 12-0-12V 1A £2.49.

15-0-15V 1A £2.68. 30-0-30V 1A £3.39.

S-DECS AND T-DECS

S-DeC £1.94.

T-DeC £3.61.

µ-DeCa £3.97.

µ-DeCb £6.97.

IC carriers with sockets—

18 d1 £1.91. 10T05 £1.78.



SINCLAIR CALCULATORS AND WATCHES

Cambridge Memory £5.95. Cambridge Scientific £8.95. Oxford Scientific £13.30. Microvision pocket TV £1.65. Mains adaptors for other models (state type) £3.20. Assembled Gray Watch with free stainless steel bracelet £16.45. White watch £13.95.

SINCLAIR PROJECT. 80 AUDIO MODULES

PZ5 £4.95. Z40 £5.75. Pro. 805Q £18.95.

BI-PAK AUDIO MODULES

S450 tuner £20.95. AL60 £4.60. PA100 £14.95.

MK60 audio kit £31.95. Teak 60 £12.95. Stereo 30

£16.95. SPM80 £3.95. BMT 80 £3.82. Send sae for free data.

SAXON ENTERTAINMENTS MODULES

SA1208 £20.50. SA1204 £14. SA608 £13. SA604


£12. PM1201/8 £12. PM1202/8 £19. PM1201/4

£12. PM1202/4 £19. PM601/8 £12.

SWANLEY ELECTRONICS

Dept E.E. PO BOX 68, 32, GOLDSSEL ROAD, SWANLEY, KENT BR8 8TQ.

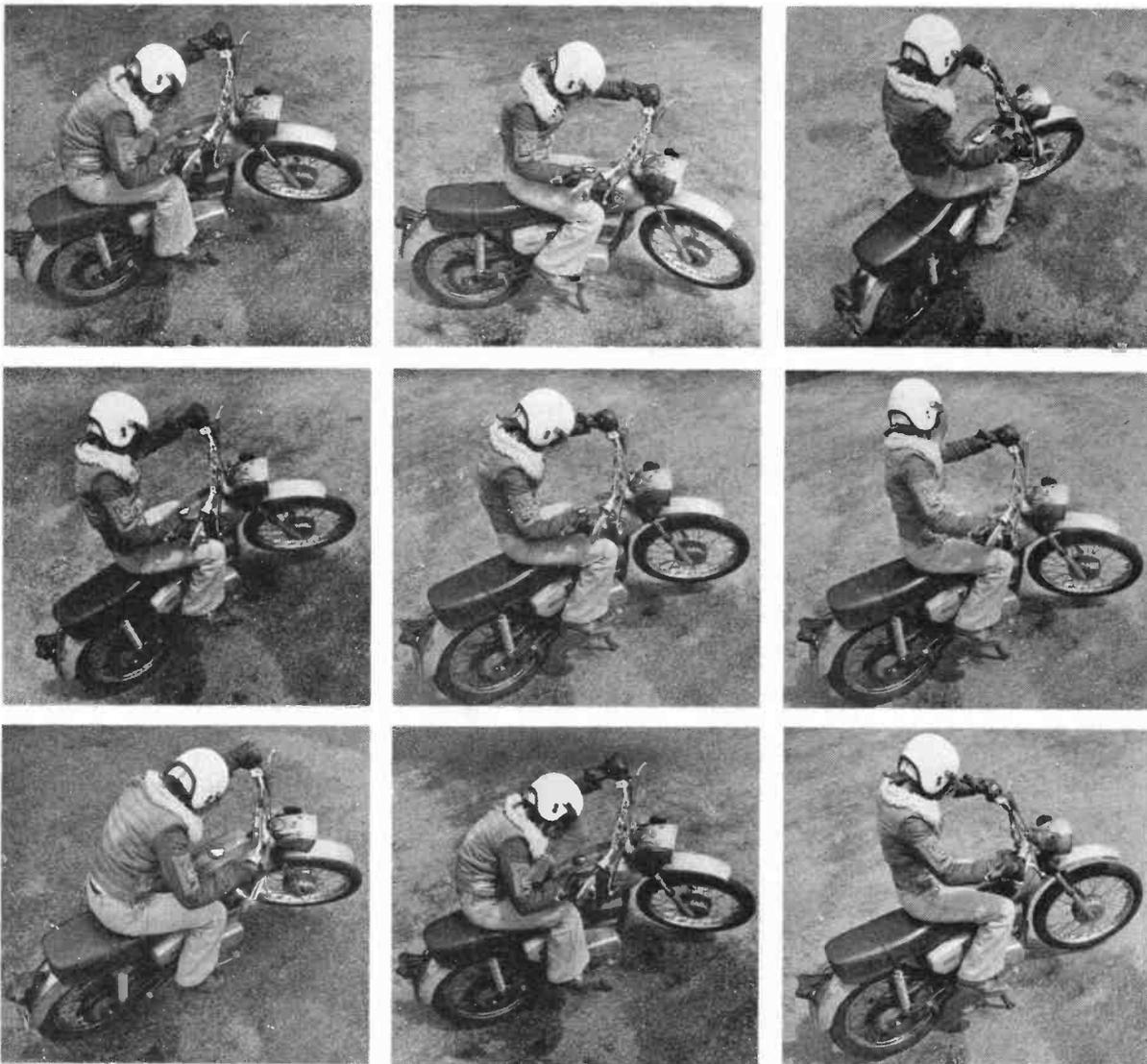Mail order only. We will not serve calls under any circumstances. Post 30p on orders under £4.50, otherwise free. Prices include VAT. Official orders welcome. Overseas customers please deduct VAT. Send S.A.E. for free leaflets on kits.



Go ride your bike

Our special feature "Begin Biking" shows you how. . .

So the biking bug's got you? Great. But first there are things you *must* know. Our special 6-page "Begin Biking" feature tells you about - the law, insurance, finance, paper-work, best buys, buying new, buying old, riding gear, training, clothing and costs.

Also ALL ABOUT FINISHES.

HONDA 125 CG Commuter bike put through its paces

Go ride your bike-in style-with

NEW
Motorcycling
Monthly

April issue, out Friday, 4th March

35p

PAKS—PARTS—AUDIO MODULES

PANEL METERS

4" RANGE

Size 4 1/2" x 3 1/2" x 1 1/2"

Value	No.	Price
0-50UA	1302	£4.50
0-100UA	1303	£4.50
0-500UA	1304	£4.50
0-1MA	1305	£5.00
0-50V	1306	£6.00

2" RANGE

Size 2 1/2" x 1 1/2" x 1 1/2"

Value	No.	Price
0-50UA	1307	£3.50
0-100UA	1308	£3.50
0-500UA	1309	£3.50
0-1MA	1310	£3.50
0-50V	1311	£3.50

MR2P TYPE

Size 42 x 42 x 30mm.

Value	No.	Price
0-50UA	1313	£4.80
0-1MA	1315	£3.20

EDGEWISE

Size 3 1/2" x 1 1/2" x 2 1/2"

Cut out 2 1/2" x 1 1/2"

Value	No.	Price
0-1MA	1316	£4.05
0-500UA	1317	£4.05

MINIATURE BALANCE/TUNING METER

Size 23 x 22 x 26mm

Sensitivity 100/0/100MA

No.	Price
1318	£1.95

BALANCE/TUNING

Size 45 x 22 x 34mm

Sensitivity 100/0/100UA

No.	Price
1319	£2.00

MIN. LEVEL METER

Size 23 x 22 x 26mm

Sensitivity 200UA

No.	Price
1320	£1.95

Vu METER

Size 40 x 40 x 29mm

Sensitivity 130UA

No.	Price
1321	£2.00

MINI MULTI-METER

Size 60 x 24 x 90mm

Sensitivity 1000 ohms/V

AC VOLTS 0-10, 50, 250, 1000	
DC VOLTS 0-10, 50, 250, 1000	
DC CURRENT 0-1-100mA	
Resistance 0-150K ohms	
No.	Price
1322	£5.95

P&P

Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.

TRANSISTORS

BRAND NEW — FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC126	0.16	BC109B	0.08	BC550	*0.14	BFY90	0.55	TIP42B	0.78	2N3707	*0.08
AC127	0.14	BC109C	0.08	BC556	*0.14	BFY50	0.14	TIP42C	0.95	2N3708	*0.07
AC128	0.12	BC147	*0.09	BC557	*0.13	BFY51	0.14	TIP2955	0.95	2N3708A	*0.07
AC128K	0.26	BC148	*0.09	BC558	*0.12	BFY52	0.14	TIP3055	0.75	2N3709	*0.07
AC132	0.15	BC149	*0.09	BC559	*0.14	BIF19	0.38	TI543	0.22	2N3710	*0.07
AC134	0.15	BC157	*0.12	BD115	0.50	BIF20	0.38	TI590	*0.18	2N3711	*0.07
AC137	0.15	BC158	*0.12	BD116	0.80	BIP19	0.80	UT46	0.20	2N3819	0.20
AC141	0.18	BC159	*0.12	BD121	0.65	20 MP	0.80	ZTX107	*0.10	2N3820	0.40
AC141K	0.30	BC167	*0.12	BD123	0.65	BRY39	0.45	ZTX108	*0.10	2N3821	0.60
AC142	0.18	BC168	*0.12	BD124	0.70	BUI105	1.90	ZTX109	*0.10	2N3823	0.40
AC176	0.12	BC169	*0.12	BD131	0.35	BUI05/02	1.95	ZTX300	*0.12	2N4058	*0.12
AC176K	0.26	BC169C	*0.12	BD132	0.38	MJE3055	0.60	2N2147	0.75	2N4059	*0.14
AC178	0.25	BC170	*0.10	BD131/	0.80	BU205	1.70	2N1613	0.20	2N4059	*0.12
AC179	0.25	BC171	*0.10	132 MP	0.80	BU208	2.40	2N1711	0.20	2N4061	*0.12
AC180	0.20	BC172	*0.10	BD133	0.60	BU208/02	2.95	2N1889	0.45	2N4062	*0.12
AC180K	0.30	BC173	*0.12	BD135	0.36	EI222	0.38	2N1890	0.45	2N4284	*0.18
AC181	0.20	BC177	0.16	BD136	0.36	MJE2955	0.88	2N1893	0.30	2N4285	*0.18
AC181K	0.30	BC178	0.16	BD137	0.38	MJE3055	0.60	2N2147	0.75	2N4286	*0.18
AC187	0.16	BC179	0.16	BD138	0.45	MJE3440	0.45	2N2148	0.70	2N4287	*0.18
AC187K	0.26	BC180	0.25	BD139	0.54	MP8113	0.45	2N2160	0.80	2N4288	*0.18
AC188	0.16	BC181	*0.25	BD140	0.60	MPF102	0.35	2N2192	0.38	2N4289	*0.18
AC188K	0.26	BC182L	*0.10	BD139/	0.60	MPF104	0.39	2N2193	0.38	2N4290	*0.18
AD140	0.60	BC183	*0.10	140 MP	1.20	MPF105	0.39	2N2194	0.38	2N4291	*0.18
AD142	0.85	BC183L	*0.10	BD155	0.60	MPS A05	*0.20	2N2217	0.22	2N4292	*0.18
AD143	0.75	BC184	*0.10	BD175	0.60	MPS A06	*0.20	2N2218	0.22	2N4293	*0.18
AD149	0.60	BC184L	*0.10	BD176	0.60	MPS A55	*0.20	2N2218A	0.20	2N4921	*0.55
AD161	0.36	BC207	*0.11	BD177	0.68	MPS A56	*0.20	2N2219	0.20	2N4923	*0.65
AD162	0.36	BC208	*0.11	BD178	0.68	OC22	1.50	2N2219A	0.24	2N5135	*0.10
162 MP	0.75	BC209	*0.12	BD179	0.75	OC23	1.50	2N2904	0.18	2N5136	*0.10
AF114	0.20	BC210	*0.11	BD201/	0.70	OC24	1.40	2N2904A	0.21	2N5138	*0.10
AF115	0.20	BC212L	*0.11	202 MP	1.70	OC25	0.60	2N2905	0.22	2N5194	0.26
AF116	0.20	BC213	*0.11	BD203	0.80	OC26	0.60	2N2905A	0.21	2N5245	*0.28
AF117	0.20	BC213L	*0.11	BD204	0.80	OC28	0.80	2N2906	0.16	2N5294	0.34
AF118	0.40	BC214	*0.12	BD203/	0.80	OC29	1.00	2N2906A	0.19	2N5296	0.35
AF124	0.30	BC214L	*0.12	204 MP	1.70	OC35	0.90	2N2907	0.20	2N5457	0.32
AF125	0.30	BC237	*0.16	BD220	0.80	OC36	0.90	2N2907A	0.22	2N5458	0.32
AF126	0.30	BC238	*0.16	BDY20	0.80	OC70	0.15	3N2926G	0.09	2N5459	0.32
AF127	0.32	BC251	*0.15	BDX77	0.90	OC71	0.15	2N2926V	*0.08	2N5551	0.38
AF139	0.58	BC251A	*0.16	BF457	0.37	TC144	*0.29	2N2926R	*0.08	2N6027	0.32
AF180	0.58	BC301	0.30	BF458	0.37	TC145	*0.29	2N2926R	*0.08	2N6121	0.70
AF181	0.58	BC302	0.28	BF459	0.38	TIP29A	0.44	2N2926B	*0.08	2N6122	0.70
AF186	0.58	BC303	0.32	BF594	*0.15	TIP2B	0.62	2N3053	0.16	40311	0.36
AF239	0.38	BC327	*0.16	BF596	*0.17	TIP2C	0.62	2N3074	0.22	40313	0.95
AL102	0.95	BC328	*0.15	BFR39	0.25	TIP30A	0.50	2N3055	0.40	40316	0.58
AL103	0.95	BC337	*0.15	BFR40	0.25	TIP30B	0.60	2N3414	*0.16	40317	0.36
AU104	1.00	BC338	*0.15	BFR79	0.28	TIP30C	0.70	2N3415	*0.16	40326	0.36
AU110	1.00	BC440	0.30	BFR80	0.28	TIP31A	0.54	2N3416	*0.29	40327	0.45
AU113	1.00	BC441	0.30	BFX29	0.25	TIP31B	0.66	2N3417	*0.29	40346	0.42
BC107A	0.08	BC461	0.38	BFX30	0.30	TIP31C	0.68	2N3614	0.85	40347	0.55
BC107B	0.08	BC477	0.20	BFX84	0.23	TIP32A	0.64	2N3615	0.90	40348	0.70
BC107C	0.08	BC478	0.19	BFX85	0.24	TIP32B	0.76	2N3616	0.90	40360	0.38
BC108A	0.08	BC479	0.20	BFX86	0.25	TIP41A	0.66	2N3646	*0.09	40361	0.38
BC108B	0.08	BC547	*0.12	BFX87	0.22	TIP41B	0.70	2N3702	*0.08	40362	0.38
BC108C	0.08	BC548	*0.12	BFX88	0.22	TIP41C	0.80	2N3703	0.08	40406	0.40
		BC549	*0.12	TIP42A	0.72	TIP42A	0.72	2N3705	*0.07	40407	0.25
								2N3706	*0.07	40408	0.48
								2N3707	*0.08	40409	0.52

74 SERIES TTL IC'S

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED ALL FAMOUS MANUFACTURERS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	0.14	7409	0.15	7441	0.64	7482	0.85	7493	0.40	74122	0.50
7401	0.14	7410	0.14	7442	0.64	7483	0.95	7494	0.88	74123	0.70
7402	0.15	7411	0.23	7445	0.90	7484	0.98	7495	0.75	74141	0.80
7403	0.15	7412	0.23	7446	0.90	7485	1.20	7496	0.80	74150	1.30
7404	0.15	7413	0.27	7447	0.70	4886	0.80	74100	0.80	74180	1.10
7405	0.15	7414	0.58	7448	0.80	7489	2.90	74110	0.50	74181	2.00
7406	0.30	7416	0.28	7475	0.48	7490	0.42	74118	0.90	74190	1.50
7407	0.30	7417	0.28	7480	0.50	7491	0.75	74119	1.85	74198	2.00
7408	0.15	7440	0.15	7481	0.95	7492	0.45	74121	0.30	74199	1.90

CMOS IC'S

Type	Price										
CD4000	0.14	CD4012	0.18	CD4022	0.95	CD4031	2.20	CD4046	1.30	CD4071	0.28
CD4001	0.18	CD4013	0.50	CD4023	0.18	CD4035	1.05	CD4047	1.10	CD4072	0.28
CD4002	0.18	CD4015	0.90	CD4024	0.72	CD4037	0.95				

The new Maplin Catalogue is no ordinary catalogue...

Hundreds of fascinating new lines

Several major new projects to build

MAPLIN ELECTRONIC SUPPLIES



SUPERSONIC SAME DAY SERVICE!
QUALITY COMPONENTS

Super Discount Voucher - saves you pounds!




We stock some super digital clocks. A mains driven clock with alarm, snooze and all the features you'd expect. A digital car clock with automatic display blanking when you switch the engine off. A very accurate timer that switches on at a preset time and off at a preset time - if you've got a tape-recorder there's no need to miss your favourite programmes ever again.



The book section contains over 150 titles of books about electronics, radio, TV, Hi-fi etc. Browse through the pages and choose from some of the best titles around including a superb set of books that will 'teach you electronics that will experiment!' (foot of catalogue page 142)

Hundreds of photos and illustrations

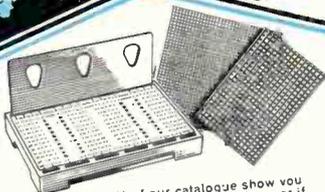

Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decks or if you prefer to make your own pcb's a range of etching systems including the novel Dalo etch-in-a-bag system, plus printed circuit transfers for that professional finish to your boards.

Catalogue includes a very wide range of components: hundreds of different capacitors; resistors; transistors; I.C.'s; diodes; wires and cables; discotheque equipment; organ components; musical effects units; microphones; turntables; cartridges; styli; test equipment; boxes and instrument cases; knobs, plugs and sockets; audio leads; switches; loudspeakers; books; tools - AND MANY MANY MORE.



* Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers (they save you pounds) - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

SEND THIS COUPON FOR **YOUR** COPY OF OUR CATALOGUE ON APPROVAL! Price 50p - SEND NO MONEY NOW. Please rush me a copy of your brand new 1977/78 catalogue by return of post. Only if I am completely satisfied that it is worth every penny, will I send 50p within 14 days of receipt. If I am not satisfied, I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____

ADDRESS _____

Maplin Electronic Supplies P.O. Box 3, Rayleigh, Essex, SS6 8LR

EE4

**DON'T DELAY
POST COUPON NOW
IT COULD BE THE BEST 50p YOU'VE EVER
SPENT**

MAPLIN

**ELECTRONIC SUPPLIES
P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR**

Telephone: Southend (0702) 715155. Call at our shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed all day Monday) Telephone: Southend (0702) 47379.

SPECIAL 8 PAGE SUPPLEMENT

GUIDE TO COMPONENT BUYING



A directory of firms advertising in EVERYDAY ELECTRONICS and the products they sell, including basic information for mail order customers.

THE information contained in this guide has been supplied by the various companies at our request. The initial list shows each company's name, address and—where submitted—telephone number and brief data about the firm and its trading policy.

The following five pages carry charts showing which of a selected list of components each firm can supply. These charts can be used in two ways, either to check on what a known firm can supply—do this by

looking up the firm's name in the left hand column and following the line across the pages, each marked square represents one type of component (listed at the top) that the firm normally holds in stock. Or to find a supplier of a particular type of component—do this by finding the component required, along the top (listed in alphabetical order) and looking down the row, each marked square represents a company (listed on the left) that can supply the required item.

Arrow Electronics Ltd., Mail Order Department, Leader House, Coptfold Road, Brentwood, Essex. Telephone: 0277 219435 (Retail) 0277 226470 (Trade), Telex: 995393.

Catalogue 40p including p & p. Prices inclusive of V.A.T. We have introduced an "availability reference" which should assist customers. Terms: Cash with order, Order under £5.00 in value 25p p & p. Orders over £5.00 postage free. The shop in Brentwood is open 9—5.30 p.m. 6 days per week (open during the lunch hour during winter months). The shop has many lines in addition to current catalogue and advertised items, and a popular feature is the wide range of semiconductor special offers.

B. Bamber Electronics, (Electronic Components and Equipment Suppliers), 5 Station Road, Littleport, Cambs, CB6 1QE. Telephone 0352 860185.

Terms of Business: Cash with order (except Government Departments). Minimum Order £2.00 post paid (U.K. only, except where stated). Goods in stock normally despatched same day, or within 36 hours. List published from time to time (s.a.e. required). Faulty goods replaced or money refunded without quibble.

B. H. Components Factors Ltd., 59 North Street, Leighton Buzzard, Beds, LU7 7EG. Telephone 05253 2316.

Bi-Pre-Pak Ltd., 222 West Road, Westcliffe-on-Sea, Essex

J. Bull (Electrical) Ltd., 102-3 Tamworth Road, Croydon, Surrey, CR9 1SG. Telephone 01 688 1833.

The company holds very large stocks and a new catalogue is in preparation, also monthly newsletters are issued which give details of new bargains as they arrive, these will be sent free upon receipt of a stamped addressed envelope and will be mailed automatically to all who subscribe £1.25p per annum, which just about covers the cost of stamps and envelopes.

Trading terms are cash with order except to schools and public institutions whose orders are accepted on a monthly credit basis. There are generous discounts for quantity orders.

Extra carriage on heavy items must be sent regardless of size of order. Letter weight items will be sent post free providing the order for these items exceeds £6.00—below this an amount of 40p should be added to cover cost of postage and the servicing of the order.

Chromasonic Electronics, 56 Fortis Green Road, London, N10 3HN.

The Components Centre, 7 Langley Road, Watford, Herts, WD1 3PS. Telephone 45335.

Créscent Radio Ltd., 164-166 High Road, London, N22 6EJ (also) 13 South Hall, Edmonton, N9. Mail order Department, 1 St. Michael's Terrace, Wood Green, London N22 4SJ. Telephone 01 888 4474.

Our minimum postage and packing charge for mail order customers is 50p per order unless otherwise stated. The postage and packing charge is subject to 8 per cent V.A.T.

Quantity trade prices will be quoted on application.

Denco (Clacton) Ltd., 355-7-9 Old Road, Clacton-on-Sea, Essex, CO15 3RH. Telephone Clacton 22807.

We offer a complete range of coils for valve and transistor useage plus a range of formers and cores, base cans etc.

Our products are available from most home constructor outlets or direct mail order. In order to cover high postal rates we require 15p postage and packing for goods up to the value of £2 and 5p per £1 thereafter, any overpayment will be refunded.

We manufacture a multitude of coils of customers own requirements and are always pleased to offer quotations to home constructors clubs, education authorities etc., for purpose wound coils, providing they can order minimum 100 quantities.

Doram Electronics Ltd., P.O. Box TR8, Wellington Road Industrial Estate, Leeds, LS12 2UF. Telephone 0532 34222 or 252548.

The Doram edition 3 catalogue carries full information on the 3,500 different items currently held in stock. The price of 60p includes free postage and update information for the duration of the catalogue.

The range of Doram construction kits is detailed in the full colour Kit Brochure, price 25p. If ordered together with the catalogue the price is 70p, which can be offset by using the two 25p vouchers on two separate orders of £5.00 or more.

Postage and packing is free for all goods with the exception of a minimum order charge of 40p for orders with a total value (excluding VAT) of less than £1.00. We offer a return of post service for all items in stock and guarantee components for one year.

Electrovalue Ltd., 28 St. Judes Road, Englefield Green, Egham, Surrey, TW20 0HB. Telephone 0748 3 3603. Telex 264475.

Catalogue 40p retail. Small order surcharge 15p if order under £2.00. Company accounts opened with suitable references. No minimum order value but minimum invoice value is £1.00.

Greenweld Electronics, 443 Millbrook Road, Southampton, SO1 0HX. Telephone 0703 772501.

Greenweld Electronics was founded in Feb. 1973 and started life as a mail-order only business in West Wickham, Kent. As trade increased, so did the need for larger premises and a shop in Deptford was purchased, which is still operating today.

As the South Coast seemed to be lacking in component shops, a move to Southampton was made where, after a year in a smaller shop, the business was transferred to its present address on the main Southampton-Bournemouth (A36) road.

From here, all mail-orders are despatched, mostly on the day of receipt. The policy of the company is to offer a broad range of components used in designs within this and other magazines at a very favourable price.

Apart from advertised goods, our catalogue (new issue out April, price 30p with discount vouchers) lists thousands of components for the home constructor.

Callers are welcome at the shop between 9 and 6 Mon.—Sat. where many odd lines at bargain prices may be found.

Home Radio (Components) Ltd., 240 London Road, Mitcham, Surrey, CR4 3HD. Telephone: 01 648 8422.

Home Radio started as a radio and television business in 1946. The company was incorporated in 1967. We branched into components in 1951.

First catalogue produced in 1959 and has been continued until present date. Present cost £1.00 plus 40p postage. Over 200 pages with separate twenty page supplement, listing about 5000 items with over 1500 illustrations. Fixed rate of postage and packing 75p, irrespective of size of parcel.

Although 90 per cent of our business is mail order we have a shop and enjoy meeting our customers personally. Shop hours are: 9a.m.—5p.m.; 9a.m.—1p.m. Wednesday; 9a.m.—5.30p.m. Saturday.

Josty Kit (UK) Ltd., 16 Borough Road, Middlesbrough, Cleveland, TS1 5DQ. Telephone 0642 44542.

Josty Kit, (U.K.) Ltd., Mail Order Division, are the Sole U.K. distributors of the range of Josty kits. Our kits use only the very best components available from the world market.

The range of kits offered are for the beginner right through to the professional, and many industrial and military establishments find them invaluable.

All kits are sold direct through mail order and are priced including VAT. Please add 25p, postage and packing with your order.

LRS Electronic Supplies, 3 Clivesway, Hinckley, Leicestershire.

We are now offering a 24 hour turn round quote service. The client sends us a list of components he requires along with a s.a.e. we will then price it or give availability and return it within 24 hours.

As regards our terms, no minimum order charge, all our prices include postage and all orders are cash only with order.

We intend to make LRS a manufacturer only and have set up a separate company to deal with mail order, this company is called **M.D. Marketing**, P.O. Box 4, Hinckley, Leicestershire

All our mail orders should now be addressed to this company.

Magenta Electronics Ltd., 61 Newton Leys, Burton-on-Trent, Staffordshire, England, DE15 0DW. Telephone: 0283 65435.

Magenta Electronics Ltd., was set up to provide a fast efficient no-nonsense source of components and hardware for constructors.

Our catalogue lists a wide range of carefully selected items all held in stock for same day despatch. It is available for 25p, and includes 25p in vouchers. To simplify ordering all our prices are fully inclusive. There is no minimum order value, but 20p must be added to orders under £2.00.

Our product range is constantly increasing to include components used in the latest projects, and those items frequently requested by our customers.

Items not listed in the catalogue can usually be obtained—a stamped addressed envelope with your requirements will bring a quote.

A range of kits is currently being introduced—including a transistor tester, an experimenters power supply, and a multimeter range extender. Send a large s.a.e. for details of kits.

Magenta's aim is to give a friendly personal service with full technical back up.

Maplin Electronic Supplies, P.O. Box 3, Rayleigh, Essex, SS6 8LR.

Maplin's 216 page catalogue is priced 50p. Over 4,000 items listed with over 1,000 photographs and drawings, and several complete projects to build: Professional 4 to 16 channel audio mixer; sine/square oscillator; organists/guitarists 13-note bass foot pedal unit; electronic Ignition system; light show with a.v.c.; stabilised power supply for cassette-players, radio etc., (mains or car battery operation). Also includes 30 pages on i.c.s with complete circuits to build.

Maplin's trading terms: Same-day-service (on in-stock items). Prices guaranteed for two monthly periods, Bi-monthly newsletter/price list details—customers can check the actual prices before buying. Anyone can join the newsletter mailing list for 30p and receive one year's issues of the newsletter. Subscribers can take advantage of special offers that can save pounds. Discount vouchers given with orders valued over £2. Reply-paid envelope returned with every order and catalogue. Handling charge 20p on orders valued under £2. Prices include VAT and postage and packing.

A. Marshall (London) Ltd., 42 Cricklewood Broadway, London, NW2 3ET. Telephone 01 452 0161/2/3. Telex 21492. Also at 85 West Regent St., Glasgow, Scotland. Telephone 041 332 4133; 1 Straits Parade, Fishponds, Bristol, Telephone 654201, and 27 Rue Danton, Issy Les Moulineaux, Paris, France. Telephone 644 2356.

No minimum charge where cash with order. Postal charges extra as per catalogue. Orders normally despatched same day as received. Orders in excess of £10.00 sent recorded delivery or registered post. Credit accounts available.

G. F. Milward, Electronics Components, 369 Alum Rock Road, Birmingham, B8 3DR. Telephone 021 327 2339.

Orchard Electronics, Flint House, High Street, Wallingford, Oxon, OX10 0DE. Telephone 0491 364588, 35529.

We re-print our stock list once a month and every item listed is in stock. All orders are dispatched 1st class post on day of receipt, we are very serious about this, we cannot afford to allow any orders to be carried over-night. Trade, authorities and account holders (amateurs) may phone by 4 p.m. goods will be dispatched by 5 p.m.

P.B. Electronics (Scotland) Ltd., 57 High Street, Saffron Walden, Essex. Telephone: 0799 228 76. Also at 62 Largo Road, St. Andrews, Fife, Scotland. Telephone St. Andrews 2641.

P.B. supply the professional and the home constructor with everything to produce printed circuit boards and also manufacture p.c.b.s

We manufacture S-DeC, T-DeC, U-DeC breadboards and accessories, Blob-Boards and Sketch-N Etch.

No minimum order charge, free information, callers welcome.

Radio Component Specialists, 337 Whitehouse Road, West Croydon, Surrey.

Radio Component Specialists was established in the early 1950's by John Ladd to provide a service in South London previously only to be found in Central London. Return of post despatch is their mail order slogan.

Counter service in the shop is given on all aspects of the products on sale. In addition to stocks there is a range of hi-fi and disco equipment, amplifiers, lights and loudspeakers.

Baker Loudspeakers Ltd., is an associated company and with their factory next door to the components showroom in Whitehouse Road, audio service and expertise is second to none!

Everything in our advertisements is in stock before advertising and we ensure that sufficient stocks are held for mail orders and callers alike.

Rownsongem Ltd., Rosebank Parade, Plough Road, Yateley, Camberley, Surrey. Telephone 0252 871388.

Radio Exchange (Bedford) Ltd., 61A High Street, Bedford, MK40 1SA. Telephone 52367.

We are manufacturers and suppliers of transistor kits. We do not supply components to clients other than those who have purchased kits and require spares.

Tandy Corporation (Branch U.K.), Bilston Road, Wednesbury, West Midlands, WS10 7JN.

We supply a large range of electronic components and equipment. The catalogue, which is free from the above address, lists over 2,000 items.

There are over 150 Tandy shops in the country, eliminating the need for mail order. There is no postal delay and most shops stock the complete range.

Trampus Electronics Ltd., 58/60 Grove Road, Windsor, Berkshire SL4 1NS. Telephone Windsor 53779.

The company was formed in 1972 to market new technology. Now specialising in fast service semiconductor sales, carrying over one million devices in stock and a wide range of passive components.



Supplement to
**EVERYDAY
 ELECTRONICS**
 April 1977

	Aerials		Amplifiers		Attenuators		Battery		Boards		Cabinets		Cable																
	Ferrite Rod	Telescopic	Complete	Modules	Aluminium Sheet	Audio	R.F.	Audible Warning Devices	Connectors	Holders	Copper Clad	Tag Panels	Insulating	Printed Wiring (Veroboard)	Plain Perforated	Plug-in Wiring	Bulb Holders	Bulbs	Steel	Plastic	Aluminium	Diecast	Co-axial	Mains	Multicore	Ribbon	Screened	Ceramic	Electrolytic
Arrow Electronics	✓	✓	✓		✓						✓	✓	✓	✓	✓	✓				✓	✓		✓	✓	✓	✓	✓	✓	✓
B. Bamber Electronics												✓								✓					✓		✓		✓
B. H. Components Factors	✓	✓		✓	✓				✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Bi-Pre-Pak			✓	✓				✓												✓	✓								✓
J. Bull (Electrical)	✓	✓	✓	✓				✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓			✓	✓	✓	✓	✓	✓	✓
Chromasonic Electronics	✓			✓					✓	✓	✓	✓		✓	✓		✓	✓			✓			✓				✓	✓
The Components Centre	✓	✓		✓	✓				✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Crescent Radio	✓	✓	✓	✓	✓				✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Denco (Clacton)	✓											✓	✓																
Doram Electronics	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Electrovalue									✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓
Greenweld Electronics	✓	✓		✓				✓	✓	✓	✓			✓	✓						✓	✓	✓	✓	✓	✓		✓	✓
Home Radio (Components)	✓	✓		✓				✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Josty Kit (UK)																					✓								
LRS Electronic Supplies	✓	✓	✓	✓	✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Magenta Electronics	✓				✓				✓		✓	✓	✓	✓	✓						✓	✓	✓	✓	✓	✓	✓	✓	✓
Maplin Electronic Supplies	✓	✓		✓				✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
A. Marshall (London)	✓			✓				✓			✓	✓		✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
G. F. Milward	✓	✓	✓	✓					✓	✓	✓	✓		✓	✓					✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Orchard Electronics	✓	✓	✓	✓					✓					✓			✓	✓			✓			✓	✓	✓	✓	✓	✓
P.B. Electronics (Scotland)											✓			✓	✓	✓					✓								
Radio Component Specials	✓	✓	✓	✓	✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Rowngem																													
Radio Exchange (Bedford)																													
Tandy Corporation		✓	✓	✓		✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Trampus Electronics	✓	✓						✓	✓	✓	✓			✓	✓		✓	✓			✓	✓						✓	✓



Supplement to
**EVERYDAY
 ELECTRONICS**
 April 1977

	L.E.D.	Neons	Interference Suppressors	Knobs	Light-Activated Switches	Light Dependent Resistor	Loudspeaker Cabinets	Miniature	Audio	High Power	Grille	Kits Construction	Meters	Microphones	Audio	R.F.	Carbon	Wirewound	Slide	Presets	Skeleton Presets	Printed Circuit Boards	Probes	Regulators	General	Heavy Duty	Miniature	Reed	Solid State
	Indicators		Loudspeakers										Modules		Potentiometers		Relays												
Arrow Electronics	✓	✓		✓	✓	✓	✓	✓	✓	✓			✓	✓			✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
B. Bamber Electronics				✓									✓				✓	✓						✓	✓	✓	✓	✓	
B. H. Components Factors	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Bi-Pre-Pak	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓				✓	✓	✓	✓	✓			✓	
J. Bull (Electrical)	✓	✓		✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Chromasonic Electronics	✓			✓		✓		✓				✓			✓		✓		✓	✓	✓	✓		✓			✓	✓	
The Components Centre	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Crescent Radio	✓	✓		✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓		✓	✓	✓				✓		
Denco (Clacton)				✓																									
Doram Electronics	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Electrovalue	✓	✓	✓	✓		✓	✓	✓			✓	✓					✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Greenweld Electronics	✓	✓		✓		✓		✓					✓	✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
Home Radio (Components)	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Josty Kit (UK)												✓																	
LRS Electronic Supplies	✓	✓	✓	✓	✓	✓		✓	✓		✓	✓	✓	✓			✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	
Magenta Electronics	✓	✓	✓	✓				✓			✓	✓					✓			✓	✓	✓							
Maplin Electronic Supplies	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
A. Marshall (London)	✓	✓		✓		✓						✓	✓		✓	✓	✓	✓	✓	✓	✓	✓		✓			✓		
G. F. Milward	✓	✓		✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓		✓					
Orchard Electronics	✓	✓		✓		✓	✓	✓	✓			✓					✓		✓		✓		✓	✓	✓		✓		
P.B. Electronics (Scotland)				✓								✓										✓							
Radio Component Specials	✓	✓		✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓					
Rowngem																													
Radio Exchange (Bedford)												✓																	
Tandy Corporation	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Trampus Electronics	✓	✓		✓	✓	✓		✓				✓	✓	✓			✓		✓		✓	✓	✓	✓	✓	✓	✓	✓	



Supplement to
**EVERYDAY
 ELECTRONICS**
 April 1977

	Sockets		Soldering		Switches														Transformers			Wire											
	Integrated Circuit	Relay	Transistor	Solder	Solder Tags	Irons	Solenoids	Spindle Couplings	Dual-In-Line	Foot	Illuminated	Lock	Micro	Push Button	Reed	Rocker	Rotary	Slide	Thumbwheel	Toggle	Terminal Blocks	Thermistors	Audio	Low Voltage	Transfers	Connecting	Extra Flexible	High Temperature	Tinned Copper				
Arrow Electronics	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
B. Bamber Electronics				✓	✓	✓							✓	✓				✓			✓												
B. H. Components Factors	✓		✓	✓	✓	✓		✓	✓	✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Bi-Pre-Pak	✓		✓	✓	✓								✓			✓	✓	✓		✓				✓									
J. Bull (Electrical)	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Chromasonic Electronics	✓			✓	✓	✓		✓						✓		✓	✓	✓		✓		✓		✓				✓					
The Components Centre	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Crescent Radio	✓			✓	✓	✓							✓	✓		✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Denco (Clacton)							✓										✓																
Doram Electronics	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Electrovalue	✓	✓	✓	✓	✓	✓	✓	✓		✓		✓	✓	✓	✓	✓	✓	✓		✓	✓	✓		✓			✓	✓	✓	✓	✓		
Greenweld Electronics	✓	✓	✓	✓	✓	✓	✓	✓				✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Home Radio (Components)	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Josty Kit (UK)																																	
LRS Electronic Supplies	✓	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓		
Magenta Electronics	✓			✓	✓	✓								✓				✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Maplin Electronic Supplies	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
A. Marshall (London)	✓		✓	✓	✓	✓			✓	✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
G. F. Milward	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Orchard Electronics	✓		✓	✓	✓	✓							✓	✓				✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
P.B. Electronics (Scotland)	✓																																
Radio Component Specials	✓		✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Rownsgem																																	
Radio Exchange (Bedford)																																	
Tandy Corporation	✓	✓	✓	✓	✓	✓			✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
Trampus Electronics	✓	✓	✓	✓	✓	✓	✓						✓	✓									✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	