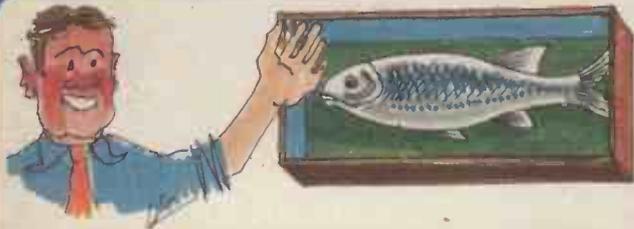


Construction and theory for everyone

# everyday electronics


JUNE 77  
35p



**... THE HOBBY  
FOR LEISURE  
AND PLEASURE**

**Low-cost easy to build useful aids**

**...for ANGLERS  
Sight & Sound**

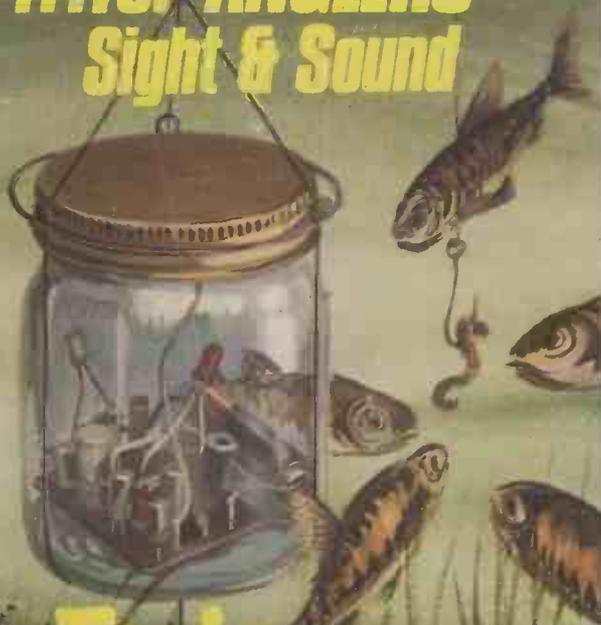

**Fish  
attractor**

**...for Plant  
Growers**



**SOIL  
MOISTURE  
MONITOR**



# This is Stirling Sound's price bombshell!

# NO MORE V.A.T. & POSTAGE PROBLEMS

**+ NEW DIRECT FROM FACTORY DELIVERY SPEED-UP**  
Another **FIRST** for Stirling Sound and B-P-P



### THE FACTORY

organised in the name of better service. Now our mail order dept. is right where the goods are made

### THE SHOP

really 3 shops—audio showroom, component bargains, modules, etc. etc. Well worth a visit



Why worry any more about working out V.A.T. (12½% on £4.87 plus 8% on £3.39\* plus 85p for p/p, or should it be 54p!) We do it for you. Just send your order with the advertised prices—we do the rest. The prices we give include V.A.T. at the appropriate rate and cost of postage and package. Buy at our shop in person and we deduct the postage charges automatically. *This is not all.* Now you send your orders direct to our factory (see below) where we make Stirling Sound products and send back your order from there even quicker—real time saving that! **AND STIRLING SOUND PRICES REMAIN KEENLY COMPETITIVE ALL THE TIME** maintaining the lead we took in 1959 by being first in the U.K. to sell bargain component packs. We've come a long way since then—with an exciting programme for the seventies we're going even further!

### YOU PAY THE PRICE YOU READ AND NOTHING MORE

subject only to (very rarely) there being a printing error or really vicious price rise in production costs. You're **SAFE** when you buy from Stirling Sound—the business that has grown on really understanding customers' needs and interests.

**SPECIAL QUOTATIONS TO QUANTITY BUYERS.**  
**U.K. & OVERSEAS TRADE ENQUIRIES INVITED**

## BEST SELLERS IN OUR 1977 RANGE OF Q.V. MODULES

### The Power Amps

- SS.103 3 watt r.m.s. mono. Uses one I.C. protected against short circuit £2.33
- SS.103-3 Stereo version of above using two I.C.s £4.33
- SS.105 5 watts r.m.s. into 3 ohms, using 12V supply £3.49
- SS.110 10 watts r.m.s. using 24V and 4 ohm load £4.05
- SS.120 20 watts r.m.s. into 4 ohms, using 34V £4.61

- SS.140 Delivers 40 watts R.M.S. into 4 ohms using 45 volts supply unit such as SS.345. Ideal for small disco, P.A., etc. £4.99
- SS.1100 100 watts R.M.S. with heatsink mounting flange and built-in protection against short-circuiting £10.43
- SS.1100/H As SS.1100 but with full size heatsink £11.82

(Heatsink alone £1.39)

### THE BARGAIN THEY ALL WANT!

IT'S THE SS.1100 100 WATT R.M.S. AMPLIFIER (£10.43) TOGETHER WITH SS.370 POWER UNIT (£14.63) plus full size heatsink for amp. (£1.39)

You pay **£24.25**

YOU SAVE **£2.20!** inc. VAT & p/p  
(Items bought separately come to £26.45—see above)

Your chance to lay the foundations of a really powerful disco or P.A. assembly at a marvellous price. This guaranteed Stirling Sound triumph is built for real hard work, so why pay more?

### Tone Control and Pre-amp Modules

- SS.100 Active stereo tone control, ±15dB on both bass and on treble £3.00
- SS.101 Stereo pre-amp for ceramic cartridges, etc. Passive tone control details supplied. £2.33
- SS.102 Stereo pre-amp for low output magnetic P.U.s. R.I.A.A. corrected. With circuit for adding passive tone control £4.04

**UNIT ONE**  
Combined pre-amp with active tone-control circuits. ±15dB at 10kHz treble and 30Hz bass. Stereo. Vol./balance/treble/bass. 200mV out for 50mV in. Operates from 10 to 16V supply. £9.00

**UNIT TWO**  
As Unit One, but for magnetic pick-ups. For inputs 1 to 5 mV per channel. R.I.A.A. corrected. Adaptable to ceramic. Designed to genuine hi-fi standards £12.43

### The F.M. Tuning Modules

- SS.201 Front end tuner, slow geared drive, two gang. A.F.C. facility. Tunes 88-108 MHz. £5.90
- SS.202 I.F. amplifier. Metering and A.F.C. facilities £3.46
- SS.203 Phase lock loop Stereo Decoder for use with the FM mono tuners. A LED may be fitted £4.19
- SS.203-1 Coil-type stereo decoder Neg. earth with I.C. £3.06. SS.203-3 Pos. earth transistor decoder £2.50

### 8 POWER UNITS

AT VERY COMPETITIVE PRICES

Firstly, the range covers well over 65% of all constructors' needs. Secondly, with 13-15 volt take off points on all models except SS.312, you get a valuable bonus; thirdly, the stabilised models with variable outputs complete a range to suit almost all requirements.

SS.312	12V/1A	£6.35
SS.318	18V/1A	£6.54
SS.324	24V/1A	£7.27
SS.334	34V/2A	£8.31
SS.345	45V/2A	£9.98
SS.350	50V/2A	£10.38
SS.370	70V/2A	£14.63

SS.310/50 Stabilised power supply with variable output from 10V to 50V/2A. Built-in protection against shorting £16.69

SS.300 Power stabilising unit 10-50V adjustable for adding to un stabilised supplies. Built-in protection against shorting £5.02

### GET MORE OUT OF YOUR CAR

with a STIRLING SOUND "SUPER SPARK" Mk5 electronic ignition unit. Adjustable for pos. or neg. earth. Simple rev. limiting control; on-off immobilising switch; switch for instant revert to normal ignition; neon indicator. In strong, totally enclosed metal box 16cm x 12cm x 10cm. 12 mths. guarantee.

Complete kit of parts **£10.28** Built & tested **£12.44**

Every effort is made to ensure correctness of information at time of going to press

## MAIL ORDERS

**STIRLING SOUND DEPT. PW6,**

37 VANGUARD WAY,  
SHOEBURYNNESS, ESSEX  
Telephone—Shoeburyness (0702-28) 5543

**SHOP AND SHOWROOM**

220-224 WEST ROAD, WESTCLIFF-ON-SEA,  
ESSEX SS0 9DF

Open all day Saturday



# EASY TO CONSTRUCT SIMPLY EXPLAINED

VOL. 6 NO. 6

JUNE 1977

## CONSTRUCTIONAL PROJECTS

<b>SIGHT AND SOUND FISH ATTRACTOR</b> Arouses the curiosity of nearby fish by A. J. Bassett	258
<b>DOOR CHIME INHIBITOR</b> Only permits a single "ding-dong" by T. I. R. de Vaux-Balbirnie	264
<b>TRANSISTOR LEAD OUT INDICATOR</b> Identifies the connections to a transistor by A. F. Olivera	276
<b>SOIL MOISTURE MONITOR</b> Moisture content controls pitch of tone produced by J. Jenkins	281
<b>MULTI-BAND TUNER Part 2</b> For receiving short, medium and longwave transmissions by F. G. Rayer	287

## GENERAL FEATURES

<b>EDITORIAL</b>	256
<b>SHOP TALK</b> Component buying problems and new products by Brian Terrell	263
<b>PLEASE TAKE NOTE</b> Doing It Digitally, Instant Info.	266
<b>PHYSICS IS FUN</b> Pitch and Volume by Derrick Daines	267
<b>JACK PLUG AND FAMILY</b> Cartoon	267
<b>DOING IT DIGITALLY</b> Part 9 Application of digital circuitry by O. N. Bishop	268
<b>FAULT FINDING</b> Part 2 Simple amplifiers by Douglas Vere	272
<b>FOR YOUR ENTERTAINMENT</b> Intercoms and the Post Office by Adrian Hope	280
<b>PROFESSOR ERNEST EVERSURE</b> The Extraordinary Experiments of. by Anthony J. Bassett	284
<b>BRIGHT IDEAS</b> Readers' hints and tips	285
<b>READERS' LETTERS</b> Your news and views	286
<b>DOWN TO EARTH</b> Using old meters by George Hylton	292

## BACK NUMBERS, LETTERS AND BINDERS

We are unable to supply back copies of *Everyday Electronics* or reprints of articles and cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, at the address shown opposite.

Binders for volumes 1 to 6 (state which) are available for £2.10, including postage, from Post Sales Department, Lavington House, 25 Lavington St., London SE1 0PF




# ...Sight & Sound



## FISH ATTRACTOR

By A. J. BASSETT

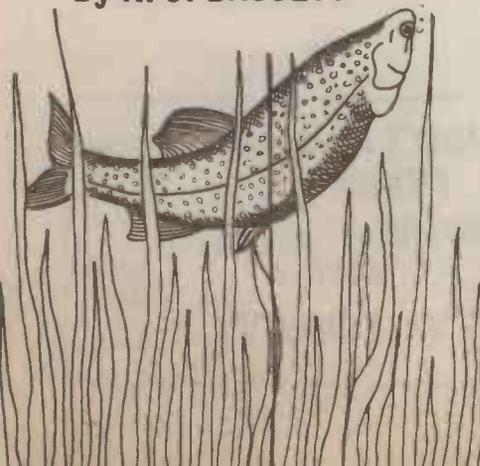

There are many ways in which fish may be attracted and caught. Some ways are legal and sportsmanlike. Other methods are illegal, unsporting and in some cases so efficient that, in the hands of irresponsible persons they could quickly clear our fishing places of stock and might, if uncontrolled, even lead to the extinction of whole species of fish.

One method which is illegal, but which might, paradoxically, be useful in helping to conserve the fish stocks if it were correctly used, involves passing electronic currents through the water in which the fish live. If a heavy current is used, the fish are stunned, paralysed or even killed by its effects.

If a weaker current is used it has an effect on the muscles and nerves of the fish, causing them to swim towards one of the electrodes in a zombie-like manner. Most fish are unable to escape this compulsion and are in effect, trapped the moment the current begins to flow in the water.

### PRINCIPLES OF OPERATION

The electronic fish attractor described here is legal and sportsmanlike; it does not cause electronic current to flow in the water or rely on anything illegal. The fish are attracted, by their own curiosity, to the vicinity of the device, and, having investigated the strange object, are free to swim away.

However, if a fisherman's hook is placed near the attractor with a suitable bait, the chances of a catch are definitely increased. The fish, having investigated the electronic attractor and found that they cannot eat it, will be quite likely to take the bait. It's this element of chance, combined with the fact that the fisherman must still exercise his skills in order to land a catch, that separates this electronic fish attractor from other less sporting methods.

Fish are naturally attracted by certain sounds and repelled by others. Low audio frequencies are for most fish a danger sign from which the fish will flee.

The clicking, buzzing and other high-pitched sounds made by insects and other potential prey are very attractive to fish, and a small flashing light is also attractive, especially at night or in a dark pool. Many highly-effective fish attractors have been made by

### THE VERY IDEA

The idea for a Sight & Sound Fish Attractor was proposed by a reader of E.E. who receives our special award.



mechanical or electrical means to produce similar sounds, or sounds in the same frequency range. The use of lights to attract fish, especially for night fishing, is also well known.

### CIRCUIT DESCRIPTION

The complete circuit diagram of the Sight And Sound Fish Attractor is shown in Fig. 1. Transistors TR1, TR2 and associated components form a circuit called an astable multivibrator (free-running square wave oscillator) which operates as follows.

When the circuit is switched on, both transistors attempt to turn on (become conducting) but due to component tolerances, one will draw current faster than the other. Say for argument's sake TR1 turns on faster than TR2, then the voltage on the collector of TR1 will become more positive, and this change will be fed back

FOR GUIDANCE ONLY

ESTIMATED COST OF COMPONENTS excluding V.A.T.

£3.00

excluding fishing line and weights

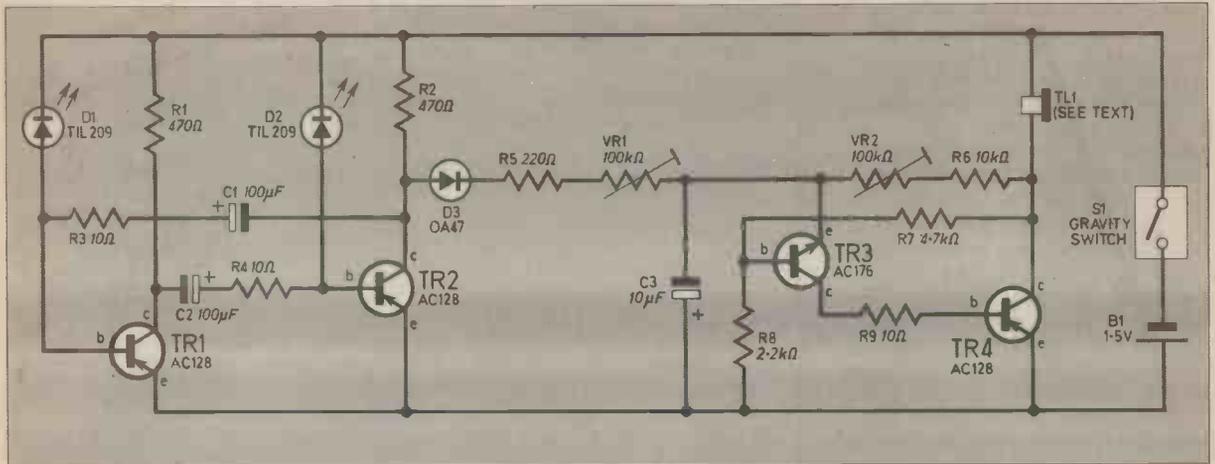


Fig. 1. Circuit diagram of the Sight and Sound Fish Attractor. Switch S1 is a home constructed gravity switch.

to the base of TR2 via C2 and R4. A positive voltage on the base of TR2 will cause TR2 collector current to fall thereby causing the collector potential to move towards the negative rail. This falling negative voltage is fed back to the base of TR1 via C1 and R3 causing TR1 to conduct more and in turn cause TR2 to move towards a non conducting state.

This regenerative action will continue until TR1 is completely on and TR2 is off. Only one transistor can be on at any one time.

Capacitor C2 now charges via D2 and R4 until the charge on the positive plate reaches a sufficiently negative potential such

that TR2 starts to conduct and switches hard on. We now have the situation where TR2 is on and TR1 is off.


Since the collector voltage of TR2 is at a low potential, capacitor C1 is free to charge via D1 and R3. The capacitor in charging reduces the collector current of TR1 and increases the voltage. This increase is fed back via C2 and R4 to the base of TR2, thus increasing the action still further. This continues until such time as when TR1 is on and TR2 is off. The entire process continues in this way illuminating the l.e.d.s, each time the transistors switch on and off, thus producing the "sight" part of the attractor.

Components TR3, TR4 and associated circuitry form a second oscillator, this one being known as a relaxation oscillator. The principle of operation of this type of oscillator is that capacitor C3 is charged up to a pre-determined value and then rapidly discharged through the transistors TR3 and TR4 and this process repeated.

At the instant of switching on, capacitor C3 is discharged, hence the emitter voltage of TR3 is more positive than its base. Therefore no current flows in TR3 and remains non-conducting. As a result no base current flows in TR4 and so this is also in a non-conducting state.

The capacitor begins to charge through TL1, VR2 and R6 and a point is reached where the emitter of R3 becomes less positive than the base and TR3 starts to switch on (conduct). This allows TR4 base current to flow i.e. TR4 begins to conduct. Because the collector/emitter resistance of TR4 has now reduced slightly due to its conduction, the potential on the base of TR3 is made to rise causing TR3 to conduct more heavily, which in turn causes TR4 to conduct more (reducing still further the collector/emitter resistance). The end result is that both transistors become saturated (turned on fully).

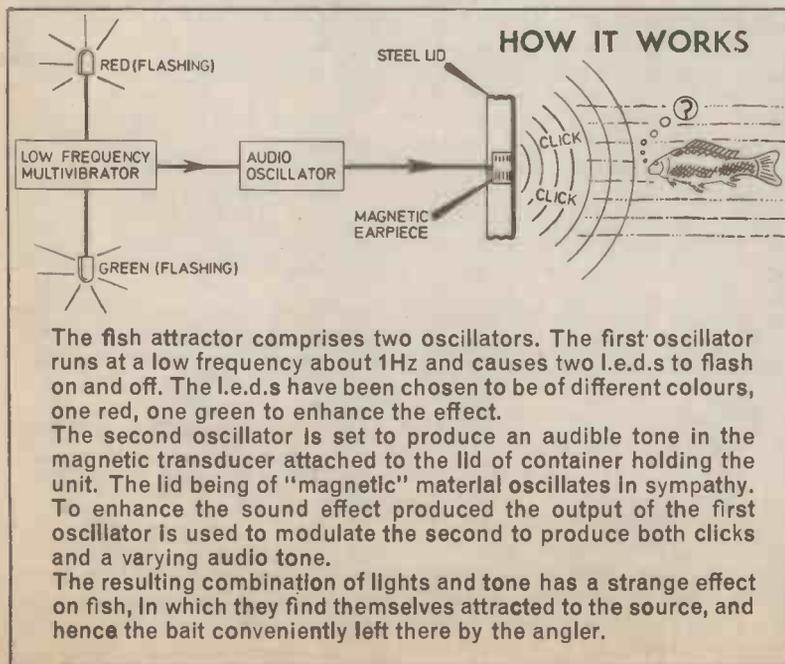The capacitor now starts to discharge through VR2, R6 and the collector/emitter resistance of TR4. As C3 discharges, TR3 emitter potential rises and so reduces TR3 collector current and hence TR4 base current. The resultant increase in the collector/emitter resistance of TR4 reduces the potential on TR3 base thereby reducing collector current. This



The fish attractor comprises two oscillators. The first oscillator runs at a low frequency about 1Hz and causes two l.e.d.s to flash on and off. The l.e.d.s have been chosen to be of different colours, one red, one green to enhance the effect.

The second oscillator is set to produce an audible tone in the magnetic transducer attached to the lid of container holding the unit. The lid being of "magnetic" material oscillates in sympathy. To enhance the sound effect produced the output of the first oscillator is used to modulate the second to produce both clicks and a varying audio tone.

The resulting combination of lights and tone has a strange effect on fish, in which they find themselves attracted to the source, and hence the bait conveniently left there by the angler.

clearly leads to both transistors being fully off with the capacitor discharged. This chain of events is repeated for as long as the supply is connected and produces an audible tone in TL1, the collector load of TR4, forming the "sound" section of the attractor.

A modulated tone is produced in TL1 by coupling the output of the first oscillator to a voltage sensitive point in the second oscillator, this point being the emitter of TR3.

The flash rate of the l.e.d.s may be altered by changing the values of R1 and R2 or C1 and C2, however the values of these capacitors determine the brightness of the l.e.d.s if they are decreased to a very low value, this will result in an apparent loss of brightness.

By varying the resistance of VR2, the basic frequency of the relaxation oscillator may be changed, and by altering the value of VR1, the modulating signal, which consists of a series of square waves may also be changed.

## TRANSDUCER

The circuit may be installed in a container such as a clear screw-top jar with a thin steel lid. A low-cost magnetic transducer causes the steel lid to vibrate at the frequency of the audio oscillator.

By this means the audio output of the oscillator is coupled to the water in the form of acoustic waves, Fig. 2a shows how the transducer operates.

A horseshoe magnet carries a coil of wire, and a pulsating current through this coil causes a soft iron diaphragm to vibrate at the frequency of the pulses.

A vast number of moving-diaphragm headphone-inserts were made for the Government and these are available at a number of Government Surplus and electronic stores. The correct type can be easily identified by unscrewing the cover, which reveals the loose iron diaphragm. When this is removed the poles of the magnet can be seen. The d.c. resistance of the coil is usually about 25 ohms.

Instead of using the iron diaphragm which comes with the headphones insert, place the magnet and coil assembly inside the lid of the jar, so that the rim of the inset automatically spaces the steel lid a little away from

the magnets, but the insert is magnetically stuck to the lid. Momentarily connect a 1.5 volt battery to the coil. A loud click should be heard from the lid. A small quantity of adhesive may then be used to attach the lid to the rim of the insert. Do not use a lot of adhesive as this may interfere with the efficiency.

Alternatively, remove the plastic ear insert and the soft iron diaphragm from a magnetic type radio or hearing-aid piece, and attach the magnet and coil assembly to the inside of the lid. In this case, there is usually a central pole-piece, around which the coil is wound, surrounded by an outer circular magnet as shown in Fig. 2b.

## GRAVITY SWITCH

The author considered a number of methods of switching the circuit on and off, without opening the jar, as it would disturb the waterproof seal each time. Magnetic switches operated by

means of the influence of a magnet through the glass, were considered, as was a mercury switch which proved successful but because the latter are not readily available, a home-made gravity switch was devised using a moving ball-bearing to make contact.

The construction of the gravity switch is shown in Fig. 3. A short piece of plastic tubing, and a ball-bearing are chosen so that the ball-bearing is a loose fit inside the tube and will easily roll about. Two small holes are drilled opposite one another about 3mm from one end of the tube, and into each hole is inserted a bent piece of solid copper wire, so that when the ball-bearing falls to this end of the tube, it bridges both pieces of wire and switches the circuit on.

A check is made to ensure that the ball-bearing makes and breaks contact freely when the tube is tilted. The opposite end of the tube is then sealed by cementing in place a plastic disc or a

## Components

### Resistors

R1	470 Ω
R2	470 Ω
R3	10 Ω
R4	10 Ω
R5	220Ω
R6	10kΩ
R7	4.7kΩ
R8	2.2kΩ
R9	10 Ω
All ½W ± 10% carbon	

### Potentiometers

VR1	100kΩ horizontal skeleton preset
VR2	100kΩ horizontal skeleton preset

### Capacitors

C1	100µF elect. 10V
C2	100µF elect. 10V
C3	10µF elect. 10V

### Semiconductors

TR1	AC128 germanium pnp
TR2	AC128 germanium pnp
TR3	AC176 germanium npn
TR4	AC128 germanium pnp
D1	TIL209 light emitting diode (green)
D2	TIL209 light emitting diode (red)
D3	OA47 or similar germanium diode.

### Miscellaneous

TL1	magnetic transducer insert (see text)
S1	gravity switch (see text)
B1	1.5V U7 battery

Stripboard 0.1 inch matrix 10 strips x 21 holes; small plastic tube; small ball-bearing; washer; wide necked screw top jar; Blu-tak or plasticine as required; 18 s.w.g. or 20 s.w.g. soft steel wire (see text); fishing line, weights as required; connecting wire; solder.

See  
**Shop  
Talk**

page 263

# ...Sight & Sound

# FISH ATTRACTOR

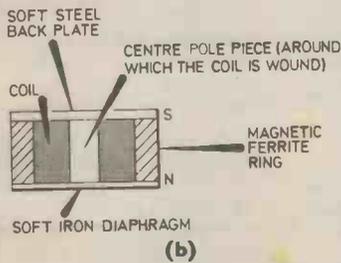
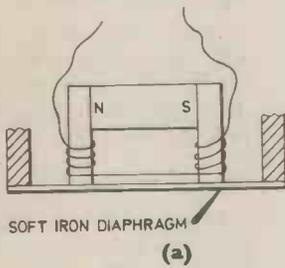


Fig. 2 (a) Illustrating the operation of a transducer. (b) A small earphone is usually constructed as in the diagram. For use in the Fish Attractor, the plastic insert and diaphragm are removed.

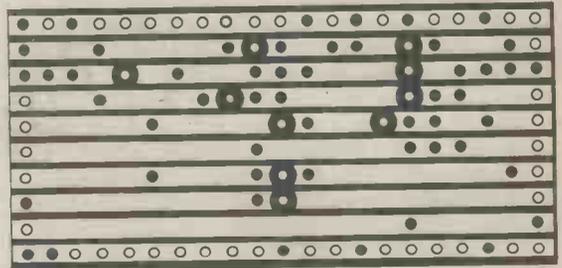
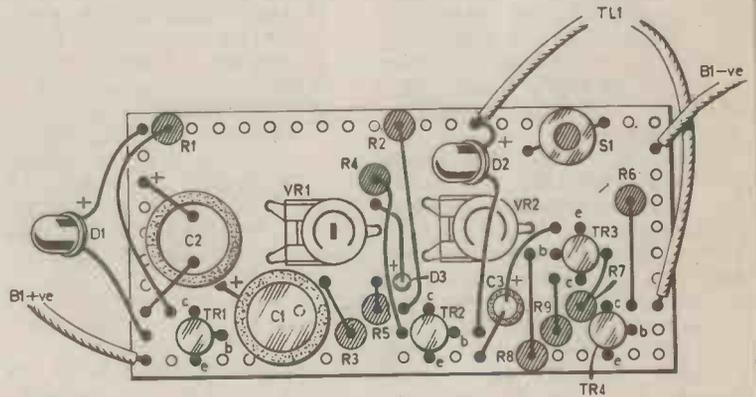


Fig. 4. Component layout on the stripboard, also showing the breaks required on the underside.

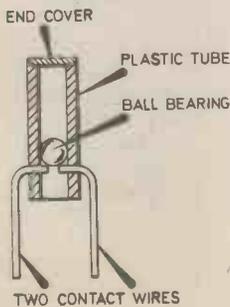


Fig. 3. Construction of the gravity switch. Ensure that the ball bearing makes and breaks contact freely.

Photograph showing the completed circuit as built on a piece of stripboard.

suitably sized washer. This traps the ball-bearing in the tube and completes the construction of the gravity switch.

## CONSTRUCTION AND TESTING

The circuit is built on a piece of 0.1 inch matrix stripboard size 10 strips by 21 holes. The layout of the components on the topside and the breaks to be made along the copper strips on the underside of the stripboard are shown in Fig. 4. The layout is not critical and may be changed to suit requirements.

Begin by making the breaks and then positioning and soldering the resistors, capacitors, potentiometers and gravity switch leaving the semiconductors until last. It is recommended that a heatshunt be used on the leads of the semiconductors when these are being soldered in position reducing the risk of thermal damage from the hot soldering iron.

The magnetic earpiece transducer is next connected to the board by means of about 15cm of thin flexible twin wire, and the battery connected by means of short lengths of wire soldered to its terminals. If the battery is not leakproof, it should be wrapped in several layers of blotting paper.

The circuit can now be tested. When the stripboard is held with the component side upwards, the gravity switch should make contact, the l.e.d.s should begin to flash alternatively, and if the transducer is placed in contact with the lid of the jar, it should produce a sound dependent upon the setting of VR1 and VR2.

The sound can be varied from a series of clicks through a low buzz to a high pitched note, which varies in sympathy with the flashing of the l.e.d.s all of these sounds appear to attract fish and the degree of attraction depends upon the type, age and size of the fish, among other factors which allow plenty of room for experiment.

To install the circuit, use a wide necked screw top jar. Press a layer of Bostik-Blu-Tak or plasticine over the bottom of the inside of the jar, which must be clean and dry in order that the material will stick. It also helps if both the jar and the material are slightly warm. Use a quantity

sufficient to ensure that the jar will float upright in water, but insufficient to cause it to sink when the circuit components and lid are added.

Press the circuit board and battery lightly into the material, as in the photograph and secure in place using several strips of plasticine.

When satisfied that it is in working order, and the gravity switch is functioning satisfactorily seal the lid in place with a thin layer of Blu-Tak or other non-setting water-resistant adhesive to act as a water resistant seal.

Although the lid should be easily removable for adjustment of VR1, VR2 and battery changing, it is best not to open the jar very frequently as this may require frequent attention to the water seal.

## WIRE CASE

Prepare a wire case for the jar as shown in Fig. 5 using soft steel wire about 18 s.w.g. or 20 s.w.g. Suitable wire is often used for binding parcels or packing cases, and this is best as it is treated with a rust-resistant coating. Alternatively thin birdcage wire can be used, and is obtainable from some pet stores. Three fixing-loops are made, equally around the neck of the jar and connected to a fourth loop underneath.

Now the jar may be used with

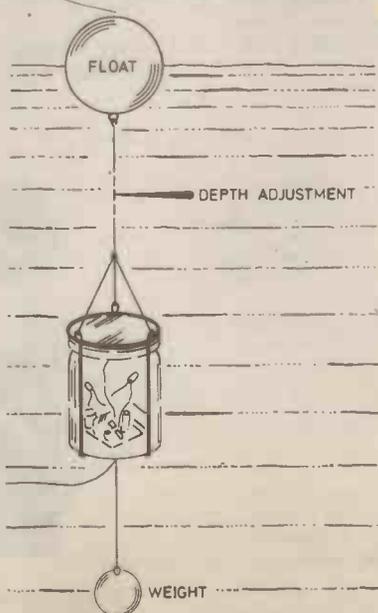


Fig. 6a. Using a float and weight to position the unit.

FIXING RINGS



Fig. 5. Details of the wire cage.

a float and weight as seen in Fig. 6a, or with a weight only as in Fig. 6b, as circumstances require, together with a recovery line for retrieval.

## USING THE ATTRACTOR

When using the attractor with a weight only, the length of line between the weight and the attractor will determine the distance between the attractor and the bottom.

The breaking-strain of this line should be less than that of the recovery line, so that if the weight is caught by some underwater obstacle, a heavy pull in the recovery line will snap the thinner line and allow the jar to float free.

A useful tip here, is that if a float is also being used, and the weight is lost in this way and, if by some misfortune the recovery line also comes off, the attractor can be recovered by casting in between the jar and the float.

Remembering too that for positive sinking in salt water a heavier weight is needed than for fresh water, and that by tying a cloth around the weight the jar is less liable to be broken.

Good Fishing!


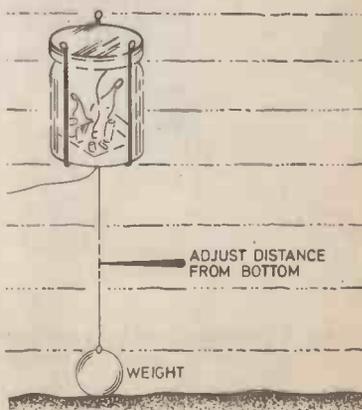


Fig. 6b. Positioning the unit using "bed" weight and own buoyancy.

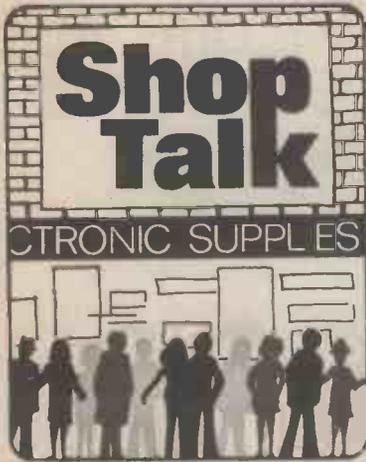

## By Brian Terrell

*New products and component buying for constructional projects.*

AS FROM this issue I shall be writing this column now that Mike Kenward has departed, and will endeavour to maintain the high standard of the services of this page that you have been accustomed to in the past years.

### Component Packs

Two packs of components arrived on my desk last month, for my inspection, from Home Radio Ltd. One contained 400 resistors with values in the E12 range from 4.7 ohms to 1 megohm, all gold band tolerance (5 per cent) with wattages in the range  $\frac{1}{4}$  to  $\frac{1}{2}$ W. This pack designated SP22 costs £6 excluding V.A.T., making the cost per resistor  $1\frac{1}{2}$ p.

The other pack, No. C121 contained many different types of capacitor and covered an extensive range. There



The contents of the SP22 resistor pack.

*Everyday Electronics, June 1977*

were 30 electrolytics, 22 silver mica, 20 paper/polyester and 32 ceramics, with values between 1.5pF and 5000 $\mu$ F. The cost of this is £7 excluding V.A.T. giving a mean unit price of 7p. These packs could make an economic start for those wishing to build up a stock of components for project building.

### Last Month

In the May '77 issue we published details for building a *Remote Reading Thermometer* which specified the use of a 10mA d.c. meter. Some readers have found difficulty in locating a meter of the type specified/used in the prototype. Only more expensive types could be found. We see from advertisements that 1mA types are more readily available at less cost. These can be used if fitted with a shunt resistor ( $R_s$ ) the value of this being determined from  $R_s = 0.11 \times$  meter resistance (ohms). The minimum wattage required is obtained from  $W = (0.009)^2 \times R_s$  watts.

### Electronic Component Kit

The Denshi electronic construction kits now available from Electroni-Kit Ltd., (advertising in this issue) are ideal for those people who want to learn about electronics but do not wish, or do not feel competent enough to handle a soldering iron, component board, wiring etc. The method employed in this system is that of plug-in components encapsulated in transparent plastic boxes which are marked with component symbol and value.

All kits are accompanied by manuals which explain technical details of projects with diagrams and explanations.

The three kits available SR-3A (100 projects), SR-3ADX (105 projects) and SR-4ADX (150 projects) also include basic electrical experiments and theory such as Ohm's law, resistors in parallel and series etc.

### Transistor Lead Out Indicator

There should be no buying problems encountered when buying components for the *Transistor Lead Out Indicator*. The 3-pole 6-way switch seen in the photograph is most difficult to locate, hence the Maka switch assembly specified—these are available from many component suppliers. Some constructors may be lucky enough to find a suitable type in a Government surplus store and save themselves some cash as the Maka switches are costly.

Almost any miniature push-pull output transformer will do for the inductor, if not you have details for a home-made version which will probably call for a larger case than that listed.

### Sight & Sound Fish Attractor

Only two components out of the ordinary are called for in the *Sight and Sound Attractor* these being the magnetic transducer insert and the gravity switch. The first component is dealt

with fully in the text and you have two alternatives. If you are going to cut open an earpiece, make sure that it's the magnetic type as this is the only one that will work.

Mechanical details are given in the text for constructing the gravity switch. Instead a mercury switch can be used, a suitable type is available from J. Bull (Electrical) Ltd., 7 Park Street, Croydon, Surrey for a cost of £1.95 including V.A.T. and post and packing.

### Remaining Constructional Projects

Very few components are used in the remaining two constructional projects this month and all should be easily obtainable. With regards the relay in the *Door Chime Inhibitor* any type that will operate from a 9 volt battery and has two sets of normally open contacts may be used. Bear in mind that if a type other than that specified is chosen, the wiring up on the component board will probably need adjustment.

### Bright Idea

An American invention, known as a Lightstick, is now available in the U.K. It provides up to 10 hours of light without using batteries, flame, sparks or heat. The light is the result of a chemical reaction contained in a 125mm long plastic tube, activated by bending the tube.

It provides sufficient light in an average sized room for reading, telephoning, repairs, etc, and can also be used with complete safety in potentially dangerous environments where petrol and gas are about.

The light produced can be seen a mile away; it is unaffected by adverse weather conditions and works underwater.

Generally available in the shops later this year priced at £1.95 per pack of three, but at present only available from Tye Security Ltd., Dolphin Road North, Sunbury-on-Thames, Middlesex.



A motorist putting a Lightstick to good use.

# DOOR CHIME Inhibitor

Only allows one "ding dong" from your chime however many times the bell-push is operated during a preset period

**T**HE simple unit to be described was designed to thwart the efforts of those bent on destroying the author's sanity. There are various ways of abusing door chimes—all of them annoying. Children sometimes give the button a very short press so that the "ding" part of the "ding-dong" hardly sounds, and they tend to do this over and over again. One tradesman, having rung our chimes and not receiving an immediate reply, rang it again and again. This sort of thing is guaranteed to disturb any sleeping baby.

Since our door chimes are loud enough to be heard with just one "ding-dong", the following circuit was devised to impose this limitation. It allows only one

"ding-dong" no matter how the button is pressed. Further pressing will give no results until about 20 seconds have elapsed and this time delay may be easily varied to suit individual requirements.

## THE CIRCUIT

The circuit is shown in Fig. 1 and is seen to be hardly "electronic" at all, in the sense that there are no active components. It consists of a general-purpose relay, which is an electro-mechanical component, a resistor of about 10 kilohms and an electrolytic capacitor of about 1,000 microfarads. Details of the relay are given later.

On pressing the bell-push, and thus closing the circuit, the relay


is energised and the capacitor begins to charge up from the 9 volt battery. This charging current falls off as the capacitor charges and, typically, takes about one second for the relay to drop out into its original state.

The relay switches the chimes via RLA2, one set of normally-open contacts, which remain closed just long enough to give the initial ding-dong. If this time is too short or too long, a different value of electrolytic capacitor can be tried, or a different relay used. A higher value of capacitor will give a long 'ding—dong', while a smaller value will have a shortening effect.

## CHARGE AND DISCHARGE TIME

Further operation of the bell-push will fail to work the chimes because the capacitor will be left in a charged state and cannot be charged further and so will not allow sufficient current to flow to energise the relay. Under such conditions the capacitor would take a long time to discharge sufficiently to render the circuit operational again and so a resistor of 10 kilohms is placed across it. This allows the

## HOW IT WORKS

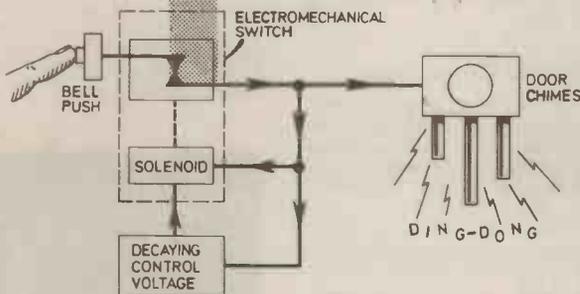

On depressing the bell-push the chimes start to sound but further chime action is prevented by the electromechanical switch becoming open circuit. It is kept in this state by the derived control voltage. Further action of the bell-push has no effect.

After a while (about 20 seconds in the prototype) the control voltage decays to a level such that the switch is once again closed (rest position). This process is repeated next time the bell-push is operated.

FOR  
GUIDANCE  
ONLY



ESTIMATED COST  
OF COMPONENTS \*  
excluding V.A.T.

£2.50  
excluding case

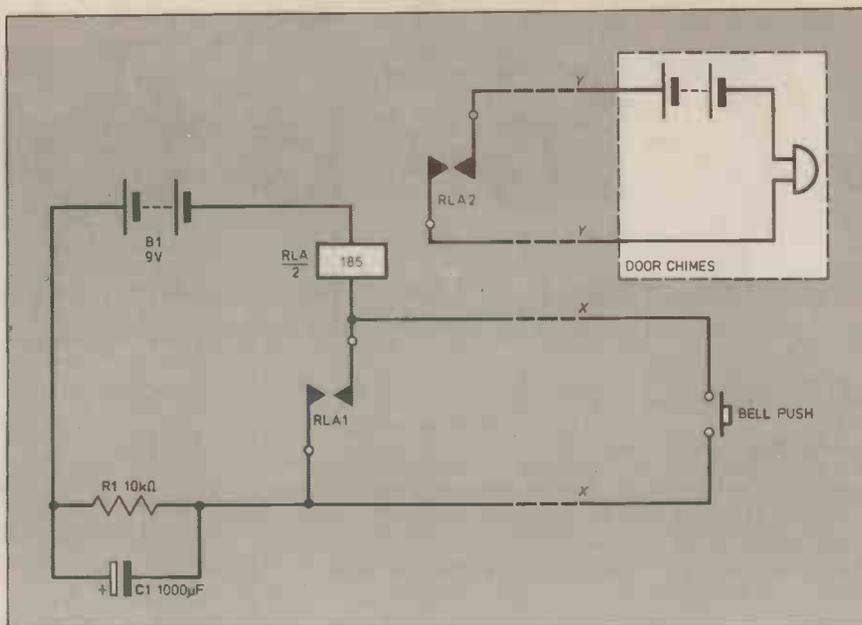


Fig. 1. The complete circuit diagram of the Door Chime Inhibitor.

capacitor to discharge through the resistor in about 20 seconds.

If it is required to shorten or lengthen this time, a lower or higher value resistor could be used, but a more flexible arrangement is to use a small preset variable resistor of about 100 kilohms which can be adjusted to give the desired time factor.

Another feature of the circuit is that even a very short press of the bell-push will give a full ding dong. This is because a second set of normally-open contacts (RLA1) on the relay short circuits the bell-push while the relay is energised.

#### OPERATION OF RELAY

Constructors who have not previously used relays may find a brief description of their action helpful. A small current flows through a coil consisting of many turns of fine copper wire. This coil is wound around a soft-iron core so that as the current flows it becomes energised and behaves as a magnet. Near the coil is an armature which is attracted to it by the magnetic field and in moving is caused to make or break various contacts which may be used to switch circuits on or off.

When the current is turned off, the magnetic field collapses and due to spring action the armature

moves away to its original position, thus rendering the relay static again.

The simplest relays have only one normally-open or one normally-closed set of contacts. Normally-open contacts will switch a circuit on when the relay coil carries current; normally-closed contacts will switch it off. Relays frequently have change-over contacts, which are a combination of normally-open and normally-closed contacts.

#### CHOICE OF RELAY

The relay to be used for this project should not have a coil which demands a high voltage for operation. Some 'surplus' or cheap relays have 24V coils and,

although they may very well work on less than this, they are unlikely to operate reliably from a 9V supply as specified here.

Some 12V relays may prove to be suitable, but reliable operation is essential and they must be checked by connecting their coils to batteries, taking care to avoid touching the bare connections with the hands. The rapid collapse of the magnetic field causes a high induced e.m.f. which can, on occasions, deliver an unpleasant shock!

The relay chosen for the prototype was a Doram type No 348-908, which has a coil resistance of 185 ohms; coils with resistances of much less than this are unsuitable. This relay operates reliably from about 6V upwards.

### Components


Resistor  
R1 10kΩ ¼W carbon ± 10%

Capacitor  
C1 1000μF 10V elect.

Miscellaneous  
RLA 9V 185 ohm relay with at least two sets of normally open contacts (Doram 348-908)  
B1 9V type PP3

Plain matrix board 0.1 inch pitch size 36 x 21 holes; p.c.b. type base to suit RLA1; Veropins; case to suit; battery clip to suit B1; connecting wire; solder.

See  
**Shop  
Talk**  
page 263

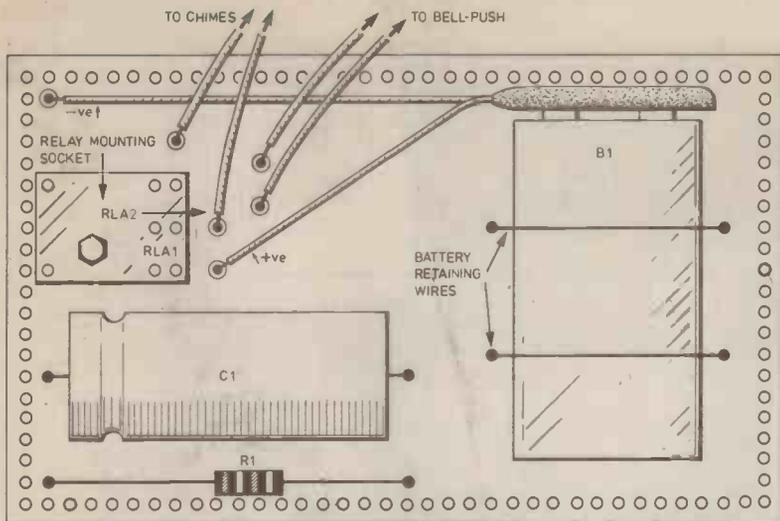

● VEROPINS

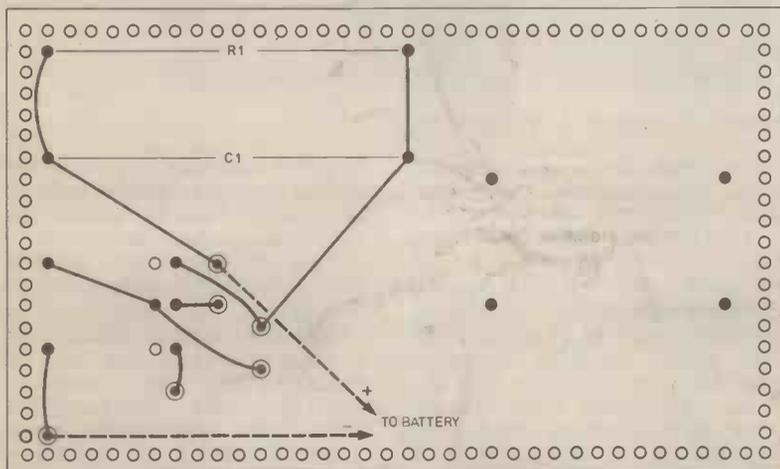


Fig. 2. The layout of the components on the topside of the plain matrix board and the interconnections on the underside.

The relay to be used must be fitted with two sets of normally-open contacts. The 348-908 has two pairs of changeover contacts which, of course, may be used as normally-open contacts. If a relay is fitted with too many unused contacts, the mechanical complexity may render it slow and perhaps unreliable. The resourceful constructor may take such a relay to pieces and remove any unwanted contacts.

It was decided to power the prototype from a small 9 volt battery mounted on the circuit panel itself. Although a battery clip is shown in the diagram, the connections could be soldered directly to the terminals since battery life will be quite long. It is possible to draw the power

from the batteries of the door chimes themselves, if they are battery operated, but if they are run from a transformer then the trouble of providing rectification

and smoothing would not be worthwhile.

## CONSTRUCTION

The layout of the project is non-critical, as the drawings of the prototype will reveal. Layout details and wiring will depend largely on the type of relay used.

When wiring up, however, be sure to observe the polarity of the electrolytic capacitor (the positive end is marked + or will be colour coded; the negative end is connected direct to the metal casing). The capacitor should have a working voltage in excess of 9V and, although small 15V types are available (and suitable), a 25V one was used in the prototype because it happened to be handy.

The battery itself was secured to the matrix board by the simple but effective method of using two loops of wire to secure it in place.

The unit should be housed in some kind of small box, preferably of wood. If a metal box is used, take care not to short circuit any of the wiring.

## CHECKING THE UNIT

Basic operation may be checked, without connecting the unit to the chimes, by listening to the clicking of the relay. Final checking, to ensure that it is working as desired, will be made by temporarily connecting it to the chimes. To do this, the two bell-push wires should be broken at some convenient point. The broken ends still leading to the bell-push are then connected to the points marked X-X in the circuit diagram (i.e. to RLA1 contacts) and the ends of the wires leading to the chimes are connected to the points Y-Y (i.e. to RLA2 contacts).

PLEASE  
**TAKE  
NOTE**

Concerning *Doing It Digitally Part 6*, there is an error in Fig. 6.5 which gives details of a tape reader. The "post" between the ones marked "recorded" and "B" should read 0V and not +6V as printed. The diagram in Fig. 7a is correct.

With reference to the *Info. Chart* presented free with the March '77 issue, there is a mistake in the capacitor colour code table. The "Tens/Units" column under "C280 Series and Ceramics" should read the same as the "Tens/Units" column under "Tantalum Capacitors".

# Physics is FUN!

By DERRICK DAINES

## Pitch and Volume

THE pitch of a note is entirely dependent upon the number of pressure waves reaching the ear in any small unit of time. This is termed its frequency, in the past expressed as c.p.s. (cycles per second) but nowadays in hertz (contracted to Hz.) The terms are synonymous. The humming top is a familiar example but observers sometimes think that the sound is getting louder when in fact it is getting higher. They are not to be scorned for this since the human ear is not too good at the differentiation at the extremes of the hearing range, generally given as about 50Hz to about 15,000Hz.

Readers with access to a variable tone generator can conduct a series of experiments on the acuity of their friends' hearing, but start with the generator giving a note outside the range of human hearing and ask them to raise a hand when they hear it and not vice-versa, as sometimes a zealous participant will insist that he can still hear the sound long after it has been switched off! It goes without saying that the speaker system used must be able to generate these very high frequencies.

A reasonable substitute to a tone generator is afforded by a paint-stirring paddle in an electric drill that is fitted with a variable-speed control see Fig. 1. The drill is mounted in a frame and a springy flap of metal is arranged so that the paddle blades strike it. If the drill is run at full speed

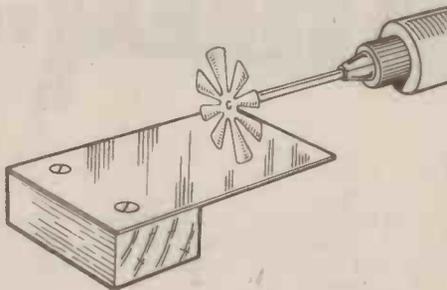


Fig. 1. A note is produced when a paint stirring paddle is struck against a springy flap of metal.

the metal flap acting like a sounding board will give off a note which is the product of the motor speed and the number of paddle blades. Slowing the drill will lower the tone, lower and lower, until the individual beats will be discernible.

## Cardboard Discs

A toy suitable for children to play with is made out of four discs of tough card, see Fig. 2. Cut them all the same size with a radius of about 10 to 12cm and pierce the centres with a knitting needle. Now round the circumference of the first disc mark out 12 teeth equidistant. The others have 24, 36 and 48 teeth respectively. Mount them on the knitting needle with a slice of cork between each, secured with a dab of glue. The whole

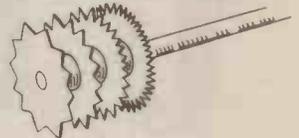


Fig. 2. If a card is held against all four discs, a chord is heard when the knitting needle is rotated.

arrangement may be spun by a small electric drill, driven by a clockwork motor, or by some domestic appliance such as a food mixer.

A strip of postcard applied to each disc in turn will produce four different notes, while if a wider strip of card is allowed to touch all four at once a pleasant chord is sounded. In fact, if we call the lowest notes the fundamental, the others are the 2nd, 3rd and 4th harmonics respectively. Incidentally, this tone-wheel system is the foundation of the Hammond organ sound.

In our cardboard toy all the discs sound at roughly the same volume or amplitude. Were we to make a sound generator with a fundamental note and (say) all of the next 16 harmonics at equal volume, the result might not be all that pleasant since some harmonics are not harmonious to the ear.

However, it is axiomatic that every musical instrument sounds some harmonics louder than others and that as a general rule the higher harmonics are softer than the lower. It is the blending of the various harmonics that gives each instrument much of its timbre or quality of sound.

## JACK PLUG & FAMILY...



# Doing it Digitally...

## Part 9

By O. N. Bishop

**T**HIS MONTH we continue with more projects illustrating the uses to which digital circuits can be put.

### DIGITAL DICE

A digital dice can be used instead of an ordinary cubical dice when playing many kinds of games—it is absolutely cheat-proof!

The dice uses a 7493 counter driven by a clock working at several hundred (or even thousand) hertz. The circuit is shown in Fig. 9.1.

The counter starts at zero (0000) but when it gets to six (0110) the two outputs B and C both go high. These outputs are fed to a NAND gate, the output of which immediately goes low. This signal is then inverted by another NAND gate giving a high which resets the counter to zero.

The reset acts immediately the counter gets to six so the actual sequence of counting is: 0-1-2-3-4-5-0-1-2-3-4-5-0... and so on.

Use a slow clock to check that this really happens, but in actual use a fast clock is necessary so that it is impossible for anyone watching to see what number the counter has reached.

To stop the clock the switch is closed, thus preventing pulses reaching the counter and freezing it at whatever state it was in. If all lamps are at zero this should be counted as six, the other numbers being indicated by their binary equivalents.

Of course this is a very simple form of dice yet it is cheat-proof because nobody can possibly know exactly when to press the switch to score any particular number. Also the counter is operating regularly so there is no bias towards any one number as there would be with a "loaded" dice.

It is also possible to design circuits which will count from one to six (instead of 0 to 5) and will also display the result on a set of seven lamps arranged like the face of an ordinary dice.

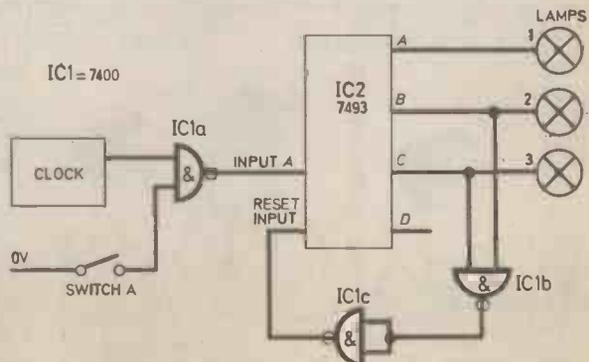


Fig. 9.1. Circuit diagram of a simple digital dice. The throw of the dice is indicated on the lamps when the switch is closed.

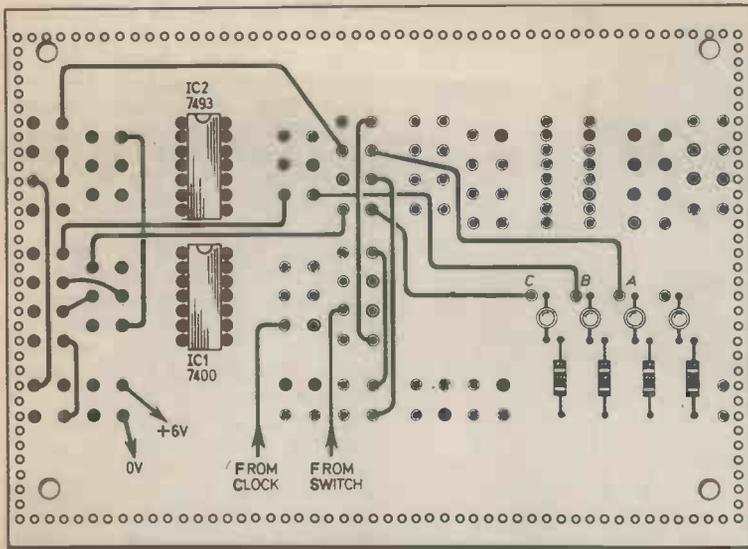


Fig. 9.2. Layout of the components for the digital dice on the experimental board.

Such circuits are more complex and the seven lamps add to the expense. Several circuits have been published in this magazine so you could try making up one of these for yourself or better still try designing one.

The layout for the Digital Dice excluding the clock is shown in Fig. 9.2. The clock can be constructed around the third i.c. socket if it has not been made permanent.

### WHO WAS FIRST?

The circuit shown in Fig. 9.3. indicates which of two events

happened first—even if one was only a millionth of a second before the other. Logic circuits act quickly!

The two "events" are the opening of switch A and switch B.

It can be seen that the two switches are connected to two bistables via NAND gates. Each bistable is connected to a lamp to show which switch was opened first.

The circuit is first reset by closing both switches and taking the reset line low. Since a low input on either of the inputs to a NAND gate causes the output to go high, this forces the outputs

of gates IC1a, IC1b and IC2d to go high. Both inputs to gates IC2a and IC2c will be high causing the outputs of these gates to go low and the lamps to be off. Providing the switches A and B are still closed, the circuit will stay in this state when the reset line is released.

Now supposing switch A is released. Both inputs to IC1a will be high so pin 6 will go low thus setting the bistable in its other state—pin 11 high (lamp on) and pin 8 low. Since pin 8 is low, gate IC1b is effectively closed—operating switch B can have no effect on the output of the gate. Thus A has blocked the action of B.

Exactly the reverse situation occurs if button B is released before A.

The circuit can be used when playing "snap" or some similar game to decide "who was first".

A pair of light-operated switches can be attached to the circuit to see which of two model racing cars wins a race. These go high in the dark so will give a brief high pulse as a car passes between the lamp and the photocell. A phototransistor circuit is required because of its fast response.

The layout on the experimental board is shown in Fig. 9.4. The switches used are those constructed on the "keyboard" in an earlier part of this series.

A set-up for a race track is shown in Fig. 9.5.

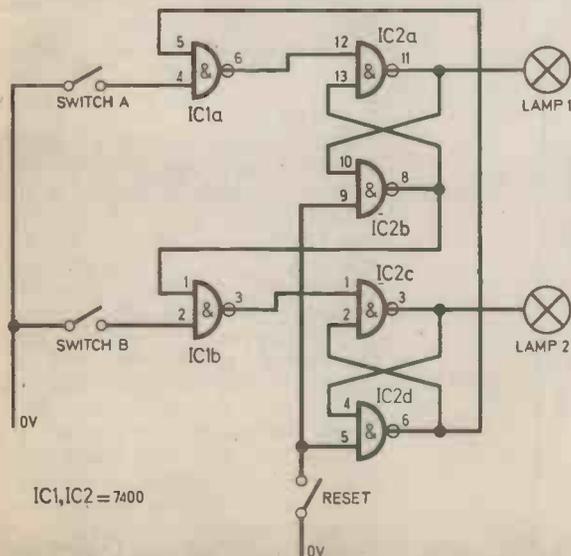


Fig. 9.3. Circuit diagram of the "Who Was First" unit. Switches A and B are normally closed. The lamp will indicate which switch was opened first.

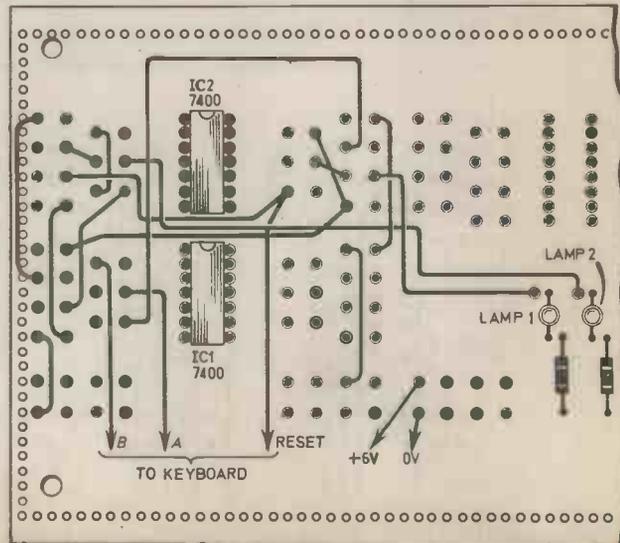


Fig. 9.4. Layout of the components on the experimental board for the "Who Was First" circuit. The switches used are those on the keyboard described earlier in the series.

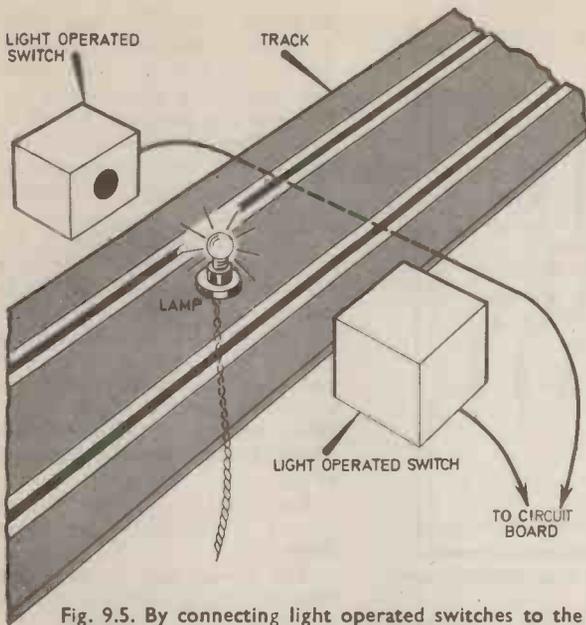


Fig. 9.5. By connecting light operated switches to the "Who Was First" circuit and placing them as shown, the first car past the lamp can be indicated.

## FLIP OR FLOP

The game "flip or flop" is just about as difficult to play as noughts and crosses and is like that game in that after playing it a few times one never loses—except by making a mistake!

The game is based on the 7472 flip flop. This i.c. has only one flip flop inside it as compared with two in the 7473 but it is cheaper. The flip flop has three each *J* and *K* inputs, also a clear which sets the *Q* output low and

a preset which sets it high. These act independently of the state of the clock pulse.

The i.c. is shown connected up in Fig. 9.6. To play the game start with all the *J* and *K* inputs low (to ground) and ground the clear input for a moment so that *Q* goes low and the lamp is out.

The two or more players play in turn. At each turn a player must change any two of the inputs. If, after he has done this, he thinks that the lamp will change state when the clock in-

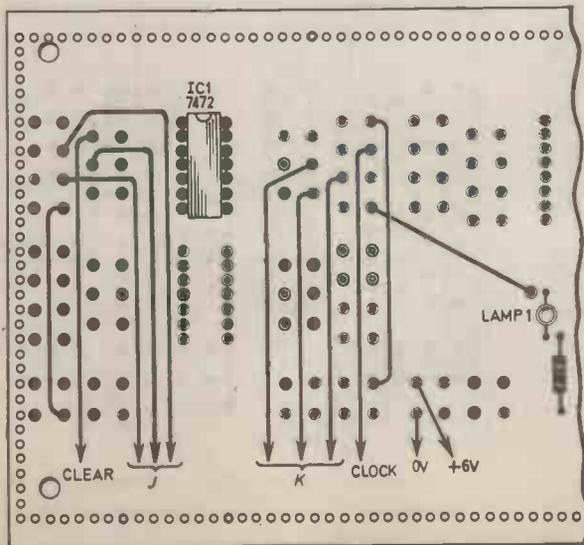


Fig. 9.6. Layout of the wiring on the experimental board for the "Flip Or Flop" game.

put is taken low he may ground the clock input. If the lamp changes he wins a point if it does not then his opponent has the point. If the player does not wish to ground the clock line the turn passes to the next player and no points are scored. The winner of the game is the first to score 20 points.

This is not a difficult circuit to build permanently. Some variations could also be incorporated. For instance, playing blind: Instead of using toggle switches where it is easy to tell the state of each input just by looking at the switch, use push-on, push-off switches. This makes the game almost one of chance.

One could also play against the clock. Instead of having a clock button to ground the clock input when a player thinks he can change the state of a lamp, this version has a slow clock with a period of about 0.2 seconds. The player who is in the middle of his turn or the player who has just completed his turn when the lamp changes scores a point.

In this version one has the additional feature of trying to get the inputs to the right state at the right time. One could wire an extra lamp to show the state of the lamp or one could just leave the players in the dark!

## EGG TIMER AND PHONE TIMER

The device to be described will time short periods and light a lamp or sound an alarm when the period is complete. There are lots of uses for this sort of device in the home.

The circuit uses a clock operating at about 0.2Hz, the output of which is connected to a 7493 counter. This will register one count every five seconds so will reach the full capacity of the counter in 75 (5 times 15) seconds. This may not be long enough for some applications but the period can be extended in several ways. The count can be passed first through a flip flop which will double the period, or through two flip flops which will extend the period to 300 seconds or five minutes (long enough for an egg timer).

The circuit with just the 7493 is shown in Fig. 9.7. and with the two extra flip flops in Fig. 9.8.

# Components

## Digital Dice

7400  
7493  
Clock circuit  
Push-to-make switch

## Who Was First?

7400 (2 off)  
Keyboard switches (2 off)

## Flip or Flop

7472  
Push-to-make, push-to-break (8 off)

## Timers

Clock: 7473 Alarm Unit: Rotary switch 1-pole 5-way  
7493  
7400  
7440

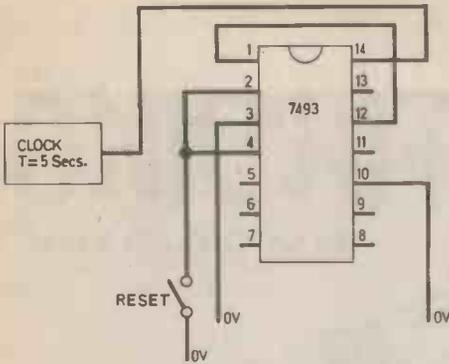


Fig. 9.7. A simple timer using a slow clock and a counter.

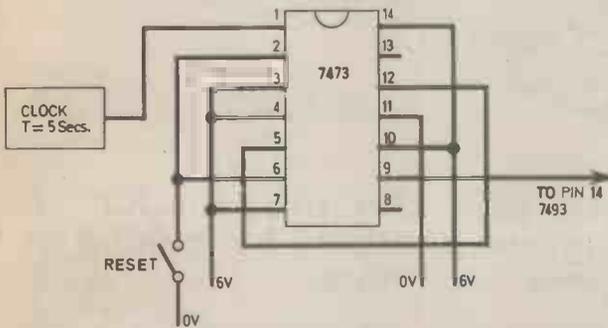


Fig. 9.8. The period of the counter may be extended placing two flip flops between the clock and the 7493.

The time is up when all the outputs of the 7493 go high. If all outputs are fed to a four-input NAND gate the output will stay high for five minutes then go low. This can be used to drive a lamp or alarm.

If the counter keeps going even after the alarm has gone off then the alarm will cease at the next count. To overcome this, the output of the NAND gate could

be fed to a bistable which feeds the alarm. This will then continue sounding even when the counter has gone back to zero.

The alarm can be made to sound after shorter periods than the full capacity of the counter.

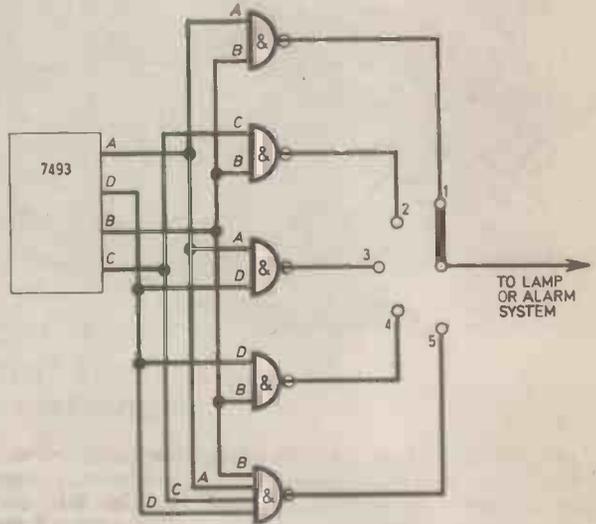


Fig. 9.10. Four two input and one four input NAND gates can be used to give timing periods of one to five minutes as selected by a rotary switch.

This can be achieved by using only some of the outputs of the 7493 fed into a NAND gate. For instance if the A and B outputs are fed into a two-input NAND gate then the alarm will sound after 60 seconds.

Thus the timer may be wired up in several ways and Fig. 9.9. shows the complete system. Parts of this may be left out depending on the application required.

Several NAND gates can be wired up if desired to give the option of different timing periods. The outputs of the gates can be taken to a rotary switch as shown in Fig. 9.10. so that the switch selects the period.

As can be seen this is the sort of circuit which can be tailor made to specific requirements. It is best to set it up on the circuit board, play around with it until the desired results are achieved (learning a lot about logic in the process) and then build up the circuit permanently.

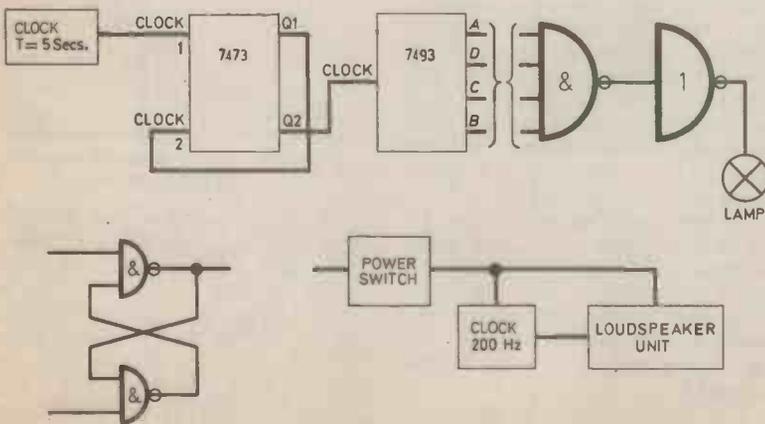



Fig. 9.9. The building blocks of a complete timer. The outputs of the 7493 can be connected to any type of NAND gate and the output of the NAND gate can be connected to the bistable, the lamp or the loudspeaker alarm.

To be continued

# FAULT

# FINDING

By DOUGLAS VERE

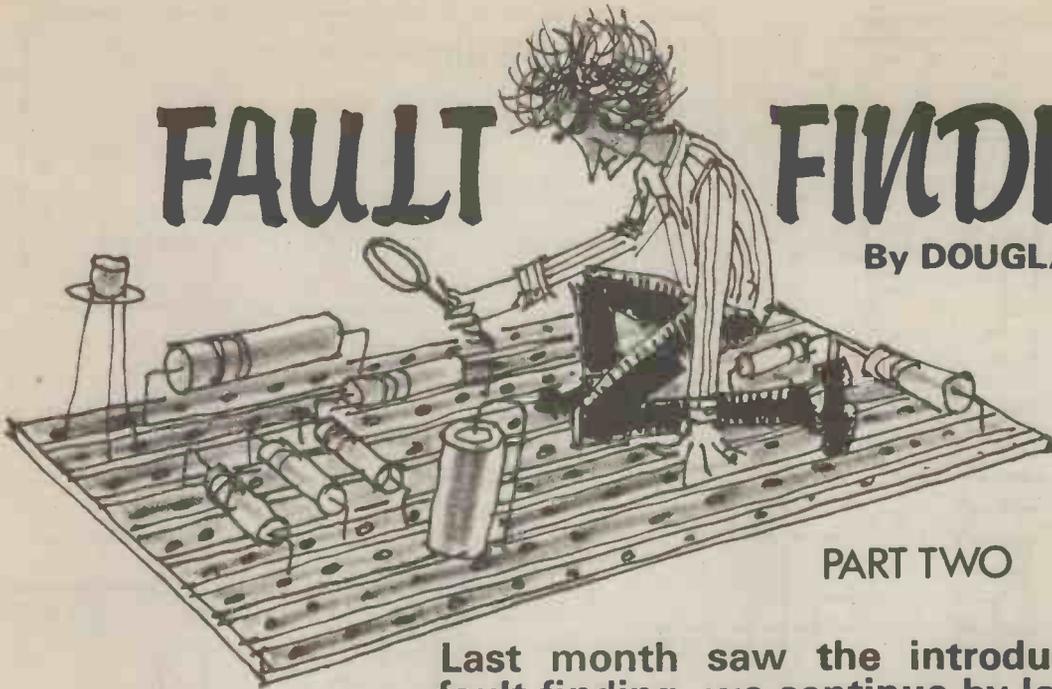

## PART TWO

Last month saw the introduction to fault finding, we continue by looking at one-transistor amplifiers.

IN ANCIENT China, it is said, patients paid their doctors only when they were healthy. It must have given the doctors a great incentive to cure diseases quickly! But it must also have raised a few problems. What is health? Until you know, it becomes hard to diagnose a disease.

It's the same with circuitry. Unless you know how a circuit should work, you are unlikely to be much good at diagnosing faults. It may seem a tall order to expect everybody to know how every circuit works, in detail, just so that he can do a bit of fault-finding.

Fortunately it isn't necessary to know anything like as much as the chap who designs circuits. If he is a competent designer, then he gets his component values right in the first place. The fault-finder only needs to know enough to see where things have gone wrong. Another fortunate circumstance is that the same types of circuit tend to repeat themselves over and over again, in slightly modified forms. Once you've got the hang of them fault-finding becomes easy.

### DEDUCTIONS

Knowledge of the d.c. voltages to be expected in a working circuit is invaluable. If a particular

voltage is wrong, some component or device associated with it is faulty. But how do you know what the circuit voltages should be? It's much easier to make intelligent deductions than you might think, because everybody, even the beginner with only a knowledge of Ohm's law and a general idea of how a transistor works has enough knowledge to do so.

We'll begin by looking at a simple single-stage transistor amplifier (Fig. 2.1a). This is an a.c. amplifier, as you can see by the input and output capacitors, put there to block d.c. Suppose you have traced a fault to this stage (by the signal-tracing methods mentioned in the last article), how can you identify the precise cause of trouble? D.c. voltage checks are normally used by repair men to do this. So what should the voltages be in a working amplifier of this type?

To work, the transistor must be turned on. This means that base current must flow in R1 and collector current in R2. In both cases the flow is down from the positive line (marked  $V_{CC}$  on many diagrams, or with the actual voltage).

The current flow in the two resistances produces voltage drops, and we can say, just by noting these, various useful things. First, the collector must

be more positive than the base, because there is a drop across R1 which goes from collector to base. Secondly, the collector must be less positive than the  $V_{CC}$  line, because of the drop in R2.

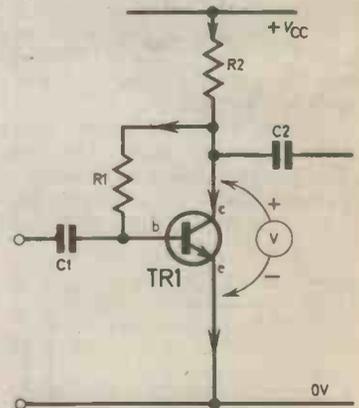


Fig. 2.1a. Single stage transistor a.c. amplifier.

A third, perhaps less obvious fact can also be deduced. Where does the base current go after entering the transistor? It can only flow to the negative terminal of the battery. In doing so it must set up a voltage drop across the base-emitter junction of the transistor, making the base more positive than the emitter.

Even without knowing anything about the actual sizes of these voltages, you can still begin to

fault-find with your voltmeter. If, on measurement, it turns out that the collector is less positive than the base, not more, as it should be, then there's obviously something amiss. (We'll discuss what it might be later.)

## EARTH

However, it is much better to get some idea of what the voltage should be. Before looking into that, let's just get one or two general points straight. First, in transistor circuits it is usual to quote voltages with respect to the common side of the power supply. In npn circuits like this, the common side is normally the negative battery line, and is normally drawn at the bottom of the diagram. (In pnp circuits all the voltages and current flows are reversed, but the principles are the same.)

To measure a voltage in this npn circuit you connect the negative terminal of the voltmeter to the negative battery connection and the positive voltmeter terminal to whatever point in the circuit you are interested in. By the way, the "common" side of the circuit is often referred to as the "earthy" or "grounded" side. British technicians just call it "earth" (whether it is really connected to the earth or not.) This is a convenient short way of talking about it which I'll use from now on.

## TRANSISTOR VOLTAGES

Where were we? Oh, yes, the voltages. The base-emitter voltage of a working silicon transistor is usually in the range 0.5 to 0.9V (at room temperature). The lower voltages are found when the transistor is passing only a small current. To a rough approximation, it's reasonable to say that the base-emitter voltage is 0.7V, and I'll do so from now on. (For germanium transistors a typical voltage is 0.25V, but the variation is much greater than for silicon, and it could be as low as 0.1V for a small audio transistor.)

The only other voltage of interest is the collector voltage. There is no way of estimating it unless you know the d.c. current amplification factor ( $h_{FE}$ ) of the transistor.

In general, the circuit designer chooses resistances which set the

collector voltage to about half the supply voltage, but variations may be quite large. The collector voltage is about half the supply voltage when R1 is  $h_{FE}$  times R2. Thus if  $V_{CC} = 6V$ ,  $R2 = 1k\Omega$  and  $h_{FE} = 100$ , the collector voltage will be about 3V if  $R1 = 100k\Omega$ .

Usually, in practice,  $h_{FE}$  is not known precisely. Transistor makers give it only between certain limits (e.g. 100 to 300) and designers use average values. Since an individual transistor may have an  $h_{FE}$  which differs quite significantly from the average, the collector voltage may deviate significantly from what is expected. Fortunately there is a certain degree of d.c. negative feedback in the circuit which helps to reduce the effects of  $h_{FE}$  variations, but it can't eliminate them. (The same applies to Fig. 2.1b, where the emitter voltage is about half  $V_{CC}$  when  $R1 = h_{FE} \times R2$ .)

A short way of referring to the d.c. voltages between the various electrodes of a transistor is to write  $V_{BE}$  for base-emitter voltage,  $V_{CB}$  for collector-base voltage,  $V_{CE}$  for collector-emitter voltage. If in Fig. 2.1a,  $V_{BE} = 0.2V$  instead of the expected 0.7V you know either that you are hot on the trail of the fault or that something has gone wrong with the measurement! I'll deal with measurement errors (caused by using an unsuitable voltmeter) later.

## SHORT

A common fault in transistors is an internal "short" between base and emitter. Often this not a complete short but has enough resistance to drop a small voltage. This could explain the 0.2V. Before unsoldering the transistor, however, ask yourself what the left-hand terminal of C1 is joined to. It's just dangling in the air in Fig. 2.1a, of course, but in a real circuit it must be connected to something.

If C1 has an internal short (or "leak" this could affect  $V_{BE}$ . For example, if C1 (left hand) were connected to earth via a low value resistance such as a 5 kilohm volume control, then an internal short could allow d.c. to flow in the 5k volume control, robbing a transistor of base current and pulling down the base voltage. A quick test checks this. Measure the voltage at C1 (left hand). If

it's not zero, C1 is leaky.

In other circuits C1 (l.h.) is connected, not to an earthed resistance but to the collector of a previous stage. In this case the l.h. side of C1 should be at a voltage above earth. A leaky C1 then allows current to flow from the previous stage collector TR1 base. This augments the a.c. base current and turns on TR1 harder, pulling down  $V_{CB}$ , and perhaps to such a low value that TR1 can no longer work properly. (With this fault,  $V_{BE}$  is raised slightly, but not necessarily enough to detect with a meter, unless you have already measured it before the fault developed and noted exactly what it should be.)

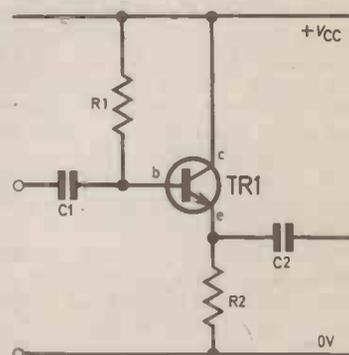


Fig. 2.1b. Emitter follower stage, Note that the transistor "load" is R2.

In the circuit shown in Fig. 2.1b the transistor "load" R2 is in the emitter connection. This "emitter follower" stage has an a.c. output voltage slightly less than the a.c. input voltage. Since the collector and base currents flow in R2, the emitter voltage is raised above earth voltage. If R1 is  $h_{FE}$  times R2, the emitter voltage is about half  $V_{CC}$ . The base must be the usual 0.7V more positive than the emitter, making the base-earth voltage that much more positive than the emitter-earth voltage.

## POTENTIAL DIVIDE BIAS

The simple circuit of Fig. 2.1c uses what is often called "potential divider bias". Here R1 and R2, which are connected across the battery, pass a current much greater than the base current of TR1. As a result, the flow of base current in R1, being so much smaller, makes little difference to the voltage drop in R1. Thus the drop in R1, and therefore the base voltage, is nearly independent of base current.

If  $R1 = R2$ , the base voltage (base to earth, that is), is half  $V_{CC}$ . If  $R1$  is three times  $R2$ , then three-quarters of  $V_{CC}$  is dropped in  $R1$  leaving one quarter across  $R2$  and so the base voltage is  $V_{CC}/4$ . In a word,  $R1$  and  $R2$  form a potential divider which applies a certain fraction of  $V_{CC}$  to the base.

Suppose  $V_{CC}$  is 12V and  $R1 = 3 \times R2$  then the base-earth voltage is  $12/4 = 3V$ . The emitter voltage is about 0.7V less, i.e. 2.3V. This 2.3V is across  $R4$  and the emitter current  $I_E$  must therefore be  $2.3V/R4$ . If  $R4 = 1k\Omega$ ,  $I_E = 2.3mA$ . The collector current is virtually the same, so if  $R3$  is 2 kilohms it drops 4.6V and the collector voltage must be about 7.4V. So if you know the resistances, the supply voltage ( $V_{CC}$ ) and  $V_{BE}$  you can make a fair estimate of all the circuit voltages. Not a 100 per cent accurate estimate, of course, but quite good enough to be of use in fault finding.

If the collector voltage is measured as 4V, for example, this should strike you as much too low. Is a leaky  $C1$  feeding current to the base from the collector of the previous stage? Is  $C2$  leaky and by-passing  $R4$  to d.c.? Has a resistor changed value, or the transistor developed a fault? Checking all the expected voltages in the circuit should help to limit the possibilities.

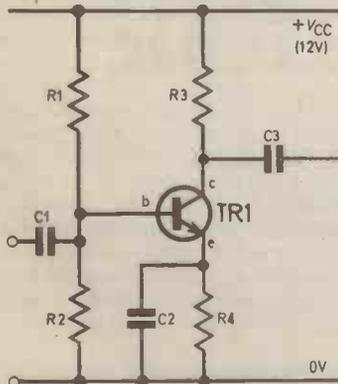


Fig. 2.1c. In this circuit "potential divider bias" is used, as explained in the text.

## OVERLOADING PROBLEMS

Incidentally, there is one quite common fault which can throw out all the circuit voltages even though every component in the circuit is perfect. This fault is "overloading" of the transistor by very strong signals. Quite often, the signals get there by accident.

For example, an audio amplifier may, because of accidental coupling between output and input, burst into radio frequency oscillation. You hear nothing (except perhaps a loud hiss) in the speaker, but the strong oscillations upset the voltages (and may easily wreck the transistors).

## SHUNTS

A small piece of auxiliary equipment takes care of the problem, temporarily. It is a genuine bit of test gear in its own right, though not often referred to in the textbooks. It's just a capacitor, of 100nF (0.1 $\mu$ F) or more, fitted with flexible leads which terminate in crocodile clips. One lead is clipped to earth. The other is attached to points in the circuit where the unwanted oscillations may be present—say the collectors or bases of transistors.

The impedance of 100nF to radio frequencies is low, usually low enough to short the r.f. to earth and so stop the oscillation. The transistor voltages should then return to normal, if the transistors have not been damaged.

In some circuits, especially radio receivers, the mere act of connecting a voltmeter to a point in the signal path may cause oscillation, and in such circuits it is a wise precaution to connect the "shunt capacitor" (I'll call it that in future) before starting to test.

In audio circuits, connecting a meter to a sensitive amplifier may accidentally introduce strong "hum" which upsets the d.c. conditions. To bypass the hum (which is at the mains frequency, a low frequency) a large shunt capacitance is required. Whereas the 100nF can with advantage be a metallised foil type, its larger hum-shorting brother will probably have to be an electrolytic, because in large capacitances these are so much cheaper.

In this case, remember to get the polarity right. And, in both cases, make sure that the working voltage is at least as high as  $V_{CC}$ . A reasonable "hum shunt" would be 10 $\mu$ F, 64V working. This will suit most circuits.

In theory, 10 $\mu$ F should perform equally efficiently both as a hum shunt and an oscillation stopper. However, theory is misleading. The impedance of electrolytic capacitors does not go on falling as the frequency is increased, as it should, but starts to rise again somewhere above the audio range. So at, say, 10MHz, your 10 $\mu$ F electrolytic may have a much higher impedance than your 100nF metallised foil, and be less effective as a shunt to h.f. signals.


If you have an assortment of capacitors, and two double ended croc-clip leads, you can, of course, lash up shunt capacitors as the occasion arises, and try out different ones on the spot.

## CIRCUITRY

To return to our circuitry. We've now looked at some common types of single-stage amplifier, and indicated the circuit voltages, or at least how to estimate them. Practical transistor circuits seldom fall neatly into one of these categories. Designers modify them or use combinations of them to suit their purposes.

For example, a designer may put a resistance in the emitter lead of Fig. 2.1a. This has the effect of increasing the input impedance and reducing distortion at the expense of gain. The circuit is then a sort of hybrid between Figs. 2.1a and 2.1b. Then again, two or more transistors may be direct-coupled, with the collector of one stage connected directly to the base of the next. This is a common arrangement in audio power amplifiers. We'll look at one of these multi-transistor combinations later.

To be continued

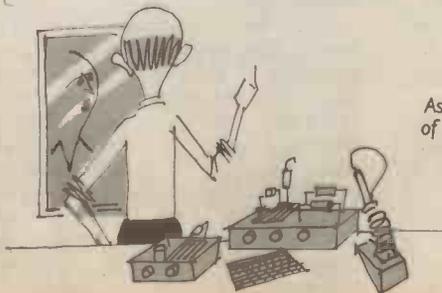


Ask yourself what the left-hand terminal of  $C1$  is joined to.

# A Selection from Next Month's issue...
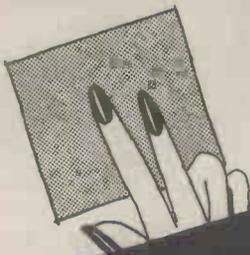
## POWER at your FINGERTIPS

This touch operated mains switch can be used to replace domestic mechanical switches. Operates rated up to 750 watts. Operates with the light touch of a finger.




## Also... Phone/Door BELL REPEATER

An electronic bell-extension system.

... NOT just for fun  
this  
indicates  
the  
**STEADY  
HAND!**

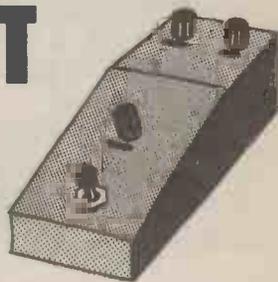
## ...FUZZTONE UNIT

More than just a fuzz box!! This unit, built in a robust case, allows complete control of tone to be obtained. Has both cut and boost of treble and bass frequencies.



# everyday electronics

JULY ISSUE  
ON SALE  
FRIDAY  
JUNE 17

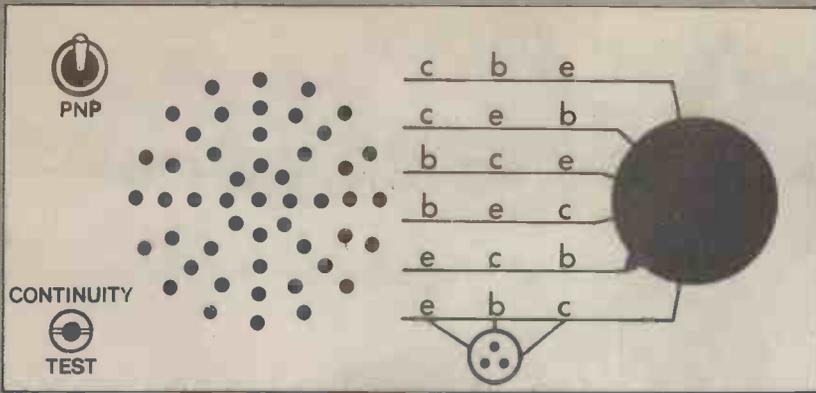

FOR  
GUIDANCE  
ONLY

ESTIMATED COST  
OF COMPONENTS  
excluding V.A.T.

£5.00

excluding case

# TRANSISTOR LEAD OUT INDICATOR

ALL electronics constructors, from the professional to the occasional dabbler, find that over a period of time a homogenous collection of electronic bits and pieces is amassed, which invariably includes a large number of transistors. Many of these will have had their markings rubbed off, while others may bear an unidentifiable code number.

It is possible with the aid of a multimeter to identify the lead-outs of unknown transistors, but the process is very tedious and one is never very sure of the results.

With the unit described in this article, however, the lead-outs of bipolar transistors can be identified in a couple of seconds, which is just what is required by those who invest in semiconductor packs containing unmarked and untested transistors.

The indicator will also identify the transistor as *npn* or *pnp*, confirm that the transistor is serviceable, and as a fringe benefit serves as a very useful audible continuity tester.

It will not, however, work with field effect or unijunction transistors.

## THE CIRCUIT


The complete circuit diagram of the indicator is shown in Fig. 1. The heart of the indicator is a Hartley oscillator. If the col-

lector, base and emitter of a transistor are connected to *c*, *b* and *e* respectively the circuit will oscillate and a tone will be produced by the loudspeaker.

If therefore an unknown transistor is connected to the oscillator via a switch capable of selecting all possible combinations of the transistor's three leads, a tone from the loudspeaker will indicate that the correct combination has been

made; the switch position can then identify the three leads.

While this switching is being carried out the full supply voltage is applied across the transistor's terminals in all possible combinations, and to avoid breakdown of the semiconductor junctions this voltage has to be kept to the minimum. In the event, tests revealed that a supply voltage of 1.5 volts was sufficient for a very adequate signal to be

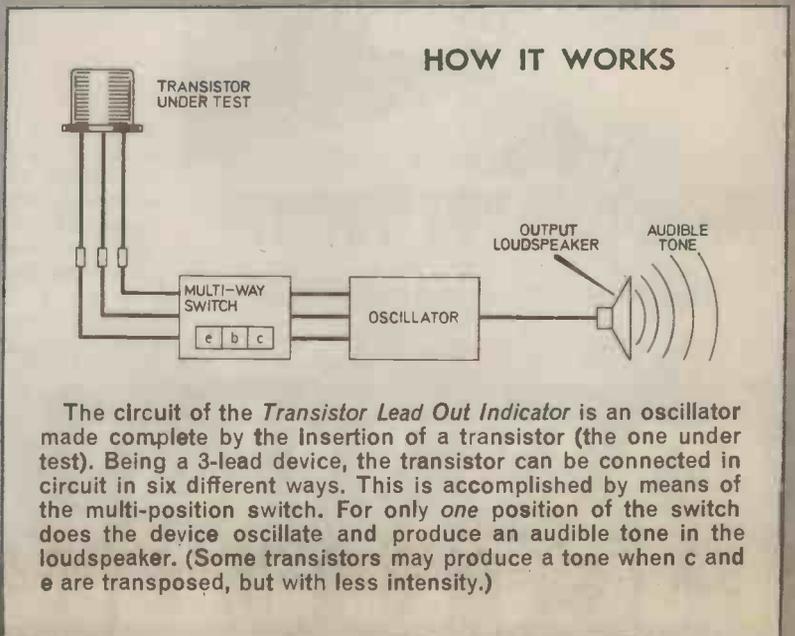

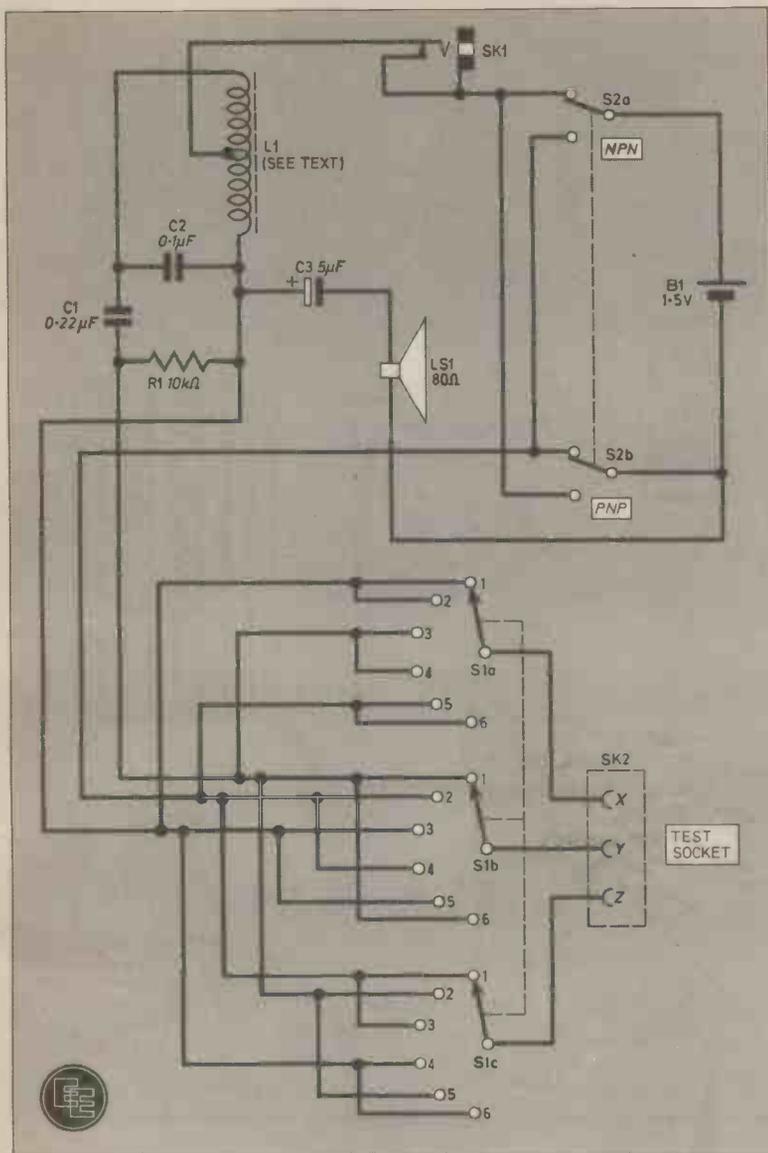


Fig. 1. Circuit diagram of the Transistor Lead Out Indicator.

produced. Some transistors gave a stronger output than others, but in all cases the tone was clearly audible.

Resistor R1 provides base bias for the transistor under test, while the positive feedback path is through C1; C3 couples the output to the loudspeaker. It is important that the ground connection of the loudspeaker be brought to the supply side of S2: this ensures that the negative terminal of electrolytic capacitor C3 is correctly connected whatever the position of S2. When S2 is in the *pnp* position the loudspeaker ground connection is made through the dry cell.

The frequency at which the unit oscillates is governed by C2 and the inductance of L1, but it is also affected by C1. It was found that the frequency varied with different transistors—some transistors in fact oscillated at near supersonic frequencies. The unit had therefore to be designed to oscillate at as low a frequency as feasible, and the values quoted for C1 and C2 were found to be the most suitable for the coil used in the prototype.

#### INDUCTOR

This coil in the prototype was a miniature push-pull output

transformer filched from an un-serviceable transistor radio. Various types from the spares box were tried and all worked with varying degrees of efficiency. Only the primary (i.e. the winding with three connections) is used. The two leads from the other winding may be used to anchor the transformer in place, but must be electrically isolated from the rest of the circuit.

A home-constructed coil was also tried, with excellent results. For those who may be interested a suitable coil can be made by pile-winding 600 turns of 30 to 40 s.w.g. enamelled copper wire on to a piece of 9mm ( $\frac{3}{8}$ in.) ferrite rod about 70mm long. A centre-tap must be drawn out at 300 turns, see Fig. 2.

Switch S1 used on the prototype was a rotary 3-pole 6-way type. It may be difficult to obtain a ready-made switch of this specification but one can very easily be assembled from "Maka-Switch" parts by using two 2-pole 6-way wafers, one of the poles being surplus.

The switching circuit is shown in Fig. 3 and is drawn using two 2-pole 6-way wafers as mentioned above. This looks rather complicated mainly because of the cross-connections involved; constructors may find it easier to make up the connections by following the switch position table.

Socket SK1 is a miniature 2.5 or 3.5mm jack socket with built-in switch, and provides the continuity testing function of the unit. A pair of prods are connected to a suitable jack plug, see Fig. 3: when this is inserted into the socket the built-in switch interrupts the supply, which is only restored when a short-circuit is presented to the prod ends.

Readers will notice that no on/off switch has been incorporated in the design. There is no need for one because the supply is always interrupted when there is no transistor in the test terminals and when the jack plug is inserted in its socket (provided, of course, the prods are not shorted!).

#### CONSTRUCTION

The prototype was built into a wooden case measuring 180 x 83 x 48mm. The sides were covered with laminate simulating wood veneer, and the lid with

# TRANSISTOR LEAD OUT INDICATOR

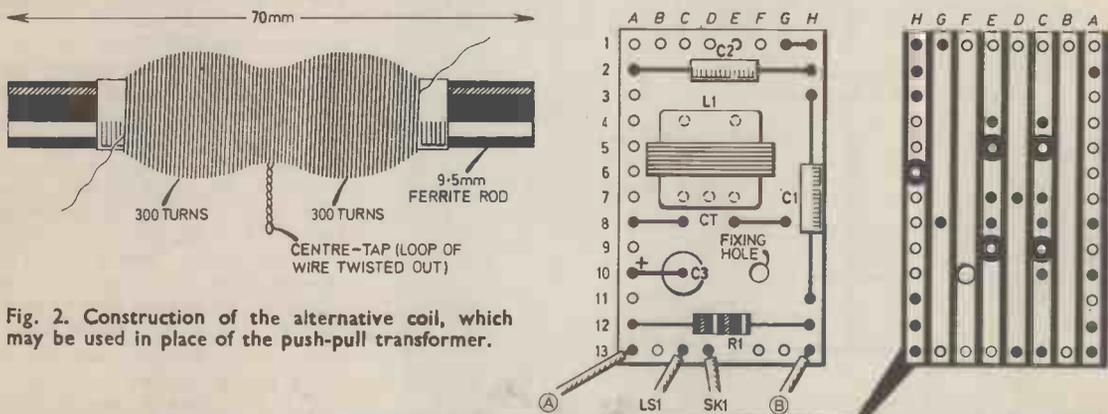


Fig. 2. Construction of the alternative coil, which may be used in place of the push-pull transformer.


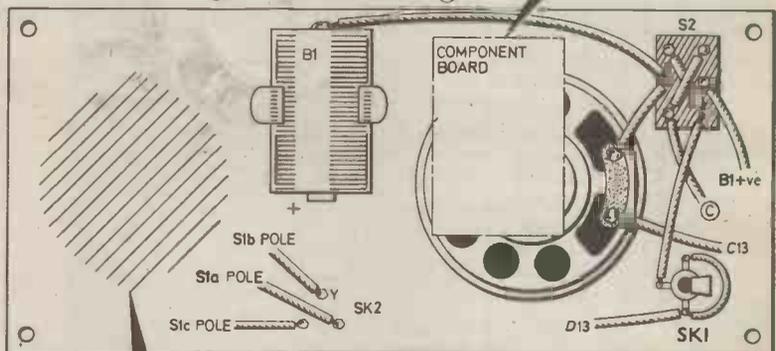


Fig. 3. Diagram showing the stripboard layout, with the breaks shown on the underside. Also shown is the wiring details for the 2 pole 6 way switches, and the connectors required on the front panel.

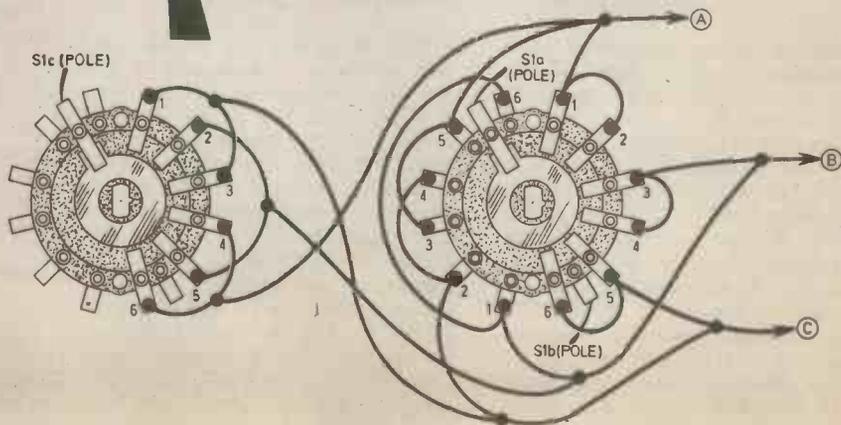

# Components



See  
**Shop  
Talk**

page 263

## Resistor

R1 10k  $\Omega$   $\frac{1}{4}$ W carbon  $\pm$  10%

## Capacitors

C1 0.22 $\mu$ F plastic or ceramic  
C2 0.1 $\mu$ F plastic or ceramic  
C3 5 $\mu$ F 3V elect.

## Miscellaneous

S1 3-pole 6-way rotary switch (see text)  
S2 2-pole 2-way toggle switch  
SK1 2.5 or 3.5mm switched jack socket  
SK2 three-pin transistor socket  
L1 miniature push-pull output transformer or home made inductor—see text  
LS1 80 ohm miniature loudspeaker approx. 60mm diameter  
B1 1.5V type U7 or similar  
Stripboard 0.15inch matrix 8 strips x 13 holes; Terry clip for B1; knob with pointer; jack plug to suit SK1; crocodile clips (2 off); case—prototype size 180 x 83 x 48mm; connecting wire.

white laminate. All the components were mounted on the lid, as can be seen in Fig. 3 and photograph. The layout and wiring of the various components is not critical and constructors may if they so wish adopt a different layout.

The dry cell, B1, is held in place by a Terry clip, the supply connections being soldered to the cell's terminals. Current consumption when the unit is in use is in the region of 2 milliamps, and since use is not continuous it should be a very long time before the cell has to be replaced.

The layout of the components on the stripboard and the breaks to be made on the underside are shown in Fig. 3. Begin by mounting the components on the prepared board as shown and then prepare the lid of the case to accept S1, S2, SK1 and SK2. The front panel (lid) can be drilled with a series of holes immediately above the location of the loudspeaker cone, or a suitably sized hole backed with speaker fret will do.


With all the components in position wiring up should be carried out according to Fig. 3. The component board was mounted on an aluminium bracket and positioned over the loudspeaker which was held in place with a few dabs of Evostik.

The panel lettering was made with Letraset transfers, which give a very professional effect. After lettering the face of the panel should be coated with a clear varnish (preferably matt) to protect it.

tone is heard, S2 (pnp/npn selector) is changed over and S1 again rotated until a signal is heard. The pointer on the knob of S1 will then indicate the identity of each of the transistor's terminals, and S2 the polarity of the device.

With some transistors the unit will oscillate in two positions of S1 i.e. with the emitter and collector transposed. In these cases there is usually a stronger output at the position corresponding to the correct terminals. In any case the base terminal will always be correctly indicated.

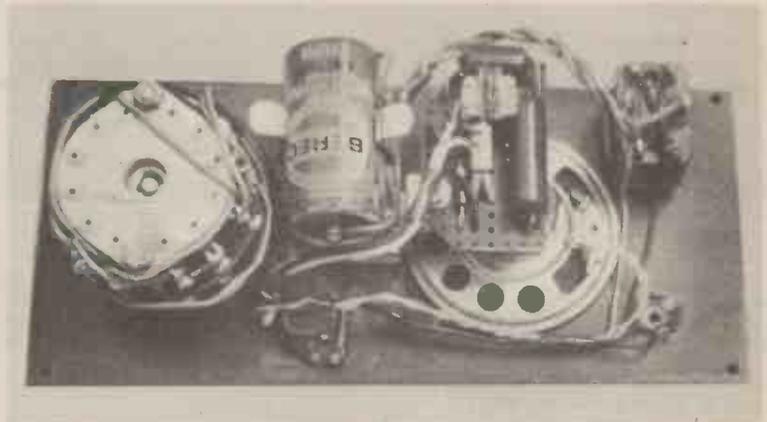To use the unit as an audible continuity tester a transistor has to be inserted and the unit adjusted until a tone is produced. The jack plug is then put in place and the tone will then sound only when the prods are




Photograph showing how the components are mounted on the lid.
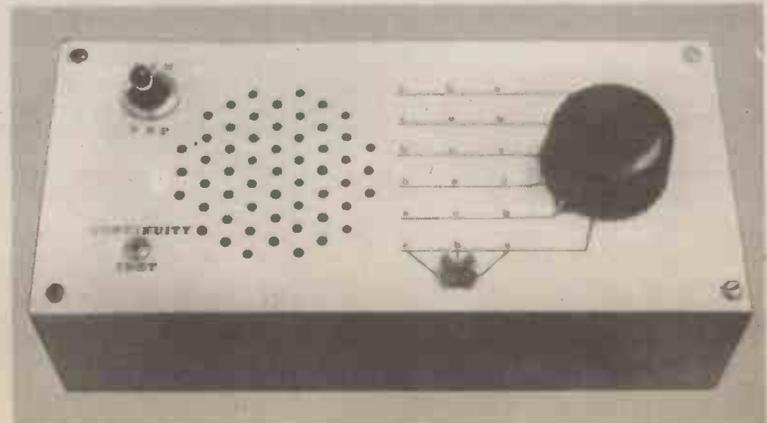
## USING THE INDICATOR

The indicator is extremely simple to use. The unknown transistor is inserted in the transistor holder and S1 rotated through its six positions; if no

shorted. In practice the presence of a resistance of a few ohms between the prods still produces a tone; there should be no confusion however because the pitch of the tone changes noticeably. □





By ADRIAN HOPE

ALMOST everyone has a love/hate relationship with their telephone. Recently the British Post Office made a gesture that should engender a little more love. We all know it costs considerably more to place a call through an operator than to dial it direct. But until recently this extra charge was levied even where the subscriber had only called the operator out of desperation, for instance, because direct dialling had produced wrong numbers or dead or crossed lines.

This surely made the Post Office one of the only firms that penalised customers for its own mistakes! But now a concession has been made, and if a call fails the operator will connect you at around the cost of dialling direct.

Incidentally, it isn't an old wives' tale that calls fail and the phones always go wrong in wet weather. It's fact. Because our skylines are now largely clear of telephone lines (think when you last saw a telephone pole, and it may surprise you), virtually all our phone cables run in channels underground. And, quite simply, when it rains the channels fill up with water, the wires get wet and circuits short. It's as simple as that; but you'd be surprised how many people don't realise it.

### Interference Problems

A reader wrote recently asking if there were any steps one can take to minimise the interference one gets on a.m. mains intercoms, i.e. wireless intercoms. Because he was thoughtful enough to enclose a stamped addressed envelope, I promptly wrote back, but with the depressing news that there is really absolutely nothing one can do.

As we have previously reported the mains is now horribly cluttered with audio interference, as generated by thermostats, fluorescent lights and worst of all thyristor dimmers. As a

result a.m. intercoms, which use the mains as their audio frequency link between station and station, are inevitably terribly noise-prone. Things got so bad in the USA that f.m. (frequency modulation) rather than a.m. (amplitude modulation) intercoms are now available, and at least one model is now sold in this country. The cost is high, over £40 a pair. However, because virtually all mains-borne interference is a.m. rather than f.m., they can provide virtually noise-free communication, just as f.m. radio reception is virtually immune from most forms of interference.

### Money In Your Pocket

With Post Office rental charges continually rising, it is opportune to recall how one can quite legally cut Post Office costs in a small business situation by using these instruments. Consider, for instance, boss in one room and secretary in another. Ideally both have a telephone extension, but the secretary has one of the type which enables her to receive calls, talk to boss, and selectively route calls through. But of course these (the Post Office call them Plan 107 installations) cost more to rent than ordinary extension phones. What you do instead is have ordinary extension phones in each room, with the boss's phone equipped with the standard Post Office switch to enable its bell to be silenced. You also have a pair of f.m. wireless intercoms, one in each room. The crucial point, often overlooked, is that when a telephone receives an incoming call it can be temporarily hung up without disconnecting that call. So when secretary receives an incoming call, she simply says "hold on", hangs up her phone and buzzes through and talks to boss on the wireless intercom to advise him of the call.

Boss then either picks up his extension phone or asks secretary to pick up hers again and deal with the call. What the secretary must never do is hang up her phone on an outgoing call before boss has picked up his, because this will disconnect it.

At current Post Office prices, you save £17.60 per year on phone rental by adopting this simple approach! All we need now is for an enterprising British electronics firm to produce a cheap and reliable f.m. wireless intercom. (Certain regulations govern the use of a.c. mains intercoms, and the Local Electricity Area Board should be consulted before installing such instruments.—Ed.)

### Regulations

Finally, although the Post Office regulations may seem irksome to anyone encountering them they are founded on sound common sense. For instance, it seems highly irritating that the Post Office insists on answering machines being connected by only a few approved firms who are willing to observe rigid technical specifications. One such requirement is that an automatic gain control must be built into the answering machine record circuitry, so that it will ignore any signal more than 35dB below the 1 volt reference level and disconnect the machine from the telephone line altogether if this minimum threshold level is not reached again after 10 seconds.

This, of course, increases the price of a machine; but it also means that no low-level conversations, which may result from crosstalk between unrelated lines, can be recorded. Think of the number of times that you have heard faint conversations in the background to your own call equate that with the number of times your own conversations must interfere with other calls, and be thankful that legitimately installed recording machines won't be able to record them.



"A computer made Nigel redundant—it took up all his office space."

FOR many amateur gardeners, the watering of plants is a rather sporadic affair, depending on luck rather than judgement when they actually are watered. For optimum results, however, it is necessary to know how wet the soil is at root level, and to a reasonable degree of accuracy.


Obviously, some sort of gadget is needed which can display this information in a clear and direct way. A design to do just this was published in E.E., March 1975. It used the principle that the moisture of the soil is proportional to its resistance. Using one transistor in an emitter follower configuration, a light emitting diode was made to light up, its brightness being proportional to the resistance between two probes inserted into the earth.

In theory, this circuit is excellent, and has the advantage of being cheap and simple. Its limitation, however, lies in the use of a light emitting diode to display the information. There is not very much difference between, say an l.e.d. which is at 40 per cent of its potential brightness, and one which is at 50 per cent. The use of a visual method means that the ambient lighting can make results seem misleading; in bright sunlight, the l.e.d. might seem to be almost off, while in subdued lighting, it might seem quite bright, even though the current flowing

FOR  
GUIDANCE  
ONLY

ESTIMATED COST  
OF COMPONENTS  
excluding V.A.T.

£2.50  
excluding case

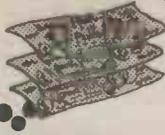

through the diode in the two cases was the same.


The author decided to try to improve the situation and toyed with the idea of using an ammeter to display the current flowing, but this idea was abandoned, mainly because of the high cost of meters. Instead the following design was evolved.

The controlling factor is the resistance of the soil between two probes, but the indication is through a loudspeaker, which emits a loud clicking noise when a circuit is made between two probes; the rate of clicking is dependent on the resistance between the probes.
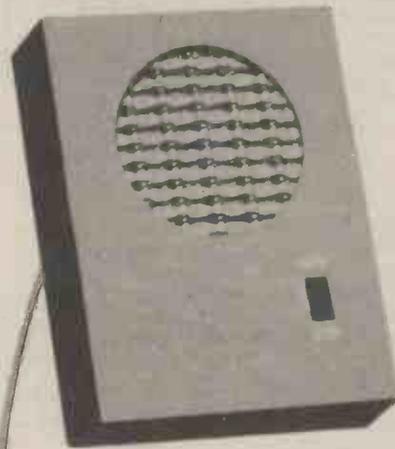
#### CIRCUIT DESCRIPTION

The circuit diagram of the Soil Moisture Monitor is shown in Fig. 1. It is in fact a relaxation oscillator. Its advantages over a standard multivibrator are that it only needs one capacitor, and it can be made to have long off periods, and short on periods, thus cutting down on current consumption.


When the voltage is applied to the circuit, capacitor C1 begins to charge up. The base of TR1, which is an npn type is almost at negative supply potential. It begins to get more and more positive as the capacitor charges up until it begins to conduct. Transistor TR2 now begins to charge



# SOIL MOISTURE MONITOR

By J. JENKINS

## HOW IT WORKS

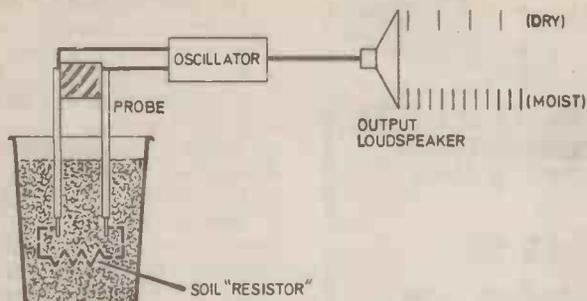

The *Soil Moisture Monitor* consists of an oscillator with a component missing—a resistor. This resistor is vital for the oscillator to work and its ohmic value determines the frequency of oscillation. This "resistor" is the d.c. resistance between two specified points in the soil and is brought into circuit by means of the probes inserted in the plant pot, usually to root level.

Moist earth has a lower resistance than dry earth so the output frequency (heard in the loudspeaker) will indicate the dampness of the earth in the vicinity of the probe tips.

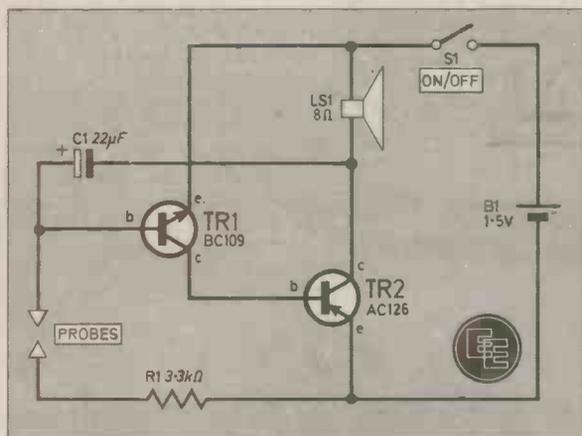


Fig. 1. The circuit diagram of the Soil Moisture Monitor.

up until it too conducts. At this point, a current is passed through LS1. The voltage on the collector of TR2 now becomes more positive, discharging C1, and starting the whole process again.

The rate at which this all happens depends on how quickly the capacitor can charge up, and its value. The former depends on the resistance between the probes, together with R1 in series with it.

It was found that almost any species of transistor will function in this circuit, the only critical factor being that one must be *npn* and the other *pnp*. The two named in the component list were chosen because of their cheapness and ready availability.

Soil resistance is typically 100,000 ohms and 2,000 ohms ranging from completely dry to saturated, and so the component values have been chosen to give between 3 clicks per second, and one click every 3 seconds.

## CONSTRUCTION

The unit was constructed on a small piece of 0.1in. stripboard, measuring 18 holes x 10 strips. The board, with components is shown in Fig. 2. Capacitor C1 is mounted upright on the board, taking note of the connections. The lead out connections to the two transistors are shown. These should be noted, as the two are different.

Just about any case could be used to house the project. An old tobacco tin covered with Fablon was used to house the prototype, but some will prefer the rather more conventional aluminium cases available. It is a good idea to put a piece of foam rubber in the box, to stop the battery rattling inside. Holes must be drilled to accommodate the switch, and for the leads to the probes. If a metal case is used, it is a good idea to have a rubber grommet on the hole to stop the wires rubbing against the metal. Holes must also be drilled to allow the sound to escape from the speaker.

## PROBES

Details for constructing the probes are given in Fig. 2. Although the dimensions given are not absolutely critical, it is a good idea to stick reasonably close to them. They are constructed from strong aluminium.

## Components

**Resistor**  
R1 3.3kΩ ¼W 10% carbon

**Capacitor**  
C1 22µF 10V elect.

**Semiconductors**  
TR1 BC109 silicon *nnp*  
TR2 AC126 germanium *pnnp*

**Miscellaneous**  
S1 d.p.d.t. slide switch  
LS1 8'ohms miniature loudspeaker approx. 56mm round  
B1 1.5V U7 battery

Stripboard 0.1 inch matrix 18 holes by 10 strips; small aluminium case; grommet; connecting wire; insulation tape; wood for probes 25mm x 40mm x 15mm; aluminium 100mm x 15mm 14 s.w.g. (2 off); No. 8 round head screws (4 off).

See  
**Shop  
Talk**

page 263

# SOIL MOISTURE MONITOR

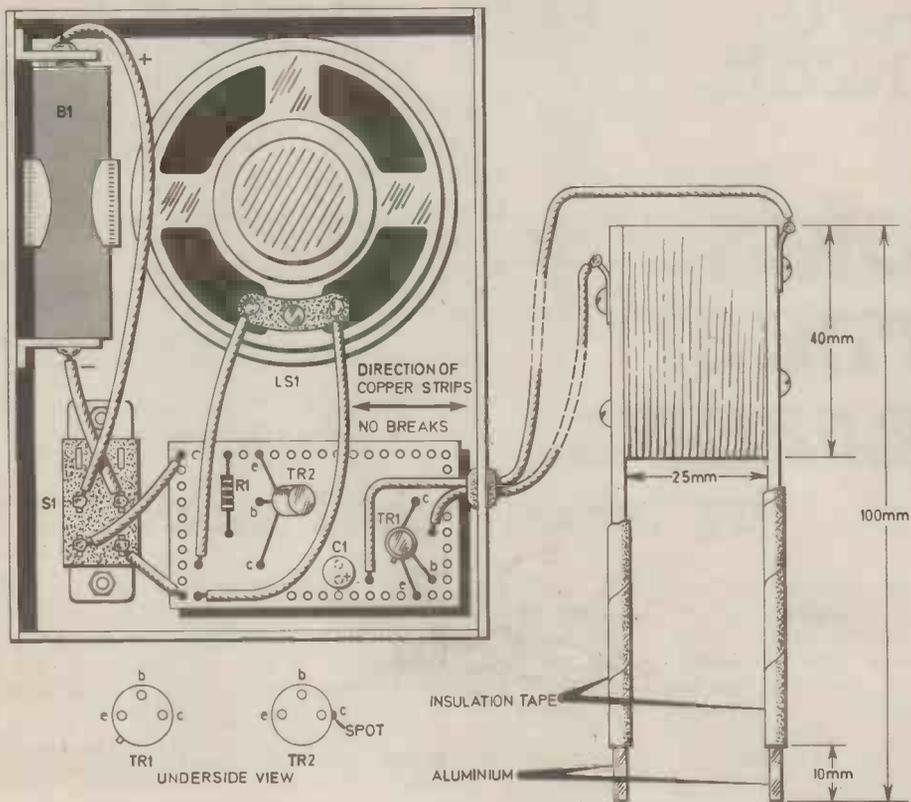


Fig. 2. Layout of the components within the case and complete wiring up details. Also shown are details of the probe.

The easiest way to cut this is with a hacksaw, and then filing down the rough edges.

The aluminium is covered with insulation tape, except for the extreme ends. Care should be taken that the screws which secure the metal do not touch inside the wood, or the probes will be shorted out.

## TESTING

After connecting the battery, switch on, and short out the probes with a short length of wire. A rapid clicking, possibly even a buzz, should be heard from the loudspeaker. If there is nothing, the things to check are battery polarity, transistor connections, the polarity of the capacitor, and to make sure that all the soldered joints are firm.


Assuming that something is heard from the speaker, grasp



the probes firmly in both hands. The clicking should continue, but much slower (body resistance is roughly the same as that of dry soil). Now insert the probes into samples of soil with varying moisture content. If, in general the clicking is too rapid, add some more insulation tape. If it is too fast, remove some. If this makes no difference try changing the value of R1. The value given should, however, be adequate.

# The Extraordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett

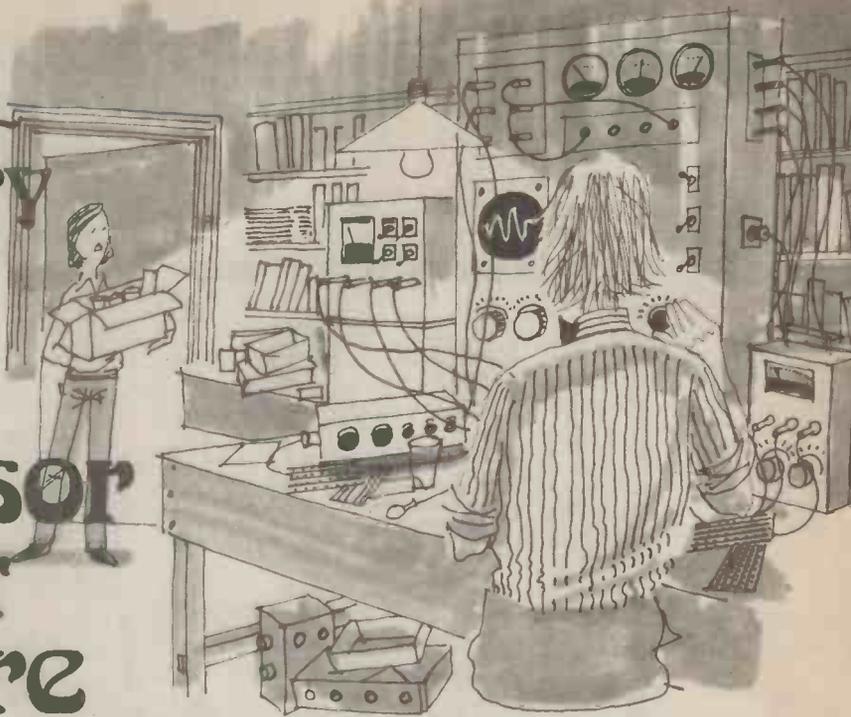

THE Prof. has just constructed a simple contact-microphone which can also be used to test various materials for piezo-electric activity. By placing a slice of material which has been coated with metal or graphite on its opposite sides, underneath a spring, the experimental samples can be changed very easily.

"Here is an interesting sample, Bob," the Prof. remarked. He carefully unwrapped a tiny disc of metallic appearance from its tissue-paper packaging. "It is a specially prepared ceramic material which has been silver-coated on its opposite faces by the manufacturer. We'll try this in the contact-microphone, as I think you'll find the result is quite surprising."

Bob turned down the volume on the audio amplifier whilst the Prof. lifted the spring and carefully substituted the ceramic disc for the previous sample. With the disc firmly in place, Bob turned the volume back up. Immediately a loud rustling and rumbling sound came from the loudspeaker, and a startled Bob quickly turned the volume back down again.

"Wow, Prof! That is amazing," Bob cried out in astonishment. "That little disc is obviously very much more sensitive than the other samples which you suggested. You were still handling

the contact-microphone when I turned up the volume and the sound was picked up and amplified to such an extent, that I thought it might damage the amplifier!

"With such high sensitivity it is hardly surprising that ceramics are used so much in pick-ups and microphones!"

"Yes," agreed the Prof., "and ceramic materials have a number of other advantages, when used for piezo-electric purposes, over grown crystals of materials such as Rochelle Salt and quartz. Although the ceramics materials are not as easy to prepare as, say, crystals of Rochelle Salt, I will describe their preparation briefly to you, and then you will see what some of these advantages are, and how they come about during the production processes.

"In many ways the production of these materials is similar to the making of other ceramics such as unglazed pottery and porcelain, which are made by carefully shaping a wet mixture of clays, drying it out, then heating it to a high temperature in a kiln.

## BLENDING

"When the claylike mixture is prepared, one obvious advantage is that other ingredients can be blended in, to modify the

properties of the product. Materials can be added to make the product stronger, to change its density or its co-efficient of thermal expansion, to make its output more linear and to modify its properties in many, many desirable ways which cannot be done with grown crystals.

## A DANGER

"A disadvantage is that many of the materials used at this point, such as lead zirconate, and barium titanate, are poisonous, and precautions must be taken to ensure that the material is not eaten or allowed to enter cuts or wounds, and that any airborne dust or fumes are not breathed in.

"When the material has been blended, it can be shaped, by pressing, moulding or stamping, into shapes which may be simple, like the disc which we have here, or rings, squares, cylinders, bowls etc, and also other more complicated shapes may be prepared with electrically conducting inserts moulded in, and each of these shapes has special uses.

"When the shapes are fired in the kiln they change slightly due to shrinkage, so that wherever accuracy is required, the final shape and dimensions are reached by grinding the ceramic after it has been fired.


## POLARISATION, MAGNET OR ELECTRET

"Thin coatings of silver, or other electrically-conducting substances, are applied and the material is then polarised." "What does this mean, Prof?" Bob enquired, "Is it something to do with magnetisation?"


"The polarisation of a ceramic material for piezo-electric purposes is very similar in some ways to magnetisation, Bob, but instead of using a magnetic field we use an electrostatic field. Instead of becoming magnetically polarised like a magnet, the material becomes electrically polarised. Sometimes a material which has been permanently electrically polarised is referred to as an *electret*.

"The effects of temperature changes are very important during the process of polarisation. If we consider the classic case of a charged capacitor with a solid dielectric, and use the concept of lines of force to represent the electric field, the capacitor can be represented by a simple diagram." The Prof. drew a sketch (Fig. 1a.)

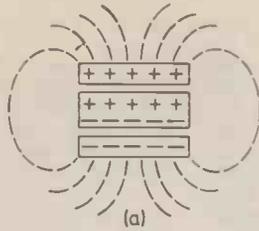"Now if we remove the conductive plates from the dielectric", the Prof. again sketched on his notepad (Fig. 1b), "the dielectric remains charged. The lines of force of the electric field are held in place in the dielectric by the electric charges which remain on its opposite faces. But the



(a)

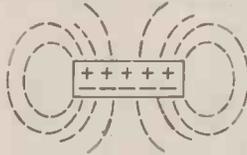

(b)

Fig. 1. Lines of force associated with a charged capacitor (a) with conductive plates (b) without plates.

dielectric is only temporarily polarised, and by removing the charges, which can be done by re-assembling the capacitor and discharging it, the electric field can be made to disappear." (This can be done with different metal plates, proving that the charged field resides in the dielectric.)

## ELECTROPHORUS

"Prof!" Bob interrupted excitedly, "that reminds me of a really interesting experiment which we did at school with a gadget called an *electrophorus*. It

produced such a powerful electric field that it caused small objects to *take off* and hover in mid air or fly through the air. After the school teacher showed us that, there was quite a crop of home-made ones which the lads made for themselves, and I was so fascinated that I made one myself at home. Next time I come to see you I'll bring it to show you!"

"Hmmm, yes" mused the Prof., it's quite a while since I last experimented with an electrophorus. It's also quite late, I must remind you."

Bob in his enthusiasm had stayed much later than he had intended, and as he looked with dismay at the time displayed in huge luminous figures on the viewscreen of one of the Prof's computers, and hastily prepared to leave, the Prof. continued: "I'll be interested to see your home-made electrophorus so I hope you'll bring it soon! It will certainly help to illustrate and demonstrate some of the points I am explaining about polarisation, and then we can continue our discussion of piezo-electric, magnetic and various types of pick-ups. See you soon, Bob."

"Yes, bye Prof.," and Bob hastily made his way out of the laboratory and sped off home, his head full of thoughts about electric polarisation pick-ups and microphones and anticipation of his next visit to show the Prof. his home-made electrophorus.

To be continued



Readers' Bright Ideas; any idea that is published will be awarded payment according to its merit. The ideas have not been proved by us.

## HEAT SHUNT

I have thought of a tip that may prove useful to constructors. It is the use of a split pin as a heat shunt for use on transistor and diode lead-outs when the latter are being soldered in place.

I have been using a 4mm thick pin with the

ends of its legs cut square, one being longer than the other. The pin then clips over the lead-out on the component side of the board and is small enough to thread its way in among other components in the vicinity.

O. Maxwell,  
I.O.M.

## P.C.B. AID

I have recently come across a way of accurately placing an integrated circuit on a piece of copper clad printed circuit board.

Take a small piece of 0.1 inch matrix strip-board and drill through the holes where the i.c. pins go through using a No. 45 drill (2mm).

This then acts as a template, for it can now be placed in the required position on the copper side of the p.c.b. and a sharp pointed pencil used to mark each hole through onto the board. The outlines produced are next filled in using an etch resist pen, and the rest of the pattern then drawn on in the usual way.

I have found this ideal for making printed circuit boards using i.c.s of various kinds.

K. Nuttall,  
Bureley,  
Lancs.



## Quasi-Quad Queries

I am one of your so called non-specialist onlookers, and whilst browsing through your March '77 issue, I decided that I would have a go at constructing the *Quasi-Quad Adaptor*. Being a potential starter, with your article my trainer, I am writing to ask a few questions and ask for tips.

I have had limited experience of electronics ('A'-level Physics failure, and I have knocked up radio's etc. from kit form and many years ago played with those early Phillips kits of electric wizardry for the under-15's), but I have never touched a circuit-board and I was confused by the diagram of Fig. 5 (page 116), of the *Quasi-Quad Adaptor* article, as I cannot differentiate between the "dots" and "circles" etc.. Could you clarify?

Another point I do not understand (or cannot visualise) is the fitting of copper strips to act as heatsinks to the whole of the stripboard (or is this because I have never seen a section of stripboard?).

Also the LM380 has a rated output of 2 watts, but in my stereo system (20 watts per channel), this would surely not suffice, as on average, the output will be at 8 to 10 watts per channel. Does this mean that the speakers will be at less power, i.e. less volume? Will this destroy the effect created (especially if four similar speakers are used)? And lastly is there any real danger to my hi fi system if I make a constructional error?

J. Westray,  
London SE23

The area of Fig. 5 you refer to (dots and circles) shows the underside of a piece of Stripboard. Stripboard consists of strips of copper (shown white) bonded to a synthetic board (shown black). The board is perforated, with holes drilled on a regular matrix at 0.1 inch or 0.15 inch pitch. Not all these holes are shown on the drawing in order to avoid a cluttered effect, in fact only those immediately inside the perimeter of the board are shown.

The black dots you refer to are the soldered connections of the component leads (sited on the topside of the board—shown adjacent to the underside view) to the copper strips. What at first sight appears to be a white dot surrounded by a black area is used to represent a break along the copper strip made by using say a twist drill.

The second part of your query should be answered by the above and by you inspecting a piece of stripboard.

Concerning the power rating of the LM380, this should be adequate. You are over-estimating the listening level. For comfortable listening in the home, your amplifier will only be delivering about 1 watt or even less.

See Please Take Note in April issue for wiring correction.

## Identification Data Service

With respect to Mr. Pascoe's plea for someone to operate a device data and identification service I am willing to undertake this operation for a cost of 10p per device for a minimum of 10 devices. An additional 15p needs to be included for postage and packing expenses. With respect to i.c.s it would be helpful if one or two of them could be sent to assist with their identification.

R. Houghton,  
49 Addington Road,  
Irthlingborough,  
Northants.

## Lin. and Log.

I am aged 12 and have been reading your magazine for quite a while now. I have constructed some of your "starter projects" and am now ready to construct the *Transistor Tester* in the May '74 issue. (I found it while looking through some of my back-copies.)

One thing that puzzles me is linear, logarithmic, anti-logarithmic etc., when referring to potentiometer slider rotation. I would be grateful if you could explain these to me. Keep up the good work publishing an excellent magazine.

Paul Bailey,  
Rutherglen, Glasgow

The terms, logarithmic (log.), linear (lin.) and anti-logarithmic (anti-log.) refer to the variation of resistance between the slider and one end of the potentiometer as the shaft is rotated. In a linear type, the resistance is directly proportional to the angle of rotation, i.e. if 45 degrees rotation produces 10 kilohms, then 90 degrees rotation produces 20 kilohms.

Now in a log. type, the variation of resistance with angle of shaft rotation, obeys a logarithmic relationship i.e. if a 45 degree rotation produces 10 kilohms, then 90 degrees rotation produces 100 kilohms. A further 45 degree step increases the resistance to 1,000 kilohms (1 megohm).

The anti-log. type potentiometer, has as its name implies an anti-log relationship of resistance with shaft rotation.

## Revival Rally

We have been informed by the Radio Society of Great Britain, that a rally, named the "East Suffolk Wireless Revival" is to take place at the Civil Service Sports Ground, Straight Road, Bucklesham, Ipswich. The rally will be open from 11am to 4pm, 29th May 1977.

It is intended to revive some of the interest and enjoyment of the "pre-black box" type of rally. The emphasis will be on finding out, participating as well as purchasing.

By holding the event out of doors rather than in a school or hall, whilst providing covered areas for traders and demonstrators, there will be freedom to move around with the family or just sit and ragchew.

Trade participation and the ability to look for that special component etc will be well catered for in a large marquee. Presenting practical demonstrations, competitions and information it is hoped to encourage attendance from licence holders, short wave listeners (swl) and those interested in the whole spectrum of amateur radio.

It is hoped that by reference to those with experience, ideas as to solutions with problems on TV and radio interference etc may be found.

A comprehensive range of equipment will be used to provide a facility for testing mobile equipment and an antenna test range to check the gain of both professional or home built aerials brought to the rally. It is hoped to arrange demonstrations, to both encourage the newcomer and interest the active participant in, RTTY, RAYNET, SSTV etc.

## Plastic Money

I have read with interest the *Counter Intelligence* article in the March '77 issue of E.E. and note the comments regarding the "Metal Strip" in pound notes. This metal is in fact a fine strip of polythene which has been sandwiched between two pieces of fine quality paper.

I note that the editor makes mention in his editorial of the "barrier" which often surrounds the whole subject of electronics. I have to date assembled a capacitive discharge electronic ignition system kit and the *Wiper Delay* unit published earlier this year in E.E. Other than this the subject is very new to me.

The greatest hurdle is understanding your abbreviations and nomenclatures of components, i.e. s.p.s.t.; 500 kilohm carbon lin.

Is it practical to publish some form of dictionary or supplement to help beginners like myself to understand what these abbreviations mean? Apart from this I find E.E. easy to follow and most interesting.

J. Little,  
Yorks.

We have recently, in the Feb. and April issues published a list of abbreviations of technical terms used in E.E. It is hoped to publish such a list from time to time and possibly extend it to include such things as explanations of... 500 kilohm carbon lin. The latter refers to a potentiometer whose maximum resistance is five-hundred-thousand ohms, is constructed (internally) of carbon and has a linear resistance/rotation relationship. See reply to Mr. Bailey's letter above.

LAST month, details of the mixer, oscillator, and i.f. amplifier were given. We continue this month with the construction and details of the optional b.f.o. unit.

Note once again that Denco coils should now be used, as mentioned in part one (May '77 issue).

## PANEL AND CHASSIS

The case sides are plywood, 190×115mm, and the chassis a 255×100mm "universal chassis" flanged member secured with four bolts through the flange holes, and set 63mm back as in Fig. 5. The chassis top is at a height of 38mm.

The panel is a similar member, but is fixed vertically with bolts through the flange holes, and leaving about 35mm clear between chassis and panel, as in Fig. 5. Holes for the lower controls are 25mm from the bottom, and 41mm and 100mm from the sides. Variable capacitor VC2 is mounted as shown in Fig. 5, so that the drive drum is about 3mm clear of the panel top.

A piece of wood 127×45×10mm thick is screwed to the panel to carry the scale.

Pivot one of the drive pulleys on a bolt as shown in Fig. 5 so that the top of the cord is level; the second pulley is mounted about level with the bottom of the drum. The cord has one complete turn round the tuning control shaft, and runs over the pulleys to the drum. Here, the ends are taken through the perimeter slot, and are tied to the spring, which keeps the cord taut.

A scale about 100mm long is needed, and in the author's model a 10cm paper rule was used, glued to card which was in turn stuck to the wood. A small piece of tinplate is bent and clipped to the cord with pliers, and the pointer is a straight wire soldered to this.

The front of the receiver is Perspex, 250×100mm, covered with self-adhesive material in which an aperture 115×28mm is cut, to match the scale position. Thin plywood or a metal front could be used instead, with an

aperture cut in it. The front is secured by four 6BA bolts (at least 25mm long) with extra nuts, and running through the holes present in the flanged member.

## ADDITIONAL WIRING

The boards are fitted as shown in Fig. 5, which also shows interconnecting wiring. Inductors L5 and L6 are secured with 6BA bolts, and wired to a tag (MC) bolted to the chassis. After making the connections of Fig. 5, reference should be made to Fig. 6, an underside plan with the panel shown flat to clarify the switch wiring. It may be preferred to first wire S1/4 for one waveband only and then test the tuner. If this system is not used, take special care to ensure that the correct tags are used in wiring up the switch.

Inductors L1 and L2 are wound on a cored former 11mm ( $\frac{7}{16}$  inch) in diameter, although formers of 9mm to 13mm ( $\frac{3}{8}$  to  $\frac{1}{2}$  inch) diameter would be suitable.

Designed to receive transmission on short, medium and long wavebands.

# Multi-band TUNER

PART 2

By F. G. RAYER



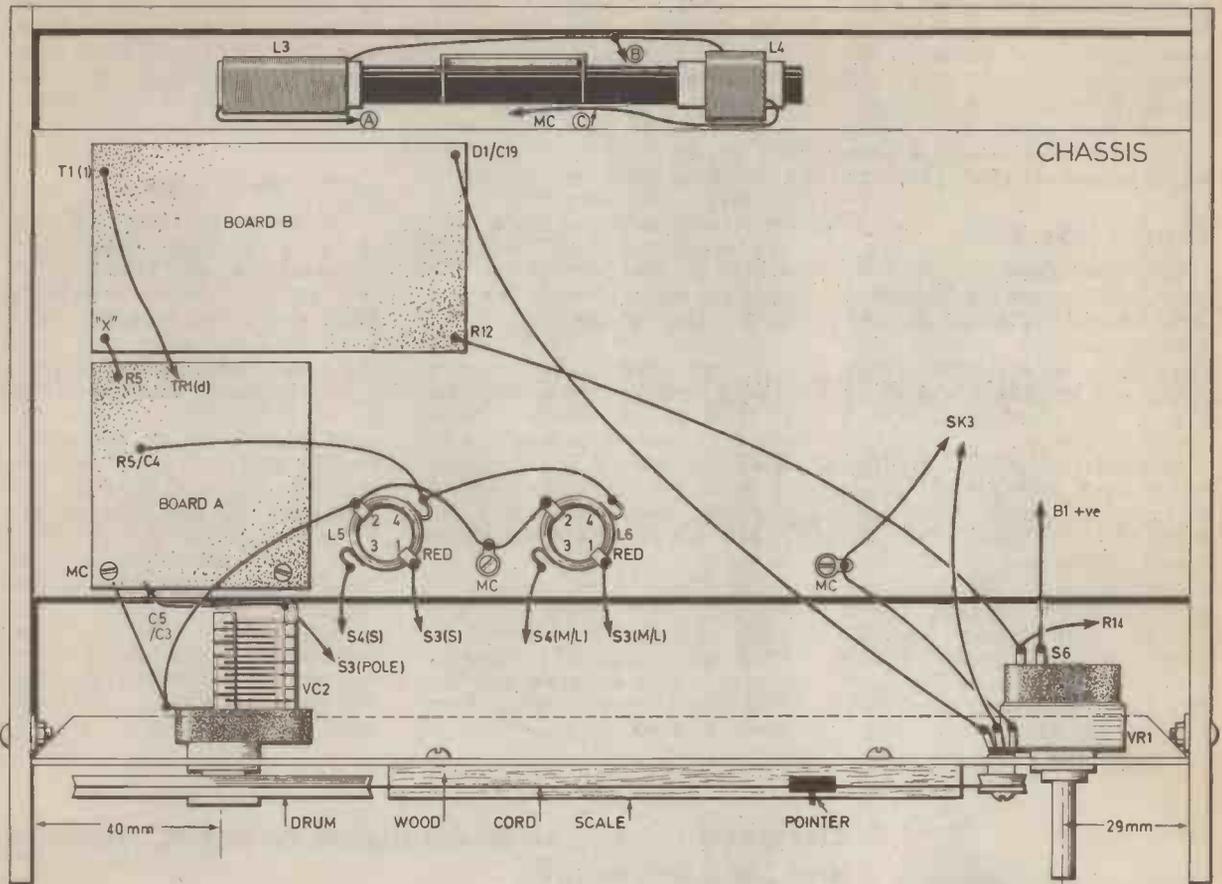


Fig. 5. Topside view showing position of component boards. Note that Wearite coils are shown as used in the prototype.

The secondary winding of L2 (points 1 to 2, Figs. 1 and 6) consists of 31 turns of 26 s.w.g. enamelled copper wire, the turns being wound side by side. The primary winding of L1 (points 3 to 4) is made up of 8 turns of cotton-covered wire (or enamelled wire on insulating tape) of 26 to 32 s.w.g. The ends of 2 and 4 should be taken to the tag MC, to which also is wired the stator connection of VC1. Ends 1 and 3 should be long enough to reach S1 and the aerial socket. A few touches of adhesive should be used to secure the coil turns in place.

A 75x25mm strip of wood or paxolin is bolted to the rear flange of the chassis (Fig. 5) and the ferrite rod is secured to this with adhesive and thread or string. Coils L3 and L4 are positioned as shown and the leadout wires are taken to a small tag strip near the rod, so that longer leads can be run to S1 and S2; L4 must be the correct way round

on the rod, as shown in the maker's leaflet, otherwise it will not be possible to obtain proper long wave tuning.

### DIAL MARKINGS

A slow-motion drive is not essential for the aerial tuning capacitor VC1, but it should be provided with a pointer. The two multiway switches will also require pointers. The scale for S1/4 should be marked up as follows:  
 Mark the L position: 125-309kHz  
 Mark the M position: 500-1685kHz  
 Mark the S position: 10-2.9MHz.

The scale for S5 should be marked up as follows:

On the L band, mark position 6 309-238, position 7 238-191, position 8 191-158, position 9 158-125.

On the M band, mark position 1 1685-885, position 2 885-620, position 3 620-500.

On the S band, mark position 1 10-7.3, position 2 7.35-7, position 3 5.75-0, position 4 5.0-4.4, position 5 4.4-3.9, position 6 3.9-

3.6, position 7 3.6-3.35, position 8 3.35-3.2, position 9 3.2-2.9.

The bands are arranged so as to discount the slight overlap which will be found at the extreme positions of VC2 rotation.

The use of three different colours will make the scale of S5 easier to read. See Fig. 9 for suggested arrangement of the markings for the two waveband switch scales.

### TUNING

Set the switches for the frequency sector required. Then tune in signals by means of VC2 and peak them with rotation of VC1. The handling of the two controls will soon become simple in practice. If VC1 cannot reach the lowest frequency on band S when fully closed, screw the core of L2 slightly into the winding. Similarly, place L3 and L4 on the ferrite rod so that VC1 covers the wanted ranges with a little to spare.

# Multi-band

# TUNER

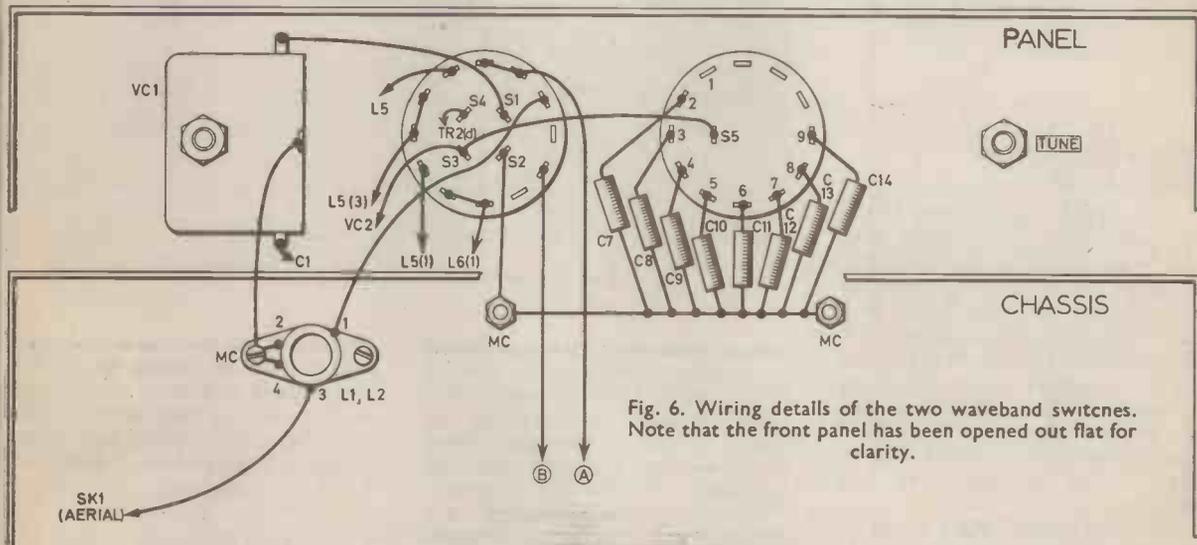


Fig. 6. Wiring details of the two waveband switches. Note that the front panel has been opened out flat for clarity.


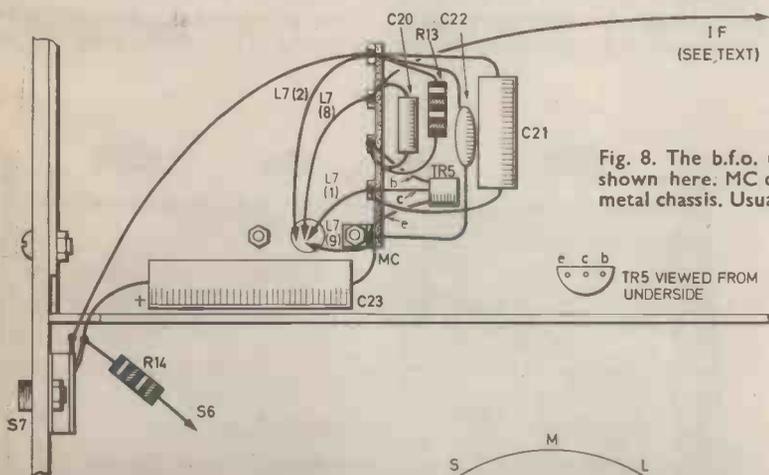


Fig. 8. The b.f.o. unit is wired on a small tagstrip as shown here. MC denotes a direct connection to the metal chassis. Usually made by fitting a solder tag with a nut and bolt.

Fig. 9. Suggested markings for the two waveband switches. These are drawn full size, and may be traced.

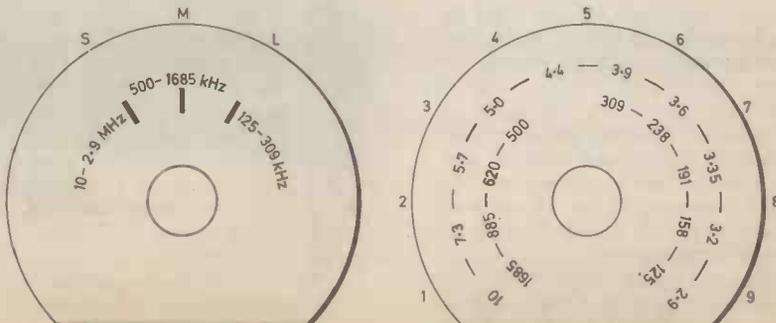

The aerial for short wave reception may be an outdoor one or a wire indoors (perhaps running along a picture rail or similarly, as high and long as practicable).

If an earth is available, this should be plugged into a socket connected to MC. A short aerial will provide reasonable results on the more powerful stations, but for the weaker signals a long outdoor wire will give considerably improved results.

## BEAT FREQUENCY OSCILLATOR

This unit is required only if the operator wants to receive c.w. and s.s.b. signals satisfactorily. Amateur and commercial stations using Morse code do so by using c.w. transmission (an interrupted unmodulated carrier wave) which normally cannot be heard on an ordinary receiver. Some stations use m.c.w., which is a c.w. signal modulated with an audio tone so that it can be heard on any receiver.

The function of the b.f.o. is to render the c.w. signal easily audible. It is basically a simple oscillator and when in use the b.f.o. signal beats with the incoming c.w. signal to produce a heterodyne signal at a predetermined audio pitch.

With single sideband signals, the carrier wave and one sideband have been removed. The carrier/b.f.o. unit supplies a carrier at the tuner, thus enabling the s.s.b. signals to be resolved as speech. This form of transmission is widely used by amateurs, particularly in the 3.5-3.8MHz band.

The circuit of the carrier/b.f.o. unit is shown in Fig. 7. The b.f.o. coil L7 is a Red Range 2 valve type coil and it has C21 in parallel across its primary winding to complete the tuned circuit. Adjustment of the coil core allows the oscillator to be tuned to the correct frequency, after which the core should be locked with a 6BA nut.

Switch S7 is the on/off switch which puts the b.f.o. off for a.m. reception. The purpose of the large value C23 is to prevent modulation of the oscillator via the battery supply.

The coil L7 is supplied in a can which serves as a screen. The lid should be bolted on the chassis behind the volume control, and

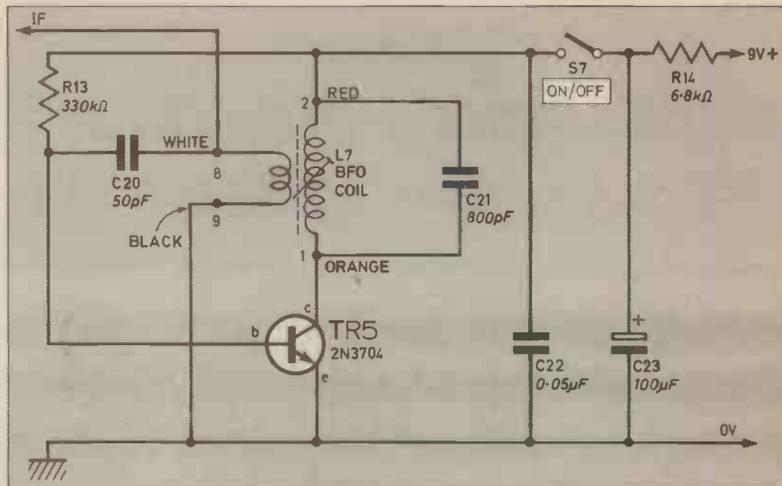


Fig. 7. Circuit for the b.f.o. unit used in the Multi-band tuner.


a 6mm hole for the leads should be provided. Next drill the bottom of the can to take the coil. Solder on four leads (which may be colour coded) to the pins shown and take the leads through the hole and out under the chassis.

The other components are mounted on a tag strip as shown in Fig. 8, the oscillator coil L7 fitting nearby on the case side. A lead should be run from the tag used as a junction for the lead from coil lead 8 and along under the chassis and up to the pin from

T1 (pin 1) on the i.f. board; this lead should be looped round the pin *without removing the insulation*. Because injection is at the i.f. amplifier input, this very small coupling capacitance is sufficient for the purpose required.
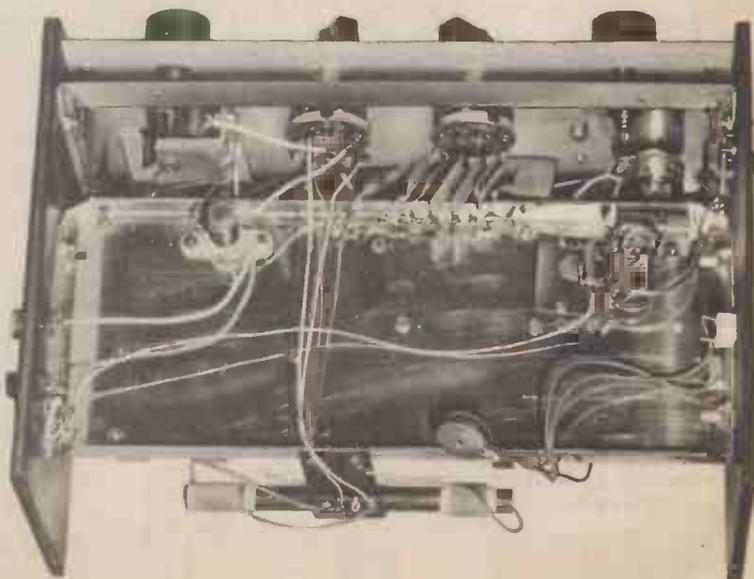
## B.F.O. ADJUSTMENT

The b.f.o. performs best with the audio gain at or near maximum; if necessary the volume can be kept down by slightly detuning VC1. First tune in any



Underside photograph, showing the waveband switches, and the b.f.o. unit.

stable broadcast with the b.f.o. switched off. Then switch on (S7) and rotate the oscillator coil core until a strong heterodyne is obtained. This will fall in pitch as the correct core position is reached and rise again as it is passed. Set the core at the position where the tone is very low in pitch, or ceases. Slight detuning by means of VC2 either way will then produce an audio tone which rises as the tuning is moved away from the correct position.

Next, find a weak s.s.b. signal, which will be recognised as distorted, chopped up speech (try the 3.5-3.9MHz amateur band) and tune it for maximum volume with S7 switched off. Then switch S7 on and very slightly adjust the core of the b.f.o. coil, if necessary, for proper resolution of the speech. The core should then be locked in position.

With a.m. signals, of course, tuning should be made for the best volume. With c.w., note the tuning will change the audio pitch. With s.s.b., tuning is more



Photograph showing the completed prototype tuner.

critical for proper reception but is aided by the bandspreading effect of VC2.

It should be remembered that a superhet tuner can provide reception of signals on its "second channel". This image appears 930kHz higher in frequency than

the proper, wanted, signal on this tuner but is only likely to cause problems on the higher frequencies and with VC1 tuned to place the aerial circuit on a higher frequency than the oscillator tuning.

## GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel:(0703) 772501

OPEN 6 DAYS A WEEK, 9 to 6.  
Callers Welcome.  
VAT INCLUSIVE PRICES—NO  
EXTRAS TO PAY, JUST ADD  
70p POST.

### RESISTORS

Miniature 1/4 Watt Carbon Film  
Hi-stabs, 5% (Over 1M 10%). All  
values from 1 ohm to 10 Megohm.  
1/4p each.

1 Watt Metal Film 5%. All values from  
22 ohms to 10 Megohms 2/4p each.

21W Wirewound, All values from  
0.22 ohms to 4.7k. 8p each.

5W Wirewound, All values from 0.47  
ohms to 47k. 10p each.

15W Wirewound from 1ohm to 100k  
15p each.

Sub-min presets, all values from  
22 ohms to 4.7 Megohms 7p each.

Standard Pots 22p each.

### TRANSFORMERS

6.0-6V 100mA 90p; 9.0-9V 75mA 90p;

12.0-12V 50mA 90p; 12.0-12V 100mA

£1; 6.0-6V 1 1/2A £2.70; 12.0-12V 1A

£2.90; 6.3V 1 1/2A £2.30; Multitapped

1/2p 0.12-15.20-30V 1A £3.60; 2A

£5.00; 20.0-20.0V 2A £4.20; 55.0-55V 5A

£8.00.

### TRANSISTORS AND IC's

AC127 15p BC184 12p 2N2926G 12p

AC128 15p BC212 14p

AC176 16p BC213 14p 2N3053 18p

AC187 18p BC214 14p 2N3054 49p

AC188 18p BCY70 15p 2N3055 38p

AD161 35p BCY71 15p 2N3440 54p

AD162 35p BCY72 15p 2N3442 52p

BC107 18p BD131 38p £1.20

BC108 10p BD132 40p 2N3702 10p

BC109 10p BFY50 15p 2N3703 10p

BC109C 15p BFY51 15p 2N3704 10p

BC147 10p BFY52 15p 2N3705 10p

BC148 10p TIP41A 60p 2N3708 10p

BC149 10p TIP42A 75p 2N3819 22p

BC157 10p TIP2955 96p 2N4059 10p

BC158 10p TIP3055 48p 2N4418 10p

BC159 10p 2N2219 28p 2N5295 30p

BC161 18p 2N2369 22p 741 25p

BC182 12p 2N2646 60p 555 40p

BC183 12p 2N2646 60p 555 40p

44 Page Illustrated Catalogue only  
10p + large S.A.E. FREE with  
orders over £3.

### DIODES & LEDS

1N4001, 25p; 1N4003, 46p; 1N4005 7p;

1N4006 18p; 1N4007 8p; 1N4148 4p;

OA81-91 etc. 5p; BY127 12p; 100V3A

12p; 400V 3A 15p; Bridges 400V 1A

30p; 800V 1A 40p; 250V 2 1/2A 40p;

200V 5A 70p; TIL209 Red LED 15p;

0.2" Red, green or yellow 24p.

### VEROBOARD

100sqths asstd. size offcuts, in 4 diff.

packs: Pack A: All 0.1" Pack B: All

0.15" Pack C: Mixed Pack D: All 0.1"

plain. All packs £1.20 each. 17 x 3 1/2"

boards 0.1" £1.80. 0.15" £1.60;

Plain 0.1" £1.40.

### DEVELOPMENT PACKS

Save £££'s by buying a full range of

components in one go! All full spec.

marked devices, no rejects or old

stock.

50V Ceramic plate Capacitors, 5%.

10 of each value from 22pF to 1000pF,

Total 210 for £2.70. Save £1.50!

Carbon Film Min. resistors, 1/4 watt

5%, 10 each value 10 ohms to 1

Megohm, total 610 for £6.00. Save

£3.15!

Electrolytics, 10 each value 1, 2, 2,

4, 7, 10, 22, 47, 100uF, All 25V. Total

70 for £3.20. Save £1.10!

### CAPACITORS

Miniature ceramic plate from 22pF to

1000pF 5% 2p; 1500pF to .047 4p.

Mylar 1000pF to 8200pF 5p each.

470uF 63V 18p; 1000uF 16V 15p;

Polyester .01 to 0.1uF 4p; .15, .22 5p;

.33 6p; .47 8p; .68 10p; 1uF 12p; 2.2

16p.

Electrolytic, 25V working: 1, 2, 2, 4, 7,

10, 22, 47uF All 6p; 100uF 7p; 220uF

9p; 470uF 16V 9p; 470uF 25V 11p;

470uF 63V 18p; 1000uF 16V 15p;

1000uF 25V 18p; 1000uF 50V 32p;

1000uF 63V 40p; 2200uF 16V 20p;

2200uF 25V 29p; 2200uF 40V 48p;

4700uF 16V 43p; 4700uF 25V 58p;

All the above are wire ended. Tag

ended 4700uF 40V 72p.

## SOLDERLESS BREADBOARDING—DECS

The famous DEC System of Solderless Breadboarding is ideal for both the young and more mature students of Electronic Engineering as it enables circuits to be tried and tested without the use of soldering and because of the specially designed contacts allows components to be used over and over again. It is also extremely useful for the Circuit Designer who wishes to experiment with and refine his circuit quickly yet economically.

### S-DEC (Model PB11)

This, the most popular Board, is designed solely for the use of discrete components and is particularly useful for basic educational purposes.

(No. of Contacts: 70) 1 off £1.98

5 off £1.76

### T-DEC (Model PB21)

This Board allows 2 TO5 or 1 DIL IC Station to be used and so is primarily intended for discrete work or for linear IC applications where considerable numbers of discrete components may be required.

(No. of Contacts: 208) 1 off £3.62

5 off £3.21

### μ-DEC 'A' (Model PB31)

The μ-DEC 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 TO5 stations to be used but will accommodate discrete components with equal facility.

(No. of Contacts: 208) 1 off £3.97

5 off £3.53

### μ-DEC 'B' (Model PB41)

The μ-DEC 'B' is for similar uses as μ-DEC 'A', but has two 16 lead IC sockets as part of the Board.

(No. of Contacts: 208) 1 off £6.97

5 off £6.19

## DEC ACCESSORIES

16 DIL adaptor (with socket) PB062 £1.92

10 TO5 adaptor (with socket) PB072 £1.80

Single ended leads (set of ten) PB101 £0.90

Double ended leads (set of ten) PB102 £0.99

1mm plugs (set of ten) PB103 £0.45

All prices include 8% VAT. P. & P. 25p.

Our retail counter is now open, stocking a large variety of audio and electronic parts and accessories, branded and surplus.

WE ARE SITUATED 2 MIN. WATFORD JUNCTION STATION

## THE COMPONENTS CENTRE

7 Langley Road, Watford, Herts., WD1 3PS.

Tel.: Watford 45335

# GEORGE HYLTON brings it down

## Using Old Meters

A READER from Kent, Mr. L. N. Buik, writes to say that he has picked up a couple of meters cheaply. He asks if they can be adapted for use as test meters.

This is a common enough situation. There are always secondhand meters around. So let's look at it.

The first thing to do (preferably before buying) is to make sure a meter is operational. When a smoothly increasing current is applied does the needle move smoothly? A lot of old meters stick at some point. Secondly, do the scale markings tell the truth? If the scale reads 0 to 10V is the meter really a voltmeter or just an ordinary moving coil galvanometer masquerading as one?

## Pocket Unit

A simple test circuit (Fig. 1) answers both questions. If you intend to go on a meter hunt to your local shops it's a good idea to make up this circuit as a pocket sized unit. To test a meter connect to the "110 $\mu$ A" range and turn up VRI. If no deflection is produced leave VRI at the halfway point and switch S2 to progressively higher current ranges until some deflection appears, however small. Then adjust VRI slowly to vary the deflection up to full scale and back again, watching for sticking points.

If all appears well, find a range which gives a substantial deflection with VRI

at maximum. In this position the currents on Fig. 1 are approximately correct. So you can see if the calibration of the meter is about right.

If the meter is a voltmeter the deflection will be about the same on all the higher current ranges. But many meters marked in volts are really current meters designed to be converted into voltmeters by adding an external series resistance (called a multiplier).

## Voltmeter

On the whole the most useful meters are voltmeters but a reasonably sensitive current meter (1mA full scale or less) can easily be converted into a voltmeter. I'll illustrate how it's done using one of our reader's meters as an example. This is a 750 $\mu$ A "galvanometer" (moving coil d.c. meter) scaled 0 to 100. Its dial carries the useful information: Resistance 14 ohms @ 20°C.

resistors the error due to the tolerance can be far greater than 14 ohms. In any case the full scale current may not be exactly 750 $\mu$ A so unless you can check this against an accurate meter you just don't know whether it's worth buying close tolerance resistors. I suggest cheap 5 per cent ones: most voltage measurements in electronics don't need to be made with great accuracy anyway.

Other voltage ranges can be obtained by using a different multiplier calculated in the same way. Thus for a 300V range the total resistance is 300V/750 $\mu$ A = 400 kilohms.

## Higher Reading Ammeter

Our reader's other bargain meter was 15mA d.c., resistance not given. This is too insensitive for use as a voltmeter but is quite handy as it stands since currents in the 0 to 15mA range are frequent in transistor circuits. If a higher range is required and you can find out the resistance

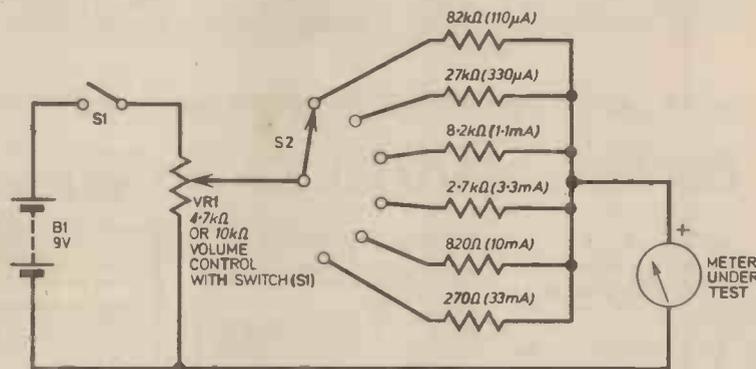


Fig. 1. The circuit diagram of the pocket meter tester. This may be constructed in a small plastic box, with VRI/S1 and S2 on the front panel. Two leads terminated in crocodile clips are used to connect the meter under test to the unit.

## Ohm's Law

To use a "0 to 100" scale the voltage range must bear some simple relation to 100. Let's make it 10V. Then with 10V applied the current has to be full scale, i.e. 750 $\mu$ A.

By Ohm's law the resistance must then be 10V/750 $\mu$ A = 13,333 ohms. The meter itself provides 14 ohms so the multiplier must provide the rest; i.e. 13,319 ohms. This is not a standard value. A fairly close approximation is given by 15 kilohm in parallel with 120 kilohm, both standard E12 series resistances. These give 13,333 ohms which as we've seen is too high by the meter's own resistance. But in practice 15 kilohm and 120 kilohm are as good as you'll get without great expense. Even if you buy 1 per cent tolerance


(please don't try to measure it on an ohmmeter or you'll wreck your bargain) it is possible to connect a "current shunt" resistance across the meter terminals.

For example suppose the 15mA meter has a resistance of 9 ohms and you want to make it read 0 to 150mA. At full scale 15mA must go through the meter and the other 135mA through the shunt. Since the voltage drop across two resistances in parallel is the same for each of them and since 135 is nine times 15 it follows that the shunt must be one-ninth of the resistance of the meter; i.e. 1 ohm in our example.

Unfortunately real-life meter resistances seldom work out quite as easily as this one and making shunts is a lot less simple than making voltage multipliers.

# to earth

# Bring 'scope' to your interest.



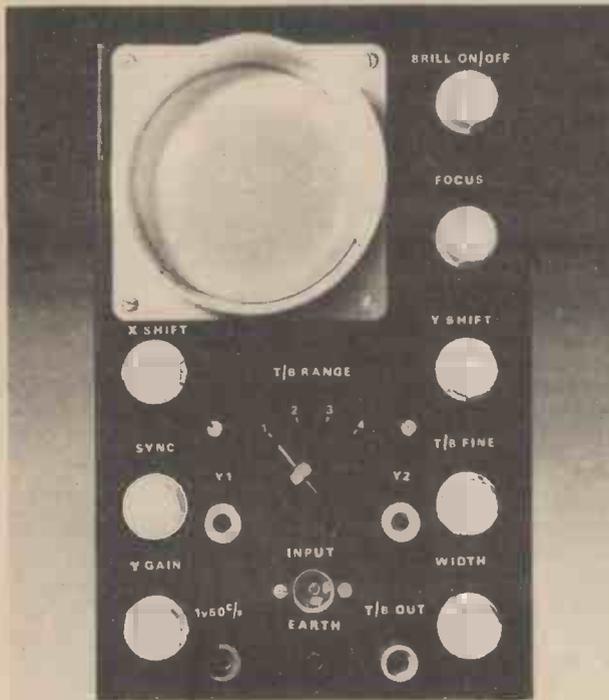


'There's only one way to master electronics... to see what is going on and learn by doing.'

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

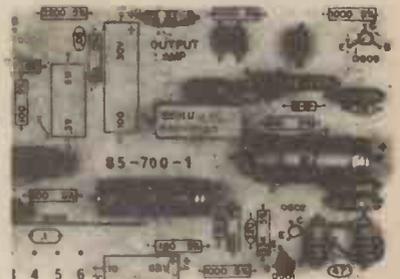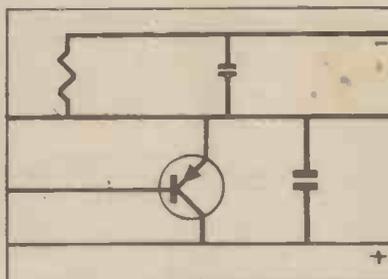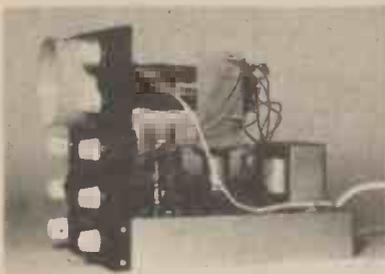All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



## 1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

## 2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

## 3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

**FREE GIFT**



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronics School,  
P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

EEB 67



## RECEIVERS and COMPONENTS

Three assorted meters £2.10. T.V. convergence Panel. 2xAC128. 3 slugged coils, 3 slide switches. 11 W.W. Pots, 3 Carbon Presets, 2 Ferrite Chokes etc. £1.40. Small audio amp, 3 Transistors, Equiv. AC128, OC72 with circuit 40p, 3 for £1. Talking Page Panel 12 allcon Transistors, SCR, 2 pots etc. £1. 100 assorted C280 polyester caps £1.15. 7lb. assorted components £2.75. List 15p, refund on purchases. Over £1 post paid, under add 20p. Insurance add 10p.

J. W. B. RADIO,

2, Barnfield Crescent, Sale, Cheshire M33 1NL

## NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £8.25 plus 20p P&P. 'Brain-Freeze' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £3.80 plus 20p P&P. Experiment with a psychodelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5.00 each plus 20p P&P. LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

## BOFFIN PROJECTS

4 Cunniffe Road, Stoneleigh  
Ewell, Surrey. (E.E.)

# SMALL ADS

The prepaid rate for classified advertisements is 14 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £9.00 per single column inch (2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

## CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publisher reserves the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

**DISCOVER ELECTRONICS.** Build twenty easy projects including: Metal Detector; Wireless Transmitter; Breathalyser; Miniature Radios; Stethoscope; Lie Detector; Touch, time switches; Burglar Alarms, etc. Circuits, plans all for £1.29 including circuit board. Mail only. Ridley photo-electronics, Box 62, 111 Rockspark Road, Uckfield, Sussex.

**ELECTRONIC DICE** as March EE. Complete kit—send £3.66. Case extra 58p. Components catalogue 25p (refundable). **MAGENTA ELECTRONICS LIMITED**, EEB, 61 Newton Leys, Burton on Trent, Staffs DE15 0DW.

## FOR SALE

**COMPLETE SET.** E.E. Issue 1 to present. Offers, BIGGS, 25 Gay Elms Road, Withywood, Bristol.

**BACK NOS.** available of E.E./P.E./P.W. Miscellaneous copies from 1967 to 1975. Also some complete volume issues. Offers, enquiries SAE please, to E. SHAW, 67 Wellstone Garth, Bramley, Leeds 13, Yorks LS15 4EJ.

**FIRST 28** Everyday Electronics plus Demo Deck £25. Buyer collects. Cheddington 668193.

## BOOKS and PUBLICATIONS

**SIMPLIFIED TV REPAIRS.** Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique TV publications. Ausee, 76 Church Street, Larkhall, Lanarkshire.

**BUILD 5 TRIED AND TESTED CIRCUITS.** Digital Precision Timer (2 30min). Sensitive burglar alarm, Voltmeter/Ammeter. A. F. Circuit tracer. Metal Detector. Diagrams 50p each + SAE (£2 for 5). Buildit, 100 Coltstead, New Ash Green, Kent DA3 8LW.

## WANTED

**WANTED.** Info on Govt. Surplus Monitor Unit Type 56. 41 Ronald Road, Liverpool L22 3XU.

## SERVICE SHEETS

**BELL'S TELEVISION SERVICE** for service sheets of Radio, TV etc. 75p plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

**SERVICE SHEETS.** Radio, TV, etc., 50p and SAE. Catalogue 20p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

## MISCELLANEOUS

**STYLIS, CARTRIDGES & AUDIO LEADS ETC.** For the best at keenest prices send SAE for free illustrated list to: **FELSTEAD ELECTRONICS**, (EE), Longley Lane, Gatley, Cheadle, Cheshire SK8 4EE.

**BARGAIN BOX for BEGINNERS** containing 2 Translator/component panels, 1 Relay, 1 Rectifier, telephone insert, 1 mike insert, 2 diodes, 1 buzzer, 3 core cord, 1 salvaged tool—an ideal collection for experiments: £1.50 inc. VAT & P.P. 5 digit counter, 10 digits/sec., 24-48v. non-rotol, brand new GPO type 85p inc. Also 3, 4, 5, 6 & 9 core cords many other telephone spares at give away prices! Trade enquiries welcome. S.A.E. for lists or orders to:

## B. B. SUPPLIES

141, Shalmsford St., Near  
Canterbury, Kent. CT4 7QZ.

# THE OPEN DOOR TO QUALITY

THE COVER IS BLACK & WHITE

UP-DATED EDITION

**ELECTROVALUE**  
Catalogue No. 8

## 4th ISSUE INCLUDES NEW METERS

This 144 page catalogue—Electrovalue Catalogue No. 8 (Issue 4, up-dated) offers items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts continue on many purchases; Access and Barclaycard orders are accepted. **FREE POSTAGE** on all C.W.O. mail orders in U.K. over £2.00 list value (excluding V.A.T.) if under add 15p handling charge.

## BUILD WITH THE EVERYDAY ELECTRONICS

**TEACH-IN KIT** nett £15.75 inc. V.A.T.

from Electrovalue as described in this journal

**ELECTROVALUE LTD**

All communications to Dept. EE4.  
28 ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY  
TW20 0HB. Phone Egham 3603. Telex 284475.  
NORTHERN BRANCH: 880 Burnage Lane, Burnage, Manchester  
M19 1NA. Phone (061) 432 4945.  
Shop hours both addresses 9-3.30 p.m. 1 Sun Sat.

144 Page

**40p**

inc. refund  
voucher worth  
40p

**TRANSFORMER BARGAIN.** 30V, 1½A output, 200 to 250V input. £2.95. Post and Package 90p VAT 8½%. MJE 3055 Transistor 48p P&P 20p VAT 12½%. **EDENCOMBE LTD.,** PO Box 276, 67 Gloucester Street, London SW1V 4DZ.

**100 RESISTORS 75p**

1/2W 5% C/FILM 2-2Ω-2-2M Ω (E12)  
10 each of any value

**C60 CASSETTES 30p** All Cassettes in Plastic Case with Index and Screwed Assembly.  
**C90 CASSETTES 45p** Case with Index and Screwed Assembly.  
All prices include V.A.T. Add Postage 10p in £1.  
Quantity Discounts: **SALOP ELECTRONICS,**  
10 Units 5% **23 WYLE COP,**  
50 Units 7% **SHREWSBURY**  
100 Units 10% **Tel. 53208**

**RECHARGEABLE NICAD BATTERIES**  
‘AA’ (HP7)—£1.26. Sub ‘C’—£1.29. ‘C’ (HP11)—£2.38. ‘D’ (HP2)—£2.92. PP3—£4.98. Matching chargers, respectively, £4.48, £4.48, £5.24, £5.24, £5.98. All prices include VAT add 10% Post & Package. SAE for full list, 1 plus, if wanted, 50p for ‘Nickel Cadmium Power’ Booklet. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands B73 6PP. Tel. 021-354 9764.

**ENAMELLED COPPER WIRE**

swg	1 lb	8oz	4oz	2oz
14-19	2.40	1.20	.60	.30
20-29	2.45	1.20	.62	.30
30-34	2.80	1.70	.80	.40
35-40	2.85	1.90	1.04	.75

Inclusive of p&p and VAT.  
SAE brings Catalogue of copper and resistance wires in all currencies.

**THE SCIENTIFIC WIRE COMPANY**  
PO Box 36, London E4 8BW  
Reg: office 22, Coningsby Gardens.

**TREASURE TRACER**

**MK III Metal Locator**

- Varicap tuning
- Britain's best selling metal locator kit: 4,000 sold
- Weighs only 22oz. Fitted with Faraday shield
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit
- Send stamped addressed envelope for leaflet

Complete Kit £14.75 Built & tested £19.75  
Post £1.00-£1.18 VAT (8½%) Post £1.00-£1.58 VAT (8%)

**MINIKITS ELECTRONICS**  
6b CLEVELAND ROAD,  
LONDON, E16 2AN (Mail order only)

**A UNIQUE OPPORTUNITY**

We can show you how to earn a lot of money working part or full time from home. We are the **ONLY** company in the U.K. offering this unique information. A basic interest in electrical engineering is necessary. Government Departments are making use of our system, why don't you. For complete return of post details send a large stamped addressed envelope to:—

**MAGNUM**

Dept. E.E., Brinkaway Trading Estate,  
Brinkaway, Stockport.

**GLASS FIBRE P.C.B.'S.**

From your own tape, film or ink masters. Send s.a.e. for quotation.  
Everyday Electronics P.C.B.'S in glass fibre, tinned, and drilled. Dec. 76 Mini Organ £2.44. C.W.O. please. Practical Electronics P.C.B.'S.  
Send S.A.E. for list. R. S. Components. All of these well known suppliers components available.

**PROTO DESIGN, 4, Highcliff Way,**  
Wickford, Essex, SS11 8LA.

**4-STATION INTERCOM**



**£18.95**  
+ V.A.T. £1.62

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 90p.

**MAINS INTERCOM NEW MODEL**

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £35.74 per pair P. & P. 90p.

**NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER**



**ONLY £14.95**  
+ V.A.T. £1.20

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for ‘conference’ calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £16.95 and V.A.T. £1.36 P. & P. 76p, 10-day price refund guarantee.

**WEST LONDON DIRECT SUPPLIES (E.E.8)**  
169 KENSINGTON HIGH STREET, LONDON, W8

**DENCO (CLACTON) LIMITED**

Dept. E.E.

357-8-9 OLD RD.,  
CLACTON-ON-SEA  
ESSEX CO15 3RH



Our components are chosen by technical authors and constructors throughout the world for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment.

General Catalogue showing full product range 34p. Overseas Customers 70p, Air-Mail Post Paid.

**U.K. & OVERSEAS MANUFACTURERS/STOCKISTS ENQUIRIES WELCOME**

Australian Readers Please Note—Our Complete Range of Coils are available from Watkin Wynne Pty. Ltd., 32, Falcon Street, CROWS NEST, 2065, AUSTRALIA. P.O. Box 392.

**TV GAMES CHIP**

AY-3-8500 £11.50. Printed circuit and kit of extra parts £7.95. Add-on colour kit P.O.A. Send sae for free data.

**NEW COMPONENTS SERVICE**

Resistors 5% carbon E12 2Ω-10M 1/2W 1p. 1W 2p. Preset pots subminiature .1W E3 100Ω to 4M7. Vertical 9p. Horizontal 9p. Potentiometers 0.25W E3 4K7 to 2M2 log or lin. Single 24p. Dual 75p. Polystyrene capacitors E12 63V 22pf to 8200pf 3ip. Ceramic capacitors vert. 50V E5 22pf to 47000pf 3ip. Mylar capacitors 100V .001, .002, .005 4p. .01, .02, .025 4ip. Polyester capacitors 250V E6 .01 to .1mf 5ip. .15, .22mf 7p. .47mf 11p. Electrolytics 50V .47, 1, 2mf 5ip. 25V 5, 10mf 5ip. 16V 22, 47mf 6ip. 100mf 7p. 220mf 9p. 470mf 11p. 1000mf 18p. Zener diodes 400mW E24 5V3 to 33V 8ip.

**MAINS TRANSFORMERS**

6-0-9V 100mA 94p. 9-0-9V 75mA 94p. 18V 1A £1.95. 0/12/15/20/24/30V 1A £3.65. 12-0-12V 50mA 94p. 0/12/15/20/24/30V 2A £4.95. 8-3V 1½A £2.10. 6-0-6V 1½A £2.55. 9-0-9V 1A £2.19. 12-0-12V 1A £2.49. 15-0-15V 1A £2.69. 30-0-30V 1A £3.39.

**PRINTED CIRCUIT KITS ETC**

Contains etching dish, 100 sq ins of pc board, 1 lb ferric chloride, 1 lb ferric resin, drill bit and laminate cutter £3.45. 100 sq ins pc board 75p. 1 lb FeCl<sub>3</sub> 95p. Etch resist pen 75p.

**S-DECS AND T-DECS\***

S-DeC £1.94. T-DeC £3.61.  
u-DeC £3.97.  
u-DeCB £6.97.  
IC carriers with sockets:—  
16 dit £1.91. 10T05 £1.79.



**SINCLAIR CALCULATORS, WATCHES AND POCKET TV\***

Sinclair pocket TV £165. Cambridge Scientific £8.45. Cambridge Memory £5.95. Oxford Scientific £10.50. Mains adaptors (State model) £3.20.

**BATTERY ELIMINATOR BARGAINS 3-WAY MODELS**

With switched output and 4-way multi-jack connector. Type 1: 3/4/9V at 100mA £2.30. Type 2: 6/7/15V 300mA £2.90.

**100MA RADIO MODELS**

With press-stud connectors. 9V £3.45. 6V £3.45. 9V + 9V £5.45. 6V + 6V £5.45. 4½V + 4½V £5.45.

**CASSETTE MAINS UNIT**

7½V with 5 pin din plug 150mA £3.65.

**FULLY STABILIZED MODEL £5.45**

Switched output of 3/6/7½/9V 400mA stabilized.

**CAR CONVERTERS 12V INPUT**

Output 9V 300mA £1.60. Output 7½V 300mA £1.80

**BATTERY ELIMINATOR KITS**

Send sae for free leaflet on range. 100mA radio types with press stud battery terminals. 4½V £2.10. 6V £2.10. 9V £2.10. 4½V + 4½V £2.50. 6V + 6V £2.50. 9V + 9V £2.50. Cassette type 7½V 100mA with din plug £2.10. Transistor stabilized 8-way type for low hum 3/4/6/7½/9/12/15/18V. 100mA £3.20. 1 Amp £6.50. Heavy duty 13-way types 4½/7/8½/11/13/14/17/21/25/28/34/42V. 1 Amp £4.95. 2 Amp £7.95. Car converter kit input 12V DC. Output 6/7½/9V DC 1A transistor stabilized £1.95. Stabilized Laboratory power kit Switched 1 to 30V in 0.1V steps. 1 Amp £12.45. 2 Amp £14.95

**SINCLAIR PROJECT 80 AUDIO MODULES**

P25 £4.95. Z40 £5.75.  
**BI-PAK AUDIO MODULES**  
S450 tuner £20.95. AL60 £4.60. PA100 £14.95. MK60 audio kit £31.95. Stereo 30 £15.50. SPM80 £3.85. BMT £3.32. Send sae for free data.

**SINCLAIR IC20**

IC20 10W+10W stereo integrated circuit amp kit with printed circuit and data £4.95. P220 Power supply kit for above £3.65. VP20 Volume, tone control and preamp kit £8.95. Send sae for free leaflet on the whole system.

**JC12 AND JC40 AMPLIFIERS**

JC12 6W IC audio amp with free data and printed circuit £1.95. Also new JC40 20W model with pcb £3.95. Send sae for free leaflet on both models and associated power supply and preamp kits.



**FERRANTI ZN414**

IC radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send sae for free data.

**SWANLEY ELECTRONICS**

Dept E.E. PO BOX 68,  
32, GOLDSSEL ROAD,  
SWANLEY, KENT BR88TQ.

Mail order only. No callers. Send sae for free data on kits. Post 30p on orders under £4.50, otherwise free. Prices include V.A.T. Official orders welcome. Overseas customers deduct 7% on items marked \* and 11% on others.

# B. BAMBER ELECTRONICS

Dept. EE, 5-STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE  
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

RED LEDs (Min. type) 5 for 70p.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £8-80 each. Brand New.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

**NEW FOR THE VHF CONSTRUCTOR.** A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.  
Type S (1/4in. square, dummy type).  
Type SA 20 to 30MHz (when 33pf fitted in parallel).  
Type SB 35 to 50MHz (with link winding).  
Type SC 70 to 100MHz (with link winding).  
Type SD 135 to 175MHz (with link winding).  
Type M (Min. 1/4in. square type).  
Type MA 19 to 28MHz (when 33pf fitted in parallel).  
Type MB 22 to 32MHz (when 33pf fitted in parallel).  
Type MC 25 to 35MHz (when 33pf fitted in parallel).  
Type MD 38 to 50MHz (when 33pf fitted in parallel).  
Type ME 45 to 60MHz (when 33pf fitted in parallel).  
Type MF 100 to 200MHz (without slug) from 0 to 30p variable fitted in parallel.  
All the above coils available in packs of five only (same type) at 50p per pack of 5.

**PLASTIC PROJECT BOXES** with screw on lids (in Black ABS) with brass inserts.  
TYPE NB1 approx. 3in. x 2 1/2in. x 1 1/2in. 40p each.  
TYPE NB2 approx. 3 1/2in. x 2 1/2in. x 1 1/2in. 60p each.  
TYPE NB3 approx. 4 1/2in. x 3 1/2in. x 1 1/2in. 80p each.

**MULLARD 88A2 85V STABILISER VALVES** (Brand New) 70p each or 2 for £1-20.

TO3 transistor/insulator sets, 10 for 50p.

2N3055 type Transistors. O.K., but unmarked, 5 for £1.

110V NEONS, SCREW-IN-TYPE, 4 for 50p.

4MHz XTAL PACKS (10 assorted stals between 4MHz and 6MHz), our selection only, £1 Pack.

MINIATURE PLIERS. High quality "Crescent", made in USA. £4-35 + VAT (35p).

SIDE CUTTERS. High quality, £3-70 + VAT 30p.

**MAINS ISOLATION TRANSFORMERS.** Tapped mains input. 240V at 3A + 12V at 500mA output. New, boxed, made by Gardners. £12.

**GARRARD 9V DC MINIATURE MOTORS.** Type 319M, 3243 RPM governed, size approx. 1 1/4in. dia. x 1 1/4in. high, with 2mm spindle. Brand New, 60p each or 2 for £1.

**SILICON HIGH VOLTAGE RECTIFIER STICKS.** BY185 (new) 35kV 2.5mA £1 each, BY140 (ex-equip) 12kV 2.5mA 45p each.

**VARIABLE STABILISED POWER SUPPLY.** mains input, 0-24V output, stabilised and current limiting at 500mA + 32V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 2 1/2 x 4in. complete with external 5A/3-turn pot for voltage control. Connection data supplied. £7.

**14 DIN REEL RELAYS,** 5 to 12V DC, 450 ohm coil. Designed to work directly from TTL Logic. Single Pole Change over. Contact ratings 28V 1/2A 3W. £1-78 each.

**SPECIAL OFFER... STARPHONE HIGH BAND RF PCB BOARDS,** with conversion data for making into a good 2M converter. (All that is needed: 1 xtal, 7 caps, 2 resistors, and 9V DC.) PCB contains 2 Dual gate Mos Fet RF stages (3N140). Diode ring mixer, 3 stage Osc/Multiplier. All on one PCB, approx. size 6" x 1 1/2", set connections. 9V DC supply. AGC (can be left fixed bias, or RF gain control) Ant. input. IF output (works from a few MHz to over 30MHz). All Brand New. £8.50 each, while stocks last.

BSX20 (VHF Osc/Mult), 3 for 60p.  
BC108 (metal can), 4 for 50p.  
PBC108 (plastic BC108), 5 for 50p.  
8Y181 Transistors, 4 for 60p.  
BCY27 Transistors, 4 for 50p.  
PNP audio type TO8 Transistors, 12 for 26p.  
BF182 (UHF amp/mixer), 3 for 50p.  
2N3819 Fet, 3 for 60p.  
BC148 NPN SILICON, 4 for 50p.  
BC188 PNP SILICON, 4 for 50p.  
8AY31 Signal Diodes, 10 for 35p.  
BA121 Varicap Diodes, 4 for 80p.

**SMALL MAINS SUPPRESSORS** (small chokes ideal for radio, Hi-Fi inputs, etc.), approx. 1/4in. x 1/4in., 3 for 50p.

**PERSPEX TUNER PANELS** (for FM Band 2 tuners) marked 88-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/2in. x 1 1/2in., 2 for 35p.

**PLUGS AND SOCKETS**  
N-Type Plugs 50ohm, 60p each, 3 for £1-50.  
PL239 Plugs (PTEE), brand new, packed with reducers, 65p or 5 for £3.  
SO239 Sockets (PTEE), brand new (4-hole fixing type), 50p each or 5 for £2-25.

**SOLDER SUCKERS** (Plunger Type). Standard Model. £4-50. Skirted Model. £6-95. Spare Nozzles 60p each.

**WELLER SOLDERING IRONS**  
EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.  
EXPERT SOLDER GUN. £8-80 + VAT (84p).  
EXPERT SOLDER GUN KIT (spare bit case, etc.), £9-80 + VAT (78p).

SPARE BITS, PAIR, 30p + VAT (2p).  
MARKSMAN SOLDERING IRONS  
SP15D 15W £3 + VAT (24p).  
SP25D 25W £3 + VAT (24p).  
SP25DK 25W + bits, etc. kit £3-85 + VAT (31p).  
SP40D 40W £3-44 + VAT (28p).

BENCH STAND with spring Marksmen Irons, £2-22 + VAT (18p).

SPARE BITS  
MT6 for 15W, 46p + VAT (4p).  
MT4 for 25W, 38p + VAT (3p).  
MT10 for 40W, 42p + VAT (3p).

**TEMPERATURE CONTROLLED IRON.** Temperature controlled iron and PSU. £27 + VAT (£2 18).

**SPARE TIPS**  
Type CC single flat. Type K double flat fine tip.  
Type P, very fine tip. £1 each + VAT (8p).

**MOST SPARES AVAILABLE.**

**MULTICORE SOLDER**  
Size 5 Savit 18 a.w.g. in alloy dispenser, 32p + VAT (8p).  
Size C1SAV18 Savit 18 a.w.g., 56p + VAT (4p).  
Size 12 Savit 18 a.w.g. on plastic reel £1-80 + VAT (18p).  
1/2kg (1-115) 80 x 40, 20 a.w.g. on plastic reel £3.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

**MIXED COMPONENT PACKS.** containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

**ALL-SOL ALUMINIUM SOLDER** (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 a.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p pack. Large reel £2-75.

**VARICAP TUNERS** Mullard Type ELC1043/05. Brand New, £4-40 + 12 1/2% VAT.

**BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS.** Up to 50V working. Geastronic Manufacture. Approx. 100. £2 per pack + 12 1/2% VAT.

Mobile Converters, 24V DC input 13-8V at approx. 3-4A DC output, fully stabilised £3-80 each (ideal for running 12V car radio from 24V lorry battery).

We now stock Spirelux Tools for the electronic enthusiast: Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

**TWIN I.F. CANS,** approx. 1in. x 1/2in. x 1in. High, around 3.5-5MHz, 2 separate transformers in 1 can. Internally screened, 5 for 50p + 12 1/2% VAT.

Dubilier Electrolytics, 50uF, 25V, 2 for 50p.  
Dubilier Electrolytics, 100uF, 45V, 2 for 50p.  
Plessey Electrolytics, 470uF, 30V, 3 for 50p.  
TCC Electrolytics, 1000uF, 30V, 3 for 50p.  
Plessey Electrolytics, 1000uF, 150V, 40p each (3 for £1).

Dubilier Electrolytics, 5000uF, 35V, 50p each.  
ITT Electrolytics, 8800uF, 25V, high grade, screw terminals, with mounting clips, 50p each.

Plessey Electrolytics, 10,000uF at 83V, 75p each.  
Plessey Cathodray Capacitors, 0-0-4uF at 12-5kV DC. Screw terminals. £1-80 each.

**PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.**

**TV PLUGS AND SOCKETS**  
TV Plugs (metal type), 5 for 50p.  
TV Sockets (metal type), 4 for 80p.  
TV Line Connectors (back-to-back sockets), 4 for 50p.

**PLEASE ADD 12 1/2% VAT.**

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE WITH ALL ENQUIRIES Please.  
PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.



HI BUFFALO BOY!  
What's cooking?

I'm cooking up a new electronic masterpiece!  
I'm off to HOME RADIO now to buy the components.

First of course you need our catalogue—all 200 pages of it! It's so packed with good things that it's known as the constructor's 'Bible'. It costs just £1 plus 40p for post and packing. With it comes a free Bargain List showing many items at such knock-down prices that the savings can pay for the catalogue several times over. Send for a catalogue today, using the coupon on the right.

A wise move—  
POST THE COUPON  
with cheque  
or P.O. for  
£1-40

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....

HOME RADIO (Components) LTD., Dept. EE  
234-240 London Road, Mitcham, Surrey CR4 3HD (Regn. No London 912966)

HOME RADIO (Components) LTD. Dept. E.E., 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

# SEMICONDUCTORS—COMPONENTS

## DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA129	£0-08	BY100	£0-16	BY211	£0-31	OA91	£0-07
AA130	£0-09	BY107	£0-12	BY212	£0-31	OA95	£0-07
AAZ13	£0-10	BY105	£0-18	BY213	£0-26	OA182	£0-07
AAZ17	£0-10	BY114	£0-12	BY215	£0-41	OA200	£0-08
BA100	£0-10	BY124	£0-12	BY217	£0-36	OA202	£0-08
BA102	£0-32	BY126	£0-15	BY218	£0-36	SD10	£0-06
BA148	£0-15	BY127	£0-16	BY219	£0-28	SD19	£0-06
BA154	£0-12	BY128	£0-16	OA10	£0-13	IN34	£0-07
BA155	£0-14	BY130	£0-17	OA47	£0-07	IN34A	£0-07
BA156	£0-14	BY133	£0-21	OA70	£0-07	IN914	£0-06
BA173	£0-15	BY164	£0-51	OA79	£0-07	IN916	£0-06
BB104	£0-15	BY176	£0-75	OA81	£0-07	IN1418	£0-06
BAX13	£0-07	BY206	£0-00	OA85	£0-09	IS44	£0-05
BA16	£0-08	BY210	£0-36	OA90	£0-07	IS920	£0-06

## SILICON RECTIFIERS

Type	Price	Type	Price	Type	Price	Type	Price
IS920	£0-06	IN4003	£0-07	IS020	£0-10	IS031	£0-25
IS921	£0-07	IN4004	£0-08	IS021	£0-11	IN5400	£0-13
IS922	£0-08	IN4005	£0-09	IS023	£0-13	IN5401	£0-15
IS923	£0-09	IN4006	£0-10	IS025	£0-14	IN5402	£0-16
IS924	£0-10	IN4007	£0-11	IS027	£0-16	IN5404	£0-17
IN4001	£0-05	IS015	£0-09	IS029	£0-20	IN5406	£0-21
IN4002	£0-06					IN5407	£0-25

## TRIACS

2 AMP T05 CASE			10 AMP T048 CASE		
Volts	No.	Price	Volts	No.	Price
100	TR12A/100	£0-31	100	TR110A/100	£0-77
200	TR12A/200	£0-51	200	TR110A/200	£0-92
400	TR12A/400	£0-71	400	TR110A/400	£1-12

6 AMP T066 CASE			10 AMP T048 CASE		
Volts	No.	Price	Volts	No.	Price
100	TR16A/100	£0-51	100	TR110A/100	£0-77
200	TR16A/200	£0-61	200	TR110A/200	£0-92
400	TR16A/400	£0-77	400	TR110A/400	£1-12

## THYRISTORS

600mA T018 CASE			7 AMP T048 CASE		
Volts	No.	Price	Volts	No.	Price
10	THY600/10	£0-13	50	THY7A/50	£0-48
20	THY600/20	£0-13	100	THY7A/100	£0-51
30	THY600/30	£0-19	200	THY7A/200	£0-57
50	THY600/50	£0-22	400	THY7A/400	£0-62
100	THY600/100	£0-25	600	THY7A/600	£0-78
200	THY600/200	£0-38	800	THY7A/800	£0-92
400	THY600/400	£0-45			

1 AMP T05 CASE			10 AMP T048 CASE		
Volts	No.	Price	Volts	No.	Price
50	THY1A/50	£0-26	100	THY10A/100	£0-57
100	THY1A/100	£0-27	200	THY10A/200	£0-62
200	THY1A/200	£0-28	400	THY10A/400	£0-71
400	THY1A/400	£0-36	600	THY10A/600	£0-99
600	THY1A/600	£0-45	800	THY10A/800	£1-22
800	THY1A/800	£0-58			

3 AMP T066 CASE			16 AMP T048 CASE		
Volts	No.	Price	Volts	No.	Price
50	THY3A/50	£0-25	50	THY16A/50	£0-54
100	THY3A/100	£0-25	100	THY16A/100	£0-58
200	THY3A/200	£0-33	200	THY16A/200	£0-62
400	THY3A/400	£0-42	400	THY16A/400	£0-77
600	THY3A/600	£0-50	600	THY16A/600	£0-90
800	THY3A/800	£0-65	800	THY16A/800	£1-39

5 AMP T066 CASE			30 AMP T094 CASE		
Volts	No.	Price	Volts	No.	Price
50	THY5A/50	£0-36	100	THY30A/100	£1-43
100	THY5A/100	£0-48	200	THY30A/200	£1-63
200	THY5A/200	£0-50	400	THY30A/400	£1-79
400	THY5A/400	£0-57	600	THY30A/600	£3-50
600	THY5A/600	£0-69			
800	THY5A/800	£0-81			

5 AMP T0220 CASE			No.		
Volts	No.	Price			
400	THY5A/400P	£0-57	BT101/500R	£0-80	
600	THY5A/600P	£0-69	BT102/500R	£0-80	
800	THY5A/800P	£0-81	BT106	£1-25	
			BT107	£0-83	
			BT108	£0-98	
			2N3228	£0-70	
			2N3525	£0-77	
			BTX30/50L	£0-33	
			BTX30/400L	£0-46	
			C106/4	£0-60	

## ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER

### VAT

ADD 12½% TO PRICES MARKED\*  
ADD 8% TO OTHERS EXCEPTING  
\*THOSE MARKED †, THESE ARE  
ZERO RATED

## SUPER UNTESTED PAKS

Pak No.	Qty.	Description	Order No.	Price
U50	100	Germ. gold bonded OA47 diode	16130	£0-60
U51	150	Germ. OA70/81 diode	16131	£0-60
U52	100	Silicon diodes 200mA OA200	16132	£0-60
U53	150	Diodes 75mA 1N4148	16133	£0-60
U54	50	Sil rect top hat 750mA	16134	£0-60
U55	20	Sil rect stud type 3 amp	16135	£0-60
U56	50	400W Zener Diode DO7 case	16136	£0-60
U57	30	PNP trans BC107/8 plastic	16137	£0-60
U58	30	PNP trans BC177/178 plastic	16138	£0-60
U59	25	PNP T039 2N697/2N1711 silicon	16139	£0-60
U60	25	PNP T059 2N2905 silicon	16140	£0-60
U61	30	PNP T018 2N706 silicon	16141	£0-60
U62	25	PNP BF950/51	16142	£0-60
U63	30	PNP plastic 2N3906 silicon	16143	£0-60
U64	30	PNP plastic 2N3905 silicon	16144	£0-60
U65	30	Germ. 0071 PNP	16145	£0-60
U66	15	Plastic power 2N3055 NPN	16146	£1-20
U67	10	T03 metal 2N3055 NPN	16147	£1-20
U68	20	Unijunction trans 1N543	16148	£0-60
U69	10	1 amp SCR T039	16149	£1-20
U70	8	3 amp SCR T066 case	16150	£1-20

Code Nos. mentioned above are given as a guide to the type of device in the pak. The device themselves are normally unmarked.

## COMPONENT PAKS

Pak No.	Qty.	Description	Order No.	Price
C1	200	Resistor mixed value approx. (count by weight)	16184	£0-60
C2	150	Capacitors mixed value approx. (count by weight)	16165	£0-60
C3	50	Precision resistors. Mixed values	16166	£0-60
C4	80	½W resistors mixed preferred values	16167	£0-60
C5	5	Places assorted ferrite rods	16168	£0-60
C6	2	Tuning gans. MW/LW VHF	16169	£0-60
C7	1	Pack wire 50 metres assorted colours single strand	16170	£0-60
C8	10	Reed switches	16171	£0-60
C9	3	Micro switches	16172	£0-60
C10	15	Assorted pots	16173	£0-60
C11	5	Metal jack sockets 3 x 3-5mm	16174	£0-60
C12	30	2x standard switch types Paper condensers preferred types mixed values	16175	£0-60
C13	20	Electrolytic trans. types	16176	£0-60
C14	1	Pak assorted hardware—nuts/bolts, gromets, etc.	16177	£0-60
C15	5	Mains slide switches ass.	16178	£0-60
C16	20	Assorted relays and panels	16179	£0-60
C17	15	Assorted control knobs	16180	£0-60
C18	4	Rotary wave change switches	16181	£0-60
C19	2	Relays 6-24V operating	16182	£0-60
C20	1	Pak. copper laminate approx. 200 sq.in.	16183	£0-60
C21	15	Assorted fuses 100mA-5 amp	16184	£0-60
C22	50	Metres PVC sleeving assorted size and colour	16185	£0-60
C23	60	½ watt resistors mixed preferred values	16188	£0-60
C24	25	Presets assorted type and value	16186	£0-60
C25	30	Metres stranded wire assorted colours	16187	£0-60

## SLIDER PAKS

Pak No.	Qty.	Description	Order No.	Price
S1	6	Slider potentiometers, mixed values	16190	£6-60
S2	6	Slider potentiometers, all 470 ohms	16191	£0-60
S3	6	Slider potentiometers, all 10k Ω in	16192	£0-60
S4	6	Slider potentiometers, all 22k Ω in	16193	£0-60
S5	6	Slider potentiometers, all 47k Ω in	16194	£0-60
S6	6	Slider potentiometers, all 47k Ω log	16195	£0-60

## CERAMIC PAK

Containing a range of first quality miniature ceramic capacitors. Unrepeatable value.

Pak No.	Qty.	Description	Order No.	Price
MC1	24	miniature ceramic capacitors, 3 of each value—22pF, 27pF, 33pF, 39pF, 47pF, 68pF, and 82pF	16160	£0-60
MC2	24	miniature ceramic capacitors, 3 of each value—100pF, 120pF, 150pF, 180pF, 200pF, 270pF, 330pF and 390pF	16161	£0-60
MC3	24	miniature ceramic capacitors, 3 of each value—470pF, 560pF, 680pF, 820pF, 1,000pF, 1,500pF, 2,200pF and 3,300pF	16162	£0-60
MCA	21	miniature ceramic capacitors, 3 of each value—4,700pF, 6,300pF, 0.01µF, 0.015µF, 0.022µF, 0.033µF and 0.047µF	16163	£0-60

Just a selection from our huge stocks!

## SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

### ORDER NOW

ONLY 50p plus 15p p & p

## LINEAR PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work.

U721—30 Assorted Linear Types, 709 741, 747, 748, 710, 588, etc.  
ORDER No. 16227 \*£1-50

U76SD FM STEREO DECODER  
5 ICs 76110 equivalent to MC1310P-MA767. Data supplied with pak.  
ORDER No. 16229 \*£1-50

U76A AUDIO POWER OUTPUT AMPLIFIERS  
8 assorted types. SL403, 76013, 76003, etc. Data supplied with pak.  
ORDER No. 16228 \*£1-00

## 74 SERIES PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work.

74G—100 Gates assorted 7400-01-04-10-50-60, etc.  
ORDER No. 16224 \*£1-20

74F—50 Flip-Flops assorted 7470-72-73-74-76-104-109, etc.  
ORDER No. 16225 \*£1-20

74M—30 MSI Assorted Types, 7441-47-90-154, etc.  
ORDER No. 16226 \*£1-20

## VEROBOARDS PAKS

VB1—Approx. 30sq.in various sizes. All 0.1in matrix.  
ORDER No. 16199

VB2—A approx. 30sq.in various sizes. 0.15in matrix.  
ORDER No. 16200 60p

## ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniature electrolytics.

EC1—Values from 0.47µF to 10µF.  
ORDER No. 16201 \*60p

EC2—Values from 10µF to 100µF.  
ORDER No. 16202 \*60p

EC3—Values from 100µF to 680µF.  
ORDER No. 16203 \*60p

## C280 CAPACITOR PAK

75 Mullard C280 capacitors, mixed values ranging from 0.01µF to 2.2µF complete with identification sheet.  
ORDER No. 16204 \*£1-20

## CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors, assorted into the following groups:

R1—60 mixed ½W 100-820 ohms.  
ORDER No. 16213 \*60p

R2—60 mixed ½W 1-8-2k Ω.  
ORDER No. 16214 \*60p

R3—60 mixed ½W 10-82k Ω.  
ORDER No. 16215 \*60p

R4—60 mixed ½W 100-820 Ω.  
ORDER No. 16216 \*60p

R5—40 mixed ½W 100-820 Ω.  
ORDER No. 16217 \*60p

R6—40 mixed ½W 1-8-2k Ω.  
ORDER No. 16218 \*60p

R7—40 mixed ½W 10-82k Ω.  
ORDER No. 16219 \*60p

R8—40 mixed ½W 100-820k Ω.  
ORDER No. 16220 \*60p


R9—60 mixed ½W 1-10M Ω.  
ORDER No. 16220 \*60p

R10—40 mixed ½W 1-10M Ω.  
ORDER No.

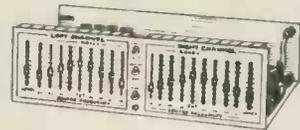
# MAPLIN




The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument! We haven't got the gimmicks (yet—they're coming soon), but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



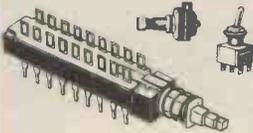
This high quality Graphic Equaliser will enhance even the most sophisticated system at a fraction of the cost of a ready-made equaliser of equal quality. You can get all the parts from us (except woodwork) including drilled and printed metalwork. Construction details in our leaflet: 15p.



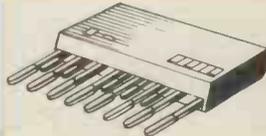We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system, which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches—there are dozens to choose from, but it's only a tiny part of our fantastic range.



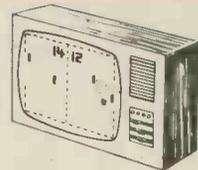A completely self-contained pedal unit. 13-note, 2-octave range, 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!



Play fascinating games NOW on your own t.v. in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets—anyone could win—with Maplin's prices everyone can win. All parts at remarkably low prices (I.C. alone £11.99), send for our latest newsletter for details. All prices include VAT and P & P.

Complete Kit £24.50. Please add 35p to Kit price for copy of constructional details.



## IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

**DON'T MISS OUT! SEND 50p NOW!**

**POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 50p**

Please rush me a copy of your 216 page catalogue by return of post. I enclose 50p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 50p refunded immediately.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

EE6



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices – our latest special offers (they save you pounds) – details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

## MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 47379