

McLeod

Easy to build projects for everyone

FEB 78

40p


Everyday ELECTRONICS

**A.C.
METER
CONVERTER**



CHASER LIGHT DISPLAY

LOW COST

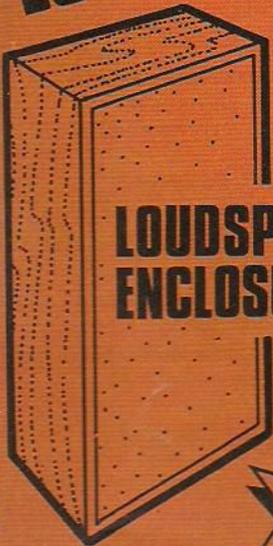


**LOUDSPEAKER
ENCLOSURE**



CAR SYSTEM ALARM

LOOK! Here's how you master electronics.




... the practical way.

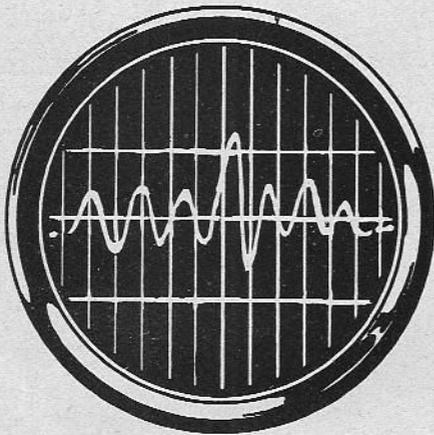

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

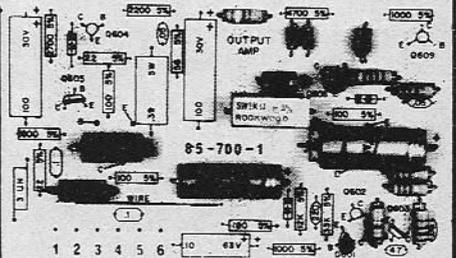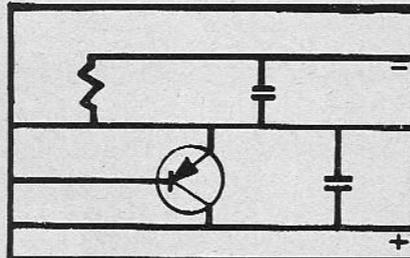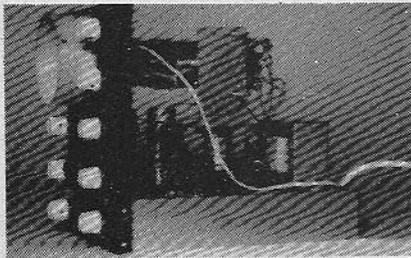All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope.


As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits.

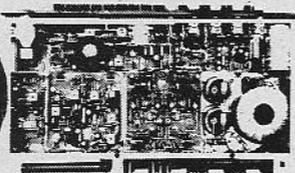We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v etc.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free!

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____
ADDRESS _____

EEB2 Block caps please

Now even better, even more powerful! The unique wrist calculator.

AVAILABLE ONLY AS A KIT.

Assembling the Science of Cambridge wrist calculator.

The wrist calculator comes as finished components, ready for assembly. All you need is two or three hours, and a fine-tip soldering iron.

If anything goes wrong, we'll replace damaged components free. We want you to enjoy building the kit, and to end up with a valuable, useful, powerful calculator.

Contents.

Acrylic/ABS case and display window parts. Two-part stitched strap and spring bar clips. PCB. Special direct-drive chip (no interface chip required). Display. Keyboard components. Batteries.

Each of the 34 components is contained in a plastic box; and neatly shrink-wrapped, accompanied by full instructions for assembling and using the calculator. All components are fully guaranteed.

A wrist calculator – the ultimate in common-sense portable calculating power. Goes where you go, ready for action at a flick of your wrist.

By virtue of its size, a wrist calculator is different to a pocket calculator. And now this wrist-machine has another difference. It has even more power than some much larger pocket calculators!

And what's more, because it's a kit, supplied to you direct from the manufacturer, it costs just £9.95 (plus 8% VAT, P&P). And for that you get a calculator with extra power, and all the satisfaction of building it yourself!

Put real calculating power up your sleeve.

The Science of Cambridge wrist calculator gives you the full range of arithmetic functions (+, -, ×, ÷, =). It uses ordinary algebraic logic, which means you enter calculations as you would write them. It has a % key, the convenience functions, \sqrt{x} , $1/x$, x^2 and a full 5-function memory.

And incredibly, it has a clear-last-entry key, pi, brackets, and $\pi/4$. It even has an automatic linear metric conversion function!

Very few ordinary calculators have the same functions for the same sort of money.


Now 10 keys can do the work of 32.

All those functions, from just 10 keys? In such a small calculator? The secret lies in the special four-level keyboard. Each level has a different set of functions. Simple two-way switching system allows you to select any keyboard level quickly and easily. Each set of functions is carefully grouped, to let you whisk through calculations with the minimum of switching.

And the answers come up bright and clear, too. The display uses 8 full-size red LED digits. It has wide-angle magnification, and is easily visible under any light conditions.

More battery power, too!

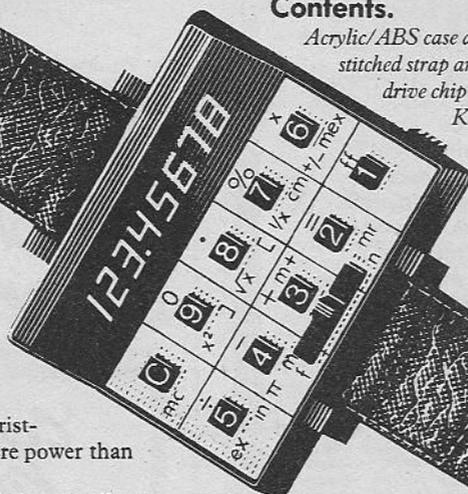With the Science of Cambridge wrist-calculator, you'll get up to 30 hours use between battery changes (that's a lot of calculating!).



KIT ONLY
£9.95
Plus VAT, P&P

The wrist calculator kit is available only direct from Science of Cambridge. If, for any reason, you're not completely satisfied with your wrist calculator, return it to us within 10 days for a full cash refund. Send the coupon today!

Science of Cambridge Ltd.

(Previously Sinclair Instrument Ltd)

6 Kings Parade, Cambridge, Cambs. CB2 1SN.

To: Science of Cambridge Ltd., 6 Kings Parade, Cambridge, Cambs. CB2 1SN.

*Please send me.....(qty) Science of Cambridge wrist calculators kits, at £9.95 plus 80p Vat and 25p P&P (total £11) each.

Overseas orders may be subject to postal surcharge .

*I enclose cheque/PO/money order for £.....


NAME _____

ADDRESS _____

*Complete as appropriate

EE
(please print)

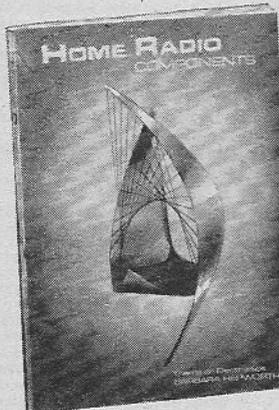Start the New Year well by buying
this famous
Component
Catalogue!



- The finest components catalogue yet published.
- Over 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1.40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.
HOME RADIO (Components) LTD.,
Dept. PW., 234-240 London Road,
Mitcham, Surrey CR4 3HD

POST THIS COUPON
with cheque or P.O. for £1.40

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. EE (Regn. No
234-240 London Road, Mitcham, Surrey CR4 3HD London 912966)

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City and Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence
Schools

Dept 268M Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Tel: Age:

Sparkrite mk2

Capacitive discharge electronic ignition kit

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE
OCT 74



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch.
Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

IMPROVE PERFORMANCE & ECONOMY NOW

Note—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. £3.35 inc. V.A.T. p & p.
E.D.A. 82 BATH STREET, WALSALL, WS1 3DE.

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept., EE 12
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80

Mk. 2 Ready Built Negative Earth @ £14.97

Mk. 2 Ready Built Positive Earth @ £14.97

Ignition Changeover switches @ £4.30

R.P.M. Limit systems in above units @ £2.42

I enclose cheque/PO's
for
£

Cheque No.

Send SAE if brochure
only required.

AUDIO MODULES - ALL REDUCED! TRANSISTOR PRICES SLASHED! MANY PAKS 33% OFF

BI-PAK GREAT SPACE

WE NEED THE SPACE

SPECIAL OFFER!

THYRISTORS

No. THY1A/50	1 Amp.	50 volt	T05	18p
No. THY1A/400	1 Amp.	400 volt	T05	32p
No. THY3A/50	3 Amp.	50 volt	T064	25p
No. THY3A/200	3 Amp.	200 volt	T064	32p
No. THY3A/400	3 Amp.	400 volt	T064	40p
No. THY5A/50	5 Amp.	50 volt	T066	25p
No. THY5A/400	5 Amp.	400 volt	T066	40p
No. THY5A/600	5 Amp.	600 volt	T066	50p
No. C106/4	6 Amp.	400 volt	T0220	42p

TRIAC

S84	8 Amp.	400 volt	T0220 Plastic (Non Isolated Tab)	80p
-----	--------	----------	----------------------------------	-----

DIACS

BR100				15p
D32				15p

SWITCHES

No. 16178	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak 4 x Assorted types multi bank and singles Latching and non-Latching	£1.00*

CAPACITOR PAKS

16201	18 Electrolytics	4.7µF - 10µF	
16202	18 Electrolytics	10µF - 100µF	
16203	18 Electrolytics	100µF - 680µF	
All 3 at SPECIAL PRICE of £1.20*			
16160	24 Ceramic Caps	22pF - 82pF	
16161	24 Ceramic Caps	100pF - 390pF	
16162	24 Ceramic Caps	470pF - 3300	
16163	21 Ceramic Caps	4700pF - 0.047µF	
All 4 at SPECIAL PRICE of £1.60			

RESISTOR PAKS

Order No.				
16213	60½W.	100 ohm - 820 ohm		
16214	60½W.	1K - 8.2K		
16215	60½W.	10K - 82K		
16216	60½W.	100K - 820K		
All 4 at SPECIAL PRICE of £1.60*				
16217	40½W.	100 ohm - 820 ohm		
16218	40½W.	1W - 8.2K		
16219	40½W.	1K - 8.2K		
16220	40½W.	100K - 820K		
All 4 at SPECIAL PRICE of £1.60*				

TRANSISTOR FALL-OUT PACK, GERM, SILICON, POWER, NPN, PNP. ALL MIXED. YOURS TO SORT AND TEST.

Approx. 500 Pieces.
Order No. S23
£1.25 per pack.

VOLTAGE REGULATORS

Positive				
No. MVR7805	µA7805	T0220		85p
No. MVR7812	µA7812	T0220		85p
No. MVR7815	µA7815	T0220		85p
No. MVR7818	µA7818	T0220		85p
No. MVR7824	µA7824	T0220		85p
Negative				
No. MVR7905	µA7905	T0220		£1.10
No. MVR7912	µA7912	T0220		£1.10
No. MVR7915	µA7915	T0220		£1.10
No. MVR7918	µA7918	T0220		£1.10
No. MVR7924	µA7924	T0220		£1.10

µA723C T099	38p	72723 14 pin Dii	38p
LM309K T03	£1.20		

MICROPHONES

DYNAMIC DUAL IMPEDANCE UNI DIRECTIONAL CARDIOID MICROPHONE Impedance 600 ohms and 50K. Response 50-14,000 Hz. Sensitivity 54db at 50K. Size 1½" Dia. x 6½" Long
Order No. 1328 £7.50*

DYNAMIC CASSETTE MIC

Fitted with On/Off switch. 1 metre of tough lead with floating 2.5 and 3.5 mm plugs. Impedance 200 ohms. Sensitivity 90db. Frequency 90-10,000 Hz. Size 20mm Dia. x 120mm Long
Order No. 1326 £1.15*

LOGIC PROBE

A pocket size instrument capable of detecting T.T.L. D.T.L. Flip Flop and other pulse circuits. It is easy to use and operates from the 5V. D.C. supply of the circuit under test. The logic levels are indicated by 2 red LED's one for High and the other for Low. There is also a green LED for the Pulse Mode of the unit.
No. S59 Our Special Price £15.95.

TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	*9p	TIP32A	34p	2N1613	15p
AC126	14p	BC178	12p	BF195	*9p	TIP32B	35p	2N1711	15p
AC127	16p	BC179	12p	BF196	*12p	TIP32C	36p	2N1893	28p
AC128	16p	BC182	*9p	BF197	*12p	TIP41A	34p	2N2218	15p
AC128K	24p	BC182L	*9p	BF200	25p	TIP41B	35p	2N2218A	18p
AC176	16p	BC183	*9p	BFX29	25p	TIP41C	36p	2N2219	15p
AC176K	24p	BC183L	*9p	BFX50	18p	TIP42A	36p	2N2219A	18p
AC187	16p	BC184	*9p	BFY84	12p	TIP42B	37p	2N2221	15p
AC187K	26p	BC184L	*9p	BFY51	12p	TIP42C	38p	2N2221A	16p
AC188	16p	BC212	*10p	BFY52	12p	TIP2955	65p	2N2222	15p
AC188K	26p	BC212L	*10p			TIP3055	42p	2N2222A	16p
AD161/1		BC213	*10p	MPSA05	*22p	ZTX107	*6p	2N2369	10p
162 MP	80p	BC231	*10p	MPSA06	*22p	ZTX108	*6p	2N2904	14p
AF139	30p	BC214	*10p	MPSA55	*22p	ZTX109	*7p	2N2904A	15p
AF239	30p	BC214L	*10p	MPSA56	*22p	ZTX300	*7p	2N2905	14p
BC107	6p	BC251	*10p	OC44	12p	ZTX301	*7p	2N2905A	15p
BC108	6p	BCY70	12p	OC45	12p	ZTX302	*9p	2N2906	12p
BC109	6p	BCY71	12p	OC71	9p	ZTX500	*9p	2N2906A	14p
BC118	*10p	BCY72	12p	OC72	12p	ZTX501	*10p	2N2907	12p
BC147	*8p	BD115	40p	OC75	10p	ZTX502	*12p	2N2907A	13p
BC148	*8p	BD131	*35p	OCB1	14p	2N696	10p	2N2926G	*8p
BC149	*8p	BD132	*37p			2N697	10p	2N2928Y	*7p
BC154	*16p	BF115	17p	TIP29A	35p	2N706	7p	2N3053	12p
BC157	*9p	BF167	19p	TIP29B	36p	2N706A	8p	2N3055	35p
BC158	*9p	BF173	20p	TIP29C	38p	2N708	8p	2N3702	*7p
BC159	*9p	BF180	25p	TIP30A	36p	2N1302	12p	2N3703	*7p
BC169C	*10p	BF181	25p	TIP30B	37p	2N1303	15p	2N3704	*6p
BC170	6p	BF182	25p	TIP30C	38p	2N1304	15p	2N3903	*11p
BC171	*6p	BF183	25p	TIP31A	32p	2N1307	18p	2N3904	*11p
BC172	*6p	BF184	25p	TIP31B	33p	2N1308	22p	2N3905	*11p
BC173	7p	BF185	25p	TIP31C	34p	2N1309	22p	2N3906	*11p

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	BAX16/		BY216	30p	OA85	7p
AA213	4p	OA202	5p	BY217	28p	OA90	6p
BA100	6p			BY218	28p	OA95	7p
BA115	5p	BY100	15p	BY219	28p	OA95	7p
BA144	5p	BY127	*10p			IN5400	10p
BA148	10p	BY210	32p	OA47	5p	IN5401	11p
BA173	10p	BY211	32p	OA70	5p	IN5402	12p
BAX13/		BY212	32p	OA79	7p	IN5403	13p
OA200	5p	BY213	30p	OA81	7p	IN5404	13p
						IN5406	16p
						IN5407	17p
						IN5408	19p

LINEAR I.C.'s

TBA800	12 pin QIL	*75p	UA711C T099	25p	UA748 T099	28p
TBA810	12 pin QIL	*£1.00	UA703 T099 (Plastic)	20p	72558 (Dual 748) T099	45p
TBA820	14 pin QIL	*80p	741P 8 pin DIL	18p	MC1310P 14 pin DIL	*£1.25
LM380	14 pin DIL	*80p	72741 14 pin DIL	20p	76115 14 pin QIL	*£1.25
LM381	14 pin DIL	*£1.35	UA741C T099	20p	NE555 8 pin DIL	32p
72709	14 pin DIL	28p	72747 14 pin DIL	55p	NE556 14 pin DIL	60p
UA709	T099	28p	748P 8 pin DIL	28p	SL414A 10 pin	*£1.80

NEW CONSIGNMENT ZN 414 RADIO CHIP 75p*

OPTOELECTRONICS

Displays		2nd QUALITY LED PAKS	
No. 1510	707 LED Display	No. 1507	10 x LED's Assorted
No. 1511	747 LED Display		
No. S53	DL33 Triple 7 Segment LED Display Character height .11" Common Cathode 12 pin DIL		
LED's		LED CLIPS	
No. S51	Red TIL209 (5 x .125")	No. 1508/125	125
No. S52	Red FLV117 (5 x .2")	No. 1508/2	2
No. 1502	Green .125"		
No. 1505	Green .2"		
No. 1503	Yellow .125"		
No. 1506	Yellow .2"		
No. S82	Clear .2" (illuminating red)		
D.I.Y. PRINTED CIRCUIT KIT		SPECIAL REDUCTIONS	
Contains 6 pieces of copper laminate board, box of etchant powder, measure, tweezers, marker pen, high quality pump drill, Stanley knife and blades and 6 in. metal rule. Full easy to follow instructions. Order No. S64 Sale Price £5.50		No. 1514	NORP 12
P.C.B. BOARDS		No. S76	OCP71
S61	8 pieces 8" x 3½" (approx.) single sided paper	No. S83	5, NIXIE Tubes ITT 5870 ST £2.00 (including Data)
S62	4 pieces 8" x 3½" (approx.) single sided fibreglass	No. S77	Neon Indicator Lamps 230V A.C. State Colour (Red, Amber and Green.)
S63	3 pieces 7" x 3½" (approx.) double sided fibreglass		
ETCH RESIST PENS			
Order No. 1609 50p each			
SOLDER			
5m of 18 sw Multi-core Solder. Order No. S60 50p			
I.C. INSERTION EXTRACTION TOOL			
Order No. 2015 30p			

UNTESTED SEMICONDUCTOR PAKS

Code No's shown below are given as a guide to the type of device. The devices themselves are normally unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40p
No. 16131	150 Germ. Point contact diodes like OA70/81	40p
No. 16132	100 200mA Sil. diodes like OA200	40p
No. 16133	150 75mA Sil. Fast switching diode like IN4148	40p
No. 16134	50 750mA Sil. top hat Rects.	40p
No. 16135	20 3 amp Sil. stud Rect.	40p
No. 16136	50 400mw Zeners D.O.7 case	40p
No. 16137	30 NPN Plastic trans. like BC107/8	40p*
No. 16138	30 PNP Plastic trans. like BC177/8	40p*
No. 16139	25 NPN trans. like 2N697/ 2N1711 T039	40p
No. 16140	25 PNP trans. like 2N2905 T039	40p
No. 16141	30 NPN trans. like 2N706 T018	40p
No. 16143	30 NPN Plastic trans. like 2N3906	40p*
No. 16144	30 NPN Plastic trans. like 2N3905	40p*
No. 16145	30 PNP Germ. trans. like OC71	40p
No. 16147	10 NPN to 3 Power trans. like 2N3055	80p

I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.00
No. S67	10 x 14 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 24 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

TRANSISTOR SOCKETS

No. S71	15 x T018 Sockets	£1.00
No. S72	10 x T05 Sockets	£1.00

MOUNTING PADS

No. S73	50 Mixed Transistor Pads T018 and T05	40p
---------	---------------------------------------	-----

TRANSISTOR HEATSINK PAK

20 Assorted types, T01, T05, T018, T092
Our Mix
Order No. S75 60p

TRANSISTOR INSULATING KITS

Mica washers and bushes assorted types i.e. T0220, T066, T03 etc. Approx. 100 pieces. (Approx. 40 sets).
Order No. S74 50p

DARLINGTON POWER TRANSISTORS

70 watt 8 amp NPN and PNP in plastic case 199 High Voltage (Typ. 80V). High gain. 10 pieces 5 NPN and 5 PNP. Data Sheet supplied.
Order No. S78 £1.00 per Pak

MATCHED PAIRS OF PNP GERMANIUM MFD. POWER TRANS

2 amp		750mW	
NKT301	VCE	VCE	HFE
NKT302	40	60	30-100
NKT303	20	60	50-150
NKT304	20	30	30-100
NKT304	20	30	50-150

ZENER PAKS

No. S55	20 mixed values 400mW Zener diodes 3-10V	£1.00
No. S56	20 mixed values 400mW Zener diodes 11-33V	£1.00
No. S57	10 mixed values 1W Zener diodes 3-10V	£1.00
No. S58	10 mixed values 1W Zener diodes 11-33V	£1.00

UNIUNION TRANSISTORS

UT46	TIS43	20p	
FET's			
2N3819	15p	2N5458	18p

2 AMP. BRIDGE RECTIFIERS

No. S45	50V (KBS 005)	28p
No. S46	100V (KBS 01)	30p
No. S47	200V (KBS 02)	34p

10 AMP. BRIDGE RECTIFIERS 200V ON HEATSINK - SPECIAL CLEARANCE ORDER NO

SAVING SALE BI-PAK

YOU MAKE THE SAVING!

OPT FOR OPTOELECTRONICS! PRINTED CIRCUIT KITS, BOARDS & PENS.

SILICON RECTIFIERS - 1/2 AMP. G.E.

No. S48	40 x 50V	60p
No. S49	30 x 200V	60p
No. S50	20 x 700V	60p

G.E. HIGH VOLTAGE SILICON RECTIFIERS

GR559 10mA 14KV (14,000)	20p each
GA432 1 AMP. 2 KV (2,000)	20p each
FD2.5 2.5 KV Voltage Doubler	20p each

POTENTIOMETERS

Slider 40mm TRAVEL		
Order No.		
16181	6 x 470 Ohm LIN Single	40p*
S24	6 x 1 K LIN Single	40p*
S25	6 x 5 K LIN Single	40p*
16192	6 x 10 K LIN Single	40p*
S26	6 x 10 K LOG Single	40p*
16193	6 x 22 K LIN Single	40p*
16195	6 x 47 K LOG Single	40p*
16194	6 x 47 K LIN Single	40p*
S27	6 x 100 K LIN Single	40p*
S28	6 x 100 K LOG Single	40p*
S29	6 x 500 K LOG Single	40p*

Slider 60mm TRAVEL		
Order No.		
S30	6 x 2.5 K LOG Single	40p*
S31	6 x 10 K LIN Single	40p*
S32	6 x 50 K LIN Single	40p*
S33	6 x 250 K LOG Single	40p*
S34	4 x 5 K LOG Dual	40p*
S35	4 x 10 K LIN Dual	40p*
S36	4 x 100 K LOG Dual	40p*
S37	4 x 1.3 MEG LOG Dual	40p*

S38 MIXED SLIDER POTS - VARIOUS VALUES AND SIZES - OUR MIX ONLY £1.00*

S39 6 x CHROME SLIDER KNOBS 40p*

WIREWOUND

A range of wirewound single gang pots. with linear tracks of 1 watt rating.

Order No.	Value	Order No.	Value
1891	10 ohms	1894	100 ohms
1893	47 ohms	1895	220 ohms
1896	470 ohms	1898	2K
1897	1K	1899	4K7

NOW 35p* each

16173	15 Rotary Potentiometers. Assorted values and types.	40p*
16186	25 Pre-set Assorted Values and types	40p*

SALE PRICE 40p

MULTI-TURN PRE-SETS

S40 3 x 100 K LIN ONLY 50p*

AUDIO PLUG AND SOCKET PAKS

Order No.		
S1	5 x 3.5 mm Plastic Jack Plugs	40p*
S2	5 x 2.5 mm Plastic Jack Plugs	40p*
S3	4 Std. Plastic Jack Plugs	50p*
S4	2 x Stereo Jack Plugs	30p*
S5	5 x 5 Pin 180° DIN Plugs	50p*
S6	8 x 2 Pin Loudspeaker Plugs	50p*
S7	6 x Phono Plugs Plastic	50p*
S8	5 x 3.5 mm Chassis Sockets (Switched)	25p*
S9	5 x 2.5 mm Chassis Sockets (Switched)	25p*
S10	4 x Metal Std. Chassis Switched Jack Sockets	50p*
S11	2 x Stereo Jack Sockets with instruction leaflet for H/Phone connection.	50p*
S12	5 x 5 Pin 180° DIN Chassis Sockets	40p*
S13	8 x 2 Pin DIN Chassis Sockets	50p*
S14	6 x Single Phono Sockets	40p*

AUDIO LEADS

Order No.		
117	A.C. Mains connecting lead for cassette recorders and radios Telefunken type	45p*
118	5 pin DIN headphone plug to stereo socket	78p*
119	2 x 2 pin plug to inline stereo socket for headphones	60p*
123	20 ft. of coiled guitar lead	£1.15*
124	3 pin to 3 pin DIN plug	50p*
125	Audio lead 5 pin plug to 5 pin DIN plug	50p*
126	Audio lead 5 pin DIN plug to tinned open ends	50p*
127	Audio lead 5 pin DIN plug to 4 phono plugs	90p*
129	Audio lead 5 pin plug to 5 pin DIN plug - Mirror Image	70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline socket	45p*
132	10 metre lead 2 pin DIN plug	65p*

HEAVY GAUGE BLACK PLASTIC BOX

With aluminium lid and fixing screws. Size 6 1/2" x 3 1/4" x 2" Order No. S16 Only 75p

74 SERIES TTL ICs

TYPE		QUANTITY		TYPE		QUANTITY		TYPE		QUANTITY	
1	100	1	100	1	100	1	100	1	100	1	100
Ep	Ep	Ep	Ep	Ep	Ep	Ep	Ep	Ep	Ep	Ep	Ep
7400	0.09	0.08	7448	0.70	0.68	74122	0.45	0.42			
7401	0.11	0.10	7450	0.12	0.10	74123	0.65	0.62			
7402	0.11	0.10	7451	0.12	0.10	74141	0.68	0.65			
7403	0.11	0.10	7453	0.12	0.10	74145	0.75	0.72			
7404	0.11	0.10	7454	0.12	0.10	74150	1.10	1.05			
7405	0.11	0.10	7460	0.12	0.10	74151	0.65	0.60			
7406	0.28	0.25	7470	0.24	0.23	74153	0.70	0.68			
7407	0.28	0.25	7472	0.20	0.19	74154	1.20	1.10			
7408	0.12	0.11	7473	0.26	0.22	74155	0.70	0.68			
7409	0.12	0.11	7474	0.24	0.23	74156	0.70	0.68			
7410	0.09	0.08	7475	0.44	0.40	74157	0.70	0.68			
7411	0.22	0.20	7476	0.26	0.25	74160	0.95	0.85			
7412	0.22	0.20	7480	0.45	0.42	74161	0.95	0.85			
7413	0.26	0.25	7481	0.90	0.88	74162	0.95	0.85			
7416	0.28	0.25	7482	0.75	0.73	74163	0.95	0.85			
7417	0.26	0.25	7483	0.88	0.82	74164	1.20	1.10			
7420	0.11	0.10	7484	0.85	0.80	74165	1.20	1.10			
7422	0.19	0.18	7485	1.10	1.00	74166	1.20	1.10			
7423	0.21	0.20	7486	0.28	0.26	74174	1.10	1.00			
7425	0.25	0.23	7489	2.70	2.50	74175	0.85	0.82			
7426	0.25	0.23	7490	0.38	0.32	74176	1.10	1.00			
7427	0.25	0.23	7491	0.65	0.62	74177	1.10	1.00			
7428	0.36	0.34	7492	0.43	0.35	74180	1.10	1.00			
7430	0.12	0.10	7493	0.38	0.35	74181	1.90	1.80			
7432	0.20	0.19	7494	0.70	0.68	74182	0.80	0.78			
7433	0.38	0.36	7495	0.60	0.58	74184	1.50	1.44			
7437	0.26	0.25	7496	0.70	0.68	74190	1.40	1.30			
7438	0.26	0.25	74100	0.95	0.90	74191	1.40	1.30			
7440	0.12	0.10	74104	0.40	0.35	74192	1.10	1.00			
7441	0.60	0.57	74105	0.30	0.25	74193	1.05	1.00			
7442	0.80	0.70	74107	0.30	0.25	74194	1.05	1.00			
7443	0.95	0.90	74110	0.48	0.45	74195	0.80	0.75			
7444	0.95	0.90	74111	0.75	0.72	74196	0.90	0.85			
7445	0.80	0.75	74118	0.85	0.82	74197	0.90	0.85			
7446	0.80	0.75	74119	1.30	1.20	74198	1.90	1.80			
7447	0.70	0.68	74121	0.28	0.26	74199	1.80	1.70			

Devices may be mixed to qualify for quantity price. Data is available for the above series of ICs in booklet form price 35p.

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.14	CD4018	£0.85	CD4035	£1.40	CD4056	£1.15
CD4001	£0.16	CD4019	£0.45	CD4037	£0.78	CD4069	£0.32
CD4002	£0.16	CD4020	£0.95	CD4040	£0.78	CD4070	£0.32
CD4006	£0.80	CD4021	£0.85	CD4041	£0.68	CD4071	£0.20
CD4007	£0.17	CD4022	£0.80	CD4042	£0.68	CD4072	£0.20
CD4008	£0.80	CD4023	£0.18	CD4043	£0.78	CD4081	£0.20
CD4009	£0.50	CD4024	£0.64	CD4044	£0.78	CD4082	£0.20
CD4010	£0.50	CD4025	£0.18	CD4045	£1.15	CD4510	£1.10
CD4011	£0.18	CD4026	£1.85	CD4046	£0.95	CD4511	£1.25
CD4012	£0.17	CD4027	£0.48	CD4047	£0.75	CD4516	£1.10
CD4013	£0.42	CD4028	£0.80	CD4049	£0.46	CD4518	£1.10
CD4015	£0.80	CD4029	£0.95	CD4050	£0.46	CD4520	£1.10
CD4016	£0.42	CD4030	£0.46	CD4054	£0.95		
CD4017	£0.80	CD4031	£1.80	CD4055	£1.60		

AUDIO MODULE SALE

Type	Description	Normal Price	Sale Price
AL30A	10W RMS Power Amp	£3.65*	£2.95*
AL60	25W RMS Power Amp	£4.35*	£3.55*
AL80	35W RMS Power Amp	£6.85*	£5.95
AL250	125 W RMS Power Amp	£16.95*	£14.45
SPM80	35V Power Supply	£3.75*	£3.10*
PS12	20-30V Power Supply for AL30A	£1.30*	£1.15*
PA12	Stereo Pre-Amp for AL30A	£6.70*	£5.95*
PA100	Stereo Pre-Amp for AL60/AL80	£13.75*	£12.45*
S450	Stereo F.M. Tuner	£20.45*	£18.65*
MPA30	Magnetic-Ceramic Pre-Amp	£2.85*	£2.55*
Stereo 30	Complete Audio Chassis 7W + 7W RMS	£16.25*	£14.95*

LOOK & LISTEN

GE 100 NINE CHANNEL MONO-GRAPHIC EQUALIZER MODULE

The GE100 has nine 1 octave adjustments using integrated circuit active filters. Boost and Cut limits are ± 12db, Max. Voltage handling 2 V RMS, T.H.D., 0.5%, input impedance 100 K, output impedance less than 10 K. Frequency response 20 Hz-20 KHz (3db). The nine gain controls are centred at 50, 100, 200, 400, 800, 1600, 3,200, 6,400 and 12,800 Hz. The suggested gain controls are 10 K LIN sliders. (Not supplied with the module). See Paks S31 and 16192.

ONLY £19.50

SG30 Power supply board for GE100 15-0-15 Volt £4.50
SEND SAE FOR TECHNICAL DATA ON ANY OF THE AUDIO MODULES.


SPECIAL OFFER! COMPONENT PAKS

Order No.	Quantity	
16164	200 approx. Resistors mixed values. (Count by weight)	40p*
16165	150 approx. Capacitors mixed values. (Count by weight)	40p*
16167	80 1/2W Resistors mixed values	40p*
16168	5 pieces Assorted Ferrite rods	40p*
16169	2 pieces Tuning gangs MW/LW	40p*
16170	50 metres Single strand wire assorted wire	40p
16171	10 Reed switches	40p*
16172	3 Micro switches	40p*
16176	20 Assorted electrolytics Trans types	40p*
16177	1 pack Assorted hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p*
16184	15 Assorted Fuses 100mA - 5 amp	40p
16188	60 1/2W resistors mixed values	40p*
16187	30 metres stranded wire assorted colours	40p

1/2 PRICE BARGAIN!

£4 worth (Min. Value) of Electronic Project Books, Technical, Semiconductor Data and Equivs - Books of Assorted Titles. OUR CLEARANCE PRICE Order No. S80 £2 per bundle

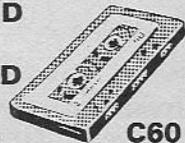SUPER SOUND SAVING METRO SOUND LOW NOISE CASSETTES



Order No. S53 10 for £2.50*
BIB GROOVE CLEAN Model 60. Chrome Finish Plastic Order No. 829 £1.40*

HOT OFFER

ANTEX SOLDERING IRONS Order No. 1931 X25 25 watt. LOW LEAKAGE Usually £3.40 SALE PRICE £2.95 PLUS FREE Heatshunt 1948 Model C 15 watt General purpose Usually £3.40 SALE PRICE £2.95 PLUS FREE Heatshunt 1939 ST3 Soldering Iron Stand suitable for either Iron. £1.20

NEW Siren Alarm Module

American Police siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down, and other security purposes. Order No. S15 £3.50

AVDEL BOND

Cyanocrylate adhesive bonds - plastic, rubber, transistors, components in seconds. Order No. 143 55p per 2 gm. phial

ORDERING

Please word your orders exactly as printed, not forgetting to include our part number.

VAT

Add 12 1/2% to prices marked* Add 8% to others excepting those marked †. These are zero.

BI-PAK

Dept. E.E.2. P.O. Box 6, Ware, Herts COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.

FOR RELIABLE JOINTS - ANTEX IRONS!

Everyday Electronics, February 1978

EDITOR

F. E. BENNETT

ASSISTANT EDITOR

B. W. TERRELL B.Sc.

PRODUCTION EDITOR

D. BARRINGTON

TECHNICAL SUB-EDITOR

T. J. JOHNSON G8MGS

ART EDITOR

R. PALMER

TECHNICAL ILLUSTRATORSP. A. LOATES
D. J. GOODING**EDITORIAL OFFICES**Kings Reach Tower,
Stamford Street,
London SE1 9LS
Phone: 01-261 6873**ADVERTISEMENT MANAGER**D. W. B. TILLEARD
Phone: 01-261 6676**REPRESENTATIVE**P. J. MEW
Phone: 01-261 6676**CLASSIFIED MANAGER**C. R. BROWN
Phone: 01-261 5762**MAKE-UP AND COPY
DEPARTMENT**

Phone 01-261 6035

ADVERTISEMENT OFFICESKings Reach Tower,
Stamford Street,
London SE1 9LS

Projects... Theory...

and Popular Features ...

With the festive season just behind us we now have to face, weatherwise, the most gloomy and and most treacherous part of the annual round. The unkind weather which is synonymous with the months of January and February is of particular concern for motorists. This time of year that generally forgotten part of the car—the battery—suddenly zooms large in the minds.

Even if we have not personally experienced trouble these cold and damp mornings, doubtless warning sounds have been heard in the neighbourhood as less fortunate fellows struggle to induce life into their dormant vehicles. At times such as these we realise just how everything depends upon that source of electrical energy.

One way to ensure that the battery is maintained in good condition ready to cope with the severe demands of winter is to avoid unnecessary consumption, at all times. Leaving side lights and accessories switched on unintentionally is a common human failing.

An easy remedy is to install an electronic "reminder" that will give instant warning if electrical circuits are left on when the ignition is turned off. So this month's article describing a *Car System Alarm* has topical interest for all who drive.

Talking of the wintry scene, there is in this issue of EVERYDAY ELECTRONICS a cheerful palliative that the younger generation will appreciate. Our *Chaser Light Display* will give the colour, sparkle and zip that nowadays is considered an essential accompaniment to any performance of pop music. For use at "home" or "away", this unit is bound to be a winner.

And now, looking ahead—which is what most of us do this time of the year... There is not just the spring to think of, to boost our morale. There is next month's EVERYDAY ELECTRONICS with a special gift for each reader. Read more about it on page 287.

It goes without saying that the wise reader will make certain of his or her copy by ordering well in advance. Of course, you are wise, but we must give this general reminder to alert those who may take a more casual view of things. We shall be sorry, but will not accept any blame if anyone misses out next month!



Our March issue will be published on Friday, February 17. See page 287 for details.


Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

Telephone enquiries should be limited to those requiring only a brief reply. We cannot undertake to engage in discussions on the telephone, technical or otherwise.

Component Supplies

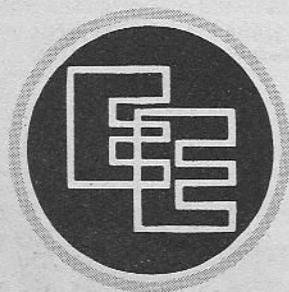Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.



Everyday ELECTRONICS

VOL. 7 NO. 6

FEBRUARY 1978

CONSTRUCTIONAL PROJECTS

- CAR SYSTEM ALARM** Look after your car battery with this lights-on reminder by P. W. Bond 256
MONO/STEREO LEAD TESTER A visual checkout for those faulty leads by M. Simpson 263
CHASER LIGHT DISPLAY A light show for pop groups and discos by J. McBride 276
A.C. METER CONVERTER An add-on range extender for simple audio testing by R. A. Penfold 282
LOW COST LOUDSPEAKER ENCLOSURE Good quality reproduction for a small outlay by J. Smith 288

GENERAL FEATURES

- EDITORIAL** 254
SHOP TALK New products and component buying for constructional projects by Brian Terrell 262
FOR YOUR ENTERTAINMENT Shocking affair, magnetic driver and explosive tune by Adrian Hope 267
TEACH-IN 78 Part 5. Impedance, resonance, inductance and amplifiers by George Hylton 268
READERS' LETTERS Your news and views 275
BOOK REVIEWS A selection of recent releases 275, 281
BRIGHT IDEAS Readers' hints and tips 290
SQUARE ONE Understanding constructional articles 291
ELECTRONIC DOORBELL An EE report on a new product 292
PROFESSOR ERNEST EVERSURE The Extraordinary Experiments of. by Anthony J. Bassett 294
COUNTER INTELLIGENCE Waiting to be invented and the kitchen table by Paul Young 296
JACK PLUG AND FAMILY Cartoon by Doug Baker 296
DOWN TO EARTH Negative resistance by George Hylton 299

Back Number Service and Binders

Back issues of EVERYDAY ELECTRONICS (June 1977 onwards) are available worldwide at a cost of 60p per copy inclusive of postage and packing. Orders and remittance should be sent to: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

Binders for Volumes 1 to 6 (state which) are available from the above address for £2.10 inclusive of postage and packing.

© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

**RESOLUTION
FOR
1978**
*PLACE A REGULAR
ORDER WITH
NEWSAGENT FOR
E.E.*



CAR SYSTEM ALARM


By P.W. Bond

INTRODUCTION

THIS article describes the construction of a simple alarm for use in the car which alerts the driver if any circuits are left switched on when the car has been parked. Hence it acts as a reminder for the driver to prevent his battery from discharging unnecessarily.

The unit described gives an audible and visual alarm when the ignition is switched off and the side or headlights or any chosen accessory is switched on.

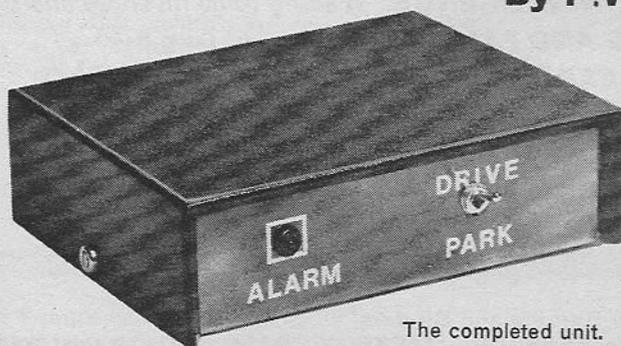The audible alarm can be silenced when the driver wishes to park the car with the lights on. This could be when the car is parked on a busy but poorly lit street at night.



The completed unit.

The circuit will accept the voltage variations produced by the regulators in the car. The actual installation in the vehicle is relatively simple and does not disturb the wiring too much. A word of advice though. If readers have not worked on car electrical systems before, get the help of someone who has. To thoughtlessly tamper

with the car electrical system could render the vehicle disabled, but what is more important it could make the car dangerous to drive.

This circuit is intended for negative earthed vehicles, which covers the majority of those on the road. A positive earth version can be made and a brief outline of how this is done is given later.

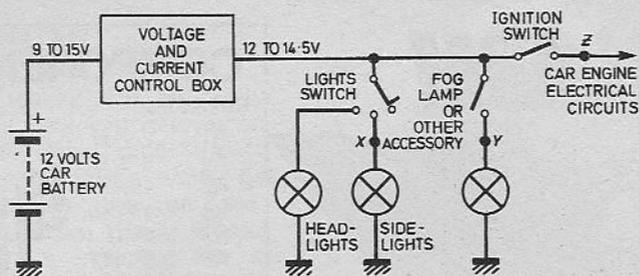


Fig. 1. A typical car electrical system.

CIRCUIT ACTION

The average car electrical system is often seen as mysterious bundles of coloured wires and connector clips, but the basic circuits are very simple.

A much simplified circuit taken from a typical car electrical system is shown in Fig. 1. The car battery has a nominal 12 volts between its terminals, but this varies when it is being charged and discharged.

To adjust the voltage and current to the various loads a control box is connected to the positive terminal of the battery. Hence when any of the circuits are energised, current flows from the battery, through the control box and switch to the load.

To economise on wiring, the chassis of the vehicle is connected to the negative battery terminal, hence the term "negative earth". The common return to the battery is thus made through the car metalwork.

SWITCHES

When the side or headlight switch is closed, point X goes to the battery potential of 12 volts and the lights illuminate. This switch is rather unusual since it has a special wiper which connects both the side and headlights to the battery simultaneously when in the headlight position.

The wiper bridges side and headlight connections so that they come on together. Consequently, when any lights are on the point X will be at 12 volts. Similarly, when the accessory is switched on, shown here as a fog lamp operated by a switch on the dashboard, the point Y will rise to 12 volts. And when the ignition is turned on the point Z will rise to 12 volts.

In the system chosen for the project, the load "on" condition represents the logic "high", and

when the load is switched "off" this is the logic "low", since the monitor points X, Y, or Z fall to earth potential. The logic levels at the monitor points can be analysed by the alarm unit and under adverse conditions, with lights or accessory on and the ignition switched off, the audible and visual alarm is produced.

**START
HERE FOR
CONSTRUCTION**

CIRCUIT BOARD


Owing to the relative simplicity of the circuit the unit was built on

a small piece of stripboard. The use of an i.c. in the design calls for some strips to be broken. The size and layout of the components and the breaks in the strips are shown in the diagram in Fig. 3. Note too that the board is mounted using two 4BA nuts and bolts through two holes in the board with rubber grommets used as spacers. A 3mm drill can be used for the holes and this may also be used for the breaking of the copper strips. Alternatively, the strips can be broken using a spot face cutter, a tool made for this job.

SOLDERING

Mount the components as shown in the diagram, but remember to solder in the transistors last. The integrated circuit is mounted in a 14 pin d.i.l. holder, this is advised because the static charges from soldering irons can damage CMOS i.c.s unless special care is taken. The i.c. should not be put in the circuit until the unit is ready for testing, and not removed from its special foam protector, sooner than necessary.

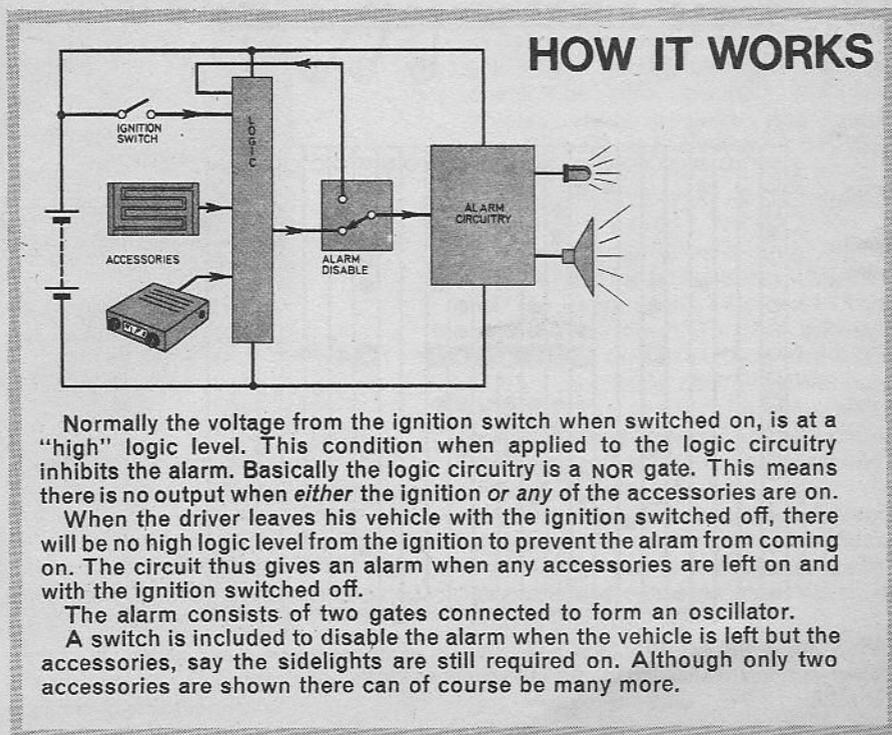The case used was a small metal one with a black vinyl covered steel top. These are commercially available at reasonable cost, so the actual shaping, and bending of a piece of aluminium is hardly worth its bother unless one has special desire to make one.









Normally the voltage from the ignition switch when switched on, is at a "high" logic level. This condition when applied to the logic circuitry inhibits the alarm. Basically the logic circuitry is a NOR gate. This means there is no output when *either* the ignition *or* any of the accessories are on.

When the driver leaves his vehicle with the ignition switched off, there will be no high logic level from the ignition to prevent the alarm from coming on. The circuit thus gives an alarm when any accessories are left on and with the ignition switched off.

The alarm consists of two gates connected to form an oscillator. A switch is included to disable the alarm when the vehicle is left but the accessories, say the sidelights are still required on. Although only two accessories are shown there can of course be many more.

CAR SYSTEM ALARM

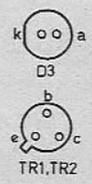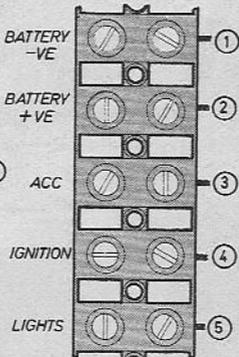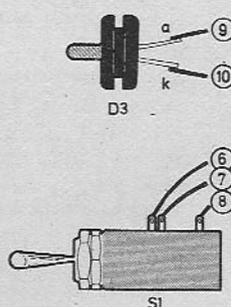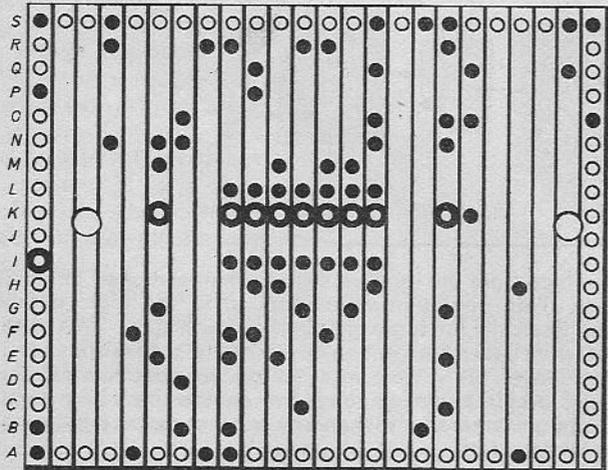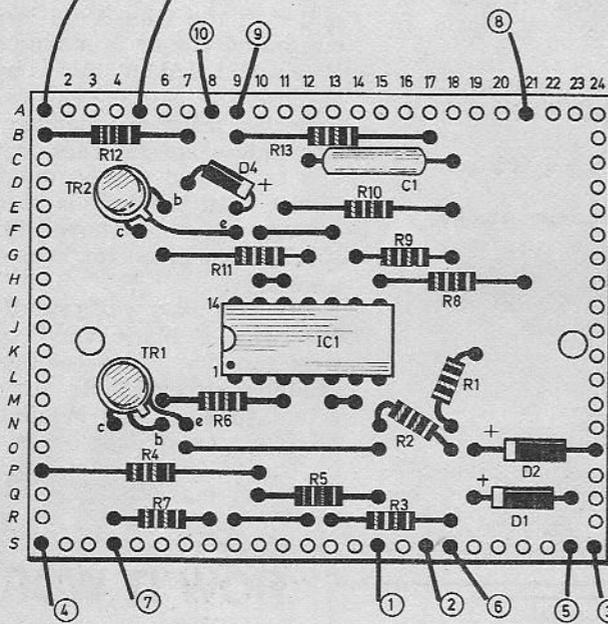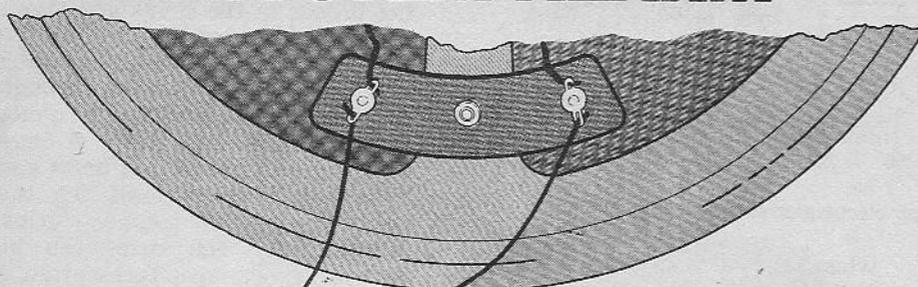

COMPONENTS

Resistors

- R1 2.2k Ω
 - R2 6.8k Ω
 - R3 15k Ω
 - R4 470k Ω
 - R5 1M Ω
 - R6 5.6k Ω
 - R7 820 Ω
 - R8 15k Ω
 - R9 1M Ω
 - R10 470k Ω
 - R11 5.6k Ω
 - R12 47 Ω see text
 - R13 100 Ω
- All $\frac{1}{4}$ watt carbon $\pm 10\%$

See
**Shop
Talk**
page 262

Capacitor

- C1 1000pF ceramic

Semiconductors

- D1 1N914 or similar silicon
- D2 1N914 or similar silicon
- D3 TIL209 red light emitting diode
- D4 BZY88C12V 12V 400mW Zener
- IC1 CD4001AE CMOS Quad 2-input NAND
- TR1 BC108 silicon *n*pn
- TR2 BCY72 silicon *p*np

Miscellaneous

- S1 miniature single-pole double-throw
- LS1 miniature loudspeaker with coil impedance 8 to 25 ohms approximately 70mm diameter

Stripboard: 0.1 inch matrix 24 strips by 19 holes; metal case type WB1 internal dimensions approximately 150 x 110 x 40mm; 5-way 2A terminal block; 14 pin d.i.l. socket for IC1; piggy-back push on connectors; 4BA fixings; connecting wire; small rubber grommet (2 off).

FOR GUIDANCE ONLY

ESTIMATED COST OF COMPONENTS

£3.50
excluding case

Fig. 3. Interwiring details, circuit board component layout and underside of the stripboard showing breaks in the copper tracks.


CASE MOUNTED COMPONENTS

The loudspeaker will be fairly small, only a few centimetres in diameter, and these generally do not have any mounting holes. So it is necessary to glue the loudspeaker in position, which means that a grille or covering for it would be impractical. What is recommended instead is to draw a circle where the loudspeaker is to be, the diameter being about 5mm smaller than the loudspeaker. Now the circle is drilled with holes of about 3mm in diameter, this is in effect a grille, and allows the sound to escape through the base of the unit.

WIRING

The l.e.d. and the switch are then mounted on the front panel, using holes of the appropriate size. Note not to cut the wires of the l.e.d. since the length of the leads identifies the electrodes of the device.

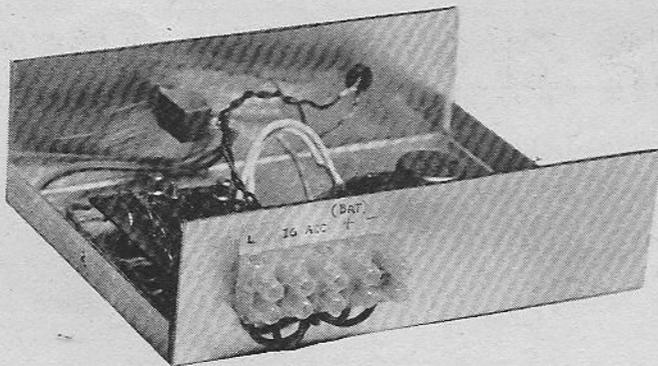Connecting wires should be left fairly long because there are several connections to be made at



Rear view of the unit showing the mounting of the terminal block for connecting to the car wiring.

the terminal strip located at the rear of the unit; it was found that 15cm long leads were adequate for this.

The board itself should be mounted using 6BA nuts and bolts, but before this is done check the strips for solder bridging the copper strips. This is likely to happen when using a large solder bit on 0.1 inch matrix stripboard as used here.

Once the board is fitted in place, it's a very destructive business taking it out again, so be sure and check the wiring thoroughly before assembly.

VOLUME

Resistor R12 is mounted separately. This is done to facilitate changing the value of this if the volume level needs altering. The maximum value should be in the order of a few hundred ohms. If the value of the resistor needs to be increased from that shown, then replace R12 by a 470 ohm preset potentiometer. By adjustment of the preset, a suitable volume level can be found with the alarm conditions present.

Remove the preset and measure its resistance. Choose the nearest preferred value fixed resistor to be the new R12. Alternatively, try various values between 47 and 220 ohms until required level is reached.


TESTING

Before the actual installation of the alarm in the car it is best to check the unit, because it's not always easy to poke and prod about under the dashboard with a screwdriver in your right hand and a copy of EVERYDAY ELECTRONICS in your left hand.

A battery such as a small radio can be used to represent the car battery conditions. Connect the positive terminal to the battery connection on the strip at the rear of the unit, and the negative terminal to the earth connector. Now connect short lengths of lead from the terminal strips connectors and leave bare wire ends.

Put S1 to the DRIVE condition, and connect the accessory and light leads to the positive terminal of the battery, and the ignition lead is left free.

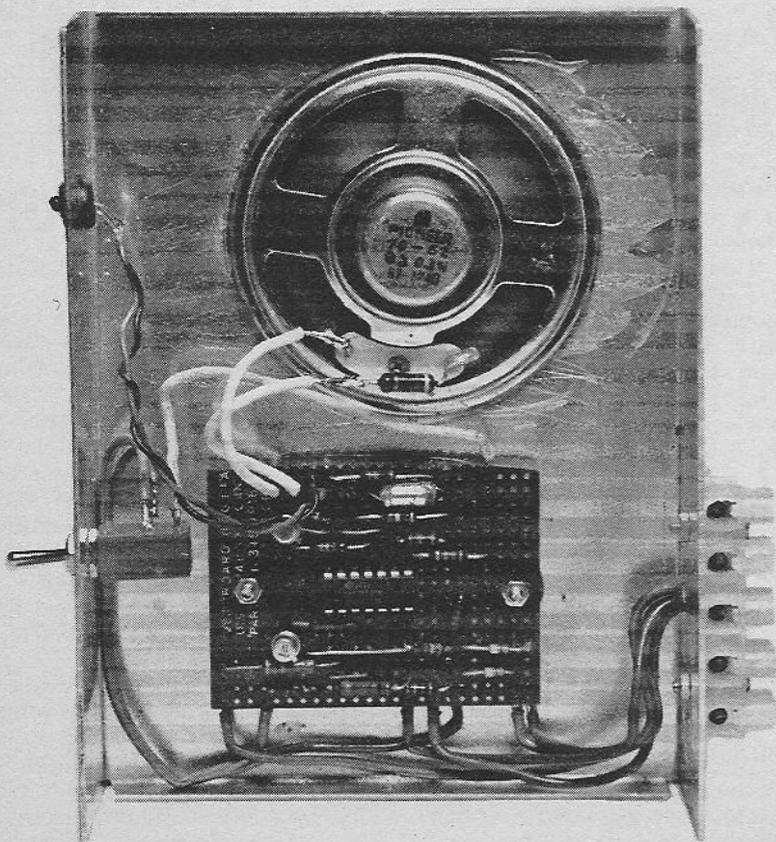The alarm should now be energised indicated by the l.e.d. and the tone bleeps. When S1 is



Interior view of the unit showing positioning of components.

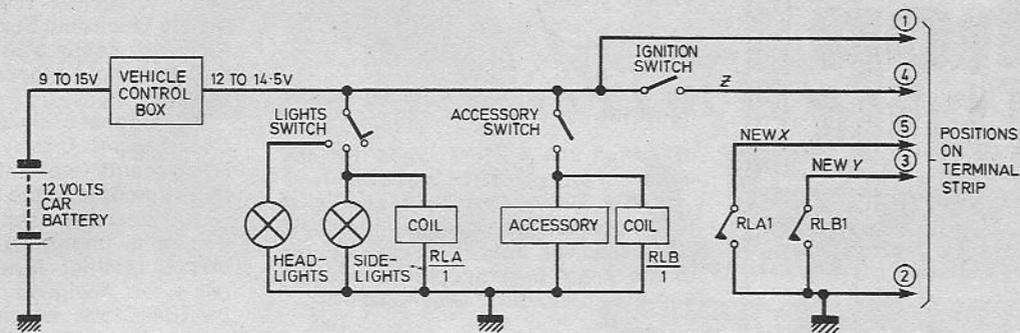


Fig. 4. Circuit diagram for use on Positive Earth vehicles.



operated the l.e.d. is still lit, but the alarm tone should stop. Now when the ignition lead is applied to the positive terminal of the battery, the l.e.d. should dim, and the alarm bleep should sound again. When S1 is restored to the DRIVE position the tone bleep will stop and the l.e.d. remains unlit.

INSTALLATION

If the test proves that the unit works then proceed with the installation as follows.

Find suitable points in the car electrical wiring to derive the battery and earth connections, in the prototype the light switch pole had a 12 volts fed to it so that was used, and a bolt was undone under

the glove compartment to provide the earth.

Any similar connection to the bodywork can be used, but after the bolt is undone for the wire to be connected to it, restore the tension in it.

Connect long lengths of coloured wire to the various parts of the system which is being monitored and run the leads neatly to the area where the unit is to be sited.

Using double connecting tags (piggy-back connectors) on the switches solder the coloured wires to matching connectors and invent some kind of colour code for identification. Re-assemble the switches into the mounting after ensuring that the electrical connections are sound.

Mount the unit as near to the driver as possible so as not to make the driver over-reach. The colour coded wires are then terminated in the unit itself after the test leads have been removed.

Finally re-test the unit when all wiring is complete, check for faults to the car lights and ignition circuits by starting the vehicle and operating the circuits which have been connected to the unit.

POSITIVE EARTH

For readers wishing to use the unit for positive earthed vehicles, the circuits to be monitored should be wired in parallel with small reed relays and the contacts of these should be fed to the alarm unit, according to the wiring diagram shown in Fig. 4.

The alarm unit should prove to be a great aid to forgetful drivers, but it is quite probable that the unit will never be used once the habit of checking switches is stuck in one's mind. ☒





By Brian Terrell

New products and component buying for constructional projects.

IT HAS been brought to our attention by followers of the *Teach-In 78* series that kits of parts for this series purchased from Bi-Pak contain some transistors with non-standard pin configurations. The particular device in question is the 2N3702.

The standard package for this device is classified as TO-92 which is a plastic case with in-line lead-outs, see Fig. 1a. This is one of the Texas Silect range (SILicon EConomy Transistor).

The types supplied by Bi-Pak have a TO-18 case, which at first sight looks identical to the TO-92, but closer inspection will show that the lead-outs are sited in a triangular configuration (called a "pin circle") as shown in Fig. 1b. You will notice that all the leads have different relative positions. The device can still be used to carry out the *Teach-In* experiments but the lead-outs will need to be preformed to fit the layouts in the article.

We are in receipt of a photostat copy of a letter sent to a reader by Bi-Pak explaining the anomaly in which they say that they were unaware of this at the time; now that this has been brought to their attention readers are assured that all future kits despatched will contain the correct transistors. Also they have told us that they will

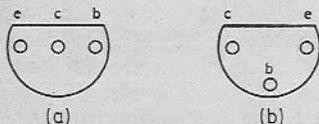


Fig. 1. Pin arrangements (a) for 2N3702 (b) Bi-Pak 2N3702

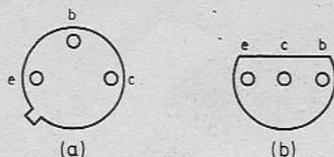


Fig. 2. Pin arrangements for (a) BC184L (b) BC184

exchange the correct types for the incorrect ones already sent out.

Bi-Pak kindly sent us a couple of the incorrect pinning types for test purposes. We tried them in a couple of the *Teach-In* experiments/modules and they functioned satisfactorily.

New type number

According to Texas literature, a particular device may be encapsulated in a different package, case and/or lead-outs or other, but to avoid confusion a new type number is given to the device. For example, the 2N3702 having a TO-92 encapsulation, is also packaged in TO-18, but is given a type number 2N5447. The electrical parameters of the two are identical.

Also, it is not uncommon to find transistors of the same basic type number with different pin configuration, but this is usually accompanied by a different casing. For example, the BC184 transistor will sometimes be found in advertisers lists followed by the letter "L". See Fig. 2a and b for the lead-out details.


A suffix letter does not always convey pinning information. The BC108 is available as BC108A, BC108B and BC108C. All have identical pinning and case, but differ basically in gain performance. Generally speaking, A, B and C suffixes refer to minor differences in electrical parameters whereas K and L are reserved for pin configuration and case alterations.

This month's constructional projects

No component buying problems are envisaged for two of this month's projects, *Stereo/Mono Lead Tester* and the *Car System Alarm*. All components should be available from a number of suppliers.

Almost in this category is the A.C.

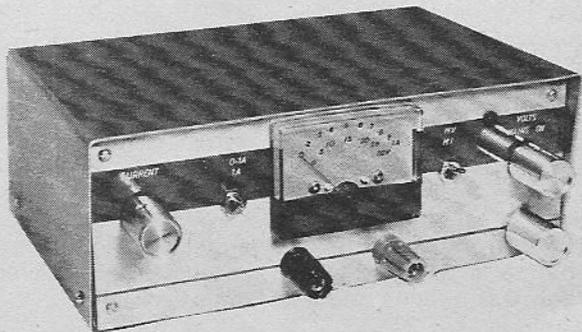Photograph of a completed Leader LPU-103 Power Supply Unit featuring variable current limiting.



Meter Converter for only the one per cent resistors could prove troublesome to locate. We have contacted Maplin Electronic Supplies, P.O. Box 3, Rayleigh, Essex SS6 8LR who tell us that they hold stocks of the required values.

Our biggest project this month is the *Chaser Light Display* but only a few components warrant a mention on this page. Due to the fact that a printed circuit board is used in the construction, it is important that the correct bridge rectifier is used. The p.c.b. has been designed to accommodate the B40C1500 which is a 1.5 amp device. If an alternative type number is to be used, ensure that the lead-outs are as the specified type otherwise disastrous results will arise.

The specified type is available from A. Marshall (London) Ltd., Dept. EE, 40-42 Cricklewood Broadway, London, NW2 3ET and costs 92p including V.A.T. postage and packing.

The triacs specified are rated at 6 amps 400 volts, but almost any device with the above rating or higher can be used. If other types are used, alternative heatsinks may need to be obtained. The TIC225D triacs and TV-4 heatsinks are available (four of each) from A. Marshall Ltd., at the above address at a total cost of £4.72 including postage, packing and V.A.T.

The "phase" switch S4 calls for a 4-pole 2-way rotary type and this may be difficult to locate. The more common 4-pole 3-way rotary wafer is recommended. The "third way" should be ignored.

Kit news

The latest news we have received from Arrow Electronics is that they are now marketing an excellent range of Leader "do-it-yourself" test gear kits.

One of the good points about these kits is that they come complete with a comprehensive instruction manual enabling the inexperienced constructor to produce a first class piece of equipment.

We hope to publish a more detailed report on the Leader kits in the near future, but further information and prices can be obtained from Arrow Electronics Ltd., Leader House, Coptfold Road, Brentwood, Essex, CM14 4BN.

Stereo/Mono

LEAD TESTER

By M. Simpson

INTRODUCTION

THE unit to be described here was designed with the guitarist and pop group in mind. With the number of foot pedals available as separate units, it is not uncommon for the guitarist to use several foot units in series to obtain certain effects.

This generally means a large number of leads inter-connecting the units to the guitar and amplifier. Thus a fault on one or several of the leads could cause problems tracking down the fault, as well as wasting a lot of time. This is undesirable especially when playing to an audience. If every lead could be rapidly tested before use, then this situation is less likely to arise.


This design was thus evolved to enable anyone to find a faulty lead and, indeed tell precisely what the fault is. Common faults that arise, which this unit will find, are as follows:

1. Open circuit on one or all wires.
2. Short circuit to any other wire.
3. Incorrectly wired jack plug.
4. Intermittent faults—usually found as crackles on the public address system.

The unit consists of four push to make switches. One is the battery/l.e.d. test switch (S4). The other switches, S1 to S3, are for each individual lead of the stereo lead. In the case of mono leads, S1 and S2 perform the same function due to the standard mono jack plug shorting out two terminals on the stereo sockets used.



HOW IT WORKS...

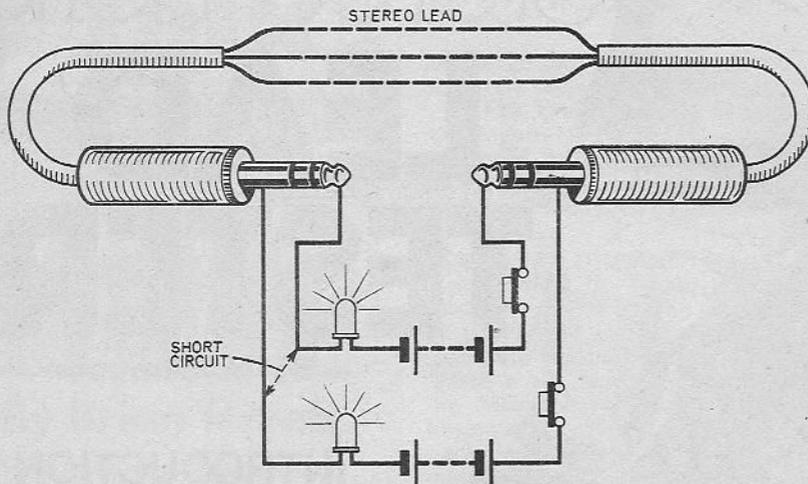

The Stereo/Mono Lead Tester is basically a three-position continuity checker. When a lead is plugged in and one of the switches is pressed the l.e.d. corresponding to that switch should light. If it does not then it would indicate that the lead is open circuit.

If the two l.e.d.s shown (there is actually three) both light together, then this would indicate a short circuit between those two leads. In practice the batteries are replaced by one and the l.e.d.s share one side of the battery supply. The unit may also be used to check intermittent faults.

**START
HERE FOR
CONSTRUCTION**

The holes are then drilled for the components (0.8mm for resistors and diodes, 1.2 mm for pre-sets and 1mm for Veropins). The components are then mounted on the p.c.b. as shown in Fig. 2 and carefully soldered in position. Take careful note of diode polarity, usually the cathode end has a black or white line near it.

WIRING

Finally the wiring to the switches and the l.e.d.s is completed following the remainder of the wiring also shown in Fig. 2.

The box used had dimensions of 115mm×75mm×40mm but any size will do so long as the components will fit inside. The size quoted is about the smallest in which all the components will fit comfortably. The box was made of a white thermo-plastic which proved easy to drill. Layout of the components is not critical but all the switches and l.e.d.s must be easy to operate and see.

It is important to get the wiring absolutely correct in the unit as a fault might cause problems later. It is, therefore, recommended that a colour code be devised and rigidly adhered to for each l.e.d./switch arrangement when wiring up.

TESTING

The unit when built should be thoroughly tested using two stereo jack plugs and six lengths of coloured wire. The wires are attached to the plugs and labelled. Thus, when the two plugs are inserted into the unit with all six ends not connected, the l.e.d.s should not light except when the BATTERY TEST switch S4 is pressed.

Now connect up the six loose wires by twisting the loose ends together so that the plugs are correctly wired. Then test the unit by pressing the test buttons individually. The l.e.d. above each button should only light and none other.

PRINTED CIRCUIT BOARD

A printed circuit board was made using a small off-cut from another project. The p.c.b. was made on a piece of fibreglass printed circuit board and etched in the usual way using ferric chloride.

A tip here is to cut the board to size, clean it up, place it underneath the diagram of the p.c.b., line it with the copper side up, and tap a compass point through the page to leave a small point on the surface of the copper in just the right place. Then draw on the areas with an etch resist pen, allow to dry and etch the boards as usual.

Components

Resistors

R1, 2, 3 680Ω (3 off)
All resistors are carbon ¼W ± 5%

Potentiometers

VR1, 2, 3 1kΩ miniature horizontal presets (3 off)

Semiconductors

D1 TIL209 green light emitting diode
D2 TIL209 yellow light emitting diode
D3 TIL209 red light emitting diode
D4, 5, 6 IN914 silicon diode

Miscellaneous

SK1, 2 standard stereo jack sockets (2 off)
S1-4 push to make, release to break push switches (4 off)
B1 PP3 9V battery
Small plastic box 115mm×75mm×40mm; four stick on rubber feet; printed circuit board; battery clip; connecting wire; solder.

See
**Shop
Talk**
page 262

Stereo/Mono LEAD TESTER

FOR GUIDANCE ONLY
ESTIMATED COST OF COMPONENTS
£3.50
excluding case


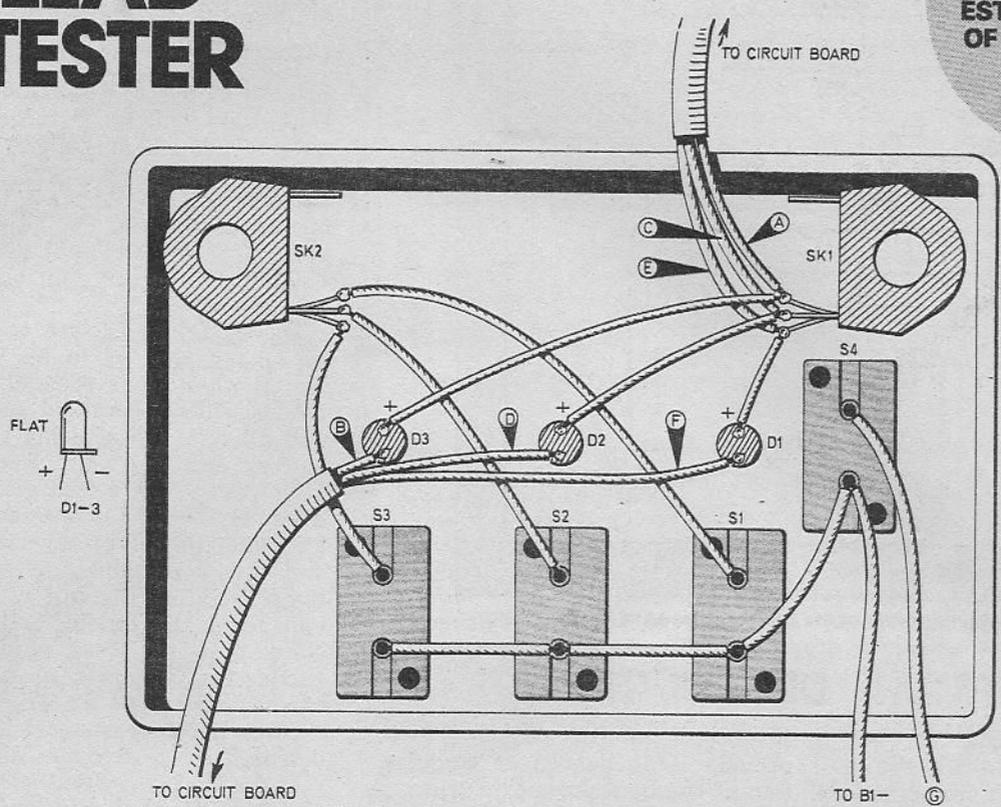


Fig. 2a. Interwiring details for the switches, light emitting diodes (l.e.d.s) and stereo jack sockets.

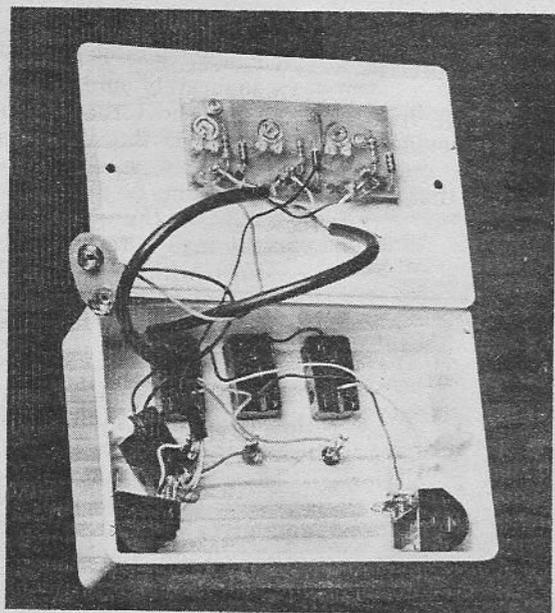

Interior view showing the circuit board mounted on the lid. The positioning of the switches, sockets and light emitting diodes can be seen.

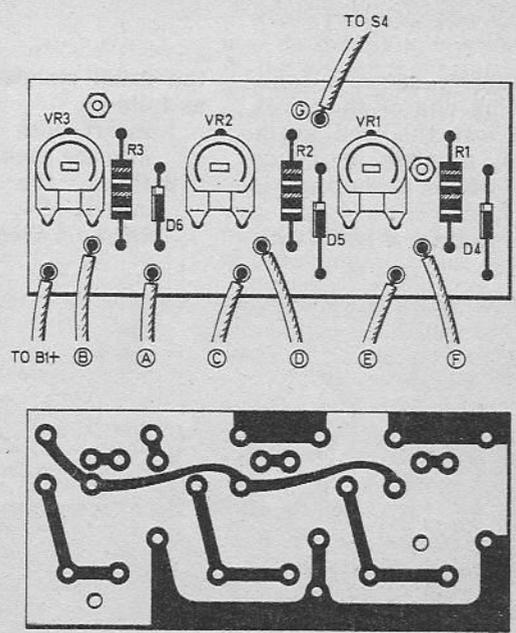


Fig. 2b. Printed circuit board component layout and the underside of the board showing copper tracks after etching (full size).

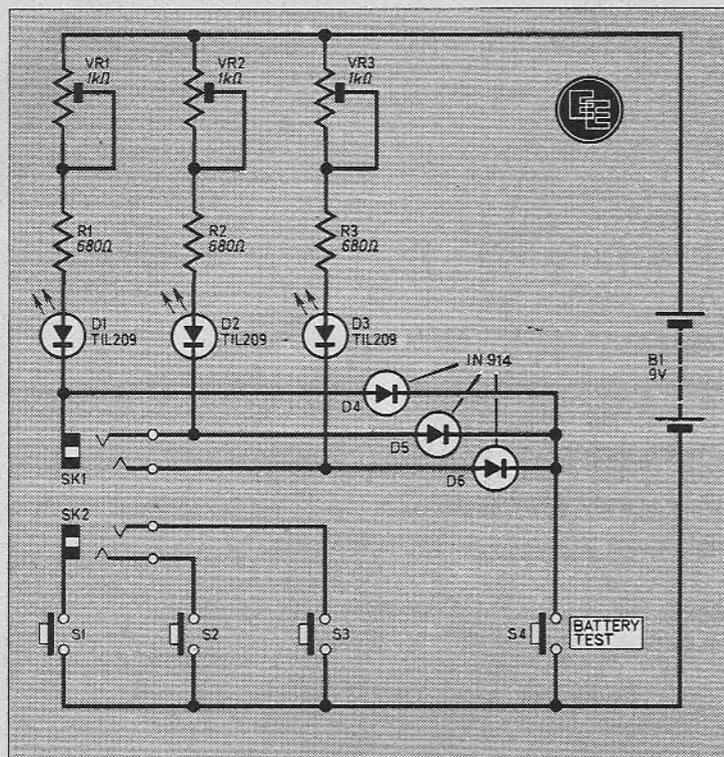


Fig. 1. Circuit diagram of the Stereo/Mono Lead Tester

CIRCUIT DESCRIPTION

The complete circuit for the Stereo/Mono Lead Tester is shown in Fig. 1. The circuit is very simple and uses three l.e.d.s to indicate the state of a lead under test. The three preset potentiometers VR1 to VR3 are used to control the

brightness of the l.e.d.s, and to provide some degree of equalisation of the light output.

This was found necessary as different colours of l.e.d. appear to give different light outputs—red being most efficient. Resistors R1


Now deliberately cause a fault by, say, shorting one of the wires to earth and test the lead again and note the number of l.e.d.s which light when a button is pressed.

The test method for a lead (with

the usual standard jack plugs) is as follows:

1. Insert both ends of the lead into the jack sockets provided.
2. Press the BATTERY CHECK switch (S4) and note that all the l.e.d.s light up.

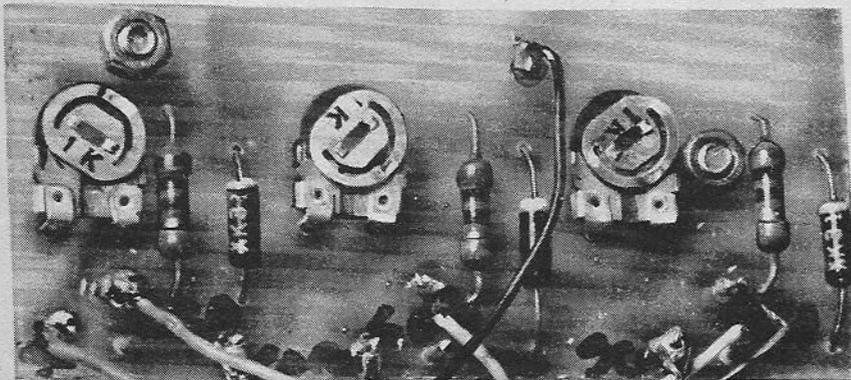3. Press switches S1 to S3 separately and note that the l.e.d. above the switch pressed lights. If this is the case, then the lead is alright. If more than one l.e.d. lights, or none light, or the wrong l.e.d. lights, the lead is faulty and, depending which l.e.d.s light, a reasonable idea of what is wrong can be deduced.



Close-up view of the printed circuit board showing the small preset potentiometers.

to R3 are to prevent the full battery voltage appearing across the l.e.d.s and to limit the maximum current from the battery. In the prototype values of 200 ohms were tried, however, it is recommended that these resistors be preferably 680 ohms.

This means that maximum brightness and the maximum current drain will be reduced. However, a good l.e.d. should still be visible in bright daylight but the battery will now last a lot longer on full brightness. The adjustment of the presets will still give good equalisation of the light output of the l.e.d.s.

Diodes D4 to D6 are connected in such a way as to be forward biased when S4 is pressed, i.e. the diodes will conduct and the l.e.d.s will all light up showing that the battery and l.e.d.s are working.


However, with a lead under test, when S1, S2 or S3 is pressed diodes D4, D5 or D6 will be reverse biased and, thus non-conducting and effectively isolating the rest of the circuit from the circuit under test. Note that the lead under test carries the current from SK1 to a corresponding contact on SK2 and thus to the depressed button. This is true if the lead is not faulty.

If the lead is faulty, then current may flow through the lead to the depressed button but the correct l.e.d. will not light—or possibly two will light, depending on the fault.

A table of common faults and their repair could be made and used for reference at a later date.

Thus, the unit is simple to operate, quick to indicate faults and gives a good idea of what is wrong so that the lead can be fixed at a later date.

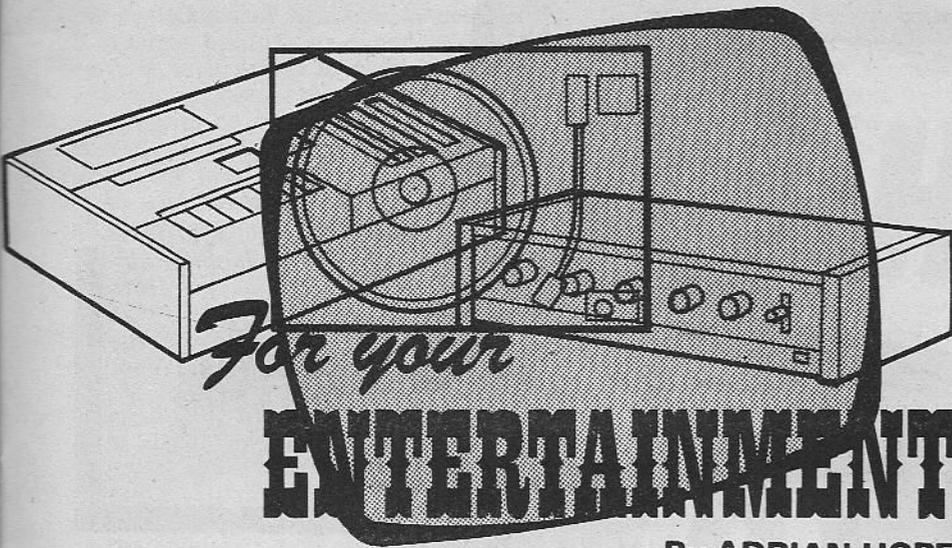Intermittent faults can be found by leaving the button(s) depressed and shaking or moving the lead until an l.e.d. flashes. □



By ADRIAN HOPE

A Shocking Affair

DON'T just breathe a sigh of relief that you weren't affected when, as reported in the national press last Autumn, three hundred families in a London council housing estate found they were without an electrical earth. For those who did not read the newspaper report of this literally shocking event, it went along these lines.

One of the three hundred families installed a new washing machine, and immediately got an electric shock from it. An engineer was called in under guarantee, and all concerned have him to thank for checking and finding that all the earth leads from all the flats ended up at one big dead end in the basement, leaving not one single flat with a hard electrical earth. This, of course, had left all the residents at risk of getting a lethal shock from any piece of equipment with a supposedly earthed chassis that went live.

Allegedly, thieves had stripped all the copper wire and then replaced the ducting so neatly that no one noticed.

Now I have no way of knowing whether the earthing wires were ever installed in the first place, but it brings other incidents to mind that prompt a reminder that everyone should at some time check that their equipment really is earthed, and not just an illusion.

Years ago in the country I knew of a schoolteacher who was getting shocks off the metal earth ducting of his house wiring. It emerged that the metal earth ducting was all electrically isolated from earth, and thus a potential death trap.

Only a few months ago I attended a press show in a large London cinema for which special equipment had been brought into the projection box. Every now and again I noticed switch clicks on the sound track, and afterwards asked why this was. The visiting

engineer told how he had found that there wasn't a proper "hard" earth for the projection box!

Bear in mind the kind of current needed to run a cinema projection box (hundreds of amps for the projector arcs), and you have an idea of how astonishing that situation was.

And was it an isolated case? I doubt it. Recently I attended another press show at a small modern London cinema, and there again switch clicks were frequently to be heard over the sound track.

So check for your own interest and safety that all your earth leads really do lead to earth, not just to thin air. To check, connect a resistance meter or a simple torch bulb and battery continuity tester between the EARTH pin of a wall socket and the kitchen cold water supply. This should show a short circuit—if it doesn't, find out why.

If in doubt call in your local electricity board.

Magnetic Driver

The shape of things to come? Recently, at one of the Philips Electrical factories on the Continent, I was astonished to see a driverless truck pulling a pallet of packing cases round the factory floor and into the storeroom.

Every now and again the battery powered truck would appear through a door at one end of the factory, weave almost in drunken manner around corners, disappear behind one production line, emerge from behind another, and trundle off out again through another door. Anyone who wanted to load anything onto the truck or take something off simply pushed the stop button as it passed and then sent it off on its way again.

There was no sign of any track guiding the truck, and I wondered

aloud what on earth would happen if such an obviously powerful object hit anyone who had failed to notice the police-like flashing light which it carried.

It turned out that the truck was guided along a predetermined route by a magnetic track buried under the factory floor, a sensor on the underside following the magnetic field and steering the truck wheels.

When someone finally did step in front of the beast, it stopped dead, sensing their presence by a flexible sensor. As it stopped, the truck flashed lights and emitted all manner of violent howls until the obstruction moved away.

Explosive Tune

Just how and when did the modern style of solid or "cricket bat" guitar begin? Charlie Christian was using one with Benny Goodman's band in the late Thirties and the very early Forties (he died in 1942); and he is generally believed to have first experimented with an electric guitar in Oklahoma City in 1937.

But was Charlie Christian using an ordinary acoustic guitar with an acoustic pickup to sense vibrations on the guitar belly and convert them into electric signals for amplification? Or was he using a magnetic pickup where vibrating metal strings directly induce a current into induction coils?

It is, of course, this type of induction pickup that makes possible the modern solid guitar, which produces electrical signals but virtually no acoustic sound.

It's an interesting question, which surprisingly involves military history. The story goes that in the early 1940's in the Battle of the Atlantic something very dangerous to shipping appeared in the water; the acoustic mine. In what seemed quite miraculous manner, these mines exploded only when a ship with a particular sound came close.

It was all thanks to a brilliant nasty idea by a German at Kiel. What he did was stretch a metallic string over a magnet and tune the string to the pitch of the sound which the engines of the hunted ship would make. So as the ship got closer to the mine the tuned string inside would start to vibrate sympathetically, and this vibration used to induce an electrical current in a coil. This induced current was then used to trigger the mine fuse and detonate it.

The story goes on that after the War someone else had the decidedly bright idea of using exactly the same technique to generate musical sounds. If this aspect of the story is true, then we have the German Navy to thank for the modern breed of electric guitars.

If the story is wrong, then the German Navy may have had jazz guitarist, Charlie Christian, to thank for the magnetic mine.

TEA

CH-

Part 5

in

78

BY
GEORGE
HYLTON

INDUCTANCE—RESONANCE—AMPLIFIERS

BEFORE continuing this month with our main subject of amplifiers, we shall take the opportunity to discuss one particular subject which has not been mentioned so far in the series. Tied in with this, is the story of coils and transformers, all of which completes the basic "elements" of electronics. First then the subject of **inductance**.

INDUCTANCE

Earlier in the series we told you how Oersted had discovered that a current in a wire creates a magnetic field which can interfere with a compass needle. In fact a current *anywhere* creates a magnetic field, but we are concerned with wires at the moment.

It was soon realised that the field can be intensified by coiling up the wire. In this way the current, as it goes round and round the coil, adds more and more field. Coils of insulated wire wound such as this are often used as electromagnets.

Now, it occurred to some people that if a current produces a magnetic field, then the process should work in reverse. A magnetic field should produce a current in a nearby conductor. But it did not seem to happen. Laying magnets beside wires or coils did not create currents.

The mystery was finally solved by Michael Faraday after years of careful research. He reasoned that the current-inducing effect of a magnetic field might be quite small. So he constructed an arrangement designed to make the effect as intense as possible. Faraday took a ring of iron and wrapped two insulated coils round it (Fig. 5.1).

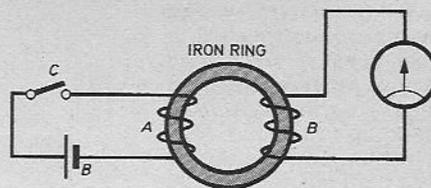


Fig. 5.1. Probably the best known of Faraday's experiments. Here the two coils A and B are coupled by the iron ring.

Coil A is an electromagnet energised by the battery. Its field is concentrated in the iron, which carries it through the receiving coil B. Any current induced in B is registered by the meter.

Faraday found that no current was registered. Then he noticed that the meter pointer gave a slight kick at the instant S was closed to energise coil A, and a much larger kick when S was opened. In between, with coil A energised constantly, nothing happened. This observation was one of the most important ever made. It led to the dynamo, the electric motor, the transformer and indirectly to radio.

As Faraday then realised, current flows in B only when there is *some change* in the magnetic field of A. In this case, the change is when the field builds up from nothing or when it decays from its steady value to nothing.

A steady field has no effect.

This is rather surprising; after all, the battery is supplying energy all the time. Where does it go? Well, in the steady state, after the field has built up, all the energy is used up in driving current through

the resistance of the wire in coil A. All this energy is wasted, because if A had no resistance the same current in it would still produce the same field. But with no resistance to overcome a battery would have no work to do. If the beginning of the coil were connected to the end current would flow round and round for ever.

An electromagnet is in real life totally inefficient, all the energy used to create the field is wasted.

The point about coils is that a current in a coil creates a magnetic field. If coil B in Faraday's arrangement is disconnected, a rising or falling field in A still has an effect. The changing field induces an e.m.f. in coil B. Naturally, a current only flows if the coil in which the voltage is induced is part of a complete circuit. But the voltage appears anyway, complete circuit or not. So the true effect of a changing magnetic field is to induce voltages rather than currents.

A changing current flowing in a coil has an effect on the coil itself. It is obvious that it must have, when you remember that the coil is in the middle of its own magnetic field. The effect is that the coil impedes the flow of current. It does so by generating a voltage which tries to push current in the reverse direction to the current flowing through it. This voltage is usually called a **back e.m.f.** and occurs in all sorts of inductive devices such as electric motors.

The size of the back e.m.f. depends partly on the coil itself, the greater the number of turns the greater the back e.m.f. and therefore the higher the impedance. But it also depends on the rate at which the current is changing.

The faster the current changes, the greater the back e.m.f. and therefore impedance. In a.c. circuits the rate of change of current is greater as the frequency is made higher. So the impedance of a coil must increase as the frequency is raised.

The ability of a coil to generate a back e.m.f. is used as a measure of the *electrical size* of the coil.

A coil which produces a back e.m.f. of 1 volt when the current through it changes at the rate of 1 ampere per second has an inductance of 1 henry.

COIL CORES

The inductance of any coil is increased by winding the coil on a "core" of iron or ferrite material. Transformers for mains and audio frequencies use cores of silicon-iron or various magnetic alloys. The cores are built up from stacks of sheetmetal stamped out as thin insulated laminations. Laminations are usually in the shape of the letters E, I, or a U with sharp corners. Some transformers often use C cores.

Iron laminations cannot be used at high frequencies. Instead, dust-iron cores are used. These are made by pressing together fine particles of iron, insulated from one another. Dust-iron is useful at frequencies from about 100kHz to 100MHz.

Ferrite is a more versatile material which is made in a number of grades and shapes. Between them they cover a frequency range of about 1kHz to 1,000MHz. Ferrite is a hard black brittle material which belongs to the same physical class of materials as pottery and china; i.e. the ceramics. It is made by moulding the powdered materials then baking them at high temperatures until the particles fuse.


The most familiar ferrite component is the aerial rod used for l.w. and m.w. reception.

The amount by which the inductance of a coil is increased by its core depends on many factors. At low frequencies, with special magnetic alloys such as Mumetal and tape-wound ring cores, the inductance can be tens or even hundreds of thousands of times what it would be if the core were absent. On the other hand at high radio frequencies, where the core is adjustable the increase may be only in the order of two times. When talking about this type of increase the word *permeability* is often used.

Permeability is the factor by which the inductance would increase if the coil were embedded in a large mass of core material, so that all the magnetic field of the coil when carrying current would be in the core. Practical coils are not like this and there is always some "stray field" outside the core, and this reduces the increase of inductance.

The practical increase of inductance is called the effective permeability.

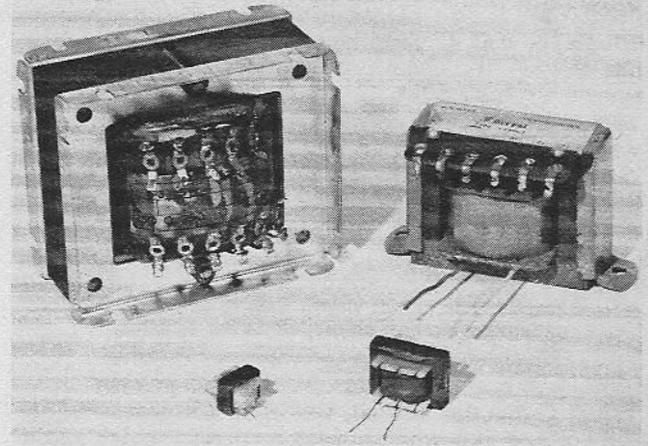Much depends on the geometry of the core. A 10cm ferrite rod aerial made of material with true permeability of 500 may have an effective permeability of five when the coil is in the centre of the rod, falling



A few examples of transformers using laminated iron cores.

to three when it is near one end. It follows that the inductance can be adjusted by sliding the coil along the rod. Much greater increases in inductance are given by cores which form closed loops of magnetic material threaded through the centre of the coil. Mains transformers always use this type of construction.

It is usually desirable in transformers to minimise the stray field, so that the magnetic field of the primary is coupled strongly by the core to the secondary winding.

Increase in inductance means that fewer turns are needed on a coil. This calls for less wire so the resistance of the winding is reduced, giving higher efficiency in a transformer and a higher quality-factor in a tuning coil. Unfortunately, all core materials are "lossy", that is, the core absorbs energy from the coil, so the improvement is less than might be expected. The core losses increase with frequency, and this effect is worst with high permeability materials.

This is why laminated metal cores are not usable at high frequencies, and why the grades of ferrite usable at v.h.f. and u.h.f. provide only modest increases in inductance. In fact, at u.h.f. it is quite common practice to use brass cores for any adjustment necessary. The brass *reduces* the effective permeability and so lowers the inductance.

TUNED CIRCUITS

Inductors and capacitors are energy-storage devices. Capacitors store energy as an electric charge, and we have already investigated the process of charging and discharging.

Inductors store energy in quite a different way. When a current flows in an inductor a magnetic field is created in and around it. The energy is in the field. To recover the stored energy you must stop the current. The field then collapses, and as it does so it induces a voltage in the inductor. The size of this voltage depends on how fast the current is switched off—the faster the greater.

An inductor and a capacitor can be connected together as in Fig. 5.2. If the switch *S* is put in position 1, and left closed long enough for the circuit to settle down after the initial inrush of current all that happens is that *C* stays fully charged to the supply voltage. If *S* is now placed in position 2, *C* discharges through the coil, *L*. This, however, gives *L* a magnetic field.

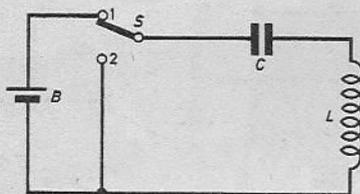


Fig. 5.2. The circuit shown here is helpful in understanding how an inductor behaves when connected to a source of energy.

When *C* has discharged, this field collapses, inducing a voltage in *L* which drives a current which again charges *C*. And so on, for ever and ever. Or, rather, it would go on for ever and ever, if there were no resistance in the circuit. In practice there is of course, in the resistance of the wire which forms the coil, so every time current flows some of the energy is used up, and the charge/discharge process is made weaker. If the resistance is small, and the oscillation dies away slowly, we say that the circuit has a high *Q*. This is the symbol for "quality factor".

The process just described has a familiar counterpart in mechanical terms. This is the pendulum. If you push the weight of a pendulum to one side, and hold it there, you might say that this represents the *LC* circuit with the switch in position 1 with *C* charged.

If you now let the weight go, corresponding to changing *S* to position 2, the energy stored in the displaced weight allows the pendulum to swing. It accelerates until it reaches the bottom of the arc through which it moves. From then on it has to climb, so it slows down and eventually reaches some height where it can go no further. It then falls back again, and so on. Each swing is a little shorter than the last, because energy is used up in overcoming air resistance, friction in the pivot, and so on.

The time it takes for the pendulum to swing from one end of its travel to the other *and back again* is called its **period**. In an *LC* circuit, the period is the time it takes from the moment when *C* begins to discharge until it becomes charged again *with the same polarity*. This is illustrated by the graph in Fig. 5.3, and shows how the voltage on the capacitor charges with time. The period need not be measured from peak to peak.

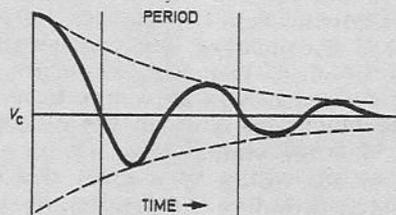


Fig. 5.3. Graph showing what the output waveform of the previous figure would look like.

For most purposes it is easier to measure from zero to zero and this is indicated in the figure. The period is the same in both cases, of course. In fact, if you measure from *any* point in one cycle of charge-discharge-recharge to the same point on the next cycle you get the same period.

In an *LC* circuit the period depends on the sizes of *L* and *C*, that is the number of henries and the number of farads. To be precise, the period depends on the product of *L* and *C*, that is *L* times *C*.

Another way of describing the behaviour of a pendulum or *LC* circuit is to count the number of cycles of oscillation in a given time. In electronics, where the oscillations are usually rapid, the standard time is one second. The oscillation is then said to go through a particular number of cycles per second. This number is called the frequency. Cycles per second is, however, an old-fashioned term, so the word Hertz, symbol Hz, has been adopted. It does of course mean the same.

The frequency of an *LC* circuit, usually called a tuned circuit, is also dependent on the sizes of *L* and *C*. But in this case, since the frequency goes *up* as the period goes *down*, the mathematics come out differently. In fact, the frequency is proportional to one divided by the square root of *L* times *C*. Also, to make the units come out right, the number 2π has also to be included. This gives the awkward-looking formula:

$$f = \frac{1}{2\pi\sqrt{LC}}$$

The frequency of oscillation is often called the natural frequency or the resonant frequency. An excellent way of understanding tuned circuits is to make a rigid pendulum by drilling a hole through a large heavy stick, or metal bar, or something similar and hanging it on a small nail through the hole, or a piece of string, so that it can swing freely to and fro. Even if the pendulum is very heavy, a tiny push given repeatedly at the right time is enough to build up the oscillation. You can prove this by pushing it with something weak, such as a piece of thin wire, which would bend if too much pressure were applied.

This build-up of oscillations, which shows that energy is being stored in the pendulum, takes place only if you push at the right times. If you try to make the pendulum swing at the wrong frequency you will find that it resists your efforts.

In circuit terms, the equivalent to this behaviour is that a small voltage or current applied to an LC tuned circuit will build up oscillations at the natural frequency but not at some other frequency remote from the natural one. If a mixture of equal currents at different frequencies is applied then stored energy builds up most at whichever frequencies are closest to the natural one. After a few tens or hundreds of cycles these natural frequency currents and voltages have become much greater than the others. This is the process of frequency selection.

A tuned circuit with a very great capability for energy storage is said to be very selective, or to have high selectivity. Obviously, selectivity is a necessary property of a radio receiver, whose aerial picks up many transmissions on different frequencies, only one of which is required by the listener.

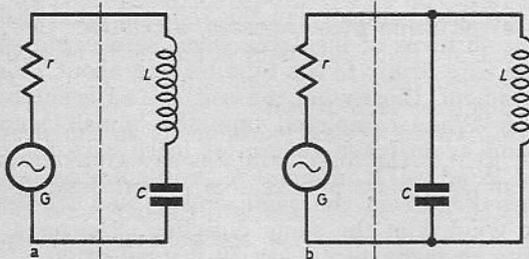


Fig. 5.4. Two ways of connecting an inductor and a capacitor. The first is in series, the second in parallel.

Now let us see how a tuned circuit behaves when an a.c. signal is applied to it. Fig. 5.4. Here the a.c. signal comes from a generator, G. There are two ways of connecting up. In Fig. 5.4a all the current flows through the generator, L and C. If the generator operates at the resonant frequency, the current builds up in such a way that a small "push" from the generator creates a large flow of current. The generator finds it easy to make a large current flow, which is the same as saying that to the generator the LC circuit offers little resistance to current flow. In fact, if L and C were electrically perfect they would offer no resistance at all at their resonant frequency, and the current would depend only on the generator's voltage and the resistance r.

At frequencies different from the natural one, the generator finds itself out of step with the stored voltage and current. The LC circuit's resistance has increased.

The circuit in Fig. 5.4b shows a different situation. Current can now surge back and forth between C and L without going through the generator. A small current from the generator at the right frequency, causes a large current to build up and circulate in L and C, but all this stored current need not flow through the generator itself. It turns out that in this case, at the resonant frequency, the LC circuit has a *high* impedance. At other frequencies remote from the natural frequency the impedance becomes *low*.

The first circuit is sometimes called an **acceptor** circuit, because it accepts current readily at the

natural resonant frequency. However, electronic engineers usually refer to it as a **series-tuned circuit** from the way in which L and C are connected. The second circuit is sometimes called a **rejector** circuit or an anti-resonant circuit but electronic engineers call it a **parallel-tuned circuit**.

RESONANCE

So far we have not explained the term resonant which is the one most frequently used in talking about tuned circuits in electronics. Resonant is really an acoustical term. You read about people speaking in resonant tones, for example. In scientific acoustics, **resonance** refers to the property of organ pipes, piano strings, etc., to be frequency selective. If you blow into the open mouth of an empty bottle in the right way you produce a musical note. This is resonance.

What happens is that the hissing sound of your breath contains a mixture of frequencies, which makes the air in the bottle vibrate as sound waves. Sound travels to the bottom of the bottle, is reflected as an echo, and arrives back at the mouth. If it arrives back at just the right moment it reinforces the sound which is now coming from your breath, and a stronger wave then travels back to the bottom of the bottle, and so on. It is like the gentle, repeated push of the pendulum all over again, but in a different form.

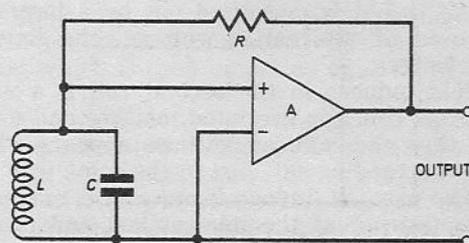


Fig. 5.5. A simple oscillator circuit. The circuit is tuned by the combination LC circuit.

In electronics, we often need to generate a particular frequency continuously. This can be arranged by connecting an LC tuned circuit to an amplifier with positive feedback, Fig. 5.5. This arrangement is the electronic equivalent of blowing into the empty bottle. All amplifiers generate electrical noise, that is, random mixtures of frequencies. As you can see, the LC circuit, fed via R, picks out the wanted frequency and feeds it back into the amplifier.

It emerges, reinforces any noise at the correct frequency, and is fed back again via R into the LC circuit and so on. The LC circuit quickly acquires a large circulating energy at its resonant frequency, which provides an input signal for the amplifier. So long as you do not take too much energy from the output, but always leave enough to sustain the oscillation, the system will generate an output for you for ever, or at least until the battery runs down or some component fails.

There are many different forms of LC oscillator. The commonest ones use a single transistor but a more complicated form of tuned circuit. The point is that a single transistor does not provide an amplified output voltage which is in step with the input. The output of a single stage voltage amplifier is exactly

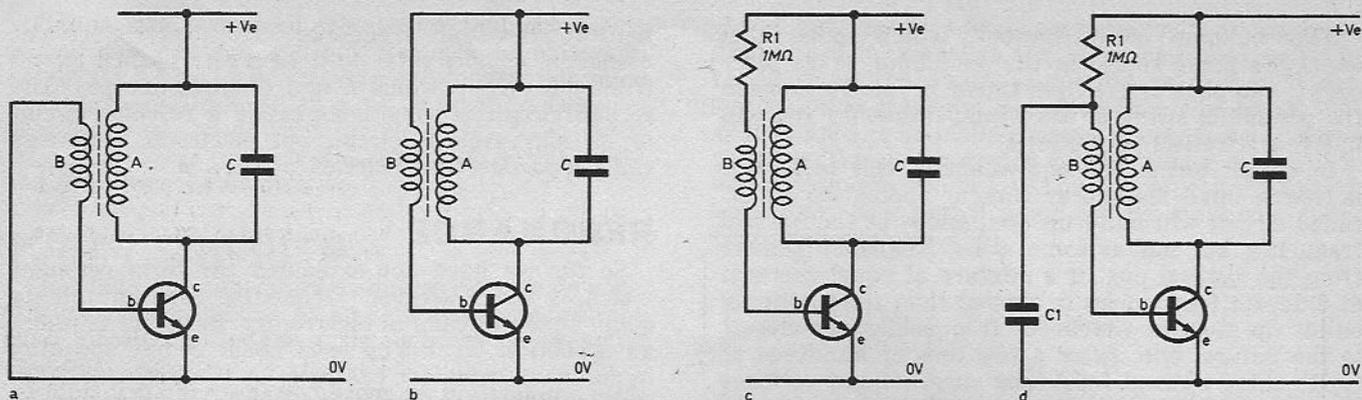


Fig. 5.7. Four ways of connecting our coil into a transistor circuit. The first (a) will not work as there is nothing to turn the transistor on. In (b) the transistor is turned on too much, whereas although (c) is satisfactory, the a.c. current is impeded. By adding a capacitor as in (d) this problem is solved.

out of step with the input. It is an inverting amplifier, if the input goes positive, the output goes negative. This is of no use for making an oscillator, since any signal fed back from output to input would oppose the existing input signal, instead of reinforcing it. To make the output signal assist the input it is necessary to turn it "upside down" so that positive becomes negative and negative positive.

One method of inverting the signal is to use a device called a transformer. The basic idea of a transformer was the iron ring in Faraday's experiment, Fig. 5.1. If coil A is energised not by a battery but by a source of alternating voltage, the field continually changes.

This field induces in the second coil B a varying voltage. Now coil B is insulated, neither end need be earthed, thus the induced voltage appears whether the coil is earthed or not. Just in the same way either end may be earthed. Indeed if one end is earthed the voltage appearing at the non-earthed end can then be in phase or could be phase inverted with respect to the voltage on coil A.

This arrangement can thus be used as a phase inverter, to turn signals "upside down".

OSCILLATORS

Up till now a great deal of theory has been discussed regarding tuned circuits, coils and phase. Now it is time to put that theory into practice by looking at a practical oscillator.

First, however, we shall make a particular kind of coil. The constructional details of which is shown in Fig. 5.6. You will notice that one coil is wound on top of the other, this form of winding means that the field of one is concentrated very nicely into the second coil. We say that the coils are tightly coupled.

The coil is wound on a piece of ferrite rod about 10cm × 9mm.

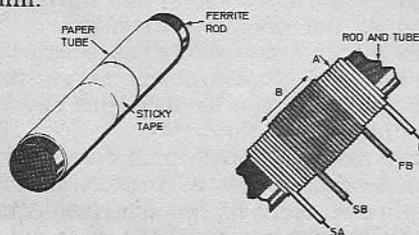


Fig. 5.6. Constructional details for our coil. Insure that the ends of the wires are clearly identified as shown.

Before winding your coils cut a long strip of thin card or thick paper, not quite as wide as the rod is long. Wrap it round the rod so that it forms a rigid tube and tape it so that it cannot unwind. You should find that it can be slid along the rod.

Put the tube centrally on the rod and wind coil A, of about 40 turns of insulated wire. Before you start, tape the wire firmly to the tube leaving about 150mm for a lead-out. Close-wind the coil, i.e. adjacent turns touching. When completed tape the "finish" end in place and again leave 150mm of loose wire for connecting. Wind coil B on top of A, proceeding as before. Start winding from the same direction as you started A at, and wind it in the same direction. You need not use quite so many turns, say 30 instead of 40.

We shall use A as the inductance L of an LC parallel-tuned circuit. C can be a polyester or polystyrene-capacitor of 10nF in value. When this LC circuit is connected correctly to a transistor, using the transformer phase inverting properties of the two coils the transistor should oscillate. The tuned coil A will be connected in the collector circuit since this is the output. Coil B will be connected to the base.

The simplest connection, Fig. 5.7a, will not work because there is nothing in it to turn the transistor on. The next simplest, Fig. 5.7b, in which the earthy end of B is connected to battery positive turns on the transistor too hard. The usual method of turning a transistor on is to feed a small current into the base. This is what you did earlier when estimating the current amplification.

The circuit in Fig. 5.7c does this but is still not satisfactory because the high resistance R1 greatly reduces the amount of a.c. current which can flow when a voltage is induced in coil B. The a.c. path is through base to emitter then through the battery to R1 and so back to the coil. The battery offers no impedance to a.c.

To enable a.c. to flow freely we connect C1 as in Fig. 5.7d. If C1 has a large enough capacitance it will offer little impedance to a.c. signals. These can then flow from coil B through the base/emitter part of the transistor and back to B via C1 without having to go through R1 at all.

For making measurements of the a.c. voltage across the coil, it is convenient to have one end earthed. Also it is more convenient when wiring up the circuit to connect the positive end of R1 to the collector rather than the battery. This makes very little dif-

ference to the operation of the circuit and in fact is a very common way of **biasing** a transistor, that is turning it on to the required degree.

The circuit we finally use is shown in Fig. 5.8. It incorporates these two conveniences, and you will see that it does all the other things we want as well.

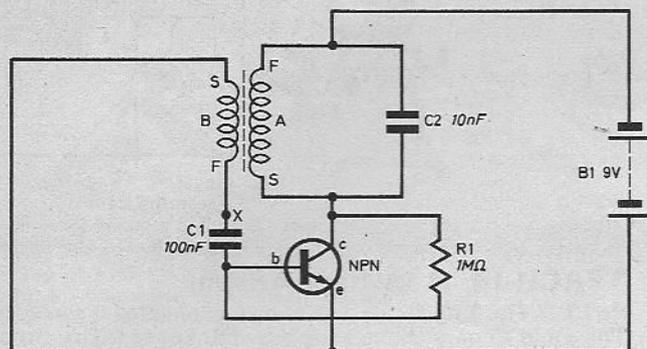


Fig. 5.8. The final circuit we use. This is constructed using the NPN module and the homewound coil. Note the connections to the coil. To check that it is working the **VOLTAGE INDICATOR** may be used.

The letter S and F refer to the start and finish of the windings. It is important to connect as shown, otherwise the circuit will not oscillate. When it does oscillate, it is at a high frequency, about 200kHz. This is far too high to hear, so we have to detect the oscillation some other way. First you can do it by connecting your **VOLTAGE INDICATOR** to point X where the coil joins C1. There is no d.c. voltage here because C1 blocks the d.c. from the battery. There can however be plenty of a.c. We measured about 5V.

The other test is to place a radio close to the ferrite rod and tune across the long and medium wavebands. At various points you hear a whistle, caused by your oscillator interfering with an incoming broadcast. To prove it is your oscillator and not the TV in the next room or something else, touch the collector of your NPN module. This produces a small change in frequency, which you can hear. You will also find that sliding the ferrite rod in and out of the coils produces a large change of frequency. Evidently the position of a coil core can have a large effect on the inductance.

AMPLIFIERS

An amplifier is a device which makes small quantities greater. In electronics the quantities which are amplified are voltage, current and power. Amplifiers can be made which will increase any of these, frequently all three at once.

An amplifier uses the energy of its battery or power supply to make enlarged copies of the quantities in question, which are known in general as the input signals. To begin with, we shall consider a *voltage amplifier*.

A common kind is the **operational amplifier** (abbreviated to op-amp), so called because it is designed to carry out certain mathematical operations in one kind of computer, the analogue computer. The input signal is a small voltage, the output signal a larger one, perhaps thousands of times larger.

The standard symbol for an operational amplifier is a triangle with two input points and one output point. Fig. 5.9.

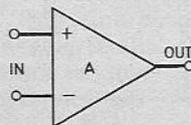


Fig. 5.9. The standard symbol for an operational amplifier. This has two inputs; the inverting (negative symbol), and the non-inverting (positive symbol).

The plus and minus signs at the input do not have their usual meaning. Here they show which direction the amplified output moves when an input is applied. The plus sign means that the output voltage changes in the same direction as the input, positive for a positive input, negative for a negative input. The minus sign means that the amplified output voltage changes in the opposite direction to the input. That is a positive input voltage produces a negative output voltage, and vice versa.

This process of changing the polarity of the signal is known as *phase-inversion* or just inversion. The terminal with the minus sign is known as the inverting input terminal, and the plus sign marks the non-inverting input terminal.

Now, what happens if the non-inverting terminal is connected to the output terminal? Any small fluctuation in the output voltage caused, say, by the battery voltage changing slightly, gets amplified, producing a larger fluctuation which reinforces the original one and which is then amplified again, and so on for ever.

If 2V is applied to both the inputs, for example, the 2V at the non-inverting input is cancelled by the 2V at the inverting input, so the amplifier behaves as if it had no input at all. This kind of amplifier is called a **differential amplifier** because it responds to the difference between the two inputs. Suppose the

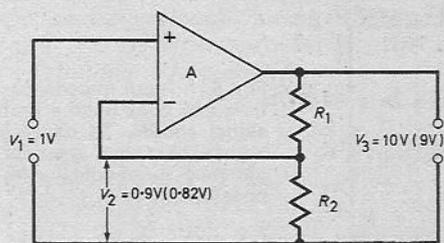


Fig. 5.10. By adding two resistors as a potential divider, the op-amp can have any gain as desired.

amplifier has a voltage gain of 100 but we need only to amplify a 1V input by 10, to produce 10V output. The amplifier can be arranged to have an effective gain of 10 by adding a feedback circuit, Fig. 5.10.

Here resistors R1 and R2 are so proportioned that 0.9V is fed back to the inverting terminal. The effective input is now $1V - 0.9V = 0.1V$. When this 0.1V is amplified 100 times the required 10V output is produced. The voltage divider formed by R1 and R2 has to divide the output voltage by about 11 in order to provide the required effective gain.

Now, so far nothing has been accomplished that could not have been done just as effectively by attenuating the input voltage to 0.1V before applying

it to the amplifier. The beauty of the negative feedback arrangement becomes clear when we consider what happens if the gain of the amplifier changes.

Suppose it falls to 50. This would normally reduce the output by half, to 5V. But as you can see from the figures in brackets the output is reduced only to 9V. The negative feedback has kept the effective gain close to the target value. It turns out that the more gain is sacrificed the more protected the effective gain is against variations.

This is most useful, because it is not at all easy to make an amplifier with a precise gain, because of variations in transistors, components, supply voltages and so on. There are other benefits, too, such as a reduction of distortion. Practical operational amplifiers often have voltage gains of around 10,000, but on data sheets the gain, called the open-loop gain, meaning the gain with no feedback, is often expressed in decibels.

A voltage gain of 10,000 is equivalent to 80 decibels.

INPUT IMPEDANCE

So far, in talking about amplifiers, we have said nothing about what an amplifier input looks like to a signal voltage. In fact, we have assumed that the impedance between an amplifier's input terminal and earth is infinitely large.

In practice, however, the input impedance may be low enough to have to be taken into careful consideration. If it is too low it may seriously affect the input signal. The reason is that most of the signals met with in practice come from signal sources; microphones, aerials, gramophone pick-ups, tape playback heads etc, which themselves have appreciable internal impedances. Such a signal source can be represented on a circuit diagram as a voltage generator V_s in series with an impedance R_s . Fig. 5.11.

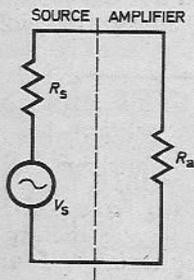


Fig. 5.11. Input impedance of amplifiers can pose quite a problem to a signal source. To obtain maximum output from the amplifier the impedance R_a should be as large as possible.

When this is connected to an amplifier whose own input impedance is R_a a current flows. This causes a voltage drop in both R_s and R_a . Only the voltage across R_a is applied to the amplifier. The other part is lost in R_s , that is, it stays inside the signal source.

To minimise this loss of signal it is necessary for R_s to be small in comparison with R_a . You can see that these two resistors form a voltage divider, whose output appears across R_a . Thus if R_s is twice the size of R_a two thirds of the signal voltage is lost.

Next month we shall continue with amplifiers and go on to build a practical working module.

See Shop Talk concerning the leadouts of the 2N3702 transistor.



TEACH-IN 78 Matters Arising

Part 3. In Fig. 3.10, the l.e.d. is shown connected incorrectly. The a and k connections should be transposed. The circuit in Fig. 3.9. is correct however.

Part 4. The answer to question one of Part Three should be 5 ohms and not 2 ohms as stated.

QUESTIONS

- A negative signal is applied to the inverting terminal of an op-amp. The output is:
 - positive
 - negative
 - zero
- A changing magnetic field in an inductor induces:
 - current
 - a voltage or e.m.f.
 - nothing
- An acceptor circuit is:
 - L and C in parallel
 - L and C in series
 - R and C in parallel
- Coils are said to be tightly coupled when:
 - they are twisted firmly round their former
 - they are close together
 - the field of one passes through the other
- To a.c. signals the impedance of a battery is normally:
 - very low
 - very high
 - voltage divided by current from the battery
- A 2 ohm resistor and 4 ohm resistor are connected in parallel. The total resistance is:
 - 6 Ω
 - 2 Ω
 - 1.33 Ω
- A transistor has a collector load of 1k Ω and a bias resistor between collector and base of 220k Ω . If its collector voltage is about half the supply voltage, its d.c. current amplification is about:
 - 220
 - 100
 - 220,000
- A transformer has a 100 turn primary and a 400 turn secondary. If 3 ohms is connected to the primary the secondary "sees":
 - 12 Ω
 - 0.75 Ω
 - 48 Ω

ANSWERS (To Part four)

- | | |
|----------------------|------------------------|
| 1. 1 mA per volt (a) | 4. 1000 seconds (c) |
| 2. 5 volts (a) | 5. 17 milliseconds (a) |
| 3. 9 milliamps (c) | |



Off the track

With reference to the December 1977 issue of EVERYDAY ELECTRONICS, I would like to point out a mistake regarding the 'Hovertrain'.

In "For your Entertainment" Mr. Hope states: "For a while a length of track and a prototype vehicle sat forlorn in a field at Cranfield; but I understand that bulldozers have now moved in...".

This is a mistake: The vehicle sat in a hanger. It was NOT at Cranfield. It was in Earith in Cambridgeshire.

The firm my father works for, bought the buildings and land. Part of the terms of purchase was that they knocked down the track. It is now the hardcore of the yard. This was 2½ years ago.

As for the train? It was transported to a train museum, but it fell off the lorry less than half a mile from its "home".

Before it went, however, I managed to see the train at very close quarters. The linear motors were very impressive.

On the train itself, at the back, there were two wheels with car tyres on which were used to stabilise the train. Mounted on the top of the train was an arrester hook for use in emergencies in case it didn't stop. On one occasion when this hook was tried, with the train going at about 15 m.p.h. the train's hook caught the wire and it stopped with just feet to spare.

The track itself was about 1¼ miles long, and ran parallel to the "Old Bedford Drain" in Earith.

The villagers were very annoyed when the project was scrapped.

V. J. Wood,
Earith,
Cambs.

Mr. Hope replies . . .

The machine and short length of track I saw were definitely in a field at Cranfield—I found them while killing time before a trip on the Goodyear airship that landed there a few years ago. I took photographs and still have the negatives buried somewhere in my files.

I met Prof. Laithwaite on a TV programme recently and it was he who told me of the scrapping etc. So perhaps there were two prototypes?

Incidentally at Cranfield (in a hanger) I also found the old TSR2 prototype.


Dynamo back-up

I read and enjoy your magazine every month and I have recently constructed the "Dynamo Back-up" published in your September '77 issue.

One problem I encountered was that my dynamo system used an earth return, and the dynamo and lamp housing was designed accordingly. For this reason, it was necessary to isolate either the lamps or the dynamo from the frame, when adding the back-up.

Also the modification shown below uses a D.P.D.T. three position slide switch instead of a 2-way toggle switch, to allow the back-up to be completely bypassed if desired.

A. Hearne,
Co. Waterford,
Eire.

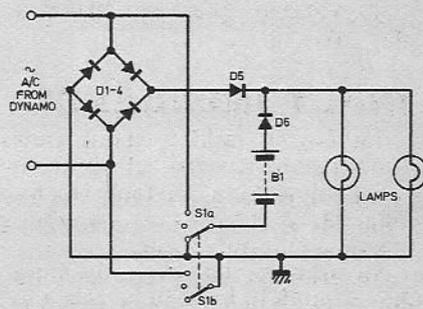

The above circuit suggested by Mr. Hearne has not been tested by us.

BOOK REVIEWS

THE FABULOUS PHONOGRAPH 1877-1977

Author Roland Gelatt

Price £6.50

Size 215 × 145mm 349 pages

Publisher Cassell

THE new world was the birthplace of the gramophone, so the American title is appropriate. A vast industry was producing cylinder and disc talking machines long before Europe got involved. Yet after a promising start, a demise set in when the novelty wore off what was chiefly seen as a rather frivolous toy. Here European countries came to the rescue. The artistic contributions made by the Old World revitalised the whole business of recorded music and elevated the gramophone to the status of a serious musical instrument where it is firmly established today.

All this we learn through this absorbing story, where commercial rivalry, not only in invention and technical development, but in wooing international

artists and orchestras, is a dominant theme. Many instruments were involved in the battle over the years. Many companies entered the arena; many subsequently disappeared or changed beyond recognition through amalgamations during these exciting 100 years.



The Fabulous Phonograph is a second revised edition of a work hailed as a classic upon its first appearance in 1955. This latest edition has been brought out to coincide with the centenary of the phonograph, invented by Edison in 1877.

The first 300 pages cover the story from first beginnings (1877) up to 1955, with an approximately even balance between technical, commercial and artistic development. The technical evolution of the phonograph is described through American eyes, and British activities ignored. Thus the word "Radiogram" does not appear in the book, and those ingenious mechanical devices for changing records get no mention.

The last 35 pages cover the 22 years from 1955 to the present, and in view of the tremendous changes brought about in this period (largely through electronic achievements) the space allocated is sadly disproportionate to the rest of the book.

Thus the introduction of the microgroove long playing record, stereo (and now quadrophony), and the phenomenal success of pop music since that first recording by Presley in 1956, receive rather summary treatment, considering their great impact on technical and, even more especially, upon social affairs.

F.E.B.

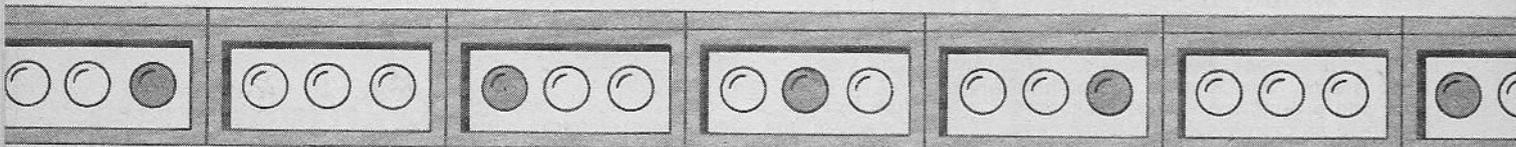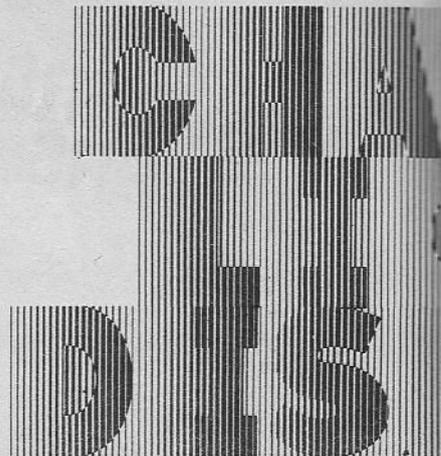

MOST disco's and "pop" bands today are equipped with lighting effects such as sound-to-light, strobe, colour wheel, ultra-violet light, etc. This article describes a further effect that is now in use on the disco/band scene. It is a four-phase sequential display or Chaser Light Display.

The unit to be described has speed, direction, freeze and effect controls and is capable of handling one kilowatt per channel (but with limitations—see later).

FOR GUIDANCE ONLY

ESTIMATED COST OF COMPONENTS
£15 excluding case and Light Boxes

ferric chloride. Care needs to be exercised when handling this chemical as it is very corrosive. Avoid contact with the skin. A photographic plastic or enamel tray is a suitable container for holding the etchant.

The board should be laid face down and the contents of the tray constantly agitated for speedy results. Inspect the board from time to time using a pair of tweezers to hold the board, and when all the unwanted copper has been removed, thoroughly wash the board


**START
HERE FOR
CONSTRUCTION**

PRINTED CIRCUIT BOARD

Most of the components are mounted on a piece of printed circuit board, the full-size pattern of which is shown in Fig. 1. A Dalo etch resist pen can be used for most of this but rub-down transfer pads are recommended for the component connection points.



When the etchant resist is completely dry the board should be placed in a saturated solution of

HOW IT WORKS...

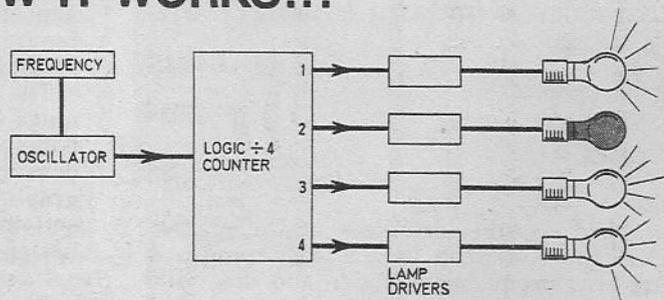

The variable frequency oscillator produces a train of square wave pulses suitable for inputting to a TTL logic section which acts as a divide by 4 counter with four independent outputs. The state of each output (high or low, logic 1 or 0) is dependant on the number of pulses received from the oscillator.

At any one time there are three high outputs (four distinct arrangements) or this can be reversed by switching to produce a single high and three low states. A high output on a particular channel turns on the lamp drivers and causes the bulbs of that channel to light. The net result from a train of input pulses is a constantly changing flashing light system, which when correctly arranged will produce a "running" light effect.

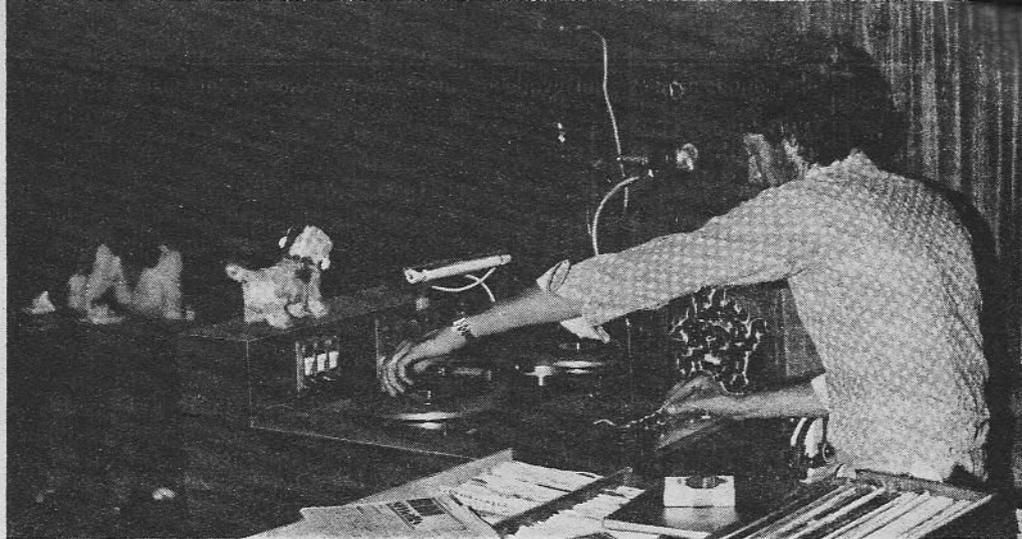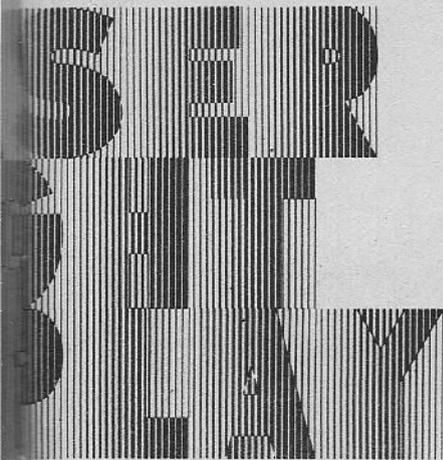

By J. McBride

under running water. Remove the etch resist using a scouring pad and then drill the board to suit the component lead-out wires. Drill 4BA clearance holes to provide fixing to the case and then assemble the components as shown in Fig. 4. Note the use of Veropins for connection to case mounted components.

TRIAC HEATSINKS

The next stage of construction concerns the triacs. These need to

be mounted on heat sinks, each one isolated from the other and all isolated completely from the case. To accomplish this the four heatsinks are mounted on a sheet of Paxolin that is bolted to the back panel with spacers interposed between board and back panel; Fig. 3 gives details and lead-out identification of the TIC225D triacs specified.

CASE AND WIRING

The case used in the prototype

was an integral aluminium base/front/rear panel type with removable fabric covered steel lid. This case is available from many sources and has a type number RB5 with dimensions 280 x 190 x 90mm although any similar size will do.

Begin by drilling the case to accept the case mounted components, including the p.c.b. and triac/heatsink assembly and then fix all these in place and wire up according to Fig. 4.

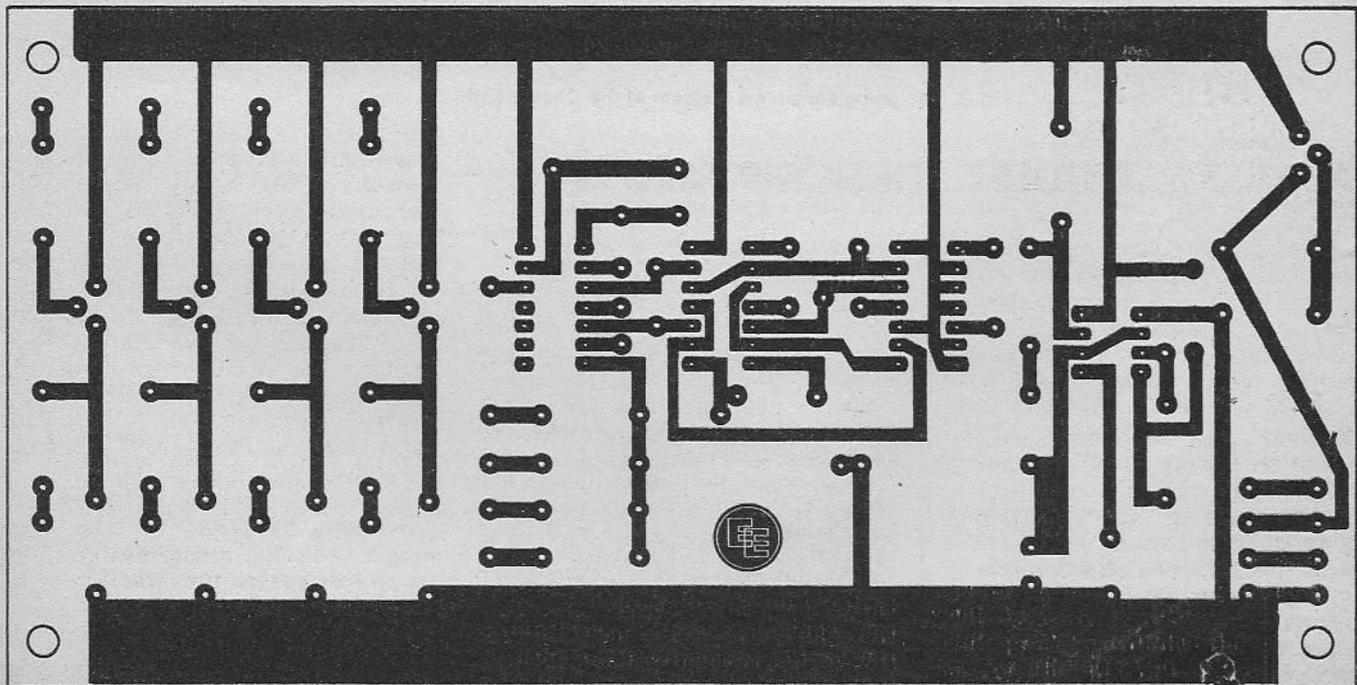


Fig. 1. The copper pattern to be etched on the Chaser Light Display component board, shown full size from copper side.

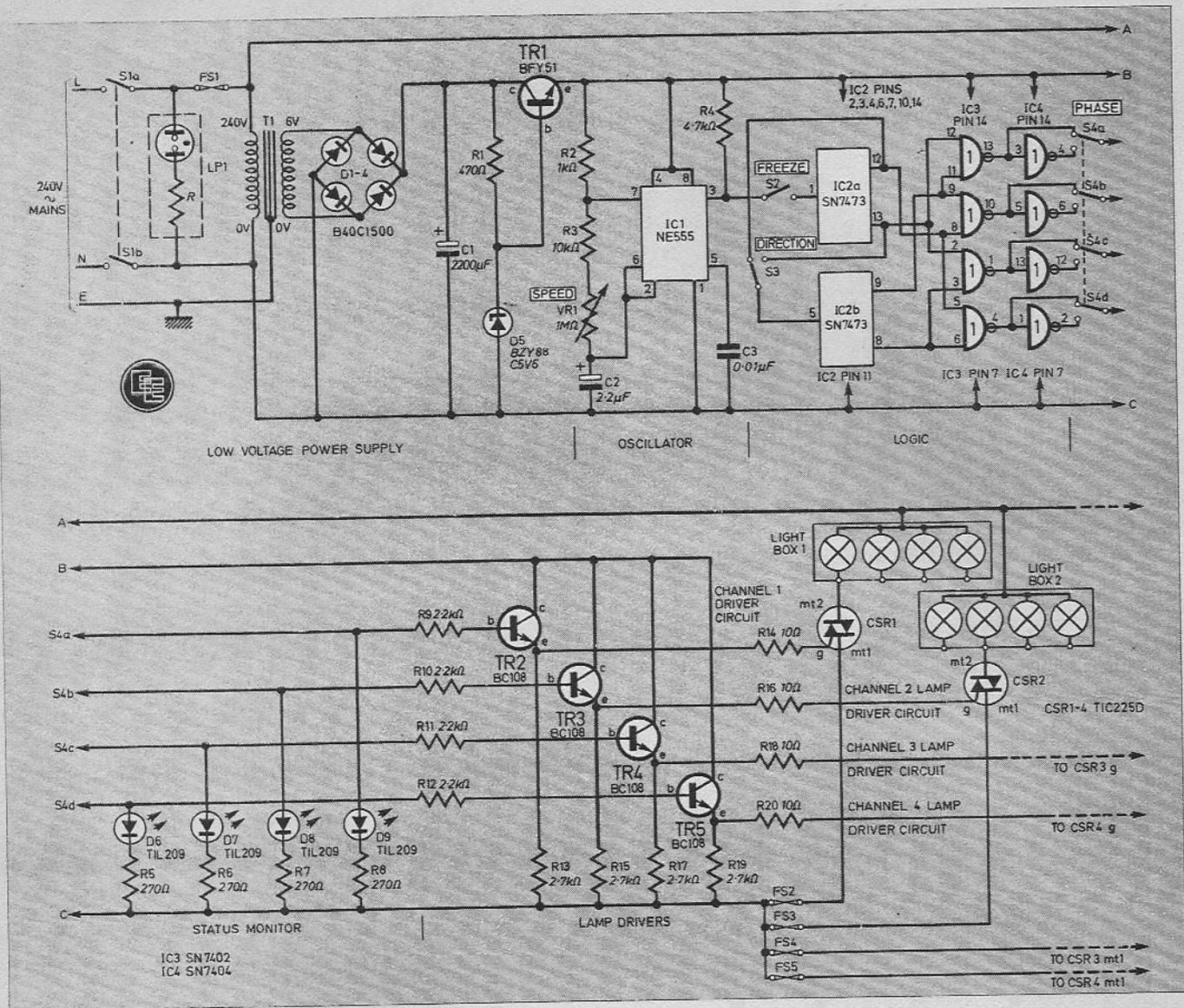


Fig. 2. The complete circuit diagram of the Chaser Light Display.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Chaser Light Display is shown in Fig. 2, and can be seen to consist of five distinct sections: a mains derived low voltage power supply unit (Zener stabilised); a square wave oscillator (clock oscillator); a logic coding section; an l.e.d. status monitor; power switches.

Mains voltage enters the unit and is stepped down by T1. Full-wave rectification is achieved by means of the diode bridge D1 to D4 and the resulting pulsed waveform smoothed by reservoir capacitor C1. The resulting d.c. voltage is placed across the Zener diode

and its series resistor.

The Zener voltage, 5.6 volts, is coupled to the base of TR1 which turns on the latter and makes available at the emitter a voltage level of 5 volts (since the base/emitter junction drops 0.6 volts). This level is required for the TTL logic i.c.s.

The oscillator consists of IC1 which is a 555 timer i.c. wired as an astable multivibrator. Output is at pin 3 which is normally at zero volts when the voltage on C2 is less than two-thirds the positive supply voltage level.

The capacitor is charged up via R2, R3 and VR1 and when the vol-

tage on the positive plate reaches two-thirds the supply rail, the internal circuitry of the i.c. switches and causes pin 3 to be at 5 volts. At the same time a discharge path is placed across C2 consisting of R3 and VR1 causing the voltage level on the positive plate to reduce. When this reaches one-third the supply line, the internal circuitry resets and pin 3 drops to zero volts and the capacitor begins to charge up again to repeat.

The output on and off times are governed by VR1, i.e. the frequency of the oscillator can be varied by means of VR1.

LOGIC CIRCUITRY

The output of IC1 is fed to the logic circuitry composed of IC2 and

IC3, two flip-flops (connected in series) feeding four NOR gates respectively interconnected to form a divide-by-four non-overlapping sequential outputs. To help understand the action of this section, consider Table 1, the truth table for the two flip-flops connected in series.

It can be seen that two 1's (high output) and two 0's (low output) are obtained at every phase. The four outputs are cross-coupled to feed four NOR gates. A NOR truth table is shown in Table 2. We can see that the output is always zero except when the two inputs are low simultaneously. The composite truth table is shown in Table 3 and shows that only one gate is producing a high output at any one time and each gate producing such an output level every fifth pulse.

Switch S2 can be operated to hold the logic section output at the last clock pulse state. In this position the lights are no longer "running". Operation of S3 changes the direction of apparent motion.

The four NOR gates are each directly coupled to the inputs of four inverters. A high or low input to these gates (as their name suggests) causes a low or high output respectively. A switch at each output allows this gate to be bypassed if desired.

If all switches are in the positions shown, one channel will be on at each phase; if all the switches are operated one channel will be extinguished at each phase. The latter gives the impression of lamps moving along in groups of three.

The outputs from the logic gates are monitored by the four l.e.d.s D6 to D9 which mimic whatever the main lamps are doing.

TRIAC DRIVERS

Transistors TR2 to TR5 act as TTL-triac interfaces and are turned on when a high state exists thereby causing a voltage step at the emitter to feed the triac gates through gate current limit resistors R13, 15, 17, 19. The triac is turned on when it receives a positive voltage at its gate which then causes the main lamps to be lit. The lamps are extinguished when the triac turns off and this results when the gate voltage/current is reduced below a threshold level when TR2 (3, 4 or 5) is turned off by its base receiving a logic zero (low state).

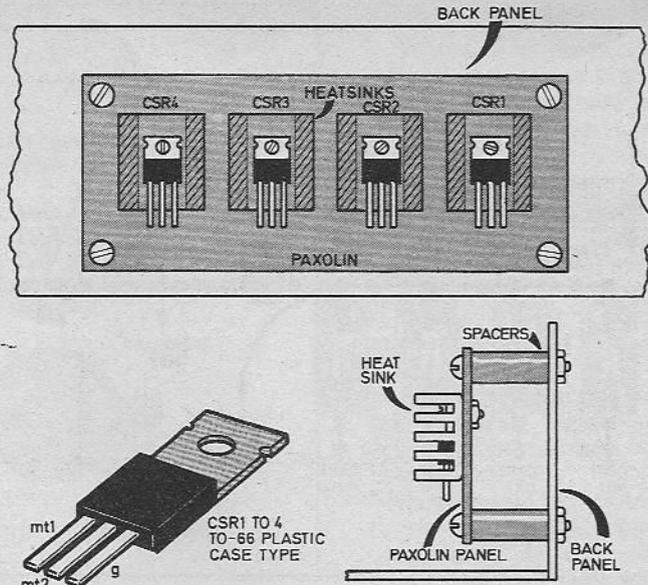


Fig. 3. Details of the triac mounting arrangement and heatsink fittings. Also shows pin configuration for the specified triacs.

Connection to the "light boxes" (or box) is made via a terminal block fitted to the rear panel of the case. Since high currents will be flowing through this terminal to the bank of light boxes, a heavy duty block is required. Use one rated at 15 amps or more to cover all eventualities.

Each terminal block will need to hold four cables (if four separate light boxes are used) or a number equal to the number of light boxes. Wiring details between the master unit and each box is shown in Fig. 5. Use 5 amp wiring to interconnect the lamps and each box to the master.

Table 1: Truth table for two flip-flops wired in series


Clock	Q _A	Q̄ _A	Q _B	Q̄ _B
0	1	0	1	0
1	1	0	1	0
0	0	1	1	0
1	0	1	1	0
0	1	0	0	1
1	1	0	0	1
0	0	1	0	1
1	0	1	0	1

Table 2: Truth table for a NOR gate

Input 1	Input 2	Output
1	1	0
0	1	0
1	0	0
0	0	1

Table 3: Composite truth table for two flip-flops in series feeding four NOR gates followed by four inverters

Clock	Q _A	Q̄ _A	Q _B	Q̄ _B	Gate Outputs				Gate Outputs			
					G3a	G3b	G3c	G3d	G4a	G4b	G4c	G4d
0	1	0	1	0	0	1	0	0	1	0	1	1
1	1	0	1	0	1	0	0	0	0	1	1	1
0	0	1	1	0	0	0	0	1	1	1	0	0
1	0	1	1	0	0	0	1	0	1	1	0	1
0	1	0	0	1	0	0	0	1	1	1	0	0
1	1	0	0	1	0	0	1	0	1	1	0	1
0	0	1	0	1	0	0	1	0	1	1	0	1
1	0	1	0	1	0	0	1	0	1	1	0	1

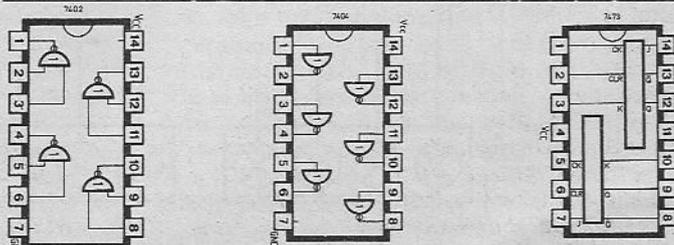

Pin and internal details of the three logic i.c.s employed in the Chaser Light Display.

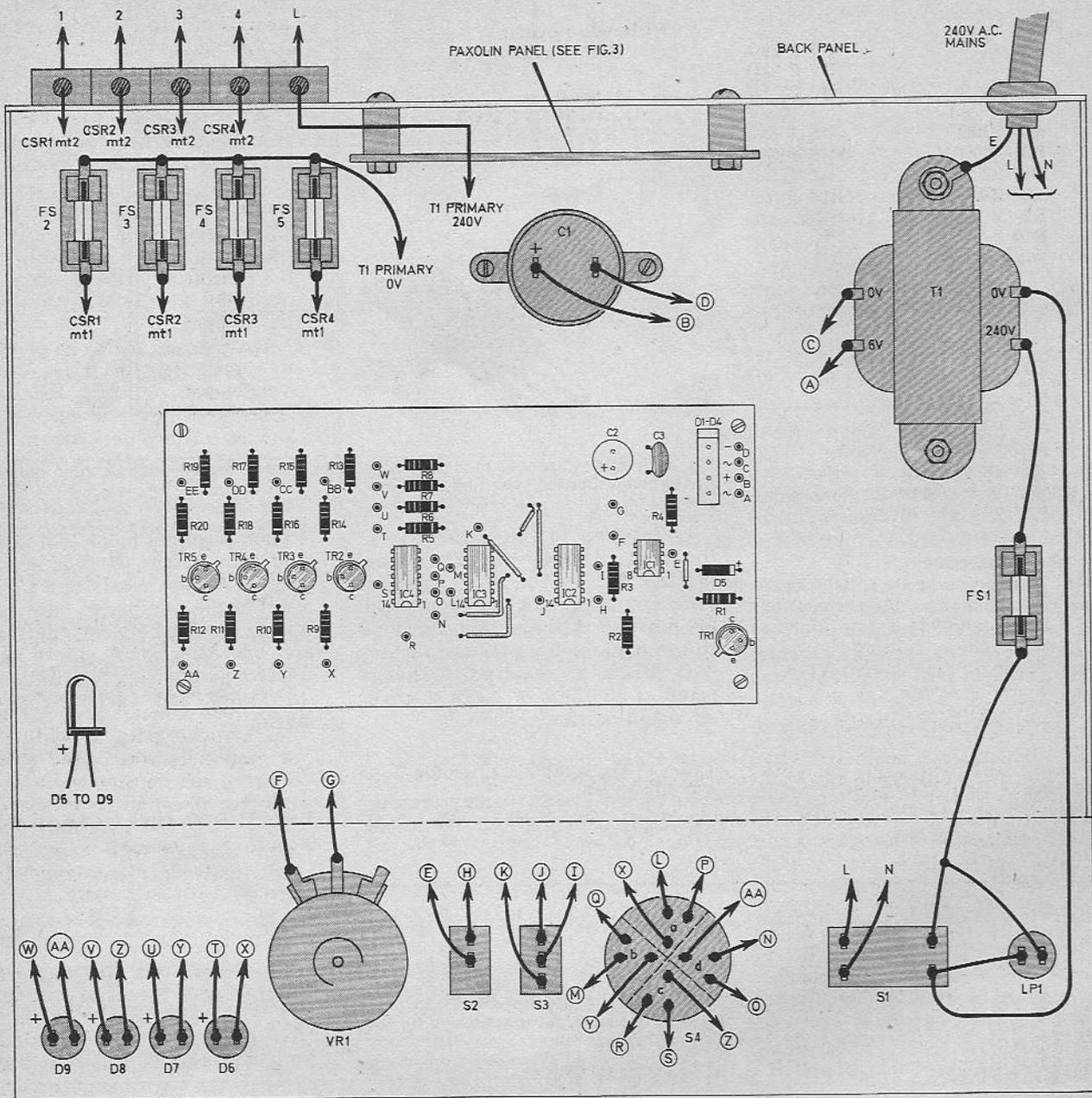


Fig. 4. The layout of the components and board within the case and complete wiring up details of the main unit.

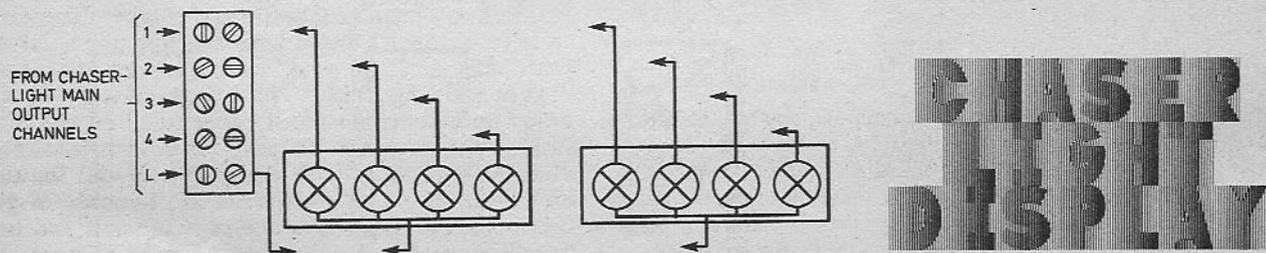


Fig. 5 Light box wiring details to the main unit.

COMPONENTS



Resistors

R1 470 Ω	R11 2.2k Ω
R2 1k Ω	R12 2.2k Ω
R3 10k Ω	R13 2.7k Ω
R4 4.7k Ω	R14 10 Ω
R5 270 Ω	R15 2.7k Ω
R6 270 Ω	R16 10 Ω
R7 270 Ω	R17 2.7k Ω
R8 270 Ω	R18 10 Ω
R9 2.2k Ω	R19 2.7k Ω
R10 2.2k Ω	R20 10 Ω

All $\frac{1}{4}$ watt carbon $\pm 10\%$

Potentiometer

VR1 1M Ω carbon lin.

Capacitors

C1 2200 μ F 10V elect.
C2 2.2 μ F 6V elect.
C3 0.01 μ F plastic or ceramic

Semiconductors

D1 to D4 B40C1500 1.5 amp bridge rectifier
D5 BZY88C5V6 5.6V 400mW Zener diode
D6, 7, 8, 9, TIL209 red light emitting diode (4 off)
IC1 NE555 timer i.c.
IC2 SN7473 Dual J-K flip-flop
IC3 SN7402 Quad 2-input NOR gates
IC4 SN7404 Hex inverter
TR1 BFY51 silicon npn
TR2, 3, 4, 5 BC108 silicon npn (4 off),
CSR1, 2, 3, 4 TIC225D

Miscellaneous

T1 mains primary/6 volt 500mA secondary
LP1 panel mounting mains neon
S1 double-pole on/off rated at 10A 250V a.c.
S2 single-pole on/off
S3 single-pole double throw
S4 4-pole 2-way
FS1 1 amp 20mm
FS2, 3, 4, 5 5 amp 20mm (4 off)
Printed circuit board size 178 \times 78mm; 20mm chassis mounting fuse-holders (5 off); fixing clip for C1; metal case type RB5 or similar (280 \times 190 \times 90mm); solder tag; 5-way 15 amp terminal block; heatsinks type Redpoint TV-4 or similar for triacs (4 off); Paxolin panel for mounting heatsinks; 4BA fixings and spacers; mains cable; rubber grommet.

See
**Shop
Talk**
page 262

USE OF CHASER

When used properly the chaser will give fascinating light-shows. The lights are best arranged in groups of four. Each fourth colour being the same. Five groups of four along the bottom of a stage gave the best effect to date.

Alternatively, four floodlights can be used to change the colour or the ambient lighting in a hall. A totally different display can be made from 4, 8, 12 or as many multiples of four as you wish of low powered bulbs arranged in concentric circles. These would need accurate positioning to give the best effect.

Care should be taken at all times to ensure that the triacs are never overloaded or over heated. The triacs specified will take 6 amps, but here a problem arises. A standard 13 amp outlet will not allow three channels (the maximum at any one time) to be used to full capacity. Check before the venue that even this can be supplied as some halls have very poor mains supply.

No suppression has been fitted to this unit for the simple reason that no interference was detectable when switching over 1 kilowatt per channel (only one channel loaded) using a wide variety of amplifiers when used at even a quarter of normal volume level. Interference on a common, un-suppressed 100 watt amplifier was about 250mW with all volume and tone controls fully advanced. \square

BOOK REVIEWS

MODEL ENGINEERING

Author Martin Evans

Price £7.95

Size 245 \times 190mm 210 pages

Publisher Pitman

THIS is a handsome book incorporating a lavish selection of photographs of models with locomotives predominating but including trams, tractors, cars, boats and even clocks. These excellent examples of the model maker's craft very nearly succeed in overshadowing the text which does nevertheless occupy 121 out of a total of 210 pages.


On practical matters there are chapters devoted to the home workshop and essential hand tools; and the more specialised machines used in model engineering: the lathe, the drilling machine, and the grinding machine. The text is aimed at the newcomer and is well illustrated with line diagrams and with photographs of typical equipment.

Other practical matters discussed include castings and materials; and the joining of metals (six different methods—from bolts and studs, to welding are explained). There is a glossary of engineering terms.

The photographs alone could well entice a reader to take up model-making as another hobby. If so, the remainder of this book will give him the essential insight into the field of light engineering. We suspect many an electronics constructor will find the prospect fascinating and not an unnatural transition for one already conversant with electronic model making. In any event, for the electronics constructor in general this book could prove a useful extension and back-up to other works of reference he may possess dealing with workshop matters.

F.E.B.

A.C. METER CONVERTER

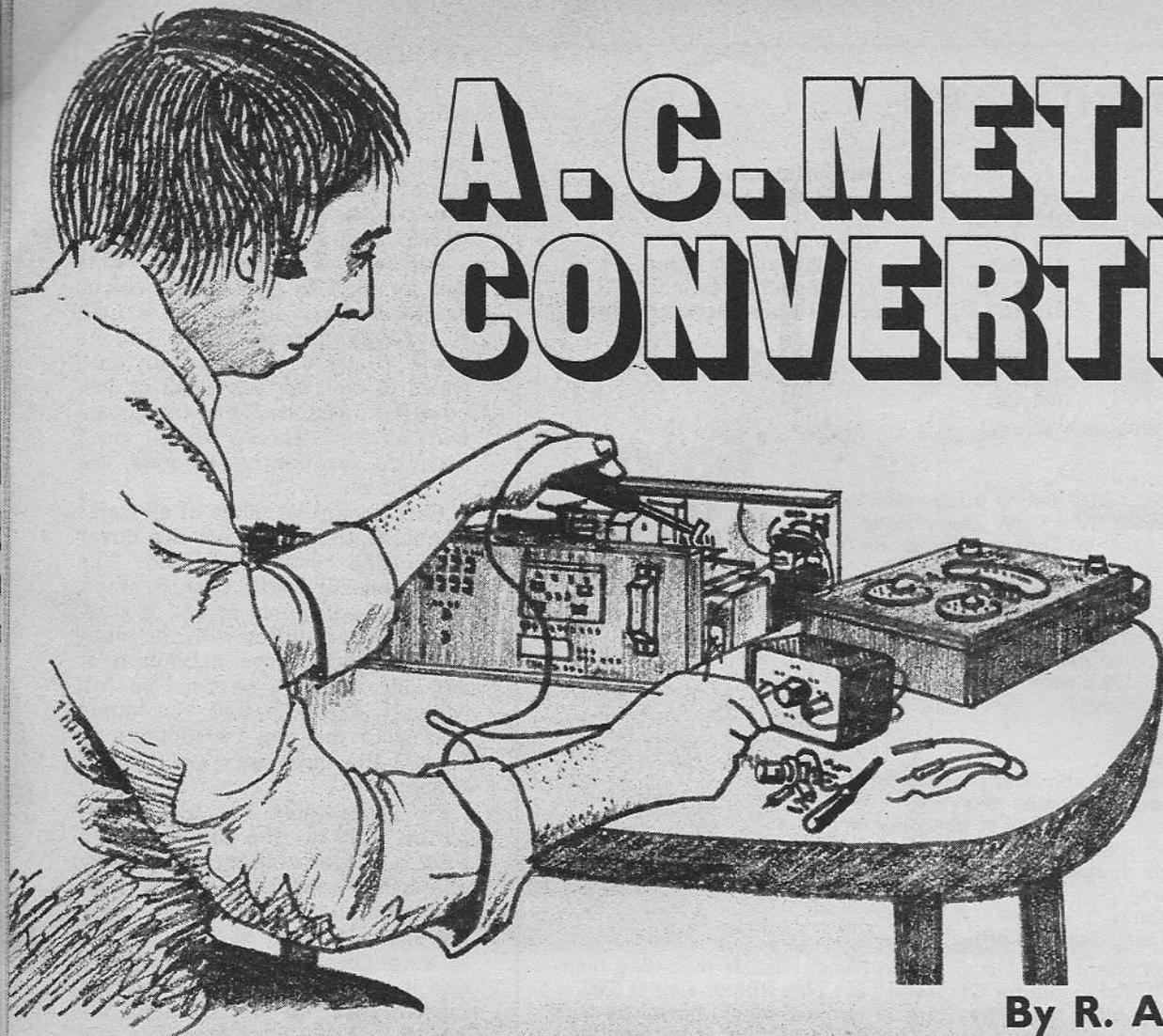

By R. A. Penfold

INTRODUCTION

WHEN working in the field of audio equipment, one of the most useful pieces of test equipment to have in the workshop is an a.c. millivoltmeter. This is needed in order to check most of the parameters of an amplifier and is also very useful for general servicing and testing purposes.

Many electronics enthusiasts, especially beginners, may be put off building an audio millivoltmeter by the cost and complexity of a good quality instrument. The unit which forms the subject of this article is designed to provide a low cost alternative to a millivoltmeter, and it can be used in conjunction with any multimeter having an a.c. range of about 5 or 6 volts f.s.d. or less.

The basic unit is really just an amplifier which has two switched

voltage gains of 10 (20dB) and 100 (40dB). Thus, if it is added ahead of a multimeter switched to its 5V a.c. range, this set-up will have an input sensitivity of 500mV with the amplifier in the x10 mode, and 50mV with it in the x100 mode. It can therefore be used to convert a multimeter into a millivoltmeter.


The number of ranges obtained and the accuracy of those ranges is largely dependent upon the specification of the multimeter used. The author's instrument has low a.c. voltage ranges of 1.5, 3, and 5V f.s.d., which provides six ranges when the converter is added (15, 30, 50, 150, 300, and 500mV f.s.d.). Accuracy has proved to be more than adequate for all normal requirements.

There are other possible uses for the unit. For instance, it can be added ahead of the Y-input of an insensitive oscilloscope in order to enable low level audio measurements to be made.

START
HERE FOR
CONSTRUCTION

The prototype is constructed in an A.B.S. case with a steel front panel, and the unit is constructed in such a way that it is tailored to fit this particular case. It is therefore advisable to use the specified case, even though the unit could be adapted to fit other cases of a similar or larger size.

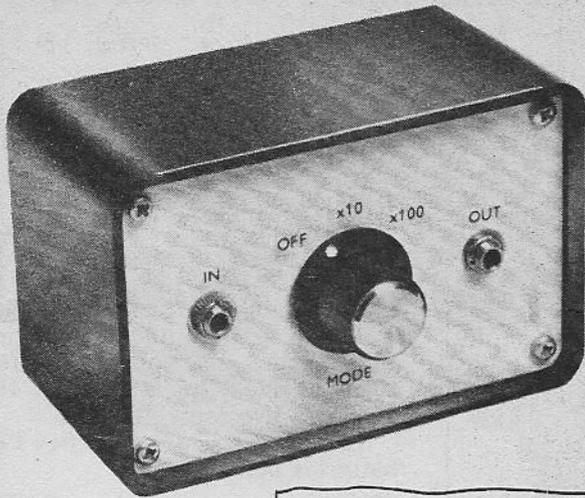The front panel is drilled with a central 10mm diameter hole to take S1, with SK1 to the left of



A.C. METER CONVERTER

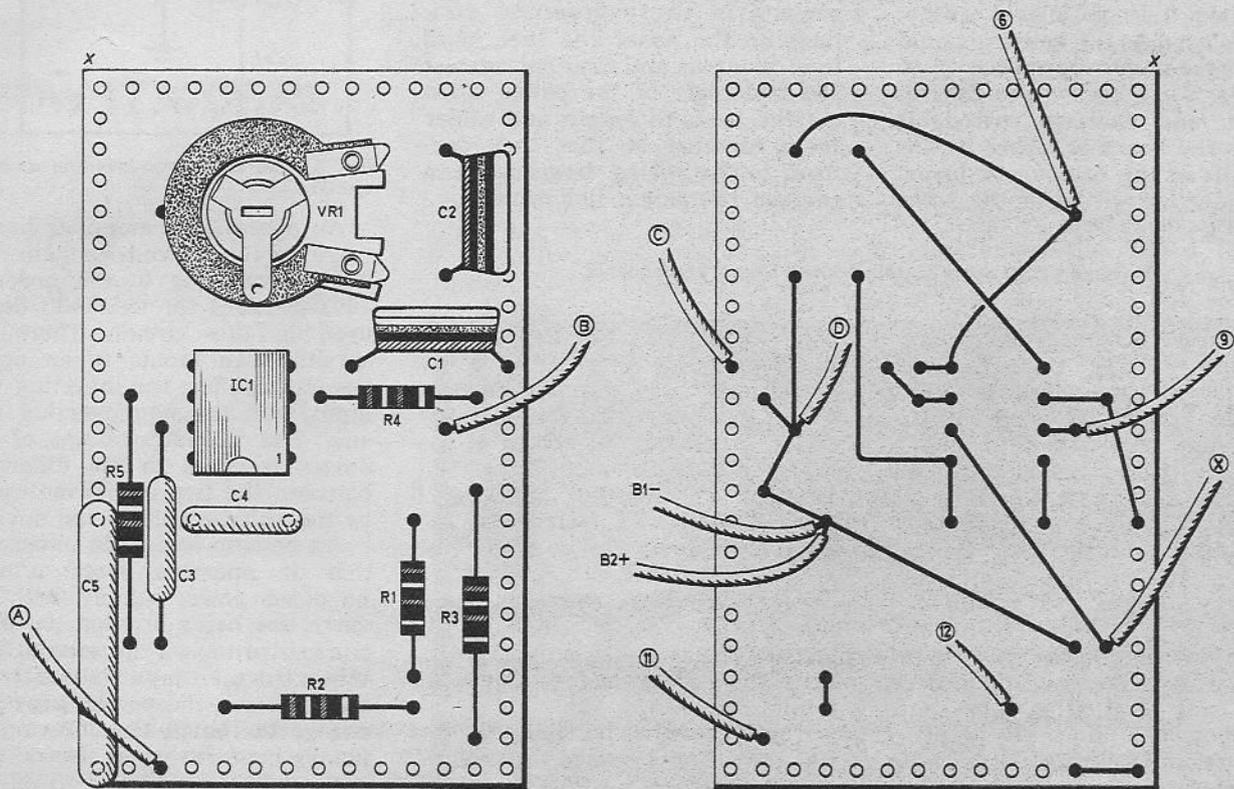
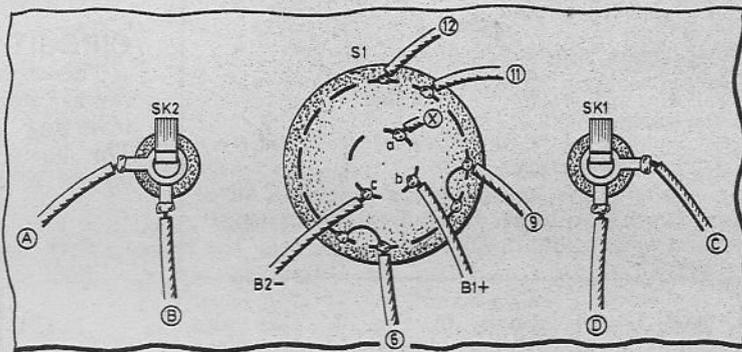


Fig. 3. Component layout and wiring for the plain perforated board. The wiring for the front panel components S1, SK1 and SK2 are also shown.

COMPONENTS

Resistors

- R1 18 Ω
- R2 1.8k Ω 1%
- R3 20k Ω 1%
- R4 1M Ω
- R5 180k Ω 1%

All resistors are carbon $\frac{1}{4}$ W \pm 5% except where stated

Potentiometers

- VR1 2.2M Ω standard horizontal preset

Capacitors

- C1 47nF
- C2 100nF
- C3 100nF
- C4 3.3pF ceramic
- C5 470nF

All capacitors are polyester except where stated

Integrated Circuit

- IC1 748C 8 pin d.i.l.

Miscellaneous

- S1 4-pole 3-way rotary wafer switch
- B1, 2 9V PP3 batteries
- SK1, 2 3.5mm jack sockets
- Perforated board 0.1 inch matrix 23 \times 14 holes; plastic case type M2 (Doram); small round knob; two battery clips; two 3.5mm jack plugs; wo crocodile clips; connecting wire; solder.

See
**Shop
Talk**

page 262

this and SK2 on the right. Both sockets are 3.5mm jack types and require a 6mm diameter mounting hole.


A plain 0.1-inch matrix s.r.b.p. panel is used as the constructional basis of the circuitry, and has 23 \times 14 holes. Use a hacksaw to cut this to size, and exercise reasonable care as the board is rather brittle.

Details of the component layout and underside wiring of the panel

are shown in Fig. 3. This also shows all the other wiring of the unit.

Start by mounting all the components in the appropriate positions on the panel and then bend their leadouts and tags flat against the underside of the panel. Then cut the leads to length and solder them together so that they conform to the wiring diagram. Then connect the single link wire.

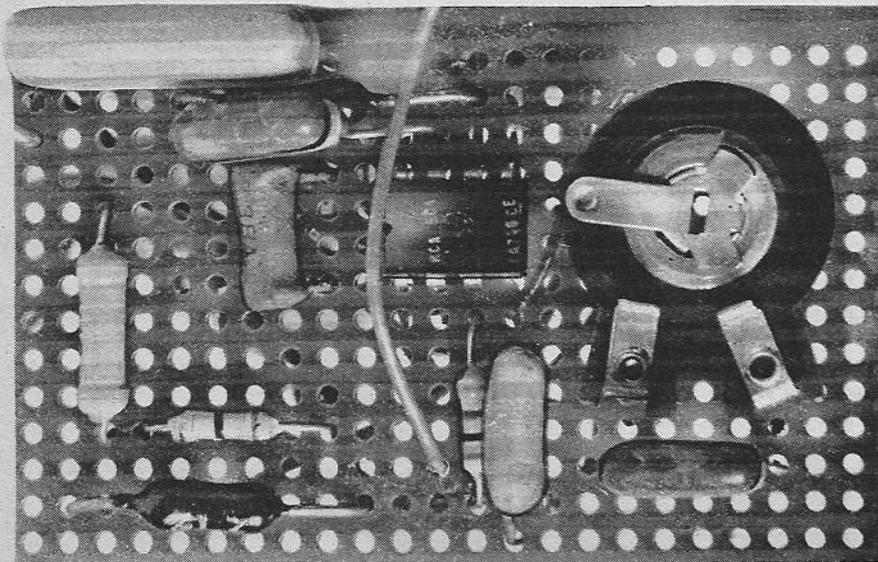Finished circuit board showing positioning of components.



Position the completed component panel between S1 and SK2 so that it has its component side facing SK2 with C5 immediately below SK2. Then wire the panel up to the rest of the unit using ordinary insulated connecting wire. The two connections to SK2 are taken to the component side of the panel and all others are made to the underside.

This is important, since the finished component panel is slotted into the appropriate set of guide rails in the case, and this effectively divides the interior of the case into two separate parts.

There is a space for the two PP3 batteries behind SK1.

CIRCUIT PRINCIPLES

The circuit uses a single operational amplifier i.c. in the non-inverting amplifier configuration. The basic non-inverting amplifier circuit is shown in Fig. 1.


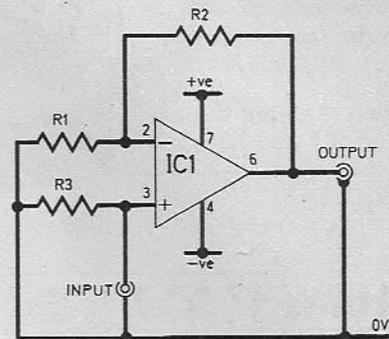


Fig. 1. The basic non-inverting amplifier circuit.

An operational amplifier has an extremely high voltage gain, this being something in the order of 100,000 times for the 748C device used in this circuit. There are actually two inputs to an operational amplifier; the inverting (-) input, and the non-inverting (+) one. The output voltage of the device is equal to the difference between the two inputs multiplied by the voltage gain of the device.

An op-amp is a little unusual in that it operates from a dual balanced power supply with the earth line being at what, in effect, is a centre tap on the supply lines. When the (+) input is positive of the (-) one, the output goes positive of the earth line. The output swings negative when the (+) input is negative of the (-) one.

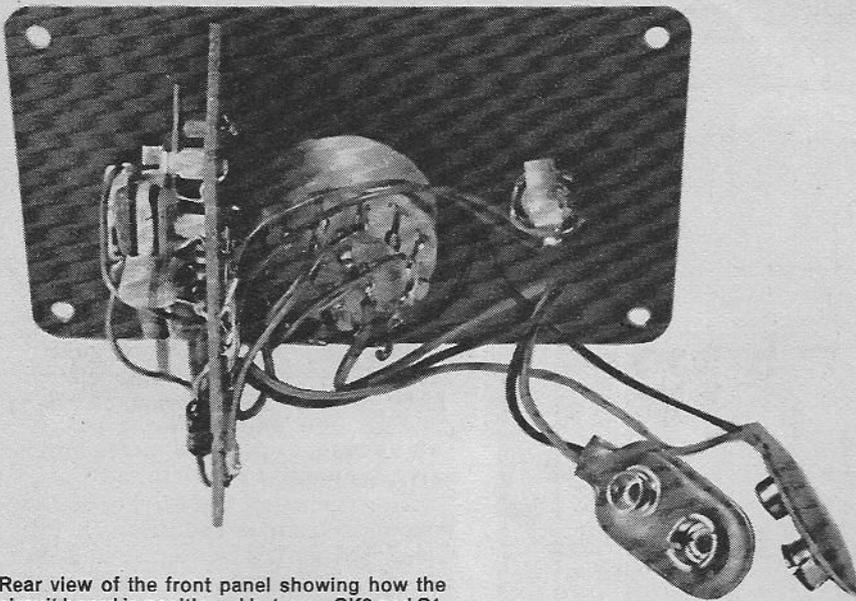Practical amplifier circuits which incorporate an op-amp rarely use the full voltage gain of the device



Rear view of the front panel showing how the circuit board is positioned between SK2 and S1.

(the "open loop voltage gain"), but use negative feedback to reduce the gain of the circuit as a whole to the required level. This gain is termed the "closed loop voltage gain".

In the skeleton circuit of Fig. 1, resistors R1 and R2 form the feedback network while R3 ties the

non-inverting input to the earth potential. Under quiescent conditions the circuit will balance itself with the inputs and the output at earth potential.

This is assured by the feedback action of the circuit. For example, due to the potential divider action across R1 and R2, the voltage at

FOR GUIDANCE ONLY


ESTIMATED COST OF COMPONENTS
£3.00
excluding case



Completed unit.

the negative input would be taken above that at the positive input if the output were to go positive for some reason. This would unbalance the inputs, causing the output to swing negative, back to earth potential.

HOW IT WORKS...

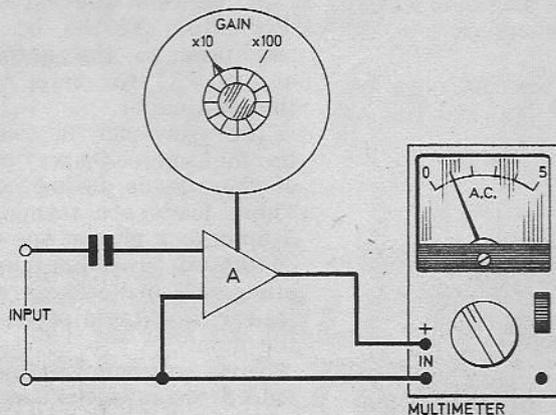

The A.C. Meter Converter is basically an a.c. amplifier with a switched gain of either 10 or 100. The gain being selected by varying the ratio of two resistors. Thus the set-up can be used to measure low level voltages which would be imperceptible using a standard multimeter alone.

For example, an input of 100mV would produce a very low reading with a multimeter switched to say, the 5V range. The converter could thus increase this value ten times to give a reading of 1V on the meter. This would produce 1/5 f.s.d. on the meter and would thus be easier to see. Naturally the reading is divided by ten to obtain the correct 100mV reading.

DETERMINATION OF GAIN

This negative feedback action also determines the closed loop voltage gain of the circuit. Assume that R2 has nine times the value of R1, and that a positive input of 1V is applied to the positive input. The inputs will be unbalanced and the output will swing positive, but only by as much as is necessary to balance the inputs once again.

In this case it must swing 10V positive so that there is 9V across R2 and 1V across R1. There will then be 1V at the (-) input, and the circuit will be balanced.

It should now be apparent from this that the gain of the circuit is set by the ratio of R1 to R2, and is ten times in this instance. The voltage gain of the circuit is equal to $R1 + R2$ divided by R1.

By giving R1 and R2 switched ratios of 1 to 9 and 1 to 99, an amplifier with gains of 10 and 100 can be produced.

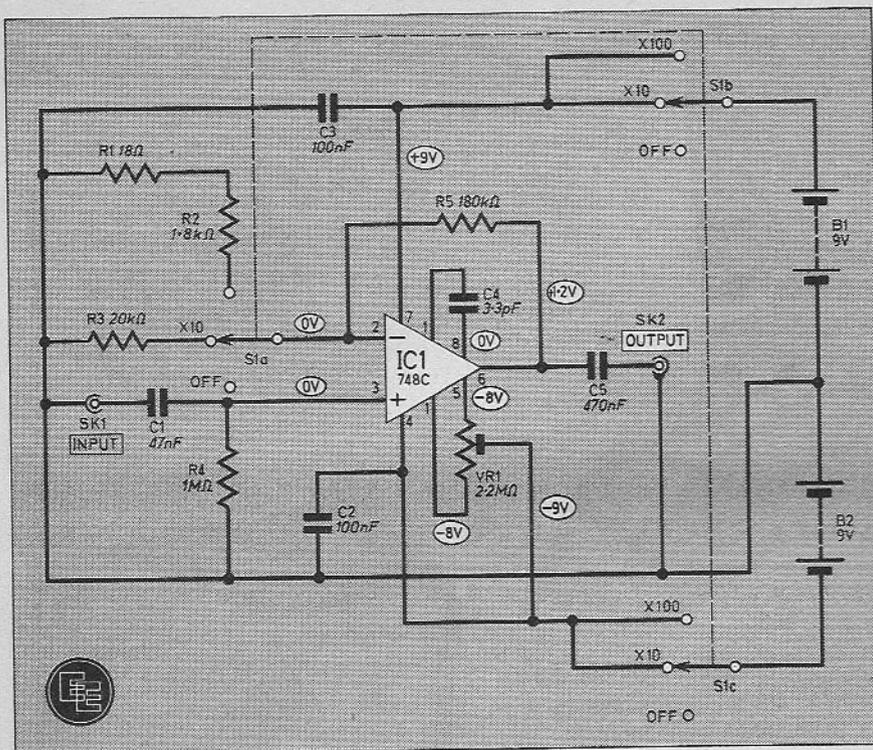


Fig. 2. The complete circuit diagram of the A.C. Meter Converter.

CIRCUIT DESCRIPTION

The circuit diagram of the A.C. Meter Converter appears in Fig. 2. When S1 is in the x10 position resistors R3 and R5 are the feedback network, and R1, R2, and R5 form this network with S1 set to the x100 position. With S1 in the first position the supply is disconnected, and the unit is switched off.

Applying negative feedback to the circuit produces an extremely high input impedance at the positive input, and the input impedance of the amplifier as a whole is approximately equal to the value given to R4. It is preferable for the unit to have a fairly high input impedance so that it only lightly loads the test circuit. Resistor R4 has therefore been given a value of 1 megohm.

Capacitor C4 is the compensation capacitor for the i.c., and this is

ADJUSTMENT AND USE


Variable resistor VR1 must be adjusted before the unit is ready for use. Start with the slider of VR1 at about the centre of its track and then switch the unit on with S1 in the x10 mode. Connect a multimeter set to read 10V d.c. f.s.d. between the earth line and the output of the i.c. (negative test prod to the output). Then adjust VR1 for zero reading on the multimeter.

The converter is connected to the multimeter by way of a couple of short leads during normal use. These leads are terminated in a 3.5mm jack plug at one end, and a couple of crocodile clips at the other. An ordinary screened test lead with suitable prods is used at the input.

This arrangement should provide a virtually flat frequency response over the audio frequency spectrum, and the unit has sufficient output voltage swing to properly drive a 5V f.s.d. meter over this frequency range. In the x100 mode though, the response and drive capability of the unit fall off quite rapidly above about 20kHz.

This presents no problems with the majority of tests. □

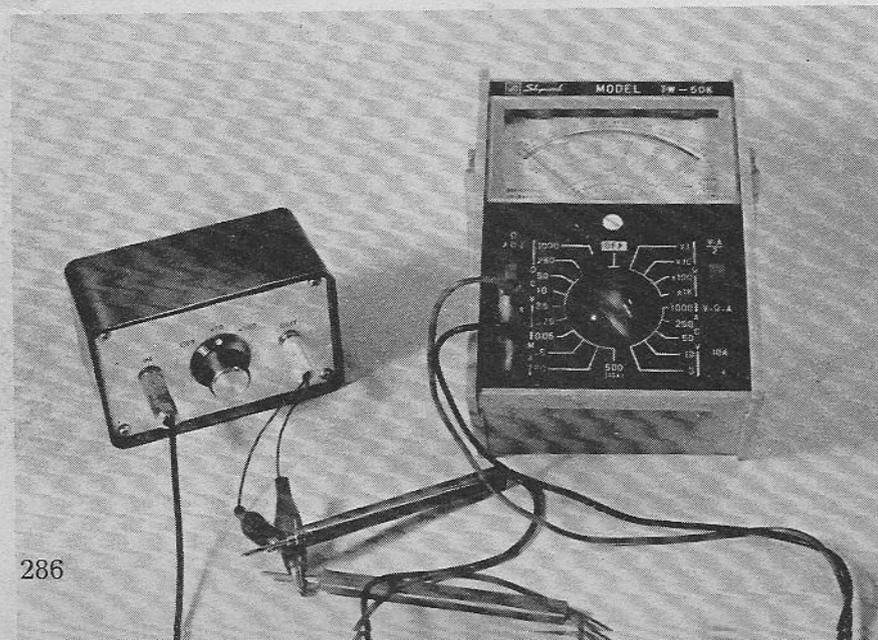The A.C. Meter Converter set-up ready for use.




needed to ensure stable operation of the device. C2 and C3 are supply decoupling components, and they also aid stability. C1 and C5 are the input and output d.c. blocking capacitors respectively.

Potentiometer VR1 is an offset null control, and is used to adjust the output of the amplifier to earth potential under quiescent conditions. In a theoretically perfect circuit this would not be required.

However, the 748C does not achieve perfection, and although theoretically no bias current should flow into either input of an op-amp, in practice a small current is needed by each input.


This can upset the biasing of the circuit causing a reduction in the available output voltage swing, or in an extreme case it could even prevent the circuit working altogether in the x100 mode. The offset null control enables compensation to be made for the inadequacies of the i.c., and ensures that good results are obtained.

next ★
month

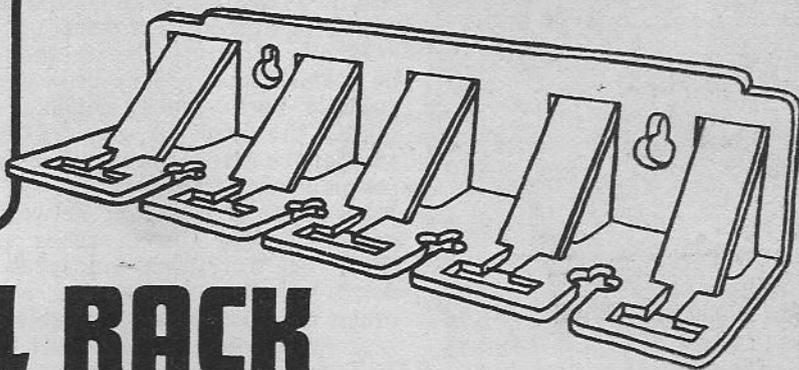

FREE TOOL RACK

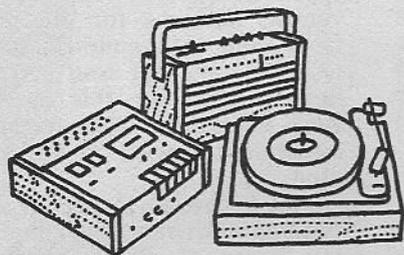Holds four small tools. A boon for every workshop.




THE AUDIOTEST

This useful piece of equipment comprises a loudspeaker and loudspeaker amplifier stage for testing radio receivers, record players, tape recorders, and pre-amplifiers having an output power not exceeding 10 watts.


A simple M. and L.W. radio tuner is incorporated as a speech and music source, and to provide entertainment in the workshop.

CATCH-A-LIGHT

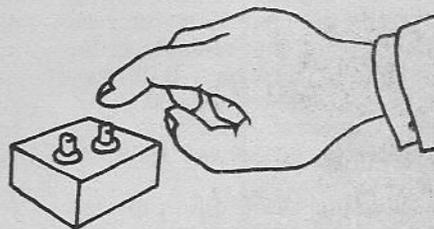A reaction game with a difference, based on six lamps numbered 1 to 6. The two players have to respond immediately a pair of lights stop blinking and switch on that one of their own pair which is nearest the stationary light. The first to do so is the winner, and there can be no argument since the winning light automatically blocks the opponent's lights.



C/R SUBSTITUTION BOX

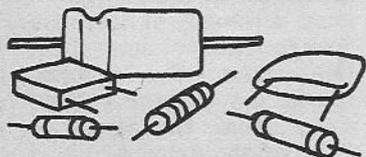

A simple project which will be found extremely valuable when designing and experimenting with circuits. Produces a variety of C and R values immediately "on tap".


**PLUS ALL THE
REGULAR FEATURES**

**Everyday
ELECTRONICS**



There is a tremendous demand every month for Everyday Electronics. Readers are strongly urged to place a firm order with their newsagent. Reliance upon casual purchase is unwise, because stocks may quickly be exhausted. So please remember, and take action now!

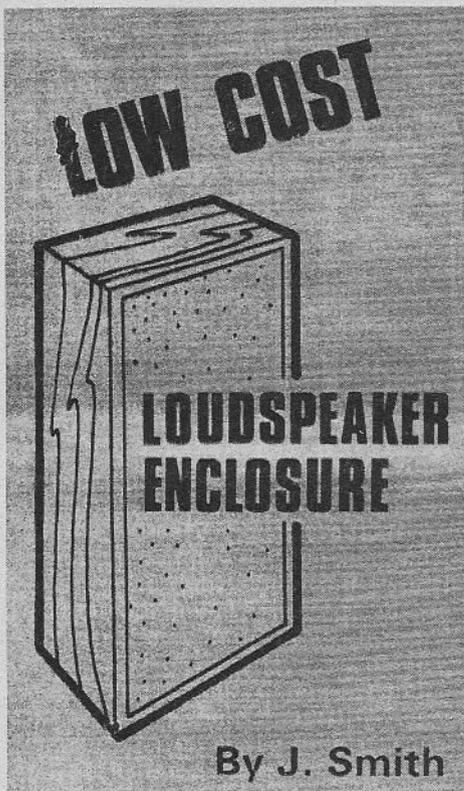**MARCH
ISSUE ON SALE
FRIDAY, FEBRUARY 17**



THERE are a large number of old 3 ohm loudspeaker drivers available from out-of-date radio and television receivers. It is possible to use these drivers with modern transistor amplifiers. The trick necessary is to use three in series.

By selecting three different size drivers and fitting them into a suitable cabinet a wide response range loudspeaker system is obtained having an impedance of 9 ohms. Very good results using simple stereo amplifiers, approximately 3 watts output, from designs published in this and other magazines are possible.

DRIVE UNIT SELECTION

Three different driver units should be selected to complement each other. All three should be fitted with back spider suspension (behind the cone) if possible. Front spider units tend to distort on loud signals.

First a bass unit is necessary; an 8in or elliptical driver will perform well here. Select a driver with a deep cone, because these perform better on bass signals. The ultimate performance obtained from the loudspeaker system depends a great deal on this bass driver unit, so look around for a good one.

The mid tones are well reproduced using either a shallow cone 8in, or a 6in unit; almost anything will do as long as it can handle the power (1 watt in each driver).

Finally the treble driver should be a small loudspeaker drive unit (with a back spider) capable of taking the load. In general, the smaller the driver the better it will reproduce high notes.

No filters or crossover networks are used. The system relies entirely on the three loudspeaker drive units complementing each other, the bass driver incapable of reproducing high notes, whilst the small treble driver will not be able to reproduce the bass. Of course, the middle drive unit reproduces a little of each.

This arrangement will make the hi-fi expert shudder, but the system works far better than most of the cheaper (under £50) stereo systems on the market.

CONSTRUCTING THE CABINET

The cabinet is very simple to build and may be any desired dimensions big enough to accommodate the loudspeaker drive units. Biggest is best for this design, so if you wish to impress friends with an elaborate enclosure by all means do so.

The principle constructional features of a cabinet to house 8in 6in and 3in units is shown in Fig. 1. The wood used is veneered chipboard for the enclosure and blockboard for the baffle.

First calculate the size of your baffle and remember that this gives the *inside* dimensions of the enclosure. Allow an extra 6mm clearance on the inside measurements to accommodate the loudspeaker cloth and construction errors.

The blockboard and chipboard can be purchased, ready cut, from your local do-it-yourself supplier, who will also cut the loudspeaker driver holes. Be absolutely sure that these holes are smaller than the driver to allow for fitting, but not so small that the cone touches the wood on its outward excursion.

CORNER BLOCKS

The "waste" from these holes is used to make the corner pieces in the enclosure. The optional hole in the baffle board is not cut until

after the unit is tested and is only of interest to those who wish to make a pseudo reflex cabinet.

The corner pieces of the enclosure are first screwed to the chipboard and the whole unit temporarily assembled to see that it fits together, persons fitting a back must allow for this when they position the rear corner brackets. Once satisfied that the unit will fit nicely together take it apart and reassemble the enclosure using Evo-Stick resin woodworking adhesive to join the chipboard and corner pieces.

FINISHING OFF

Finally finish the exposed chipboard ends with "iron on" wood veneer, obtained for this purpose from your do-it-yourself supplier. (An ordinary flat iron set to low heat is used for this operation.) Keep everything clean during construction and wipe off any surplus glue.


Finish the enclosure by lightly rubbing with sandpaper and apply two coats of clear polyurethane varnish, allowing 24 hours between coats. With reasonable care the finished enclosure should look very attractive.

FINISHING BAFFLE

Anyone wishing to make a pseudo reflex cabinet should follow the instructions given later, but those wishing to have an open back, or a back with holes cut into it may finish the baffle board. First glue a sheet of 3mm or 6mm sponge rubber across the front. Use ordinary Evo-Stick, and when this is dry cut the sponge rubber away from the round holes in front of the drivers.

Next stretch a piece of loudspeaker cloth right over the unit and tack to the rear of the baffle board. Stretch this cloth very tightly over the sponge rubber securing with drawing pins before tacking, otherwise it will sag and not look very professional.

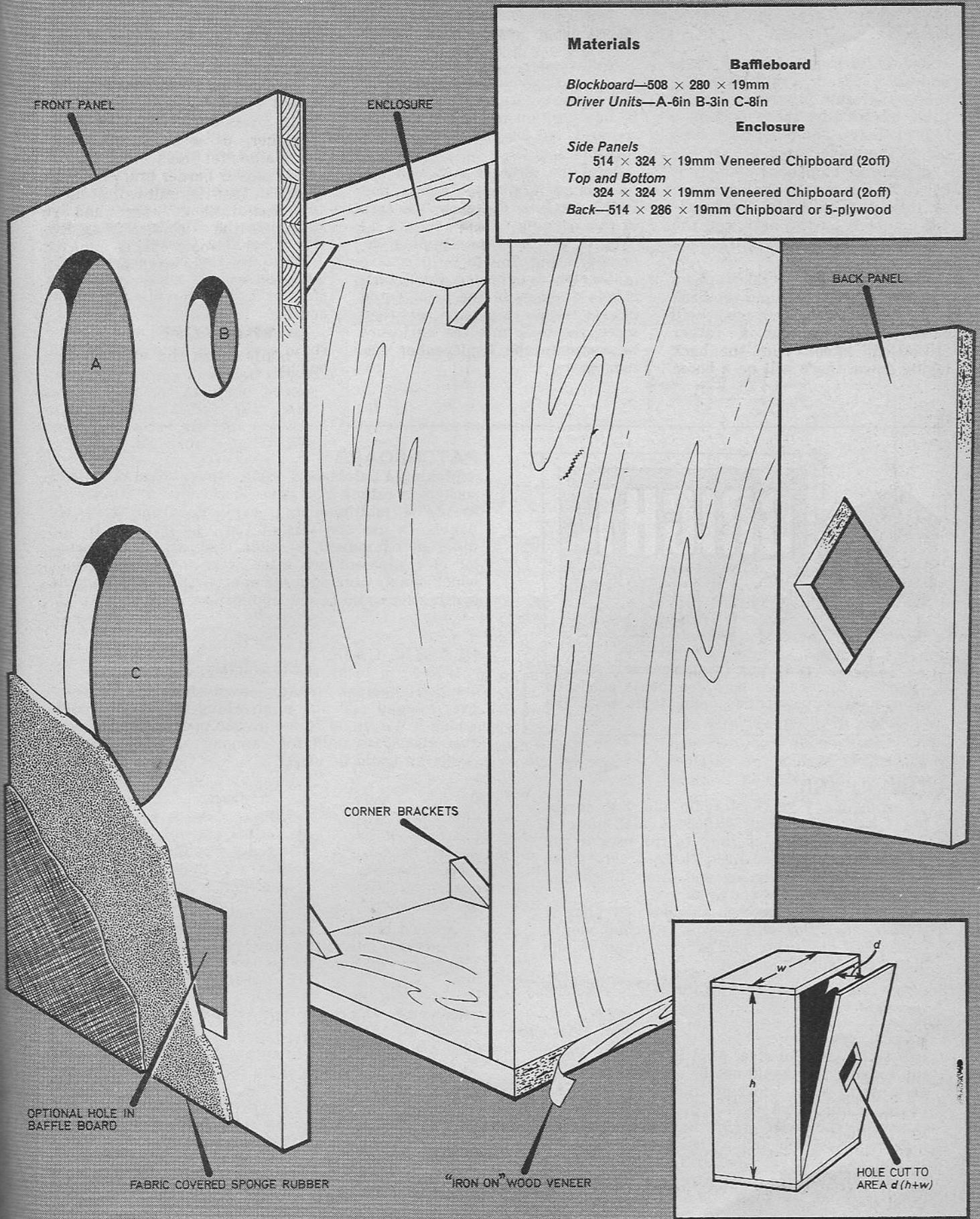Bolt the driver units to the baffle and wire in series. Screw the baffle into the enclosure using four screws fitted from the back through the corner pieces. The clearance hole for the screws should be drilled at an angle which allows the screwdriver to be handled easily from the rear of the enclosure.



Materials

Baffleboard
 Blockboard—508 × 280 × 19mm
 Driver Units—A-6in B-3in C-8in

Enclosure

Side Panels
 514 × 324 × 19mm Veneered Chipboard (2off)
 Top and Bottom
 324 × 324 × 19mm Veneered Chipboard (2off)
 Back—514 × 286 × 19mm Chipboard or 5-plywood

Fig. 1. Constructional details for a low cost loudspeaker enclosure. The method of working out the size of hole required to "tune" the enclosure for best response is shown inset.

BACK

Readers fitting a back or those making a pseudo reflex unit will follow the same procedure for the back, except that those making a reflex cabinet should not have completed the baffle board.

A piece of chipboard or 5-ply is cut to fit the rear of the enclosure as tightly as possible. Terminals are mounted on the back and the loudspeaker is connected to an amplifier.

Play music rich in bass frequencies and notice that when the back is pushed into the enclosure it will cause distortion and a rather "throttled" effect. With the back laying down, there will be a boom

on certain passages as the cabinet resonates.

Hold the back as shown in Fig. 1 and find the "best" position. This will not be critical but there should be one position where the boom is reduced, but the speakers are not throttled.


Note the distance d , which will be around 12mm to 50mm, possibly even less. Calculate the area of this opening $(d \times h) + (d \times w)$ to give the size of opening required, about 760 to 1270 square millimetres is expected. Finally cut a hole or holes in the back, equal in area to that calculated, and then screw the back into the enclosure to complete the loudspeaker system.

REFLEX HOLE

Readers making a pseudo reflex cabinet obviously leave the back alone and cut *their* hole in the baffle board. The driver units should be removed first, otherwise wood dust will get into the voice-coil air-gap and cause distortion.

Having cut the "reflex" hole the baffle is covered with the foam rubber and speaker cloth as described earlier. The finished unit is assembled and tested.

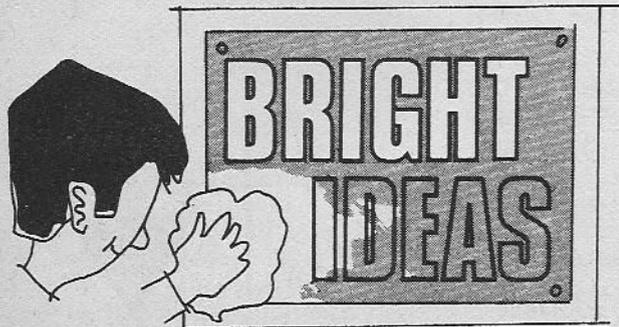Providing the reader has selected good drivers whose cones are clear of dust or iron filings and "on centre", they will be pleasantly surprised at how good and efficient these very cheap loudspeakers will sound. □



Readers' Bright Ideas; any idea that is published will be awarded payment according to its merit. The ideas have not been proved by us.

THIRD HAND

During many years of radio and T.V. servicing, I have never been without a small piece of Plasticine. There is no limit to the uses it can be put to. It may be used to hold very small components for soldering and other items that require that "third hand".

A small amount pressed out in a matchbox or similar small box will hold small components, transistors, diodes etc. and prevents them rolling about and being damaged.

T. A. Myers, Cheshire.

STEEL WOOL

A small piece of steel wool is one item which the constructor should not be without. It can be very useful when soldering components to Vero-board, a quick rub with a piece of steel wool cleans all the oxide which has formed on the copper strips and makes soldering easier. A second use of steel wool is for removing the enamel coating on copper wire, a quick rub will remove all but the most stubborn of enamels.

R. S. Patel, Leicester.


PATCHBOARD

Making a patchboard using conventional plugs and sockets is rather expensive. A cheaper alternative is to use a multipin plug, available from computer panels. In use one side of the plug is wired to the different equipment. Flexible leads from the second lot of equipment are fitted with spade connections which simply plug onto the appropriate pins. A simple synthesiser could be one application.

P. Baily, Glasgow.

PLASTIC CASE

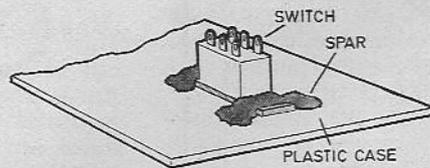Instead of using the recommended metal case for the *Soil Moisture Monitor I* used a plastic case. However I found difficulty in attaching the on/off switch, which had a metal frame, to the plastic case. I found that the spars used for carrying parts of a model Airfix kit could be used.



A short length is cut and used as a batten to affix the metal frame to the plastic lid. The diagram shows this more clearly.

N. J. Phillips, London N20.


PRINTED CIRCUIT BOARD

I have found an alternative to the normal types of printed circuit board. In my version hardboard is used as the base and strips of tin foil as the current carrying conductors.

The foil is cut to the required shape and stuck onto the hardboard, holes are then drilled as required, and nuts and bolts fitted. The leads of the components are then simply wound round the bolts and screwed in place. To prevent short circuits from occurring insulating tape may be stuck on the underside.

V. Bennett, Surrey

SQUARE

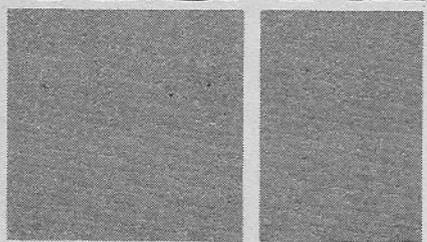

ONE

...FOR BEGINNERS

WE ARE HERE TO HELP YOU -

NO MATTER HOW NON-TECHNICAL
YOU MAY BE, JUST READ ON!

CONSTRUCTIONAL ARTICLES

All constructional articles in *EVERYDAY ELECTRONICS* are presented according to a standard pattern. The intention is to make it easy for the constructor to get to grips with the essentials.

Newcomers should note this standard arrangement, which includes the following major sections:

Introduction; How It Works; Start Here For Construction; Components; and Circuit Description.

INTRODUCTION

The very first section is the *Introduction* and is of course required reading. The general information given here will enable you to decide whether the project is one that appeals and has some immediate use.

HOW IT WORKS

In its own "box" (not always on the first page, please note), *How It Works* gives the reader a brief overall description of the circuit operation, and the kind of situation in which the project is employed. The accompanying illustration is usually a combination of *block diagram* and pictorial representation of some typical parts or associated equipment or apparatus with which the electronic unit is used.

BLOCK DIAGRAM. This is a very simple kind of diagram, where every important section of a *circuit diagram* is represented by a block—usually a rectangle, but some other shapes are used for certain forms of circuitry.

For example, an *amplifier stage* is conventionally indicated by a triangle, like an arrow-head pointing to the right. This "block" is "read" from left to right, as is conventional in all circuit diagrams, thus the input is applied to the left-hand side of the triangle and the output appears at the right hand tip (see Fig. 1).

The individual blocks are always labelled so that it is quite clear what portions or stages of the main circuit they represent.

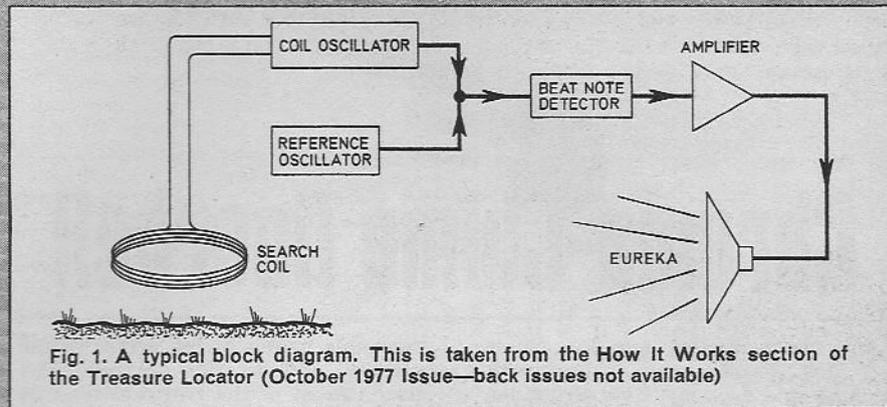


Fig. 1. A typical block diagram. This is taken from the *How It Works* section of the *Treasure Locator* (October 1977 Issue—back issues not available)

For brevity and simplicity, single lines are used to show the interconnections between the blocks. Arrows are often included to show direction of signals. These single lines must be interpreted as meaning actually *two* conductors in practice, to make the normal kind of circuit connections. But sometimes the connections are depicted in full detail, as when individual components are drawn.

EARTH SIGNS indicate a common connection. In other words, one can mentally link all such signs together. This applies, equally to circuit diagrams. (We shall be discussing circuit diagrams in a future *Square One*).

Apart from their use in *How It Works* block diagrams are commonly used to supplement circuit diagrams. They provide an overall key to the circuit and are especially important and helpful when the circuit is large and complex.

The block diagram helps the reader to "break down" the complete circuit into recognisable sections, thus enabling one to quickly understand and find one's way around the main diagram, no matter how involved it may appear at first glance.

START HERE FOR CONSTRUCTION

Having read the *Introduction* and *How It Works*, one can move on to the *Constructional Details*.

This part of the text (well signposted with an arrow head) describes, step by step, the building of the project. The accompanying illustrations showing the construction and assembly in detail must be carefully studied as well. They provide a complete blueprint for the constructor to follow. Every component and every connection is shown. So all you really have to do is follow the illustrations!


COMPONENTS

Before any building can commence, the necessary components and other items must be obtained. This brings us to the final essential department in our constructional articles—*Components*. This provides a complete list of all you will require. Note carefully any reference to *Shop Talk*, since this regular feature enlarges on particular shopping matters, suggesting sources of supply, or possible alternative types in light of current experience concerning availability and so on.

CIRCUIT DESCRIPTION

So now you are all set to go ahead. However, if you really are interested in electronics you are bound to read the *Circuit Description*—sooner or later. Although this is by no means essential before starting on your very first project. Good luck!

EE SPECIAL REPORT

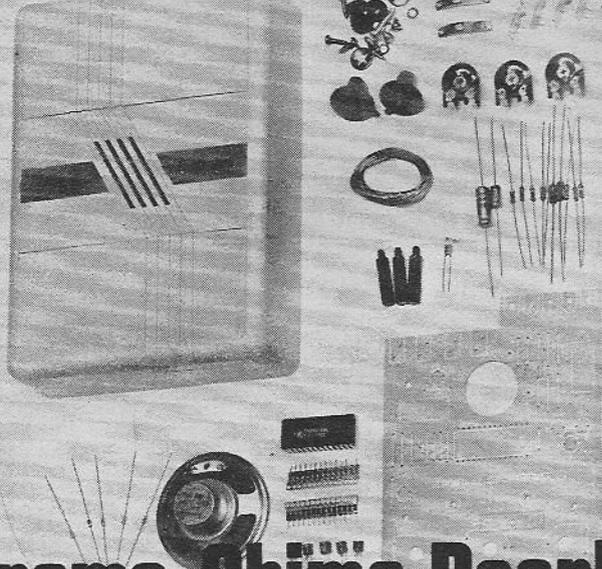

Chroma-Chime Doorbell

How about an electronic door chime that greets your caller with *Oranges and Lemons*, *Rule Britannia*, or *Colonel Bogey*—or any one from twenty-four jingles available at the turn of a switch? This is not all, however; a second bell-push can be fitted and a different tune allocated to it so you know instantly whether your caller is at the front or the back door.

All of this comes in the form of one small compact self-contained unit, housed in a white plastic case with

removable panels giving access to the batteries and to the controls. The latter consist of the two tune-selector controls, providing a choice from the total repertoire of 24 tunes, a tempo (or speed) control, a tone control, and a volume control.

This then is the Chroma-Chime, which first appeared on the market last summer.

The Chroma-Chime is powered by two PP3 batteries and under average conditions a life of at least one year

is obtainable before replacement is necessary.

As well as the ready-made unit, the Chroma-Chime is now also available as a kit for the home constructor. Before we discuss this kit, a few words about the Chroma-Chime in general.

A MINICOMPUTER


How is this all achieved in such a small (and deceptively simple) unit? The answer is—a microprocessor, which forms the heart of the Chroma-Chime circuit.

Microprocessors are the very latest technological development and they are now beginning to play a very significant role in electronics. Most of their applications so far have been in industrial equipment but they have a great future in the consumer area. The Chroma-Chime is amongst the very first of microprocessor-based products designed especially for the domestic market. It is a point of especial interest that this instrument has been designed by a British Engineer.

The Chroma-Chime designer conceived the general idea and then compiled the necessary programme, using his extensive experience with conventional full-size digital computers. The resultant programme was then implanted into the mini-computer chip during manufacture by Texas Instruments. The uniquely programmed chip is given its own identification mark.

This is a typical example of how a custom-designed dedicated microprocessor is originated. Dedicated means that the microprocessor is assigned one particular task (which may be extremely complex) and will perform that task once it is fitted into the appropriate circuit with (usually) a

Fig. 1. Block diagram of the Chroma-Chime electronic doorbell.

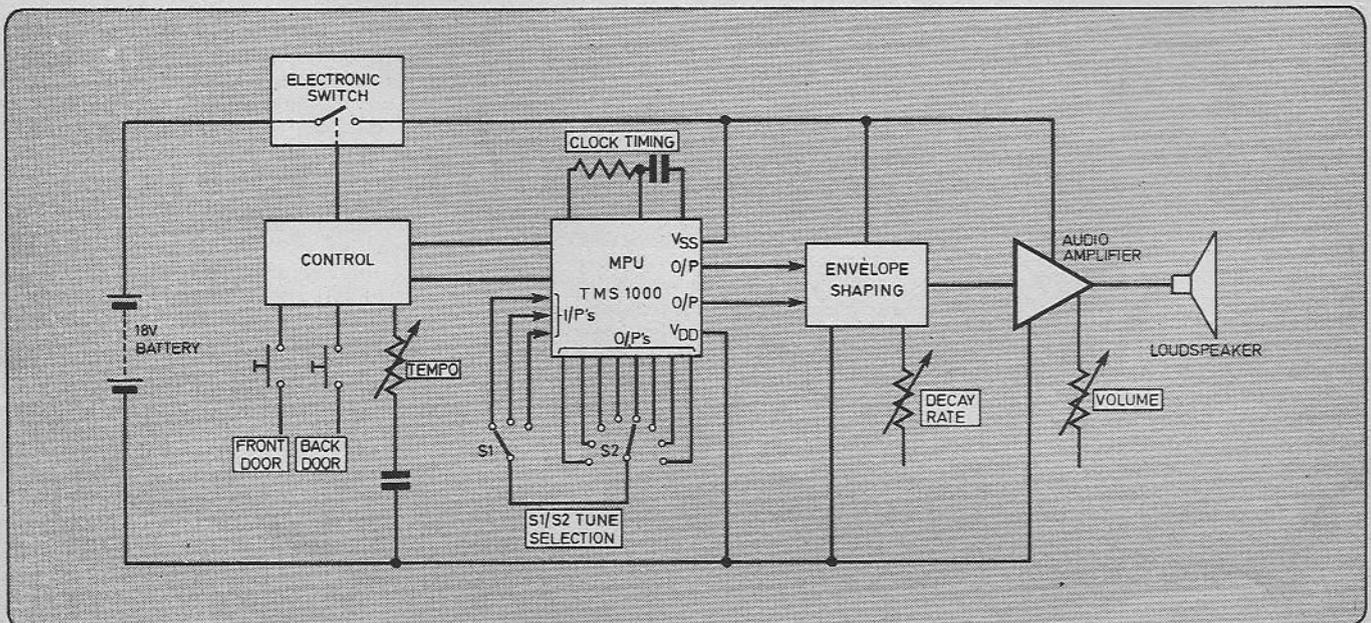

HOME CONSTRUCTION KIT

The Chroma-Chime is available as a kit, and apart from an appreciable saving in money compared with purchasing a factory built unit, the assembly of this kit is a rewarding exercise for the amateur for it provides him with his first experience in handling a microprocessor and also, of course, a lasting object he can take pride in. The sound of the Chroma-Chime is bound to provide comment from every new visitor. What better way to demonstrate one's ability as an electronics enthusiast!

Here we are dealing with one of the very latest developments in microelectronics. Yet the constructor need have no fears about tackling this project, provided he has already handled a lightweight soldering iron and has a general awareness of components and how one assembles them on to a printed circuit board.

If necessary, a short soldering practice session making wire connections to a few pins or small nails tapped into a small block of wood would be a wise precaution and provide confidence to go ahead.

There are two good reasons for recommending this kit to the average constructor.

First, the "mechanical" design is well planned. All parts (other than the loudspeaker) are mounted on one printed circuit board. This is clearly marked with the location for every part.

Second, the assembly manual provided with the kit is an excellent guide. It explains everything in clear language and close-up photographs show in detail various stages in the assembly. No one need ever feel lost if constant reference to the manual is made during the actual assembly work. A technical description and complete circuit diagram are also included.

The few tools required are listed in the manual. A further point might be made in connection with the soldering iron. This must be a miniature instrument, with a rating of 10-30 watts. The bit size is crucial. The manual advises a bit of less than $\frac{1}{8}$ in (3mm) at the tip. We suggest one of $1\frac{1}{2}$ mm, as we used when assembling our sample kit, though a 2mm bit should be quite suitable. (A somewhat larger bit could be an advantage when soldering the battery contacts since here comparatively large areas are involved. A 3mm bit is ideal for this purpose).

Multi-core solder (22 s.w.g.) is provided, in more than sufficient quantity for the entire operation.

ASSEMBLY WORK

The first step should be a careful reading of the entire manual. Then

one will have acquired a good overall appreciation of the task ahead.

Organise your workplace. Unpack the components, carefully checking each item against the list in the manual. Familiarise yourself with each component.

Be especially careful when examining the semiconductors. The transistor leads are identified in a chart in the manual, but earlier versions of the manual contained an error concerning the pin configuration for the transistors type BC172 and BC327. This was rectified by an amendment slip enclosed with our sample.

Alternative types of transistor may be supplied with some kits, but all should be clear from details in the manual.

The miniature diodes need careful scrutiny to establish their polarity, the identification marks being very small.


We would suggest that during the assembly and soldering operations the p.c.b. is placed on a soft pad, such as a folded cloth, to retain the p.c.b. in position and also to prevent damage to components.

Follow the instructions precisely, checking and double checking the identity and position of each component as it is mounted on the board.

Soldering is a task calling for the utmost care and concentration. The manual gives the sound advice that the soldering iron should not remain in contact with a semiconductor for longer than 5 seconds. This is a sound rule to follow in general, for all soldering operations.

Once the p.c.b. is completed, the remaining work is straightforward, all items fitting into their allotted places in the plastic case. After installing two PP3 batteries the unit is ready for testing according to the procedure given in the manual. If you haven't made any mistakes the Chroma-Chime will burst forth with tune A3, which is Beethoven's 5th Symphony theme. But if, perchance, nothing happens at first the manual gives a detailed checking routine to follow.

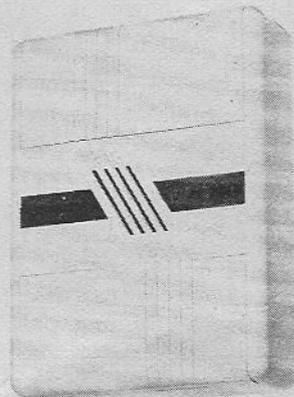A separate leaflet provides full Installation and Operating Instructions.



The above photos are reproduced from the Chroma-Chime assembly Manual.

Top: Breaking off the i.c. socket retaining strips after wiring has been completed.

Bottom: Soldering the battery contacts onto the p.c.b.

Our heading picture shows the complete kit of parts for the Chroma-Chime.

number of additional standard components including, probably, discrete semiconductors or other integrated circuits.


To most users, including constructors, the microprocessor can be considered as just another building block. We don't have to know anything about its internal organisation. But if we are project or equipment designers then an intimate knowledge of the microprocessor is necessary in order to design the surrounding or peripheral circuitry (just mentioned above) to complete the entire project.

As a matter of general interest, the microprocessor used in the Chroma-Chime is Texas Instruments type TMS1000 (CS107-01/MP0027A). This device (MPU in Fig. 1) is actually a minicomputer, because it includes in the single chip in addition to the processing unit (MPU), a 256 bit Random Access Memory (RAM) and a Read Only Memory (ROM) with 1,024 Bytes. In the latter is permanently stored a complete set of instructions needed to digitally encode each of the 24 different tunes. There is a total of 318 notes in the program.

The block diagram (Fig. 1) shows the general arrangement of the Chroma-Chime. The control, envelope shaping, audio amplifier and electronic switch sections are built up from conventional discrete components.

The Extraordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett

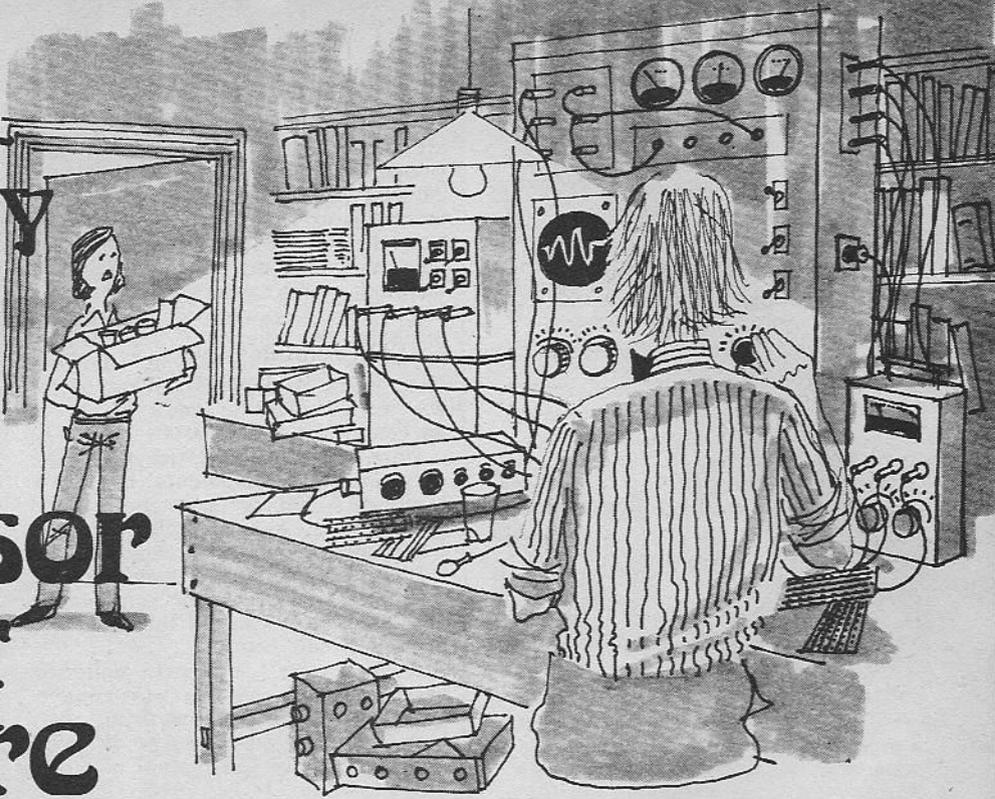

LAST month the Prof. and two of his friends, Lilian Whiteley and Dr. Angus R. Paterson, together with Bob discussed an experiment that they were going to carry out with the radiaesthetic preamplifier that Lilian had brought along to the Prof's laboratory.

We join them this month with Bob helping to set up the experiment.

SETTING UP THE EXPERIMENT

Bob secretly chose one of the five different substances which the Prof's experimental robot had supplied and placed behind an opaque screen arranged to divide one of the work-benches in the laboratory as shown in Fig. 1. Under cover of the opaque screen he tipped a small sample of the chosen substances on to the small copper plate attached to the input of the preamplifier, as the Prof. had instructed.

"Ready" he announced, and Lilian began to swing her small Perspex pendulum above the copper plate attached to the output of the preamplifier by way of a screened lead extending past the opaque screen. After a few moments she announced, to Bob's amazement:

"You forgot to switch on the preamplifier, Bob."

"How did you know that?" he asked,

"It has a completely silent on/off switch!"

"Because the action of the preamplifier considerably modifies the responses I get when swinging the pendulum above the output plate; ah, that's better!" she informed him as he switched the preamplifier on, "now I will be able to let you know which one of the five substances you have chosen."

Bob watched fascinated as Lilian swung the small Perspex pendulum alternatively over the output plate, and over each of the five reference samples which the robot had supplied. These were

separate samples of the same five substances, each consisting of a small heap of the substance on a sheet of paper numbered to correspond with the container from which the samples had been taken.

Lilian carefully adjusted the effective length of the pendulum by rolling the thread up on the plastic rod, or by releasing it, until at a certain length adjustment, she observed that the pendulum would

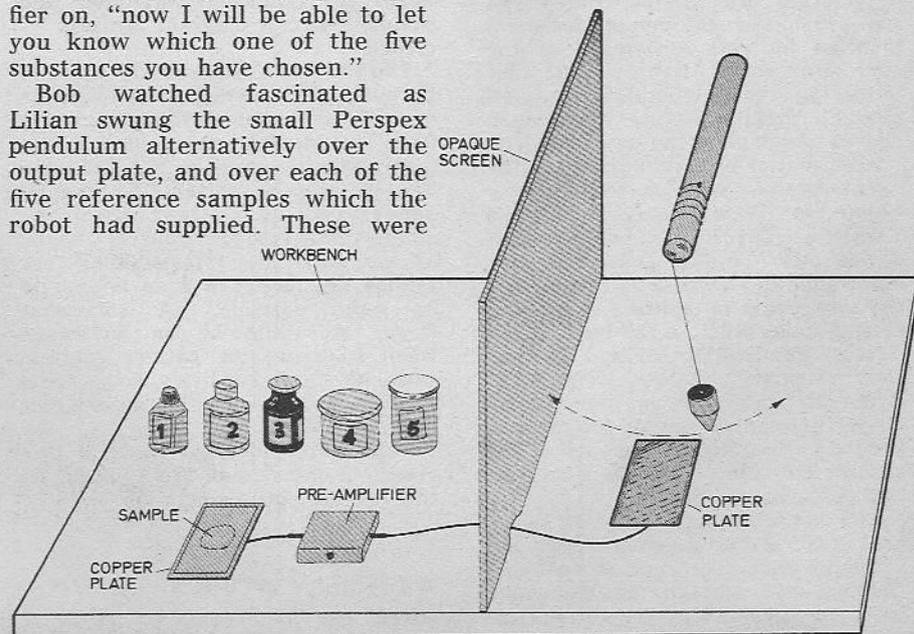


Fig. 2. The various parts of the Radiaesthetic Amplifier

gyrate, swinging in horizontal circles, over the output plate and also when swinging above a particular one of the samples. Over the other four samples, however, it did not gyrate but simply swung back and forth.

"It's Number 3!" she announced.

Now Angus, who had been quietly watching this procedure together with the Prof., secretly changed the samples on the input plate of the preamplifier.

EXPLANATION

"Will you explain to us just how you arrive at this conclusion?" he asked.

"Certainly, Angus", Lilian agreed obligingly.

"I have the pendulum adjusted to a certain length so that when I swing it over samples 1, 2, 4, 5, I just start it swinging back and forth then let it take its course. It just continues to swing back and forth. But when I swing it over sample Number 3 a dowsing reaction becomes evident, through my own nerves and muscles, causing the pendulum to change from back and forth oscillation to a horizontal gyration.

I don't try to make it gyrate, just start it swinging back and forth, then let it take its course to either continue back and forth, or else change to gyration. By changing the length of the pendulum I can adjust it so that it will gyrate in this manner over any one of the sample, each at a different length.

"Now I can make tests by swinging the pendulum over the output plate of the pre-amplifier. The influence of the sample on the input plate is boosted by the pre-amplifier and passes along the centre wire of the screened cable, becoming evident by pendulum indicated neurophysiological reactions over the output plate.

"This is how I discovered that Bob had placed a sample of substance Number 3 on the input plate. I have adjusted the pendulum to gyrate over my reference sample of substance Number 3, then when I swung it over the output plate it also gyrated."

ANOMALOUS RESULT

Lilian once again swung the pendulum over the output plate, but it failed to gyrate—and just continued back and forth.

"Angus!" she looked at him suspiciously, "you have removed the sample!"

She continued to make tests, swinging the pendulum alternately over the output plate and the various samples, until at a certain length it would gyrate over either the output plate, or over one of her reference samples, but not over the others.

"It's Number 1!" she announced. "You changed the sample on the input plate from Number 3 to Number 1!"

"That's right", said Bob, "the sample I first put on the input plate was from container Number 3—and I can see that now a sample from container Number 1 has been substituted. But Prof.," he remarked, "this is amazing! I do not understand it; we have not learned anything like this at school. What I want to know is . . . what does the preamplifier do, for a start? If the influence will travel along a wire why not just have a length of wire with a copper plate at each end and no preamplifier in between?"

"No sooner said than done!"

To be continued

TV GAMES

AY-3-8500 £5-95.
AY-3-8550 £9-95.
AY-3-8600
£13-95. 4-43MHz
crystals £1-95.
Black and white
TV games kits—
standard model £11-95. Economy model
£9-95. Colour TV games kits—standard
£19-45. Economy £14-45. Colour gener-
ator kit adds colour to most black and
white games £7-50. Rifle kit £4-95. Send
sae for giant free data leaflet.

NEW COMPONENT SERVICE
resistors 5% carbon E12 10 to 10M. 1W
1/4p. 1W 3p. preset pots subminiature
0-1W 100 to 4M7 9p. Potentiometers
1W 4K7 to 2M2 log or lin. Single 30p.

Dual 95p. Polystyrene capacitors
E12 63V 22pF to 8200pF 3p. Ceramic
capacitors 50V E6 22pF to 47000pF 3p.
Polyester capacitors 250V E6 0-1 to
1mf 5p. 15, 22, 33mf 7p. 47 11p.
Electrolytics 50V 47, 1, 2mf 5p. 25V 5,
10mf 5p. 16V 22, 33, 47mf 6p. 100mf 7p.
220 330 9p. 470 11p. 1000mf 18p. Zener
diodes 400 mW E24 3V3 to 33V 8p.

MAINS TRANSFORMERS
6-0-6V 100ma 94p. 9-0-9V 75ma 94p.
12-0-12V 50ma 94p. 13V 1A £1-10.
6-3V 1A £1-89. 6-3V 1A £1-99. 6-0-6V
1A £2-35. 9-0-9V 1A £2-79. 12-0-12V
1A £2-49. 15-0-15V 1A £2-79. 30-0-30V
1A £3-59. 9-0-9V 2A £2-80.

PRINTED CIRCUIT MATERIALS
PC etching kits—economy £1-70.
Standard £3-82 50 sq ins pcb 40p. 11b
FeCl₃ £1-95. Etch resist pens—economy
45p. Dalo 83p. Small drill bit 20p.
Laminated cutter 75p. Etching dish 68p.

S-DECS AND T-DECS*
S-DeC £2-23.
T-DeC £3-98.
u-DeCA £3-97.
u-DeCB £3-67.
16 di! adaptors—
plain 99p. With
socket £1-91.
New S-de-kit £4-95.

FERRANTI ZN414
IC radio chip £1-44. Extra parts and pcb
for radio £3-85. Case £1. Send sae for
free data.



SINCLAIR PRODUCTS*

Cambridge scientific programmable
calculator £13-95. Prog library £4-95.
Mains adaptor £3-20. Cambridge
scientific £3-45. Oxford scientific
£10-90. Enterprise £3-95. President
£16-95. PDM35 digital multimeter
£25-95. Adaptor £3-24.

BI-PAK AUDIO MODULES
S450 tuner £21-95. AL50 £4-36. PA100
£14-95. MK60 audio kit £38-45. Stereo
30 £17-95. SPM50 £3-75. BMT30 £5-95.
Send sae for free data.

JC12, JC20 AND JC40 AMPLIFIERS
A range of
integrated circuit
audio amplifiers
supplied with
free data and
printed circuits.
JC12 6 Watts £1-95. JC20 10 Watts
£2-95. JC40 20 Watts £4-20. Send sae
for free data on all 3 models.

**BATTERY ELIMINATOR
BARGAINS**
TV games power unit stabilized
7-7V 100ma £3-25. 3-way models with
switched output and 4-way multi-jack—
3/4/6V 100ma £2-92. 6/7/9V 150ma
£3-30. 100ma radio models with press
stud connectors. 9V £2-85. 6V £2-85.
4.5V £2-85. 9V+9V £4-50. 6V+6V £4-50.
4.5V+4.5V £4-50. Cassette recorder
mains unit 7.5V 100ma with 5 pin din
plug £2-85. Fully stabilized model
switched output of 3/6/7.5/9V 400ma
stabilized £6-40. Car converters 12V
DC input. Output 6V 300ma £1-80. Out-
put 7.5V 300ma £1-80.

BATTERY ELIMINATOR KITS
Send sae for free leaflet on range.
100ma radio types with press stud
battery terminals. 4.5V £1-80. 6V £1-80.
9V £1-80. 4.5V+4.5V £2-50. 6V+6V
£2-50. 9V+9V £2-50. Cassette type
7.5V 100ma with din plug £1-80. Trans-
istor stabilized 8-way type for low
hum. 3/4/6/7.5/9/12/15/18V. 100ma £3-20.
1Amp £6-40. Heavy duty 13-way types
4.5/6/7.5/9/11/13/14/17/21/25/28/34/42V.
2 Amp £4-85. 2 Amp £7-95. Car conver-
tor kit input 12V DC. Output 6/7.5/9V
DC 1A transistor stabilized £1-95.
Stabilized power kits 3-18V 100ma
£3-80. 3-30V 1A £9-95. 3-60V 1A £10-95.
3-60V 2A £13-95.



HAVE YOU DONE IT LATELY!

Fit a
new tape head
and transform the
performance of
your tape
recorder

MONOLITH
THE MONOLITH ELECTRONICS CO LTD

QUALITY
REEL TO REEL
AND CASSETTE TAPE HEADS



Please enclose

Full Catalogue 25p

20p P&P with order

B24-RP stereo cassette glass/ferrite record/playback £9.84
B12-01 mono cass. playbk. £1.60 B24-Q1 stereo cass. playbk. £2.80
A28-05 stereo 8tk cartridge £1.80 E12-09 stereo/mono cass. erase £1.80

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321

FREE

CATALOGUE/ORDER FORM

SEND S.A.E

500+ Top quality Transis-
tors, I.C.'s, Resistors, Capacitors, Plugs/
Sockets, Veroboard/cases, Indicators, Knobs,
Switches, Wire and Books at prices you can afford.

741
ONLY
30p

555
ONLY
50p

TIL209
ONLY
15p

IN4001
ONLY
5p

All prices include VAT. P&P FREE over £2.

Name _____

Address _____

Get an ACE up your sleeve!

ACE
MAILTRONIX LTD
Dept. E.E. Tootal Street
Wakefield, W. Yorkshire WF1 5JR

SWANLEY ELECTRONICS

DEPT. EE. PO Box 68, 32 Goldsel Rd., Swanley, Kent BR8 8TQ

Mail order only. Please add 3p to total cost of order for postage. Prices include
VAT. Overseas customers deduct 7% on items marked * and 11% on others. Official
credit orders welcome.



there was no suitable insulating material.

Without delving too deeply into the intricacies of the problem, the losses in the cable would amount to about 1,000 volts per mile. The distance across from Norway to England at the nearest points is 600 miles. To have anything left say, at Newcastle, it would need to leave Bergen with a pressure of 600,000 volts and no insulating material has yet been made that can stand up to that voltage.

I expect I should qualify this, because I have no doubt an insulating material has been made with this capability but, as you will appreciate it must also be a viable proposition to produce it commercially.

The Kitchen Table

I often wonder what conditions most of you work under. Some no doubt have a spare room, beautifully converted, some a corner in the garage and some work on the kitchen table. It is pure guesswork, but I would say the latter were by far the largest group. This method poses problems, at the most inconvenient moment, Mum wants to lay for dinner.

For two or three years I have been toying with the idea of a table top bench come work shop that you would lay on the table and immediately have everything to hand, Soldering Iron, Tools, Mains, Aerial and Earth, but as soon as you received the signal to scram, you picked it up by the handle, stuck it in the corner of the garage until the washing-up was completed. I was therefore most interested to see the review of an electronic workshop, in EVERYDAY ELECTRONICS last month. I congratulate the firm concerned on their enterprise in meeting a definite need.

AGE cannot wither her, nor custom stale, her infinite variety. Naturally all our readers know that this was written by a lad called Will Shakespeare about an Egyptian dolly called Cleopatra, but seeing it quoted the other day made me think what an apt description it was of the electronics hobby, especially the "infinite variety" bit! Just consider the range of projects that EVERYDAY ELECTRONICS has offered you.

In addition to all this, there is the wonderful prospect of branching out and experimenting on your own. In other words to be an inventor.

The first requisite of an inventor is to be inquisitive. I well remember at school we had a dear old chemistry master who told us, if you put A on B hydrogen would be produced, or X on Y would produce carbon dioxide. Being incorrigible even at that early age, I wanted to know what happens if I put A on Y or B on X!

As the dear old gentleman would often leave us for long periods alone in the laboratory I was able to indulge my whims and carry out such unique experiments as dropping large lumps of sodium down the school drains.

The school was rebuilt many years ago and I suffered only from slightly singed eyebrows.

However, the readers of this magazine are more sensible and better informed and I am convinced we have many a lurking Edison or Marconi among their ranks.

Waiting To Be Invented

Do not be put off by the dismal Jimmys who tell you there is nothing left to invent. Professor George Russell Harrison, in his book *Atoms in Action* explodes this theory. He quotes two examples of urgent need.

One, a source of portable power, something the size of a match box, two ounces in weight, that would give out the power of a twelve-volt car battery. Invent that, and you would put the oil sheikhs in the dole queue overnight.

Two, the perfect insulator. An idea was seriously considered several years ago to pipe electricity across from Norway, where they have an abundance due to unlimited water power. It was abandoned because

JACK PLUG & FAMILY...

THAT FIND-THE-PAIR ELECTRONIC GAME THAT YOU CAN FRUSTRATE YOUR FRIENDS WITH LOOKS AS THOUGH IT'S GOING TO BE GREAT FUN.




YES, ALREADY YOUR FATHER IS THOROUGHLY ENJOYING HIMSELF FROM THE...



The Sinclair PDM35.

A personal digital multimeter for only £29.95

(+8% VAT)

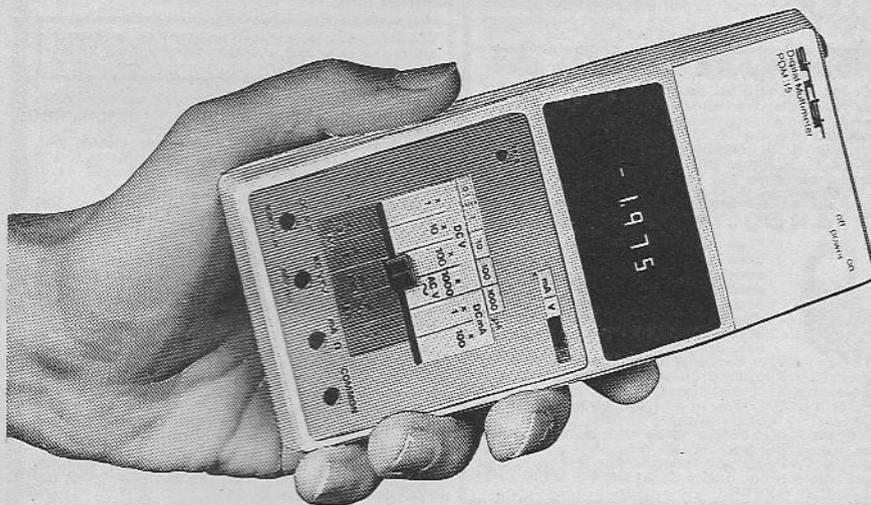

Technical specification

DC Volts (4 ranges)

Range: 1 mV to 1000 V.

Accuracy of reading 1.0% ± 1 count.

Note: 10 M Ω input impedance.

AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading: 1.0% ± 2 counts.

DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading: 1.0% ± 1 count.

Note: Max. resolution 0.1 nA.

Resistance (5 ranges)

Range: 1 Ω to 20 M Ω .

Accuracy of reading: 1.5% ± 1 count.

Also provides 5 junction-test ranges.

Dimensions: 6 in x 3 in x 1 1/2 in.

Weight: 6 1/2 oz.

Power supply: 9 V battery or Sinclair AC adaptor.

Sockets: Standard 4 mm for resilient plugs.

Options: AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts – from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ, England. Regd No: 699483.

Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

What you get with a PDM35

3 1/2 digit resolution.

Sharp, bright, easily read LED display, reading to ± 1.999.

Automatic polarity selection.

Resolution of 1 mV and 0.1 nA (0.0001 μ A).

Direct reading of semiconductor forward voltages at 5 different currents.

Resistance measured up to 20 M Ω .

1% of reading accuracy.

Operation from replaceable battery or AC adaptor.

Industry standard 10 M Ω input impedance.

Compare it with an analogue meter!

The PDM35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 M Ω is 50 times higher than a 20 k Ω /volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.

Please send me _____ (qty) PDM35(s)

@ £33.00 (inc £2.40 VAT and 65p P&P)

each: _____ £

_____ (qty) De-luxe padded

carrying case(s) @ £3.00 (inc VAT

and P&P) each: _____ £

_____ (qty) AC adaptor(s) for

240 V 50 Hz power @ £3.00

(inc VAT and P&P) each: _____ £

I enclose cheque/PO made payable

to Sinclair Radionics Ltd for

(indicate total amount): _____ £

I understand that if I am not completely

satisfied with my PDM35, I may return it

within ten days for a full cash refund.

Name: _____

Address: _____

EE 2



sinclair

World leaders in fingertip electronics

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Plessey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14.00 including VAT and postage.



ROOM THERMOSTAT

Famous Satchwell, elegant design, intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0-30°C. Special snip this month £3.00 post and VAT paid.



SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £7.95 plus 95p VAT & Postage.



MICRO SWITCH BARGAINS

Rated at 5 amps 250 volts. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 for £1.00, VAT and post paid.



RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set. £3.95 VAT and postage inc.



MULTISPEED MOTORS

Six speeds are available 500, 850 and 1,100 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 1/8" diameter and approximately 1" long. 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2" dia. x 5" long. Price £2.00 including Post & VAT.



RECTANGULAR HOT PLATE

Aluminium panel with ridged top and angled underneath to strengthen it. This is approx. 10" x 4 1/2" of flat plate. Beneath plate is 100w element and sensor switch which will maintain the surface of the plate just too hot to touch. With leads and tags. This is ideal if you are making up a food warmer or for an airing cupboard, etc. Price £1.03.




HUMIDITY SWITCH

American made by Ranco, their type No. 311. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive microswitch adjustable by a screw, quite sensitive—breathing on it for instance will switch it on. Micro 3 amp at 250V AC. Overall size of the device approx. 3 1/2" long, 1" wide and 1 1/2" deep. 75p.



MAINS RELAY

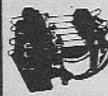With triple 10 amp changeover contacts—operating coil wound for 230 volts AC, chassis mounting, one screw fixing, ex unused equipment 80p each, post and VAT paid.



PP3/PP9 REPLACEMENT MAINS UNIT

Japanese made in plastic container with leads size 2" x 1 1/2" x 1 1/2", this is ideal to power a calculator or radio. It has a full wave rectified and smoothed output of 9 volts suitable for a loading of up to 100mA. £2.53.



MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.50. Postage 50p.

DRILL CONTROLLER



Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45 including post & VAT. Made up model £1.00 extra.

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output £1.50 including Post & VAT. Model 1172 1W, power output £1.85 including Post & VAT. Model EP9000 4 watt power output £2.90 including Post & VAT. EP 9001 twin channel or stereo pre-amp. £2.90 including Post & VAT.



SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1.90—crystal earphone 55p including VAT and postage.



BREAKDOWN PARCEL


Four unused, made for computer units containing most useful components, and these components unlike those from most computer panels, have wire ends of usable length. The transistors for instance have leads over 1" long—the diodes have approx. 1/2" leads.

List of the major components is as follows:—17 assorted transistors—38 assorted diodes—60 assorted resistors and condensers—4 gold plated plugs in units which can serve as multi-pin plugs or as hook up boards for experiments or quickly changed circuits (note we can supply the socket boards which were made to receive these units). The price of this four units parcel is £1 including VAT and post (considerably less than value of the transistors or diodes alone) DON'T MISS THIS SPLENDID OFFER.



FLUORESCENT TUBE INVERTER

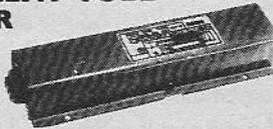For camping—car repairing—emergency lighting from a 12v battery you can't beat fluorescent lighting, it will offer plenty of well distributed light and is economical. We offer inverter for 21" 13 watt miniature tube for only £3.75 with tube and tube holders as well.



TEACH IN '78

Start right away. Order the part for this series—send £3 deposit and £2 monthly for 5 months or £12 cash. Past lessons also available.

EXTRACTOR FAN

Ex computers—made by Woods of Colchester, ideal for fixing through panel—reasonably quiet running—very powerful 2500 rpm. Choice of two sizes 5" or 6 1/2" dia. £4.43, and £6.



SPIT MOTOR WITH CARTER G/BOX

Probably one of the best spit motors made. Originally intended to be used in very high priced cookers, however this can be put to plenty of other uses, for instance your garden barbecue or to drive a tumbler for stone polishing; in fact there are no ends to its uses. Normal mains operation. £4.32 including POST & VAT.



LATCHING RELAY

by Guardian Electric, mains operated it is in fact two relays mounted on a metal base plate. The relays being mounted in such a way to ensure that when one closes the other opens and vice versa thus when closed relay A would remain locked until manually released or electrically released by energising relay B. Each relay has 2 sets of 10 amp changeover contacts. Should be ideal for burglar alarms and similar applications £2.11.



TERMS:

Cash with order—prices includes VAT and carriage unless stated but orders under £6 must add 50p to offset packing etc. BULK ENQUIRIES WELCOMED. Phone 01-688 1833

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

FM Tuner and decoder, two very well made (Japan) units, nice clear dial, excellent reproduction £9.95 the pair £1.25 VAT.

12 Volt Heavy Duty Relay, plug in type has three pairs of 10 amp changeover contacts. A transparent dust cover, price £1 + 8p, suitable 11 pin base 27p + 2p. 4 Changeover Mains Relay, upright mounting with perspex type dust cover, the really interesting feature is 4 sets of 10 amp changeover contacts price £1.62 + 12p.

12 Volt Pump. Designed we believe as a bilge pump, this is 12 volt AC/DC motor coupled by a long enclosed shaft to a submersible pump. Suitable for water or most any fluid. Price £1. Post 80p.

Just arrived. Fruit machines, working order very impressive choice of several but very heavy so you must collect. £50. High Load 24 Hour Clock Switch, made by the famous AEG Company for normal mains but with clockwork reserve has load capacity of 80 amps at 240V 50Hz. Therefore suitable for dealing with large loads of say shop lighting, water heating, storage heaters etc. extra. Has triggers for on and off once per 24 hours but extra triggers will be available. Price £1.50 per pair. Size of clock approximately 8" x 5" x 5", totally encased but has lift up flap for ease of altering switching times. Price, new and unused £10.65 or used but guaranteed o.k. £6.50.

Enclosed 24 Hour Clock, with contacts for breaking 10-12 amps at 240 volts. This one has two sets of on/off per 24 hours, price £7.00.

Smiths 24 hr. Timers-Heart only, with over-ride similar to those used in the auto set etc. £4.75 + 38p.

Light Dimmer, our timer module with small mods makes an excellent light dimmer. Contains a 4 amp 400V 1kW. Price of module with variable resistor and instructions £2.25.

Push Pull Solenoids, mains operated solenoids which will push as well as or instead of pull. Very heavy duty estimate this at 20lbs push or pull 1 1/2" x 3 1/2" x 4" made Magnetic Devices Co. £7.50.

Flashing Lights, chasing lights, random flashes, strobe effects etc. etc. can easily be achieved using our disco switches and with Christmas just around the corner you can do something special for your home or business. These switches are offered at approximately one-fifth of their proper price are ex-equipment but guaranteed perfect and supplied with an adaptor suitable for mains working. To get some idea of the loading number, each switch is 10 amp which is approx 2 1/2kW so the 6 switch model could handle over 12kW's. For the light pipe or Catherine Wheel effect we suggest 12 switch model, interconnecting the switches to give fastest speed. 6 switch model £5, 9 switch model £9.75, 12 switch model £6.20. Also add 50p post per switch. If you want the light pipe diagram please request this.

Always in Stock. Turntables with pick-up lift, ideal for disco's at £11.95, post £2.25. We are also expecting some professional belt drive type at £25. Call or ring us for more information.

Reed Switches, standard 60 watt glass type. Normal open contacts glass lengths 2" diameter 3/16" 10 for £1 + 8p, 100 for £8 + 64p, 1000 for £65 + 25.20.

Flat Reed Switches, for stacking, greater quantity in confined space. Price 50p each.

Single Ended Types for jobs where it is not easy to bring a lead to each end 75p each. All these switches are normally open but can be biased to a normally closed position by fitting a magnet adjacent. The reed switch would then be opened by a magnet of opposite polarity being brought up to it.

Ceramic Magnets suitable for operating reed switches, central fixing hole. 10 for £1.

Music Centre Transformer 12-0-12 at 1 amp and 9 volt at 1/2 amp. Normal primary, upright mounting, impregnated and varnished for quiet operation. Price £2.95. Post 54p.

'W' Shaped Fluorescent Tubes for porch light, box confined area of approx. 10" x 10", 30 watts, made by Philips price £1.60. Post 54p.

Plinth for BSR Record Player still available at the record price of 95p + 12p. This is excellent value but unfortunately being a bulky and delicate item the postage has to be £1.50 + 12p so this is obviously only a bargain for callers.

Our Smokey Cover can be used with the above plinths, four small locating pins are fitted to the motor board. Size approx. 12 1/2" x 14 1/2". Price £2.50 + 32p Post £2.00 + 16p.

Extension Speakers 8 ohm 4.5 watts handling power. We have 5 or 6 different models in stock, cheapest being the Partytime at £3.95 each, again only really a bargain for callers as postage is £1.50 per speaker.

T.V. Monitor, an item for callers, believed to be in good working order, switchable thro' 405-525 & 625. 21" tube line systems, normal controls, volume, brightness, contrast, width etc. Price £16.20, 12" model £18, suitable for conversion into special purpose scope, etc.

Auto transformers for working American tools and equipment, completely enclosed in sheet metal case with American type flat output socket made for computer so obviously first class, 500 watts with carrying handle, offered at about half price only £15 + 80p, carriage £2 + 16p. These may be a bit soiled but are fully guaranteed. Similar but 1000 watt £29.50 or £6.48. Post £1.62.

J. BULL (ELECTRICAL) LTD

(Dept. EE), 103 TAMWORTH RD.

GROYDON CR9 1SG

GEORGE HYLTON brings it down

Negative Resistance

NEGATIVE resistance is a rather puzzling term. It is often used in connection with oscillators of various special kinds. A negative resistance oscillator is, in general terms any kind of "black box" which oscillates when the right kind of impedance is connected to it—a tuned circuit for example.

In other words a negative resistance is something which supplies energy, unlike an ordinary positive resistance which of course absorbs energy or at any rate turns electrical energy into heat. Positive resistance, or just plain common or garden resistance if you like, is in many ways like friction. Mechanical friction resists movement—it tends to prevent one surface from sliding over another. Resistance also inhibits movement, only in this case it is the movement of electrons through a circuit.

Friction

Friction, like the Roman god Janus, has two faces. The one we are mostly concerned with in life is the bad face, the friction which resists smooth movement of machinery and consumes energy to no purpose. But friction has a good face too, and this good aspect is so widespread that we just do not give it a thought. Yet friction is a sort of glue that holds the world together. Without it no nail would stay for long in a piece of wood; screws would fail to grip; zips would unzip; knots would untie and stitches loosen. Things would just fall apart.

In the electrical world resistance likewise prevents disasters. If resistance were to disappear no battery could stay charged because current would run out of it through the air or any insulator. All voltage differences would instantly disappear, short-circuited by

the things which at present hold them apart, resistances and insulators. Electronics would be impossible.

Like friction, we just take for granted this helpful aspect of resistance. It is the unhelpful aspect that bothers us, the nasty habit resistance has of getting in the way of the currents we want to have flowing. If only you could buy negative resistors how useful they would be! If a relay coil had a positive resistance of 100 ohms and your circuit could not drive enough current through it for lack of voltage all you would need to do would be to connect minus 100 ohms in series. This would cancel the coil resistance and allow current to flow unimpeded.

Or should the minus 100 ohms be connected in parallel?

Negative or Positive

That's an interesting question because there are two kinds of negative resistance, a series kind and a parallel kind. Before showing you how to experiment with them however let me ask one question. What happens if instead of connecting minus 100 ohms in series with your 100 ohm coil to cancel its resistance you connect only minus 80 ohms? Simply arithmetic says that there is still 20 ohms left uncancelled. What you have done is to reduce the coil's effective resistance but not to cancel it. But what if you over-cancel, so to speak, by connecting say minus 150 ohms? Then you should still have minus 50 ohms left. What effect does this have on the circuit?

This uncancelled negative resistance supplies energy to the circuit. You can see why it must do so by thinking about positive resistance and then reversing things. If you apply 10 volts to a positive resistance, a certain current flows. Halve the voltage to 5 volts and the current drops to half and so on. With negative resistance the opposite must happen. Reducing the voltage must increase the current. If you go on halving the voltage so it gets closer and closer to zero the current must get bigger and bigger. Evidently the current is coming, not from the battery but from the negative resistance itself. This after all is just what you could expect: positive resistance absorbs energy but negative resistance must emit energy. In other words a negative resistor, if you could find one, would be a source of energy!

Oscillators

Well, there are plenty of sources of energy about; generators; batteries and so on. So a battery must be a negative resistance, OK? Well yes, except that if you connect a battery to say a tuned circuit it doesn't oscillate, not after the first few moments anyway. But if you connect a negative resistance to a tuned circuit it does oscillate.

Unfortunately you cannot go into a shop and buy a negative resistor. To do so would be the same sort of thing as buying an amplifier which works without a power supply. Amplifiers amplify all right. But only because they are supplied with more watts of mains or battery power than ever comes out as audio power. What they really do is convert power in one form, say d.c. power, into another form, say a.c. In the process some energy is wasted; the amplifier's transistors get warm.

It is just the same with negative resistance. You can make circuits and devices which

have negative resistance all right. But in order to make them work you have to put in more energy than you get out. If you try to take out more than you put in the thing just stops being a negative resistance.

Practical Circuit

That is why real life negative resistances are always sort of embedded in positive resistances. One practical negative resistance circuit is illustrated in Fig. 1.

This "artificial negative resistance" circuit may be constructed in any convenient way, the layout is not at all critical.

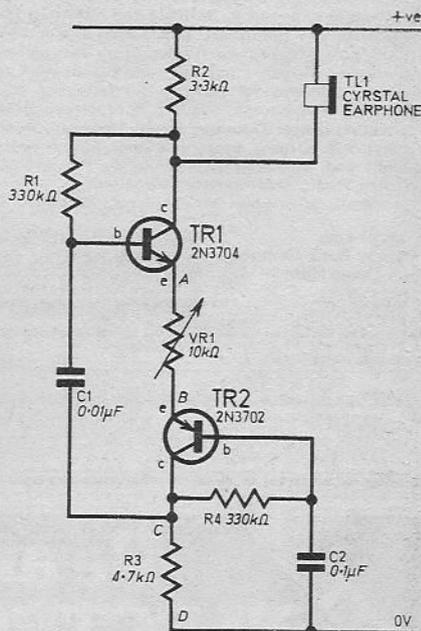



Fig. 1. A simple circuit to illustrate the effect of negative resistance.

When finished with this "negative resistance" you can use the parts for something else! Incidentally, this circuit is not fussy about transistor types, supply voltage, or component values.

Adjusting VR1 produces an audio tone in the earphone. When it is at maximum there is no oscillation. As it is reduced, oscillation begins and continues (with change of frequency) even when zero. If VR1 and R3 are now exchanged it is found that in its new position (C and D) VR1 stops the oscillation when set to zero but allows it when set to maximum—the opposite state of affairs from the original one. The explanation is that in the original (A and B) position VR1 is in series with a negative resistance so when too large the net resistance is still positive. In the C and D position it is in parallel with a negative resistance and so must be larger than the negative resistance if it is not to swamp it.

There is no tuned circuit in Fig. 1 and this "negative resistance oscillator" operates as a relaxation oscillator or astable R/C oscillator. If VR1 is in the A and B position (where it acts as a regeneration control) and a parallel-tuned circuit is connected across C and D the circuit can be set to oscillate at the natural frequency of the tuned circuit.

to earth

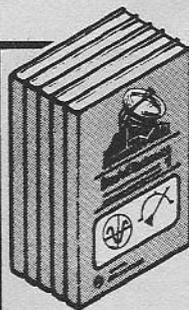

ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.
Bound in stiff linen. Cover size 8 1/2 in x 5 in.
Price £7.50 per set (we pay the postage).

- Book 1. Introducing Electronics
Book 2. Resistor/Capacitors
Book 3. Inductors/Diodes
Book 4. Meters/Voltage-dividers
Book 5. Transistor Project Circuitry

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm, Sound effects oscillator. Variable time-delay switch.

Order now:
Selray Book Company
60 Hayes Hill
Bromley
BR2 7HP

OUR 100% GUARANTEE

Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £

Name:

Address:

ET3

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

TEACH-IN '78

Complete kit of parts for the
New Series started last
month. Everything for £13.50
including Post and VAT.
Order Early!!

DEVELOPMENT PACKS

Buy a complete range of components in one go and save time and money!!
All packs contain full spec brand new marked devices, sent by return of post. All prices include VAT, just add 25p post for any quantity.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210, £3.35.

K002 Extended range, 22pF to 0.1µF. 330 values £4.90.

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75.

K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for £4.45.

K006 Tantalum bead capacitors. 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tants for £14.20.

K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50.

K021 Miniature carbon film 5%, resistors, CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors, £5.00.

K022 Extended range, total 850 resistors from 1R to 10M £8.30.

K041 Zener diodes, 400mW 5%. BZY88 etc. 10 of each value from 27V to 36V, E24 series. Total 280 for £15.30.

1977/78 CATALOGUE

Big new illustrated catalogue
with 50p discount vouchers!
Complete range of resistors,
capacitors, semiconductors,
knobs and boxes, etc., all at
discount prices!! Only 30p +
15p post.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.15 inc. post and VAT.

VERO OFFCUTS

Pack A, All 0.1"
Pack B, All 0.15"
Pack C, Mixed
Pack D, All 0.1" plain
Each pack contains 7 or 8 pieces with a total area of 100 sq. ins. Each pack is £1.45 inc. post and VAT.

CRESCENT RADIO LTD.

MAIL ORDER DEPT. 1 St Michaels Terrace, Wood Green
London N22 4SJ Phone 888-4474

MULTIMETER BARGAINS

A special bulk purchase of Eagle Multimeters enables us to offer three from their range at up to 15% off Eagle's own recommended retail price.

KEW 7

1,000 opv pocket multimeter with 'off' damping.

All basic ranges included. Leads, battery and instructions supplied.

Spec. as follows:—

DC volts: 0 to 10, 50, 250, 1,000 volts. AC volts: 0 to 10, 50, 250, 1,000 volts. DC current: 0 to 100 mA. Resistance: 0 to 150 K ohms (mid-scale); 3 K ohms. Decibels: —10 to +22dB. Dimensions: 90x60x27 mm. PRICE: £5.97+8% VAT

POWER SUPPLY UNIT TYPE 'PPI'

Switched 3, 4.5, 6, 7.5, 9 and 12 volts at 500mA. With on/off switch and pilot light.

Size: 130mm x 55mm x 75mm approx.
OUR PRICE:
Only £6.00 + 8% VAT

C1095 20,000 opv multimeter with hinged 4-position scale for easy-reading bench use. Anti-parallax mirror, 3-colour scale, overload protection.

Ranges: DC volts: 5, 25, 50, 250, 500, 2,500 (20,000 opv). AC volts: 10, 50, 100, 500, 1,000 (10,000 opv). DC current: 50 µA, 2.5 mA, 250 mA. Resistance: 50 K, 5 meg. Decibels: —20 to +22 dB. Dimensions: 140 x 85 x 35 mm.
PRICE: £14.31 + 8% VAT

EM1200

100,000 opv multimeter. Comprehensive meter with 3-colour scale, anti-parallax mirror, taut band movement, electronic protection, reversible polarity, 15 amps AC current range. Supplied with leather carrying case, shoulder strap and probes.

DC Voltage: 0-0.15, 0.5, 1.5, 5, 15, 50, 150, 500, 1500 volts (100,000 opv). AC voltage: 0-1.5, 5, 15, 150, 250, 500, 1500 volts (30,000 opv). DC current: 10 µA, 15 µA, 500 µA, 15 mA, 500 mA, 1.5 amps, 15 amps. AC Current: 15 amps. Resistance: 0-20 K ohms, 200 K ohms, 2 megohms, 20 megohms, 200 megohms. (Mid-scale): 100 ohms, 1 K ohm, 10 K ohms, 100 K ohms, 1 megohm. Accuracy: DC-2%, AC-3%. Dimensions (inc case): 210 x 178 x 80 mm.
PRICE: £40.23 + 8% VAT.

H2009 STEREO HEADPHONES

Eagle headphones available at new reduced price.

Spec. — Frequency range: 20-20,000 Hz ±5 dB. Second harmonic distortion: 0.7% maximum. Third harmonic distortion: 1.0% maximum. Matching impedance: 8-16 ohms. Weight: 360 gm. Switching: ±5 dB @ 100 Hz (Popular), Flat @ 100 Hz (Classical), —5 dB @ 100 Hz (Vocal). These headphones have a bass cut/limit control on each earpiece.
PRICE: £15.50 + 12% VAT.

'BARGAIN TRANSFORMERS'

240v PRIMARY 12-0-12v, 500mA/SEC. Approx. size: 60 x 40 x 50mm. Fixing centres: 75mm.

PRICE: £1.80 + 8% VAT.
Also available MAINS TRANSFORMER with 18v 500mA SEC.
Price and size same as above.

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED, ALL PRICES INCLUDE POSTAGE—PLEASE ADD VAT AS SHOWN—S.A.E. WITH ALL ENQUIRIES PLEASE.
Personal Callers Welcome at: 164-166 HIGH ROAD, WOOD GREEN, LONDON N22 Phone: 888-3206 and 13 SOUTH MALL, EDMONTON, N9. Phone: 803-1685.

TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future.

Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course—or refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

Courses in
C & G Elect. Technicians
C & G Elect. Installations
Telecomms. Technicians Exams
Television Servicing
Radio Maint. & Repairs (BIET)
Pract. Radio & Electronics
Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept. TEE 30 Reading RG7 4PF.

NAME (Block capitals please) _____


ADDRESS _____

POSTCODE _____

Other Subjects _____ AGE _____

Accredited by CACC Member of ABCC

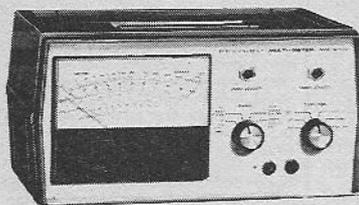
Over 200 kits in the free Heathkit Catalogue



NEW 4 Function
Solid State Multimeter
— One of a whole range
of test equipment



NEW Digital Clock —
with repeater alarm

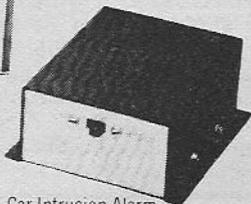


Car Intrusion Alarm
— Gives a distinctive
'yelping' sound-signal
the moment your car
is tampered with

Freezer Alarm — Gives audible signal
if freezer temperature rises to -6°C
for any reason



NEW Electronic
Chess Game

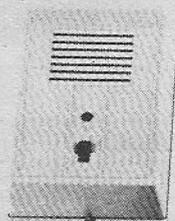

Right now, there's a brand new edition of the Heathkit Catalogue — packed with hundreds of practical and fascinating items which you can build yourself.

Send for your copy now!

To Heath (Gloucester) Ltd.
Department EE-28,
Bristol Road, Gloucester, GL2 6EE.

Please send a copy of the Heathkit Catalogue.
I enclose 11p in stamps to cover postage only.

Name

Address

**Soldering
iron offer
FREE**


When you receive
your catalogue
you'll get details of
this free offer worth
approximately £4.75.

HEATH
Schlumberger
The world's
biggest producers
of electronic kits.

**ACCESS AND
BARCLAYCARD
WELCOMED**

There are Heathkit Electronics Centres at 233 Tottenham Court Road,
London (01-636 7349) and at Bristol Road, Gloucester (Gloucester 29451).

MAINS INTERCOM

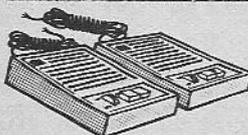

NO BATTERIES NO WIRES

The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1/2-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom between office and warehouse in surgery and in homes P. & P. 99p.

ONLY **£29.99** PER PAIR
+ VAT £3.75

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY
£14.95
+ V.A.T. £1.20

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increases efficiency in office, shop, workshop. Perfect for "conference" calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control. Conversation recording model at £18.95 + VAT £1.36. P. & P. 89p.

10-day price refund guarantee on all items.

WEST LONDON DIRECT SUPPLIES (EEL2) 169 KENSINGTON HIGH STREET, LONDON, W8
01-837 5548

ITS EASY WHEN YOU KNOW!

To avoid missing your copy of EVERYDAY ELECTRONICS—simply complete this order form and hand it to your newsagent.

ORDER FORM

To.....
(name of newsagent)

Address

Please reserve/deliver every month one copy of EVERYDAY ELECTRONICS until further notice.

My Name.....

Address

For Semi-conductors including

Small Signal Transistors
Power Semi-conductors
TTL, CMOS, I.Cs
Linear I.Cs
Signal and Power Diodes
Zener Diodes
Magneto Resistors
Magnetic Proximity Switches
Opto-electronic devices

Go to
ELECTROVALUE
TO MAKE THE BEST OF

For passive components

including
Plastic Film Capacitors
Electrolytics
Semi-precision capacitors
Transformers
Pot, R.M and Ring Cores etc.

E.E. TEACH-IN '78
Complete Kit as specified **£12.50**

Go to
ELECTROVALUE
THE PROJECTS YOU BUILD

The Open Door to Quality

It's the Electrovalue Catalogue No. 8 (4th edition black and white cover) with completely up-dated prices. 144 pages, well illustrated and informative. 40p post free with 40p voucher usable on orders for £5 or more. Send for yours now and order in confidence.

GOODS SENT POST FREE IN U.K. FOR C.W.O. ORDERS. Keenly competitive prices plus **ATTRACTIVE DISCOUNTS** and only best quality goods.

ELECTROVALUE LTD

(Dept. EE.178), 28 St. Jude's Rd., Englefield
Green, Egham, Surrey TW20 0HB
Phone Egham 3603, Telex 264475

North—680 Burnage Lane, Burnage, Manchester.
Phone (061) 432 4945.



SMALL ADS

The prepaid rate for classified advertisements is 16 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £4.00 per single column centimetre. All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

Receivers and Components

71b ASSORTED COMPONENTS £2.95. Small Audio Amplifiers, 3 transistors equivalent to AC128, OC72, with circuit. 3 for £1.300 small components, Transistors, Diodes £1.30. No Postage, list 15p refundable. Insurance add 15p. J.W.B. Radio, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

COMPONENTS FOR E.E. PROJECTS.

Component lists with prices available for all E.E. projects from October 1977 onwards, including Teach-In 78. Send S.A.E. stating project and month of publication (maximum 4 projects per S.A.E.). List sent by return together with ACE order form/catalogue.

ACE MAILTRONIX, Tootal Street, Wakefield, W. Yorks. WF1 5JR.

DISCOVER ELECTRONICS. Build forty easy projects including: Metal Detector, Wireless Transmitter, Breathalyser, Radios, Stethoscope, Lie detector, Touch time switches, Burglar Alarms, etc. Circuits, plans; all for £1.29 including FREE circuit board. Mail only. RIDLEY Photo/electronics, Box 62, 111 Rockspark Rd, Uckfield, Sussex.

I.C.s., TTL.C/Mos, Linear, Capacitors, Resistors (E12) SIL/Rectifiers, Diodes, LED, Thyristors, Zenors, Voltage Reg, DIL Sockets, Bridge Rectifiers, Potentiometers, Presets, Triacs, Diac, Plugs, Sockets, Cable, Vero. Carefully selected range, excellent despatch service. Same day turn round. S.A.E. List. Suppliers to A.E.R.E., U.K.A.E.A., Government Depts, Schools, Universities, Manufacturers. Accounts opened for trade and amateur. Join the professionals. Phone by 4 p.m. Goods out 1st class by 5 p.m. Try us and prove it!

ORCHARD ELECTRONICS

Flint House, High Street, Wallingford, Oxon. Telephone 0491-35523.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P&P. 'Brain-Freezer' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.10 plus 20p P&P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5.00 each plus 20p P&P. LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh Ewell, Surrey. (E.E.)

TRANSISTOR TESTER. Drilled and labelled case, components, construction details and transistor data. Measures GAIN and LEAKAGE, also tests DIODES. KIT—send £4.95. BUILT—£6.95. Details 2 x 9p stamps. MAGENTA ED1, 61 Newton Lays, Burton on Trent, Staffs DE15 0DW.

Large Clear L.E.D.s	25p	MINIATURE SWITCHES	
Large Red L.E.D.s	20p	Push to Test	18p
Croc Clips Red/Black	7p	Push TO Break	32p
Small Reed Switch	10p	Slide DPDT	18p
Large Reed Switch	12p	Bank of 6 Large Reed	
Magnets For Above	12p	Switches	48p
Mini Buzzer 12v A/C	50p	GPO 4 Digit Counter	
Large 250v Glass, Bright		500 Ohms 1" x 4 1/2"	42p
Neons 25p, Bases 12p		Loud Sirens 6v D.C.	30p
Japanese Radio Tuning		£1.30 ea. Buzzer Alarms	65p
Capacitors 35p, Knobs 5p		1 1/2 Volt D.C.	65p
Pots 10K, 1M, Lin	16p	Modern Calculator	
8Ω Earphone & Plug	18p	Keyboards 23 Way	55p
15 pf Tuning Caps	30p	25 Untested I.C.s.	30p
BC107/8/9, 147/8/9	15p	20 Untested AC128	30p
1N4148 8p, OA81/91	10p	30 Untested OA81	20p
Vero Pak 1 or 15	65p	40 Assortment Pak	40p
Mains Motor 250 RPM	48p	50 Assd Capacitors	40p
250v AC	48p	50 Assd Resistors	25p

Resistors 1W 5% 10 ohms—10 Meg 2p ea. Prices include VAT. Add 16p Postage.

GRIMSBY ELECTRONICS

64 Tennyson Road, Cleethorpes, Humberside. Callers to our Lambert Rd. Components shop, 100's of bargains—components, meters, ferric chloride, etc., lowest prices in S.Humberside. List No. 14 10p.

Miscellaneous

TIMESWITCHES, cheap timeswitches, Sangamo 20 amp reconditioned, guaranteed for one year. Only £3.70. Also Electric Eyes. Write: J. DONOHUE, 1 Upper Norfolk Street, North Shields, Tyne & Wear.

ENAMELLED COPPER WIRE

swg	1 lb	8 oz	4 oz	2 oz
14-19	2.40	1.20	.69	.50
20-29	2.45	1.60	.82	.59
30-34	2.60	1.70	.89	.64
35-40	2.85	1.90	1.04	.75

Inclusive of p&p and VAT. SAE brings Catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4 9BW. Reg. office 22, Coningsby Gardens.

LOW COST ALUMINIUM BOXES with lids and screws, 3x2x1 42p, 4x3x1 1/2 49p, 4x3x2 56p, 6x4x2 62p, 6x4x3 72p, 8x6x2 97p, 8x6x3 £1.08. Prices include p&p. HARRISON BROS., P.O. Box 55, Milton Road, Westcliffe-on-Sea, Essex SS0 7LQ.

100 RESISTORS 75p

1W 5% c/FILM 2-2Ω-2.2M Ω (E12)

10 each of any value

Send stamped envelope for free sample

C50 CASSETTES 30p All Cassettes in Plastic Case

690 CASSETTES 45p with Index and Screwed Assembly.

All prices include VAT. Add Postage 10p in £1

Quantity Discounts

10 Units 5%

50 Units 7%

100 Units 10%

SALOP ELECTRONICS,

23 WYLE COP,

SHREWSBURY.

Tel.53206

LIST No. 28 NOW READY. Styli illustrated equivalents also cartridges, leads, etc. Free for long SAE. FELSTEAD ELECTRONICS (EE), Longley Lane, Gatley, Cheadle, Cheshire.

RECHARGEABLE BATTERIES

'AA' Pencil (HP7) £1.32; Sub 'C' £1.64; 'C' (HP11) £2.43; 'D' (HP2) £3.56; PP3 £4.98. Matching chargers £6.33 each except PP3 charger £4.99. Charging holders for 2, 3, 4, 5 or 6 pencils 50p. 'C' & 'D' size holders, 4 cells only 80p. Prices include VAT. Add 10% post package and insurance orders under £20. 5% over £20. SAE for full details plus 75p for 'Nickel Cadmium Power' booklet. Mail orders to SANDWELL PLANT LTD., Dept. EE, 201 Monmouth Drive, Sutton Coldfield, West Midlands. Tel 021 354 9764. Callers to T.L.C., 32 Craven Street, Charing Cross, London W.C.2.

"250/12 Volt Inverters now available"

Tape Exchanges

SPEAK to the World without Licence!! WORLDWIDE TAPETALK, 35 The Gardens, Harrow; Britain's largest Tape-X change (cassette or reel).

Service Sheets

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICE for service sheets of Radio, TV etc. 75p plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 558855.

Books and Publications

RADIO BOOK SERVICE

50 Projects using IC CA3130 (R. A. Penfold)	£1.05
50 CMOS IC Projects (R. A. Penfold)	£1.05
A Practical Introduction to Digital IC's	£1.05
28 Tested Transistor Projects (R. Torrioni)	£1.05
50 Projects using Relays, SCRs & TRIACs (F. G. Rayer)	£1.20
How to build your own Metal & Treasure Locators (F. G. Rayer)	£0.95
Practical Repair & Renovation of Colour TVs (C. F. Miller)	£1.05
Fun & Games with your Electronic Calculator (J. Vine)	£0.85
How to build Advanced Short Wave Receivers (R. A. Penfold)	£1.30
Radio Antenna H'book for Long Distance Reception	£0.45
50 (Fac) Field Effect Transistor Projects (F. G. Rayer)	£1.35
Servicing Transistor Radio Receivers	£0.95
Solid State Short Wave Receivers for Beginners	£1.05

PRICES INCLUDE POSTAGE & PACKING... S.A.E. FOR FULL LIST
4 CHILCHESTER COURT, WICKHAM RD, BECKENHAM KENT BR3 20W

WHAT'S THE SECRET OF MAKING MONEY? The Knowledge, and ability, that very few people possess, to undertake work in a specialised field that is crammed with opportunities. We are supplying a MANUAL that will enable you, in your own home, WITH NO PREVIOUS EXPERIENCE, to repair VACUUM CLEANERS, DRILLS, and PORTABLE TOOLS, by showing in easy, step by step stages, how to diagnose faults, rewind ARMATURES and FIELDS and make up test equipment, 13 chapters covering test procedures, apparatus required, test charts, where to obtain materials and where to find work. Packed with diagrams and information. Get your copy now. Only £4 plus 30p P&P. CWO. COPPER SUPPLIES, 102 Parrwood Road, Wittington, Manchester 20, Dept. EE1.

Books and Publications

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4-50, request free circuit diagram. Stamp brings details unique TV publications. Ausee, 76 Church Street, Larkhall, Lanarkshire.

EVERYDAY ELECTRONICS KNOW-HOW made easy. 30-stage speedlearn program. Unique Timesaver breadboards, terminals, plans, and circuit Know-how. Ideal for beginners, students, clubs, schools, colleges. Special intro-offer £4-75. Money back if not delighted. TECHNOCENTRE (EE), P.O. Box 33, 54 Adcott Road, Middlesbrough.

For Sale

CLOSED WORKSHOP; 2N3773 215P. AD161/162 30p, BC107, 108, 109 8p, BFY51 12p, AF2.39 30p, TBA 800 70p, TBA810 90p. SAE bargain list. J.A.I., 39 Balvernie Gro, London SW18 5RR.

EVERYDAY ELECTRONICS, November 1971 (No. 1) to April 1977; OFFERS: Wrist, 55 Albany Park Road, Kingston, Surrey.

OFFERS for complete issues January 1972 to December 1977, EVERYDAY ELECTRONICS; buyer to collect. SAE. GRAY, 7 Ennerdale, Birtley DH3 2LA.

Educational

COURSES—RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination and obtain your G3 licence, with an RRC home study course. For details of this, and other courses (GCE, professional examinations, etc.), write or phone: THE RAPID RESULTS COLLEGE, Dept. JR1, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service), or phone for a prospectus only, ring 01-946 1102 (24hr recording service).

HOLIDAYS FOR BOYS, 14-16 years, July/August 1978. Tuition and practical work in Engineering (Karting), Electronics, Radio Production and Tape Recording and Photography. Nine days in Norfolk, £34. Write for free brochure. Inter School Christian Fellowship, c/o Ashcroft, Old Bolingbroke, Nr. Spilsby, Lincs.


Wanted

SURPLUS?? Turn it into cash. Phone: 0491 35529 (Oxon).

DENCO (CLACTON) LIMITED

Dept. E.E.

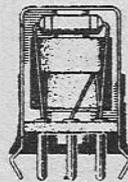357-8-9 OLD ROAD
CLACTON-ON-SEA
ESSEX CO15 3RH



Our components are chosen by technical authors and constructors throughout the world for their performance and reliability, every coil being inspected twice plus a final test and

near spot-on alignment. General Catalogue showing full product range 34p. Overseas Customers 70p, Air-Mail Post Paid.

U.K. & OVERSEAS MANUFACTURERS/STOCKISTS ENQUIRIES WELCOME

Australian Readers Please Note—Our Complete Range of Coils are available from Watkin Wynne Pty. Ltd., 32, Falcon Street, CROWS NEST, 2065, AUSTRALIA. P.O. Box 392.

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA
EEK2

Brochure, without obligation to:

**BRITISH NATIONAL RADIO
& ELECTRONICS SCHOOL,**

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ (Block caps please)

E.E. PROJECTS

AUDIO-VISUAL METRONOME. Jan. £3-98 inc. case.
PHOTOFLASH SLAVE. Dec. £3-68 inc. case. Less lead.
VHF RADIO. Nov. £10-20 inc. case.
TREASURE LOCATOR. Oct. £7-87. Case £2-26.
TRANSISTOR TESTER. Oct. £6-40. Case £2-98.
SHORT WAVE RECEIVER. Aug. £8-65. Case £1-45.
DICE. March. £4-24 inc. case.
METRONOME. May. £3-80 inc. case.

Prices inclusive. Articles extra 25p. Projects not listed, please write.
SOIL MOISTURE. June. £2-95 inc. case and probe.
PHONE/DOORBELL REPEATER. July. £4-70 inc. case.
TOUCH SWITCH. July. £8-40 inc. case.
FUZZTONE UNIT. July. £5-75 exc. case.
ADD ON CAPACITANCE UNIT. Sept. £4-50 inc. case.

Prices inclusive. Articles extra 25p each.

1978 COMPONENTS CATALOGUE • MAGENTA •

Magenta gives you a wide range of the things you need—components—tools—hardware—and lots more. First-class delivery. NO minimum order. Inclusive prices. All products stock lines. Illustrated catalogue with data. New products daily. Send 2 x 9p stamps.

This Catalogue is a MUST for constructors. Write Today!

AMPLIFIER MODULE—STEREO 1½ x 1½W. 8 ohms. Tone/Vol. controls plus Fascia 9V D.C. £4-99.
PRE-AMP—STEREO. Matches Magnetic cartridge to above amplifier. 9V D.C. £6-45.
CAPACITANCE SUB. BOX. 9 valves 1000pF to 22µF £2-95.
DIODE TESTER. With leads £1-68.
SIGNAL INJECTOR AF/RF probe and leads £4-98.
MULTIMETER. TYPE 1. 1,000 o.p.v. with probes 2" x 3½" x 1" £5-95
MULTIMETER. TYPE 2. 20,000 o.p.v. with case and probes 3" x 3½" x 12" £10-95.
ANTEX X25 SOLDERING IRON 25W. Ideal for electronics £3-68.
SOLDERING IRON STAND. ANTEX ST3 £1-55.
DESOLDER BRAID. 62p.
HEAT SINK TWEEZERS 12½p.
DRILL. 12 VOLT. 10,000 r.p.m. Hand or stand use £10-05.
DRILL STAND. Adjustable height. £5-51.
TRANSFORMER for 12V drill £8-37.
POWER SUPPLY. Safe, economical plug type 6, 7-5, 9V D.C. 300mA, with lead £3-98.
NIGHT LIGHT. Safe. Built in 13A plug. Very cheap to run £1-18.
MORSE KEY. Use with 6V buzzer for practice set. Code included. £1-18.
BUZZER. 6V. 74p.


INTERCOM. 2 station desk model. Cable and battery £5-95.
HEADPHONES. STEREO. 8 ohm. 13-15 KHz. Padded £3-85.
HEADPHONES. MONO. 2K ohms. Sensitive. £2-50.
PANEL METERS. Nominal 2" matt black Fascia. 0-50µA, 0-100µA, 0-1mA £4-12.
LEVEL METER 0-200µA, 1200 ohms £1-10.
PHONE PICK-UP COIL. 3-5mm plug. 65p.
EYEGLASS. Jewellers magnification X3. 93p.
TRIPLE MAGNIFIER. Each lens x5 magnification. £1-15.
DENTISTS MIRROR. Adjustable £1-70.
SCREWDRIVER. SET. 6 miniature jewellers type in case. £2-48.
NEEDLE FILES. 3mm square and round. 68p.
AERIAL. 6 section telescopic, 70cm. 95p.
SPEAKERS. Miniature 8 ohm 59p. 64 ohm 85p. 80 ohm £1-15.
EARPIECES. Crystal 38p, magnetic 15p. Also capacitors, resistors, semi-conductors, knobs, connectors, p.c.b. materials, potentiometers, variable capacitors, switches, cases, transformers, etc., etc.
All prices include VAT and FIRST CLASS POST. Orders under £5-00 please add 15p.

MAGENTA ELECTRONICS LTD., EAI, 61 Newton Leys, Burton-on-Trent, Staffs. DE15 0DW. 0283-65435.

TEACH-IN '78 COMPLETE KIT £13.95

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

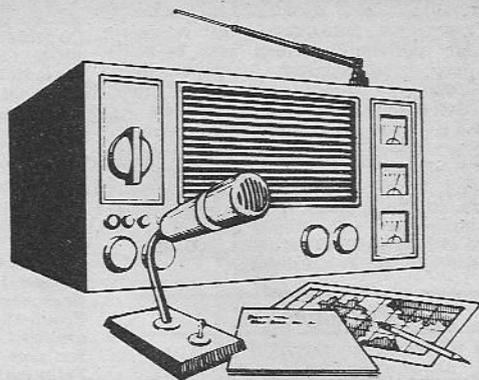

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME

ADDRESS

EELZ Block caps please

Free!

B. BAMBER ELECTRONICS

Dept. E.E., 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

A RANGE OF DRAPER TOOLS FOR THE ELECTRONICS ENTHUSIAST

MAINS TESTER SCREWDRIVERS 100 to 500V
Standard size 80p, Large 70p
RADIO PLIERS 5 $\frac{1}{2}$ " £1.60, 6 $\frac{1}{2}$ " £1.80
DIAGONAL SIDE CUTTERS 6 $\frac{1}{2}$ " £1.90
SMALL SIDE CUTTERS L2 Standard £3.70
L7 (with wire holding device) £4.10
MIDGET OPEN ENDED SPANNER SETS
0+1, 2+2, 3+3, 4+4, 6+6A SIZES £2.85
set of 5
4+4.5, 5+5.5, 4+6, 6+7, 8+9, 10+11 MM
SIZES £3.50 set of 6
MINIATURE FILE SETS Set of 6 £1.90 Set of 10
£3.25 (Round, flat, etc.)
TAP AND DIE SETS (18 piece) contain 1 each
of 0, 2, 4, 6, 8, BA SIZES in Dies, Plug Taps,
Taper Taps + American type tap wrench,
T type tap wrench, Die Holder. £11.60

LARGE ELECTROLYTIC PACKS, Contain
range of large electrolytic capacitors, low
and high voltage types, over 40 pieces, £3.90
per pack (+ 12 $\frac{1}{2}$ % VAT).

Slider Switches, 2 pole make and break (or can
be used as 1 pole change-over by linking the two
centre pins), 4 for 50p.

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES.

Aluminium Boxes with Lids.

AB10	5 $\frac{1}{2}$ x 4 x 1 $\frac{1}{2}$	60p
AB13	6 x 4 x 2	60p
AB14	7 x 5 x 2 $\frac{1}{2}$	£1.00
AB15	8 x 6 x 3	£1.30
AB16	10 x 7 x 3	£1.50
AB17	10 x 4 $\frac{1}{2}$ x 3	£1.30
AB25	6 x 4 x 3	£1.00

Vinyl Coated Instrument Cases

Light Blue tops and White lower sections. Very
smart finish.

WB1	5 x 2 $\frac{1}{2}$ x 2 $\frac{1}{2}$	60p
WB2	6 x 4 x 1 $\frac{1}{2}$	£1.10
WB3	8 x 5 x 2	£1.60
WB4	9 x 5 $\frac{1}{2}$ x 2 $\frac{1}{2}$	£1.80
WB5	11 x 6 $\frac{1}{2}$ x 3	£2.00
WB6	11 x 7 $\frac{1}{2}$ x 3	£2.25
WB7	12 x 6 $\frac{1}{2}$ x 5 $\frac{1}{2}$	£2.50
WB853	8 x 5 $\frac{1}{2}$ x 3 $\frac{1}{2}$	£2.00

MAINS TRANSFORMERS, Type 60/2, Mains
input 200-210-220-230-240-250V a.c., output 0-20-
40-60V at 2A, in Metal and Plastic case, approx.
7 $\frac{1}{2}$ x 4 $\frac{1}{2}$ x 4, fully fused (ideal for PSU) £3.00
each.

MAGNETIC DEVICES PROGRAMMERS. Contain
9 fully adjustable cams and 9 change over
micro-switches (rated approx. 1A at 240VAC)
Needs slow-motion motor to drive (not sup-
plied). Ideal for disco lights, sequence switch-
ing, etc. ex equipment £1.50 each.

VIDICON SCAN COILS (Transistor type, but no
data) complete with vidicon base £8.50 each.
Brand New.

**FULL RANGE OF BERNARDS/BABANI
ELECTRONICS BOOKS IN STOCK. S.A.E. FOR
LIST.**

NEW FOR THE VHF CONSTRUCTOR. A range of
tuned circuits on formers with slugs and screening
caps. Frequencies quoted are approximate, and range
can be greatly extended by using varying capacitors in
parallel.

Type S (1/4 in. square, dummy type).
Type SA 20 to 30MHz (when 33pF fitted in parallel).
Type SB 35 to 50MHz (with link winding).
Type SC 70 to 100MHz (with link winding).
Type SD 135 to 175MHz (with link winding).
Type M (Min. 1/4 in. square types).
Type MA 19 to 28MHz (when 33pF fitted in parallel).
Type MB 22 to 32MHz (when 33pF fitted in parallel).
Type MC 35 to 50MHz (when 33pF fitted in parallel).
Type MD 38 to 50MHz (when 33pF fitted in parallel).
Type ME 45 to 60MHz (when 33pF fitted in parallel).
Type MF 100 to 200MHz (without slug) when 0 to 30pF
variable fitted in parallel.
All the above coils available in packs of five only (same
type) at 50p per pack of 5.

SEMICONDUCTORS

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type TO5 Transistors, 12 for 25p.
BF152 (UH-F amp/mixer), 3 for 50p.
2N3819 Fet., 3 for 50p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAY31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 50p.

741CG op amps by RCA, 4 for £1.

RED LEDs (Min. type) 5 for 70p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

PLASTIC PROJECT BOXES with screw on lids
(In black ABS) with brass inserts.
Type NB1 approx. 3in. x 2in. x 1 $\frac{1}{2}$ in. 40p each.
Type NB2 approx. 3 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. 50p each.
Type NB3 approx. 4 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. 60p each.

MULLARD 85A2 85V STABILISER VALVES
(Brand New) 70p each or 2 for £1.20.

TO3 transistor insulator sets, 10 for 50p

PERSPEX TUNER PANELS (for FM Band 2
tuners) marked 80-108MHz and Channels 0-70,
clear numbers, rest blacked out, smart modern
appearance, size approx. 8 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in., 2 for
35p.

PLUGS AND SOCKETS

N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
PL259 Plugs (PTFE), brand new, packed with
reducers, 65p each
SO239 Sockets (PTFE), brand new (4-hole fixing
type), 50p each

SOLDER SUCKERS (Plunger type), Standard
Model, £5. Skirted Model £5.50. Spare Nozzles
60p each.

NEW MARKSMAN RANGE OF SOLDERING IRONS.

S125D 25W 240V £3.80.

S140D 40W 240V £4.20.

S125DK 25W 240V + bits etc.. KIT £4.90.

BENCH STAND with spring and sponge for
Marksmen irons £2.38.
Spare bits MT9 (for 15W) 50p, MT5 (for 25W) 45p,
MT10 (for 40W) 50p.

ALL PRICES + 8% VAT.

TOPZ TEMPERATURE CONTROLLED IRON.
Temperature controlled iron and PSU. £30 + VAT
(£2.40).

SPARE TIPS

Type CC single flat. Type K double flat fine tip.
Type P, very fine tip. £1 each + VAT (8p).
MOST SPARES AVAILABLE.

MULTICORE SOLDER

Size 5 Savbit 18 s.w.g. in alloy dispenser,
32p + VAT (3p).
Size C1SAV18 Savbit 18 s.w.g., 56p + VAT (4p).
1 Kg. (1 $\frac{1}{2}$ lb) 60 x 40, 20 s.w.g. on plastic reel
£3 + VAT (24p).

WELLER SOLDERING IRONS

EXPERT. Built-in-spotlight illuminates work.
Pistol grip with fingertip trigger. High efficiency
copper soldering tip.
EXPERT SOLDER GUN £100D £9.90.
EXPERT SOLDER GUN KIT (spare bits, case,
etc.) £12.90.
Spare bits 35p pair.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

MIXED COMPONENT PACKS, containing
resistors, capacitors, pots, etc. All new.
Hundreds of items. £2 per pack, while stocks
last.

ALU-SOL ALUMINIUM SOLDER (made by
Multicore). Solders aluminium to itself or
copper, brass, steel, nickel or tinplate, 16 s.w.g.
with multicore flux, with instructions, Approx. 1
metre coil 40p pack. Large reel £2.75.

VARICAP TUNERS Mullard type ELC1043/05.
Brand New, £4.40 + 12 $\frac{1}{2}$ % VAT.

**BARGAIN PACK OF LOW VOLTAGE
ELECTROLYTIC CAPACITORS**. Up to 50V
working. Seatronic Manufacture. Approx. 100.
£1.50 per pack + 12 $\frac{1}{2}$ % VAT.

OSMOR REED RELAY COILS (for reed relays up
to 1/4 in dia., not supplied) 12V, 500 ohm coil, 2 for
50p.

We now stock Spiralux Tools for the electronic
enthusiast. Screwdrivers, Nut spanners, BA and
Metric sizes, pop rivet guns, etc. S.A.E. for list.

Dubilier Electrolytics, 500uF, 450V, 2 for 50p.
Dubilier Electrolytics, 100uF, 275V, 2 for 50p.
Plessey Electrolytics, 470uF, 63V, 3 for 50p.
TCC Electrolytics, 1000uF, 30V, 3 for 60p.

Dubilier Electrolytics, 5000uF, 35V, 50p each.
Dubilier Electrolytics, 5000uF, 50V, 60p each.
ITT Electrolytics, 6800uF, 25V, high grade, screw
terminals, with mounting clips, 50p each.

**PLEASE ADD 12 $\frac{1}{2}$ % VAT TO ALL
CAPACITORS.**

TV PLUGS AND SOCKETS

TV Plugs (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for
50p.
Please add 12 $\frac{1}{2}$ % VAT.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES
Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.

Get a great deal from

Marshall's

A. MARSHALL (LONDON) LTD. DEPT. E.E.
 LONDON—40-42 Cricklewood Broadway, NW2 3ET
 Tel. 01-452 0181 Telex 21492
 LONDON—325 Edgware Road W2. Tel. 01-723 4242/3
 GLASGOW—35 West Regent Street, G2 2QD
 Tel. 041-332 4133
 BRISTOL—1 Straits Parade, Fishponds Rd. BS16 2LX
 Tel. 0272 654201

NEW CATALOGUE 77

2ND EDITION FOR AUTUMN
 OVER 8,000 LINE ITEMS
 Plenty of New Products and Ideas
 35p POST PAID (25p to callers)

TOP 400 SEMICONDUCTORS FROM THE LARGEST RANGE IN THE U.K.

EXPRESS M.O. SERVICE BY RETURN POST—all orders received despatched same day on stock items

2N696	35	2N3703	15	2N6126	45	BC159	76	BD116	1 20	BFX84	35
2N697	30	2N3704	15	40361	50	BC160	51	BC131	51	BFY35	35
2N698	62	2N3705	15	40362	55	BC161	35	BD132	54	BFX87	30
2N699	55	2N3706	16	40363	1 30	BC167	12	BD136	37	BFX98	30
2N706	28	2N3707	18	40406	60	BC168	12	BD138	37	BFY39	1 25
2N706A	28	2N3708	13	40407	52	BC169	12	BD137	38	BFY50	25
2N708	28	2N3709	15	40408	75	BC170	18	BD138	38	BFY51	25
2N709	20	2N3710	16	40409	75	BC171	16	BD139	40	BFY52	30
2N712	27	2N3711	16	40410	75	BC172	14	BD140	40	BFY53	34
2N718A	20	2N3712	1 20	40411	2 85	BC177	20	BD240	45	BRV39	50
2N720A	80	2N3713	2 30	40594	80	BC178	20	BD239	40	BSX20	33
2N914	35	2N3714	2 45	40595	90	BC179	23	BD241	45	BSX21	32
2N916	30	2N3715	2 55	40673	75	BC182	11	BD242	50	BO105	1 40
2N918	38	2N3716	3 00	AC126	45	BC192L	14	BD243	60	BO105	1 40
2N929	25	2N3717	1 45	AC127	45	BC193	11	BD244	65	BO205	2 20
2N930	25	2N3718	2 00	AC128	45	BC193L	14	BD245	65	ME0402	20
2N1131	30	2N3719	2 90	AC151V	40	BC194	12	BD248	66	ME0404	15
2N1132	37	2N3789	2 90	AC152V	50	BC194L	14	BD259	45	ME0412	20
2N1613	30	2N3790	3 10	AC153	55	BC207	16	BD530	50	ME1402	1 00
2N1711	30	2N3791	3 10	AC153K	55	BC208	16	BDY20	1 00	ME1404	1 00
2N1893	30	2N3792	3 50	AC176	50	BC212	14	BF115	38	MJ481	1 55
2N2102	88	2N3793	3 50	BC174L	65	BC212L	14	BF121	55	MJ490	1 35
2N2218	33	2N3819	36	AC187K	60	BC213	14	BF123	55	MJ491	85
2N2218A	37	2N3820	38	AC188K	60	BC213L	16	BF125	55	MJ301A	67
2N2219	35	2N3823	80	AD161	1 00	BC214	16	BF153	25	MJ340	58
2N2219A	36	2N3904	21	AD162	1 00	BC214L	17	BF154	25	MJ370	58
2N2220	30	2N3904	21	AD162	1 00	BC214L	17	BF154	25	MJ370	58
2N2221	25	2N4036	67	AF106	55	BC237	14	BF159	35	MJ371	60
2N2221A	26	2N4037	52	AF106	55	BC237	14	BF159	35	MJ371	60
2N2222	25	2N4058	20	AF124	65	BC239	15	BF160	40	MJE251	65
2N2222A	25	2N4059	15	AF126	65	BC251	16	BF161	40	MJE251	65
2N2368	25	2N4060	20	AF139	69	BC257A	17	BF167	35	MP811	35
2N2369	25	2N4061	17	AF186	50	BC258A	17	BF177	35	MP812	40
2N2369A	25	2N4062	18	AF200	1 20	BC258B	20	BF178	25	MPF13	45
2N2648	75	2N4126	17	AF239	65	BC261A	24	BF178	25	MPF102	30
2N1647	1 40	2N4289	20	AF240	1 14	BC262B	24	BF179	30	MPSA05	25
2N2904	36	2N4919	65	AF279	80	BC263C	30	BF180	35	MPSA06	25
2N2904A	37	2N4920	75	AF280	85	BC300	40	BF182	35	MPSA12	40
2N2905	35	2N4921	75	AF280	85	BC300	40	BF182	35	MPSA12	40
2N2905A	38	2N4922	55	BC108	15	BC301	40	BF183	40	MPSA55	25
2N2906	28	2N4923	70	BC109	15	BC307	15	BF184	38	MPSU05	50
2N2906A	35	2N5190	60	BC113	20	BC308	15	BF185	35	MPSU06	56
2N2907	25	2N5191	70	BC115	20	BC309C	15	BF194	15	MPSU55	55
2N2907A	25	2N5192	75	BC116	19	BC317	14	BF195	15	MPSU56	60
2N2924	15	2N5195	90	BC116A	20	BC318	13	BF196	15	TIP29A	45
2N2925	17	2N5245	34	BC117	22	BC319	17	BF197	17	LM300	98
2N3019	55	2N5294	40	BC118	20	BC328	19	BF198	18	TIP30A	49
2N3053	26	2N5295	40	BC119	30	BC337	19	BF200	35	TIP30C	65
2N3054	60	2N5296	40	BC121	45	BC336	21	BF225J	25	TIP31A	50
2N3055	20	2N5298	40	BC132	30	BC547	12	BF244	35	TIP31C	66
2N3300	20	2N5447	15	BC142	30	BC548	12	BF245	40	TIP32A	55
2N3391	20	2N5448	15	BC135	20	BC549	12	BF246	45	TIP32A	55
2N3391A	20	2N5449	19	BC136	19	BCY30	10	BF254	24	TIP38A	80
2N3392	16	2N5457	32	BC137	20	BCY31	10	BF255	24	TIP38A	80
2N3393	15	2N5458	33	BC140	35	BCY32	10	BF257	37	TIP33C	1 10
2N3394	15	2N5459	29	BC141	40	BCY33	10	BF258	45	TIP34C	1 20
2N3439	50	2N5484	34	BC142	30	BCY34	10	BF259	49	TIP35A	2 50
2N3440	64	2N5486	38	BC143	30	BCY38	2 00	BF459	50	TIP38A	2 80
2N3441	81	2N6027	60	BC147	12	BCY42	60	BF493	28	TIP41A	70
2N3442	1 35	2N6181	45	BC148	12	BCY58	25	BFS21A	2 80	TIP41C	90
2N3638	16	2N6107	42	BC149	14	BCY59	25	BFS28	1 38	TIP42A	80
2N3638A	16	2N6109	30	BC153	27	BCY70	25	BFS61	30	TIP42C	1 00
2N3639	30	2N6121	38	BC154	27	BCY71	25	BFS98	30	TIP295	85
2N3641	20	2N6122	41	BC157	14	BCY72	14	BCY72	14	TIP295	85
2N3702	13	2N6123	43	BC158	14	BD115	20	BFX30	35	TIS43	43

INTEGRATED CIRCUITS

CA3020	2 00	LM748-B	55	TAA5702-30	1 50
CA3020A	2 29	LM748N	55	TAA611B	1 85
CA3028B	1 80	LM1800	1 76	TAA621-2 15	1 50
CA3028A	1 29	LM1828	1 75	TAA661A	1 50
CA3030	1 08	LM3001N	85	TAA661B	1 50
CA3030A	1 35	LM3401	70	TAA700-3 91	1 50
CA3030A	2 00	LM3905	1 60	TAA930B	1 30
CA3045	1 40	LM3909	68	TAD100-1 95	1 30
CA3046	29	MC1035	1 75	TAA930B	1 30
CA3048	2 23	MC1303	1 03	TAA930B	1 30
CA3049	1 80	MC1304	1 40	TAD100-1 95	1 30
CA3050	2 42	MC1305	1 40	TBA1200-75	1 30
CA3052	1 62	MC1310	1 91	TBA400-2 00	2 21
CA3080	75	MC1327	1 54	TBA500-2 21	2 21
CA3080A	15	MC1330	1 00	TBA500Q	2 30
CA3086	60	MC1350	90	TBA510-2 30	2 30
CA3088	1 70	MC1351	2 10	TBA510Q	2 30
CA3089	2 52	MC1352	1 91	TBA510Q	2 30
CA3200	4 00	NE555	40	TBA520-2 21	2 21
CA3131	98	NE566	1 10	TBA520Q	2 21
LM301A	67	NE565	1 30	TBA530Q	2 30
LM301N	40	NE566	1 65	TBA530Q	2 30
LM304	2 45	NE567	1 80	TBA540-2 21	2 21
LM307N	65	SAS560	2 50	TBA540Q	2 21
LM308C	1 82	SAS570	2 50	TBA540Q	2 21
LM309K	85	SO42	2 25	TBA550-3 13	3 13
LM309K	1 85	76001N	1 30	TBA550Q	3 13
LM317K	3 00	76003N	2 20	TBA560Q	3 22
LM318N	2 26	76008K	1 50	TBA570-2 30	2 30
LM323K	6 46	76013N	1 50	TBA570Q	2 30
LM329N	1 40	76013ND	3 00	TBA641B	2 70
LM348N	1 50	76018K	1 50	TBA651-2 20	2 20
LM360N	2 75	76023N	1 45	TBA700Q	3 13
LM370N	2 50	76023ND	2 20	TBA700Q	3 13
LM371N	1 70	76033N	2 26	TBA720Q	3 13
LM372N	1 70	76110N	1 18	TBA750-2 30	2 30
LM373N	2 80	76115N	1 51	TBA750Q	2 30
LM374N	1 10	76116N	1 66	TCA160C	1 85
LM377N	1 05	76131N	1 20	TCA160B	1 85
LM378N	2 25	76226N	1 56	TCA160C	1 85
LM379S	3 95	76227N	1 20	TCA160B	1 85
LM380	90	76228N	1 41	TCA270-2 25	2 25
LM380A	98	76530N	75	TCA280A	1 30
LM381A	2 45	76532N	1 40	TCA290A	3 13
LM381N	1 60	76533N	1 20	TCA290A	3 13
LM382N	1 25	76544N	1 44	TCA560-1 75	1 75
LM384N	1 45	76545N	1 65	TCA560-1 75	1 75
LM386N	80	76546N	1 44	TCA560-1 75	1 75
LM387N	1 05	76550N	35	TCA560-1 75	1 75
LM388N	90	76550N	35	TCA560-1 75	1 75
LM389N	1 00	76570N	1 65	TCA560-1 75	1 75
LM702C	75	78620N	90	TCA560-1 75	1 75
LM709C	65	78650N	1 10	TCA560-1 75	1 75
LM709N	40	78660N	60	TCA560-1 75	1 75
LM710C	60	78660N	92	TCA560-1 75	1 75
LM710N	70	LM710N	70	TAA320A	1 61
LM720C	85	1 10	1 61	TAA320A	1 61
LM723N	75	TA350A	2 48	TAA320A	1 61
LM741C	85	TAA521-1 90	1 30	TAA320A	1 61
LM741N	40	TAA522-1 90	1 30	TAA320A	1 61
LM741B	80	TAA550	60	TAA320A	1 61
LM747N	90	TAA560-1 75	1 75	TAA320A	1 61

WE STOCK MORE

- CRYSTALS
- VALVES
- HOOKS
- KNIVES
- CABLES
- CASES
- FUSES
- METERS
- TOOLS
- SPRAYS
- PRESSES
- NEONS
- HEAT SINKS
- INDICATORS

FROM NATIONAL TEXAS INSTRUMENTS MOTOROLA SIGNETICS RCA, SGS

NATIONWIDE SERVICE

12 00 CLOCK MODULES DIGITAL


Built and tested—requires only switches and transformer to complete. 12 or 24hr alarm modules.
 MA1002F 12 hr 5in display £10 90
 MA1002H 24hr 5in display £10 90
 MA1010E 12hr 84in display £14 50
 MA1010G

MAPLIN

in a modern world of electronics

AUDIO MIXER

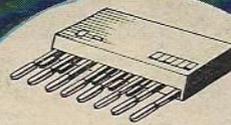A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape-recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request



PEDAL UNIT

A completely self-contained pedal unit. 13-note, 2-Octave range, 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!


BOARDS AND PCB'S

Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decs or if you prefer to make your own pcb's a range of etching systems including the novel etch-in-a-bag system, plus printed circuit transfers for that professional finish to your boards.



10 CHANNEL STEREO GRAPHIC EQUALISER

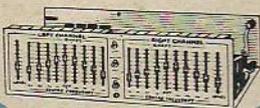A new design with no difficult coils to wind, but a specification that puts it in the top-flight hi-fi class. All this for less than £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 40p.



Who says the Maplin Catalogue's worth having?

"in our 'musts' for readers-to-collect list"—P.E.

"contains . . . just about everything the DIY electronics enthusiast requires"—P.W.

"probably the most comprehensive catalogue we have ever come across"—E.E.

"has been carefully prepared and is very well presented..."—R.E.C.

"make the job of ordering components an easy, accurate and enjoyable pastime"—P.W.

"Only one word describes the publication—superb!"—E.T.I.

OVER 60,000 COPIES SOLD DON'T MISS OUT!
SEND 60p NOW


MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3, RAYLEIGH, ESSEX SS6 8LR
Telephone: Southend (0702) 715155

Shop: 284 London Road,
Westcliff-on-Sea, Essex.

(Closed on Monday)
Telephone: Southend
(0702) 715157

THE 'DRUMSETTE' RYTHM GENERATOR

Organists, pianists, guitarists . . . an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £65 including smart teak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES 49 price 25p

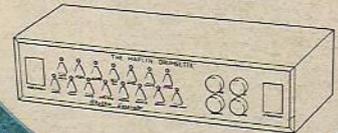

Our bi-monthly newsletter keeps you up to date with latest guaranteed prices—our latest special offers—details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME

ADDRESS.....

.....

.....

.....

.....

