

Easy to build projects for everyone


Everyday

DEC. 78
40p

ELECTRONICS

KIOSKE KIOSKS

Me. Cloud

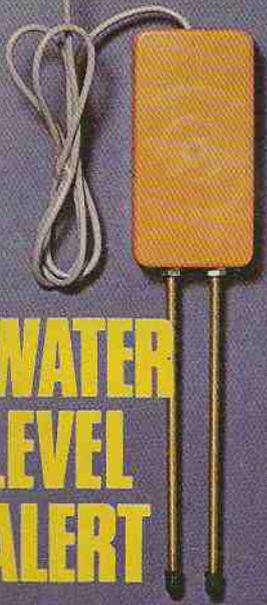

**WATER
LEVEL
ALERT**



VEHICLE IMMOBILISER

**FUZZ
'BOX**


Simple
**MICROPHONE
AMPLIFIER**

**HI-FI
PROJECT
PART 1**


EE2020 TUNER AMPLIFIER



Iron out the little problems...

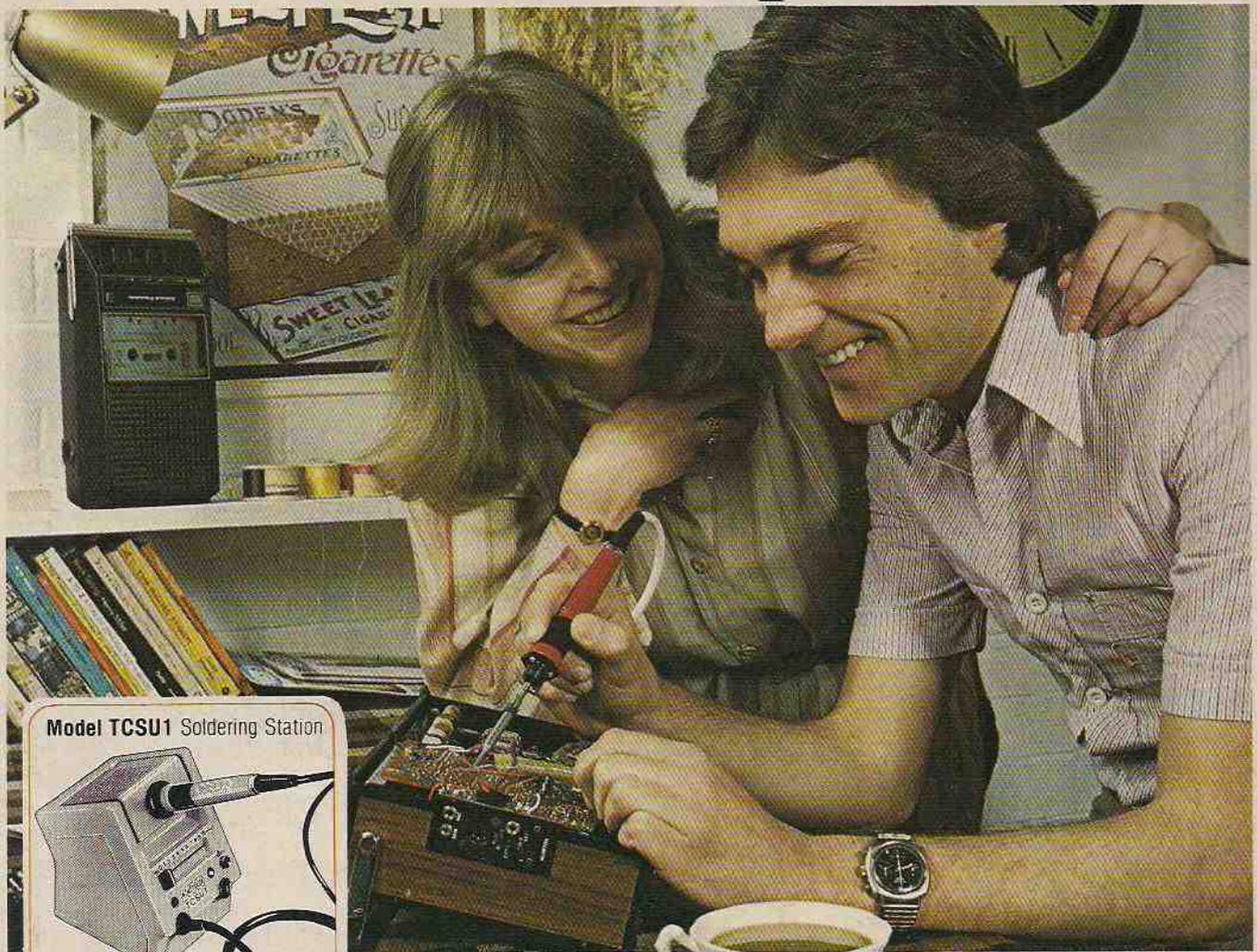

Model TCSU1 Soldering Station

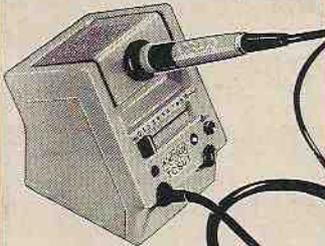

CTC 35 watt



The TCSU1 soldering station with either the XTC 50 watt — 24/26 volt soldering iron or the CTC 35 watt — soldering iron for pin point precision and exceptionally fast recovery time. We have put at least twice as much power into irons which are already well known for good recovery time. The temperature control stops them from over-heating; the "fail safe" electronic circuit provides protection even if the thermocouple fails. TCSU1 soldering station **£38.10** XTC and CTC irons **£14.85** inclusive of VAT and P & P.

Model SK3 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at **£5.99** inclusive of VAT and P & P. It makes an excellent present for the radio amateur, modelmaker or hobbyist.

Model SK4 Kit



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at **£5.99** inclusive of VAT and P & P.

Model CX 17 watts



A miniature iron with the element enclosed first in a ceramic shaft, then in a stainless steel. Virtually leak free. Only 7 1/2" long. Fitted with a 3/32" bit. **£4.15** inclusive of VAT and P & P. Range of 5 other bits available from 1/4" down to 3/64"

Model X25 - 25 watts

(illustrated)



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at **£4.15** inclusive of VAT and P & P. Range of 4 other bits available.


Model MLX Kit

The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price **£4.83** inclusive of VAT and P & P.



Model SK1 Kit

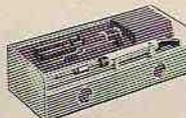This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet "How to solder". Priced at **£6.48** inclusive of VAT and P & P.



...with Antex

The ANTEX multi purpose range of soldering equipment is fast becoming a must for every home. Built with precision for long life, each iron is fully tested and guaranteed.

ANTEX soldering irons are made in England to strict local and international standards of safety.

Our name for reliability is spreading from all over Europe to U.S.A.

to Japan and to many other countries.

Stocked by many wholesalers and retailers or direct from us if you are desperate.



Mayflower House, Armada Way,
Plymouth, Devon.
Tel: 0752 67377/8
Telex: 45296

Please send me the Antex colour brochure I enclose cheque P.O. Order No. 238 1000

Please send the following
Name _____
Address _____

Antex Ltd. Freepost, Plymouth PL1 1BR Tel: 0752 67377

EE1

FOR THE BEST IN T.V. GAMES

BLASTOFF
WITH
SILICON CHIP

**THE
FORCE
IS
WITH
YOU**

**Have a
Close
Encounter
of a
completely
different
kind**

Go where no man has gone before. Pilot your own starship. Trek for light years. Penetrate the boundaries of the galaxy, but beware the gravity of a strange sun. Blast alien spaceships before you run out of missiles or fuel.

**THE NEW WORLD
OF HOME
ENTERTAINMENT**

Become a gunslinger in the Old West. Plan your strategy before the big showdown, but make sure you do not run out of bullets. Take cover behind a cactus or moving stagecoach, or you will end up on your back.

OTHER GAMES AVAILABLE

Tank Battles, Stunt Cycle, Tennis, Football, Ice Hockey, Spitfire, Mastermind, Robot War, Noughts and Crosses, Gridball, Nim.

Educate yourself and your children by solving basic maths quizzes set by the computer. Get the answer wrong and watch your T.V. screen become the school blackboard while the computer shows you the correct answer.

OTHER GAMES AVAILABLE

Breakout, Car Racing, Shooting, Volleyball, Basketball, Air and Sea Battle, Space War, Blackjack, Drag Race, American Baseball.

THIS IS JUST A SAMPLE OF THE GAMES THAT YOU CAN SEE AT

The First Specialist T.V. Game Shop — PRICES FROM £10 to £170

SILICON CHIP

The people that put respectability into TV Games


SILICON CHIP, 46 LONDON RD., KINGSTON, SURREY 01-549 6657

The latest kit innovation!

from **Sparkrite**

Sparkrite was featured by Shaw Taylor in "DRIVE IN"

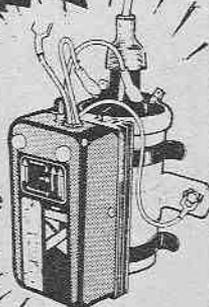the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing. (U.K. only).

Electronics Design Associates, Dept. EE 7
82 Bath Street, Walsall, WS1 3DE. Phone: (0) 614791

Electronics Design Associates, Dept. EE12
82 Bath Street, Walsall, WS1 3DE. Phone: (0) 614791

Name: _____
Address: _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P. QUANTITY REQD. Send SAE if brochure only required.

X4 KIT	£14.95	I enclose cheque/PO's for £ Cheque No. _____
TACHS PULSE SLAVE UNIT	£3.35	

PLEASE STATE POLARITY POS OR NEG EARTH.
Access or Barclaycard No. _____

SINCLAIR PRODUCTS*
Microvision TV £172. PDM35 £27.25. Mains adaptor £3.24. Case £3.25. 30kv probe £18.95. DM255 £27.50. Rechargeable battery units £7.95. Adaptor/charger £3.70. Case £8.50. 30kv probe £18.95. Cambridge prog calculator £13.15. Prog library £2.95. Mains adaptor £3.20. Enterprise Programmable Calculator £21.95.

S-DECS AND T-DECS*
S-Dec £3.39. T-Dec £4.44. u-DeCA £4.52. u-DeCB £6.73. 16dlil or 10T05 adaptors with sockets £2.14.

CONTINENTAL SPECIALITIES
PRODUCTS
EXP300 £6.21. EXP350 £3.40. EXP600 £6.80. EXP650 £3.88. EXP4PB £2.48. PB6 £9.94. PB100 £12.74. LM1 £30.95. LP1 £33.48. LP2 £19.44.

TV GAMES
Send sae for data. AY-3-8500—chip £4.95. economy kit £4. Tank battles—AY-3-8710 chip £6.90. economy kit £7.05. Stunt cycle—AY-3-8760 chip £8.90. economy kit £6.90. 10 game paddle 2 chip AY-3-8800—economy kit £12.50. Racing car chip AY-3-8893—economy kit £19.95. Modified shoot kit £4.95. Rifle kit £4.95. Colour generator kit £7.50.

MAINS TRANSFORMERS
6-0-6V 100ma 79p. 11a £2.35. 5 3V 11a £1.88. 9-0-9V 75ma 79p. 1a £1.99. 2a £2.60. 12-0-12V 50ma 79p. 100ma 90p. 1a £2.49. 13V 1a 95p. 15-0-15V 1a £2.79. 30-0-30V 1a £3.59.

JC12, JC20 AND JC40 AMPLIFIERS
A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 watts £11.60. JC20 10 watts £2.95. JC40 20 watts £2.95. Send sae for free data on our range of matching power and preamp kits.

FERRANTI Z4M4
IC radio chip £1.05. Extra parts and pcb for radio £3.85. Case £1. Send sae for free data.

PRINTED CIRCUIT MATERIALS
PC etching kits—economy £1.70. standard £3.82. 50 sq ins p.c.b. 40p. 1 lb FeCl £1.05. Etch resist pens—economy 45p. dato 74p. Small drill bits 1/32 ins or 1mm 20p each. Etching dish 63p. Laminator cutter 75p.

BI-PAK AUDIO MODULES
Send sae for data. S450 tuner £23.51. AL50 £24.86. PA100 £18.71. SP1800 £4.47. BMT30 £5.95. MK60 £38.74. Stereo 30 £20.12.

BATTERY ELIMINATORS
3-way models with switched output and 4 way multi-jack—3/4/16V 100ma £2.71. 6/12/18V 300ma £2.95. 100ma radio models same size as a PP9 battery with press stud connectors. 9V £3.35. 6V £3.35. 4 1/2V £3.35. 9V + 9V £4.50. 6V + 6V £4.50. 4 1/2V + 4 1/2V £4.50. Cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug £3.35. Car converters 12V dc input. Output 9V 300ma £1.50. Output 7 1/2V 300ma £1.50. Output 3/4/16/7 1/2/9/12V 800ma £2.50.

BATTERY ELIMINATOR KITS
Send sae for free leaflet on range. 100ma radio types with press stud connectors. 4 1/2V £1.80. 6V £1.80. 9V £1.80. 4 1/2 + 4 1/2V £2.50. 6 + 6V £2.50. 9 + 9V £2.50. Cassette type 7 1/2V 100ma with din plug £1.30. Heavy-duty 13 way types 4 1/2/6/7/8/11/13/14/17/21/25/28/34/42V. 1 amp £4.65. 2 Amp £7.25. Transistor stabilized 8-way types for low hum 3/4/16/7 1/2/9/12/15/18V 100ma £3.20. 1 Amp £8.40. Variable voltage stabilised models. 2-15V 100ma £3.60. 2-30V 1A £6.95. 2-30V 2A £10.95. Car converters 12V dc input. Output 9/7 1/2/16V 1 Amp stabilized £1.95.

BULK BUY OFFERS
Minimum purchase £3 any mix from this section. IN4148 1-4p. IN4002 3-6p. BC212 8p. 741 8dlil 15p. NE555 8dlil 23p. 723 14dlil 43p. AC76023N exact equiv. of SN76023N with improved heat sink 85p. Plastic equivs. of popular transistors—BC107 4-7p. BC109 4-7p. BCY 71 4-8p. ECV 72 4-7p. fuses 20mm x 5mm cartridge .25, .5, 1, 2, 3, 5 Amp. Quickblow type 1p. Antisurge type 3 4p. Resistors 5% E12 10 ohm to 10M. 1W 9-9p. 1W 1 1/2p. Polyester capacitors 250V/.01, .022, .033, .047mf 2-7p. 015mf 1-5p. .068mf 1-5p. 0-1mf 1-5p. 0-22mf 3p. 0-33mf 2-5p. 0-47mf 4-8p. Polystyrene capacitors E12 63V 15 to 10,000pf 2 1/2p. Ceramic capacitors 50V E12 22pf to 10000pf 1-7p. E6 1500 to 33000pf 1-7p. 47000pf 2p. Electrolytics 50V .47, 1, 1.2mf 5p. 25V 5mf, 10mf, 5p. 16V 22mf 5p. 33, 47, 100mf 6p. 220, 330mf 9p. 470mf 11p. 1000mf 10p. Zeners 400mV E24 2V7 to 33V 6-1p. Preset pots sub miniature 0-1W horiz or vert 100 to 4M 6-8p. Potentiometers 1W 4K7 to 2M2 log or lin. Single 26p. Dual 76p.

SWANLEY ELECTRONICS

DEPT. EE, 32 Goldsel Rd., Swanley, Kent BR8 8EZ
Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked * and 11% on others. Official credit orders welcome.

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

- City and Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

- Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept B268 Intertext House, London SW8 4UJ or telephone 622 9911
Subject of Interest _____
Name _____
Address _____
Tel: _____ Age: _____

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS: OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY: INSTANT P&P ADD 30p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. Send 50p for our catalogue.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12.1%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am-6.00 pm. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in μF)
400V: 0-001, 0-0015, 0-0022, 0-0033 7p; 0-0047, 0-0068, 0-01, 0-015, 0-018 9p; 0-022, 0-033, 10p; 0-047, 0-068 14p; 0-10 15p; 0-15, 0-22 22p; 0-33, 0-47 33p; 0-68 45p.
160V: 0-039, 0-15, 0-22, 11p; 0-33, 0-47 19p; 0-68, 1-0 29p; 1-5 29p; 2-2 32p; 4-7 48p.
DUBILIER: 1000V: 0-01, 0-015 20p; 0-022 22p; 0-047 26p; 0-1 38p; 0-47 48p; 1-0 175p.

POLYESTER RADIAL LEAD (Values in μF) 250V:
0-01, 0-015, 0-022, 0-027 5p; 0-033, 0-047, 0-068, 0-1 7p; 0-15 11p;
0-22, 0-33 13p; 0-47 15p; 0-68 18p; 1-0 24p; 1-5 27p; 2-2 31p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in SF) 500V: 10 40p; 47 68p; 250V: 100 65p; 83V 0-47, 1-0, 1-5, 2-2, 2-5, 3-3, 4-7, 6-8, 8, 10, 15, 22 8p; 47, 32, 50 11p; 83, 100 27p
50V: 1-0 7p; 50, 100, 220 25p; 470 50p; 1000: 40V: 22, 33, 9p; 100 11p; 220 68p; 330 62p; 470 64p; 55V: 10, 33 7p; 330, 470 32p; 1000 48p; 25V: 10, 22, 47 5p; 80, 100, 150, 220, 250, 330 10p; 1000 27p; 1500 30p; 2200 41p; 3300 52p; 4700 54p; 18V: 1-0, 47, 68 7p; 100, 125 9p; 220, 330, 470 14p; 1000, 1500 20p; 2200 34p; 10V: 100 6p; 640 10p; 1000 14p.
TAG-LEAD TYPE: 70V: 2000 86p; 4700 121p; 50V: 10,000 255p; 40V: 2500 65p; 3300, 4700 70p; 15,000 450p; 25V: 4700 48p; 2200 37p; 325V: 200+100+50+100 190p.

TANTALUM BEAD CAPACITORS: 35V: 0-1uF, 0-22, 0-33, 0-47, 0-68, 1-0, 2-2uF, 3-3, 4-7, 6-8 20p; 1-5, 10 20p; 1-5 15V: 10uF 13p each 47, 100 40p; 10V: 22pF, 33, 47, 68, 100, 3V: 68, 100uF, 20p each

MYLAR FILM CAPACITORS: 100V: 0-001, 0-002, 0-005, 0-01 4p; 0-015, 0-02, 0-04, 0-05, 0-056uF 7p; 0-1uF, 0-2 9p; 50V: 0-47 11p

MINIATURE TYPE TRIMMERS: 2-5-6pF, 3-10pF, 10-40pF 22p; 5-25pF, 5-45pF, 60pF, 88pF 38p

COMPRESSION TRIMMERS: 3-40pF, 10-80pF, 25-190pF 25p; 100-500pF 38p

POLYSTYRENE CAPACITORS: 100F to 1nF 8p; 1-5nF to 47nF 10p.

SILVER MICA (Values in pF) 3-3, 4-7, 6-8, 10, 12, 15, 22, 33, 47, 50, 68, 75, 82, 85, 100, 125, 150, 200 9p each 250, 300, 330, 360, 390, 600, 820 16p each 1000, 1800, 2000, 2200 20p each

CERAMIC TRIMMER CAPACITORS: 2-7pF, 4-15pF, 5-25pF, 8-30pF 20p

SOLDERCON PINS: 100 50p; 1000 35p

JACK PLUGS

Screened chrome	Plastic body	open metal	moulded with T-DEC	S-DEC 325*
2-5mm 12p	8p	8p	break	U-DEC 'A'
3-5mm 15p	10p	8p	contacts	450p*
MONO 23p	15p	13p	20p	U-DEC 'B'
STEREO 31p	18p	15p	24p	695p*

DIN 2 PIN Loudspkr. 3.4 S Pin Audio

Plugs	Sockets	In Line
11p	7p	14p
13p	8p	20p

CO-AXIAL (TV)

Plugs	Sockets	In Line
14p	14p	20p

PHONO assorted colours Metal Screened

Plugs	Sockets	In Line
9p	5p single	15p
12p	10p 3-way	20p

BANANA 4mm 11p; 2mm 10p; 1mm 7p; 1/2" 9p

WANDER 3 pin 7p; 4 pin 9p

JACKSONS VARIABLE CAPACITORS

Dielectric	100/300pF	140p	265pF with slow motion
500pF	15p	Drive	325p
6.1 Ball Drive	15p	0.208/176	285p
4511/DAF 115p*
Dial Drive 4103	C804-50	10 15	6/36
Drum 34mm 30p	25.50 pF	17.5p	...
0.1-365pF 245p	1.1 FT 18/16	215p*	...
0.2-365pF 275p	0.1 3 x 10pF	495p	...


DENCO COILS RDT2 92p; RDT3 91p; RDT4 91p; RDT5 91p; RDT6 91p; RDT834 91p; RDT835

DAWES ELECTRONIC

121 Dawes Road, London SW6
Tel 01 381 3975


All prices are inclusive V.A.T., please add 20p. P & P. Minimum £3.00 orders.

Transistors	BC338 9p	BD650 93p	2N2221 20p	4013 39p
BC107 11p	BC413 8p	BD677 75p	2N2221A 22p	4017 70p
BC107B 10p	BC414 8p	BF468 78p	2N2222 22p	4018 42p
BC108A 11p	BC415 8p	BD678 78p	2N2368 24p	4020 80p
BC108B 11p	BC416 8p	BD680 78p	2N2222A 23p	4022 70p
BC108C 11p	BC516 23p	BF167 24p	2N2369 24p	4023 15p
BC109B 11p	BC517 20p	BF173 25p	2N2369A 24p	4024 16p
BC109C 12p	BC545 6p	BF177 38p	2N2434 22p	4025 16p
BC114 8p	BC547 6p	BF184 33p	2N2904 22p	4027 39p
BC140 47p	BC548 6p	BF185 33p	2N2904A 24p	4030 38p
BC141 48p	BC549 6p	BF194 23p	2N2905 28p	4042 80p
BC147 10p	BC550 6p	BF185 23p	2N2905A 28p	4049 38p
BC148 8p	BC557 6p	BF196 10p	2N2906 21p	4069 18p
BC149 9p	BC558 6p	BF197 10p	2N2907 21p	4071 16p
BC157 11p	BC559 6p	BF198 17p	2N2907A 22p	4040 55p
BC158 11p	BC560 9p	BF199 17p	2N3019 30p	
BC159 11p	BC635 14p	BF240 17p	2N3904 6p	I.C.'s
BC160 21p	BC636 15p	BF241 17p	2N3906 6p	301 25p
BC161 21p	BC637 15p	BF245 47p	2N3906 6p	308 75p
BC167 9p	BC638 15p	BF254 11p	2N4402 6p	311H 44p
BC168 8p	BC639 16p	BF255 19p	2N4404 6p	312H 225p
BC169 9p	BC640 17p	BF256 47p	MJE2355 68p	324 134p
BC170 8p	BD109 76p	BF263 47p	MJE3055 68p	340K 45p
BC171 8p	BD115 43p	BF440 29p	2N3054 77p	380 40p
BC172 8p	BD127 68p	BF441 29p	2N3055 50p	387 35p
BC173 8p	BD128 68p	BF442 29p	2N3055P 77p	390 13p
BC174 9p	BD135 35p	BF450 19p	MJ2501 140p	709C 13p
BC177 12p	BD136 36p	BF451 15p	MJ3001 135p	727 38p
BC178 12p	BD137 37p	BF457 41p	MJ4031 281p	727 38p
BC179 12p	BD138 37p	BF458 49p	MJ4034 284p	733 42p
BC181 13p	BD139 37p	BF459 51p	2N2906A 22p	739 46p
BC182 9p	BD140 35p	BFW11 90p		741 23p
BC183 8p	BD142 62p	BFW12 90p	Diodes	7812 60p
BC184 8p	BD175 46p	BFW16 147p	BY127 19p	7815 40p
BC209 19p	BD176 46p	BFW30 147p	BY133 23p	7912 60p
BC212 8p	BD179 47p	BFW92 63p	BY187 150p	7918 45p
BC213 8p	BD180 47p	BFX89 75p	BY209 125p	L129 75p
BC214 8p	BD235 51p	BFY30 132p	BY255 23p	3501 120p
BC237 6p	BD236 51p	BRV39 63p		
BC238 6p	BD237 51p	BRV56 63p	Zeners 4w	
BC239 6p	BD238 51p	BU105 120p	3-3/39V 10p	
BC251 8p	BD433 45p	BU114 154p	IN914X10 40p	
BC252 8p	BD434 45p	BU126 135p	IN916X10 50p	
BC257 8p	BD435 51p	BU205 144p	IN4148X10 25p	
BC261 23p	BD436 51p	BU208 199p	IN4001 3p	
BC264 40p	BD437 54p	BU209 212p	IN4004 4p	
BC301 35p	BD438 57p	BU310 145p	IN4007 5p	
BC302 32p	BD439 58p	BU311 145p		
BC303 37p	BD440 58p	BU526 220p	CMOS	
BC304 38p	BD441 59p	2N1613 21p	4000 14p	
BC307 6p	BD442 105p	2N1711 22p	4001 14p	
BC308 6p	BD512 399p	2N1893 25p	4002 14p	
BC309 6p	BD522 475p	2N2102 25p	4006 80p	
BC327 8p	BD845 89p	2N2218 22p	4009 16p	
BC328 8p	BD846 89p	2N2218A 25p	4010 28p	
BC337 9p	BD649 93p	2N2219 22p	4011 14p	
		2N2219A 23p	4012 14p	

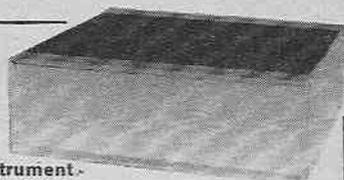

New Style Elegant Instrument Cases in anodised aluminium black vinyl top and bottoms. Gives a professional finish to your assemblies.

Type	Width	Height	Price	Type	Width	Height	Price
A	8 1/2"	3"	4-72	F	16 1/2"	4 1/2"	8-89
B	12"	3"	5-97	G	8 1/2"	6"	6-85
C	16 1/2"	3"	7-68	H	12"	6"	8-38
D	8 1/2"	4 1/2"	5-62	I	16 1/2"	6"	10-42
E	12"	4 1/2"	7-00	all cases depth 9"			please add 80p for P & P of cases

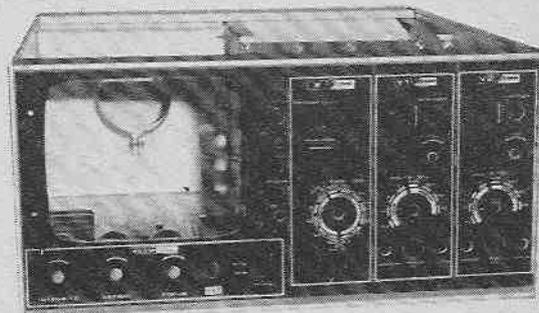

5/25Mhz 2 Channel OSCILLOSCOPE Kit
Build this kit for £85.00 later you can take the unit up to 25Mhz complete kit or parts S.A.E. for list. (assembled £150)

1Ghz Counter Kit.
Build this kit for £120 or less a professional 250Mhz counter send S.A.E. for list. (assembled £180)

Dorachime. The 8-Tune Door Chime Kit

at £12.50 + P&P
Sounds Simply Wonderful

(Offer closes 31st January 1979)

If you're the sort of person who delights in novel possessions, this will appeal to you.

Ready to surprise your visitors as their fingers press the bell-push are 8 tunes, stored in Dorachime's micro-circuitry. You can switch between them as you like, merely with a movement to the 'Tune Select' control. Tempo control speeds or slows the music to suit your mood. Ranging from 'Greensleeves' to 'Sailor's Hornpipe', the selection has been carefully made to ensure you have something appropriate for every visitor.

The effect on your guests is both stunning and amusing. It is worth the price of the Dorachime, for instance, if just once your bell can play 'O Come All Ye Faithful' to surprise your friends at Christmas.

You can see the possibilities.

Technologically advanced

You may have read in the prestige national press of the research effort currently devoted to micro-computer chips. The Dorachime is a musical revelation of its progress.

It produces, from its powerful little loudspeaker, notes similar in value to a miniature electric organ.



NOW AVAILABLE
8 Chime ready built
at £15.50 + P&P
ALSO 24 Chime version
Kit £15.95 + P&P
Ready built £19.40 + P&P

- A1 Greensleeves
- B1 God Save The Queen
- *C1 Rule Britannia
- D1 Land of Hope and Glory
- E1 O Come All Ye Faithful
- F1 Oranges and Lemons
- *G1 Westminster Chimes
- H1 Sailor's Hornpipe

* These tunes play longer if the push button is kept pressed.

MADE IN ENGLAND

You can connect the Chime in seconds to your existing bell circuitry; the only things needed to complete are two standard PP3 (P) batteries, wiring and bell push.

REMINDER

The Doram Electronic Hobbies Catalogue is now available.

FREE

Blends with any decor

Many ordinary door chimes are bulky, even unsightly. The Dorachime measures a trim 5 1/4" x 3 1/2" x 1 1/2" and its smart white lines will blend sweetly with any colour scheme. Easily assembled in a couple of hours using a soldering iron, small screwdriver, pliers and wire cutters.

Order now. Guarantee of Satisfaction.

Send the coupon immediately. Your Dorachime will be delivered within 21-28 days. If you are not completely satisfied you may return your purchase within 30 days for a full refund.

Doram Electronics Ltd., PO Box TR8, Wellington Road Estate, Wellington Bridge, Leeds LS12 2UF

An Electrocomponents Group Company

To Doram Electronics Ltd., PO Box TR8, Wellington Road Estate, Wellington Bridge, Leeds LS12 2UF.

- Please send 8-Chime Kit(s) at £12.95 ea (£12.50 + 45p p&p)
- Please send 8-Chime(s) Ready-Built at £15.95 ea (£15.50 + 45p p&p)
- Please send 24-Chime Kit(s) at £16.50 ea (£15.95 + 55p p&p)
- Please send 24-Chime(s) Ready-Built at £19.95 ea (£19.40 + 55p p&p)

Please send a Hobbies Catalogue

I enclose cheque/PO for £

I am paying via National Giro Centre Bootle Lancs. to your Account

Number 00/843/7257

Please debit my ACCESS Card No

I expect delivery within 21-28 days.

Signature.....

Name.....

(BLOCK LETTERS)

Address.....

Doram Electronics Ltd. Reg 1155866.

EE11

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround; 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS, 20 watts max. 8 ohm impedance.

£14.95 Per stereo pair + £3.40 p&p.

★ As above but complete with all woodwork in kit form, finished in simulated teak veneer, with instructions. Per stereo pair. Size approx 20" x 11" x 9 1/2". **£28.00** + £5.00 p&p.

EASY BUILD RECORD PLAYER KIT



for the D-I-Y man who requires a stereo unit at a budget price, comprising ready assembled stereo amp. module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record/replay socket including 2 SPHERICAL HIFI speakers. **£19.95** p&p £4.05

BARGAINS FOR PERSONAL SHOPPERS

PORTABLE STEREO RADIO CASSETTE RECORDER UNREPEATABLE

MW, LW, SW and Stereo VHF. 8 watts output Battery/Mains operation. 160 16 VOLT MAINS TRANSFORMER, 2 1/2 amp.

£69.95

£2.50

BSR Record auto deck on plinth with stereo cartridge ready wired. LED 5 function men's digital watch stainless steel finish.

£11.95

LCD 5 function men's digital watch stainless steel finish.

£5.95

LCD 8 Function CHROMOGRAPH men's digital watch, stainless steel finish.

£6.95

POCKET CALCULATOR. With LED display, memory and percentage key.

£13.95

AM/FM DIGITAL CLOCK RADIO. Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.

£2.95

£11.95

125 Watt Power Amp Module

£13.95

Mains power supply for above unit.

£3.50

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/4" x 14 1/2" x 7 1/4" approx.

£5.95

MULLARD Built power supply

£1.50

DECCA DC 1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape heads.

£2.95

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers

£20.00

VIDEOMASTER Super Score TV Game with pistol mains operation

£14.95

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock.

£41.95

LW, MW, SW, VHF mains/battery operation. 7" TAPE TRANSPORT Mechanism—a selection of models from

£8.95

SANYO Nic/cad battery with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 3/4" x 1 1/4" x 2" approx.

£7.50 p&p £1.50p



AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE

Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vol On/DR, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW and 5 button rotary selection switch.

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz (150mV/100K) deviation

FM signal Frequency Range (Audio) 50Hz to 17KHz within ± 1dB

Radio FM sensitivity for 3dB below limiting better than 10 uV

AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre

Size approx length 16" x height 2 1/2" x depth 4 1/2"

240 Volts AC Complete with Circuit diagram. **£19.95** p&p £2.25

Mullard

AUDIO MODULES IN BARGAIN PACKS CURRENT CATALOGUE

PRICE & AT OVER **25** PER PACK

SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1184/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£4.95** p&p £1.00

2 PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. OUR PRICE **£7.45** p&p £1.00

3 PACK 3. 1 x LP1179/2 FM Tuning head with AM gang, 1 x LP1165/1 AM/FM IF module, 2 x LP1173/10w. RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£9.95** p&p £1.00

ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. **£1.00** p&p **£1.95**

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE. **p+p 50p 95p**

THIS MONTHS OFFER

added to our bargain packs. When you buy Pack 3 at £9.95, together with a mains transformer at £1.95 and a set of controls for 95p you receive FREE a Mullard LP1400 Decoder to match. Listed at £11.90 **£12.85**

TRADE ENQUIRIES INVITED

20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak finished cabinet. Silver fascia with aluminium rotary controls/pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers. **£29.90** + £2.50 p&p

SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

FREE: 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output, 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet, p&p £2.50 in each case.

£23.00 + £2.50 (NOTE Cabinet not available separately.) **£29.00** + p&p £2.50 complete with cabinet.

SPECIAL OFFER COMPLETE WITH 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3 1/4" approx. tweeters and crossovers. **£49.00** + p&p £4.00

BUILT AND READY TO PLAY

30x30 Viscount. Available fully built and tested. **39.00** + p&p £2.50

BARGAIN PORTABLE DISCO CONSOLE



with built-in pre-amp

Here's the big value portable disco console from RT-VC! It features a pair of BSR MP 80 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simple connects into your existing slave or external amplifier.

£64.00 p & p £6.50

50 WATT MONO DISCO AMP

£29.95

P&P £2.50

Size approx 13 1/4" x 5 1/4" x 6 1/4"

50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

SPECIAL OFFER. The above 50 watt amp plus 4 Goodmans Type 8P 8" speakers. Package price **£45.00** + £4.00 P&P.

70 & 100 WATT MONO DISCO AMP

Size approx 14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls

five vertical slide controls master volume, tape level, mic level, deck level, PLUS INTER DECK FADER

for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control 70 watt (PFL) lets YOU hear next disc before fading 140 watt peak

rt in. VU meter monitors output level. **£57** p & p £4.00

Output 100 watts RMS 200 watts peak 100 watt **£65**

BDS 95 TYPE Belt drive chassis turntable

less cartridge. **£2.55** p & p **£24.95**

BSR MP60 TYPE Single play record player less cartridge **£15.95**

£2.55 p & p

CARTRIDGES to suit above Tanorel magnetic stereo. **£4.95**

GARRARD DECK CC1DA. Record changer with cue and stereo

ceramic cartridge. Size 12" x 8" approx. **£7.95**

£2.00 p & p

BARGAINS FOR PERSONAL SHOPPERS

GARRARD 86SB Deck **£26.95**

GARRARD 355S Deck **£24.95**

GARRARD SP25 MKIV Deck with Shure head. **£25.95**

Plinth and cover for BSR decks **£6.00**



323 EDGWARE ROAD, LONDON W2

21 B HIGH STREET, ACTON W3 6NG


ALL PRICES INCLUDE VAT AT 12 1/2%

All items subject to availability. Price correct at 1.11.78 and subject to change without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON: Mail Order only. No callers. GOODS NOT DESPATCHED OUTSIDE UK

ANNOUNCING

THE NEW EUROREADBOARD

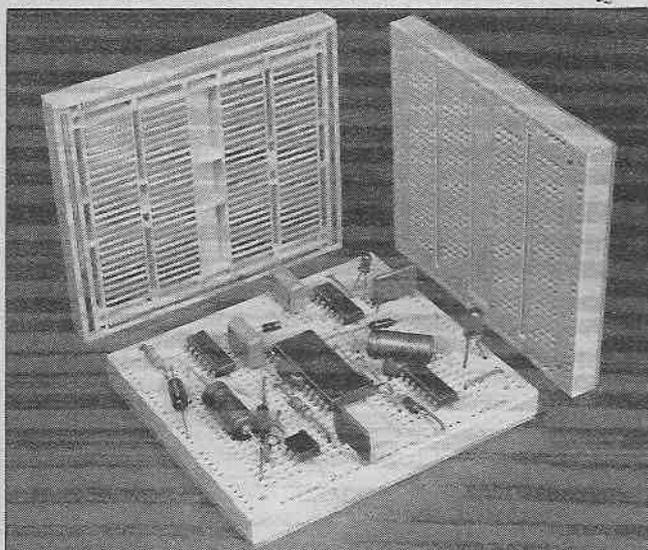

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points.

4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

Double-sided, nickel silver contacts for long life (10K insertions) and low contact resistance (<10m.ohms)

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

What other breadboarding system has as many individual contacts, offers all these features and only costs £5.80 inclusive of VAT and P.P. — NONE.

At £5.80 each The EuroBreadBoard is unique value for money. At £11 for 2 The EuroBreadBoard is an indispensable design aid.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent, DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

Please send me 1 EuroBreadBoard @ £5.80 Please
or 2 EuroBreadBoards @ £11.00 Tick

(All prices include VAT and P.P., but add 15% for overseas orders).

Name

Company

Address

Tel. No. EE12/78

Please make cheque/P.O.'s payable to David George Sales

the **MIGHTY MIDGETS**



Please quote your number when ordering

**MINIATURE
SOLDERING
IRONS AND
ACCESSORIES**



	RETAIL PRICE each inc. v.a.t.	POSTAGE extra.
NOW AVAILABLE 18 watt Iron for 12 volts	£3.78	22p
SPARE BITS	44p	—
SOLDER: SAVBIT 20'	52p	9p
" 10'	26p	4p
LOWMELT 10'	65p	9p

BIT SIZES: No.19 (1.5 mm) No. 20 (3 mm)
No.21 (4.5 mm) No. 22 (6 mm)

From your Local Dealer or Direct from Manufacturers

S. & R. BREWSTER LTD

86-88 Union St. Plymouth PL1 3HG

Tel: 0752 65011 **TRADE ENQUIRIES WELCOME**

NEW! **BUILD-IT-YOURSELF TEST GEAR KIT**

BASIC SERVICING INSTRUMENTS WITH EASY STAGE BY STAGE BUILDING INSTRUCTIONS—IDEAL FOR THE AMATEUR

MULTI RANGE TEST METER

A general purpose meter covering all usual ranges of A.C. and D.C. volts current and resistance measurements

AUDIO SIGNAL GENERATOR

New design covering 10Hz to 10KHz and variable output. Distortion less than 0.01% Ideal for HIFI Testing.

OSCILLOSCOPE

A basic 3" general purpose cathode ray oscilloscope for simple testing and servicing work. Sensitivity 0.3 volts/cm

SEND NOW FOR FREE DETAILS

To LERNAKITS, P.O. Box 156, Jersey.

Name

Address

EEL12

ELECTROVALUE Buying Guide

Section 5

If you have bought from us before, you will know just how large and varied our stocks are. For those who have yet to know, we are publishing a series of five advertisements month by month to give up-to-date information and prices on the most important items we carry. These advertisements will appear in stepped rotation in five journals — E.T.L., Elektor, Practical Wireless,

Practical Electronics and Everyday Electronics, so that the complete series will be available each month. In this way, no matter which journals you read, BY DETACHING AND SAVING THESE PAGES, YOU WILL HAVE A VALUABLE AND COMPREHENSIVE MONEY SAVING CATALOGUE. Next month — Section One.

HARDWARE/SOLDER TOOLS

SOLDER TOOLS

ORYX50 Temp. controlled
Spare element **£8.90N**
Bits (11 types) **£9.0pN**
ORYX Super 30
Spare element **£3.50N**
Bits as for ORYX50

ISO-TIP Quick Charge cordless iron **£18.50N**
Bits micro 7566 **£2.30N**
fine 7545 **£2.30N**
h.d. 7546 **£2.30N**
Std. 7535 **£2.30N**
PC drill attachment 6500 **£10.60N**

Spare bulb **35pN**
ERSA Sprint
Solder gun **£8.62N**
Spare element **£5.00N**
Bn No. 862VN **40pN**
ERSA solder station
Temp. controlled iron with stand **£59.00N**

GREENWOOD PYROMETER **£25.00N**

DESOLDER TOOL
SR3A **£5.95N**
Spare nozzle, PTFE SR3AN **65pN**
ANTEX C-240V 15W **£3.60N**
Spare element **£1.60N**
Nickel plated bits **46pN**
No. 2 094, No. 4 187, No. 6 047
Iron coated bits **46pN**
No. 102, 104, 106
ANTEX CCN-240V **£3.80N**
(low capacitance) 15W
Spare element **£1.90N**
Iron coated bits **46pN**
1100 094, 1101 225, 1102 187

ANTEX CX 240V **£3.60N**
Spare element **£1.60N**
Bits for CCN above
ANTEX X25-240V 25W **£3.60N**
Spare element **£1.60N**
Iron coated bits **50pN**
50 094, 51 125, 52 187
ANTEX STAND ST3 **£1.50N**
No. 665 Sponge **6pN**

SOLDERSTAT RANGE
HMS 240V 15W **£4.75N**
HMS 240V 24W **£4.75N**
HMS 110V 16W **£4.75N**
HMS 110V 24W **£4.75N**
Spare elements **£2.35N**
Nickel plated bits
2037 3 2mm **80pN**
2038 2 4mm **80pN**
2003 2mm stub **80pN**
Iron plated
2032 4 5mm **£1.90N**
2033 6 5mm **£1.90N**
IC desolder head for HMS
Irons
14-way **£5.70N**
16-way **£5.70N**
HMS 240V Solder Kit in presentation box **£8.90N**
HMS 12V solder kit in wallet **£7.60N**

POT CORES
FERRITES
BOOKS
Latest price list of all ranges free on request.

VERO PRODUCTS

VEROBOARD
0.1" matrix copper clad 3.75" x 2.5" **46p**
5" x 2.5" **55p**
5" x 3.75" **55p**
5" x 3.75" **62p**
8.45" x 1.5" **53p**
DIP-BOARD **£2.24**
VQ Dip-Board **91p**
24-way plug-in **£2.20**
32-way **£2.40**
EURO Dip-Board **£3.57**
0.1" matrix unclad.
3.75" x 2.5" **31p** 5" x 3.75" **50p**
EURO Board **89p**
0.15" matrix, copper clad
3.75" x 2.5" **30p** 5" x 2.5" **50p**
3.75" x 3.75" **50p** 5" x 3.75" **67p**
8.45" x 1.5" **53p**
0.2" matrix, copper clad
5" x 3.4" **76p**

PIN INSERTION TOOLS
No. P111 for 0.040" pins (0.1" matrix) **£1.10**
No. P115 for 0.052" pins (0.15" matrix) **£1.10**
SPOT FACE CUTTER
Suitable for any matrix **81p**

TRANSFORMERS
All mains transformer primaries suitable for 240V input except for 50TS2A
GP302 30V 2A tapped at 12, 15, 20, 24V **£4.80**
GP501 50V 1A tapped 19, 25, 33, 40V **£4.30**
GP502 50V 2A tapped 19, 25, 33, 40V **£6.30**
GP601 60V 1A tapped 24, 30, 40, 48V **£4.60**
GP602 50V 2A tapped 24, 30, 40, 48V **£6.70**
50TS 50V 2A tapped 25, 45V Pri/sec shield **£6.55**

PRINTED CIRCUIT MATERIALS
COPPER CLAD BOARD 300 x 150mm
Single Sided **£1.65**
SRBP 85p; Fibreglass **£1.00**
Double sided SRBP **£1.00**
UNCLAD SRBP 300 x 150mm **56p**
FERRIC CHLORIDE, Lab. grade 100gm pack **47p**; 500gm jar **£2.30**
POSITIV-20 Aerosol, 75cc with instructions **£1.30**
ETCH RESIST PEN
Dacon With spare tip 73, 00 63.00 **85p**
SILVER CONDUCTIVE PAINT
3gm. vial Elecotip 340 **£1.92** **£1.68** **£2.20**

TERMINAL PINS
(Not made by Vero)
0.040" dia for 0.1" matrix per 100 **35p** per 500 **£1.15**
0.052" dia for 0.15" matrix per 100 **40p** (Both types double ended)
VEROBOX STANDARD BOXES
High Impact polystyrene light grey top, dark grey bottom section.
Type L W H
2514F 100 50 25 **£1.64**
2516G 100 50 40 **£1.86**
2518H 120 65 40 **£2.07**
2520J 150 80 50 **£2.35**
2522K 188 110 60 **£3.13**
VEROBOX CASES
Constructed from ABS material light grey top & dark grey bottom section. Anodised all front and rear panels Internal guides for PC boards.
Type L W H D
1237J 154 40 85 **£2.56**
1238D 154 60 85 **£2.82**
1239K 154 80 85 **£3.38**
1410J 205 40 140 **£3.53**
1411D 205 75 140 **£3.96**
1412K 205 110 140 **£5.12**

RELAYS
MINIATURE CONTINENTAL TYPE
Type R42 12V 185n 2 C/OE **1.80**
Type R44 12V 185n 4 C/OE **2.00**
PC socket type P40 **97p**
Ordinary wiring kit, W40 **88p**
Mounting strip 6 posn R40 **26p**
PIGMY MAINS RELAY 3 C/O 10 amp 6V 29n, 12V 110n, 24V 475n all d.c. each **£2.30**
240V a.c. 8200n coil **£2.55**

REED RELAYS open construction
5V 106n CSA5 single n/o **90p**
12V 645n CSA 12 single n/o **90p**
5V 57n CDA5 double n/o **£1.28**
12V 320n CDA 12 double n/o **£1.19**
REED RELAYS enclosed type n/o
LPS12 single 590n **98p**
LPD12 double 355n **£1.32**
LATCHING RELAYS enclosed n/o
CLA5, 5V 400n **£2.30**
CLA12, 12V 225n **£2.30**

SLOPING FRONT PLASTIC CASES
The 1798k has white top and grey bottom section, the 2523E has light grey top and dark grey bottom section.
Both have anodised aluminium panels.
Type W H1 H2 D Price
1798K 171 38 75 121 **£4.19**
2523E 220 52 100 156 **£6.36**

18" CARD/FRAME CASE SYSTEM
accepts plug-in modules and standard European size circuit boards.
Light blue with natural anodised aluminium end plates.
Can be rack-mounted.
Type Item Price
3841L Case **£20.71N**
3842F End plate angles (pr.) **83pN**
3843A 8" Module **£4.00N**
3844G 4" Module **£3.05N**
3845B 2" Front panel **£1.02N**
3846H 1" Front panel **97pN**
3979K Board for module **£1.39**
1034E Veroboard, clad **£1.42**
1041J DIP-board **£3.59**
0267H 31-way plug **97pN**
0258C 31-way socket **£1.06N**

EUROCARD CONNECTORS
2876D 64-way plug **£2.47N**
2874C 64-way socket **£4.48N**

NEW ANOTHER SPECIAL FROM ELECTROVALUE
WE ARE NOW NATIONAL DISTRIBUTORS FOR

NASCOM 1 MICROCOMPUTER KITS

FOR DELIVERY FROM STOCK
NETT PRICES FROM £187.50 + V.A.T.
QUANTITY DISCOUNTS
TRADE ENQUIRIES INVITED

50TS2A 50V 2A (110/120V pri) tapped 25, 45V Pri/sec shield **£6.55**
28T05 12V, 12V, 2.0-2V 0.5A **£3.85**
28T1 12V, 12V, 2.0-2V 1A **£4.90**
28T2 12V, 12V, 2.0-2V 2A **£5.30**
12T05 6V 6V, 0.5A **£3.30**
CT1 17V 1A charger duty tapped 9V **£2.95**
CT2 17V 2A charger duty tapped at 9V **£3.25**
CT4 17V 4A charger duty **£3.85**
FT1 6.3V 1.5A **£2.45**
GP12 12V 1 5A **£2.30**

606/1 6-0-6V 100mA **£1.00**
MT280 6V, 6V, 250mA **£1.40**
909/1 9-0-9V 75mA **£1.00**
GP909 9-0-9V 0.5A **£2.10**
12012/1 12-0-12V 50mA **£1.00**
12010 12-0-12V 100mA **£1.20**
MT150 12V, 12V, 150mA **£1.70**
151A 15-0-15V 1A **£3.20**
GP202 20-0-20V 0.75A **£2.30**
301A 30-0-30V 1A **£3.80**
Miniature L.S. transformer **LT700** Pri. 1K2 C.T. Sec. 3.2n **39p**

SWITCHES
ERG Dual in Line
One pole change over SDC1 **42p**
Two-SDC2 **78p** 3—SDC3 **£1.08**
On Off 2 pole SDC2 **42p** 4 pole SDC4 **75p** 6p SDC6 **£1.08** 8p—SDS8 **£1.32**
Multiple — 1p/8 way DS16A1—9 **99p** 2p/4W DS 16A2-4 **£1.08**
ROTARY MAINS
Lorin MS 4 amp **48p**
WAVECHANGE
Lorin CK series, MBB contacts
12W **37p** 1p
6W **37p** 2p
4W **37p** 3p
3W **37p** 4p
ROTARY SWITCH KIT Type RA
6 wafers **60p**
RA Wafers MBB
1P 1W or 2P 5W **66p**
RA Wafers BSM
1P 12W, 2P 6W, 3P 4W, 4P 3W, 6P 2W **66p**
RA Shorting wafer, MBB
Rotating open-circuit **66p**
PUSH BUTTONS
Standard Size
SSP10, 250V 3A a.c. push on, push off panel hole 0.5" **59p**
SSP11, as SSP10 push to make **52p**
Sub-Miniature 250V 0.5A a.c. 8531 push to make **62p**
8533 push to break **62p**
(Panel hole 0.25")
CASTELCO RANGE 250V 1A a.c.
0.375" hole with long white fixing ring unless otherwise fixed
No. 2644 SP make **18p**
No. 3244 DP make **34p**
No. 2648 SP break **18p**
No. 3248 DP break **34p**
No. 2634 SP on/off **30p**
No. 3234 DP on/off **30p**
No. 4434 as 3234 but switch sections reversed **30p**
No. 4444 as 3244 but switch sections reversed **34p**
Spare rings in black, red, yellow, green, blue, white or pink **each 1p**
TOGGLE 250V 1.5A a.c.
Chrome finish
1011C SPST **56p**
1016C SPDT **61p**
1019C SPDT centre-off **64p**
409 DPDT **77p**
Sub-Miniature 250V 2A a.c. Panel hole 0.25"
S7101 SPDT **63p**
S7201 DPDT **84p**
S7203 DPDT centre-off **84p**
S7205 DPDT biased each side **£1.20**
S7207 DPDT biased one side **£1.51**
S7211 SP 3-way **£1.10**
S7301 3PDT **£1.42**
S7401 4PDT **£1.80**
MICROSWITCHES SPDT
SSU01 button, lever or roller **85p**
TIME SWITCHES (Smith's)
For electrical use, 13A rating
IMERSET for wired-in situations, 2 on & 2 off actions per day **£11.60N**
AUTOSET 13A socket outlet. Otherwise as Imerset **£10.95N**

MEET US AT BREADBOARD '78—STAND B8

Post Orders & Communications to Dept. EE12

*GOODS SENT POST FREE U.K. on C.W.O. orders over £5 list value. If under, add 27p handling charge.
*ATTRACTIVE DISCOUNTS on C.W.O. orders — 5% where list value is over £10, 10% where list value is of £25.
*TOP QUALITY MERCHANDISE — ALL BRAND NEW GUARANTEED.

*V.A.T. — 8% to value of order. For items marked *, add 12½%
*FOR ACCESS OR BARCLAY-CARD orders, just phone or write your number.
No discounts allowable on prices marked Net or N.

TEAR OUT AND TAKE GOOD CARE OF THIS PAGE AND REMEMBER TO LOOK OUT FOR NEXT MONTH'S ADVERTISEMENT TO ADD TO IT
OUR COMPUTER-AIDED SERVICE TAKES GOOD CARE OF YOUR ORDER NO MATTER HOW LARGE OR SMALL.

ELECTROVALUE LTD
28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 2644475
Northern Branch - 680, BURNAGE LANE, BURNAGE, MANCHESTER M19 1NA(061)432 4945

EDITOR

F. E. BENNETT

ASSISTANT EDITOR

B. W. TERRELL B.Sc.

PRODUCTION EDITOR

D. G. BARRINGTON

TECHNICAL SUB-EDITOR

T. J. JOHNSON G8MGS

ART EDITOR

R. F. PALMER

ASSISTANT ART EDITOR

P. A. LOATES

TECHNICAL ILLUSTRATOR

D. J. GOODING

EDITORIAL OFFICES

Kings Reach Tower,
Stamford Street,
London SE1 9LS
Phone: 01-261 6873

ADVERTISEMENT MANAGER

V. PIERI
Phone: 01-261 6727

REPRESENTATIVE

N. BELLWOOD
Phone: 01-261 6727

CLASSIFIED MANAGER

C. R. BROWN
Phone: 01-261 5762

MAKE-UP AND COPY DEPARTMENT

Phone 01-261 6035

ADVERTISEMENT OFFICES

Kings Reach Tower
Stamford Street,
London SE1 9LS

Projects... Theory ... and Popular Features ...

Taking into account the large numbers now participating in this hobby it must be a fair assumption that the majority of home constructors operate on what might be termed a modest level, that is to say they derive ample satisfaction through building small or medium sized low cost projects and items of equipment. The average constructor we reckon builds a couple of such projects or so each month as the fancy or need of the moment dictates. Typically, each project will take a few evenings or a weekend to complete.

EVERYDAY ELECTRONICS serves the requirements of this great band of enthusiasts who want to make use of modern technology for their own purposes, yet without excessive or total committal of either their spare time or spare cash to this one area of interest.

Having said that we know there also exists an appreciable number of constructors who are deeply absorbed in electronics and who are quite willing to devote the maximum time and effort possible in pursuit of what is, for them, a main leisure activity.

Requests reach us from time to time from representatives of this "minority." Overall, what they ask for is the occasional heavyweight project—something they can get their teeth into, a meal as distinct to a snack or a "starter." Well these requests have not fallen upon unsympathetic or unheeding ears, and after careful deliberation we now launch a major pro-


ject series warranted to satisfy the most ravenous constructor. We refer to our *2020 Tuner Amplifier*.

This comprehensive hi-fi equipment will appeal to those who desire a major building job to tackle during the coming winter months. In the *Twenty-twenty* we offer them an ambitious and worthwhile project that should give much enjoyment, exercise their practical skills and broaden their experience during its construction; and be a lasting source of satisfaction and pleasure upon its completion. But we do emphasise that this is a project for the experienced constructor.

To return to our "average" constructor, previously defined, who represents the majority: we are sure the *Twenty-twenty* opening article will provide interesting and instructive reading between those practical sessions occupied in building the *Fuzz Box*, the *Mini-Module* or whatever else takes your immediate fancy from our enticing assortment of projects listed on the facing page. In any event do carefully preserve your copies of EE, for who knows, you may be tempted by the big one ere the series has run its course.



Our January issue will be published on Friday, December 15. See page 865 for details.

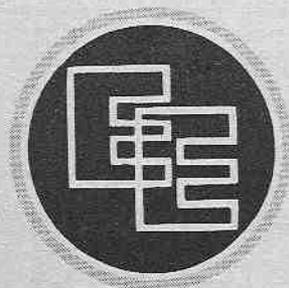**Readers' Enquiries**

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

Telephone enquiries should be limited to those requiring only a brief reply. We cannot undertake to engage in discussions on the telephone, technical or otherwise.

Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

Everyday ELECTRONICS

VOL. 7 NO. 16

DECEMBER 1978

CONSTRUCTIONAL PROJECTS

VEHICLE IMMOBILISER Protection for your car by G. D. Southern	850
FUZZ BOX A music effects unit for the pop group by E. M. Lyndsell	854
MINI-MODULE: 3—MICROPHONE AMPLIFIER For the newcomer (and others) by George Hylton	862
WATER LEVEL ALERT A simple solution to the overflow problem by A. R. Winstanley	866
EE2020 TUNER AMPLIFIER Part 1: Introduction and technical description by E. A. Rule	872
AUDIBLE FLASHER An add-on warning to your car indicators by B. N. Ryerson	883

GENERAL FEATURES

EDITORIAL	848
SHOP TALK New products and component buying problems by Dave Barrington	857
DOING IT DIGITALLY Part 3: TTL clock and latch by O. N. Bishop	858
JACK PLUG AND FAMILY Cartoon by Doug Baker	863
SQUARE ONE Beginner's page. Buying components; Soldering	864
FOR YOUR ENTERTAINMENT Paging systems—2	869
EVERYDAY NEWS What's happening in the world of electronics	870
BRIGHT IDEAS Readers' hints and tips	880
COUNTER INTELLIGENCE A retailer comments by Paul Young	884
CROSSWORD No. 10 by D. P. Newton	884
RADIO WORLD A commentary by Pat Hawker G3VA	886
BOX IT Making your own cabinets by George Hylton	889
WORKSHOP MATTERS Fuses by Harry T. Kitchen	893
INDEX FOR VOLUME 7	894

Back issues of **EVERYDAY ELECTRONICS** June 1977 onwards (October to December 1977, January to March 1978 NOT available) are available world-wide at a cost of 60p per copy inclusive of postage and packing. Orders and remittance should be sent to: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.









Binders for Volumes 1 to 7 (state which) are available from the above address for £2.85 inclusive of postage and packing.

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



VEHICLE

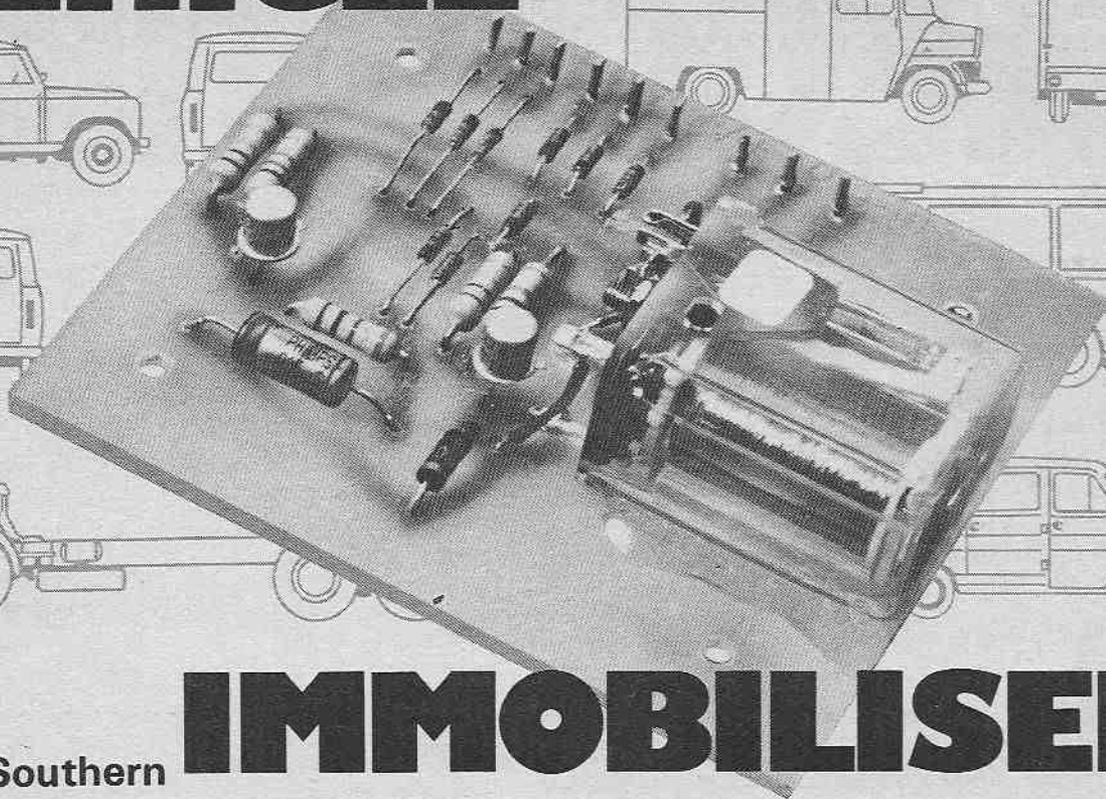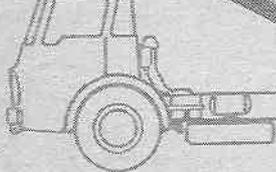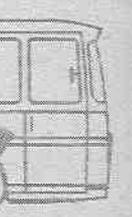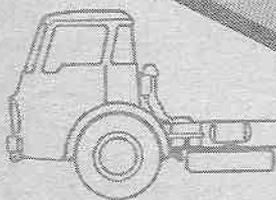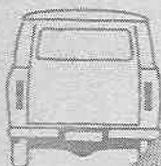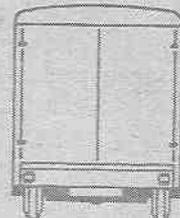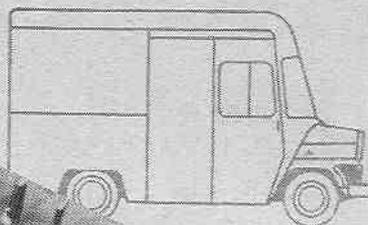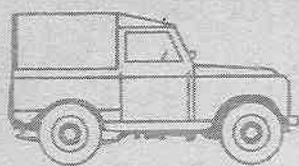

By
G. D. Southern

IMMOBILISER

EVERY day an average of 62 cars are stolen in the area where the author lives. It is claimed that at least 94 per cent of these cars are returned to their legal owners in due course. The majority of cars stolen are used by members of the community for joy-riding or late-night transport. Some of the cars returned have been driven to a remote area and accessories removed from them before the vehicle was abandoned.

The unit to be described here will offer some protection against theft by automatically immobilising the ignition system of the vehicle each time the ignition is switched off. Its degree of protection is far greater if the device is used with an electronic ignition system, especially one of the contactless type. With a conventional ignition system, the first thing a car thief will attempt is to bypass the ignition switch of the vehicle with a lead from the battery to the ignition coil.

With a contactless electronic system the above link will not have any effect and the car thief will have to find and eliminate the isolation system. This delays the

thief further and as time is usually at a premium, it should prove to be an adequate deterrent.

One of the main advantages of the immobiliser is that no hidden switches or links are required. When the ignition is switched off, the engine is immediately immobilised. If the ignition is switched on again the engine will not start.

In order to start the engine the correct accessory switches must be operated before the ignition is switched on. If the ignition is switched on first before the relevant accessory switches are operated, the ignition system will still remain immobilised. So there is no point in a car thief switching the ignition on and then searching for a sequence of accessory switches.

COMPONENTS
approximate
cost **£3.50**
excluding case

CIRCUIT DESCRIPTION

The complete circuit is shown in Fig. 1 and for the purpose of the following explanation, resistor R3 is considered to be open circuit.

When capacitor C1 is discharged, the initial charge current will be at a maximum value, whereas when it is fully charged, the charge current will be at a minimum value, typically just adequate to overcome leakage losses. The charging circuit for the capacitor is via diode D8, resistor R4 and the parallel combination of resistor R5 with the base/emitter junction of transistor TR2.

Thus when the ignition is switched on, capacitor C1 will commence charging and transistor TR1 will tend toward saturation. The speed of transition from cut off to saturation will be limited by the inductive value of the relay coil.

At approximately 10 to 15 milliseconds after the closure of the ignition switch, the relay contacts will close. Once the contacts have closed, the base current for transistor TR1 is supplied from the positive line via the relay contacts, diode D9 and resistor R4, thus "latching" the circuit. The time

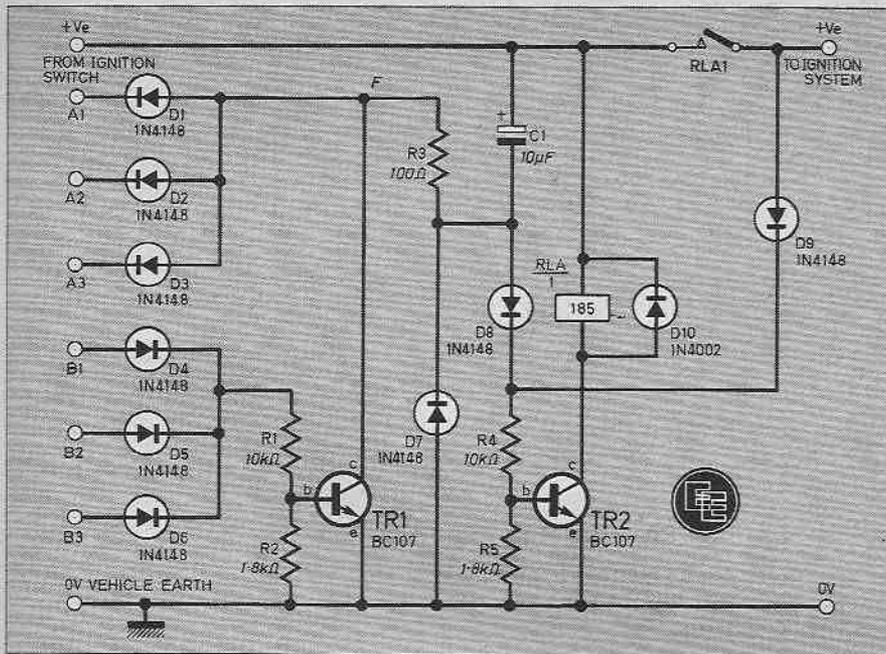


Fig. 1. Complete circuit diagram of the Vehicle Immobiliser.

constant of the charging circuit for capacitor C1, via diode D8, resistor R4 etc is far longer than the operate time of the relay, thus allowing the relay to operate and "latch".

Now it can be seen that if the capacitor is charged in a shorter period than the operating time of relay RLA1, the relay will not operate.

TRUTH TABLES

With reference to the Truth Table, Fig. 2a., assume that inputs A1, A2 and A3 equal to +12V and C1 is discharged. The "0" level in the truth table is considered to be 0 volts and the "1" level is considered to be the battery voltage of the vehicle. From the Truth Table it can be seen that the part of the circuit consisting of diodes D4, D5, D6 and resistors R1 and R2 together with transistor TR1 and resistor R3 form a NOR gate. Thus when all inputs are equal to 0, the collector voltage of TR1 will be high, equal to 1.

From the second Truth Table, Fig. 2b it can be seen that the circuit consisting of diodes D1, D2, D3 resistor R3 and the collector/emitter circuit of TR1 form an AND gate. Thus when inputs A1, A2 and A3 are equal to 1, the output voltage at point F will be equal to 1.

To demonstrate the overall operation of the circuit, consider a case where the brake light

circuitry is connected to input A1 as illustrated in Fig. 3a with all other inputs left disconnected.

When the ignition is switched on, capacitor C1 is charged via resistor R3, diode D1, and the filaments of the lamps, providing the brake light switch is open. Thus the capacitor is charged before the relay can operate, so the ignition will remain disabled even though the ignition switch is on.

If the authorised driver now realises his/her mistake, the ignition switch would be switched off and the correct sequence of switching attempted. However, this would still not operate the relay because capacitor C1 would still be charged. To overcome this problem a further diode has been added to the circuit, D7.

When the ignition switch is switched off, a discharge path is provided for capacitor C1 through external loads, for example the vehicle's ignition system via diode D7.

Now if the ignition is switched off, the brake light switch closed and the ignition switched on again, the ignition system will function correctly. When the brake light switch is closed before the ignition switch is switched on, the charging path for C1 is now via diode D8, resistor R4 etc, so the relay can operate.

Similarly if inputs A1, A2, A3, B2 and B3 are open circuit and for instance the screen-wash pump

TRUTH TABLES

INPUTS			OUTPUT
B1	B2	B3	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

(a)

Fig. 2a. Truth Table for a NOR gate.

INPUTS			OUTPUT
A1	A2	A3	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(b)

Fig. 2b. Truth Table for an AND gate.

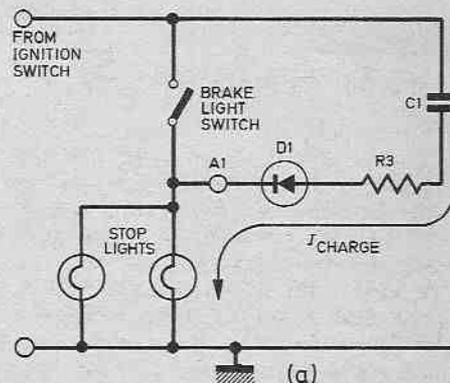


Fig. 3a. Illustrating the operation of the circuit when using an "A" input.


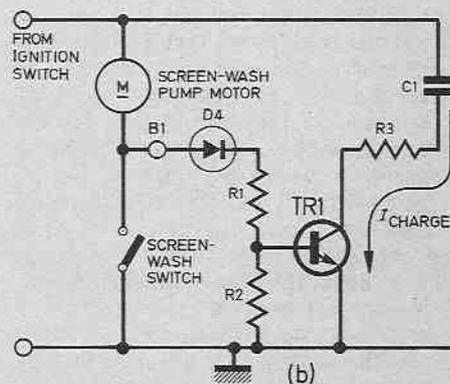


Fig. 3b. This time a "B" input is being used to illustrate the operation.

HOW IT WORKS

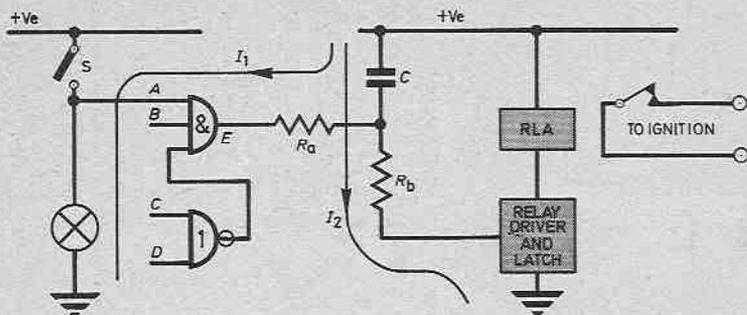

The circuit consists basically of a timing circuit with two different time constants, the longer of the two is adequate to allow a relay to operate. Once operated the relay is held on by a simple latching circuit.

Consider the case where the inputs A and B are low, or C or D high. The capacitor will begin to charge via R_a , the AND gate and the lamp. This constitutes the short time constant and is too fast for the relay to operate. Now if A and B are high (switch S operated and lamp on) and C and D low, the capacitor will now charge via R_b and is the longest time constant. The relay will now have sufficient time to operate, and thus connect power to the ignition circuit.

In practice one or more inputs as the example shows, are connected to various accessories, such that a certain combination will enable the ignition circuit.

motor circuit is connected to B1, as shown in Fig. 3b capacitor C1 can charge via resistor R3 and the collector/emitter junction of transistor TR1, if the washer switch is off. However, if the washer switch is operated before (and during) the operation of the ignition switch the capacitor will again charge via diode D8, resistor R4 etc, and the relay will latch thus allowing the ignition system to operate normally.

ACCESSORIES

It should be noted that the "A" inputs are for accessories which have a switch connected to the ignition switch line, whereas the "B" inputs are for accessories with a switch connected to earth.

Thus the circuit can be inhibited by only one accessory switch as in Fig. 3, or by several, thus utilising its multiple inputs. For instance, a seat belt warning system could be connected to one of the inputs, with the brake light circuit to another.

So unless the driver, and front seat passenger if present has his/her seat belt on and has operated the brakes before the ignition switch is switched on, the engine will remain immobilised. This illustrates how the device could be used as a safety feature as well as an anti-theft engine immobiliser.

Care should be exercised at this stage, in the selection of a suitable input connection, because on certain makes of car, the starter motor cannot be re-engaged until the ignition switch is firstly moved to the off position and then switched on again. This means that the engine will be immediately

COMPONENTS

See
**Shop
Talk**
page 857

Resistors

R1	10k Ω
R2	1.8k Ω
R3	100 Ω
R4	10k Ω
R5	1.8k Ω

All $\frac{1}{2}$ W carbon film $\pm 2\%$

Capacitors

C1 10 μ F 25V elect.

Semiconductors

TR1	BC107 silicon npn
TR2	BC107 silicon npn
D1 to D9	1N4148 silicon (9 off)
D10	1N4002 rectifier

Miscellaneous


RLA Relay: 185 ohm coil with single pole contacts to suit load. (RS type 348 908); Printed circuit board as described; connecting wire; small aluminium box if required.

immobilised and the correct starting sequence will have to be applied. The worst case condition for this would be if the engine cuts out when the vehicle is on the move.

Use of the brake light switch in this situation could be somewhat hazardous. In the average car there are many other alternatives including for instance, the screen-wash circuit, headlamp flasher, etc.

FORD ESCORT MK II

Fig.5. Typical wiring details and layout for accessories in the Ford Escort Mark 2.

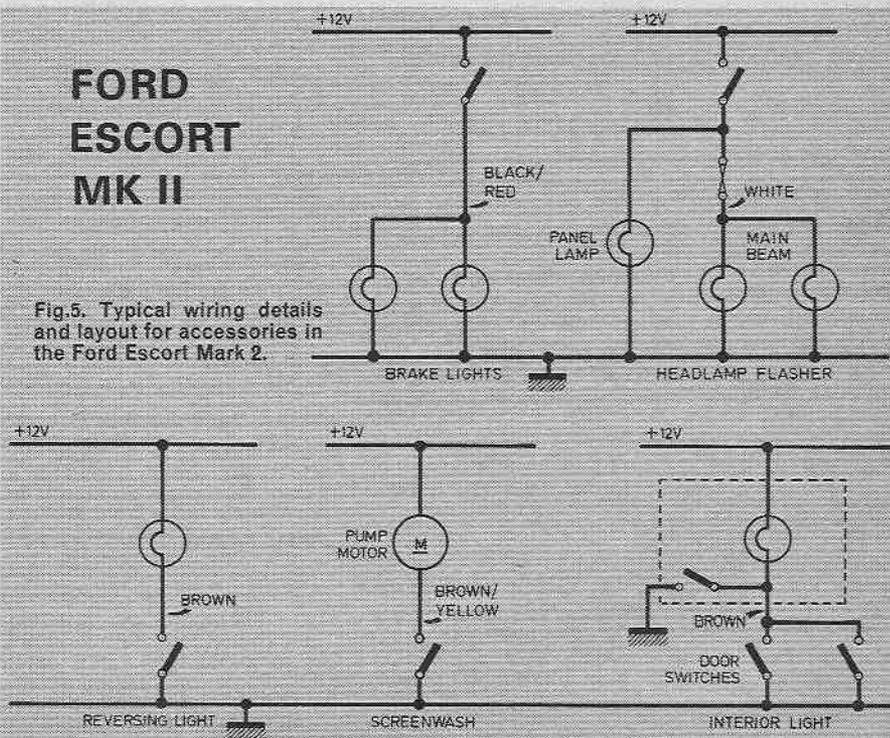


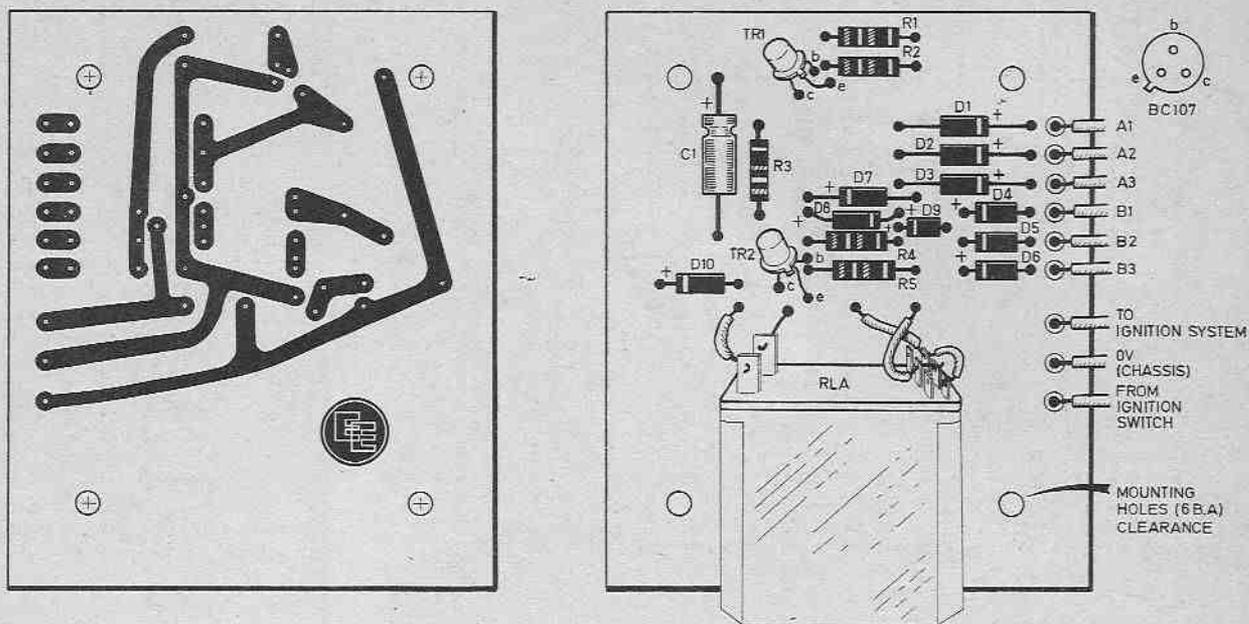


Fig. 4. Printed circuit board required. In the prototype the relay is mounted on the board using an epoxy glue.

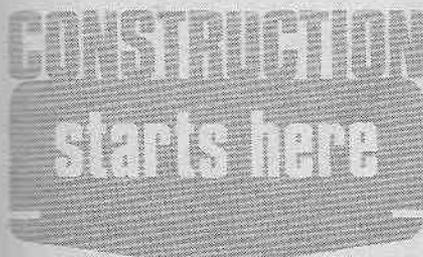

Construction is simplified by the use of a printed circuit board

which carries all the components and wiring. The layout of the board is shown in Fig. 4 which is reproduced full size.

One method of making the board is as follows. First, either photocopy or trace the copper pattern, position the tracing on the copper side of the board and mark with a sharp pointed tool, the position of the connecting holes. Remove the paper, thoroughly clean the board

and draw in the rest of the copper pattern with an etch resist pen. Once dry the board can be etched in the normal way.

Once etched and the board checked for any errors, the components can then be mounted. Here again the layout is shown in Fig. 4. It should be noted that the layout is not critical and can be varied to suit, although a good strong finish is required, hence a printed circuit board.

Good quality connecting wire can be used to connect to the various accessories, and Fig. 5 and Fig 6 show the many possibilities on two popular cars. The top two circuits of each set of drawings relate to "B" inputs, whereas the arrangements below relate to "A" inputs. When wiring to the car accessories the manual applicable to the make of car should be consulted.

AUSTIN MAXI


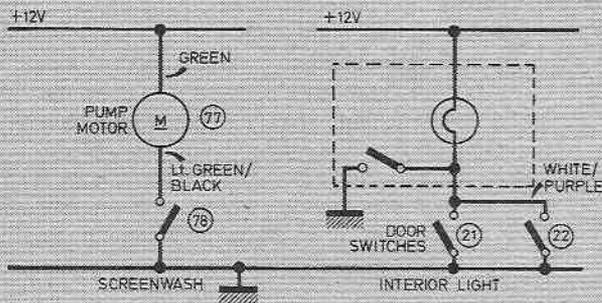


Fig. 6. Wiring layout for accessories in an Austin Maxi.

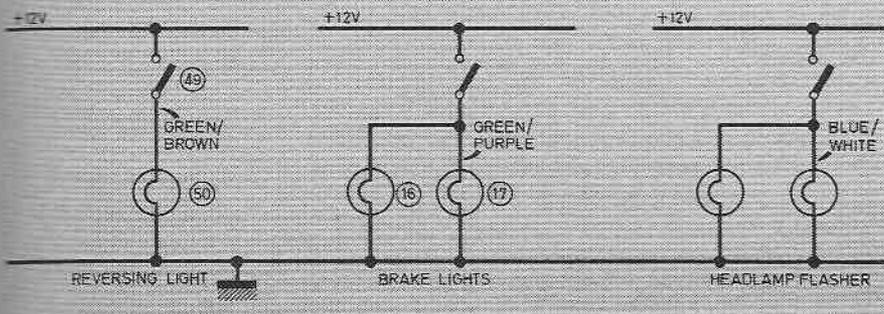


INSTALLATION

The author's prototype circuit board was mounted inside the box of his electronic ignition system. The system used was basically a Bi-Pak kit but had been modified to provide space for the additional board and wiring.

A second unit was then built and fitted into a small aluminium box which was then installed in the engine compartment. If this method is used the box should be positioned away from heat and the weather.

Fuzz Box

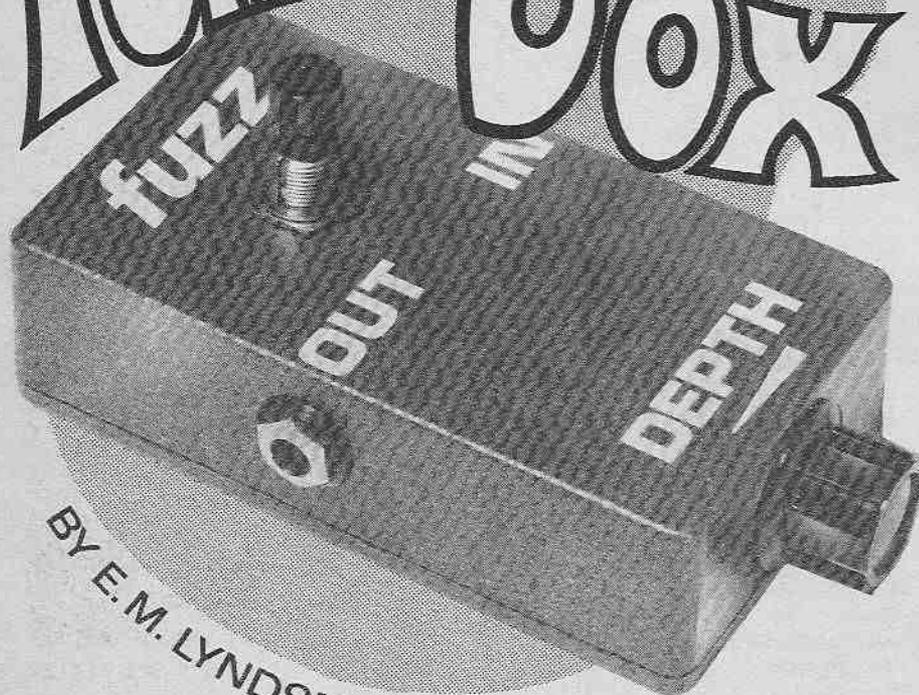

BY E. M. LYNDSELL

THE POP musician is being constantly bombarded with new and improved musical effects units, but still polling high in the popularity charts is the "old" Fuzz Box.

Some of the earlier designs were not completely satisfactory requiring high input signal level and producing premature cut-off as the input signal decayed. Those fuzz units employing discrete components operated on the verge of instability due to the high gain required. The design appearing below has none of these deficiencies and will produce a fuzz gradually decaying into a "clean signal" sound.


The fuzz sound is derived by clipping the input waveform thereby enriching the signal with odd harmonics which provide the harsh sound.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Fuzz Box is shown in Fig. 1.

Use is made of the industry standard op-amp type 741 which is used in a non-inverting configuration.

Fig. 1. The complete circuit diagram of the Fuzz Box.

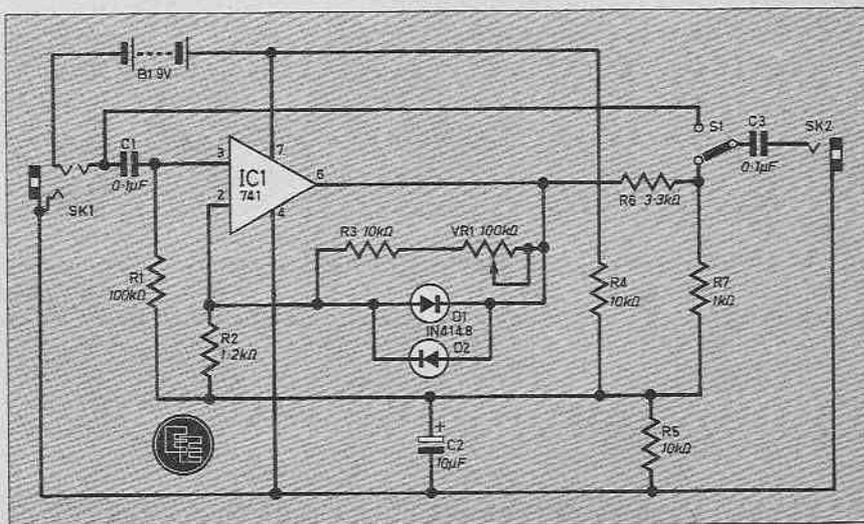

The gain of this arrangement is controlled by the feedback network VR1, R3 and R2 and is equal to

$$\frac{VR1 + R3 + R2}{R2}$$


Thus minimum gain is approximately nine and maximum gain approximately 92. However, the input signal never actually receives this boost for the anti-parallel diode arrangement comes into play and limits any amplified excursion, positive and negative going, to about 600 millivolts (the voltage drop across a forward biased silicon diode).

With this limitation on amplitude, it appears that the setting of VR1 has little effect. This is not so, for this control determines the rate of climb up to the clipped level or the rise time as it is called.

This time is inversely proportional to the harmonic content, i.e. the faster the rise the more harmonics produced resulting in a harsher tone; VR1 therefore controls the "depth" of fuzz.

It is apparent from the gain figures quoted that some signals will not reach the clipping levels; those below 6mV for maximum VR1 and those below 60mV for minimum setting of VR1. This is intentional to allow a gradual reduction in "fuzz" as the input signal decays naturally, being a smooth transaction from fuzz to no-fuzz.

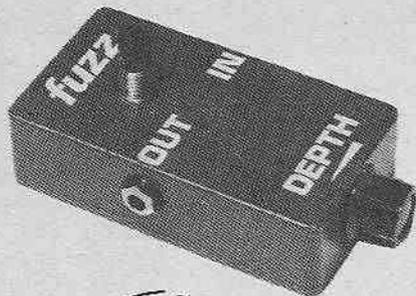Input to the unit is at SK1 a stereo jack socket wired to complete the d.c. power circuit when



fuzz box

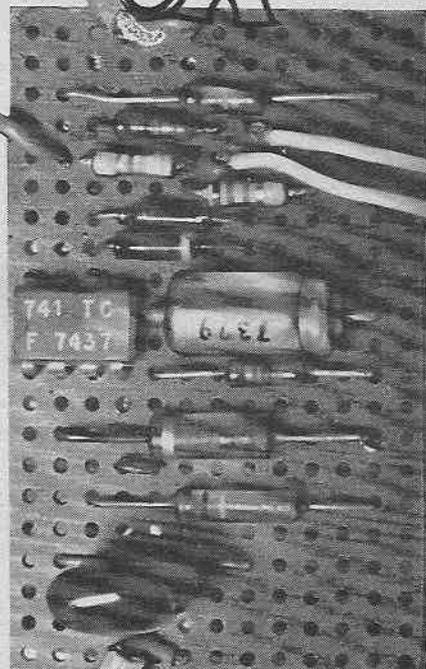
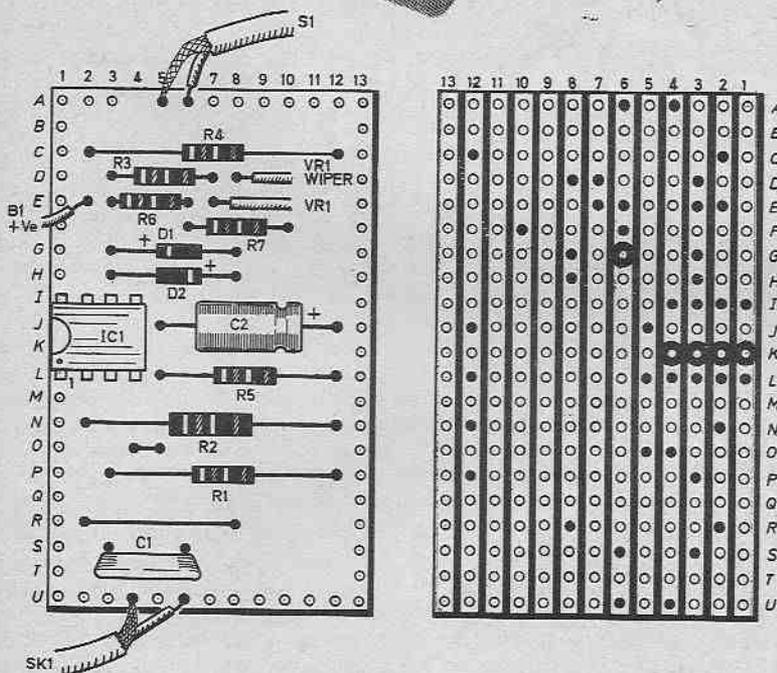


Fig. 2. The layout of the components on the topside of the board and the breaks to be made along the copper strips on the underside.

Photo of the completed prototype board.

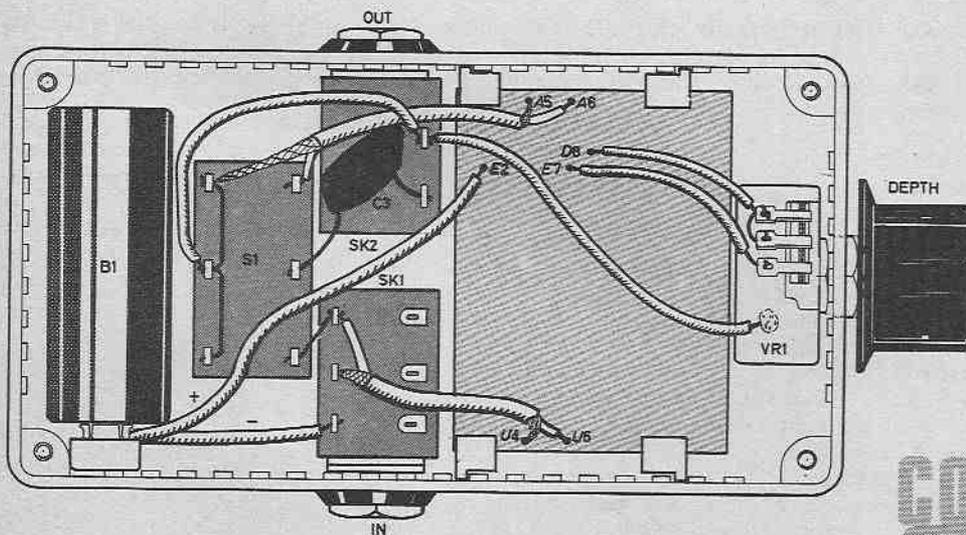


Fig. 3. The positioning of the components and board within the case showing complete wiring up details. Note the connection to the body of VR1 to "earth" the case.


COMPONENTS
 approximate
 cost £5

the input jack is inserted. The signal then passes to the op-amp via d.c. blocking capacitor C1. Resistor R1 sets the input impedance at 100 kilohms which should suit most guitars and electronic organs.

The resulting signal from the op-amp is reduced in amplitude by the potential divide action of R6 and R7, giving an attenuation factor of approximately four. Thus the maximum output signal via C3 available for inputting to an amplifier is about 150mV. This level will be maintained during the period of clipping (fuzz) and will then decay naturally to zero.

The 741 requires a split supply and this is derived by the potential divide action of R4 and R5 producing ± 4.5 volts with respect to the op-amp reference line which is decoupled by C2.

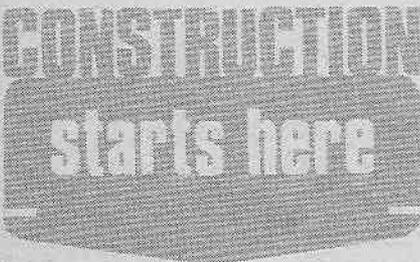A foot-switch S1 is incorporated to allow the unit to be readily bypassed when desired.



The prototype unit was built using a piece of 0.1 inch matrix stripboard size 13 strips \times 21 holes and mounted horizontally in a die-cast aluminium Bimbox type 5003/13 by use of special adaptors. This eliminates the use of fixing screws on board or case.

The layout of the components on the topside of the board is shown in Fig. 2. Make the breaks on the underside and then assemble the components as shown. It was not thought necessary to mount IC1 in a socket as this is quite a robust device. However the usual care should be exercised when soldering this and the diodes in place.

Attach the flying leads including the battery connector and then proceed with drilling the case. The layout of the components in the case is not critical.

With the components positioned in the case, attach the adaptors to the board and slot in position and wire up according to Fig. 3. Screened lead was used in the prototype for input/output connec-

COMPONENTS



See
**Shop
Talk**
page 857

Resistors

R1	100k Ω
R2	1.2k Ω
R3	10k Ω
R4	10k Ω
R5	10k Ω
R6	3.3k Ω
R7	1k Ω

All $\frac{1}{4}$ watt carbon film $\pm 10\%$

Capacitors

C1	0.1 μ F plastic or ceramic
C2	10 μ F 6V elect.
C3	0.1 μ F plastic or ceramic


Semiconductors

IC1	741 operational amplifier 8 pin d.i.l.
D1, D2	1N4148 or similar silicon diode

Miscellaneous

SK1	standard stereo jack socket
SK2	standard jack socket
S1	s.p.d.t. successional action foot-switch
B1	9V PP3
VR1	100 kilohm carbon lin.

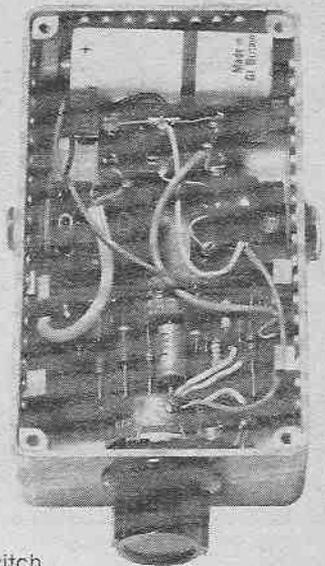Stripboard: 0.1 inch matrix 13 strips \times 21 holes; PP3 battery clip; Bimbox aluminium diecast box type 5003/13; Bimadaptors for holding board; knob for VR1; connecting wire.



tions as can be seen in the photograph but this is not essential as the case is earthed via VR1 framework. Insert and connect the battery and secure the lid.

The lid forms the base of the Fuzz Box. If the lid is fitted with self-adhesive rubber feet, this will prevent the unit slipping when in use.

IN USE AND TESTING

The box is to be situated between the musical instrument and amplifier. Inserting the input jack plug turns on the unit.

Set VR1 fully clockwise. On playing your musical instrument the sound emanating from your speaker will be fuzzed or clean, depending on the setting of S1. Assuming it is the latter, depress S1 and fuzz should be heard. Playing and turning VR1 anticlockwise should reduce the "depth" of fuzz.

No volume control was found to be required on the author's prototype as resistors R6 and R7 were tailored to give the required balance between fuzz and no-fuzz for the author's guitar. Assuming the initial output signal from the guitar before decaying is 60 millivolts, then switching from no-fuzz to fuzz by S1 will boost the amplitude by 8dB during the fuzz period.

If other boost factors are required change the value of R6 and


R7 or both to suit your requirements. This combination could be replaced by a log. potentiometer to give continuously variable output level.

Unless sub-miniature potentiometers are used, if a volume control is incorporated, a larger case than specified will be required.

Battery drain is low and a PP3 should provide many hours of use. A Duracell battery will allow even longer periods between battery changes.

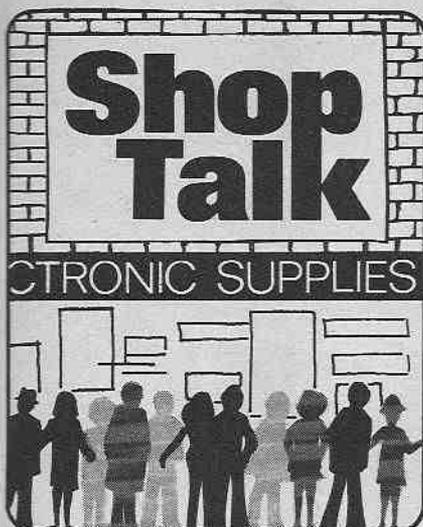The case specified and used by the author has a durable grey enamel finish and thus required only socket and control lettering to complete the unit. Letraset with spray-on protective varnish was found satisfactory for this. □





By Dave Barrington

Calculators

With so much "hysteria" in the media lately about silicon chips (microprocessors) and their possible impact on our future way of life, people tend to forget that the electronic calculator is a prime example where they have been used and accepted, without any fuss, into our everyday life. In fact, the range, popularity and versatility of these machines is so wide that any new additions are now taken for granted.

Two new additions we should like to mention which highlights the latest trends are the TI-2550-IV from Texas and the Casio ST-24 Time Card.

Featuring a built-in instant replay facility allowing the user to check back on the last 20 entries, the TI-2550-IV is obviously aimed at the accountant/student and could be used in place of some of the more expensive paper printout calculators.

The calculator is a general purpose hand-held type with the normal addition, subtraction, multiplication and division functions together with percentage and sign-change keys and full-function memory. The machine uses an 8-digit vacuum fluorescent display, with a floating decimal point (adjusts its position in the readout automatically) and negative sign, plus overflow error indication.

The replay facility, which operates with up to 20 steps, is activated by pressing a single key. The playback key allows the user to check through calculations step by step and any necessary corrections made by keying in the new entry and pressing the "equals" key. This saves re-entering the entire program.

The TI-2550-IV operates from a rechargeable battery pack and an a.c. adaptor/charger is included in the recommended retail price of £29.95 (inclusive of VAT).

For the busy executive, travelling salesman or the housewife, the Casio ST-24 Time Card could be classed as the latest "state-of-the-art" in the current craze for the credit card size of small calculator. Not content with a miniature machine they have incorporated a time/stopwatch with alarm setting facilities, ideal for those important meetings and elapsed time when leaving the car parked to make calls or do some shopping.

The calculator section is a four-function type with the usual standard facilities including memory and percentage.

The 24 hour timer has two kinds of alarm setting: straightforward alarm setting for a single specified interval, or to sound repeatedly at predetermined intervals. In both cases, capacity of the timer is from a few seconds up to 23 hours, 59 minutes, 59 seconds. A countdown is possible as the display shows time remaining before alarm is due.

Operating modes for the stopwatch are normal start/stop, lap timing, or first/second place timing. Indication is to one-tenth of a second up to 10 hours, or to one second beyond 10 hours. Use of calculating facilities does not affect function of alarm timers or stopwatch.

The Casio ST-24 Time Card is supplied in a leatherette pouch with a separate compartment for credit or business cards, and has a recommended retail price of £24.95 (including VAT). For addresses of nearest stockists readers should write to Casio Electronics Co. Ltd., Dept EE, 28 Scrutton Street, London EC2A 4TY.



Beginners Kit

Designed with the very young in mind, the Tutronik Timesaver System introduces the total beginner to the very fundamentals of electronics. A "course" of 30 different circuits is provided, covering a wide range from a simple series circuit to a novel police siren.

Each circuit is accompanied by an instruction sheet giving essential information on what components you need, what you have to do, how and why the circuit behaves as it does. Throughout the course experimentation is encouraged. Written in an easy to follow language, sometimes distractingly lighthearted, every detail is

covered to ensure the beginner does not go astray.

An unusual type of breadboarding system using the actual circuit as the wiring diagram, and plastic screw terminals to hold the component leads is used throughout. Rather disappointingly components are not provided. Full details from: Technocentre, Dept EE, 54 Adcott Road, Acklam, Middlesbrough, Cleveland.

Constructional Projects

This month there should be no difficulties with component availabilities except possibly the major constructional project, *EE2020 Tuner Amplifier*, which we shall deal with separately.

The relay for the *Ignition Immobiliser* should be able to handle the current requirements of the ignition circuit. In the prototype the relay used had two sets of contacts wired in parallel.

For the *Water Level Alert* a 35Ω 40mm diameter loudspeaker can be used in place of the Post Office earpiece. If any difficulties are experienced with the rocker switch S1 this can be ordered from Maplin as a "Hekla Switch".

There should be no problems with the rest of the constructional articles in this issue.

2020 Tuner Amplifier

The *EE 2020 Tuner Amplifier* is larger than our usual run of projects, and so it follows that the components used add up to an impressive list. Yet because of the large quantity of similar components called for, the constructor should be able to purchase many items at especially favourable rates.


Capacitors should be of the kind as specified in the Bulk Components List; this is to ensure suitability for mounting on the printed circuit boards. This is particularly important in the case of electrolytic capacitors. Here RS Components types have been specified. In most instances a voltage rating of 63V is stated. This is higher than actually needed in the 2020 circuit and lower rated capacitors of an alternative make may be used provided the physical dimensions and the lead spacing are as the RS types specified.

The r.f. unit and some related parts are obtainable direct from Ambient Ltd, 2 Gresham Road, Brentwood, Essex. This firm can also supply the special multi-turn potentiometers for varicap diode tuning.

The pushbutton switches specified are marketed by both RS Components and ITT, under these firms own stock numbers (see Bulk Components List).

Readers should note that manufacturers such as RS Components and ITT (and Mullard and Texas) do not supply to individuals. But their components are readily obtainable from distributors and retailers who cater for the retail market.

DOING IT DIGITALLY

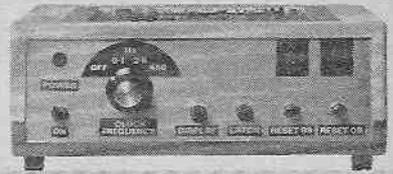

PART 3

By O. N. Bishop

LAST month we used the NAND gates of a 7400 i.c. to build a NOR gate and a bistable. These two logic elements, as well as the NAND gate itself, are often required in building logic circuits that it is useful to have them ready-wired on the patchboard. On the Test-Bed these elements are permanently wired in, the form of IC3, see Figs. 3.1 and 3.2.

FAN-OUT

Each of the inputs of these elements has a single input pin and each output has a pair of output pins. Though each input of a logic gate can receive its input from only one source, the output is able to be connected to several other gate inputs. The number of inputs that may be connected to an output is known as the *fan-out* of the output. Here we provide pins for a fan-out of two, since this is as many as we shall normally need. However, most outputs have a fan-out of eight loads.

These circuits have already been tested when building the Test-Bed, but it is a good idea to test them again. This time you know a little more of what you are doing.

With the supply pin P34 connected to be +5V line first test the NAND gate. Connect the output V26 or V28 to l.e.d. D7 at location V40. The l.e.d. should be dark (off) but should light when either of the input pins at S25 or T25 are grounded to one of the pins on strip N, the 0V rail.

Unconnected inputs of a NAND gate are effectively "high" so there is no need to connect them to the positive rail for testing. You can easily check this by linking one of the inputs to ground and

noticing no change in the state of the l.e.d. when the other input is connected to one of the pins on strip L, the +5V rail.

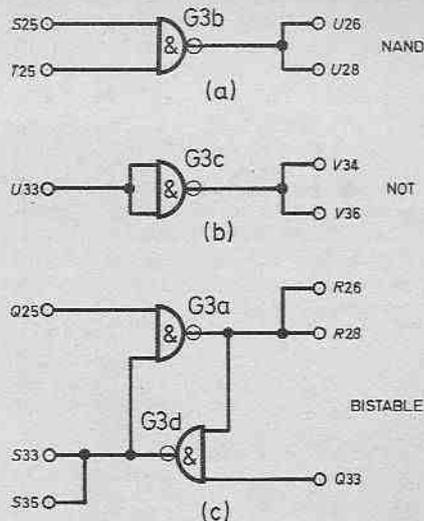


Fig. 3.1. The three basic elements contained in IC3 with pin locations for inputs and outputs on the Test-Bed.

To test the NOR gate, connect one of the NOR outputs, pins V34 or V36 to one of the l.e.d.s, e.g. U43 for D8. The l.e.d. remains dark when the input is unconnected (effectively "high") or connected to strip L. The l.e.d. lights when its input, pin U33 is grounded (connected to 0V rail).

Finally to test the bistable: connect each bistable output to an l.e.d. e.g. pin S36 to U49 and R28 to U40. One l.e.d. should light and the other remain dark. When the appropriate input pin Q24 or Q33 is briefly grounded, the l.e.d.s change state.

A TTL CLOCK

Compare the circuits shown in Fig. 3.3 with the bistable circuit of Fig. 3.1c. Their similarity suggests that they may behave in a similar way—for example, they can both alternate between two opposite states. The bistable changes state when one of its inputs is grounded. The clock circuit changes state automatically after a fixed period

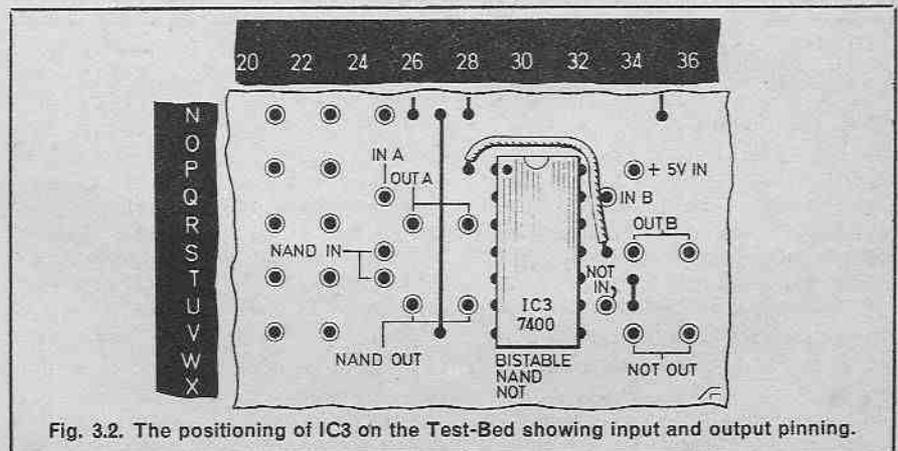


Fig. 3.2. The positioning of IC3 on the Test-Bed showing input and output pinning.

of time. Suppose that it has just changed to the state shown in Fig. 3.3a. The output of G1 (gate 1) has just gone high (as indicated by the shading) and the l.e.d. at its output has just come on.

The sudden increase in output voltage raises the voltage of both sides of capacitor C1 to a "high" level. Both inputs of G2 are now high (remember the unconnected input is effectively "high") so its output goes "low". This lowers the voltage of both sides of C2; G1 now has one "high" input and one "low" input, so its output is "high". The circuit has the state indicated in Fig. 3.3a. Why is it not stable in this state?

For the answer to this question, look at R1. This has a high voltage at one end and is grounded at the other. A current I flows through R1, as indicated by the arrow. As current flows, the voltage on one side

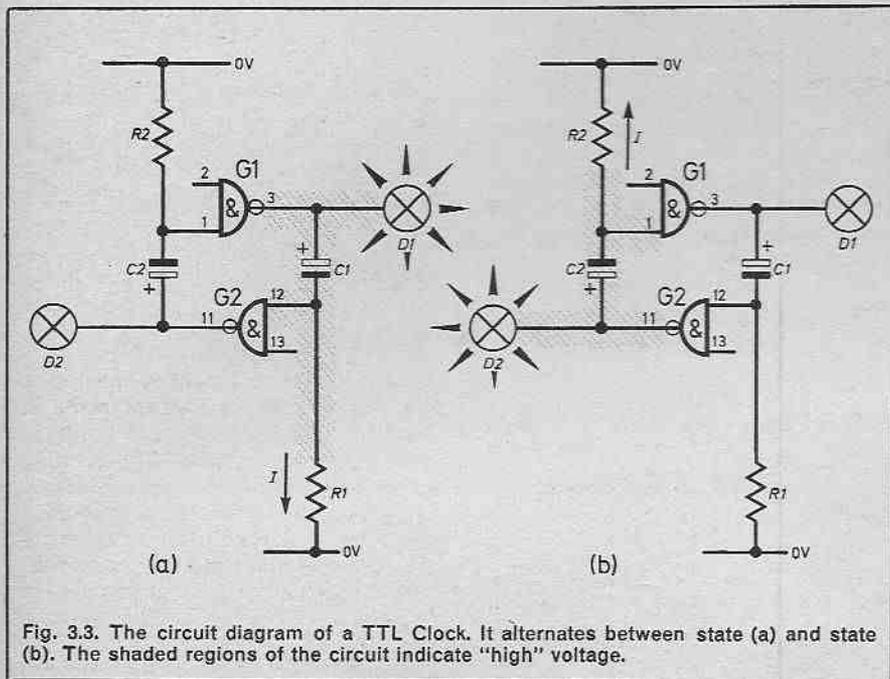


Fig. 3.3. The circuit diagram of a TTL Clock. It alternates between state (a) and state (b). The shaded regions of the circuit indicate "high" voltage.

of C1 falls and finally reaches a "low" level that acts as a "low" input to G2.

Now the output of G2 suddenly goes high; D2 lights; the voltage on both sides of C2 is raised; G1 now has two "high" inputs; its output goes low and D1 is extinguished; the voltage on both sides of C1 is lowered. We have reached that stage shown in Fig. 3.3b. The circuit remains in this state while a current flows to ground through R2; as soon as the voltage has fallen low enough at the input to G1, the circuit reverts to the state

of Fig. 3.3a and the cycle repeats.

The clock circuit is unstable (we call it an *astable multivibrator*) in either of its states. The length of time it remains in either state depends on how long it takes for the voltage on one side of each capacitor to fall from "high" to "low". This time depends on the values of the capacitors and resistors involved.

With high capacitance and high resistance a small current flows and gives a relatively small rate of change in voltage, resulting in a long period of time in each state.

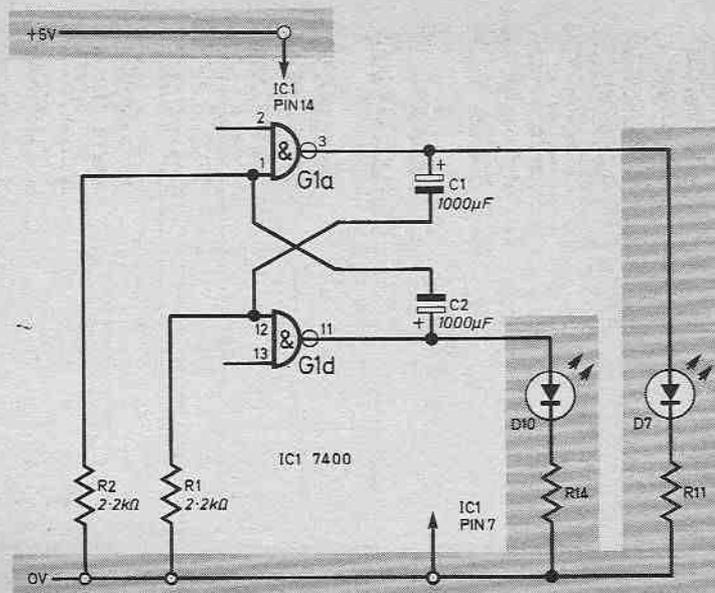


Fig. 3.4. The circuit of Fig. 3.3 redrawn in a more conventional form with the state of its outputs indicated by l.e.d.s.

EXPERIMENTAL TTL CLOCK

We shall now observe the operation of this circuit which is redrawn in its more common form in Fig. 3.4 is shown wired up on the Test-Bed in Fig. 3.5. The clock should change state approximately every 5 seconds. In other words, it takes 10 seconds to complete its cycle of operation, from the time D7 comes on to the time it comes on again. We say the clock is oscillating or vibrating at 0.1Hz.

Different value capacitors will produce different frequencies. If capacitors with a value of 0.47µF are substituted, the l.e.d.s glow at about half their normal intensity but no flashing can be detected. The frequency is so great that the eye cannot follow.

To prove that the clock is really working connect a crystal earpiece across one of the l.e.d.s and the 0V rail. This is done easily with two pairs of leads terminated in crocodile clips. You will then hear a note of about 400Hz (around the same pitch as middle A on a musical instrument).

We have been calling this circuit a clock, but it is simply the equivalent of the pendulum or balance wheel that is used to regulate the speed of mechanism of an ordinary mechanical clock; it is an astable multivibrator.

In a clock there are gear wheels, hands and a dial to indicate the time, which is related to the number of times the pendulum has swung to and fro. Similarly we can connect further logic circuits to the

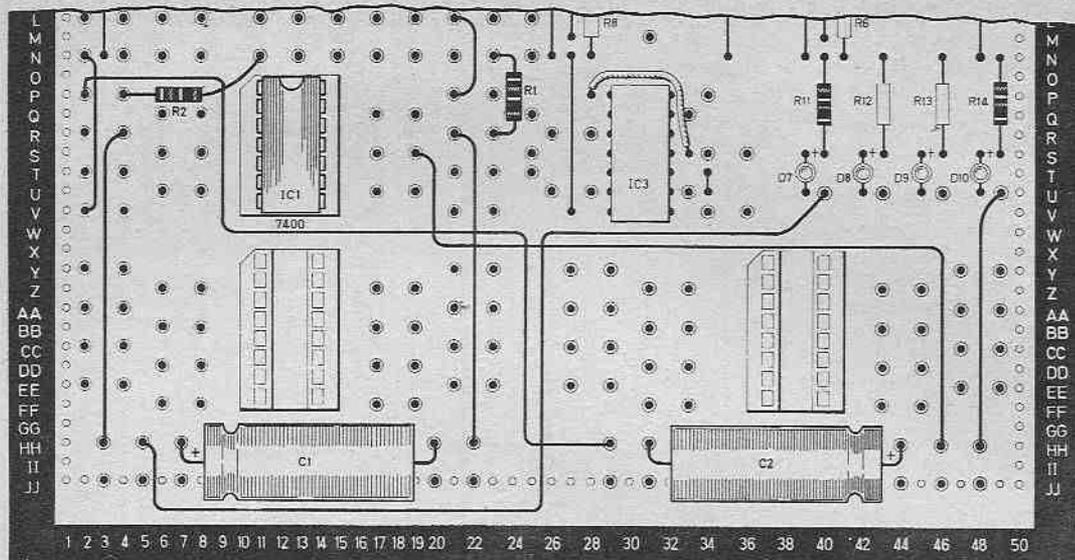


Fig. 3.5. The layout of the components on the Test-Bed for the circuit shown in Fig. 3.4. Experiment with different values for the capacitors and use a crystal earpiece for observing high frequency oscillations. The earpiece can be wired across either of the l.e.d.s.

TTL clock to count the number of times it changes state and so allow us to measure elapsed time. We shall return to this idea later in the series.

A clock or oscillator is a vital piece of equipment when testing logic circuitry and has been included in the Test-Bed on the internal component board. Three pairs of capacitors are fitted, any one of these pairs being selected by front panel switch S2. The output from this clock is available at

pins D14, 16 and 18 on the Test-Bed.

LATCH

The output of a latch is identical to its input, but at any moment the output can be "frozen" or "latched" and then remains in the state that it was in when latched, even though the input may subsequently change.

Part of the latch circuit consists of a bistable discussed last month. In Fig. 3.6 the bistable in this cir-

cuit is drawn in a slightly different manner to that shown before, comparison with Fig. 3.1c shows that the connections are identical.

The bistable changes state when a low input is applied to it from one of the NAND gates. To find out how these work we shall use the NAND gate and NOT gate wired in IC3 on the Test-Bed; the remaining NAND gate is supplied by a further 7400 (IC1) inserted in a socket on the Test-Bed. We shall first examine the outputs from the two

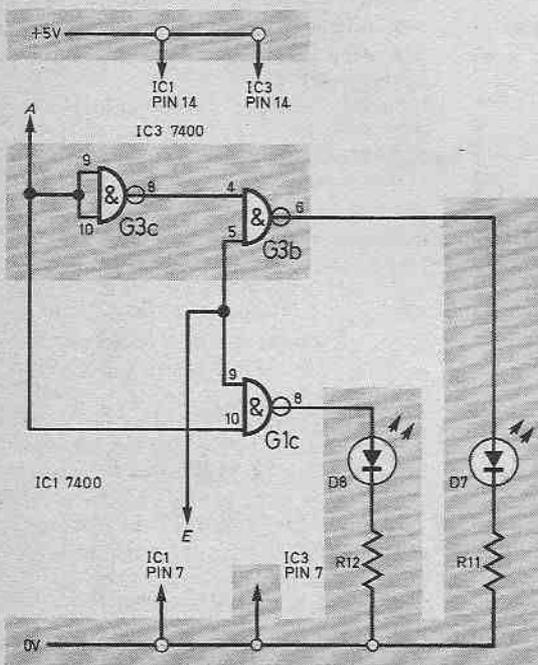


Fig. 3.6(a). Circuit of the front section of a "latch" circuit to observe the outputs which form the inputs to the remaining bistable section to be added later.

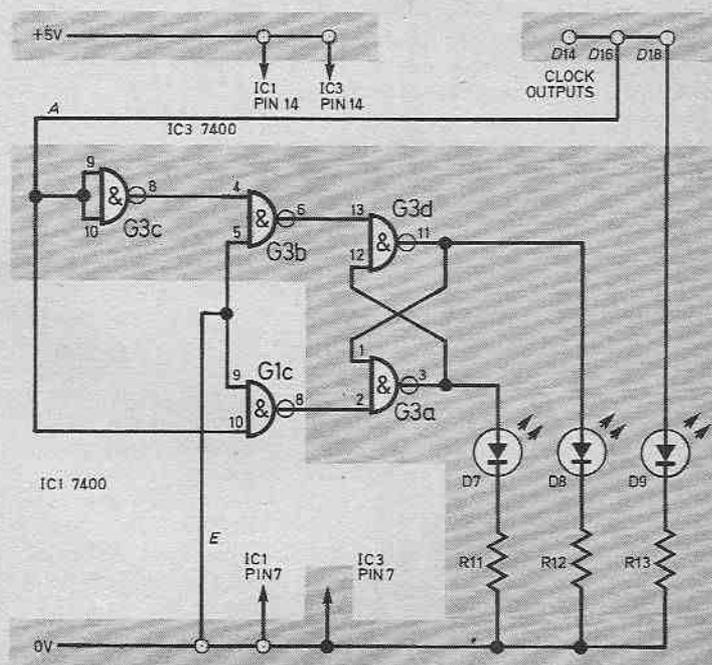


Fig. 3.6(b). The circuit diagram of a complete "latch" being driven by the in-built clock and outputs observed by means of l.e.d.s connected to the outputs.

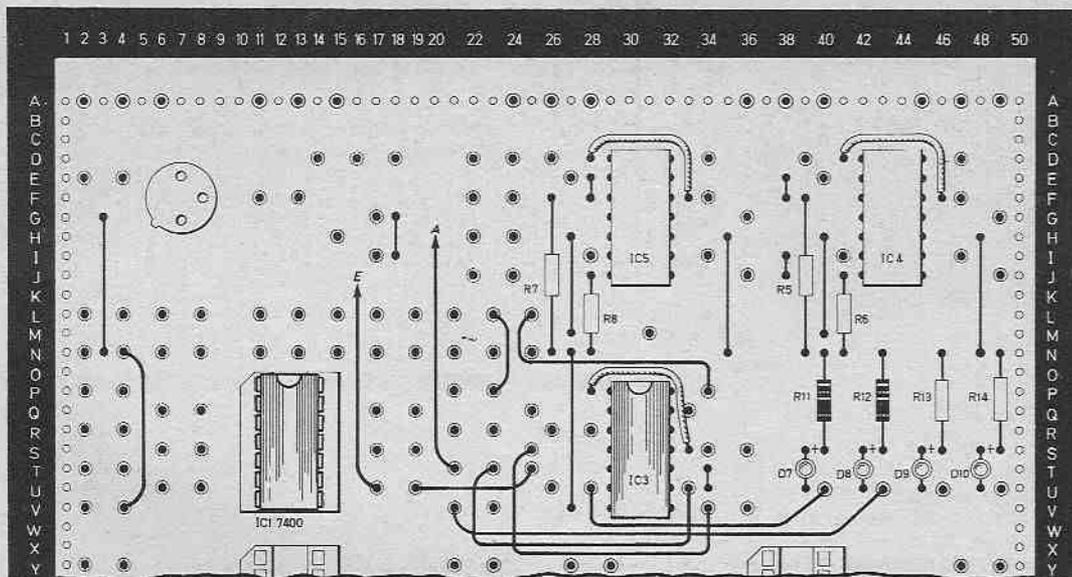


Fig. 3.7. The layout of the components and interwiring for the circuit of Fig. 3.6(a). For the circuit of Fig. 3.6(b) amend this layout according to the text.

NAND gates, see Fig. 3.7 for connection details.

USING THE IN-BUILT CLOCK

Connect wire *E* to the +5V rail, strip *L*. Now connect wire *A* alternately to the +5V rail and to the 0V rail and observe how the outputs change. Instead of changing wire *A* back and forth between +5V and 0V, make use of the in-built clock. Connect wire *A* to clock outputs (D16) and set the clock to low or medium frequency. The clock output automatically alternates between +5V and 0V, which can be observed by connecting another clock output pin to l.e.d. D9. You can now concentrate on watching the l.e.s.

Repeat your observations after having removed wire *E* from +5V and connecting it to 0V. Then return *E* to +5V and note what happens.

You will find that when *E* is "high" the l.e.s go on and off in time with the changes in clock outputs; always one lamp is on and the other off. When *E* is "low", both lamps are on all the time. This means that there is no "low" output, so a bistable connected to the outputs of the NAND gates will not change state. This is just what we need for a latch circuit, so the next step is to add the bistable.

Disconnect the output wires from l.e.s D7 and D8 and run them to the bistable input terminals instead (Q25 and Q33). From the bistable output terminals (R26 and S34) run wires to D7 and D8. This

completes the latch circuit with two outputs—one following the input, and the other the inverse of the input.

Test this circuit to see the effect of first making *E* "high" and then making it "low." Run the clock at medium frequency and see if you can ground wire *E* at just the right moment to latch the circuit with D7 lit and the other dark. With a certain amount of skill you can do this, but with the clock running at a high frequency it is entirely a matter of chance—equivalent to tossing a coin for "heads" or "tails".


This provides an idea for a simple project that can be built from three 7400 i.c.s two l.e.s a few resistors and capacitors, with

a push-button for grounding *E*. This can be wired up on a small piece of circuit board and mounted in a small plastic case. Depending on whether the capacitors give you medium or high frequency operation, you have either a game of skill or a heads-and-tails gambling machine that could be fun at parties, or help raise money at the local fête.

A latch facility is very useful when experimenting with logic and this same circuit has been incorporated in the Test-Bed. It appears on the lower board with input and output terminals on the top board. The wire labelled *E* in Fig. 3.7 can be grounded by means of a front panel switch.

(To be continued)

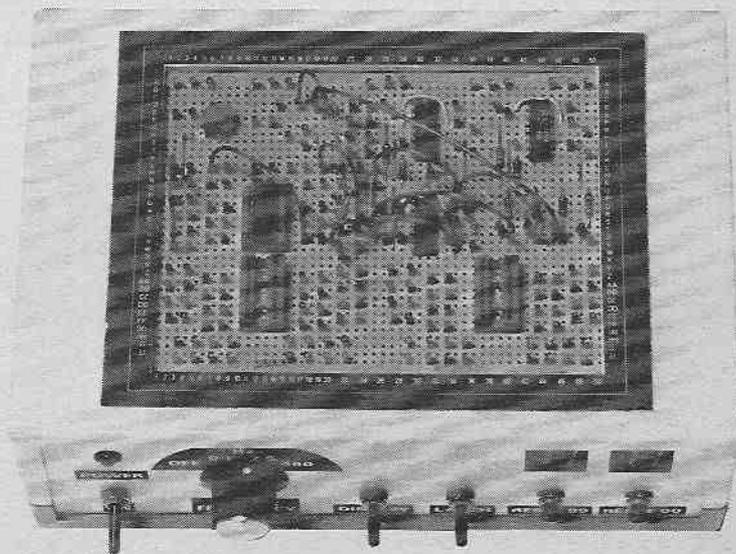Photograph of the interwiring on the Electronic Test-Bed for the circuit in Fig. 3.6(b).



mini-modules By George Hylton

Handy "Beginner" projects based on simple circuits and featuring a variety of building methods.

3 MICROPHONE AMPLIFIER



THIS microphone amplifier is really a general-purpose amplifier for small audio voltages. It has a high input impedance and a gain which is adjustable from about 20 to a maximum of over 1,000, by means of a preset potentiometer.

The amplifier is designed for dynamic microphones of medium to high impedance. The prototype worked well with a popular type of microphone whose impedance can be set to either 600 ohms or 50 kilohms.

THE CIRCUIT

The circuit is a conventional two-stage amplifier of the type once known as a "d.c. feedback pair". TR1 is operated at a low collector current to minimise noise. Overall negative feedback via R3 sets the gain, in conjunction with the preset potentiometer VR1. Gain is maximum when VR1 is minimum.

For the moderate gains, which are all that is needed in practice, the gain is very nearly $R5/VR1$ so if it is known in advance of building the circuit just how much gain is needed it is possible to use the appropriate value of VR1 in the form of a fixed resistor. For example if a gain of 100 is required VR1 should be $1k\Omega$.

The input impedance varies with the gain but at low to moderate gains

it is likely to be in the region of $200k\Omega$. It cannot exceed $330k\Omega$ because of R1 which is connected across the input as far as audio signals go, since its lower end is "earthed" via C3 to audio frequencies.

Because the input impedance is quite high it is possible to use a low-impedance microphone (for example 30 ohms) and a step-up transformer to increase the signal voltage. The inset diagram shows how to connect a transformer with a hum-reducing "balanced" input winding.

The maximum output voltage before overloading is about 2V peak and the output impedance is fairly low. However the amplifier should not be used to drive loads of less than about $10k\Omega$ or output will be severely restricted.

C2 is a radio frequency bypass capacitor to attenuate any r.f. signals accidentally fed in via the microphone cable. These can cause "breakthrough" of radio programmes into audio circuits.

CONSTRUCTION

Since this kind of amplifier is designed for low-level signals hum can be a problem and a metal screening box is needed. The input must also be capable of screening; the microphone used with the prototype had a screened lead which terminated in a jack plug so a suitable jack socket was fitted to the screening box.

Obviously, other types of screened input socket may be needed for other types of microphone or signal source.

The main part of the circuitry can be accommodated on a tag strip. With this type of construction the components are soldered to a simple tag strip with the solder tags in a straight line. Interconnections are made with insulated wire.

This is a relatively cheap form of construction as tag strips cost only a few pence and can often be salvaged from old equipment and cleaned up for re-use. It is not a type of construction which has much use for high-frequency circuits because it is rather hard to avoid accidental couplings between input and output, which cause r.f. instability. But it is usually all right for audio.

COMPONENTS

Resistors

R1	330k Ω	R4	10k Ω
R2	100k Ω	R5	3.3k Ω
R3	100k Ω	R6	1k Ω

All carbon film 5% \pm W

Potentiometer

VR1 5k Ω carbon miniature preset 20% tol.

Capacitors

C1	100nF (0.1 μ F) polyester
C2	1nF (1,000pF) ceramic disc
C3	47 μ F 3V miniature elect.
C4	3.3 μ F 12V elect.
C5	47 μ F 12V elect.

Transistors

TR1, TR2 BC109 (or any high-gain low-noise silicon npn type) 2 off

Miscellaneous

Metal box about 100 x 70 x 40mm (Norman AB9). Tag strip with 12 insulated tags, to fit box. Jack socket (SK1). Output terminals: 3-terminal chocolate block or similar. 6BA bolts, nuts, earth tags, and spacers.

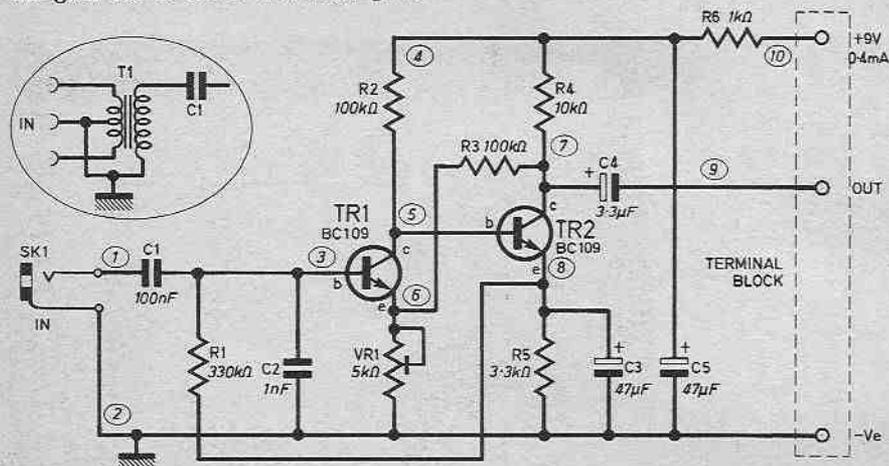


Fig. 1. The circuit of the microphone amplifier. The encircled numbers (1 to 10) are common connecting points on the tag strip, see Fig. 2. The small inset diagram shows how a step-up transformer can be used to suit a low-impedance microphone.

DESIGNING TAG STRIP LAYOUTS

If you design your own tag-strip component layouts a fairly careful pen-and-paper design is needed to ensure that the circuit will fit an available tag strip. To begin with, you should study the circuit diagram and mark each connecting point with a number (as in Fig. 1). Points which are connected directly to one another by plain connections count as one and the same point and are given just one number. (The "earth line" is a typical example.)

The present circuit has ten such connecting points which means that at least ten tags will be needed. In practice it usually turns out that a few extra tags are needed because of the physical limitations of the components, whose leads can only span a limited distance. A typical case is the preset "pot" VR1 which must be firmly soldered to two adjacent tags: (with some types of "pot" three tags may be required).

The resulting layout bears little relationship to the layout of the symbols on the circuit diagram; this may make fault-tracing tedious so tag-strip construction is perhaps best restricted to simple circuits.

When a finished tag strip circuit is fitted into a metal box provision must be made to hold it away from the metal to prevent short circuits. In the prototype long fixing bolts were used; stand-off spacers were slipped over the bolts to hold the tag strip well clear of the metal. These stand-offs were cut from the barrel of an old ball-pen.

BOXING

The screening box must be substantial enough to withstand repeated pluggings-in of the microphone. A small aluminium case is suitable and is easily drilled to take the input socket, etc. The prototype was built in a "Norman" case Type AB9, which

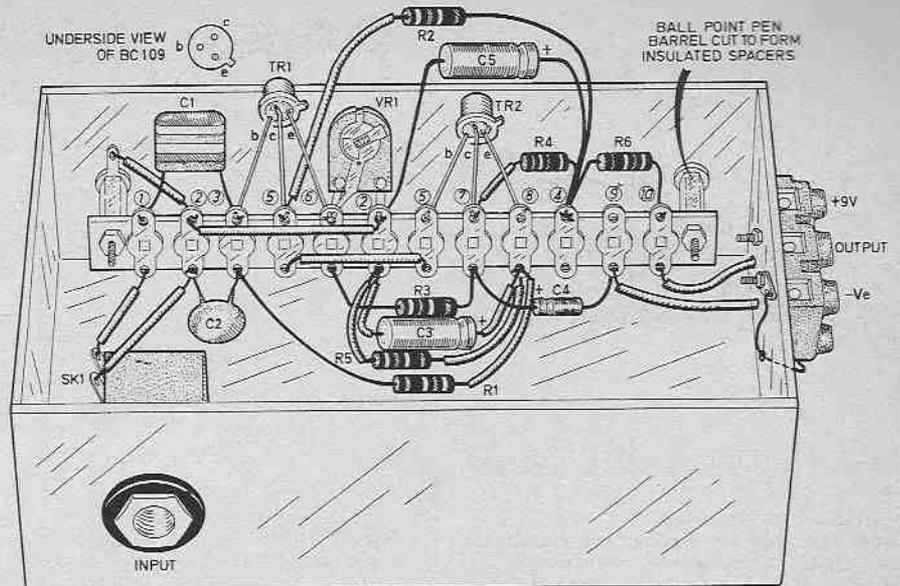


Fig. 2. Interior of completed unit. Certain components (R2, C5, TR1 and TR2) have been swung away from their normal position in this drawing for clarity. Encircled numbers on a tag strip correspond with those on the circuit diagram.

measures about 100×70×40mm and accepted the 12-way tag strip comfortably.

The type of output connection is not crucial and can be chosen to suit the needs of the user. Some type of multi-way socket is possible: the connections needed are power supply positive, live output and common (earth) so a three-way connection (or two plus "earth") is needed.

SCREW CONNECTOR BLOCKS

For the prototype the leads were brought out through small holes and taken to a strip of screw-terminal connectors (of the type sold in electrical shops and sometimes called a "chocolate block" from the colour of some makes).

The plastic kinds of chocolate block (which are usually made of transparent polythene these days) are easily cut into convenient lengths with a sharp knife. This kind of output connector can be used for either

permanent or temporary connections and is easily adapted to quick hook-ups with croc-clip leads by fitting short pieces of thick bare wire to the terminals.

USING THE AMPLIFIER

The only adjustment needed is to set VR1 to suit the microphone. (It is assumed, of course that there will be a volume control elsewhere in the complete audio system of which the amplifier forms part.) For this reason VR1 should be positioned so that it is easily accessible when the lid is removed. It can then be adjusted while the microphone is in use.

If for some reason a higher gain than normal is needed VR1 should be given a lower value. (Presets down to about 100 ohms are readily obtainable.) However it should always be remembered in audio work that it is a good rule to use the lowest gain that will do the job in hand.

Next Month: Continuity Tester


JACK PLUG & FAMILY...

BY DOUG BAKER

YOUR BURGLAR ALARM, DADDY—I'VE SMASHED IT TO PIECES BECAUSE IT DIDN'T WORK.



WHAT! HOW DO YOU KNOW IT DIDN'T WORK?

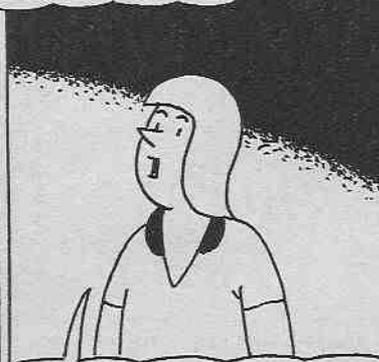

IF IT HAD WE WOULD'VE HEARD IT IN THE NIGHT...

... WHEN FATHER CHRISTMAS GOT INTO THE HOUSE.



SQUARE One

FOR BEGINNERS

In the two previous SQUARE ONE articles we have talked about the materials used to assemble circuit components and the essential tools for constructors; and we have had a look at the three most significant and widely used electronic components, the resistor, the capacitor, and the transistor.

Now it is time to consider putting these items together—that means soldering. But first of all we have to obtain our components.

BUYING COMPONENTS

If you are lucky, there may be an electronic component shop in your town or within easy reach. But it is a fact that the majority of constructors obtain their components by mail order. A look through our advertisement pages will show many retailers who operate a mail order service (some of these do also have retail shops for personal shoppers).

The first step should be to obtain two or three or more catalogues from different advertisers. The charge made for catalogues varies, from a few pence upwards to a £1, and reflects the size of the publication, the range of stock described, the technical detail included, and the amount of illustrations. A small collection of retailer's catalogues will prove a most valuable source of reference.

Component retailers include those who offer a very wide, nearly comprehensive, range of electronic components and those who specialise in a more restricted range of particular items. In the course of time, the constructor finds himself dealing with both kinds of retailers.

Studying these catalogues will make you familiar with components and the typical sizes and values usually stocked.

When ordering from a catalogue, do follow carefully the retailer's instructions; quote appropriate catalogue or stock number for each item and use the order form if one is provided. In the absence of any particular instructions from the supplier, describe the

required components in the same manner as in our Components Lists (see any EE Constructional Projects).

SOLDERING

The essence of practical circuit building is soldering. This is the technique—some will call it an Art—of permanently joining together two or more wires or metal parts so that a good electrical contact is made. The joint must be (1) sound mechanically, and (2) it must form a very low resistance path.

While a soldered joint might appear to satisfy (1), it could fail on (2). This is where the ART of soldering comes in.

The two surfaces to be joined must be clean and free from grease. The wire leads of resistors, capacitors, and transistors are pre-tinned and no other preparation is normally required for brand new components.

Insert the component leads into the appropriate holes in the circuit board. Check once again the correctness of the connections by referring to the component layout diagram and/or the circuit diagram.

Make each lead mechanically secure by bending its protruding end to a slight angle with a pair of thin-nosed pliers. Fig. 1a.

Switch on the soldering iron. Wait about 15 seconds and then touch the end of a piece of resin core solder to the tip. If the solder runs instantly over the bit surface, the iron is sufficiently hot for work. Fig. 1b.

Well "tin" the iron bit with molten solder (a thin covering—NOT a pool) then apply the bit to the point of contact of the lead strip and at the same time apply the solder. Solder should flow almost immediately. As soon as the immediate area of connection is covered with molten solder quickly remove first the solder and then the iron. Fig. 1c.

Take care not to disturb the leads or components at any time during this operation, or for a few seconds after the iron has been removed. A good reliable joint will have a bright lustre. A bad (possibly "dry joint") will have a dull surface.

PRACTISE IS ESSENTIAL

Before working with actual components knock a few copper panel pins into a block of wood. Practise tinning the tops of these pins. Next hook short lengths of thin tinned copper wire (of about 22 or 24 s.w.g.) around these pins, squeeze tight with thin-nosed pliers; and solder.

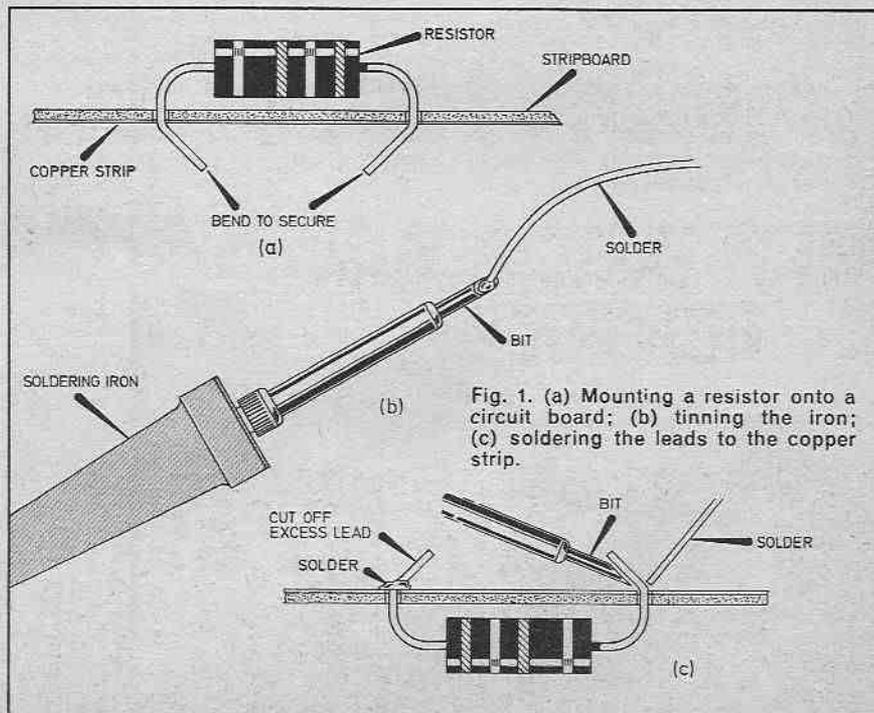


Fig. 1. (a) Mounting a resistor onto a circuit board; (b) tinning the iron; (c) soldering the leads to the copper strip.

NEXT MONTH

LIGHT REMINDER

For forgetful drivers. Emits a loud two-tone warning when the lights are on and ignition off. Includes a useful parking over-ride facility.

**2 SIMPLE
PROJECTS**


CONTINUITY TESTER

Our latest Mini-Module is a useful piece of test gear. Easy and inexpensive, of course.

HI FI HEADPHONE ENHANCER

An extremely simple circuit device that gives an additional dimension to two-channel sound.

**"What are they
playing?..."**

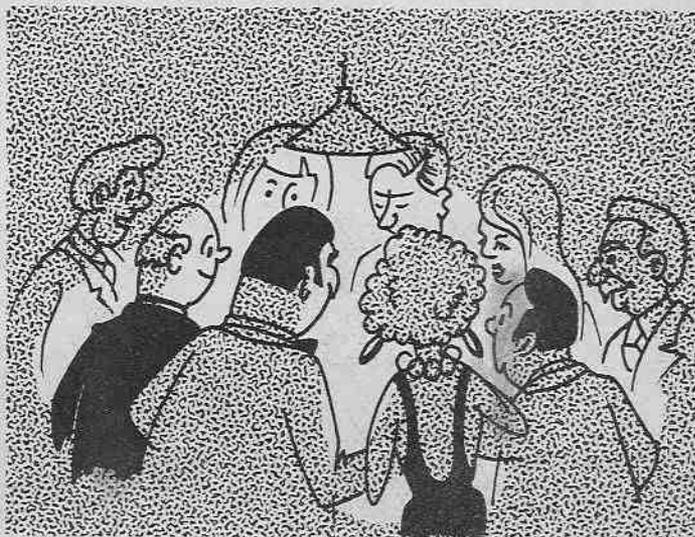

... our SOLID-STATE ROULETTE GAME"

Bring the excitement of the casino into your own home with this electronic version of the No. 1 sport in Monte Carlo. The Unit has a full thirty-seven position wheel and table.


Special Feature MAKING PCB'S

If you are interested in making your own printed circuit boards you will not want to miss this special feature containing all the steps involved from raw materials through to the completed board.

Everyday ELECTRONICS

JANUARY

ISSUE ON SALE
FRIDAY, DECEMBER 15

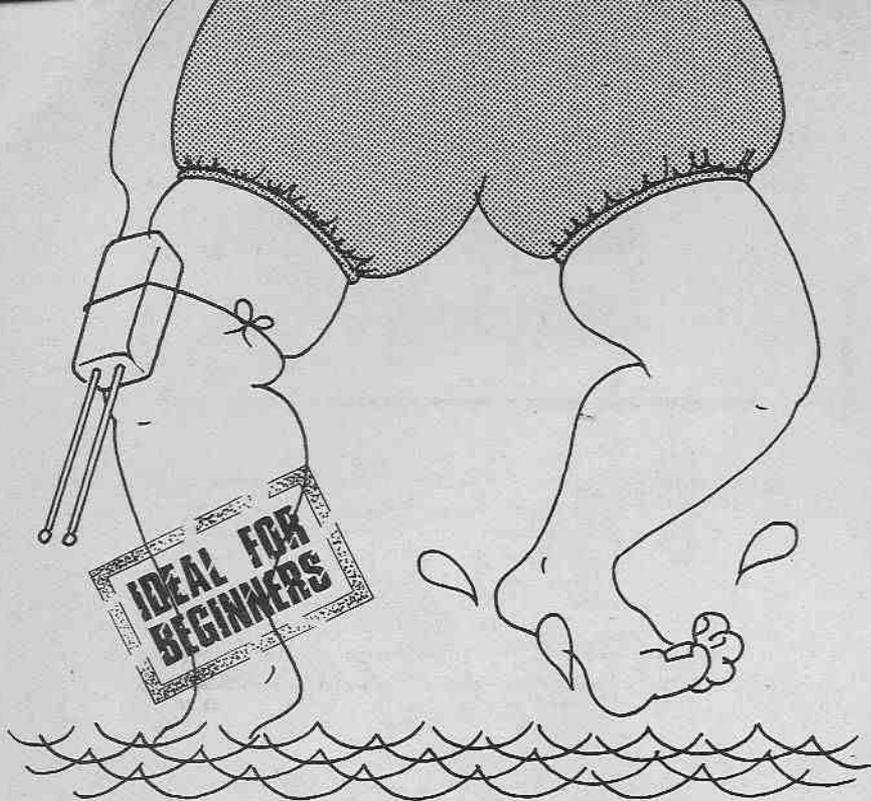

Water Level Alert

By A. R. Winstanley

APPEARANCE

This device is a little different from others previously described in that the actual physical appearance of it has been kept as aesthetic as possible. In particular the design of the sensor has, in the author's opinion, been greatly

NO DOUBT we have all at one time or another been somewhat unpopular with the other members of the household because all of the available hot water has been consumed by a certain person whilst taking a bath!

Possibly one of the safer plays here is to ardently deny using up the hot water and blame the inherent inefficiency of the water heating system, but somehow this does not seem to work.

Whilst the device to be described would not indicate how much hot water is left it will tell you in no uncertain terms when to let up on the taps, and thus hopefully keep the peace.

A specially designed sensor is placed inside the bath, and when the rising water touches the sensor, an alarm tone sounds. At this point you should turn off the taps or continue to draw water at your peril! On a slightly more serious note though, its main use, of course, is to enable the user to run a bath and leave it unattended, the alarm sounding when the water has reached the required level.

improved. After all, the appearance of a unit which is to be used in a domestic environment is important.

It is recognised that Veroboard-type sensors, where the water bridges adjacent strips of copper, thus sounding the alarm, are quite cheap and effective, but their appearance is none too pleasing and the actual construction does not make them suitable for use in the bathroom. On the other hand, custom designed printed circuit board sensors look very pleasing, but it is reckoned that not too many people have printed-circuit etching facilities.

One of the design criteria, therefore, was to come up with a water level sensor which could be assembled out of readily available materials, but which was quite cheap, durable and most of all attractive.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Water Level Alert appears in Fig. 1.

When water bridges the two probes, C1 charges up very quickly and turns on TR1 and TR2, which form a high-gain transistor switch. Each npn transistor requires the base to be about 0.6V more positive than the emitter for the device to switch hard on.

Thus when the base of TR1 is at 1.2V both transistors will switch on. The emitter current of TR1 becomes the base current of TR2, and so only a very tiny current is required in the base of TR1 to switch TR2 hard on.


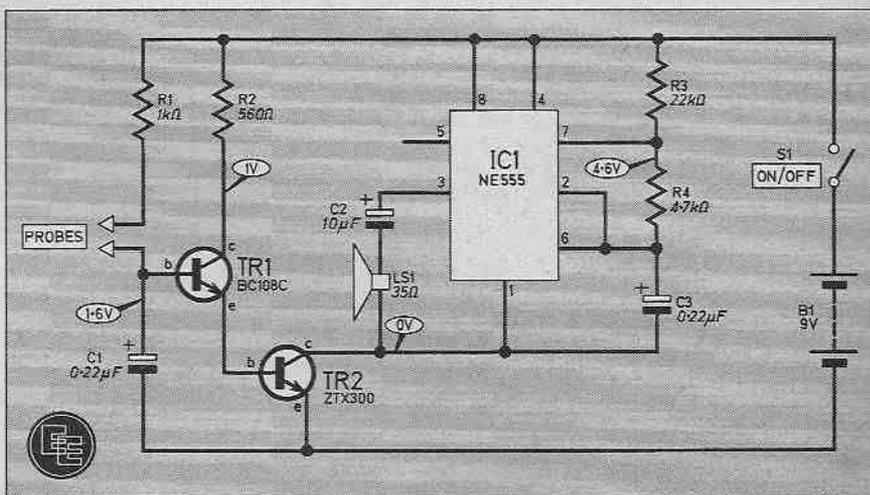
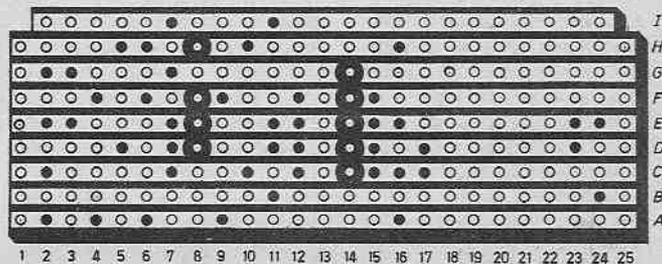


Fig. 1. Circuit diagram of the Water Level Alert.

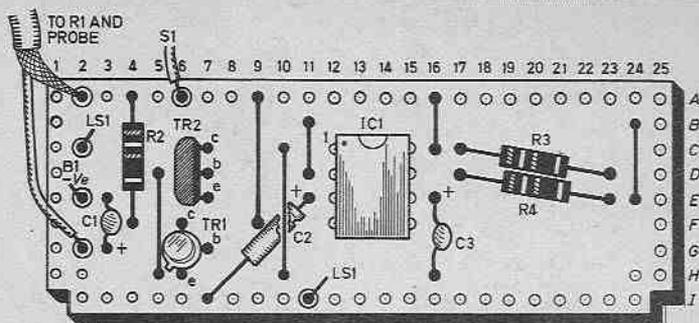COMPONENTS
approximate
cost **£3.00**
 excluding cases



● VEROPINS

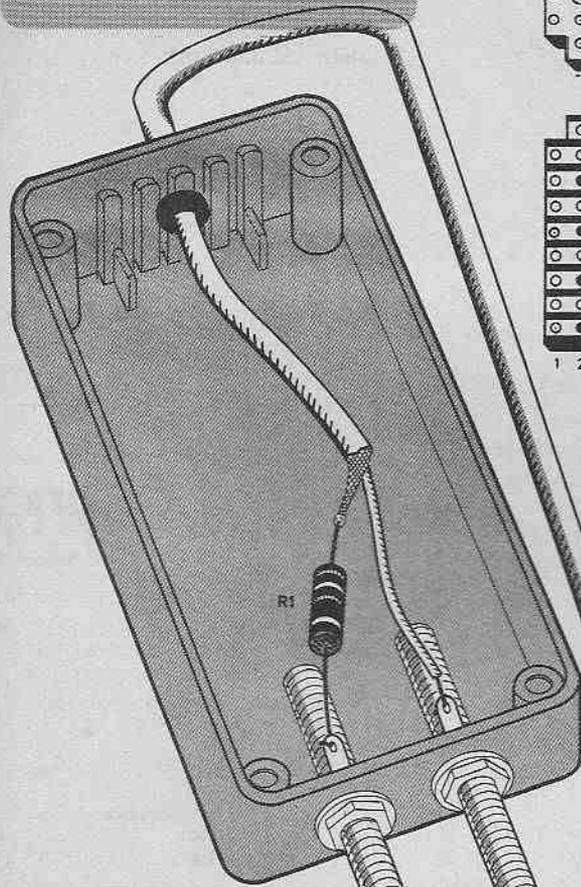


Fig. 2. Probe construction details. A series of small holes are also drilled on the underside to allow for drainage.

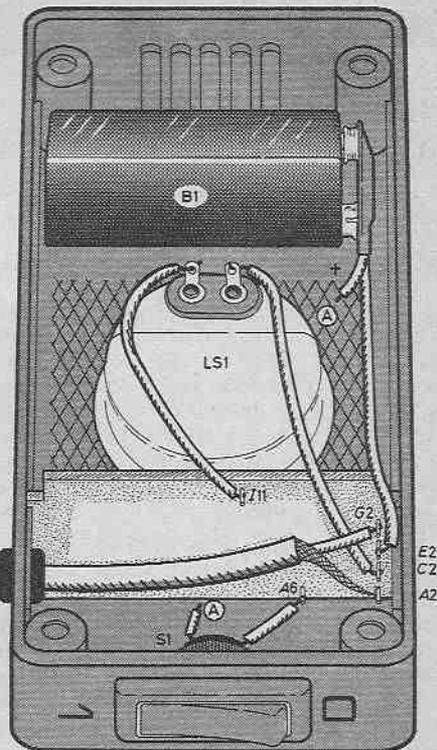
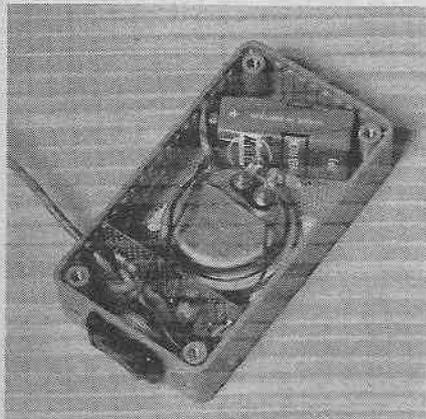


Fig. 3. Complete wiring details for the unit. Veropins are used as required.

Integrated circuit, IC1 and its associated components form an astable oscillator, and power is applied to this when TR2 switches on. The output, pin 3, is differentiated by C2 and LS1 which converts the rough square wave into a positive and negative spike.

CONSTRUCTION starts here

The system is housed in two plastic boxes. The first measures 100 × 50 × 25mm and forms the probe; the second measures 110 × 60 × 30mm and carries the electronics.


PROBE

The construction of the probe unit is illustrated in Fig. 2. Two 2BA threaded brass rods are used, each 150mm in length, and these are bolted to the case so that two 130mm probes protrude outwards. Connections to the rods are made by using a couple of 2BA solder tags, and a length of single core screened cable connects them to the other case. Note how R1 is included in the sensor unit.

DRAINAGE

Finish off the sensor by lettering it as necessary. Then glue two end pieces onto the ends of the brass rods. This will prevent the rods from scratching the bath enamel, and it will further enhance the appearance. Two plastic caps from some discarded Biro refill tubes were used on the prototype.

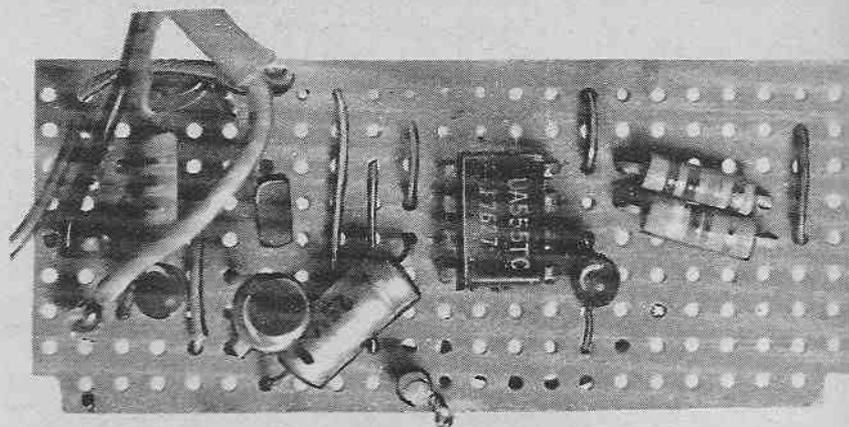If water does manage to get into the sensor case, it will accumulate inside at the bottom and eventually short the probes, sounding the alarm tone. To counter this, a series of 1mm holes are drilled near the bottom of the back panel to allow the water to drain away. The use of brass rods in the manner described has resulted in a quite attractive and very strong probe unit.



Component layout for the alarm circuit board.

COMPONENTS

Resistors

R1 1k Ω
R2 560 Ω
R3 22k Ω
R4 4.7k Ω
All $\frac{1}{4}$ W carbon $\pm 5\%$

Capacitors

C1 0.22 μ F 25V tantalum
C2 10 μ F 25V elect.
C3 0.22 μ F 25V tantalum

Semiconductors

IC1 NE555V timer i.c.
TR1 BC108C npn silicon
TR2 ZTX300 npn silicon

Miscellaneous

LS1 35 ohm earpiece (or similar moving coil loudspeaker approx. 40mm diameter)
S1 single pole, single throw rocker switch
B1 9V PP3 battery

Stripboard 0.1 inch matrix 23 holes by 9 strips; clip to suit battery; two 150mm lengths of 2BA studding; 2BA hardware; 8 pin socket to suit IC1; length of screened cable; piece of aluminium speaker grille; one plastic case 100 × 50 × 25mm, one plastic case 110 × 60 × 30mm; epoxy glue; connecting wire.

See
**Shop
Talk**
page 857

ALARM UNIT

The remainder of the circuit is built on a small piece of stripboard 23 holes by 9 strips. These dimensions allowed the circuit board to be retained by the guides in the case, and a different size (and layout) could be used if necessary, to suit the type of case purchased by the constructor.

The stripboard arrangement and other wiring is shown in Fig. 3. During construction, make certain that the capacitors are soldered in the right way round. Tantalum capacitors are used for C1 and C3 because of their small size, but they are very polarity sensitive.

It is recommended that an 8 pin d.i.l. socket is used with IC1. This will prevent damage being caused to the NE555 through excessive heating during soldering.

In particular observe the orientation of the transistor leads.


Drill the larger case to take the on/off switch and cable entry from the sensor. A 30mm cut-out was

made for the loudspeaker. A small piece of aluminium mesh was stuck inside the case over the cut-out, and then the earpiece was fixed over this using epoxy glue. Finally letter the case as necessary and apply a coat of clear protective lacquer.

With both cases completed, and all interconnections made, thoroughly check out the circuit board for mistakes. Look out for reversed polarities of components, whiskers of solder bridging adjacent strips, etc.

If all is well, connect the battery and switch on. Bridge the probes with a finger and thumb, this should cause the alarm to sound. Release the sensor and the tone should cease.

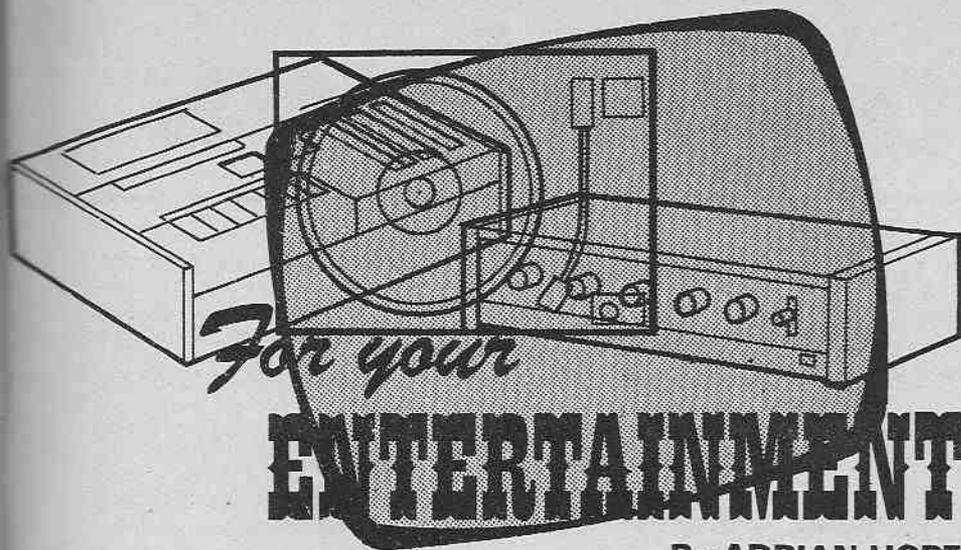The device is now completed and ready for use. The probe can be stuck inside the bath using double-sided adhesive strip. The main unit should be positioned where it can be heard with the bath running. \square



By ADRIAN HOPE

Last month we looked at paging but left unmentioned the important matter of the transmission frequencies used.

Inductive systems, relying on a closed loop running round the site to be paged, operate on a frequency of between 16 and 150kHz, often around 35kHz. But closed loop induction is inflexible and can't possibly serve a large site, for instance a sprawling factory or airport. So radio systems must be used on many sites, the transmission power being very carefully calculated and controlled to ensure that the paging signals do not stray off site.

The power involved can be remarkably low; the whole of London airport is paged with just a two-watt transmitter. Only occasionally will on-site powers reach 5 watts.

Radio transmission is, of course, also used for public paging. In London, the Post Office uses nine transmitters each of a hundred watts. Their aerial patterns overlap so the receivers have to be carefully designed to ignore phasing errors. This isn't too difficult because the signals being transmitted are in digital code rather than analogue speech. But clearly there is unlikely ever to be city area paging with speech.

Wave lengths

Now, the actual wavelengths. In Britain legitimate on-site walkie-talkie paging systems are split between u.h.f. and v.h.f., the speech is sent out from control on u.h.f. (at around 458MHz) and speech back to control comes in on v.h.f. (around 161MHz). The Post Office Radio Paging, bleep-only digital system also operates on v.h.f., at around 150MHz.

But the majority of on-site bleep systems are on 27MHz and hospitals are by a special dispensation allowed in emergencies to transmit real or synthesised speech as well as bleeps on this frequency. Return speech, that is from the bleeped doctor, is again on

161MHz. In fact return speech, whether in response to a message sent out on an inductive loop on 27MHz or on 458MHz, is always on the 161MHz band in the UK.

Citizen Band

Finally does that frequency 27MHz ring any bells with you? It should, because it's the frequency on which most Citizens Band walkie-talkies operate. If CB on 27MHz were to be legalised in the UK, it would effectively cripple the hospitals of England overnight, by jamming their bleep and emergency speech communication systems. This, more than anything else, confirms that if we do get CB in the UK it won't be on 27MHz.

Ultrasonics

Although the Home Office and Post Office together strictly regulate any transmissions (whether of bleeps, speech, radio control or anything else) their terms of reference leave some methods of transmission unregulated. Thus although it is illegal to remote-control a television or Hi-Fi System using modulated radio waves, it is quite legal and legitimate to remote-control using modulated sound waves.

For obvious reasons the sound waves used for remote-control are ultra-sonic, that is of too high a pitch to be heard by human beings, and more and more domestic systems are now using ultrasonic remote control.

The only snag is that some people, especially very young children, and most animals can hear frequencies inaudible to the average middle-aged engineer. So ultrasonic controls are not welcome in all households. This is why another type of control—infra red, is becoming popular.

The Post Office and Home Office only have powers to regulate *radio* transmission and the infra red band comes next to the radio bands in the electro-magnetic spectrum. It is in fact sandwiched between visible light

and the very highest radio frequencies as used for radar. Infra red beams can be used not only for remote control but high quality speech transmission as well.

There are already conference systems and cordless HiFi headphones that rely on modulated infra red as the unseen connecting link, and very good they can be. The only snag with infra red links is that they are, like visible light, directional. Whereas a radio aerial can send out control signals in virtually all directions, at the same time, an infra red transmitter has to be aimed fairly accurately at the receiver.

Light Links

Another type of link that falls outside the Post Office and Home Office regulations is the light link. In practice this usually means laser links and it is possible to carry very high fidelity audio, and even video, signals by modulating a laser beam. The beam can either be carried along optical fibres, and thereby round corners, or can be beamed direct like a pencil-thin searchlight.

Bugging

Already laser links are being used to replace hard wire electrical links in some situations (for example; for security against fire, interference or illegitimate tapping) and for the most part they involve the use of optical fibres.

Clearly it is for the most part unsatisfactory to carry messages via a direct laser beam travelling in space from A to B. But there is however one case where direct laser beams are used as links and that is in the rather shady area of bugging.

However shady the area may be, laser beam bugging devices come outside the wavelength regulations and have already been openly advertised for sale to the public through the press.

The beam from a low power laser is aimed at a window of a room to be bugged. The window will be vibrating to a minute extent in sympathy with whatever speech is going on in the room and the laser beam is so angled on the window surface that it reflects back to the source where there is a light detector.

The reflected beam carries an exact replica of the window vibrations and on demodulation produces an exact reproduction of the speech in the room. Perhaps fortunately such systems can be defeated. For one thing the beam is fairly easily visible, especially if you wear polarising spectacles.

For another thing it is possible to muffle the sound reproduced by drawing curtains across the window or confuse the sound by playing a radio set close to the window pane.

Everyday News



FULLY IN COMMAND

About 75 per cent of military communications are carried out on f.m. at very high frequencies (v.h.f.). Yet under tactical conditions in the field, the local terrain may make v.h.f. communication difficult, or impossible.

A major breakthrough by Plessey is likely to overcome the direct-line-of-sight "problem" and so have a major

impact in battlefield v.h.f. communications. This new concept in radio technology, Groundsat, provides common-channel automatic repeater facilities for both the command post and soldiers on the battlefield using an un-manned station which operates on the same frequency.

Groundsat is no larger than a conventional man-pack radio. Whilst being carried to a position for deployment it may be used as a conventional v.h.f. f.m. man-pack radio. Once deployed in position Groundsat works entirely unattended and can be easily hidden. Groundsat only goes into operation on demand. The radio operator can summon Groundsat to his aid by simply depressing his press-to-talk switch twice.

Unlike conventional rebroadcast stations which require the use of several different frequencies to avoid interference, Groundsat allows reception and transmission of messages simultaneously on the same channel.

In military operations the Command Post and the detachments can take full advantage of hollows for concealment and protection, while reliable communication is assured through the unattended relay station Groundsat deployed on a nearby hillside.

During field demonstration in hilly terrain witnessed by EE a 100mW Groundsat relay station sited on a hill permitted good communication to be maintained over a distance of 3 to 4 kilometres between base and mobile stations. Whereas from the same locations direct contact with the base was impossible, even when using a higher-powered packset with 20W output. At the relay site the two vertical rod aerials placed 18 metres apart were unobtrusive and apparently were not adversely affected by nearby trees.

The Ministry of Defence has expressed the view that Groundsat will have great potentials and has ordered equipment for field tests by the Army.

Space for Communications

The United Kingdom was the 16th nation to sign up as a partner in the European Communications Satellite (ECS) project. The satellite is expected to be launched in 1981 and will be used for trials until 1983 when a second, standby, will be launched and the service will commence. Design aim is for 12,000 telephone channels and two TV channels which can all be used simultaneously.

Each nation's cash contribution is proportional to the estimated use of the satellite. Britain's share is 15 per cent, equal with France, the largest contributors. The estimated overall cost of the project is not revealed. As well as the satellites, in geostationary orbit

over the equator, it is expected that a network of at least 15 major earth stations plus six TV-only smaller dishes will be installed.

Marine Links

Increased use of satellites has in no way diminished the need for submarine cables which are also used to contain the international communications explosion. New cables are currently being laid between Eastbourne and St Valery-en-Caux, France, and between the Norfolk coast and Denmark to expand the Nordic service to Denmark, Norway, Sweden and Finland.

Each will carry 4,000 simultaneous telephone channels and the repeaters, of which 108 will be used in the Nordic link, will use the latest type 40 long-life transistors developed by the British Post Office.

An experimental fibre optic data communication link 550 metres long has been installed at a pulp mill in Sweden. It links a micro-computer-based remote terminal to a central computer.

MACS on the way


"Early next year" is scheduled for the introduction of Motorola Advanced Computer System (MACS). MACS is the 16-bit micro-computer which will be developed into a micro-computer family".

The single-chip central processor will have 70,000 devices packed into the same size as present MPU chips and will have ten times the throughput of the original Motorola M6800 MPU. It is forecast, in fact, that MACS will exceed the performance of many of today's mini-computers—on a single chip!

PERSONAL "SHRINK"

The microcomputer software people, Petsoft, have just released a new catalogue of over one hundred business, educational and applications programs for the Commodore PET home computer, including the long awaited Microchess program (£14).

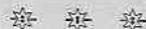One program from the new range which is already causing a stir is "Eliza", which simulates a consultation with a psychiatrist. The program runs on the standard 8K PET, and is believed to be the first conversation simulator available in UK.



The popular PET micro-computer is now being assembled in the UK at Eaglescliffe. Commodore Business Machines (UK) Ltd forecasts that production in the UK will reach 250 units a week by the end of the year.



In Camera

Five independent TV companies in the UK have now joined the shopping list for Marconi Mk IX family of colour TV cameras introduced to the market last April.

Biggest single order came from Granada Television, Manchester, for 27 cameras valued at over £1 million. Eighteen are for studio use and nine portables for outside broadcasts. The other four users are Scottish TV, Tyne Tees, Anglia TV and Southern TV.

Marconi have also been busy supplying new medium wave transmitters for the big programme wavelength reshuffle due this month (November). Of 24 new transmitters, each of 50kW output, eleven were contracted to be installed and operational by mid-November and the remainder during next year.

Back To School

Our Photograph shows the Speak & Spell microprocessor learning aid from Texas that was mentioned in these pages last month.

The learning aid is aimed at helping children to spell and pronounce over 200 basic vocabulary words and has been developed with the guidance of leading educators. The aid helps children learn by letting them hear, see and spell a word; keying in the correct answer scores points, incorrect gives a "try again" readout.

Further news from Texas is the announcement that their popular maths learning calculator "Little Professor" has been reduced in price to £11.50 including VAT.



The Sinclair 2-inch Microvision TV is used as the basis of a video monitor, now available as either a stand-alone portable unit with internal batteries or as a panel-mounted unit.

Picture resolution is stated to be 325 lines and used as a data terminal the unit can resolve up to 40 characters per line, 24 lines.



World First

The IBA-developed system of digital video recording, claimed to be the most advanced system yet demonstrated, is being taken up by two of the world's leading VTR (Video Tape Recording) manufacturers, and negotiations are at an advanced stage with several others.

Agreements have been signed between the Independent Broadcasting Authority and Bosch Fernseh (Robert Bosch Ltd) and Sony Broadcast, representing major broadcast engineering companies with headquarters in West Germany and Japan respectively.

Under the agreements IBA engineers will provide full know-how and technical advice on the world's first digital system capable of producing colour television pictures on one inch magnetic tape at tape speeds of under ten inches per second.

RANDOM TIME

It seems likely that Texas Instruments will be first in the field with the 64k random access memory (RAM). Samples are expected to be available to the trade this month (November) and production quantities should be available soon afterwards.

ANALYSIS

VERY WELL, THANK YOU!

The silicon chip and, by implication, the whole of electronics has experienced this year an unprecedented barrage of popular publicity, much of it adverse. Instant opinions, mainly from the technologically illiterate, have even suggested that the chip, harmless in itself, is inherently evil and that its widespread application can do nothing but harm. Well, we must all form our own judgements. Almost anything you can think of can be put to use for good or bad.

There is one application of electronics, however, on which there should be no disagreement that the outcome is wholly beneficial and that is in health care. Medical electronics is now fully established as a specialist branch of the electronics industry.

It all started before the chip, in the valve era of the 1930's, with radio diathermy for the relief of aches and pains. It was in those days too, that advances in valve technology allowed the development of high-gain low-noise amplifiers to detect and amplify to a useable level the feeble electrical impulses then only suspected to be generated in the brain, the heart, and in other parts of the human frame.

Electronics soon became a powerful ally in medical research and in the relief of human suffering. What a revolution! Remember that for three hundred years medical science had, as its best tool, only the optical microscope. The advent of the electron microscope, infinitely more powerful, revealed tissue structures and other tiny details, perhaps imagined but never before actually observed.

Similarly with X-ray technology, much refined since Rontgen's discovery of X-rays in 1895, but still with inherent defects in its application until Hounsfield's brilliant concept in 1967 which led to the first clinical trials of the EMI Scanner in 1971 and world-wide adoption since then.

The solid-state era and component miniaturisation made possible the first body implants. The first endoradiosondes ("radio pills") for measuring internal temperatures and pressures. Later, the cardiac pacemaker which has prolonged the lives of countless people, keeping them actively involved in affairs rather than confined to home or hospital.

No operating theatre today is complete without its battery of electronic instruments to display and record parameters like respiration, temperature, heart rate. CCTV allows students to observe every detail of surgery in colour close-up, although at some distance away.

Intensive-care wards have elaborate patient monitoring systems with recorders and alarms which respond to the slightest change in physical condition. And the electroencephalograph (EEG) is a most valuable tool both for research and treatment of mental disorders.

Electronics has transformed the practice of "conventional" medicine and surgery. Now I note with some interest it is also penetrating the areas of "fringe" medicine. A Racal company is supplying £15,000 worth of special panel meters to a West German medical supply company for inclusion in electroacupuncture equipment. Even this ancient Chinese science can apparently benefit from an electronic up-date.

Electronics and the silicon chip which it is now based will remain a good friend, whatever the critics say. Many of us have cause to thank the contribution of electronics when greeted with "How d'you do?" and being able to respond with a heartfelt "Very well, thank you!"

Brian G. Peck



Atomic Surveillance

The new nuclear power stations being built at Hartlepool and Heysham will have TV surveillance for remote handling of irradiated fuel in the underwater storage ponds.

The submerged cameras will be in stainless steel waterproof casings which also contain the remote focus and iris controls.



EE2020

TUNER A

HI-FI SERIES

THE EVERYDAY ELECTRONICS 2020 TUNER AMPLIFIER is primarily intended for the more advanced constructor who would like to build a quality stereo equipment at a cost well below that of a commercial unit of similar performance.

The total outlay for components and materials will be in the region of £90-£120 for the completed project.

All components are readily available and no special equipment is needed for setting up or alignment. The amplifier section has been designed for 20+20 watts output, which, together with a very sensitive f.m. radio section will provide top quality signals under almost any conditions.

Included in the amplifier section are separate controls for bass, treble, volume, balance, high and low frequency filters, and tape monitoring. There is provision for adding a quadrasonic decoder or perhaps a graphic equaliser at a later date.

The tuner section uses the latest techniques including a mosfet r.f. stage, band pass coupling, varicap tuning, separate oscillator with automatic frequency control (d.f.c.), ceramic i.f. filters, quadrature discriminator and a phase lock stereo decoder. Five preset stations are provided in addition to manual tuning.

This may seem a large project to undertake, but in fact, any one who can solder properly and follow the step by step instructions should be able to produce a tuner amplifier equal to those available commercially at a much higher price. The secret of success is to take each section in turn and look upon it as a project in its own right. Thus, instead of one mammoth project, treat the 2020 as a series of small ones.

This is a practical project and no technical knowhow is required other than to be able to follow the diagrams and instructions. Don't rush the construction, take your time, carefully checking each completed section and you will finish up with a tuner amplifier with which you can justifiably be proud to say "I built it myself".

GENERAL DESCRIPTION

The EE 2020 Tuner Amplifier is assembled on a metal chassis consisting of a base plate and front and rear panels.

All operating controls appear at the front panel; input and output sockets and terminals are located on the back panel. Complete enclosure can be effected by means of a simple wooden case or "sleeve", and details will be provided for the construction of such a case.

Most of the electronics are assembled on printed circuit boards. There are five p.c.b.s in all. This arrangement is most convenient for the construction, and enables the work to proceed by instalments in an orderly fashion, section by section.

The plan of the 2020 series of articles is as follows:

- Part 1 Introduction, Specification, Circuit Diagrams and Technical Description. Bulk Components List.
- Part 2 & 3 Construction of the p.c.b.s and Individual Component Lists.
- Part 4 Construction of Chassis
- Part 5 Assembly within the Chassis and Inter-unit Wiring
- Part 6 Setting Up and Operation

BULK COMPONENTS LIST

All resistors, potentiometers, capacitors, semiconductors and pushbutton switches required are listed below. This will assist the constructor to obtain the advantages of bulk buying.

Fully detailed Components Lists for each sub-section will accompany the p.c.b. and component layout diagrams to be published in the next two articles.

All miscellaneous items including hardware and material for the chassis will be specified in the appropriate parts of this series.

CIRCUIT DESCRIPTION

An overall view of the EE 2020 Tuner Amplifier System is given in the block diagram Fig. 1.1. Apart from showing the electronic organisation, this block diagram broadly indicates the physical arrangement: the subdivision of the whole into easily

manageable sections, each built on a printed circuit board. These boards are designated A, B, C, D and E.

Interconnections between boards are made via terminal pins. These are shown as open circles on the circuit diagrams Fig. 1.2a and Fig. 1.2b and each has a unique identification. Following "T" the second letter indicates the board; TA1, TE8 and so on. The useful function provided by these terminal pins will become apparent when the practical building work is in hand.

Where the circuitry is duplicated for the left and right stereo channels, terminal pins are marked in all layout and wiring diagrams with an additional letter "(a)" or "(b)" signifying left or right channel respectively. For example, TB9a, TB9b. The circuit diagram however shows only one channel ("a" or "left") and all terminal pins which are duplicated are shown with a suffix "a".

Beyond the stereo decoder IC2 and up to and including the Power Amplifier stages the circuitry divides into two identical channels. Only one channel ("a" or "left") is shown in the circuit diagrams, but the second is an exact replica of that shown. All these additional components are fully accounted for in the component lists and in the detailed layouts for the appropriate p.c.b.s.

In all these lists and diagrams duplicated or "twinned" components are distinguished by the suffix ("a") for left hand channel and ("b") for right hand channel.


In the circuit diagrams Fig. 1.2a and Fig. 1.2b one channel only is shown, and all the components in these areas can be considered as having the suffix ("a") (for example, R41(a) and TR5(a)), although only a few components, such as the pushbutton switches and the phono sockets, have actually been so labelled in Fig. 1.2a and Fig. 1.2b.

R.F. SECTION

In any hi-fi receiver system one of the most important parts is the radio frequency (r.f.) section. Radio signals can range in strength from a few microvolts in a fringe area, to perhaps a hundred millivolts or more close to a transmitter. The weaker signals

BY E.A. RULE*

AMPLIFIER PART 1

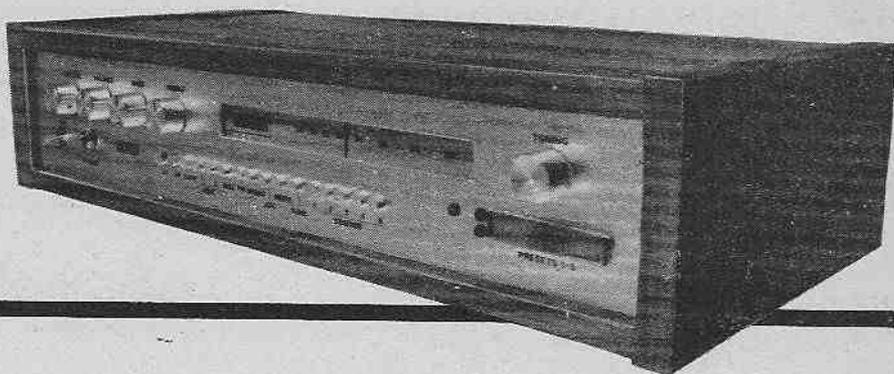

must be amplified without adding any noise or distortion (as this could not be removed later) to a suitable level for the mixer stage, and very strong signals may need to be reduced in level to prevent overload of the mixer.

A range of signal levels from 1 microvolt to 100 millivolts is a working range of 100dB and in some locations signals of over 1 volt could be encountered (a range of 120dB!). Should the r.f. sections fail to handle this range of signal levels, then cross modulation and other undesirable effects could take place.

Under practical conditions, there would be more than one signal presented to the r.f. section at any one time and another important requirement is r.f. selectivity. The r.f. section must select the wanted signal and reject all the others. In general the more tuned circuits before the mixer stage the higher the r.f. selectivity.

The selected signal is mixed with a local oscillator signal to produce the intermediate frequency (i.f.), the difference between the two, at which all further processing of the signal takes place. As a narrow bandwidth (250kHz approximately) is used in the i.f. amplifier to provide good adjacent channel selectivity the local oscillator must be very stable in frequency, otherwise the resulting i.f. signal would drift out of the i.f. pass band and distortion of the signal would result.

For the Everyday Electronics 2020 tuner amplifier it was decided to use a commercial r.f. section and the unit selected for this is the excellent TOKO EF5600U. This uses a dual gate MOSFET r.f. amplifier with automatic gain control and is capable of handling signals over a range from 0.8 microvolts to well over 100 millivolts. It has four varicap tuned circuits before the mixer which provide a very high degree of r.f. selectivity—with over 90dB of rejection at the image and other unwanted frequencies being obtained.

*T and T Electronics

Our author has been engaged in research and development in the Hi Fi field for the last 30 years, and has been responsible for many commercial products.

SPECIFICATION

AUDIO SECTION

Power Output (both channels driven) into 8 ohm load 20 + 20 watts r.m.s.

Power Bandwidth at -1dB: 20Hz—20kHz

Harmonic distortion at rated power:

at 10kHz	0.24%
at 1kHz	0.18%
at 40Hz	0.10%
at 1 watt	0.16%

Damping Factor: 40

Rise Time: Power Amplifier only

5μsec

Overall

7μsec

Stability

unconditional

Frequency response:

Power Amplifier only -1dB	20Hz—20kHz
Overall: Aux inputs ±1dB	20Hz—20kHz
Disc inputs RIAA ±1dB	20Hz—20kHz

Input	Sensitivity	Overload	Impedance	Hum/Noise
Aux (1+2)*	90mV	2.5V	1 MΩ+200pF	-68dB
Tape	90mV	—	50kΩ approx.	-67dB
Disc**	4mV	110mV	47kΩ approx.	-67dB

* For ceramic or crystal pickup ** For magnetic pickup

Tape Output: 90mV

Tone Controls:

Bass	±15dB at 70Hz
Treble	±15db at 14kHz

Filters:

HF (See curves)	-3dB at 4.5kHz
LF (" ")	-3dB at 26Hz

RADIO SECTION


Frequency range 88—102 MHz

	Mono	Stereo
Sensitivity 1HF 30dB (EMF)	1.6μV	
S/N 50dB "	2μV	20μV
Ultimate signal/noise "	72dB	69dB
Harmonic distortion at 100% 1kHz modulation	0.3%	
Image rejection	-100dB	
Repeat spot (F1 + 1/2F)	-100dB	
Capture ratio	2dB	
Selectivity ±400kHz	60dB	
Signal strength meter range	1μV—100mV	
Mute signal level	0.5μV	
" Deviation ±	45kHz	
A.F.C. Hold ±	1MHz	
" Pull in ±	500kHz	

GENERAL

Headphone Jack mutes loudspeakers and couples phones to Power Amplifier output

Cost to make, between £90—£120.

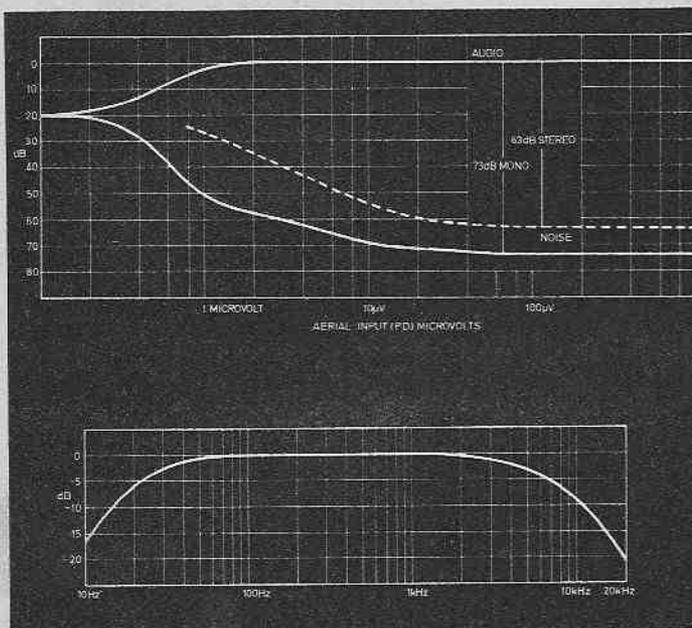

2020 TUNER AMPLIFIER CHARACTERISTIC CURVES

- (a) F.M. Radio. Overall signal to noise for various input signals
- (b) Frequency response of i.f. and h.f. filters
- (c) Frequency response of tone controls showing maximum and minimum settings.

Board A

I.F. AMPLIFIER

The main job of the i.f. amplifier is to provide selectivity, remove unwanted impulse noise and any other amplitude modulation (a.m.) on the signal. The f.m. detector is included in this section, which as well as converting the frequency modulated signal to audio, provides control voltages for automatic frequency correction (a.f.c.). Automatic gain control (a.g.c.) voltage for the r.f. stage is also obtained from the i.f. amplifier section.

A single integrated circuit IC1 provides all these functions except selectivity, which is obtained by using two 10.7MHz ceramic filters F1, F2, which do not require alignment.

IC1 is the RCA CA3198E, a later version of the CA3089. This is a monolithic integrated circuit that provides all the functions of a f.m. i.f. system. It includes a three-stage amplifier/limiter with level detectors for each stage, a double-balanced quadrature detector and a low distortion audio amplifier which features a muting circuit. It also has a programmable delayed a.g.c. for the r.f. section. An output voltage with a log. law is available to drive a signal strength meter, ME1, which will show a useful range of inputs from 1 microvolt to 100 millivolts when used with the EF5600 r.f. unit.

An a.f.c. voltage is provided and this is further amplified by transistors TR1 and TR2 so that it can be operated in conjunction with the main varicap tuning voltage. This method ensures that all the r.f. circuits remain correctly tuned to the required frequency. (The other method of only applying a.f.c. voltage

to the oscillator tuned circuit can cause loss of sensitivity due to mistuning of the r.f. tuned circuits with that of the oscillator.)

A single coil L1 is used with the quadrature detector and provides a low distortion signal to the audio section of the IC1. A double-tuned circuit would give lower distortion, but special equipment would be needed to correctly align the two coils—the single-coil circuit can be simply adjusted using the tuning meter.

The output from the audio section (pin 6) IC1 is at the correct level for feeding into the stereo decoder.

STEREO DECODER

The stereo decoder is designed around the Texas Instruments SN76115AN phase lock loop stereo decoder IC2.

The composite audio signal from IC1 is fed into IC2 at pin 2. IC2 demodulates the audio difference information from the 38kHz subcarrier contained in the composite audio signal. The 38kHz subcarrier is regenerated using an internal 76kHz oscillator phase locked to the pilot tone, the internal oscillator requiring no inductors. The level of the 19kHz pilot tone in the composite signal is detected and used to automatically switch a stereo/mono switch.

The stereo beacon lamp D1 is switched by a signal appearing at pin 6.

Channel 1 (left) signal appears at pin 4 of IC2 and is fed via C18 to a two-stage low distortion amplifier TR3, TR4.

This provides some amplification and also the correct matching for the low-pass stereo filter F3. This filter removes any unwanted 19kHz and 38kHz signals produced by the decoding process and prevents these beat-

ing with a tape recorder bias oscillator. If this happened, recordings from stereo radio would be almost impossible due to unwanted whistles.

Channel 2 (right) signal appears at pin 5 of IC2 and follows a similar route as Channel 1 to the second input of F3. The circuitry between IC2 pin 4 and F3 involving TR3, TR4 and associated components is thus duplicated—appearing between IC2 pin 5 and the second input of F3, although not shown in the circuit diagram.

In all component lists and layout diagrams duplicated components are distinguished by the suffix "a" for left hand channel and "b" for right hand channel.

The two outputs from F3 are fed to their respective pushbutton switches S13a (left hand channel) and S13b (right hand channel) located on Board B.

Only a single preset potentiometer (VR2) requires adjustment to set the correct frequency of the phase lock for optimum stereo separation.

VARICAP TUNING

The varicap diode circuit consists of two main sections: the manual tuning and the pre-set tuning.

The 14.5V stabilised d.c. supply from the power supply module provides the voltage required for tuning. This supply is fed in via TA3 and applied via R28 to the top end of the manual and preset potentiometers, VR3 to VR8 inclusive. The bottom ends of these potentiometers go via the preset VR10 to earth. VR10 is used to set the voltage at the bottom end of the potentiometer to exactly 3.2 volts.

The a.f.c. control circuit is connected to the junction of R28 and the top ends of the tuning potentiometers.

As the current through TR2 varies due to the a.f.c. voltage from the i.f. section it will cause the voltage at the end of R28 to vary and correct any tendency to drift or errors in tuning, by changing the actual voltage supply to the varicap diodes.

This change in voltage is of course arranged to be in the correct phase. If the tuning voltage goes higher the varicaps will adjust to a lower capacity and therefore the frequency of the tuned circuits will go higher. This change will cause the i.f. frequency to also go higher which will mean that the detector will be off tune. A voltage will occur at its output which will increase the current through TR1 and TR2 and in turn cause the voltage drop across R28 to increase thus lowering the varicap voltage and off-setting the original increase. Similarly with the reverse process.

L.E.D. TUNING INDICATOR

The output of each potentiometer goes to a pushbutton switch and any one can be selected for use. In order that the presets can be correctly adjusted to a wanted station it is necessary to provide some means of showing the correct turning point. An op-amp, IC3b, is used for this. One input of the op-amp is connected to the manual tuning potentiometer VR3 and the other input is connected to the selected preset. The output of the op-amp goes to two l.e.d.s connected in parallel but with reverse polarity and these are connected to

a d.c. supply exactly half the supply rail voltage of the op-amp.

If both inputs of the op-amp are equal, the output will be exactly half of the supply voltage and in theory neither l.e.d. will light up. (In practice some unbalance may cause one to light). Now, by first tuning the manual control to the required station and then selecting a preset, at the same time keeping the manual tune button pressed, the voltage from each will be fed to opposite inputs of the op-amp. Adjusting the preset until the l.e.d.s go out (or just change over) will mean that the preset voltage is the same as the manual tuning voltage and that the pre-set is tuned to the same station.

The l.e.d.s will show if the preset is high or low in frequency relative to the manual tuning potentiometer. Final adjustment is made using the tuning meter as an indicator.

Preset VR9 is provided to adjust the offset voltage of IC3.

The other half of the dual op-amp, IC3a, is used to isolate the r.f. unit from the varicap tuning so that its loading effect does not cause inaccurate settings of the presets. It also provides a low impedance drive voltage for the varicap diodes in the r.f. unit.

Board B

CONTROL UNIT

The lower half of Fig. 1.2a is now to be described. All circuitry in this area is, in reality, duplicated, although

only one channel is shown in the diagram.

Apart from the small bottom left corner section (which is the Pick-up Pre-amplifier) the whole of this lower portion of Fig. 1.2a is the Control Unit. All this circuitry is assembled on Board B, except for the four variable controls and the phono sockets which are mounted on the front and rear panels respectively.

Two auxiliary inputs are provided, SK2 and SK3. Either of these may be used with a crystal or ceramic pick-up as their high input impedance of 1 megohm would provide a reasonable match. These inputs are also suitable for any other signal source whatever its output impedance, providing that the signal is approximately 90mV.

A disc input is provided at SK4 (see Pick-up Pre-amplifier).

The output from the pick-up pre-amplifier, along with the AUX inputs from the FM tuner section go to the pushbutton input selector switches S9 to S13 inclusive. All unselected inputs are shorted to earth.

After the required input has been selected it goes to the first stage in the control unit, comprising TR5 and TR6. This is a boot-strapped two-stage amplifier with a high amount of negative feedback. The stage gives around 8dB of gain and has a 1 megohm plus 200pF input impedance and low output impedance.

Following this stage are the high- and low-pass filters. These are active filters giving approximately 12dB/octave slopes. The active stage uses


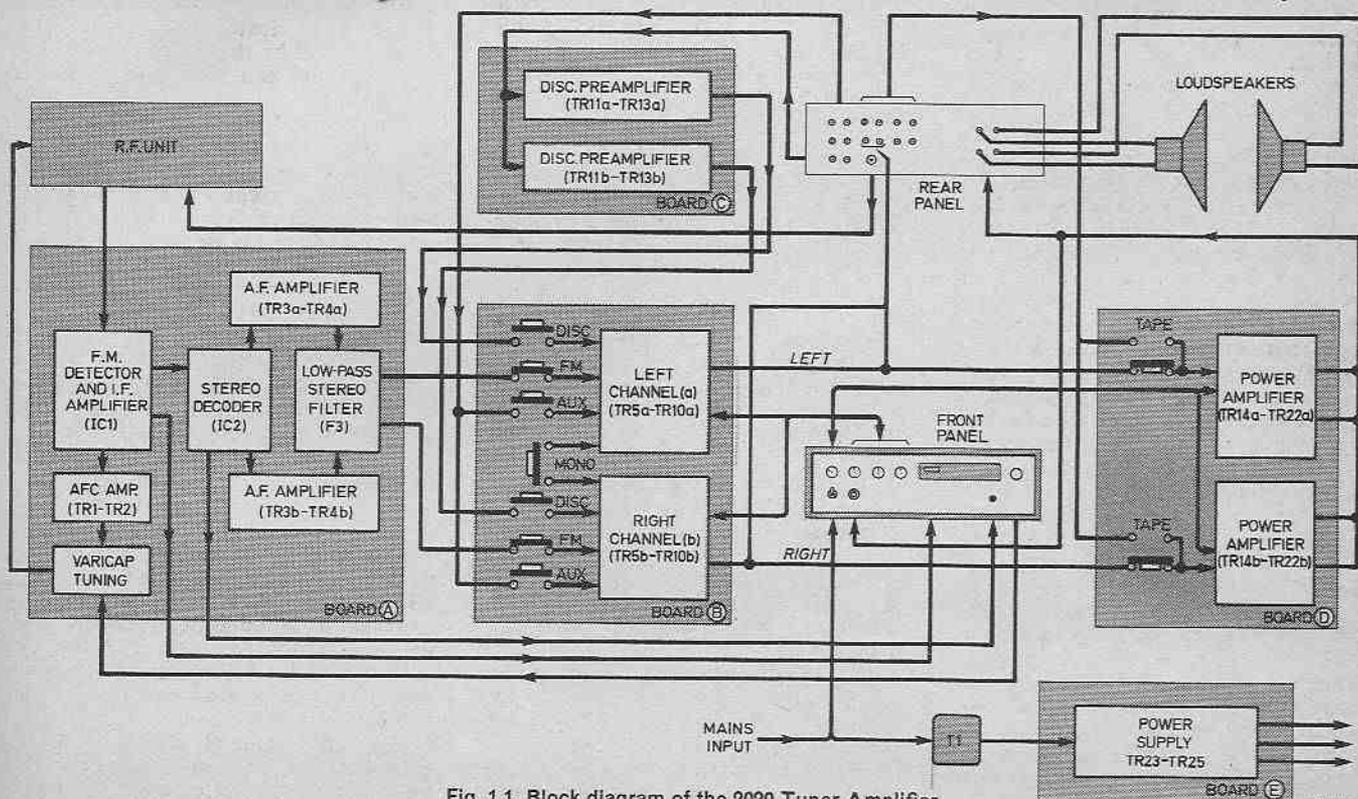
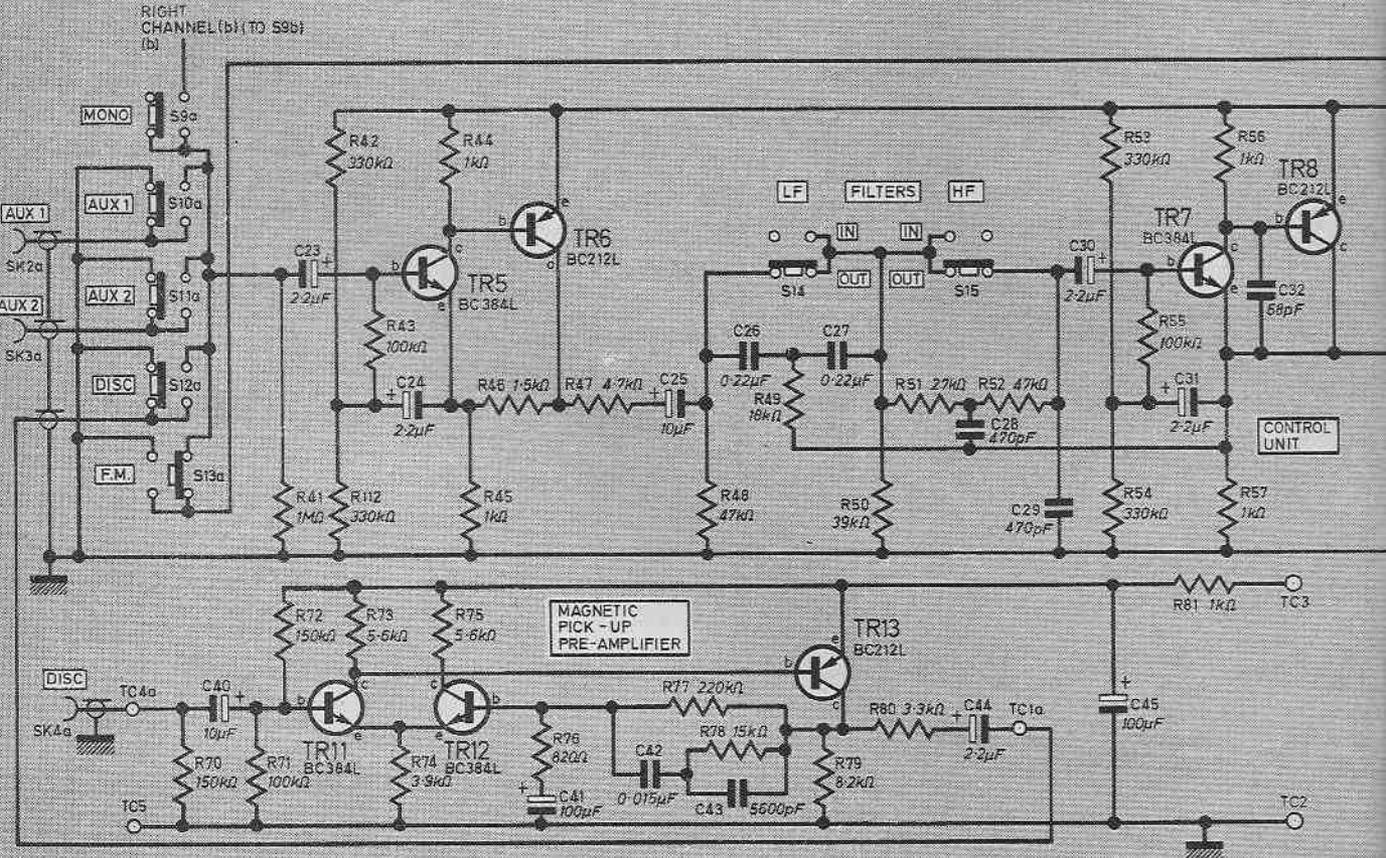


Fig. 1.1. Block diagram of the 2020 Tuner Amplifier

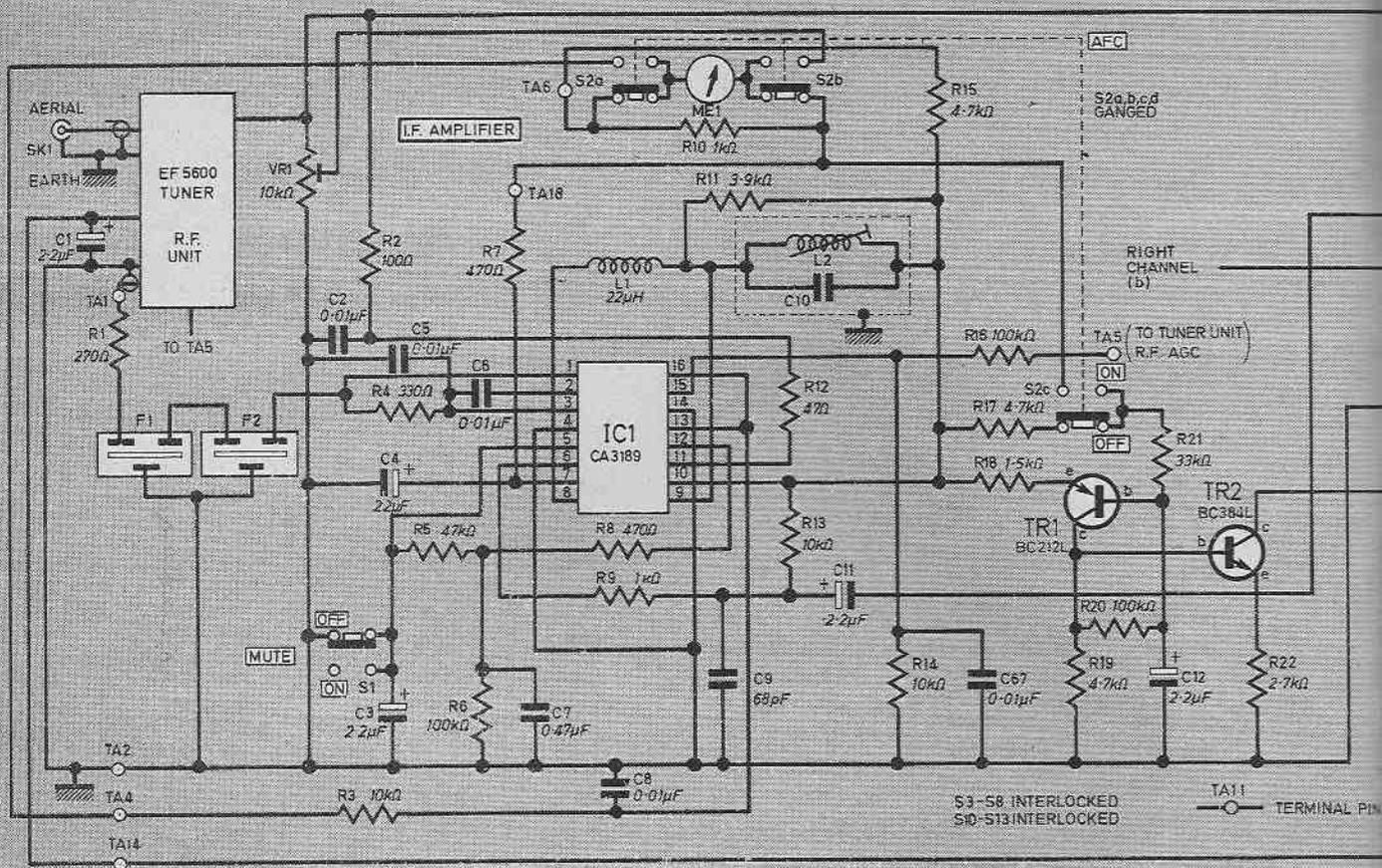


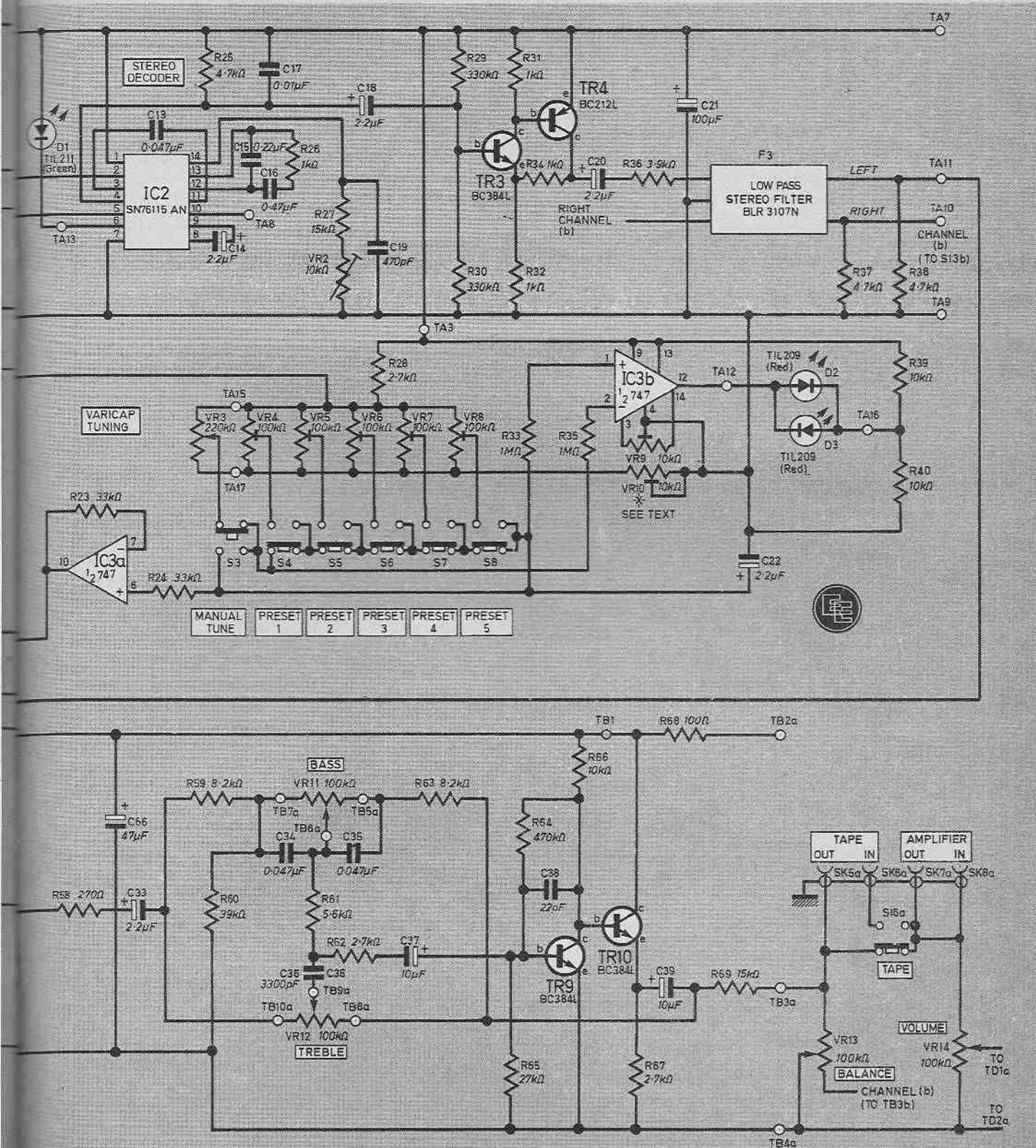


Fig. 1.2a. Circuit diagram of the 2020 Tuner Amplifier: r.f. and i.f. stages; a.f. preamplifier; control and switching stages.

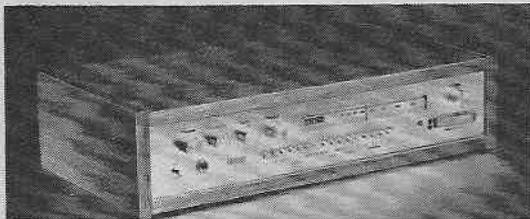

EE2020

BULK COMPONENTS

See page 872

Open Skeleton Cermet Presets,
Miniature Horizontal Mounting
RS type 185-432

SEMICONDUCTORS

Transistors

Type	Qty
BC182L—TO5 silicon npn	10
BC212L—TO5 silicon pnp	13
BC384L—TO5 silicon npn	16
BFY51 silicon npn	2
TIP33A silicon npn	2
TIP34A silicon pnp	2

NOTE

Type BC384L—TO5 is a very low noise transistor and has been used throughout the receiver to standardise on types. Type BC184L—TO5 may be used instead with a slight increase in noise.

Most transistors used in the equipment have the suffix TO5. This means that the leads are performed by the maker to the TO5 pin circle. If devices with a different suffix (or none) are obtained it will be necessary for the constructor to form the leads to suit the TO5 configuration before using.

Diodes

Type	Qty
1N4001 silicon rectifier 1 A	4
TIL209 i.e.d., red	2
TIL211 i.e.d., green	1
BZY88C 12V Zener, 400mW	1

Integrated Circuits

Type	Qty
CA3189E f.m. i.f. system (RCA)	1
SN76115AN stereo decoder (Texas)	1
SN72747 dual op-amp.	1
μ A723 voltage regulator	1

PUSHBUTTON SWITCHES

Description	Qty
2-pole changeover (RS type 338-434)	15
4-pole changeover (RS type 338-636)	1
4-switch latching assembly (RS type 338-254)	1
6-switch latching assembly (RS type 338-614)	1

R. F. UNIT

R. F. Unit	EF5600
Stereo Filter	BLR3107N
Choke	220K/22 μ H
Coil	KACSK 586HM
Tuning Meter	906
10.7MHz filters CFSE/SFE 10.7 (2 off)	
(Available from Ambit Ltd.)	

FIXED RESISTORS

$\frac{1}{2}$ W 5% High Stability Carbon Film

Value	Quantity
47 Ω	1
100 Ω	2
270 Ω	3
330 Ω	1
470 Ω	2
820 Ω	4
1k Ω	23
1.5k Ω	3
2.2k Ω	3
2.7k Ω	7
3.3k Ω	2
3.9k Ω	7
4.7k Ω	14
5.6k Ω	8
8.2k Ω	6
10k Ω	10
15k Ω	9
18k Ω	2
27k Ω	4
33k Ω	3
39k Ω	4
47k Ω	5
82k Ω	2
100k Ω	17
120k Ω	2
150k Ω	4
180k Ω	2
220k Ω	2
330k Ω	10
470k Ω	2
1M Ω	4

$\frac{1}{2}$ W 10% carbon

Value	Quantity
2.2 Ω	1

1W 5% Carbon

Value	Quantity
1k Ω	2

2.5W 10% Wirewound

Value	Quantity
0.22 Ω	4

25W 10% Wirewound RS type 157-588

Value	Quantity
100 Ω	1

POTENTIOMETERS

Open Skeleton Presets,
Miniature Horizontal Mounting
(RS type 184/5)

Value	Quantity
2.2k Ω	2
10k Ω	4
47k Ω	2

Value	Quantity
10k Ω	1

Ganged Potentiometers \pm 20%,
Tracks Matched To 2dB
(RS type 161/162)

Value	Quantity
100k Ω log. law	1
100k Ω Lin. law	2

Single Potentiometers \pm 20%

Value	Quantity
100k Ω	1
220k Ω	1

Multi-turn Potentiometers,
Special Log. Law For Diode
Tuning

(Ambit type AB47)

Value	Quantity
100k Ω	5

CAPACITORS

Disc ceramic, low voltage

Value	Quantity
0.01 μ F	5

Polyester, Mullard type C280

Value	Quantity
0.001 μ F	2
0.047 μ F	7
0.1 μ F	2
0.22 μ F	8
0.47 μ F	2

Polystyrene 5% or better; or
sub-miniature Plate Ceramic

Value	Quantity
68pF	3
470pF	5
3300pF	2
100pF	5
15pF	2
22pF	2
5600pF	2
4700pF	1

Polyester 5%

Value	Quantity
0.015 μ F	2

Electrolytic, Printed Circuit type

Value	Quantity
2.2 μ F 63V	22
4.7 μ F 63V	2
10 μ F 63V	11
22 μ F 63V	1
100 μ F 16V	5
220 μ F 63V	3
47 μ F 63V	3
22 μ F 63V	2

Electrolytic, Single-ended

Value	Quantity
4700 μ F 63V	1
2200 μ F 63V	2

Electrolytic, Double-ended

Value	Quantity
47 μ F 63V	2

two transistors TR7, TR8 with a bootstrapped input to provide a high impedance load for the low-pass filter. Hundred per cent negative feedback is used to keep distortion to a negligible level.

The low impedance output goes to the following tone control stage, which uses a Baxandall circuit with voltage amplifier and emitter follower stages TR9, TR10. Some high frequency roll-off is introduced to limit the frequency response above 20kHz as this helps prevent transient intermodulation distortion by ensuring that the rise time of the control unit is longer than that of the power amplifier.

The output from the tone control stage is fed to the balance control VR15, and to the tape output and tape monitor switch S16. The tape monitor switch selects either the output from the control unit or tape. As the tape input goes directly from this switch to the power amplifier, the tone

controls and filters do not operate on tape replay. However, they are operated on tape record. This method enables a tape to be corrected during recording and means it can be replayed on any amplifier with a flat frequency response.

From the tape monitor switch the signal goes via the "pre-amp out" "main amp in" link to the volume control VR14, which is a dual-ganged potentiometer matched to within 2dB, and ensures a balanced output over a wide range of control settings.

The signal then goes to the power amplifier input. See Fig. 1.2b.

tivity is 4 millivolts with an overload limit of 110 millivolts, i.e. approx. 29dB. Pick-ups rated at more than 4 millivolts/cm/Sec may need an external attenuator. As the noise level with reference to 4 millivolts is 67dB a full dynamic range of some 96dB is available. Using a pick-up rated at around 1 to 2 millivolts/cm/sec should be about optimum to make full use of the excellent dynamic range available.

The magnetic pick-up pre-amplifier (TR11 to TR13) uses a differential input configuration. This isolates the pick-up from the effects of any feedback used for RIAA equalisation and enables an almost pure resistive load to be obtained. RIAA equalisation is obtained with an RC network in the negative feedback path and this method ensures low distortion as well as the correct RIAA frequency response. The distortion of the magnetic pre-amplifier alone, is less than 0.1 per cent.

Board C

PICK-UP PRE-AMPLIFIER

A disc input of 47 kilohms impedance is also provided and this will match most magnetic cartridges available at the present time. Its sensi-

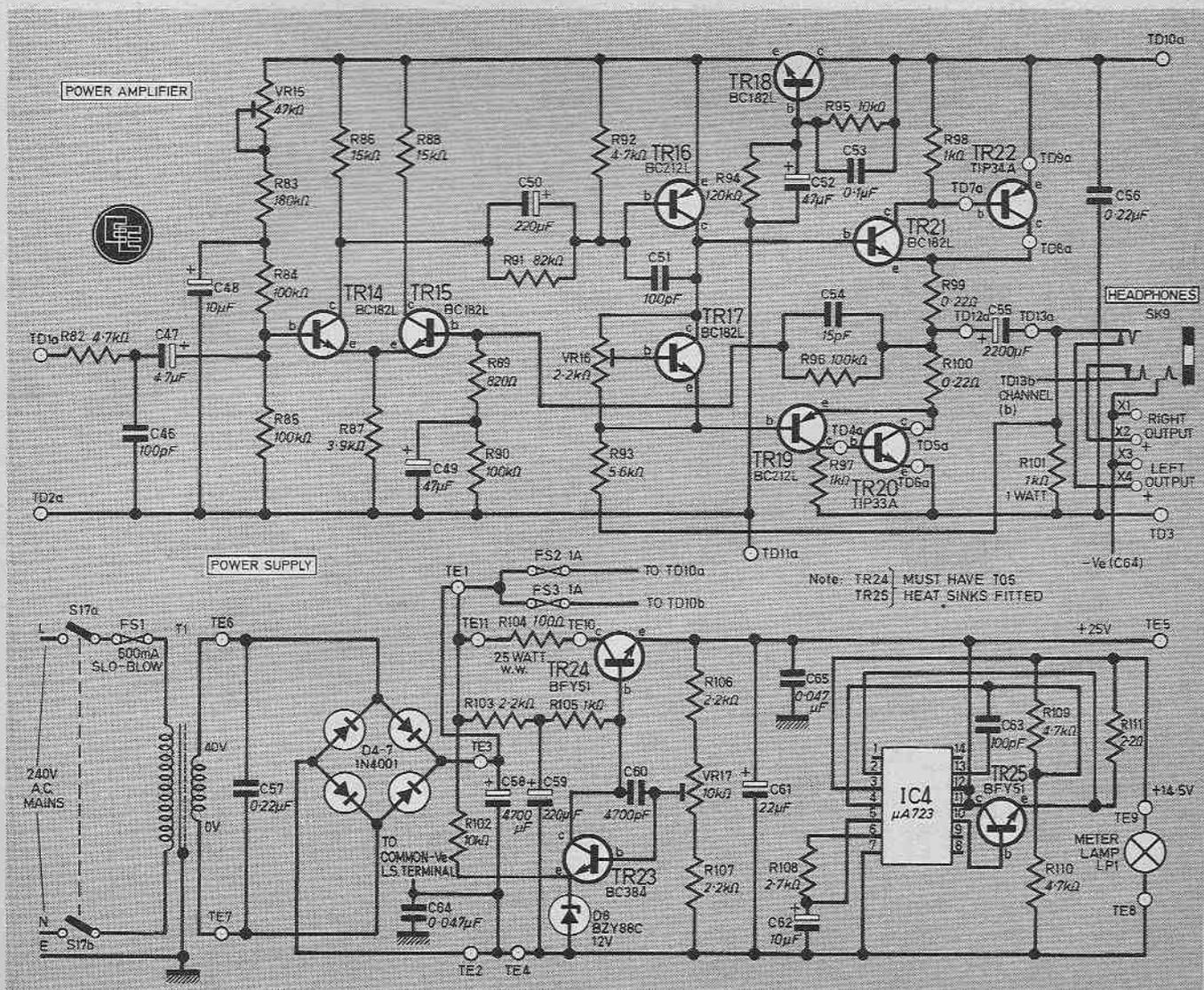


Fig. 2b. Circuit diagram of the 2020 Tuner Amplifier: Power Amplifier and Power Supply stages.

Board D

POWER AMPLIFIER

The power amplifier section of the 2020 is of a well known Texas Instruments design and was chosen because of its excellent performance and reliability. The circuit forms the top half of Fig. 1.2b.

The input signal from the volume control VR14 is fed in at TD1 and applied via a low pass filter comprising R82, C46, which helps prevent radio frequency interference (r.f.i.) and also helps prevent transient inter-modulation distortion.

The input stage consists of a long-tailed pair TR14, TR15. This arrangement offers the following advantages: (a) Excellent temperature stability on the d.c. level of the output mid-point voltage, since any changes in the base emitter voltage of transistor TR14 due to temperature changes will be cancelled by a similar change in the base emitter voltage of transistor TR15. Also since resistors of similar value are used in the input and feedback paths connected to the bases of the two transistors, any changes in base current requirements of the transistors due to temperature changes produce almost equal off-sets on the two sides of the circuit and prevent any drift of the output mid-point.

(b) A high impedance input to both sides of the long-tailed pair allows a smaller value capacitor to be used to decouple the negative feedback circuit. Transistor TR18 is an addition to the original Texas circuit. This provides electronic smoothing of the supply line to the early stages and reduces supply line ripple to a neg-

ligible level. It also reduces "switch on" thump as the output voltage from TR18 is only able to increase slowly due to C52 having to charge up, which in turn causes a slow build-up of the mid-point voltage.

Preset VR15 sets the current through the input transistor which in turn sets the mid voltage point of the output transistors. VR16 adjusts the quiescent current.

Both d.c. and a.c. negative feedback is applied to the base of TR15. The action of the circuit is that the d.c. level of the output mid-point changes until the base voltages of the transistors TR14 and TR15 are equal. If the mid-point voltage tends to rise (say) then the base voltage of TR15 will also tend to rise, this will increase its collector current and hence decrease the collector current of TR14. This reduces the collector current of TR16 reducing the voltage drop across R93 and corrects the tendency of the mid-point voltage to rise.

The a.c. feedback applied to the base of TR15 takes the same path as the d.c. feedback, but in this case C49 in effect shorts out R90. The total amount of a.c. feedback is approximately 40dB. As the input long-tailed pair is a subtractive arrangement the feedback signal can be said to be subtracted from the input signal.

A full description of the power amplifier circuit is given in the Texas Instruments book "High Fidelity Audio Amplifier Circuits".

Board E

POWER SUPPLY

The power supply section is shown in the lower half of Fig. 1.2b.

A toroidal type of mains trans-

former is used; this has advantages of the virtual absence of an external magnetic field as well as a low physical profile. The two 0-20V secondaries of T1 are connected in series to provide 0-40V. This feeds a full-wave bridge rectifier D4-D7. The d.c. output from the reservoir capacitor C58 is fed to the power amplifier via fuses FS2 and FS3. Output from C58 also goes to stabiliser circuit TR23, TR24.

A series pass transistor TR24 is used as an emitter follower to provide the stabilised supply. The emitter of TR24 is held at 25V by the action of the regulator transistor TR23. The preset potentiometer VR17 controls the current through TR23 which in turn adjusts the voltage on its collector to the required 25 volts. Any variation in output voltage is fed back via VR17 to the base of TR23 and the negative feedback action will correct and maintain the voltage to that set by VR17. The 25V stabilised supply is taken from the emitter of TR24 to TE5.

To ensure that the voltage to the varicaps is stable enough for varicap tuning a μ A723 voltage regulator IC4 is used to provide the required 14.5 volts. Input to the voltage regulator IC4 is from the 25V stabilised line. The 14.5V regulated output is fed via an emitter follower TR25 to TE9. This double stabilising ensures complete freedom from drift due to mains or supply voltage fluctuations.

The 14.5V line also supplies the pick-up pre-amplifier, the double stabilising ensuring complete decoupling from the power amplifier supply rail and preventing hum and noise entering the pre-amplifier.

To be continued

BRIGHT IDEAS

SLEEVING

Those little sticks with cotton wool on each end are these days most useful for the electronics enthusiast. When mother has finished doing incredible things to baby with "Q Tips" or "Cotton Buds", to name a couple of brand names, salvage them, cut the ends away, and presto, 60 to 70 mm of stiff sleeving—for free.

Even some ice lollies have plastic tubular sticks, so through the summer you can also keep plenty of sleeving in stock whatever the weather—you can ignore the flavours and choose the colour stick that suits your current project!

And don't forget your own electronics bench—Ersin Multicore solder size 5 dispenser has 80mm of transparent plastic tubing inside.

K. Croft,
Broadstairs,
Kent.


PLUG CONVERSION

I have devised a very simple method of using a 2.5mm earpiece with a 3.5mm socket, thus solving a very old problem.

Take a 3.5mm plug and remove the barrel, cut the connectors to a length of 3mm. Now take a 2.5mm socket, cut off the part shown and solder two thin wires to the contacts. Now screw the socket into the barrel, and solder the wires to the plug contacts.

Finally screw the barrel onto the plug. It is important to ensure the connecting wires are long enough to allow for the twisting they will experience when the barrel is screwed on.

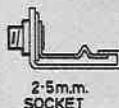
A. R. Jones,
Loughborough,
Leicestershire.



SOCKET MOUNTED IN 3.5mm. JACK PLUG



Electronics. Make a job of it....

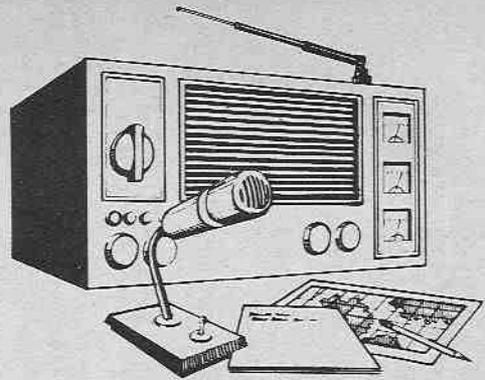

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

EEL12/78

Block caps please

Get kitted out for winter.

Heathkit electronics kits are perfect for the winter evenings. There are hundreds of things you can make yourself, with easy-to-follow instructions to guide you.

There are kits for the home or car, and there's a whole range of computers and peripherals too.

And for a thorough and practical understanding of the principles of electronics, there's a complete range of educational courses and experimenter-trainers.

Full details are in the Heathkit catalogues. Send the coupon now.

**10% OFF
SELECTED
ITEMS**
until 15th December
1978.



FREE
Soldering iron worth \$4.50. Full details when you send the coupon.

There are Heathkit Electronics Centres at 257 Tottenham Court Road, London (01-850 7548) and at Bristol Road, Gloucester (Gloucester 29461).




Digital weather computer.



Electronic air cleaner.



Digital car clock.

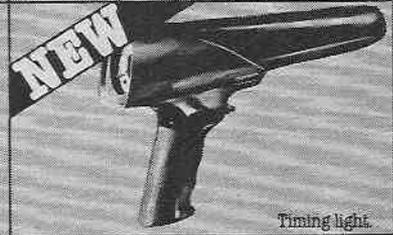

Timing light.

To: Heath (Gloucester) Ltd., Dept. _____, Bristol Road, Gloucester, GL2 6EE.
Please tick the literature you want and include the appropriate amount in postage stamps. Heathkit Catalogue only (enclose 20p). 16 page Computer Brochure only (enclose 20p).

Name _____

Address _____

HEATH
Schlumberger



Registered in England, number 6146177.

EE12/78

Audible Flasher

By B. N. Ryerson

IN MANY cars on the roads there is no indication, save just a bulb, to alert the driver that his indicators are working correctly. This simple add-on unit to be described here does just that by emitting a loud click with each flash of the indicators.

CIRCUIT DESCRIPTION

The unit is simplicity itself in operation, and the circuit diagram is shown in Fig. 1. Each time the warning lamp receives a pulse from the flasher unit, part of it is passed to C1. This capacitor

charges up, in doing so it will produce a loud click in the speaker.

In the interval between pulses the capacitor is discharged through R1, ready to charge up again on the next pulse.

CONSTRUCTION

As there are few components, point to point wiring is used. First of all decide where to mount the speaker. A position somewhere behind the dashboard is suitable, and it can be mounted with glue, or metal brackets. The capacitor and resistor are both mounted on the speaker in some convenient position and glued in place. The diagram of Fig. 2 shows the components opened out for clarity.

Leads long enough to reach the flasher unit and a convenient point on the car chassis are connected as shown.

Some experimenting may be required to find suitable values for the capacitor and resistor to give

COMPONENTS

Resistor

R1 220Ω ¼W ± 10%

Capacitor

C1 470µF 16V elect.

Miscellaneous

LS1 8 ohm 50mm speaker
Connecting wire.

See
**Shop
Talk** page 857

a reasonably loud click, and so as not to load the flasher unit. The values given should prove suitable in most cases.

The unit has been installed in the author's car for some time now and does its job effectively. It is always audible and the click is less offensive than some electronic whine. ✧

COMPONENTS
approximate
cost **£1.20**

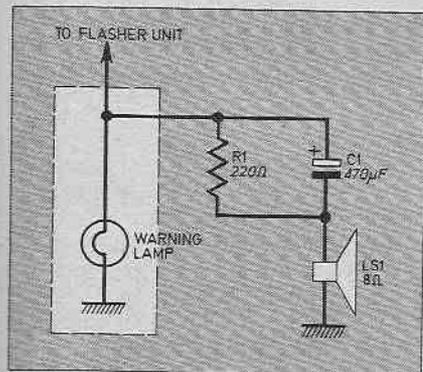


Fig. 1. Circuit diagram of the unit. The wiring shown inside the dotted box is the existing car wiring.

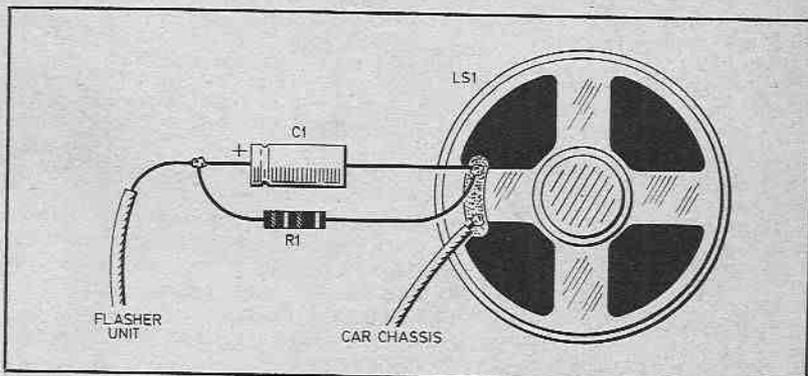


Fig. 2. Wiring details. The speaker can be mounted in any convenient position behind the dashboard. All wiring is point to point using stranded connecting wire. For positive earth systems, reverse the polarity of C1.

COUNTER INTELLIGENCE

By PAUL YOUNG



MOST of us scribbling chaps are fascinated by etymology, and when a few months ago I was asked by the Editor of *The Educationalist*, if I would write a series of articles on "Learning Electronics" the first thing I did was to find out exactly what the word meant. I quote "Electronics is a branch of Electrical Engineering dealing with the theory, design and application of apparatus based on the flow of electrons outside ordinary conductors in which Ohm's laws is valid".

Fifteen years ago that was an apt description, but the term is now used so widely that it would appear, that, "The tail is wagging the dog" and it would not surprise me, if future scholars reverse this definition and say "That Electrical Engineering is a branch of Electronics".

Setting a New Course

I was delighted to read in the *Sunday Times* recently, that if the appropriate

examining board approves there will be a new O-level course in electronics tried out in schools this year. I quote "The experiment reflects growing concern that schools are failing to prepare children for a world in which electronics will dominate part of their lives".

It appears that of the 40,000 children in London who took C.S.E. only 461 took a paper in electronics which is just over 1 per cent. One lecturer said that in his opinion children should be given plenty of electronic projects to build as an aid to their learning. He can say that again, and I would add also, make EVERYDAY ELECTRONICS compulsory reading.

In The Bag

One sees a lot of amusing things happen if they stand behind a counter all day. Normally it is my staff who man the front line, but occasionally

on a busy day I get pressed into service.

I remember several years ago when we had one of those Mullard Valve Testers and on a Saturday it was quite usual to have a line of customers each with a bag full of valves to be tested. The explanation was simple enough. The night before the television had broken down. So next day off would come the back, out would come all the valves and they would come to us to help find the culprit.

We had to get rid of it in the end as it was too time consuming. So their next ploy was to make a list of all the valves in the set (any number up to 20) come in and buy a complete new set. They would then go home and find the trouble by a process of elimination, come back on Monday morning with nineteen valves and expect you to take them back and refund their money! No wonder some of us wound up on the analyst's couch! Needless to say we soon squashed that one too!

Even so I still find it hard to keep a straight face when someone comes in with a small paper bag and tips the contents out on the counter and says "Have you anything like that?" "That" usually being something that was originally a half-watt resistor, charred to a cinder and in about four pieces.

Being a whimsical chap, I would dearly love to have some burnt and broken resistors, so I could whip one out, present it to the customer, while saying "Yes certainly Sir, here you are!"

EE CROSSWORD No 10

BY D.P. NEWTON

CLUES ACROSS

- 1 Storm fear is potentially a changer (Anag.)
- 5 A tiny morsel
- 6 Sin without the nineteenth letter
- 7 His physical laws are very forceful
- 9 Way beyond the usual vibration rate
- 10 Senior citizen
- 12 Better than half-wave rectification
- 13 A reverse rail which tells untruths
- 15 A.C. waveform left its autograph
- 17 To use up
- 18 Half an insulator
- 20 Repaired
- 21 The head blanked out the tape
- 24 A mite out of a transistor
- 25 Electrical snakes?
- 28 Less and yet more than none
- 29 The males are in the omen
- 31 Wet, short-life oscillations
- 32 A wizard in every dozen
- 33 Once a radio call of extreme distress


- 34 Oscillations which are not quite with it in a rectangular sort of way

CLUES DOWN

- 1 Devices for inducing electrical resonance
- 2 An expensive punishment from a nife cell (Anag.)
- 3 Not off
- 4 Ohm gives us a short wait (Anag.)
- 5 Reverse the lead for a fair one
- 8 Lathe waste, clipped a bit
- 9 Singularly a transistorised join
- 10 Mismatching might reduce it
- 11 A flattish sort of transistor?
- 14 A mains repair turned down?
- 16 Crack the signal
- 18 Two speakers who sound things out in depth
- 19 A handy unit
- 22 Mighty small
- 23 One-track mind devices
- 26 Some can't make them meet

- 27 Dad's old cutting tool?
- 32 A NOR gate does not give us the option

Solution on page 886

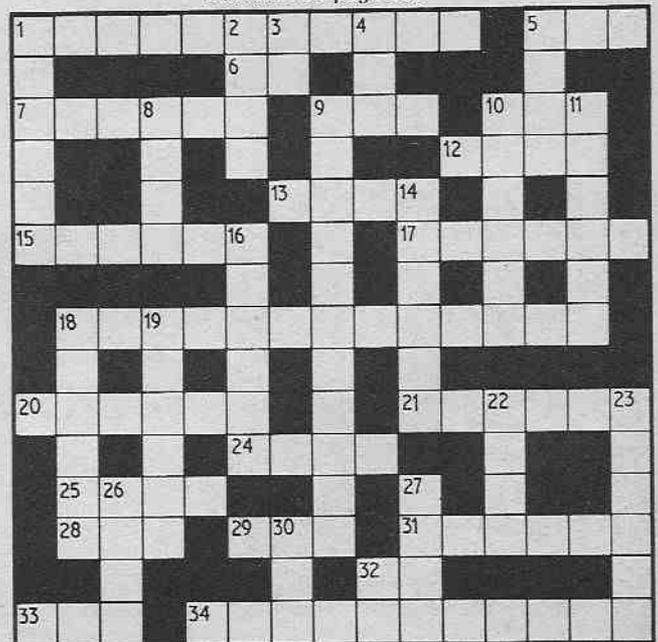

FAST AND EASY FAST AND EASY

FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY

Complete the Circuit at Breadboard '78

Lektrokit have made sure that, no matter how often you go round the exhibits at Breadboard '78, you'll keep coming back to Stands D8 and D9. "Completing the circuit" every time.

Because Lektrokit—as only Lektrokit could—have combined their vast array of components with those of AP Products Inc to bring you the most comprehensive

range of breadboarding and testing devices on earth.

Nowhere else at Breadboard '78 will you see everything you're likely to need all in one place, all in one go, and at the right price.

If you can't get to Breadboard '78 contact us for more details and the name of your nearest Lektrokit dealer and take a look at how much you can get for how little.


Lektrokit Breadboards

FROM £3.25, inc p & p and VAT

Hole for hole, top value! Lektrokit Breadboards are modular, so they can be linked together to form any size. With a pitch of 0.1", even the smallest breadboard—217L—can accept 8, 14, 16 or 18 pin DIL devices. You just take a component, choose a hole, and push it in.

Model No.	Contacts	Price, each
217L	170	£3.25
234L	340	£5.75
248L	480	£6.65
264R	512	£6.65
264L	640	£8.32

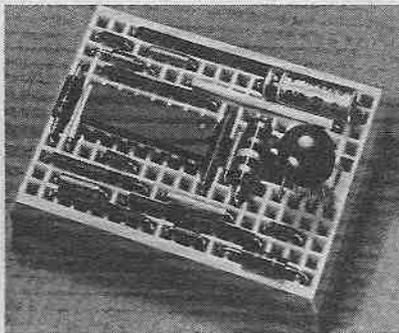(All prices include packing, postage and VAT)




Lektrokit IC Test Clips

FROM £3.08 inc p & p and VAT

Eleven models, from TC-8 to TC-40 to fit all DIP sizes. Prices from £3.08 for the TC-14, £3.25 for the TC-16, etc.

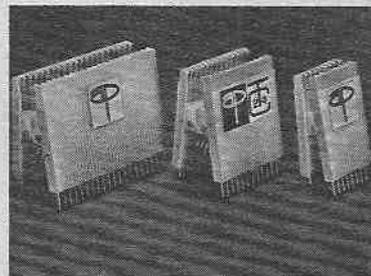Test clip grips IC's without slipping or shorting between pins—makes testing IC's on boards easier, aids removing and inserting DIP's without damage. Each IC pin can be brought up to a convenient contact post for test leads or probe connections.




Lektrokit Super Strip SS2

ONLY £11.05 inc p & p and VAT

Super Strip accepts ALL DIP's—as many as nine 14-pin at a time—and/or TO-5's and discrete components. With interconnections of any solid wire up to 20 AWG.

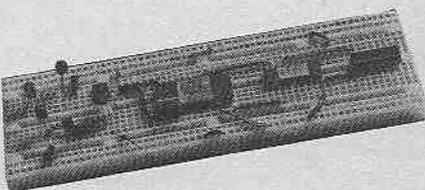Super Strip has 840 contact points, combining a power/signal distribution system with a matrix of 640 contacts in groups of 5. Distribution system has eight bus-bars, each with 25 contact points.



Lektrokit All-Circuit Evaluator FROM £12.53 inc p & p and VAT

"ACE" in the hole for home constructors and project builders who do things faster and easier! No laying out circuit diagrams, printed circuit boards, soldering everything together, trouble-shooting, making mods, then chucking it and starting the whole time-consuming business all over again!

With ACE, you just plug in components and make connections with ordinary 22-gauge solid wire. No soldering. You can build any working project complete, as fast as you could lay out a circuit diagram before.


Seven ACE models altogether—with from 728 to 3,648 contacts. IC capacity (all 14-pin DIP's) from 9 to 36. Buses from 2 to 36. Posts from 2 to 4. Prices from £12.53 including packing and postage and VAT.

Lektrokit's policy is the right product, whatever the project, at the right price. And it's backed by a nationwide network of retailers.

Send for the name of the dealer nearest you—plus a FREE full-colour catalogue.

And, if you can, see and try out the great Lektrokit range at Breadboard '78—from Nov. 21 to Nov. 25 at Seymour Hall, Seymour Place, London.

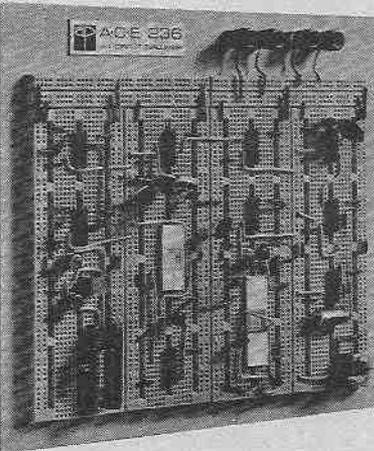Write to:—LEKTROKIT LTD., London Road, Reading, Berks. RG6 1AZ. Or send coupon.



To Lektrokit Limited, London Road, Reading, Berks, RG6 1AZ. Tel. Reading (0734) 669116/7. Please send me the name of my nearest Lektrokit dealer—plus FREE catalogue. Please supply the following (list items required)

..... I enclose P.O./cheque for £.....
(Allow 28 days for delivery. All prices above include packing, postage and VAT).

Name

Address

E.E. 2.

LEKTROKIT

COMPLETES THE CIRCUIT

SEE LEKTROKIT ON STANDS D8 AND D9 AT BREADBOARD '78!

15-240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag. cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; input impedance 4-7k Ω at 1kHz.


OUTPUTS: Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0-1% at 1kHz. Signal/Noise Ratio 68dB.

OVERLOAD: 30dB on Magnetic Pick-up. **SUPPLY VOLTAGE** \pm 16-50V.

Price £6.27 + 78p VAT P&P free.

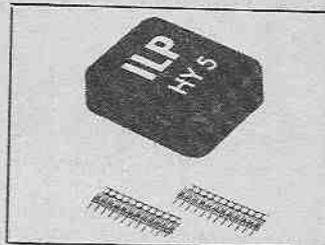

HY30

15 Watts
into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω ; **DISTORTION** 0-1% at 1-5W.

INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

SUPPLY VOLTAGE \pm 12V.

Price £8.27 + 78p VAT P&P free.



HY50

25 Watts
into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust high Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components.

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


SPECIFICATIONS: **INPUT SENSITIVITY** 500mV

OUTPUT POWER 25W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-04% at 25W

at 1kHz **SIGNAL/NOISE RATIO** 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

SUPPLY VOLTAGE \pm 25V **SIZE** 105 50 25mm

Price £8.18 + £1.02 VAT P&P free

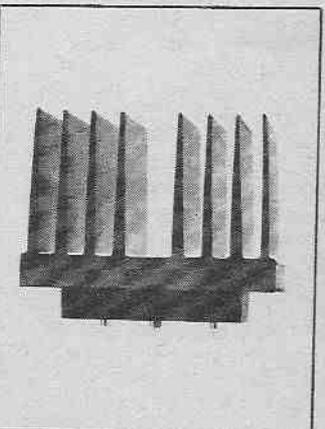

HY120

60 Watts
into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS

INPUT SENSITIVITY 500mV.


OUTPUT POWER 60W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-04% at 60W

at 1kHz **SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 35V

SIZE 114 50 85mm

Price £19.01 + £1.52 VAT P&P free.

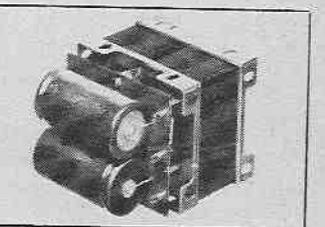

HY200

120 Watts
into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-05% at 100W

at 1kHz **SIGNAL/NOISE RATIO** 96dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 45V

SIZE 114 50 85mm

Price £27.99 + £2.24 VAT P&P free.

HY400

240 Watts
into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS

OUTPUT POWER 240W RMS into 4 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-1% at 240W

at 1kHz **SIGNAL NOISE RATIO** 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 45V

INPUT SENSITIVITY 500mV **SIZE** 114 100 85mm

Price £38.61 + £3.09 VAT P&P free.

POWER SUPPLIES

PSU36 suitable for two HY30's £6.44 plus 81p VAT. P/P free.
PSU50 suitable for two HY50's £8.18 plus £1.02 VAT. P/P free.
PSU70 suitable for two HY120's £14.58 plus £1.17 VAT. P/P free.
PSU90 suitable for one HY200 £15.19 plus £1.21 VAT. P/P free.
PSU180 £25.42 + £2.03 VAT.
B1 £0.48 + £0.06 VAT.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., GROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.

I.L.P. ELECTRONICS LTD.,

GROSSLAND HOUSE, NACKINGTON,
CANTERBURY, KENT, CT4 7AD.

Tel: (0227) 64723.

Regd No. 1032630.

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name and Address _____
Signature _____

MAINS TRANSFORMERS

All these have 230/240V 50Hz

All these have 230/240V 50Hz Primary

Voltage	Our Ref.	Price	Post
1v	2 amp TM 1	£1.94	40p
2-4v	5 amp TM 2	£1.62	45p
4v	7 amp TM 32	£2.70	60p
6v	3 amp TM 3	85p	40p
6-5v	3 amp TM37	85p	40p
6-5v	200 mA TM 21	£1.78	40p
6-5v-0-6-5v	100 mA TM 21	£1.62	40p
6-5v-0-6-5v	750 mA TM 7	£2.16	45p
6-3v-0-6-3v	100 mA TM 33	£1.62	40p
6-3v	2 amp TM 4	£1.89	50p
8-5v	1 amp TM 12	£1.62	40p
8-5v	1 amp TM 12	£1.62	40p
8-5v+8-5v sep. winding	1 amp TM 5	£1.62	45p
9v	3 1/2 amp TM11	£2.70	50p
9v	5 amp TM 38	£3.24	60p
10v	25 amp TM 15	£4.86	£1.25
10v-0-10v	4 amp TM 50	£3.78	£1.25
10v-0-10v	12 1/2 amp TM 15	£4.86	£1.25
12v	3 amp TM 9	£1.05	50p
12v	100 mA TM 21	£1.62	40p
13v	1 amp TM 7	£2.16	50p
12v	1 amp TM 10	£1.89	50p
12v-0-12v	50 mA TM 19	£3.24	50p
12v-0-12v	1 amp TM 41	£2.70	50p
15v tapped 9v	2 amp TM 11	£2.70	50p
17v	1 amp TM 12	£1.62	50p
18v	1 amp TM 13	£1.90	50p
20v	1 amp TM 14	£1.62	50p
20v (with 6 1/2 amp)	2 amp TM 20	£3.24	£1.25
20v	6 amp TM 46	£4.32	£1.25
20v	12 1/2 amp TM 15	£4.86	£1.25
20v-0-20v	8 amp TM 15	£4.86	£1.25
24v	1 1/2 amp TM 16	£2.12	60p
24v	2 amp TM 17	£2.70	60p
24v+2v 7 amp	2 amp TM 39	£2.97	70p
24v	4 amp TM 40	£3.78	80p
25v	1 1/2 amp TM 18	£2.43	60p
26v	2 amp TM 39	£2.98	60p
30v	8 amp TM 15	£4.86	£1.25
37v	37 amp TM 34	£31.86	enquire
40v	3 amp TM 48	£4.32	£1.25
40v	5 amp TM 48	£5.02	£1.25
40v	6 amp TM 15	£4.86	£1.25
40v-0-40v	2 1/2 amp TM 48	£5.02	£1.25
50v & 6-3v	2 amp TM 22	£4.86	£1.25
50v	8 amp TM 29	£11.85	£1.25
50v	2 amp TM 46	£4.32	£1.25
50v tapped 40v & 20v	4 1/2 amp TM 24	£7.02	£2.50
70v	3 amp TM 33	£8.10	£2.00
75v and 63v	4 1/2 amp TM 24	£7.02	£2.50
75v	4 amp TM 24	£7.02	£2.50
80v tapped 70v & 75v	2 1/2 amp TM 48	£5.02	£1.25
80v centre tapped	1 amp TM 25	£7.02	£1.75
100v	1 1/2 amp TM 25	£7.02	£1.75
100v-0-100v	1 amp TM 25	£7.02	£1.75
200v	1 amp TM 25	£7.02	£1.75
250v-0-250v & 6-3v	50 mA TM 36	£3.78	£1.00
000v	100 mA TM 36	£3.78	£1.00
500v	50 mA TM 36	£3.78	£1.00
260v	60 mA TM 26	£3.24	£1.00
1000v	60 mA TM 43	£6.50	£2.00
4 kv	5 mA TM 49	£4.05	70p
5 kv	5 mA TM 30	£7.02	£1.00
8 kv	5 mA TM 45	£4.05	£1.00
8-5 kv	10 mA TM 31	£4.26	£2.00

Full range of Mains to 120v. All transformers available.
Pot Cores. We have now received our delivery of Ferro pot cores. These are ex unused equipment. They contain the bobbins but of course these have to be wound and you would have to unwind. Three pairs available.

Diameter	Thickness	Price
FX 2243	4.5 cm	31
FX 2242	3.5 cm	70
FX 2240	3.5 cm	60

per pair

Quantity discounts apply.
Component Panel Ref. 3055. Taken from unused P.S.U.'s, these contain 4 x 2N 3055 power transistors with mica insulators all on heat sink and 4 variable pots, preset type with spindle locks. Real bargain at £1.08 each.

Component Board 421. Again from unused equipment, major items on these are two power silicon transistors, Motor Rola ref. SJ 5433 mounted on a heat sink with mica insulators, also behind the panel are two power rectifiers ST NS 1008. Price 96p.

E.H.T. Mains Transformer. With inductance control, normal primary and output voltage approx. 4kv 3mA. Voltage can be varied by applying DC to lower bobbin. Unused, ex P.S.U.'s. Price £4.32.

Music Centre Dust Cover. Size 12" x 10" x 1 1/2" with attachments for hinging. Price £3.95. Callers only.


Telephone Answering Machines. Used, but apparently complete and probably in working order. However, they should be very suitable for conversion to open reel tape recorder, background music machine, echo chamber, etc. All untested but we guarantee to replace any major item in the machine should it be faulty. Machines less outer case £1.50, case slightly broken but substantially whole £10.25. Unbroken cases £12.45, and finally with new looking cases £14.50. Post £2.50 per machine. Many accessories available for these machines. Please enquire.

Wall Mounting Thermostat. The Satchwell room stat. Mains 20 amp settable over normal air temperatures between 20-80°F. Suitable also for greenhouse control. Nicely finished in white enamel. Price £3.25.

10 r.p.m. Motor with 230v mains coil, not like the usual of these geared motors this has a good length of 1" shaft. Price £2.50 + 20p.

Rigonda Intermexzo 10 + 10 hi-fi amplifier with belt driven record deck with speed control and probe check. The best hi-fi offered by Rigonda original selling price was in excess of £125. We have approx. 50 of these unused but with various faults. Untested, believed complete except for cartridge and speakers. Offered at £33.50, less than the price of the very high quality deck incorporated. It cannot collect add £3.00 to cover the special packing and carriage charge.

MINI-MULTI TESTER

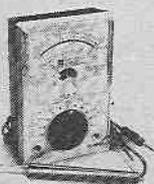

Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—1000 opy—mirrored scale.
 11 instant ranges measure—
 DC volts 10, 50, 250, 1000,
 AC volts 10, 50, 150, 1000.
 DC amps 0-1 mA and 0-100 mA
 Continuity and resistance 0-150K ohms.
 Complete with insulated probes, leads, battery, circuit diagram and instructions.
 Unbelievable value only £6.50 + 50p post and insurance.

MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of Pleassey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.




42 HOUR TIMERS

As illustrated with sun correction made for G.P.O. phone boxes used perfect £2.95 20 amp switching contacts.

SHORTWAVE CRYSTAL SET

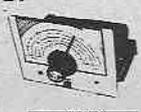Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1.94—crystal earphone 55p including VAT and postage.



SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £9.95.



BREAKDOWN PARCEL

Four unused, made for computer units containing most useful components, and these components unlike those from most computer panels, have wire ends of usable length. The transistors for instance have leads over 1" long—the diodes have approx. 3/4" leads.

List of the major components is as follows—17 assorted transistors—38 assorted diodes—60 assorted resistors and condensers—4 gold plated plugs in units which can serve as multi-pin plugs or as hook up boards for experimental or quickly changed circuits (note we can supply the socket boards which we made to receive these units). The price of this four unit parcel is £1 including VAT and post (considerably less than value of the transistors or diodes alone). DON'T MISS THIS SPLENDID OFFER.


TANGENTIAL HEATER UNIT

A most efficient and quiet running blower-heater by Solatron—same type as is fitted to many famous name heaters—Comprises mains induction motor—long turbo fan—split 2 kw heating element and thermostatic safety trip—simply connect to the mains for immediate heat—mount in a simple wooden or metal case or mount direct onto base of say kitchen unit—Price £4.95 post £1.50 control switch to give 2kw, 1kw, cold blow or off available 60p extra.

2 kw. model made in metal case with control switch £12.00


MOTORISED DISCO SWITCH

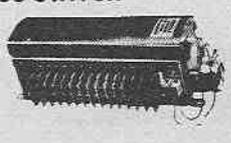With 10 amp change-over switches. Multi adjustable switches are rated at 10 amps. This would provide a magnificent display. For mains operating, 8 switch model £5.25, 12 switch model £5.75, 12 switch model £6.75.



FLUORESCENT TUBE INVERTOR

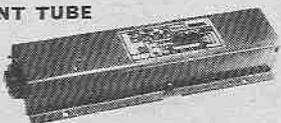For camping — car repairing — emergency lighting. It will offer plenty of well distributed light and is economical. We offer inverter for 21" 13 watt miniature tube for only £3.75 with tube and tube holders as well.



RELAYS

12 volt 20 amp changeover plug in 95p.
 12v three 10 amp changeover plug in £1.25.
 12v two changeover miniature wire ended 95p.
 12 volt open single screw fixing two 10 amp changeovers 85p.
 12 volt open three 10 amp changeovers £1.25.
 Latching relay mains operated 2 c/o contacts £2.11.
 Mains operated three 10 amp changeovers open type one screw fixing £1.25.
 Many other types with different coil voltages and contact arrangements are in stock, enquiries invited.



Terms: Prices include Post & VAT. But orders under £6.00 please add 50p to offset packing. Bulk enquiries—Please Phone for Generous Discounts 688 1833.

J. BULL (ELECTRICAL) LTD
 (Dept. E. E.), 103 TAMWORTH RD.,
 CROYDON CR8 1SG

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free! Send S.A.E. Below are a few of the Bargains still available from previous lines.

Pot Cores. These are ex-unused equipment. They contain the bobbins. Three sizes available.

FX	Diameter	Thickness	Price
FX 2243	4.5 cm	31	
FX 2242	3.5 cm	70	per pair
FX 2240	3.5 cm	60	

Quantity Discounts apply.

Component Panel Ref. 3055. Taken from unused P.S.U.'s, these contain 4 x 2N 3055 power transistors with mica insulators all on heat sink and 4 x 3W type variable pots, preset type with spindle locks. Real bargain at £1.08.

Component Board 421. Again from unused equipment, major items on these are two power silicon transistors, Motor Rola ref. SJ 5433 mounted on a heat sink with mica insulators, also behind the panel are two power rectifiers ST NS 1008. Price 96p.

Heavy Duty 3 Core Appliances Lead. 15 Amp wire 6ft long, conventional yellow green, brown and blue cores, grey pvc coating, prepared and ready for use. Sells at 30p per metre, 10 leads for £2.50 + 20p. Post £1.08. Good quantity available.

E.H.T. Mains Transformer. With inductance control, normal primary and output voltage 3-5kv. The core, however, is made of a very good quality grain oriented transformer steel, and its flux can be varied by applying a DC voltage to the lower bobbin. We are not sure how much the output voltage may be increased or decreased but using a 9 volt battery we seem to get a rise or fall of about 50 volts. These transformers are unused ex-P.S.U.'s which we are breaking down. Price £4.35.

Music Centre Dust Cover. Size 12" x 10 1/2" x 1 1/2" with attachments for hinging. Price £3.95. Callers only.

Hi Fi Console. This is a pleasantly designed shelving arrangement which could tidy up your room, sorry but it's another callers only item but a real bargain at £5.50.

Battery Charger Kit. Soon the dark nights will be with us and chances are your battery will become gradually discharged. Keep it topped up at low cost from the mains. Our kit consists of transformer, full wave rectifier, charging meter and battery clips. Bargain price £4.90.

Electrical Wiring Cables. 2.5mm twin and earth, flat p.v.c. covered grey, 100 metre coils, price £15.00. This is the cable you need for ring main circuits but for lighting a smaller iron cable will do. We can supply this at £8.00.

Power Packs for the Telephone Answering Machines have just arrived, these isolate the machine from the mains and provide the correct voltages for driving the record and playback motors, etc. On metal chassis with voltage selector and fuse, these are a plastic cover to make them safe. Not new of course but fully guaranteed. Price £5.95.

Telephone Answering Machines. We have sold all last month's delivery and the new lot we find rather varied. There are some without cases, some with slightly broken cases and some which look perfect. The description we gave in our last month's newsletter cannot apply to this new lot. So we have restated this as follows—**Telephone Answering Machine**, used, but so far as we can see complete and quite possibly in working order. However, we are allowed to supply these only for breaking up, they should be very suitable for conversion to open reel tape recorder, background music machine, echo chamber, etc. The list of parts contained in the machine are as in our August newsletter (copy on request). They are all untested but we guarantee to replace any major item in the machine should this item be faulty. We are pricing these as follows. Machines less outer case £1.50 with outer case slightly broken but substantially whole £10.50. Machines with unbroken outer cases £12.50 and finally machines with very good, new looking outer cases £14.50. Post £2.00 per machine less case, others £2.50."

Wall Mounting Thermostat. The Satchwell room stat. This will handle mains heaters up to a total of 20 amp and is settable for normal air temperatures between 20-80°F. Suitable also for greenhouse control. Nicely finished in white enamel. Also has a cover to prevent interference with control setting. Price £3.20.

10 r.p.m. Motor with 230v mains coil, not like the usual of these geared motors, this has a good length of 1" shaft price. £3.00 + 20p.

Can Anyone Help US? We are looking for fairly large quantities of the items listed below. If you have any stock yourself or can put us on to a reasonably priced supplier we would be obliged.

7-5 segment displays common anode red or green.
 BZY88CV6 Zener.
 TIL209 red i.e.d.s.
 Soldercon pins.

0-1 inch matrix Veroboard 52 holes x 46 strips.

0-1 inch matrix Veroboard size 34 holes x 34 strips.

CS1300 C Operational amplifier 1C.

MPF102 Transistor.

We are also looking for VDU's, oscilloscopes, computers and most instruments. If you know of any surplus please send details or phone Mr. J. Bull, 01-688 1833.

Charge Discharge inductance meter. This is a heavy panel mounting instrument made originally for the GPO, rather old design but still we feel will fill an urgent need. Basically the operation of this depends upon a Mercury motor which revolves clockwise or anti-clockwise depending upon whether the batteries are charging or discharging, a pointer shows the state of charge of the batteries at any time. Also fitted within the instrument are auxiliary contacts which could be used to set off alarms like lamps, etc. Price £5.95.

Resettable Fuses (thermal trips). Two new types have come in, one made by E.T.A. is a 6 amp model which is mounted through a single hole rather like a fuse, the other is a 10 amp model made by AEG is held by two screws thus a bank of these could be mounted between metal strips. Price 54p.

Disc Motor, mains operated. This is very thin in fact less than 1/2" thick and only approx. 2 1/2" dia. Spindle revolves at 250 rpm and the spindle which is approx. 1/8" dia. pushes through 50 motor coils.

The spindle could be used to drive clockwise or anti-clockwise. The spindle using a friction fit can be pushed completely out and replaced by your own spindle, a knitting needle for instance. Price only 38p.

75 rpm Mains Induction Motor with gearbox. This motor is quite powerful and has 1 1/2" stock and the final 75 rpm drive shaft is 1 1/2" long by 3/8" dia. The motor also has a spindle coming from the opposite end to which could be fitted another pulley. Overall size approx. 3" x 5" x 2 1/2" + spindles. Price £3.35.

24 Hour Motor, beautifully made by Sangamo. This is 200-240v mains driven motor with gearbox together in one housing, size approx. 1 1/2" dia. by 1 1/2" deep. If you are contemplating making a 24 hour switch with a lot of on/off's, then this is obviously the motor. Price £1.99.

BOX IT

By George Hylton

SMALL cabinets for electronic equipment are easily and cheaply made from readily-available materials. They can also be improvised from other containers, such as tobacco tins, or electricians' switch boxes. Of course, if you wish you can purchase one of the many standard plastic and metal cabinets which can be obtained from components stockists. —But it's not the same as building your own!

This article deals with the cheapest home-constructed and improvised cabinets, suitable for the smaller types of equipment, up to the size of a portable radio.

HARDBOARD

The common hardboard is the cheapest do-it-yourself cabinet material, and one of the easiest to work with. It is often obtainable from timber merchants and do-it-yourself shops as "offcuts", with the advantage that quite narrow strips, down to about an inch wide, are still quite useful for small cabinet construction but generally go cheaply in the shops because they are too narrow for most household jobs.

Hardboard has no grain and is easily cut with a wood saw. If kept dry it is an excellent insulator and can be used for circuit boards. (The "outdoor" variety of hardboard, which is waterproofed with an oily substance, is even better.)

GLUING

Small hardboard boxes can be made simply by gluing pieces of hardboard together at the edges (Fig. 1). It is easiest first to cut the top, bottom and end pieces and glue them to form a short open-ended "tube". Front and rear panels can be added later. Alternatively, you can make a "tray" by

starting with the back panel and gluing four sides to it.

Almost any type of adhesive can be used but a good general-purpose type is the so-called "impact" adhesive, available as Evo-Stik Impact Adhesive or Dunlop Thixofix. The instructions on the tube tell you to coat the mating surfaces with the glue then let them dry for about 15 minutes, then press them together, whereupon they stick.

The trouble with this method is that it is difficult to make any adjustments once the surfaces are brought into contact. You may find it easier just to let the surfaces get tacky then bring them together, when they can still be slid over one another. Used this way the glue needs to be left to dry for a few hours but this is advisable anyway.

FINISHES

Hardboard has a rough side and a smooth side, and you can use it "rough side out" or "smooth side out" according to taste. The ordinary non-oiled kind can be tinted with a dye or coloured ink, and the rough side gives a more even colour. The smooth side can be covered with "Fablon" adhesive plastic film which is available in a variety of decorative finishes.

If you want to paint hardboard it will suck up the paint like blotting paper unless you give it a coat of "size" first.

Hardboard is also available with a decorative plastic film bonded to one or both surfaces. Plain finishes are good for front panels, and the lighter colours can be marked with waterproof ink for calibrating controls.

It is often advantageous to use a front panel of a thinner material than hardboard, which can be too thick to accommodate some

switches and potentiometers. Aluminium sheeting and laminates such as Formica are best suited for front panels.

To make the front panel easily removable stick small pieces of square-section wooden beading to the inside of the box to provide pillars to insert screws through the front panel, Fig. 1.

THIN-WALLED BOXES

When the entire box is to be made of Formica or some other thin-walled laminate sheeting this cannot be glued by its own edges because there is just not enough width to the edges to give a strong joint. So use corner braces. These are just bits of square-section beading ("moulding") which costs about 3p per foot (or 10p per metre) from timber merchants.

Quarter-inch (6mm) square beading is suitable for small cabinets and three-eighths inch (9 or 10mm) for larger ones. (Other shapes of beading such as quadrant or half-square may look better but they provide less target area for fixing screws.) A suitable construction is shown in Fig. 2.

CUTTING LAMINATES

The best method of cutting the laminate sheets is with a hacksaw or a tenon saw but the professional way is the score-and-snap method. This is rather like glass-cutting, but a lot easier.

The line of cut is marked with a deep scratch through the decorative surface and the material is then snapped along the score mark.

There is a standard type of scoring knife designed for the job. It is made by fitting a hooked blade, called a Stanley scoring knife blade, to one of the same maker's Type 199 handles. (These are the handles which also accept the ubiquitous trimming knife blades, which are NOT suitable for scoring laminates.)

A deep scratch is made by repeated scoring along the line of cut, which must be straight and must go right across the sheet from one side to the other. The scored sheet is placed on a firm, level surface, with the scored (decorative) side up. The piece to be cut away is then bent upwards along the score mark while the rest of the sheet is pressed down on the level surface. Eventually it breaks, often with a loud crack.

The broken edge may be a bit rough but can be smoothed off with glass paper or a file. Once you have learned the knack (preferably by practising on scrap material) it becomes very quick and easy.

METAL BOXES

The two-ounce square tobacco tin is a godsend to the electronics enthusiast since it is big enough to house many small circuits and to provide screening as well (see our *Mini Module* series).

More clumsy and heavy, but still useful, are the galvanised steel "boxes" used to mount switches in walls. Lids (front panels) can be cut from aluminium sheeting which, like Formica and hardboard, is also obtainable as cheap offcuts.

Metal cabinets are useful for audio circuits where the signals are small, since if earthed they then screen out stray mains voltages which can cause hum. Note that they are of no use for

radio receivers with ferrite rod aerials because they screen out the radio signals as well!

INPUTS AND OUTPUTS

Many cabinets require connections to the outside world. Mains leads should be brought in through holes fitted with rubber grommets to prevent chafing of the insulation. Inside the box the mains flex should be anchored firmly by means of a clamp or clip, preferably insulated. If the cabinet is of metal it should be connected to the Earth lead of a three-core mains cable (usually coloured with green and yellow stripes in the UK).

Where signals are taken into or out of the cabinet and standard plugs and sockets are not available several makeshift types of lead-through connectors can be used. When the panel is metal these lead-throughs must be insulated. Fig. 3 shows a cheap and simple way to do this.

With hardboard panels, pins or screws can be driven straight through. Laminate board is rather too thin to hold pins firmly and in any case holes must be drilled in it to allow the pins to pass. It, too, can be thickened up by sticking strips of hardboard behind it.

Ordinary bolts can also be used as lead-throughs, fixed by a nut on each side of the panel. Earth-tags on the inside make handy soldering points.

FIXING CIRCUIT BOARDS

It is often tempting to use the back of the panel or the bottom of the box as a "breadboard" for mounting components. In many cases, however, it is better to construct the circuit on its own separate board so that it can be removed for servicing or modification. Some method of holding it in place is then needed. Fig. 4 shows two simple but effective arrangements. □

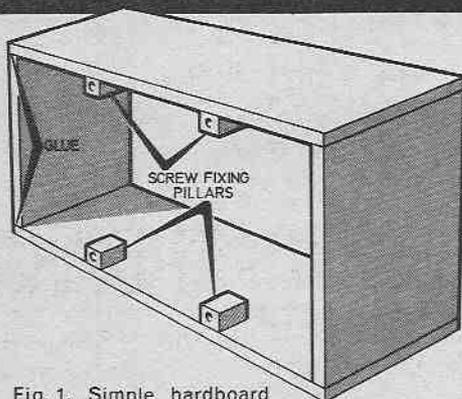


Fig. 1. Simple hardboard box "tube".

Fig. 2. Thin-walled box "tube" with corner braces.

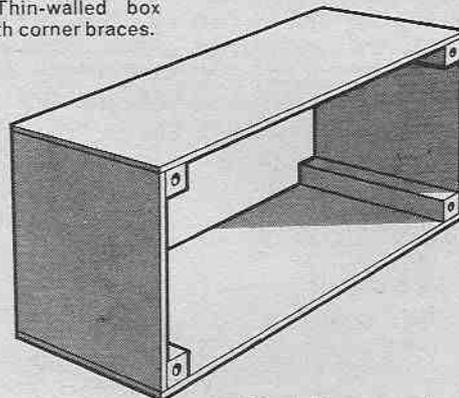


Fig. 4. Two ways of securing circuit boards in the cabinet.



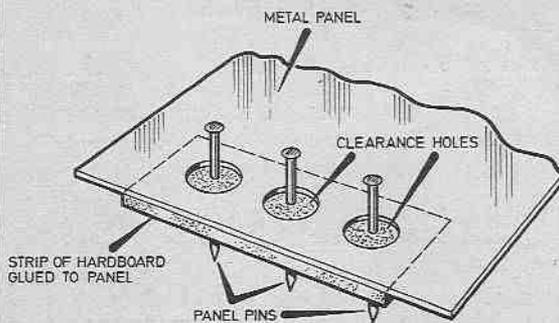


Fig. 3. Method of making feed-through connections on metal panels.

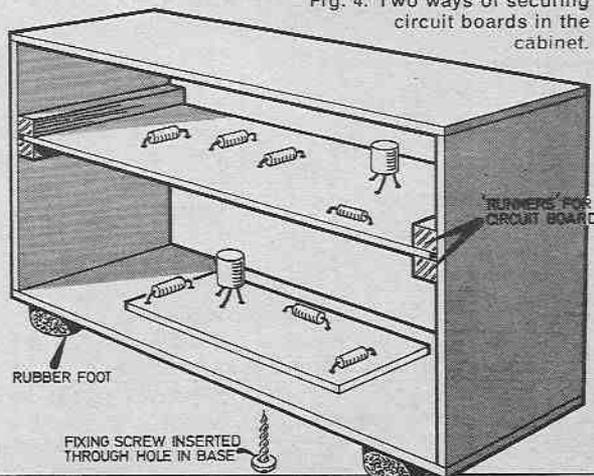

vero

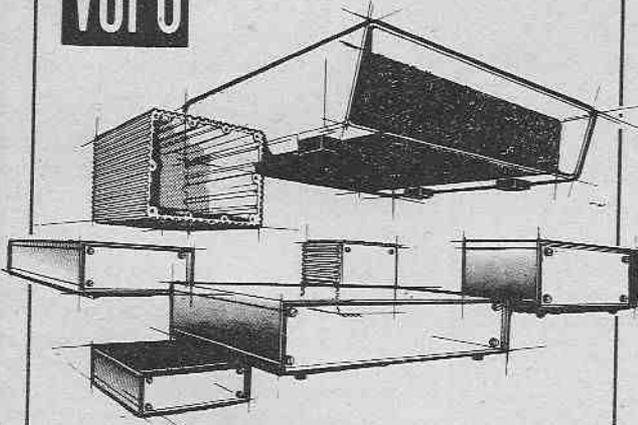

Our new 1978 catalogue lists a whole range of metal cases to house all your projects. And we've got circuit boards, accessories, module systems, and plastic boxes — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VISIT US AT BREADBOARD STAND E6
VERO ELECTRONICS LTD. RETAIL DEPT.
 Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
 Telephone Chandlers Ford (04215) 2956

METAC OFFER

5 FUNCTIONAL LCD

Hours, mins, secs, month, date, auto calendar, back-light, quality metal bracelet.

£8.65

Guaranteed same day despatch
THOUSANDS SOLD
11 FUNCTION SLIM CHRONO

6 digit 11 functions
 * Hours, mins, secs
 * Day, date, day of week
 * 1/100, 1/10, secs.
 * 10 x secs, mins.
 * Split and lap modes.
 * Back light, auto calendar.
 * Only 8mm thick.
 This same watch is being sold for **£22.00** in newspaper and magazine special offer ads.

Metac Price
£12.65

Guaranteed same day despatch



Very slim, only 6mm thick




HANIMEX

Electronic

LED Alarm Clock

Thousands sold

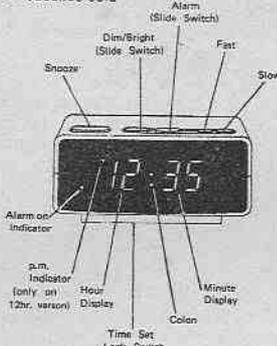

Feature and Specification

- * Hour/minute display.
- * Large LED display with p.m. and alarm on indicator
- * 24 Hours alarm with on-off control
- * Display flashing for power loss indication
- * Repeatable 9-minute snooze
- * Display bright/dim modes control
- Size 5-15 x 3-83 x 2-36 (131mm x 100mm x 80mm).
- Weight: 1.43 lbs (0.65 kg).

Guaranteed same day despatch

£8.65

GUARANTEED SAME DAY DESPATCH

- * All prices include VAT and carry 12 month written guarantee, with our 10 day money back assurance.
- * All watches sent 1st class post.
- * Shops open 9.30-6.00 daily.

Metac Electronics has been selling digital quartz watches probably longer than any other company in the UK. We carry a very wide range of models and our shops stock most watch batteries. Fitting is free and this service is open to all.

PLEASE ADD 30p P & P ALL ORDERS Barclay & Access welcome Phone or Send Card Number

METAC Electronics & Time Centre
 Dept. E



67 HIGH STREET
 DAVENTRY, NORTHANTS
 Tel: (032 72) 76545

327 EDGWARE ROAD
 LONDON W2
 Tel: (01) 723 4753



For a merry musical Christmas an electronic musical door chime which can play 24 different tunes!



A complete
CHROMA-CHIME
Kit for only £15.95
 includes P & P + V.A.T.

Plays:

- Greensleeves
- God Save the Queen
- Rule Britannia*
- Land of Hope and Glory
- Oh Come All Ye Faithful
- Oranges and Lemons
- Westminster Chimes*
- Sailor's Hornpipe
- Beethoven's "Fate Knocking"
- The Marseillaise
- Mozart
- Wedding March

- Cook House Door
- The Stars & Stripes*
- Beethoven's Ode to Joy
- William Tell Overture
- Soldier's Chorus
- Twinkle, Twinkle Little Star
- Great Gate of Kiev
- Maryland
- Deutschland über Alles
- Bach
- Colonel Bogie
- The Lullaby

*These tunes play longer if the push button is kept pressed.

- * *A great introduction to the fascinating world of microcomputers.*
- * *Save pounds on normal retail price by building yourself.*

The CHROMA-CHIME is exclusively designed by

CHROMATRONICS

River Way, Harlow, Essex.

To CHROMATRONICS, River Way, Harlow, Essex, U.K.

Please send Chroma-Chime Kits at £15.95 each including VAT and post and packing

PLEASE USE BLOCK CAPITALS

Name _____

Address _____

EE

I enclose cheque/PO value £ _____
 or debit my ACCESS/BARCLAYCARD account No. _____

Signature _____

N.B. The CHROMA-CHIME is also available, fully assembled, price £24.95 inc VAT and post and packing.

Please allow 7-21 days for delivery.

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200/250V. PRICE \pounds 15.00. P. & P. \pounds 1.20.

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200/250V. PRICE \pounds 15.00. P. & P. \pounds 1.20.

HARVERSONIC MODEL P.A.

TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mv into 47k. Input 2, 15mv into 47k. (suitable for use with mic. or guitar etc.). Input 3 200mv into 1 meg. suitable for gram. tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240V. Size approx. 12 1/2" w. \times 5" h. \times 7 1/2" d. Special introductory Price \pounds 28.00 + \pounds 2.50 carr. & pkg.

Mullard LP1159 RF-IF Module 470 kHz \pounds 2.25 + P. & P. 20p. Full spec. and connection details supplied. Pvc VHF/FM Tuner Head covering 88-108 MHz, 10.7 M/Hz I.F. output. 7-8 Volt \pm earth. Supplied pre-aligned, with full circuit diagram with precision-ganged FM gang and 323Pf - 323Pf A.M. Tuning gang only \pounds 3.15 + P. & P. 35p.

STEREO DECODER

SIZE 2" \times 3" \times 1" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. \pounds 6.00 plus 20p. P. & P. Stereo beacon light if required 40p extra.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp

Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w. \times 4" h. \times 9 1/2" d approx.

LIMITED NUMBER ONLY at \pounds 28.00 + \pounds 1.50 P. & P.

MAINS TRANSFORMER

Pri. 0-110 and 240. Sec. 25v at 1.8 amps. Also tapped at 12v - 3 amp. Overall size 2 1/2" h. \times 3 1/2" w. \times 2 1/2" d. \pounds 2.50 + \pounds 1.00 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. ONLY \pounds 14.50 P. & P. \pounds 1.40. Also available ready built and tested \pounds 19.00 P. & P. \pounds 1.40.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" \times 14 1/2" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only \pounds 8.40 each + P. & P. (one 90p, two \pounds 1.10).

Now available in either 8" round version or 4 1/2" \times 8 1/2" rectangular. 10 watts RMS 60Hz-20KHz \pounds 5.25 + P. & P. (one 65p, two 75p).

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2" \times 2 1/2" \times 5 1/2" H. \pounds 2.60 + 20p P. & P.

2" PLASTIC CONE HF TWEETER 4 ohm, \pounds 3.50 per matched pair + 50p P. & P.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω ; Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v at 1.0 amp. Overall Size 12" w. \times 8" d. \times 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT \pounds 13.50 P. & P. 80p

(Magnetic input components 33p extra)

POWER PACK KIT \pounds 5.50 P. & P. 95p

CABINET \pounds 5.50 P. & P. 95p

SPECIAL OFFER—only \pounds 23.75 if all 3 items ordered at one time plus \pounds 1.25 p. & p.

Also avail. ready built and tested \pounds 31.25. P. & P. \pounds 1.50.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier, smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec. play socket are mounted on the printed circuit panel, size approx. 9 1/2" \times 2 1/2" \times 1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only \pounds 9.00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at \pounds 1.50 + 40p P. & P. if required. Full connection details supplied.

HA34 3 Valve Audio Amp. 4 1/2" w. output ready built and tested \pounds 8.50 + \pounds 1.40 P. & P. Also HSL 'FOUR' amplifier kit. \pounds 8.00 + \pounds 1.40 P. & P.

All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSON SURPLUS CO. LTD.

(Dept. E.E.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.
Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

BUILD A SYNTHESISER!

NO SPECIAL SKILLS REQUIRED
SPECIAL EQUIPMENT



Using **Dewtron** (Reg'd)
PROFESSIONAL MODULES


Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

D.E.W. LTD.

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR

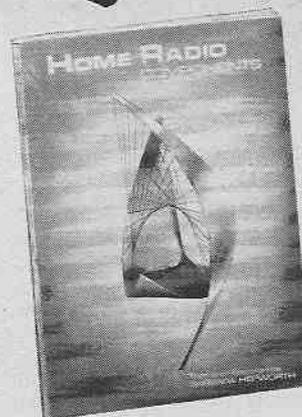THIS is the Catalogue you need to solve your component buying problems!



- The finest components catalogue yet published.
- Over 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Nearly 1,000 illustrations.
- Bargain list sent free.
- At \pounds 1.25 incl. p. & p. the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD., Dept. EE, 234-240 London Road, Mitcham, Surrey CR4 3HD

POST THIS COUPON with cheque or P.O. for \pounds 1.25

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. EE 234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No London 912966)

WORKSHOP MATTERS

By Harry T. Kitchen

The Great 13A Fuse Fallacy

The flat pin 13-amp plug has been the standard British domestic plug for a number of years, and whilst the concept is a laudable one, the realisation of that concept leaves much to be desired. The concept was, of course, that the user of the plug fitted a fuse appropriate to the equipment in use, up to a maximum of 13 amps, and if necessary a fuse having a much lower rupturing value could be fitted, so affording the maximum protection to the equipment being protected.

So much for the concept, but what of the realisation? The realisation was the sale of plugs already fitted with a 13-amp fuse, with no thought of the equipment to be protected, and certainly with no thought of giving advice to the hapless user, who cheerfully fitted the plug onto anything and everything, and thereby, albeit quite innocently, created potential hazards to life limb and property.

Now why should a 13-amp fuse be a hazard?

In order to answer this, we have to ask the question: "what is a fuse and why is it fitted, and where?" The answer is that a fuse is a specially designed weak link placed in series with any circuit to protect that circuit and the user should the current exceed a *specified value*. And this is where the conceptual realisation of the 13-amp plug has so dismally failed, in my opinion, because the equipment may not draw 13 amps, and in many cases will draw significantly smaller currents.

Let us return, momentarily, to the 13-amp plug, and consider its implications. Now we know that the total consumption of any equipment is the wattage, and the wattage in turn is given by multiplying the current drawn by the voltage applied. Conversely, the current drawn can be calculated by dividing the wattage by the voltage, and the voltage can be calculated by dividing the wattage by the current.

The nominal mains voltage in the UK is 240 volts, within a tolerance decided by the CEBG, but the actual tolerance can be greatly influenced by the loading on the "spur" and upon the time of day or evening. For example, I live in the country, and my own mains voltage drops quite significantly when all the neighbourhood ladies, bless 'em, are indulging their culinary prowesses! To continue: 13 amps times 240 volts gives a wattage of 3,120,

and that, if you care to think about it, is a lot of expensive wattages.

How often do you cheerfully consume 3,120 watts? An electric fire, going flat out, will approach this figure, but what else that you have, that is portable, that is not an electric cooker, consumes so much electricity? Precious little I'll warrant. Think about it for a moment, and if necessary do a few simple sums about the electrical or electronic equipment that you use, and when you've done so you will see the utter fallacy of selling 13-amp plugs complete with 13-amp fuses; in my book it ought to be a criminal offence.

Rules of Thumb

There are regulations which, if one cares to study them, and perhaps more important, if one can understand the legalistic jargon, will outline the precise measures to be adopted. Such pedantic accuracy is by no means essential, and a few simple rules of thumb will enable all equipment to be fused such that the maximum of protection can be obtained.

The first rule of thumb is to use a fuse value no larger than is necessary, the value being calculated by dividing the wattage by the voltage.

Here we come up against a practical difficulty, that of obtaining suitably rated fuses; the lowest current rated fuse is the 1-amp fuse, and here we are talking strictly of the 13-amp plug itself. So, perforce, we must use a 1-amp fuse even if the calculated current is significantly lower, and this value will be perfectly safe.

However, mains surges, or equipments having higher current consumptions than calculated, or fuses having a lower rupturing current than marked, may cause the fuse to blow, even though there is no actual fault in the equipment. It is therefore prudent to add a contingency allowance to the *calculated* rating, and a value between 50 per cent and 100 per cent is normal. So if your calculated current is, say, 1 amp, use a fuse of $1\frac{1}{2}$ amps or even 2 amps. But no higher.

An Exception

An exception to the rule involves inductive, capacitive, or tungsten circuits, where for a finite time a current greater, or much greater, than calculated flows, and then reduces to the calculated value.


The surge current for inductive and capacitive circuits will depend on the inductance or capacitance present, but it is interesting to note that, with car bulbs at any rate, the filament resistance when cold is approximately one eleventh the hot or working temperature, and so for a finite time the current is eleven times that calculated. Fortunately, that time is measurable in milliseconds, and one does not have to use fuses uprated by a factor of eleven! A factor of three or four times is adequate for domestic lighting.

Anti-surge Fuses

With inductive or capacitive loads, the only method of fusing that is likely to be effective all round is that of using anti-surge fuses which will withstand an increased load for a finite time, typically ten times rated current for a period of 10 milliseconds to 20 milliseconds. Such fuses will withstand the initial surge of current, but will still blow, usually with time to spare—but not always—so be careful if the current exceeds the nominal value for an appreciable period of time.

Fusing equipment is *essential*, and the above maligned 13-amp plug, which let me repeat is fundamentally sound in concept, may very well prove to be better than nothing at all. But the margin of safety is so much greater when just a little time is taken to work out a few simple maths, and then use the fuses most appropriate to the application.

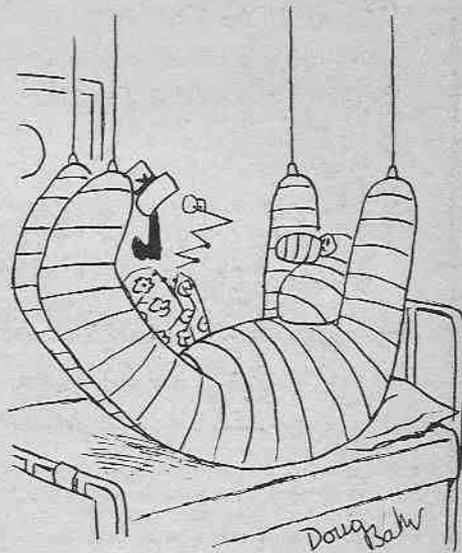Until the authorities see fit to ban the sale of plugs complete with 13-amp fuse and also offer concrete and simple advice on choosing the most appropriate fuse, it is up to the intending user to help himself. Its very simple and well worth while.



"When you come home, will you carry on making your special gadget that minimises the risk of accidents in the home?"

Everyday ELECTRONICS VOLUME 7 INDEX

SEPTEMBER 1977 TO DECEMBER 1978

(Sixteen issues following introduction of larger format)

Pages	Issue	Pages	Issue
1-48	September	417-472	May
49-96	October	473-528	June
97-144	November	529-584	July
145-192	December	585-640	August
193-248	January	641-704	September
249-304	February	705-768	October
305-360	March	769-840	November
361-416	April	841-904	December

CONSTRUCTIONAL FEATURES

A.C. METER CONVERTER by R. A. Penfold	282	ELECTRONICALLY CONTROLLED AIR FRESHENER by D. Warwick	804
ADD-ON CAPACITANCE UNIT by R. A. Penfold	32	EMERGENCY LIGHTING by M. Hughes	170
A.F. SIGNAL GENERATOR by F. G. Rayer	622	ENLARGER TIMER by R. A. Penfold	76
AIR FRESHENER, ELECTRONICALLY CONTROLLED	804	FIND THE PAIR by F. G. Saddler	131
ALARM, CAR SYSTEM	256	FLASHER BLEEPER by T. R. de Vaux-Balbirnie	24
ALARM, ROOF RACK	368	FLASHMETER by R. A. Penfold	424
AUDIBLE FLASHER WARNING by B. N. Ryerson	883	FUSE CHECKER by A. R. Winstanley	721
AUDIBLE/VISUAL METRONOME by M. E. Theaker	200	FUZZ BOX by E. M. Lyndsell	854
AUDIOTEST, THE	312	GENERATOR, A.F. SIGNAL	622
AUTOMATIC PHASE BOX by E. M. Lyndsell	154	GENERATOR, R.F. SIGNAL	668
AUTO NIGHTLIGHT by A. R. Winstanley	536	HAZARD WARNING SYSTEM by T. R. de Vaux-Balbirnie	160
BACK-UP, DYNAMO	14	HOT LINE by P. J. Homer	786
BATTERY STATE INDICATOR by W. B. Jones	654	HUNTER, TREASURE	714
BLEEPER, FLASHER	24	INDICATOR, BATTERY STATE	654
BOOSTER, TONE	648	IN SITU TRANSISTOR TESTER by R. A. Penfold	486
CAPACITANCE UNIT, ADD-ON	32	LEAD TESTER, MONO/STEREO	263
CAR SYSTEM ALARM by P. W. Bond	256	LIGHT, CATCH-A-	332
CATCH-A-LIGHT by R. A. Penfold	332	LIGHT DISPLAY, CHASER	276
CHASER LIGHT DISPLAY by J. McBride	276	LIGHTING, EMERGENCY	170
CHECKER, FUSE	721	LIGHT, SOUND TO	676
CHRONOSTOP by R. W. Coles and B. Cullen	612	LOCK, COMBINATION	798
CODE SCRAMBLER by O. N. Bishop	226	LOGIC PROBE by P. W. Bond	568
CONTINUITY TESTER, PROBELESS	109	LOW COST LOUDSPEAKER ENCLOSURE by J. Smith	288
CONTINUITY TESTER, VISUAL	516	MAINS DELAY SWITCH by A. R. Winstanley	394
CONTROLLER, TRAIN	64	MAINS TESTER by J. C. May	430
COMBINATION LOCK by T. J. Johnson	798	METRONOME, AUDIBLE/VISUAL	200
C-R SUBSTITUTION BOX by P. G. O'Neil	320	MONO/STEREO LEAD TESTER by M. Simpson	263
DIODE CHECK, RAPID	232	M.W. MINI by A. J. Crighton	596
DISPLAY, CHASER LIGHT	276	MW/LW RADIO by R. A. Penfold	740
DYNAMO BACK-UP by R. Everson	14	NIGHTLIGHT, AUTO	536
EE 100W POWER SLAVE by E. M. Lyndsell	504	NINE VOLT D.C. POWER PACK by E. M. Lyndsell	455
EE TELEPLAY STUNT CYCLE by C. Cary	444		
EE 2020 TUNER/AMP by E. A. Rule Part One	872		
EFFECTS GENERATOR, WEIRD SOUND	348		
ELECTRONIC TEST BED, TTL	725		
ELECTRONIC TOUCH SWITCH by R. A. Penfold	204		

CONSTRUCTIONAL FEATURES—continued

PHASE BOX, AUTOMATIC	154	TELE-BELL by F. G. Rayer	480
PHOTOFLASH SLAVE UNIT by R. A. Penfold	181	TELE-TEL by F. G. Rayer	780
POCKET TIMER by O. N. Bishop	402	TESTER, IN SITU TRANSISTOR	486
PORTABLE RADIO, V.H.F.	125	TESTER, MAINS	430
POWER SLAVE, EE 100W	504	TESTER, MONO/STEREO LEAD	263
PROBELESS CONTINUITY TESTER by C. J. Mair	109	TESTER, PROBELESS CONTINUITY	109
PROBE, LOGIC	568	TESTER, TRANSISTOR	84
PROBOPHONE by D. C. Jenkins	8	TESTER, VISUAL CONTINUITY	516
		THE AUDIOTEST by D. W. Easterling	312
QUAGMIRE by O. N. Bishop	556	TIMER, ENLARGER	76
		TIMER, POCKET	402
RADIO, MW/LW	740	TONE BOOSTER by D. S. Gibbs and I. M. Shaw	648
RADIO, SHORT WAVE	542	TOUCH SWITCH, ELECTRONIC	204
RADIO V.H.F. PORTABLE	125	TRAIN CONTROLLER	64
RAPID DIODE CHECK by R. Dudley	232	TRANSISTOR TESTER by D. J. Stephenson	84
REMOTE CONTROL SYSTEM, ULTRASONIC		TREASURE HUNTER by N. Hunter	714
Part One	104	TREASURE LOCATOR by F. G. Rayer	58
Part Two	176	TTL ELECTRONIC TEST BED by O. N. Bishop	725
R.F. SIGNAL GENERATOR by F. G. Rayer	668	TUNER/AMP, EE 2020	872
ROOF RACK ALARM by T. R. de Vaux-Balbirnie	368		
		ULTRASONIC REMOTE CONTROL SYSTEM Part One	104
SHORT WAVE RADIO by F. G. Rayer	542	by R. A. Penfold	Part Two 176
SIGNAL GENERATOR, A.F.	622	VEHICLE IMMOBILISER by G. D. Southern	849
SIGNAL GENERATOR, R.F.	668	V.H.F. PORTABLE RADIO by F. G. Rayer	125
SLAVE FLASH by R. A. Penfold	592	VISUAL CONTINUITY TESTER by A. Sproston	516
SOUND EFFECTS GENERATOR, WEIRD	348		
SOUND TO LIGHT by J. R. W. Barnes	676	WATER LEVEL ALERT by A. R. Winstanley	866
STUNT CYCLE, EE TELEPLAY	444	WEIRD SOUND EFFECTS GENERATOR by D. Edwards	348

GENERAL FEATURES

BOOK REVIEWS	22, 275, 281, 571, 667	C-R Substitution Box March 1978	429
BOX IT	889	EE 100W Power Slave June 1978	546
BRIGHT IDEAS	20, 63, 66, 115, 172, 242, 290, 351, 408, 454, 490, 744, 756, 822, 880	Enlarger Timer October 1977	113
COUNTER INTELLIGENCE by Paul Young	63, 224, 296, 384, 579, 611, 652, 750, 814, 884	Fish Attractor June 1977	44
CROSSWORD by D. P. Newton	343, 384, 429, 484, 547, 611, 667, 747, 814, 884	Fuzztone July 1977	44, 89
EE SPECIAL REPORT		Mains Delay Switch April 1978	429
CRYSTAL SET	753	Mains Tester May 1978	546
ELECTRONIC DOORBELL	292	Physics is Fun November 1977	180
ELECTRONIC MULTIMETER	682	Probophone September 1977	113
ELECTRONIC WORKSHOP	236	Quagmire July 1978	628, 696
WONDERBOARD	820	Soil Moisture Monitor June 1977	44, 89
EDITORIAL	6, 56, 102, 152, 198, 254, 310, 366, 422, 478, 534, 590, 646, 712, 778, 848	Teach-In '78 Part Six March 1978	412
EVERYDAY NEWS	338, 406, 458, 514, 566, 620, 674, 738, 810, 870	Teach-In '78 Part Seven April 1978	429
JACK PLUG AND FAMILY by Doug Baker	39, 81, 130, 224, 296, 351, 412, 454, 495, 575, 610, 693, 750, 803, 863	The Audiotest March 1978	429
PLEASE TAKE NOTE:		Touch Switch July 1977	44
Automatic Phase Box December 1977	412	Treasure Locator October 1977	113
Capacitance Unit September 1977	89, 412	V.H.F. Portable Radio November 1977	180
Car System Alarm February 1978	412		
Chaser Light Display February 1978	412	RADIO WORLD by Pat Hawker G3VA	748, 812, 886
		READERS LETTERS	27, 89, 130, 275, 347, 372, 454, 513, 632, 680, 754, 825
		SHOP TALK by Brian Terrell	13, 67, 108, 174, 207, 262, 342, 373, 595
		by Dave Barrington	433, 485, 547, 595, 653, 720, 790, 857
		SQUARE ONE	19, 83, 112, 173, 220, 291, 340, 752, 789, 864

SPECIAL FEATURES

ABBREVIATIONS	221	NO-FLASH FOR YOUR POLAROID CAMERA	
AIRPORT RADAR by G. A. G. Brooke	344	by R. H. Marco	565
BRAIN ON A GRAIN by S. McClelland Part One	434	POWER SLAVES IN ACTION by E. M. Lyndsell	553
Part Two	492	RADIO ASTRONOMY AT CAMBRIDGE	
BRITISH ARMY EQUIPMENT EXHIBITION	629	by S. McClelland	28
CLUB CORNER	491	THE OSCILLOSCOPE by J. Smith	18
FEMININE LOGIC? by Julie Hurst	405	TV GAMES by N. Hunter Part One	607
IMPLANTABLE MEDICAL ELECTRONICS		Part Two	683
by S. McClelland	216	WHAT DO YOU KNOW	35, 66, 172

SPECIAL SERIES

DOING IT DIGITALLY by O. N. Bishop		Diode Logic	90
1 Introduction to Logic, AND, OR and NOT gates	734	A.C. Measurement	114
2 Investigating the 7400	792	Voicing Circuits	222
3 TTL Clocks and Latches	858		
DOWN TO EARTH by George Hylton		PROFESSOR ERNEST EVERSURE by Anthony J. Bassett	
Mains Hum and Earth	44	Electret Microphones	42
Beat Frequency Oscillator	180	Response Curves	135
Negative Resistance	299	Quantisation	184
Measuring Low Resistance	354	Radioesthetic Preamplifier Part One	240
When is a Capacitor not a Capacitor?	411	Part Two	294
Measuring Impedance	464	Part Three	352
Analogue or Digital	576	Dowsing	409
Super Conductivity	635	The "Thing"	460
Show Time and Response Time	694	The VOX AC30 Amplifier	520
Gain and Decibels	760	Colouration	574
Making use of the Doppler Effect	832	Automatic Bias	627
		Crossover Distortion	692
		Reforming Capacitors	757
FOR YOUR ENTERTAINMENT by Adrian Hope		WORKSHOP MATTERS by Harry T. Kitchen	
Video Cassettes	40	Planning out your workshop	830
Multitrack Master Tapes	82	Fuses and their current ratings	893
Hi Fi Journalism	113		
Linear Motors, Teletext Paging System	159	YOUR CAREER IN ELECTRONICS by Peter Verwig	
TV Games, Video Recording, Film Loops and		Selling Components	36
Telephone Lines	215	Is there a spot for you in this ever expanding industry?	237
Shocking Affair, Magnetic Driver and Explosive tune	267		
Pioneers in Audio	331	TEACH-IN '78 by George Hylton	
Close Shave and Mains Frequency	383	1 Introduction	68
Videotape, Passive Switch, Ident-Chips and Light Help	443	2 Module Construction	116
Video at the Summit, Compatibility Check	491	3 Resistance, Capacitance and Module Construction	164
Hall Effect, Effective Resistance, all charged up	572	4 Ohm's Law, Timing Circuits	208
Mains Frequency Variations, Buzz-Phrases	606	5 Impedance, Resonance, Inductance and Amplifiers	268
Matter of Distortion	664	6 Conductance, Matching, Gain	324
Development of Microwaves	724	7 Valves, F.e.t.s and Transistors	374
Paging Systems—1	796	8 Power, Waveforms, Amplifier module	436
—2	869	9 Radio, Modulation, Receivers	496
MINI-MODULE by George Hylton		10 Logic Circuits	548
1 Passive Mixer	746	11 Power Supplies and Transducers	598
2 Audio Effects Oscillator	818	12 Maths and Measurements	656
3 Microphone Amplifier	862	End of Term Questions and Answers	659
PHYSICS IS FUN by Derrick Daines		Glossary	662, 663
Shocking Coils	23		

SPECIAL INSERTS AND OFFERS

SOLDERING IRON SPECIAL OFFER	November 1977	AVOMETER COMPETITION	September 1978
TOOL RACK	March 1978	HANDY GUIDE	October 1978
POPULAR CIRCUITS—8 page supplement	April 1978	CONSTRUCTORS GUIDE TO HARDWARE—	
SEMICONDUCTORS FOR CONSTRUCTORS	May 1978	8 page supplement	November 1978

VARIABLE CAPACITORS With Direct Drive. 5pf @ 75p, 10pf @ 75p, 30pf @ 85p, 50pf @ 50p, 125 + 125pf @ 55p, 100 + 200pf @ 55p, 250 + 250 + 20 + 20pf @ 55p, 500 + 500pf @ 60p, with S.M. Drive. 250 + 250 + 25 + 25 + 25pf @ 75p, 265 + 365 + 365pf @ 65p. **10X CRYSTAL** 100kHz + 1MHz with CMOS Calibrator Circuit @ £2. **SOLDER-IN FEED THRU'S** 6-8pf, 300pf, 1000pf All at 20p doz. $\frac{1}{4}$ " **COIL FORMERS** With Core @ 6 for 25p, $\frac{1}{2}$ " **COIL FORMERS** With Can @ 3 for 10p. **285 KHz CRYSTALS FT 241A TYPE** @ 20p, 10 for £1-20. **CMOS I.C.'s** CD 4001 @ 10p, CD 4007 @ 10p, CD 4011 @ 10p, CD 4020 @ 60p, 4029 @ 60p. **VHF FETS** J 310 @ 20p, 2N 3819 Type @ 6 for 75p, 40673 Type @ 33p.

MINIATURE ROTARY SWITCHES 2 Pole 4 way @ 20p, 3 Pole 3 way @ 40p, 1 Pole 10 way 2 Bank @ 40p. **100 MINIATURE DIODES** CV 9637 Preformed Leads @ 50p.

RCA I.C. I.F. CA 3011 @ 50p. **3 PIN PLUG AND SOCKET LIKE RS EUROPEAN TYPE** with 2 Metres of Cable at 75p pair. **200 ASSORTED** $\frac{1}{2}$ " W. **RESISTORS** @ 75p. **50 ZENER DIODES** 2 Watt Assorted Untested @ 57p.

MULLARD SEMI-AIRSPACED TRIMMERS 10pf @ 15p, 20pf @ 15p.

VHF TETTER TRIMMERS 10pf @ 18p, **DAU TRIMMERS** 9pf @ 10p, 38pf @ 10p, 45pf @ 10p, 125pf @ 12p, 140pf @ 15p.

100 ASSORTED C280 CAPACITORS for 57p. **2 GHz STRIPLINE NPN TRANSISTORS** @ £1. **MIDGET ROTARY SWITCHES** 1 Pole 24 way 4 Bank @ £1. **VHF AERIAL FILTER** with BNC SOCKET Box size 3. $\frac{1}{2}$ " x 1" x 1" at 55p each. **50 ELECTROLYTIC CAPACITORS** Assorted @ 57p. **50 BC 107-8-9 TRANSISTORS** Assorted Untested @ 57p, **50 AC 128 TRANSISTORS** Branded but Untested @ 57p. **50 VARI-CAP DIODES LIKE BA 102** Untested @ 57p. **6 PIN DIN PLUG AND SOCKETS** @ 25p pr. $\frac{1}{2}$ " Dia. by 3" Long **RIBBED CERAMIC COIL FORMERS** @ 35p. **FINNED HEAT SINK** For Two Plastic Power Transistors @ 75p (P&P 15p). **50 TUBULAR TANTALUM CAPACITORS** for £1. **30 ASSORTED 10XAJ CRYSTALS** @ £1-10. **20 ASSORTED FT 243 CRYSTALS** @ £1-50. **20 ASSORTED FT 241A CRYSTALS** @ £1-10. **MINIATURE MYLAR CAPACITORS** -01uf 50v.w., -1uf 50v.w., both 20p doz. **10 AMP S.C.R.'s** 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p. **LM 380 AUDIO I.C.** with various circuits @ 80p, **800 MHz NPN STRIPLINE TRANSISTOR** BF 362 @ 25p.

1uf 25v.w. ELECTROLYTIC CAPACITORS @ 6 for 25p. **SPECIAL 3 GANG MINIATURE VARIABLE CAPACITOR** 25 + 25 + 25pf @ 75p.

MAINS TRANSFORMERS 240 volt Input. Type 1, 24 volt Tapped at 14 volt 1 amp @ £1-30 (P&P 25p). Type 2, 22-0-22 volt 500mA @ £1-60 (P&P 25p). Type 3, 45 volt 6 amp @ £4-50 (P&P 95p). Type 4, 20 volt 2 amp Twice 10 volt 1 amp Twice @ £4-50 (P&P 95p). Type 5, 45 volt 2 amp 45 volt 500mA @ £3-50 (P&P 85p).

400mW GOOD UNMARKED ZENERS 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36 volt. All at 10 for 40p.

Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas orders at cost.

J. BIRKETT

RADIO COMPONENT SUPPLIERS

25 The Strait, Lincoln LN2 1JF Tel. 20767

CHROMASONIC electronics

56 FORTIS GREEN RD., MUSWELL HILL, N10 3HN
TELEPHONE: 01-883 3705

OUR LATEST CATALOGUE CONTAINS FREE 45 pence WORTH OF VOUCHERS

40p INC P.&P.

CONTAINS MICROPROCESSORS + BOARDS, MEMORIES, TTL, CMOS, ICs, PASSIVES, ETC., ETC.

SUPERSAVERS

ALL FULL SPEC DEVICES

TEXAS 741

TIMER 555

RED LED TIL209 (INC. CLIP)

5 for
£1.00

4 for
£1.00

10 for
£1.00

VAT INCLUSIVE PRICE + 25p P. & P.

A4 IC BOOKLET

SUPPLIED FREE WITH ORDERS OF ANY ICs WORTH £5.00 OR MORE, CONTAINS CIRCUITS, PIN CONNECTIONS AND DATA (35p + SAE IF SOLD ALONE)



ACE MAILTRONIX LTD
Dept. Tootal Street
Wakefield, W. Yorkshire. WF1 5JR

KITS! * KITS! * KITS!

You must try our fabulous new range of 'ELEKITS' for an easy build introduction to electronics. All kits, and there are many to choose from, come complete with case, easy to follow instructions and ALL COMPONENTS. Battery powered (not supplied) for safety and economy - ELEKITS will give hours of enjoyment - learning as you build. A small selection from the 'ELEKIT' range is shown below.

Watch this space for future kits!

NEW FABULOUS 'ELEKITS'
FOR FREE BROCHURE SEND S.A.E.

only **£11.45** **ROULETTE**

MINI ORGAN **£7.95 only**

MORSE TRAINER **£4.95 VALUE**

ALL KIT PRICES INCLUDE V.A.T

COMPONENTS

The ACE 2nd edition illustrated catalogue shows a considerably enlarged range of components, modules, 'Elekits'. Many PRICE REDUCTIONS from edition one. Component range includes - CAPACITORS, HARDWARE, CASES, LED'S, VERO PRODUCTS, RESISTORS, RS COMPONENTS, TRANSISTORS, DIODES, SCR'S, IC'S (Linear, TTL, CMOS, Audio), SWITCHES, PLUG/SOCKETS, BOOKS, TRANSFORMERS, TOOLS, SPEAKERS AND TEST EQUIPMENT. Typical VAT inclusive prices:-

LED'S RED	15p	2N3055	54p
LED'S GREEN	25p	2N3702/3/4/5	11p
8-pin IC SKT	15p	2N3819	24p
AC126	20p	OA90/91	7p
AC128	27p	IN4148	4p
BC107/8/9	13p	IN4001	5p
BC177/8/9	19p	W04	25p
BC182/3/4L	11p	Zener BZY88	12p
BC212/3/4L	11p	741 8-pin.	22p
BC547/8/9	13p	555	35p
BC557/8/9	15p	4001	20p
BCY70/71	20p	7400	15p
BFY50/1/2	23p	7490	62p
OC71	16p	Push sw.	16p
TIS43	35p	Slide toggle	19p
ZTX107/8/9	14p	W/C switches	54p
2N2926G	13p	O.25 CF Res.	6p per 3

COMPONENTS FOR 'EE' PROJECTS

Component lists with prices available for all 'EE' projects from October 1977 onwards. Send s.a.e. stating project and month of publication (max. 4 projects per s.a.e.).

TEACH-IN-78 KIT **£16.00**
DOING IT DIGITALLY TEST BED **£19.95**
Components for first six parts £2.50 all prices incl. VAT and p+p.

SEND 30p FOR THE ACE ILLUSTRATED CATALOGUE WHICH INCLUDES FULL LIST OF COMPONENTS, KITS AND READY-MADE MODULES. 30p REFUNDED WITH FIRST ORDER OF £5 OR MORE.

NAME _____
ADDRESS _____

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

THE NEW 1978-9

GREENWELD CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

KITS OF BITS FOR THIS MONTH'S EE PROJECTS

FUZZ BOX

All parts including die cast box £4.00

WATER LEVEL ALERT

All components inc. earpiece, vero, studding, cable and 2 boxes 115 x 75 x 36mm. £3.95 (without boxes £2.75)

VEHICLE IMMOBILISER

All parts including relay but not PCB £2.00

MICROPHONE AMPLIFIER

All compartments including case and hardware £2.00

E.E. 20+20 TUNER AMPLIFIER

We can supply all parts required except the components for the RF unit for approx. £40. Send SAE for detailed list.

CAR FLASHER

The three components required for just 80p

AIR-FRESHENER KIT

See our half-page ad, elsewhere in this issue for details.

NOTE: A more detailed list of parts supplied in these and other kits is available on receipt of a SAE.

Kits of last month's projects still available.

"DOING IT DIGITALLY"

This new series which started last month is bound to be a big success. We supply a complete set of parts (as we did for last year's 'Teach-in' series) for just £19.75 + £1 post for the Electronic Test Bed, and £2.75 for additional parts required for first 6 parts.

The GREENWELD Amplifier Kit

Ideal for the beginner to make, this kit is complete right down to the last screw!! Easily constructed on the PCB provided, the 4 transistor circuit will give 2W output from a crystal cartridge. Battery version £1.75, or with transformer for mains operation £3.95

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!

★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210. £3.35

K002 Extended range. 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF, 110 altogether for £4.75

K004 Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 150V. Total 370 for £12.30

K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tants for £14.20

K007 Electrolytic capacitors 25V working small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors, £6.00

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 2.7V to 35V. E24 series. Total 280 for £15.30

K042 As above but 5 of each value £8.70

TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 95p; 1A £2.50; 6-0-6V 100mA 85p; 1.5A £2.40; 9-0-9V 75mA 85p; 1A £2.10; Multitapped type 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.90; 20V 22A £3.90; 25V 12A £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50; 12V @ 250mA twice £2.00

RELAYS

W847 Low profile PC mntg 10x33x20mm 6V coil, SPCO 3A contacts. 93p

W832 Sub. min type, 10x19x10mm 12V coil DPCO 2A contacts £1.15

W706 6V SPCO 1A contacts 20x30x25mm Only 56p

W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A, 95p

W819 12V 1250R DPCO 1A contacts. Size 29x22x18mm, min plug-in type 72p

W838 50V ac (24V DC) coil, 11 pin plug in type, 3 pole c/o 10A contacts. Only 85p

W846 Open construction mains relay, 3 sets 10A c/o contacts. £1.20

Send SAE for our relay list—84 types listed and illustrated.

HEAT SINK OFFER


Copper TOS sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1000 for £25

POLYTHENE SHEET

Size 36 x 18" 200g. Hundreds of uses around the home, 100 sheets for £1.50. Box of 1500 for £19

wonderboard

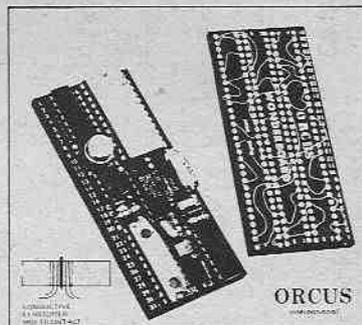Build
Your Circuits
Just Once
In Minutes...



SOLDERLESS CIRCUIT BOARDS
"One for each circuit!"

It's crazy to build, unbuild, construct and destruct your circuits on expensive "Breadboards". Now very economically on WONDERBOARD, you plug your components into one side of the board, the wires into the other, and you install the finished circuit in your equipment. They're like PC boards, but no soldering (which is enemy No. 1 of prototypes). Change any wire or component any time without disturbing others. Up to six interconnecting wires and one component lead into one multicontact. WONDERBOARDS accept all IC's from 4 to 60 pins and discrete components too.

Reliable? They conform to applicable sections of USA Military Standard MIL-A-46 146 and are used by the US Navy. You can't ask for better. WONDERBOARDS the universal board for equivalents of single-sided, double-sided, plated-thru hole, and multilayer printed circuits.

"Small Wonder"
12 IC DIL—14 capacity
(Equiv. No. tie-points 1302)

£2.80


"Big Wonder"
48 IC DIL—14 capacity
(Equiv. No. tie-points 5208)

£11.20

All prices include VAT and P&P. Send cheque or postal order to:—

CHARCROFT ELECTRONICS LIMITED
Charcroft House, Sturmer, Haverhill, Suffolk CB9 7XR
Telephone: Haverhill (0440) 5700 Telex: 817574

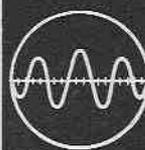See us at BREADBOARD '78 21st—25th November '78
Seymour Hall, London W1, Stand F10




TUAC


TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING CONTROL SYSTEMS

NEW FROM TUAC

TD500

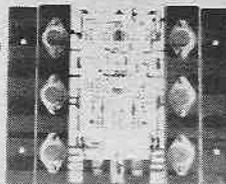

TD150

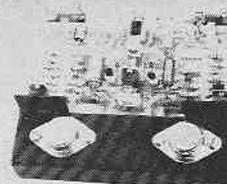

7" x 9" x 1 3/4" ULTRA QUALITY HIGH POWER 5" x 5" x 2" New D.C. Coupled Design AMPLIFIERS

Featuring—Electronic Short Open and Thermal Overload Protection.
Brief Spec.—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms.
Frequency Response 20 Hz - 20 KHz, T.H.D. at full power 0.1%.
Hum and Noise—100 dB Relative full output.

T.D. 500 300W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms. £45.00

Power supply P.S.300 £30.00

T.D.150 150W into 4 Ohms. 100W into 8 Ohms. £26.25

Power supply P.S. 150 £18.50

T.D. 150 60 Version 60W into 8 Ohms. 40W into 15 Ohms. £17.75

Power supply P.S.60 £15.50

Note—P.S. 300 will drive 2 T.D. 150 amplifiers

All output ratings are R.M.S. continuous sine wave output.

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD (EE108) or quote Access/Barclay Card No. (We accept holders) phone orders 01 672 9080/1

Post to—

TUAC LTD., (EE108), 119 CHARLMONT ROAD, LONDON SW17 9AB.

Send stamp for our free 28 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.

LOOK!

Here's how you master electronics.

.... the practical way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.


1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



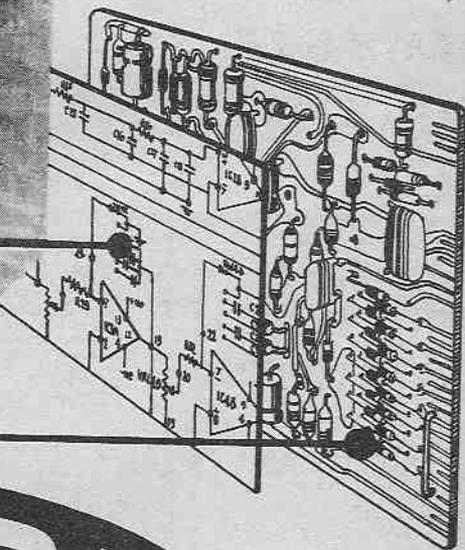2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

FREE


Post now, without obligation, to:-

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.

NAME _____


ADDRESS _____

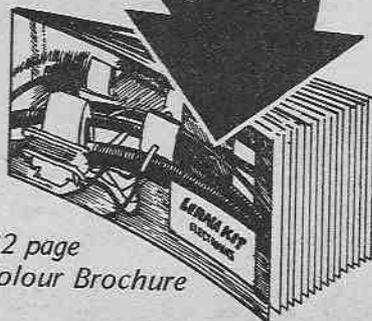

32 page
Colour Brochure

EEB12/78
Block caps please

GREENWELD Electronic Air Freshener Kit

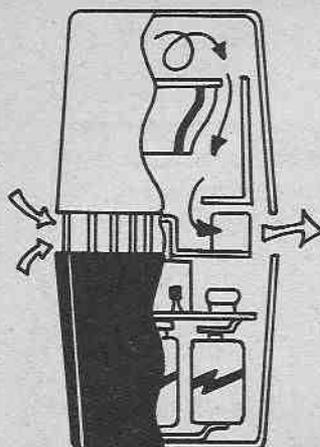

This novel kit contains everything you need to make one of the most advanced air fresheners of its kind. Styled to take its place in any room in your home and do its job quietly and unobtrusively.

ONLY £7.95 + 55p POSTAGE & PACKING

The automatic timing circuit switches on a fan for a few seconds at regular intervals to send an odour neutralising fragrance into every corner of your room.

The kit includes components for EITHER a 4 or 15 minute timing circuit, miniature D.C. motor and moulded parts in high impact styrene to provide an easily maintained, elegant appearance.

As featured in Nov issue of EE

Send To
GREENWELD ELECTRONICS
443, MILLBROOK ROAD
SOUTHAMPTON
SO1 0HX

Please send me air freshener kit(s)
with 4/15 minute timer at £8.50 (inc. p. & p.)
KIT INCLUDES A SUITABLE GEL FRESHENER FREE
I enclose a cheque/P.O. for £ payable
to Greenweld Electronics. NAME
ADDRESS

TAMTRONIK LTD

217, Toll End Road, TIPTON, West Midlands DY4 0HW

(DEPT. E.E.)

Tel: 021-557-9144

Mag Issue	Project	Ref	PCB	Comp. Pack	Hardware Pack	Case	Total
Jan. 78	Audio Visual Metronome	E001	65*	1-99	2-17	79	5-50
	Touch Switch	E002	74*	1-06	—	—	1-80
	Code Scrambler	E003	81*	2-78	1-50	45	5-54
	Rapid Diode Check	E004	52*	78	48	45	2-23
Feb. 78	Car Alarm	E005	80*	1-32	1-71	1-65	5-48
	Lead Tester	E006	51*	1-25	1-61	79	4-17
	Chaser Light Display	E007	1-75	8-19	6-79	3-15	19-88
	A.C. Meter Converter	E008	60*	1-74	1-38	1-65	5-37
Mar. 78	Audio Test (2 p.c.b.'s)	E009	1-74*	7-08	5-88	—	14-78
	G.R. Substitution Box	E010	—	3-48	3-98	99	8-32
	Catch-a-Light	E011	82*	2-55	2-70	2-15	8-42
	Weird Sound	E012	62*	2-71	1-17	79	5-29
Apr. 78	Roof Rack Alarm	E013	60*	1-52	1-71	—	3-83
	Mains Delay Switch	E014	94*	1-71	7-68	2-15	12-48
	Packet Timer	E015	60*	1-45	96	45	3-46
May 78	Flash Meter	E016	75*	3-15	5-40	79	11-09
	Mains Meter	E017	54*	41	40	—	1-35
	Power Amp-Teach-In	E018	—	1-55	—	—	1-55
	Power Pack	E019	70*	1-32	1-45	2-24	5-71
Jun. 78	Tele-Bell	E020	1-00*	2-84	6-85	—	10-69
	Inafu Transistor Tester	E021	65*	1-22	2-44	79	5-10
	S.W. Receiver-Teach-In	E022	—	2-61	—	—	2-61
	Power Slave	E023	1-75	—	—	—	1-75
Jul. 78	Visual Continuity Tester	E024	—	56	1-88	1-65	4-09
	Auto Night Light	E025	85*	3-17	3-32	2-05	9-39
	Short Wave Radio	E026	—	5-05	2-81	—	7-86
	Quagmire	E027	1-40*	4-78	1-21	—	7-39
Aug. 78	Logic Probe	E028	50*	92	45	79	2-66
	Slave Flash	E029	55*	2-17	—	—	2-72
	M.W. Mini Radio	E030	50*	2-08	1-75	45	4-78
	Audio Frequency Signal Generator	E031	85*	7-75	1-41	2-40	12-41
Sept. 78	RF Signal Generator	E033	—	13-24	2-58	—	15-82
	Sound to Light	E034	—	1-82	2-53	79	5-14
	Guitar Tone Booster	E035	75	1-12	84	1-35	4-96
	Car Battery State Indicator	E036	65*	97	—	—	1-62
Oct. 78	CMOS Radio	E037	1-45*	3-28	3-05	2-54	10-32
	Fuse Checker	E038	—	49	32	79	1-60
	Treasure Hunter	E039	1-25	4-86	5-37	2-54	14-02
Nov. 78	Audio Effects Oscillator	E042	—	1-31	30	79	1-40
	Water Level Alert	E043	70*	1-25	45	1-58	3-98
	Combination Lock	E045	2-35*	4-35	8-50	2-08	17-48
	Hot Line Game	E046	75*	1-00	2-82	—	4-57
Dec. 78	Car flasher warning	048	—	—	—	—	—
	Fuzz Box	049	—	—	—	—	—
	Ignition Immobiliser	050	—	—	—	—	—
	Mini-Module Micro Amp	051	—	—	—	—	—

Prices available on request.

ONE STOP SHOPPING. PCB's, Components, Hardware, Cases, Part Kits and Full Kits. A comprehensive service to the E.E. Constructor. **PRICES inc. VAT. P & P 30p per order.**

DOING-IT-DIGITALLY

TTL ELECTRONIC TEST BED
Full kit £21-50

Additional components for first six parts only £3-00

BOTH KITS (special price) £24-20

Price include VAT and P & P

PLUS —Special Free Offer with every Test Bed Kit purchased
50 Asst. 1/4 carbon resistors
10 Asst. Capacitors
Voucher worth 50p for next purchase.

CHRONOSTOP

Aug 78 EE32
Complete Kit including
CASE with Screen printed facia
PCB with screened component
layout
Full assembly instructions
PRICE inc. VAT and P & P.
£29-50

A Kit with a professional finish
Part kits available on request.

TELE-TEL METER

Nov '78 EE44
Complete Kit including
CASE with Screen printed facia
PCB with screened component
layout
Full assembly instructions
PRICE inc. VAT and P & P.
£19-50

An optional extra Display and Drive inc. components is available at £2-75.

OVER 150 KITS NOW AVAILABLE for projects from EVERYDAY ELECTRONICS; HOBBY ELECTRONICS & ELECTRONICS TODAY INTERNATIONAL. TRADE & EDUCATIONAL ENQUIRIES WELCOME.

Please send S.A.E. for details, naming kit and kit ref. and free Catalogue P.C.B.'s designed to E.E. circuit specifications.

VISIT OUR SHOP AT
32 Market Place,
Great Bridge, Tipton,
West Midlands.

Telephone
or Letter



CRESCENT RADIO LTD.I, ST. MICHAELS TERRACE, WOOD GREEN, LONDON, N22. 4SJ.
PHONE 01-888 3206**"FLIP"!**

AN ELECTRONIC VERSION OF TWO-UP OR ODDS AND EVENS. We supply a complete kit of parts which includes a strong case and attractive front panel to give the finished game a long life and professional appearance. Full assembly instructions are supplied.

"If you can solder you can make this great game." An ideal first project to introduce you to electronics. Not only will "FLIP" start you on a great hobby but you will own a game which will amuse you and your friends for hours.

COMPLETE KIT: £5.25 + 8% VAT

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed 1lb. 'poly packs'.

PRCIE: 65p per lb. + 8% VAT

HEAVY DUTY XOVER

2 WAY 8 OHM

A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100 watt.

Fitted with screw terminals for input and a three position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB.

ONLY £3.00 + 8% VAT

A CRESCENT 'SUPERBUY'

Goodmans 5" 8 ohm long throw H/D loudspeaker.

Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5/8" (diagonally).

ONLY £5.00 + 12 1/2% VAT

TELESCOPIC AERIAL + 12 1/2% VAT

11 section telescopic aerial.

Extended length: 1 metre (39 1/2")

Fully closed: 135mm (5 1/4")

Fixing: nut and bolt fixing through recess at base of aerial.

ONLY 75p EACH!

LOUDSPEAKERS + 12 1/2% V.A.T.

2 1/2" (57mm) 8 or 75 ohm 90p

(please state impedance req'd)

2 3/4" (60mm) 8 ohm (limited stocks) 60p

2 3/4" (70mm) 8 ohm (limited stocks) 60p

5" 8 ohm Ceramic £1.50

8" "ELAC" 8 ohm 15W dual cone £5.00

8" "GOODMANS" 'Audiom 8PA' £4.95

8 ohm 15W £2.00

7" x 4" 8 ohm 4W

LOUDSPEAKERS + 8% VAT.

12" "McKENZIE" 8 ohm 75W Bass £23.62

12" "McKENZIE" 8 ohm 75W dual cone £23.62

12" "McKENZIE" 8 ohm 75W general purpose £18.37

3 KILOWATT PSYCHEDELIC**LIGHT CONTROL UNIT**


1000W lighting per channel, max.

This 3 channel sound to light unit is housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions supplied. S.A.E. for spec. sheet.

ONLY £20.00 + 8% VAT

MINIATURE TOOL SET

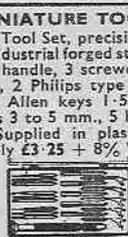A 20 pc. Tool Set, precision made from quality industrial forged steel. Contents: 1 swivel handle, 3 screwdrivers 1.5 to 3.5 mm., 2 Philips type screwdrivers, 1 awl, 3 Allen keys 1.5 to 2.5 mm., 5 sockets 3 to 5 mm., 5 hex. keys 4 to 6 mm. Supplied in plastic case. Our price: only £3.25 + 8% VAT.



'P&P' ORDERS UP TO £5, Add 30p

ORDERS £5-£10, Add 50p


All orders over £10 post free!

Please add VAT as shown.

S.A.E. with all enquiries please.



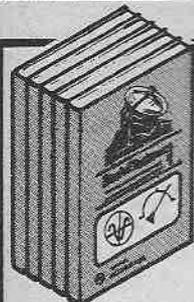Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N13.
ALSO: 13 SOUTH MALL, EDMONTON GREEN, EDMONTON.



ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.
Bound in stiff linen. Cover size 8 1/2 in x 5 in.
Price £7.50 per set (we pay the postage).

Book 1. Introducing Electronics
Book 2. Resistors/Capacitors
Book 3. Inductors/Diodes

Book 4. Meters/Voltage-dividers
Book 5. Transistor Project Circuitry

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order now:
Selray Book Company
60 Hayes Hill
Bromley
BR2 7HP

OUR 100% GUARANTEE

Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £


Name:

Address:

EE10

ELECTRONI-KIT**"EDUCATIONAL KITS OF
EXCEPTIONAL QUALITY"**

(AUDIO magazine)

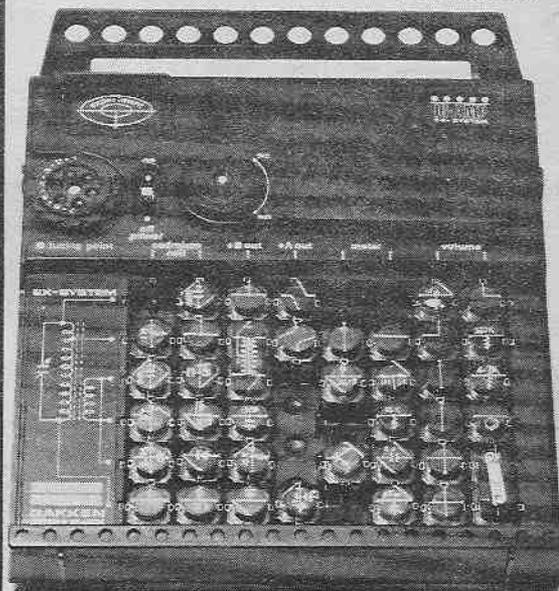**THIS IS A POWERFUL
RADIO RECEIVER!**

The same kit is also 150 other different actual working projects e.g.:

Computer & Logic Circuits,
Electronic Organ, Timer, Light
Control, Agility Tester, Lie
Detector, Siren, Horn, Buzzer,
Bird, Metronome,
Cds cell light & sound control,
Photogun, Light Oscillator,
Light Switch, Light and Sound
Morse Code,
Field Strength Meter,
Hygrometer, Sphygmometer, Etc.,
Etc.

Radio Receiver, Transmitter,
Amplifier, Audio Generator,
Signal Tracer & Injector,
Continuity Tester, Telegraph,
Photodiode Receiver, Radio
Receiver/Microphone Mixer,
Illuminometer, Voltmeter,
Ammeter, Sound Level Meter,
Ohmmeter, Diode & Transistor
Tester, Transparency Indicator
Etc., Etc.

The above is just a selection of the circuits available—you can also design your own circuits with these superb new Denshi-Gakken "EX" construction kits.

No previous experience of electronics is required but you learn as you construct and have a great deal of fun too. The kits are completely safe for anyone to use.

Kits are complete with very extensive construction manuals PLUS Hamlyn's "All-Colour" 160 page book "Electronics" (free of charge whilst stocks last).

ALL KITS ARE FULLY GUARANTEED. Add-on sets (to increase the scope of each kit) are available, plus spares and accessories as required.

150 PROJECT KIT £39.75 60 PROJECT KIT £25.75

120 PROJECT KIT £33.75 30 PROJECT KIT £18.95

100 PROJECT KIT £29.25 15 PROJECT KIT £16.75

Prices include educational manuals, free book, VAT, p & p (in the U.K.).

Callers at 20 Bride Lane will be very welcome. Trade and Educational enquiries invited.

Cheque/P.O./Barclaycard/Access No. (or 14p for illustrated literature) to DEPT. EE.


ELECTRONI-KIT LTD.

20 BRIDE LANE, LUDGATE CIRCUS,
LONDON EC4Y 8DX (01-353 6430)



ALL ITEMS DISPLAYED AT BREADBOARD '78 EXHIBITION, SEYMOUR HALL LONDON 21-26 NOV

METAL BOXES

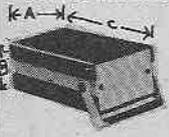

3005 Series

Finished in brushed aluminium with a contrasting finish on the top and bottom and plastic grips on shaped aluminium handles.



SIZES	A	B	C
00	82	54	145
40	343	106	198
70	283	68	216



PRICES incl. VAT & P + P			
00	£4.95		
40	£13.95		
70	£10.23		

3008.00

Finished in brushed aluminium and opaque bronze glass.




SIZE	A	B	C
	228.5	635	216

PRICE incl VAT & P + P
£6.99

3009.00

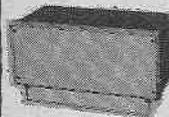Finished in matt blue and heavy anodised aluminium with front tilt support.



SIZE	A	B	C
	295	130	150

PRICE incl VAT & P + P
£6.75


SEND S.A.E. FOR NEW CATALOGUE & PRICE LIST ALSO OUR PAMPHLET ON OUR NEW RANGE OF 19 LOW PRICED METAL CABINETS.

UK 677




0-20VDC 2.5 Amp Stabilised power supply. Regulation 0.15% Max Ripple 1M/V Adjustable current limiting. Uses 2N3055 BD138 - BC160 - IC LN723-C. Led current limiting Display £39.67 inc VAT & P + P

UK 527

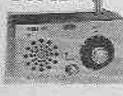

110 - 150 MHz VHF receiver uses AF239 - AF124 - 2N3819 Audio Amp TAA 611 B12. High sensitivity super-regenerative with R.F. stage. £19.95 inc VAT & P + P

UK 263/W

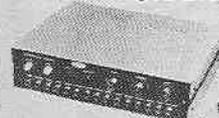

15 Rhythmn Generator—Fully wired and tested. 240V AC input, output level 250M/V. IMP 10K.ohm. 6 I.C. 7 Trans. 17 Diodes. £75.35 inc. VAT & P + P

AMTRON (UK) LTD
7, HUGHENDEN ROAD, HASTINGS,
SUSSEX, TN34 3TG
Telephone: (0424) 436004

SMALL ADS

The prepaid rate for classified advertisements is 16 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £4.40 per single column centimetre. All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

Tapes

C60 CASSETTE TAPES in library cases 32p each, POST PAID. Send your order to: A. W. & J. M. West, 56 Frankwell Drive, Coventry CV2 2FB.

Receivers and Components

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P&P. 'Brain-Freeze', 'em with a MINI STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.10 plus 20p P&P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5.00 each plus 20p P&P. LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS

4 CUNLIFFE ROAD, STONELEIGH
EWELL, SURREY. (E.E.)

DISCOVER ELECTRONICS. Build forty easy projects including: Metal Detector; Wireless Transmitter; Breathalyser; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms, etc. Circuits, plans all for £1.29 including FREE circuit board. Mail only. RIDLEY PHOTO/ELECTRONICS, Box 62, 111 Rockspark Road, Uckfield, Sussex.

71b ASSORTED COMPONENTS £3.60. 3 1/2 lb £1.95. Small Audio Amplifiers. 3 Transistors equivalent to AC128, OC72, with circuit, 3 for £1. 300 small components, Transistors, Diodes £1.50. Wire ended Neon's 7p. 20 for £1. No postage. List 15p refundable. Insurance add 15p. J.W.B. RADIO, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

Mercury Switch	75p	TIL209 Red 15p, Clips	3p
Electronic Timer Unit	240V A.C./6-12V D.C.	TIL209 Green Leds	25p
240V A.C./6-12V D.C.	49p	Large Red/Clear Leds	20p
Mini Electronic Buzzers	6/9/12 volt D.C.	BC107/8/9 12p, ORP12	75p
Small Reed Switch	16p	Texas 555 Timers	36p
Large Reed Switch	12p	8 Ω Earphone & Plug	18p
Changeover Type	35p	Crystal Earphone	45p
Reed Magnets	6p & 14p	Trimphone Warbler Unit	85p
Large "circular"	16p	85p. Chrome Telescopic Aerial	65p
Reed Relay 3-12V DC	46p	ABS Project Box and Lid	Black 80 × 60 × 42
Reed Bank 6 way	48p	Black 72 × 49 × 25	59p
Electro Magnet Coil 4-12V DC	16p	White 115 × 78 × 37	59p
Tape Recorder Motor Reg 9V DC 1 1/2" × 2"	75p	B/W 120 × 100 × 45	89p
Enamelled Copper Wire 32, 34, 36, 38, 40 SWG 1p ft	90v Neons	Pots 10k, 1M, LIN	16p
90v Neons	10p.	Vero -1 offsets	75p
Copper Capillary Tube	7p ft	Vero Type -1 Pins	3p ea
Key Switch & Key	£1.25	Rubber Sucker or Feet	2p
Loud Drivers 6 volt DC	£1.40 ea.	Croc Clips Red/Black	7p
Buzzer Alarms 1 1/2 volt DC	75p	Croc Jumper Leads	12p
R.F. Chokes 6p. 240V AC Motors 2500rpm	55p	GPO 4 Digit Counter	500 ohms 1" × 4 1/2"
Miniature Push to Test Switch Red Button	15p	Micro Switches Coin Operated 45p, DPDT 50 Assd Springs	45p
Push to Break	25p	30 Untested OA91	20p
8 Ω Speaker 2 1/2"	75p	25 I.C.s	30p
		30 " Transistors 30p	
		50 Assd Resistors	35p

Resistors 1W 5% 10 ohms—10 mm 2p each Prices include V.A.T., add 18p postage

GRIMSBY ELECTRONICS

64 Tennyson Road, Cleethorpes, Humberside
Callers to our Lambert Rd., Grimsby Shop. 100's of bargains—components, cases, surplus, etc. List 10p.

FULL SPEC COMPONENTS. Brand new no surplus. 9p for list. TERO, 109 Clitheroe Road, Sabden, Blackburn, Lancs.

PCB with 3 power transistors, heat sink, 20 general purpose silicon transistors, many diodes and other useful components £1.20; Mercury switches, 30p; Sprague 50uF, 350v capacitors, 15p. 10 for £1; P.S.U. in case ex. equipment, contains transformer with many taps, 3 power transistors and other good components, £2.25; MC 1458 (Dual 741) plus data sheet, 70p; 150 assorted components £1. Postage free. S.N.D. Electronics, 170 Belgrave Gate, Leicester LE1 5XL.

NOTE ALL PRICES INCLUDE V.A.T. TERMS C.W.O. CHEQUES & P/O PAYABLE FURAMA ELECTRONICS, P/P 15p—KITS 25p. CALLERS WELCOME.

BRAND NEW & FULL SPEC DEVICES ONLY

L.E.D.s 6" 2"/5mm	L.E.D.7 SEGMENT DISPLAYS
RED 10 £1.00	0/6"-15mm single digit com/anode
YELLOW 10 £1.60	£1.60
GREEN 10 £1.60	four digit com/cathode
CLEAR 10 £1.30	£4.50

SPECIAL OFFER 10 OF EACH COLOUR 40 FOR £5.00 FREE CIRCUIT OF OUR L.E.D. CHRISTMAS TREE LIGHT CHASER WITH EVERY PURCHASE.

ELECTRONIC KITS
0-35volt, 3amp, variable power supply S/C protected P.C.B. & ALL parts EXCEPT TRANSFORMER £26.50, WITH TRANSFORMER £13.90 post free.
0-45volt, 3-5amp, variable power supply, S.C.R. S/C protected.

P.C.B. & all parts except transformer £7.50.
32 L.E.D.V.U. TYPE DISPLAY (STEREO) P.C.B. & ALL PARTS NEEDS 12-18volt 500ma DC SUPPLY. £9.50, suitable supply £3.50 + 50p p/p, display box £2.40.

THE FULL KIT £15.00, post free.
FLUORESCENT INVERTER WILL RUN 4-40watt tube H/V VERY EFFICIENT £2.50.

POSITIVE FIXED VOLTAGE REGULATORS 1AMP MC7805/6/8/12/15/18/24volt 55p.
ZENER DIODES 4.3mw/2W 2-7.33volt 10p.

DIODES In4001 & 2, 5p, 3/4/5 6p, 6/7 7p, In4148, 4p, OA47/90/91/95/202 10p, BY127 12p.

TRANSISTORS BC107/8/9 10p, BC147/8/9 10p, BC161 34p, BC170/71/72 13p, BC182/3/4 13p, BC186 20p, BC187 24p, BC212/13L/14L 12p, BCY70/71/72 17p, BFY50/51/52 2p, TE107/11P/3055 50p, 2N677 60p.

THYRISTORS C106D 55p, C106M 65p.
I.C.s 741 25p, NE555 30p, 7400 13p, 13/16/17/32/70/74/121 30p, 7490 33p, 92 42p, 7447/875p, 123 55p, 141 56p, 145 95p, 154 £1.10, 190 £1.15.

FERRIC CHLORIDE 2lb in FREE ETCHING TRAY £1.40 plus 60p.
BATTERY CHARGING TRANSFORMER 15-0-15 volt 2 amp, PLUS 2, 3-amp diodes, £4.50.

FURAMA ELECTRONICS

32/34 SCOT LANE, DONCASTER,
YORKSHIRE DN1 1ES.
Tel: Doncaster (0302) 65234.

Educational

COURSES—RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination and obtain your G8 Licence, with an RRC home study course. For details of this, and other courses (GCE, professional examinations etc), write or phone:—THE RAPID RESULTS COLLEGE, Dept. JR1 Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service) or phone for a prospectus only ring 01-946 1102 (24hr recording service).

Record Accessories

STYL for Hi-Fi, Music Centres. Ill list free for SAE. Also cartridges, leads, accessories details. Felstead Electronics (EE), Longley Lane, Gatley, Cheadle, Ches. SK8 4EE.

Miscellaneous

RESISTORS \pm W 5% 2R2-2M2 (E12).

10 each or more of each value 90p/100. 100 assorted, ou mixture 75p/100. C50 cassettes in library cases 30p each. miniature relays 17 x 30 x 28mm 600 Ω coil 4 sets change over contacts 50p each.

Prices include V.A.T. Add 10% postage.

SALOP ELECTRONICS, 23 Wyle Cop, Shrewsbury.

BELL'S TELEVISION SERVICE for service sheets of Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55895.

SAVE TIME on PCB drilling. Steel jig for dils, presets only **FIFTY PENCE POST PAID**. W. L. Hampson, 221 Hodges St., Wigan.

ENAMELLED COPPER WIRE

swg	1 lb	8 oz	4 oz	2 oz
14-19	2-40	1-20	.69	.50
20-29	2-45	1-60	.82	.59
30-34	2-60	1-70	.89	.64
35-40	2-85	1-90	1-04	.75

Inclusive of p&p and VAT. SAE brings Catalogue of copper and resistance wires in all coverings. **THE SCIENTIFIC WIRE COMPANY**
PO Box 30, London E4 9BW
Reg. Office: 22 Coningsby Gardens

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE S.A.E. FOR LISTS. £1-00 for booklet "Nickel Cadmium Power". Write or call, 2 Union Drive, Bolders, Sutton Coldfield, West Midlands. 021-354 9764. Or see them at TLC, 32 Craven Street, Charing Cross, London WC2

AERIAL BOOSTERS improve weak VHF radio and television reception, price £5. SAE for leaflets, Electronic Mailorder Ltd., Ramsbottom, Bury, Lancashire, BL0 9AG.

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Phone 31803. No lists, enquiries S.A.E.

For Sale

NEW BACK ISSUES of "EVERYDAY ELECTRONICS". Available 60p each Post Free, open PO/Cheque returned if not in stock. **BELL'S TELEVISION SERVICES** 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

ELECTRONIC KITS—SAE for new catalogue, and clearance list of obsolete kits. **AMTRON UK**, 7 Hughenden Road, Hastings, Sussex.

Wanted

GOOD PRICES for recent Electronics/Computing/Radio books and magazines. Projects, Theory, etc. Details to: **HART**, 41 Luton Place, Edinburgh.

Books and Publications

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4-50, request free circuit diagram. Stamp brings details unique TV publications. Ausee, 76 Church Street, Larkhall, Lanarkshire.

RADIO BOOK SERVICE

WORLD RADIO TV HANDBOOK 1978 Edition	£8-25
30 CMOS IC Projects (R. A. Penfold)	£1-05
A Practical Introduction to Digital IC's	£1-25
25 Tested Transistor Projects (R. Torrens)	£1-25
30 Projects using Relays, SCR's & TRIAC's (F. G. Rayer)	£1-20
How to Build your own Metal & Transistor Loudspeakers (F. G. Rayer)	£0-95
Practical Repair & Renovation of Colour TV's (C. F. Miller)	£1-25
Fun & Games with your Electronic Calculator (J. Vine)	£0-85
How to Build Advanced Short Wave Receivers (R. A. Penfold)	£1-20
Radio Antennas Handbook for Long Distance Reception	£0-95
50 (Feb) Field Effect Transistor Projects (F. G. Rayer)	£1-25
Servicing Transistor Radio Receivers	£0-95
Solid State Short Wave Receivers for Beginners	£1-05

PRICES INCLUDE POSTAGE & PACKING... S.A.E. FOR FULL LIST
4 CHICHESTER COURT, WICKHAM RD, BECKENHAM KENT BR5 2JW

Service Sheets

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

ALL GOODS TOP QUALITY, NEW AND BRANDED AT TREMENDOUS PRICES

TRANSISTORS	BC 478	0-25	OPTOELECTRICS
AC 126	BD 132	0-24	7 Seg. display Red 0-8"
AC 127	BF 245A	0-24	c.a.
AC 128	BFY 51	0-20	Board 5
BC 107	BSY 95A	0-20	9 Seg. Alphametric display Red. 0-8"
BC 108	2N2219	0-25	c.a.
BC 109	2N3055	0-50	c.c.
BC 109C	2N3702	0-11	L.e.d.s
BC 177	2N3704	0-12	3mm red
BC 178	2N3706	0-12	3mm green
BC 184	2N3819	0-25	3mm yellow
BC 262	2N3459	0-22	clips

C/MOS	4000	0-15	4026	1-60
	4001	0-15	4027	0-50
	4002	0-15	4028	0-75
	4006	0-78	4029	0-95
	4007	0-17	4030	0-50
	4009	0-45	4032	0-90
	4011	0-15	4033	1-20
	4012	0-15	4041	0-40
	4013	0-45	4049	0-40
	4015	0-78	4050	0-40
	4016	0-40	4054	0-90
	4017	0-78	4055	1-35
	4018	0-85	4056	1-35
	4020	0-95	4060	1-10
	4022	0-90	4066	0-53
	4023	0-18	4093	0-70
	4024	0-65	4510	1-10
	4025	0-18	4511	1-15


TRANSFORMERS	p&p 35p
210V 12V or 6-0-6V @ 200mA	0-90
220V 12V or 6-0-6V @ 200mA	0-28
240V & 12V both @ 250mA	0-95
240V 12V @ 2A	3-95

LINEAR	348 Quad 741 14 di	1-13
	348 Quad Reg. TO-202 200mA	1-13
	+5V, +12V, +24V.	
	Please state	0-79
	317 Adj. Volt Reg @ 500 mA	1-48
	741 Op Amp. 8 di	0-27
	555 Timer 8 di	0-23

CASH/PO's/DRAFTS/CHEQUES/IMOs/ACCESS No. ACCEPTED. TELEPHONE US WITH YOUR ACCESS No. FOR REALLY FAST SERVICE

TERMS: p&p 25p (unless otherwise stated) plus VAT @ 8 per cent

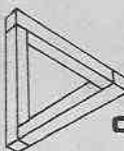TRADE/EXPORT/EDUCATION AUTHORITY ORDERS WELCOME



75 Willowtree Avenue
Gilesgate Moor
Durham DH1 1DZ
(0385) 62760 or 61765

ELTA Distribution Company

MAGENTA ELECTRONICS LTD

EK11, 88 CALAIS ROAD, BURTON-ON-TRENT, STAFFS. DE13 0UL. PHONE 02 83 65435

E.E. PROJECT KITS

Make us YOUR No. 1 SUPPLIER of KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Appropriate hardware—nuts, screws, I.C. sockets are included. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply—You construct.

FUZZ BOX Dec. 78. £4-36 inc. case.	WEIRD SOUND EFFECTS GENERATOR Mar. 78. £3-64 inc. case.
VEHICLE IMMOBILISER Dec. 78. £3-77 case extra 71p	CATCH-A-LIGHT Mar. 78. £4-36 case extra £1-34. Switch cases 47p. each.
WATER LEVEL ALERT Nov. 78. £4-77 inc. cases.	CHASER LIGHT DISPLAY Feb. 78. £19-78. inc. p.c.b. case extra £3-54.
"HOT LINE" GAME Nov. 78. £3-83 less case & rod.	AUDIO VISUAL METRONOME Jan. 78. £4-17 inc. case.
AUDIO EFFECTS OSCILLATOR Nov. 78. £2-75 inc. board & case.	RAPID DIODE CHECK Jan. 78. £1-97 inc. case.
SUBSCRIBERS TEL TEL METER Nov. 78. £15-35 case extra £3-75.	AUTOMATIC PHASE BOX Dec. 77. £9-45 inc. p.c.b. & case.
FUSE CHECKER Oct. 78. £1-40 inc. case.	VHF RADIO Nov. 77. £11-06 inc. case.
C/MOS RADIO Oct. 78. £7-55 inc. case.	ULTRASONIC REMOTE CONTROL Nov./Dec. 77. £13-22 inc. cases.
TREASURE HUNTER Oct. 78. £14-20 inc. case less handle & coil former.	TRANSISTOR TESTER Oct. 77. £6-34 case extra £3-35.
R.F. SIGNAL GENERATOR Sept. 78. £15-30 less case.	TREASURE LOCATOR Oct. 77. £9-77 case extra £2-92. Less handle & coil former.
GUITAR TONE BOOSTER Sept. 78. £4-13 inc. case and p.c.b.	ELECTRONIC DICE March 77. £4-09 inc. case.
SOUND TO LIGHT Sept. 78. £5-77 inc. case.	SOIL MOISTURE INDIC TOR June 77. £2-89 inc. case and probe.
FILTER £1-25.	PHONE/DOORBELL REPEATER July 77. £4-92 inc. case.
SLAVE FLASH Aug. 78. £2-66 inc. case less SK1.	SHORT WAVE RECEIVER Aug. 77. £10-88 case extra £1-25.
A.F. SIGNAL GEN. Aug. 78. £8-21. Case extra £2-59 less "dial" materials.	FUZZTONE UNIT July 77. £5-68 less case.
LOGIC PROBE July 78. £2-29 inc. case.	ADD-ON CAPACITANCE UNIT Sept 77. £4-48 inc. case.
QUAGMIRE July 78. £7-31 less case pins etc.	
IN SITU TRANSISTOR TESTER June 78. £4-49 inc. case.	
VISUAL CONTINUITY CHECKER June 78. £2-96 inc. case & probes.	
TELE BELL June 78. £10-14 case extra £2-59.	
FLASHMETER May 78. £8-67. case extra £1-25.	
POCKET TIMER April 78. £2-82 inc. case.	

ALL PRICES INCLUDE VAT AND FIRST CLASS POST. ADD 15p TO ORDERS UNDER 25. COPIES OF E.E. CONSTRUCTIONAL ARTICLES 39p.

CATALOGUE—SEND 3 x 9p STAMPS.

TEACH - IN - 78

COMPLETE KIT £14-50

INCLUDES FREE COMPONENT IDENTIFICATION CHART. TEACH-IN REPRINTS 39p. EACH PART. ALL 12 PARTS AVAILABLE.



1979 ELECTRONICS CONSTRUCTORS CATALOGUE

HAVE YOU GOT YOUR COPY YET? MAGENTA'S NEW CATALOGUE INCLUDES MANY NEW PRODUCTS — CAREFULLY CHOSEN FOR EVERYDAY ELECTRONICS READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR CONSTRUCTORS. FULLY INCLUSIVE PRICES RIGHT NEXT TO THE PRODUCTS MAKE ORDERING EASY. NO MINIMUM ORDER — ALL PRODUCTS STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE!

WRITE TODAY ENCLOSING 3 x 9p STAMPS.

MULTIMETER TYPE 1 , 1,000 o.p.v. with probes 2" x 3 1/2" x 1" £5-95.	F.M. INDOOR AERIAL , 49p.
MULTIMETER TYPE 2 , 20,000 o.p.v. with case and probes 5" x 3 1/2" x 1 1/2" £12-45.	TELEPHONE PICK-UP COIL , 65p.
ANTEX X25 SOLDERING IRON 25W . Ideal for electronics £3-95.	SPEAKERS , Miniature 8 ohm 59p. 64 ohm 35p. 80 ohm £1-15.
SOLDERING IRON STAND , ANTEX ST3 £1-85.	EARPIECES , Crystal 36p. Magnetic 15p.
DESOLDER BRAID , 62p.	STETHOSCOPE ATTACHMENT fits our earpieces 59p.
HEAT SINK TWEEZERS , 13p.	HEADPHONES , MONO. 2K. Padded Superior Sensitive. £2-98.
DESOLDER PUMP , Easy to use £5-98.	HEADPHONES , STEREO. 8 ohm. £2-85.
SIGNAL INJECTOR , £4-98.	INTERCOM , 2 STATION. £5-95.
DENTIST'S MIRROR , Adjustable £1-70.	CABINET SPEAKER , 8 ohm 5 watt 10" x 7" x 4" £8-75.
JEWELLERS EYEGLASS , 95p.	F.M. TUNER MODULE —feeds any amplifier with scale & pointer £8-35.
TRIPLE MAGNIFIER , £1-15.	
BUZZER , 6V 74p. 12V 77p.	


DOING IT DIGITALLY

New Series—complete kit or separate parts **IN STOCK NOW** for FAST DELIVERY by **FIRST CLASS POST**. All top quality components as specified by Everyday Electronics. Our kit comes complete with **FREE TTL and COMPONENT IDENTIFICATION CHART**. Follow this educational series—start today—and learn about digital electronics. SEND £22-95 for the **TTL TEST BED**, £3-75 for **ADDITIONAL COMPONENTS** (6 months).

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

STEREO PRE-AMPLIFIERS

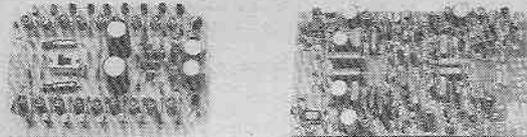

MC 1

CPR 1

CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < 0.05% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 85dB; slew-rate 3V/μS; T.H.D. 20Hz–20kHz < 0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 29mm. Supply to be ± 15 volts.

MC 1—PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS



It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically 0.1% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μS; signal to noise ratio 110dB; frequency response 10Hz–35kHz, –3dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120–240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER AMPLIFIER KIT

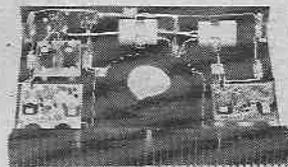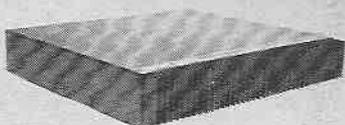The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-0-35v £16 30
CE 1004 100W/4 ohms 35-0-35v £19 22
CE 1008 100W/8 ohms 45-0-45v £23 22
CE 1704 170W/8 ohms 45-0-45v £29 12
CE 1708 170W/8 ohms 80-0-80v £31 90

TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £14 47
CPS2 for 2 x CE 1004 or 2/4 x CE 608 £16 82
CPS3 for 2 x CE 1008 or 1 x CE 1704 £17 86
CPS4 for 1 x CE 1008 £15 31
CPS5 for 1 x CE 1708 £22 68
CPS6 for 2 x CE 1704 or 2 x CE 1708 £23 98

HEATSINKS

Light duty, 50mm, 2°C/W £1 30
Medium power, 100mm, 1.4°C/W £2 20
Disc/group, 150mm, 1.1°C/W £2 85
Fan, 30mm, static 120 or 240v £18 50
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules £29 16
THERMAL CUT-OUT, 70°C £1 90

POWER AMP KIT

..... £32 40

PRE-AMPS:

These are available in two versions—one uses standard components, and the other (the S) uses where necessary and tantalum capacitors.
CPR1 £29 49
CPRIS £39 98
MC1 £19 50
MCIS £29 49

POWER SUPPLY

REG1 £6 75
TR6 £1 75

BRIDGE DRIVER, BDI

Obtain up to 340W using 2 x 170W amps and this module BDI £5 40

CRIMSON ELEKTRIK

1 ESTAMFORD STREET,

LEICESTER, LE1 5NL

Tel: (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

Distributor—

"MINIC TELEPRODUKTER
BOX 12035: S-750 12
UPPSALA 12, SWEDEN"

4-STATION INTERCOM



£22-95
V.A.T. £1.84

Solve your communication problems with this 4-station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. A Battery and other accessories. Adaptable for mains. Battery eliminator £6.75 (optional) P. & P. 89p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY
£16-95
+ V.A.T. £1.36

Latest improved transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increases efficiency in the office, shop and surgery. Perfect for "conferencing" calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control. Conversation recording model at £19.95 + V.A.T. £1.60. P. & P. 89p.


10-day price refund guarantee on all items.
WEST LONDON DIRECT SUPPLIES (E812) 169 KENSINGTON HIGH STREET,
LONDON, W8 6SH. 01-837 5545

HAVE YOU DONE IT LATELY!

Fit a new tape head and transform the performance of your tape recorder

MONOLITH
THE MONOLITH ELECTRONICS CO. LTD.

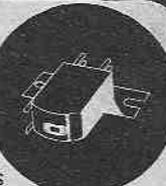QUALITY
REEL TO REEL
AND CASSETTE TAPE HEADS



Please enclose

Full Catalogue 25p

20p P&P with order

B24—RP stereo cassette glass/ferrite record/playback £9.84
B12—01 mono cass. playbk. £1.60 B24—Q1 stereo cass. playbk. £2.80
A28—05 stereo 8tk cartridge £1.80 E12—09 stereo/mono cass. erase £1.80

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321

INDEX TO ADVERTISERS

Ace Mailtronix	...	897
Amtron	...	902
Antex	...	Cov II
Bi-Pak	...	881
Birkett J.	...	897
B.N.R.E.S.	...	846, 882, 899
Boffin Projects	...	902
Brewster S. R.	...	846
Bull J.	...	888
Charcroft Electronics	...	898
Chromatronics	...	891
Chromasonics	...	897
Crescent Radio	...	901
Crimson Electronics	...	904
David George Sales	...	846

Dawes	...	844
Delta	...	903
Dewtron Electronics Ltd.	...	892
Doram	...	844
E.D.A.	...	842
Electroni-Kit	...	901
Electrovalue	...	847
Felstead Electronics	...	903
Furama Electronics	...	902
Greenweld	...	898, 900
Grimsey Electronics	...	902
Harversons	...	892
Heath-Kit	...	882
Home Radio	...	892
I.L.P. Electronics Ltd.	...	887
Interext (ICS)	...	842
Letrokit Ltd.	...	885

Magenta Electronics	...	903
Maplin	...	Cov IV
Marshall A.	...	Cov III
Metac	...	891
Monolith Electronics	...	904
Radio Book Service	...	903
Radio & TV Components	...	845
Salop Electronics	...	903
Sandwell Plant Ltd.	...	903
Scientific Wire Co.	...	903
Selray Book Co.	...	901
Silicon Chip	...	841
Swanley Electronics	...	842
Tamtronik	...	900
TUAC	...	898
Vero Electronics	...	891
Watford Electronics	...	843
West London Direct Supplies	...	904

Marshall's

Come and get a great deal

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat
Tel orders on credit cards £10 min.
Trade and export enquiries welcome


A. Marshall (London) Ltd. Dept. EE Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 8005.
Retail Sales London: 40-42 Cricklewood Bdw, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Rd., W2. Tel: 01-723 4242. Glasgow: 85 West Regent St., G2 2QD. Tel: 041-332 4133. Bristol: 1 Straits Pde., Fishponds Rd., BS16 2LX. Tel: 0272 654201.

TRANSISTORS

2N696	0-39	2N2195A	0-40	2N3390	0-50	2N3905	0-18	2N5086	0-30	2N6107	0-45	AD161	1-00	BC168B	0-13	BC184LC	0-15	BC303	0-54	BD139	0-43	BD530	0-55
2N697	0-31	2N2217	0-55	2N3391	0-40	2N3906	0-18	2N5087	0-30	2N6108	0-55	AD162	1-00	BC168C	0-13	BC212	0-15	BC307	0-16	BD140	0-43	BD535	0-70
2N698	0-49	2N2218	0-35	2N3392	0-45	2N3907	0-55	2N5088	0-30	2N6109	0-55	AF106	0-60	BC169A	0-13	BC212A	0-15	BC307A	0-16	BD181	1-90	BD536	0-70
2N699	0-58	2N2218A	0-38	2N3393	0-17	2N3908	0-72	2N5089	0-30	2N6111	0-49	AF109	0-52	BC169B	0-13	BC212B	0-15	BC307B	0-16	BD182	2-20	BD537	0-74
2N706	3-36	2N2219	0-38	2N3394	0-17	2N3909	0-60	2N5090	0-30	2N6122	0-41	BC107	0-16	BC177A	0-22	BC212C	0-18	BC308	0-16	BD183	2-35	BD538	0-77
2N706A	0-30	2N2218A	0-39	2N3395	0-19	2N3910	0-60	2N5091	0-30	2N6123	0-48	BC107B	0-16	BC177B	0-22	BC212D	0-18	BC308A	0-16	BD187	0-95	BD539	0-80
2N708	0-30	2N2220	0-39	2N3396	0-19	2N3911	0-60	2N5092	0-30	2N6124	0-45	BC108	0-16	BC178	0-22	BC213	0-15	BC309	0-16	BD235	0-46	BD540	0-80
2N718	0-54	2N2221	0-25	2N3397	0-19	2N3912	0-60	2N5093	0-30	2N6125	0-47	BC108A	0-16	BC178A	0-25	BC213A	0-15	BC309A	0-16	BD236	0-44	BD541	1-32
2N718A	0-54	2N2221A	0-25	2N3398	0-19	2N3913	0-60	2N5094	0-30	2N6126	0-47	BC108B	0-16	BC178B	0-35	BC213B	0-15	BC309C	0-16	BD237	0-44	BD542	1-90
2N720A	0-65	2N2222	0-25	2N3399	0-19	2N3914	0-60	2N5095	0-30	2N6127	0-47	BC108C	0-16	BC179	0-25	BC213C	0-15	BC327	0-22	BD238	0-44	BDY20	1-10
2N722	0-45	2N2222A	0-25	2N3400	0-19	2N3915	0-60	2N5096	0-30	2N6128	0-47	BC109	0-16	BC179A	0-25	BC213D	0-15	BC328	0-20	BD239A	0-44	BDY55	1-90
2N727	0-50	2N2369	0-27	2N3401	0-92	2N3916	1-35	2N5097	0-38	2N6129	0-48	BC109B	0-17	BC179B	0-25	BC213E	0-17	BC337	0-20	BD239C	0-59	BDY56	2-10
2N914	0-38	2N2369A	0-27	2N3402	1-45	2N3917	1-41	2N5098	0-44	2N6130	0-48	BC109C	0-18	BC179C	0-25	BC214	0-17	BC338	0-23	BD240C	0-49	BF155	0-39
2N916	0-33	2N2646	0-80	2N3403	0-17	2N3918	0-42	2N5099	0-44	2N6131	0-48	BC110	0-18	BC179D	0-25	BC214A	0-17	BC339	0-23	BD240C	0-59	BF160	0-33
2N917	0-38	2N2647	1-55	2N3404	0-14	2N3919	0-42	2N5100	0-44	2N6132	0-48	BC111	0-30	BC182	0-12	BC214B	0-17	BC340	0-13	BD241A	0-49	BF161	0-65
2N918	0-45	2N2903	1-60	2N3405	0-14	2N3920	0-42	2N5101	0-44	2N6133	0-48	BC112	0-13	BC182A	0-12	BC214C	0-17	BC341	0-14	BD241C	0-65	BF167	0-37
2N923	0-37	2N2904	0-31	2N3406	0-14	2N3921	0-42	2N5102	0-44	2N6134	0-48	BC113	0-13	BC182B	0-13	BC214D	0-17	BC342	0-14	BD242A	0-65	BF173	0-37
2N929A	0-37	2N2904A	0-31	2N3407	0-14	2N3922	0-42	2N5103	0-44	2N6135	0-48	BC114	0-13	BC182C	0-13	BC214E	0-17	BC343	0-14	BD242C	0-62	BF177	0-27
2N930	0-37	2N2905	0-31	2N3408	0-14	2N3923	0-42	2N5104	0-44	2N6136	0-48	BC115	0-13	BC182D	0-13	BC214F	0-17	BC344	0-14	BD243C	0-65	BF178	0-27
2N930A	0-37	2N2905A	0-31	2N3409	0-14	2N3924	0-42	2N5105	0-44	2N6137	0-48	BC116	0-13	BC182E	0-13	BC214G	0-17	BC345	0-14	BD243C	0-67	BF179	0-37
2N931	0-37	2N2906	0-25	2N3410	0-12	2N3925	0-42	2N5106	0-44	2N6138	0-48	BC117	0-15	BC183	0-12	BC214H	0-17	BC346	0-14	BD244C	0-65	BF180	0-37
2N932	0-37	2N2907	0-25	2N3411	0-12	2N3926	0-42	2N5107	0-44	2N6139	0-48	BC118	0-15	BC183A	0-12	BC214I	0-17	BC347	0-14	BD244C	0-67	BF181	0-37
2N933	0-37	2N2908	0-25	2N3412	0-12	2N3927	0-42	2N5108	0-44	2N6140	0-48	BC119	0-15	BC183B	0-12	BC214J	0-17	BC348	0-14	BD245A	0-69	BF182	0-37
2N934	0-37	2N2909	0-25	2N3413	0-12	2N3928	0-42	2N5109	0-44	2N6141	0-48	BC120	0-15	BC183C	0-13	BC214K	0-17	BC349	0-14	BD245C	0-65	BF183	0-44
2N935	0-37	2N2910	0-25	2N3414	0-12	2N3929	0-42	2N5110	0-44	2N6142	0-48	BC121	0-15	BC183D	0-13	BC214L	0-17	BC350	0-14	BD246A	0-72	BF184	0-41
2N936	0-37	2N2911	0-25	2N3415	0-12	2N3930	0-42	2N5111	0-44	2N6143	0-48	BC122	0-15	BC183E	0-13	BC214M	0-17	BC351	0-14	BD246C	0-63	BF185	0-37
2N937	0-37	2N2912	0-17	2N3416	0-12	2N3931	0-42	2N5112	0-44	2N6144	0-48	BC123	0-15	BC183F	0-13	BC214N	0-17	BC352	0-14	BD246C	0-65	BF186	0-37
2N938	0-37	2N2913	0-17	2N3417	0-12	2N3932	0-42	2N5113	0-44	2N6145	0-48	BC124	0-15	BC183G	0-13	BC214O	0-17	BC353	0-14	BD246C	0-65	BF187	0-37
2N939	0-37	2N2914	0-17	2N3418	0-12	2N3933	0-42	2N5114	0-44	2N6146	0-48	BC125	0-15	BC183H	0-13	BC214P	0-17	BC354	0-14	BD246C	0-65	BF188	0-37
2N940	0-37	2N2915	0-17	2N3419	0-12	2N3934	0-42	2N5115	0-44	2N6147	0-48	BC126	0-15	BC183I	0-13	BC214Q	0-17	BC355	0-14	BD246C	0-65	BF189	0-37
2N941	0-37	2N2916	0-17	2N3420	0-12	2N3935	0-42	2N5116	0-44	2N6148	0-48	BC127	0-15	BC183J	0-13	BC214R	0-17	BC356	0-14	BD246C	0-65	BF190	0-37
2N942	0-37	2N2917	0-17	2N3421	0-12	2N3936	0-42	2N5117	0-44	2N6149	0-48	BC128	0-15	BC183K	0-13	BC214S	0-17	BC357	0-14	BD246C	0-65	BF191	0-37
2N943	0-37	2N2918	0-17	2N3422	0-12	2N3937	0-42	2N5118	0-44	2N6150	0-48	BC129	0-15	BC183L	0-13	BC214T	0-17	BC358	0-14	BD246C	0-65	BF192	0-37
2N944	0-37	2N2919	0-17	2N3423	0-12	2N3938	0-42	2N5119	0-44	2N6151	0-48	BC130	0-15	BC183M	0-13	BC214U	0-17	BC359	0-14	BD246C	0-65	BF193	0-37
2N945	0-37	2N2920	0-17	2N3424	0-12	2N3939	0-42	2N5120	0-44	2N6152	0-48	BC131	0-15	BC183N	0-13	BC214V	0-17	BC360	0-14	BD246C	0-65	BF194	0-37
2N946	0-37	2N2921	0-17	2N3425	0-12	2N3940	0-42	2N5121	0-44	2N6153	0-48	BC132	0-15	BC183O	0-13	BC214W	0-17	BC361	0-14	BD246C	0-65	BF195	0-37
2N947	0-37	2N2922	0-17	2N3426	0-12	2N3941	0-42	2N5122	0-44	2N6154	0-48	BC133	0-15	BC183P	0-13	BC214X	0-17	BC362	0-14	BD246C	0-65	BF196	0-37
2N948	0-37	2N2923	0-17	2N3427	0-12	2N3942	0-42	2N5123	0-44	2N6155	0-48	BC134	0-15	BC183Q	0-13	BC214Y	0-17	BC363	0-14	BD246C	0-65	BF197	0-37
2N949	0-37	2N2924	0-17	2N3428	0-12	2N3943	0-42	2N5124	0-44	2N6156	0-48	BC135	0-15	BC183R	0-13	BC214Z	0-17	BC364	0-14	BD246C	0-65	BF198	0-37
2N950	0-37	2N2925	0-17	2N3429	0-12	2N3944	0-42	2N5125	0-44	2N6157	0-48	BC136	0-15	BC183S	0-13	BC215	0-17	BC365	0-14	BD246C	0-65	BF199	0-37
2N951	0-37	2N2926	0-17	2N3430	0-12	2N3945	0-42	2N5126	0-44	2N6158	0-48	BC137	0-15	BC183T	0-13	BC215A	0-17	BC366	0-14	BD246C	0-65	BF200	0-37
2N952	0-37	2N2927	0-17	2N3431	0-12	2N3946	0-42	2N5127	0-44	2N6159	0-48	BC138	0-15	BC183U	0-13	BC215B	0-17	BC367	0-14	BD246C	0-65	BF201	0-37
2N953	0-37	2N2928	0-17	2N3432	0-12	2N3947	0-42	2N5128	0-44	2N6160	0-48	BC139	0-15	BC183V	0-13	BC215C	0-17	BC368	0-14	BD246C	0-65	BF202	0-37
2N954	0-37	2N2929	0-17	2N3433	0-12	2N3948	0-42	2N5129	0-44	2N6161	0-48	BC140	0-15	BC183W	0-13	BC215D	0-17	BC369	0-14	BD246C	0-65	BF203	0-37
2N955	0-37	2N2930	0-17	2N3434	0-12	2N3949	0-42	2N5130	0-44	2N6162	0-48	BC141	0-15	BC183X	0-13	BC215E	0-17	BC370	0-14	BD246C	0-65	BF204	0-37
2N956	0-37	2N2931	0-17	2N3435	0-12	2N3950	0-42	2N5131	0-44	2N6163	0-48	BC142	0-15	BC183Y	0-13	BC215F	0-17	BC371	0-14	BD246C	0-65	BF205	0-37
2N957	0-37	2N2932	0-17	2N3436	0-12	2N3951	0-42	2N5132	0-44	2N6164	0-48	BC143	0-15	BC183Z	0-13	BC215G	0-17	BC372	0-14	BD246C	0-65	BF206	0-37
2N958	0-37	2N2933	0-17	2N3437	0-12	2N3952	0-42	2N5133	0-44	2N6165	0-48	BC144	0-15	BC184	0-12	BC215H	0-17	BC373	0-14	BD246C	0-65	BF207	0-37
2N959	0-37	2N2934	0-17	2N3438	0-12	2N3953	0-42	2N5134	0-44	2N6166	0-48	BC145	0-15	BC184A	0-12	BC215I	0-17	BC374	0-14	BD246C	0-65	BF208	0-37
2N960	0-37	2N2935	0-17	2N3439	0-12	2N3954	0-42	2N5135	0-44	2N6167	0-48	BC146	0-15	BC184B	0-12	BC215J	0-17	BC375	0-14	BD246C	0-65	BF209	0-37


MAPLIN

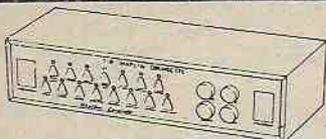everything for the modern D.I.Y. electronics enthusiast and more.




THE 'DRUMSETTE' RHYTHM GENERATOR

Organists, pianists, guitarists... an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £85 including smart teak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES49 price 25p. (All prices include V.A.T. and p & p).

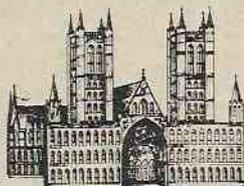

REVERBERATION SYSTEMS

High quality spring line driver module uses 4 integrated circuits and two transistors. Built and tested circuit board with wiring instructions for spring line. XB85G, price £6.00. Power supply to suit driver module costs around £2.50 and construction details are in catalogue, or ask for leaflet MES24. Mechanical spring lines: Short line (XL08J) £4.49; Long line (XB84F) £10.39. (All prices include V.A.T. and p & p).

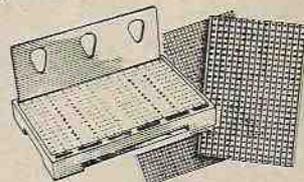

BOARDS AND PCB'S


Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decs or if you prefer to make your own pcb's a range of etching systems including the novel etch-in-a-bag system, plus printed circuit transfers for the professional finish to your boards.



9-CHANNEL RADIO CONTROL SYSTEM


A comprehensive model control system, featuring nine independent fully proportional channels achieved by a design using very few components thus keeping the cost to a minimum. Full construction details in our booklet (XF03D)

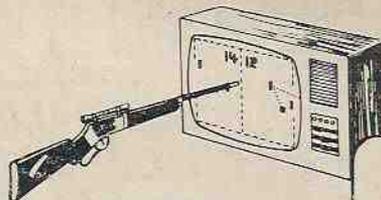price £1.20.
(All prices include V.A.T. and p & p).



T.V. GAME

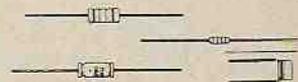A fascinating TV game kit that plays football, tennis, squash and practice for only £21.59. Reprint of construction details 25p. Add on rifle kit only £10.60. (All prices include V.A.T. and p&p).



MASSIVE RANGE OF COMPONENTS

For instance the capacitor section in our catalogue includes non-polarised electrolytics and our resistor section includes even 1% tolerance types. Get our fascinating catalogue now—you won't regret it.



AUDIO MIXER

A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape-recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request.




ELECTRONIC ORGAN

The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument. We haven't got the gimmicks yet—they're coming soon) but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



MICROPROCESSOR

Build a mini-computer with our microprocessor kit. Features: 40 different instruction types; 256 bytes of read/write memory (more are easily added) microprocessor can address up to 65,536 8 bit-bytes. Complete kit for use with teletype etc. (XB91Y) £68.74
20-key keyboard for use with above (in place of teletype) (XB92A) £65.97 Both kits with detailed instruction books. See our newsletters for details of additional RAM's, tri-state interfacing chips, number-cruncher and standard cassette tape-recorder interface to store your programmes. (All prices include V.A.T. and p&p).

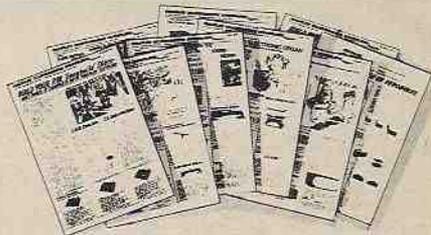

Our bi-monthly newsletter keeps you up to date with latest guaranteed prices — our latest special offers — details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).



POST THIS COUPON NOW FOR YOUR COPY OF OUR 1979-80 CATALOGUE PRICE 75p

Please rush me a copy of your 280 page catalogue as soon as it is published (8th January, 1979). I enclose 75p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately.

NAME _____

ADDRESS _____

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 715157