

Easy to build projects for everyone

# Everyday ELECTRONICS


APRIL 79

40p

KIOSKE KIOSKE KIOSKS

McLeod

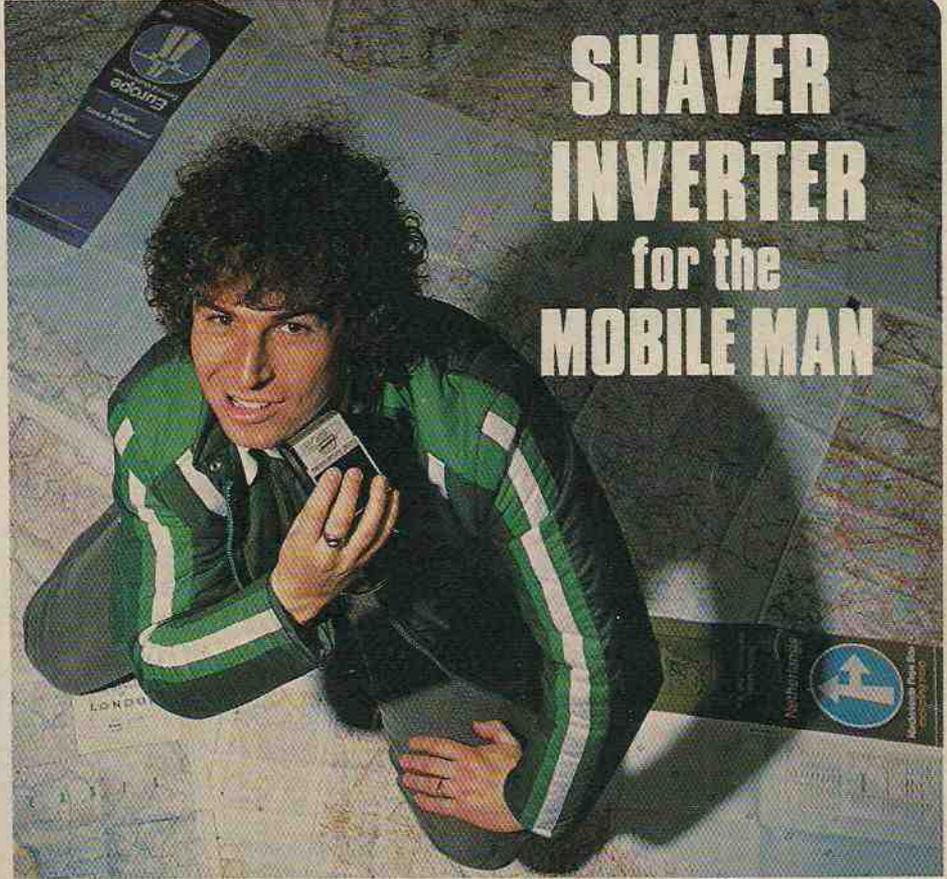**FREE**  
ENTRY  
COMPETITION  
**25 ANTEX**  
KITS & IRONS  
TO BE WON



**SHAVER  
INVERTER**  
for the  
**MOBILE MAN**

**TOUCH  
BLEEPER**

**TRANSISTOR  
TESTER**

**CHOKE**



**WARNING DEVICE**

# Iron out the little problems...



Model TCSU1 Soldering Station



CTC 35 watt



The TCSU1 soldering station with the XTC50 watt—24/26 volt soldering iron or the CTC 35 watt—soldering iron for pin point precision and exceptionally fast recovery time. We have put at least twice as much power into irons which are already well known for good recovery time. The temperature control stops them from over-heating; the 'fail-safe' electronic circuit provides protection even if the thermocouple fails. TCSU1 soldering station with XTC or CTC iron £38.88 inclusive of VAT postage extra.

Model SK3 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at £6.21 inclusive of VAT and P&P. It makes an excellent present for the radio amateur, modelmaker or hobbyist.

Model SK4 Kit



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at £6.21 inclusive of VAT and P&P.

Model CX 17 watts

(illustrated)



a miniature iron with the element enclosed first in a ceramic shaft then in a stainless steel. Virtually leak-free. Only 7 1/2" long. Fitted with a 3/32" bit £4.37 inclusive of VAT and P&P. Range of 5 other bits available from 1/4" down to 3/64"

Model X25 - 25 watts




A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near perfect insulation. Fitted with 1/8" bit and priced at £4.37 inclusive of VAT and P&P. Range of 4 other bits available.

Model MLX Kit



The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope—it can be left in a car, a boat or a caravan ready for soldering in the field. Price £4.83 inclusive of VAT and P&P.

Model SK1 Kit

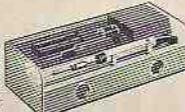

This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet 'How to solder'. Priced at £6.48 inclusive of VAT and P&P.

## ...with Antex

The ANTEX multi purpose range of soldering equipment is fast becoming a must for every home. Built with precision for long life, each iron is fully tested and guaranteed.

ANTEX soldering irons are made in England to strict local and international standards of safety.

Our name for reliability is spreading from all over Europe to U.S.A. to Japan and to many other countries.

Stocked by many wholesalers and retailers or direct from us if you are desperate.



Mayflower House, Armada Way,  
Plymouth, Devon.  
Tel: 0752 67377/8  
Telex: 45296

Please send me the Antex colour brochure  I enclose cheque/P.O. Order No. 258 1000

Please send the following

Name \_\_\_\_\_ Address \_\_\_\_\_

Antex Ltd, Freeport, Plymouth PL1 1BR Tel. 0752 67377 EE 4.79



# MAGENTA ELECTRONICS LTD

EC3, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS DE13 0UL  
PHONE 02 83 65435. 9 a.m.-12. 2 p.m. 5. MON.-FRI.

ALL PRICES INCLUDE VAT AND FIRST CLASS  
POST. ADD 25p TO ORDERS UNDER £5. EE  
ARTICLE REPRINTS 39p EACH.  
MAIL ORDER ONLY.  
CATALOGUE - SEND 4 9p STAMPS.



## E.E. PROJECT KITS

Make us YOUR No. 1 SUPPLIER of KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Appropriate hardware—nuts, screws, I.C. sockets are included. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply—You construct.  
PRICES INCLUDE CASES UNLESS OTHERWISE STATED.  
ARTICLE REPRINTS EXTRA 39p EACH.

**CHOKE WARNING DEVICE**, Feb. 79. £5.05 case 71p.  
**AUDIO MODULATOR**, Feb. 79. £1.44 less case and pins.  
**LW CONVERTER**, Feb. 79. £3.98, case £1.26.  
**THYRISTOR TESTER**, Feb. 79. £2.08  
**ADJUSTABLE PSU**, Feb. 79. £21.54. Case (horizontal layout) £3.54 extra.  
**ROULETTE**, Jan. 79. £16.99 less case.  
**I'M FIRST**, Jan. 79. £3.06 less cases.  
**LIGHTS REMINDER**, Jan. 79. £4.05  
**CONTINUITY TESTER**, Jan. 79. £2.91 less case.  
**MIC AMP**, Dec. 78. £2.19  
**FUZZ BOX**, Dec. 78. £4.36  
**VEHICLE IMMOBILISER**, Inc. PCB, Dec. 78. £3.77 case extra 71p.  
**WATER LEVEL ALERT**, Nov. 78. £4.82  
"HOT LINE" GAME, Nov. 78. £4.23 less case & rod.  
**AUDIO EFFECTS OSCILLATOR**, Nov. 78. £2.75 inc. board.  
**SUBSCRIBERS TELE METER**, Nov. 78. £19.55 case extra £3.75.  
**FUSE CHECKER**, Oct. 78. £1.40.  
**C.MOS RADIO**, Oct. 78. £7.55.  
**TREASURE HUNTER**, Oct. 78. £14.20 less handle & coil former.  
**GUITAR TONE BOOSTER**, Sept. 78. £4.13 inc. p.c.b.  
**SOUND TO LIGHT**, Sept. 78. £5.77  
**FILTER**, £1.25.  
**SLAVE FLASH**, Aug. 78. £2.66 less SK1.  
**LOGIC PROBE**, July 78. £2.99  
**IN SITU TRANSISTOR TESTER**, June 78. £4.49.  
**VISUAL CONTINUITY CHECKER**, June 78. £2.96 inc. probes.  
**FLASHMETER**, May 78. £10.99. less calc and diffuser.  
**POCKET TIMER**, April 78. £2.82  
**WEIRD SOUND EFFECTS GENERATOR**, Mar. 78. £3.64.  
**CHASER LIGHT DISPLAY**, Feb. 78. £19.78. inc. p.c.b. case extra £3.54.  
**AUDIO VISUAL METRONOME**, Jan. 79. £4.22.  
**RAPID DIODE CHECK**, Jan. 78. £1.97  
**AUTOMATIC PHASE BOX**, Dec. 77. £9.45 inc. p.c.b.  
**VHF RADIO**, Nov. 77. £11.46.  
**ULTRASONIC REMOTE CONTROL**, Nov./Dec. 77. £13.64.  
**TREASURE LOCATOR**, Oct. 77. £8.77 case extra. £2.32. Less handle, etc.  
**ELECTRONIC DICE**, March 77. £4.09.  
**SOIL MOISTURE INDICATOR**, June 77. £3.09 inc. probe.  
**PHONE/DOORBELL REPEATER**, July 77. £5.27.  
**SHORT WAVE RECEIVER**, Aug. 77. £10.98 case extra £1.25.  
**CAR BATTERY STATE INDICATOR**, Sept. 78. £1.54 less case inc. PCB.  
**R.F. SIGNAL GENERATOR**, Sept. 78. £15.30 less case.  
**TRANSISTOR TESTER**, Oct. 77. £6.34 case extra £3.35.  
**CATCH-A-LIGHT**, Mar. 78. £5.74.  
**HEADPHONE ENHANCER**, Jan. 79. £2.24.  
**PASSIVE MIXER**, Oct. 78. £2.68.  
**ELECTRONIC TOUCH SWITCH**, Jan. 78. £1.44.  
**AUDIBLE FLASHER**, Dec. 78. £1.08.  
**ADD-ON CAPACITANCE UNIT**, Sept. 77. £4.46.

## TEACH-IN-78

COMPLETE KIT £14.50

INCLUDES FREE COMPONENT IDENTIFICATION CHART. TEACH-IN REPRINTS EXTRA 39p. EACH PART. ALL 12 PARTS AVAILABLE.

## 1979 ELECTRONICS CONSTRUCTORS CATALOGUE

HAVE YOU GOT YOUR COPY YET? MAGENTA'S NEW CATALOGUE INCLUDES MANY NEW PRODUCTS — CAREFULLY CHOSEN FOR EVERYDAY ELECTRONICS READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR CONSTRUCTORS. FULLY INCLUSIVE PRICES RIGHT NEXT TO THE PRODUCTS MAKE ORDERING EASY. NO MINIMUM ORDER — ALL PRODUCTS STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE!

WRITE TODAY ENCLOSING 4 x 9p STAMPS.

**BUZZER**, 6V 74p. 12V 77p.  
**F.M. INDOOR AERIAL**, 49p.  
**TELEPHONE PICK-UP COIL**, 65p.  
**SPEAKERS**, Miniature 6 ohm 79p. 64 ohm 89p. 80 ohm £1.15.  
**EARPIECES**, Crystal 38p. Magnetic 15p.  
**STETHOSCOPE ATTACHMENT** fits our earpieces 58p.  
**HEADPHONES, MONO**, 2K Padded Superior Sensitive. £2.98.  
**HEADPHONES, STEREO**, 8 ohm. £3.85.  
**INTERCOM**, 2 STATION, £5.95.  
**MICROPHONE DYNAMIC 600 OHM**  
**CASSETTE TYPE** with 3.5mm jack plug and plastic desk stand. £1.25.  
**MULTIMETER TYPE 1**, 1,000 o.p.v. with probes 2" x 3 1/2" x 1" £5.95.  
**MULTIMETER TYPE 2**, 20,000 o.p.v. with case and probes 5" x 3 1/2" x 1 1/2" £12.45.  
**ANTEX X25 SOLDERING IRON 25W**. Ideal for electronics £3.95.  
**SOLDERING IRON STAND**. ANTEX ST3 £1.84.  
**DESOLDER BRAID**, 52p.  
**HEAT SINK TWEEZERS**, 13p.  
**DESOLDER PUMP**, Easy to use £5.98.  
**SIGNAL INJECTOR**, £4.98.  
**DENTISTS MIRROR**, Adjustable £2.15.  
**JEWELLERS EYEGLASS**, 93p.  
**TRIPLE MAGNIFIER**, £1.48.  
**SPRINGS—SMALL** 100 Assd. 98p.  
**CROC CLIP TEST LEAD SET** 10 leads with 20 clips 96p.

## DOING IT DIGITALLY

New Series—complete kit or separate parts **IN STOCK NOW** for **FAST DELIVERY** by **FIRST CLASS POST**. All top quality components as specified by Everyday Electronics. Our kit comes complete with **FREE TTL** and **COMPONENT IDENTIFICATION CHART**. Follow this educational series—start today—and learn about digital electronics. SEND £22.95 for the TTL TEST BED. £3.75 for **ADDITIONAL COMPONENTS** (6 months).

TRAIN AT HOME

# Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future.

Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course—or refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

Courses in  
C & G Elect. Technicians  
C & G Elect. Installations  
Telecomms. Technicians Exams  
Television Servicing  
Radio Maint. & Repairs (BIET)  
Pract. Radio & Electronics  
Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept. TEE42 Reading RG7 4PF.

NAME (Block capitals please) \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_


Other Subjects \_\_\_\_\_

AGE \_\_\_\_\_

Accredited by CACC

Member of ABCC

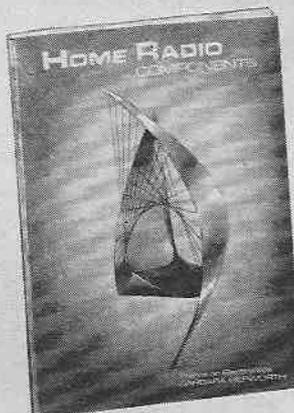SOLVE your component buying problems with this famous Catalogue



- The finest components catalogue yet published.
- Over 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Nearly 1,000 illustrations.
- Bargain list sent free.
- At £1.25 incl. p. & p. the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD., Dept. EE, 234-240 London Road, Mitcham, Surrey CR4 3HD

POST THIS COUPON with cheque or P.O. for £1.25

Please write your Name and Address in block capitals


NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

HOME RADIO (Components) LTD., Dept. EE  
234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No London 912966)




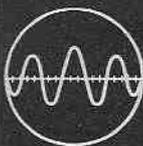

# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING  
CONTROL SYSTEMS

## NEW FROM TUAC

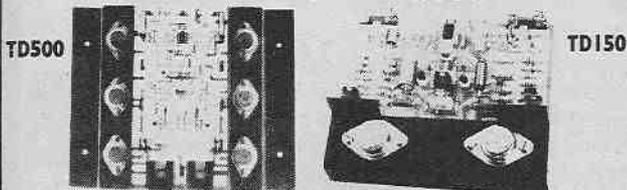

### 7" x 9" x 1 3/4" ULTRA QUALITY HIGH POWER 5" x 5" x 2" New D.C. Coupled Design AMPLIFIERS

**Featuring**—Electronic Short-Open and Thermal Overload Protection.  
**Brief Spec.**—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms.  
Frequency Response 20 Hz - 20 KHz. T.H.D. at full power 0.1%.  
Hum and Noise—100 dB Relative full output.

**T.D. 500** 300W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms. .... **£45.00**  
Power supply P.S.300 ..... **£30.00**

**T.D.150** 150W into 4 Ohms. 100W into 8 Ohms. .... **£26.25**  
Power supply P.S. 150 ..... **£18.50**

**T.D. 150** 60 Version 60W into 8 Ohms. 40W into 15 Ohms. .... **£17.75**  
Power supply P.S.60 ..... **£15.50**

Note—P.S. 300 will drive 2 T.D. 150 amplifiers  
All output ratings are R.M.S. continuous sine wave output.

#### TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD., or quote Access/Barclay Card No. (We accept holders phone orders 01-672 9080).

Post to—

**TUAC LTD., 121 CHARLTON ROAD, LONDON SW 17 9AB.**

Send stamp for our free 36 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.

# ELECTROVALUE

## FOR A GOOD DEAL BETTER THAN MOST

**WE PAY POSTAGE** on C.W.O. orders in U.K. over £5.00 list value. If under, add 27p handling charge.

**WE GIVE DISCOUNTS** on C.W.O. orders—5% on list value over £10.00; 10% on list value over £25.00.

**WE GUARANTEE** all goods are brand new clean and to specification—no seconds, no surplus.

**WE GIVE SERVICE** to all orders large or small—we use microfilm order storage, computer processing and double check personal supervision.

## This month's special offers of ELECTROVALUABLES

Specialist  
Mail Order  
Suppliers  
since 1964

'Electrovaluables' are our own overstocked items offered from time to time at greatly reduced prices. Orders should quote 'Electrovaluables' and description and price as advertised. **PRICES ARE NET AND V.A.T. MUST BE ADDED @ 8% or 12 1/2% where prices show**

### CAPACITORS

- Ceramic** B37448 40V .022 100 for £2
- Disc** .02 (professional)
- Lacquer film** 4 for £1
- Siemens B32110** 1uF 250V each £1
- B32120** 4-7uF 160V 10uF 63V each £1.50
- Polystyrene Siemens** 4 for £1
- B31110** .7uF, 150, 200, 500pF (160V) 820pF (63V) any 100 for £2
- B31310** 4700pF (63V) 100 for £2.50
- Polypropylene Siemens** 220/100, 2200/3 2200/10 any 10 for £1
- B53063** 100, 470, 2200, 4700, 5100, 100, 10000 pF any 100 for £4.00
- 8900**, 10000 pF any 100 for £4.00
- Polyester Siemens B32231** .047 axial lead .033/400, .047/250, .15/250, .39/250 any 15 for £1
- 82/250**
- High voltage polyester** 1KV Siemens B32227 0.25uF each 30p
- Polyester PC Mounting** 0.68/250V Siemens B32234 each 10p
- Mullard 344 series** .047/100 5p
- Polycarbonate Siemens B32551** PC mounting 10mm 0.015, 0.022, 0.047, 0.055, any 100 £2
- Electrolytic cans by Daly** each 40p, 55p, 85p, £1.20
- 1000uF 50V** each £1
- 1000uF 100V** each £1.50
- 2200uF 100V** each £1.50
- Electrolytic pluggable** Siemens B41316 2.2/63, 22/63, any 25 for £1.25
- 220/3** each 12p
- 100/63** any 20 for £1
- 22/100, 47/3, 47/100, 100/3** any 20 for £1
- 220/100, 2200/3 2200/10** any 10 for £1
- Miscellaneous, mostly Mul-** lard 016 10/63, 22/63, 47/140, 220/25, 470/10, any 20 for £1
- Tantalum Siemens B45134** 10 for 50p
- Veroboard 5" x 3.4" x .2"** 20p
- matrix**
- Transformer cores** 0.5W 50Hz Unisil, Belclere Kit ES 20p
- Rocker switches 15A 250V** 25p
- DPST No 30A**
- DPDT No 50D centre-off** 25p

## WE ARE NATIONAL DISTRIBUTORS FOR



**NASCOM MICROCOMPUTER KITS**  
for delivery from stock from £185.00 net + V.A.T.  
Also full range of supporting Nascom items. Enquiries invited.  
Leaflet on request.

**MOTOROLA D.2. MICROPROCESSOR EVALUATION KIT** (for the M.680 Microcomputer—£175.87 net + V.A.T.)

## CATALOGUE 9

**YOURS FOR THE ASKING**—Write, phone or call.

Completely revised and up-dated 120 pages semi-conductors, I.C.s, Opto-electronics, Rs, Cs, etc. etc. And you'll be delighted with our three-month stabilised price list.



## ELECTROVALUE LTD

28 ST. JUDES ROAD, ENGLEFIELD GREEN,  
EGHAM, SURREY TW20 0HB

Telephone Egham 3603 Telex 264475

Northern Branch—680 BURNAGE LANE,

BURNAGE, MANCHESTER M19 1NA (061) 432 4945



## ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.  
Bound in stiff linen. Cover size 8 1/2 in x 5 in.  
Price £7.50 per set (we pay the postage).

- Book 1. Introducing Electronics
- Book 2. Resistors/Capacitors
- Book 3. Inductors/Diodes
- Book 4. Meters/Voltage-dividers
- Book 5. Transistor Project Circuitry

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order now:  
Selray Book Company  
60 Hayes Hill  
Bromley  
BR2 7HP

### OUR 100% GUARANTEE

Should you decide to return the set after 10 days examination, your money will be refunded by return of post.


Amount enclosed: £

Name:


Address:

EE15

# The professional scopes you've always needed.

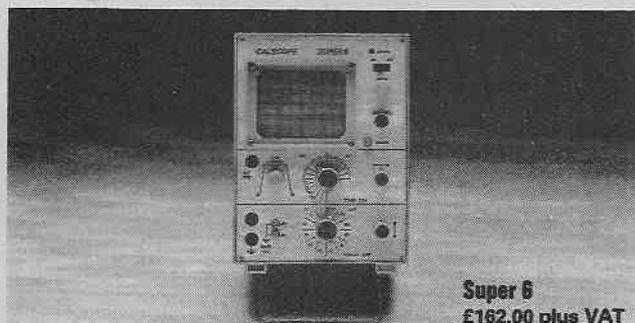

**Super 6**  
£162.00 plus VAT

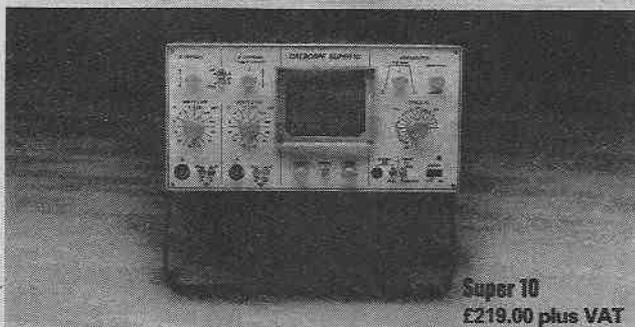

**Super 10**  
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

Prices correct at time of going to Press.

## CALSCOPE DISTRIBUTED BY

**Marshalls Electronic Components,**  
Kingsgate House,  
Kingsgate Place,  
London, N.W.6.

**Audio Electronics,**  
301 Edgware Road, London W.2.  
Tel: 01-724 3564

Access and Barclay card facilities  
(Personal Shoppers)

**Watford Electronics,**  
33-35 Cardiff Road,  
Watford, Herts.  
Tel: 0923 40588

**Maplin Electronics Supplies Ltd.**  
P.O. Box 3  
Rayleigh, Essex.  
Tel: 0702 715 155  
Mail Order

# CALSCOPE

## TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

**City and Guilds Certificates:**  
Telecommunications Technicians  
Radio, TV, Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
MPT Radio Communications Certificate

**Diploma Courses:**  
Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV, Audio Engineering and Servicing  
Electrical Engineering, Installation  
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

**ICS To: International Correspondence  
Schools**

Dept F268 Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest .....

Name .....

Address .....

Tel: ..... Age: .....

Semi-conductors	R2008B/10B*	TTL	Bargain Paks	A19 2x BD695A or 6A
AC176/187	18 TIP29/30*	39 7400	11 Pak No. All full spec.	A20 3x BF180, 1 or 5
AU110*	173 TIP31A	39 7401	12 A1 5x741 8 pin	90
BC107/8/9	8 TIP32A	46 7404	11 A2 4x855 8 pin	100 *A21 5x BF180
BC147/8/9	8 TIP41	41 7405	10 *A3 25x AA119	75 A22 4x BF324
BC157/8/9*	9 TIP42A	82 7408	13 A4 5x AC128	75 *A23 4x BFR80
BCY70/1/2	14 ZTX301/2*	12 7409	13 A5 3x AD161 or 162	A24 5x BFY50 or 52
BD131/2	34 IN4001/2	5 7420	12 *A6 25x BAX13	70 A25 5x B5 x19 or 20
BD135/6/7	35 IN4004/5	6 7427	23 *A7 5x BB105A or 5	70 *A26 10x BY127
BD138/9/40	38 IN4006/7	7 7430	11 *A8 5x BC117 or 118	A27 3x C106D
BF115	18 2N706	12 7440	62 *A9 10x BC132	90
BF167*	23 2N1304/6	40 7445	22 *A10 10x BC147, 8 or 24	90 A29 5x 2N930
BF180/1/4	28 2N1305	30 7472	24 9	70 *A30 10x 2N3702, 3, 4
BF194/5	9 2N3053	20 7474	62 *A11 10x BC172	65
BF197*	10 2N3054	46 7474	96 *A12 10x BC182, 3 or 6	*A31 10x1 Megohm preset 0-25W
BF200	28 2N3055	46 7474	68 4	70
BF237/8/9	26 2N3319	21 7480	32 A13 10x BC204B	A32 50x mixed W/W resistors
BF335*	32 2N4443	60 7482	45 cropped leads	50 2-5W, 5W, 10W, etc.
BF337*	28	7483	50 4	70
BT106*	110 Linear I.C.'s	7490	23 A15 5x BC301 or 303	*A33 50x 2-5W W/W resistors
BU205*	150 741 8 pin	19 7491	23 A16 10x BC547, 8 or 74	90
BU208	160 555 8 pin	27 7495	49 A17 10x BCY70	110 A35 50x 74 series with preformed pins
BU208A	175 LM3900N	60 7498	50 A18 3x BD115	110
MJE340	43 78003N*	170 74107	OC28	88 78033N*
MJE320	43 78013N*	130 74121	OC28	78 TBA750*
OA200*	7 78023N*	130 74123	OC28	78 TBA800*
OC28	88 78033N*	170 74128	OC28	78 TBA8105*
OC28	78 TBA750*	160 74151	OC28	78 TBA8105*
OC140/202	82 TBA800*	89 74155	OC28	78 TBA8105*
OC140	72 TBA8105*	100 74157	OC28	78 TBA8105*

Min. order £2.00 P & P 30p. VAT—please add 8% except those marked \* which are 12.5%. S.A.E. for lists. Wholesale and Industrial enquiries welcome.  
**K & A DISTRIBUTORS, 52 Barkby Road, Syston, Leicester, LE17 8AF. Tel: 0533 606931**

### SINCLAIR PRODUCTS

Microvision TV UK model £89.95.  
PDM35 £27.25. Mains Adaptor £3.24.  
Case £3.25. DM350 £67.80, DM450  
£89.50, DM235 £49.45. Rechargeable  
batter £7.50. Mains adaptor £3.70. Enter-  
prise prog calculator £24.95. Cambridge  
prog calculator £12.15. Prog library  
£4.45. Mains adaptor £3.20.

### COMPONENTS

Send see for full list. 1 lb FeCl £1.95.  
Dallo pen 79p. 60 sq ins pcb 55p.  
Laminite cutter 75p. Small drill 20p.  
2N414 £1.95. Pcb and extra parts for  
radio £3.85. Case £1. IN4148 1.4p.  
IN4002 2-9p. 723 28p. 741 15p. NE555 23p.  
BC182b, bc183b, bc184b, bc212b, bc213b,  
bc214c 4-9p. Plastic equiv bc107 4-8p.  
1W 5%. £12 resistors 10R to 10M 1p.  
0-8p for 50+ of one value. Electrolytics  
16v .5/12/5/10 22mf 5p, 100mf 6p, 1000mf  
10p, 1500mf (PC) 3-4p, 10v 2mf 1-7p.

### T-DEC AND CSC PRODUCTS

S-dec £3.17, I-dec £4.92, u-deca £4.40,  
u-decb £5.73. 16 dii adaptor £2.14,  
Exp300 £6.21, exp350 £3.40. Exp 650  
£3.89. Exp 4b £2.48.

### TV GAMES

Send see for data. AY-3-8500 + kit  
£8.95. Rifle kit £4.95. AY-3-8600 + kit  
£12.50. Stunt cycle chip + kit £10.90.  
Tank batteries chip + kit £13.95.

### TRANSFORMERS

6-0-6v 100ma 74p, 1 1/2 £2.35. 6-3v 1 1/2  
£1.80. 9-0-9v 75ma 74p, 1a £2.2a, 2a £2.60.  
12-0-12v 100ma 90p, 1a £2.49.

### IC AUDIO AMPS

with pcb. JCI2 6W £1.60. JC20 10W  
£2.95. Send see for data.

### BATTERY ELIMINATORS

3-way type 6/7/9v 300ma £2.95. 100ma  
radio type with press-studs 9v £3.35,  
9+9v £4.50. Stabilized type 3/6/7/9v  
400ma £5.30. 12v car converters 3 1/2/6/7/9v  
800ma £2.50.

### BATTERY ELIMINATOR KITS

Send see for data. 100ma radio types  
with press-studs 4 1/2v £1.40, 6v £1.40,  
9v £1.40, 4 1/2+4 1/2v £1.80, 6+6v £1.80,  
9+9v £1.80. Stabilized 8-way types  
3 1/2/6/7/9/12/15/18v 100ma £2.80, 1amp  
£6.40. Stabilized power kits 2-18v  
100ma £3.80, 2-30v 1A £6.95, 2-30v 2a  
£10.95. 12v car converter 6/7 1/2v 1a  
£1.35.

### BI-PAK AUDIO MODULES

S450 £23.51. AL60 £4.95. Pa100 £16.95.  
Spm80 £4.47. Bmt 80 £3.95. Stereo  
30 £20.12.

### SWANLEY ELECTRONICS

DEPT. EE, 32 Goldsel Rd., Swanley,  
Kent.  
Post 30p extra. Prices include VAT.

# Marshall's

Head office and mail order to DEPT EE  
A. Marshall (London) Ltd.  
Kingsgate House, Kingsgate Place, London NW6 4TA  
Tel: 01-624-0805 Telex 21492

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 also 325 Edgware Road, W2. Tel: 01-723 4242.  
Glasgow: 85 West Regent Street, G2 2QD Tel: 041-332 4133 and Bristol: 1 Straits Parade, Fishponds Road, BS16 2LX. Tel: 0272 654201.

## LEDS + OPTO

### BY SIEMENS

Displays 7 seg	LEDS	Red	Gr	Yell
Com anode or cath	5mm 3ml	18	19	19
	Extra 5mm	20	20	20
8mm HT	£1.50	Extra	40	40
10mm HT	£1.55	LDZ71	£0.55	
14mm HT	£1.57	lred LDZ71	£1.45	
18mm HT	£1.85	IR receiver	£1.45	
		Opto coupler	£1.55	

Full range + data in our '79 catalogue

## RAACO STORAGE BOXES

Strong durable high impact polystyrene boxes with brass hinge pins.

B5	£1-62	B18	£1-78
----	-------	-----	-------

## LINEAR (See catalogue for full range)

LM339N	0.80	LM1828N	1.90	CA3025	0.70
LM340T-5	0.88	LM1830N	1.90	CA3028A	0.90
LM340T-12	0.88	LM1845N	1.90	CA3028B	1.25
LM340T-15	0.88	LM1848N	1.98	CA3029	0.75
LM340T-24	0.88	LM1850N	1.90	CA3029A	0.90
LM341P-5	0.56	LM1889N	2.50	CA3030	1.50
LM341P-12	0.56	LM1890N P.O.A.	2.20	CA3030A	2.20
LM341P-15	0.56	LM2907N-8	1.80	CA3033	3.75
LM341P-24	0.56	LM2917N-8	1.80	CA3034	2.75
LM345K	6.97	LM3301N	0.60	CA3035	1.95
LM348N	0.95	LM3302N	0.55	CA3036	1.21
LM350K	6.50	LM3401N	0.55	CA3038	2.90
LM358N	0.60	LM3900N	0.88	CA3038A	1.10
LM360N	3.00	LM3905N	1.15	CA3039	0.77
LM370N	3.30	LM3909N	0.78	CA3040	3.75
LM371H	2.38	LM3911N	1.10	CA3041	1.65
LM373N	3.35	LM3913N P.O.A.	CA3042	1.65	
LM374N	3.35	LM3914N	2.79	CA3043	2.20
LM377N	1.60	LM4250CN	0.58	CA3045	1.55
LM378N	2.40	LM78105CH	0.55	CA3046	0.77
LM379S	4.25	LM7812CH	0.85	CA3047	2.20
LM380N-8	0.96	LM7815CH	0.85	CA3047A	3.70
LM380N-14	1.08	LM78124CH	0.85	CA3048	2.45
LM381AN	2.70	LM7805KC	1.56	CA3049	1.98
LM381N	1.60	LM7810KC	1.56	CA3050	1.10
LM382N	1.32	LM7815KC	1.56	CA3051	1.82
LM384N	1.55	LM7824KC	1.56	CA3052	1.78
LM388N	0.88	LM78105CZ	0.30	CA3053	0.77
LM387N	1.10	LM7812CZ	0.30	CA3054	1.10
LM388N	1.00	LM7815CZ	0.30	CA3059	2.10
LM389N	1.00	LM78124CZ	0.30	CA3062	2.50
LM392N	0.87	MC68	0.82	CA3062	3.75
LM7018	2.99	MC671P	1.75	CA3064	1.10
LM701C	2.99	MC672P	1.75	CA3065	1.10
LM702C	0.81	MC724P	2.10	CA3066	3.80
LM703LN	1.15	MC789P	1.80	CA3070	1.90
LM709CH	0.70	MC790P	1.80	CA3071	1.90
LM709-8	0.50	MC798P	2.20	CA3072	1.90
LM709-14	0.49	MC799P	2.20	CA3075	1.70
LM710CH	0.87	MC832P	0.70	CA3076	2.12
LM710-14	0.48	MC833P	0.70	CA3080	0.85
LM711CN	0.48	MC836P	0.82	CA3080A	2.10
LM716	1.00	MC837P	0.82	CA3085	0.50
LM723CH	0.62	MC838P	2.35	CA3088F	0.87
LM723C-14	0.45	MC840P	1.65	CA3089E	2.90
LM741CH	0.50	MC844P	0.70	CA3090C	4.40
LM741C-8	0.30	MC846P	0.70	CA3130	1.06
LM741C-14	0.60	MC848P	1.10	CA3140	1.06
LM747CN	1.78	MC925P	0.80	LF3571	0.80
LM746-8	0.50	MC957P	0.85	LF358N	0.80
LM746-14	0.50	MC961P	0.85	LF359N	0.80
LM900	0.50	MC1035P	1.90	LF3201N	3.00
LM911	0.50	CA3000	3.30	LF13331N	3.00
LM921	0.50	CA3001	4.25	LF13332N	3.00
LM923	0.50	CA3002	4.50	LF13741N	3.75
LM1303N	1.15	CA3006	4.60	LF1144H	0.38
LM1304N	1.52	CA3007	4.15	LM1144H	2.75
LM1305N	1.02	CA3008	2.55	LM301A.H	0.40
LM1307N	1.22	CA3012	1.65	LM301-8	0.30
LM1310N	2.10	CA3013	1.85	LM804H	1.50
LM1312N	1.00	CA3014	1.85	LM805H	1.50
LM1458N	0.45	CA3018	0.75	LM806H	0.95
LM1496N	0.97	CA3018A	1.10	LM308N	0.55
LM1800N	1.94	CA3020	2.26	LM309KC	1.85
LM1801N	2.25	CA3020A	2.50	LM317K	3.35
LM1808N	2.10	CA3021	2.40	LM817MP	1.35
LM1812N	1.80	CA3022	2.20	LM317T	2.20
LM1820N	1.18	CA3023	2.20	LM318N	2.45

## MEMORIES (see catalogue for full range)

MM2708Q	8.00	MM88C30N	2.08	TMS4043-2NL	2.88	TMS9903NL	13.74
MM5204Q	9.00	MM5314N	4.47	TMS4044-20NL	8.85	TMS9904	P.O.A.
MM5303N	8.83	MM57105N	10.43	TMS4045-20NL	8.85	TMS9905	P.O.A.
MM5307AA/N13	65	MM57109N	13.41	TMS4050-2NL	6.48	ADC0817CCN	
MM5314	4.60	MM57161N	6.71	TMS4060-2NL	6.48	ADC3511CCN	8.30
MM5316	4.60	MM57160N	6.71	TMS4116-25JL		ADC3711CCN	9.35
MM5330N	4.20	TMS2716JL	19.50			ADD3501CCN	8.30
MM80C95N	0.58	TMS4027-25NL				ADD3701CCN	9.35
MM80C96N	0.66					AY2515	8.75
MM80C97N	0.58	TMS4033NL	6.10	TMS4164NL P.O.A.		AY3-8500	5.50
MM80C98N	0.66	TMS4036-2NL	3.28	TMS9900JL	44.41	AY-3-8710	12.75
MM82C19N	2.90	TMS4039-2NL	2.78	TMS9901NL	10.66	SFF77301A	8.95
MM82C29N	2.08	TMS4042-2NL	2.98	TMS9902NL	9.16	SFF96364	16.00

## CMOS (see catalogue for full range)

74C00N	0.24	74C48N	1.38	74C95N	1.04	CD4000	0.20	CD4013B	0.52
74C02N	0.24	74C75N	0.54	74C107N	1.22	CD4019B	0.20	CD4014	1.00
74C04N	0.24	74C74N	0.55	74C150N	4.14	CD4002	0.18	CD4015	0.75
74C08N	0.24	74C78N	0.54	74C151N	2.47	CD4006	1.25	CD4018	0.32
74C10N	0.24	74C83N	1.30	74C154N	3.68	CD4007	0.18	CD4017B	1.05
74C14N	0.95	74C85N	1.30	74C157N	2.21	CD4008B	0.99	CD4918B	1.05
74C20N	0.24	74C86N	0.54	74C160N	1.11	CD4009	0.58	CD4019B	0.52
74C30N	0.24	74C89N	4.39	74C161N	1.11	CD4910	0.58	CD4902B	1.15
74C32N	0.24	74C90N	0.85	74C162N	1.11	CD4011B	0.20	CD4021	1.05
74C42N	0.92	74C93N	0.85	74C163N	1.11	CD4012	0.20	CD4022B	1.00

## NEW 1979 CATALOGUE

48 page catalogue—new enlarged micro section—large range of quality components from franchised suppliers available in UK. All VAT inclusive prices. Over 8,000 line items plus lots more. 45p post paid or 35p to callers at any of our four branches.

**★ MAIL ORDER ★**  
Quick service on all orders—please add 40p for p/p to all orders. Telephone orders on credit cards £10.00 minimum.

Buy it with Access


Credit cards welcome

## PORTABLE DIGITAL MULT-TESTERS (complete with charger)

Mains/battery operated c.w. rechargeable Nicad batteries plus charger. Measures DC-AC Volts, ohms and current. Large LED display, guaranteed one year. Ranges: Volts DC and AC 0-1, 10, 100, 1000 Volts. Case optional £8-75 extra.

NEW LOW PRICES LM3A £70.00, LM3-5A £90.00 (3 digit 1% Acc.) (3 1/2 digit 0.5% Acc.)

## DIGITAL ALARM CLOCK MODULES

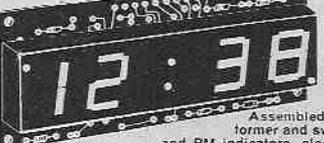

Assembled and pre-tested, just add transformer and switches. Features include alarm and PM indicators, sleep, snooze timers and variable brightness.

5" digits	12hr £9.60	84" digits	12hr £8.50
	24hr £6.60		24hr £8.50

## TRIACS

POWER PRICES AT UNBEATABLE PRICES	TYPE	RATING	CASE	PRICE
TIC206D	Plastic TO86	400v	4A	£0.50
TIC225D	Plastic TO86	400v	6A	£0.70
TIC235D	Plastic TO86	400v	12A	£1.00
TIC236D	Plastic TO86	400v	12A	£1.00
TIC245D	Plastic TO86	400v	16A	£1.21
TIC253D	Plastic TO3	400v	20A	£1.87
TIC263D	Plastic TO3	400v	25A	£2.20
40579				£1.30
40579				£1.30
40842				£1.25
2N4444				£1.95

## THYRISTORS

TYPE	RATING	CASE	PRICE
TIC44+	0-6A 30v	TO18	£0.30
TIC48+	0-6A 100v	TO18	£0.50
TIC477	0-6A 200v	TO18	£0.60
2N5060	0-5A 25v	TO18	£0.32
2N5061	0-5A 50v	TO18	£0.33
2N5062	0-5A 100v	TO18	£0.40
2N5063	0-5A 150v	TO18	£0.43
2N5064	0-5A 200v	TO18	£0.45
BS180246	4-7A 700v	Plastic Mounting	£1.48
BT120 (XK3139/3156/3132)			£1.10
BT121 (XK3134)			£1.10

## TTL (see catalogue for full range)

SN74H05N	0.60	74LS63N	1.25	74LS183N	2.70
SN74H10N	0.56	74LS73N	0.42	74LS189N	3.74
SN74H11N	0.55	74LS74N	0.42	74LS190N	1.00
SN74H20N	0.55	74LS75N	0.58	74LS191N	1.00
SN74H21N	0.55	74LS76N	0.42	74LS192N	0.95
SN74H22N	0.55	74LS78N	0.42	74LS193N	0.95
SN74H40N	0.55	74LS83AN	0.90	74LS194N	0.70
SN74H53N	0.55	74LS85N	0.95	74LS195N	0.70
SN74H54N	0.56	74LS86N	0.44	74LS196N	0.80
SN74H55N	0.55	74LS90N	0.84	74LS197N	0.80
SN74H62N	0.55	74LS91N	1.20	74LS221N	0.80
SN74H65N	0.55	74LS92N	0.70	74LS240N	1.50
SN74H66N	0.55	74LS93N	0.64	74LS241N	1.50
SN74L00N	0.55	74LS95AN	0.90	74LS242N	1.25
SN74L02N	0.56	74LS96N	1.35	74LS243N	1.25
SN74L04N	0.60	74LS107N	0.42	74LS244N	1.50
SN74L47N	3.10	74LS109N	0.42	74LS245N	1.65
SN74L74N	0.90	74LS112N	0.42	74LS247N	1.89
SN74L83N	2.30	74LS113N	0.42	74LS248N	1.09
SN74L85N	2.30	74LS114N	0.42	74LS249N	1.09
74LS00N	0.26	74LS122N	0.82	74LS251N	1.00
74LS01N	0.28	74LS123N	0.83	74LS253N	1.00
74LS02N	0.26	74LS124N	1.70	74LS257N	1.00
74LS03N	0.26	74LS125N	0.60	74LS258N	1.00
74LS05N	0.29	74LS132N	0.85	74LS261N	3.25
74LS06N	0.26	74LS136N	0.42	74LS266N	0.44
74LS09N	0.26	74LS138N	0.65	74LS273N	1.30
74LS10N	0.26	74LS139N	0.65	74LS275N	3.20
74LS11N	0.26	74LS145N	1.30	74LS279N	0.58
74LS12N	0.26	74LS147N	0.65	74LS280N	1.65
74LS13N	0.58	74LS148N	1.35	74LS283N	2.10
74LS14N	0.75	74LS151N	0.58	74LS289N	3.74
74LS15N	0.26	74LS153N	0.58	74LS290N	1.00
74LS20N	0.26	74LS154N	1.45	74LS293N	1.00
74LS21N	0.26	74LS155N	0.90	74LS295N	1.35
74					

# NEW PRODUCTS AND LOWER PRICES!!

FROM TIMETRON Recommended by TEMPUS

**NEW**


## THE INCREDIBLE AQ 2000 Universal calendar watch

LC Display of hours, minutes, seconds, am/pm, full calendar display of day, date & every Sunday. Also digital date, month, year, with day, Sundays. Three date memories. Two independent alarms with hold and recall. Countdown alarm/timer or Time Memory (24hr), or 1/10th second stopwatch. Will display any monthly calendar from 1901 to 2099. Memorises and displays three optional important dates. Calculator with full memory, %, K, √. Battery life approx. 1 year. 1 1/2 x 2 1/4 x 4 1/2 ins. Leatherette wallet.



RRP £29.95 An incredible £24.95

**NEW**

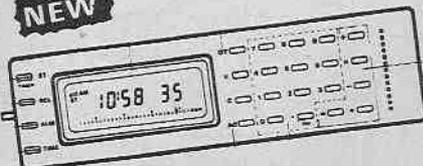

### MQ-10

Specification as AQ-2000 but in 1 1/2 x 4 1/2 x 1 1/2 ins. case with sensor touch keys. Complete with pouch and neck chain. (£39.95).


£35.95

MQ-11. As above but Sensor touch keys. 1 1/2 x 2 1/4 x 3 1/2 ins. Leatherette wallet with window. (£34.95).

£29.95

**NEW**
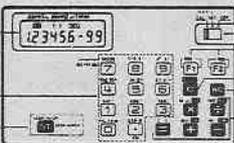
## MINI CARD SCIENTIFIC CALCULATING ALARM CLOCK AND STOPWATCH FX-58



Two alarms, count-down alarm timer. Stopwatch measuring net times to 1/10th sec. Calculator with full memory, Logs, trigs, pi, sexagesimal to decimal conversion, two levels of parenthesis etc. 1 1/2 x 3 1/4 x 2 1/2 inches.

RRP £29.95 £24.95

**NEW**

## LCD SCIENTIFIC CALCULATOR COLLEGE FX-80

Approx. 4000 hours continuous use from 2 AA size batteries. Trigs, logs, exponentiations etc. Statistical—standard deviations. Polar to rectangular and R-P. Sexagesimal to decimal conversion. Engineering key, pi, cube root, 6 levels of parenthesis. Full memory 1 1/2 x 3 x 5 1/2 inches. RRP £21.95.



£16.95

Other LCD scientifics: FX-48 £14.95 FX-2500 £21.95 FX-3100 £25.95 FX-8000 £29.95. CQ-81 £14.95. CQ-82 £19.95 LC-79 £15.95 LC-84 £12.95 HL-801 £9.95 HL-101 £12.95 HL-121 £19.95

**NEW**

## VANICA RADIO AND LCD ALARM CLOCK (Battery powered)



AM/FM Radio Alarm setting, buzzer or radio. Sleep setting, 60 min. switch off. Snooze facility. Night light. Earphone 6 1/2 x 1 1/2 x 3 1/4 ins.

£22.95

Most CASIO products in stock. Send 15p for brochures. Prices include VAT. P. & P. Send cheque, P.O. or phone your Access or Barclaycard no. to:

A well known consumer magazine has published a report on digital watches which supports our conviction that CASIO and SEIKO are probably the best watches in the world, with CASIO offering unbeatable value for money.

All CASIO watches have a calendar display, night illumination, mineral glass and stainless steel cases, water resistant to 100 ft (except sports watches and 50QS—66 feet).

**NOW**

## A QUALITY WATCH FOR UNDER £20

### 50QS-17B

Stopwatch, Dual Time, Water Resistant

Stopwatch measures net times from 1 second to 13 hours. Displays hours, minutes, ten seconds, seconds (by flash), am/pm; And with day, date and month calendar. Water resistant to 66 feet. Stainless steel encased. 8mm thick Mineral glass.



RRP £24.95  
£19.95

## SPORTS WATCHES



### F-100

Left: 9.45mm Was £29.95  
£19.95



### 52QS-14B

Right: 8mm Was £44.95  
£27.95

Up to 25 functions. Net, lap and first and second place times to 1/100th sec. F-100 Resin case, strap 52QS-14B. S/S encased version and bracelet.

## 4 DIGIT WATCH Specification as 50QS-17B

### 31QR-20B

Left: 8.5mm 4 digits Was £35.95  
£22.95



### 54QS-16B

Right: 7.5mm 6 digits Was £49.95  
£29.95



Not illustrated

51QR-19B 6 digits. Round face. Was £44.95 £24.95

51QR-18B 6 digits. Round face. Was £49.95 £26.95

6 DIGIT WATCHES (Not Sports) Hours, minutes, seconds and day of week. (Model 54QS has an optional display of hrs, mins, date, day, ten seconds, seconds by flash). And day, date, month, year calendar. Selectable 12 hour (with am/pm) or 24 hour clock.

## CHRONOGRAPH AND ALARM CHRONOGRAPH



### 45CS-22B

Left: Chrono Was £69.95  
£39.95



### 46CS-27B

Right: A/C 7.8mm Was £89.95  
£74.95

CHRONOGRAPH. 6 digits as above, with stopwatch measuring net, lap and 1st & 2nd place times from 1/100 sec to 6 hrs. Dual time facility. ALARM CHRONO. As chrono above but without dual time 24 hour alarm with optional hourly chime feature.

## THIS MONTHS STAR BUY MULTI ALARM WATCH

### TG-MA (Not Casio)

Alarm, Calendar Alarm, Countdown Alarm/Timer, Dual Time facility LC Display of hours, minutes, seconds, or hours, minutes, date, and day date and month calendar. 24 hour alarm with preliminary beep. Calendar alarm can be set to any day and time in the coming month. Alarm setting at 5 minute intervals. Superb satin finish case, stainless steel fully adjustable bracelet.



£24.95

# YOU'RE RIDING HIGH AND SAFELY...



## with our 8-page DAVE TAYLOR safety supplement

Riding techniques, road sense, preparing your bike for the road, clothing, helmets and much more.

★ Electronic ignition for your bike – the pros and cons to help you decide.

★ "Fault-Finder" – Clutch problems and adjustments for most of the popular bikes.

★ HONDA CBX 1000 Road and Track Test.

★ TRAIL TEST HONDA XL 250 SUZUKI TS 185 FANTIC TRIAL 125

APRIL ISSUE OUT NOW!

# Motorcycling MONTHLY

**TIMETRON**  
Callers welcome by appointment

Dept EE, Beamont Suite, 164-167 East Road, Cambridge CBI 1DB Telephone 0223 67503

# 15-240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (Mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all i.l.p. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

**APPLICATIONS:** Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; input Impedance 4-7k $\Omega$  at 1kHz.


**OUTPUTS:** Tape 100mV; Main output 500mV R.M.S.

**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz; Bass  $\pm$  at 100Hz.

**DISTORTION:** 0-1% at 1kHz. Signal/Noise Ratio 68dB.

**OVERLOAD:** 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE  $\pm$  16-50V.**

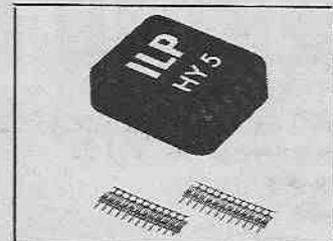**Price  $\pounds$  27 + 78p VAT P&P free.**



## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 5 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

**APPLICATIONS:** Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.


**SPECIFICATIONS:**

**OUTPUT POWER 15W R.M.S. into 8 $\Omega$ ; DISTORTION 0-1% at 1-5W.**

**INPUT SENSITIVITY 500mV. FREQUENCY RESPONSE 10Hz-16kHz—3dB.**

**SUPPLY VOLTAGE  $\pm$  16V.**

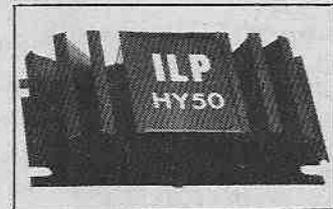**Price  $\pounds$  27 + 78p VAT P&P free.**



## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

**APPLICATIONS:** Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


**SPECIFICATIONS:** INPUT SENSITIVITY 500mV

**OUTPUT POWER 25W RMS into 8 $\Omega$  LOAD IMPEDANCE 4-16 $\Omega$  DISTORTION 0-04% at 25W**

**SIGNAL/NOISE RATIO 75dB FREQUENCY RESPONSE 10Hz-45kHz—3dB.**

**SUPPLY VOLTAGE  $\pm$  25V SIZE 105 50 25mm**

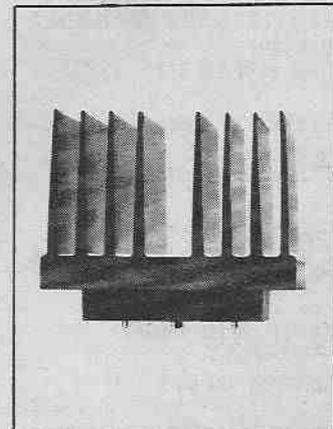**Price  $\pounds$  18 +  $\pounds$  1-02 VAT P&P free**



## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

**APPLICATIONS:** Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

**SPECIFICATIONS**

**INPUT SENSITIVITY 500mV.**


**OUTPUT POWER 60W RMS into 8 $\Omega$  LOAD IMPEDANCE 4-16 $\Omega$  DISTORTION 0-04% at 60W**

**SIGNAL/NOISE RATIO 90dB FREQUENCY RESPONSE 10Hz-45kHz—3dB**

**SUPPLY VOLTAGE  $\pm$  35V**

**SIZE 114 50 85mm**

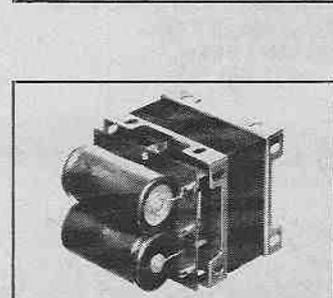**Price  $\pounds$  19-01 +  $\pounds$  1-52 VAT P&P free.**



## HY200 120 Watts into 8 $\Omega$

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

**APPLICATIONS:** Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

**SPECIFICATIONS**

**INPUT SENSITIVITY 500mV**

**OUTPUT POWER 120W RMS into 8 $\Omega$  LOAD IMPEDANCE 4-16 $\Omega$  DISTORTION 0-05% at 100W**

**SIGNAL/NOISE RATIO 96dB FREQUENCY RESPONSE 10Hz-45kHz—3dB**

**SUPPLY VOLTAGE  $\pm$  45V**

**SIZE 114 50 85mm**

**Price  $\pounds$  27-99 +  $\pounds$  2-24 VAT P&P free.**

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—No external components.

**APPLICATIONS:** Public address—Disco—Power slave—Industrial

**SPECIFICATIONS**

**OUTPUT POWER 240W RMS into 4 $\Omega$  LOAD IMPEDANCE 4-16 $\Omega$  DISTORTION 0-1% at 240W**

**SIGNAL/NOISE RATIO 94dB FREQUENCY RESPONSE 10Hz-45kHz—3dB**

**SUPPLY VOLTAGE  $\pm$  45V**

**INPUT SENSITIVITY 500mV SIZE 114 100 85mm**

**Price  $\pounds$  38-61 +  $\pounds$  3-09 VAT P&P free.**

## POWER SUPPLIES

PSU36 suitable for two HY30's  $\pounds$  6-44 plus 81p VAT. P/P free.

PSU50 suitable for two HY50's  $\pounds$  18-18 plus  $\pounds$  1-02 VAT. P/P free.

PSU70 suitable for two HY120's  $\pounds$  14-58 plus  $\pounds$  1-17 VAT. P/P free.

PSU90 suitable for one HY200  $\pounds$  15-19 plus  $\pounds$  1-21 VAT. P/P free.

PSU180  $\pounds$  25-42 +  $\pounds$  2-03 VAT.

B1  $\pounds$  20-48 +  $\pounds$  2-06 VAT.

**P. & P. FREE U.K. ONLY**

**TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS**

**I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.**

## I.L.P. ELECTRONICS LTD.,

**GRAHAM BELL HOUSE,  
ROPER CLOSE, CANTERBURY,  
KENT, CT2 7EP. Tel: (0227) 54778.**

Regd No. 1032630.

Please Supply \_\_\_\_\_

Total Purchase Price \_\_\_\_\_

I Enclose Cheque  Postal Orders  Money Order

Please debit my Access account  Barclaycard account

Account number \_\_\_\_\_

Name and Address \_\_\_\_\_

Signature \_\_\_\_\_

**EDITOR**

F. E. BENNETT

**ASSISTANT EDITOR**

B. W. TERRELL B.Sc.

**PRODUCTION EDITOR**

D. G. BARRINGTON

**TECHNICAL SUB-EDITOR**

T. J. JOHNSON G8MGS

**ART EDITOR**

R. F. PALMER

**ASSISTANT ART EDITOR**

P. A. LOATES

**TECHNICAL ILLUSTRATOR**

D. J. GOODING

**EDITORIAL OFFICES**

Kings Reach Tower,  
Stamford Street,  
London SE1 9LS  
Phone: 01-261 6873

**ADVERTISEMENT MANAGER**

V. PIERI  
Phone: 01-261 6727

**REPRESENTATIVE**

N. BELLWOOD  
Phone: 01-261 6727

**CLASSIFIED MANAGER**

C. R. BROWN  
Phone: 01-261 5762

**MAKE-UP AND COPY DEPARTMENT**

Phone 01-261 6818

**ADVERTISEMENT OFFICES**

Kings Reach Tower  
Stamford Street,  
London SE1 9LS

# Projects... Theory...

## and Popular Features ...

Spring is a curtain raiser. It is the time plans are made for holidays in those long, bright and warm days we confidently anticipate in the months ahead.

Amongst our readers will be many motorists who are already preparing for that touring/camping holiday. They should include in their plans the building of our *Shaver Inverter*. Then no matter where their car may rest, whether here in the UK or abroad, a 240V 50Hz supply will be available at all times to run an electric shaver.

Looking back, one of the advantages of an absorbing indoor hobby is that it does take your mind off unpleasant things like the weather, the last winter especially. Constructors working on the *2020 Tuner Amplifier* will at any rate have had plenty to occupy themselves with, and we imagine the winter passed quite rapidly for them!

This month the penultimate article in the 2020 Series gets to grips with the final and major building operation. Now the fruits of the last few months' labours are gathered together and the task of integrating all into one equipment commences. At this stage the work takes on a greater significance with completion now clearly within sight. The rising expectancy of soon listening and enjoying the results of one's handiwork will inject extra incentive and excitement into the current task.

Now a seasonal message to those interested in electronics but who have not yet taken the plunge into the constructional business. Remember electronics is a hobby for all seasons. Throughout the year the constructor can enjoy this pastime. Most projects featured in EE are of a modest nature, and inexpensive in cost of parts. These designs are often of direct use in other indoor or outdoor activities. The time you spend at the workbench can be the odd half-hour or longer sessions, as you are so disposed. The smaller designs can be built in the course of an evening. A week-end should be sufficient for all but the largest projects.

Spring is the time of awakening and growth. It's a very good time to discover a new exciting and rewarding hobby. So why not give it a try now?

Sorry about this final piece, but I have now to advise readers that the price of EVERYDAY ELECTRONICS will be increased to 45p as from the May issue. Despite this, EE still remains unrivalled in value for money. And be assured we're going to keep it this way!



*Our May issue will be published on Friday, April 20. See page 227 for details.*


**Readers' Enquiries**

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

Telephone enquiries should be limited to those requiring only a brief reply. We cannot undertake to engage in discussions on the telephone, technical or otherwise.

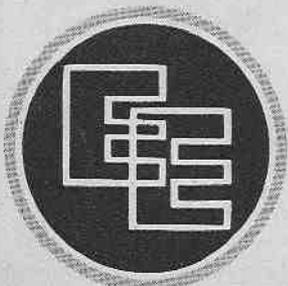**Component Supplies**

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.



# Everyday ELECTRONICS

VOL. 8 NO. 4

APRIL 1979

## CONSTRUCTIONALS

- SHAVER INVERTER** A 20W battery/mains inverter for the motorist/camper by D. S. Gibbs and I. M. Shaw 202
- TOUCH BLEEPER** A finger sensitive audible alarm by T. J. Herklots 206
- EE LABCENTRE** Part 2: PCB component assembly and console construction by R. W. Coles and B. Cullen 215
- MINI MODULE: 7-TRANSISTOR TESTER** Useful for checking those "bargain packs" by George Hylton 220
- CHOKE WARNING DEVICE** Gives visual warning when choke is left out by T. R. de Vaux-Balbirnie 233
- EE2020 TUNER AMPLIFIER** Part 5: Final assembly and interwiring by E. A. Rule 238

## GENERAL FEATURES

### EDITORIAL

- DOING IT DIGITALLY** Part 7: Modules and systems by O. N. Bishop 200
- JACK PLUG AND FAMILY** Cartoon by Doug Baker 208
- FOR YOUR ENTERTAINMENT** Keys of the future by Adrian Hope 212
- SQUARE ONE** Beginner's page. Component codes 213
- MICROPROCESSOR BASICS** Part 2: Getting to grips with the "chips" revolution by R. W. Coles 222
- EVERYDAY NEWS** What's happening in the world of electronics 223
- COUNTER INTELLIGENCE** A retailer comments by Paul Young 228
- CROSSWORD NO. 14** by D. P. Newton 230
- SHOP TALK** Guidance on component buying by Dave Barrington 236
- RADIO WORLD** A commentary by Pat Hawker 245
- PROFESSOR ERNEST EVERSURE** The Extraordinary Experiments of. by Anthony J. Bassett 246

- FREE ENTRY COMPETITION** Antex soldering kits and irons to be won 214


Back issues of EVERYDAY ELECTRONICS June 1977 onwards (October to December 1977, January to March 1978 NOT available) are available world-wide at a cost of 60p per copy inclusive of postage and packing. Orders and remittance should be sent to: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

Binders for Volumes 1 to 8 (state which) are available from the above address for £2.85 inclusive of postage and packing. Subscriptions (for one year)—UK: £8.50. Overseas: £9.50.

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

## Colour Codes

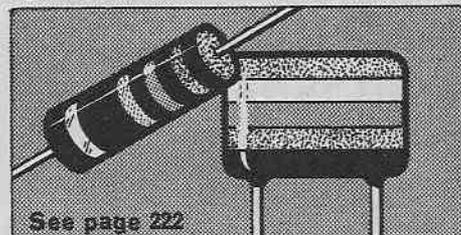

See page 222



● FOR THE SMART  
MOTORIST/CAMPER

● 12V d.c. to 240V a.c. 20W

By D. S. Gibbs & I. M. Shaw

# shaver inverter

ANYONE who has had to use a battery shaver whilst on holiday will know that these devices are a very poor substitute for the real thing. This unit is designed to operate a normal 50Hz mains shaver from a 12 volt car battery and so is ideal for caravan and camping enthusiasts.

When loaded with a shaver it takes just about 1 amp from a 12 volt battery, which is quite acceptable since it is only required for a few minutes per day. If a somewhat heavier drain on the battery can be tolerated the unit will supply a small soldering iron (25 watts maximum). This will enable keen constructors to continue their hobby whilst on holiday.

**COMPONENTS**  
approximate  
cost **£10**

## CIRCUIT CONSIDERATIONS

Many shavers contain a vibrator which is mechanically tuned to 50Hz and so it is important that the inverter should operate at exactly 50Hz or the shaver will not operate at maximum efficiency. This ruled out a simple self oscillating inverter circuit since the frequency would then be a function of the transformer, the supply voltage and the load presented by the shaver. Instead, in this design, the output transistors are driven by a multivibrator which oscillates at 50Hz.

## CIRCUIT DESCRIPTION

The circuit diagram of the Shaver Inverter is shown in Fig.1.

Transistors TR2 and TR3 form the heart of the multivibrator. The extra diodes, D2, D3, D4, and D5 make the circuit look more complicated than the usual astable multivibrator but it works in just the same way.

Assume that TR2 has just been turned on. This turns on the output transistor TR1 via R1 and R2

and at the same time diode D3 conducts and takes the top end of R3 to about +10.5 volts. This in turn takes the base of TR3 up to about +21 volts and cuts off TR3.

However C1 now starts to discharge through R4 and as it does so the voltage on TR3 base drops. When the base voltage drops to +10.5 volts TR3 starts to turn on and its collector voltage rises. Diode D4 now conducts and the top end of R7 starts to go positive. This turns off TR2 and the collector voltage of TR2 drops to zero. Diode D3 is cut off and capacitor C1 recharges via R3 and the base of TR3, turning TR3 and its associated output transistor TR4 hard on.

The same sequence then repeats ending with TR2 being turned on and TR3 cuts off.


## PROTECTION DIODES

Now we come to the functions of diodes D2, D3, D4 and D5. Silicon transistors generally cannot stand a reverse bias on their base of more

than about 5 volts. If this is exceeded the base/emitter junction breaks down and a reverse current flows, which upsets the timing of the circuit and may also cause long term damage to the transistor. In this circuit TR2 and TR3 are subjected to a reverse bias of about 10 volts, but the bases are protected from breakdown by D2 and D5 which prevent any reverse current flowing in the base/emitter junctions.

Now to diodes D3 and D4. If these diodes were not present the circuit would still operate, but when, for example, TR2 turned off its collector voltage would not immediately drop to zero because of the need to recharge C1. This would delay the turn off of TR1 and there would be short periods when both TR1 and TR4 would be conducting at the same time. This would reduce the efficiency of the circuit and result in overheating. Diodes D3 and D4 solve the problem by isolating the collectors of TR2 and TR3 from the timing capacitors.

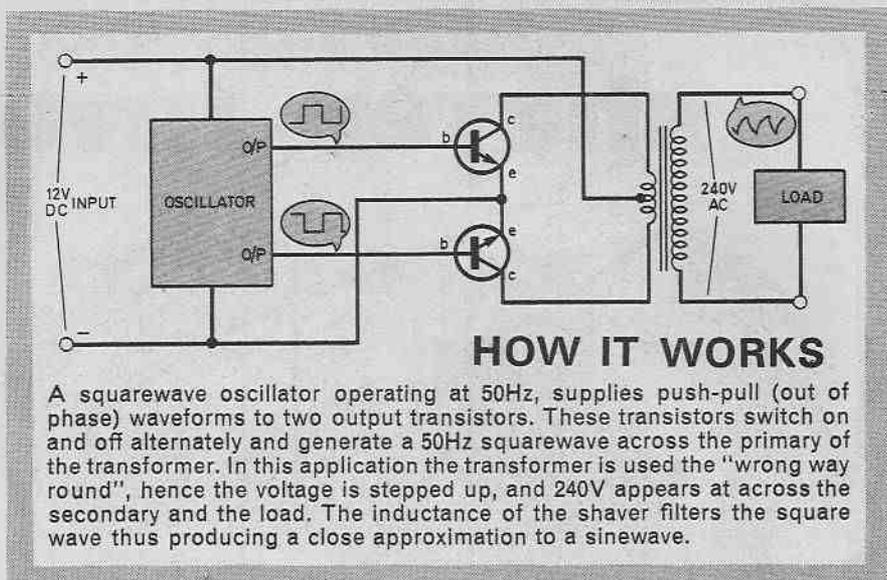The only other components whose function might not be obvious are D1 and D6. These diodes are required because a shaver presents a highly inductive load to




the inverter. This causes overshoots on the collector voltage waveform which could result in the collectors of TR1 and TR4 being driven negative momentarily, with a risk of damage to the transistors. This is prevented by D1 and D6 which conduct if the collectors are driven negative and hence prevent any reverse current from flowing in TR1 and TR4.

Finally, it will be noted that the transformer secondary is con-

nected in series with the primary. This increases the output voltage by 10 per cent to compensate for voltage drops in the transistors and in the winding resistance of the transformer. If you use a different transformer to the one specified it will be necessary to experiment with the connections to determine the correct phasing, since if the phasing is incorrect the output voltage will be *reduced* by 10 per cent.

Fig. 1. Complete circuit diagram of the Shaver Inverter.

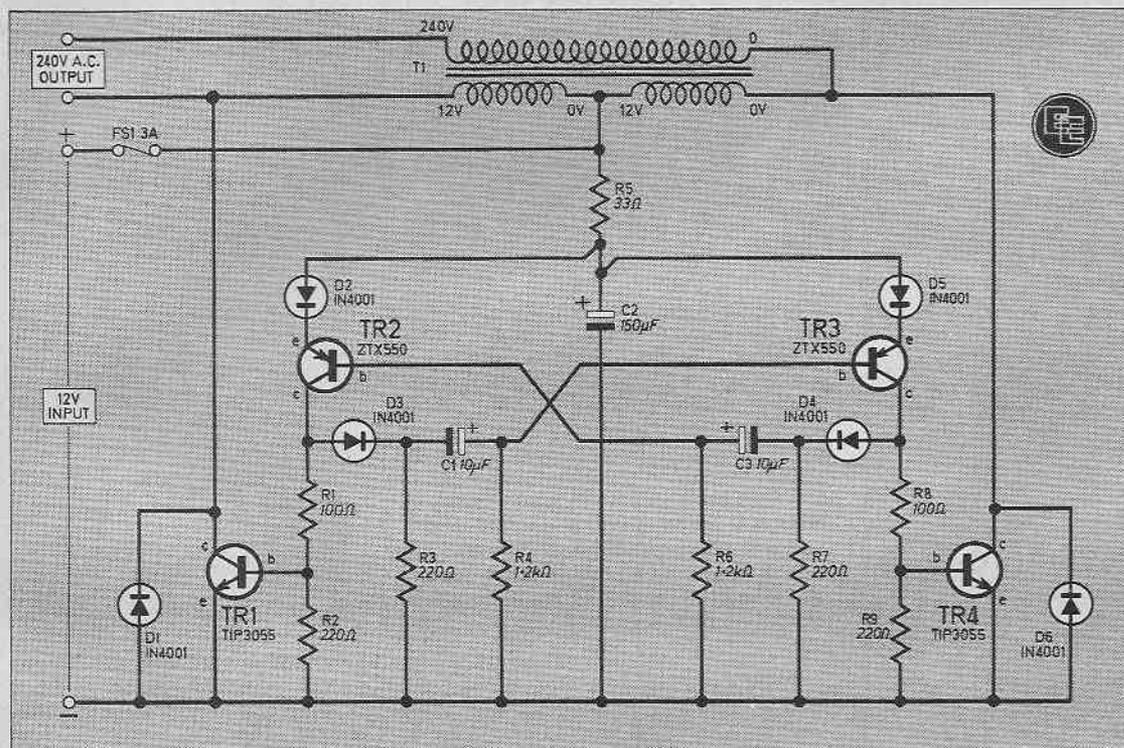

# shaver inverter

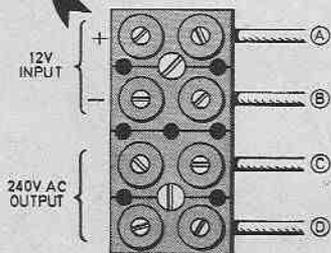
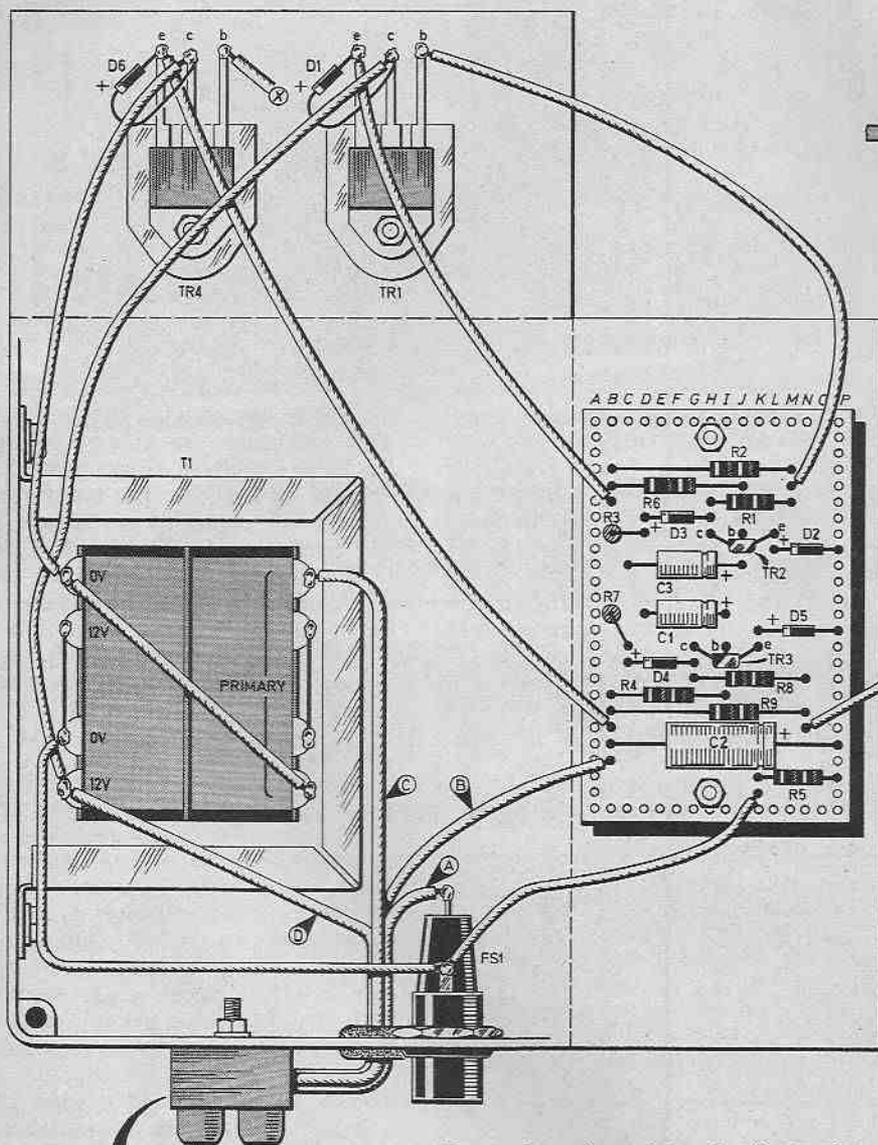


Fig. 3. Complete wiring details for the Shaver Inverter. Also shown is the stripboard layout. The only breaks to be made are those which isolate the mounting screws. Be very careful when mounting the two power transistors to ensure that they do not short to each other or to the side of the case. It would be advisable to place sleeving over the leads also to prevent short circuits. Ensure also that the tags of the transformer are bent down as far as possible otherwise they may touch the lid when this is in place.



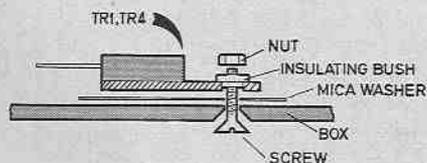


Fig. 4. Power transistor mounting details.

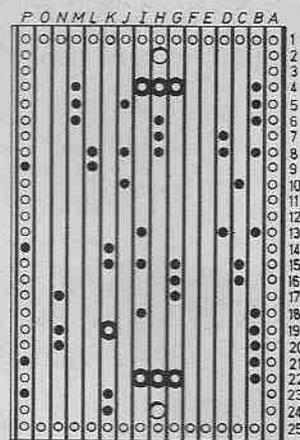

TR2 & 3 UNDERSIDE VIEW

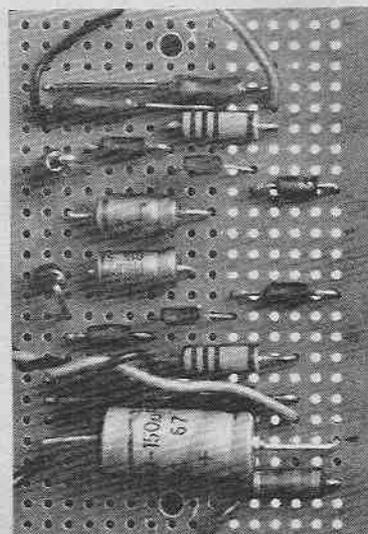

Photograph of the completed circuit board.

# CONSTRUCTION

## starts here

### CONSTRUCTION

The unit is constructed in an aluminium diecast box with dimensions of 118×90×55mm, which provides both a rugged "drop proof" enclosure and also a heatsink for the output transistors. The box should be drilled taking particular care to remove any burrs from the transistor mounting holes.

Most of the components are mounted on a piece of 0.1 inch matrix stripboard having 16 strips by 25 holes. Take care to clip off all component leads as close to the board as possible as they may otherwise short to the box. All the components are standard readily

## COMPONENTS

### Resistors

R1 100Ω	R4 1.2kΩ	R7 220Ω
R2 220Ω	R5 33Ω	R8 100Ω
R3 220Ω	R6 1.2kΩ	R9 220Ω

All ¼W carbon film ± 5%

### Capacitors

C1 10μF 25V elect.
C2 150μF 16V elect.
C3 10μF 25V elect.



### Semiconductors

TR1 TIP3055 silicon <i>n</i> pn
TR2 ZTX550 silicon <i>p</i> np
TR3 ZTX550 silicon <i>p</i> np
TR4 TIP3055 silicon <i>n</i> pn
D1 to D6 1N4001 silicon rectifier (6 off)

### Miscellaneous

T1 Mains transformer, 0-20V, 0-20V 1.6A secondaries (RS type 207 144 or similar).  
 FS1 3A 20mm fuse.  
 Stripboard 0.1 inch matrix, 16 strips × 25 holes; diecast box 118 × 90 × 55mm or similar; panel mounting fuseholder for FS1; mica insulating kits for TR1 and TR4 (2 off); four-way 5A plastic connecting block; ¼ inch grommet; 4BA and 6BA hardware as required; connecting wire.

See  
**Shop  
 Talk**  
 page 236

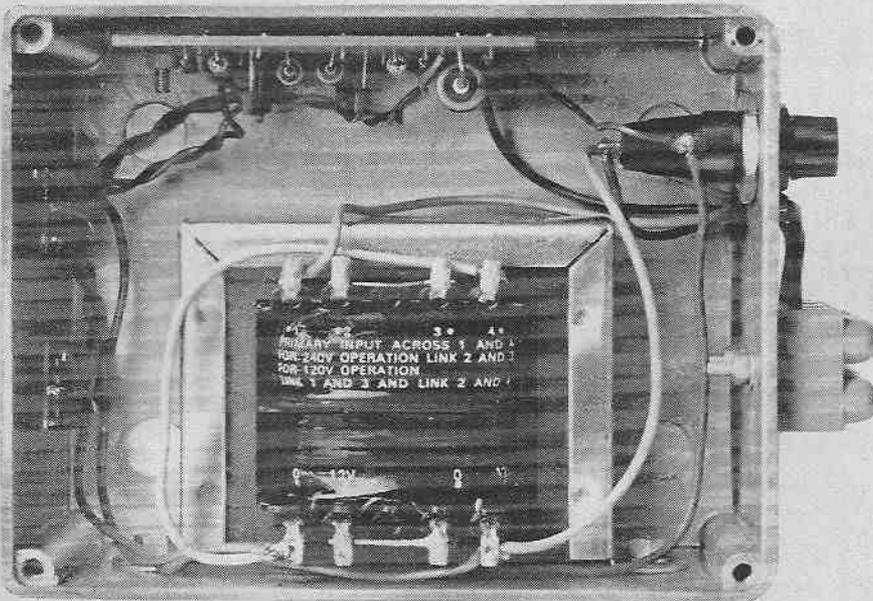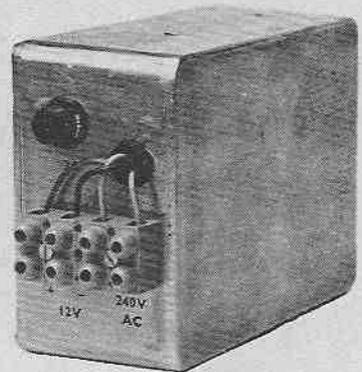

Internal view of the Shaver Inverter showing the relative positions of the components. Note how the component board is mounted using 6BA hardware. As a further safety measure to that already mentioned, some insulating tape can be stuck to the inside of the lid to prevent the tags of the transformer touching, and possibly causing a short circuit.

available types and should not present any problems.

A full wiring diagram is shown in Fig.3. Note that the output transistors should be mounted with insulators and mica washers and that diodes D1 and D6 are connected directly between the collec-

tor and emitter of the output transistors. Mounting details for these transistors are shown in Fig.4.

The tags of the transformer come rather close to the lid of the box and so to avoid the possibility of shorts a small piece of insulating material should be glued


inside the lid, over the transformer. The tags should also be bent down as far as possible.
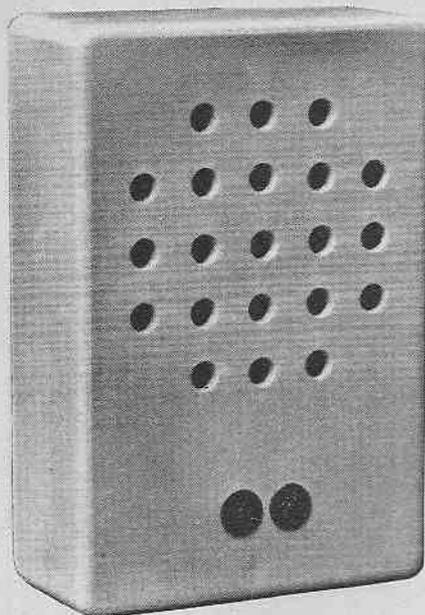
### IN USE

There is no connection between the circuit and the case, so the unit may be used with either positive or negative earth systems. When testing the unit initially it might be as well to reduce the fuse rating to 1 amp in case there has been a wiring error. If all seems to be in order the fuse can then be increased to 3 amps and the unit installed.

So now you no longer have an excuse to come home from holiday with a beard!





# touch bleeper

BY T. J. HERKLOTS

**I**F YOU HAVE ever had the problem of trying to work when a child with the irritating habit of playing with and inevitably breaking the equipment on your workbench is present, this is the project for you. The author has found that it keeps most children quiet and occupied, the only problem being to get it back!

The Touch Bleeper is operated by means of a pair of touch contacts, a finger on the contacts produces a loud tone. The tone ceases when the finger is removed from the contacts. The device needs no mechanical on/off switch as the standing current is nearly negligible—a question of microamps—and so batteries should last a long time.

The unit could also be used for, say, a doorbell, or perhaps the audio stage of an alarm system, or even as a rain or moisture sensor. The applications are possibly endless.

## CIRCUIT DESCRIPTION

The circuit for the Touch Bleeper is shown in Fig. 1 and can be conveniently separated into two sections: a touch switch and an oscillator.

The touch switch is basically a very high gain amplifier consisting of TR1 and TR2. To achieve very high gain, the Darlington pair configuration has been used. The total gain of this arrangement is approximately equal to the product

of the individual gains of TR1 and TR2—a gain of at least 15,000.


To turn on the device, a finger is placed across the touch contacts. This allows base current for TR1 to flow through the finger. Resistor R1 limits the base current of TR1 to about 21 microamps in the event of a dead short-circuit across the contacts.

The resistance of the finger across the touch contacts controls to an extent the purity of the note, as it controls the amount of base current to TR1. If a moist finger is used, the Darlington pair saturates and the note is clear. A dry finger produces a fuzzier tone.

The oscillator is a complementary pair relaxation oscillator comprising TR3 and TR4, which produces a squarewave at audio frequency. This type of oscillator must drive a low impedance loudspeaker, and if a speaker with a coil impedance above 15 ohms is used, the circuit may become unstable.

The circuit draws about 30 milliamps when the tone is being produced, so if another battery is substituted—the circuit will also work on 9 volts—be sure that it can supply this current.

Fig. 1. Complete circuit diagram for the Touch Bleeper.

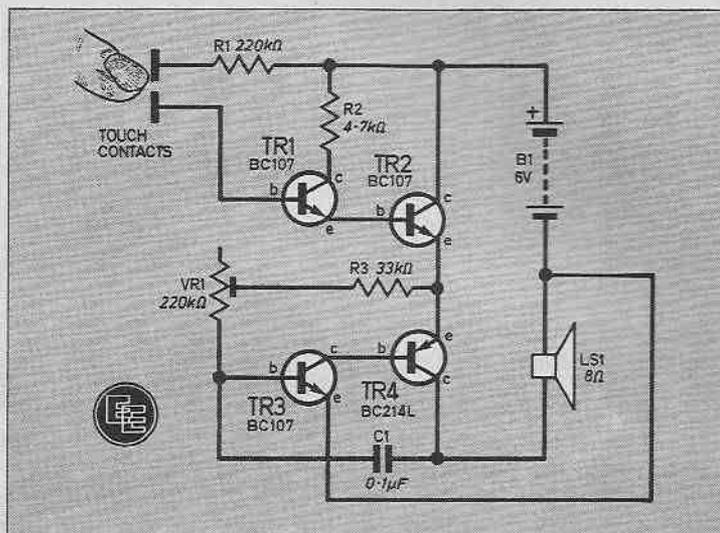

**COMPONENTS**  
 approximate  
 cost £2.50

# CONSTRUCTION starts here

The unit is constructed in a plastic case type PB1 with approximate dimensions of 114mm by 76mm by 38mm. It is recommended that this case be used, but another can be substituted providing it is no smaller than the dimensions given.

The case has a lid secured by two self-tapping screws. This is regarded as the base. The top is drilled with a pattern of 5mm holes to form an aperture for the speaker. The speaker can be glued in place behind the aperture with a strong glue such as Araldite.

Two plated drawing pins are used as the touch contacts. Two 1.5mm holes are drilled to accommodate the drawing pins, but the pins are not put in place yet.

## STRIPBOARD

Most of the components, excluding the battery and the speaker, are mounted on a piece of 0.15-inch matrix stripboard 16 strips by 16 holes. This has to be cut from a larger piece of board. There is only one break in the copper strips as indicated in Fig. 2.


The two links should be soldered first, then the resistors, the capacitor and the four transistors. Keep all the components, including the transistors, as close to the circuit board as possible.

The battery leads can now be soldered to the circuit board, and the speaker leads connected similarly.

Next solder one end of each of the leads to the touch contacts (drawing pins) to the circuit board, and pass the other ends through their holes from the inside to the outside of the case.

Solder the outside ends of the leads to the shaft of each drawing pin. Now the touch contacts can be pushed into their holes, and their shafts (with leads soldered on) bent flat against the inside of the case. A smear of Araldite can be used to secure them.

The battery, which consists simply of four HP7 cells in a battery holder, can now be connected to the battery clip, and the circuit tested by placing a finger on the touch contacts. A loud tone, which can be varied to some extent by turning VR1, should be heard. If this does not happen, check the wiring, or adjacent copper strips on the board which may be bridged by a blob of solder. If all is well however, the battery can now be put in place beside the speaker. A large blob of Blu-Tack is used to secure the battery in place. Another blob is put on the speaker magnet, and the circuit board with the components facing the front of the case, pushed firmly in place on top. The lid can now be secured with the screws supplied after which the unit is ready for use.

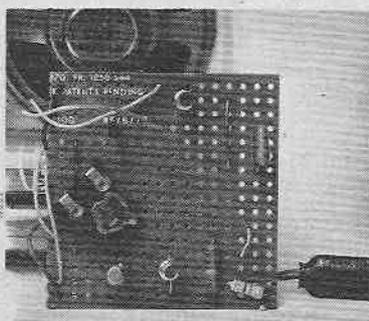

## touch bleeper

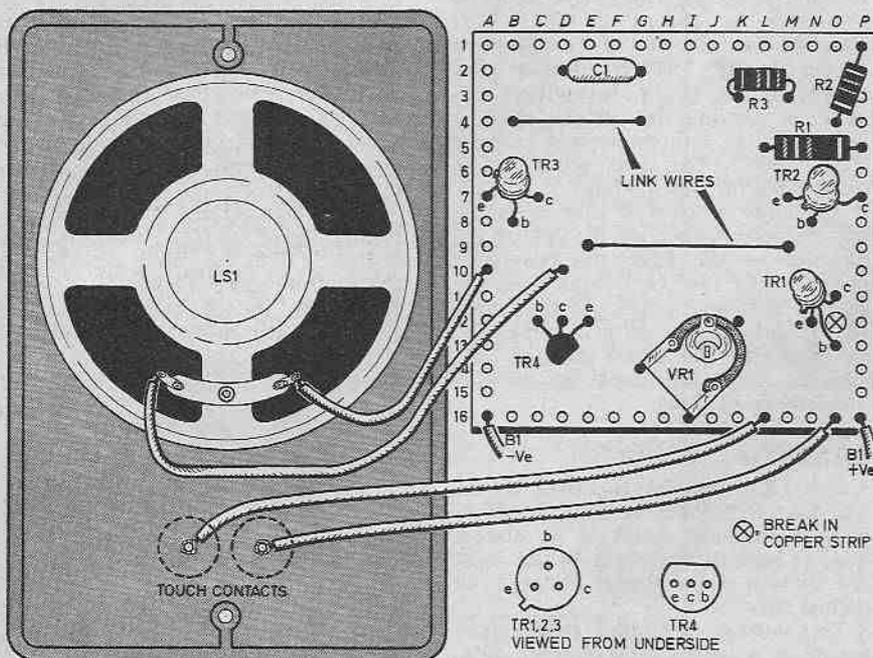


Fig. 2. Complete wiring details for the unit. There is only one break to be made, and is at O12. Resistor R3 is a vertically mounted component.

## COMPONENTS

See  
**Shop  
Talk**  
page 236

### Resistors

- R1 220k $\Omega$
- R2 4.7k $\Omega$
- R3 33k $\Omega$
- All  $\frac{1}{4}$ W carbon  $\pm 10\%$

### Potentiometer

- VR1 220k $\Omega$  standard horizontal preset

### Capacitor

- C1 0.1 $\mu$ F polyester

### Semiconductors

- TR1 BC107 silicon npn
- TR2 BC107 silicon npn
- TR3 BC107 silicon npn
- TR4 BC214L silicon pnp

### Miscellaneous

- LS1 8 ohm 66mm diameter speaker
- B1 6V battery (4 off HP7)
- Stripboard, 0.15 inch matrix 16 strips by 16 holes; battery holder to suit four HP7 batteries; battery clip to suit holder; small plastic box type PB1, 114 x 76 x 38mm or similar (Maplin); two drawing pins for touch contacts; connecting wire.

# DOING IT DIGITALLY



## By O. N. Bishop **PART 7**

LAST month we showed a system for displaying the numbers 0 to 99. It counted pulses produced by the in-built clock. We can think of this system as being made up from a number of sub-systems, or *modules* connected together, see Fig. 7.1. Some of the modules (clock, latch) are built up from several logic gates and additional components. Other modules are complete and ready-assembled on a single i.c.

The switch and the display modules are different from the others because they connect the system to the outside world—we can call them *interface* modules. By means of these, information or data can enter or leave the system. If we look at digital systems in this way, it is much easier to understand what they do and how they operate *as systems*, even though we may not be entirely clear about how some of the individual modules work.

For example, we know that the 7447 receives four BCD inputs and gives seven outputs for driving the display, but we have never gone into any detail about the internal circuitry of this i.c. We have treated it as a *black box*, and this is all we need to do when designing digital systems.

From a few different kinds of module it is easy to design and build scores of different digital systems. The Test-Bed already has several useful built-in modules—clock, latch, bi-stable, counters, decoders, displays—and also now a keyboard module. With these and a few extra gates we can already build quite a number of digital systems. But before we go on to do this, we need a few more modules—particularly interfaces. Let us look at the circuits for these, and test them on the Test-Bed before building them into more elaborate systems.

### LIGHT SENSOR

A light sensor interface module allows information about light intensity to be fed into a logical system.

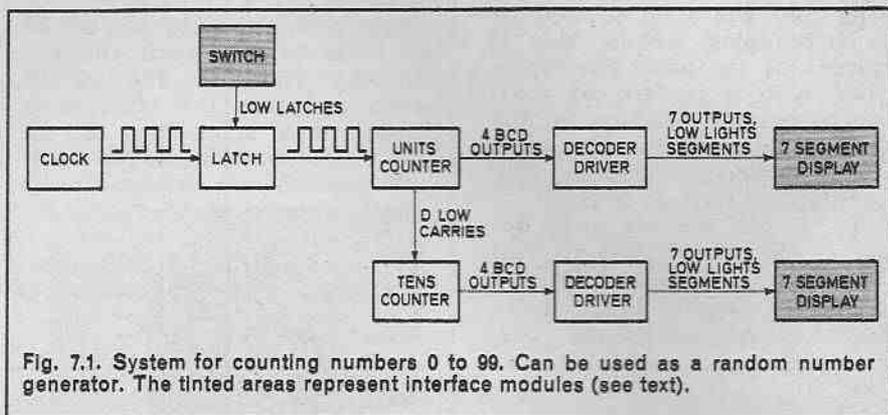


Fig. 7.1. System for counting numbers 0 to 99. Can be used as a random number generator. The tinted areas represent interface modules (see text).

It detects whether light intensity is above or below a predetermined level and accordingly produces a high or low digital output that can be fed to other modules. The circuit for such a sensor is shown in Fig. 7.2a. Assembly details on the Test-Bed are shown in Fig. 7.2b. Its output goes to one of the i.e.d.s. Investigate the effect of varying the amount of light falling on the light-dependent resistor (l.d.r.) PCC1. Can you write out a truth table for this module?

The l.d.r. consists of a semiconductor material, cadmium disulphide. In darkness or low light, the resistance of the l.d.r. is very high, usually several thousand ohms. As the intensity of light falling on it is increased, its resistance decreases until, in full daylight, its resistance is only a hundred or so ohms.

### POTENTIAL DIVIDER

The l.d.r. and R1 together act as a potential divider so that, in darkness, voltage at point A is almost  $V_{CC}$ , or logical "high". In bright light the voltage falls almost to zero, or logical "low".

This voltage is applied to the four inputs of a special type of NAND gate. Since all inputs are connected, it is acting as a NOT or INVERT gate in this circuit. This gate has the special

feature that its output does not go high until the input has fallen below a certain level, called the *lower threshold level* see Fig. 7.3. Once this change-over has occurred, a slight increase of input voltage does not cause output to change back to its former state. Input voltage must rise as high as the *upper threshold level* before the output changes back to low again. The difference between upper and lower threshold levels is approximately 0.8 volts.

Small fluctuations in the rising or falling input voltage, such as those shown in Fig. 7.3, have no effect on the output. The result is a single clean-cut switch-over instead of several erratic changes of output.

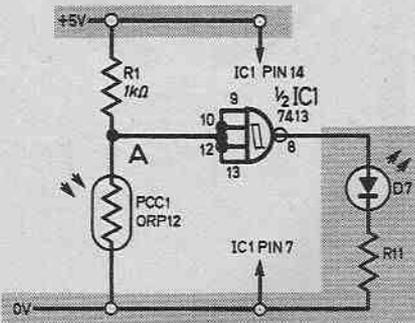


Fig. 7.2 (a). The circuit diagram for a Light Sensor.

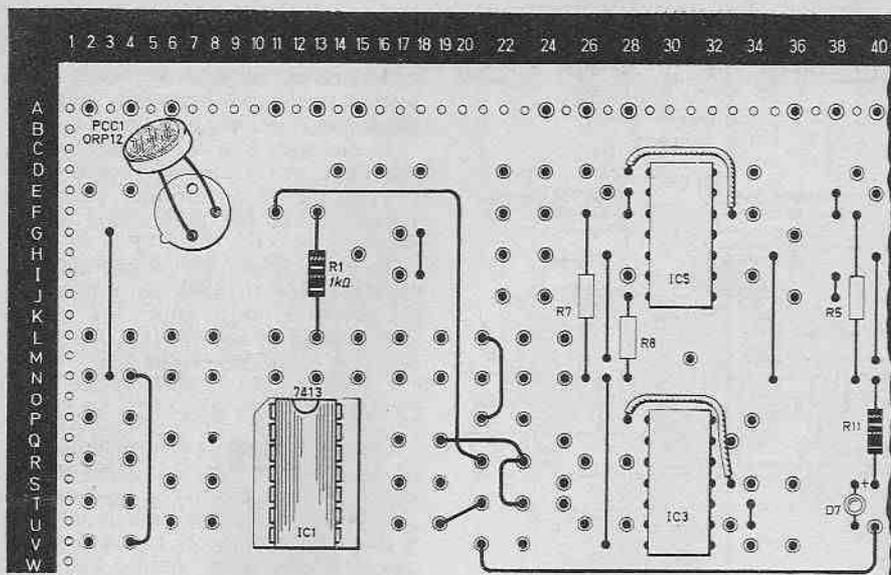


Fig. 7.2 (b). The circuit of Fig. 7.2 (a) wired up on the Test-Bed.

For example, imagine a cloud drifting across the Sun, causing an overall fall of light intensity followed by a rise. The ragged edge of the cloud would produce small fluctuations superimposed on the overall fall and rise; the corresponding voltage changes would be much like those in the figure. The output however would change sharply to high when the input voltage first reached the lower threshold, and would remain high until it eventually rose above the upper threshold level. A single, well-defined output pulse is the result. In general, this Schmitt trigger NAND gate (7413, pinning details in Fig. 7.4) is useful for producing clean-cut outputs from slowly-changing and irregularly shaped input waveforms.

The sensor circuit can be modified to suit requirements. As drawn, it produces low output with low light intensity. To reverse this action, the l.d.r. and resistor are interchanged. To alter the level at which triggering occurs, alter the value of R1. To allow triggering level to be set to a range of values, substitute a variable resistor for R1. Modified versions should be set up on the Test-Bed, tested and modified again if necessary until they perform in the required way.

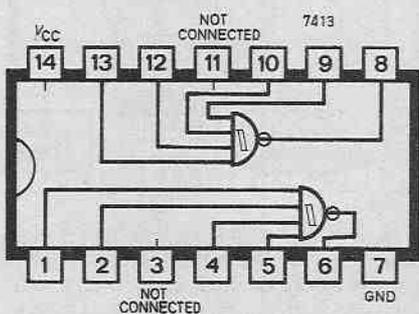


Fig. 7.4. Pinning details for the 7413 dual 4-input NAND Schmitt i.c.

### LOUDSPEAKER MODULE

To obtain a louder sound than you get from the crystal earphone used earlier in this series for listening to audio-frequency trains of pulses, such as those obtained from the clock operating at high frequency, a loudspeaker module, Fig. 7.5a is required.

A loudspeaker module has obvious applications in warning and alarm systems. The input, taken from any TTL output, turns TR1 on or off as it goes high or low. This causes larger and intermittent current to flow through the loudspeaker, energising

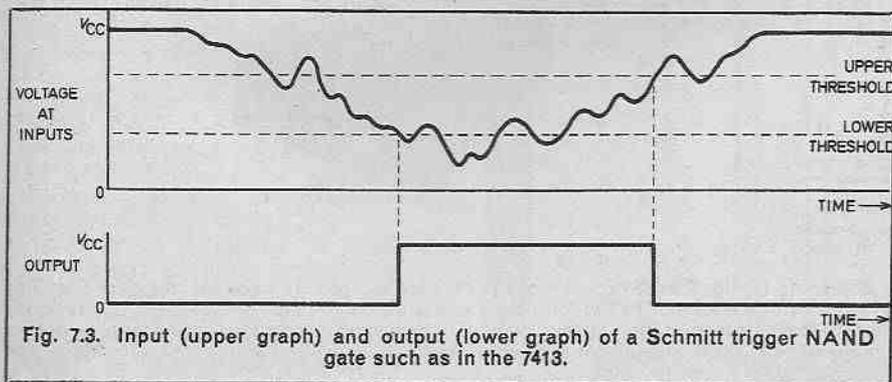


Fig. 7.3. Input (upper graph) and output (lower graph) of a Schmitt trigger NAND gate such as in the 7413.

the coil intermittently, and so giving rise to an audible sound. Connect up this circuit on the Test-Bed and connect its input to one clock output, see Fig. 7.5b.

With the clock at low or medium frequency, a regular series of clicks will be heard as the clock output changes from low to high, and from high to low. When the clock is at high frequency the clicks come closer together, merging to give an audible note of approximately 450Hz.

Another interesting experiment is to feed the clock output to the input of one of the 7490 counters and then listen to the notes obtained when the loudspeaker module is wired to each of the counter output terminals in turn. In this instance the counter is acting as a frequency divider.

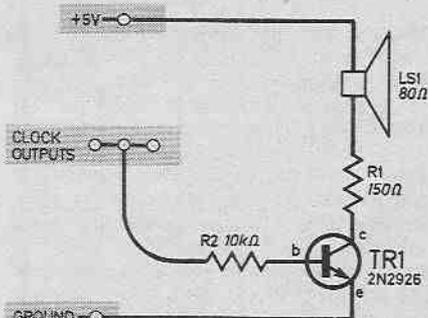


Fig. 7.5 (a). Circuit diagram of a Loudspeaker Module for increasing volume output when listening to a.f. pulse trains.

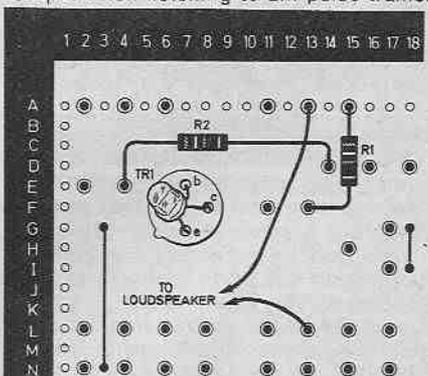


Fig. 7.5 (b). The circuit of Fig. 7.5 (a) wired up on the Test-Bed.

### SOME USEFUL DIGITAL SYSTEMS

A few of the many systems that can be built up on the Test-Bed are shown in Fig. 7.6.

Study the diagrams and try to see how they work. Then connect the circuits on the Test-Bed—mainly a matter of joining together the modules already built-in to the Test-Bed—and study their action at first hand. You may think of ways of improving a system, of modifying it to suit your needs more exactly. If so, try it out on the Test-Bed until you get it right. When you have done this, you may prefer to build your system into a more permanent form.

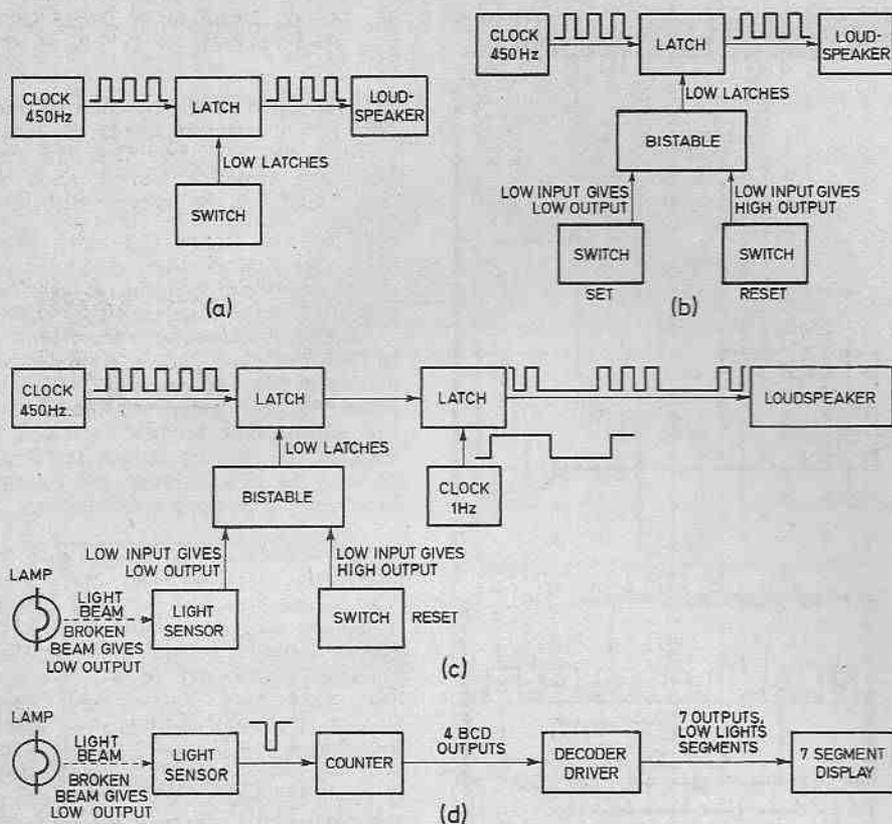


Fig. 7.6. Logical systems. (a) Morse practice buzzer (b) Alarm activated by SET switch (c) Light activated intruder alarm with intermittent tone (d) system for counting goods on a conveyor belt, or people passing through a doorway.

## PERMANENT UNITS

If there are certain modules that you need to use often, it is worth while to assemble each of these on a separate piece of circuit board. Then you have convenient units which may quickly be connected with each other and to the Test-Bed when you are building logical systems. Also you have greater reliability for there is less chance of loose connections causing faulty operation.

Finally, by assembling some modules off-board, you clear space on the Test-Bed, allowing more room there

for the more complicated systems that you may want to build.

Similarly, when you have worked out a complete system you may wish to keep this for future use; the whole system can be built up permanently on a separate circuit board, as described later.

The light sensor can be made into a self-contained module, in a case as shown in Fig. 7.7. If you are thinking of making several different modules it is a good idea to buy enough small cases to match. Each can then bear terminals in standard colours, for example red for  $V_{CC}$ , black for ground,

green for inputs and yellow for outputs.

Connecting modules together, using leads terminated by 4mm plugs, is quick and relatively error-free.

To cut costs you may dispense with the case and terminal sockets, and use double-sided terminal pins, the lower half of the pins acting as leg stands.

To make it simpler to join modules together, try to keep to a standard layout of terminal pins:  $V_{CC}$  at top left, ground at bottom left, inputs on left side, outputs on right side.

## COMPLETE SYSTEMS

Complete systems will usually best be built up on a single large circuit board. It is a good idea to make up the system in stages, one module at a time. Each stage is tested and put into working order before the next stage is tackled.

For example, in building a clock-driven numerical display (Fig. 7.1) for use in various games of chance or as a random-number generator, the first stage is to assemble the clock module on the Test-Bed. This is tested, particularly to check that the chosen capacitors produce the desired frequency of operation. The clock components are then transferred to their locations on the new circuit board, soldered in place with flying leads if required. This permanently wired module is then checked for correct functioning.

Next the switch and latch are connected on the Test-Bed, but fed by output from the permanently wired clock (remember to connect  $V_{CC}$  and ground terminals on the circuit board to the corresponding terminals on the Test-Bed). The latch is tested, then transferred to its location on the circuit board, permanently soldered, and permanently wired to clock.

Working in this way, each module is first assembled and tested on the Test-Bed, then transferred to the circuit board. Ultimately the complete

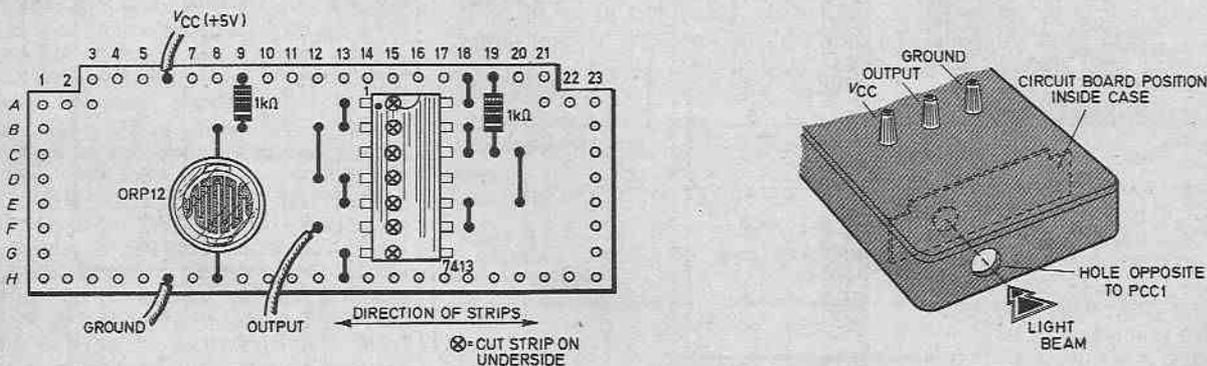


Fig. 7.7. Permanent version of the Light Sensor appearing in Fig. 7.2 (a) except that the first NAND gate is used instead (see Fig. 7.4). A pull-up resistor is connected between positive rail and gate 2 input to reduce power consumption of the unused gate. Instead, this gate could be wired to the output of the other gate (F13 to C19, omitting the 1 kilohm resistor at this point) giving an inverted output—high in darkness. Also shown is the board mounted in a plastic case with cut-out for incident light beam and fitted with screw terminals. The board is shaped and sized to fit in a Bimbox type 2003/13.

system is ready on the circuit board and in full working order. The board can then be cased, with control switches mounted on a panel.

## DIGITAL DICE

We have used the 7490 counters to give BCD digits from 0 to 9, but for a dice we need digits from 1 to 6. The counter must be made to reset itself immediately it reaches the count of 7. Then it must reset to 1, and here is the problem, for the 7490 is designed to reset to 0 or to 9, but not to 1.

One solution to the problem is shown in Fig. 7.8a and wired up on the Test-Bed in Fig. 7.8b. It uses an i.c. we have not met before, the 7410, which contains three 3-input NAND gates, see Fig. 7.9 for pinning details.

If you are not sure what a 3-input NAND gate should do, investigate the action of one of these gates on the Test-Bed, before building the dice circuit. Work out its truth table.

As the clock runs, the flip-flop output *Q* alternates between high (1) and low (0). Whenever *Q* changes from high to low, the 7490 counter is advanced by one stage. The result is shown in table 7.1.

Table 7.1. Truth table for a digital dice.

Counter outputs Decoder inputs	7490		7473	Equivalent decimal unit
	<i>B</i>	<i>A</i>	<i>Q</i>	
	0	0	1	1
	0	1	0	2
	0	1	1	3
	1	0	0	4
	1	0	1	5
	1	1	0	6
	1	1	1	7
Transitional stage, very short	reset to 00			(not seen)
	0	0	1	1
	0	1	0	2
	... and so on			

When all three outputs are high, the NAND output goes low; this is inverted to high by the NOR gate, and so the counter is reset to zero. The 7473 output is *not* reset, but remains high, giving the decimal digit 1, as required.

If the clock is set to run at high frequency the display changes so rapidly that it is impossible to follow. By pressing the latch switch counting is in effect stopped at random. We have the digital equivalent of an unloaded cheat-proof dice.

This circuit is suitable for building into permanent form, powered by a 6 volt battery.

For clock and latch you need seven 2-input NAND gates, so two 7400s will provide these, with one gate to spare.

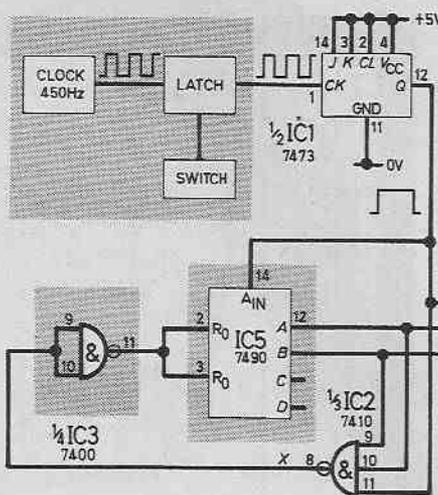


Fig. 7.8 (a). Circuit for a Digital Dice. The tinted systems are built-in on the Test-Bed.

and build a dual digital dice system, with two numerical displays? Many board games need two dice and also there are two-dice games, such as Craps, that can be played with this system.

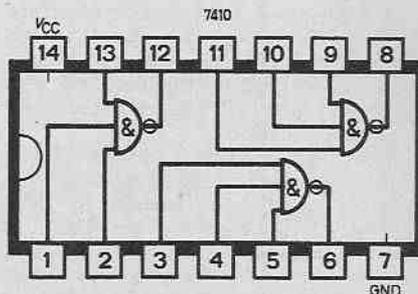


Fig. 7.9. Pinning details for the 7410, triple 3-input NAND gate i.c.

The spare gate can have its inputs wired together to make the required NOR gate. Yet there are still two spare gates in the 7410 and a spare flip-flop so why not extend the system

It is essential that the two dice be independent (otherwise we shall "throw" nothing but doubles) but it is not necessary to build two completely separate systems. The second counting system can be driven from the output of the triple-input NAND gate of the first system. Its output goes low every time the first counter is reset, causing the second flip-flop to change state. The result is a sequence like this: 11, 12, 13, 14, 15, 16, 21, 22, 23, 24, 25, 26, 31, 32 . . . . . 64, 65, 66, 11, 12, and so on.

There are 36 steps in this sequence and all combinations of the numbers 1 to 6 occur once each. If the clock runs at 450Hz the sequence is repeated about 12 times each second, so that pressing the latch is

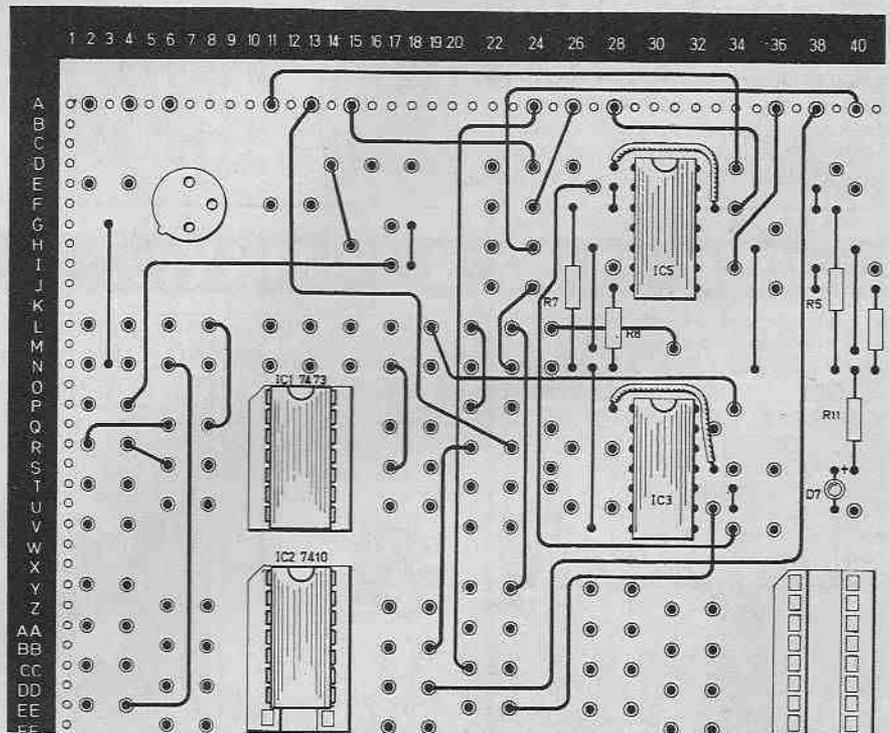


Fig. 7.8 (b). The circuit of Fig. 7.8 (a) wired up on the Test-Bed.

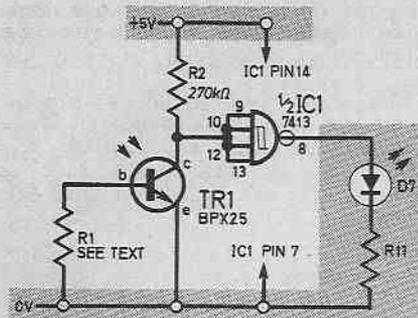


Fig. 7.10 (a). The circuit of a High Speed Light Sensor using a phototransistor which can respond rapidly to light intensity variations.

equivalent to throwing two dice independently.

The Double Digital Dice system can be built on the Test-Bed, and if desired transferred to a circuit board as a permanently wired unit. Table 7.2 lists the i.c.s required for each version, and the allocation of gates.

Thus the permanent version needs only two 7400s, a 7410, a 7473 and the counters and decoders—a total of eight i.c.s.

The system diagram is like that of Fig. 7.8 with a second complete counting module (7473 + 7490 + 3-input NAND gate + NOT gate) and display module, wired as in Fig. 7.8 and joined to point X.

Table 7.2. Requirements for the Double Dice on the Test-Bed and in permanent form on circuit board.

Function	Requirements	Test-Bed	Gate and i.c.	
			Test-Bed	Permanent version
Clock	2 NAND gates	Built in clock		½ 7400
Latch	5 NAND gates	Built in latch		1 7400 plus one gate from 7410
Flip-flops	2 flip-flops	1 7473		1 7473
3-input NAND	2 gates	1 7410		¾ 7410
NOT	2 gates	Built in NOT and NAND		½ 7400
Counters	2 7490	Built-in 7490s		2 7490
Decoder/drivers	2 7447	Built-in 7447s		2 7447
Displays	2 displays	Built-in displays		2 displays

### HIGH-SPEED LIGHT SENSOR

A high-speed light sensor interface module completes this month's collection of modules, see Fig. 7.10a. This can be built on the Test-Bed, Fig. 7.10b and later, if required, made into a permanent unit.

The light-sensitive device is a phototransistor. This responds extremely rapidly to changes in light intensity. By contrast an i.d.r. is slow; it takes several seconds or even minutes to fully respond to large changes of intensity and while its response rate is adequate for many

purposes it will fail to respond when a small object passes rapidly through a light beam—even though the object may be just large enough to obscure the whole beam for an instant.

The light level at which the output of the module changes state can be set by choosing an appropriate value for R1. If R1 is 10 megohms the module is triggered by twilight levels. For triggering in daylight or bright indoor light, make R1 100 kilohms. Alternatively, a 2 megohm variable resistor can be used and allows adjustment of triggering level over a wide range.

In the version of Fig. 7.10 the output goes low as light intensity falls below the triggering level. Because the phototransistor has a rapid response and provided that the objects to be detected are reasonably sharp in outline, the Schmitt gate can be omitted; the output then comes directly from the collector terminal of TR1, and goes low as light intensity rises above the triggering level. Test both versions on the Test-Bed to see which meets your requirements.

To be continued

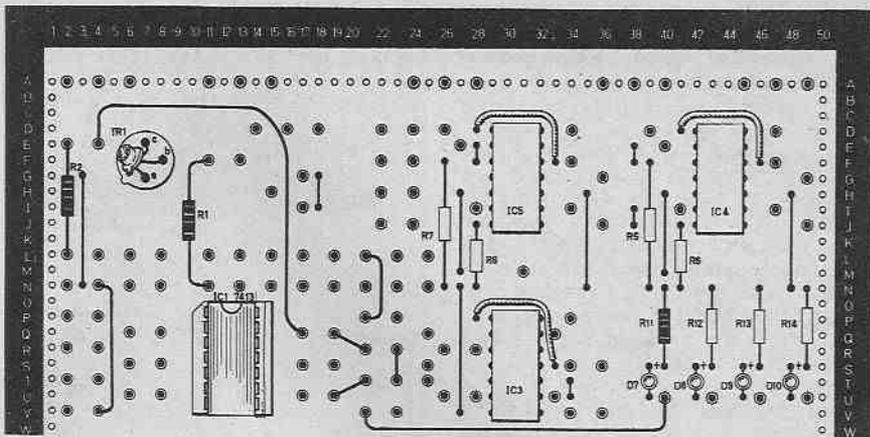


Fig. 7.10 (b). The circuitry of Fig. 7.10 (a) wired up on the Test-Bed.

## JACK PLUG & FAMILY...


BY DOUG BAKER

BECAUSE OF INCREDIBLY HIGH BILLS LATELY, I'M HAVING INSTALLED A TELEPHONE CHARGE CLOCK WHICH WILL ENABLE US TO SEE THE COST OF A CALL ACCUMULATING.



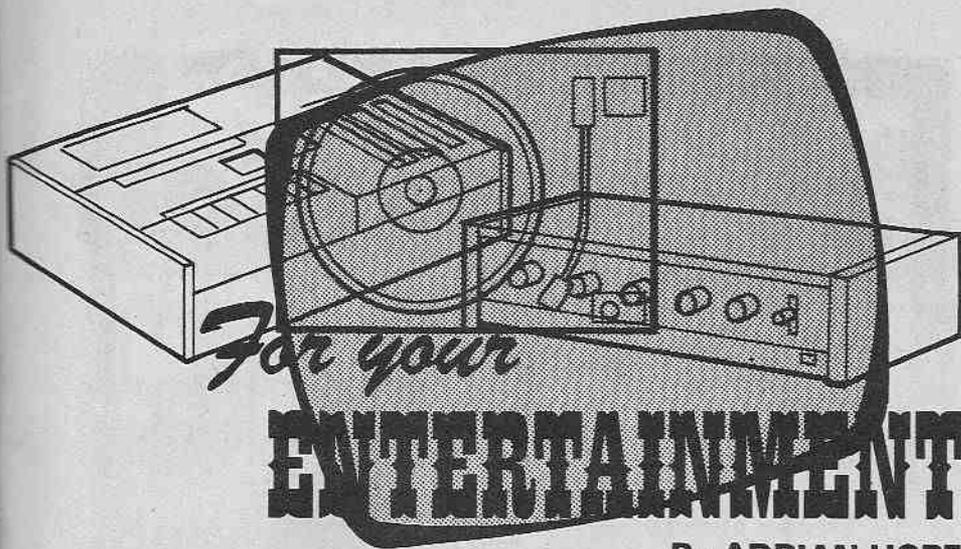OH, GOOD. I'VE OFTEN WONDERED HOW MUCH ALL THE CALLS ARE WHEN I PLAY RECORDS TO COUSIN JOHN IN AUSTRALIA.





By ADRIAN HOPE

### Magnetic Coding

Within a few years, keys, as we now know them, could be obsolete. Our future keys will look like credit cards.

The secret lies in magnetic coding. Already some banks are coating cash cards with magnetic material, into which there is permanently encoded an identifying word which "belongs" to the user. When the card is fed into a machine it "unlocks" circuitry which enables the release of ready cash per the customer's instructions.

To ensure that a lost card cannot be used without authority, the rightful owner must key into the cash machine a secret number which matches the number coded magnetically onto the card.

### Just The Ticket

Many stations on the London underground already issue tickets which carry a magnetic code and so enable the owner to pass through a magnetically triggered entry turnstyle. This system will only offer a real advantage when, as planned for the future, machines are installed which can read the code on a ticket when it is presented by a passenger *leaving* the station. The turnstyle will only open if the ticket carries a code denoting the correct fare for the journey which the passenger has made.

The Paris Metro is already highly automated in this respect but has the advantage that all journeys cost the same. There is thus no need for the French turnstyles to read the value of the ticket at the end of a journey and compare the fare paid with the distance travelled.

The French have built a very clever facility into their ticket system. It is possible now to buy a so-called "orange card" ticket which for a once and for all cost gives unlimited travel on the Metro for one month. The ticket is magnetically coded with an instruction which renders it useless after one

month has expired. Also, the magnetic decoder in the turnstyle is programmed to reject the same ticket if it is presented twice within six minutes. This prevents the owner of an orange card going through the turnstyle and handing the ticket over to a friend for free access.

I asked London Transport whether the system adopted for the London Underground had the facility to upgrade in this fashion. In fact, I asked London Transport twice, and in each case they stalled and never came back with a reply. The inference is that the British magnetic tube ticket system can't be upgraded to such sophistication.

Indeed, recently London Transport were reported as having finally found a way of defeating ticket cheats who pass the same magnetic yellow ticket through the turnstyle more than once. To prevent this LT are now fitting magnetic rollers to the turnstyles which prevent the re-use of a ticket by wiping off its magnetic coding after one use.

The plan is to equip all automatic turnstyles with this solution to the fare dodging problem. But once the turnstyles have been fitted with magnetic "bulk" erase rollers there will presumably be no possibility of LT adopting a season ticket system similar to the French, because, of course, such a season ticket must by definition remain permanently magnetized with fare dodging blocked by code recognition and timer circuits inside the turnstyle.

What a pity London Transport didn't think things through more carefully before starting to install the present system, with which London tube goers are now stuck for many years to come.

### Combination Key

The use of a magnetic card as a key is, of course, a logical extension of the use of a magnetic card to trigger the supply of cash or let people on or off

a transport system. The British company Tann Synchronome Ltd. has made some enterprising steps in this logical direction.

The basic Tann system (which costs less than £500) centres round a door lock which can be opened only when the correct magnetically coded card is pushed through a letter box slot. The advantage is that you can't pick a magnetic lock like an ordinary key lock and there is no way that a potential burglar can get a duplicate magnetic card key cut at the hardware store.

A more sophisticated system has a calculator style keyboard on the lock and requires the user to punch in a memorised code number that matches the number invisibly coded on the card. This obviously increases security even further. With such systems the individual locks can all be hooked to a central computer and give an instant read-out of who has passed through which lock position with their card and so on.

Perhaps one day, if all the obvious bureaucratic obstacles don't prove insuperable, we shall carry around just one card in our pocket that can be used as a door key, a cash card, a credit card and an identification card carrying coded information on name, address, blood group and allergies.

### Government Warning

Although it didn't attract much publicity the government recently put out a sobering safety warning on some of the exotic domestic lighting gadgetry which is now in many shops and homes.


One visually impressive beast is a liquid filled lamp which contains fragments of metal foil; these circulate in the liquid and glitter when the lamp is switched on and gets hot. The fluid used in these lamps is a chlorinated hydrocarbon, for instance trichloroethylene, trichloromethane or perchlorethylene.

These liquids, similar to dry cleaning fluids, evaporate very quickly on exposure to air. Indeed it's this characteristic that makes a sealed volume of the liquid so active. But the fumes, like those that sometimes leak out of faulty dry cleaning machines, are decidedly unpleasant and can quite literally anaesthetize someone who inhales them.

The Government is thus warning that anyone who uses a lamp of this type should be ready to open all doors and windows and clear the room if ever it is shattered. Users could also be in danger from using too strong a bulb because anything other than a 40 watt bulb may produce enough heat to drive some of the liquid out of the screw-cap vapour seal.

Anyone tempted to make a DIY exotic lamp of this type should be very well aware of these dangers.
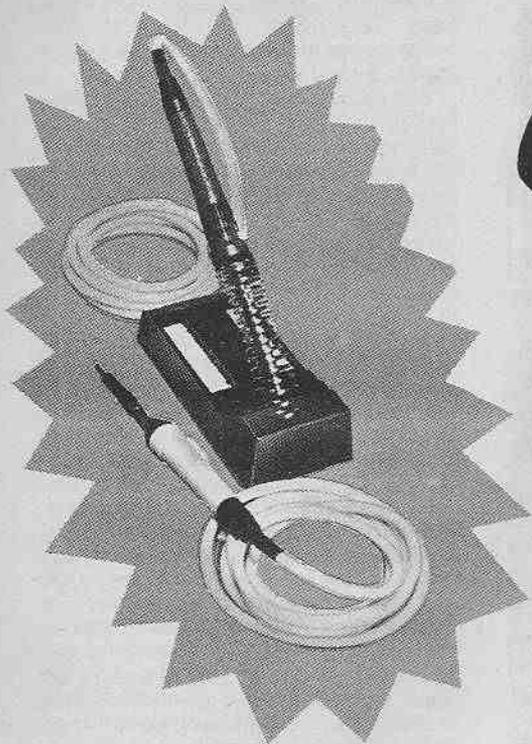
# FREE ENTRY Competition 25 ANTEX SOLDERING KITS & IRONS TO BE WON



★ **FIRST PRIZE**—A special soldering kit containing TWO soldering irons, TWO stands, SIX iron-coated bits, solder and a heatsink.

PLUS

★ **SIX**—CX or X25 soldering irons plus stands.

★ **EIGHTEEN**—CX or X25 soldering irons.

The most ESSENTIAL tool for the constructor of electronic circuits is undoubtedly a soldering iron, since the majority of electrical connections are made by means of a soldered joint.

In view of this, we have arranged with **Antex Limited**, the well known manufacturers of soldering irons, a FREE entry competition in which a grand total of TWENTY-FIVE prizes may be won which feature two mains powered irons from the Antex range, the miniature 17 watt CX and the general purpose 25 watt X25.

## HOW TO ENTER

Listed below are 8 aspects of soldering any or all of which are important in getting good results. How do you rate them for getting the very best results?

Write the key letters of the eight aspects—in ink, pen or ballpen—in order of choice in the spaces on your entry coupon. For example if you consider that "Correct bit size" is of paramount importance put D in the first space, the letter of your next choice goes against 2nd, and so for all eight. Complete the coupon with your own full name and address and post in a sealed envelope to EVERYDAY ELECTRONICS, ANTEX COMPETITION, 55 EWER STREET, LONDON SE99 6YP, to arrive not later than Monday, 30th April, 1979, the closing date. Don't forget to indicate your choice of iron on coupon.

## HOW DO YOU RATE THESE ASPECTS OF SOLDERING?

- |                         |                           |
|-------------------------|---------------------------|
| A Adequate iron wattage | E Clean contact surfaces  |
| B Good mechanical joint | J Flux-cored solder       |
| C Well-tinned bit       | K Correct bit temperature |
| D Correct bit size      | L Execution time          |

## IMPORTANT

Before sealing, copy out—on the outside back of the envelope—the key letters of the eight aspects in exactly the same order as they appear on your completed coupon. Do not enclose any correspondence or matter other than the coupon.

## RULES

There is no entry fee but each attempt must be on a proper entry coupon cut from EVERYDAY ELECTRONICS and must bear the entrant's own name and address.

All accepted entries will be examined and the judges will award the first prize to the entrant they consider has shown the most skill and judgement in placing the eight aspects of soldering in their best order of importance. Remaining prizes will be awarded for next best entries in order of merit, and no entrant may win more than one award.

In the event of a tie for any prize(s) those tying will take part in an eliminating contest, to be held by post, to determine such winner(s) or winning order.

Entries arriving after the closing date or received incomplete, illegible, mutilated or altered or not complying with the instructions and rules exactly will be disqualified. No responsibility can be taken for entries lost or delayed in the post or otherwise.

Decisions of the judges and of the Editor in all other matters affecting the competition will be final and legally binding. No correspondence will be entered into.

The competition is open to all readers in the UK and Eire other than employees (and their families) of IPC Magazines Ltd., the printers of EVERYDAY ELECTRONICS and of Antex Ltd.

Winners will be notified and the result will be published later in EVERYDAY ELECTRONICS.

## FREE ENTRY COUPON

Please post to:

EVERYDAY ELECTRONICS, ANTEX COMPETITION,  
55 EWER STREET, LONDON SE99 6YP

My order of importance for the eight aspects of soldering is listed on the right. In entering the competition, I agree to the rules as final and legally binding.

NAME .....  
(Mr/Mrs/Miss)

ADDRESS .....  
(Block letters)


Closing date for entries: Monday, April 30, 1979.

1st	
2nd	
3rd	
4th	
5th	
6th	
7th	
8th	

MY CHOICE  
CX  X25

CUT ALONG THIS LINE

# LAB CENTRE

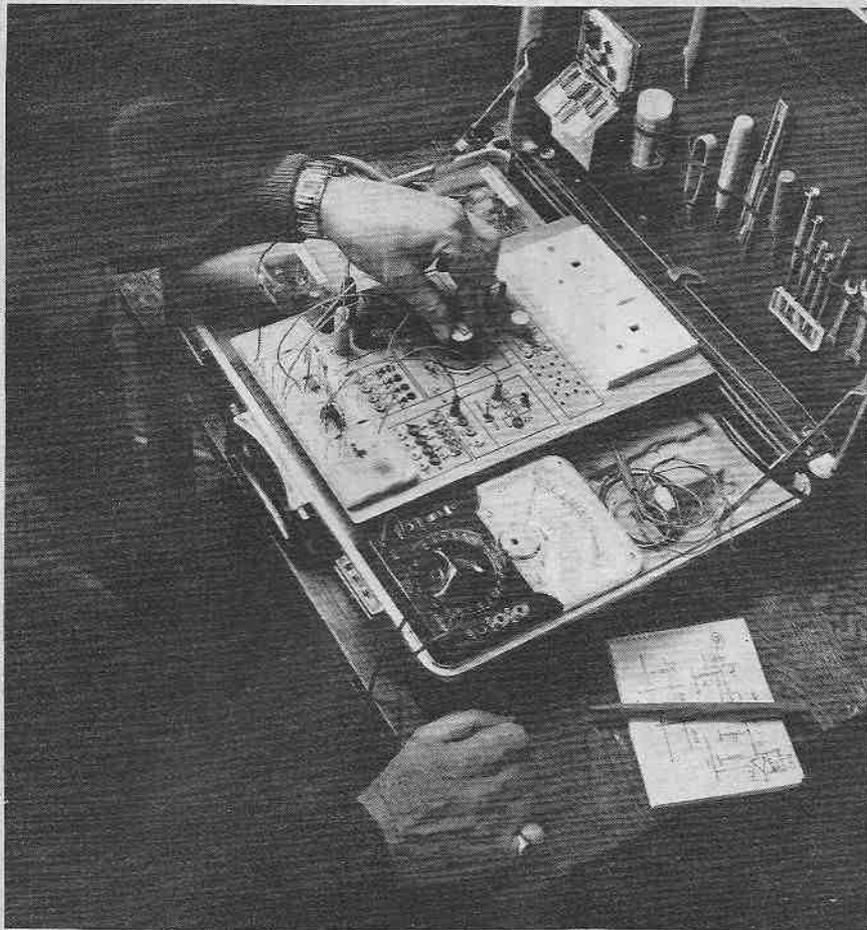

## PART 2

By R. W. Coles  
and B. Cullen

**T**HE use of a printed circuit board makes the assembly of Labcentre quite straightforward. The circuit board used carries all of the active components, including the voltage regulators, and the only wiring which must be carried out by hand is the connection of front panel controls and the mains transformer connections.

The mains and transformer wiring requires attention to safety precautions for obvious reasons, but is otherwise quite straightforward. The front panel wiring on the other hand, is quite complex because of the sheer number of connections required. It is

therefore necessary to take particular care over these interconnections so as to avoid mistakes and also to produce a neat appearance.

The wiring should be formed into looms, either by using traditional techniques (knotted looming string as employed in the prototype), or the now popular plastic ties or Spiralwrap.

Three versions of the Labcentre prototype have been built during development, and virtually no trouble has been experienced with leakage and/or crosstalk in the front panel wiring. Even so, it is advisable to be on the lookout for this sort of effect

when your own wiring looms have been assembled.

A cure for any loom-induced crosstalk of instability can probably be effected by altering the routing of any sensitive wires. It is expected that the wiring to the Audio Amplifier and the Function Generator to be most at risk from this sort of problem, although in the prototypes no re-arrangement of loom connections or recourse to screened wire was ever found to be necessary.

Construction of the case and other hardware may be easy or difficult, depending on your own facilities and expertise. Every effort has been made to keep case construction as simple as possible, where this has been consistent with the production of a professional looking and versatile piece of laboratory equipment. Some further simplification can optionally be achieved by those with limited facilities, by dispensing with the component drawer in the main console.

The appearance of the prototype has attracted a good deal of favourable comment, and it is therefore felt that the results achieved have fully justified the small degree of extra care required during the painting and labelling of the front panel.

### PRINTED CIRCUIT BOARD

All the principal components of Labcentre apart from the mains transformers and front panel controls, are mounted on a single Fibreglass printed circuit board measuring 12cm by 22cm. A full-size master pattern is shown in Fig. 2.1. The black regions are the copper areas to remain after etching.

For those not wishing to become involved in the manufacture of the board, this is available ready made, roller tinned and drilled from C. C. Consultants, whose address appeared in *Shop Talk* last month.

It can also be produced at home by readers with the proper facilities. The circuit board layout requires the accurate registration of several integrated circuit packages and the drilling of a large number of holes of three different sizes and therefore home production cannot be recommended for beginners in this field.

For those who are past-masters at the gentle art of board-etch, or those who feel that they can economise with a home-brew board, the following instructions are offered as a guide.

- (1) Use Fibreglass board of good quality, s.r.b.p. is not suitable.
- (2) Adhere to the published layout and the track widths as shown.
- (3) Don't try to lay out your board using only an etch resist pen or a paint brush.
- (4) Use etch resist transfers (or a photographic technique if you have the facilities).

If you can comply with the above requirements, then you are ready to start.

### MAKING THE P.C.B.

Cut your copper-clad Fibreglass board to size and trim the edges. After cleaning the board well to remove dirt and grease, use the master as a guide to mark some critical registration points on the copper using the point of a pair of compasses or a similar implement. By critical registration points we mean, for example, the corner pins of an i.c. package or the mounting holes for the regulators. Readers should use their own judgement as to how many such points should be used, possibly all hole positions.

Points can be marked all at once, or a fraction of the board can be done and transfers applied, before moving on.

The next step is to apply the transfers, and here a great deal of care is necessary. It should be possible to lay out the complete board using only five sheets of transfers. You will need one sheet of 16-pin d.i.l. pads, two sheets of circular pads (in two sizes) and two sheets of circuit tracks (in two widths).

The larger track widths and the large copper areas can be filled in with an etch resist pen after the transfers have been applied.

There are now several types of etch resistant transfers on the market and most of these would be suitable.

### ETCHING

The board is now ready for the etch bath, and a suitable solution should be prepared from ferric chloride crystals, following the suppliers instructions. A glass or plastic tray can be used for the bath, and the board should be left in the solution, with occasional agitation, until all the exposed copper has been removed.

When the etch is complete, the board should be carefully removed from the bath using tweezers and sluiced with cold water to remove any remaining ferric chloride solution. The transfers and ink-resist can be removed with wire wool or a household abrasive cleaner to reveal the bright copper underneath. We find it a good idea at this stage to coat the board with an aerosol cleaning fluid such as WD40. A coating of this sort helps prevent surface tarnish and makes soldering easier later.

Drilling the board is a tedious job if you don't have access to a printed circuit board drilling machine, but it *must* be carried out with great care or you may find that your integrated circuit packages will not fit!

Remember, if you have any doubts about making the Labcentre printed


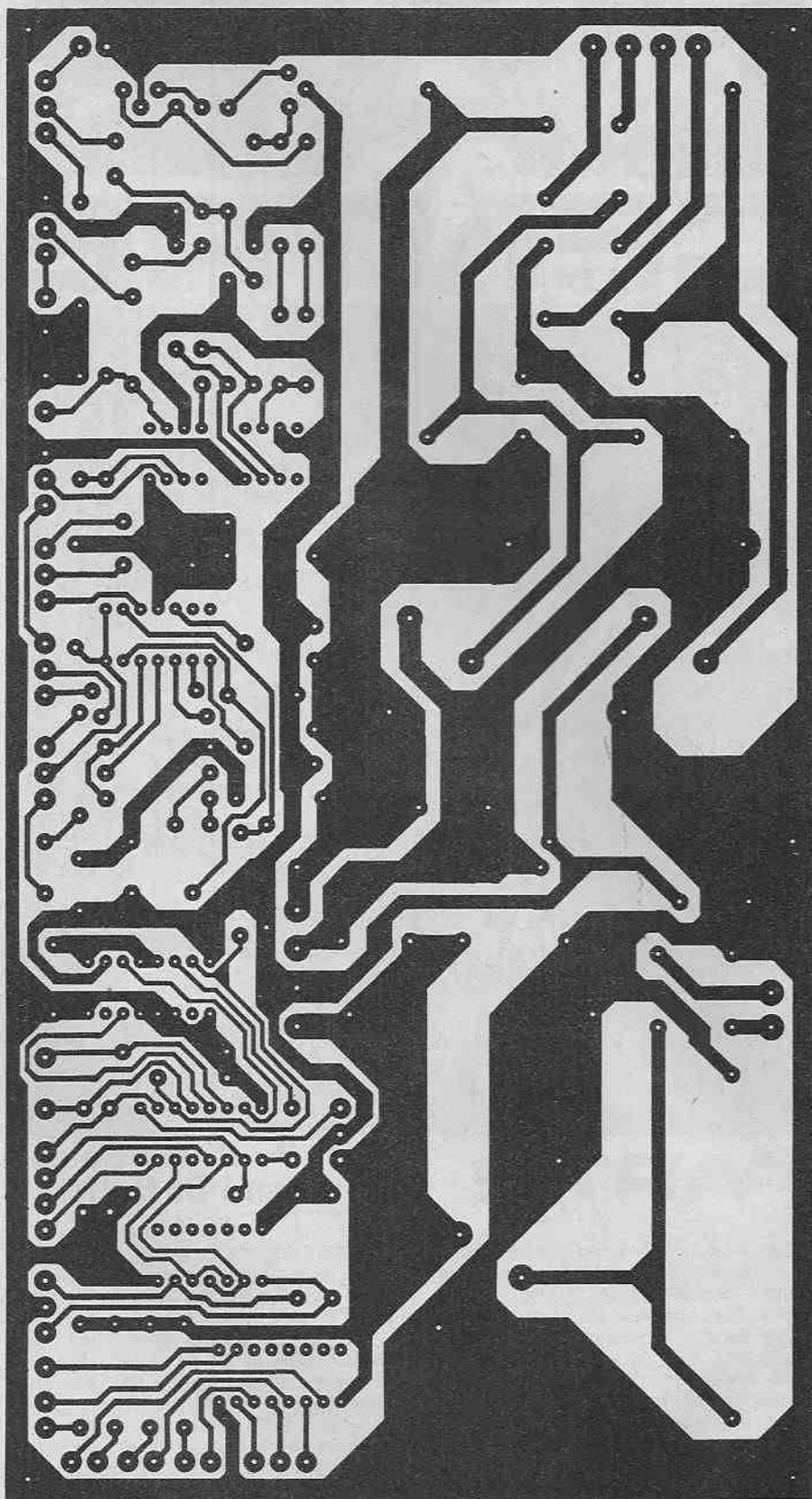
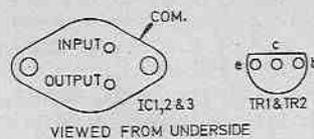


Fig. 2.1. The full-size master of the printed circuit pattern viewed from the copper side of the board. The black regions are the areas of copper to remain after etching.

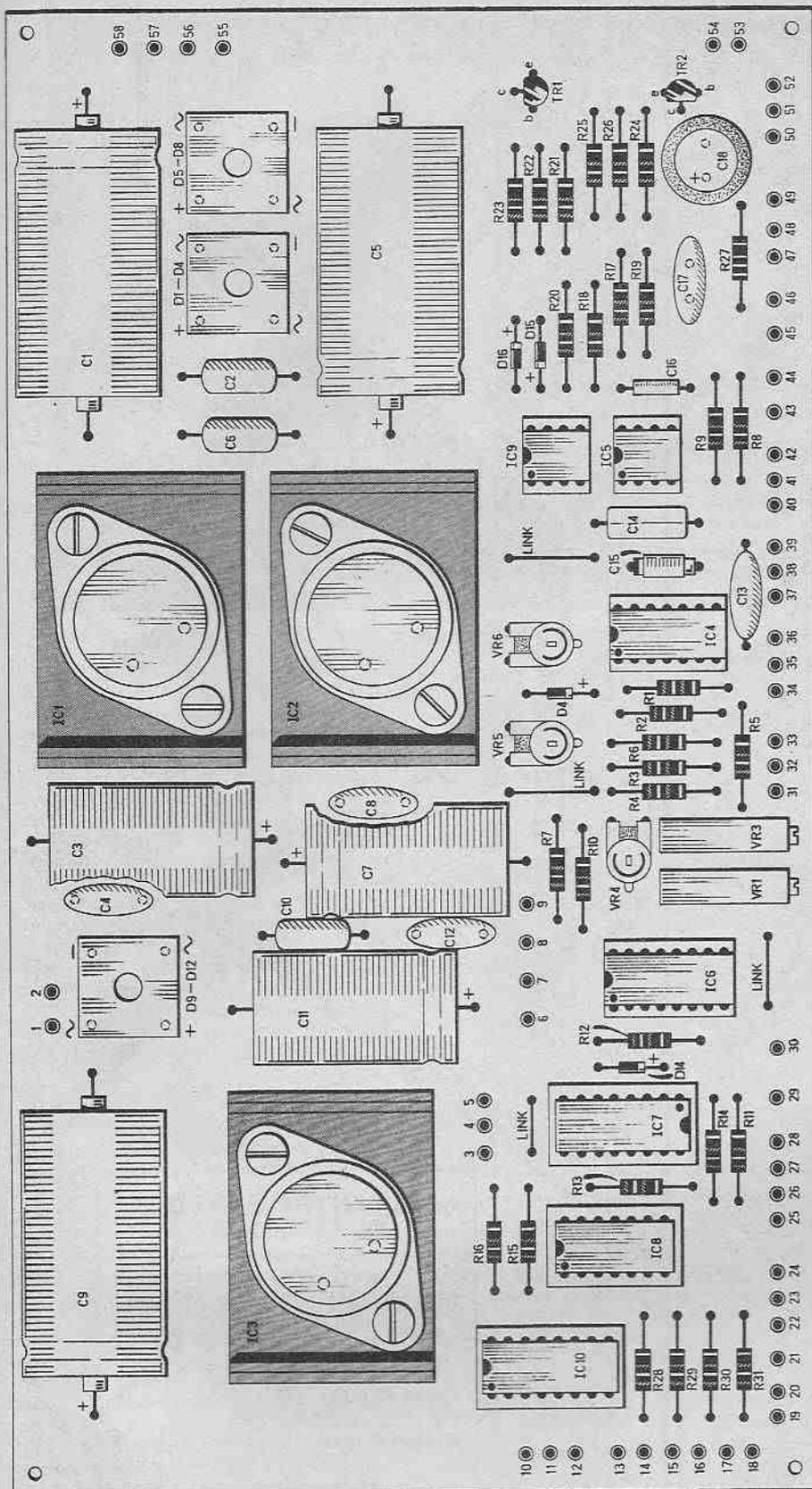

circuit board, it would be wise to purchase a ready made designer approved board. It could be cheaper in the long run!

### MOUNTING PCB COMPONENTS

Construction can begin in earnest with the assembly of the components on the completed p.c.b. The complete layout of the components on the board is shown in Fig. 2.2.

Begin by mounting the i.c. voltage regulators (IC1, 2 and 3) and their associated heatsinks. Care should be taken to ensure a good fit between the heatsink and the i.c. package, and the use of silicon grease or other thermal compound is highly recommended to ensure efficient heat transfer. No mica washers or insulating bushes are necessary, providing that the heatsinks do not touch each other. This is particularly important with IC1 and IC2, since their packages are at different potentials.

Care must be exercised when tightening the regulator securing bolts, to avoid cracking the circuit board. Nylon nuts and bolts could be used to advantage in this position.

### CONNECTING PINS

Terminal pins are best for "off-board" connections, because they make disconnection and reconnection easier if it ever becomes necessary. If you plan to use these pins, now is the time to solder them in. After the terminal pins, the power supply components, capacitors and bridge rectifiers and then the i.c. sockets can be soldered in. You don't have to use i.c. sockets of course, but once again we would strongly recommend their use because they make device replacement and test so easy. If you *don't* use sockets, leave the i.c.s until last anyway. When all the sockets have been soldered in, check very carefully between their pins to ensure that no "solder-bridges" have occurred.

Now you can apply all the smaller components, resistors first, followed by the wire links, capacitors, and pre-set potentiometers. You may experience some trouble with the leads of the skeleton presets being too large for the p.c.b. holes. This can be cured by suitably enlarging the holes or trimming the lead thickness with sharp wire cutters or a file.

The audio output transistors should be positioned very carefully in accordance with Fig. 2.2. The hole positions

Fig. 2.2 The layout of the components on the top side of the p.c.b. It is important that the heatsinks of IC1 and IC2 do not touch. All connections to the p.c.b. are made at terminal pins numbered 1 to 58. (Semiconductor pin-details are shown top right.)

may seem awkward, depending on the type of transistor package you use, and so confirmation from the layout diagram and/or the circuit diagram should be sought.

At this point the board should be checked very carefully for inadvertent short circuits and open circuits, and also for correct component orientation. It is quite safe to plug the integrated circuits into their sockets, but care must be exercised with the CMOS logic parts to avoid damage from static discharge. Safety is assured if:

- (1) You do not work in an area with nylon carpets.
- (2) You keep the CMOS devices on their conductive foam or foil until the last minute.
- (3) You make sure you, the circuit board and the CMOS circuits are all at the same potential by doing your assembly on an earthed metal, or other conductive surface. (A large baking sheet or roasting tin is ideal!)
- (4) You keep i.c. handling to an absolute minimum.

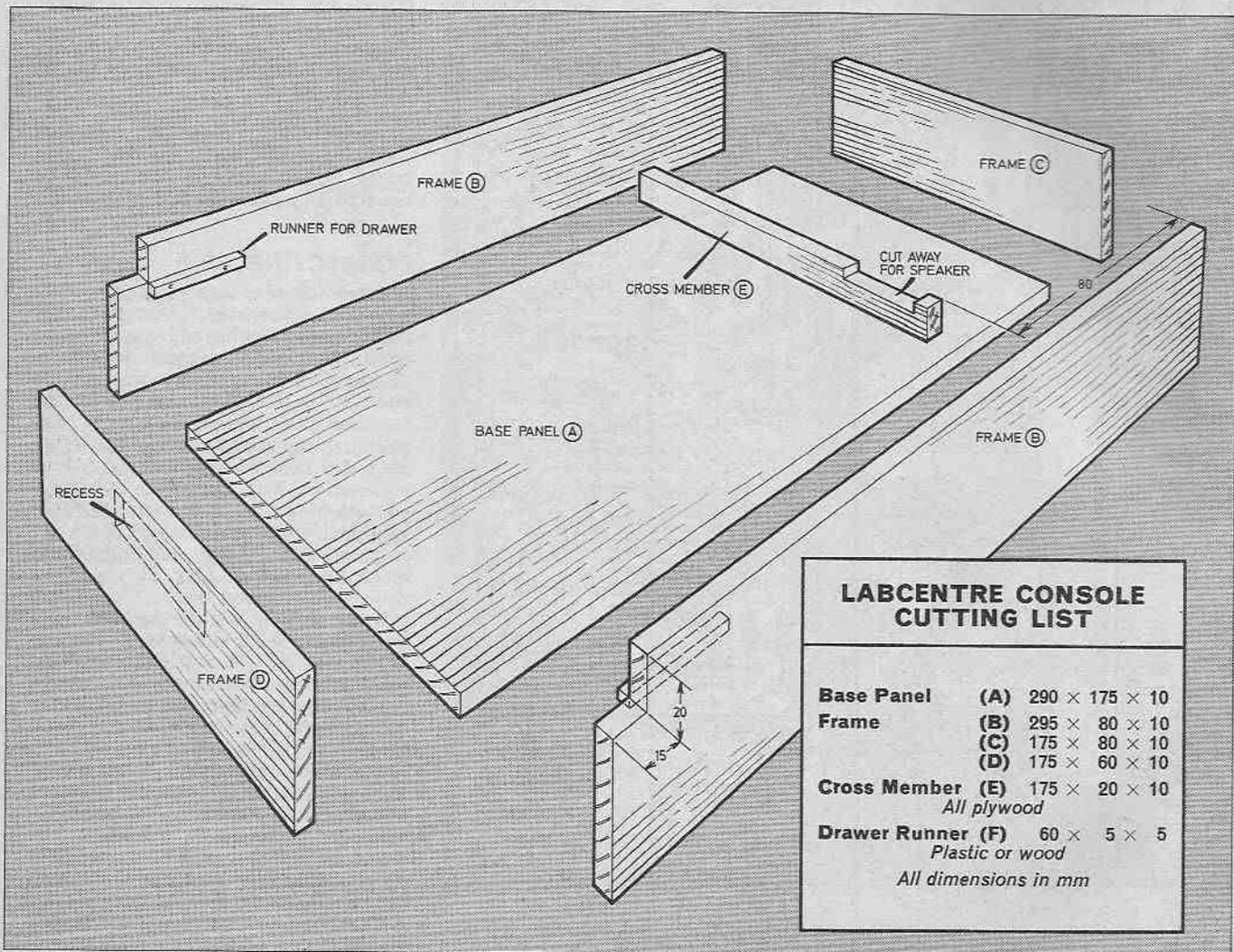


Fig. 2.3. Exploded view of the woodwork construction of the Console with a component drawer.

(5) If you are soldering your i.c.s in directly, you must remember to discharge your soldering iron bit to the conductive surface before each joint.

Following the above procedures will guarantee success, but CMOS devices are not as fragile as they sound, so don't assume you have ruined an i.c. just because you accidentally break one or more of the rules, chances are you will get away with it! But who wants to risk valuable i.c.s?

When assembly is complete, the board can be set aside. If you can't wait it is possible to test the board at this stage, with the aid of external d.c. supplies and a temporary control hook-up. You will need two unregulated 20 volt a.c. or d.c. supplies, which can be connected (either way round) to the a.c. terminals on the bridge rectifiers D1 to D4 and D5 to D8 and a similar 10 volt a.c. or d.c. supply to connect to the a.c. terminals on D9 to D12 (again, either way round).

### CONSOLE CONSTRUCTION

The next stage of construction concerns the frame which forms the sides of the console. Cut all pieces as accurately as possible to the dimensions given in Fig. 2.3, keeping the edges square and sanding to a smooth finish. The side frame should be pinned and glued using a woodworking adhesive such as Resin-W, keeping the assembly square.

When the sides have dried properly, use the *inside* edges of the frame as a template to mark out the base. Cut the base to size and sand to a smooth finish, then drill the four screw holes in the two longer sides of the frame. These will be used to secure the base to the sides.

The finishing and attachment of the cross member should be left until the front panel has been cut to size.

### FRONT PANEL

The overall size and drilling details of the front panel are shown in Fig. 2.4. Scribe out the shape of the front panel and the hole drilling centres on a sheet of 1.5mm aluminium and then cut this out with a nibbling tool such as Goscut or metalwork shears. At this stage the panel/frame fixing holes can be drilled and the panel screwed to the frame before final filing and sanding to achieve a perfect fit. Next remove the front panel and carry out the drilling for the terminals and controls. The larger cut-outs can be made with further use of the nibbling tool or by drilling multiple holes around the edges and then filing smooth and to size. It is advisable to ensure that all your front panel components are compatible with the given layout *before* drilling takes place because there is room for manoeuvre,

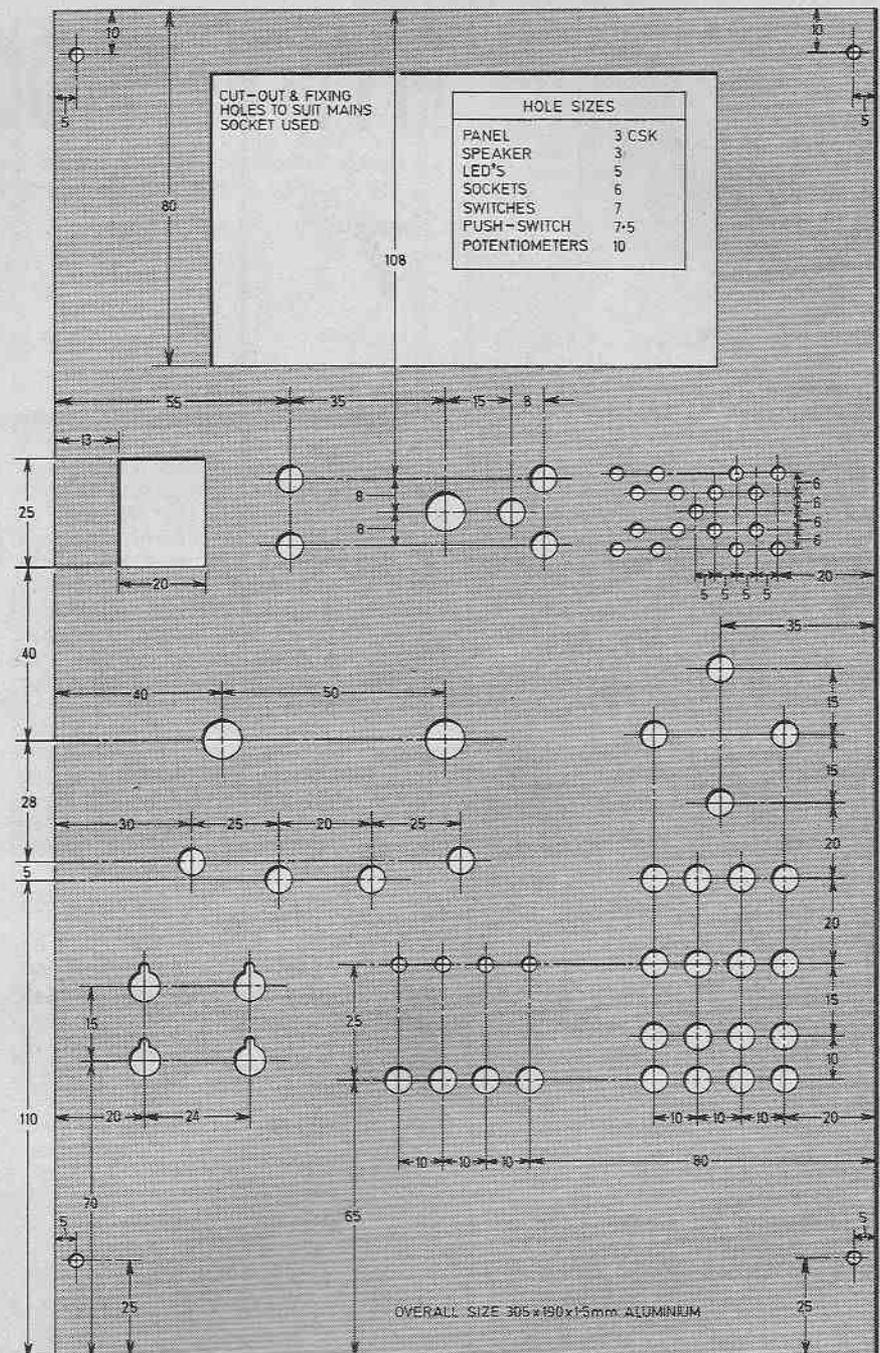


Fig. 2.4 Complete drilling details for the top panel of the Console. Dimensions in mm.

and non-specified components can be used if the panel layout is re-designed before drilling. In any event, hole sizes should be checked for compatibility, even if your components are superficially the same as those on the prototype.

### CROSS MEMBER

With the front panel holes and cut-outs complete, the twin 13 amp switched socket and the rocker switch should be temporarily fitted and the assembly used as a guide to fit the cross-member into the plywood console. It should be mounted as close as

possible to the 13 amp socket, for which it acts as a support.

With the cross member properly located, it can be pinned and glued into position between the two console long side pieces. The case is now substantially complete, requiring only the construction of the component drawer, which will be described later.

This drawer is intended to be lined with conductive foam and used to house integrated circuits, but it can be left out of the design if not required, provided that its absence is taken into account before console construction is started.


**To be continued**

# MINI-MODULES By George Hylton

Handy "Beginner" projects based on simple circuits and featuring a variety of building methods.

## 7

# TRANSISTOR TESTER

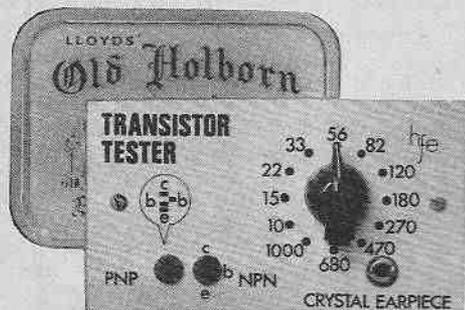

THE MAJORITY of simple transistor testers are very sensitive to variations in battery voltage. For example, a tester designed to operate from 9V will usually read low by at least 33 per cent if the battery voltage falls to 6V. Some testers require individual calibration. Some use expensive meters.

The present tester is simple, cheap and within its limits accurate. It needs no calibration and it is relatively insensitive to battery voltage variations. It measures the transistor parameter known as the small-signal current amplification factor or the forward current transfer factor and usually represented by the symbol  $h_{fe}$ . (This is generally about 20 per cent greater than the large-signal or "d.c." amplification factor,  $h_{FE}$ .)

### PRINCIPLE

The transistor under test (either *npn* or *pnp* as in Fig.1) is placed in a positive feedback circuit. The feedback is varied by switching in different resistances using S1 until the circuit just oscillates. The current amplification  $h_{fe}$  can then be read off the switch setting, within limits.

A selection of twelve feedback resistances gives twelve bands of current amplification. These bands are narrow enough (30 per cent each side of the middle-of-the-band value) to give a useful indication of  $h_{fe}$  without the need for individual calibration. The overall range of  $h_{fe}$  covered is 10 to 1,000, which spans practically the entire range of practical transistor gains.

The tester deals with both silicon and germanium bipolar transistors, *npn* or *pnp*. Tests are made at a collector current of about 1mA and a collector voltage of about 3V.

### CIRCUIT OPERATION

Transistor TR1 is a common-base a.c. amplifier with a current gain of almost exactly one. All the effective current amplification in the circuit must come from the transistor under test. This is connected as an emitter follower with a current gain of  $h_{fe} + 1$ .

The a.c. output of this transistor is fed to the emitter of TR1 and appears virtually unchanged in strength at TR1 collector. The current therefore divides between TR1 load resistance, R1+R2 and whichever range resistance is in circuit. The portion which flows through the range resistance forms the base current of the test transistor and if large enough keeps the oscillation going.

If the range resistance is just low enough to permit oscillation the current gain of the test transistor is the range resistance divided by R2. Since R2 is 1k $\Omega$  this means that  $h_{fe}$  is given by the number of kilohms in the range resistance; for example, for a range resistance of about 100k $\Omega$   $h_{fe} = 100$ , and so on.

Simple theory says that R1+R2 should add up to 1k $\Omega$  but various factors conspire to make the circuit "read low" and R1 is added to compensate for these. (It is ignored in calibrating the tester.) The "+1" part of the gain of the emitter follower

conveniently disappears because it just compensates for the loading of R1+R2 by the range resistances.


### CONSTRUCTION

This project provided the opportunity of trying out an inexpensive plastic box which was seen at last year's Breadboard exhibition. This was described as a "potting box" and is a square, lidless box with two projecting rounded flanges which can be used as fixing brackets for a homemade Formica panel.

The particular "potting box" used for this project is larger than some other types and measures approximately 83x63x45mm. The depth of this particular size is useful for housing the range switch S1.

In practice the resistors were not attached to the switch tags like the spokes of a wheel, as shown for clarity in the diagram of Fig.2 but positioned vertically above the wafer. This reduces sideways spread and enables the common ends of the re-

Fig. 1. Circuit diagram of the Transistor Tester.

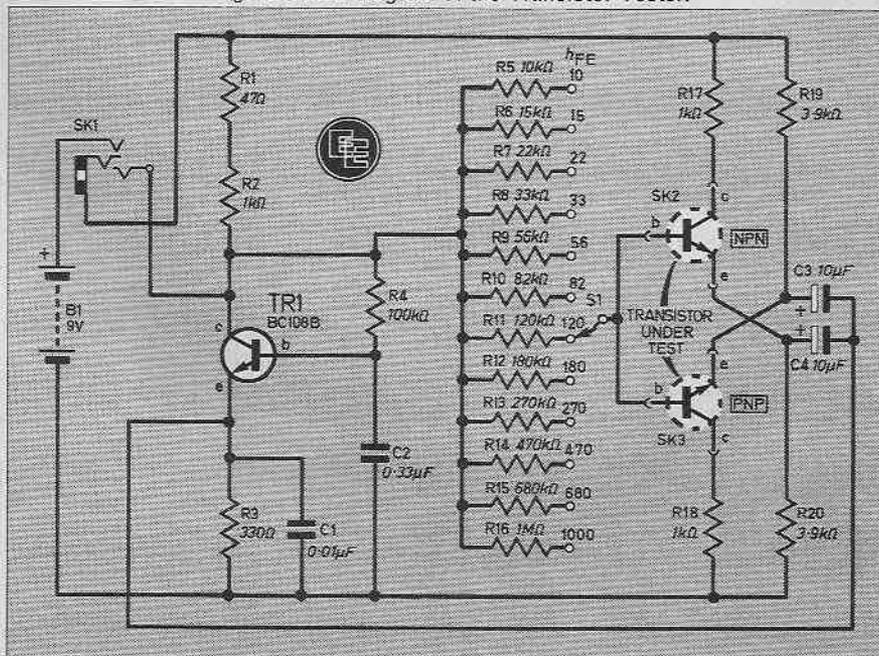

sistors to have their leads interconnected by twisting them all together and soldering instead of using separate linking conductors.

By using the usual small  $\frac{1}{4}$ W or  $\frac{1}{2}$ W resistors and keeping the leads short the overall depth can be fitted into the box. (Note. Solder the connection to the central tag before attaching the resistors.)

It is an advantage to mount all the circuitry on the back of the panel and so avoid connections between panel and "inside". To achieve the required compactness the circuitry around the transistor TR1 was assembled on a small piece of 0.15 inch matrix stripboard having nine strips by 11 holes. The finished board is held in place by its connecting leads.

## SOCKETS

The jack socket SK1 for the crystal earpiece is also used to switch on the circuit when the plug is inserted. Many commercial jacks are equipped with "break" contacts rather than the required "make" contact but can generally be modified by bending the contact strips to the necessary shape.

At least two transistor sockets are needed, one for *npn* (SK2) and the other (SK3) for *mpn* transistors. The Eagle TS10 socket used in the prototype has three contacts arranged like the most common small metal-cased transistors (TO-5 or TO-18 case with their lugs near the emitter lead-out) plus an extra contact near the middle. By connecting this extra contact to the one which takes the base lead-out the socket takes some plastic transistors with in-line lead-outs and base in the middle.

Other types of small transistor with different lead-out configurations can usually be made to fit by bending their leads.

It is of course in order to add extra transistor holders wired for other lead-out configurations if desired. The base contacts are commoned with the existing holders and collector contacts of like polarity connected together, similarly emitter contacts of like polarity.

## USING THE TESTER

Plug the transistor under test into the appropriate socket. Plug in the crystal earphone, it must be crystal: a magnetic earphone will not work. Turn S1 until a position is found where the oscillation just stops. The range marking indicates the upper limit of  $h_{fe}$ . The next lowest range where oscillation just starts, gives the lower limit. So if the circuit oscillates on "120" but not on "180"  $h_{fe}$  lies in the range 120 to 180.

If no oscillation is obtained either

## COMPONENTS

### Resistors

R1 47 $\Omega$	R11 120k $\Omega$
R2 1k $\Omega$	R12 180k $\Omega$
R3 330 $\Omega$	R13 270k $\Omega$
R4 100k $\Omega$	R14 470k $\Omega$
R5 10k $\Omega$	R15 680k $\Omega$
R6 15k $\Omega$	R16 1M $\Omega$
R7 22k $\Omega$	R17 1k $\Omega$
R8 33k $\Omega$	R18 1k $\Omega$
R9 56k $\Omega$	R19 3.9k $\Omega$
R10 82k $\Omega$	R20 3.9k $\Omega$

All  $\frac{1}{4}$ W carbon  $\pm 5\%$ , except R2 which is  $\pm 2\%$

### Capacitors

C1 0.01 $\mu$ F polyester
C2 0.33 $\mu$ F polyester
C3 10 $\mu$ F 10V elect.
C4 10 $\mu$ F 10V elect.

### Semiconductor

TR1 BC108B silicon *npn*

### Miscellaneous

S1 1 pole 12 way rotary switch
SK1 3.5mm jack socket
SK2,3 Small transistor holders
(2 off, see text)
B1 9V PP3 battery

Stripboard, 0.15 inch matrix 9 strips by 11 holes; plastic "potting" box, 83 x 63 x 43mm (see text); Formica panel 120 x 75mm; screws for fixing panel; one pointer knob; battery connector to suit B1; crystal earpiece with 3.5mm plug.

the transistor is a dud or of very low gain or is incorrectly connected. Protection resistors are included in the circuit to prevent damage from incorrect connection. An "unknown

quantity" transistor can be tried in different positions and polarities to establish its polarity and lead-out connections.

Some transistors oscillate when the collector and emitter connections are reversed; that is they work in two positions. In this case the position which gives the higher gain is the correct one.

## CONTINUOUS CALIBRATION

The tester relies on resistor tolerances for its accuracy. Even with the worst possible combination of high-limit and low-limit resistors  $h_{fe}$  should still be indicated within 35 per cent, which is a lot less than most manufacturing tolerances.

For some purposes (such as matching) a continuous adjustment of the range resistance is preferable to switched steps. This can be arranged (at the cost of having to calibrate a variable resistance) by substituting for the switched range resistors a 1 megohm carbon track potentiometer connected as a variable resistance.

For covering a wide range of  $h_{fe}$  a log. law or inverse log. law potentiometer is best, despite its erratic calibration. For a narrower range such as 11 to 1,000, a linear potentiometer may be used to cover the entire range of  $h_{fe}$  but it will not be accurately readable at the low end.

The principle of improving discrimination by restricting the range can also be applied to the circuit with S1. If an overall coverage of 100 to 820 were acceptable the twelve resistances could then be 100k $\Omega$  through to 820k $\Omega$  as in the standard "E12" series, giving 20 per cent (that is 10 per cent each side of nominal mid-range value) increments.

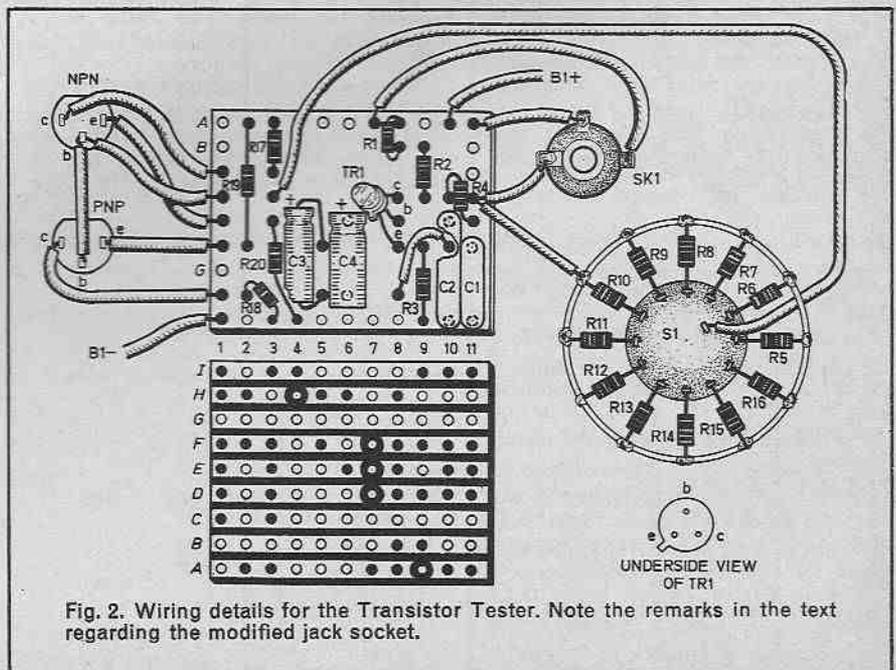


Fig. 2. Wiring details for the Transistor Tester. Note the remarks in the text regarding the modified jack socket.

# SQUARE one

## FOR BEGINNERS

**E**LECTRONIC components are manufactured in all sorts of different shapes sizes and colours and each marked with a type number, and where applicable, values.

Components marked with values include resistors, capacitors, inductors, potentiometers, Zener diodes.

These markings are either alpha-numerically printed on the body or "colour coded", the latter usually appearing as coloured bands or dots.


### RESISTORS

A typical colour-coded resistor is shown in Fig. 1. You will note there are four bands (sometimes a pink, fifth band is included to indicate a high-stability resistor) displaced towards one end of the body. A table for "decoding" these bands appear in Table 1.

Begin decoding with the band nearest to the body end.

The first band gives the most significant digit of the value, with the second band producing the next most significant digit. The third band tells you the factor with which to multiply the first two digits to obtain the nominal value in ohms.

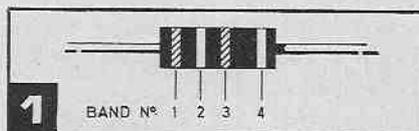The fourth (and last) band provides information regarding the tolerance about the nominal value. This is a percentage figure and tells you the maximum difference to expect from the nominal value.



For example, a resistor coded RED, VIOLET, YELLOW, GOLD, has a value of  $27 \times 10^4$  ohms  $\pm 5$  per cent. For those unfamiliar with index notation,  $10^4$  is the same as 10,000, so the resistor value is 270,000 ohms abbreviated usually to 270 kilohms (270k $\Omega$ ). As can be seen, a number of zeros equal to the power of ten (in our example—four) is written after the first two digits.

The absence of a fourth band means that the tolerance is  $\pm 20$  per cent.

### CAPACITORS


Non-electrolytic capacitors, in particular the Mullard C280 series, are also colour-coded and may be decoded by using Table 1. See Fig. 2 for C280 banding system.

Band 1 is the band farthest from the leads working through to band 5 nearest the leads. The value is in picofarads, pF ( $10^{-12}$  farads or  $1 \div 1,000,000,000,000$  farads).

For some C280 values e.g., 0.22 $\mu$ F, 0.033 $\mu$ F, at first sight it will appear that there are only four bands and sometimes only three. This is due to neighbouring bands being of the same


colour, but this is soon apparent from the width of the bands.

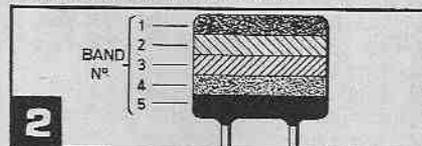Unlike resistors, capacitors have a fifth band which informs the user of the maximum a.c. voltage that may be applied before destruction or breakdown of the device occurs.



For example, a C280 capacitor with band colours (from top) reading YELLOW, VIOLET, ORANGE, BLACK, RED, has a value of  $47 \times 10^3$  pF  $\pm 20\%$  250V;  $47 \times 10^3$  pF = 47,000 pF which is more usually written as 0.047 $\mu$ F (microfarads).

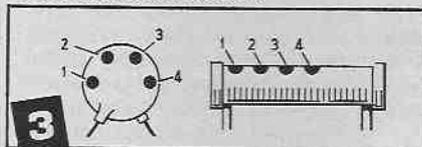Older types of ceramic disc and tubular capacitors are dot coded as shown in Fig. 3 and are decoded by Table 1, second section.



### TANTALUM CAPACITORS

Some tantalum bead capacitors use a colour code system, see Fig. 4. There are in fact two similar systems although that at (a) is more common. The code unit is microfarads ( $\mu$ F) and the working voltage in volts (V).

For example, a type (a) tantalum capacitor with zone coding: BLUE, GREY, WHITE, GREEN, has a value equal to 6.8 $\mu$ F 16V.

The tolerance of tantalum capacitors is usually  $\pm 20$  per cent.

Tantalum capacitors are polarised and must be connected in circuit the correct way round to avoid destruction.

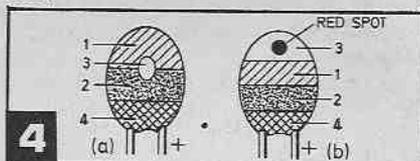


Table 1. Composite resistor and capacitor colour code "decoding" table.

Colour	Resistors (ohms $\Omega$ )				Capacitors (picofarads pF)					Tantalum Capacitors (microfarads $\mu$ F)			
	Band No.				Band No.					Zone			
	1	2	3	4	1	2	3	4	5	1	2	3	4
Black	—	0	1	—	—	0	1	20%	—	—	0	1	10V
Brown	1	1	10	1%	1	1	10	—	100V	1	1	10	—
Red	2	2	$10^2$	2%	2	2	$10^2$	—	250V	2	2	$10^2$	—
Orange	3	3	$10^3$	—	3	3	$10^3$	—	—	3	3	—	—
Yellow	4	4	$10^4$	—	4	4	$10^4$	—	400V	4	4	—	6.3V
Green	5	5	$10^5$	—	5	5	$10^5$	5%	—	5	5	—	16V
Blue	6	6	$10^6$	—	6	6	$10^6$	—	—	6	6	—	20V
Violet	7	7	$10^7$	—	7	7	$10^{-1}$	—	—	7	7	—	—
Grey	8	8	$10^8$	—	8	8	$10^{-2}$	—	—	8	8	$10^{-2}$	25V
White	9	9	$10^9$	—	9	9	—	10%	—	9	9	$10^{-1}$	3V
Gold	—	—	$10^{-1}$	5%	—	—	—	—	—	—	—	—	—
Silver	—	—	$10^{-2}$	10%	—	—	—	—	—	—	—	—	—
Pink	—	—	—	—	—	—	—	—	—	—	—	—	35V

# MICROPROCESSOR BASICS

## 2

By R. W. Coles

A MICROPROCESSOR system will consist of a microprocessor chip combined with a variety of other semiconductor components and some peripheral hardware (Fig. 2.1). The microprocessor itself forms the heart of the system, but to understand how it works, it is first necessary to take a brief look at the environment in which it operates, and the various "life-support" systems it requires.

Most fundamental of all perhaps, it needs a power supply. Voltages vary depending on the semiconductor technology used, but there is a definite trend towards a single 5 volt supply these days. Microprocessors *do* require V.I.P. treatment, and so their supplies should be well regulated and within a fraction of a volt of their data sheet needs. Running a micro' from your 'bike dynamo just isn't on I'm afraid!

### CRYSTAL CLOCK

Microprocessors are very time conscious, and do require a regular supply of "clock" pulses for proper operation. The actual frequency of the clock pulses varies from chip to chip, but a few MHz is common.

Because speed of operation is usually important, micro's are

clocked at frequencies near to their data sheet maximum, and that's one of the reasons why crystals are used to set the clock frequency. Resistor-capacitor networks just couldn't be relied upon for stability.

Another reason is that with use of a crystal clock, basic computer operations such as ADD always take a fixed time, and therefore by cascading the required number of simple operations it is possible to count down to say, seconds.

### RESET

The reset switch shown in Fig. 2.1 is there to symbolise the fact that a microprocessor chip *must* be started off at the *beginning* of its program (obvious really, isn't it?) Simple systems use a resistor/capacitor circuit to ensure that a reset operation is carried out when power is first applied, but evaluation cards let you reset the system whenever you like, by depressing a button. This is *very* useful when your programs go wrong (mine always do at first!).

### BUSES

Most of the microprocessor chip pins are dedicated to one of the three "buses".

The data-bus carries parallel binary data to and from the memory and peripherals. It is a *bi-directional* bus, and for most microprocessors it is eight bits "wide". (That is, to wire it up, you need eight wires!)

The address-bus is a unidirectional bus driven by the microprocessor itself, and it carries parallel binary information which represents the "address" of the unique location in memory with which the microprocessor wishes to communicate. The "width" of the address-bus determines the range of unique memory locations which can be addressed. A common width is sixteen bits, giving access to 65,536 ( $2^{16}$ ) separate locations, each of which may contain an eight-bit data value.

The control-bus is the name usually applied to the assorted control signals which are sent to, or received from, the memory and peripheral components of a system. Each individual control bus line will have its own specific significance, and examples are DBE (Data Bus Enable) and VMA (Valid Memory Access).

The nature of control-bus lines, and the control-bus width, varies from chip to chip, whereas the binary symmetry of the data and address buses is a standard feature of most microprocessor chips.

### MEMORY

Memory is an essential part of any microprocessor system, it holds not only the data to be operated on, but also the program which tells the micro' *what* operations it must carry out.

Sometimes data and programs are segregated into Read/Write memory and Read Only Memory respectively, but this isn't necessarily so, since data can be stored in ROM and programs in RAM (RAM is a rather unfortunate shorthand for Read/Write Memory), where this is useful.

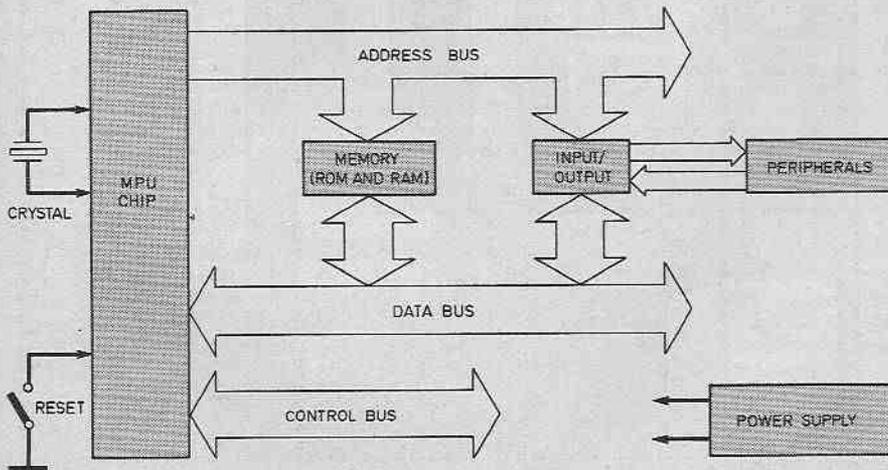


Fig. 2.1. A simple microprocessor system.

We will be examining memory devices in more detail in future articles, but for the moment just think of this important system resource as a series of pigeon holes, each of which has its own binary reference number, or address, and the ability to store one *word*, (a word is a parallel collection of bits) of either data or program instructions.

## INPUT/OUTPUT

The last system ingredient we need to consider is what I have called, in Fig. 2.1, Input/Output. Obviously a microprocessor which is unable to communicate with the outside world is worse than useless. Inputs and Outputs in the form of switch closures, keyboard data, lights and printed text, are the bread and butter of most systems. They are also the only way the microprocessor has of receiving instructions and delivering the results to its human masters!

Input and Output circuitry comes in many shapes and sizes, some very simple (eight toggle switches or eight lamps for example) and some quite complicated (an interface for a printer or a tape cassette for example).

Once again, we will be examining I/O as it is called in future articles and in more depth. But now, back to the *Prima Donna* of the system, the microprocessor chip itself!

## THE MICRO' CHIP

To start with, let's zoom in on a microprocessor. First, we see a plastic or ceramic dual-in-line package; it has forty pins and is 0.6 inches wide and about two inches long. The pins are actually the visible part of a gold-plated "lead-frame" which appears on closer inspection to radiate from the very centre of the package.

At the focus of this golden tracery is an almost insignificant sliver of a shiny metallic material. Closer still we can see that this sliver is roughly square in shape, measures about 0.25 inch on each side and is connected to the lead-frame via square pads around its periphery and spidery links made of fine gold wire.

Through a magnifying lense, we can see that the surface of this sliver, now revealed as the silicon chip itself, is criss-crossed with an aluminium interconnection pattern

of breathtaking complexity! At this point the information that there are more than 5,000 individual transistors on the chip seems to have the ring of truth.

Further study reveals that the interconnection pattern forms regular geometric arrays on certain areas of the chip's surface. These multi-transistor arrays obviously form the separate functional blocks which go to make up the complete microprocessor. But what blocks are required and what do they do? At this point our eyes fail us. Only the chip makers themselves can recognise the purpose of an integrated array by its appearance, we must content ourselves with a simpler model!

## A FUNCTIONAL MODEL

The block diagram Fig. 2.2 shows, in simplified form, the sort of circuit blocks which are integrated on to a single silicon semiconductor chip to form a microprocessor. This is of course a functional *model* of a microprocessor chip; it says nothing about the relative complexity of each block, nor does it fully describe the necessary block interconnections.

The internal data bus used in this diagram can be considered to be an "everything" bus, which, for our convenience, can carry binary data of any necessary word length, in any direction. In the microprocessor chip itself the designers have to provide a whole collection of buses to achieve the same result!

## TIMING AND CONTROL

On the left of the diagram is the important Timing and Control section which produces all necessary internal and external control signals together with clock or strobe pulses to ensure that all parts of the system act in synchronism. Exactly which control signals are produced is determined by

- (a) A fixed time sequence
- (b) The Control bus inputs and
- (c) The contents of the Instruction register.

By feeding the instruction register with a regular diet of new binary words, *Instruction* words in fact, we can control the resources within the microprocessor chip, and hence the entire system, in a sequential fashion.

A sequence of instruction words is normally called a program, and this can be held outside the microprocessor chip in RAM or ROM, as discussed earlier.

To get instructions from the memory and into the Instruction register, the Timing/Control section of the microprocessor generates a sequence of control signals to implement what is known as an "Instruction-cycle."

The first part of an instruction cycle is called a "Fetch", because during this period an instruction word is "fetched" from memory.

The second part of the cycle is referred to as an "Execute", because during this period the control signals generated depend on the nature of the instruction which

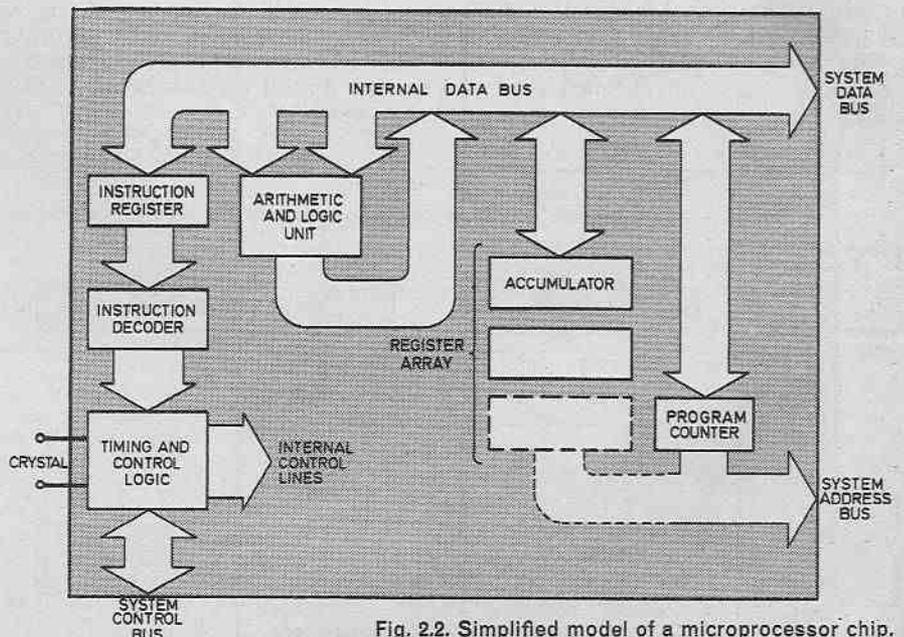


Fig. 2.2. Simplified model of a microprocessor chip.

## MICROPROFILE: THE NATIONAL SC/MP

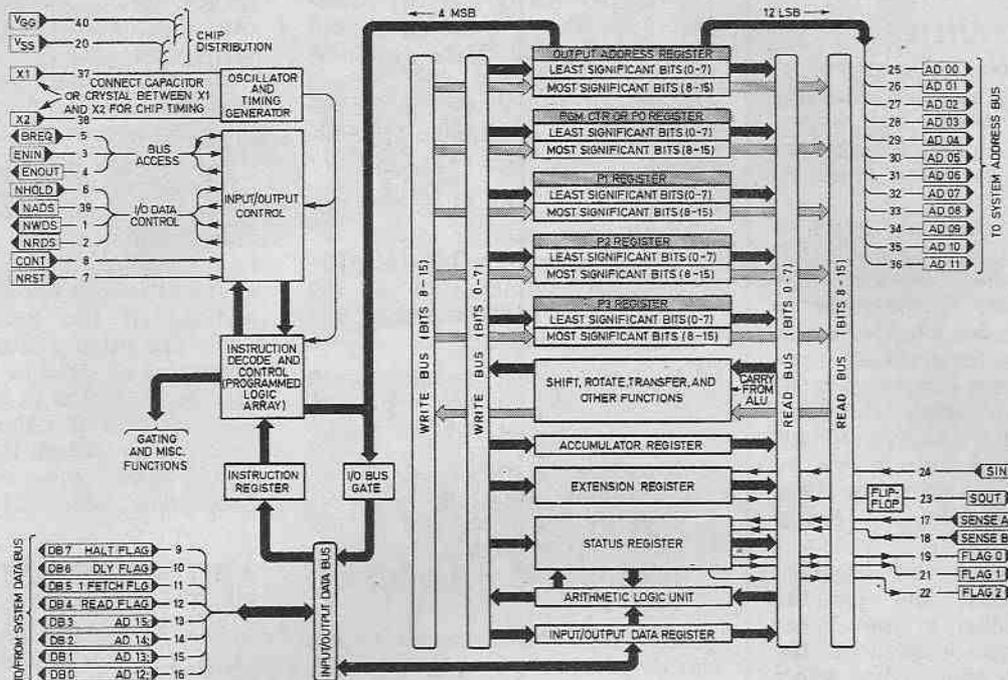


Fig. 2.3. Block diagram of the National SC/MP microprocessor.


The SC/MP microprocessor is a fairly simple eight-bit device, intended mainly for controller type applications. It was originally fabricated using the cheaper PMOS technology, but is now made in NMOS which means it can operate from 5 volt supplies and is faster too. The chip has proved popular with microprocessor hobbyists because of its ease of use and low cost, and it is currently used in the Bywood "SCRUMPI" kits and in the Science of Cambridge MK14, see photo.

One nice feature of the SC/MP is the provision of an on-chip clock oscillator, so that only a crystal is needed externally. One major problem is that the address bus is only 12 bits wide and can therefore directly address only 4096 ( $2^{12}$ ) memory locations. Another four bits is sent out on the data bus during strobe time, but this extension to 16 bits is not incremented automatically and has to be deliberately changed by program instructions. This in effect splits the 64K ( $K=1024$ ) memory space up into 16 4K "pages", where the current page number has to be selected by the programmer.

The chip has one eight-bit accumulator and also has the rather unusual feature of an extension register, which among other things is used to implement a serial (bit by bit rather than word by word) input/output channel. Serial I/O is used for things like teletypes and cassette storage, so having this facility available on chip can save a lot of external hardware.

Four 16-bit registers are provided (called "pointers" by National because they can be used to hold a value which points to an address in memory), and one of these is used as the program counter. The remaining three pointers can also be used to hold two data words, rather than a single 16-bit address, because each eight-bit register half is separately accessible.

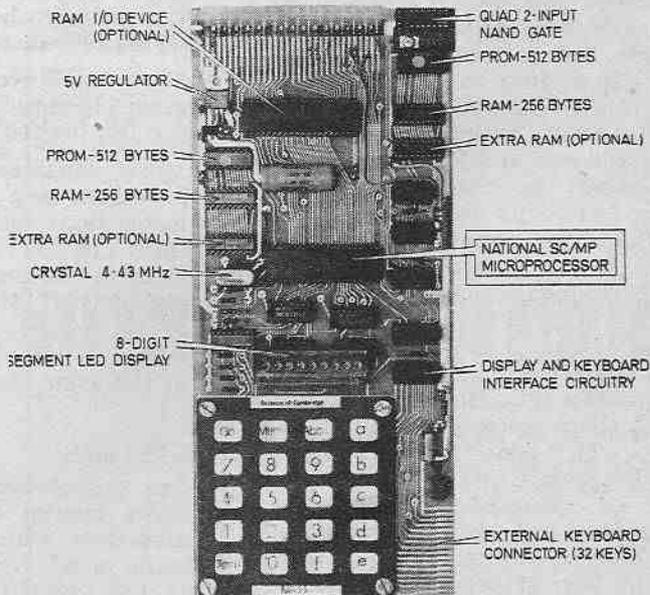The instruction set of this microprocessor is rather basic in comparison to other eight-bit chips, but this can be an advantage for beginners who find it easier to learn!



One unusual and useful feature is a DELAY instruction which causes the chip to pause for a time count which can be selected by the programmer. Accurate time periods can easily be generated with this instruction, provided that a crystal is used with the on-chip clock oscillator.

SC/MP is housed in a 40-pin d.i.l. package and is readily available from numerous advertisers. Remember that to build a system using any microprocessor you will need a number of other components such as memory and power supplies, so it may be advisable either to buy a kit, or to wait until you have read the rest of this series before committing any hard earned cash!

was fetched, so that the microprocessor can be made to carry out the wishes of the programmer.

## PROGRAM COUNTER

So far so good, the microprocessor can fetch instructions and even execute them. But where does it look for its instructions and how does it know what order to execute them in?

To take this step, we need to consider one more block in Fig. 2.2, the Program Counter. The Program Counter (P.C.) is a register which holds a binary word, rather like the Instruction register, but it has the extra facility of automatic incrementing or "counting" logic so that whatever binary number is loaded into it can be stepped up by a count of one after each operation of the Fetch-Execute cycle.

The contents of the Program Counter are sent out on the Address bus during the Fetch activity and are decoded in the memory circuits and used to select the location of the next instruction to be executed.

To start a microprocessor off on the right foot, a Reset signal must be applied to set up starting conditions. One of the things the Reset signal does is to clear the Program Counter to zero, and this means that program execution always starts at address zero and increments up through memory when left to its own devices.

What this means to us, the users, is that we must ensure that our first instruction is located at address zero, so that the microprocessor comes under *our* control immediately after Reset.

To add a little spice to programming, there are several instruction types which allow the contents of the Program Counter to be modified or replaced by the programmer, and these instructions can be used to force a "Jump" out of the normal sequential flow of instructions when necessary. We will see how useful this can be in later articles.

## CHIP RESOURCES

We can now get instruction words from memory and let them influence the generation of control signals, but we haven't seen them do anything particularly useful yet. What we need to look at next are the remaining chip resources

and how they can be made to do useful work.

What we have left in Fig. 2.2 are the Register Array and the Arithmetic and Logic Unit (ALU), and these are the key to the power of the microprocessor.

To do useful work, the microprocessor must be capable of carrying out instructions to:

- Manipulate data at the bit and word level,
- Carry out simple binary arithmetic operations such as the addition or subtraction of one word from another,
- Perform logical operations such as AND and OR on a pair of words, and last but not least,
- Test bits or words for certain conditions such as positive, negative, or zero, and to use the result of such a test to decide what part of a program to do next.

All of the above operations use one or more of the registers and the Arithmetic and Logic Unit. A register is a storage area which will hold one word of binary data. Registers differ from RAM locations (which also hold one word of binary data) because they are:

- More easily accessed by a program because they have a special, limited address range.
- More capable, because they have their own set of dedicated instructions which may allow them to be directly incremented, decremented, tested and shifted. (Memory data has to be loaded into a register before it can be manipulated in the same way.)

## REGISTERS

Most microprocessors have one or more special registers called accumulators, which are the most versatile of all. An accumulator is often the implied source of one operand in an instruction, and also the implied destination for the result. For example the instruction line:

ADD FRED

means "Add the contents of the main memory location known as FRED to the accumulator register, and store the result back into the accumulator."

The registers within a microprocessor chip can also be used to

form addresses for memory reference operations. In a microprocessor with an eight-bit word length, a pair of eight-bit registers can often be used together to form a 16-bit address.

In other cases special address registers called Index-registers are provided exclusively to hold and to step through, memory addresses.

The difference between general or Index registers being used to hold addresses and the Program Counter (which also holds an address) is that the P.C. holds the address of the next *instruction* while the other registers hold the addresses of *data* to be used during the execution of an instruction. The contents of either can appear on the address bus, the P.C. during Fetch and the other during Execute.

## ARITHMETIC AND LOGIC UNIT

The Arithmetic and Logic Unit (ALU) can be thought of as the "Engine Room" of the microprocessor because it contains a complex collection of logic circuitry to carry out the activities demanded by Arithmetic, Logical and Manipulative instructions, under the control of the Instruction Decoder.

In an eight-bit ALU there will be at least eight binary full adders, detection logic for zero, positive, or negative data values, Logic to shift bits right or left, logic to detect carry or borrow conditions, and lots more.


Associated with the ALU there is a special register used to hold the results of tests. The length of this register depends on the number of conditions which can be tested, because one bit is used to "flag" the result of each test.

All Flag Registers, as they are called, have one bit for arithmetic carry between words, and other bits can signal the arithmetic sign of an ALU result, the fact that the contents of an accumulator are zero, and so on.

Information on individual microprocessors can be found in their respective data sheets. They all have their strengths and weaknesses and often some strange idiosyncrasies! Why not have a look at the data on the National SC/MP chip and see if you can find all of its facilities, as I have described them?

To be continued
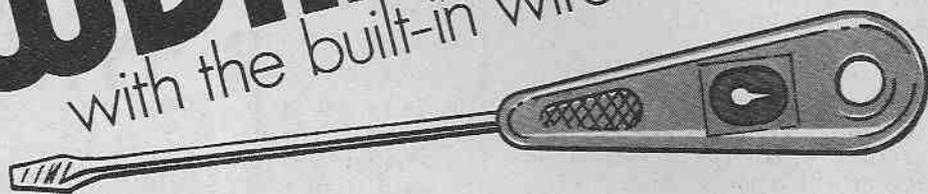
# FREE dual purpose tool SCREWDRIVER with the built-in wirestripper



## NEXT MONTH

OUR CONSTRUCTIONAL  
PROJECTS INCLUDE:

### ELECTRONIC DICE

Two independent counters and displays which can be operated separately or together. Thus suitable for games such as Monopoly and Backgammon as well as those requiring only one dice.

### S.W. CONVERTER

Simple 2-transistor converter which covers the popular Short Wave Broadcast Bands. Output is about 1-6MHz at the high end of the Medium Wave Band.

### XENON STROBE

Designed for a large disco hall, has brighter illumination than normal lamps. Can be used in other "strobe" applications, such as in the physics laboratory.

### INTRUDER ALARM

An effective protection system for the home. Uses a very simple circuit incorporating series and parallel loops. Mains powered with battery back-up and remote alarm facility.

PLUS ALL THE REGULAR FEATURES

# Everyday ELECTRONICS

**MAY**  
ISSUE ON SALE  
FRIDAY, APRIL 20  
Price 45p

# Everyday News



## TRAINING FOR THE FUTURE

Recognising the tremendous thirst for further knowledge on the understanding and practical applications of microprocessors Texas Instruments have opened a Microprocessor Training Centre at its plant in Bedford.

Heading the new training school is Mike Hughes, Training Manager at TI Supply Division. He commented: "Engineers from all industries are finding it necessary to become familiar with microprocessing techniques, but it is difficult for many of them to find the time or opportunity to do so.

The new training centre will alleviate this problem with a series of courses designed as short but intensive training modules with the emphasis on 'hand-on' training."

The centre is designed to give a high teacher-student ratio, and is equipped with four complete sets of hardware to support the practical sessions.

The first courses available at the centre include a special low-cost two day "Introduction to Microprocessing" course. This serves as a starting point for anyone who has only minimal knowledge of logic gates and storage elements, and provides a firm grounding in microprocessor technology.

Run on a strictly "first to enrol first to be served" basis, the courses are open

to all interested parties. Engineers can enrol at any level in the course structure, dependent on their requirements and current knowledge of microprocessors.

The courses will be regularly updated to keep pace with the rapid progress in microprocessor technology and applications.

For further information on proposed courses readers should write to: Microprocessor Training Centre, Texas Instruments Ltd, Supply Division, Manton Lane, Bedford MK41 7PA.

### Market Trends

British manufacturers of small-screen portable monochrome TV's report a 66 per cent upsurge in deliveries with over half a million sets supplied last year. But larger sizes of monochrome sets were less popular with a decline in deliveries from 159,000 to 134,000. Deliveries of colour sets were on a level with 1977.

Clock radios were popular with big increases in sales but the fastest growth area was in videocassette recorders (VCRs) which quadrupled sales to 80,000 units last year. What a pity they all had to be imported!

### CITIZENS ARREST

The prospect of Citizens band (CB) radio in the UK received another knock with reports that the Association of Chief Police Officers are at best lukewarm, at worst decidedly anti-CB.

Fears of continuous abuse of such a privilege appear to be the chief reason, including its use by criminal elements.

### JUST THE JOB FOR MICRO'S

A recent announcement by the Minister of State for Industry, Mr. Alan Williams, of a £7m Government aid for the construction of a new manufacturing plant should bring up to 1,100 new jobs to the high unemployment area of Merseyside.

The plant is for the manufacture of microelectronic devices and is to be built by GEC Fairchild Ltd, a jointly owned subsidiary of Britain's GEC and the Fairchild Camera and Instrument Corporation of the USA. The plant is being erected on a site made available under the Community Land Scheme at Neston, Cheshire.

This project is part of the Government's strategy to couple its vast investment in new technology to help establish jobs in arrears of high unemployment.

### CHIPS ON THE LINE

Control switching on British Rail's Midland Region suburban lines from London to Bedford is to be monitored by a twin microprocessor system supplied by GEC-Elliott Process Automation under a £100,000 contract.

This is the first time MPUs have been used by BR for remote control of traction power supplies.

### Electronics Bazaar

A new show, The Great Britain Electronics Bazaar, is to be staged at London's Alexandra Palace between June 20 to 30. It will be aimed at the electronics hobbyist and admission is free to all those who register in advance to attend the show.

### Talkback

Automatic telephone answering machines are now quite common. Ansafone, a leading manufacturer has now produced a machine allowing the owner to tele-



Dr. R. W. Burns, in a talk at the IEE recently, reminded us that the first patent for a colour TV system was taken out in 1895 and that a shadow mask tube was patented in 1938. Ideas were not lacking but it was many years before the technology was able to catch up and make colour TV for all a practical reality.

phone from anywhere in the world and using a special personalised code activate the machine to replay all the recorded messages and to record, if required, instruction or orders.

This system, the mark-7, has obvious advantages for the long distance traveller who can access the machine at any time in the 24 hours from any time zone.

### —RECRUITING—

The British semiconductor manufacturer INMOS has started a full-scale recruiting campaign for the technical HQ at Bristol. The plan is to develop MPUs in the UK and complementary memory devices in a parallel operation in the USA.

The location of the four production plants has not yet been announced but are expected to be in geographically dispersed areas scheduled for industrial development.

... from the World of Electronics

## BUSINESS CALL

The office phone of the future, with the sort of "extras" executives usually only dream about, will become a reality next year when the Post Office launches a new system.


Known as small business system (SBS), this new phone will harness the power and flexibility of microprocessor control to offer many more facilities over those of ordinary telephones.

Typical facilities to be provided by SBS include: Hold an incoming call to make a call on the same phone to another phone on the system (and transfer the call to that phone if necessary). Automatic diversion of incoming calls to another phone on the system so that calls can be answered in someone's absence. Executive break-in on internal calls, allowing someone to cut in on an existing conversation to reach someone urgently.

Conference calls, enabling people on up to six phones

on the system to talk together. Storage and automatic calling of frequently-called numbers at the touch of a button. Direct calling between phones on the system for internal office communication.

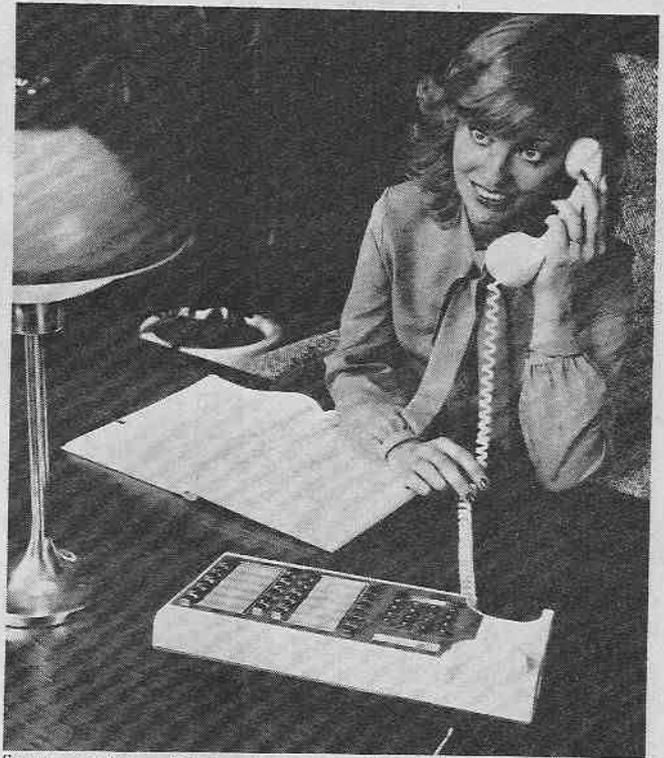The basic system can take up to ten exchange lines and serve up to 30 phone extensions—but for the smaller company or business office it need involve no more than two lines and, say, ten phones, with the minimum of extras. The system is designed to grow with the



firm; extra lines, more phones and new facilities can be added later when needed.

Each phone has push-buttons instead of a dial—

making for easier calling—and also "function" keys that are pressed to obtain the extra facilities. Each facility is clearly identified by its own key.

### On the road

The EMI-Scanner 7000 series of advanced computerised X-ray equipment is being taken on a four-month European tour by the Medical

Division of EMI. The 40ft trailer of the demonstration vehicle has two air-conditioned compartments, one for discussion, the other housing a diagnostic viewing console.

### ANALYSIS

#### COMMUNICATING WITH LIGHT

What could be the biggest breakthrough in telecommunications since the original invention of the electric telegraph in the early 19th century is now becoming a reality. Instead of using a metallic wire and an electric current to carry intelligence from one point to another, why not use a modulated light beam and convey the light through an optical duct?

A light beam is capable of carrying vast amounts of information expressed in terms of bits per second. Far more than radio waves, even the microwave systems used in space satellites and from those horn antennas which grace the upper reaches of the Post Office towers in London and other great cities.

Serious work on optical fibre communications systems started in the mid-1960s with the UK in the forefront in Europe with work at STL at Harlow and in the Post Office laboratories. It was an uphill slog involving the development of low-loss fibres and methods of manufacture, the laser and l.e.d. transmitters, the photodiode detectors. After some ten years of laboratory development, experimental systems are now undergoing field trials in many parts of the world. What is more, they seem to be successful.

What is exciting telecommunications engineers throughout the world is that now we have learnt how to make fibre-optic cables they look like being cheaper, lighter, more flexible and yet just as rugged as their metal counterparts. A cable with eight fibres can carry 8,000 two-way telephone conversations. Moreover, the very wide band-width available means that you could have video conferences for business people over telephone lines and more versatile cable TV services for the home

Brian G. Peck

Although sales to the US have fallen away due to spending cuts by American hospitals, the EMI-Scanner is doing well elsewhere in the world, especially in West Germany. Twenty-five systems were sold in a three-month period.

### New TTL family The possible replacement

of CMOS is just one of the many areas of impact that Texas Instruments foresee for their new range of Schottky TTL devices.

This claim was made at a recent press conference announcing the introduction of a Texas third generation TTL family.

### HOME RUN

A microprocessor-controlled electronic baseball game has been introduced to the UK by Micro Electronics Ltd. It uses l.e.d.s to simulate the movements of players and the ball. Sound effects include cheers for a hit and booing (actually a buzz) for an "out".

A feature is that the players can be made to tire during the progress of the game and a realistic alphanumeric score board gives running totals and other indications of the progress of the game.





## Fringe Members

THE other day a friend of mine came out with an extraordinary statement. He told me that the devotees of Model Railways were far more numerous than those of Electronics. I must say I very much doubted that statement but I think I would have had quite a job disproving it, because of the difficulty deciding who were the genuine Electronic Hobbyists. In our hobby there are so many fringe members. For example is the chap who makes an Electronic Flash a genuine electronic enthusiast? With the model railway buffs it is more clear cut.

I rather went off Model Railways ever since a colleague invited my wife and I to see his layout. He had it going round a huge table and when we were seated, he said "You are now going to have a railway tea". The goods trucks were loaded with comestibles and the train set in motion. The idea being, that when it passed you, you took out anything you fancied.

Unfortunately, before it reached us it passed by three small voracious thugs which my friend, in a moment of misguided enthusiasm called his offspring. By the time it reached us it was denuded of everything except two sticks of stringy celery. We left the table with empty stomachs and long faces.

However, as the indigenous African native said when asked how he happened to be in the Judges hen yard, "Well sah, I must have digressed". To get back to electronics the range of TV electronic childrens games is truly impressive, both in number and sophistication. Aeroplanes that fly across a blue sky and drop bombs and anti-aircraft guns that can be aimed at them and shoot them down.

I was discussing this with a retailer friend who did good business over Christmas by selling the parts for a small Crystal Set. He said "I wonder if the children who are given these

expensive toys, really get as much fun out of them as the little lad with an inexpensive crystal set kit, who puts it together and enjoys the thrill of hearing it actually work! I do not think they do! I must say I am inclined to agree with him. On a purely practical level, the latter is much more likely to be a convert to the hobby than the former.

## Readers Problems


Being in the trade, I sometimes feel I should air customers grievances, because although I am pleased to report that we receive surprisingly few complaints, I always have the nagging suspicion, that the same thing may have upset other customers, who just could not be bothered to write. If this is so, then clearing up one problem may set other customers minds at rest.

The first point I would like to make is this. If you suffer a long delay on the arrival of your goods, make sure it is not the Post Office, before you throw the book at your supplier! My house is only eight miles away from our Editors Office, and yet it sometimes takes a week for my letters to reach him.

Sometimes goods are delayed because the supplier himself is held up by the manufacturer, and this brings me to the second point. Customers are sometimes surprised and indignant, because we have paid their cheque into the Bank before they have received the goods. Let me assure all customers, that it is done from the kindest possible motives. That is, by paying it in promptly the customer has proof that his order has arrived safely.

## EE CROSSWORD No 14

BY D. P. NEWTON

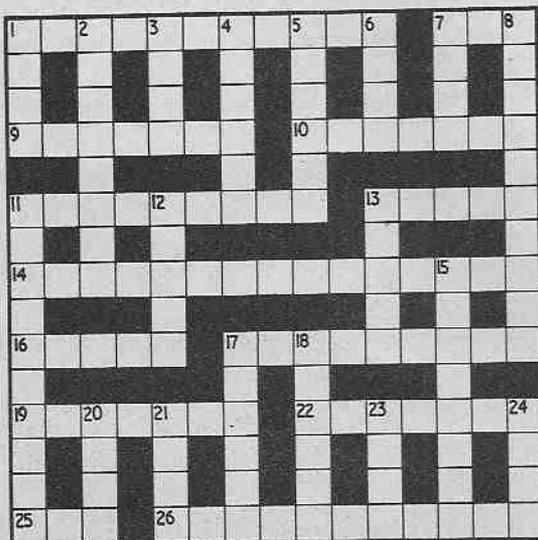

### ACROSS

- 1 Basic unit (6, 5)
- 7 Transmitter, but not commercial?
- 9 Circuitous delay from a reaction.
- 10 Dig up and disconnect dangerously.
- 11 Touched for electrical purposes.
- 13 Deep and noisy channel.
- 14 Communications code for one-to-one connections (9, 6)
- 16 Lengthy unit.
- 17 Extremely short-tempered with certain meter-like connections (4, 5).
- 19 Devices for component privacy?
- 22 Spectral schizophrenia, best known to be yellow.
- 25 Trial.
- 26 This musical device is without analytical ability.

### DOWN

- 1 Aerial elevator.
- 2 This far and no further! Unless another connection is made.

- 3 False god.
- 4 Intensely intelligent.
- 5 Lots everywhere make a jump.
- 6 Temporal location on a daily basis.
- 7 Coat hanger from a telephone.
- 8 Emitted from a negative electrode in a vacuum under high tension (7, 3).
- 11 Sharp scholarly deed in making a disc (3, 1, 6).
- 12 Core and all in a fruity way.
- 13 By-pass.
- 15 Transistor on two legs with its bottom knocked out.
- 17 Prophetic imagery on the TV.
- 18 A hot salad dish in the radar aerial?
- 20 Precipitation generally.
- 21 A pair is needed for the phones.
- 23 Runs to the pots (Anag.).
- 24 Rip a sad drip.

Solution on page 248

# BOOKS AND COMPONENTS

## BOOKS BY BABANI

244	Beginners Guide to IC's	£2.75*
BP6	Engineers & Machinists Ref. Tables	40p*
BP14	2nd Book Transistor Equivs & Subs	£1.10*
BP22	79 Electronic Novelty Circuits	75p*
BP24	52 Projects Using IC741 (or Equiv)	75p*
BP26	Radio Antenna Book Long Distance Reception & Transmission	85p*
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	60p*
BP32	Build Metal & Treasure Locators	85p*
BP34	Practical Repair/Renovation C/TV	85p*
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	85p*
BP36	50 Clots use Germ/Si/II Zener Diodes	75p*
BP37	50 Projects Using Relays/SCR/Triacs	£1.10*
BP39	50 Field Effect Trans Projects	£1.25*
BP40	Digital IC Equivs & Pin Connection	£2.50*
BP41	Linear IC Equivs & Pin Connection	£1.35*
BP42	50 Simple LED Circuits	75p*
BP43	How to make Walkie-Talkies	£1.25*
BP44	IC 555 Timer Projects	£1.45*
BP45	Projects on Opto-electronics	£1.25*
BP46	Radio Circuits Using IC's	£1.35*
BP47	Mobile Discotheque Handbook	£1.35*
BP48	Electronic Projects for Beginners	£1.45*
BP49	Popular Electronic Projects	£1.35*
BP50	IC LM3900 Projects	£1.45*
BP55	Radio Stations Guide	85p*
BP100	Coil Design & Construction Manual	85p*
BP202	Handbook of Integrated Circuits Equivalents & Substitutes	75p*
BP205	1st Book Hi-Fi Speaker Enclosures	75p*
BP213	Circuits for Model Railways	85p*
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	85p*
BP216	Electronic Gadgets & Games	85p*
BP217	Solid State Power Supply Handbook	85p*
BP221	28 Tested Transistor Projects	85p*
BP222	Short-wave Receivers for Beginners	85p*
BP223	50 Projects using IC CA3130	85p*
BP224	50 CMOS IC Projects	85p*
BP225	A Practical Intro to Digital IC's	85p*
BP226	Built Advanced Short-wave Receivers	£1.20*
BP227	Beginners Guide to Building Electronic Projects	£1.25*

## NEWNES BOOKS—NEW V.A.T. Zero Rated

Order No.	Description	Price
216	Transistors 3rd Ed.	£1.00
217	Integrated Circuits	£1.00
218	Radio & Television	£1.00
219	Electronics	£1.15
220	Colour TV 2nd Ed.	£1.15
221	Hi-Fi	£1.15
222	20 Solid State Proj. for Car	£1.95
223	20 Solid State Proj. for Home	£1.95
224	110 Int. Circ. Proj. for Home	£2.95
225	110 Thyristor Projects	£2.50
226	Operational Amp. Proj. for Home	£2.50
227	110 Practical IC Proj. for Home	£2.75
228	Electricity	£1.15
229	Beginners Guide to Electronics	£2.25
230	Beginners Guide to Television	£2.25
231	Beginners Guide to Transistors	£2.25
232	Beginners Guide to Electric Wiring	£2.25
233	Beginners Guide to Radio	£2.25
234	Guide to Colour T.V.	£2.25
235	Electronic Diagrams	£1.80
236	Electronic Components	£1.80
237	Printed Circuit Assembly	£1.80
238	Transistor Pocket Book	£3.90
239	50 Photoelectric Circuits	£1.80
240	Semiconductor Handbook Part 1	£5.25
241	Semiconductor Handbook Part 2	£4.25
242	Electronics Pocket Book	£3.90
243	Radio Valve & Semiconductor Data	£2.40
244	Beginners Guide to Integrated Circuits	£2.75
209	BI-PAK TTL Data Book	50p
209	BI-PAK CMOS Data Book	45p

## OPTOELECTRONICS

**NEW INCREASED RANGE—ALL 1ST QUALITY LED'S (diffused)**

O/no. Type	Size	Colour	Price
1501 ARL209 (TIL209)	3mm (125)	RED	£0.10
1502 MIL3232(TIL211)	3mm (125)	GREEN	£0.15
1503 MIL3331 (OPL212A)	3mm (125)	YELLOW	£0.15
1504 ARL4850 (FLV117)	5mm (2)	RED	£0.15
1505 MIL3531 (TIL222)	3mm (2)	GREEN	£0.15
1506 MIL3533 (MVS333)	3mm (2)	YELLOW	£0.15
1509 FLV111	5mm (2)	CLEAR (Ill. Red)	£0.11

**SUPER 'Hi-Brite' Type**

1521 MIL32	3mm (125)	RED	£0.10
1522 MIL32	5mm (2)	RED	£0.10
1514	ORP12 Light dependent resistor		£0.35
1520	OC71 Photo transistor		£0.35

**LED CLIPS**

1508/125	pack of 5	125 clips	£0.15
1508/2	pack of 5	2 clips	£0.18

ALL @ 8% V.A.T.

**DISPLAYS:**

DL303	7 segment D.P. left (.30" height)	Common Anode	O/NO. 1523	£0.70
RED	Single Digit	Common Anode	O/NO. 1510	£0.95
DL170	7 segment D.P. left (.0-3" height)	Common Anode	O/NO. 1524	£1.70
RED	Single Digit	Common Anode	O/NO. 1511	£1.70
DL527	7 segment D.P. left (.50" height)	Common Anode	O/NO. 1524	£1.70
RED	Two-Digit Reflector	Common Anode	O/NO. 1511	£1.70
DL727	7 segment D.P. right (.510" height)	Common Anode	O/NO. 1511	£1.70
RED	Single Digit Light Pipe	Common Anode	O/NO. 1511	£1.70

ALL @ 8% V.A.T.

**OPTO-ISOLATORS**

Isolation Breakdown—Voltage 1500—continuous fwd current 100mA			
CIL74	Single-Channel 6 pin DIP standard type—optically coupled pair with Infra-red LED Emitter and NPN Silicon Photo Transistor	O/NO. 1497	£0.50
CILD74	Multi-Channel 8 pin DIP Two Isolated Channels	O/NO. 1498	£1.00
CILQ74	Multi-Channel 16 pin DIP Four Isolated Channels	O/NO. 1499	£2.20

ALL @ 8% V.A.T.

## SWITCHES

Description	No.	Price
DPDT miniature slide	1973	14p*
DPDT standard slide	1974	15p*
Toggle switch SPST 1/2 amp 250V a.c.	1975	33p*
Toggle switch DPDT 1 amp 250V a.c.	1976	42p*
Rotary on-off mains switch	1977	50p*
Push switch—Push to make	1978	14p*
Push switch—Push to break	1979	18p*

**ROCKER SWITCH**

Colour	No.	Price
RED	1980	30p*
BLACK	1981	30p*
WHITE	1982	30p*
BLUE	1983	30p*
YELLOW	1984	30p*
LUMINOUS	1985	30p*

A range of rocker switches SPST—moulded in high insulation. Material available in a choice of colours ideal for small apparatus.

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	70p*
Miniature SPST toggle, 2 amp 250V a.c.	1959	75p*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	80p*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	85p*
Push button SPST, 2 amp 250V a.c.	1962	90p*
Push button SPST, 2 amp 250V a.c.	1963	95p*
Push button DPDT, 2 amp 250V a.c.	1964	98p*

**MIDGET WAFER SWITCHES**

Single-bank wafer type—suitable for switching at 250V a.c. 100mA or 150V d.c. in non-reactive loads make-before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing.

Description	Order No.	Price
1 pole 12 way	1965	48p*
2 pole 6 way	1966	48p*
3 pole 4 way	1967	48p*
4 pole 3 way	1968	48p*

**MICRO SWITCHES**

Description	Order No.	Price
Plastic button gives simple 1 pole change over action	1970	25p
Rating 10 amp 250V a.c.		

**QUICK BLOW 20mm**

Type	No.	Price
150mA	611 6p	1A 615 5p
250mA	612 5p	1.5A 616 6p
550mA	613 3p	2A 617 5p
800mA	614 7p	2.5A 618 6p

**ANTI-SURGE 20mm**

Type	No.	Price
100mA	622 1A 625	2.5A 626
250mA	623 1.5A 627	3-15A 628
500mA	624 2A 627	5A 630

**QUICK BLOW 1 1/2in**

Type	No.	Price
250mA	631	500mA 632
1A	635	2.5A 638
1A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

**QUICK BLOW 1 1/2in**

Type	No.	Price
1A	635	2.5A 638
2A	637	3A 639

## TRANSFORMERS

**MINIATURE MAINS** Primary 240V

No.	Secondary	Price
2021	6V-0-6V 100mA	90p*
2022	9V-0-9V 100mA	90p*
2023	12V-0-12V 100mA	85p*

**MINIATURE MAINS** Primary 240V with two independent secondary windings

No.	Type	Price
2024	MT280-0-6V, 0-6V RMS	£1.00
2025	MT150-0-12V, 0-12V RMS	£1.00

**1 AMP MAINS** Primary 240V

No.	Secondary	Price
2026	6V-0-6V 1 amp	£2.50*
2027	9V-0-9V 1 amp	£2.00*
2028	12V-0-12V 1 amp	£2.60*
2029	15V-0-15V 1 amp	£2.75*
2030	30V-0-30V 1 amp	£3.45*

**STANDARD MAINS** Primary 240V

Multi-tapped secondary mains transformers available in 1 amp, 1 amp and 2 amp current rating. Secondary taps are 0.10-25-33-40-50V.

Volts available by use of taps.

No.	Rating	Price
2031	1 amp	£3.40
2032	1 amp	£4.40
2033	2 amp	£5.45

Volts available by use of taps.

No.	Rating	Price
2031	1 amp	£3.40
2032	1 amp	£4.40
2033	2 amp	£5.45

## AUDIO LEADS

107	FM Indoor Ribbon Aerial	60p*
113	3.5mm Jack plug to 3.5mm jack plug. Length 1.5m	75p*
114	5 pin DIN plug to 3.5mm. Jack connected to pins 3 & 5. Length 1.5m	85p*
115	5 pin DIN plug to 3.5mm. Jack connected to pins 1 & 4. Length 1.5m	85p*
116	Car aerial extension. Screened insulated lead. Fitted plug & skt.	£1.25*
117	AC mains connecting lead for cassette recorders & radios. 2 metres	68p*
118	5 pin DIN phono plug to stereo headphone jack socket	£1.08*
119	2+2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m	90p*
120	Car stereo connector. Variable geometry plug to fit most car cassette. 3 track cartridge & combination units. Supplied with inline fused power lead and instructions.	80p*
123	6.8m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK	£1.80
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	75p*
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	75p*
126	5 pin DIN plug to Tinned open end. Length 1.5m	75p*
127	5 pin DIN plug to 4 Phone Plugs. All colour coded. Length 1.5m	£1.30*
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	80p*
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.05*
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	68p*
131	5 pin DIN plug to 3 pin DIN plug. 1 & 4 and 3 & 5. Length 1.5m	83p*
132	2 pin DIN plug to 2 pin DIN socket. Length 1.0m	98p*
133	5 pin DIN plug to 2 phono plugs. Connected pins 3 & 5. Length 1.5m	75p*
134	5 pin DIN plug to 2 phono sockets. Connected pins 3 & 5. Length 23cm	68p*
135	5 pin DIN socket to 2 phono plugs. Connected pins 3 & 5. Length 23cm	68p*
136	Coiled stereo headphone extension lead. Black. Length 6m	£1.75*
178	AC mains lead for calculators etc.	45p*

## CASES AND BOXES


**INSTRUMENT CASES.** In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.25
156	4in	6in	3in	£2.12
157	6in	4 1/2in	1 1/2in	£1.30
158	9in	5 1/2in	2 1/2in	£1.78

**ALUMINIUM BOXES.** Made from bright ali., folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	62p
160	4in	4in	1 1/2in	62p
161	4in	2 1/2in	1 1/2in	62p
162	5 1/2in	4in	1 1/2in	70p
163	4in	2 1/2in	2in	84p
164	3in	2in	1in	44p
165	7in	3in	2 1/2in	£1.04
166	8in	6in	3in	
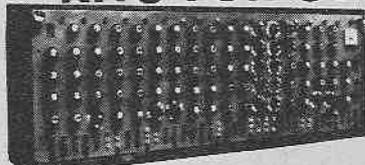
# KITS FOR SOUND EFFECTS AND OTHER PROJECTS



## GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7.89  
Alternative component set with panel switches £5.05  
Printed circuit board £1.43

## GUITAR FREQUENCY DOUBLER

(P.E. Aug. 77)

A modified and extended version of the circuit published.

Component set and PCB £4.52

## GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual rotary pot £6.89  
Printed circuit board £1.62

## GUITAR SUSTAIN (P.E. Oct. 77)

Maintains the natural attack whilst extending note duration.

Component set, PCB and foot switches £5.13  
Component set, PCB and panel switches £3.71

## WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) £4.26

## COMPONENTS SETS

Include all necessary resistors, capacitors, semi-conductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately.

## 10% DISCOUNT VOUCHER (E154)

TERMS: Goods in current advert and lists over £50 goods value (excl. P&P & VAT). Correctly coded. C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of E.E.

Fuller details of kits, PCBs and parts are shown in our lists.

**CIRCUIT AND LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

## ADD: POST & HANDLING

U.K. orders—Keyboards add £2.00 each plus VAT. Other goods; under £15 add 25p plus VAT; over £15 add 50p plus VAT. Recommended; optional insurance against postal mishaps, add 50p for cover up to £50, £1.00 for £100 cover, etc. pro-rata. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

PHOTOCOPIES of texts for most of the kits are available—prices in our lists.

**LIST**—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

## ADD 12½% VAT

(or current rate if changed). Must be added to full total of goods. Discount, post & handling, on all U.K. orders. Does not apply to Exports.

**EXPORT ORDERS ARE WELCOME** but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list—Europe send 20p, other countries send 50p.

**PRICES ARE CORRECT AT TIME OF PRESS. E.&O.E. DELIVERY SUBJECT TO AVAILABILITY.**

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL: 01-392 6184)

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.



## FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit

Component set (incl. PCB) £2.05

## P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.

Main component set (incl. PCB) £14.93

Power supply set (incl. PCB) £5.28

## SYNTHESIZER TUNING INDICATOR

(P.E. July 77)

A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl. sw.) £7.45

## DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4.58

## CONSTANT DISPLAY FREQUENCY

METER (P.E. Aug. 78)

A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.

Component set £24.05\*

Printed circuit board £3.83\*

\*This kit & PCB are at 8% VAT (all others are 12½%)

## MANY MORE KITS

For Synthesizers, Rhythm Generators, Electronic Pianos and other projects, big, small, simple or complex, are available, plus a range of keyboards, separate components and accessories. Details in our lists.


## PHOTOGRAPHS

in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

PHONOSONICS • DEPT. EE94 • 22 HIGH STREET • SIDCUP • KENT DA14 6EH
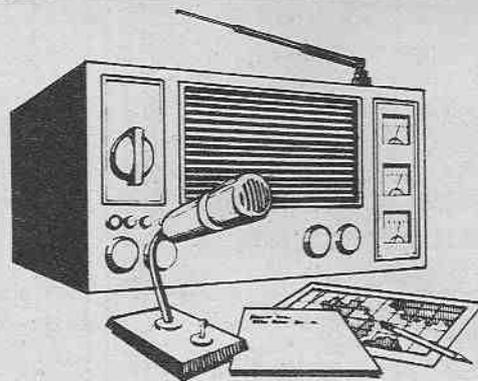
# Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.



## Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure without obligation to:

## British National Radio & Electronic School


P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

EE/L4

Block caps please

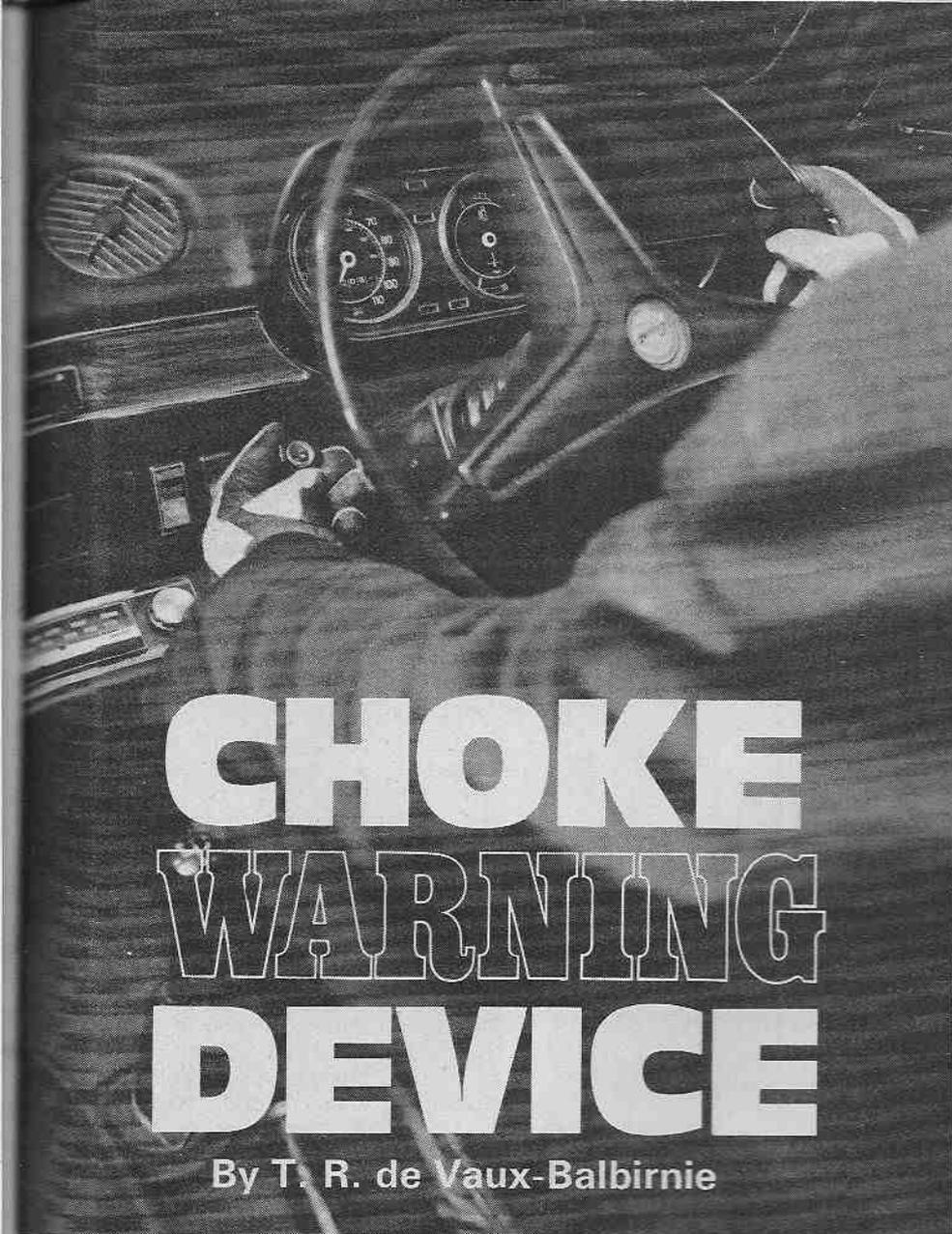

# CHOKES WARNING DEVICE

By T. R. de Vaux-Balbirnie

**M**ost car owners know that it is very bad practice to leave the choke control pulled out for longer than necessary. Doing this habitually has two bad effects. Firstly, and most immediately, the fuel consumption rises alarmingly. Secondly—in the longer term—engine wear is greatly increased due to the extra fuel delivered by the carburettor washing the protective oil film from the cylinder walls.

Short and long term interests are protected by this project which automatically signals the driver when the choke control remains out after the engine has reached a predetermined temperature.

The project is suitable for both positive and negative-earth

vehicles and requires very little mechanical aptitude to fit it.

The circuit is provided with two sensing devices. The first is a microswitch at the choke control which is in the main battery line and switches on power to the circuit as soon as the choke control is moved out a little. Secondly, there is a thermistor which causes the circuit to activate and the warning lamp to light when the temperature of the engine reaches a certain level providing, of course, the choke control is out (i.e. choke is in use).

## CIRCUIT

The circuit diagram of the Choke Warning Device is shown in Fig. 1 and uses an operational

amplifier (op-amp), IC1. The cheapest type—the 741—is specified. For those constructors who have not used operational amplifiers before, a much-simplified description is included. The operational amplifier, which is housed in an 8-pin d.i.l. package, has two inputs and one output as well as positive and negative power supply connections. The input to pin 2 is called the “-” or “inverting” input whilst the input to pin 3 is called the “+” or “non-inverting” input. The output is at pin 6. If the non-inverting input is at a higher voltage than the inverting input, the output will be high, otherwise it will be low. These voltages are measured with respect to the earth (negative) line.

## CIRCUIT DESCRIPTION

In the circuit of Fig. 1 the inverting input voltage is obtained from the slider of the potentiometer VR1 which is connected between supply positive and negative. In this way any voltage between zero and full battery voltage (nominally 12 volts) may be supplied to pin 2.

The voltage to the non-inverting input is derived from the potential divided formed by the fixed resistor R1 and the thermistor RTH1 which has a negative temperature coefficient of resistance, that is to say, its resistance reduces as the temperature of the device rises. The thermistor will be remote from the rest of the circuit where it can sense the temperature of the engine.

With VR1 correctly adjusted, the output from the op-amp will be high at and above a certain engine temperature. This will only be indicated on LP1, of course, if the choke control is not in use the circuit does not receive power and LP1 is off.

As the output from the op-amp is not sufficient to operate a filament panel light the rest of the circuit is designed to do this. It consists of two transistors connected as a *Darlington pair*. This gives a very sharp response. When the op-amp switches on, it turns on TR1 which turns on TR2 and hence the indicator. When the engine reaches a certain temperature, then, the indicator lamp will switch on sharply. It will be noted that the variations in voltage which always occur in car battery systems are of no consequence.

Preset VR2 is provided to match the output from the op-amp to the Darlington pair. This will be set to give the correct operation since there are variations in transistors even of the same type.

The panel light will be chosen to blend with the rest of the equipment on the dashboard and can be a 12 volt type rated at up to 3 watts. It may be mounted anywhere to give a neat appearance although a conspicuous position is needed. The author used a panel indicator of the throw-away type. These are particularly small and neat but the bulb cannot be replaced.

The author drilled a very small hole in the position illustrated in Fig. 2. An ordinary lever arm microswitch was then modified by bending the arm very gently then filing the end to a needle.

A suitable bracket was made out of aluminium to support the switch behind the dashboard in such a way that the filed end protruded through the hole a short distance. The switch was so positioned that the choke control knob just switched it off when it was pushed fully in. This may not be possible with some cars.

In more difficult cases the rotary type of microswitch which is

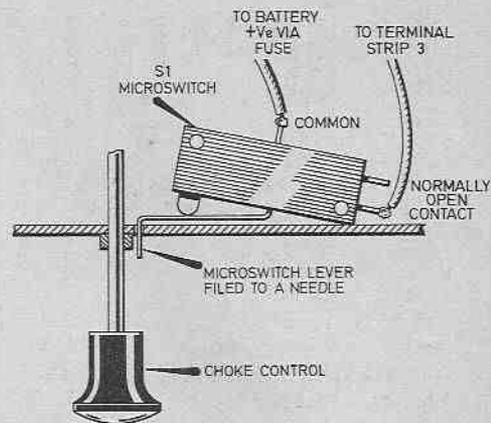


Fig. 2. One method of mounting the micro-switch.

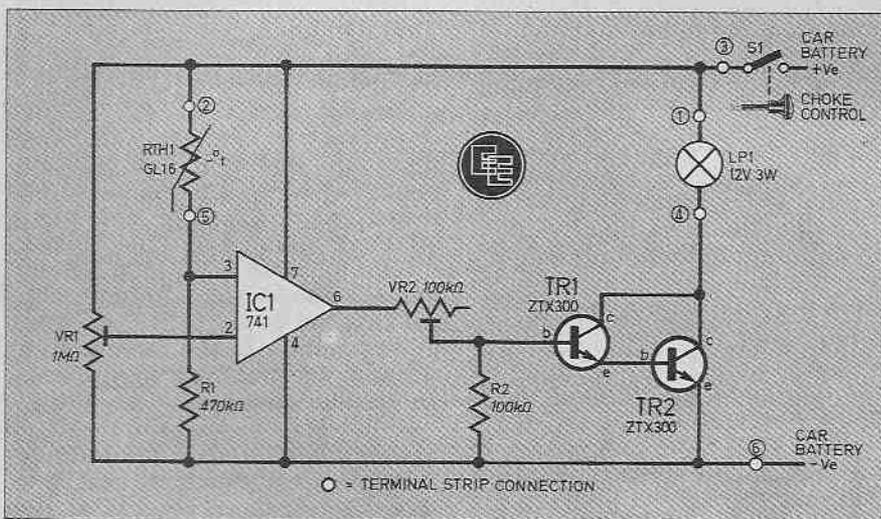


Fig. 1. Complete circuit diagram of the Choke Warning Device.

arrangements on the body of the switch itself.

## THERMISTOR

The thermistor is a very delicate component and must be adequately protected. At the same time it must efficiently pick up engine heat. When considering any other method than that suggested it must be remembered that cool air flows freely in the engine compartment so unless the thermal contact is efficient the device will give all sorts of false results depending on the speed of the car. Thin aluminium was used to make the holder for RTH1 as illustrated in Fig. 3. For the prototype the aluminium from an old "Anadin" tin was used. Any other thin aluminium container may be cut up to serve the same purpose.

The channel for the thermistor was made using a nail—the aluminium being squeezed around it using pliers. This nail should be slightly larger than the diameter of the thermistor so that this may be secured deeply in the channel using quick setting epoxy resin adhesive or similar.

The delicate leads from the thermistor should be sleeved with short lengths of plastic insulation.

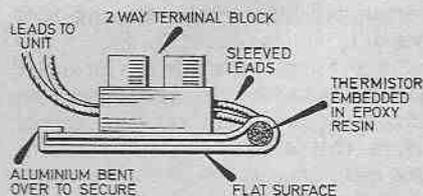


Fig. 3. A small holder is constructed as shown to accommodate the thermistor.



## MICROSWITCH

The microswitch at the choke control presents the greater problem and the constructor is strongly advised to check his particular car to make sure that it is possible to fit it before building the actual circuit.

Although certain models and light vans have a lever-operated choke control which lends well to direct operation of a microswitch, most cars have a knob which is pulled out from the dashboard.

operated by a piece of wire may be considered. The controlling wire may be bent into a variety of shapes so that the switch may be sited conveniently. In this case care must be taken in choosing suitable wire.

In all this work one thing must be borne in mind. The action of the microswitch must on no account interfere with the operation of the choke control. The control knob must be able to return to its "off" position without obstruction. Only when the constructor is certain that the job can be done should he continue.

As stated previously, the microswitch will switch off when the lever is held in. This means that normally open contacts will be used. The correct contacts may be found by checking with a simple battery and bulb circuit but there is often a diagram of the contact

# COMPONENTS

approximate  
cost £3.60

Neither lead must be in contact with the aluminium. The leads should then be brought to a small two-way connector block stuck to the top of the aluminium using the same adhesive.

All materials must be capable of withstanding boiling water temperature at least. The complete assembly should then be attached, again using epoxy resin adhesive, to a suitable metal part of the car engine. It should be kept well clear of the exhaust system and any moving parts.


The author found that the best position was horizontal as no support was needed as the adhesive hardened. It is best to spend some time finding the most suitable place by running the car for a short while then, with the engine switched off, feeling for a good flat surface which is warm to the touch.

Before attaching the thermistor assembly make sure that all traces of oil and dirt have been removed—detergent may be used—to ensure good adhesion. It was found that the clip could be subsequently lifted with one's finger nail, so the device is easy to replace at any time.
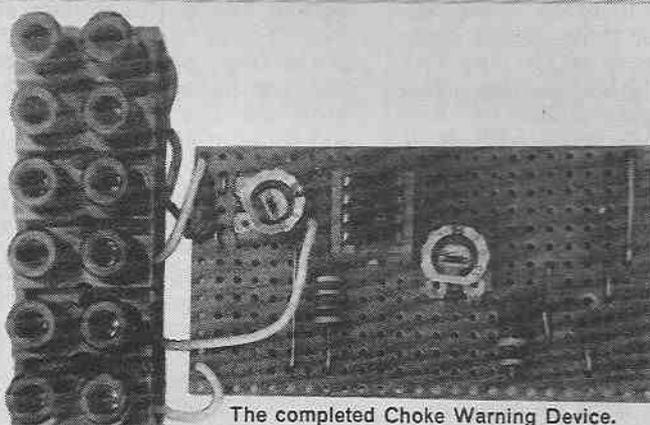
## CONSTRUCTION

Construction of the circuit panel itself is very straightforward and non-critical. The suggested layout is shown in Fig. 4 and is based on 0.1 inch pitch stripboard 25 holes by 15 strips. The copper strip must be broken in the places indicated using either a special stripboard tool, a small twist drill or a pen-knife. Although an i.c. holder is recommended for the op-amp it is possible to solder it direct to the circuit board. This saves a little money but is hardly worthwhile as the i.c. could easily be damaged by excessive heat from the soldering iron.

Be careful to insert the op-amp the correct way round in the holder. Soldering the components



The completed Choke Warning Device.

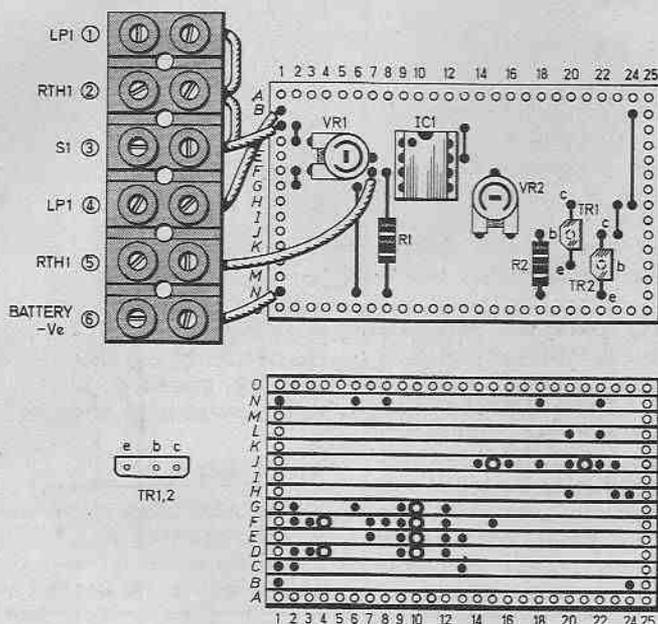


Fig. 4. Stripboard layout, also showing the breaks to be made and other wiring.

## COMPONENTS

### Resistors

- R1 470k  $\Omega$
- R2 100k  $\Omega$
- Both 2 watt carbon  $\pm 10\%$

### Potentiometers

- VR1 1M  $\Omega$  miniature preset
- VR2 100k  $\Omega$  miniature preset

### Semiconductors

- TR1, 2 ZTX300 silicon *npn* (2 off)
- IC1 741 operational amplifier (8 pin d.i.l.)

### Miscellaneous

- RTH1 GL16 or similar bead type thermistor approximately 1 megohm at 20°C
- LP1 12 volts up to 3 watts
- S1 lever-operated microswitch with one normally open contact

Stripboard: 0.1 inch matrix 15 strips  $\times$  25 holes; 8-pin d.i.l. socket to suit IC1; 5A terminal block 8-way; standard connecting wire.

See  
**Shop  
Talk**

page 236

must be carried out with great care especially to avoid "bridging" between copper strips. Use a heat-shunt on the leads of TR1 and TR2 when soldering in position. The whole circuit should then be carefully checked. To begin with, both VR1 and VR2 should be set at approximately mid-position. The external connections—i.e. thermistor leads, microswitch and panel light connections are brought out to a small strip of terminal block. The circuit may then be mounted in a small plastic box. All external wiring to the terminal block must be done with stranded wire as single wire soon fails under vibration.

### NEGATIVE EARTH

If the car is *negative earth* i.e. the car's battery negative terminal is connected directly to the car body then the negative connection for the circuit is also earthed by taking the lead to a small eyelet and securing it to a self-tapping screw attached to a nearby metal body part.

The positive connection will then be taken to the microswitch and the other microswitch terminal taken to the battery positive. This must not be a direct connection but to a fuse which is only 'live' when the ignition is switched on. There are usually spare outlets from the fuse made with spade type connectors readily available from a motor accessory shop.

It is important to make the connection to the correct side of the fuse. If it is taken to the live side of the fuse (direct to the battery) then, although the circuit will work, the fuse will be ineffective and this could be dangerous in the event of a short circuit. If in doubt a simple check may be made with a 12 volt bulb.

With the fuse removed and one side of the bulb earthed the live side of the fuse may be found. The connection should then be made to the other side of the fuse which is then replaced. During this check the ignition should be switched on.

### POSITIVE EARTH

If the car is of the *positive earth* type then the procedure is slightly different. In this case, the positive lead from the circuit panel is earthed and the negative lead taken to the microswitch and then to the fuse. The connections are made in exactly the same way.

Make sure that the wires leading from the thermistor unit into the car are protected by a rubber grommet as they pass through the chassis. In many cases space in an existing grommet can be found which saves a lot of time.

### SETTING UP

The unit is checked and set up in the following way. With the ignition switched on and the choke pulled out a little (but with the

engine not running), VR1 should be adjusted one way and then the other. The panel light should come on and go off; VR2 should be adjusted if necessary to give the best effect. When the choke control is pushed in the lamp should go off.

It should be noted that the choke control should not be used excessively during checking as it could lead to difficult starting next time. Preset VR1 should then be left so that the light is just off. The engine should then be started and allowed to run a little. The light should come on as the engine warms up (the choke has to be out, of course). A test drive with an assistant will be needed to set VR1 correctly and over the next day or two further adjustment may be needed. The light should come on when the engine will run comfortably without choke.

It is important to regard this as a device to act as a reminder should the choke be left out. It is not intended as a device to signal the driver when to put the choke in. The choke should be used progressively in the usual way. It should be pushed completely in as soon as possible—the driver should not wait for the light to come on.

Some high-quality cars are already fitted with a choke warning light as standard equipment. You can now put your car into the same category—cheaply! ☞



### By Dave Barrington Component Catalogue

It was only recently that we had cause to pass the comment on a catalogue received, "... and feel it

does not do justice to the service this company provides". We are happy to report that the complete opposite is true of the latest components catalogue received from Watford Electronics.

In keeping with the quality of service this company provides, it would seem that no expense has been spared in the production of their very first components catalogue. Using top quality paper, the pages of the catalogue are clearly laid out with a large main heading and page number at the top.

Most pages are sub-divided into various types under the main heading and contain details of the products, including prices. Also included on most pages is a photograph or illustration of the listed components.

The 13 page transistor section is very good and lists the main parameters and case outlines of over 600 devices. The pages covering integrated circuits lists the type number and function, but do not give pinning details. Apart from components, complete construction kits, audio equipment and test gear are also listed.

It's refreshing to see that Watford have devoted two pages, one in the form of a specimen order, on how to order components. At 50p (plus 25p post and packing) the cost of the 92 page Watford Electronics Components Catalogue is money well spent.

### CONSTRUCTIONAL PROJECTS

The components for this month's constructional projects are listed in most of our advertisers' catalogues. Provided readers have taken our advice over the past months and stocked up on new editions, as they became available, there should be no component buying problems.

However, regarding the *Shaver Inverter* this calls for some Ferranti transistors which may prove troublesome to locate. A complete kit of parts can be obtained from Davian Electronics, 13 Deepdale Avenue, Royton, Oldham OL2 6XD. Price £10.80, including p & p.


### POWER SUPPLY

It would appear from correspondence received that some readers are experiencing difficulty in obtaining the CA3085 specified in the *General Purpose Power Supply* published in our February issue.

The LM305H from Watford Electronics is a direct pin-for-pin replacement.

# From Science of Cambridge: the new MK 14. Simplest, most advanced, most flexible microcomputer - in kit form.

**only  
£39.95  
(+ 8% VAT)**

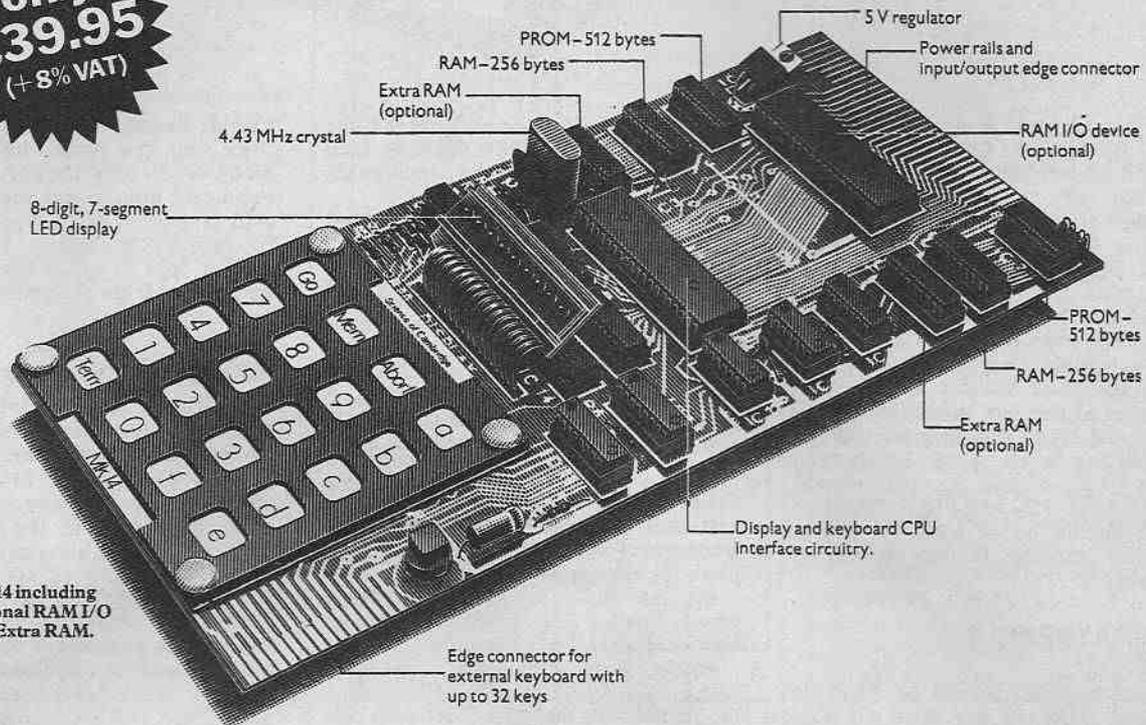

**MK 14 including optional RAM I/O and Extra RAM.**

The MK 14 is a complete microcomputer with a keyboard, a display, 8 x 512-byte pre-programmed PROMs, and a 256-byte RAM programmable through the keyboard.

As such the MK 14 can handle dozens of user-written programs through the hexadecimal keyboard.

Yet in kit form, the MK 14 costs only £39.95 (+£3.20 VAT, and p&p).

#### More memory - and peripherals!

Optional extras include:

1. Extra RAM - 256 bytes.
2. 16-line RAM I/O device (allowed for on the PCB) giving further 128 bytes of RAM.
3. Low-cost cassette interface module - which means you can use ordinary tape cassettes/recorder for storage of data and programs.
4. Revised monitor, to get the most from the cassette interface module. It consists of 2 replacement PROMs, pre-programmed with sub-routines for the interface, offset calculations and single step, and single-operation data entry.
5. PROM programmer and blank PROMs to set up your own pre-programmed dedicated applications.

All are available now to owners of MK 14.

#### A valuable tool - and a training aid

As a computer, it handles operations of all types - from complex games to digital alarm clock functioning, from basic maths to a pulse delay chain. Programs are in the Manual, together with instructions for creating your own genuinely valuable programs. And, of course, it's a superb education and training aid - providing an ideal introduction to computer technology.

#### SPECIFICATIONS

- Hexadecimal keyboard • 8-digit, 7-segment LED display • 8 x 512 PROM, containing monitor program and interface instructions
- 256 bytes of RAM • 4 MHz crystal • 5 V regulator • Single 8 V power supply • Space available for extra 256-byte RAM and 16 port I/O • Edge connector access to all data lines and I/O ports

#### Free Manual

Every MK 14 kit includes a Manual which deals with procedures from soldering techniques to interfacing with complex external equipment. It includes 20 sample programs including math routines (square root, etc), digital alarm clock, single-step, music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

#### Designed for fast, easy assembly

The MK 14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

#### How to get your MK 14

Getting your MK 14 kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK 14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,  
6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me the following, plus details of other peripherals:

- MK 14 Standard Microcomputer Kit @ £43.55 (inc 40p p&p.)
- Extra RAM @ £3.88 (inc p&p.)
- RAM I/O device @ £8.42 (inc p&p.)

I enclose cheque/money order/PO for £ \_\_\_\_\_ (indicate total amount.)

Name \_\_\_\_\_

Address (please print) \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

EE4


Allow 21 days for delivery.

# Science of Cambridge

# TUNER AMPLIFIER

## PART 5

HI-FI SERIES

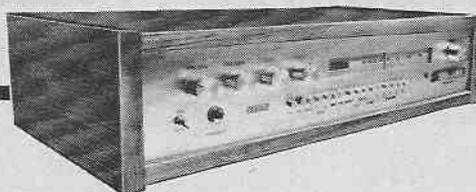

**W**E have now arrived at what is likely to be the most interesting and absorbing stage in the construction of the 2020: the final assembly of parts and wiring up. The latter is a comparatively large task calling for close attention and care throughout, but this work is readily divided into logical stages and can be carried out over a number of sessions, as convenient to the individual constructor.

First read through the whole of this article and study the diagrams. When commencing work, have before you Parts 1, 2, 3 and 4. The circuit diagrams Fig. 1.2a and Fig. 1.2b in particular should be at hand for cross-reference throughout the wiring-up operation.

### FINAL ASSEMBLY

#### Rear Panel

The rear panel should be fitted to the base plate (as per Part 4). Now assemble the rear panel components as shown in Fig. 5.3.

See Fig. 5.1 for details of performing the power transistor leads and assembly of associated items. Correct positioning of the mica washer is most important.

The aerial coaxial socket, the four power transistors, the two fuse

holders, the solder tag and the resistor R104 are secured with 6BA 1/2 inch screws and nuts. All other components have their own locking nuts.

Fit a grommet to the mains lead hole.

#### Main Base Plate

Secure the mains transformer. Secure the three electrolytic capacitors C55a, b and C58 (as shown in Fig. 5.3) in their clips with 6BA 1 inch screws and nuts. Fit the R. F. Unit with 4BA 3/8 inch screws and nuts.

#### Front Panel

It will be more convenient if the front panel is removed from the base plate for the following operation.

Fit the three l.e.d.s to the front panel, having first fitted the correct bushes in each hole, Fig. 5.2a.

Solder two thin leads (about 6 inches in length) to each of the three l.e.d.s, D1, D2 and D3. Now refit the front panel (with the scale panel assembly mounted) to the base plate (five 8BA C/SK screws and nuts). Bring the six l.e.d. leads up and hook temporarily over the tuning drum bracket to clear the area for Board A.

**NOTE.** The mains switch and the phones jack should NOT be fitted at this stage.

#### Circuit Boards

Fit the five p.c.b.s on to the base plate, Fig. 5.3. Locate boards over mounting pillars and push down onto seat of pillars. (If it is ever necessary to remove a board, pinch in the sprung legs to allow the board to be withdrawn from the pillars.)

### INTER-UNIT WIRING

Providing that the specified components have been used and the wiring diagrams are studied carefully, no difficulty should be encountered with the final wiring. Position the wires as shown in the photographs, since the wiring diagrams have been drawn for clarity of connections and do not show the actual physical routing or layout of the wires and cables. The position of the wires is not critical and if in doubt take the shortest route around the p.c.b.s. Do not drape wires across the p.c.b.s except where there is no alternative.

Longer "runs" such as wires from the front panel to the rear panel should be dressed closely against the flanges of the base plate, along the side and near edges.

Use plastic covered tinned stranded copper wire 7/0.2mm for all wiring, except where otherwise stated.

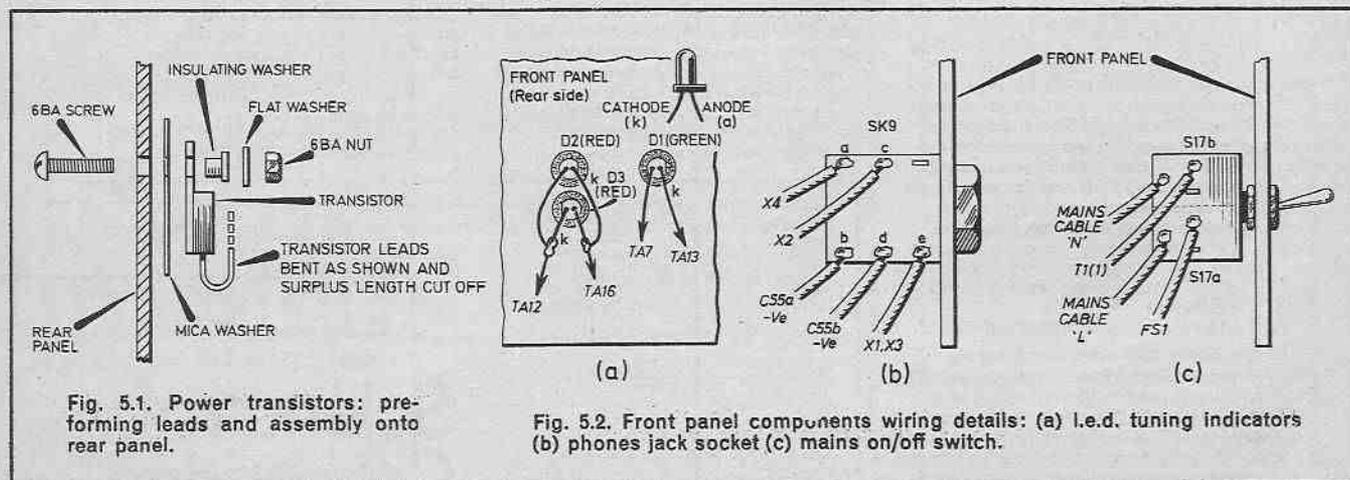


Fig. 5.1. Power transistors: performing leads and assembly onto rear panel.

Fig. 5.2. Front panel components wiring details: (a) i.e.d. tuning indicators (b) phones jack socket (c) mains on/off switch.

# WIRING SCHEDULE

## STAGE 1—BOARD A

First complete the on-board wiring, that is TA3, TA7 and the three l.e.d.s, D1, D2 and D3. The leads already attached to D2 and D3 should be shortened to about two inches, which will be adequate to reach TA12 and TA16.

Care is required when making connections to TA12, TA14 and TA16 which are immediately under the tuning drum.

Proceed with remainder of Terminal Pins in numerical order as given in table.

NOTE: Tuning meter/pushbutton wiring is dealt with later under Stage 11.

See Figs. 5.2a, 5.3, 5.4, 5.5.

Terminal Pin	Wire to
TA1	R.F. Unit(8)
TA2	R.F. Unit(6) (screen)
TA3	TA7
TA4	S2a
TA5	R.F. Unit(3)
TA6	S2a
TA7	(i) R.F. Unit(4)
	(ii) TA3
	(iii) D1

TA8	not used
TA9	not used
TA10	S13a (Board B)
TA11	S13b (Board B)
TA12	D2, D3
TA13	D1
TA14	R.F. Unit(5)
TA15	VR3
TA16	D2 and D3
TA17	VR3
TA18	S2b

P.B. Switches (topside)	
S2a	ME1(a)
S2b	ME1(b)
S3	VR3 (slider)

## STAGE 2—R.F. UNIT

See Fig. 5.3.

Pin	Wire to
1	Aerial socket SK1
2	Aerial socket SK1 (screen)
3	TA5
4	(i) TA7
	(ii) TC3
5	(i) TA14
	(ii) C1+ve
8	TA1
6	(i) TA2 (screen)
7	(ii) C1-ve

## STAGE 3—BOARD B

NOTE: Screened wiring to push-button switches S10, S11, S12, and S16 is dealt with later, under Stage 10. Likewise, screened cables to VR13 and VR14.

See Figs. 5.3, 5.4.

Terminal Pin	Wire to
TB1	not used
TB2	TE5
TB3a	VR13
TB3b	VR13
TB4	VR14

TB5a	VR11a
TB5b	VR11b
TB6a	VR11a slider
TB6b	VR11b slider
TB7a	VR11a
TB7b	VR11b
TB8a	VR12a
TB8b	VR12b
TB9a	VR12a slider
TB9b	VR12b slider
TB10a	VR12a
TB10b	VR12b

### P.B. Switches (Topside)

Switch	Wire to
S9	no connection
S13a	TA10 (Board A)
S13b	TA11 (Board A)
S12a	TC1a
S12b	TC1b
S11	Stage 10
S10	
S16	
S15	no connection
S14	no connection

## STAGE 4—BOARD C

NOTE: Connection of screened cables to TC1a and TC1b should be left until Stage 10.

See Figs 5.3, 5.4

Terminal Pin	Wire to
TC1a	S12a
TC1b	S12b
TC2	not used
TC3	(i) R.F. Unit(4)
	(ii) TE9
TC4a	SK4a
TC4b	SK4b
TC5	SK4a, b (earth)

## STAGE 5—BOARD D

All connections to be made with 16/0.2mm wire.

NOTE: Connection of screened cables to TD1a and TD1b should be left to Stage 10.

See Figs. 5.3, 5.4.

Terminal Pin	Wire to
TD1a	VR14a slider
TD1b	VR14b slider
TD2	common screens
TD3	C58-ve
TD4a	TR20a, base
TD4b	TR20b, base
TD5a	TR20a, collector
TD5b	TR20b, collector
TD6a	TR20a, emitter
TD6b	TR20b, emitter
TD7a	TR22a, base
TD7b	TR22b, base
TD8a	TR22a, collector
TD8b	TR22b, collector
TD9a	TR22a, emitter
TD9b	TR22b, emitter
TD10a	FS2
TD10b	FS3
TD11	C58-ve
TD12a	C55a+ve
TD12b	C55b+ve
TD13a	C55a-ve
TD13b	C55b-ve

## STAGE 6—BOARD E

All connections (except pair to ME1) to be made with 16/0.2 mm wire. For ME1 use 7/0.2mm, or thinner wire.

ME1 connections should be left until Stage 11.

Other side of C65 is connected to base plate by solder tag.

See Figs. 5.3, 5.4.

Terminal Pin	Wire to
TE1	R104
TE2	C58-ve
TE3	C58+ve
TE4	C58-ve
TE5	(i) TB2
	(ii) C65
TE6	T1(20V)
TE7	T1(OV)
TE8	ME1(c)
TE9	(i) ME1(d)
	(ii) TC3
TE10	R104
TE11	not used

## STAGE 7—MAINS TRANSFORMER

Use 16/0.2mm wire.

See Figs. 5.2c, 5.3.

Primary	Wire to
1	S17b
2	linked
3	
4	FS1
SCREEN	Earth terminal
Secondary	
0	TE7
20V	linked
0V	
20V	TE6

## STAGE 8—FRONT PANEL COMPONENTS

First fit SK9 to the front panel, and wire up. Then fit S17 and wire up. Feed mains cable through grommet in rear panel. Connect earth lead to Earth Terminal tag.

Use 16/0.2mm wire for S17 connections.

See Figs. 5.2, 5.3.

SK9a	Wire to
b	X4
c	C55a-ve
d	X2
e	C55b-ve
S17a	X1, X3
S17a	Mains Cable "L"
S17b	FS1
S17b	Mains Cable "N"
S17b	T1(1)

## STAGE 9—REAR PANEL COMPONENTS

Other side of C64 is connected to base plate by solder tag.

Use 16/0.2mm wire for all connections.

See Figs. 5.3, 5.4

Component	Wire to
FS2	TD10a
FS3	TD10b



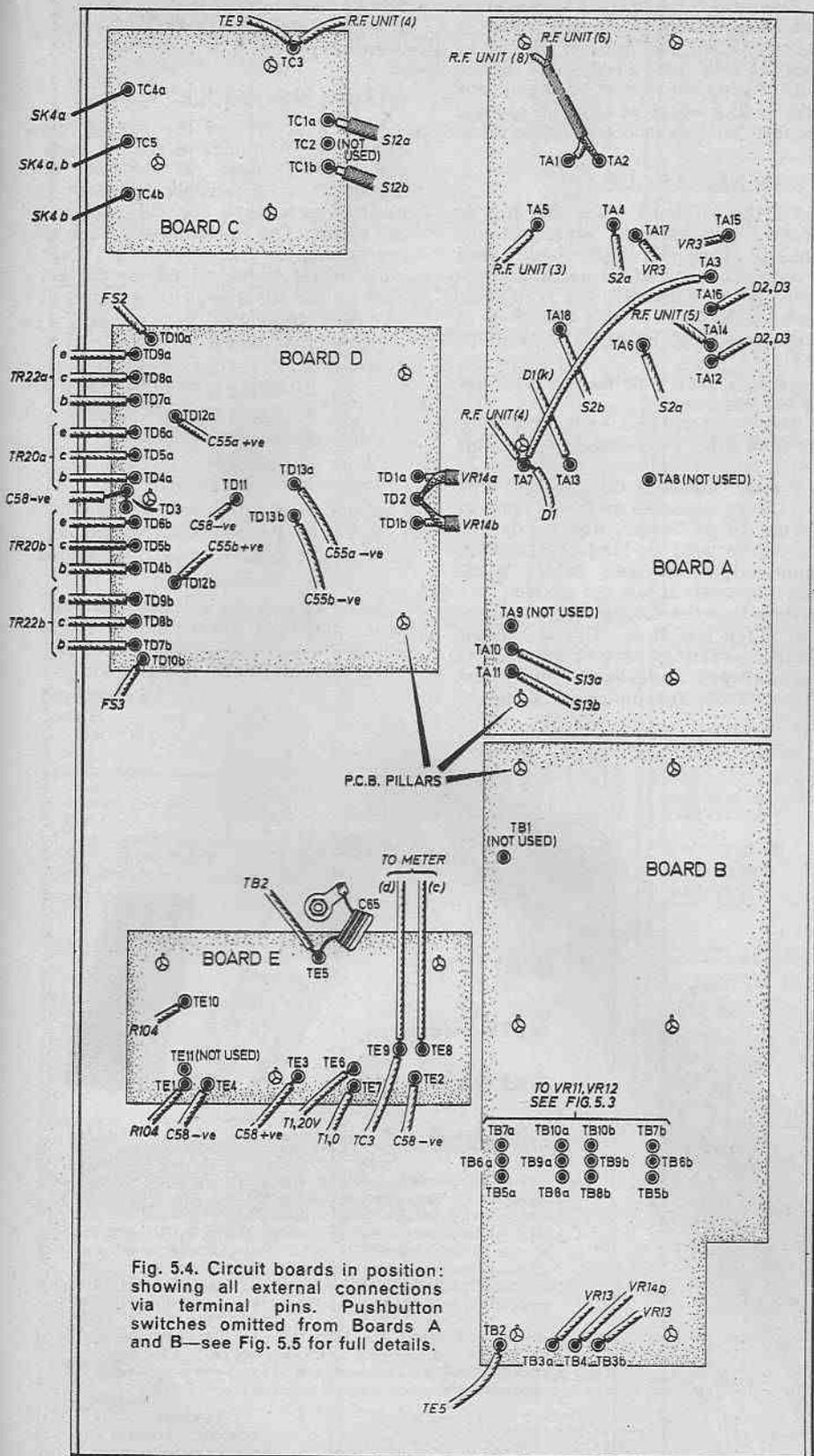


Fig. 5.4. Circuit boards in position: showing all external connections via terminal pins. Pushbutton switches omitted from Boards A and B—see Fig. 5.5 for full details.

Fig. 5.3. (Left) Main assembly: chassis-mounted components with wiring details. For circuit boards see Fig. 5.4. Observe carefully the screen arrangements for each individual cable; on some, no connection is made to the screen at this end.

FS2,3 (com.)	C58+ve
TR22a (base)	TD7a
(collector)	TD8a
(emitter)	TD9a
TR20a (base)	TD4a
(collector)	TD5a
(emitter)	TD6a
TR20b (base)	TD4b
(collector)	TD5b
(emitter)	TD6b
TR22b (base)	TD7b
(collector)	TD8b
(emitter)	TD9b
X4 (Red)	SK9(a)
X2 (Red)	SK9(c)
X1,2 (Black)	(i) SK9(e)
	(ii) C58-ve
	(iii) C64
SK4a	TC4a
SK4b	TC4b
SK4a, b (earth)	TC5
R104	(i) C58+ve
	(ii) TE1
	TE10
FS1	(i) S17a
	(ii) T1(4)
Earth terminal	(i) Mains cable "E"
	(ii) T1(screen)

### STAGE 10—SCREENED CABLES

Use coaxial cable for SK1. For all other connections use lightweight screened cable. Note the correct termination for each cable. Screening must be earthed ONLY where indicated in the diagrams.

See Figs. 5.3, 5.4, 5.5.

#### (a) Input/Output Sockets

Socket	Name	Wire to
SK1	Aerial	R.F. Unit (1) inner (2) screen
SK2a	Aux. 1	S10a
SK2b	Aux. 1	S10b
SK3a	Aux. 2	S11a
SK3b	Aux. 2	S11b
SK5a	Tape Out	VR13
SK5b	Tape Out	VR13
SK6a	Tape in	S16a
SK6b	Tape in	S16b
SK7a	Amp. Out	S16a
SK7b	Amp. Out	S16b
SK8a	Amp. in	VR14a
SK8b	Amp. in	VR14b

(b) Complete all remaining screened cable connections, see stages 3, 4 and 5. Add links to SK7—8.

### STAGE 11—TUNING METER AND POTENTIOMETER

See Fig. 5.3, 5.4, 5.5.

ME1	Wire to
a	S2a
b	S2b
c	TE8
d	TE9
VR3	S3b
Slider	TA15
	TA17

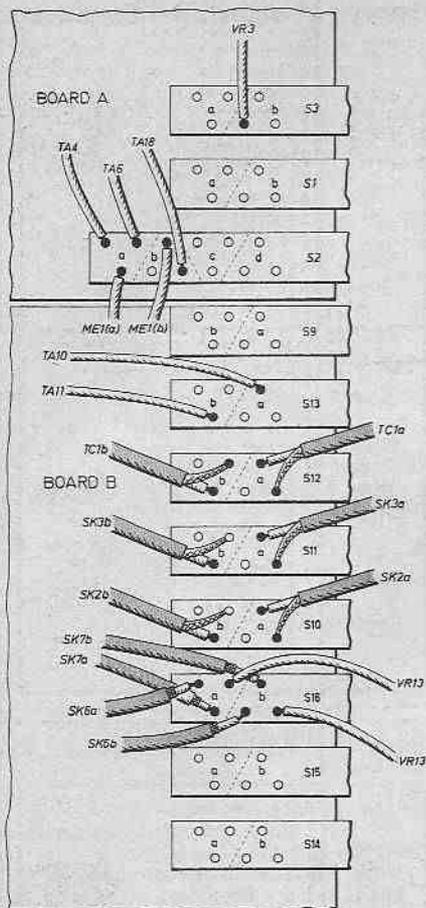


Fig. 5.5. Pushbutton switches: wiring details. Observe carefully the screen arrangements for each individual cable. The screening on cables associated with S16 is NOT connected at this end.

This kind of connecting wire is available in a variety of colours, and it is recommended that several colours be used to help identification of wiring both during the initial wiring-up and also in the event of any subsequent trouble-shooting or maintenance work.

### SCREENED LEADS

Fit the screened leads last but do observe the earthing arrangements: not all screened leads have their braiding connected to earth at both ends: this is deliberate and is to avoid hum loops. Use 7/0.1mm (single core) p.v.c. insulated lightweight screened cable.

Tick off each wire on the diagrams as you progress.

Twist and tin the ends of flexible wires to avoid "whiskers" which could cause shorts to adjacent pins etc.

Plastic cable ties can be used with advantage to secure groups of leads or cables. In particular, five or six ties should be used to bind together the input/output screened cables which run diagonally across the chassis.

Note that the tuning meter is fitted and wired last of all. This is because some connections have to be made to the switches underneath the meter. When fitting the meter it should be

held in place by double-sided Sellotape at each end, between the meter and the scale pan.


### WIRING SCHEDULE

With a project of the size of the 2020 Tuner Amplifier where the work will extend over a number of "sessions" it is sensible to adopt a planned procedure for carrying out the wiring. The following sequence of operations is recommended. Each item should be ticked off on the list (and on the diagrams) immediately it has been completed.

- Stage 1 Board A
- Stage 2 R. F. Unit
- Stage 3 Board B
- Stage 4 Board C
- Stage 5 Board D
- Stage 6 Board E
- Stage 7 Mains Transformer
- Stage 8 Front Panel Components
- Stage 9 Rear Panel Components
- Stage 10 Input/Output Connections
- Stage 11 Tuning Meter

Some operations will have already been completed, during earlier stages—but this comprehensive listing provides a useful double check.


**To be continued**

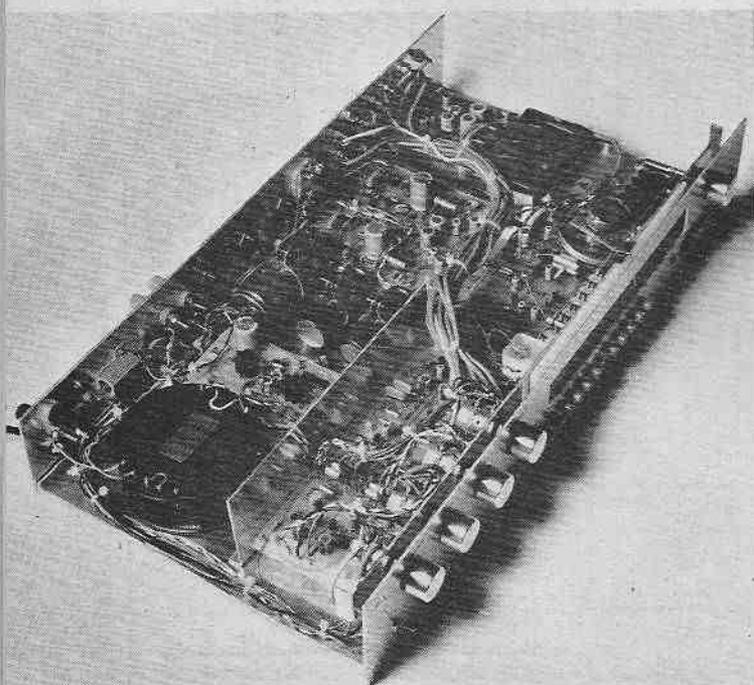
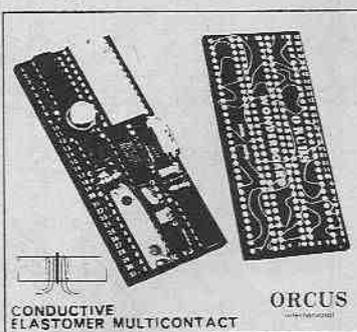
## wonderboard

patents pending

SOLDERLESS CIRCUIT BOARDS  
"One for each circuit"



**Build  
Your Circuits  
Just Once  
In Minutes...**

CONDUCTIVE  
ELASTOMER MULTICONTACT

ORCUS

It's crazy to build, unbuild, construct and destruct your circuits on expensive "Breadboards". Now very economically on WONDERBOARD, you plug your components into one side of the board, the wires into the other, and you install the finished circuit in your equipment. They're like PC boards, but no soldering (which is enemy No. 1 of prototypes). Change any wire or component any time without disturbing others. Up to six interconnecting wires and one component lead into one multicontact. WONDERBOARDS accept all IC's from 4 to 60 pins and discrete components too.

Reliable? They conform to applicable sections of USA Military Standard MIL-A-46 146 and are used by the US Navy. You can't ask for better. WONDERBOARDS the universal board for equivalents of single-sided, double-sided, plated-thru hole, and multilayer printed circuits.

"Small Wonder"  
12 IC DIL-14 capacity  
(Equiv. No. tie-points 1302)

"Big Wonder"  
48 IC DIL-14 capacity  
(Equiv. No. tie-points 5208)

**£2.80**

**£11.20**

All prices include VAT and P&P. Send cheque or postal order to:-

**CHARCROFT ELECTRONICS LIMITED**  
Charcroft House, Sturmer, Haverhill, Suffolk CB9 7XR  
Telephone: Haverhill (0440) 5700 Telex: 817574

**QUARTZ LCD  
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M1

**QUARTZ LCD  
7 Function**

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOP WATCH.

**£9.65**

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M2

**QUARTZ LCD  
11 Function SLIM CHRONO**

6 digit, 11 functions. Hours, mins., secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.

Metac Price  
**£12.65** Thousands sold!

Guaranteed same day despatch.



M3

**QUARTZ LCD  
ALARM 6 Function**

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

**£16.65**



M4

**QUARTZ LCD  
ALARM 7 Function**

Hours, mins., secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

**£19.65**



M5

**QUARTZ LCD Alarm  
Chronograph with Dual  
Time Zone Facility**

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night lights. Only 9mm thick.

**£27.65**



M6

**QUARTZ LCD Alarm  
Chrono with front alarm**

Dual time. Ten function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light.

**£29.65**



M7

**QUARTZ LCD  
Alarm Chrono**

Ten function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

**£29.65**



M8

**SOLAR QUARTZ LCD  
Chronograph**

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins. Split and lap modes. Auto calendar and back light. Powered from solar panel with battery back-up.

**£15.95**



M9

**SEIKO Alarm Chrono**

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00  
METAC PRICE  
**£105.00**



M10

**SEIKO Chronograph**

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap-time. Back light, stainless steel water resistant, HARDLEX glass.

List Price £85.00  
METAC PRICE  
**£68.00**



M11

**SOLAR QUARTZ LCD  
5 Function**

Genuine Solar. Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.

**£ 9.95**

Guaranteed same day despatch.



M12

**HANIMEX  
Electronic  
LED Alarm Clock**



Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 6.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.85 kg).

**£8.65**

Guaranteed same day despatch.

M13

**QUARTZ LCD  
Ladies Slim Bracelet**

5 function.

Hours, mins., secs., day, date and back light and auto calendar.

Elegant metal bracelet in silver or gold. State preference.

**£15.95**

Guaranteed same day despatch.



M14

**QUARTZ LCD  
Ladies 5 Function**

Only 25 x 20mm and 6mm thick.

5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£9.95**

Guaranteed same day despatch.



M15

**DIGITAL  
LED CLOCK**



Automatic brightness control. Weekend alarm cancel.

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

**£10.95**

M16

**HOW TO ORDER**

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100.  
Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME  
Shops open 9.30 - 6.00.

**Metac**

**ELECTRONICS  
& TIME CENTRES**


**North & Midlands**  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

**South of England**  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753
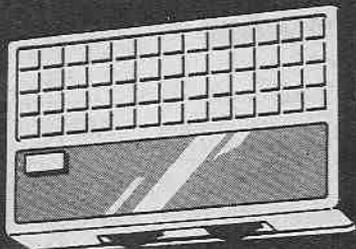
# MICRO CHIMES

FROM THE INVENTORS  
OF MICROPROCESSOR  
MUSICAL CHIMES

A COMPLETE  
KIT FOR THE  
EE  
MICRO  
CHIME



This easy to build kit includes:

- \* TMS1000 Custom MPU Chip
- \* Special purpose designed case
- \* Fully drilled and legended PCB
- \* All transistors, Resistors and Capacitors
- \* Full set of mechanical parts
- \* Smart fascia labels
- \* IC Socket and Loudspeaker
- \* Really Low Price!

only **£8.95** + 55p p&p

**TMS 1000N** - MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.

New low price only **£4.95** inc. p&p  
(Only present 24 tune repertoire currently available.)

New price for the original  
**CHROMA-CHIME 24 tune model!**

Due to the fantastic success of this product right across the World we are able to offer it at

only **£9.95** + 75p p&p

Comes complete with:

- \* TMS1000 Micro
- \* Superb cabinet
- \* All R's & C's
- \* Switches & pots
- \* Fully prepared PCB
- \* All semiconductors
- \* Loudspeaker
- \* Socket & Hardware
- \* Fully detailed kit manual

ALL CHROMATRONICS PRODUCTS  
SUPPLIED WITH MONEY BACK GUARANTEE

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX, UK.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

EE3

I enclose cheque/PO value £ \_\_\_\_\_  
or debit my ACCESS/BARCLAYCARD account no. \_\_\_\_\_

Signature \_\_\_\_\_

# CHROMATRONICS


THE NEW

## EUROSOLDERSUCKER

This 195mm long, all metal, high suction desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £6.80 inc. VAT & P.P.

THE UNIQUE

## EUROBREADBOARD

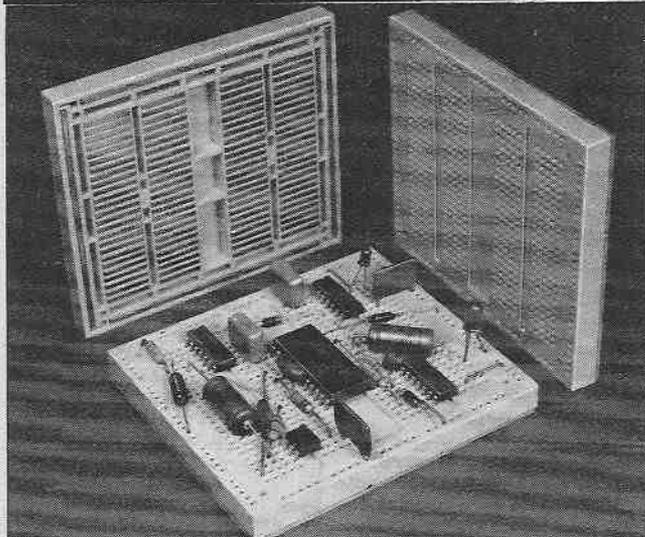

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

**All connection rows and columns are now numbered or lettered enabling exact location indexing.**

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (<10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF



David George Sales  
r/o 74 Crayford High Street,  
Crayford, Kent, DA1 4EF.

Please send me 1 EuroSolderSucker @ £6.80  Please  
or 1 EuroBreadBoard @ £5.80  Tick  
or 2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).

Name \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Tel. No. \_\_\_\_\_

Please make cheque/P.O.'s payable to David George Sales

# RADIO WORLD

By Pat Hawker, G3VA

## A Balanced Level

ONE COMPLAINT which all broadcasting organisations receive frequently is that some listeners consider the balance between the levels of speech and music (or between programmes and advertisements) is poor and results in having to keep adjusting the volume control.

In practice broadcasters go to considerable trouble to try to ensure a correct balance (the IBA for example specifies peak programme levels in nine different categories to take into account subjective differences between music and speech in differing degrees of comparison). Of course, sometimes operational mistakes are made but the simple truth is that it is impossible to please all listeners all of the time—and for very good technical reasons.

Work carried out in Finland some years ago, involving over 3000 listeners, showed conclusively that: (a) young people have preference towards music sounding louder than that preferred by older listeners; (b) what is recognised as a "good balance" between speech and music differs for light and pop music and classical music; (c) preferred listening levels may fall by as much as 6dB in the 20 minutes following the start of listening; (d) people living in cities are appreciably less critical of "loud" sounding music than those living in the country; and (e) in a noisy environment (particularly applicable to listening to car radios) listeners require speech to be some 6dB louder, compared to music, than in a quiet domestic environment.

With all these variations, it is no wonder that broadcasters are still, after 50 years of broadcasting, unable to satisfy all listeners, all of the time.

## Exorcising TV Ghosts

One of the most common defects of TV pictures as seen by the ordinary viewer is the ghost image(s) caused by multipath reception due to the radio signals bouncing off high buildings, towers, hills and mountains. Multipath can also produce problems in the reception of "teletext" pages since even short "echoes" can sometimes result in errors. Of course, it is often possible to reduce or even eliminate ghosts by careful choice and adjustment of aerials but at times one comes up against the really persistent ghost.

Today there is a promising technique that seems capable of

eliminating one or more ghosts: the charge-coupled-device (c.c.d.) which can be used as a delay line in order to provide a signal which cancels out the ghost(s). Some very successful work along these lines has been reported by the Technical Research Laboratories of NHK, Japan. They have shown that a 64-element (or preferably a 128-element) c.c.d. could bring a substantial improvement.

It still remains to be seen whether the cost of such devices, in mass production, can be reduced to a price that would enable them to be put into the ordinary TV set.

## Amateurs into Space

Amateur radio enthusiasts have long been proud of the contribution made to space communications by the OSCAR ("Orbiting Satellite Carrying Amateur Radio") series of satellites of which the first was launched as long ago as December 1961. Apart from making possible long-distance contacts on 144 and 432MHz transmissions they have proved of enormous educational value in space techniques.

Today there are a number of amateur satellites in orbit, both American and Russian, with the equipment built by amateur groups in a number of countries, including West Germany and Australia. But so far no amateur satellite equipment built in Britain has ever been launched.

Now however a serious attempt to build the first such spacecraft is being undertaken at the University of Surrey, with the support of British industry and the AMSAT-UK group. One of the aims of this work is to provide "real-time" ionospheric data of interest to h.f. as well as v.h.f. amateur operators, as well as a number of experiments of general interest. The project is under the management of Martin Sweeting, G3-YJO.

Another specialised field of amateur radio that seems to be attracting increasing support and practical activity in the U.K. is the use of the moon as a large passive reflector: in other words bouncing signals off its surface (moonbounce) to provide a earth-moon-earth path for v.h.f. or u.h.f. signals.

This is no easy task and indeed is difficult to achieve even with a special 1kW transmitter permit, since it requires a highly sensitive and stable receiver of restricted bandwidth and

very high-gain aerials in order to wrinkle out the very weak returning echoes. The path loss is between about 258dB at 300MHz increasing to some 290dB at about 10GHz, and a path loss of 280dB means that to receive back one microwatt of power, an effective radiated power of some 10-million-million kilowatts would have to be shot along the line of the aerial beam!

Because higher aerial gains can be more readily achieved at 432MHz and above, most amateur moonbounce operations have been on u.h.f., but recently a South Wales amateur, David Price, GW4CQT has completed a "worked all continents" feat on 144MHz, possibly a world first for amateur moonbounce.

Commercial and professional interest in moonbounce largely disappeared with the development of the active communications satellite and its main attraction even to amateurs is that, like Everest, it is there. To adapt an old nursery rhyme:

*"The moon shines bright,  
The stars give light,  
And little fading signals,  
Will come tomorrow night."*

The moon has many peculiarities which affect the bounced signals. Early workers believed that returning signals would be too blurred by the large size of this spherical mirror in the sky to be useful. A breakthrough came some 20 years ago with the realisation that the moon appears to radio signals as a partially polished sphere with an efficient central reflecting area, rather like a bright point on a matt ball bearing.

The leading echo thus contains rather more than half the total echo power and is largely unblurred. In fact the moon is about 7 per cent effective as a reflector when compared to the theoretical "equivalent target cross section" in radar terms. Lunar echoes however do have both slow and rapid fading.


## World at their Fingertips

By the time these words appear, the BBC2 Open Door programme on amateur radio ("World at their Fingertips") will already have been transmitted. The Radio Society of Great Britain took responsibility for the programme at very short notice and, at the time of writing, are in the thick of preparations.

Fortunately Brian Rix, G2DQU, was willing to present the programme which it is hoped will underline how this unique hobby appeals to enthusiasts of all ages, performs valuable community services including emergency communications and involvement with the handicapped, continues to contribute significantly to the development and scientific study of radio, and generates goodwill across international frontiers.

# The Extraordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett

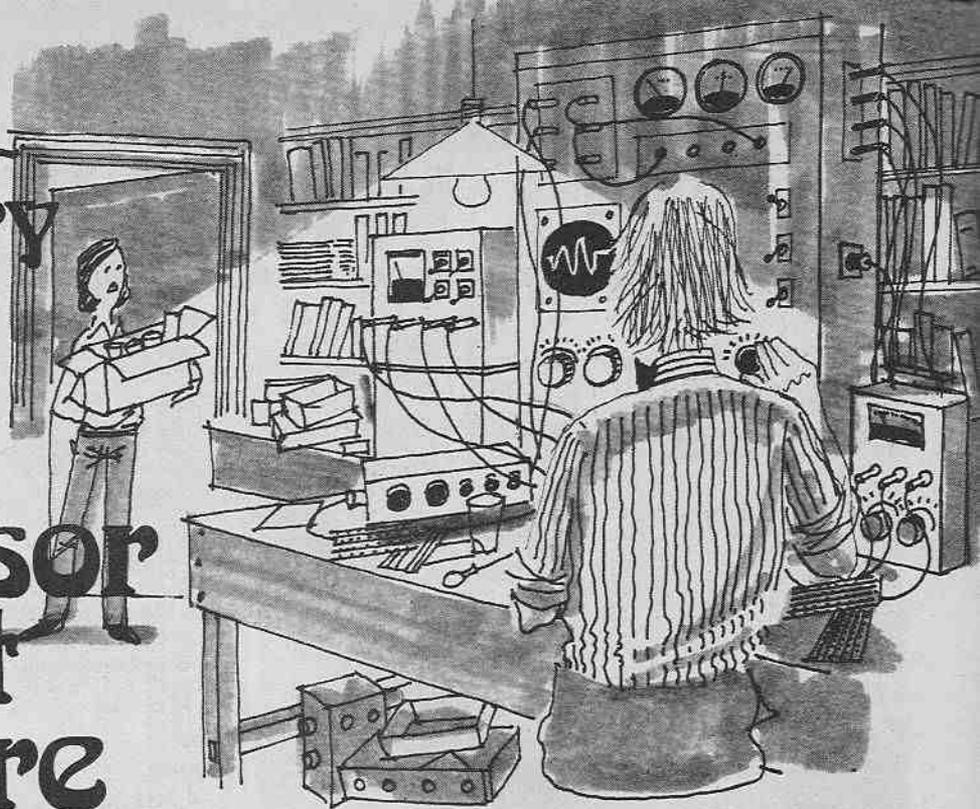

WHILST Professor Ernest Eversure and his young friend Bob had been discussing and carrying out various modifications and improvements to an Audio amplifier, a team of the Prof's experimental robots had been busily constructing a huge device in another part of the Prof's laboratory. Bob has just been shown this device, and reacted with amazement.

"Your comment that it resembles a giant bathysphere is very appropriate, Bob, as the main structural shell is designed to withstand high pressures both from within and from without.

## VACUUM CHAMBER

"Although this device is intended mainly for use as a large vacuum chamber it can also be pressurised for experiments with gases under pressure, and I intend to use it for all sorts of experiments which I found were difficult in my smaller vacuum chambers. Many of these experiments will demonstrate how electronics can be made to work not only here but also in the vacuum of outer space; not only now, but also in the future."

"Prof., this is tremendous, its like something from a science fiction story."

"Do you read much 'Science Fiction', Bob?"

"Yes, Prof., when I have the time. But recently I've found myself disappointed with a lot of the stories. The trouble is that so many of them are written by people who are against scientific progress, so they describe all sorts of harmful results. These are 'Anti-Science' fiction writers who describe all sorts of really great amazing inventions, which makes the story really interesting at first. Then they make all the inventions go wrong, explode, destroy themselves and kill people. It makes science look very bad; and something makes me feel quite bad too after I've read such terrible things!

"There does seem to be a shortage of fiction that is 'pro-science' Bob. Remember that there are those people in the world who will try very hard to misuse the tremendous new powers made available by science. Possibly in the future, more authors will become inspired by the great potentials of scientific discovery correctly used, to usher in a 'New Age of Science', which I think is only just the beginning. Then pro-science fiction will begin to prevail over the current spate from the anti-science writers, and give people a more balanced and positive feeling, especially regarding the advances

in electronics which is the biggest growth area of science-based technologies!"

## SPACE SUIT

"Now I am about to inspect my new experimental vacuum chamber, as the air has now been removed from inside it. One of the advantages of such a large chamber is that I will be able to actually go inside it, unlike the others which are too small!"

"But Prof., how can you go inside a vacuum-chamber? I have been told that it is not possible to survive in a vacuum."

"Of course, Bob, exposure of the human body to vacuum would have immediate dire consequences. So I have designed a special suit which I will wear. It is similar to the space-suits worn for extra vehicular activity in the latest manned space explorations."

The Prof. whistled up one of his robots which brought the gleaming new space suit and helped him into it as Bob watched enviously.


After careful checks, the Prof. opened the door of the airlock and went inside. Bob watched through the transparent panels of the airlock and vacuum chamber as the Prof. emerged from the airlock into the larger space inside the chamber.

# TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK


— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

## STEREO PRE-AMPLIFIERS

MC 1

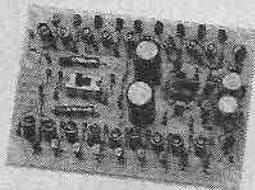

CPR 1

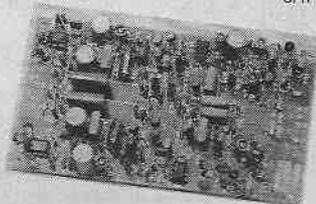

### CPR 1 - THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tone, tuner, etc. up to power amp; signal levels. Signal to noise ratio 86dB; slew-rate 3V/μS; T.H.D. 20Hz - 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 130 x 80 x 20mm. Supply to be ±15 volts.

### MC 1 - PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details. X02 - X03 - ACTIVE CROSSOVERS X02 - two way, X03 - three way. Slope 24dB/Octave. Crossover points set to order within 10%.

### REG 1 - POWER SUPPLY

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

## POWER AMPLIFIERS



It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types; they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μS; signal to noise ratio 110dB; frequency response 10Hz-35kHz; -3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

## POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).
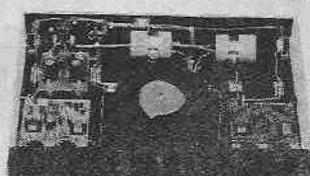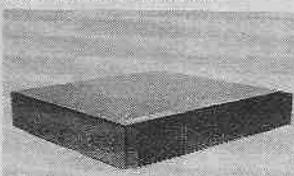
## POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



### ACTIVE CROSSOVERS

X02 £14.83  
X03 £23.06

### POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-035v £16.30  
CE 1004 100W/4 ohms 35-0-35v £19.22  
CE 1008 100W/8 ohms 45-0-45v £23.22  
CE 1704 170W/4 ohms 45-0-45v £29.12  
CE 1708 170W/8 ohms 60-0-60v £31.90

### TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £14.47  
CPS2 for 2 x CE 1004 or 2/4 x CE 608 £16.82  
CPS3 for 2 x CE 1008 or 1 x CE 1704 £17.86  
CPS4 for 1 x CE 1008 £15.31  
CPS5 for 1 x CE 1708 £22.88  
CPS6 for 2 x CE 1704 or 2 x CE 1708 £23.98

### HEATSINKS

Light duty, 50mm, 2°C/W £1.30  
Medium power, 100mm, 1-4°C/W £2.20  
Disc/group, 150mm, 1-1°C/W £2.85  
Fan, 80mm, static 120 or 240v £18.80  
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules. £29.16

### THERMAL CUT-OUT, 70°C

£1.38

### POWER AMP KIT . . . £32.40

#### PRE-AMPS:

These are available in two versions - one uses standard components, and the other (the SI) uses MO resistors where necessary and tantalum capacitors.

CPR1 £25.48 CPR1S £39.98

MCI £18.50 MC1S £29.49

POWER SUPPLY:

REG1 £8.75 TR6 £1.75

#### BRIDGE DRIVER, BDI

Obtain up to 340W using 2 x 170W amps and this module. £6.40

**CRIMSON ELEKTRIK**  
1A STAMFORD STREET,  
LEICESTER LE1 6NLL  
Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra. £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 international Reply Coupons for detailed information. UK - please allow up to 21 days for delivery.

Distributor: Minic Teleproducts, Box 12035, S-750 12 Uppsala 12, Sweden.

Newnes

# constructors projects

☆ This new series has been specially compiled for the electronics enthusiast.

Each book contains a collection of constructional projects, giving details of how the circuit works, how it may be assembled and how setting-up and trouble-shooting problems may be solved. The skilful use of colour in the text helps to clarify circuit operation, and circuit board layouts are suggested. Shopping lists of components are drawn up for each project.

☆ The first four titles are available now at £2.25 each (US \$5.25)

Electronic Projects in Audio R. A. Penfold

Electronic Projects in Hobbies F.G. Rayer

Electronic Projects in the Home Owen Bishop

Projects in Radio and Electronics Ian R. Sinclair

☆ Also available six Constructors Guides:

Electronic Diagrams £1.80 US \$4.25

Electronic Components £1.80 US \$4.25

Simple Circuit Building £1.90 US \$4.50

Printed Circuit Assembly £1.80 US \$4.25

Project Planning and Building £1.90 US \$4.50

Practical Electronic Project Building £1.90 US \$4.50

Write for a free colour brochure about all our hobby books to

**Newnes Technical Books**

Borough Green, Sevenoaks, Kent TN15 8PH



They could converse through a nearby intercom as the Prof. carefully checked some of the apparatus. "I feel left out, Prof.," Bob complained as he watched. "I wish I could wear a spacesuit and come inside the vacuum chamber! It looks almost as exciting as being a real explorer in outer space!"

"Okay Bob, if you stand on that platform I will get the robots to measure you for a suit!" Bob eagerly clambered onto the nearby platform and stood with his arms slightly raised as the Prof. instructed from inside the vacuum chamber.

## LASER METROLOGY

Now three robots carefully positioned themselves at equal distances from the platform and pointed strange pieces of electronic apparatus in the direction of Bob's body.

"Prof., what are they doing?" Bob asked apprehensively. "It looks as if the robots are about to blow me apart with ray guns!"

"Too much anti-science fiction, Bob! What the robots are about to do is quite harmless. They will use a modern electronic method of 'Laser Metrology' to measure you. This combines electronic sensors and measuring devices with low-power laser optics."

The platform began to rotate very slowly and pale laser beams flickered over Bob as the robots used their laser metrology devices to measure him for the spacesuit. "Don't worry, they are specially programmed not to shine their lasers into your eyes, Bob", the Prof. reassured him.

"For something as important as a space suit, the measurements must be accurate as possible and the suit is specially made to fit the wearer. Laser metrology gives the advantage of accurate measurement in three dimensions and will produce a much better fit.

"In the future, similar techniques may be used to measure clients for ordinary clothes. Then, combined with an electronic machine which will make a suit in a matter of moments when fed with the measurements, electronics will have a huge impact on the world of fashion, and enable people to have more appropriate and better clothing according to their needs, conditions, the weather and so on!"

"Wow, Prof. Soon we'll see the instant spray-on suit of clothes in an aerosol can with a disposable micro-processor built into the bio-degradable plastic push-button!"

Next the robots brought the materials for Bob's space suit and took them through the airlock into the vacuum chamber where, under the Prof's supervision they began to use a number of interesting electronic devices to aid them in making the spacesuit. One was a laser cutter which they used to trim the plastic material to size.

"The robots will use a number of techniques of fabrication which rely heavily upon electronics for their effectiveness," the Prof. informed him, "and these same techniques will, I expect, be used more in future space missions. In most instances results will be better than could be obtained in open air due to the lack of atmospheric contamination. However, this will mean more electronics yet again. Many of these operations, involving use of heating, are carried out with heat from fuels such as coal, oil and gas here in the Earth's atmosphere.

## SOLAR RADIATION

"To carry out similar operation in space the heat will be produced either by using direct solar radiation with electronically position and focused mirrors, by mechanical friction for operation such as friction welding, or by electrical and electronic means. Experience with these methods could mean an increasing use of electronic methods of heat processing on earth and a reduction in the use of fuels which pollute the environment, as most of these electronic methods produce clean heat with very accurate control."

Bob watched as the laser sliced neatly through the shining plastic and the robots carefully manoeuvred diffusers to dissipate the energy of reflected portions of the beams. "I can see," he observed, "that even inflammable materials may be laser-cut in a vacuum without catching fire, and with some fusible materials the cut portions would be sealed by heat fusion."

"Yes, Bob, and in cutting, joining and heat-treating metals and semiconductors with the aid of electronics in a vacuum, the quality of the final product can be much better than when similar

operations are carried out in air. Many metals and semiconductors, when hot, would absorb oxygen, nitrogen, hydrogen and other gases with which they come into contact, and this can ruin the properties of a highly purified substance."

## DIELECTRIC WELDING

Now the robots began to use a high-frequency dielectric welder to join the seams of the suit.

"This is a method which may be used to join dress materials and clothing fabrics, sheet plastics and small components. When applied to clothing and similar fabrics it has many advantages over older traditional methods such as stitching.

"Dielectric welding doesn't have to be done in a vacuum, it can be done in the air; however, when it is done in a vacuum this avoids the trapping of air-bubbles and airborne dust and impurities within the weld.

"This means that in your space suit the fabrics are being joined with strong, fault-free seams which could not be done so easily by other methods."

"That is good to know," Bob watched as the space suit rapidly took shape before his eyes. "Prof., some of the uses of electronics in space and other environments are really fascinating and I would really like to know a lot more about these things."

"You'll be able to learn about some of them by first hand practical experience very shortly, Bob."

To be continued

## Crossword No. 14—Solution

1	M	A	2	T	R	3	I	X	4	B	5	A	6	R	6	D	7	B	8	C
A	E	D	R	B	A	U	A													
S	R	O	I	O	T	R	T													
9	T	I	M	E	L	A	G	10	U	N	E	A	R	T	H					
11	C	O	N	T	12	A	C	T	E	D	13	O	U	N	D					
U	A	P																		
14	T	E	L	E	P	H	O	N	E	N	U	M	15	B	E	R				
A																				
16	M	E	T	R	E	17	V	E	18	R	Y	T	E	S	T	Y				
A																				
19	C	20	R	E	21	E	N	S	22	O	23	U	B	L	E	24				
T	A	A	I	I	R	E														
E	I	R	O	S	N	S	A													
25	U	N	26	Y	N	T	H	E	S	I	S	E	R							

MAIL ORDER DEPT.

# CRESCENT RADIO LTD.

1, ST. MICHAELS TERRACE, WOOD GREEN, LONDON, N22. 4SJ.  
PHONE 01-888 3206



"FLIP"

Push button heads or tails.  
Complete kit and full instructions supplied.  
A pocket game.  
Easy to build and great to play.  
Kit price—£5.25 + 8% VAT. Post free.

## 4 OHM DOOR MOUNTING CAR LOUSPEAKERS



High performance, door mounting, 5 1/2 inch units with smart front grill, 10 oz magnet, 12 watts, 4 ohms. In attractive see-through carton. £12.60 + 12 1/2% VAT. per pair.

## HEAVY DUTY XOVER 2 WAY 8 OHM

A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100 watt. Fitted with screw terminals for input and a three position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB. ONLY £3.00 + 8% VAT

## A CRESCENT 'SUPERBUY' Goodman's 5" 8 ohm long throw H/D loudspeaker.

Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5 1/2" (diagonally). ONLY £5.00 + 12 1/2% VAT

## LOUDSPEAKERS + 12 1/2% V.A.T.

- 2 1/2" (57mm) 8 or 75 ohm 90p (please state impedance req'd)
- 2 1/2" (60mm) 8 ohm (limited stocks) 60p
- 2 1/2" (70mm) 8 ohm (limited stocks) 60p
- 5" 8 ohm Ceramic £1.50
- 8" "ELAC" 8 ohm 15W dual cone £5.00
- 8" "GOODMANS" 'Audiom 8PA' 8 ohm 15W £4.95
- 7" x 4" 8 ohm 4W £2.00

## CR 4110 DESOLDERING PUMP



ONLY £6 + 8% VAT

High suction pump with automatic ejection. Knurled, anti corrosive casing. Teflon nozzle.

## 3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000W lighting per channel, max. This 3 channel sound to light unit is housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions supplied. S.A.E. for spec. sheet. ONLY £20.00 + 8% VAT

## CR LV1 12v DRILL



£12.00 8% VAT  
BRITISH MADE "Versadrill", 12 volts DC. Compact battery operated power tool, sufficiently powerful to perform all the operations associated with 240v drills. Dimensions:— 150 x 50mm (dia.)



'P&P' ORDERS UP TO £5, Add 30p  
ORDERS £5-£10, Add 50p  
All orders over £10 post free!  
Please add VAT as shown.  
S.A.E. with all enquiries please



Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N13.  
ALSO: 13 SOUTH MALL, EDMONTON GREEN, EDMONTON.

## INTRODUCTORY 2-WAY OFFER!!

1. Try the C-More BATTERY CONDITION DISPLAY with a 10 DAY MONEY BACK OFFER.
2. Order promptly and buy at 20% BELOW NORMAL COST (offer must end soon)



NEAT  
DASHBOARD  
INSTALLATION  
—takes only  
a few minutes

The C-More mounts easily on the dash with adhesive pads (supplied), and connects to earth and an ignition wire through a quick connector (also supplied).

The battery voltage is electronically monitored immediately the Ignition is switched on, and presented through a LED display using a novel split colour comparator.

The all electronic display shows both red and yellow when all is well. Red only shows low battery or charge, and yellow only shows over-charge. Full fitting and operating instructions even highlight probable cause of faults when they occur. Helps prevent those unnecessary and expensive replacements.

Not £5.95 but £4.75 + 25p P. & P.

An exclusive offer to readers of Everyday Electronics who care about the state of their battery and charging system, and want the best instrument to show them—simply, accurately and reliably. Cut out and post the coupon today, to:

## HARVELEC

(Dept. EE), 1 Formby Avenue, St Helens, Merseyside, WA10 3NW. (Registered no. 2121208)

Please send..... C-Mores at £5.00 ea. (Inc.) (+ 25% for export please) to:

..... Cheque/P.O. Value: .....


I understand this order will be despatched within 4 days of receipt, and that if I'm not fully satisfied I can return the units within 10 days for a full refund of the purchase price.

# The latest kit innovation!
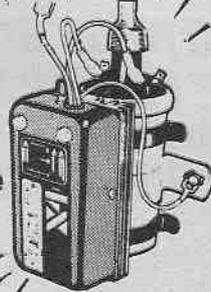
## from Sparkrite



the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing. Electronics Design Associates, Dept. EE 2 (U.K. only).  
82 Bath Street, Walsall, WS1 3DE, Phone: (9) 614791

Electronics Design Associates, Dept. EE 4  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name .....

Address .....

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P. (U.K. only.) QUANTITY REQ'D. Send SAE if brochure only required.

X4 KIT	£16.65	
TACHO PULSE SLAVE UNIT	£3.85	

I enclose cheque/PO's for £ .....

Cheque No. ....

PLEASE STATE POLARITY POS OR NEG EARTH.  
Access or Barclaycard No. ....

# GREENWELD

443D Millbrook Road, Southampton  
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## THE NEW 1978-9 GREENWELD CATALOGUE

### FEATURES INCLUDE:

- 50p Discount Vouchers
  - Quantity prices for bulk buyers
  - Bargain List Supplement
  - Reply Paid Envelope
  - Priority Order Form
  - VAT inclusive prices
- PRICE 30p + 15p POST

## KITS OF BITS FOR THIS MONTH'S EE PROJECTS

### LABCENTRE

A portable "instant" electronic workshop with tools, power supplies and test equipment for design work in logic (TTL and CMOS), audio, r.f. etc.

### CAR DIRECTION INDICATOR ONE-TRANSISTOR RADIO

Prices not available at time of going to press. Please send S.A.E. for full details.

### OLD FAVOURITES

Still available from previous months.

M.W. MINI	£2.50
SOUND TO LIGHT UNIT	£1.85
HOT LINE GAME	£2.25
AUDIO EFFECTS OSCILLATOR	£2.25
AIR FRESHENER	£7.95

### JANUARY PROJECTS CONTINUITY TESTER

All parts except box ... £2.40

### LIGHTS REMINDER

All parts including box ... £3.35

### I'M FIRST

All parts excluding containers ... £1.55

### ROULETTE

All parts as specified except materials for case and bowl for £11.95  
I.C. sockets £1 extra if required.

### E.E. 20+20 TUNER AMPLIFIER

We can supply all parts required except the components for the RF unit for approx. £40. Send SAE for detailed list.

NOTE: A more detailed list of parts supplied in these and other kits is available on receipt of a SAE.

## "DOING IT DIGITALLY"

This new series which started October 1978 is bound to be a big success. We supply a complete set of parts (as we did for last year's Teach-in series) for just £19.75 + £1 post for the Electronic Test Bed, and £2.75 for additional parts required for first 6 parts.

### THE GREENWELD Amplifier Kit

Ideal for the beginner to make, this kit is complete right down to the last screw! Easily constructed on the PCB provided, the 4 transistor circuit will give 2W output from a crystal cartridge. Battery version £1.75, or with transformer for mains operation £3.95

### PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

\* **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

\* **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!

\* **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

**K001** 50V ceramic plate capacitors, 5%. 10 of each value 22pF to 1000pF. Total 210. £3.35

**K002** Extended range. 22pF to 0.1µF. 330 values £4.90

**K003** Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF, 110 altogether for £4.75

**K004** Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

**K005** Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30

**K006** Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 parts for £14.20

**K007** Electrolytic capacitors 25V working small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

**K008** Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

**K021** Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors, £6.00

**K022** Extended range, total 850 resistors from 1R to 10M £3.30

**K041** Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V. E24 series. Total 260 for £15.30

**K042** As above but 5 of each value £8.70

### TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 85p; 1A £2.50, 6-0-6V 100mA 85p; 1½A £2.40, 9-0-9V 75mA 85p; 1A £2.10. Multitapped type 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £8.90; 20V 2½A £3.90; 25V 1½A £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50; 12V @ 250mA twice £2.90

### RELAYS

**W847** Low profile PC mntg 10×33×20mm 6V coil, SPCO 3A contacts. 83p  
**W817** 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A. 85p  
**W829** 50V ac (24V DC) coil, 11 pin plug in type, 3 pole c/o 10A contacts. Only 85p  
**W846** Open construction mains relay, 3 sets 10A c/o contacts. £1.20  
**W877** 675R 12-27V. DPCO 23 × 20 × 10mm sealed can 88p.  
**W899** 250V a/c. DPCO 10A contacts, enclosed case £1.30.  
**W830** 200R 6-12V DPCO, 23 × 20 × 10mm, sealed can 88p.  
Send SAE for our relay list—84 types listed and illustrated.

### HEAT SINK OFFER


Copper TO5 sink 17mm dia × 20mm, 10 for 49p; 100 for £3; 1000 for £25

### POLYTHENE SHEET

Size 36 × 18" 200g. Hundreds of uses around the home. 100 sheets for £1.50. Box of 1500 for £19
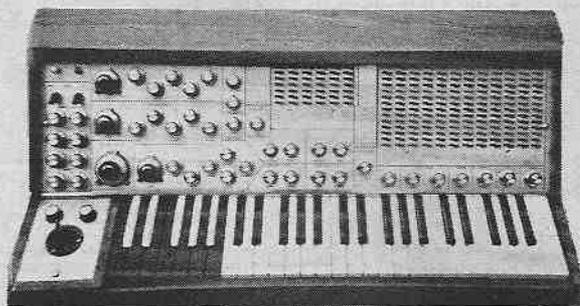
## BUILD A SYNTHESISER!

NO SPECIAL SKILLS  
SPECIAL EQUIPMENT REQUIRED



Using **Dewtron** (Reg'd)  
PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

## D.E.W. LTD.

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR

### 4-STATION INTERCOM



£22.95  
V.A.T. £1.84

Solve your communication problems with this 4-station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Offices. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. A Battery and other accessories. Adaptable for mains. Battery eliminator £6.75 (optional) P. & P. 99p.

### NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY  
£16.95  
+ V.A.T. £1.36

Latest improved transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increases efficiency in the office, shop and surgery. Perfect for "conference" calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control. Conversation recording model at £19.95 + VAT £1.60. P. & P. 89p.

10-day price refund guarantee on all items.  
WEST LONDON DIRECT SUPPLIES (KE12) 189 KENSINGTON HIGH STREET,  
LONDON, W8 8BN. 01-837 5548

## HAVE YOU DONE IT LATELY!

Fit a new tape head and transform the performance of your tape recorder

**MENLITH**

THE MENLITH ELECTRONICS CO. LTD.

QUALITY  
REEL TO REEL  
AND CASSETTE TAPE HEADS




Full Catalogue 25p

Please enclose  
20p P&P with order


B24-RP stereo cassette glass/ferrite record/playback £9.84  
B12-01 mono cass. playbk. £1.60 B24-Q1 stereo cass. playbk. £2.80  
A28-05 stereo 8tk cartridge £1.80 E12-09 stereo/mono cass. erase £1.80

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321

### BUSH "PARTY AMP"

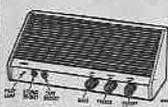


This very attractive unit is a complete mono amplifier originally designed as the second channel BUSH record players. All solid state, the case houses good quality speaker, power supply, pre-amp and controls. Standard DIN socket input accepts ceramic cartridge direct 240v operation. Brand new and boxed complete and screened DIN to DIN connection lead and instruction leaflet. Many uses include baby alarm, guitar practice amp, booster amp for transistor radios, etc. etc.

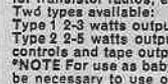
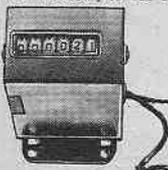
### 6 DIGIT COUNTER

one pulse at mains voltage moves 1 digit—not resettable—real bargain @ 80p.



### MAINS BLOWER

The Torrin—quiet but powerful outlet size 2 1/2 x 1 1/2 for cooling equipment etc. will extract of outlet is blowing outwards price £5.50. Other models from £2.00.

### PP3/PP9 REPLACEMENT

Japanese made in plastic container with leads size 2in. x 1 1/2in. x 1 1/2in. complete power a calculator or radio. It has a full wave rectifier and smoothed output of 9V suitable for loading of up to 100mA. £2.53.



### MICRO SWITCH BARGAINS

Rated at 5 amps 250V. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 (two types) for £1.25.



### INDUCTION MOTORS

One illustrated is our reference MM11 made for ITT 3 stack 1 1/2 spindle £2.25, 4 stack model £1.75, 1 stack £2.75, 1 1/2 stack £3.25.




### MOTORISED DISCO SWITCH

With 10 amp change-over switches. Multi adjustable switches are rated at 10 amps. This would provide a magnificent display. For mains operating. 8 switch model £2.25, 10 switch model £3.75, 12 switch model £4.75.


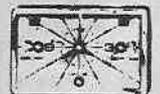
### 25A ELECTRIC PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp on/off switch. Switch on time can be set anywhere to stay on up to 6 hours independent 60 minute memory jogger. A beautiful unit. £3.50.



### SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £9.95.



### CAR STARTER CHARGER

Our own kit this has proved a godsend to many motorists contains 20 amp transformer and bridge rectifier switch HD resistor and full instruction £9.95.




### RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set £3.95.
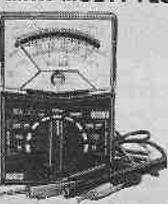
### MINI-MULTI TESTER

Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—1000 opv—mirrored scale. 11 instant ranges measure:—DC volts 10, 50, 250, 1000, AC volts 10, 50, 150, 1000, DC amps 0-1 mA and 0-100 mA continuity and resistance 0-50K Ohms. Complete with insulated probes, leads, battery, circuit diagram and instructions. Unbelievable value only £6.99 + 50p post and insurance.



### MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of Plesey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.



### ELECTRONIC VOLTMETER/SENSITIVE RELAY

Consists of a large, extremely readable, 4 1/2" square, extremely drop through panel volt meter, 0-0-1 f.s.d. Built into the front of the meter are two screw adjusters which move two separate pointers, one red and one green, up and down the scale, the purpose being to set a minimum and maximum level so that when the needle falls below or rises above the preset levels a unique 'under' and 'over' circuit inside the meter operates one of two relays to bring an 'under' or 'over' circuit into action. The scale plate is detachable via two screws to be calibrated to your own individual requirements. The 10 transistor 'under' and 'over' circuit is completely separate from the meter movement so does not have to be connected to use this as a standard 0-1 meter. Many uses including level controls, light controls, auto battery chargers, alarm units, etc. etc. Manufacturer's list price of over £120 each. An unbelievable snip at £17.75 + 62p, p. & p. 90p. (Less than value of the meter alone). Circuit diagram included.

### G.P.O. HIGH GAIN AMP/SIGNAL TRACER

In case measures 5 1/2 x 3 1/2 x 1 1/2 extremely high gain (70 DB) solid state amplifier designed for use as a signal tracer on GPO cables etc. Functions very well as a signal tracer for fault finding in radios etc. etc. By connecting a simple coil to the input it becomes a useful mains cable tracer. Uses standard 4.5v battery and has input, output sockets and on-off volume control mounted flush on the top. Many other uses include general purpose amp, cueing amp etc. etc. An absolute bargain at only £2.25. Suitable 80 ohm earpiece 80p + 5p.

### PLUG IN MODULES



MODULES Neat 'plug-in' size approximately 2" long x 2 1/2" wide x 1 1/2" high. Japanese made, 6v operation, solid state, eight different types to perform various functions as follows—

**FIRE ALARM MODULE (BM71)** Used with thermostatic switch or switches and 6v battery this will drive a speaker and give audible alarm. Note: Ceiling type, white, fire operated thermal switches available £2.50 + 12p ea.

**ELECTRONIC ORGAN MODULE (BM31)** This is a tone oscillator especially designed for an electric organ. Requires an external 10k resistor miniature variable type to provide various notes.

**RAIN ALARM MODULE (BM61)** Intended to detect rain or moisture and will operate a loud speaker with a high frequency sound which will vary in intensity to a degree which depends on the amount of moisture collected. A grid type pick up is recommended with a spacing about 1/16" between grids (the raindrops short the grids).

**PHONO PREAMPLIFIER (BM1)** Will amplify the output of a magnetic cartridge, tape head, timer etc., up to about 1 volt, and give a reasonably flat response curve, should suit most amplifiers.

**DUAL LAMP FLASHER (BM100)** An electronic switch designed to flash two miniature bulbs alternately at 1/2 sec. intervals with any 6v, 1 to 3 amp bulb. Ideal for flasher of model car, model plant and boat, warning of railroad crossing of HO gauge; display attention gear, car emergency warning, etc.

**MORSE CODE OSCILLATOR (BM42)** Miniature transmitter, it transmits a modulated signal (400-3000hz) which can be picked up with normal AM radio receiver. Also ideal for a signal source on test bench for tracing troubles in AM radios.

**METRONOME MODULE (BM32)** Designed to vary the tempo from approximately 40 to 208 beats per minute a complete solid state electronic timer only a speaker, a potentiometer and a 6v DC supply are required to complete. Could easily be tucked away into our £4 extension speaker to make a nice looking instrument.

**BURGLAR ALARM MODULE (BM70)** This module enables connection to as many trigger mats, window switches, micros etc. as you require, and when the circuit is closed will emit a horn type sound from the speaker. No power is consumed in the nonalarm condition, therefore giving long battery life. PRICES any module £1.95, bases optional 85p.

**Terms: Prices include Post & VAT. But orders under £6.00 please add 50p to offset packing. Bulk enquiries—Please Phone for Generous Discounts 688 1833. BARCLAYCARD & ACCESS ACCEPTED**

### IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—It's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

**COMPUTER EQUIPMENT** We are stocking a wide range of computer equipment including:

**MEMOREX 8" floppy disc drives**, as new, £180.56 + £14.44 VAT  
**TELETYPES ASR33** from £295, KSR33 from £175

**SPERRY UNIVAC Display Keyboard** with VDU Unicopac 300 from £90.00  
**5V 2.5 AMP P.S.U.** With Circuit £6.71 + 54p, pp £1.75  
**CLO RACAL Supergrade cassettes** with library cases 2 for £1, 10 for £5.20

A range of TTL and other components is now stocked at the Shop.

**OSCILLOSCOPES** We now have a good range of scopes ex stock at the shop, prices range from £40—£275 for example: Double Beam Scope—working order £45  
Phillips Single Beam—working order £35  
CT436 Double Beam DC-8mhz, as soon £75

Marconi TF 2200 Double Beam DC-22mhz perfect order £225  
Tektronix 545A double DC-24mhz £175  
Scopes sell very fast we strongly advise a visit to the shop where personal callers can snap up bargain! Mail customers please telephone for availability.

**Constant Voltage Auto-Transformers** made for operating American made computer equipment of standard 230-240v mains. Input voltage can be plus or minus 20%, output voltage would be a steady 115v. They are beautifully made regardless of cost. We have two models, one 300w price £49.50 or 750w price £75. Carriage depending on distance.

**Telephone Headset and Mouthpiece** As used by switch-board operators, made for the GPO so obviously best quality. Very lightweight so not uncomfortable to wear. £3.75.  
**Telephone Plug Short GPO 4 pole type**, reference number 420, as currently used with plug-in telephones, ex equipment but unused. 85p.  
**Telephone Socket Panel** mounted, 4 pole, will take the 420 plug. 75p + 6p.

**Strong Metal Box** Just the right size to hold in your hand approx. 5 1/2" x 3 1/2" x 1 1/2", removable lid and top punched to take controls. This has dozens of uses, particularly suitable for making rugged portable test systems. £1.98.  
**1000 Watt Heat and Light Lamp** Mullard type, suitable for high speed drying, or for quick heat, especially where localised heating is required in workshops are warehouses where general heating is impossible costwise. Supplied complete with holder and mounting clips. £4.90.

**Making a Convexor Heater?** We can offer a bank of four 1kw metal clad elements all mounted on a 3" square iron plate. By comparatively simple switching 8 heat outputs ranging from approximately 250 watt to 4000 watt can be achieved. The elements, which are in the form of loops with push on tag connectors, extend to a length of approx. 17" from the plate, so a relatively compact simple convexor heater could be made using this; if a blower is also fitted then the overall size can be kept relatively small. Suitable blowers are available price £2 each. Price of the element £3.50 plus 28p, pp £1.25.

**Waterproof Heating Element** Many uses include, winding round water pipes to prevent freezing, under seed boxes to assist germination in gloves or boots to keep them warm etc. 13 yard length gives approximately 30 watts at 230 volts, has self regulating temperature control. Price 85p + 7p.

**0-40 amp AC Panel Meter** This is a surface mounted meter 2 1/2" dia. calibrated at 50hz being moving iron it should also be suitable for DC. Reasonably linear scale gives very clear readings at 1 amp intervals up to 40 amps. No external shunts necessary. £2.20.

**Dual Range Panel Meter Scale** calibrated 0-10v and 0-500v. 2 1/2" flush mounting this has internal resistor for the 10v range but would require external resistor for the 500v range. A very sensitive 20k per volt movement. First class British Manufacturer. £3.24.

**SUPER VALUE HARDWARE PACK** Ever been stuck for the right nut, bolt, giant hardware pack, contents include nuts, bolts, screws, washers, spacers etc. Mixed in BA, whitworth and metric threads, contents are in brass, bronze, steel, etc. 2lb per bag, average contents 400-600 pieces. £2.50.

**900 WATT TRANSFORMER** 110v 8 amps centre tapped. The winding however is extra heavy gauge so this will carry up to 16 amps at 55 volts. Made by Foster this is impregnated and varnished with very substantial clamps and punched for base mounting, also has a terminal platform with screw down terminals—weight approximately 30lbs. Has many applications including welding. £17.28 carriage £3 (mainland only). Order transformer free. TMS.

**TELEPHONE CABLE MODULE** The GPO to verify rigid specification, circular PVC overall, 15 core colour coded 46p per metre. 10 colour coded cores 30p per metre, 6 colour coded cores 25p per metre, 4 colour coded cores 22p per metre, 2 core, but made of extra strong wire for straining across open wires etc. 30p per metre. Plus 25% to the price to cover cost of post and packing and VAT.

**TELESCOPIC AERIAL** 5 sections 21" when extended, Nickel plated superior make, one nut fixing, fold over for FM. 97p.

**HALF PRICE OFFERS.** 1. Cassette player recorder not second hand but because of a small technical defect or case blemish or something similar we are not asking the recommended retail price of £19.90. Our price is £12.15. Don't miss this bargain.

2. 8 Transistor Radios again new but slightly faulty, 10 for £11.25. 12" GONG ALARM BELL Mains operated for fixing outside. Metal cases and gongs are made from heavy cast iron, this is a real quality product suitable for factory, warehouse, block of flats etc. £25.00 + carriage £3. Mainland only.

**CONTINENTAL RELAYS** Plug in standard bases or can have wires soldered directly to tags.—Ref Rel Ct 700 ohm (18-24v) coil 4/0/54p, Ref Ct 180 ohm (6-12v) coil 4/0/21.08.

**SLEEPER** Makes a sound very similar to the Black & Decker smoke alarm. 12ac, or 12-24v ac. Ideal for fire and smoke alarm, anti-mugging device, car or motor anti-theft. American made, compact about the size of an egg. £1.35. Order Delta Sleeper. A large quantity in stock so we will be glad to quote special price for quantity user.

**8 TRACK CASSETTE PLAYER** 12 volt Japanese make stereo amplifier for car sound entertainment. Perfect order £7.35. Speakers in sloping cases only £4 per pair if ordered with player.

**VARIABLE INDUCTANCE CHOKE** A choke will oppose the flow of AC depending on how much its core is saturated, therefore, if the choke is built with a separate coil for deliberately saturating the core, a small variable dc current will act as a voltage regulator for lamp dimming and a multitude of other purposes. We offer such a choke of 8 amps AC rating requiring 75mA DC control current at bargain price of £24.34. Carriage £5.00 + 40p. This choke weighs approx. 60lbs.

**PANEL METER** 0-1mA Japanese made full vision perspex front, flush mounting. Price £3.24.  
**PHOTO MULTIPLIER TUBE** American RCA, their type no. 4555. Have a gain of a million or more, regular price over £20 but we offer these brand new at £4.95 + 36p.

# ELECTRONI-KIT

**"EDUCATIONAL KITS OF EXCEPTIONAL QUALITY"**

(AUDIO magazine)



## THIS IS A POWERFUL RADIO RECEIVER!

The same kit is also 150 other different actual working projects e.g.:

Computer & Logic Circuits, Electronic Organ, Timer, Light Control, Agility Tester, Lie Detector, Siren, Horn, Buzzer, Bird, Metronome, Cds cell light & sound control, Photogun, Light Oscillator, Light Switch, Light and Sound Morse Code, Field Strength Meter, Hygrometer, Sphygmometer, Etc., Etc.

Radio Receiver, Transmitter, Amplifier, Audio Generator, Signal Tracer & Injector, Continuity Tester, Telegraph, Photoradio Receiver, Radio Receiver/Microphone Mixer, Illuminometer, Voltmeter, Ammeter, Sound Level Meter, Ohmmeter, Diode & Transistor Tester, Transparency Indicator Etc., Etc.

The above is just a selection of the circuits available—you can also design your own circuits with these superb new Denshi-Gakken "EX" construction kits.

No previous experience of electronics is required but you learn as you construct and have a great deal of fun too. The kits are completely safe for anyone to use.

Kits are complete with very extensive construction manuals PLUS Hamlyn's "All-Colour" 160 page book "Electronics" (free of charge whilst stocks last).

**ALL KITS ARE FULLY GUARANTEED.** Add-on sets (to increase the scope of each kit) are available, plus spares and accessories as required.  
 150 PROJECT KIT £39.75 60 PROJECT KIT £25.75  
 120 PROJECT KIT £33.75 30 PROJECT KIT £18.95  
 100 PROJECT KIT £29.25 15 PROJECT KIT £16.75

Prices include educational manuals, free book, VAT, p & p (in the U.K.). Free Introduction to the British Amateur Electronic Club. Free list of low price electronic books.

Callers at 20 Bride Lane will be very welcome. Trade and Educational enquiries invited.

Cheque/P.O./Barclaycard/Access No. (or 14p for illustrated literature) to DEPT. EE.

**SEE US AT BREADBOARD**  
 BINGLEY HALL, BIRMINGHAM, 23rd-26th MAY 1979

**ELECTRONI-KIT LTD.**  
 20 BRIDE LANE, LUDGATE CIRCUS,  
 LONDON EC4Y 8DX (01-353 6430)

MINIATURE VARIABLE CAPACITORS 25+25+25pf @ 75p.  
 SUB-MINIATURE TANTALUM CAPACITORS 4-7uf 10v.w. @ 6 for 25p.  
 TRANSISTORS BC 548 or BC 549 at 10p, 6 for 50p.  
 DAU TRIMMERS 2 to 9pf @ 10p, 8 to 45pf @ 10p, 0 to 125pf @ 12p, 8 to 140pf @ 15p.  
 POSTAGE STAMP TRIMMERS 10pf @ 10p, 30pf @ 10p, 1000pf @ 10p.  
 VERNITRON FM 4 10-7 MHz FILTERS @ 50p, 3 for £1.  
 50 AC 128 TRANSISTORS Branded but untested @ 57p.  
 1uf 25v.w. ELECTROLYTICS @ 6 for 25p.  
 10 AMP S.C.R.'s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.  
 MULLARD SOLID DIELECTRIC VARIABLE CAPACITORS 195+80pf @ 40p.  
 COIL FORMERS 1/2" dia. with core @ 6 for 25p.  
 McMURDO 8 PIN PLUGS @ 20p, 8 PIN SOCKETS @ 20p, COVERS @ 15p.  
 20 PHOTO TRANSISTORS AND DARLINGTONS Assorted untested @ £1.  
 ELECTRET MICROPHONE INSERTS with FET PRE-AMP @ £1.85.  
 10 ASSORTED PUSH BUTTON BANKS less knobs for £1.30.  
 200 RESISTORS Assorted 1/4, 1/2 watt for 75p.  
 PLASTIC TRIAC 400 PIV 8 Amp @ 60p each.  
 UNIJUNCTION TRANSISTORS 2N 4871 @ 22p, 2N 8028 @ 25p, 2N 6028 @ 25p, MEU 21 @ 22p, MU 4884 @ 22p, 4J2E28 @ 22p, T15 43 Type @ 20p.  
 VARIABLE CAPACITORS Direct Drive 5pf @ 75p, 10pf @ 75p, 15pf @ 75p, 30pf @ 85p, 125+125pf @ 55p, 100+200pf @ 55p, 200+200+25+25pf @ 55p. With S.M. Drive. 500+500+25+25pf @ 55p, 250+250+20+20+20pf @ 75p, 365+365+365pf @ 65p.  
 MINIATURE ROTARY SWITCHES 2 Pole 4 way @ 20p, 1 Pole 10 way 2 Bank @ 40p, 3 Pole 3 way @ 40p.  
 LM 380 AUDIO I.C. with circuits @ 80p.  
 50 ASSORTED 2 WATT ZENER Untested @ 57p.  
 50 VARI-CAP DIODES LIKE BA 102 Untested @ 57p.  
 TANTALUM CAPACITORS 1uf 35v.w., 33uf 35v.w., 1uf 35v.w., 2-2uf 35v.w., 4-7uf 35v.w., 8-8uf 35v.w., 10uf 25v.w., 22uf 16v.w., 33uf 25v.w., 47uf 6v.w. All at 9p each.  
 MAINS TRANSFORMERS 240 volt Input. Type 1. 24 volt Tapped at 14 volt 1 amp @ £1.30 (P&P 25p). Type 2. 22-0-22 volt 500mA @ £1.80 (P&P 25p). Type 3. 45 volt 6 amp @ £4.50 (P&P 95p).  
 600 MHz FREQUENCY 8 DIGIT COUNTER @ £115.  
 1N 4148 SILICON DIODES 10 for 40p.  
 DIE-CAST ALLOY BOXES Size 6" x 3-1/2" x 2" @ £1.15.  
 800 MHz T PACK NPN TRANSISTORS BF 362 @ 25p each.  
 ELECTROLYTIC CAPACITORS Screw Terminals. 680uf 160v.w. @ 20p, 3,300uf 63v.w. @ 50p, 15,000uf 40v.w. @ 75p, 33,000uf 16v.w. @ 75p, 47,000uf 10v.w. @ 75p, Tag Ended Types. 500uf 70v.w. @ 15p, 500uf 100v.w. @ 15p, 1000uf 100v.w. @ 50p, 3000uf 25v.w. @ 50p, 4700uf 25v.w. @ 50p.  
 50 BC 107-8-9 TRANSISTORS Untested @ 57p.  
 HC 5U CRYSTALS 40MHz, 44-3MHz, 45-9MHz, 46-5MHz, 46-7MHz, 48-3MHz, 50-1MHz. All at 50p each.  
 3 PIN PLUG AND SOCKET like R.S. European type with 2 metres of Cable @ 75p pair.  
 Please add 20p for post and packing on U.K. orders under £2. Overseas postage at cost.

**J. BIRKETT**

**RADIO COMPONENT SUPPLIERS**

25 The Strait, Lincoln LN2 1JF Tel. 20767

**ACE**

## TOPS THE PACK!

COMPONENTS - Now over 1,000 types in stock.  
 KITS - See the new range of low-cost 'ELEKITS'.  
 MODULES - New ready-built functions.  
 SERVICE - 1st Class same day despatch.  
 QUALITY - All guaranteed products.  
 PRICES - Many reductions!  
 MAGAZINE PROJECTS - Trouble-free!

ACE MAILTRONIX LTD  
 Dept. EE, Tontal Street  
 Wakefield, W. Yorkshire WF1 5UR

Our 2nd edition illustrated catalogue is now available. The much increased range shows many welcome price reductions.

**FABULOUS**  
 HOURS OF PLEASURE  
**'ELEKITS'**  
 EASY BUILD INTRODUCTION  
 TO ELECTRONICS

The new range of easy build kits complete with simple to follow instructions. Battery powered (not supplied). With case.

- \* BURGLAR ALARM \* ROULETTE
- \* BICYCLE SOUND FLASHER
- \* MINI ORGAN \* SIREN
- \* BLINKER \* TIME SWITCH

Many others in preparation - included in full ACE catalogue - send S.A.E. for free brochure of kit range.



I enclose 30p\*, please send catalogue.

Name \_\_\_\_\_  
 Address \_\_\_\_\_

\* Refundable with future orders over £5.00.

# LOOK!

## Here's how you master electronics.

... the **practical** way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

### 1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

### 2. Read, draw and understand circuit diagrams.


In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

### 3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.
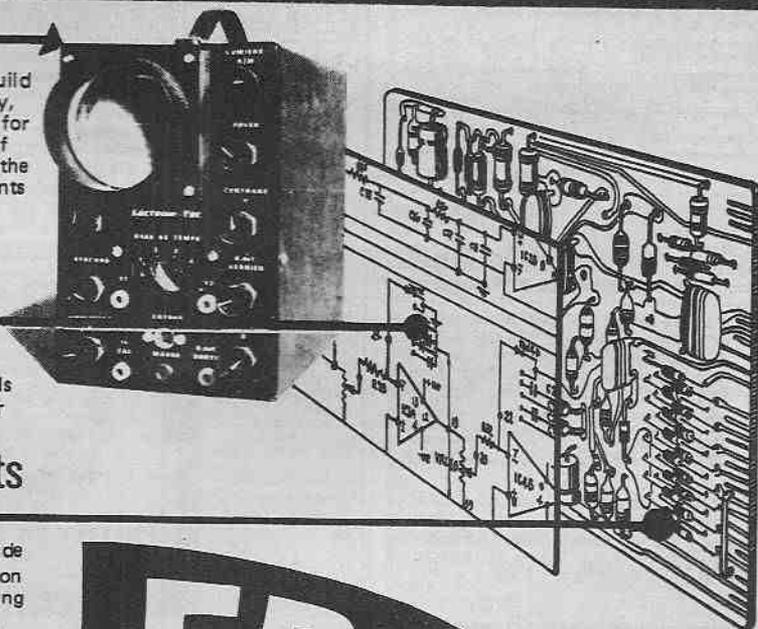
### 4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



# FREE

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**


P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

EEB4

Block caps please

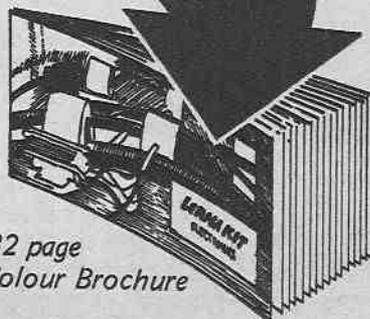

32 page  
Colour Brochure



# SMALL ADS

The prepaid rate for classified advertisements is 16 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £4.40 per single column centimetre. All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

## CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

### For Sale

100 I.C.'s (reject). Only 99p inc. post. All orders to: Michael Jones, 26 Whitchurch Avenue, Broadstone, Dorset.

NEW BACK ISSUES of "EVERYDAY ELECTRONICS". Available 60p each Post Free, open PO/Cheque returned if not in stock. BELL'S TELEVISION SERVICES 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

### Receivers and Components

DISCOVER ELECTRONICS. Build forty easy projects including: Metal Detector; Wireless Transmitter; Breathalyser; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms; etc. Circuits, plans all for £1.29 including FREE circuit board. Mail only. RIDLEY PHOTO/ELECTRONICS, Box 62, 111 Rockspark Road, Uckfield, Sussex.

### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-25 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4-50 plus 25p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P.

LOTS MORE! Send 25p for lists.

Prices include VAT.

### BOFFIN PROJECTS

4 CUNLIFFE ROAD, STONELEIGH  
EWELL, SURREY. (E.E.)

ELECTRONIC COMPONENTS and E.E. project kits 1973-now. Catalogue SAE, plus 30p. Jadebond Ltd. Midsbridge Drift Ind. Est., Midsbridge, Shildon, Co. Durham. Tel: Shildon (038 884) 3845.

GUARANTEED ICs. 7400/10p 7447/55p  
7473/24p 74121/24p 4000/15p 4011/15p  
4017/15p 4027/32p 709/22p 741/22p 7805/60p  
NE555/25p. Many more! SAE full list CP  
ICs 22 Oakfield Road, Croydon, Surrey.

TIRRO's new mail order price list of electronic components now available on receipt of SAE. TIRRO Electronics, Grenfell Place, Maidenhead, Berks.

11b ASSORTED COMPONENTS £5.60. 3 1/2 lb £2.10. Small Audio Amplifiers. 3 Transistors equivalent to AC128, OC72, with circuit, 3 for £1. 300 small components, Transistors, Diodes £1.50. Wire ended Neon's, 20 for £1. Panel with 40 74 series ICs, £1.50. No postage. List 15p, Refundable insurance add 15p. J.W.B. RADIO, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

FULL SPEC COMPONENTS. Brand new no surplus. 9p for list. TERO, 109 Clitheroe Road, Sabden, Blackburn, Lancs.

PARCELS. Caps, Res, Trans, Diodes, items. Over 100 parts, £2.25. 200, £3.50. List s.a.e. Sole, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

### Miscellaneous

AERIAL BOOSTERS improve weak VHF radio and television reception, price £5. SAE for leaflets, Electronic Mailorder Ltd., Ramsbottom, Bury, Lancashire, BL0 9AG.

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Phone 51803. No lists, enquiries S.A.E.

SINGLES / HOLIDAYS / HOUSEPARTIES. Friendship introductions. Free details—Christian Friendship Fellowship, Dept. B94, Edenthorpe, Doncaster (SAE).

LABORATORY CONTENTS: test equipment, rocket assemblies, analysers, photographic, recorders, spares, furnace, tapes, etc. 0403 76236.

### NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### Service Sheets

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICE for service sheets of Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

### Tapes

SUPER SOUND OFFER. 9p stamp brings you our new list of stereo cassettes and C60 cassettes. A. W. & J. M. West, 56 Frankwell Drive, Coventry CV2 2FB (EE).

### Books and Publications

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £5.00, request free circuit diagram. Stamp brings details unique TV publications. Ausee, 76 Church Street, Larkhall, Lanarkshire.

### RADIO BOOK SERVICE

WORLD RADIO TV HANDBOOK 1979 Edition	£9-25
Radio Station Guide	£1-35
Long distance Television Reception for the Enthusiast	£1-35
Familiar Electronic Projects	£1-35
Electronic Projects for Beginners	£1-45
Mobile Discographic Handbook	£1-45
Radio Circuits using ICs	£1-45
Projects in Opto-Electronics	£1-45
How to make Walkie-Talkies	£1-45
Radio Antenna H'book for Long Distance Reception	£2-95
How to build your own Metal & Treasure Locator	£1-30
How to build Advanced Short Wave Receivers	£1-30
Solid State Short Wave Receivers for Beginners	£1-30

PRICES INCLUDE POSTAGE & PACKING... S.A.E. FOR FULL LIST  
4 GILCHESTER COURT, WICKHAM RD, BECKENHAM KE11 8RS-20W

### Record Accessories

STYL! for Hi-Fi, Music Centres. Ill list free for SAE. Also cartridges, leads, accessories. Details—Felstead Electronics (EE), Longley Lane, Gatley, Cheshire, Chas. SK8 4EE.

## THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4.  
Reg. Office, 22 Coningsby Gardens.

### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10-19	2-65	1-45	.75	.60
20-29	2-85	1-65	.90	.70
30-34	3-05	1-75	1-00	.75
35-40	3-40	1-95	1-15	.84
41-43	4-55	2-55	1-95	1-30
44-48	5-05	3-05	2-15	1-70
47	8-00	5-00	3-00	1-80
48	15-00	9-00	6-00	3-30

### SILVER PLATED COPPER WIRE

14 & 18	4-50	2-25	1-44	1-08
20 & 22	5-00	2-55	1-74	1-08
24 & 26	5-70	3-31	2-00	1-22
28 & 30	6-67	3-86	2-35	1-44

Prices include P & P and VAT.  
SAE brings list of copper & resistance wires.  
Dealer enquiries invited.

## RECHARGEABLE BATTERIES

### TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus catalogue. Write or call, Sandwell Plant Ltd, 2 Union Drive, Boldmers, Sutton Coldfield, West Midlands. 021-354 9764. Or see them at TLC, 32 Craven Street, Charing Cross, London WC3.

Please mention

# Everyday Electronics

when replying to advertisements

# You know it's easy with Heathkit.

## Electronics Courses

New series of courses on car electrical systems.  
 New series of courses on electronic equipment.  
 DC electronics.  
 AC electronics.  
 Semi-conductors.  
 Electronic circuits.  
 Digital techniques.  
 Microprocessors.

Heathkit self-instruction electronics courses are complete, low-cost learning systems. All you need is the will to learn and the Heathkit courses will teach you at your own pace.

It's easy because the courses are based on step-by-step programmed instructions, with audio records (or optional cassettes), self evaluation quizzes to test your understanding, and interesting experiments that encourage you to learn the easy "hands-on" way with the optional Heathkit experimenter-trainers.

Thousands of people just like you have already learnt electronics the easy Heathkit way - at home, in educational establishments and in industry throughout the world.

You'll find it easy too. Full details are in the Heathkit catalogue, together with hundreds of kits you can build yourself, for the home, car and workshop.

Send for your copy now.



## New Kits

Line printer.  
 Dual floppy disc.  
 Dual trace 5MHz and 35MHz oscilloscopes.  
 Memory expansion for digital trainer.  
 2M hand-held transceiver.

To Heath (Gloucester) Limited, Dept \_\_\_\_\_, Bristol Road, Gloucester GL2 6EE. Please send the items I have ticked.  
 Heathkit catalogue (enclose 20p in stamps).  16 page computer brochure (enclose 20p in stamps).

Name \_\_\_\_\_

Address \_\_\_\_\_

HEATH  
Schlumberger

EE4/79

NB. If you are already on the Heathkit mailing list then you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon. Registered in England, number 606177.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester. (Gloucester 29451).

## Clef Kits



Designer approved quality kits for Electronic Musical Instrument Construction.

### JOANNA 72 & 88 PIANOS

Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia—a feature not available in any other design. A new physical layout has been adopted to simplify construction.

### P.E. STRING ENSEMBLE

The only kit available to the proven A. J. Boothman Design for this versatile String Machine.

Sent S.A.E. to:

Clef Products (Dept E.E.)  
 16 Mayfield Road, Bramhall, Cheshire SK7 1JU.

TIL200 Green Leds 25p	ABS Project Boxes & Lid	Miniature Push to Test Switch Red Button 18p
TIL200 red 15p, Clips 3p	Black 80 x 60 x 42 59p	Push to Break 25p
Large red/clear Leds 20p	Black 72 x 48 x 25 59p	Rocker Switch 10A 75p
BC107/8/9 12p, ORP12 75p	White 115 x 78 x 37 59p	Mercury Switch 75p
Texas 555 Timers 38p	B/W 120 x 100 x 45 88p	Small Reed Switch 10p
8Q Earphone & Plug 18p	Pots 10K, 1M, LIN 16p	Large Reed Switch 15p
Crystal Earphone 45p	Vero -1 Offcuts 75p	Changeover Type 35p
Trimphone Warbler Unit 85p	Vero Type-1 pins 1p ea	Slide Switch DPDT 18p
85p, Chrome Telescopic Aerial 6½" to 35½" 85p	Rubber Sucker or Feet 2p	Intercom Switch 35p
F.M. Room Aerial 85p	Croc Clips Red/Black 7p	Key Switch & Key £1.25
Electronic Timer Unit 240v A.C./6-12v D.C. 49p	Croc Jumper Leads 12p	Micro Switches Coin Operated 45p, DPDT 25p
Magnets 5p & 14p	GPO 4 Digit Counter 500 ohms 1½" x 4½" 42p	50 Ass'd Springs 45p
Large Circ. Magnets 16p	3 Digit Mec Counter 18p	30 Untested OA91 20p
Reed Relay 3-12v DC 40p	Loud Sirens 6 volt DC £1.40 ea, Buzzer Alarms 25	25 " " ICs 30p
Reed Bank 6 way 48p	1½ volt DC 75p, Buzzer 6/12v DC 2" dia. 99p	25 " " Transistors 30p
Electro Magnet Coil 4-12v DC 16p	Neon 90v, 10p, 240v 35p	50 Ass'd Resistors 35p
Tape Recorder Motor Reg 9v DC 1½" x 2" 75p	RF Chokes 9p, 240v AC	BABANI BOOKS
Enamelled Copper Wire 32, 34, 36, 38, 40 SWG 1p ft	Motors 250 rpm 55p	50 Led Circuits 75p
Resistors ¼W 5% 2p ea	8Q Speaker 2½" x 2½" 85p	50 Diode Circuits £1.10
	8Q " 4½" SW £1.85	50 SCR Circuits £1.10
		TTL or CMOS Data 55p

PRICES INCLUDE VAT

ADD 18p POSTAGE

## GRIMSBY ELECTRONICS

64 TENNYSON ROAD, CLEETHORPES, S. HUMBERSIDE  
 Callers to our Lambert Rd., Grimsby Shop, 100's of bargains—relays, cases, components etc., list 10p.  
 Open Tues., Wed., Fri., Sat., 10-3.30pm

## a digitizer adds another dimension

The Bit Pad computer digitizer converts graphic information into digital form for direct entry into a computer. By touching a pen like stylus or a cursor, to any position on a drawing, diagram, photograph, or other graphic presentation, the position co-ordinates are converted to digital equivalents.


- Bit Pad interfaces with almost any micro computer.
- Bit Pad consists of a 15" sq. digitizer tablet (11" sq. active area), a stylus, and a controller cabinet.
- Bit Pad costs only £450 (excluding VAT). Fill in the coupon and we will send you full information and details.

Terminal Display Systems Ltd., Hillside, Whitebirk Industrial Estate, Blackburn BB1 5SM, Lancs, England

Send to: Department CPED, Terminal Display Systems Ltd., Hillside, Whitebirk Industrial Estate Blackburn BB1 5SM, Lancs, England.

Name \_\_\_\_\_

Address \_\_\_\_\_

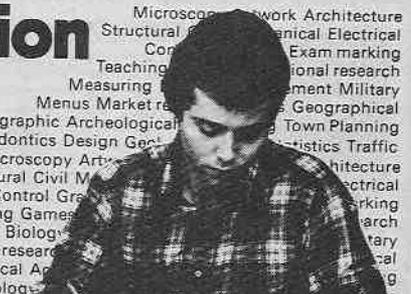

# TAMTRONIK LTD (DEPT EE)

217, Toll End Road, TIPTON, West Midlands DY4 0HW TEL: 021-557-9144

## Printed Circuit Boards & KITS for EE projects

Mag Issue	PROJECT	Ref	P.C.B.	KIT	KIT CONTENTS (see key)
1978 Jan	Audio Visual Metronome	E001	+ 65	5-50	B.E.H.L.
	Touch Switch	E002	+ 74	1-80	B.E.H.L.
	Rapid Diode Check	E004	+ 52	2-23	B.E.H.L.
Feb	Car Alarm	E005	+ 80	5-48	B.E.G.J.L.
	Lead Tester	E006	+ 80	4-17	B.E.H.L.
	Chaser Light Display	E007	+ 1-75	20-32	B.E.H.L.
	A.C. Meter Converter	E008	+ 60	5-37	B.E.H.L.
Mar	Audio Test (2 Pcb's)	E009	+1-74	14-96	B.F.G.J.
	C.R. Substitution Box	E010	+ 82	8-32	B.E.H.L.
	Catch-a-Light	E012	+ 62	5-29	B.E.H.L.
	Weird Sound	E013	+ 60	—	—
	Roof Rack Alarm	E014	+ 94	12-48	B.E.J.L.
Apr	Mains Delay Switch	E015	+ 80	3-48	B.E.H.L.
	Pocket Timer	E016	+ 75	11-09	B.E.H.L.
	Flash Meter	E017	+ 54	1-35	B.E.H.L.
May	Mains Tester	E018	+ 70	1-55	E.
	Teach In—Power Amp	E019	+ 70	5-71	B.E.H.L.
	Power Pack	E019	+ 70	5-71	B.E.H.L.
Jun	Tele-Bell	E020	+1-00	10-69	B.E.H.L.
	Inaite—Transistor Tester	E021	+ 65	5-10	B.E.G.H.L.
	Teach In—S.W. Receiver	E022	—	2-81	E.
	Power Slave	E023	—	1-75	—
Jul	Visual Continuity Tester	E024	—	4-09	E.H.L.
	Auto Night Light	E025	+ 85	0-39	B.E.G.H.L.
	Short Wave Radio	E026	+ 85	7-86	E.J.
	Quagmire	E027	+1-40	7-39	B.E.G.H.
Aug	Logic Probe	E028	+ 30	2-76	B.E.G.H.L.
	Sieve Flask	E029	+ 55	2-72	B.E.
	M.W. Mini Radio	E030	+ 85	12-41	B.E.J.L.
	Audio Freq. Signal Generator	E031	+ 85	12-41	B.E.J.L.
Sep	CHRONOSTOP	E032	+2-50	29-20	C.E.G.K.M.P.
	R.F. Signal Generator	E033	—	18-82	E.H.
	Sound to Light Unit	E034	—	8-14	B.E.H.L.
	Guitar Tone Booster	E035	75	4-06	B.E.H.L.
Oct	Car Battery State Indicator	E036	85	1-82	B.E.H.L.
	C.M.O.S. Radio	E037	+1-45	10-76	B.E.G.H.L.
	Fuse Checker	E038	—	1-80	B.E.H.L.
	Treasure Hunter	E039	1-25	15-95	B.E.G.H.L.
Nov	DOING-IT-DIGITALLY—TTL TEST BED	E040	—	20-65	N. (inc. add. comp.)
	DOING-IT-DIGITALLY—1st 6 PARTS	E041	—	3-65	—
	Audio Effects Oscillator	E042	—	2-40	E.H.L.
	Water Level Alert	E043	+ 70	3-98	B.E.G.J.L.
Dec	SUBSCRIBERS TELE-TELL METER	E044	+2-80	19-00	C.E.G.K.M.P.
	Components to add 3rd digit to kit E044	E044A	—	3-00	E.
	Combination Lock (2 x PCB's)	E045	+2-55	19-90	B.E.H.L.
	Hotline Game	E046	+ 75	4-87	B.E.H.
1979 Jan	Mini-Module—Passive Mixer	E047	—	2-47	B.E.H.
	Audible Flasher	E048	—	1-21	E.H.
	Fuze Box	E049	+ 75	5-20	B.E.H.L.
	Vehicle Immobiliser	E050	+ 1-00	4-86	B.E.H.L.
DEC	Mini-Module—Microphone Amp	E051	—	2-45	D.E.H.
	Mini Module—Continuity Tester	E052	+ 80	3-75	B.E.H.
	Lights Reminder	E053	+ 80	6-02	B.E.G.H.L.
	I'm First	E054	—	1-55	E.H.
TO	Roulette inc. colour printed wheel (2 x PCB's)	E055	+3-40	17-90	B.E.H.
	Headphone Enhancer	E056	—	2-06	E.H.L.
	EE 2020 Tuner Amp—Board A inc. RF unit	E057	3-85	54-44	B.E.G.H.
	EE 2020 Tuner Amp—Board B	E058	3-40	22-38	B.E.H.
FEB	EE 2020 Tuner Amp—Board C	E059	1-45	4-30	B.E.H.
	EE 2020 Tuner Amp—Board D	E060	2-20	18-53	B.E.H.
	EE 2020 Tuner Amp—Board E Hardware & wire	E061	1-40	22-29	B.E.G.H.
	EE 2020	E062	—	11-96	K.
	E063	10-50	123-00	B.E.G.K.	

+ P.c.b.'s designed by Tamtronik to EE circuit specifications

### KEY TO KIT CONTENTS

- A Vero-board(s)
- B Printed Circuit Board(s)
- C With screen printed component layout
- D Tag strip
- E ALL Resistors, potentiometers, capacitors, Semi-conductors
- F As E but with exclusions—Please ask for details
- G DIL and/or transistor sockets and/or soldercon pins
- H Hardware includes Switches, Knobs, Lamps & Holders, Fuses & Holders, Plugs & Sockets, Microphones, Transformers, Speakers, Meters, Relays, Terminal Blocks, Battery Connectors, etc. BUT excludes nuts, bolts, washers, connecting wire, Batteries and special miscellaneous items.
- J As H but with exclusions—Please ask for details
- K As H but including connecting wire
- L Suitable Case(s)
- M Suitable Case with Screen printed facia.
- N Full kit to magazine specified standards
- P Kit with professional finish incorporating all prime features including screen printed PCB and case where appropriate

### Doing-it-Digitally TTL ELECTRONIC TEST BED

Complete kit E040 £20.65  
 Components for first 6 parts E041 £3.60 (including additional components)  
**BOTH KITS (special price) £24.00**

### TELE-TEL

Nov. 78 Ref. E044  
 Subscribers phone call charge meter  
 A kit with a professional finish CASE with screen printed facia similar to magazine photograph but includes provision for 3rd digit.  
 An aluminium sub-facia panel is also provided with screen printed hole centres to allow access to preset potentiometers.  
 PCB designed to incorporate 3rd digit facility and is screen printed for ease of assembly.  
 Basic kit (2 digits) £19.90  
 (3 digits) £22.90

### BARGAIN CORNER

- 100 x 1/4w 1k carbon resistors 30p
- 10 x 1w 5% 1k5 resistors 16p
- 10 x 1w 5% 7k5 resistors 12p
- 10 x 1w 5% 100R resistors 12p
- 10 x 8w 5% 300R wirewound 50p
- 10 x 47u 10v Axial Elec. Caps 25p
- 4 x NE555 Timer £1.00
- Plug in mains PSU 3v/6v/9v/12v DC
- 300mA suitable for calculators & T.V. Games £2.99

### CHRONOSTOP

Aug. 78 Ref. E032  
 SPLIT 6 TAYLOR lap timing modes plus normal start/stop operation.  
 A kit with a professional finish including CASE with screen printed facia  
 PCB with screen printed component layout  
 Full Assembly Instructions  
**PRICE INC. VAT £29.20**

### SOLDERING IRONS & ACCESSORIES

- SRB 18 watt iron inc. No 20 Bit £3.78
- Stand £3.25
- Solder-Savbit 20 inch 52p
- Bit sizes No. 90 (1.5mm) 20 (3mm) 21 (4.5mm) 22 (6mm)
- Ideal for Home Constructor

Tamtronik Ltd. reserves the right to change kit content without notice, where necessary to incorporate current modifications or to make valid substitution for temporarily unavailable components. The majority of the kits we advertise can be supplied from stock or compiled at short notice from component stocks held, but when ordering you should be prepared to allow at least ten days, and up to one month, for us to complete your order. Upon receipt of your order, acknowledgement will be made by return post within 48 hours detailing our control number for that transaction. In case of any enquiry please quote this number.


Kits can be supplied excluding P.C.B.'s and/or case. Send SAE for details naming kit and kit reference and free catalogue.  
**TRADE & EDUCATIONAL ENQUIRIES WELCOME**  
 PRICES INCLUDE VAT  
**P & P 30p**

VISIT OUR SHOP AT Telephone or Letter  
 32 Market Place,  
 Great Bridge, Tipton,  
 West Midlands.  
  


### INDEX TO ADVERTISERS

Ace Mailtronix ... ..	252	E.D.A. ... ..	249	Newnes-Butterworth ... ..	247
Antex ... ..	Cover II	Electroni-Kit ... ..	252	Phonosonics ... ..	232
Bi-Pak... ..	231	Electrovalue ... ..	195	Radio Book Services ... ..	254
Birkett J. ... ..	252	George Sales, David Greenwell ... ..	244	Radio & TV Components ... ..	Cover III
B.N.R.E.S. ... ..	232, 253	Grimsby Electronics ... ..	255	Sandwell Plant ... ..	254
Boffin Projects ... ..	254	Harvelec ... ..	249	Science of Cambridge ... ..	237
Bull J. ... ..	251	Heath-Kit ... ..	255	Scientific Wire Co. ... ..	254
Charcroft Electronics ... ..	242	Home Radio ... ..	194	Scopex Book Co. ... ..	196
Chromatronics ... ..	244	ILP Electronics ... ..	199	Selray Book Co. ... ..	195
Clef Projects ... ..	255	Intertext (ICS) ... ..	196	Swanley Electronics ... ..	196
Collier McMillan (B.I.E.T.) ... ..	194	K. & A. Distributors ... ..	196	Tamtronik ... ..	256
Crescent Radio ... ..	249	Magenta Electronics ... ..	194	Terminal Display Systems ... ..	255
Crimson Elektrik ... ..	247	Maplin Electronic Supplies Ltd. ... ..	Cover iv	Timatron ... ..	198
Dewtron ... ..	250	Marshall A. ... ..	197	TUAC ... ..	195
		Metac ... ..	243	Watford Electronics ... ..	193
		Monolith Electronics Ltd. ... ..	250	West London ... ..	250

Published approximately the third Friday of each month by IPC Magazines Ltd., Kings Reach Tower, Stamford St., London SE1 9LS. Printed in England by Index Printers Ltd., Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/S) Ltd. South Africa—Central News Agency Ltd. Subscriptions: Inland £8.50, Overseas £9.50 per annum payable to IPC Services, Oakfield House, Ferry Mount Road, Haywards Heath, Sussex. Everyday Electronics is sold subject to the following conditions namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on cover, excluding where the selling price is subject to V.A.T., and that it shall not be lent, resold, or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

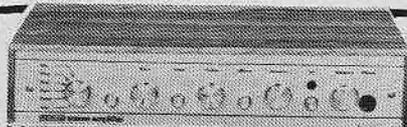

### 20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.

£29.90  
£2.50 p&p

#### SPECIAL OFFER

#### FOR PERSONAL SHOPPERS ONLY

FREE 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4.15 ohms speakers.

£29.00  
£2.50 p&p

#### SPECIAL OFFER

### 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3/4" approx. tweeters and crossovers.

£49.00  
£4.00 p&p

### BUILT AND READY TO PLAY

30x30 Viscount. Available fully built and tested

39.00  
£2.50 p&p

### EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround; 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95  
£3.40 p&p

### BSR P200

Belt drive chassis turntable unit semi automatic, cueing device.

£24.95  
£2.50 p&p

A.D.C. BLM 30 Mk III Magnetic Cartridge to suit.

£7.75



BSR Manual single play record deck with auto-return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use.

OUR PRICE £10.95  
£2.55 p&p

### GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£7.95  
£2.00 p&p

Size 12" x 8 1/2"

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type cells. Size 3 1/2" x 1 1/2" x 2" approx.

£7.50  
£1.50 p&p



### AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE WITH DECODER

Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vol On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW.

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz. (1.50mV/100K) deviation

FM signal Frequency Range (Audio) 50Hz to 17KHz within ± 1 dB

Radio FM sensitivity for 3dB below limiting better than 10 uV AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre

Size approx length 16" x height 2 1/2" x depth 4 1/2"

240 Vols AC Complete with tuning dial

Circuit diagram.

£19.95  
£2.25 p&p

# Mullard

## AUDIO MODULES IN BARGAIN PACKS

### CURRENT CATALOGUE

PRICE £25 AT OVER PER PACK

### SEE OUR PRICES

**1** PACK 1. 2 x LP1173 10w RMS output power audio amp modules; + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.

OUR PRICE £4.95  
p+p £1.00

**2** PACK 2. 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.

OUR PRICE £7.45  
p+p £1.00

### ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing capacitors.

£1.00 p+p £1.95

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE


p+p 50p 95p



### 10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.

p&p £2.05 £11.95

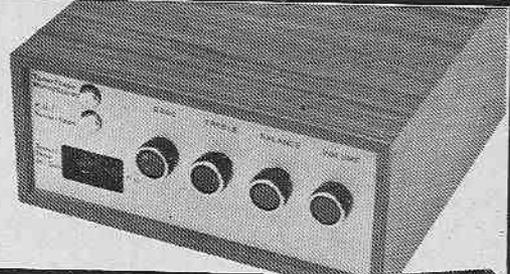

### BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish

£5.95

LCD 5 function men's digital watch stainless steel finish

£6.95

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish

£12.95

POCKET CALCULATOR. With LED display, memory and percentage key

£2.95

AM/FM DIGITAL CLOCK

RADIO Accurate 4 Digit

Electronic Clock with 1/2" LED

display. Buzzer and snooze timer.

£11.95



125 Watt Power Amp Module

£13.95

Mains power supply for above unit

£3.50

MULLARD Built power supply

£1.50

DECCA 20w Stereo speaker kit comprising

£20.00

2 8" approx. bass units + 2 3 1/2" approx.

tweeter inc. crossovers

VIDEOMASTER Super Score TV Game

£14.95

with pistol mains operation

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock

£41.95

LW, MW, SW, VHF mains/battery operation

VIDEOMASTER COLOUR

SHOT TV GAME

Choice of three games—Football, Tennis

and Squash. Ready to play—one or two

players. MAINS OPERATED.

OPPORTUNITY AT £9.95 ONLY



323 EDGWARE ROAD, LONDON W2  
21A HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers

ALL PRICES INCLUDE VAT AT 12 1/2%

All items subject to availability. Price correct at

and subject to change without notice.

30.1.79

### 50 WATT MONO DISCO AMP

£29.95

P&P £2.50

Size approx. 13 1/2" x 5 1/4" x 6 1/4"

50 watts rms. 100 watts peak output. Big features include two disc

inputs, both for ceramic cartridges, tape input and microphone input.

Level mixing controls fitted with integral push-pull switches. Independent

bass and treble controls and master volume.

SPECIAL OFFER. The above 50 watt amp plus 4 Goodmans Type 8P, 8"

speakers. Package price £45.00 + £4.00 P&P



### 70 & 100 WATT MONO DISCO AMP

£57

£65

Size approx. 14" x 4" x 10 1/4"

Brushed aluminium fascia and rotary controls.

Five vertical slide controls, master volume.

tape level, mic level, deck level, PLUS INTER DECK FADER

for perfect graduated change from record deck No. 1 to

No. 2, or vice versa. Pre fade level control

(PFL) lets YOU hear next disc before fading

it in. VU meter monitors output level.


Output 100 watts RMS 200 watts peak.



### DUO II SPEAKERS

Attractive teak finish, modern design, incorporating 2 speaker units—8" approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz impedance 8 ohms. Power 15 watts RMS. 20 watts max.

Per stereo pair  
£17.00  
£6.50 p&p

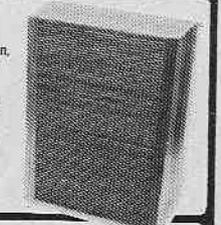

### FOR PERSONAL SHOPPERS ONLY

TANNOY 15" Lancaster corner cabinets, traditional design.

£20.95 each

NOTE DUE TO INDUSTRIAL UNREST, PLEASE ALLOW EXTRA TIME FOR YOUR ORDER TO REACH YOU.




Our catalogue even includes some popular car accessories at marvellous prices.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



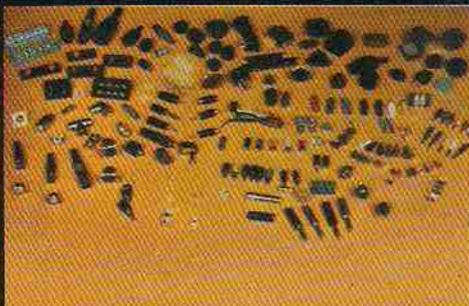Speakers from 1 1/2 inch to 15 inch; megaphone, P.A. horns, crossovers etc. They're all in our catalogue. Send the coupon now!



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.




61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 103 to 168 for details.



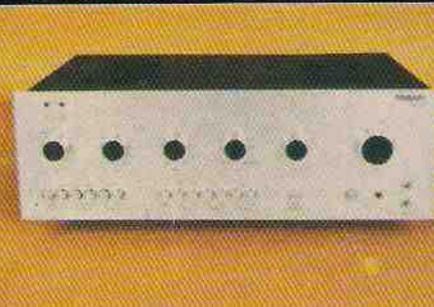A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.




These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

# MAPLIN

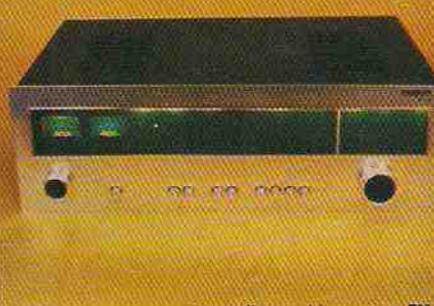**ELECTRONIC SUPPLIES LTD**

All mail to:-  
P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Telephone: Southend (0702) 554155.

Shop: 284 London Road,  
Westcliff-on-Sea, Essex.  
(Closed on Monday).  
Telephone: Southend (0702) 554155.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.** Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_