

Easy to build projects for everyone

**Everyday**

JUNE 79

45p

# ELECTRONICS


## ELECTRONIC CANARY




A NOVEL DOORBELL

LOW  
COST

## METAL LOCATOR

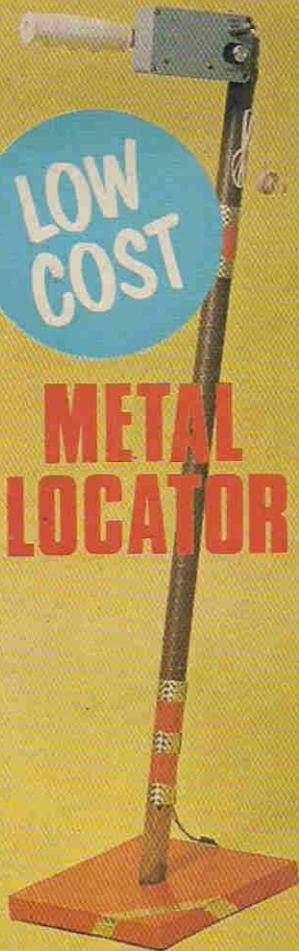

## TREMOLO UNIT

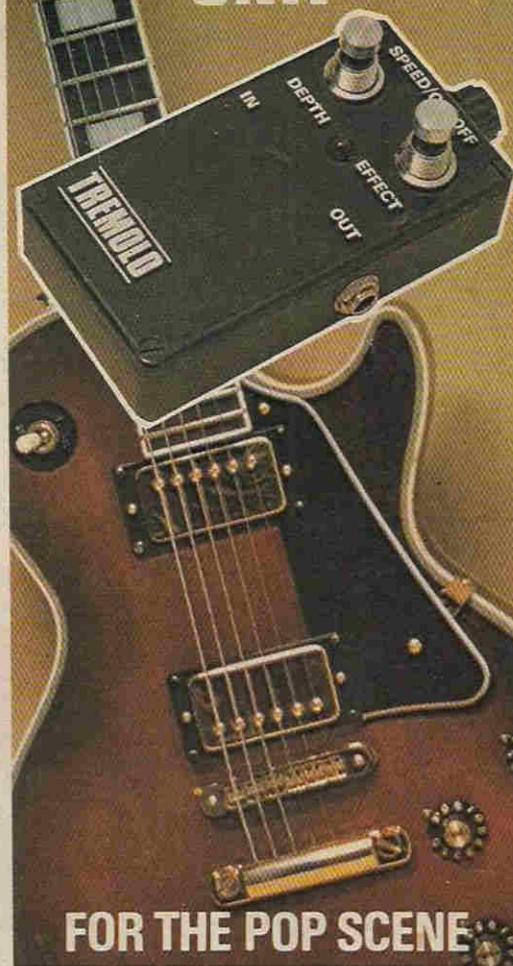

FOR THE POP SCENE



## METER AMPLIFIER

EXTEND THE RANGE OF YOUR MULTIMETER  
WITH THIS MONTHS MINI-MODULE

*Ideal for Measuring Small Audio Voltages*



# Micro\*-soldering!

*Antex TCSU1 & CTC  
... the perfect kit  
for miniature  
work*

\*CTC No. 71010  
Tip size: 0.5mm-02

Heat to any level between 145°-400° (with accuracy of 2%)



## Model CX - 17 watts



...a miniature iron with the elements enclosed first in a ceramic shaft, then in a stainless steel. Virtually leak-free. Only 7 1/2" long. Fitted with a 3/32" bit £4.37 inclusive of VAT and P.&P. Range of 5 other bits available from 1/8" down to 3/64".

## Model X25 - 25 watts



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at £4.37 inclusive of VAT and P.&P. Range of 4 other bits available.



## Model SK3 Kit

Contains both the model CX230 soldering iron and the stand ST3. Priced at £6.21 inclusive of VAT and P.&P. It makes an excellent present for the radio amateur, modelmaker or hobbyist.




## Model SK4 Kit

With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at £6.21 inclusive of VAT and P.&P.

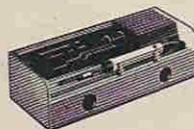
## Model SK1 Kit

This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet. 'How to solder'. Priced at £6.48 inclusive of VAT and P.&P.


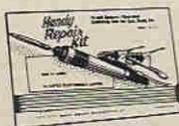
## Model MLX Kit

The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price £4.83 inclusive of VAT and P.&P.



Finger-tip accuracy combined with strict control of temperature set anywhere between 145 and 400°C.

Negligible leakage current. Earthed and protected by 'fail-safe' circuit. Operates at 24 volts.

TCSU1 station complete with soldering iron (XTC or CTC) £36. nett to industry plus VAT.

Our multi purpose range of soldering irons are all made in England and fully guaranteed. They are stocked by many wholesalers and retailers in the U.K. but if unobtainable locally we will supply direct.



Electronics Ltd.

Mayflower House, Armada Way, Plymouth, Devon Tel: 0752 67377/8 Telex: 45296

Please send the following .....

Please send the ANTEX colour brochure   
I enclose cheque/PO/Giro No. 258 1000

Name .....

Address .....

Antex Ltd. Freepost, Plymouth PL11BR Tel. 075267377

EE 6 79

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

**ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 30p\* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. Send 50p (plus 25p p&p) for our catalogue.**

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked \*. To the rest add 12 1/2%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am-6.00 pm. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type (Values are in  $\mu F$ )  
400V: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 11p;  
0.047, 0.068 14p; 0.10 17p; 0.15, 0.22 24p; 0.33, 0.47 41p; 0.68 48p.  
160V: 0.009, 0.15, 0.22, 11p; 0.33, 0.47 17p; 0.68, 1.0 22p; 1.5 29p; 2.2 32p; 4.7 48p.  
**DUBILIER:** 1000V: 0.01, 0.015 20p; 0.022 22p; 0.047 28p; 0.1 38p; 0.47 48p; 1.0 175p.

**POLYESTER RADIAL LEAD (Values in  $\mu F$ ) 250V:**  
0.01, 0.015, 0.022, 0.027 5p; 0.033, 0.047, 0.068, 0.1 7p; 0.15-12p;  
0.22, 0.33 13p; 0.47 17p; 0.68 19p; 1.0 24p; 1.5 30p; 2.2 34p.

**ELECTROLYTIC CAPACITORS:** Axial lead type (Values are in SF) 500V: 10 40p; 47 60p;  
250V: 100 65p; 63V 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22 8p; 47, 32, 50 15p; 63, 100 22p;  
50, 10, 100 22p; 47 32p; 1000 50p; 40V: 22, 33, 50p; 100 12p; 2200 60p; 3300 82p; 4700 85p;  
35V: 10, 33 7p; 330, 470 32p; 1000 48p; 25V: 10, 22, 47 8p; 80, 100, 160 8p; 220, 250 13p; 470, 540 20p;  
25p; 1000 27p; 1500 30p; 2200 45p; 3300 80p; 4700 85p; 16V: 10, 40, 47, 68 7p; 100, 125 8p; 220, 330 14p; 470 16p; 1000, 1500 20p; 2200 34p; 10V: 1.0 9p; 540 12p; 1000 14p.

**W.G. END TYPE:** 10V: 2000 80p; 4700 135p; 80V: 10,000 250p; 40V: 250 65p; 3300, 4700 70p;  
15,000 450p; 25V: 4700 2200 48p; 325V: 200-1000-50+100 190p; 32-32 175p.

**TANTALUM BEAD CAPACITORS:** 35V: 0.1 2p; 0.15 2.2p; 0.2 3p; 0.47 4p; 0.68 5p; 1.0 2.2uF, 3.3, 4.7, 6.8 25V:  
1.5, 10 20V; 1.5 16V; 10uF 13p each  
47, 100 40p; 10V: 22uF, 33 20p 6V:  
47, 68, 100 30p 3V: 68, 100uF 20p

**MYLAR FILM CAPACITORS**  
100V: 0.001, 0.002, 0.005, 0.01 1uF 5p  
0.015, 0.02, 0.04, 0.05, 0.055uF 7p  
0.1uF, 0.2 2p 50V: 0.47 12p

**MINIATURE TYPE TRIMMERS**  
2-5 80p, 3-10pF, 10-40pF 22p  
5-250pF, 5-450pF, 90pF, 80pF 30p

**COMPRESSION TRIMMERS**  
3-40pF, 10-30pF 30p; 25-190pF 33p  
100-500pF 85p; 1250pF 80p

**POLYSTYRENE CAPACITORS**  
10pF to 1nF 8p; 1.5nF to 10nF 10p.

**SILVER MICA (Values in pF) 3-3, 4-7, 6-10, 12-15, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 220 9p each  
250, 300, 330, 360, 220 9p each  
500, 820, 1000, 1800, 2000 16p each  
1000, 1200, 1800, 2000 20p each**

**CERAMIC TRIMMER CAPACITORS**  
2-7pF, 4-15pF, 6-25pF, 8-30pF 20p

**SOLDERCON PINS\***  
100 50p; 500 200p

JACK PLUGS		SOCKETS	
Screened chrome body	Plastic body	open metal	moulded with break contacts
2.5mm 15p	10p	8p	8p
3.5mm 15p	10p	13p	20p
MONO 25p	14p	15p	24p
STEREO 32p	18p		

DIN	Plugs	Sockets	In Line
2 PIN Loudspeaker	10p	6p	20p
3.5 Pin Audio	13p	10p	20p

CO-AXIAL	plastic	metal
	10p	12p
	15p	18p

PHONO	8p single	8p double
assorted colours	10p	15p
Metal Screened	15p	4-way 20p

BANANA	4mm	11p	12p
	2mm <td>10p</td> <td>10p</td>	10p	10p
	1mm <td>6p</td> <td>6p</td>	6p	6p
	3mm <td>6p</td> <td>6p</td>	6p	6p

JACKSONS VARIABLE CAPACITORS	Dielectric	0.2	3850pF with slow motion	140p
	Drive <td>5000F <td>165p <td>325p</td> </td></td>	5000F <td>165p <td>325p</td> </td>	165p <td>325p</td>	325p
	6.1 Ball Drive <td>4511/DAF <td>115p</td> <td>285p</td> </td>	4511/DAF <td>115p</td> <td>285p</td>	115p	285p
	Dial Drive 4103 <td>6/136 <td>1</td> <td>650p</td> </td>	6/136 <td>1</td> <td>650p</td>	1	650p
	Drum 54mm 30p <td>100, 150pF <td>215p</td> <td></td> </td>	100, 150pF <td>215p</td> <td></td>	215p	
	0.1-385pF 24p <td>"L" 3 x 310pF <td>485p</td> <td></td> </td>	"L" 3 x 310pF <td>485p</td> <td></td>	485p	
	0.2-385pF 27p <td>0.3 x 25pF <td>430p</td> <td></td> </td>	0.3 x 25pF <td>430p</td> <td></td>	430p	

DIODES	AA119	18	Range 2V7 to 1A50V	38
	AA129 <td>20 <td>39V 400mV <td>38 </td></td></td>	20 <td>39V 400mV <td>38 </td></td>	39V 400mV <td>38 </td>	38
	BA100	12	9p each	
	BY128	14	Range 3V3 to 33V, 1.3W	32
	BY127	14	17p each	
	CRO33*	148	5A100V 32	
	OA9	75	5A300V 35	
	OA47	10	25J 180	
	OA70	12	8A300V 48	
	OA79	15	15A500V 54	
	OA81	15	12A300V 52	
	OA85	14	1A/50V 20	12A500V 92
	OA90	7	1A/100V 22	BT108 150
	OA91	6	1A/200V 25	C106 38
	OA95	8	1A/400V 29	TIC44 25
	OA200	9	1A/600V 34	TIC45 45
	OA202	8	2A/50V 35	
	IN814	4	2A/100V 44	
	IN816	5	2A/200V 46	
	IN4004/2*	5	2A/400V 53	
	IN4004/5*	6	2A/600V 65	
	IN4006/7*	7	4A/100V 72	
	IN4148	4	4A/200V 75	
	IS44	20	4A/400V 79	
	3A100V*	15	4A/800V 105	
	3A400V*	15	4A/800V 120	
	3A600V*	20	6A/100V 120	
	3A1000V*	24	6A/200V 78	40569 120
	6A/600V 60			

ZENERS	AS129	18	Range 2V7 to 1A50V	38	
	AS126*	AS127*	9	BC107*	10
	BC107B*	10	BC108*	12	
	BC108B*	12	BC109*	12	
	BC109C*	12	BC110*	12	
	BC113	20	BC114	20	
	BC115	20	BC116	20	
	BC118	20	BC119	20	
	BC120	20	BC121	20	
	BC122	20	BC123	20	
	BC368	20	BC369	20	
	BC370				

# ELECTRONI-KIT

**"EDUCATIONAL KITS OF EXCEPTIONAL QUALITY"**

(AUDIO magazine)



**THIS IS A POWERFUL RADIO RECEIVER!**

The same kit is also 150 other different actual working projects e.g.:

Computer & Logic Circuits, Electronic Organ, Timer, Light Control, Agility Tester, Lie Detector, Siren, Horn, Buzzer, BIRD, Metronome, Cds cell light & sound control, Photogun, Light Oscillator, Light Switch, Light and Sound Morse Code, Field Strength Meter, Hygrometer, Sphygmometer, Etc., Etc.

Radio Receiver, Transmitter, Amplifier, Audio Generator, Signal Tracer & Injector, Continuity Tester, Telegraph, Photoradio Receiver, Radio Receiver/Microphone Mixer, Illuminometer, Voltmeter, Ammeter, Sound Level Meter, Ohmmeter, Diode & Transistor Tester, Transparency Indicator Etc., Etc.

The above is just a selection of the circuits available—you can also design your own circuits with these superb new Denshi-Gakken "EX" construction kits.

No previous experience of electronics is required but you learn as you construct and have a great deal of fun too. The kits are completely safe for anyone to use.

Kits are complete with very extensive construction manuals PLUS Hamlyn's "All-Colour" 160 page book "Electronics" (free of charge whilst stocks last).

**ALL KITS ARE FULLY GUARANTEED.** Add-on sets (to increase the scope of each kit) are available, plus spares and accessories as required.

150 PROJECT KIT **£39.75** 60 PROJECT KIT **£25.75**  
120 PROJECT KIT **£33.75** 30 PROJECT KIT **£18.95**  
100 PROJECT KIT **£29.25** 15 PROJECT KIT **£16.75**

Prices include educational manuals, free book, VAT, p & p (in the U.K.). Free introduction to the British Amateur Electronics Club. Free list of low price electronics books.

Callers at 20 Bride Lane will be very welcome. Trade and Educational enquiries invited.

Cheque/P.O./Barclaycard/Access No. (or 14p for illustrated literature) to DEPT. EE.

See us at

**THE GREAT BRITISH ELECTRONICS BAZAAR,**  
Alexandra Palace, London, 28-30 June.

**ELECTRONI-KIT LTD.**

20 BRIDE LANE, LUDGATE CIRCUS,  
LONDON EC4Y 8DX (01-353 6430)

**VARIABLE CAPACITORS** Direct Drive, 5pf @ 75p, 10pf @ 75p, 25+25+25pf @ 75p, 125+125pf @ 55p, 100+200pf @ 55p, 200+200+25+25pf @ 85p. With slow Motion Drive 500+500+25+25pf @ 55p, 250+250+20+20+20pf @ 75p, 365+365+385pf @ 85p.

**ROTARY SWITCHES** 3p. 3 way @ 40p, 2P 4 way @ 20p, 1 Pole 10 way 2 Bank @ 40p, 1 Pole 24 way 2 Bank @ £1.

**ELECTROLYTICS** 1500uf 63v.w. @ 40p each.

**AUDIO I.C.'s** SN 76001N @ 60p, TBA 800 @ 85p, TBA 810 @ £1, TBA 820 @ 55p, TCA 940 @ £1, LM 380 @ 80p.

**UNMARKED GOOD 400mW ZENERS** 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 38volt. All at 10 for 40p.

**TRANSISTORS** BC 548, BC 549, BC 107, BC 108, BC 109, BC 177 All at 10p, 6 for 50p.

**TANTALUM BEAD CAPACITORS** 4.7uf 16v.w., @ 9p, 10uf 10v.w. @ 9p, 33uf 10v.w., @ 9p, 100uf 10v.w., @ 25p.

**50. OC 71 TRANSISTORS** untested for 75p.

**HFC 600 HIGH FREQUENCY COUNTER** 1 Hz to 600 MHz 240 volt input. S.A.E. for leaflet price £115.

**3/16" COIL FORMERS** with core at 6 for 25p.

**STUD MOUNTING DIODES** 100 PIV 10 amp @ 15p, 100 PIV 20 amp @ 25p.

**1 AMP TRIACS** 400 PIV at 35p each.

**LED'S** -2" Red @ 15p, Green @ 18p, TIL 209 @ 15p.

**MES LAMPS** 6.3 volt -3 amp @ 10p, 6.3 volt 40mA @ 10p.

**50 AC 128 TRANSISTORS** Branded but untested @ 57p.

**50 BC 107-8-9 TRANSISTORS** Assorted untested @ 57p.

**50 VARI-CAP DIODES LIKE BA 102** untested @ 57p.

**200 RESISTORS** 1/2, 1 watt assorted for 75p.

**VERNITRON FM 4 FILTERS** at 50p each, 3 for £1.

1uf 25v.w. **ELECTROLYTICS** at 6 for 25p.

**ERIE RED CAP MINIATURE** .01uf 100v.w. CAPACITORS @ 5p each.

**DAU TRIMMERS** 2 to 9pf @ 15p, 7 to 35pf @ 15p, 6 to 45pf @ 15p, 8 to 125pf @ 15p, 8 to 140pf @ 15p.

**100 ASSORTED C280 CAPACITORS** for 57p.

**DUAL GATE MOS FET LIKE 40673** @ 33p, 4 for £1.10.

**FERRITE BEADS FX 1115** at 12 for 15p.

**THYRISTORS** 10 amp Type. 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.

**SAW 62 HIGH SPEED SILICON DIODES** 12 for 35p.

**BOOKS** By Geo. Dobbs. "Practical Test Equipment" @ 74p, "Simple Short Wave Receiver" @ 60p, "Practical Electronic Projects" @ 75p, The three for £1.60.

**50 ASSORTED 2 WATT ZENERS** untested @ 57p.

**R.F. TRANSISTORS** AF 239 @ 50p, 2N 5179 @ 50p, BF 362 @ 25p, BFY 90 @ 50p, MFS 6514 @ 10p, BF 177 @ 15p, 2N 5180 @ 50p.

**MAINS TRANSFORMERS** 240 volt input, Type 1. 24 volt tapped at 14 volt 1 amp @ £1.30 (P&P 25p), Type 2. 30-0-30 volt 500mA @ £1.30 (P&P 25p), Type 3. 45 volt 6 amp @ £4.50 (P&P 95p), Type 6. 16 volt 2 amp @ £1.60 (P&P 25p).

Please add 20p for post and packing on U.K. orders under £2, unless otherwise stated. Overseas postage at cost.

**J. BIRKETT**

**RADIO COMPONENT SUPPLIERS**

25 The Strait, Lincoln LN2 1JF Tel. 20767

## TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

**City and Guilds Certificates:**  
Telecommunications Technicians  
Radio, TV, Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
MPT Radio Communications Certificate

**Diploma Courses:**  
Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV, Audio Engineering and Servicing  
Electrical Engineering, Installation  
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

**ICS** To: International Correspondence  
Schools

Dept J268 Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest .....

Name .....

Address .....

Tel: ..... Age: .....

# STEVENSON

## Electronic Components

### REGULATORS

78L05 30p	7805 60p	79L05 70p	7912 80p
78L12 30p	7812 60p	79L12 70p	7915 80p
78L15 30p	7815 60p	7905 80p	LM723 35p

### HARDWARE


#### MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.

Available with secondaries of:

6-0-6	9-0-9	and
12-0-12		92p. each.

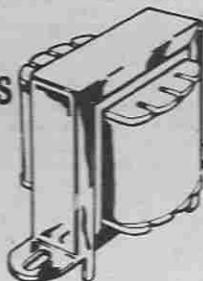

### LOUDSPEAKERS

56mm dia. 8 ohms	70p
64mm dia. 8 ohms	75p
64mm dia. 64 ohms	75p
70mm dia. 8 ohms	100p
70mm dia. 80 ohms	110p



### TERMINALS

Rated at 10A. Accepts 4mm plug, black, blue, green, brown and red . . . 22p

### SWITCHES

Subminiature toggle. Rated at 3A 250V.

SPDT 70p	SPDT centre off 75p
DPDT 80p	DPDT centre off 95p

Standard toggle

SPST 34p	DPDT 48p
----------	----------

Wavechange switches.

1P12W, 2P6W, 3P4W or 4P3W all 43p ea.

Miniature switches (non-locking)

Push to make 15p Push to break 20p

Slide switches (DPDT)

Miniature 14p Standard 15p



### CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p




WHY NOT VISIT OUR
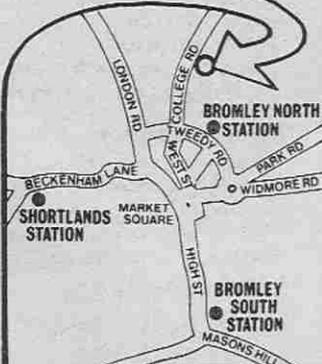
## NEW SHOP

We welcome callers at our new premises at the address below (5 mins. from High St.). We are open Mon - Sat, 9am - 6pm. Special offers available.

Express telephone order service. Orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Tel: 01-464 2951/5770.



**ORDERS  
DESPATCHED  
BY RETURN  
POST**

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.

BARCLAYCARD & ACCESS WELCOME.



Mail orders to: STEVENSON (Dept EE)

### TRANSISTORS

AC127 17p	BCY71 14p	ZTX109 14p
AC128 16p	BCY72 14p	ZTX300 16p
AC176 18p	BD131 35p	2N697 12p
AD161 38p	BD132 35p	3N1302 38p
AD162 38p	BD135 38p	2N2905 22p
BC107 8p	BD139 35p	2N3055 50p
BC108 8p	BD140 35p	2N3442 135p
BC109 8p	BF2448 36p	2N3702 8p
BC147 7p	BFY50 15p	2N3704 8p
BC148 7p	BFY51 15p	2N3705 9p
BC149 8p	BFY52 15p	2N3708 8p
BC148 9p	MJ2955 98p	2N3819 22p
BC177 14p	MPSA06 20p	2N3904 8p
BC178 14p	MPSA56 20p	2N3905 8p
BC179 14p	TIP29C 60p	2N3906 8p
BC182 10p	TIP30C 70p	2N4058 12p
BC182L 10p	TIP31C 65p	2N5457 32p
BC184 10p	TIP32C 80p	2N5458 30p
BC184L 10p	ZTX107 14p	2N5459 32p
BC212 10p	ZTX108 14p	2N5777 50p
BC212L 10p		
BC214 10p		
BC214L 10p		
BC477 19p		
BC478 19p		
BC479 19p		
BC548 10p		
BCY70 14p		

### DIODES

1N914 3p	1N5401 13p
1N4001 4p	BZY88ser. 8p
Full spec. product.	
1N4148 £1.40/100. £11/1000	

### LINEAR

CA3140 38p	NE555 21p
LM301AN 26p	NE566 50p
LM318N 85p	NE565 85p
LM324 45p	NE567 170p
LM339 45p	SN76003 200p
709 28p	SN76013 140p
741 16p	SN76023 140p
747 40p	SN76033 200p
748 30p	SN76477 220p
CA3046 55p	LM3909 65p
CA3080 70p	MC1496 60p
CA3130 90p	MC1458 32p
	ZN414 75p

### CAPACITORS

#### TANTALUM BEAD

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	each
4.7, 6.8, 10uF @ 25V	8p
22 @ 16V, 47 @ 6V, 100 @ 3V	13p
	16p

#### MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047	3p
0.068, 0.1	4p

#### POLYESTER

Mullard C280 series	
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

#### CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF

#### RADIAL LEAD ELECTROLYTIC

63V 0.47 1.0 2.2 4.7 10	5p
	7p
	13p
100	20p
	220
	20p
25V 10 22 33 47	5p
	8p
	10p
	220
	470
	15p
1000	23p

### CONNECTORS

#### JACK PLUGS AND SOCKETS

2.5mm	screened	unscreened	socket
	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

#### DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

#### 1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

#### 4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each


#### PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p Double socket 10p

### VERO

Size in.	0.1in.	0.15in.	Veropins
2.5 x 1	14p	13p	single sided
2.5 x 3.75	42p	40p	per 100
2.5 x 5	52p	50p	0.1in 35p
3.75 x 5	60p	60p	0.15in 40p
3.75 x 17	195p	180p	

### BOXES

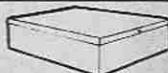

Aluminium boxes with lid and screws

	Length	width	height	
AL1	3	2	1	48p
AL2	4	3	1 1/2	58p
AL3	4	3	2	65p
AL4	6	4	2	70p
AL5	6	4	3	85p
AL6	8	6	2	116p

### THYRISTORS

	4A	8A	12A
100V	36p	45p	62p
200V	42p	53p	68p
400V	51p	66p	86p

### TRIACS

Plastic cased Triacs. Texas. All rated at 400V.

4A 70p	12A 90p	20A 185p
8A 80p	16A 95p	25A 215p

### CMOS

4001 12p	4026 90p	4069 12p
4002 12p	4027 30p	4071 12p
4007 12p	4028 48p	4081 13p
4011 12p	4029 50p	4093 45p
4013 28p	4040 60p	4510 65p
4015 50p	4042 50p	4511 65p
4016 30p	4046 90p	4518 65p
4017 48p	4049 25p	4520 60p

FULL DETAILS IN CATALOGUE!

### SKTS

Low profile by Texas



8 pin	8p	16 pin	11p	28 pin	22p
14 pin	10p	24 pin	18p	40 pin	32p

Soldercon pins: 100-50p. 1000-370p

### OPTO

LED's	0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p	8p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		

### DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

### RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:	
0.25W	each 100+ 1000+
0.5W	1p 0.9p 0.8p
	1.5p 1.2p 1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W E7.50. 0.25W E5.70.

#### METAL FILM RESISTORS

Very high stability, low noise rated at 1/4W 1%. Available from 51ohms to 330k in E24 series. Any mix.

0.25W	each 100+ 1000+
	4p 3.5p 3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 64 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.



# 76 College Road, Bromley, Kent, England

## ELECTRONIC BOOKS

Ref. No.	Title	Price
126	Boys Book of Crystal Sets	25p
138	How to Make Aerials for TV (Band 1—2—3)	25p
160	Coil Design and Construction Manual	75p
196	AF—RF Reactance—Frequency Chart for Constructors	15p
200	Handbook of Practical Electronic Musical Novelties	50p
201	Practical Transistorised Novelties for Hi-Fi Enthusiasts	35p
202	Handbook of Integrated Circuits (IC's) Equivalents and Substitutes	1.00p
203	IC's and Transistor Gadgets Construction Handbook	60p
205	First Book on Hi-Fi Loudspeaker Enclosures	75p
206	Practical Transistor Circuits for Modern Test Equipment	60p
207	Practical Electronic Science Projects	75p
208	Practical Stereo and Quadrophony Handbook	75p
210	The Complete Car Radio Manual	1.00p
211	First Book of Diode Characteristics Equivalents and Substitutes	95p
213	Electronic Circuits for Model Railways (Reprinting)	1.00p
214	Audio Enthusiasts Handbook	85p
215	Shortwave Circuits and Gear for Experimenters and Radio Hams	85p
216	Electronic Gadgets and Games	1.00p
217	Solid State Power Supply Handbook	85p
218	Build Your Own Electronic Experimenters Laboratory	85p
219	Solid State Novelty Projects	85p
220	Build Your Own Solid State Hi-Fi and Audio Accessories	85p
221	28 Tested Transistor Projects	95p
222	Solid State Short Wave Receivers for Beginners	95p
223	50 Projects Using IC CA 3130	95p
224	50 CMOS IC Projects	95p
225	A Practical Introduction to Digital IC's	95p
226	How to Build Advanced Short Wave Receivers	1.20p
227	Beginners Guide to Building Electronic Projects	1.25p
228	Essential Theory for the Electronics Hobbyist	1.25p
RCC	Resistor Colour Code Disc Calculator	10p
BP1	First Book of Transistor Equivalents and Substitutes	50p
BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60p
BP6	Engineers and Machinists Reference Tables	50p
BP7	Radio and Electronic Colour Codes and Data Chart (Reprinting)	25p
BP11	Practical Transistor Novelty Circuits	40p
BP14	Second Book of Transistor Equivalents and Substitutes	1.10p
BP22	79 Electronic Novelty Circuits	75p
BP23	First Book of Practical Electronic Projects	75p
BP24	52 Projects Using IC741	95p
BP25	How to Build Your Own Electronic and Quartz Controlled Watches & Clocks	85p
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p
BP28	Resistor Selection Handbook (International Edition)	60p
BP29	Major Solid State Audio Hi-Fi Construction Projects	85p
BP30	Two Transistor Electronic Projects	85p
BP31	Practical Electrical Re-Wiring and Repairs	85p
BP32	How to Build Your Own Metal and Treasure Locators	1.00p
BP33	Electronic Calculator Users Handbook	95p
BP34	Practical Repair and Renovation of Colour TVs (Reprinting)	95p
BP35	Handbook of IC Audio Preamplifier and Power Amplifier Construction (Reprinting)	95p
BP36	50 Circuits Using Germanium Silicon and Zener Diodes	75p
BP37	50 Projects Using Relays, SCR's and TRIACS	1.10p
BP38	Fun and Games with your Electronic Calculator	75p
BP39	50 (FET) Field Effect Transistor Projects	1.25p
BP40	Digital IC Equivalents and Pin Connections	2.50p
BP41	Linear IC Equivalents and Pin Connections	2.75p
BP42	50 Simple L.E.D. Circuits	75p
BP43	How to Make Walkie-Talkies	1.25p
BP44	IC555 Projects	1.45p
BP45	Project in Opto-Electronics	1.25p
BP46	Radio Circuits Using IC's	1.35p
BP47	Mobile Discotheque Handbook	1.35p
BP48	Electronic Projects for Beginners	1.35p
BP49	Popular Electronic Projects	1.45p
BP50	IC LM3900 Projects	1.35p
BP51	Electronic Music and Creative Tape Recording	1.25p
BP52	Long Distance Television Reception (TV-DX) For The Enthusiast	1.45p
BP53	Practical Electronic Calculations and Formulae	2.25p
BP54	Your Electronic Calculator and Your Money	1.35p
BP55	Radio Stations Guide	1.45p

Please add 20p p. & p. per book  
Send SAE for our large range of Components

## TECHNOMATIC LTD


17 BURNLEY ROAD, LONDON NW10 1ED  
(2 minutes from Dollis Hill Tube station)

(Ample parking space)

Telephone: 01-452 1500  
Telex: 922800

vero

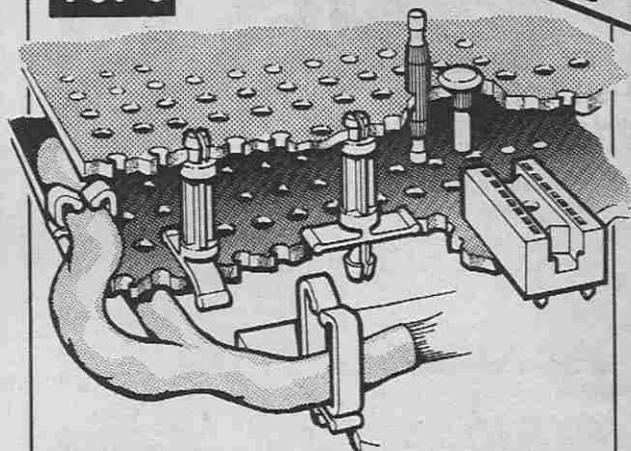OUR RANGE OF  
PRODUCTS ARE NOW INDIVIDUALLY  
AND ATTRACTIVELY PACKAGED



Our new catalogue lists circuit board accessories for all your projects — DIP sockets, pins, stand-offs, cable clips, hand tools. And we've got circuit boards, module systems, cases and boxes — everything you need to give your equipment the quality you demand. Send 25p to cover postage and packing, and the catalogue's yours.



**VERO ELECTRONICS LTD. RETAIL DEPT.**  
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR  
Telephone Chandlers Ford (04215) 2956

## Random Electronic

# EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box and descriptive instructions.

Complete  
or  
Kit

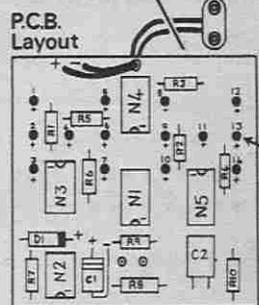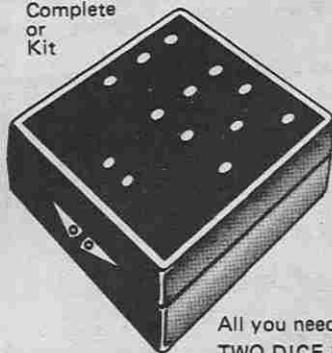

All you need is a soldering iron (14 LEDs)  
TWO DICE FACES TOUCH CONTROL...

- a \*Self Assemble Kit £3.95
- b \*Ready built 'Roll Out Dice' £5.25 (INCL. P+P)
- c \*Ready built 'Easy Dice' £4.75

Order now from: Menorcrest Electronics Ltd  
1 Hatton Court Ipswich Suffolk 0473-210151

Amount enclosed £

Name

Address

please state amount required in appropriate box  a  b  c


# BUILD TWO FREE PROJECTS ON CSC

ELECTRONICS BY NUMBERS  
FREE PROJECTS  
NO 1 & NO 2

## ELECTRONICS BY NUMBERS FISH'N'CLIKS

Now using **EXPERIMENTOR BREADBOARDS** and following the instructions in "Electronics by Numbers" ANYBODY can build electronic projects. Look at the diagram, this has the same letter/number system as all EXP. BOARDS. Look at the "YOU WILL NEED" list and select Q1 this is PNP transistor type HEP-230. This plugs into hole X9, A7 and C9. NOW take C1, a 50 uF capacitor, and put into holes J6 and J14 and do the same with all the components.

### NOW YOU HAVE FISH'N'CLIKS

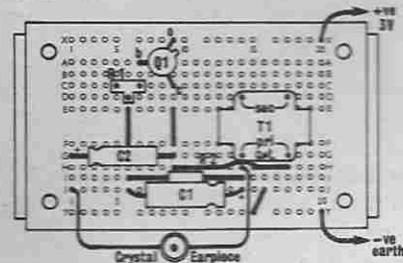

### YOU WILL NEED

- B1, B2 - 2x1.5V AAA batteries
- C1, C2 - 50 uF, 12-VDC electrolytic capacitor
- E1 - Crystal earphone
- Q1 - Motorola HEP-230 pnp transistor
- R1 - 5000-ohm pot
- R2 - 27000-ohm, 1/4 watt resistor
- S1 - Spst switch part of R1
- T1 - Mini transistor output transformer; 500-ohm center tapped primary to 8-ohm secondary
- EXP - ANY EXP. BREADBOARD.

The anglers dream come true. This electronic marvel emits a CLIK-CLIK sound that makes fish really hungry. Shove the whole works in a watertight container lower it over the side and wait for the fish to grab the hook.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE A COPY OF THE FULL PROJECT FISH'N'CLIKS, AND A COPY OF PROJECT No 1 "TWO TRANSISTOR RADIO".

### PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



- PC - 16 pin. £2.75.
- PC - 16 pin with cable, £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.

CONTINENTAL SPECIALTIES CORPORATION



Europe, Africa, Mid-East: CSC UK LTD.  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: SAFFRON WALDEN 21682.  
Telex: 817477.

## EXPERIMENTOR BREADBOARDS.


No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


**EXP.325.** The ideal breadboard for 1 chip circuits. Accepts 8,14,16 and up to 22 pin IC's. **ONLY £1.60.**




**EXP.350. £3.15.** 270 contact points with two 20-point bus-bars.

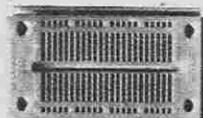

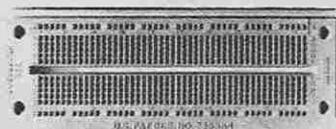**EXP. 300.** 550 contacts with two 40-point bus-bars. **£5.75.**



**EXP. 650** for Micro-processors. **£3.60.**

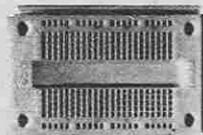

**EXP 4B.** More bus-bars. **£2.30.**



ALL EXP.300 Breadboards mix and match with 600 series.


## PROTO-BOARDS.

THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST. TWO EASILY ASSEMBLED KITS.



PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

**PROTO-BOARD 6 KIT. £9.20.**

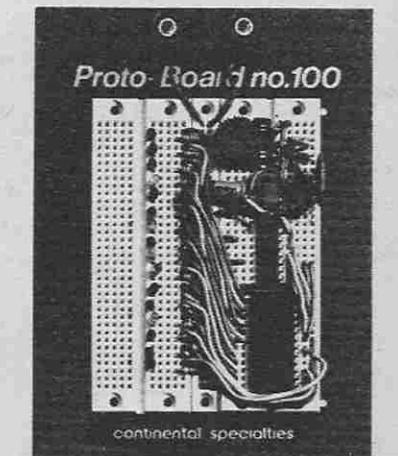

PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

**PROTO-BOARD 100 KIT £11.80.**

### HOW TO ORDER AND RECEIVE FREE COPY OF FISH'N'CLIKS PROJECT WITH BONUS OF FREE TWO TRANSISTOR RADIO PROJECT.

**CSC UK LTD.** Dept. 4P, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
TEST CLIPS			
PC. 16.			£ 3.78
PC.16-18.			£ 7.56
PC. 16-18 Dual Clip.			£12.15
PROTO-BOARDS.			
PB. 6.	630	6	£11.01
PB. 100.	760	10	£13.82

NAME .....

ADDRESS .....

4P

FILL IN COUPON & RECEIVE FREE COPY OF  
ELECTRONICS BY NUMBERS PROJECTS No 1 AND No 2



- ACCESS
- BARCLAYCARD
- CASH
- CHEQUE

**FREEPOST ON ORDERS**  
**VAT INCLUSIVE PRICES**  
**ADD 30p P&P**  
**24 HR TELEPHONE ANSWERING SERVICE**

**GMT ELECTRONICS**  
**Freepost**  
**Birmingham B19 1BR**  
 TEL. ORDERS WELCOME

**DIGITAL INTEGRATED CIRCUITS**

4000 Buffered C-MOS - High Speed

5-15V 'B' Series, Up to 20MHz

7400 T.T.L.

HEF4001 14	HEF4046 100	HEF4514 250	N7400N 0	N7444N 83	N74122N 39	N74192N 60	N74LS28N 32	N74LS138N 85	N74LS253N 105
HEF4001 14	HEF4047 87	HEF4515 295	N7401N 11	N7445N 65	N74123N 37	N74194N 80	N74LS30N 16	N74LS139N 85	N74LS257N 104
HEF4002 14	HEF4049 28	HEF4516 90	N7402N 11	N7446N 62	N74125N 32	N74195N 79	N74LS32N 24	N74LS153N 76	N74LS258N 107
HEF4006 95	HEF4051 28	HEF4517 382	N7403N 11	N7447AN 51	N74126N 32	N74198N 120	N74LS33N 34	N74LS154N 127	N74LS259N 108
HEF4007 14	HEF4051 69	HEF4518 69	N7404N 12	N7448AN 12	N74128N 44	N74199N 139	N74LS37N 24	N74LS155N 80	N74LS261N 300
HEF4008 80	HEF4052 22	HEF4519 95	N7405N 12	N7449N 13	N74132N 46	N74221N 160	N74LS38N 24	N74LS156N 80	N74LS266N 40
HEF4011 14	HEF4053 22	HEF4520 25	N7406N 25	N7451N 13	N74135N 46	N74279N 116	N74LS40N 22	N74LS157N 54	N74LS273N 130
HEF4012 14	HEF4066 37	HEF4521 188	N7407N 27	N7453N 15	N74147N 125	N74298N 200	N74LS42N 53	N74LS158N 60	N74LS283N 116
HEF4013 32	HEF4067 390	HEF4528 99	N7408N 13	N7454N 13	N74148N 85	N74365N 150	N74LS51N 22	N74LS160N 120	N74LS290N 90
HEF4014 84	HEF4068 14	HEF4532 120	N7409N 13	N7456N 13	N74150N 65	N74368N 150	N74LS54N 16	N74LS161N 78	N74LS293N 100
HEF4015 84	HEF4069 14	HEF4534 110	N7410N 11	N7470N 26	N74151N 45	N74369N 120	N74LS55N 22	N74LS162N 130	N74LS296N 100
HEF4016 35	HEF4070 14	HEF4539 110	N7411N 18	N7472N 23	N74153N 55	N74368N 150	N74LS73N 29	N74LS163N 78	N74LS324N 170
HEF4017 55	HEF4071 14	HEF4543 155	N7412N 17	N7473N 23	N74154N 96		N74LS75N 40	N74LS164N 90	N74LS368N 105
HEF4018 66	HEF4072 16	HEF4555 76	N7413N 23	N7474N 23	N74155N 53		N74LS78N 33	N74LS170N 200	N74LS386N 105
HEF4019 46	HEF4073 16	HEF4556 78	N7414N 46	N7475N 28	N74156N 48		N74LS79N 33	N74LS173N 100	N74LS388N 105
HEF4020 88	HEF4079 16	HEF4557 396	N7416N 22	N7476N 25	N74157N 45	N74LS00N 15	N74LS83AN 97	N74LS174N 100	N74LS389N 105
HEF4021 86	HEF4076 85	HEF4568 97	N7417N 23	N7480N 43	N74158N 54	N74LS01N 18	N74LS85N 70	N74LS175N 100	N74LS393N 150
HEF4022 82	HEF4077 14	HEF4574 71	N7420N 11	N7483N 63	N74160N 74	N74LS02N 18	N74LS86N 33	N74LS181N 320	N74LS374N 150
HEF4023 14	HEF4078 16	HEF40097 90	N7421N 26	N7485N 65	N74161N 74	N74LS03N 16	N74LS90N 45	N74LS182N 91	N74LS378N 100
HEF4024 45	HEF4081 16	HEF40098 73	N7422N 27	N7486N 23	N74162N 74	N74LS04N 16	N74LS92N 70	N74LS191N 95	N74LS379N 100
HEF4025 32	HEF4082 16	HEF40106 82	N7423N 22	N7489N 30	N74163N 74	N74LS05N 23	N74LS93N 45	N74LS192N 128	N74LS380N 150
HEF4027 42	HEF4086 64	HEF40190 119	N7427N 22	N7491AN 60	N74164N 65	N74LS06N 16	N74LS95AN 65	N74LS193N 130	N74LS380N 170
HEF4028 62	HEF4086 64	HEF40161 119	N7428N 30	N7492N 33	N74165N 65	N74LS09N 22	N74LS96N 116	N74LS194N 150	N74LS383N 170
HEF4029 60	HEF4083 50	HEF40162 119	N7430N 11	N7493N 31	N74166N 93	N74LS10N 16	N74LS107N 38	N74LS195AN 120	N74LS389N 180
HEF4030 46	HEF4094 175	HEF40163 119	N7432N 21	N7494N 44	N74170N 134	N74LS11N 22	N74LS109N 38	N74LS196N 80	N74LS400N 130
HEF4031 200	HEF4104 166	HEF40174 119	N7433N 30	N7495AN 48	N74173N 63	N74LS12N 22	N74LS112N 40	N74LS197N 115	N74LS407N 170
HEF4035 110	HEF4502 91	HEF40175 119	N7437N 21	N7496N 48	N74174N 68	N74LS13N 38	N74LS113N 38	N74LS240N 160	N74LS408N 160
HEF4040 65	HEF4506 571	HEF40192 140	N7438N 21	N74100N 85	N74175N 67	N74LS14N 24	N74LS114N 38	N74LS241N 160	N74LS409N 160
HEF4041 79	HEF4509 151	HEF40193 140	N7439N 80	N74107N 28	N74180N 80	N74LS15N 74	N74LS125N 40	N74LS242N 160	N74LS410N 160
HEF4042 54	HEF4510 70	HEF40194 119	N7440N 12	N74109N 42	N74181N 165	N74LS20N 16	N74LS126N 40	N74LS243N 160	N74LS411N 160
HEF4043 79	HEF4511 110	HEF40195 119	N7442N 40	N74116N 148	N74182N 69	N74LS21N 22	N74LS132N 60	N74LS244N 160	N74LS412N 160
HEF4044 84	HEF4512 98		N7443N 79	N74121N 23	N74192N 65	N74LS22N 24	N74LS135N 37	N74LS251N 90	

**LINEAR INTEGRATED CIRCUITS**

CA3011 92	NE692K 162
CA3018 75	RC4136 130
CA3020 191	TBA120S 79
CA3028A 86	TCA580 346
CA3046 76	TCA730 450
CA3046 245	TCA740 450
CA3080E 70	TDA1008 262
CA3089E 253	TDA1022 848
CA3130E 90	TDI1028 338
CA3140E 38	TDI1028 338
CA3188E 266	TDI1034E 217
LM301AN 130	TDI2551 262
LM308N 91	TDI2640 282
LM318N 200	TL081CP 75
LM319N 216	TL084CN 140
LM324N 70	UA709CT 46
LM339N 71	UA709CN 40
LM381N 110	UA7110CN 61
LM381AN 180	UA7111CN 65
LM392 120	UA711CT 42
	UA741CN 18
	UA747CN 50
	UA748CN 35
MC1458N 35	
MC1496N 97	
NEK31 119	
NE536T 218	
NE540 228	
NE555N 26	
NE556N 60	
NE580N 351	
NE581N 427	
NE582N 461	
NE585N 120	
NE586N 155	
NE587N 170	
NE5870N 400	
NE571N 459	

**OPTO ELECTRONICS**

<b>Light Emitting Diodes, Individual</b>		<b>Order Code</b>
.125" (3mm)	Red	14 CCY54
	Green	17 CCY96
	Yellow	19 CCY97
Panel Mounting Clip to suit.		3 LEDs Clip
2" (5mm)	Red	15 CCY24A
	Green	17 CCY94
	Yellow	19 CCY96
Panel Mounting Clip to suit.		5 LEDs Clip
<b>Light Emitting Diodes - 7 Segment Display</b>		
3" (7.6mm) C. Anode R.H. Decimal Pt.		160 XAN3061
	Green	199 XAN3051
	C. Cathode R.H. Decimal Pt. Red, Low current drain	160 XAN3074
5" (12.2mm) C. Anode L.H. Decimal Pt. Red		230 XAN6620
	Pt. Green	230 XAN6520
	C. Cathode L.H. Decimal Pt. Red	230 XAN6640
<b>Photorsistors</b>		
	ORP12	90 ORP12
	ORP61	90 ORP61
<b>Phototransistors</b>		
	OCF71	180 OCF71
	BPX25	175 BPX25
	BPX29	175 BPX29
<b>Photocoupler</b>		
	FC0820	150 FC0820

**SWITCHES**

<b>Miniature Toggle - Honeywell</b>		<b>Order Code</b>
SPDT	2A/250V A.C., 5A/28V D.C.	58 SW 8A1011
SPDT	C/OH	67 SW 8A1021
SPDT	Double Bias To Centre	75 SW 8A1041
SPDT	Single Bias To Centre	76 SW 8A1061
SPDT	Slits	70 SW 8A1081
DPDT	C/OH	92 SW 8A2021
DPDT	Double Bias To Centre	102 SW 8A2041
DPDT	Single Bias To Centre	102 SW 8A2051
DPDT	Slits	96 SW 8A2061
<b>Miniature Push - C &amp; K</b>		
SP	Push To Make, Momentary	0.5A/260V A.C., 1A/28V D.C.
SP	Push To Break, Momentary	54 SW 8531
		54 SW 8533
<b>Slide - Switchcraft</b>		
DPDT	Standard Actuator	36 SW 46206
DPDT	Slot Actuator, Voltage Change, Marked 110/240	43 SW 46206F

**SEMICONDUCTORS**

<b>Diodes</b>			
IN827	193	IN4006	7
IN814	4	IN4007	8
IN916	5	IN4148	3
IN4001	4	IN5402	15
IN4002	4	IN5404	16
IN4003	6	2A13	5
IN4004	6	2N5416	106
IN4005	7	BB106(4)	122
		BB110G	61
		BY127	15
		EY206	34
		BYX10	19
		OA47	10
		OA80	7
		OA81	7
		OA200	9
		OA201	9
<b>Zener Diodes</b>			
400mW CAV7-C33		1.3W C7V5-C75	
BZV58/BZV79 + Voltage	8	BZV81 + Voltage	16

**TRANSISTORS**

2N929	37	2N4427	206
2N1833	30	2N4856	158
2N218A	28	2N4858	134
2N2222	21	2N4860	122
2N2369	19	2N5294	43
2N2269A	20	2N5416	106
2N2646	42	2N5457	35
2N2894	49	2N5458	30
2N2895	28	2N5459	32
2N2904	24	2N6258	432
2N2904A	24	40673	80
2N2905	22	AC188	22
2N2906	19	AD162	38
2N2907	22	BC107	10
2N2907A	25	BC107B	14
2N2919	300	BC108	10
2N2926G	11	BC108B	14
2N3053	17	BC108C	16
2N3054	50	BC109	10
		BC109B	16
		BC147	7
		BC148	9
		BC149	8
		BC157	10
		BC158	9
		BC159	11
		BC177	15
		BC178	15
		BC179	18
		BC182	10
		BC182L	11
		BC183	10
		BC183L	11
		BC184	10
		BC184L	11
		BC212	10
		BC212L	11
		BC213	10
		BC213L	11
		BC214	10
		BC214L	11
		BC227	227
		BC228	15
		BC237	17
		BC238	15
		BC239	16
		BC240	16
		BC241	16
		BC242	16
		BC243	16
		BC244	16
		BC245	16
		BC246	16
		BC247	16
		BC248	16
		BC249	16
		BC250	16
		BC251	16
		BC252	16
		BC253	16
		BC254	16
		BC255	16
		BC256	16
		BC257	16
		BC258	16
		BC259	16
		BC260	16
		BC261	16
		BC262	16
		BC263	16
		BC264	16
		BC265	16
		BC266	16
		BC267	

**EDITOR**

F. E. BENNETT

**ASSISTANT EDITOR**

B. W. TERRELL B.Sc.

**PRODUCTION EDITOR**

D. G. BARRINGTON

**TECHNICAL SUB-EDITOR**

T. J. JOHNSON G8MGS

**ART EDITOR**

R. F. PALMER

**ASSISTANT ART EDITOR**

P. A. LOATES

**TECHNICAL ILLUSTRATOR**

D. J. GOODING

**EDITORIAL OFFICES**

Kings Reach Tower,  
Stamford Street,  
London SE1 9LS  
Phone: 01-261 6873

**ADVERTISEMENT MANAGER**

V. PIERI  
Phone: 01-261 6727

**REPRESENTATIVE**

N. BELLWOOD  
Phone: 01-261 6727

**CLASSIFIED MANAGER**

C. R. BROWN  
Phone: 01-261 5762

**MAKE-UP AND COPY DEPARTMENT**

Phone 01-261 6618

**ADVERTISEMENT OFFICES**

Kings Reach Tower  
Stamford Street,  
London SE1 9LS

# Projects... Theory...

# and Popular Features ...

It can be argued that complete overall dependence upon commercial parts and materials is not desirable in a creative pastime. We believe the exercise of inventive and innovative ability is very much an important element in this hobby and should be encouraged, for its own sake, no matter if "Heath Robinsonish" results are sometimes the outcome. Certainly the thought that unfavourable comparisons will be made with the elegant and professional-looking standards we now take as the norm in our projects, should never be the reason for failing to experiment, at least on the odd occasion, with different and less formal ways for building electronic circuits.

The young, and others whose pockets are not especially capacious, find the use of alternative materials a necessity—and we know what necessity is the mother of, so the point hardly needs labouring. But it is no bad thing for everyone, no matter the size of their pocket, to cultivate the knack of converting for their special purpose some humble run of the mill article or to make use of discarded materials. As an example we can think of the boundless supply of plastic receptacles in infinite variety that have but a fleeting life once taken from the supermarket shelves. As our enterprising readers have demonstrated on innumeral occasions there are possibilities for extending the life of these plastic containers in our own special field.

Make and do for oneself is the underlying purpose of our *Mini Module* Series. The tobacco tin motif is not a leaning back to the good old days when do-it-yourself actually meant just that. But it symbolises the home-spun as against modern orthodox construction. These useful projects have been used as vehicles to demonstrate simple but effective methods in assembling simple circuits. Cardboard, plywood, pins and nails, have all shared the honours, along with more orthodox items such as tag strips, terminal blocks and stripboard; and the tobacco tin after its inaugural appearance has been superseded by electricians' switch boxes and purpose built plastic boxes.

As readers will already have noticed another contributor has just joined our pages and *Rummaging Around* is intended to reinforce the make and do aspect, albeit in a lighthearted way. And why not, for it is fun.

In any activity, a certain degree of self-sufficiency must always be admired, and in electronics construction it provides a beneficial antidote to the all-too-easy-just-assemble-a-kit attitude which maybe we are in danger of slipping into.



Our July issue will be published on Friday, June 15. See page 343 for details.


**Readers' Enquiries**

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

Telephone enquiries should be limited to those requiring only a brief reply. We cannot undertake to engage in discussions on the telephone, technical or otherwise.

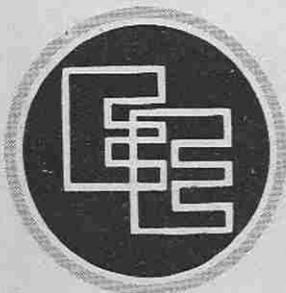**Component Supplies**

Readers should note that we do not supply electronic components for building the projects featured in **EVERYDAY ELECTRONICS**, but these requirements can be met by our advertisers.



# Everyday ELECTRONICS

VOL. 8 NO. 6

JUNE 1979

## CONSTRUCTIONAL PROJECTS

<b>TREMOLO UNIT</b> Sound effects for your guitar or organ by E. M. Lyndsell	330
<b>ELECTRONIC CANARY</b> Novel "twittering" doorbell by F. G. Rayer	334
<b>EE LABCENTRE</b> Part 4: Tool tray and final testing by R. W. Coles and B. Cullen	344
<b>LOW COST METAL LOCATOR</b> Simple b.f.o. detector using a CMOS device by R. A. Penfold	348
<b>MINI-MODULE: 8-METER AMPLIFIER</b> Extends the range of your meter by George Hylton	354
<b>POCKET RADIO</b> Simple medium wave receiver using the ZN414 "chip" by J. Herron	366
<b>QUAD SIMULATOR</b> "Surround sound" from your stereo by B. York	371

## GENERAL FEATURES

<b>EDITORIAL</b>	328
<b>SHOP TALK</b> Guidance on component buying by Dave Barrington	333
<b>CROSSWORD NO. 16</b> by D. P. Newton	336
<b>FOR YOUR ENTERTAINMENT</b> Sound, speech and translating by Adrian Hope	337
<b>DOING IT DIGITALLY</b> Part 9: Problem solving and games with TTL by O. N. Bishop	338
<b>COUNTER INTELLIGENCE</b> A retailer comments by Paul Young	342
<b>MINI MODULES IN COMBINATION</b> Various applications for the published projects by George Hylton	353
<b>MICROPROCESSOR BASICS</b> Part 4: ROMS, UART and build your own ROM by R. W. Coles	356
<b>RADIO WORLD</b> A commentary by Pat Hawker	361
<b>EVERYDAY NEWS</b> What's happening in the world of electronics	362
<b>RUMMAGING AROUND</b> Money-saving ideas for the constructor by Keith Cadbury	364
<b>JACK PLUG AND FAMILY</b> Cartoon by Doug Baker	373
<b>WORKSHOP MATTERS</b> Organising the workshop and buying components by Harry T. Kitchen	374
<b>EE SPECIAL REPORT</b> Connoisseur Package Deal	377
<b>SQUARE ONE</b> Beginners page. Component coding	378
<b>PROFESSOR ERNEST EVERSURE</b> The Extraordinary Experiments of. by Anthony J. Bassett	381

Back issues of EVERYDAY ELECTRONICS June 1977 onwards (October to December 1977, January to March 1978 NOT available) are available worldwide at a cost of 70p per copy inclusive of postage and packing. Orders and remittance should be sent to: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

Binders for Volumes 1 to 8 (state which) are available from the above address for £2.85 (£3.45 overseas) inclusive of postage and packing. Subscriptions (for one year)—UK: £8.50. Overseas: £9.50.

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

B  
E  
G  
I  
N  
N  
E  
R  
S  
YOUR INTRO  
TO ELECTRONICS  
SQUARE  
ONE

**T**HE TREMOLO is believed to be one of the first musical effects units—certainly for use with the electronic guitar—and was featured prominently in “pop” music of the fifties. It is used to a lesser extent in present day music but is still required for certain musical numbers.

In the past many methods have been used to obtain the tremolo effect both electronic and mechanical. One of the mechanical methods was to open and close a shutter sited in front of the loud-speaker.

continuously variable by changing one component. The Tremolo is suitable for guitar, organ and voice.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the Tremolo Unit is shown in Fig. 2. It is powered by a single

The input impedance of the circuit is approximately 8 kilohms which should suit most electric guitars.

Preset VR1 is used to control the overall gain by setting the quiescent current flowing into pin 5 via R6.

## OSCILLATOR

The oscillator is composed of IC2 and associated components connected as a phase-shift oscillator. The output is sinusoidal at a frequency set by VR3 (the SPEED control) which varies the frequency from about 3 to 10Hz. The peak-to-peak amplitude of the oscillator output is 5 volts about mid-supply, which is fed via R3 and C4 to R6 and then into pin 5. Thus the gain IC1 is controlled by the oscillator output. The result is to cause the output signal from IC1 to be amplitude modulated as depicted in Fig. 1.

Resistors R13 and R14 effectively produce a split supply for IC2 with decoupling by C8.

The depth of modulation is controlled by R8 and S1, the DEPTH switch. For a deep effect S1 is set to short out R8. This resistor is in circuit for a shallow effect.

The oscillator is caused to cease oscillating by closing S2, the EFFECT control. The musical signal appears at SK2 unaffected with an amplitude controlled only by VR1.

If a continuously variable depth control is required, R8 should be

9V battery. Current consumption is very low typically 1.7 to 2.1 milliamps, so the battery should have a long life.


The circuit is seen to be in two distinct sections: a current controlled amplifier and an oscillator.

## CURRENT AMPLIFIER

The amplifier uses a transconductance operational amplifier IC1. In many respects this is similar to “normal” op-amps and has the same pinning as the common 741. The gain of the amplifier however, is controlled by the current flowing into pin 5, producing an output current into a fixed load, R7 in this circuit.

Resistors R1 and R2 effectively produce a split supply for IC1 with C2 performing decoupling.

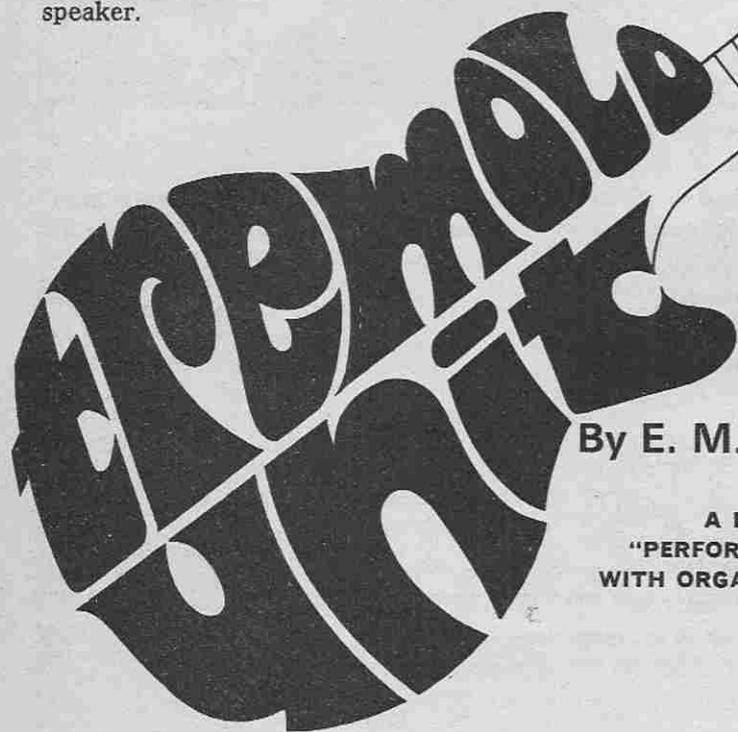**COMPONENTS**  
approximate  
cost **£6**



By E. M. Lyndsell

**A PROFESSIONAL  
“PERFORMER” FOR USE  
WITH ORGAN, GUITAR OR  
VOICE**

Tremolo is the name given to the amplitude modulation of the guitar signal by a very low frequency, typically 3 to 10Hz. The result is to produce “packets” of musical signal, see Fig. 1. Varying the speed and depth of the modulation produces different effects.

The unit to be described here has two set depths—deep and shallow, but can easily be made

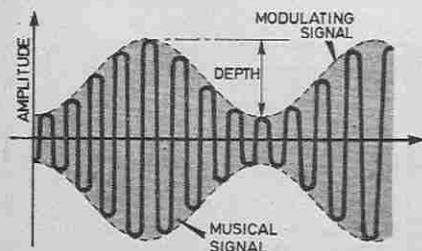


Fig. 1. The tremolo effect in graphical form. A sinewave “music signal” has been shown for clarity.

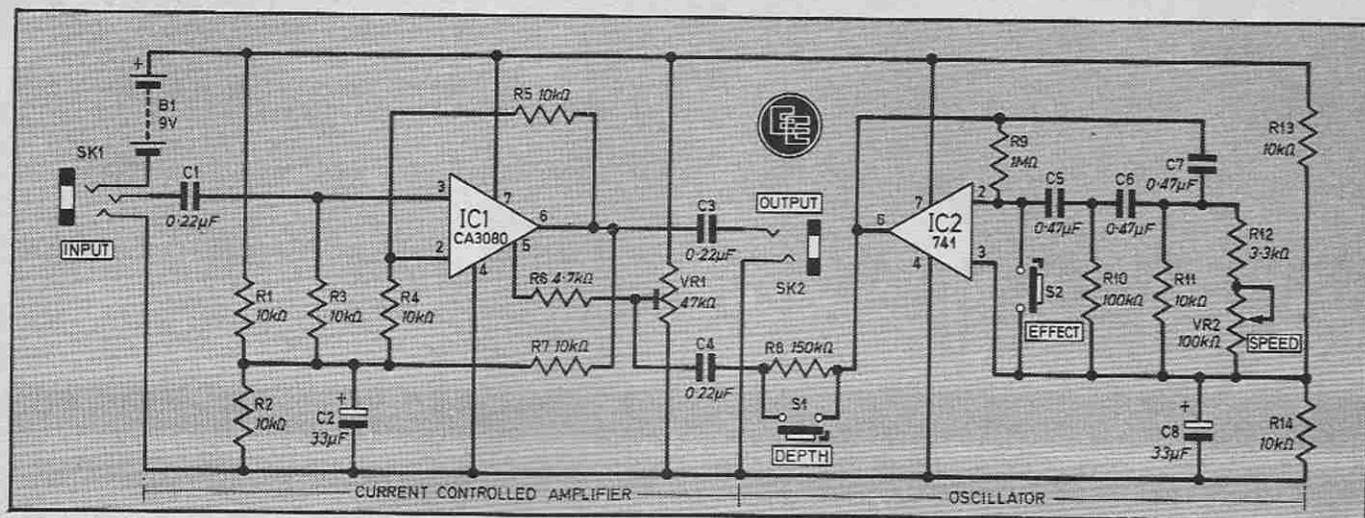


Fig. 2. The complete circuit diagram of the Tremolo Unit.

replaced with a 220 kilohm potentiometer wired as a variable resistor, S1 would then of course not be needed.



The construction of the unit differs a little from that shown on the front cover as the design has been modified slightly, to improve its performance. The l.e.d. has been removed in the interests of battery economy and a larger case has been employed to make construction more easy.

### CIRCUIT BOARD

The circuit is built on a piece of 0.1 inch matrix stripboard, size 31 strips x 29 holes. The layout of the components on the topside of the board and the breaks to be made along the strips on the underside are shown in Fig. 3.

No fixing of the board was found necessary on the prototype. It was laid on a piece of polystyrene tile and the case mounted switch and sockets held the board steady. If board fixings are required holes should be made in the case and board before proceeding; spacers to hold the board clear of the case are essential as well as fixing isolating breaks on the copper strips.



Begin by mounting the resistors, capacitors, link wires and preset followed by the i.c.s.; IC1 is a TO-5 type and its legs have been formed to suit a d.i.l. arrangement. Pin 8 is adjacent to the tag on the body. These devices can also be obtained with pre-formed d.i.l. arrangement and IC2 is available also in a plastic d.i.l. package as is more commonly found.

Attach sufficient lengths of flying leads to reach the case mounted components. Note that some

## COMPONENTS

### Resistors

R1 10kΩ	R8 150kΩ
R2 10kΩ	R9 1MΩ
R3 10kΩ	R10 100kΩ
R4 10kΩ	R11 10kΩ
R5 10kΩ	R12 3.3kΩ
R6 4.7kΩ	R13 10kΩ
R7 10kΩ	R14 10kΩ

All ¼ watt (or less) carbon ± 10%

### Capacitors

C1 0.22μF polyester	C5 0.47μF polyester
C2 33μF 6V elect.	C6 0.47μF polyester
C3 0.22μF polyester	C7 0.47μF polyester
C4 0.22μF polyester	C8 33μF 6V elect.

### Integrated Circuits

IC1 CA3080 transconductance op-amp. 8 pin d.i.l. (preferable)
IC2 741 differential op-amp 8 pin d.i.l.

### Miscellaneous

VR1 47kΩ horizontal carbon preset
VR2 100kΩ carbon Lin. potentiometer
S1, 2 single-pole successional action footswitch (2 off)
SK1 stereo jack socket
SK2 mono jack socket
B1 PP3 9 volt battery

Stripboard: 0.1 inch matrix 31 strips x 29 holes; PP3 battery clip; knob for VR2; aluminium diecast box approximate size 115 x 90 x 50mm; screened cable; connecting wire.

See  
**Shop  
Talk**  
page 333


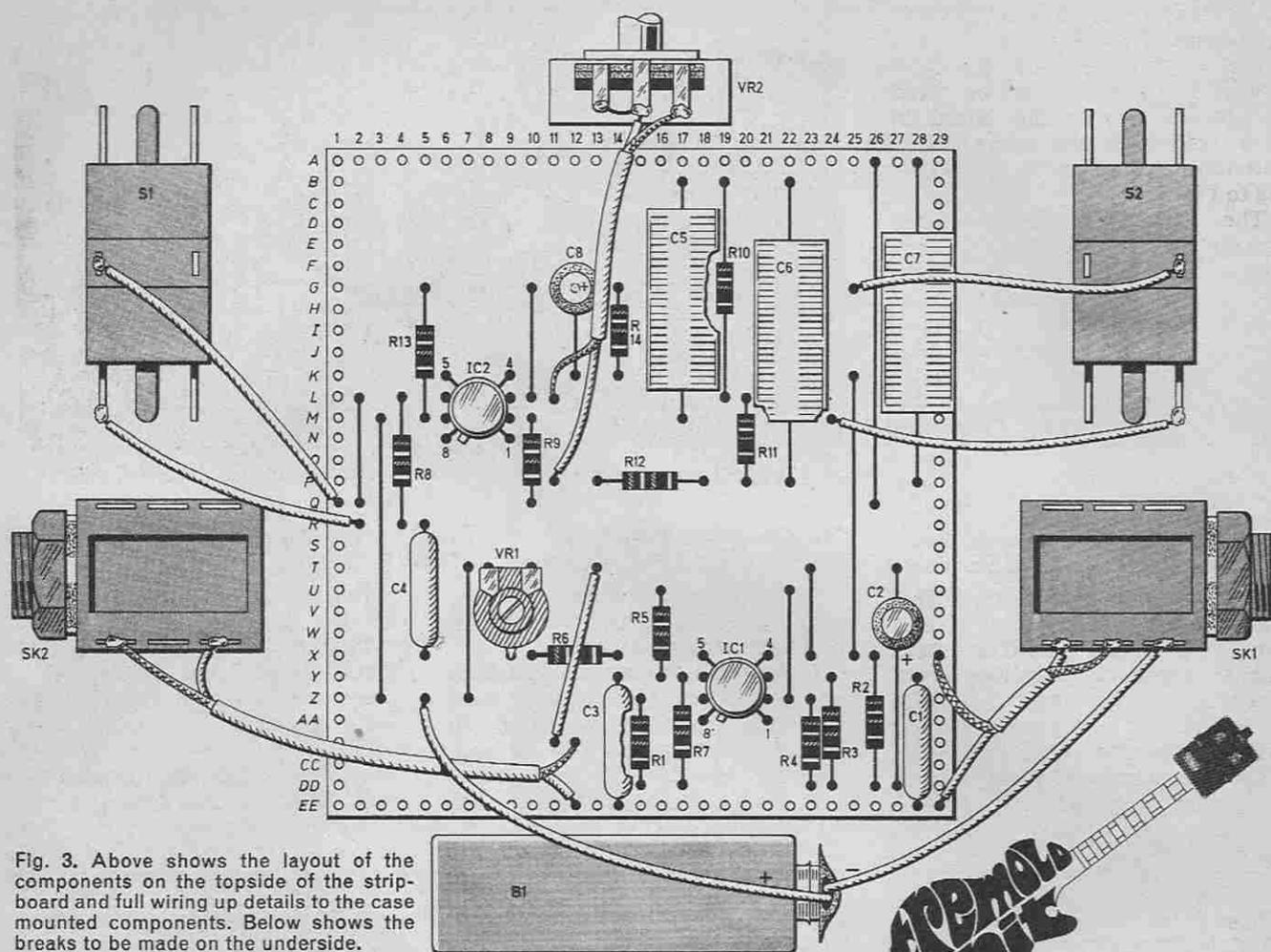
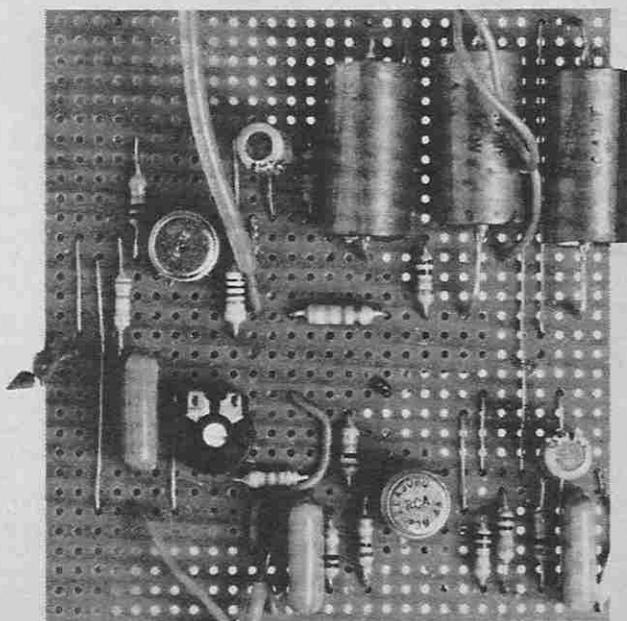


Fig. 3. Above shows the layout of the components on the topside of the strip-board and full wiring up details to the case mounted components. Below shows the breaks to be made on the underside.

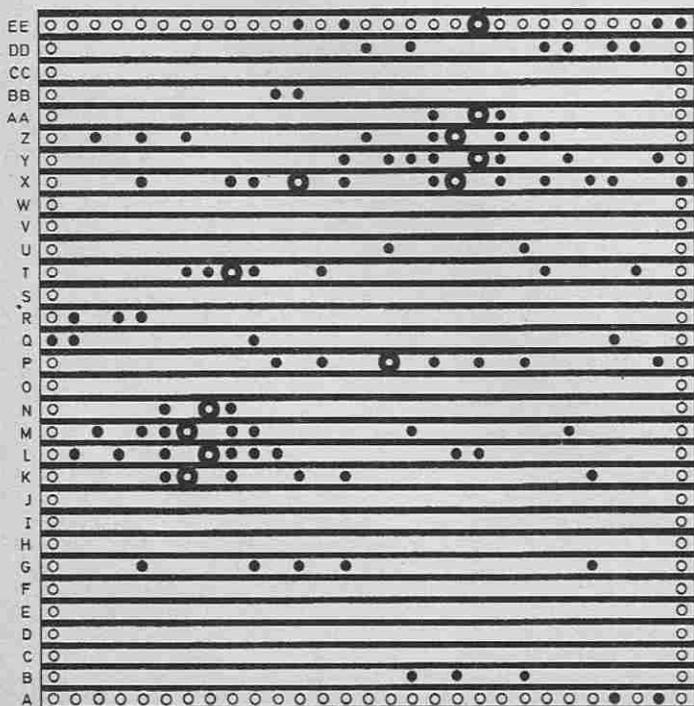

The completed component board removed from its case.

of these are screened cable to reduce extraneous hum and noise.

Prepare the case to accept the sockets, switches and potentiometer. The switches can be fitted to the lid. Secure the board in place and then the sockets and potentiometer and wire up according to Fig. 3.


The prototype used stereo sockets but a stereo type is only required for SK1. The rear earth tag is used as the battery on/off switch. This is made along the shank of the input mono jack plug when inserted. The unit is automatically switched off when the input jack is removed from the unit.

Before connecting the battery set VR1 fully anti-clockwise.
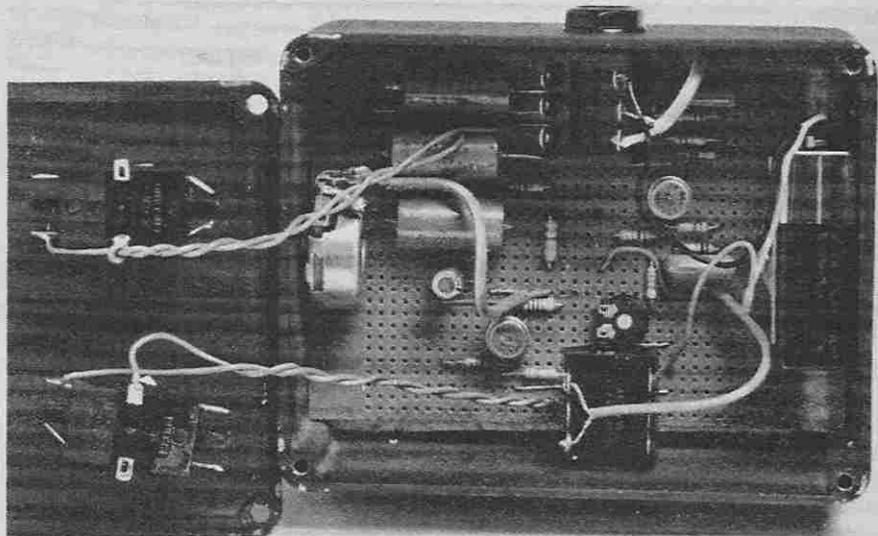
## SETTING UP AND USE

Plug the instrument in at SK1 and connect via a suitable lead from SK2 to the amplifier input. A high impedance amplifier input is required for best results.

With S2 set for EFFECT, S1 for maximum DEPTH, and VR2 fully clockwise (maximum SPEED), strum the guitar and finely adjust VR1 with a small screwdriver until the



The completed prototype unit with lid removed showing case mounted components, board positioning and wiring to the lid mounted switches.


tremelo sound is obtained. Turn VR2 anticlockwise and the modulation rate should decrease.

Operate S1 to obtain a less deep effect. The value of R8 may need altering to suit but will probably be in the range 100 to 220 kilohms.

Operate S1 to inhibit the effect and allow straight-through playing.

If all the above tests are successful, the unit is ready for use.

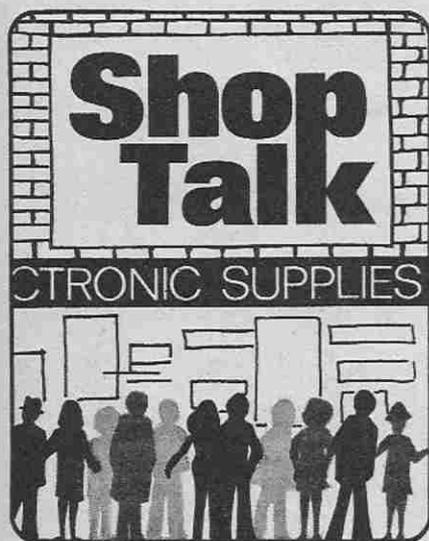The prototype was sprayed matt black (after application of a primer) and labelled using Letra-set to produce a professional looking unit. Four rubber feet glued to the case underside prevents the unit sliding under operation.



By Dave Barrington

### Mail Order Only

IT IS sad that Home Radio Components Ltd, one of the oldest names in the electronic components business (at least on the retail side) had to move due to rent increase. To soften the blow, I am informed by the managing director that despite their enforced move they were in good heart and delighted with results of

their moving sale. He reported that at the moment they cannot forecast the restoration of a counter service and at the moment only trade by mail order.

He does advise that if you require something in a hurry to telephone first, the number is 01-648 8422.

## Constructional Projects

Some readers may experience difficulty in obtaining the tuning capacitor C2 called for in the *Pocket Radio*. The final value of this component is not critical and provided the value is near to 126pF any type may be used.

The one used in our prototype was a miniature 4-gang a.m./f.m. type for printed circuit board mounting. These are quite common and ours was ordered as a "Min Tuner", Cat. No. FF52G, from Maplin.

The length of the ferrite aerial is non-standard and will have to be cut to size. This material is very brittle and extreme care must be taken during cutting. We suggest you "score" around the rod before final cutting as sometimes it tends to snap unexpectedly.

Our *Low Cost Metal Locator* this month is a very simple design, but the results have been very good, and should not present any problems re-

garding purchase of components. The p.v.c. insulated wire for the search coil is available generally and the final housing is left to individual choice.


In respect of the housing, the original search coil cover called for in our last article and available from Arrow Electronics, Dept. EE, Leader House, Coptfold Road, Brentwood, Essex, or a moulded plastic search coil head case available from Ambit International, Dept. EE, 2 Gresham Road, Brentwood, Essex, could be used.

The only component likely to cause any concern in the *Electronic Canary* is the transformer. Practically any type can be used in this project, but component values may have to be changed to obtain the desired sound effects if other than the specified type is used.

The LT700 transformer is available from Electrovalue at a cost of 44p, including VAT, plus 27p handling charge if ordered as a separate item.


The only point to be made regarding the *Quad Simulator* is that wirewound components rated as specified or greater must be used.

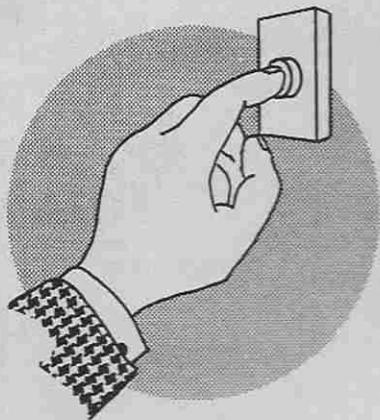The *Tremolo Unit* and this month's *Mini Module* project use standard easy to obtain components and should not give any buying problems.



# Electronic Canary

By F. G. Rayer

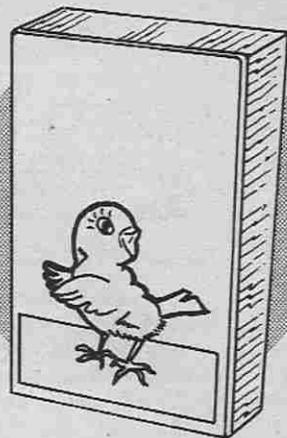

THE TWITTERING or chirping sound from this Electronic Canary unit is very distinctive, and will find use in replacing the traditional door bell or buzzer. Children will also find the sound novel, and will doubtless play with it purely for fun. Operation is economical, the current drain from a PP6 battery being very low and will give many hours of use.

## CIRCUIT DESCRIPTION

The circuit diagram for the Electronic Canary is shown in Fig. 1.

The oscillator is the type known as "self-quenching" or "squegging", and is based on the effects of phase reversal in a transformer.

The primary of the centre-tapped speaker transformer T1 is connected between collector and base of TR1 and drives the base in the correct phase to produce audio oscillation. In a short interval the charging of C1 cuts off the oscillator, which however recommences when the charge leaks away. This effect continues so long as the push is held closed. When the push is released oscillation is maintained for a short while by the charge in C5, but falls away and ceases.

The capacitors C2, C3 and C4 are selected to produce a clear chirping or whistling sound, and the preset potentiometer VR1 allows some adjustment to this.

**COMPONENTS**  
approximate  
cost £5

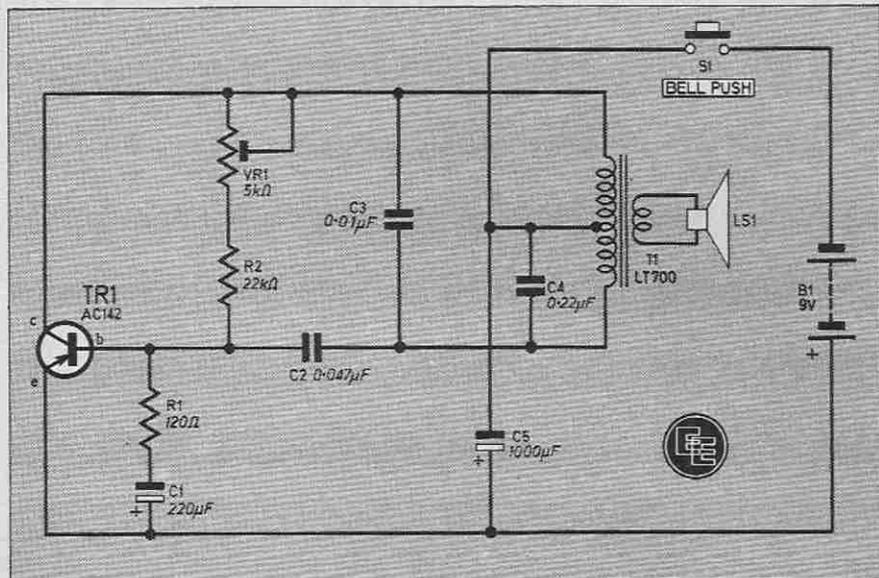


Fig. 1. Complete circuit diagram of the Electronic Canary.

Experiment shows that none of the values need be exactly as shown, but that all influence the result obtained. Changes to values are not recommended except as a basis for tests and experimenting for other sounds.

The author's prototype in fact used a different type to that specified in the components list, being a type T/T7. As far as we know, this is not generally available and the circuit has been slightly modified to use an Eagle LT700 type.

If any constructors are able to obtain or already have this type three component values need to be changed back to their original values to use the T/T7. These are R1 to 470 ohms, R2 to 10 kilohms and C1 to 100 microfarads.

If other types of audio output transformers are to hand, these could be used but will almost certainly need resistor and capacitor value changes to obtain the same result—or other sounds and effects

**CONSTRUCTION**  
starts here

## CIRCUIT BOARD

The circuit is constructed on a piece of 0.15 inch plain matrix board having 19 x 12 holes and is shown in Fig. 2. The transformer has two tabs which project through slots in the board—these can be made by drilling a few holes closely side by side. The tabs are bent or twisted to hold the transformer.

The variable resistor, VR1, is fitted in a similar manner. Its wiper and one outer tag are connected together. If a fixed resistor is substituted for VR1 and R2, connect this from collector to base of

## COMPONENTS

Resistors  
 R1 120 $\Omega$   
 R2 22k $\Omega$   
 $\frac{1}{4}$ W carbon  $\pm 10\%$

Potentiometer  
 VR1 5k $\Omega$  miniature preset

Capacitors  
 C1 220 $\mu$ F 10V elect.  
 C2 0.047 $\mu$ F polyester  
 C3 0.1 $\mu$ F polyester  
 C4 0.22 $\mu$ F polyester  
 C5 1000 $\mu$ F 10V elect.

Semiconductor  
 TR1 AC142 germanium *pnp*

Miscellaneous  
 T1 Eagle LT700 audio output transformer  
 LS1 8 $\Omega$  60mm diameter or similar speaker  
 S1 single-pole push switch (door bell type)  
 B1 PP6 9V battery  
 Matrix board, 0.15 inch 19 x 12 holes; plastic or metal case —or— material for a home made case; aluminium for mounting brackets; connecting wire; battery clip to suit B1.

See  
**Shop  
 Talk**

page 333

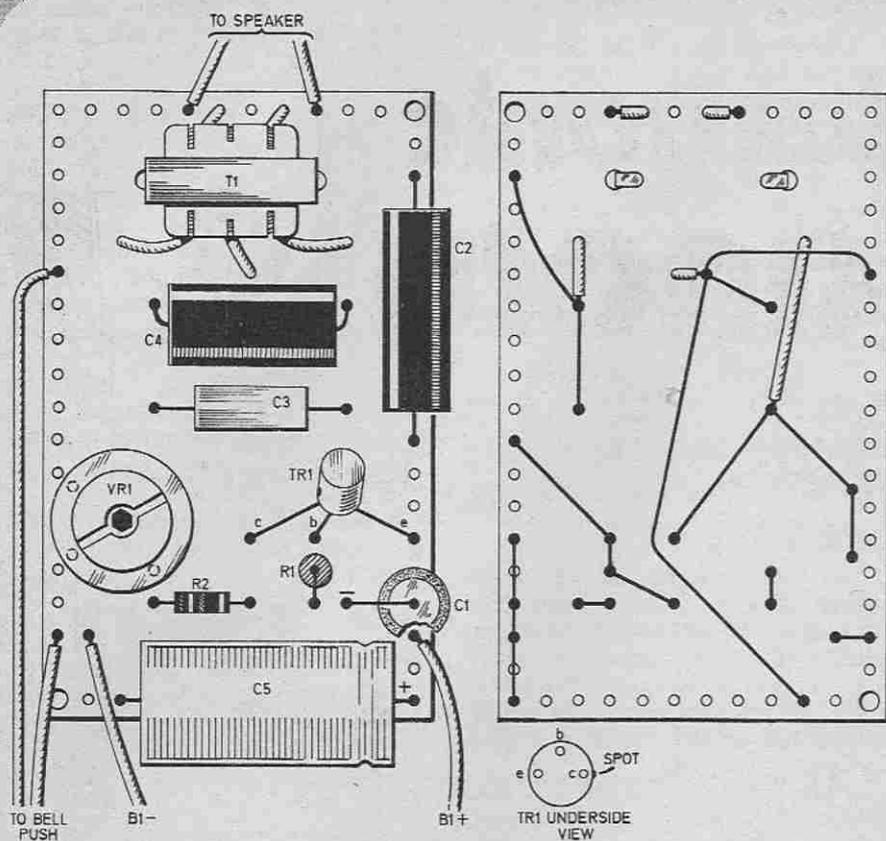


Fig. 2. Matrix board layout. The style of the preset may differ from that shown, but the connections will remain the same.



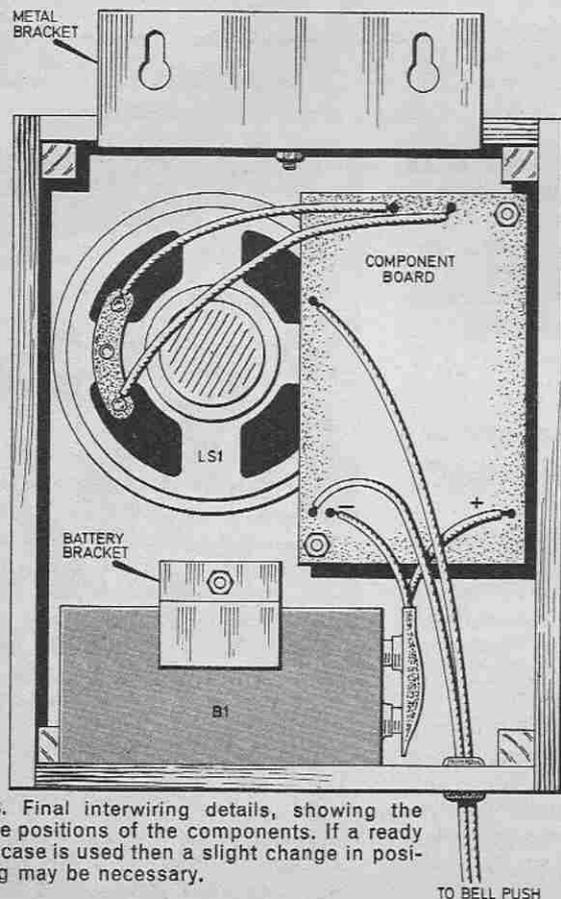


Fig. 3. Final interwiring details, showing the relative positions of the components. If a ready made case is used then a slight change in positioning may be necessary.

## Electronic Canary

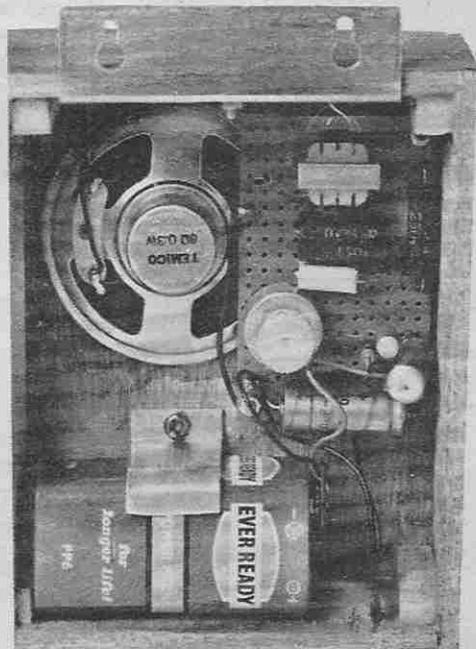

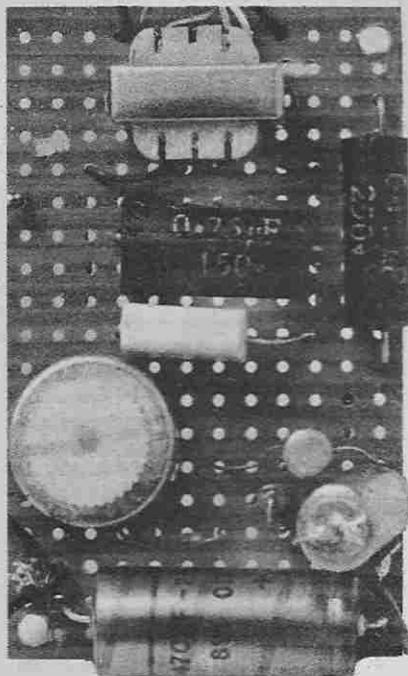The completed Electronic Canary showing positioning of components. The preset potentiometer UR1 can be any common "skeleton" type.



Layout of components on the completed circuit board.

TR1. If the value is rather high, say over 27 kilohms, chirping is less strong. But if the resistor is too low in value, say under about 15 kilohms, only a continuous whistle is obtained. It is for this reason that VR1 is included.

Note the polarity for C1 and C5. Solder on the battery connector.

Two Veropins are inserted for the bell push connections.

Twin flexible bell wire runs from these two pins, through a small hole in the bottom of the case, and to the bell push.

## CASE

A ready-made plastic or metal box can be used, or a case may be easily constructed from 6mm plywood as used on the prototype. The front panel is 145 x 115mm, the top and bottom edges 100 x 65mm and 100 x 38mm respectively. The sides are sloped from 65mm at the top to 38mm at the bottom, and are 145mm long. An aperture to match the speaker cone is first cut in the front.

The sections are secured together with woodworking adhesive. Four 10mm square or similar strips in the corners will give additional strength.

## WIRING

The remainder of the wiring is shown in Fig. 3, and shows the connections to the board and other components. The mounting bracket can easily be made from 18 s.w.g. aluminium and is screwed to the top so the whole unit can be hung on a wall.

A small bracket for holding the battery in place is required and can be made from the same aluminium. Alternatively a self-adhesive strip or Blu-Tak can be employed.


Place the circuit board as in Fig. 3 (speaker omitted) and drill through both board and case front for countersunk 6BA bolts. These are about 25mm long so that the board will clear the speaker when fitted with spacers or "spacing" nuts.

A piece of suitable material about 180 x 140mm is placed over the front and held taut with adhesive spread along the sides of the case. A strip of woodgrain or other self-adhesive material about 560mm long is fitted to cover sides of the case to improve appearance.

The bird motif was cut from a greetings card and various decorations of this kind would be in keeping with the unit. A bird outline could be cut from coloured paper for use here instead.

Once completed the unit can be installed in any convenient position. The sound produced is quite loud and should be heard over quite a distance.

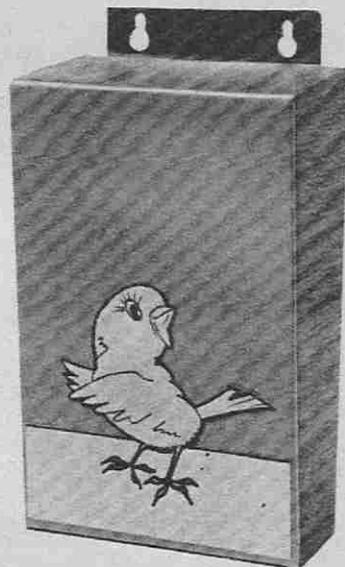Once fitted it will certainly add that touch of individuality to your front door!



## EE CROSSWORD No 16 BY D. P. NEWTON


### ACROSS

- 1 Wiry and identical at the heart of it (4, 4).
- 4 Audible indicator due to electromagnetic action.
- 7 Wiry but like air.
- 8 Fine feathers for a set of clues.
- 9 Spacer.
- 10 Have a strong dislike.
- 12 Set of eight.
- 14 Puzzle variation.
- 17 Knee-deep in want.
- 19 Unlicensed radio station.
- 21 Base material.
- 24 Register a light garment of some calculators.
- 26 To charge up a battery in the generalised sense.
- 27 Necessary computing characteristic.
- 29 Horse-drawn carriages.
- 30 Patron Saint of sparks?
- 31 If you can't make these meet there's an open circuit.

- 32 Underground device for keeping the feline whiskers in trim?
- 33 A contract it LED for heading one of the nobility.
- 34 Tuneful set of calculator digits.

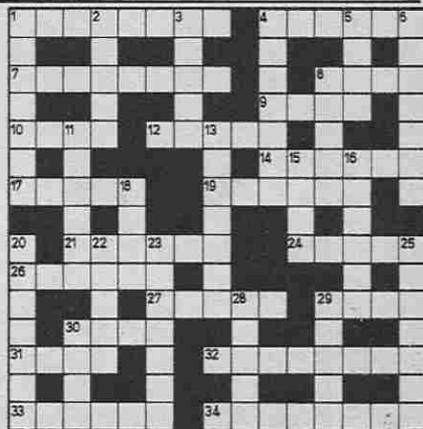
### DOWN

- 1 An educational series (5, 2).
- 2 One is about a discord (Anag.).
- 3 Reversed ancient object.
- 4 Amplifier, of a kind.
- 5 High-powered optical amplifier in a hurry.
- 6 Electrons getting out of hand, usually on a thermal basis.
- 8 It figures in a computer.
- 11 Entrusted with aerial defence from afar (3, 3).
- 13 Repetitive noise on coils.
- 15 A reverse span.
- 16 Spacecraft from a stellar twin.
- 18 Transforms a core with a burdensome device.
- 20 Throw an electronic task.
- 22 Found before storms.



- 23 Adulterated with another metal.
- 25 No sleep on this for the prototype (4, 3).
- 28 Not the object of the screen.
- 29 Lizard.
- 30 Cut a tape, but not to open a fete.

Solution on page 382

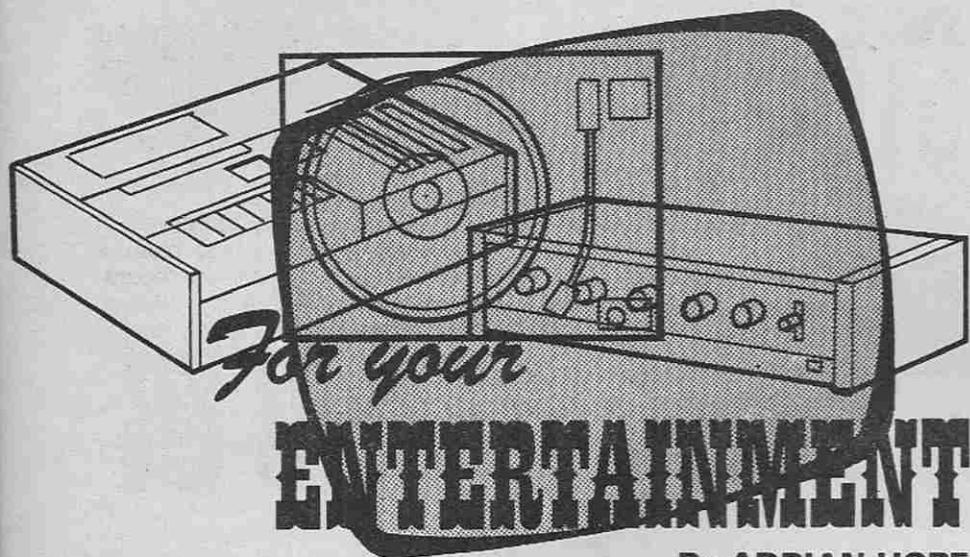

By ADRIAN HOPE

## Sound Off

As far as I know there has never yet been a divorce action based solely on the grounds of over-loud hi fi. But disputes over home listening levels have certainly undermined many a state of marital bliss. The scenario will be familiar to many a male; listening to a favourite piece of music he turns up the volume of the hi fi system and is berated with a "why must you play it so loud". Recently I chanced on some fascinating research work in the USA which explains why this should be.

Around 10 years ago the CBS laboratories in Stamford, Connecticut were commissioned to investigate modern methods of measuring the true loudness of sound. It's important to realise that there is a world of difference between volume level (as for instance) measured by a VU (volume unit) meter and subjective loudness.

In fact for a given VU meter reading, tones of different frequency may differ in loudness level by as much as 20 to 30dB. Likewise although a sound level meter can provide an accurate measure of energy in a sound field, there is still no agreement on how the meter circuits should be "weighted" or filtered to bring their electronic characteristics into conformity with the sensory characteristics of the human ear and brain.

There are also more subtle factors. For instance if two recordings are made at identical energy levels, one of someone shouting and the other of the same person speaking, the shout recording will always sound subjectively louder. CBS argue that this is probably because of the feeling of urgency in the shouting voice.

Recording engineers and broadcasters have long since recognized that it is possible to make an announcement, of solo voice or instrument sound artificially loud by

doctoring its frequency characteristic. The Tamla Motown sound of a few years ago was achieved by packing as much energy as possible into every band of the frequency range; likewise radio commercials can be made artificially obtrusive by a similar technique.

Unfortunately existing sound level and VU meters may not show up such artificial loudness tricks and CBS was looking at new approaches to metering. For this research they asked teams of guinea pig listeners to compare the relative loudness of wide band signals. Some of the guinea pig teams were male and others female.

What CBS discovered to their surprise was that women hear high frequencies better than men. The maximum sensitivity in women being 4.5kHz and in men 3kHz.

This could well explain why women do object to loud hi fi sounds. Modern music has a very high energy content at around these levels, so it just sounds louder to women than men. And any distortion will be much more noticeable.

Quite *why* this should be is not entirely clear. Certainly the pitch of female speech is higher than male speech; but surely female ears should be equally well tuned to hearing both male and female sounds.

## Miniature Chatter Box

"We ain't seen nothing yet", as Jolson once said. In the USA recently a life sized robot called Argon walked into a bar and freaked out staff and drinkers alike by proclaiming "It sure is cold outside, I need a scotch".

In the event it turned out that the exercise was part hoax, because although the robot walked well enough on its own, it wasn't talking on its own. The words were coming from a man outside the bar transmitting by radio to a receiver and amplifier inside the robot's head. But talking gadgetry

is now a reality. There are two major developments in this area.

For years now audio engineers have been able to replicate human speech with reasonable intelligibility, by gating, filtering and modulating tones and hisses produced by generator circuits. But the circuits have been daunting in their complexity and Texas Instruments deserves the most hearty congratulations for now miniaturizing the essential elements into a package the size of a calculator. In fact the heart of the Texas speech synthesis package is a single mos chip made in the same way as a calculator chip.

The details routinely released to the press by Texas in the UK so far have been very sparse, and written as if either the writer doesn't really understand how the system works or is a computer freak unable to speak plain English. Texas talk of LPC or linear predictive coding which appears to be a rather grand way of describing a filter which varies its parameters under fairly rough digital control to modify input signals so that acceptable analogue speech sounds result.

There are two forms of input signal, periodic or pitched and random noise.

The periodic input signals are used as the basis for vowels or voiced fricatives such as the sounds Z, B or D. The random input signal is used for unvoiced sounds such as S, F, T and SH. Two ROMs, each with the capacity to store enough digital instructions for 100 seconds of speech, control the filter action on the periodic and random inputs.

## Translating Calculator

The inevitable next step will be to mate the voice synthesis chips with a fascinating new type of calculator which is being sold in the USA for around 200 dollars. These look like normal calculators, and perform all function calculations and metric conversions, but the calculator display is alpha-numeric; that is to say it reads off both numbers and letters. So a word punched into the keyboard comes up on the display.

Now here's the clever part. The calculator is designed to take plug-in memory modules, which contain well over a thousand words and phrases of a foreign language. With a French, Italian, German, Spanish or Japanese module plugged into the calculator a word or phrase punched into the keyboard in English will appear in the appropriate foreign language on the display.

A Russian translation module is planned in time for the 1980 Moscow Olympics and the logical, in fact inevitable, next step must be to couple speech synthesis with translation display. After all, most foreign phrases are quite worthless, unless you know how to pronounce them correctly.

# DOING IT DIGITALLY



## PART 9

By O. N. Bishop

**T**HIS month we use TTL for solving a logical problem and making a game.

Jack Plug was browsing through his back numbers of *EVERYDAY ELECTRONICS*.

"It seems," he said, "that I have made everything except the *Roulette Game*, the *Power Supply*, the *Air Freshener*, and the *Hot Line Game*. What shall I make next?"

"The *Roulette Game* and the *Power Supply* are big projects", he added, "and I can't afford to make them both."

Jack's daughter was first off the mark.

"Please make at least one of the games", she begged.

Mother said, "*Hot Line* would be useful for my stall at the fête, but if you decide not to make that, then please make me the *Air Freshener* for the kitchen".

Jack's son said, "If you make one or both of the small projects for the home—I mean the *Air Freshener* or *Hot Line*—to be fair you should make the *Power Supply* for the workshop".

"Well I hope I can please everybody," said Jack, "for if I make the *Power Supply* I will not have time to make the *Air Freshener* too."

This set the family off again, each repeating their requests to Jack and to each other. But Jack strolled off and sat down quietly at the table. He began to connect together a few i.c.s. on his Test Bed. After a while an l.e.d. flashed.

"I've solved it", Jack exclaimed, "there is only one way of pleasing all of you—I'll make the . . .".

What project or projects did Jack decide to make?

### LOGIC CIRCUIT LANGUAGE

This problem is not a difficult one and you can easily solve it on paper in a few minutes, but we will take it as an example of the way in which problems may be solved by logical i.c.s.

A computer or microprocessor system can be programmed to solve

problems much more difficult than this one and to produce an error-free answer in a few minutes (or less), but we shall learn more by "doing it digitally" with a few simple i.c.s on the Test Bed.

First we need to set out the problem in a way that a logic circuit can understand. We need a set of symbols for the projects that Jack might make, or might not make:

If R stands for making the *Roulette Game*, P for the *Power Supply*, F for the *Air Freshener* and H for *Hot Line*, and if R, P, F, and H stand for *not* making the project indicated, we can put the statements of Jack and his family in simpler form:

Jack (1st): not R and P (cannot afford to make both)

Daughter: R or H or both

Mother: If H, then F

Son: If F or H, then P

Jack (2nd): If P, then F

The next step is to sort out what logical relationships occur in these statements. To remind you of the main ones, see Table 9.1.

Table 9.1. Composite truth table.

Inputs		Outputs			
A	B	AND	OR	NAND	NOR
0	0	0	0	1	1
0	1	0	1	1	0
1	0	0	1	1	0
1	1	1	1	0	0

In the input columns of Table 9.2, 0 means not make, that is to say R and P respectively. In the output column, 0 means false, i.e. not consistent with Jack's statement. Conversely, 1 means true, i.e. consistent with his statement. From this we can see that the only action that is incon-

Table 9.2. The first condition in truth table form.

Inputs		Output
R	P	
0	0	1
0	1	1
1	0	1
1	1	0

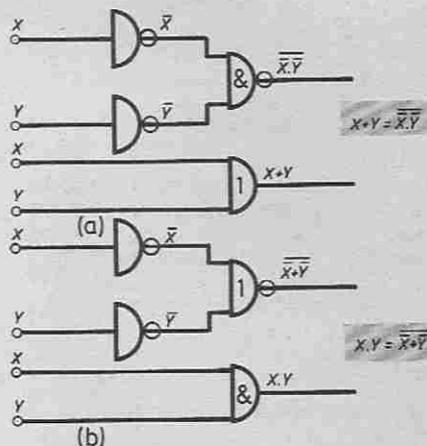


Fig. 9.1. Using basic logic gates to illustrate De Morgan's Laws.

sistent with his statement is to make both P and R—which is precisely what he said he would not do.

The sequence of outputs shows that this is a truth table for the NAND of P and R. A NAND gate will give electronic form to this statement. In symbolic form we write the statement:  $\overline{R.P}$ .

The full-stop signifies the operation AND; the line above signifies NOT; combined they indicate AND followed by NOT, which we usually refer to as NAND, or negative AND.

Daughter's statement is obviously an OR, and can be written:  $R+H$ . The "+" sign signifies the OR operation.

Mother's statement is less obvious, but if you set out the possibilities in a truth table you will recognise that the relationship is OR (remember that Mother does not say what she wants Jack to do about making F if he does make H). We write mother's statement as:  $F+H$ .

By writing a truth table for Jack's second statement we find that this reduces to a NAND, giving us  $\overline{P.F}$ .

The son's statement is a little more difficult to analyse, as it has three terms in it. We can try re-wording it.

If Jack makes  $P$ , his son will certainly be satisfied. But if Jack does not make  $P$  then he must not make  $F$  and not make  $H$ . In short, make  $P$  or not  $F$  and not  $H$ . In symbols this is written:  $P + \bar{F}\bar{H}$ .

To suit all the family we have to find a solution  $Z$  consistent with every one of the separate statements. We AND all the statements together:

$$Z = \bar{R}\bar{P} \cdot (R + H) \cdot (H + F) \cdot (P + \bar{F}\bar{H}) \cdot \bar{P}\bar{F}$$

Three more lines of Boolean algebra would reduce this equation to its final solution but let us make the i.c.s. take over the work for us, as explained below.

### DE MORGAN'S LAW


The equation for  $Z$  contains a number of ORS and ANDS yet most of our i.c.s. contain NORs and NANDS. To convert from ORS and ANDS to NORs and NANDS we make use of two simple equations:

$$X + Y = \overline{\bar{X}\bar{Y}}$$

$$X \cdot Y = \overline{\bar{X} + \bar{Y}}$$

In words—to OR two (or more) quantities, invert them, then NAND them; to AND two (or more) quantities, invert them, then NOR them. There is no space here to prove these two equations, but you can check that they really do work by wiring up the circuits shown in Fig. 9.1.

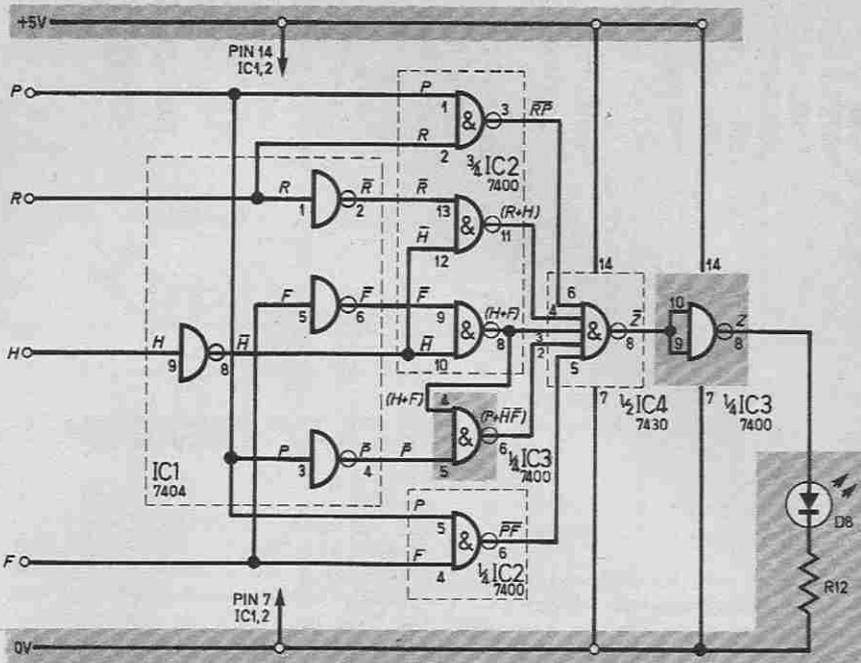Using the upper equation we can see that the daughter's and mother's statements can be re-written as  $\bar{R}\bar{H}$  (the NAND of the inverted  $R$  and  $H$ ) and  $\bar{H}\bar{F}$  respectively. Then we can notice that the son's statement can be rewritten as the NAND of the inverted  $P$  and the inverted mother's statement. Now we are ready to turn this into a TTL circuit.



### TTL SOLUTION

The realisation of these conditions in terms of logic gates appears in Fig. 9.2a and built up on the Test-Bed in Fig. 9.2b. The circuit has four inputs,  $R$ ,  $P$ ,  $F$  and  $H$  and only one output,  $Z$ .

Fig. 9.2a. Circuit diagram for solving Jack Plug's project building problem. Below shows pinning details for two of the i.c.s. used.

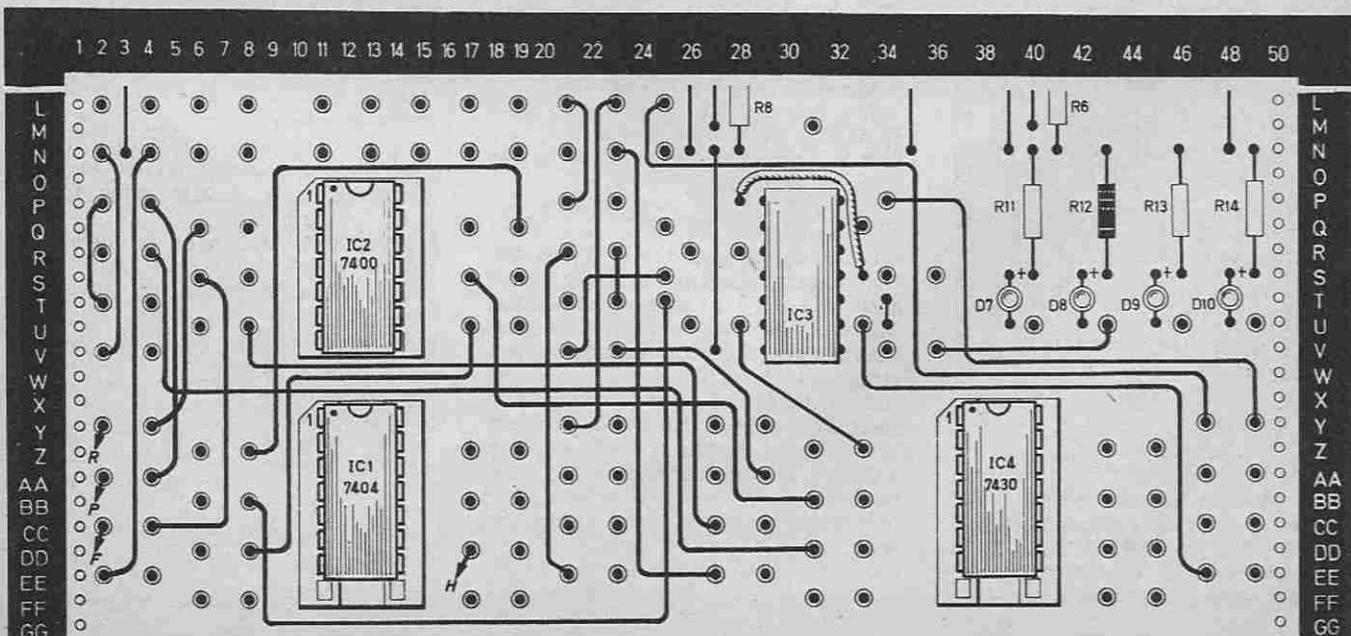
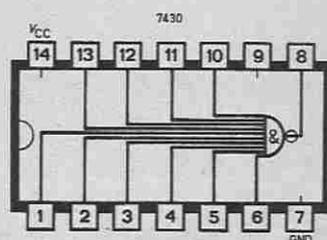
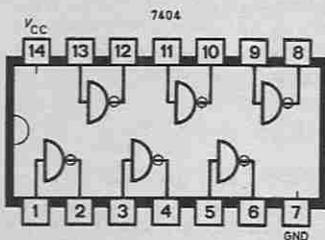


Fig. 9.2b. The circuit of Fig. 9.2a built up on the Test-Bed.

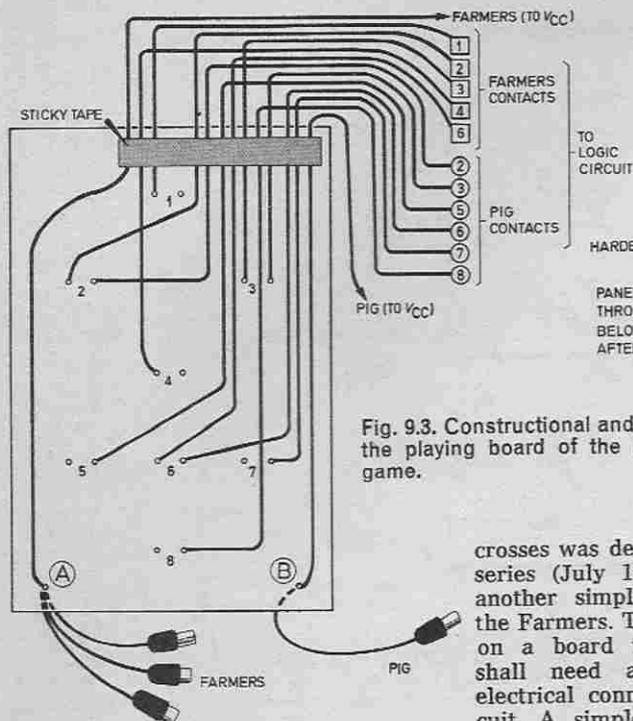


Fig. 9.3. Constructional and wiring details for the playing board of the Pig and Farmers game.

There are five NAND gates each corresponding to one of the statements, and each fed by two inputs either direct or inverted.

The son's NAND receives one of its inputs from the output of the mother's NAND. The five NAND outputs are all ANDED (to please everybody) by using a five-input NAND followed by an INVERT gate. Actually we have to use an eight-input NAND (the 7430) and let the three unused inputs float "high" (logic 1).

To find out which solutions (if any) are possible we need to apply all possible combinations of high and low inputs to the circuit. To do this systematically we can apply a four-digit binary count, from 0000 (build nothing) to 1111 (build all). Any set of inputs which causes the l.e.d. to light indicates a combination of projects that satisfies all the requests of Jack and his family. If the l.e.d. never lights, there is no way of satisfying everybody.

The keyboard coder (Figs. 5.4 and 5.5) is useful for providing the binary inputs 0000 to 1001 (0 to 9 decimal); simply operate keys 0 to 9 in turn. To obtain inputs from 1010 to 1111, hold key 8 down and press keys 2 to 7 in turn. Try it and find out what Jack decided to build.

## PLAYING GAMES

If you want to play Chess against a logical circuit you will have to spend more than £100 on a microprocessor-based system. To learn a little about how logic circuits can be used for playing certain kinds of game, we must be content to analyse one of the more simple games.

A circuit that plays noughts-and-

crosses was described in the first DID series (July 1977). Now we present another simple game—The Pig and the Farmers. This game can be played on a board with counters but we shall need a special board with electrical connections to the TTL circuit. A simple version is shown in Fig. 9.3.

When the Pig or a Farmer is to occupy a certain position on the board, the corresponding crocodile clip is attached to the appropriate contact. Note that there are two contacts at each position—one for the Pig and one for a Farmer. This makes the logic simpler. Pig and a Farmer may not occupy a contact at the same position at any time.

## RULES OF THE GAME

The three farmers begin at the positions marked 1 to 3, the Pig begins at any one of the positions marked 5 to 8. The Pig moves first and may move in any direction along one of the lines to the next contact along that line.


The Farmers move (one each turn) along the lines from contact to contact, but may not move backward. No jumping is allowed.

The Pig (which is played by the logic circuit) is aiming to move from his end of the board to the opposite end. If he reaches one of the contacts marked 1 to 3 he wins, scoring one point: if he reaches that at the extreme end, (No. 1), he scores two points.

The aim of the Farmers (played by you) is to corner the Pig at his end of the board, in which event you win a point. If the Pig is able to move backward and forward between the two same contacts three times, he wins.
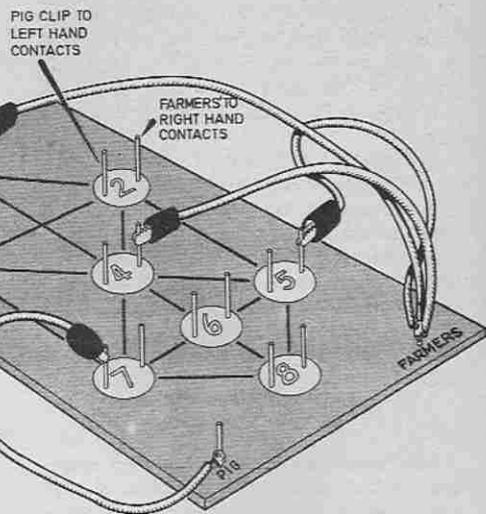
## ANALYSING THE GAME

The logic circuit is designed so that it recognises the positions of the



Farmers and instructs the Pig what to do. There are 280 ways in which Pig and Farmers may be set out on the board, so obviously we shall not be able to arrange for three i.c.s to recognise all these positions.

We can begin to simplify the logical requirements by eliminating from our discussion those positions in which (a) Pig is trapped and has no move available and (b) Pig has only one contact available to move to. We can also eliminate those positions in which Pig has choice but among these choices is free to move in a forward direction. In general Pig should always take a forward move if this is open, so we can make this a "standing instruction to Pig". Also in the rare cases where Pig has no forward or sideways move available he can take any backward move. Thus the standing instructions to the person moving the Pig are:

- (1) If you have no move available—stay put—you have probably lost.
- (2) If you have only one move available—take it.
- (3) If you have a forward move available—take it.
- (4) If you have no forward or sideways moves available—move back.
- (5) If none of the above instructions apply, refer to the logic circuit.

This leaves to the logic circuit the task of deciding what to do when the

Table 9.3. Required logic positions for Pig/Farmers game.

Pig on	Farmers on*	Pig should move
8	2 and 6	left (to 7)
8	3 and 6	right (to 5)
7	3 and 4	right (to 6)
6	2 and 4	left (to 7)
6	3 and 4	right (to 5)
5	2 and 4	left (to 6)
3	1	right (to 2)
2	1	left (to 3)

\* only two farmers matter; the position of the third farmer, if it is important, is taken care of by applying the standing instructions.

Pig has a choice of sideways moves. There are only a few such positions, which is why it is possible to cover the logic required using only the three i.c.s that can be accommodated on the Test Bed. The positions in which logic is required are listed in Table 9.3.

From this table we can see that the circuit needs six inputs to describe the position of the Pig, and five inputs to describe the position of the Farmers. It needs two outputs, one to indicate "move left", the other to indicate "move right".

Certain combinations of positions occur twice in the table, see Table 9.4.

Table 9.4.

Pig on	Farmers on
8	6
—	3 and 4
—	2 and 4

We can make use of this fact to simplify the gate connections. These pairs of inputs can be ANDed and each used as a single input at later stages in the logic.

### AND-OR-NOT GATE

There is a combination of gates in one i.c. that will solve the logical problems of playing Pig and Farmers, the 7454. The pin-out details are shown in Fig. 9.5. It has eight inputs and one output. The output is normally high, but goes low when the following inputs go high:

A AND B OR C AND D OR E AND F OR G AND H OR any two or more pairs of inputs listed above.

In short, the inputs are ANDed in pairs, the AND outputs are all ORed, and the OR output is inverted (NOT), so giving this combination of gates its rather lengthy name; Fig. 9.4(a) shows

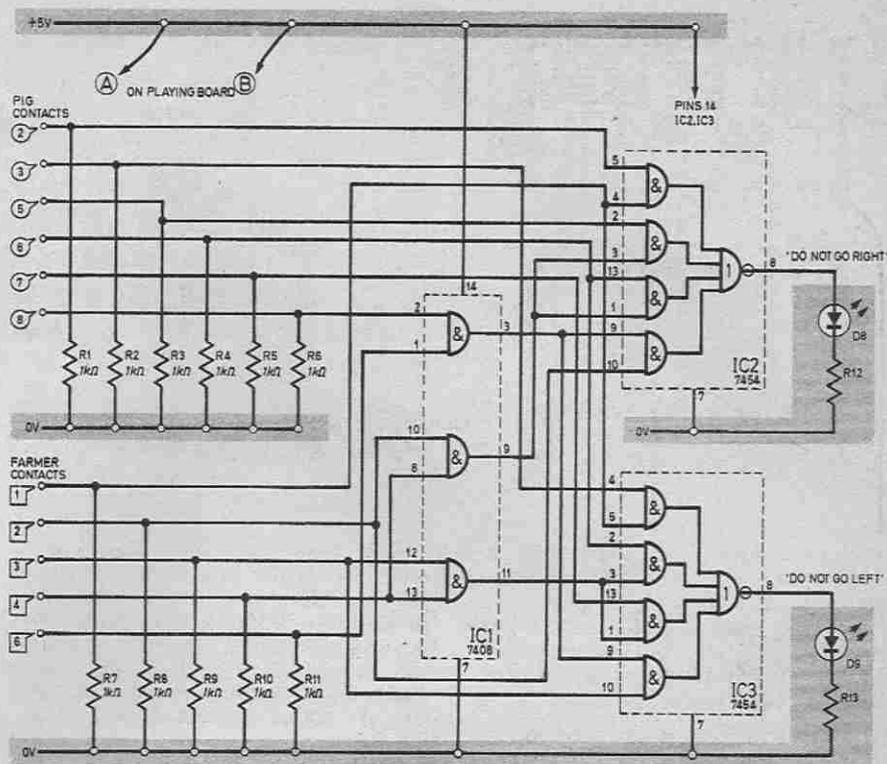


Fig. 9.4a. The circuit diagram for the Pig and Farmers game.

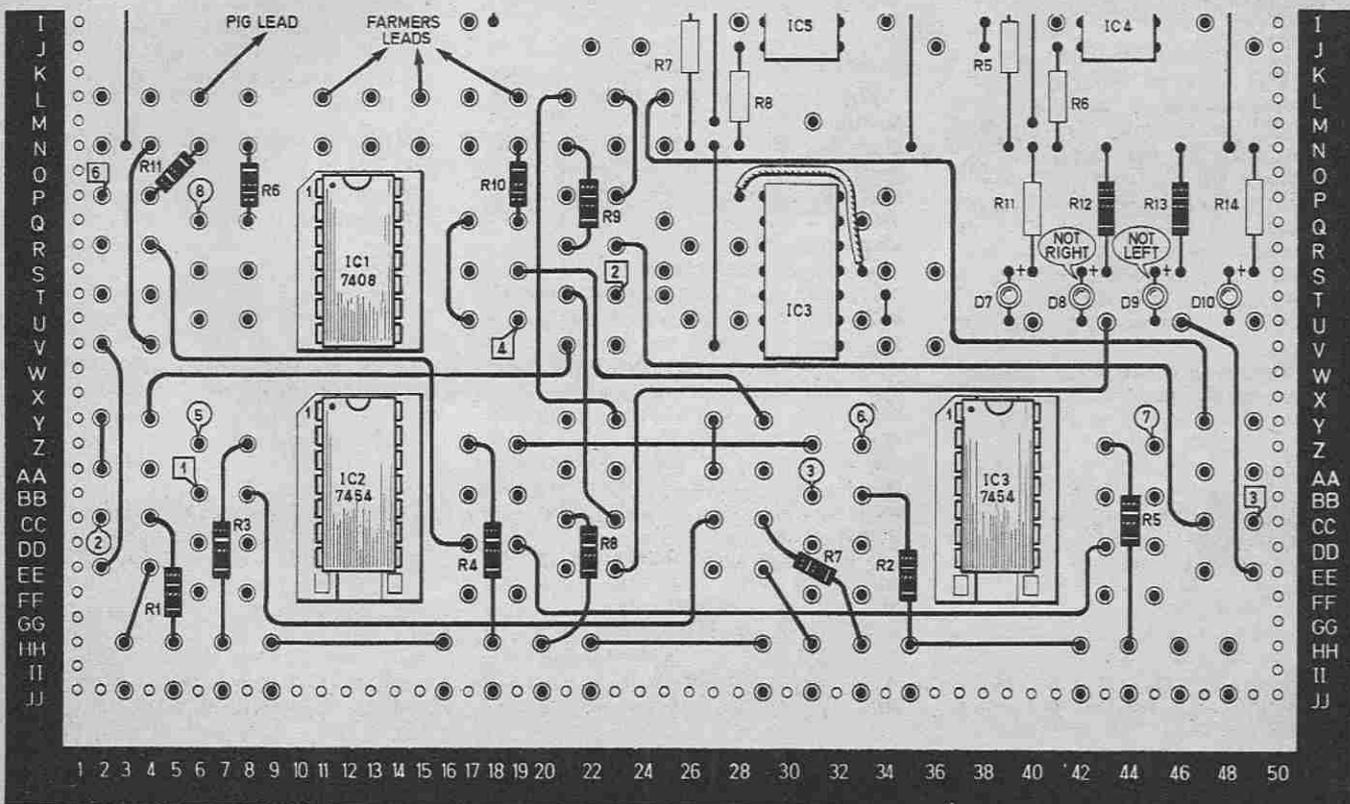


Fig. 9.4b. The circuit of Fig. 9.4a wired up on the Test-Bed.

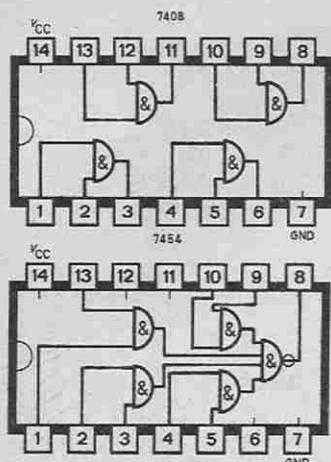


Fig. 9.5. Pinning details for the 7408 and 7454 logic i.c.s.

how we use it in the game.

The AND-OR-NOT gate needs high inputs to activate it, and most of these come directly from the contacts on the playing board. The contacts are normally held low by the grounded resistors, R1-R11, but any given input becomes high when contacted by a Pig or Farmer occupying that position on the board. To obtain the combinations of positions listed in the previous section, we use three AND gates in a 7408 i.c. (pin out details in Fig. 9.5).

The complete layout of the logic circuit on the Test Bed is given in Fig. 9.4(b).

When both members of any pair of inputs of the 7454 is made high, the output goes low and the l.e.d. is extinguished. Thus the normal state is for both l.e.d.s to be lit, and this is to be interpreted as a red warning "do not go left or right, but keep straight on if possible". If one l.e.d. goes out, this is interpreted as advice to move to that side, and a warning not to go to the opposite side.

## COMPUTER GAMES

The Pig and Farmer circuit is designed for that game and for no other. The circuit has fixed wiring so connected as to maximise the Pig's chance of victory. The wiring is in effect part of the programming.

Note also that *immediately* contacts are made, the circuit indicates the recommended move (ignoring propagation delays in the gates). This scheme is different from that found in most computer games. The computer and microprocessor are extremely complex *general-purpose* logic circuits, not dedicated to any particular game.

The logic of the game exists not in the way gates are connected together,

but in the program stored in memory. A memory programmed to play Pig and Farmers would instruct the microprocessor to scan the contacts regularly and very frequently to find out and record which positions were occupied. The program would then cause the inputs from occupied positions to be ANDed, and the resulting outputs ORed, then inverted. But the difference is that in our circuit we have an AND gate an OR gate and an INVERT gate for each logical operation.

In the microprocessor or computer the ANDING and other logical operations are all done by one special part of the device, the arithmetic and logic unit (ALU) which is used over and over again for each operation. Results of one operation are stored temporarily in memory, and recalled for the next operation. Thus analysis of the state of play involves a sequence of operations and at the end of perhaps a hundred steps the final output is used to control the indicator l.e.d.s.

Although microprocessors are very much in fashion these days, there are still many instances when their great flexibility and versatility are of no particular advantage, and the logical operations can be more cheaply and directly performed by a few simple logic i.c.s. **To be continued**



Talking recently to the managing director of one well-established purveyor of electronic components, he reminded me of the Credit, Deposit Account Scheme which he started some twelve years ago. The scheme is so good, that I think it deserves to be more widely known. Let me just say a brief word about it.

It had always been the directors dream, to provide facilities where it was possible for any customer to pick the phone up and say to their supplier "Please send ten of your XYZ capacitors" and get them, perhaps the next day. The problem he had to solve was this: he could not open up accounts for all and sundry, without the time consuming and irritating process of taking up references, for obvious reasons.

He finally solved it in a quite ingenious way. He laid down that the customer made a deposit for half the amount of credit he required, that is to

say, if he wanted £10 credit, he deposited £5, and this obviated the need for any references, he just signed a simple form and he, (the customer) was in business. To make the scheme more attractive he supplied all account customers with prepaid envelopes.

He even went to the lengths of promoting an advertising campaign, called "Shopper A" and "Shopper B". Shopper "A" trudging from shop to shop, and likely to die of exposure and shopper "B", by the fire, with his feet up, buttered toast in one hand and the telephone in the other, completing the same exercise in comfort. He tells me that he has over 1200 customers who use this method of purchase and he is surprised that the idea has not been adopted by other component retailers. With a scheme like that, who needs a counter service.

When I was a humble service engineer, my wages were such that I never expected to own anything more lux-

urious than a second hand push bike. Today, if the charges are anything to go by, I would expect a service engineer to call on me in a chauffeur driven Rolls. This was forcibly brought to my attention the other day when one of our electronic calculators went wrong.

As it will do almost any calculation and give you a print out, it is invaluable and I was anxious to get it back into service as soon as possible. I telephoned to the makers, who asked "Have you a maintenance contract?" When I answered in the negative, they informed me that their terms are £21 for the first half hour and £12 for each subsequent half hour.


It seemed to me that the minimum bill would be £33. If these charges cannot be justified, and I am sure they cannot, one wonders if it is done to encourage customers to buy a new machine. Perhaps the manufacturers argue if it lasts too long, then they will not, so let's kill it off by making repair charges impossibly high.

I am reminded of course of one of the first electric light bulbs, made 75 years ago and still working in a Chicago Fire Station. The company, sad to report went bankrupt. To me, the moral of the story, is not that they should have made a less durable lamp, but, that they needed better communication. Just imagine a company today advertising a product that would last a lifetime, customers would fight to buy it and the company's factories would be working 24 hours a day for years to meet the demand.

# NEXT MONTH
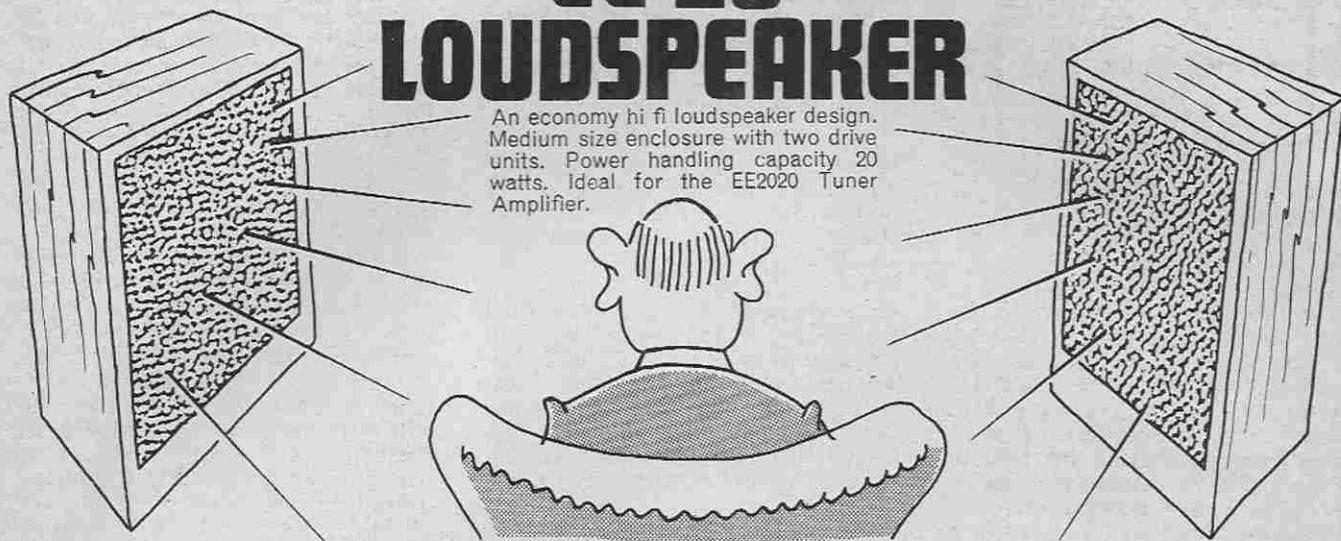
## EE 20 LOUDSPEAKER

An economy hi fi loudspeaker design. Medium size enclosure with two drive units. Power handling capacity 20 watts. Ideal for the EE2020 Tuner Amplifier.



## CONFERENCE TIMER

YOUTH CLUBS • COLLEGES • SOCIETIES • INSTITUTES • SCHOOLS • FETES

A lamp automatically lights when the speaker's preset time has expired. Has interrupt facility, presettable "wind-up" indicator and remote secondary indicator panel.

**WATER LEVEL  
INDICATOR**


**DARKROOM TIMER**

**2  
SIMPLE  
PROJECTS**

# Everyday ELECTRONICS

**JULY**  
ISSUE ON SALE  
FRIDAY, JUNE 15  
Price 45p

# LAB CENTRE

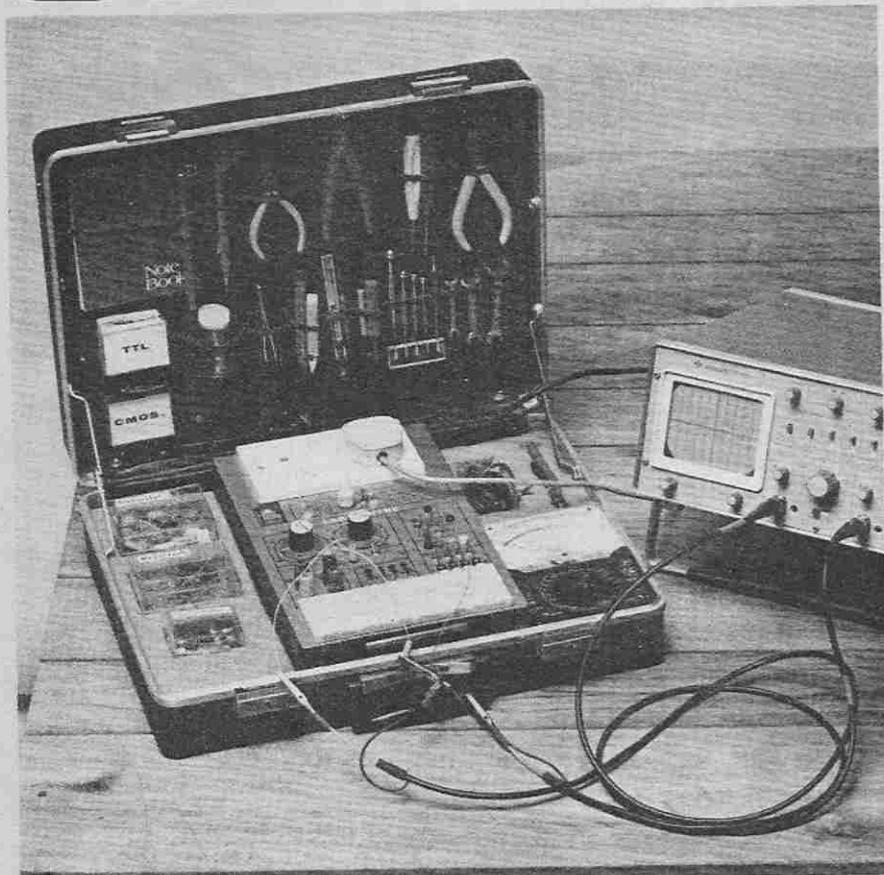

## PART 4

WITH the construction of Labcentre completed we can now move on to testing the various facilities which the system offers, and to the important task of setting up the function generator.

Most of the testing is straightforward and can be carried out using the other Labcentre circuits and a simple multimeter. The function generator is rather different because there are five potentiometers which can be used to coax the maximum performance from the circuit, and these must be adjusted with care to achieve the very best results.

Ideally, the setting up of the function generator should be carried out with the aid of an oscilloscope, but many constructors will not have

access to an oscilloscope, and so a simplified setting up procedure has been produced which will provide adequate results for most purposes.

A supply of jumper leads with 2mm plugs at each end should be made up to facilitate testing. These should be made up on several colours to avoid confusion, and will also be found useful during the use of Labcentre for experiments at a later date.

### TESTING LABCENTRE

If all wiring has been completed and thoroughly checked, a three-pin plug fitted with a 2 amp fuse can be fitted to the end of the mains cable and the power turned on. First, the 13 amp distribution sockets can be

checked by plugging in an appliance such as a table lamp and turning it on with the switches mounted adjacent to the sockets.

Please note that this is *not* a safety check, merely a final operational check. It is vital that the wiring to these sockets should have been very carefully checked before final assembly. A proper safety check can be carried out at this stage with the aid of a "Tester-Plug", of which there are several examples now available from electrical shops.

If the sockets are operational, the mains on/off switch can be set to on, at which point the neon-lamp within the rocker switch should illuminate to show that the mains supplies are now available to the Labcentre power supply circuits.

Using a multimeter set to an appropriate d.c. voltage range, the +5 volts +15 volt -15 volt supplies can now be checked at the front panel screw terminals, SK1 to SK4. Remember to check not only that the correct voltages are available, but also that they are wired up to the correct terminal, (+5V to yellow, +15V to red, -15V to black and 0V to green).

A further check of correct power supply operation can be carried out by shorting each supply in turn to the 0V terminal using the multimeter set to a 5 amp or greater d.c. current range. This test ensures that the current limiting circuitry within the regulator i.c.s is operating correctly.

Do not maintain the meter connections for more than a few seconds, as this could cause the regulators to get quite hot. If you wish to omit this test due to pure cowardice, you have my fullest sympathy! If, however, you do carry it out, the actual currents measured will vary depending on the type of regulators you have used.

Typically the 5V supply will limit at about 1 amp, and the 15V supplies will limit at about 750mA. The precise current is unimportant, but it is wise to recheck the voltages to make sure they have returned to their operational levels when the short circuit test has been completed.

### PUSH BUTTON PULSER

With complete confidence in the power supply circuitry now established, it is time to move on to the logic circuitry.

Set the CMOS/TTL switch to TTL and connect a multimeter set to the 20 volt range between the Q output of the push-button pulser and 0 volts. A reading of 0 volts should be obtained which changes to +5 volts when the button is depressed and back to 0 volts when released. Transfer the positive meter lead to the  $\bar{Q}$  output and check that it behaves in the opposite way to the Q output.

Now switch the CMOS/TTL switch to CMOS and recheck the pulser outputs.

This time they should swing between 0 volts and 15 volts as the button is operated. Switch back to TTL and connect the Q output to each of the l.e.d. inputs in turn using a jumper lead. Operation of the button should cause each l.e.d. to blink on and off. Try this again with the switch in the CMOS position, there should be no difference in l.e.d. operation.

Also, to test the four switches, you can wire one input of each uncommitted switch to the +5 volt supply and connect jumper leads from the other inputs to the l.e.d.s. Operation of each switch should control the appropriate l.e.d.

## FUNCTION GENERATOR

The function generator has to be set-up as well as tested, and this means that access to the five preset potentiometers and the circuit board will be required. The function of these presets is shown in Table 4.1.

With the circuit board accessible all five preset potentiometers should be set to mid travel (note that VR1 and VR3 are multi-turn components), before power is applied.

If no oscilloscope is available, access to the front panel will also be necessary so that the l.e.d.s and other facilities can be used to advantage to aid with the setting up process.

## LOW FREQUENCY

Connect the  $f$  and  $f/8$  outputs of the clock divider to convenient l.e.d.s using jumper leads, and set the function generator range switch to x10 and the frequency control to the counter-clockwise position. With these control settings the function generator frequency is required to be about 10Hz, and therefore the output of the  $f/8$  divider stage will be about 1.25Hz.

This is a low enough frequency to be directly observed on the l.e.d. and so the setting up procedure can begin with the adjustment of VR3 until an l.e.d. on period of about half a second is observed. With the low frequency roughly set, VR4 can be adjusted to obtain equal on and off times on the l.e.d. connected to the  $f$  divider output. This will be quite difficult to judge unfortunately, although it is worth spending some time to try to get it right because VR4 controls the half cycle duration ratio or "symmetry" of the sine and triangular waveforms as well as that of the square output.

If you do find this is too difficult to judge at the normal 10Hz low frequency limit, try readjusting VR3 to get the very lowest frequency at which the 8038 still oscillates before adjusting VR4 for equal on and off times. But remember you must watch the  $f$  output, not the  $f/8$ , which will always have a symmetrical output due to the action of the binary counter stages.

When you are satisfied with the on-off ratios of the  $f$  waveform, readjust VR3 while watching the  $f/8$  l.e.d. to set the lowest frequency to about 10Hz; l.e.d. on periods of from a half to 1 second will be quite satisfactory in view of the lack of precise dial calibration. The Labcentre function generator is not, after all, meant to provide an absolute calibration standard, but can claim to be a flexible tool for experimentation and design.

With the low frequency setting of the function generator completed the other divider outputs of  $f/2$  and  $f/4$  can be checked out by connecting them in turn (or at the same time) to the l.e.d.s on the front panel.

When this has been carried out, the jumper leads can be removed from the dividers, the function generator "triangle/sine" S2 switch should be set to "sine" and the output voltage control should be set about one quarter clockwise, in readiness for the setting of the high frequency preset.

### CAUTION!

**Removal of the front panel exposes dangerous mains voltages. It is essential that power is turned off at the wall switch before removal, and that every precaution is taken to avoid contact with the mains wiring while adjustments are being made with the power applied. Failure to observe these precautions could result in electrocution.**

## HIGH FREQUENCY

Without the aid of an oscilloscope or frequency counter, the high frequency setting will have to be done by ear, and for this the audio amplifier is needed.

Set the function generator frequency dial (VR2) fully clockwise and connect a jumper from the red output socket (SK5) to the blue audio amplifier input socket SK13. (No earth connection is required.)

Turn the loudspeaker switch to the "on" position whereupon an audio tone should be heard from the speaker. Reduce the volume to a comfortable level using either the amplifier volume control or the function generator output level control and then adjust the VR1 preset to achieve a tone frequency of about 1kHz.

Most people can judge a 1kHz tone frequency fairly accurately, it being the *brrr* . . . and below the *see* . . . in about the *whee* . . . area! Those with musical inclinations will no doubt be able to use their skills (and their instruments) to good effect to facilitate the more accurate setting of this preset control.

Table 4.1. Preset Functions

Potentiometer	Function
VR1	Set high frequency
VR3	Set low frequency
VR4	Set mark/space symmetry
VR5	Set sine shape (+ve)
VR6	Set sine shape (-ve)

The setting-up process described above also takes care of the x1000 range, although of course the absolute frequencies achieved will depend upon the value of the capacitor C15.

The last two presets to be adjusted are VR5 and VR6 which control the action of the sine control and the action of the sine converter in the 8038.


The sine converter, you may remember, "whittles away" sharp corners of the triangular waveform which is produced across the capacitors C14 and C15 to produce a very good approximation to a sine waveform. The positive and negative half cycles of the sine waveform are tailored by individual transistor "trees", and the presets VR5 and VR6 are provided so that each half cycle can be separately adjusted.

Adjusting these presets for the best sine shape is difficult without an oscilloscope, but fortunately the range of adjustment is not large, and if you are unable to detect any difference by ear, the skeleton pots can be set to mid travel and left there.

With the function generator now set up, the Labcentre console is now ready for use and so the mains power can be turned off at the wall switch and the system reassembled.
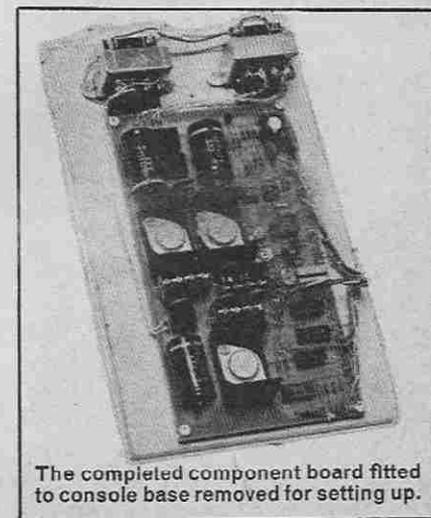
## FINISHING THE JOB

If you plan to invest in a briefcase for your Labcentre system, then you will no doubt wish to achieve a really professional looking finish. Careful attention to detail at this stage will allow you to produce a portable laboratory which is not only extremely



The completed component board fitted to console base removed for setting up.

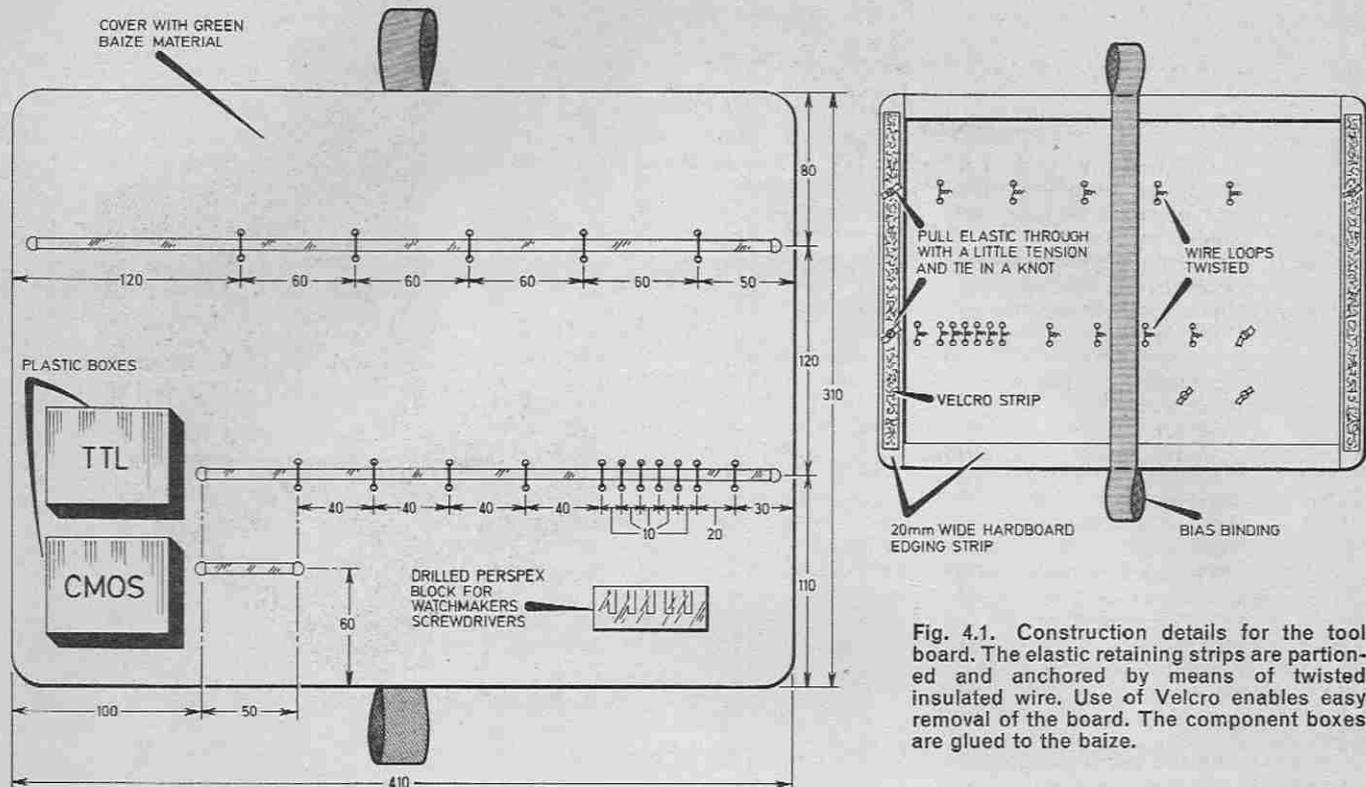


Fig. 4.1. Construction details for the tool board. The elastic retaining strips are partitioned and anchored by means of twisted insulated wire. Use of Velcro enables easy removal of the board. The component boxes are glued to the baize.

practical, but also attractive enough to be the envy of all your friends!

After fitting the console, it is necessary to take stock of what other items need to be carried in the Labcentre case. The most useful accessory is an analogue multimeter, and no doubt many constructors will already possess one of these. Those who haven't will find the small investment well worth it.

Other items which you may wish to use include: a logic probe, a signal injector or tracer, a digital multimeter or counter and perhaps even a calculator for those tricky design calculations!

When you have decided just what other test instruments are to go into the Labcentre case you should obtain a quantity of polyurethane foam and fit it around the central console using a hobby knife or razor blade to trim it to shape.

Cut-outs for the various accessories can also be made by careful application of the blade, and delicate items can also be given a foam "lid" to ensure their protection during the possible rough and tumble of the Labcentre existence.

In the prototype, the only extra equipment added was a multimeter, but a quantity of small plastic boxes were obtained and used to house components such as resistors, capacitors and semiconductors.

## TOOL BOARD

The final touch, and a very important one, is the tool board which fits in the lid of the case. The owners of

the prototype wanted to be able to remove the tool board and so it was mounted using Velcro strips. This allows the briefcase to be used for other purposes when necessary, and it can be useful to be able to move the tool board to the workbench when a constructional session is in full swing.

The construction of the toolboard is detailed in Fig. 4.1. The exact size may need to be changed to fit your own particular case design, and of course, everyone will have their own ideas about what tools are needed and so the drilling details for the anchor points may need modification.

The hardboard can be cut to size with a saw, or better still, one of the nibbling tools available for the purpose. The covering material used on the prototype was green baize, which gave a very businesslike finish.

Various other materials could be used, and another possibility would be to paint the hardboard, say, green, and then paint on the tool outlines in white so that you can see at a glance if any tool is missing.

The tools can be supported with elastic as shown, and the bias binding is added to make the removal of the board a simple process.




The prototype tool board removed from the lid of the briefcase for use on the construction bench.
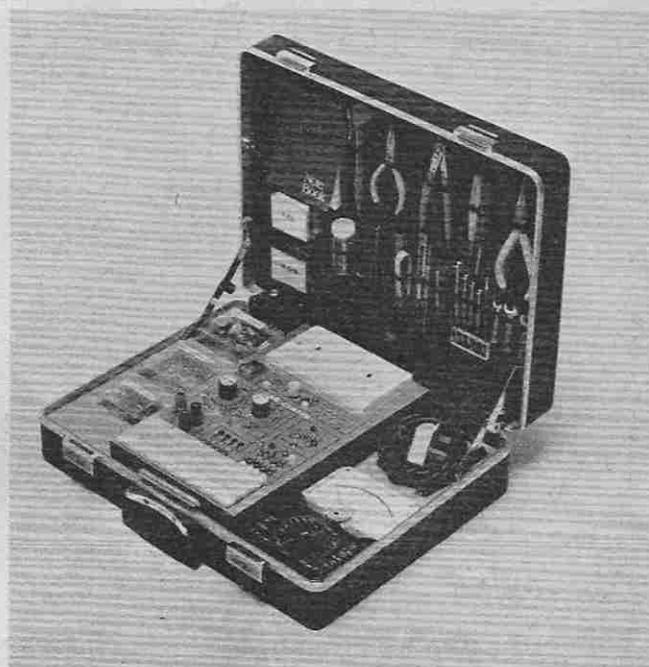
## SOME SUGGESTED TOOLS

Tools for use with Labcentre can be chosen from the following list to suit personal preferences:

- Solder sucker
- Soldering iron (miniature)
- Screwdrivers (various)
- Pliers (pointed nose)
- Wire cutters
- Wire Strippers
- Spanners (BA or metric)
- Modelling Knife
- Trimming Tools
- Spot face cutter (for stripboard)
- Terminal pin insertion tool
- Wiring Pen
- Wire Wrap Tool
- Heat Shunt
- Wire Bending Gauge
- I.C. Insertion Tool
- I.C. Extractor Tool
- Small files
- Contact burnisher
- Tweezers



## USING THE LABCENTRE


There is no set procedure for using Labcentre, everyone will have their own ideas on how to use it, and what to use it for. It can be used in many different fields, such as design, experimentation, tutoring and trouble shooting, and for all kinds of circuits including the digital and analogue variety. Most of the detailed uses for Labcentre haven't even been invented yet!

Despite this wide scope, a few operational guidelines may help.

## PRECAUTIONS

1. To ensure circuit safety, *always* turn off the mains switch while making interconnections.
2. Be sure to check the position of the CMOS/TTL switch before using the pulser or divider outputs. Remember, the CMOS position will damage TTL and CMOS circuits powered from 5V rails.
3. Be careful not to short the pulser, divider, or function generator outputs to any of the supply rails as this can result in ruined i.c.s.
4. Do try and avoid power supply short circuits. The regulators are short circuit protected to 0 volts but extended shorts could cause overheating. Short circuits between power rails could destroy the regulators.
5. *Never* try to wire up any circuits on the breadboard which use mains or other high voltages.

Fig. 4.2. Using a Zener diode and series current limit resistor to provide intermediate voltage levels: (a) positive (b) negative with respect to 0V.

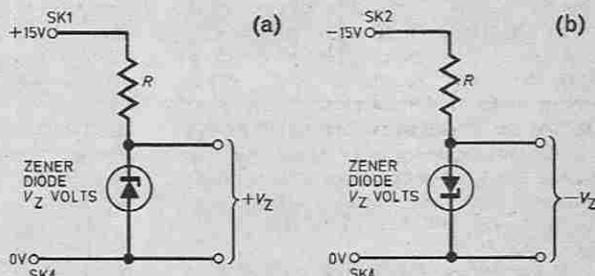


## OPERATING TIPS

1. Use insulated, solid, tinned copper wire of about 24 s.w.g. for breadboard wiring. Using wires with different insulation colours for different types of signal can make life a lot easier.
2. Keep breadboard wiring neat and don't let a birdsnest situation develop. Tidy wiring reduces stray capacitance and helps to avoid short circuits.
3. Most breadboard sockets come complete with power bus lines at top and bottom. Using these bus lines for power distribution is very desirable. Power coupling can be achieved between each supply rail and 0 volts by using an appropriate combination of electrolytic and ceramic capacitors. This is particularly necessary for high speed logic circuitry.
4. When connecting the function generator output to the breadboard it is advisable to carry the earth connection through on a separate wire, even though the function generator earth is connected to 0 volts internally. The two wires from the function generator can be formed into a "twisted pair" to reduce radiation.

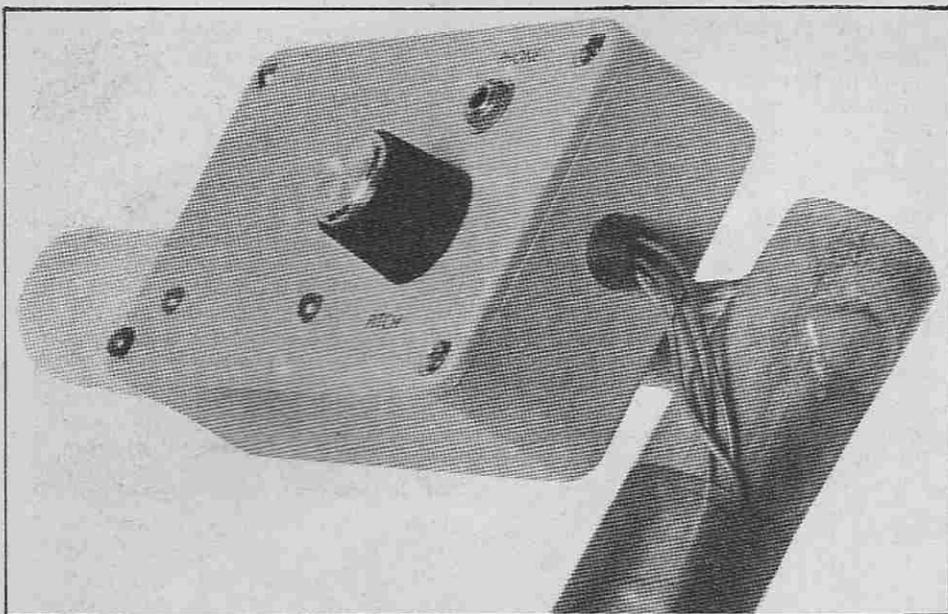5. Voltage rails between 5 and 15 volts can be generated with a Zener diode and a resistor as shown in Fig. 4.2. The resistor should be chosen so that the voltage drop across it is equal to  $(15 - V_z)V$  at the maximum load current of your circuit, where  $V_z$  is the Zener voltage. To get a useful output current range, 1 watt Zener diodes are best for general use.





# LOW COST METAL LOCATOR

By R. A. Penfold

**T**HE MAIN design requirement for this metal locator was for the most simple and inexpensive unit that would give a good level of performance.

A beat frequency oscillator (b.f.o.) type circuit is used, and this is based on a single inexpensive CMOS i.c. and very few passive components. The performance of the unit is very much in line with that of other simple locators with small coins; 1/2p, 1p, or similar are detectable at depths of up to approximately 25mm, and larger coins such as 2p, 10p and 50p pieces detectable at depths of up to about 50 or 80mm. Large pieces of metal can be detected at depths in excess of 300mm.

The unit is self-contained apart from the crystal earpiece which is used to provide the output tone. The presence of metal is indicated by a small change in the pitch of this tone.

## B.F.O. PRINCIPLE

This type of locator uses an inductive/capacitive (LC) type oscillator as the basis of the unit. The frequency at which the oscillator operates is dependent upon both the value of the inductor and

the capacitor used in the tuned circuit, and a change in either will result in a change in operating frequency. The inductor is a large air-core type and it is usually termed the search coil.

## FREQUENCY SHIFT

If a piece of metal is brought close to the search coil it will cause a change in its inductance, and hence also a change in the operating frequency of the oscillator. The problem with this system is that the frequency shift produced will usually be only about 0.1 per cent or less, and is too small for the human hearing mechanism to readily perceive.

This is overcome by using the b.f.o. principle which is outlined in Fig. 1. Here the output from the oscillator is fed to one input of a circuit known as a product detector. The other input of the product detector is fed from a second oscillator which is termed a beat frequency oscillator. The output from the product detector will contain a number of frequencies, most of which are filtered out by an r.f. filter leaving just the difference frequency which is fed to the earpiece.

In practice the search oscillator operates at quite a high frequency, and this design employs a nominal frequency of 125kHz. The b.f.o. is adjusted to a frequency just above or below the search oscillator frequency so that the difference frequency at the output of the product detector is a low audio one, which will be reproduced by the earpiece.

If a piece of metal is brought close to the search coil, causing a change in frequency by about 0.1 per cent, with a nominal operating frequency of 125kHz this represents a frequency shift of 125Hz (0.1 per cent of one thousandth of 125,000Hz = 125Hz). The difference in the frequency of the two oscillators will obviously change by this amount, causing the output tone from the earpiece to change by about 125Hz. Since the tone from the earpiece could have previously been less than 125Hz if desired, this shift in output frequency can produce a significant change in the output tone that will be readily apparent to the user.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the detector is given in Fig. 2. The only active component in the unit is a CMOS quad 2-input NOR gate. Although this is a logic i.c. it readily lends itself to use in this type of circuit.

Gates G1a and G1b of the i.c. are used as the b.f.o., and these are connected in a conventional CMOS astable or free running multivibrator circuit. This can be tuned several kilohertz either side of the search oscillator frequency by means of VR1.

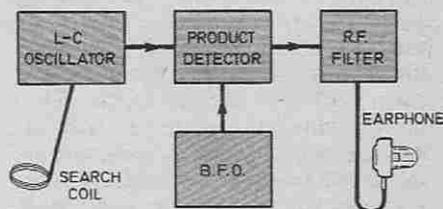


Fig. 1. Principle of the beat frequency oscillator circuit. Here two oscillators run at very nearly the same frequency thus producing an audible beat note in the earpiece. Any slight shift in the LC oscillator frequency will cause a change in the beat note heard. This change in frequency is caused by bringing a piece of metal in the vicinity of the search coil. This alters the inductance of the coil, thus changing the frequency of the tuned circuit.

Conventionally an LC oscillator is used as the b.f.o., but this is comparatively expensive due to the need for an inductor and a variable capacitor. This CR alternative seems to work perfectly well and give good stability provided it is operated from a stabilised supply. The unit is therefore powered from a simple Zener shunt stabiliser circuit formed by R5 and D1.

Gate G1d is used as the basis for the search oscillator and this uses a rather unusual configuration. The two inputs of the gate are connected together so that it functions as an inverter. Search coil L1 then biases the inverter to act as an amplifier. The series capacitance of C4 and C5 acts as the

unusual configuration. The output from the b.f.o. is coupled to one input of G1c via R2, and the output from the search oscillator is coupled to the other input by way of R3. The output from a NOR gate will be high, virtually equal to the positive supply voltage if both inputs are low, almost at the negative supply voltage. Any other combination of input states will produce a low output state.

Therefore, an input from the search oscillator as in Fig. 3a and a slightly higher frequency from the b.f.o. as in Fig. 3b would produce the output waveform of Fig 3c. If this output is then passed through a suitable r.f. filter so that the rapid changes in the signal are smoothed out and the pulses are

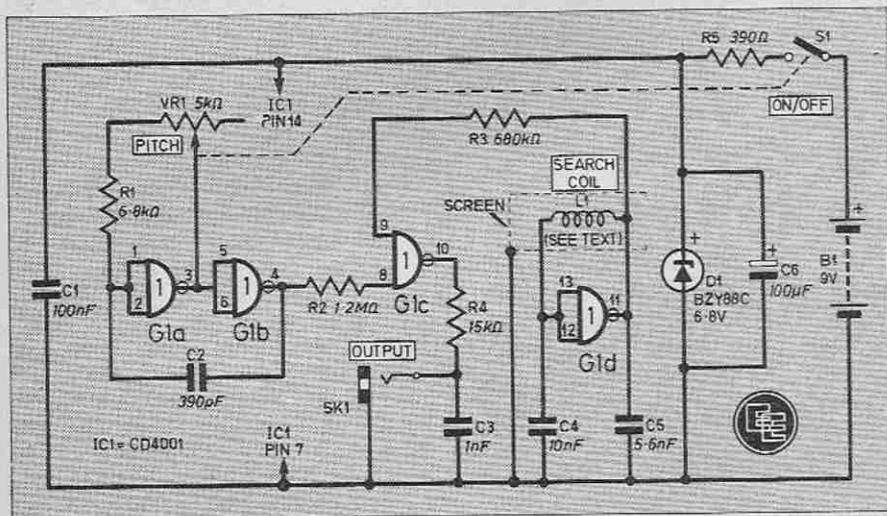


Fig. 2. Complete circuit diagram of the Metal Locator.

capacitive part of the tuned circuit and the junction of these two acts as an earthed tapping.

This produces a phase inversion through the tuned circuit at its resonant frequency, which with the inversion through the amplifier results in positive feedback and oscillation at the resonant frequency of the tuned circuit. This has a nominal frequency of 125kHz, and the prototype had a measured operating frequency of 123.86kHz.

There will be minor variations between various units built to this design, but provided the correct components are used and the search coil is constructed exactly as described, the unit will operate well within the permitted frequency band used for metal locators.

Gate G1c is used as the product detector, and again this is a rather

integrated to produce a sort of averaging of the output level, a waveform something like that of Fig. 3c will be obtained. This final signal is the required difference signal, as is demonstrated by the fact that the total number of pulses in a and b equals the number of pulses in c.

#### R.F. FILTER

Resistor R4 and C3 are the r.f. filter network. The inputs to G1c are coupled via high value resistors rather than directly as it is advisable to use a very loose coupling here. With a tighter coupling there is a tendency for the two oscillators to lock onto the same frequency even when they should be a few hundred cycles apart. This would make the unit difficult to use and insensitive. The use of

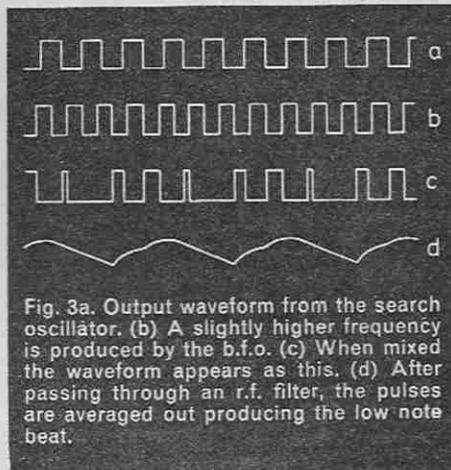


Fig. 3a. Output waveform from the search oscillator. (b) A slightly higher frequency is produced by the b.f.o. (c) When mixed the waveform appears as this. (d) After passing through an r.f. filter, the pulses are averaged out producing the low note beat.

loose couplings and supply decoupling capacitors C1 and C6 virtually eliminates this effect, and the oscillators have to be within a very few cycles of each other's frequency before locking will occur.

Switch S1 is an ordinary ON/OFF switch and is ganged with VR1. The unit has a current consumption of about 5.5mA which gives many hours of operation from a PP3 battery.




# CONSTRUCTION starts here

## COMPONENT BOARD

All the small components are assembled on a piece of 0.1 inch matrix stripboard using the component layout given in Fig. 4. The board has 16 strips by 24 holes and is cut down from a larger piece using a hacksaw.

The two 3.2mm diameter mounting holes and the breaks in the copper strips are then made, after which all the components and link wires are soldered into place.

The i.c. is a CMOS device and will be supplied in some form of protective packaging to prevent damage due to high static voltages. This should be the last component to be soldered into circuit and it should not be removed from the packaging until then. It is advisable to use a soldering iron having an earthed bit when connecting this device. A socket could be used for the i.c., but due to the low cost of the device this is probably not justified.

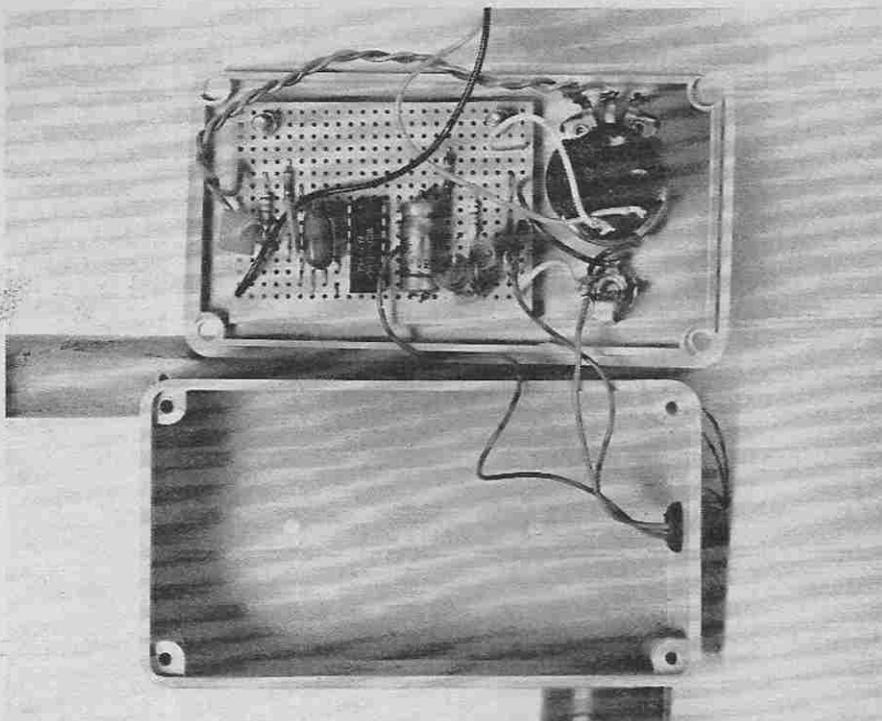

The case is a small plastic box which measures about 111 x 60 x 27mm, and VR1 and the output socket are mounted at one end of the lid. This leaves sufficient room for the completed component panel to be mounted on the lid using two short 6BA screws.

It is advisable to earth the body of VR1 to the negative supply rail of the unit, as otherwise a slight hand capacity effect will make precise tuning of the unit a little difficult. This earthing can be accomplished by looping the bare end of a short insulated wire around the mounting bush of VR1 when it is being mounted. This lead will then be trapped against the body of VR1, and the free end of the lead can be earthed to the appropriate tag of SK1.

## COMPONENTS

### Resistors

- R1 6.8k $\Omega$
- R2 1.2M $\Omega$
- R3 680k $\Omega$
- R4 15k $\Omega$

All are  $\frac{1}{4}$ W carbon  $\pm 5\%$

### Capacitors

- C1 100nF polyester
- C2 390pF ceramic plate  $\pm 5\%$  or better
- C3 1nF ceramic plate
- C4 10nF polystyrene  $\pm 5\%$  or better
- C5 5.6nF polystyrene  $\pm 5\%$  or better
- C6 100 $\mu$ F 10V elect.

### Potentiometer

- VR1/S1 5k $\Omega$  Lin. carbon with double-pole switch

### Semiconductors

- IC1 CD4001 Quad 2-input NOR gate
- D1 BZY88C6V8 6.8V 400mW Zener diode

### Miscellaneous

- B1 9V PP3 battery
- L1 35 turns 10/0.1mm wire (see text)
- SK1 3.5mm jack socket

Stripboard, 0.1 inch matrix 16 strips by 24 holes; small plastic box, 111 x 60 x 27mm or similar; battery connector to suit B1; small round control knob; crystal earpiece with 3.5mm plug; connecting wire.

Materials for framework; (see text), 800 x 25mm dowel (broomstick or similar), 250 x 15mm dowel, hardboard or thin plywood 200 x 180mm (2 off) insulating tape, bicycle handgrip, aluminium foil if required.

See  
**Shop  
Talk**

page 333

## SEARCH COIL

To make the search coil a temporary coil former having a perimeter or circumference of 508mm is required. The author used a 152 x 102mm chassis that was at hand, but a suitable former can easily be constructed from wooden battens if no ready made alternative is available.

The winding consists of 35 turns of 10/0.1mm p.v.c. insulated wire wound fairly tightly around the former (but not so tightly that it will be difficult to remove the coil) with leadout wires one metre long. Four bands of insulation tape are used to hold the winding together so that it can be removed from the former.

These initial steps of the search coil construction are illustrated in Fig. 5.

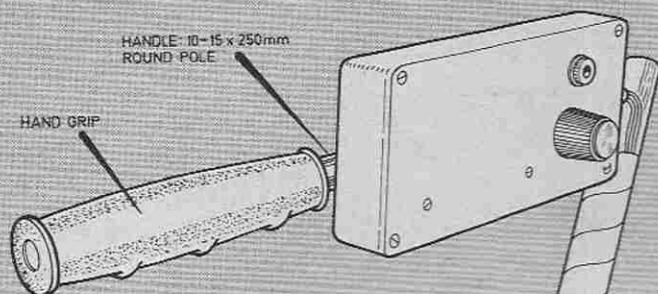


Fig. 6. Constructional details for the framework as used on the prototype. Dimensions are not critical and if required can be varied to suit individual requirements.

# LOW COST METAL LOCATOR


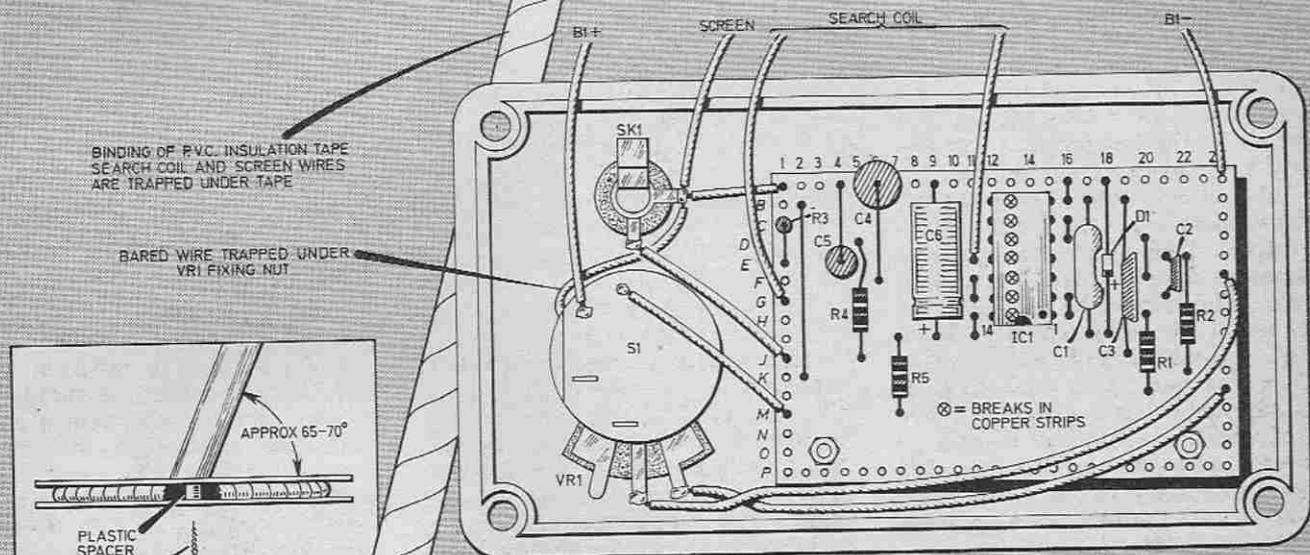


Fig. 4. Stripboard layout also showing connections to VR1 and the output socket. The board is mounted on the lid of the case using short 6BA screws.

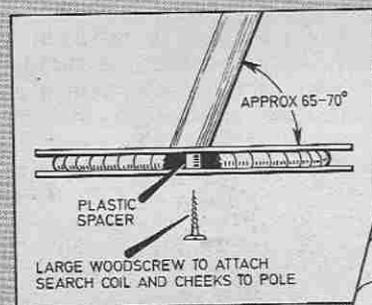

LARGE WOODSCREW TO ATTACH SEARCH COIL AND CHEEKS TO POLE

APPROX 65-70°

PLASTIC SPACER

SQUARE OR ROUND POLE APPROX 25 x 800mm

SCREEN

SCREEN (ALUMINIUM FOIL)

INSULATION TAPE WRAPPED ROUND COIL

HARDBOARD OR THIN PLYWOOD 200 x 180mm


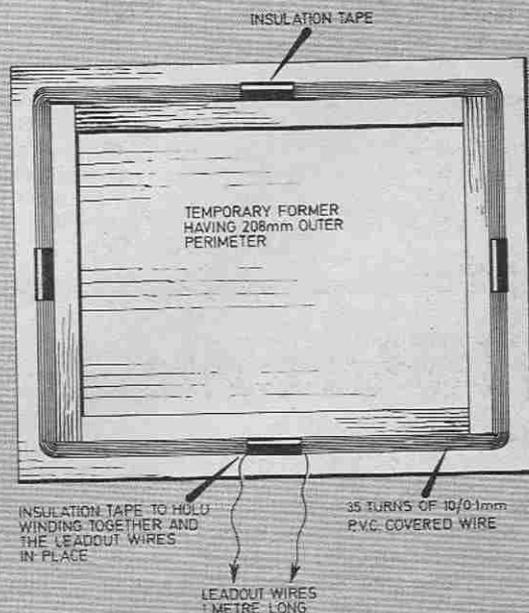


Fig. 5. Construction details for the coil. About 15 metres of wire is required. If a shield is required it should be fitted at this stage.

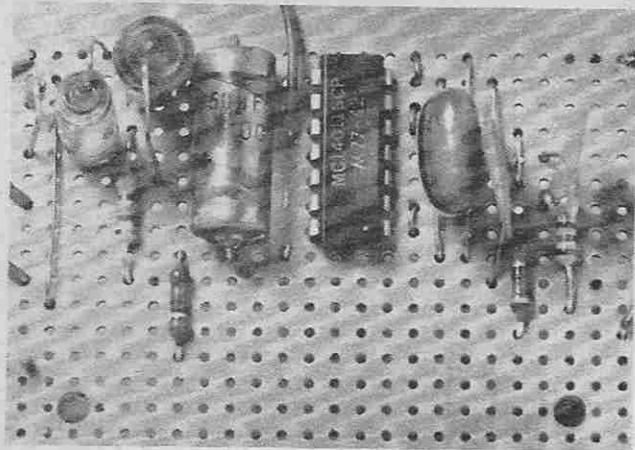

Layout of components on the completed circuit board for the Low Cost Metal Locator.

## SHIELD

The search coil is formed into an oval shape about 180 x 150mm, and it is then a good idea to fit it with a shield. This is not essential, but without a shield there will be a small change in the output frequency when the search coil is placed close to the ground, even in the absence of any metal there. This would make the unit more difficult to use with a consequent indirect loss of performance.

A shield can simply consist of strips of aluminium cooking foil used to completely cover the coil, except over the band of insulation tape at the point where the two leadout wires emerge from the coil.

A lead about one metre long must be attached to the shield so that it can be earthed to the negative supply. This can be achieved by baring about 40mm at one end of a p.v.c. multistrand lead one metre or so long. The bare wires are twisted together, heavily tinned with solder, and then tightly wound around the shield close to where the two leadout wires emerge from the coil.

To complete the search coil it is tightly bound with a layer of insulation tape to hold the whole assembly together.

## FRAMEWORK

Details of the wooden framework used on the prototype locator are provided in Fig. 6. This can of course be altered slightly to suit the particular materials to hand or locally available, but make sure that the search coil is held very firmly in place and that

its leadout wires are not allowed to simply flap around.

Strong, rigid construction is essential, or as the detector is moved around there will be small changes in the output frequency without any metal in the vicinity of the search coil.

The main part of the case is screwed to the handle part of the framework using a couple of small woodscrews. A hole is drilled in the side of the case near to the upright pole to provide an access point for the leadout wires from the search coil and shield (if fitted). The final wiring of the unit can then be completed. The lead from the shield connects to the earthed tag of SK1.

It is a good idea to fit a handle-bar grip (as sold by cycle shops) over the end of the handle. The handle will almost certainly be too small in diameter for the grip to be a good tight fit over the end, but this can be rectified by using some bands of insulation tape around the end of the handle.

## IN USE


With a crystal earpiece plugged into SK1 and the unit switched on,

### OPERATING LICENCE

Under the terms of the Wireless Telegraphy Act 1949, a licence is required to operate this Metal Locator in the UK. The unit has been designed to operate on a frequency of 125kHz, as such the design should not be altered. Applications for a licence should be made to the Home Office, Waterloo Bridge House, Waterloo Road, London SE1.

by adjusting VR1 (PITCH) it should be possible to produce a strong audio tone from the earpiece. It is likely that it will be possible to produce an output tone at virtually any setting of VR1, but most of these signals are weak spurious ones, and it will be obvious when the main response has been found due to the far higher output volume.

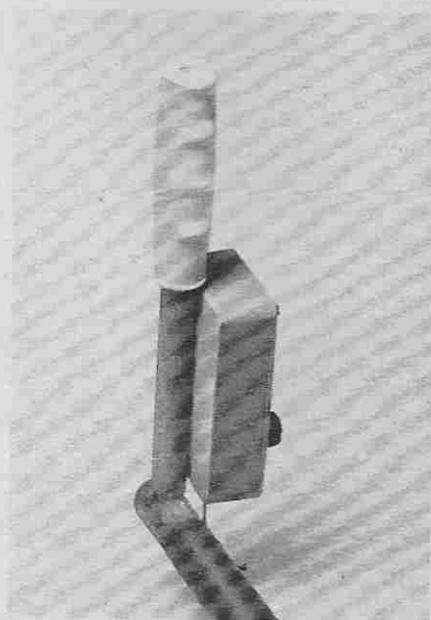The variable resistor VR1 will control the pitch of the output tone, and if this is adjusted for the lowest possible tone, the two oscillators should lock to the same frequency, producing a null in the output. In use VR1 is just slightly offset from this setting so that a very low pitched tone is produced.



Positioning of the circuit case and the handle grip.

A very low output note will provide the best sensitivity since, for example, a frequency shift of 10Hz is quite significant on a 20Hz signal, but would probably not be perceptible on a signal at a frequency of, say, 2kHz.

With VR1 set one side of the null point it will be found that the presence of most types of metal produces a reduction in the output tone, whereas an increase in the tone will usually occur if it is offset in the other direction.

Sensitivity is best if it is adjusted so that a reduction in the output pitch is provided, as a small reduction in the pitch of a tone is a little more easily detected than a similar increase in pitch. □

# MINI-MODULES By George Hylton

## .... in combination

So far in this series, a number of audio modules have appeared. We thought it might be a good idea to demonstrate how these can be connected together and used in combination.

The **Audio Effects Oscillator** (November 1978, p. 818) is a good starting point because it forms a handy source of signals. It can be used in conjunction with the **Audio Modulators** (February 1979, p. 86) to manipulate the signal from some other audio source such as a radio tuner or the output of the **Microphone Amplifier** (December 1978, p. 862).

Several signals can be mixed and faded in or out with the help of the **Passive Mixer** (October 1978, p. 746). And, of course, for more ambitious setups you can build more modules and add them to your system.

If you don't want to be stuck with battery power, the **Versatile Power Supply** (March 1979, p. 157) enables them all to be worked off the mains.

This really exhausts the ostensibly audio modules, but if you happen to have built the **Meter Amplifier** (this issue) it can be pressed into service as a low-power monitor amplifier for driving a high-impedance speaker (though its quality of reproduction is poor) and even the **Continuity Tester** (January 1979, p. 24) could be operated as a second variable frequency audio source!

One important general point is that none of the audio modules produces any appreciable output power. They are designed for use in conjunction with a normal audio chain consisting of a power amplifier with its own power supply unit and preferably its own tone controls because these are always a useful adjunct to a sound effects "kitchen" where weird noises have to be cooked up.

### DRAMATIC EFFECTS

The Audio Effects Oscillator in its original form has a frequency control, an output level control and an input terminal for applying a modulating voltage if required. The modulation facility is optional and the oscillator can be used as a straightforward tone source.

It is very useful to build two oscillators, one for frequencies in the speech and music range and the other for very low frequencies. In my original article I suggested a range of 1-30Hz for the v.l.f. version. This, with suitable application of tone controls, can produce passable imitations of clocks ticking, hearts beating and similar repetitive noises.

The other, higher-frequency oscillator can be used on its own to make whistles

and lower tones. Switched on and off it can give "time pips" or "morse code".

When modulated by the v.l.f. oscillator it can produce quite a good imitation of a two-note police siren. The quality of the modulated output varies with the amount of modulation voltage. A few tenths of a volt produces continuously varying pitch. A volt or so produced on-off modulation; interrupted bursts of tone.

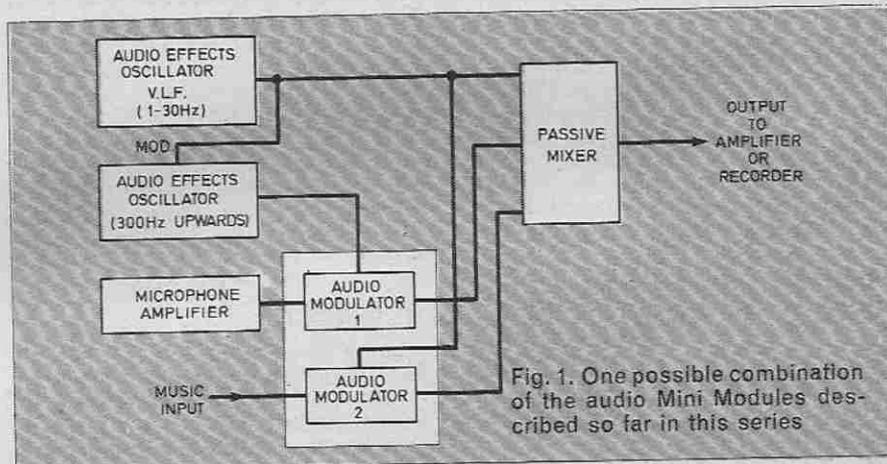


Fig. 1. One possible combination of the audio Mini Modules described so far in this series

Using a pair of effects oscillators (one v.l.f., the other audio) you can equip yourself to make tape recordings of stories or plays with at least some of the sounds needed for dramatic effects. You can, with the aid of a gram deck and the mixer, bring in background music as well. In no time at all you can be your own radio programme producer!

### INTERCONNECTIONS

The most versatile means of interconnecting the various modules is old-fashioned flexible leads with crocodile clips at each end. With these you can connect anything to anything and see what happens. The snag is that you can

easily get into a muddle, with leads going in all directions, so for any sort of permanent or semi-permanent installation it may be preferable to settle for a fixed arrangement whose facilities though limited are quickly got used to. Building an extra Passive Mixer will enable a fair degree of flexibility to be preserved.

A possible arrangement is shown in Fig. 1 (but it must be stressed that the user is at liberty to make any interconnections he likes and that this one is merely for the purposes of illustration). Here the v.l.f. oscillator output is tied permanently to the audio oscillator's modulation input. The audio oscillator can still be used unmodulated, however, by turning down the v.l.f. output.

The output of the microphone amplifier is taken to one of the modulators. Modulating speech with a very low frequency can produce "Dalek" type sounds. Modulating with a high frequency produces odd sounding distortions. Modulating with both at once... well, why don't you try it and see!

Connecting the audio oscillator via a slide switch is useful for producing morse-code-like sounds. Choose a switch which can be operated quickly and silently.

Modulating music (from a radio, tape deck or gramophone playback unit) at v.l.f. produces a tremolo effect.

No doubt readers will develop their own tricks for making use of these audio modules. If you hit on something useful, please tell us about it!



## at THE GREAT BRITISH Electronics Bazaar

ALEXANDRA PALACE, LONDON N22. 28-30 JUNE 1979  
YOU WILL FIND US RIGHT IN THE CENTRE OF THE GREAT HALL ON  
STAND NUMBER 163

EDUCATIONAL SEMINARS


O. N. Bishop, author of "Doing It Digitally" will deliver the EE lecture/demonstration *Getting Started In Electronics Construction* daily.

# mini~MODULES By George Hylton

Handy "Beginner" projects based on simple circuits and featuring a variety of building methods.

## 8

# METER AMPLIFIER

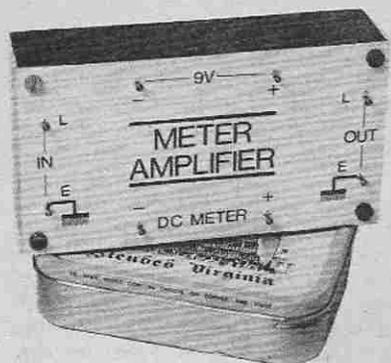

MANY otherwise very good multi-meters fall down rather badly when it comes to measuring small a.c. voltages. I have an excellent general purpose multimeter, for example, which in theory will measure down to 1 volt a.c. full-scale. Unfortunately, on this 1V a.c. range its internal resistance is a mere 300 ohms or so; this is so low that in many situations accurate measurement is impossible because the meter's impedance loads the circuit to which it is connected so much that the voltage I'm trying to measure falls.

Another problem is that a good many of the audio voltages one would like to measure are 100mV or less and a 1-volt a.c. range cannot measure them accurately.

An answer to this problem is to provide the meter with a pre-amplifier which does three jobs.

Firstly, it amplifies by some convenient small amount such as 10 times, which is enough to convert the meter 1V range to a 0.1V (100mV) range.

Secondly, it has a high enough input impedance (in the present circuit about 90 kilohms) to avoid serious loading of the majority of sources of audio signals.

Thirdly, it has the ability to supply large enough output currents at a low enough impedance to drive the meter.

The amplifier in this Mini Module does all this but can do more besides.

In addition to driving an a.c. voltmeter it can also act as a self-rectifying circuit to drive a d.c. meter with a current proportional to the a.c. input voltage. In this way almost any standard d.c. milliammeter or microammeter can be turned into a sensitive a.f. voltmeter with a full-scale deflection of around 100mV r.m.s.

The same d.c. meter can also be converted into a linear frequency meter or a capacitance meter with the aid of an external audio oscillator, which need not be accurately calibrated.

### THE CIRCUIT

The circuit consists of an operational amplifier in i.c. form (which provides the required gain) and a complementary class B output stage (which provides the output current). Negative feedback (via R5 and R4 in Fig. 1) sets the gain and removes most of the distortion of the unbiased output pair TR1, TR2.

With the values of R5 and R4 shown the gain is 11. This is a very useful gain when a d.c. meter is used for a.c. voltage measurement because it corrects for a cause of error which would make the meter "read low".

For use as a pre-amplifier for an a.c. meter however a gain of exactly 10 is needed and can be arranged by increasing R4 to 11 kilohms (for example, two 22 kilohms in parallel) or by connecting 1 megohm across R5.

### CONSTRUCTION

The prototype is housed in an electrician's metal switch box of the type designed to hold two standard sized square light switches. These are the boxes ("patresses") which are often buried in house walls to take flush-mounting switches.

The older kinds, designed for deeper switches than the modern "plaster depth" switches are more useful for electronics construction and are still obtainable. The box I used measures 130 x 70 x 32mm deep but anything similar should be usable.

The front panel is a piece of Formica and to the back of this is glued the circuit board, which in this case is a piece of plywood. This was converted into a component board by tracing the layout diagram and sticking it to the plywood, then inserting pins at every junction to act as solder tags.

Miniature household pins were used, of the kind known to stationers as "lills". These are about 15mm long and can be inserted with pliers. They are pushed right in until they hit the Formica.

For lead-through connections I used coppered hardboard pins. To avoid damage to the panel and base, holes were drilled for the pins, just large enough to enable them to be pushed through. They were then locked in place by applying a "collar" of solder where they emerged on either side.

It seemed hardly worth providing an internal battery for a piece of equipment which may only occasionally be needed so the 9V supply was also terminated on pins to enable an external battery to be connected.


The component layout (Fig. 2) is not critical and may be altered to suit some other shape and size of container.

### USING THE AMPLIFIER

#### (1) As a Meter Pre-amp

For use as a "x10" meter pre-amp the a.c. voltmeter is connected to the output terminals. The gain is set to 10 as described earlier, by adjusting R4 or R5. For gains other than 10 which may be needed for some meters, keep R5 at 100 kilohms but

Fig. 1. Circuit diagram of the meter amplifier

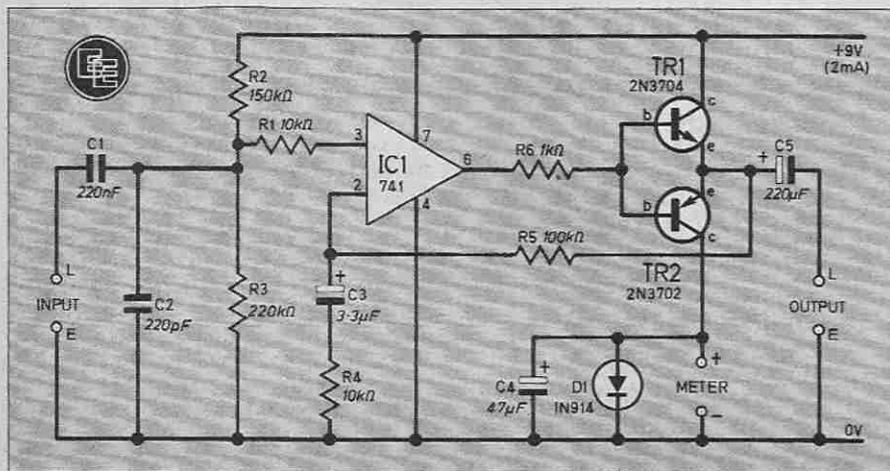

use a new value for R4, calculated from:  $R4 \text{ (new)} = 100 \text{ kilohms} (A - 1)$  where  $A$  is the required gain.

This formula should work for gains up to about 100. Example: your a.c. meter has a range 0-300mV and you want to use the meter to convert this to 0-50mV. The gain required is  $300/50 = 6$  and the formula shows that the new R4 must be  $100 \text{ kilohms} / (6 - 1) = 20 \text{ kilohms}$ .

Note that the meter amplifier will not give outputs of much more than 1V r.m.s., so whatever meter you use in this mode must have a full-scale deflection of 1V r.m.s. or less.

## (2) As Self-Rectifying Meter Amp

To use as a self-rectifying meter amplifier the meter must be a d.c. moving coil type, with a linear scale and full-scale deflection of not more than about 10mA. The d.c. voltage drop across the meter should not exceed 500mV (0.5V), at full-scale current. (Most detached milliammeters and microammeters meet this requirement but some multi-meters on their d.c. ranges do not.)

It is not always realised that a class B amplifier functions as a rectifier. It does so in that the current drain from the battery is in proportion to the amplitude of the driving signal. Measure the d.c. which flows through either output transistor and you have measured the strength of the signal. If the amplifier is linear (distortionless) then so is the meter indication.

Ordinary class B audio amplifiers are not suitable because the output transistors are biased so as to pass a small current even without an input signal and a meter would read this all the time. The class B output stage in the Meter Amplifier is unbiased and passes no current until an input is applied. Most of the resulting distortion is removed by negative feedback and the circuit gives good linearity in meter terms though not in hi-fi terms.

## COMPONENTS

### Resistors

R1	10k $\Omega$
R2	150k $\Omega$
R3	220k $\Omega$
R4	10k $\Omega$ see text
R5	100k $\Omega$ see text
R6	1k $\Omega$

All carbon film  $\pm 5\%$  tolerance or better,  $\frac{1}{4}$  or  $\frac{1}{2}$ W.

### Capacitors

C1	220nF (0.22 $\mu$ F)
C2	220pF
C3	3-3 $\mu$ F
C4	47 $\mu$ F
C5	220 $\mu$ F

Working voltage 12V d.c. or over. Type and tolerance not important.

### Semiconductors

IC1	741 operational amplifier in 8-pin DIL package
D1	1N914 or any small silicon diode
TR1	2N3704 silicon <i>n</i> p <i>n</i>
TR2	2N3702 silicon <i>p</i> n <i>p</i>

### Miscellaneous

Electrician's box for two switches, deep type (or any box about 130 x 70 x 30mm). Formica for front panel (Light coloured plain design so that lettering can be put on). Bolts for fixing panel (usually 4BA); 4 off. Plywood for base. Not too thin. Pins for use as tags. 15mm long "lills".  $\frac{1}{2}$  inch hardboard pins, coppered, for lead-throughs. Earth tag.

Since no output current can flow unless there is an a.c. load it is necessary to connect a load resistance to the OUTPUT terminals when the circuit is used in this way. The required value depends on the meter but is easily calculated:

Load resistance =  $1000 / (\text{twice meter full-scale current})$ .

If the meter current is in mA the answer comes out in ohms; if in  $\mu$ A, in kilohms. Example: Meter current,

2mA full-scale d.c.; load required =  $1000/4 = 250 \text{ ohms}$ . Remember to set the gain at 11 for this application. The d.c. meter is connected to the METER terminals.

## CAPACITANCE

If the load is a capacitance rather than a resistance the current taken depends on the frequency of the input signal since the reactance (impedance) of a capacitance goes down as the frequency goes up. If an audio oscillator with adjustable frequency and output level is available this effect enables the Meter Amplifier in its self-rectifying connection to be used as a capacitance meter.

Some sort of standard capacitance is needed to set up the circuit. This can take the form of any close-tolerance capacitance of very roughly the size you want to measure.

Connect the standard capacitance to OUTPUT. Apply about 100mV of audio to INPUT. Adjust the frequency until the scale reading fits the standard: for example: if your standard is 47nF adjust for a reading of 47. Leave the audio oscillator as set and remove the standard. Connecting the capacitor to be measured will now give a reading proportional to its capacitance; for example: 33nF will read 33, and so on. The waveform of the oscillator is not important. (Readers who built Mini Module 2, the Audio Effects Oscillator, may like to try using it for this purpose.)

## FREQUENCY

Frequency can be measured by much the same means as capacitance. If a certain frequency gives half-scale reading when a certain capacitance is connected as the load then twice the frequency will give full scale reading and all lower frequencies will give readings in proportion.

This is strictly true only if the strength and waveform of the input signal are kept constant. This is not always possible, but variations can be largely ironed out by applying an oversized input signal, big enough to overload the op. amp. The op. amp output will then be a square wave of constant amplitude.

An input voltage of around 1V is suitable: don't apply huge inputs or you will damage something.

Example: You want to use the 50Hz mains (at low voltage from an insulated step-down transformer) as the standard of frequency. Apply about 1V. Connect various capacitors to the output until you find one (or several in parallel) that makes the meter read "50". It will read other frequencies in proportion, e.g. 33Hz will now read "33" and so on.

Next month: Voltage Splitter

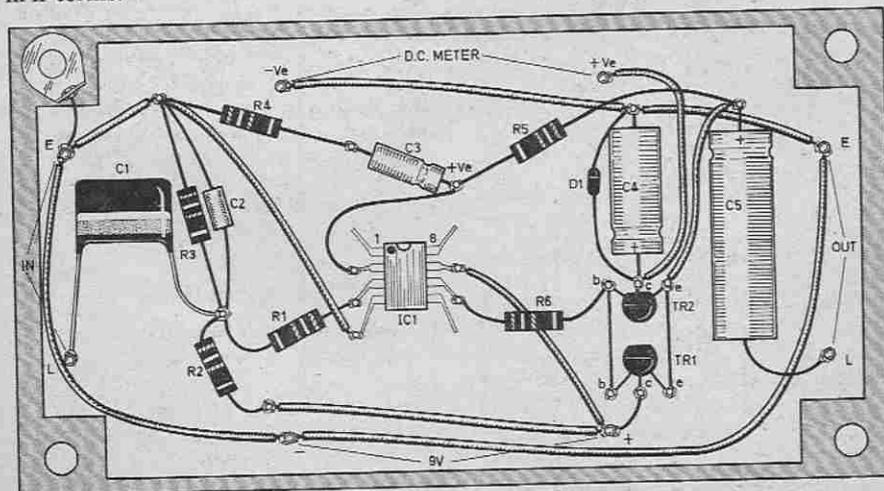


Fig. 2. Plywood circuit board glued to Formica front panel. All components and wiring soldered to miniature household pins.

# MICROPROCESSOR BASICS

By R. W. Coles

# 4

As explained in Part 3, static RAM will be the likely choice for most hobby purposes.

The 2112 (Fig. 4.1) is a typical example of a static RAM. This device is organised as 256 words of four bits and is therefore a 1K RAM. Two of these chips used together will provide 256 bytes of memory which can be used for programs or data in small microprocessor systems. By adding further pairs of 2112 devices and an external chip-select decoder, a memory array of almost any size can be constructed.

If you study the block diagram of the 2112 you will see that there are a total of eight address inputs ( $2^8=256$ ) and four bidirectional lines which provide the data input/

output connection to the microprocessor data bus. The four remaining pins are used for 5 volt power ( $V_{CC}$  and GND), Read/Write selection (R/W), and finally Chip Enable (CE) which gates the data at the current address on to the I/O bus, and can therefore be used as a chip select input in a large memory array.

Notice that the memory latches themselves are organised into a  $32 \times 32$  array (not  $256 \times 4$ ) and that the low address bits select a complete row of 32 locations from which the three high address bits select the required four data bits.

The select circuits are actually logic gates, arranged as a decoder in the row case, and as a data selector for the COLUMN case. The

data out of the column selection circuits is connected back to the data I/O pins via three-state buffers controlled by CE and R/W to ensure that memory data will only be gated on to the bus when this chip is selected and is in the READ state. This ensures that during a WRITE operation the data out of an addressed location does not conflict with the input data, the outputs of the three-state buffers being forced to the third, or high impedance, state.

Well, so much for ROM and RAM. Now let's have a look at input/output circuits.

## INPUT/OUTPUT PORTS

Microprocessors operate very rapidly. So when they carry out an

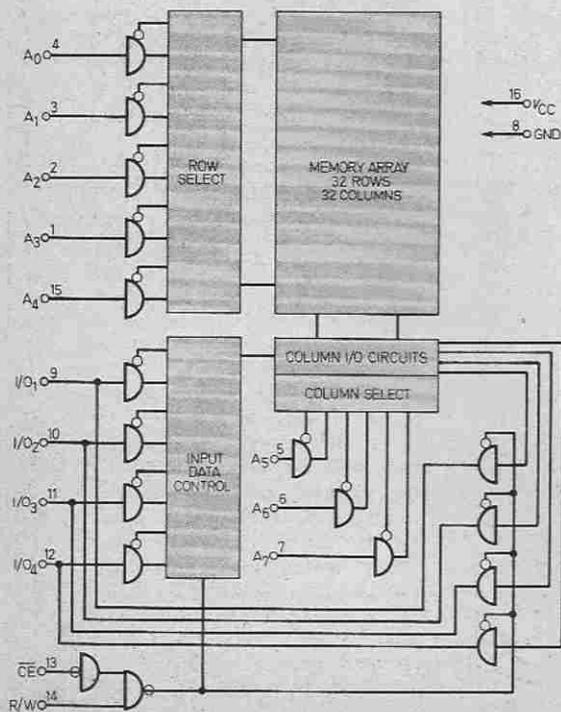


Fig. 4.1. The Intel 2112 1,024-bit Static Random Access Memory. No "refreshing" is required with this type of RAM.

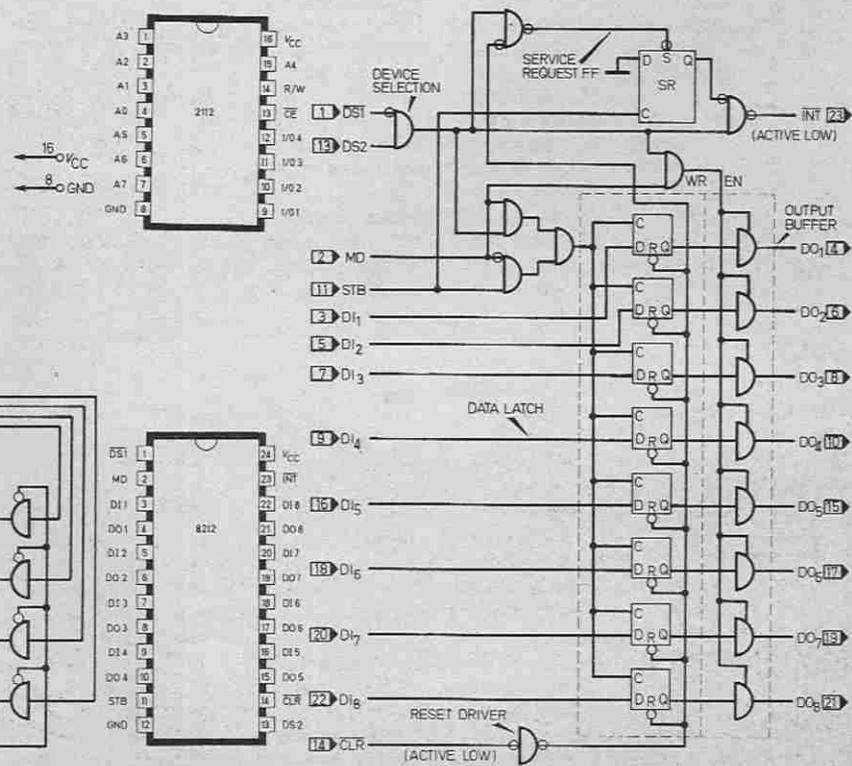


Fig. 4.2. The Intel 8212 8-bit Input/Output Port. All principal functions of a microprocessor system can be implemented.



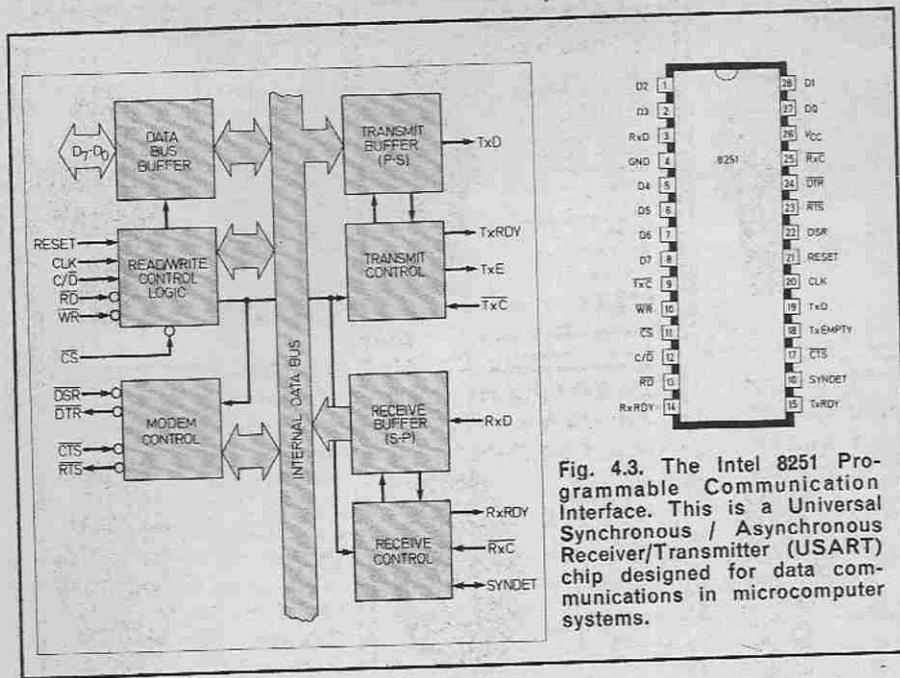


Fig. 4.3. The Intel 8251 Programmable Communication Interface. This is a Universal Synchronous / Asynchronous Receiver/Transmitter (USART) chip designed for data communications in microcomputer systems.

A reset line, CLR, is provided to clear the latches. This can be connected to the microprocessor reset line so that the system is initialised when power is applied.

The three-state output buffers only need their third state when the 8212 is used as an input port. In this case the DS1 and DS2 inputs control the three state outputs, only allowing the latch data through to the bus when the port is selected.

For output port use, this three-state facility isn't required, and so a mode input, MD, is provided so that microprocessor output data can remain available whether the 8212 is selected or not.

The other flip-flop and gates are for use in a very powerful type of microprocessor input/output scheme called Interrupt Driven I/O, and we may return to this in later articles.

output operation, to send an eight-bit word to a peripheral device such as a seven-segment l.e.d. display for example, the data word remains on the microprocessor data bus for only a few microseconds. This isn't much use to the display as it stands of course, and so it is necessary to add an eight-bit storage latch to the system which is strobed at just the right time to catch the data sent by the microprocessor and hold it for the peripheral as long as may be necessary.

### LATCH REQUIREMENTS

Now an eight-bit latch is no great problem, a flick through your old "steam-TTL" data book will reveal lots of likely candidates, but before declaring "problem solved" let's think about what other features we need in this application.

First of all, the latch inputs must not load the data bus too much. (Rule out the rusty old 7475 latches you had in the junk box!)

Secondly, the microprocessor may need many of these output ports, and so it sends out a port address to select the one it is about to talk to. We therefore need a latch which can be "selected" as well as "clocked."

Finally, we need to consider the requirement for input ports because latches are used for output and input, and a device which can do both jobs will be an asset.

For input ports, the latch is simply connected the "other way round" so that its inputs are con-

trolled by the peripheral (say a keyboard) and its outputs are connected to the data bus. In this case the microprocessor does not want the latch outputs controlling the bus when the port is deselected and so we add the further requirement of three-state outputs, so that a high impedance is presented to the bus for most of the time.

### INPUT/OUTPUT CHIP

One device which meets all of these requirements is the 8212 eight-bit input/output chip made by Intel and others. (Fig. 4.2.) When used as an output port the inputs DI 1 to DI 8 are connected to the data bus, and the outputs DO 1 to DO 8 are connected to whatever peripheral component (lamps, displays, relays, printer, etc) the system needs to drive.

To make an input port, just connect up the other way round, although in this case the peripheral components may be switches, sensors, or a keyboard, for example.

Address selection is carried out by means of the DS1 and DS2 inputs, which may be enough by themselves in some smaller systems, or may be driven by the outputs of a memory decoder chip in larger ones.

Data is clocked into the latches with the STB line which is connected to the control bus in the case of an output port, or is controlled by the peripheral device for an input port.

### L.S.I. CHIPS

The 8212 is a very handy chip to have around, but really it's no more than a super-TTL part and is quite modest in its capabilities despite the appearances of its bulky 24-pin package!

By using MOS LSI technology, chip manufacturers are able to produce much more useful devices than the simple 8212. Chips which can be changed from input to output under software control, and chips with three eight-bit I/O ports in a single 40-pin package are all available, at a price!

These input/output "systems" make microprocessors even more powerful and at the same time they reduce the amount of software needed for some jobs. Some of the many complex peripheral chips now available do special dedicated jobs, and one such device is known as a UART (Universal, Asynchronous, Receiver/Transmitter).

A UART lets a microprocessor system talk not in parallel eight-bit bytes, but in a serial bit-by-bit fashion to peripherals such as teletypewriters or VDUs. The UART contains a serial transmitter, a serial receiver, and all the control circuitry to make the communication timing and formatting "transparent" to the microprocessor. One example of this type of device is the Intel 8251 Programmable Communication Interface. (Fig. 4.3.)

To be continued

### QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M1

### QUARTZ LCD 7 Function

Hours, mins, secs., month, date, auto calendar, back-light, seconds STOP WATCH.

**£9.65**

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M2

### QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions, Hours, mins, secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back, Adjustable bracelet.

Metac Price

**£12.65** Thousands sold!

Guaranteed same day despatch.



M3

### QUARTZ LCD ALARM 6 Function

Hours, mins, secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

**£12.65**

Guaranteed same day despatch.



M4

### QUARTZ LCD ALARM 7 Function

Hours, mins, secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

**£17.65**

Guaranteed same day despatch.



M5

### QUARTZ LCD Alarm Chronograph with Dual Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

**£22.65**



M6

### SOLAR QUARTZ LCD Chronograph with Alarm Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

**£25.65**



M7

### QUARTZ LCD Alarm Chrono

22 function, 6 digit. Hours, mins, secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

**£22.65**

Guaranteed same day despatch.

METAC  PRICE



M8

### SOLAR QUARTZ LCD Chronograph

6 digit, 11 function. Hours, mins, secs., 1/100, 1/10 secs., mins. Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

**£13.95**



M9

### SEIKO Alarm Chrono

LCD, hours, mins, secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00

METAC PRICE

**£105.00**



M10

### SEIKO Chronograph

LCD, hours, mins, secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap-time. Back light, stainless steel water resistant, HARDLEX glass.

List Price £85.00

METAC PRICE

**£68.00**



M11

### SOLAR QUARTZ LCD 5 Function

Genuine Solar Solar panel with battery back-up. Back light and auto calendar. Hours, mins, secs., day, date. Quality metal bracelet.

**£8.95**

Guaranteed same day despatch.



M12

### HANIMEX Electronic LED Alarm Clock



Features and Specification:

Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

**£8.65** Thousands sold!

Guaranteed same day despatch.

M13

### QUARTZ LCD Ladies Slim Bracelet

5 function. Hours, mins, secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£15.95**

Guaranteed same day despatch.



M14

### QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins, secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.


**£9.95**

Guaranteed same day despatch.



M15

### DIGITAL LED CLOCK

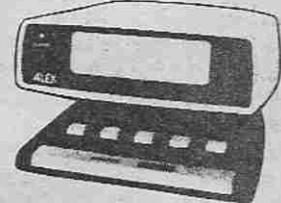

Automatic brightness control. Weekend alarm cancel.

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on-off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

**£10.95**

Guaranteed same day despatch.

M16

#### HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly. Enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME  
Shops open 9.30 - 6.00.

# Metac

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.

# Mullard

## AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE  
PRICE £ **25**  
AT OVER PER PACK

SEE OUR PRICES

**1** PACK 1. 2 x LP1173 10w. RMS output power audio amp modules. + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.  
OUR PRICE p+p £1.00 **£4.95**

**2** PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.  
OUR PRICE p+p £1.00 **£7.45**

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

### 10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.  
Size approximately 9" x 8 1/2" x 4"  
p+p £2.05 **£11.95**

### ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£2.90** plus £1.50 p+p

### Two Way Speaker Kit

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£3.95** per stereo pair plus £1.50 p+p



### 20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus 8 x 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.

**£29.90**  
£2.50 p+p

### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4 to 15 ohms speakers.

**£29.00** p+p **£2.50**


### SPECIAL OFFER

**30 x 30 WATT AMPLIFIER KIT** with BSR P200 belt drive deck and Shure M75 cartridge. **£55.00** + p+p £5.00

### EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance.

**£14.95** Per stereo pair + £3.40 p+p

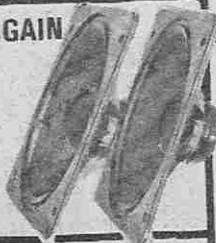

### BSR P200

Belt drive chassis turntable unit semi automatic, cueing device. A.B.C. DLM 30 Mk III Magnetic Cartridge to suit.

**£24.95** p+p £2.55 **£7.75**



**BSR** Manual single play record deck with auto return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **OUR PRICE £10.95** p+p £2.55

### GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

**£7.95** p+p £2.00 Size 12" x 8 1/2"



**SANYO** Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/4" x 1 1/4" x 2" approx.

**£7.50** p+p £1.50p



### BARGAIN FOR PERSONAL SHOPPERS ONLY Altone UA4 Stereo System

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones complete with speakers. **£34.95**

### Micro Cassette Recorder

Pocket size—home or office use or when travelling. **£13.95**

### Battery operated fluorescent camping lamp.

Runs off 8 U2 batteries. **£4.50**

### BARGAINS FOR PERSONAL SHOPPERS


LED 5 function men's digital watch stainless steel finish **£5.95**

LED 5 function men's digital watch stainless steel finish **£6.95**

LED 8 Function CHRONOGRAPH men's digital watch, stainless steel finish **£12.95**

POCKET CALCULATOR. With LED display, memory and percentage key **£2.95**

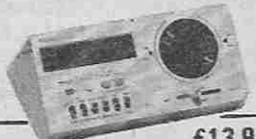AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer **£11.95**



125 Watt Power Amp Module **£13.95**

Mains power supply for above unit **£3.50**

MULLARD Built power supply **£1.50**

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3/4" approx. tweeter inc. crossovers **£20.00**

VIDEOMASTER Super Score TV Game with pistol mains operation. **£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF, mains/battery operation. **£41.95**

VIDEOMASTER COLOUR SHOT TV GAME Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED. OPPORTUNITY AT **£9.95 ONLY**



323 EDGWARE ROAD, LONDON W2  
21 A HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
ALL PRICES INCLUDE VAT AT 12 1/2%  
All items subject to availability. Price correct at 4/4/79 and subject to change without notice.

### 50 WATT MONO DISCO AMP

**£29.95** P&P £2.50

Size approx. 13 1/2" x 5 1/4" x 6 1/4"  
50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



### 70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"  
Brushed aluminium fascia and rotary controls. Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YDU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **70 watt £57**  
**140 watt peak p+p £4.00**  
**100 watt £65**



### FOR PERSONAL SHOPPERS ONLY

#### DUO II SPEAKERS

Attractive teak finish, modern design, incorporating 2 speaker units—6" approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz. Impedance 8 ohms. Power 15 watts RMS. 20 watts max. Per stereo pair **£17.00**



### FOR PERSONAL SHOPPERS ONLY

#### STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**  
Size approximately 47" x 15 1/2" x 15"

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK

# RADIO WORLD

By Pat Hawker, G3VA

RECENTLY, BBC audience research has suggested that more than 40 per cent of all radio listeners tend to keep their receivers tuned to just one single channel. It is by no means certain whether this is due primarily to preference (channel loyalty), lack of information on programme schedules, ingrained sloth, or as I suspect, lack of confidence in their ability to tune to other channels.

Very few listeners really bother to memorise wavelengths or frequencies and at best tend to remember the "spot on the dial". In some parts of the world "channel numbers" are used, particularly for v.h.f./f.m. stations. Almost certainly a large number of radio listeners cannot readily find their way among the radio waves without the distortion that comes from inaccurate tuning or (on v.h.f.) the unpleasant sounds that stem from signals below the "f.m. threshold" unless some adjustment or repositioning is made at the same time to the telescopic rod aerial.

A couple of years ago, Duncan MacEwan, BBC's Chief Engineer, Radio, described his "ideal" radio set of the future. First on a long list of requirements was the elimination of the conventional dial and the elimination of all manual tuning in favour of touch-button or "memorised" selection.

In support of this view, I consider that one of the more important benefits to the viewer that came from moving television on to u.h.f. instead of v.h.f. was the general adoption of push-button channel selection instead of the old "turret plus fine tuner". Anyone of any age can readily change channels even if they do have to get up from their chairs to do so. The recent attempts to popularise quite complex remote control systems for television (some including "multi-function" buttons which do different things at different times) seems to me a retrograde step, at least for older viewers.

For some years I used a three-position switch-tuned v.h.f. tuner which, in combination with automatic frequency control, proved extremely easy and reliable to use; however when LBC and Capital Radio opened in the London area I was forced to modify the unit so that it now includes a manual tuning knob.

Simple to operate is not necessarily the same thing as electronically

simple, of course. Indeed some of the latest tuning systems on the new, better-class of shortwave receivers are often electronically complex but, almost for the first time, make it reasonably simple for the owner to tune to a required station without having "safe-cracker's fingers"—though the constantly changing conditions of h.f. will never make short-wave broadcast reception (unless we eventually have 26MHz satellite transmissions) really granny-proof.

## Saturday's private army

The dreadful news of the brutal death of Airey Neave, M.P., in the House of Commons car-bomb explosion brought back to me memories of the month I spent as an "unofficial" radio operator for his Escape-line Unit (IS9) in Holland in 1944.

At the end of October, that grim winter, I had come with an MI6 officer to Nijmegen where there existed, unknown to the enemy, a private power-supply telephone network over which it was possible to talk directly to Dutch Resistance groups in the occupied north of the country. But hardly had I set up my radio station in a house on the outskirts of the town when Major Fraser (Hugh Fraser, M.P., one-time SAS and Phantom officer) then second-in-command to Airey Neave ("Saturday" of MI9) arrived next door with his own signals operator. Foreseeing mutual interference, I attempted to argue prior rights but my claims were cheerfully swept aside by the simple expedient of IS9 moving into both houses and taking me over in a manner, I soon realised, that had characterised the Escape Unit's roystering campaign across France, Belgium and Holland.

It had certainly been an imaginative War Office appointment to put Airey Neave, the first British officer to escape successfully from Colditz, in charge of IS9 whose official task was to recover "evaders" (aircrew and others hidden in occupied territory)—but it was asking a lot of an essentially gentle character, no matter how resourceful, to keep fully under his control the cheerful tearaways and tough romantics who made up his small "private army", which had by then expanded to include sundry Canadians, Belgian SAS parachutists, Belgian and Dutch resistance workers.

They came to Nijmegen fresh from the first highly successful "Pegasus"

operation which brought back some 140 Arnhem survivors, but still embarrassed by the loss of Peter Baker ("Harrier", later to be first an M.P. and then a guest of HM Prisons) who had gone bravely but foolishly and against orders across the rivers into occupied territory. IS9 began planning a "Pegasus 2" operation but from the first such plans seemed doomed. Baker had been in close touch with "King Kong" (the Dutch resistance leader who had been turned by the Germans) and there had also been an ill-advised press conference at which one of the senior officers brought out in Pegasus had spoken openly of the many Arnhem evaders still hidden on the wrong side of the rivers, Maas and Waal.

However, Pegasus 2 was helped by unusually good communications: apart from the power-supply telephone and 450MHz "S-phones" there were clandestine h.f. links via London and Eindhoven, including those of the Dutch internal radio service of the RVV and OD resistance groups. After several weeks of preparation, the operation proved, as Airey Neave described it in his book "Saturday at MI9", a grim disappointment. Many of the evaders were killed or captured in a carefully prepared ambush and it was clear that the Germans knew in advance what was afoot.

But although Pegasus 2, the last major evader operation mounted by IS9, was a tragedy, it should not be forgotten that the exploits of the escape-lines of MI9 as a whole were remarkably successful, with several thousands brought out of occupied Europe.

Shortly afterwards I left Nijmegen and the private army of IS9 to pursue a rather different aspect of the secret radio war that continued until May 1945, taking as a souvenir of those interesting weeks one of IS9's silk escape maps that is on my wall now as I write this small tribute to the man who led it.

## New Contacts

Those short-wave enthusiasts and radio amateurs who assume that reflection from the F2 layer of the ionosphere always fades out above about 30MHz have been caught out already in this high maximum sunspot cycle.

Apart from reports of the reception of British television signals in the United States, many long-distance signals have been heard in Europe on the 50MHz amateur band (not normally available to amateurs in the UK). Signals from North America, South America and southern Africa have all been heard at good strength.

A new world record has been set up with a two-way 50MHz contact between amateur stations in Argentina and Korea.

# Everyday News

## MADLEY-1

With phone calls to and from Britain doubling every four to five years, and telex and computer data growing just as fast, the strain on the Post Office resources increases each year.

Currently running at 12 million a month, of which 4 million are accounted for by Intercontinental calls and six out of every ten go by satellite.

To help cater for this huge growth in overseas phone calls, the Post Office has just brought a new satellite communications station, Madley 1, into operation at Madley near Hereford.



With a diameter of 32m (105ft), this dish aerial is the biggest so far built for the Post Office, and will eventually be carrying up to 2,000 phone, telex or computer data calls, as well as TV transmissions, between Britain and East Africa, the Middle and Far East, India, Australia and New Zealand. Its powerful microwave radio signal, operating in the 4/6GHz band, is beamed to an Intelsat IVa satellite positioned 22,300 miles out in space over the Indian Ocean.

The site at Madley was selected, after a three-year search, for several reasons, namely: an "electrically quiet" area free from radio interference, particularly from the inland microwave network which uses the same frequencies. Plenty of room for expansion, altogether six such aerial complexes are planned. And, finally, easy access to good telecommunication links with London.

Work first began in autumn 1976 and it was built for the Post Office under a contract in which Marconi Communications Systems Ltd., was prime contractor, supplying the radio and communications equipment and supervised the main sub-contractors IDC Ltd. (buildings) and the Mitsubishi Electric Corporation (aerial dish). As

prime contractor, Marconi Communication Systems also co-ordinated the efforts of an international team of subcontractors including Mitsubishi Electric Corporation, Japan, for the antenna sub-system and Comtech, in the USA for the low-noise amplifiers.

It is foreseen that Madley 1 will be used with the next generation of international telecommunication satellites, Intelsat V, where the system channel capacity will be doubled. In terms of quantity of equipment, Madley 1, with its 32-metre antenna, is one of the largest satellite earth stations operating in the Intelsat system. In all, 55 chains of receiving equipment, 14 chains of transmitting equipment and 10 high power amplifiers give Madley 1 the capability to communicate with about 40 countries simultaneously and Marconi is already manufacturing equipment to extend this capacity.

So far, the Post Office has spent about £10 million at Madley, under its £1,000 million-a-year programme of investment in new plant needed to cater for growth and provide for new services in the future. Of this Marconi's share has been £6 million and IDC of Stratford on Avon share £1 million.

### Olympic Feat

Seventy radio and 18 TV studios will be used at the Moscow Olympic Games in 1980. They will need 135 mixing consoles and to achieve all the programme, switching and talkback lines a total of 500 full-sized 19-inch racks of equipment will be needed.

Among the other equipment needed are 576 monitoring loudspeaker systems and 77 technical checking and control desks.

### Shetland growth

New primary and secondary radars are being supplied to Sumburgh Airport in the Shetland Isles by Marconi and Cossor as part of a £30 million airport development programme.

North Sea oil has made Sumburgh Britain's fastest growing airport. Last year it averaged nearly 1,000 aircraft movements a week and handled nearly 700,000 passengers.

### NEW LAUNCH

The latest in the UK/Ariel series of scientific satellites, UK6, is scheduled for launch on Ascension Day, May 24, from Wallops Island, Virginia.

### Just the Byte

Believed to be London's first "walk-around" Computer Store has just been opened in Tottenham Court Road, a well known landmark amongst amateur electronics enthusiasts.

At the Byte Shop, its name is derived from the computer technical term for a unit of information, everything needed to computerise a small to medium sized business is on show, from a few hundred to thousands of pounds.

In parallel with the rising

demand for business and educational-type systems, the leisure and home computer markets have come into their own in recent times. For these, the Byte Shop offers a broad selection of advanced computer games, with shoppers being invited to pit their skills against chess, poker and backgammon programs compiled by "experts". Small computers that help with personal budgeting, calculate the income tax and look after the timing of H.P. instalments, are also on view.

It will carry cosmic ray and X-ray experiments designed by Leicester and Birmingham Universities, and University College London, to extend knowledge of high-energy astrophysics. The Royal Aircraft Establishment also has two experiments in the payload in the field of solar and CMOS arrays.

The project is funded by the Science Research Council and cost £4.0 million with Marconi Space and Defence Systems as main contractor for the spacecraft.

### China Trade

Trading with China, now the "in" thing, is nothing new to SE Labs (EMI) Ltd. Recent orders worth £500,000 for transducers and recording equipment are only a follow-on from trading links first established some 15 years ago.



## ANALYSIS

### DOING TRICKS WITH PACKETS

During the next few years we can expect to hear quite a lot about packet switching. The idea is to load international communications networks far more effectively and thus help to contain the enormous increase in traffic already forecast without a proportionate increase in the number of communications channels.

One way of obtaining higher utilisation is to increase the speed of transmission so that for any given length of time a longer message can be transmitted or, conversely, for a given message length the transmission time is reduced. This is already happening but once a channel is "seized" it is occupied by the subscriber for the duration of his call whether or not a message is actually being transmitted. And if there are pauses, then the time taken for pauses is wasted. But if the channel is shared by a number of subscribers or users and they are sending and receiving at comparatively low data rates on their local lines, all their messages can be interleaved at a high data rate on the trunk channel and it can be used continually by all subscribers rather than intermittently by single subscribers.

One way of doing this is to break up each message into small "packets" of information at local packet switching exchanges and squirt the packets down the high speed link.

The packets are then re-assembled into the complete message at the remote exchange and passed to the recipient. Although the user has lost exclusive use of a line because other peoples packets are also being transmitted, it all happens so quickly that the user appears to have a continuous and exclusive path.

You can see the snag right away. Imagine yourself at the receiving exchange of the high speed trunk channel with all these bits of messages coming in a constant stream, none of them as complete messages and for different destinations. Happily electronics comes to the rescue in the form of the mini and micro computer. Each packet of message is tagged with destination and with error protection codes and the sorting and switching is all automatic. So is automatic routing so that if long-distance satellite links are full your message can go by submarine cable or vice versa. Conversion of local low-speed data to the high-speed long-distance links and reconversion at the remote end is also automatic.

Packet switching is already in use on some private data networks. With the huge growth in data traffic it must come universally on the public networks and electronics will make it possible. The British Post Office has just started a packet switching service to the USA and will start extending the system to internal use next year.

Brian G. Peck

### New Standards

The first part of a major revision of BS3549 "Methods of Measuring and Expressing the Performance of Television Receivers" has just been published by the British Standards Institute.

Of particular interest to television manufacturers and service engineers, it is being extended to include appropriate requirements for colour television.

Part one is entitled "General Considerations and Electrical Measurements Other Than Those at Audio Frequencies" and copies can

be obtained from BSI Sales Department, price £12.20. The complete works will consist of four parts and will be issued at a later date.



A solid-state matrix camera for industrial and commercial use has been developed by Reticon Corp. It has 10,000 photodiodes on a 6mm square silicon chip. It can be used for generating a TV picture or for applications like optical character recognition and pattern and shape recognition. UK agent is Herbert Sigma, Letchworth, Herts.

### Take-overs

Taking over the former Tandberg colour TV factory in Scotland is Mitsubishi. The Japanese audio company Aiwa is reported as being in negotiation for a plant in Ulster.

Japanese electronics companies already manufacturing in the UK as Sony, National Panasonic (Matsushita), Hitachi (with GEC) and Toshiba (with Rank), the last two being joint ventures.

The latest entry into the great large scale memory race is IIT Semiconductors. Their Footscray, Kent, division is to produce a 64k random access memory (RAM) with samples available by mid-year and production by the end of the year.

At present they manufacture 4k and 16k memories and the 64k device is part of a £10 million development programme, of which £2 million is being funded from the Department of Industry.

## PRESTEL GOES PUBLIC

The Post Office Prestel viewdata system (available only in the London area), got away to a "low-key" start with only 400 or so private subscribers due, it was said, to non-availability of suitably adapted TV sets. Rapid expansion of the service is, however, expected with a hoped-for million customers in the UK after five years.

Later this year the public service will become available to business users as well, and will be extended to Birmingham, Manchester and Edinburgh.

Prestel is based on the world-leading viewdata system invented at the Post Office's Research Centre. It puts, it is claimed, Britain years ahead of any other country in the mass marketing of electronic information.

### Overseas Sales

The Post Office has exploited this world lead by selling the technology to West Germany, The Netherlands, Hong Kong and the USA, and is currently engaged in sales discussion with many other countries.

The latest country to sign an agreement to purchase Prestel software is Switzerland. This takes the form of programmes, or instructions, which control the operation

of the computer on which the information is stored.

Like those with Germany and Holland, the Swiss deal is for the "pilot trial" software, designed primarily for demonstration and information development. Because Switzerland is multilingual, all the index pages will be translated into French and German.

The Post Office budget for Prestel this year is £30 million and the technology is selling world-wide.





# RUMMAGING AROUND

with Keith Cadbury

ONCE one "goes into" electronics, and friends and relatives discover one's new interest, the well-meaning darlings start to off-load all manner of old electrical fittings and super-heterodyne white elephants. We smile and thank them politely, dumping ninety per cent of it straight in the dustbin, but we do not discourage them, for the odd ten per cent of their junk may prove of value.


Such was the case when I took delivery of a car boot-load of old 15A ceramic wall sockets and plugs, from a relative whose house had recently been rewired. Having decided that 15A plugs do not marry easily with 0.1 inch Veroboard transistor and i.c. layouts, the screws were removed, and the rest dumped.

Amongst this stuff was also a few yards of heavy duty wiring cable, which was kept, for some unthinkable contingency. This cable, some 15mm wide, and 8mm thick, and covered in heavy grey plastic sleeving, has made a fine headband for the home-made stereo headphones which I describe this month.

The Stereo Headphones described here can be constructed with items that will be found in many a junk box, yet the prototype was found, after many comparisons, to be capable of better sound reproduction than some commercial phones.

First, acquire two plastic measuring cups, as found in tins of Smash instant potatoes. Purchase two 76mm plastic flowerpot saucers. After drilling a  $\frac{1}{8}$  inch hole through the centre of each flowerpot saucer, you will find that a 57mm diameter loudspeaker will fit snugly between the flanges on the underside of the saucer, and that the Smash measuring cup will fit over the two, with an amount of swivel adjustment available from the "ball-and cup" movement.

## CUP AND SAUCER STEREO HEADPHONES

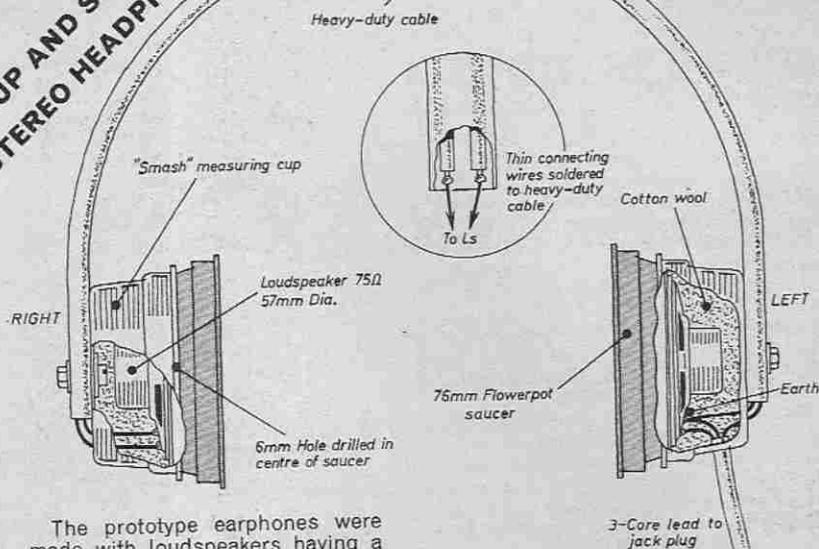

The prototype earphones were made with loudspeakers having a nominal impedance of 75 ohms, which allows them to be used of course with any output up to that impedance, and the higher rating means that they are slightly reduced in sensitivity, which is an asset particularly when the phones are to be connected to the loudspeaker outputs of equipment that does not boast an earphones socket.

Obtain a length of heavy duty electrical cable (as referred to above). About 460mm should be sufficient.

The beauty of a headband made from such cable is that it is suitably bendable, already covered, and has insulated conductors through the middle. With a little manoeuvring, the copper conductors can be cut and worked back into the outer sleeving, after soldering a length of single- or multi-stranded wire of more manageable diameter, to the ends of the two outer conductors.

Drill a  $\frac{1}{8}$  inch hole through the centre of the cable, about 20mm from each end, make a similar diameter hole through the centres of the Smash measuring cups, and fix with suitable bolts, washers and nuts.

Now fix the speakers to the flowerpot saucers, a suitable adhesive being UHU, or aircraft glue. After making two tiny holes in suitable places in each cup, thread the small wires through, and allowing the minimum working length, cut, bare and solder to the speaker at one end, soldering the wires to the speaker at the other end.

A suitable hole is made in the second cup also for the supply lead, which must have three cores—low-current mains cable would suffice, although the writer used four-core GPO cable, one core being cut back, and not used.

Having bent the headband into shape, and checked that all is working OK, the saucer baffles and cup enclosures are now adjusted to suit the wearer, and then glued together.

After fixing a stereo jack plug to the other end of the supply flex, the headphones are ready to be used. Some sort of lambswool, chamois leather or plastic edging could be affixed to the edges of the plastic saucers, but the bare rims have proved to be very comfortable when worn for long periods of recording, and certainly less "sweaty" than conventional padded plastic muffs previously endured.

The omission of such material probably also improved the bass response, through direct contact with the bone area around the ears. In tests, there seemed to be response even when a 100Hz Baxandall bass circuit was adjusted.

Such a claim would appear to be unlikely, and the only explanation seems to be that there is a direct transmission of bass notes through the bone. The 76mm flowerpot saucer does however allow a greater area for resonance than conventional headphones, and this may also contribute to the increased sound spectrum evident.

# SAXON ENTERTAINMENTS

P.A. & DISCOTHEQUE  
EQUIPMENT AT  
INCOMPARABLE PRICES

## STANDARD CENTAUR 100W

£249 + Carr £15 & VAT £21.12 Deposit **£57.12**  
12 months @ £21.94 or 24 months @ £12.54

## SUPER CENTAUR 200W

£299 + Carr £15 & VAT £25.12 Deposit **£68.12**  
12 months @ £26.19 or 24 months @ £14.90

## GXL 200W

With Twin 200 Watt Cabinets

£389 + Carr £15 & VAT £32.32 Deposit **£87.32**  
12 months @ £33.64 or 24 months @ £14.90

## GXL WITH PDF BINS (illus)

£417 + Carr £15 & VAT £34.56 Deposit **£93.56**  
12 months @ £36.36 or 24 months @ £20.81

## CUSTOM CENTAUR 400/600W WITH FOUR PDF 100A BINS

£699 + Carr & VAT £57.52 Deposit **£155.52**  
12 months @ £60.54 or 24 months @ £34.66

## CENTAUR

STEREO DISCOS  
C/W LIGHT SHOW & DISPLAY  
TWIN LOUDSPEAKERS & LEADS  
100W-600W

20%  
DEPOSIT  
CREDIT  
TERMS



6XL + PDF BINS

- ★ 2 Year warranty
- ★ Full Mixing + Crossfade + Mic/Tape Inputs
- ★ Headphone & Cue Light Monitoring
- ★ Full Range Bass/Treble Controls + Mic Tone
- ★ 4 Channel Soundlight + Display

**JUST PLUG IN AND GO!!**  
SEND TODAY FOR YOUR FREE BROCHURE

## MINI DISCO 100 WATT

MONO SYSTEM WITH LOUDSPEAKERS

£179.50 + Carr £15 & VAT £15.56 Deposit **£42.06**  
12 months @ £16.22 or 24 months @ £9.24

## P.A. SYSTEMS

2 YEAR GUARANTEE

### 100 WATT £159.90

+ Carr £15 & VAT £13.99 Deposit **£37.89**  
12 months @ £14.77 or 24 months @ £8.48

- ★ Four Mixing Inputs
- ★ Bass & Treble Controls
- ★ Twin Piezo Horn Columns

### 200 WATT £249.00

+ Carr £15 & VAT £21.12 Deposit **£57.12**  
12 months @ £22.23 or 24 months @ £12.73

## AMPLIFIER UNITS ONLY

AP100 AMPLIFIER

£49.50 + Carr £1.50 & VAT £3.96

- ★ 4 Mixed Inputs
- ★ Bass/Treble Controls
- ★ Vynide Case
- ★ 100 Watts Output

AP200 AMPLIFIER

£89.50 + Carr £1.50 & VAT £7.16

- ★ Six Mixed Inputs
- ★ Three Sets Bass/Treble
- ★ 200 Watts Output
- ★ Slave Socket



## NEW SAXON KLAXON

UK Police Hawaii 50  
US Police Destroyer

Four Sirens in  
one package **£17.50**  
+ VAT £1.40

Individual Sirens **£7.50** + VAT 60p

## NEW SAXON SMASH

ALIEN VOICE  
SIMULATOR

Add a new dimension  
to your disco with  
this press button effect unit  
Insert between mic & amp **£7.50** + VAT 60p

## PLUTO PROJECTORS

P140 **£38.50**  
150 WATT  
INC WHEEL



P5000 **£89.50** + VAT £7.16

250 watt Q.L. inc Cassette/Wheel  
(Full range of wheels - ask for list)

ELECTRECT MIC DISO1 **£18.50\***  
TOP QUALITY UNIT + VAT £2.31

ECM105 LOW COST ELECTRECT  
CONDENSER MIC + VAT 62p **£5.00\***

MELOS CASSETTE ECHO-  
REVERB UNIT - Twin input **£65.00**  
VARIABLE SPEED & DEPTH + VAT £5.20


## AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers



SA308 8 ohms 30W 45V **£10.75\*** + £1.34  
Supply for 2 modules **£11.90\*** + £1.49  
SA604 4 ohms 50V **£14.50** + £1.16  
Supply for 1 or 2 modules **£14.95** + £1.20  
SA608 8 ohms 60W 65V **£15.50** + £1.24  
Supply for 1 or 2 modules **£14.95** + £1.20  
SA1204 4 ohms 120W 75V **£17.50** + £1.40  
Supply for 1 module **£14.95** + £1.20  
SA1208 8 ohms 120W 95V **£21.00** + £1.68  
Supply for 2 modules **£24.75** + £1.98

## DISCO MIXERS - COMPLETE OR MODULAR

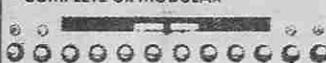

### MONO OR STEREO WITH AUTOFADE

Available complete and ready to plug in or  
as an easy to connect module with all  
controls except monitor switch already fitted  
- Full instructions supplied.

**FEATURES INCLUDE:**  
Twin Deck - Mic & Tape Inputs - Wide range  
bass & treble controls - Full headphone  
monitoring - Crossfade - Professional stan-  
dard performance.

### COMPLETE MIXERS

(with case)  
Mono mains **£45.75** + £3.66  
Stereo mains **£63.75** + £5.10

### MODULES

Mono module **£27.50** + £2.20  
Stereo module **£37.50** + £3.00  
Panel **£3.95** + 32p  
Kit of knobs/sockets etc **£5.50** + 44p

## D.I.Y. MODULES FOR P.A. SYSTEMS MONO/STEREO

Input Modules

Mono PCB only **£6.50**

+ 52p

Stereo PCB only **£10.50**

+ 84p

Mono C/W

Front panel **£9.50** + 76p

Stereo C/W

Front panel **£13.75** + £1.10

Mixer/Monitor Modules

Mono PCB only **£6.50**

+ 52p

Stereo PCB only **£10.50**

+ 84p

Mono C/W

Front panel **£9.50** + 76p

Stereo C/W

Front panel **£13.75** + £1.10

Power supply to suit **£9.50**

send for full details. +VAT 76p



Make your own mixer  
Mono/  
Stereo  
up to 20  
channels  
accept all  
inputs  
available  
as PCB  
only or  
complete  
on front  
panels.

## SOUND-TO-LIGHT UNITS



**3 CHANNEL - 3kW £29.50**

Operates from 1W upwards + VAT £2.36

Bass/middle/treble/master + £1 corr. complete.

Module only **£19.75** + VAT £1.58

Panel **£2.95** + VAT 24p

**4 CHANNEL -**

**£39.50** Carr £1 + VAT £3.16

Dimmer on each channel

Automatic sound light level

Logic circuitry throughout

Module only **£26.75** Panel **£2.95**

+ VAT £2.14 + VAT 24p

**MOTOROLA PIEZO HORNS £4.50. YES!!**  
+ VAT 36p

**FUZZ LIGHTS** Red, Blue, Yellow, Green **£22.80**  
+ VAT £1.82

**HEAVY DUTY SPOT BANKS -  
MATCHES LOUDSPEAKERS**

3 way 600W **£35.50** 4 way 800W **£39.50** Carr £2  
+ VAT £2.84 + VAT £3.16

**100W SPOTS**  
Red - Blue - Amber - Green **£1.50 ea.** + VAT 12p

**CABINET FITTINGS**

ICI Vynide 50" wide **£3.50m** + VAT 28p  
Kick-res grille 50" wide **£3.50m** + VAT 28p  
Nylon kick proof 24" wide **£3.50m** + VAT 28p  
Corners/feet/recess plates **15p ea.** + VAT 1p  
Recess handle **45p** + VAT 3p  
Bar handles **£2.50** + VAT 20p  
Jack plugs/sockets **25p** + VAT 2p

## LOUDSPEAKER CABINETS - COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim - black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24) **£39.00**

Carr £3 + VAT £3.12

Large 100W 1 x 12 (65 x 48 x 24) **£49.50**

Carr £3 + VAT £3.96

P.A. 1 x 12 (+ 2 Piezos) (80 x 38 x 24) **£66.50**

Carr £3 + VAT £5.32

P.A. 2 x 12 200W (100 x 38 x 24) **£99.00**

Carr £3 + VAT £7.92

Disco 2 x 12 200W (80 x 63 x 24) **£85.00**

Carr £3 + VAT £6.80

PDF reflex bin (80 x 40 x 41) **£95.00**

Carr £3 + VAT £7.60

**PDF100 Reflex Bin - Twin Horns - Integrated Slave**

**Amplifier - Accepts mono or stereo signals**

- Use with all types of mixer
- Pan and volume controls
- Send for details **£130** Carr £3 Deposit £28.40 + VAT £10.64

All prices subject to 8% VAT except where asterisked  
(12.4%) Shop premises open Tues to Sat 9 am - 5 pm  
Lunch 12.30 - 1.30 pm Mail order dept open Mon to Fri  
10 am - 4 pm Ring 01-684 6385

## TO ORDER

By Post Send your requirements with cheque crossed  
P.O. or 60p COD charge to address below or  
just send your Access or Barclaycard Number  
NOT THE CARD.

By Phone You may order COD, Access or Barclaycard.  
Post & Packing 50p on all orders except where stated.

## SAXON ENTERTAINMENTS

327 Whitehorse Road, Croydon, Surrey.

All Enquiries - Large SAE Please Brochures on request

MANCHESTER DISCO CENTRE, 237 DEANS GATE, MANCHESTER  
CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY



# POCKET RADIO

By J. Herron

IT IS VIRTUALLY impossible today to build a pocket radio which can compare in price and performance with the mass produced Japanese radios which are currently on the market. To build a radio of similar performance would involve a great deal of time and would probably cost much more than if you had purchased one in the first place.

However, the cost is not the most important factor in this hobby, it is the experience and knowledge gained and the excitement of putting together electronic components to produce, in this case, a source of entertainment and information.

This receiver is not intended to compete with the far superior superheterodyne type of radio, but was designed with simplicity in mind and the use of a p.c.b. makes it a suitable project for the novice constructor.

## CIRCUIT DESCRIPTION

Two integrated circuits are used, one is the ZN414 t.r.f. radio i.c., the other an LM380 small power amplifier i.c. The circuit diagram of the radio is shown in Fig. 1.

The ZN414 is in itself a complete a.m. receiver (less aerial and tuning capacitor) and as such could be used on its own without an amplifier if only headphone reception is required.

This i.c. requires a supply of between 1.1 and 1.5 volts, and unless this is reasonably stable, whistles and distortion will result. Perhaps the easiest method of obtaining this voltage is the system shown in the circuit. Here two diodes are connected in series across the supply voltage.

In a silicon diode, the junction does not conduct until the potential across it reaches a certain minimum, about 0.6V. When the diode does conduct the voltage across it remains steady at this voltage. Thus with two diodes connected in series we obtain 1.2V, which is within the limits of the i.c. Resistor R3 is a current limiting resistor for the diodes.

## TUNED CIRCUIT

The tuned circuit, consisting of L1 and C2 selects the required frequency. After amplification and detection within the i.c. an audio output is available at pin 3, and thus across the volume control VR1.

Resistor R1 provides feedback between the output of IC1 and its input. Resistor R2 together with the supply voltage sets the overall gain, and in most cases will be sufficient. However there may be times where more sensitivity is required, if this is so then the value may be adjusted to suit.

However, the value is rather critical, and if a value very different from that specified is used, it may result in instability.

With the given values for L1 and C1, a high Q tuned circuit is produced resulting in good selectivity. The values of both coil and capacitor may be altered if a tuning range other than medium waves is required. It is possible by careful changes in values to tune from the long wave band up to the 160m Amateur band.

## AUDIO AMPLIFIER


As the output from the ZN414 is unsuitable for direct connection to a loudspeaker an amplification stage is incorporated in the form of IC2, a general purpose audio i.c. type LM380. This i.c. has a fixed gain of 50 and can deliver up to 2 watts.

The only component which needs to be mentioned is C5. This decouples the power supply and eliminates instability. It is important that this is mounted close to the i.c.



All the wiring details are shown in Fig. 2. A printed circuit board layout is shown and in the interests of stability this should be used. It is possible to use some other form of wiring, such as strip-board but this is not really to be

Fig. 1. The complete diagram of the Pocket Radio.

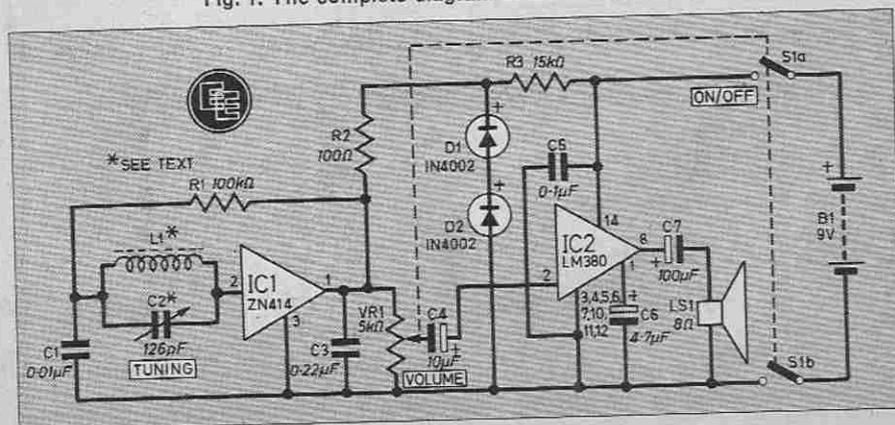



recommended. Incidentally for those who have never made a p.c.b., this is an ideal project to start with as it is very simple to build.


All interconnecting wires should be as short as possible, particularly the leads from the coil to the tuning capacitor, and from the capacitor to the board.

If the beginner is unsure about his ability to solder, particularly IC1, it is recommended that a three-pin transistor socket is used.
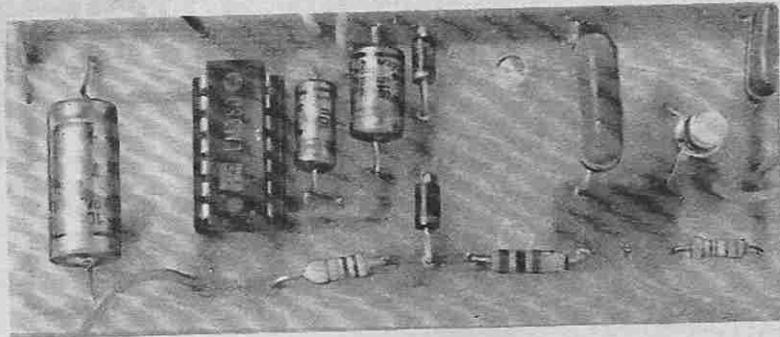
## CASE

The prototype was built in a commercial plastic case, type PBI. There is of course no reason why a different case already to hand cannot be used, providing it is not metal and has minimum dimensions of 115 x 75 x 38mm. No drilling details are given as they and the size of the case will depend to a large extent on the size of components used.

The p.c.b. was mounted on the bottom of the case using two 6BA screws and nuts. The battery can be held in place by double-sided adhesive tape or Blu-Tak.



Components mounted on the printed circuit board.

## COIL


The coil, L1, is a home-made component and is constructed by winding 80 turns of 28 s.w.g. enamelled copper wire, close wound on a paper former, which is then slid over a 10mm ( $\frac{3}{8}$  inch) ferrite rod. The length is unimportant providing it is at least 75mm long and can also fit in the case.

The tuning capacitor C2 was salvaged from an old miniature radio, but a readily available type can be obtained from a number of suppliers. It is not essential to keep to the value specified as the tuning range is quite wide. Indeed, it may be an advantage to use an old capacitor already to hand, and change the number of turns on the coil, particularly if a different tuning range is envisaged.
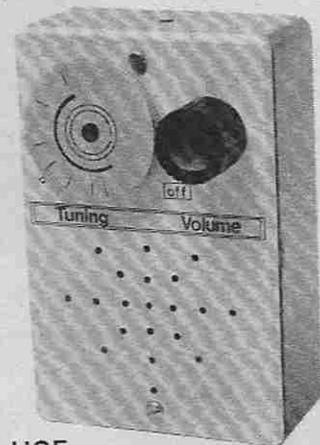
## SPEAKER

The speaker was attached to the front panel using two small clamps and countersunk 6BA screws. Alternatively the speaker can be stuck down using an impact adhesive if it is desired not to mar the front panel.

Letraset or similar can then be used to label the front panel as required.



## IN USE


After construction has been completed, and the board and other wiring checked for errors the battery may be connected.

Connect the battery and switch on, rotate the volume control until a "hissing" sound is heard—this is white noise being picked up by the radio and suggests that it is working correctly.

Rotate the knob of C2, whereupon a number of stations should become audible. If none are heard then this is probably due to the coil being in the wrong position on the ferrite rod. Sliding the coil along the rod while at the same time adjusting C2, you should be able to find a position where a number of stations come in at roughly the same level. If all is well the coil can be stuck in position. Blu-Tak or similar is suitable.

The receiver gives good reception of local stations, and after dark many overseas stations can be picked up. The number and their level depends to a large extent on your location and of course the time of day.

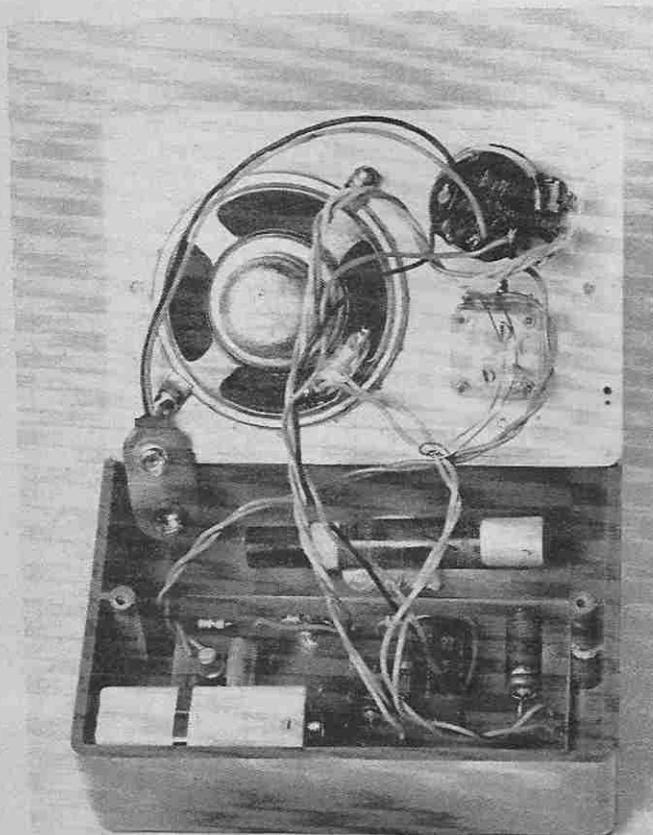Although the ZN414 is not being utilised to its full capacity, it nevertheless gives quite good results despite its simplicity. □






# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING CONTROL SYSTEMS

## NEW FROM TUAC

TD500

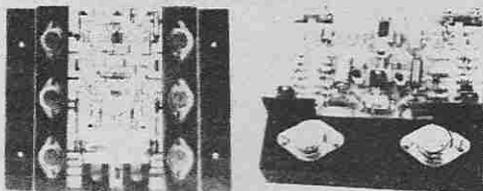

TD150

### 7" x 9" x 1 3/4" ULTRA QUALITY HIGH POWER 5" x 5" x 2" New D.C. Coupled Design AMPLIFIERS

**Featuring**—Electronic Short Open and Thermal Overload Protection.  
**Brief Spec.**—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms.  
Frequency Response 20 Hz - 20 KHz. T.H.D. at full power 0.1%.  
Hum and Noise—100 dB Relative full output.

**T.D. 500** 300W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms. £45.00  
Power supply P.S.300 £30.00

**T.D.150** 150W into 4 Ohms. 100W into 8 Ohms. £26.25  
Power supply P.S. 150 £19.75

**T.D. 150** 60 Version 60W into 8 Ohms. 40W into 15 Ohms. £19.75  
Power supply P.S.60 £15.50

Note—P.S. 300 will drive 2 T.D. 150 amplifiers

All output ratings are R.M.S. continuous sine wave output.

#### TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD., or quote Access/Barclay Card No. (We accept holders phone orders 01-672 9080).

Post to—

**TUAC LTD., 121 CHARLMONT ROAD, LONDON SW 17 9AB.**

Send stamp for our free 36 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.

#### LINEAR

AY38500	450p	LM382	90p	SN78227N	160p	TBA810	100p
CA3039	70p	LM391	180p	SN78228N	180p	TBA820	100p
CA3046	80p	LM555	25p	SN78660N	75p	TBA920Q	280p
CA3080	225p	LM709C	40p	TAA300	100p	TCA270Q	220p
CA3085	290p	LM710T05	60p	TAA350	190p	TCA270S	220p
CA3076	250p	LM710DIL	65p	TAA550	35p	TCAT60	300p
CA3080	75p	LM723T05	40p	TAA570	220p	TCA4500A	450p
CA3084	250p	LM723DIL	40p	TAA661B	140p	TDA1008	350p
CA3085	85p	LM733	120p	TAA700	350p	TDA1034	450p
CA3086	80p	LM741	20p	TAA790	350p	TDA2002	300p
CA3088	190p	LM748	80p	TAD100	150p	TDA2020	300p
CA3089	190p	LM1303N	100p	TAD110	130p	TL084	120p
CA3090AQ	360p	LM1458	100p	TBA120S	80p	XR320	250p
CA3123E	130p	LM3080	75p	TBA120T	85p	XR2206	450p
CA3130	100p	LM3900	55p	TBA480Q	200p	XR2207	450p
CA3140	80p	LM3909N	85p	TBA520Q	200p	XR2208	600p
LF357	80p	MC1310P	140p	TBA530Q	200p	XR2216	650p
LM211H	250p	MC1312P	150p	TBA540	200p	XR2587	250p
LM300TRS	170p	MC1314P	180p	TBA550Q	250p	XR4136	150p
LM301AN	30p	MK50398	650p	TBA560C	250p	XR4202	150p
LM304	200p	MM5314	380p	TBA641A	120p	XR4212	150p
LM307N	85p	MM5316	480p	TBA700	180p	XR4739	150p
LM308T05	100p	NE529K	150p	TBA720Q	225p	ZN414	100p
LM308DIL	80p	NE555	25p	TBA750Q	200p	95H90	700p
LM309K	100p	NE568	400p	TBA800	80p		
LM310T05	150p	NE568B	400p				
LM311T05	150p	SAD1024	1500p				
LM317K	325p	SL917B	650p				
LM324	70p	SN7603N	150p				
LM335	60p	SN7603N	110p				
LM348N	90p	SN7603ND	125p				
LM380	60p	SN7603N	110p				
LM381N	90p	SN7603ND	125p				
		SN7603N	150p				

In 4148 diodes by I.T.T./Texas 100

for £1.50

Static Ram 2102 1024 x 1 bit 450 nanosec

£1.00 each

2112 256 x 4 bit 450 nano sec £2.50

Murata ultrasonic transducers 40kHz

£2.00 each or £3.50 pair

ALL PRICES INCLUDE POST AND VAT

7400	10p	7433	28p	7484	70p	74131	90p	74157	45p	74182	50p
7401	10p	7437	20p	7485	60p	74132	45p	74160	55p	74184	120p
7402	10p	7438	20p	7486	25p	74135	90p	74161	55p	74185	100p
7403	10p	7440	12p	7489	130p	74136	80p	74162	55p	74188	320p
7404	12p	7441	45p	7490	25p	74137	90p	74163	55p	74190	70p
7405	12p	7442	40p	7491	40p	74138	100p	74164	60p	74191	70p
7406	25p	7443	40p	7492	35p	74141	50p	74165	60p	74192	60p
7407	25p	7444	80p	7493	30p	74142	180p	74166	75p	74193	60p
7408	12p	7445	85p	7494	70p	74143	270p	74167	160p	74194	55p
7409	12p	7446	50p	7495	45p	74144	270p	74170	100p	74195	50p
7410	12p	7447	30p	7496	45p	74145	85p	74173	80p	74196	50p
7411	15p	7448	50p	7497	120p	74147	100p	74174	80p	74197	50p
7412	15p	7450	12p	74100	80p	74148	80p	74175	60p	74198	100p
7413	25p	7451	12p	74104	40p	74150	85p	74176	50p	74199	100p
7414	45p	7453	12p	74105	40p	74151	45p	74177	50p	74203	80p
7416	25p	7454	12p	74107	25p	74153	45p	74178	75p	741500	18p
7417	25p	7480	12p	74108	100p	74154	70p	74179	120p	745112	80p
7420	12p	7470	25p	74109	25p	74155	45p	74180	90p		
7421	20p	7472	20p	74118	75p	74156	45p	74181	130p		
7422	15p	7473	25p	74120	80p						
7423	20p	7474	25p	74121	25p						
7425	20p	7475	25p	74122	35p						
7426	22p	7476	25p	74123	40p						
7427	22p	7480	40p	74125	35p						
7428	25p	7481	85p	74126	35p						
7430	12p	7482	75p	74128	60p						
7432	20p	7483	75p	74130	120p						

## T. POWELL

308 St Paul's Road London N1  
Telephone 01-226 1489

Barclay/Access credit cards accepted

# GREENWELD

443D Millbrook Road, Southampton  
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## THE NEW 1978-9

# GREENWELD

## CATALOGUE

#### FEATURES INCLUDE:

- 50p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

## KITS OF BITS FOR THIS MONTH'S EE PROJECTS

MAY 1979

ELECTRONIC DICE  
XENON STROBE  
S.W. CONVERTER  
INTRUDER ALARM

APRIL 1979

SHAVEN INVERTER  
TOUCH BLEEPER  
TRANSISTOR TESTER  
TOUCH BLEEPER

MARCH 1979

## LABCENTRE

A portable "instant" electronic workshop with tools, power supplies and test equipment for design work in logic (TTL and CMOS), audio, r.f. etc.

CAR DIRECTION  
INDICATOR  
ONE-TRANSISTOR  
RADIO

Prices not available at time of going to press. Please send S.A.E. for full details.

E.E. 20+20 TUNER  
AMPLIFIER

We can supply all parts required except the components for the RF unit for approx. £40. Send SAE for detailed list.

NOTE: A more detailed list of parts supplied in these and other kits is available on receipt of a SAE.

Most E.E. Projects back to  
SEPTEMBER 1978 available.

## PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resistant pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.50

## COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors diodes and I.C.'s All useful valves, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts!

All parts contained in clearly marked bags in a plastic storage cabinet 232 x 121 x 165mm with 9 drawers into which all parts can be neatly located.

If bought individually parts plus case would cost over £45 but we are offering this for ONLY £29.95 + £1 p & p. Simply send a cheque or P/O for £30.95 for immediate despatch.

#### CONTENTS:

- 200 1/2 watt resistors
- 20 Wire wound resistors
- 20 Ceramic Capacitors
- 70 Mylar Capacitors
- 50 Polyester Capacitors
- 56 Electrolytic Capacitors
- 61 Transistors
- 12 I.C.'s
- 20 L.E.D.'s
- 55 Diodes and rectifiers

Altogether 614 components.

Price includes current catalogue and Greenweld pen for reordering supplies. Plus free surprise gift.

## TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 95p; 1A £2.50; 6-0-6V 100mA 85p; 1 1/2A £2.40; 9-0-9V 75mA 85p; 1A £2.16; Multitapped type 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.90; 20V 2 1/2A £3.90; 25V 1 1/2A £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50; 12V @ 250mA twice £2.90

## RELAYS

W847 Low profile PC mntg 10x33x20mm 6V coil, SPCO 3A contacts. 85p  
W847 14 pin plug in relay. Rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A, 85p  
W848 Open construction mains relay. 3 sets 10A c/o contacts, £1.20  
W877 675R 12-27V. DPCCO 23 x 20 x 10mm sealed can 85p.  
W890 220V a/c DPCCO 10A contacts, enclosed case £1.30.  
W830 200R 6-12V DPCCO, 23 x 20 x 10mm, sealed can 85p.  
Send SAE for our relay list—84 types listed and illustrated.

## HEAT SINK RELAY

Copper T05 sink 17mm dia x 20mm. 10 for 46p; 100 for £3; 1000 for £25

## POLYTHENE SHEET

Size 36 x 18" 200g. Hundreds of uses around the home. 100 sheets for £1.50. Box of 1500 for £18

## "DOING IT DIGITALLY"

This new series which started October 1978 is bound to be a big success. We supply a complete set of parts (as we did for last year's 'Teach-in' series) for just £19.75 + £1 post for the Electronic Test Bed, and £2.75 for additional parts required for first 6 parts.

## The GREENWELD Amplifier Kit

Ideal for the beginner to make, this kit is complete right down to the last screw! Easily constructed on the PCB provided, the 4 transistor circuit will give 2W output from a crystal cartridge. Battery version £1.75, or with transformer for mains operation £3.95

# 15-240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

**APPLICATIONS:** Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4-7k $\Omega$  at 1kHz.


**OUTPUTS:** Tape 100mV; Main output 500mV R.M.S.

**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz; Bass  $\pm$  at 100Hz.

**DISTORTION:** 0-1% at 1kHz. Signal/Noise Ratio 58dB.

**OVERLOAD:** 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE  $\pm$  16-50V.**

Price £5-27 + 78p VAT P&P free.

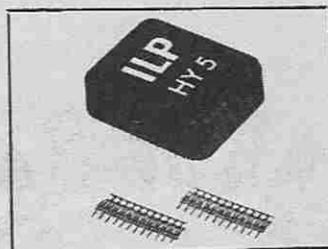

## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

**APPLICATIONS:** Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

**SPECIFICATIONS:**

**OUTPUT POWER** 10W R.M.S. into 8 $\Omega$ ; **DISTORTION** 0-1% at 1-5W.

**INPUT SENSITIVITY** 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz-3dB.

**SUPPLY VOLTAGE  $\pm$  18V.**

Price £6-27 + 78p VAT P&P free.



## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

**APPLICATIONS:** Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


**SPECIFICATIONS:** **INPUT SENSITIVITY** 500mV

**OUTPUT POWER** 25W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-04% at 25W

at 1kHz **SIGNAL/NOISE RATIO** 75dB **FREQUENCY RESPONSE** 10Hz-45kHz-3dB.

**SUPPLY VOLTAGE  $\pm$  25V** **SIZE** 105 50 25mm

Price £8-18 + £1-02 VAT P&P free

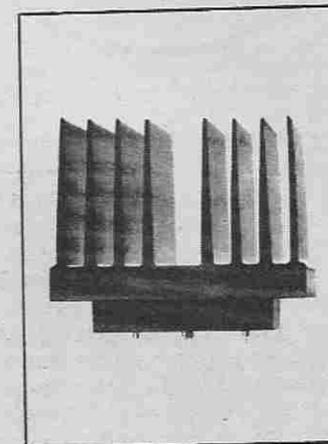

## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

**APPLICATIONS:** Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

**SPECIFICATIONS:**

**INPUT SENSITIVITY** 500mV.


**OUTPUT POWER** 80W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-04% at 60W

at 1kHz **SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz-3dB **SUPPLY VOLTAGE**

$\pm$  35V

**SIZE** 114 50 85mm

Price £19-01 + £1-52 VAT P&P free.

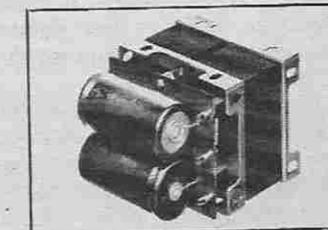

## HY200 120 Watts into 8 $\Omega$

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

**APPLICATIONS:** Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

**SPECIFICATIONS:**

**INPUT SENSITIVITY** 500mV

**OUTPUT POWER** 120W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-05% at 100W

at 1kHz **SIGNAL/NOISE RATIO** 96dB **FREQUENCY RESPONSE** 10Hz-45kHz-3dB **SUPPLY VOLTAGE**

$\pm$  45V

**SIZE** 114 50 85mm

Price £27-99 + £2-24 VAT P&P free.

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—No external components.

**APPLICATIONS:** Public address—Disco—Power slave—Industrial

**SPECIFICATIONS:**

**OUTPUT POWER** 240W RMS into 4 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-1% at 240W

at 1kHz **SIGNAL/NOISE RATIO** 94dB **FREQUENCY RESPONSE** 10Hz-45kHz-3dB **SUPPLY VOLTAGE**

$\pm$  45V

**INPUT SENSITIVITY** 500mV **SIZE** 114 100 85mm

Price £38-61 + £3-09 VAT P&P free.

## POWER SUPPLIES

PSU36 suitable for two HY30's £8-44 plus 81p VAT. P/P free.  
PSU50 suitable for two HY50's £8-18 plus £1-02 VAT. P/P free.  
PSU70 suitable for two HY120's £14-58 plus £1-17 VAT. P/P free.  
PSU90 suitable for one HY200 £15-19 plus £1-21 VAT. P/P free.  
PSU180 £25-42 + £2-03 VAT.  
B1 £0-46 + £0-06 VAT.

P. & P. FREE U.K. ONLY

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.

## I.L.P. ELECTRONICS LTD.,

GRAHAM BELL HOUSE,  
ROPER CLOSE, CANTERBURY,  
KENT, CT2 7EP. Tel: (0227) 54778.

Regd No. 1032630.

Please Supply \_\_\_\_\_  
Total Purchase Price \_\_\_\_\_  
I Enclose Cheque  Postal Orders  Money Order   
Please debit my Access account  Barclaycard account   
Account number \_\_\_\_\_  
Name and Address \_\_\_\_\_  
Signature \_\_\_\_\_

# QUAD

# SIMULATOR

BY B. YORK

## FOR THREE OR FOUR SPEAKER SYSTEMS

**Optional headphone output available.  
Stunning results from stereo records!**

**T**RUE QUADRAPHONIC systems often use complex electronic circuitry to achieve the end result, which to many people is basically a surround-sound type of effect.

The original concept has probably been largely forgotten due to the often fanciful "gimmicky quad" type of records. It would seem therefore perfectly acceptable to relate the "surround-sound" type of effect to true Quad, although one must make the statement that the two are completely different but in most instances the effect is hardly noticeable.

This has in fact been proved by the prototype which has been in use by the author now for several months, and on many occasions has fooled a few "hi fi knowalls" in believing that they are listening to true quadrasonic.

The purpose of this article is to describe an add-on unit, which when connected to your existing stereo equipment will give quite a good quadrasonic effect. The difference in signals between the two rear speakers is sufficient to be detected, the resulting overall

sound akin to that of "surround-sound". In fact the more the stereo separation in the original recording, the greater and more dramatic the quadrasonic effect will be.

### PRINCIPLES

The basis of the Quadrasonic Simulator is a modification of the Hafler configuration.

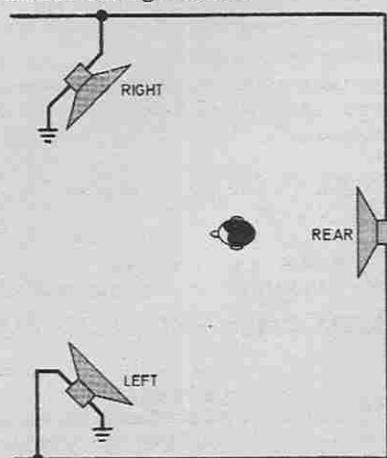


Fig. 1. Hafler's basic idea of adding a single speaker.

Hafler demonstrated, that by adding a single speaker behind the listener and using the difference signals between left and right channels, interesting quadrasonic effects could be achieved, Fig. 1. However by using two speakers out of phase with each other a more realistic effect can be achieved, Fig. 2.

There are at least two disadvantages to the arrangement of Fig. 2.

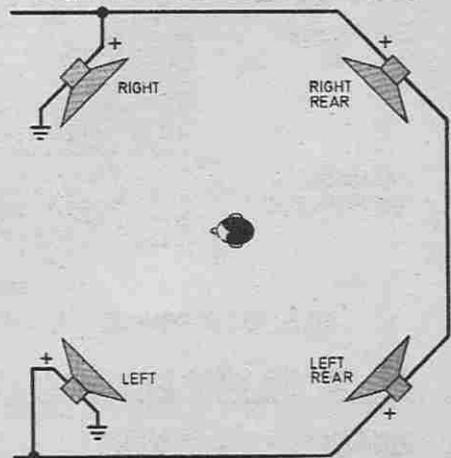


Fig. 2. By using two speakers, a more dramatic effect is obtained.

# QUAD SIMULATOR

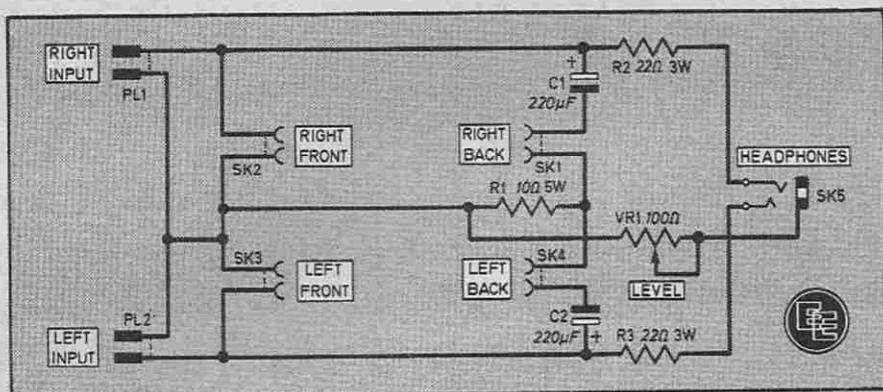


Fig. 3. Circuit diagram of the Quad Simulator. This is suitable for systems up to 10W r.m.s. output.


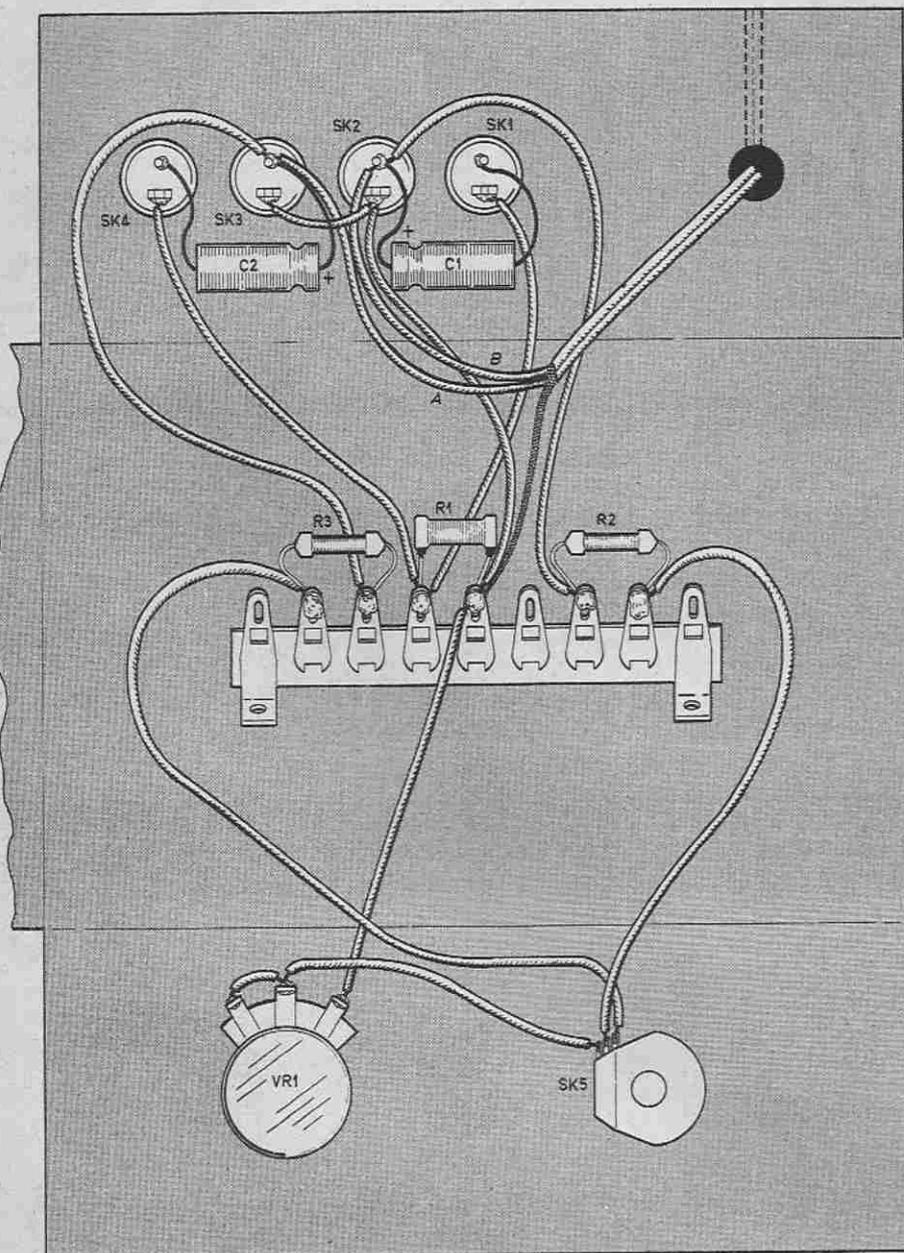


Fig. 4. Complete wiring details for the unit. Note the case has been "opened out" for clarity. There is nothing critical about the layout and could be varied as required.

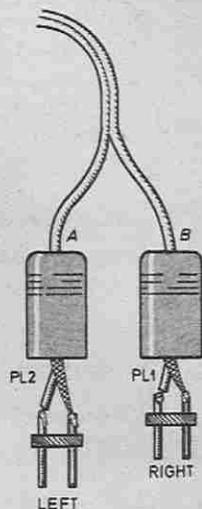

END VIEW OF  
PL1 AND PL2

## COMPONENTS

### Resistors

- R1 10Ω 5W
  - R2 22Ω 3W
  - R3 22Ω 3W
- All are wirewound  $\pm 5\%$

### Potentiometers

- VR1 100Ω 3W wirewound

### Capacitors

- C1 220μF 16V elect.
- C2 220μF 16V elect.

### Miscellaneous

- PL1, 2 2 pin DIN plug (2 off)
- SK1-4 2 pin chassis mounting DIN socket (4 off)
- SK5 standard insulated stereo jack socket

Aluminium or plastic case to choice, approximate dimensions: 152 × 102 × 57mm; small round plastic knob; length of twin screened cable; nine way tag strip with two tags earthed; connecting wire.

# COMPONENTS

approximate  
cost £3.25

One being that the connection of the extra speakers tends to reduce the separation between the main channels. Secondly, the volume of the rear speakers can only be adjusted by adding low value resistors in the main speaker circuit: this may be inconvenient and could cause a mismatch.

Despite these disadvantages the circuit here seems to function quite well.

## CIRCUIT DESCRIPTION

The complete circuit diagram for the Quadraphonic Simulator is shown in Fig. 3.

The first point to notice about the circuit is the similarity between it and the Hafler configuration. The one major difference being the inclusion of R1. This is basically included to reduce the level of signal applied to the rear speakers.

Remember of course that not a great deal of volume is needed in the rear speakers, thus the reduction in volume is hardly noticeable.

## HEADPHONE OUTPUT

An addition to the basic circuit is the provision of a headphone output, this part of the circuit consists of R2, R3, VR1 and the output socket, SK5. Here the two

fixed resistors set the basic limit on the volume through the headphones.

Since you are mixing both front and back signals, the effect in the headphones is not the same as with speakers, nevertheless, the effect is still quite original. From this point of view, the variable resistor VR1 is included to be able to mix the two signals in varying degrees, to produce the most pleasing effect.

## CONSTRUCTION

starts here

The unit is quite easy to build, and could if desired be incorporated inside your hi fi system. This would mean a fair amount of change in the hi fi set-up so is not recommended for the beginner.

An option is available whereby the headphone output components could be omitted. If this is done, wiring it into the hi fi system would be that much easier. The option also exists if the unit is to be as originally intended, and that is as an outboard item.

All the wiring details are shown in Fig. 4. There is nothing critical about the layout and could be varied if required. A tag strip is used as a central connection point for most of the wiring. Note that although twin screened cable is shown for the input connection, this is by no means essential and ordinary four core cable can be used.

The choice of case is also up to the constructor, either a metal or plastic type can be used, and it is not essential to keep to the dimensions specified. Thus any case which the constructor has to hand can be used.

When using a metal case it is important to use insulated sockets, particularly for SK5. If this is not observed then a situation will occur where the jack plug could possibly come into contact with earth, the resulting large increase in volume doing something terrible to the listeners nerves!

## IN USE

Once constructed and checked for any mistakes the unit can then be put to use.

Simply disconnect the original loudspeakers from the hi fi and plug them into the unit sockets marked LEFT FRONT and RIGHT FRONT. Connect an additional pair of speakers to the remaining two sockets, and connect the two leads into the speaker output sockets of the hi fi. When completed the unit is ready for use.

As stated earlier, VR1 is used to give a reasonable balance when using headphones.


The Quad Simulator has now been used by the author for some time, and has been found of sufficiently high quality to solicit several requests for the circuit and other details.

It is for this reason that the design has been presented here with the hope that many who build the simulator will have many hours of pleasure rediscovering old stereo recordings. ✧
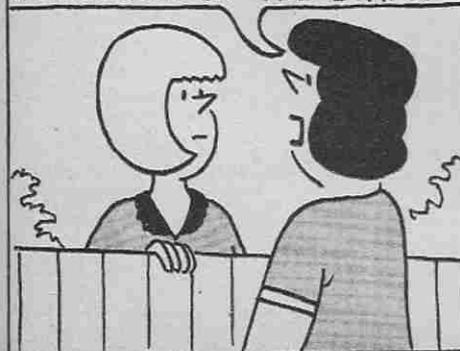
## JACK PLUG & FAMILY...

BY DOUG BAKER

JACK'S BEING INTERVIEWED FOR PROMOTION, AND AS HIS BEARD GROWS QUICKLY, HE'S GOING TO USE HIS SHAVER INVERTER WHEN HE GETS TO WORK, TO MAKE A GOOD IMPRESSION ON THE BOARD.




LATER

HOW DID YOU GET ON, DEAR?

THE CAR WAS STOLEN BY JOY-RIDERS. I'VE JUST GOT IT BACK.



I DON'T THINK I'LL BE PROMOTED.

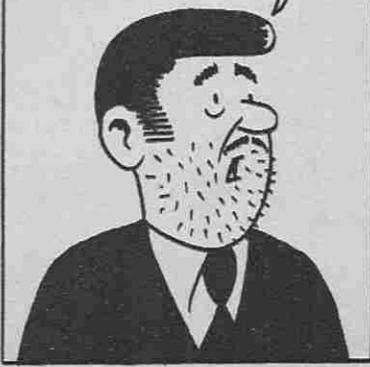

# WORKSHOP MATTERS

By Harry T. Kitchen

## Organisation

The pleasure that is derived from the construction of electronic equipment is very largely governed by the quality of that construction, and that in turn can be governed by the facilities available. My earliest forays in this direction were in a tiny bedroom that constituted my "digs", and this in turn required a very surreptitious manner of working. I now have the luxury of a room devoted to photography and electronics. In between I have made do in all sorts of ways. The advice that follows is therefore exceedingly practical.

Firstly, always endeavour to avoid falling foul of the authorities, be they wife, mother, landlady, or who ever. This is plain commonsense, since falling foul of them may mean that your activities may be curtailed; terminated even. There is a more basic reason than this, and this is good old fashioned courtesy. Let courtesy be your key word, and if anything fails, at least you will have a clear conscience.

## Component Storage

Assume you have been granted certain facilities. Off you go. Then comes the time to clear all up after you. Where do you store everything? The less storage space, the greater the need for a disciplined mind. You can stuff everything into cardboard boxes, and of course they will suffice. Until they disintegrate. Jam jars are more durable if handled with care, and the contents can be reasonably easily identified. Better, but not ideal.

I have yet to find anything better, for the storage of most electronics components, than the plastic drawers that slot into one another, both vertically and horizontally. They are available in several sizes, all compatible. Labels can be inserted into the fronts of the drawers aiding identification of the contents; the transparent fronts are an aid here. I have a large number of these drawers, bought over a period of several years. These house all my resistors, capacitors, transistors, diodes, as well as the veritable multitude of "small things" that are such an adjunct to our hobby.

The resistors and capacitors are housed in decade increments. Resistors of differing wattages or tolerances are segregated. Similarly, capacitors are segregated into types; electrolytic,

polycarbonate, polystyrene. Transistors are segregated into types: germanium or silicon; r.f. or a.f.; high power or low power.

Rigid segregation is the key to efficiency and speed, and whilst it may sound profligate, remember that you can buy drawers as you require them; I bought mine in lots of two dozen. I have never regretted doing so.

## Tool Care

Tools cost money. In the interests of reliability and longevity, they should be treated with care and not chucked carelessly into a pile. Cardboard boxes can be pressed into use, within the foregoing proviso. Tool rolls can be made or bought, and are to be preferred.

If your tool collection is at all extensive, a proper tool box is well worth while. I have several "engineers" tool boxes, bought when they were around £4 each. They very probably cost double that now, but they are to be recommended. A useful compromise is the partitioned drawer sold for the storage of cutlery.

When you have completed a constructional session, particularly on "borrowed" premises, i.e. the kitchen table (beware, I have a patent on 'em!), always clear up properly after you. It takes very little time, but it can go a very long way indeed towards the maintenance of cordial relations all round.

## Buying Components

We have so far considered the organisation of the home workshop as though it were *fait accompli*. This it will not always be. There will be the occasional constructor who will buy his components as he requires them. No storage problem for him. Others, like myself, will like to keep a large variety of components in stock so that almost any project can be commenced without the infuriating delay of obtaining components to suit.

My decade storage may be a clue to my buying philosophy. Yes, I buy my resistors and capacitors in decades, in every sense of the word. Several years ago I saw an advertisement for 5 per cent  $\frac{1}{2}W$  carbon film resistors at ridiculous prices. I bought a few to check. They were eminently satisfactory, so in I plunged.

I bought 10 off every decade in the E12 series from 10 $\Omega$  to 10M $\Omega$ . A lot of

resistors indeed, and they have been very well worth while. At a later date I added 5 per cent  $\frac{1}{2}W$  carbon film resistors, and a variety of wire wound types. Then came a consignment of "computer stock" 2 per cent  $\frac{1}{2}W$  metal film.

Similarly with capacitors. I bought 10 off every decade in the Mullard C280E series, plus a wide variety of electrolytics and polystyrenes. The electrolytics are axial-ended, and I set an upper limit of 16 volts working as I did not envisage frequent use of higher voltages. Besides, my money had run out!

## Transistors

The transistor problems were solved by buying a selection of the most commonly used types, a.f. and r.f., low and high power. Some complementary types were also bought. For diodes, I decided to standardise on the 1N4004 and 1N914 types, and these fulfil the vast majority of existing equipments. These semiconductors augmented an existing stock, and not for worlds would I part with my "red spot", "white spot" or "top hat" germanium transistors, or the equally venerable GEX34 series of diodes, plus the odd GET1 transistor. They're almost museum pieces!

My philosophy is designed primarily for convenience, and if you agree with it, fine. If not, modify it to suit yourself. Many firms now advertise resistors and capacitors at very low prices, and give a small discount if 10 or more of each value are bought.

The same sometimes applies to semiconductors. I have never, ever, bought dubious ("unmarked", "re-marked", or whatever) semiconductors. Use such components, and what do you do if your equipment fails to function? You could end up mystified and miserable, all for the sake of a few coppers. Is it worth it?



"Make me happy, darling—give me the run of your electronic components shop."

# BOOKS AND COMPONENTS

## BOOKS BY BABANI

### V.A.T. Zero Rated

No.	Description	Price
244	Beginners Guide to IC's	£2.75†
BP6	Engineers & Machinists Ref. Tables	40p†
BP14	2nd Book Transistor Equivs & Subs	£1.10†
BP22	79 Electronic Novelty Circuits	75p†
BP24	52 Projects Using IC741 (or Equiv)	75p†
BP26	Radio Antenna Book Long Distance Reception & Transmission	85p†
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	60p†
BP32	Build Metal & Treasure Locators	85p†
BP34	Practical Repair/Renovation C/TV	95p†
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	95p†
BP36	50 Ccts use Germ/Sil/Zener Diodes	75p†
BP37	50 Projects Using Relays/SCR/Triacs	£1.10†
BP39	50 Field Effect Trans Projects	£1.25†
BP40	Digital IC Equivs & Pin Connection	£2.50†
BP41	Linear IC Equivs & Pin Connection	£2.75†
BP42	50 Simple LED Circuits	75p†
BP43	How to make Walkie-Talkies	£1.25†
BP44	IC 555 Timer Projects	£1.45†
BP45	Projects on Opto-electronics	£1.25†
BP46	Radio Circuits Using IC's	£1.35†
BP47	Mobile Discotheque Handbook	£1.35†
BP48	Electronics Projects for Beginners	£1.35†
BP49	Popular Electronic Projects	£1.45†
BP50	IC LM3900 Projects	£1.35†
BP55	Radio Stations Guide	£1.45†
BP180	Coil Design & Construction Manual	85p†
BP202	Handbook of Integrated Circuits Equivalents & Substitutes	75p†
BP205	1st Book Hi-Fi Speaker Enclosures	75p†
BP213	Circuits for Model Railways	85p†
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	85p†
BP216	Electronic Gadgets & Games	85p†
BP217	Solid State Power Supply Handbook	85p†
BP221	28 Tested Transistor Projects	95p†
BP222	Short-wave Receivers for Beginners	95p†
BP223	50 Projects using IC CA3130	95p†
BP224	50 CMOS IC Projects	95p†
BP225	A Practical Intro to Digital IC's	95p†
BP226	Build Advanced Short-wave Receivers	£1.20†
BP227	Beginners Guide to Building Electronic Projects	£1.25†

## NEWNES BOOKS

### V.A.T. Zero Rated

Order No.	Description	Price
	<b>QUESTIONS &amp; ANSWERS:</b>	
216	Transistors 3rd Ed.	£1.00
217	Integrated Circuits	£1.00
218	Radio & Television	£1.25
219	Electronics	£1.15
220	Colour TV 2nd Ed.	£1.15
221	Hi-Fi	£1.15
222	20 Solid State Proj. for Car	£1.95
223	20 Solid State Proj. for Home	£1.95
224	110 Int. Circ. Proj. for Home	£2.95
225	110 Thyristor Projects	£2.50
226	Operational Amp. Proj. for Home	£2.50
227	110 Practical IC Proj. for Home	£2.75
228	Electricity	£1.15
229	Beginners Guide to Electronics	£2.25
230	Beginners Guide to Television	£2.25
231	Beginners Guide to Transistors	£2.25
232	Beginners Guide to Electric Wiring	£2.25
233	Beginners Guide to Radio	£2.75
234	Guide to Colour T.V.	£2.25
235	Electronic Diagrams	£1.80
236	Electronic Components	£1.80
237	Printed Circuit Assembly	£1.80
238	Transistor Pocket Book	£3.90
239	50 Photoelectric Circuits	£1.80
240	Semiconductor Handbook Part 1	£5.25
241	Semiconductor Handbook Part 2	£4.25
242	Electronics Pocket Book	£3.90
243	Radio Value & Semiconductor Data	£2.40
244	Beginners Guide to Integrated Circuits	£2.75
209	BI-PAK TTL Data Book	50p
	BI-PAK CMOS Data Book	45p

## P.C.B. BOARDS

C26 4 pieces 8" x 3 1/2" (approx.) Single-sided fibreglass 80p  
C27 3 pieces 7" x 3 1/2" (approx.) Double-sided fibreglass 60p

## SWITCHES

Description	No.	Price
DPDT miniature slide	1973	14p*
DPDT standard slide	1974	15p*
Toggle switch SPST 1/2 amp 250V a.c.	1975	33p*
Toggle switch DPDT 1 amp 250V a.c.	1976	42p*
Rotary on-off mains switch	1977	50p*
Push switch—Push to make	1978	14p*
Push switch—Push to break	1979	18p*

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST—moulded in high insulation. Material available in a choice of colours ideal for small appliances.	RED	1980	30p*
	BLACK	1981	30p*
	WHITE	1982	30p*
	BLUE	1983	30p*
	YELLOW	1984	30p*
	LUMINOUS	1985	30p*

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	70p*
Miniature SPST toggle, 2 amp 250V a.c.	1959	75p*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	80p*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	85p*
Push button SPST, 2 amp 250V a.c.	1962	90p*
Push button SPST, 2 amp 250V a.c.	1963	95p*
Push button DPDT, 2 amp 250V a.c.	1964	£1.20

**MIDGET WAFER SWITCHES**  
Single-bank wafer type—suitable for switching at 250V a.c.—100mA or 150V d.c. in non-reactive loads make-before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing.

Description	Order No.	Price
1 pole 12 way	1965	48p*
2 pole 6 way	1966	48p*
3 pole 4 way	1967	48p*
4 pole 3 way	1968	48p*

MICRO SWITCHES	Order No.	Price
Plastic button gives simple 1 pole change over action Rating 10 amp 250V a.c.	1970	25p

## FUSE HOLDERS AND FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	506	7p*
1 1/2in x 1/2in chassis mounting	507	12p*
1 1/2in car inline type	508	19p*
Panel mounting 20mm	509	20p*
Panel mounting 1 1/2in	510	30p*

QUICK BLOW 20mm	Type	No.	Type	No.
150mA	611	5p	1A	615
250mA	612	5p	1.5A	616
350mA	613	5p	2A	617
800mA	614	7p	2.5A	618

ANTI-SURGE 20mm	Type	No.	Type	No.
100mA	622	1A	625	2.5A
250mA	623	2A	626	3-15A
500mA	624	1-6A	627	5A
All 7p each				

QUICK BLOW 1 1/2in	Type	No.	Type	No.
250mA	631	500mA	632	800mA
All 7p each				
1A	635	2.5A	638	4A
2A	637	3A	639	5A
All 6p each				

## NUTS AND BOLTS

**BA BOLTS**—packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
1in 08A	839	£1.20	1in 4BA	846	32p
1in 08A	840	75p	1in 4BA	847	25p
1in 2BA	842	65p	1in 6BA	848	40p
1in 2BA	843	45p	1in 6BA	849	21p
1in 2BA	844	52p	1in 6BA	850	25p
1in 4BA	845	44p			

**BA NUTS**—packs of cadmium plated full nuts in multiples of 50.

Type	No.	Price	Type	No.	Price
08A	855	72p	4BA	857	30p
2BA	856	48p	6BA	858	24p

**BA WASHERS**—flat cadmium plated plain stamped washers supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
08A	859	14p	4BA	861	12p
2BA	860	12p	6BA	862	12p

**SOLDER TAGS**—not tinned supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
08A	851	40p	4BA	853	22p
2BA	852	28p	6BA	854	22p

## TRANSFORMERS

MINIATURE MAINS Primary 240V	Secondary	Price
No. 2021	6V-0-6V 100mA	90p*
2022	9V-0-9V 100mA	90p*
2023	12V-0-12V 100mA	95p*

MINIATURE MAINS Primary 240V	Secondary	Price
with two independent secondary windings		
No. 2024	MT280-0-6V, 0-6V RMS	£1.00
2025	MT150-0-12V, 0-12V RMS	£1.00

1 AMP MAINS Primary 240V	Secondary	Price	P. & P.
2026	6V-0-6V 1 amp	£2.50*	P. & P. 45p
2027	9V-0-9V 1 amp	£2.00*	P. & P. 45p
2028	12V-0-12V 1 amp	£2.60*	P. & P. 55p
2029	15V-0-15V 1 amp	£2.75*	P. & P. 60p
2030	30V-0-30V 1 amp	£3.45*	P. & P. 65p

**STANDARD MAINS Primary 240V**  
Multi-tapped secondary mains transformers available in 1 amp, 1 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50V.

Volts available by use of taps. 4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 25-0-25V.

No.	Rating	Price	P. & P.
2031	1/2 amp	£3.40	P. & P. 85p
2032	1 amp	£4.40	P. & P. 85p
2033	2 amp	£5.45	P. & P. £11.10

## AUDIO LEADS

107	FM Indoor Ribbon Aerial	60p*
113	3.5mm Jack plug to 3.5mm jack plug. Length 1.5m	75p*
114	5 pin DIN plug to 3.5mm. Jack connected to pins 3 & 5. Length 1.5m	85p*
115	5 pin DIN plug to 3.5mm. Jack connected to pins 1 & 4. Length 1.5m	85p*
116	Car aerial extension. Screened insulated lead. Fitted plug & skt.	£1.25*
117	AC mains connecting lead for cassette recorders & radios. 2 metres	80p*
118	5 pin DIN phone plug to stereo headphone jack socket	£1.08*
119	2+2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m	90p*
120	Car stereo connector. Variable geometry plug to fit most car cassette, 8 track cartridge & combination units. Supplied with inline fused power lead and instructions.	80p*
123	5.6m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK	£1.80
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	75p*
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	75p*
126	5 pin DIN plug to Tinned open end. Length 1.5m	75p*
127	5 pin Din plug to 4 Phone Plugs. All colour coded. Length 1.5m	£1.30*
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	80p*
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.05*
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	80p*
131	5 pin DIN plug to 3 pin DIN plug. 1 & 4 and 3 & 5. Length 1.5m	83p*
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	90p*
133	5 pin DIN plug to 2 phono plugs. Connected pins 3 & 5. Length 1.5m	75p*
134	5 pin DIN plug to 2 phono sockets. Connected pins 3 & 5. Length 23cm	68p*
135	5 pin DIN socket to 2 phono plugs. Connected pins 3 & 5. Length 23cm	80p*
136	Coiled stereo headphone extension lead. Black. Length 6m	£1.75*
178	AC mains lead for calculators etc.	45p*

## CASES AND BOXES

**INSTRUMENT CASES.** In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
135	8in	5 1/2in	2 1/2in	£1.25
136	11in	6in	3in	£2.12
137	6in	4 1/2in	1 1/2in	£1.30
138	8in	5 1/2in	2 1/2in	£1.78

**ALUMINIUM BOXES.** Made from bright ali., folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	62p
160	4in	4in	1 1/2in	62p
161	4in	2 1/2in	1 1/2in	62p
162	5 1/2in	4in	1 1/2in	70p
163	6in	2 1/2in	2in	64p
164	3in	2in	1in	44p
165	7in	5in	2 1/2in	£1.04
166	8in	6in	3in	£1.32
167	6in	4in	2in	85p

V.A.T. Add 12 1/2% to prices marked \*. 8% to those unmarked items marked are zero rated. P&P. 35p unless otherwise shown. Giro Acc No. 388-7006

# BI-PAK


DEPT. EE6, P.O. Box 6, Ware, Herts.  
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.

# TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK


— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

## STEREO PRE-AMPLIFIERS

MC 1

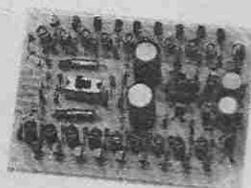

CPR 1

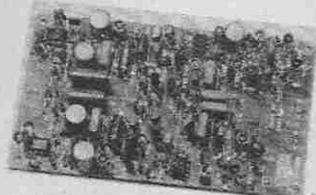

### CPR 1 - THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. P.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 86dB; slew-rate 3V/μs; T.H.D. 20Hz - 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 130 x 80 x 20mm. Supply to be ±15 volts.

### MC 1 - PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details. X02 : X03 - ACTIVE CROSSOVERS X02 - two way, X03 - three way. Slope 24dB/Octave. Crossover points set to order within 10%.

### REG 1 - POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

## POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

## POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).
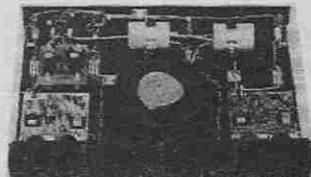
## POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



### ACTIVE CROSSOVERS

X02 £14.93  
X03 £23.06

### POWER AMPLIFIER MODULES

CE 608 80W/8 ohms 35-035v £16.30  
CE 1004 100W/4 ohms 35-0-35v £19.22  
CE 1008 100W/8 ohms 45-0-45v £23.22  
CE 1704 170W/4 ohms 45-0-45v £29.12  
CE 1708 170W/8 ohms 60-0-60v £31.90

### TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £14.47  
CPS2 for 2 x CE 1004 or 2/4 x CE 608 £16.82  
CPS3 for 2 x CE 1008 or 1 x CE 1704 £17.66  
CPS4 for 1 x CE 1008 £15.31  
CPS5 for 1 x CE 1708 £22.88  
CPS6 for 2 x CE 1704 or 2 x CE 1708 £23.98

### HEATSINKS

Light duty, 50mm, 2°C/W £1.30  
Medium power, 100mm, 1.4°C/W £2.20  
Disc/group, 150mm, 1.1°C/W £2.38  
Fan, 80mm, state 120 or 240v £18.50  
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules. £29.16

THERMAL CUT-OUT, 70°C £1.38

### POWER AMP KIT £32.40

### PRE-AMPS:

These are available in two versions - one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPRI £29.49 CPRI S £39.98  
MCI £18.50 MCIS £29.49  
POWER SUPPLY:  
REG1 £6.75 TR6 £1.75

### BRIDGE DRIVER, BDI

Obtain up to 340W using 2 x 170W amps and this module. £5.40

**CRIMSON ELEKTRIK**  
1A STAMFORD STREET,  
LEICESTER LE1 6NL  
Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 international Reply Coupons for detailed information. UK - please allow up to 21 days for delivery.

Distributor: Minic Teleproducer, Box 12035, S-750 12 Uppsala 12, Sweden.

## New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

## New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.

Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself - computers, oscilloscopes, transceivers etc. ... Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451). Registered in England, No. 606177.

Soldering iron offer FREE



## New Heathkit CI 1265 Digital Tach/Speedometer.

Push-button digital readout. Displays engine speed/rpm. Accurate to 1mph or rpm variations of 100.

To: Heath (Gloucester) Limited, Dept. EE6/79 Bristol Road, Gloucester, GL2 6EE.  
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.   
Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name \_\_\_\_\_

Address \_\_\_\_\_

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

When you receive your catalogue you will get details of this free offer.



# HEATHKIT

HEATH  
Schlumberger

## EE SPECIAL REPORT



# CONNOISSEUR PACKAGE DEAL

**D**OUTBLESS some builders of the DEE2020 Tuner Amplifier will be looking around for a pickup-turntable unit. For them, and others starting out into the hi fi field, the choice has to be made from a large range of record playing equipment, and many factors have to be taken into account.

There is one particularly interesting possibility for the handyman to consider. That is the purchase of a kit of parts for assembly at home. This is precisely what is offered by Connoisseur with their new "Package Deal" which has been announced at an opportune time. It comprises the BD1 Turntable Kit, SAU2 Pickup Arm, and Plinth with acrylic cover.

The BD1 Belt Drive Turntable Kit has been available for home assembly for many years, and is justifiably popular. It operates at 33 $\frac{1}{3}$  and 45 r.p.m. using a flexible belt drive system. The Connoisseur Pickup Arm Type SAU2 is equally popular and is an ideal complementary precision instrument. The wooden Plinth provides stylish housing and completes the ensemble.

The work involved in assembling this kit is by no means onerous, and requires hardly anything more than a screwdriver and a pair of pliers, save a special spanner—and that's provided.

### BD1 BELT DRIVE TURNTABLE KIT

The eight-page instruction booklet gives minutely detailed assembly instructions for the BD1 Belt Drive Turntable Kit and is well illustrated with practical diagrams.

This booklet, however, requires revising, for our copy states on the

front page "Speed change is accomplished by push button . . ." In fact, a lever is used for this purpose on the actual equipment submitted to us.

We followed the stage-by-stage directions, during which it became apparent that further revisions are required to this booklet. "Operation 1" revealed that a different type of connector block was supplied to that illustrated.

### KIT SPECIFICATION

#### MAINS SUPPLY

200/240 or 100/125 volts a.c. Adjustable by user. Power. 5W.

#### MOTOR

Synchronous constant speed motor runs at 375 r.p.m. at 50Hz; 450 r.p.m. at 60Hz. Drive pulleys for 50Hz or 60Hz available.

#### TURNTABLE

10 $\frac{1}{4}$  in (260mm) lathe turned aluminium casting. Precision ground spindle. Manganese bronze bearing.

#### DRIVE

Precision ground round section rubber belt. Unique drive arrangement via groove in outer surface of turntable rim.

#### PERFORMANCE

Rumble: -60dB } (Maker's figures)  
Hum: -80dB }  
Wow and flutter: Less than 0.1%

#### FINISH

Black hammer with satin silver and matt black trim.

Control knob: bright finish turned aluminium.

Plinth: Afrosia wood, waxed finish. Dust cover: transparent acrylic.

The mains switch panel assembly came as a completed unit. The 10W ballast resistor in the mains input line was mounted in such a way that one end would have made direct contact with the brass spacing pillar when this was fitted. (Mains to chassis!) Disaster was averted by easing the resistor upwards and away from the pillar hole by a distance of  $\frac{1}{4}$  inch. (In addition to this action, it would be a wise precaution to fit a piece of plastic sleeving to this pillar.) NOTE: A plastic-sleeved pillar is now being provided by the manufacturer.

The motor came with the two-speed pulley already fitted. After the motor was mounted, the turntable and belt in position, it was found necessary to move the pulley slightly upwards on spindle to align correctly with turntable belt groove.

Hand rotation of the turntable proved the correct operation of the speed change device: the belt moving from one pulley groove to the other as the lever was thrown.

A hinged plastic cover protects the pulley. There is not too much room for comfort. When initially closed the cover was found to foul the pulley. The only remedy was to slacken the motor screws and ease the motor away (towards the rear corner of the platform). This cleared the trouble.

Then mains was applied and the action of the speed change checked. It functioned perfectly, at 33 $\frac{1}{3}$  and 45 r.p.m.

### SAU2 PICKUP ARM

A template is provided to ensure correct positioning of pickup base in relation to the turntable centre spindle. But this was not required in the present case since the mounting board (part of the BD1 Plinth and Cover Kit) came already drilled for the pickup and the arm rest. It was therefore a simple task to mount and secure the pickup with its locking nut.

Dual signal output leads are supplied. These terminate at one end in a 5-pin plug and this fits into the socket on pickup base. The other end of the cables are fitted with phono plugs. A separate earth lead is provided and is intended to be connected to the preamplifier chassis.

The head shell is suitable for all standard cartridges with  $\frac{1}{2}$ in fixing centres. Lateral adjustment is provided to give minimum tracking error.

The SAU2 instruction leaflet explains how to adjust for required height of arm; for required tracking weight, which is performed with the aid of the precision balance supplied; and for correct bias weight. An additional small weight is supplied to substitute for the larger weight when lower tracking weights are used.

A hydraulic arm lifting device is incorporated. This is set correctly at the factory.

The Connoisseur BD1/SAU2 "Package Deal" is currently available from retailers at a price of less than £50.00 (VAT extra).



**T**HIS month we explain some of the alpha, and alpha-numeric codes to be found on resistors, capacitors and transistors to aid value and application identification.

### BS1852 RESISTANCE CODE

It is common nowadays to find the value of a resistor printed on the body in the form of an alpha-numeric code.

Letters R, K, and M, are used as multipliers  $R = \times 1$ ,  $K = \times 1,000$  and  $M = \times 1,000,000$ . The position of these letters among the two most significant digits also acts as the position of the decimal point. For example,  $4K7 = 4.7$  kilohms,  $M22 = 0.22$  megohms = 220 kilohms.

The tolerance of the resistors is indicated by the addition of a second letter appearing in the last position: F=1%, G=2%, H=2.5%, J=5%, K=10%, M=20%.

Example of the full code:  $4K7J = 4.7$  kilohms  $\pm 5\%$ ;  $2R2K = 2.2$  ohms  $\pm 10\%$ .

### ALPHA-NUMERIC CAPACITOR CODING

Ceramic plate capacitors of Russian origin are commonplace nowadays and these use an alpha-numeric coding similar to the above-resistor system. For example 33K, 4K7, the K acting as a  $\times 1000$  multiplier and decimal point position giving the value in picofarads. Therefore  $33K = 33,000pF$  or  $0.033\mu F$ , and  $4K7 = 4,700pF$  or  $0.0047\mu F$ . The K can also be used merely as a decimal point with the units in nanofarads, (nF), i.e.,  $4K7 = 4.7nF$ .

The letter H is sometimes used in place of K for some values (reason unknown) e.g.,  $1H5 = 1.5nF$  or  $1,500pF$  or  $0.0015\mu F$ .

We have also in our possession some ceramic capacitors (unknown origin) marked 4n7 which is  $4.7nF$ . Also another tiny bead type ceramic marked with only 10, the value being  $10pF$ .

## FOR BEGINNERS

### TRANSISTOR CODING

Since the invention of the transistor in 1948 there have been tens of thousands of transistors manufactured and marketed. There are many different shapes, sizes, pinning configurations and employing various numbering systems for identifying the devices.

At present there are three main numbering systems and a number of "house" systems from different manufacturers.

In the USA, the "Jedec" system is used and prefixes three and four digit numbers by "2N". Tables have to be consulted for all information concerning the device.

In Europe the "Proelectron" system is employed. Two letters followed by three numbers (eg BC109) are classified as consumer devices while three letters/two numbers (eg BFY52) identifies an industrial device.

The first letter is always A (germanium) or B (silicon), see Table 1 for decoding of second letter.

### JAPANESE SYSTEM

The Japanese Institute of Standards has the "2S" system. The 2S is followed by a letter and then

TABLE 1: Explanation of the Pro-electron coding system for transistors.

Germanium	Silicon	Applications
AC	BC	Low power, low frequency
ACY	BCW BCX BCY BCZ	
AD	BD	Power, low frequency
ADY ADZ	BDX BDY	
AF	BF	Low power, high frequency
AFY AFZ	BFR BFS BFT BFV BFW BFX BFY	
AL	BLX BLY	
ASY ASZ	BSS BSV BSW BSX	
AU	BU	Power, switching
AUY	BUY BPX BPY	

numerals, the letter having application significance: **A** pnp/high frequency; **B** pnp/low frequency; **C** npn/high frequency; **D** npn/low frequency; **H** unijunction; **J** p-channel f.e.t.; **K** n-channel f.e.t.; **OS** photo-device.

Some Texas Instruments devices are coded with a 2S followed by up to four numerals.

### HOUSE CODES

Some of the popular "house" codes are:

Motorola:	MJ	—Silicon, power, metal
	MJE	—Silicon, power, plastic
	MP	—Germanium, power, metal
	MPF	—f.e.t., plastic
	MPS	—small signal, plastic
Texas:	TIP	—power, plastic
	TIS	—Small signal
Ferranti:	ZTX	—Small signal, plastic

### ABBREVIATIONS

The direct meaning of some common abbreviations to be found in EVERYDAY ELECTRONICS are shown below.

a.c.	alternating current
a.f.	audio frequency
a.m.	amplitude modulation
BA	British Association (nut and bolt sizes)
d.c.	direct current
d.p.d.t.	double-pole double-throw elect.
e.m.f.	electromotive force
f.e.t.	field effect transistor
f.s.d.	full scale deflection
f.m.	frequency modulation
i.c.	integrated circuit
l.d.r.	light dependent resistor
lin.	linear
log.	logarithmic
mm	millimetre
m.w.	medium wave
npn	transistor structure (two types)
pnp	
p.v.c.	polyvinyl chloride
r.f.	radio frequency
r.m.s.	root mean square
s.p.s.t.	single-pole single-throw
s.r.b.p.	synthetic resin bonded paper
s.w.g.	standard wire gauge
t.r.f.	tuned radio frequency
u.j.t.	unijunction transistor
v.h.f.	very high frequency
%	per cent
A	ampere (amp)
dB	decibel
F	Farad
H	Henry
Hz	Hertz (cycles per second)
$\Omega$	ohm
V	volt
W	watt
p	pico ( $\div 1,000,000,000,000$ )
$\mu$	micro ( $\div 1,000,000$ )
m	milli ( $\div 1,000$ )
k	kilo ( $\times 1,000$ )
M	mega ( $\times 1,000,000$ )

Largest range of quality components in the U.K.—over 8,000 types stocked

# Marshall's

Head office and mail order to DEPT EE  
A. Marshall (London) Ltd.  
Kingsgate House, Kingsgate Place, London NW6 4TA  
Tel: 01-624-0805 Telex 21492

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 also 325 Edgware Road, W2. Tel: 01-723 4242.  
Glasgow: 85 West Regent Street, G2 2QD Tel: 041-332 4133 and Bristol: 108A Stoke's Croft, Bristol. Tel: 0272 654201.

## BRIDGE RECTIFIERS (Full range in cat.)

Type	Rating	Price	Type	Rating	Price
W005/1	1A	50V 0.28	S10	2A	100V 1.35
W01	1A	100V 0.30	B40C1500	1.5A	100V 0.53
W02	1A	200V 0.32	B80C1500	1.5A	200V 0.82
W04	1A	400V 0.40	B80C3200	3.2A	200V 1.25
W06	1A	500V 0.50	PW05	6A	50V 0.90
W08	1A	800V 0.60	PW01	6A	100V 0.95
VM18	1A	100V 0.44	PW02	6A	200V 0.97
VM28	1A	200V 0.48	PW04	6A	400V 1.08
VM48	1A	400V 0.50	PW06	6A	600V 1.18
BY164	1.4A	120V 0.75	PW08	6A	800V 1.28
BY179	1A	800V 0.70	PW10	6A	1000V 1.60
S005	2A	50V 0.39	K05	25A	50V 2.20
S01	2A	100V 0.44	K01	25A	100V 2.37
S02	2A	200V 0.48	K02	25A	200V 2.75
S04	2A	400V 0.60	K04	25A	400V 3.40
S06	2A	800V 0.70	K06	25A	600V 3.99
S08	2A	800V 0.84			

## SINGLE IN LINE PLUGS AND SOCKETS

Providing a simple and economical alternative to edge connectors for bringing cable into a pcb.  
12 WAY £0.90  
24 WAY £1.20

## SIEMENS TURN-SLIDE SWITCHES

This new version of the rotary switch is especially suitable for setting programs. The rotary switch is of a 1 element no stops.  
Voltage rating 80V  
Current rating 0.5A  
fixed contacts gold-plated

PRICE £2.85

## TTL (See catalogue for full range)

SN74H05N	0.60	SN74S00N	0.77	74LS160N	0.80
SN74H10N	0.55	SN74S03N	0.77	74LS181N	0.85
SN74H11N	0.55	SN74S04N	0.84	74LS182N	0.85
SN74H20N	0.55	SN74S10N	0.77	74LS183N	0.85
SN74H21N	0.55	SN74S20N	0.77	74LS164N	1.10
SN74H30N	0.55	SN74S40N	0.77	74LS165N	1.15
SN74H40N	0.55	SN74S48N	0.77	74LS166N	1.65
SN74H51N	0.55	SN74S65N	0.77	74LS188N	1.45
SN74H53N	0.55	SN74S112N	1.70	74LS189N	1.45
SN74H54N	0.55	SN74S114N	1.70	74LS190N	1.45
SN74H55N	0.55	SN74S140N	0.77	74LS173N	1.10
SN74H60N	0.55	SN74S157N	2.95	74LS174N	0.75
SN74H62N	0.55	SN74S188N	2.70	74LS175N	0.75
SN74L00N	0.55	SN74S189N	1.81	74LS181N	2.75
SN74L02N	0.55	SN74S200N	3.50	74LS183N	2.70
SN74L04N	0.60	SN74S201N	3.71	74LS184N	3.74
SN74L47N	3.10	SN74S282N	1.50	74LS190N	1.00
SN74L48N	0.90	SN74S287N	2.95	74LS191N	1.00
SN74L55N	2.82	SN74S288N	2.70	74LS192N	0.95
SN74L59N	2.30	SN74S289N	1.81	74LS193N	0.95
SN74S00N	0.55	SN74S300N	3.08	74LS194N	0.70
SN74S01N	0.55	SN74S301N	3.71	74LS195N	0.80
SN74S02N	0.55	SN74S367N	3.05	74LS196N	0.70
SN74S03N	0.26	SN74S470N	5.06	74LS197N	0.80
SN74S04N	0.29	SN74S471N	5.06	74LS221N	0.80
SN74S05N	0.29	SN74S472N	4.88	74LS240N	1.50
SN74S08N	0.28	SN74S473N	4.88	74LS241N	1.50
SN74S09N	0.28	SN74S474N	4.88	74LS242N	1.25
SN74S10N	0.28	SN74S475N	4.88	74LS243N	1.25
SN74S11N	0.26	SN74S490A	0.36	74LS244N	1.25
SN74S12N	0.26	SN74S491A	0.60	74LS245N	1.85
SN74S13N	0.38	SN74S492N	0.36	74LS247N	1.09
SN74S14N	0.75	SN74S493N	0.36	74LS248N	1.09
SN74S15N	0.26	SN74S494N	0.90	74LS249N	1.09
SN74S20N	0.26	SN74S495N	0.75	74LS251N	1.00
SN74S21N	0.26	SN74S496N	0.54	74LS253N	1.00
SN74S22N	0.26	SN74S497N	1.95	74LS257N	1.00
SN74S26N	0.32	SN74S100N	1.40	74LS258N	1.00
SN74S27N	0.26	SN74S107N	0.24	74LS259N	1.55
SN74S28N	0.29	SN74S118N	0.95	74LS261N	3.25
SN74S30N	0.26	SN74S119N	1.40	74LS266N	0.44
SN74S32N	0.27	SN74S121N	0.55	74LS273N	3.20
SN74S33N	0.29	SN74S122N	0.55	74LS275N	3.20
SN74S37N	0.32	SN74S123N	0.55	74LS279N	0.58
SN74S38N	0.32	SN74S124N	1.20	74LS280N	1.65
SN74S40N	0.26	SN74S125N	0.45	74LS283N	1.20

## CMOS (see catalogue for full range)

74C00N	0.24	74C48N	1.38	74C95N	1.04	74C164N	1.04	74C373N	1.87
74C02N	0.24	74C73N	0.54	74C107N	1.22	74C165N	1.04	74C374N	1.87
74C04N	0.24	74C74N	0.58	74C150N	4.14	74C173N	0.90	74C901N	0.54
74C08N	0.24	74C76N	0.54	74C151N	2.47	74C174N	0.90	74C902N	0.54
74C10N	0.24	74C83N	1.30	74C154N	3.68	74C175N	0.90	74C903N	0.54
74C14N	0.95	74C85N	1.30	74C157N	2.21	74C192N	1.11	74C904N	0.54
74C20N	0.24	74C86N	0.64	74C160N	1.11	74C193N	1.11	74C905N	7.28
74C30N	0.24	74C89N	4.39	74C161N	1.11	74C195N	1.04	74C906N	0.54
74C32N	0.24	74C90N	0.85	74C162N	1.11	74C200N	6.70	74C907N	0.54
74C42N	0.92	74C93N	0.85	74C163N	1.11	74C221N	1.36	74C908N	0.96

## RESISTORS

**CARBON FIXED**  
0.25 watt ± 5% Tol. Available in E12 range 10Ω to 1 meg 2p each  
0.5 watt ± 5% Tol available in E12 range 10Ω to 10 meg 3p each  
1.0 watt ± 10% Tol Available in E12 range 10Ω to 10 meg 5p each  
2.0 watt ± 10% Tol. Available in E12 range 10Ω to 10 meg 9p each

**WIRE WOUND**  
2.5 watt ± 5% Tol -22 to 330 ohms  
5 watt ± 5% Tol -5 to 12k  
10 watt ± 5% Tol 1 to 25k

**METAL OXIDE**  
0.5 watt ± 2% Tol E24 range 10Ω to 1 meg

10p each  
12p each  
14p each  
4p each

see catalogue for full list of available values

## MULTI-WAY EDGE CONNECTORS

2.54mm (1 inch)	Price
16 Way Single	£3.90
24 Way Single	£3.95
32 Way Single	£5.25

3.96mm

6 Way Double	£2.65
10 Way Double	£2.65
15 Way Double	£3.08
22 Way Double	£4.60

## BRINLEY TOOLS AND CUTTERS

**GENERAL PURPOSE 100mm (4")**

Diagonal Cutters £3.40  
Round Nose Pliers £3.25  
Flat Nose Pliers £3.20  
Snipe Nose Pliers £3.20  
End/Top Cutters £3.80

Also in stock—BAHCO Quality Tool range. See catalogue for full details

## NEW 1979 CATALOGUE

48 page catalogue—new enlarged micro section—largest range of quality components from franchised suppliers available in UK. All VAT inclusive prices. Over 8,000 line items plus lots more. 50p post paid or 40p to callers at any of our four branches.

### ★ MAIL ORDER ★

Please add 40p for p/p to all orders. Telephone orders on credit cards £10.00 minimum.

## NEW TELETEXT CHIPS

from Mullard—available now from Marshall's—Sole UK distributor to the hobbyist market.

**SAA Series**, for the reception, display and control of television based text display systems. Suitable for 'CEE-FAX' and 'ORACLE' Remote Control

SAA5000 Infrared/Ultrasonic	£3.48
SAA 5010 Station selector/DICS	£8.13
SAA5012 Binary Input Tuners	P.O.A.
TELETEXT (Dedicated I.C.'s)	
SAA5020 TIC (Timing Chain)	£8.71
SAA5030 VIP (Video Input Processor)	£11.61
SAA5040 TAC (Teletext Data Acquisition and Control)	£31.82
SAA5050 TROM (Teletext Read-Only Memory)	£18.86

TIC, TAC & TROM are NMOS—VIP is linear bipolar

We recommend using DIL sockets with these chips

## TRANSISTORS (See catalogue for full range)

2N335	N70	3-00	2N706A	N70	-30	2N1370	P70	-55	2N2218	N70	-35	2N187	NF92	1-80	AC153K	P54	-50
2N338	N70	-80	2N708	N70	-30	2N1420	N70	-55	2N2218A	N70	-38	3N200	NF92	2-85	AC175K	N54	-70
2N388A	N70	-77	2N181A	N70	-54	2N1483	N70	-1.85	2N2219	N70	-38	3N201	NF92	1-35	AC176	N54	-54
2N390	N70	80	2N720A	N70	-85	2N1485	N70	2-20	2N2219A	N70	-39	40050	P66	1-70	AC187	N54	-59
2N456	P66	2-20	2N721	P70	-1.88	2N1507	N70	3-50	2N2220	N70	-39	40051	N70	1-20	AC187K	P54	-59
2N489	U71	4-00	2N722	P70	-45	2N1524	P54	-80	2N2221	N70	-25	40052	N70	-25	AC188	P54	-54
2N489A	U71	5-40	2N727	P70	-50	2N1553	P66	1-50	2N2221A	N70	-25	40053	N70	-70	AC188K	P54	-54
2N489B	U71	5-90	2N744	N70	-35	2N1613	N70	-30	2N2222	N70	-25	40055	N65	-65	AD136	P59	2-75
2N490	U71	4-90	2N753	N70	-35	2N1637	P70	-72	2N2222A	N70	-25	40037	N65	-45	AD142	P66	1-45
2N490B	U71	6-50	2N760	N70	-35	2N1638	P54	-70	2N2223	N70	6-78	40024	N65	-65	AD143	P66	1-45
2N490C	U71	6-90	2N809	N70	-35	2N1711	N70	-30	2N2223A	N70	6-99	40025	N66	-1-15	AD149	P66	2-85
2N491A	U71	5-75	2N814	N70	-35	2N1839	N70	7-00	2N2224	N70	-49	40025A	N66	-1-38	AD150	P66	3-10
2N491B	U71	6-25	2N816	N70	-33	2N1890	N70	-30	2N2227	N70	-49	40028	N70	-60	AD151	P66	1-00
2N491	U71	7-50	2N817	N65	-38	2N1893	N70	-30	2N2303	P70	1-54	40009	N70	3-70	AD162	P66	1-00
2N492	U71	6-25	2N818	N65	-45	2N1907	P66	5-95	2N2368	N70	-27	40039	N70	-60	AF106	P65	-80
2N492A	U71	7-75	2N829	N70	-37	2N1974	N70	-98	2N2369	N70	-27	40031	N66	-85	AF109	P65	-82
2N492B	U71	6-75	2N829A	N70	-37	2N1990	N70	-45	2N3369A	N70	-27	40031	N70	-55	AF114	P64	-70
2N492C	U71	10-00	2N930	N70	-37	2N1991	N70	1-10	2N3405	N70	-86	40032	N66	-99	AF115	P64	-70
2N493A	U71	7-99	2N930A	N70	-85	2N1992	N70	3-25	2N1402	NF92	-70	AC126	P54	-48	AF116	P65	-75
2N493B	U71	8-75	2N1131	P70	-32	2N2102	N70	-50	3N81	SCS90	3-50	40033	N66	-1-38	AF117	P64	-70
2N494	U71	6-90	2N1132	P70	-35	2N2147	P66	1-55	3N128	NF92	1-35						

# MAGENTA ELECTRONICS LTD

ECA, 85 CALAIS ROAD, BURTON-ON-TRENT, STAFFS DE13 0UL  
PHONE 02 83 65435. 9 a.m.-12. 2 p.m.-5. MON.-FRI. Callers by appointment.

## E.E. PROJECT KITS

Make us YOUR No. 1 SUPPLIER of KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Appropriate hardware—nuts, screws, I.C. sockets are included. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply—You construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. "PROJECT INSTRUCTIONS ONLY SUPPLIED AS EXTRA 39p EACH".

**SHAVEN INVERTER.** April 79. £10-99.  
**TRANSISTOR TESTER.** April 79. £3-18.  
**TOUCH BLEEPER.** April 79. £2-99.  
**ONE TRANSISTOR RADIO.** Mar. 79. With Amplifier & Headset. Less case. £5-84.  
**TIME DELAY INDICATOR.** Mar. 79. £4-08.  
**VERSATILE POWER SUPPLY.** Mar. 79. £7-38.  
**CHOKE WARNING DEVICE.** Apr. 79. £8-05 case 71p.  
**AUDIO MODULATOR.** Feb. 79. £1-44 less case and pins.  
**LW CONVERTER.** Feb. 79. £3-98, case £1-49.  
**THYRISTOR TESTER.** Feb. 79. £2-99  
**ADJUSTABLE PSU.** Feb. 79. £21-54. Case (horizontal layout) £3-54 extra.  
**I'M FIRST.** Jan. 79. £3-06 less cases.  
**LIGHTS REMINDER.** Jan. 79. £4-15  
**CONTINUITY TESTER.** Jan. 79. £2-91 less case.  
**FUZZ BOX.** Dec. 78. £4-36  
**VEHICLE IMMOBILISER.** Inc. PCB. Dec. 78. £3-77 case extra 71p.  
**WATER LEVEL ALERT.** Nov. 78. £4-82  
**"HOT LINE" GAME.** Nov. 78. £4-23 less case & rod.  
**AUDIO EFFECTS OSCILLATOR.** Nov. 78. £2-75 inc. board.  
**SUBSCRIBERS TELE TEL METER.** Nov. 79. £15-55 case extra £3-75.  
**FUSE CHECKER.** Oct. 78. £1-51.  
**C.MOS RADIO.** Oct. 78. £7-79.  
**TREASURE HUNTER.** Oct. 78. £14-44 less handle & coil former.  
**GUITAR TONE BOOSTER.** Sept. 78. £4-13 inc. p.c.b.

**SOUND TO LIGHT.** Sept. 78. £5-99  
**FILTER.** £1-25.  
**SLAVE FLASH.** Aug. 78. £2-66 less SK1.  
**LOGIC PROBE.** July 78. £2-29.  
**IN SITU TRANSISTOR TESTER.** June 78. £4-73.  
**VISUAL CONTINUITY CHECKER.** June 78. £2-95 inc. probes.  
**FLASHMETER.** May 78. £11-29. less calc and diffuser.  
**POCKET TIMER.** April 78. £2-82  
**WEIRD SOUND EFFECTS GENERATOR.** Mar. 78. £3-64.  
**CHASER LIGHT DISPLAY.** Feb. 78. £19-78. Inc. p.c.b. case extra £3-54.  
**AUDIO VISUAL METRONOME.** Jan. 78. £4-22.  
**RAPID DIODE CHECK.** Jan. 78. £1-97  
**AUTOMATIC PHASE BOX.** Dec. 77. £9-45 inc. p.c.b.  
**VHF RADIO.** Nov. 77. £11-46.  
**ULTRASONIC REMOTE CONTROL.** Nov./Dec. 77. £13-75.  
**TREASURE LOCATOR.** Oct. 77. £8-77 case extra. £2-32. Less handle, etc.  
**ELECTRONIC DICE.** March 77. £4-20.  
**SOIL MOISTURE INDICATOR.** June 77. £3-09 inc. probe.  
**PHONE/DOORBELL REPEATER.** July 77. £5-27.  
**SHORT WAVE RECEIVER.** Aug. 77. £10-95 case extra £1-49.  
**CAR BATTERY STATE INDICATOR.** Sept. 78. £1-54 less case inc. PCB.  
**R.F. SIGNAL GENERATOR.** Sept. 78. £15-30 less case.  
**TRANSISTOR TESTER.** Oct. 77. £5-34 case extra £3-55.  
**ELECTRONIC TOUCH SWITCH.** Jan. 78. £1-44.  
**ADD-ON CAPACITANCE UNIT.** Sept. 77. £4-46.

ALL PRICES INCLUDE VAT AND FIRST CLASS POST. ADD 25p TO ORDERS UNDER £5.



## TEACH-IN-78 COMPLETE KIT £14-98

INCLUDES FREE COMPONENT IDENTIFICATION CHART. TEACH-IN REPRINTS EXTRA 39p. EACH PART. ALL 12 PARTS AVAILABLE.

## 1979 ELECTRONICS CONSTRUCTORS CATALOGUE

HAVE YOU GOT YOUR COPY YET? MAGENTA'S NEW CATALOGUE INCLUDES MANY NEW PRODUCTS — CAREFULLY CHOSEN FOR EVERYDAY ELECTRONICS READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR CONSTRUCTORS. FULLY INCLUSIVE PRICES RIGHT NEXT TO THE PRODUCTS MAKE ORDERING EASY. NO MINIMUM ORDER — ALL PRODUCTS STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE!  
WRITE TODAY ENCLOSING 4 x 9p STAMPS.

**BUZZER.** 6V 74p. 12V 77p.  
**F.M. INDOOR AERIAL.** 49p.  
**TELEPHONE PICK-UP COIL.** 65p.  
**SPEAKERS.** Miniature 8 ohm 79p. 64 ohm 89p. 80 ohm £1-15.  
**EARPIECES.** Crystal 38p. Magnetic 15p.  
**STETHOSCOPE ATTACHMENT** fits our earpieces 58p.  
**HEADPHONES. MONO.** 2K Padded Superior Sensitive. £2-98.  
**HEADPHONES. STEREO.** 8 ohm. £3-85.  
**INTERCOM. 2 STATION.** £5-45.  
**MICROPHONE DYNAMIC 600 OHM CASSETTE TYPE** with 3-5mm jack plug and plastic desk stand. £1-25.

**MULTIMETER TYPE 1.** 1,000 o.p.v. with probes 2" x 3/4" x 1" £5-95.  
**MULTIMETER TYPE 2.** 20,000 o.p.v. with case and probes 5" x 3 1/2" x 1 1/2" £12-45.  
**ANTEX X25 SOLDERING IRON 25W.** Ideal for electronics £3-95.  
**SOLDERING IRON STAND.** ANTEX ST3 £1-84.  
**DESOLDER BRAID.** 62p.  
**HEAT SINK TWEEZERS.** 13p.  
**DESOLDER PUMP.** Easy to use £5-98.  
**SIGNAL INJECTOR.** £4-98.  
**DENTISTS MIRROR.** Adjustable £2-15.  
**JEWELLERS EYEGGLASS.** 95p.  
**TRIPLE MAGNIFIER.** £1-48.  
**SPRINGS—SMALL 100 Ass'd.** 98p.  
**CROC CLIP TEST LEAD SET 10 leads** with 20 clips 96p.

## DOING IT DIGITALLY

Complete kit IN STOCK NOW for FAST DELIVERY by FIRST CLASS POST. All top quality components as specified by Everyday Electronics. Our kit comes complete with FREE TTL and COMPONENT IDENTIFICATION CHART. £22-95 for the TTL TEST BED. £3-75 for ADDITIONAL COMPONENTS for first 6 Months. NEXT 6 MONTHS PARTS—Send Stamped Addressed Envelope for details.

TRAIN AT HOME

# Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs. Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer. You risk nothing! We promise to get you through your chosen course—or refund your fee! So, join the thousands who have built a new future through home study Engineering courses.

- Courses in
- C & G Elect. Technicians
  - C & G Elect. Installations
  - Telecomms. Technicians Exams
  - Television Servicing
  - Radio Maint. & Repairs (BIET)
  - Pract. Radio & Electronics
- Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE


## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept. TEE44 Reading RG7 4PF.

NAME (Block capitals please) \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
POSTCODE \_\_\_\_\_  
Other Subjects \_\_\_\_\_ AGE \_\_\_\_\_  
Accredited by CACC Member of ABCC

**SINCLAIR PRODUCTS** microvision tv world model £147-95. UK model £89-95, mains adaptor £6-78. PDM35 £29-95, mains adaptor £3-18, case £3-19. DM350 £68-95. DM450 £97-95. DM235 £49-45, rechargeable batts £7-50, mains adaptor £3-70, case £8-45. Enterprise prog calculator with accessories £22-95. Cambridge prog calculator £12-13, prog library £4-45, mains adaptor £3-29. PFM200 £49-48. CSC MAX100 freq. meter £75-40.  
**CALSCOPE** oscilloscopes send see for data or see the Calscope advert in this magazine. Super 6 £174. Super 10 £236.  
**COMPUTER GAMES** chess challenger 10 £167. Chess challenger 7 £79. Checker challenger £24. Checker challenger 2 £50. Atari videocomputer £138. Cartridges £13-45.  
**COMPONENTS** send see for full list. 1N4148 1-4p. 1N4002 2-9p. 741 15p. Bc182b, Bc183b, Bc184b, Bc212b, Bc213b, Bc214c. 4-5p resistors 1W 5% £12 10R to 10M 1p. 0-9p for 50% of one value. 16V electrolytics 5/12/5/10/22uf 5p, 100uf 8p, 1000uf 10p. 1 lb FeCl £1-05. Dalo pen 79p. 60sq ins pcb 55p.  
**TV GAMES** send see for data. AY-3-8500 + kit £8-95. Rifle kit £4-95. AY-3-8600 + kit £12-98. Stunt cycle chip + kit £15-70. Tank battle kit £4-50.  
**TRANSFORMERS** 6-0-6v 100ma 74p, 1ja £2-35. 6-3v 1ja £1-89. 9-0-9v 75ma 74p, 1a £2, 2a £2-60. 12-0-12v 100ma 96p, 1a £2-49.  
**IC AUDIO AMPS** with pcb. JC12 6W £1-60. JC20 10W £2-95. Send see for data.  
**BATTERY ELIMINATORS** 3-way type 6/7/9v 300 ma £2-95. 100ma radio type with press-studs 9v £3-35. 9v+9v £4-50. Car converter 12v input, output 4 1/2/6/7/9v 300ma £2-50.  
**BATTERY ELIMINATOR KITS** send see for data. 100ma radio types with press-studs 4 1/2v £1-40, 6v £1-40, 9v £1-40, 4 1/2v £1-80, 6+6v £1-80, 9+9v £1-80. Stabilized 8-way types 3/4 1/2/7/9/12/15/18v 100ma £2-80. 1Amp £2-40. Stabilized power kits 2-18v 100ma £3-60. 2-30v 1A £6-95. 2-30v 2a £10-95. 12v car converter 6/7/9v 1a £1-35.  
**T-DEC AND CSC BREADBOARDS** i-dec £4-62, u-deca £4-40, u-dach £6-73. exp300 £6-21, exp350 £3-40, exp325 £1-73. exp4b £2-48.  
**BI-PAK AUDIO MODULES** £450 £23-51. AL60 £4-96. Pa100 £16-95. Spm80 £4-47. Bmt80 £5-95. Stereo 30 £20-12. AL30 £3-95. PA12 £7-60. PS12 £1-39. MA60 £35-44.  
**SWANLEY ELECTRONICS**  
Dept. EE, 32 Goldsai Rd., Swanley, Kent.  
Post 30p extra. Prices include VAT. Official and overseas orders welcome.


## PRECISION HAND TOOLS

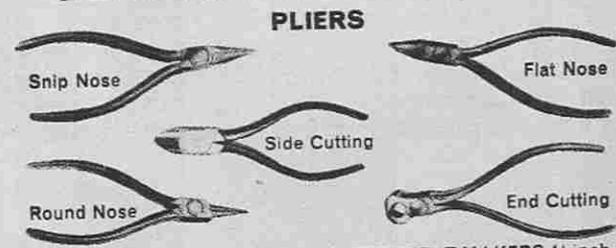

SIZES: WATCHMAKERS 4 inch; INSTRUMENT MAKERS 4 1/2 inch  
British-made precision box-jointed hand tools with insulated handles, each tool packed in an attractive pvc wallet.  
Only £3-95 each OR any 3 tools FOR ONLY £11-25 inc P&P

C.W.O. to QUINTON TOOL SUPPLIES, Dept. E.E., 52 Grayswood Park Road, Birmingham B32 1HE
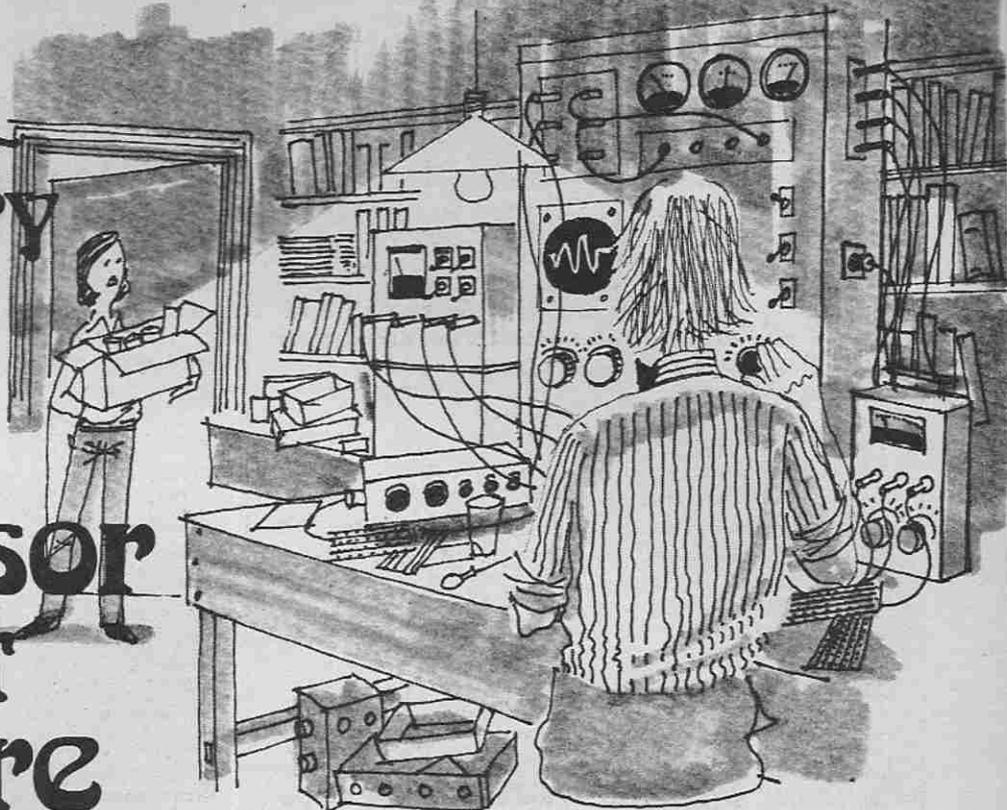
# The Extraordinary Experiments of Professor Ernest Eversure



by Anthony John Bassett

Bob and the Prof. are inside a giant vacuum chamber. Dressed in "space suits" which the Prof's robots have made to protect them from the vacuum, they are carrying out experiments on uses of electronics in vacuum conditions. As Bob and the Prof. are both keen followers of the Space Explorations which are in progress, they can see that there is certain to be a large expansion in the use of electronics in the vacuum of Space; a very interesting field to follow and one which will in future provide an increasing number of really interesting jobs for electronics experts.

Who knows, some of today's readers of this magazine might be fortunate enough to participate in this exciting work!

## ELECTRON BEAM

Bob has noticed that an electron beam when passed through various vapours which the Prof. has released into the vacuum chamber, does not appear to be scattered by collision with the molecules of vapour; rather to his surprise, the opposite seems to happen and the presence of the vapour molecules seems to improve the focusing of the electron beams.

They can observe the electron

beam directly in the presence of certain vapours which glow with the spectral colours of the elements or ions present along the path of the beam.

"It is the presence of a trail of positive ions along the path of the electron beam which keeps the path of the beam narrow and prevents the electrons from being scattered," the Prof. informed Bob.

"When an electron beam passes through a vapour or gas at low pressure, it produces mainly positive ions from the atoms or molecules which it encounters. Thus the presence of a gas vapour is necessary in order to observe this effect."

"I find this very puzzling, Prof. Surely the beam should produce equal numbers of positive ions and negative ions? At school we are taught that when an ionising beam passes through a gas or vapour, it spits the molecules into equal numbers of opposite charges! How can the electron beam produce more positive ions than negative ions when the molecules of the substance are neutral to start with?"

The Prof. explained: "This is because the mechanism of ion production is different. With a beam of ionising radiation, the

radiation is so energetic that it splits the molecules up into ions of opposite charge. The oppositely charged ions fly apart under the influence of the radiation bombardment, and exist as charged particles for a time until they become neutralised.

"The electron beam which we are using behaves differently and the predominant mechanism of ion production is by 'knocking off' electrons from the outer electronic shells of atoms to produce simple ions, or vapour molecules to produce more-complex positive ions. Only a small number of molecules are split, so the production of negative ions along the path of the electron beam is comparatively little."

## CORE OF POSITIVE IONS

"The positive ions are much heavier than electrons and they remain in the path of the electron beam to give a 'pencil' of positive charge along the path of the beam, and this tends to keep any electrons which tend to stray or scatter, attracted back to the path of the beam, thus improving the focus of the beam and the 'point size' where it may hit a fluorescent viewscreen or radar screen.

"Most of the electrons which are

picked off to do not join the main electron beam, but travel for a short distance away from the beam, and then combine with a neutral molecule to form a negative ion. Thus, surrounding the beam and its core of positive ions is a tube of negative ions which help to keep the electrons of the beam on the correct path, as any which stray are repelled back by the negative charge.

## BETTER RADAR

"This combined action of attraction by a positive column of ions and repulsion by a surrounding tube of negative ions, is a powerful influence in keeping the electrons to a narrow path to give a finely focused radar display.

"Use of this technique has resulted in very considerable savings in cost of production of radar sets, because the electron beam can remain focused with a much lower e.h.t. voltage than would be needed for a radar tube which used a high vacuum. The radar tube itself can be cheaper because it does not need a separate e.h.t.

connection. Due to the lower voltage used, this may be connected in some cases on an ordinary tube base.

"The power supply is much simpler, and because the velocity of the electrons in the beam is lower, less deflection energy is needed, which means that the deflection circuits are less critical and less likely to go wrong!

"So, just by introducing a very small quantity of gas into each radar tube, the makers have contributed to the spread of the safety which has been brought about by the increased use of radar, both by making it affordable for more users and more reliable!

"Just as the developments in rocketry by the Germans during World War II were very important in forming the basis for the development of modern space rockets, so the British developments in radar and ion beam technology are now being taken further, and the behaviour of such beams in the conditions of space will be very important for future

explorations and uses. Such beams may be used to probe areas where men cannot go!"

"This sounds really interesting, Prof., can you tell me more about the use of electronically produced beams in space?"


"Yes, certainly, Bob."

To be continued

## Crossword No. 16—Solution

1	T	W	I	2	N	C	O	3	R	E	4	B	U	Z	5	Z	6	R
	E				O		E		O		O							U
7	R	E	R	I	A	R	L	L	Y	O	8	D	O	W	N			
	C	S			I						9	S	H	I	M	A		
10	H	A	11	T	E	12	C	13	E	T	G							W
	I	H					A		14	E	15	N	I	16	M	A		
17	N	E	E	D	18	Y			19	P	I	R	A	T	E	Y		
							R	O		P		P	M					
20	P		21	A	22	K	23	L	I		24	H	I	F	25			
26	E	F	U	E	L		N								N	E		
	O	L			27	O	G	28	C		29	I	G	S				
J		30	L	M	O				M					E				T
31	E	N	D	S	Y			32	R	T	A	C	O	M	B			
	C	I			E				G					K				E
33	I	T	L	E	D			34	K	E	Y	B	O	R	R	D		
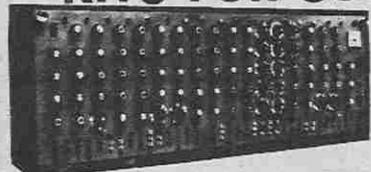
## KITS FOR SOUND EFFECTS AND OTHER PROJECTS



### GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7-89

Alternative component set with panel switches £5-85

Printed circuit board £1-43

### GUITAR FREQUENCY DOUBLER

(P.E. Aug. 77)

A modified and extended version of the circuit published.

Component set and PCB £4-52

### GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual rotary pot £6-89

Printed circuit board £1-62

### GUITAR SUSTAIN (P.E. Oct. 77)

Maintains the natural attack whilst extending note duration.

Component set, PCB and foot switches £3-13

Component set, PCB and panel switches £3-71

### WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) £4-26

### COMPONENTS SETS

Include all necessary resistors, capacitors, semi-conductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately.

### 10% DISCOUNT VOUCHER (EE94)

TERMS: Goods in current adverts & lists over £50 goods value (excl. P&P & VAT). Correctly copied. C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of E.E.

ADD: POST & HANDLING U.K. orders—Keyboards add £2-00 each plus VAT. Other goods: under £15 add 25p plus VAT, over £15 add 50p plus VAT. Recommended: optional insurance against postal mishaps, add 50p for cover up to £50, £1-00 for £100 cover, etc. pro-rata.

N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

## PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

### VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3-97

### PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the phasing sound into live or recorded music.

Component set (incl. PCB) £3-20

### PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4-74

### TREMOLO UNIT

Based upon P.E. Sound Design circuit

Component set (incl. PCB) £2-94

### TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) £2-51

### WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3-63

### AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7-67

Component set and PCB, with panel switches £4-83

### PHOTOCOPIES

of texts for most of the kits are available—prices in our lists.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

### ADD 12% VAT

(or current rate if changed). Must be added to full total of goods. Discount, post & handling, on all U.K. orders. Does not apply to Exports.

### EXPORT ORDERS

ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list—Europe send 20p, other countries send 50p.

PRICES ARE CORRECT AT TIME OF PRESS. E.O.E. DELIVERY SUBJECT TO AVAILABILITY.



### FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit

Component set (incl. PCB) £2-05

### P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.

Main component set (incl. PCB) £14-93

Power supply set (incl. PCB) £6-20

### SYNTHESISER TUNING INDICATOR

(P.E. July 77)

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl. sw.) £7-45

### DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4-58

### CONSTANT DISPLAY FREQUENCY

METER (P.E. Aug. 78)

A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.

Component set £24-05\*

Printed circuit board £3-03\*

\*This kit & PCB are at 8% VAT (all others are 12%)

### MANY MORE KITS

for Synthesisers, Rhythm Generators, Electronic Pianos and other projects, big, small, simple or complex, are available, plus a range of keyboards, separate components and accessories. Details in our lists.

### PHOTOGRAPHS

in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL: 01-382 8184)

PHONOSONICS • DEPT. EE94 • 22 HIGH STREET • SIDCUP • KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL: 01-382 8184)

## ROOM THERMOSTAT

Famous Satchwell, elegant design. Intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0.30 C. Special snip this month £3.25.  
**ROD THERMOSTAT—£3.00.**

## WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make £3.75.

## MICRO SWITCH BARGAINS

Rated at 5 amps 250V. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 (two types) for £1.25.

## RADIO STETHOSCOPE

Easiest way to fault find, traces, signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set £3.95.

## MULTISPEED MOTORS

Six speeds are available 500, 800 and 1,000 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 1/2 in. diameter and approximately 1 in. long. 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price £2.

## 12V MINIATURE RELAY

Operated with two sets of change over contacts. The unique feature of this relay is its heavy lead out wires; these provide adequate support and therefore the relay needs no fixing; on the other hand there is a fixing bolt protruding through one side so if you wish you can fix the relay and use its very strong lead outs to secure circuit components—an expensive relay; but we are offering it for only 37p each. Don't miss this exceptional bargain!

## EXTRACTOR FAN

Ex computers—made by Woods of Colchester. Ideal for fixing through panel—reasonably quiet running—very powerful 2500 rpm. Choice of two sizes 5" or 6 1/2" dia. £5. £6.

## MAIN RELAYS

With triple 10 amp changeover contacts—operating coil wound for 230V a.c. Chassis mounting one screw fixing. Price £1.25.

## BURGLAR ALARM ITEMS

(Circuit free on application)

Trigger mats 24" x 18" 13" x 10"

Relay 24 volt 95p

9-12 volt 95p

Alarm Bell 24 volt £7.50

9-12 volt £2.25

Reset, Switch, ordinary 45p

Secret type with key 95p

Wire—100 metres £1.50

24v Power unit mains operated £2.35

## MERCURY BATTERIES

Bank of 7 Mercury cells type 625 which are approx. 1/2 in. diameter by 7/8 in. thick in plastic tube giving a total of 10-17V. Being in a plastic tube it is very easy to break up the battery into separate cells and use these for radio control and similar equipment. Carton of 25 batteries £1.60.

## PP3/PP9 REPLACEMENT

Japanese made in plastic container with leads size 2in. x 1 1/2in. x 1 1/2in., this is ideal to power a calculator or radio. It has a full wave rectifier and smoothed output of 9V suitable for loading of up to 100mA. £2.33.

## SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on slightest pressure. For burglar alarms, shop doors, etc. 24in. x 13in. x 10in. £1.95.

## MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.95.

## CONTROL DRILL SPEEDS

## DRILL CONTROLLER

Electronically changes speed from approximately 10 rps to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45

Made up model £1.00 extra

## 8 POWERFUL BATTERY MOTORS

For models, Meccanos, drills, remote control planes, boats, etc. £2.

## ROTARY PUMP

Self priming, portable, fits drill or electric motor, pumps up to 200 gallons per hour depending upon revs. Virtually uncorrodable, use to suck water, oil, petrol, fertiliser, chemicals, anything liquid. Hose connectors each end. £2.

## SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 10, 20, 25, 31 metre bands. Kit contains chassis front panel and all the parts £1.94—crystal earphone 35p including VAT and postage.

## MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of speakers this should sell at about £30—but due to a special bulk-buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.

## HUMIDITY SWITCH

American made by Ranco, their type No. J11. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive micro-switch adjustable by a screw, quite sensitive—breathing on it for instance will switch it on. Micro 3 amp, at 250V a.c. Overall size of the device approx. 3 1/2 in. long, 1 in. wide and 1 1/2 in. deep 75p.

## DELAY SWITCH

Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact 95p.

## 25A ELECTRIC PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours independent 60 minute memory jogger. A beautiful unit. £3.50.

## MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied Model 1153 500mW, power, output £1.69.  
Model 1172—10 watts power output £3.94  
Model 1173—1W, power output £2.25.  
Model EP9000 4 watt power output £2.80  
EP 9001 twin channel or stereo pre-amp £2.90.

## G.P.O. HIGH GAIN AMP/SIGNAL TRACER

In case measures 5 1/2 x 3 1/2 x 1 1/2 extremely high gain (70 dB) solid state amplifier designed or use as a signal tracer on GPO cables etc. Functions very well as a signal tracer for fault finding in radios etc. etc. By connecting a simple coil to the input it becomes a useful mains cable tracer. Uses standard 4 1/2v battery and has input, output sockets and on-off volume control mounted flush on the top. Many other uses include general purpose amp, cueing amp etc. An absolute bargain at only £2.25. Suitable 80 ohm earpiece 60p + 5p.

## THERMOSTATS

Refrigeration as illustrated with 36" capillary £1.62.  
Limpet Stat must be mounted in close contact calibrated 90°-190°F 15 amp contacts £1.62.

Appliance Stat fix like a volume control—15 amp contact 30°-30°F 85p, ditto but for high temps £1.25.  
Over Switch—with Serson and capillary 85p

Wall Mounting by Satchwell £3.00

## SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £9.95.

## MINI-MULTI TESTER

Amazing, deluxe pocket size precision moving coil instrument jewelled bearings—1000 opv—mirrored scale. 11 instant ranges measure—DC volts 10, 50, 250, 1000 AC volts 10, 50, 250, 1000 DC amps 0-1mA and 0-100 mA. Continuity and resistance 0-150k Ohms. Complete with insulated probes, leads, battery, circuit diagram and test instructions.

Unbelievable value only £6.50 + 50p post and insurance.  
FREE Amps ranges kit enable you to read DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester would like one send £1.50p.

TERMS: Cash with order—but orders under £8 must add 50p to offset packing, etc.  
BULK ENQUIRIES INVITED. PHONE: 01-688 1833.  
ACCESS & BARCLAYCARD ACCEPTED.

**J. BULL (ELECTRICAL) LTD**  
(Dept. E.E.), 103 TAMWORTH RD.,  
CROYDON CR9 1SG

## IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

**Telephone Ringing Mains Unit** Rather novel unit as it not only reduces mains to 50 volts but also reduces the mains frequency to 25 Hz, this frequency gives correct ringing note for GPO bells. These units were made for the GPO so obviously are first class. Completely enclosed and safe to mount on the wall or stand on a shelf. Price £3.20.

**Telephone Extension Bells** in bakelite wall box, these will save you missing calls when you are out in the garden or shed, etc. Price £3.16.

**Variable Mains Supply** A bench mounting unit which contains an isolation transformer for safety and a 2 amp variac for adaptability. With this you will be able to get continuously variable mains supply from zero to full voltage at 2 amps. A real time saving device, price only £20.75.

**Answering Machines** still available, see this month's newsletter but supplies are going down rapidly and this may well be your last chance to acquire one of these. Spares + accessories also available.

A very large purchase this month enables us to offer a range of radio items. You will find the prices well below average. **Cassette Recorder/Player** Japanese or Hong Kong made, these have all the normal facilities record, playback, fast rewind, etc., also sockets for stop/start, microphone, earphone and lead for mains as these operate from mains or HP1 batteries. £9.50.

**AM/FM Radios** There's no doubt that FM does give better reproduction in good areas so a more ardent member of the family will be pleased with one of these. The ones we have are in leatherette cases and are battery/mains or with silver finish mains unit built in and are complete with mains plug. These cover medium wave and VHF with optional AFC. Price £6.75.

**Soft Toy Radios** Not necessarily only for the younger members of the family as these are soft and cute and have universal appeal. Dolls, poodles, elephants and rabbits each with zip compartment at the bottom where the radio fits. Medium wave only, working from PP3 batteries. When ordering please state preference and if possible give an alternative. £4.50.

**Car Battery Power Unit** made for Rank Radio. This unit has been designed to operate 6V battery powered equipment from a 12V car battery, it provides a reliable source of stabilised voltage and gives protection to your equipment in case of accident reversal of connections also against excessive car battery voltage should this occur. The unit is very robust and virtually everlasting if used sensibly. It uses a negative earth circuit but it will operate in a positive earth car providing the instrument being played is not connected to the car chassis. A real bargain at £2.20.

**Extension Speaker Cabinets** A new delivery of these enables us to bring down the price quite a lot. We can now supply the smaller ones (1 1/2 in. x 8 in. x 4 1/2 in. approx.) at £1.95. Post £1.00 and we have a larger one with silver finish size approximately 12 1/2 in. x 9 in. x 5 1/2 in. Price of this is £1.69, post £1.50. If you can call and collect these cabinets you can save yourself the quite considerable postage and you only have to pay a few to get a discount as well. The quantity discount for these is a special rate of 25% if you buy four or more. Note these cabinets are very good quality (made for Rank Audio Systems) the grill material is Durox.

**Slide Switch Bargain** Double pole changeover standard size with good length of connecting wire soldered to each tag—10 for £1.38.

**Six Digit Counter** Mains operated, 1 pulse moves counter through one digit, not resettable but all you have to do is to make note of the numbers before the start of each count. Real bargain at 80p.

We still have the fluorescent outfits for operating 12in tubes from 12V car battery and the price is still the same £3.95 plus 50p post complete with a 2in tube.

**Stereo Car Speakers** usual type in neat compact enclosures for the rear shelf of the car. 8 ohms 5 Watt. £4.50 per pair. **Bleepers** 6/12V battery or transformer operated, ideal for using in many alarm circuits but particularly for car and motor cycle alarms. These give a loud shrill note. American made by Delta Alarms. Price £1.08 + 8p. Large quantities available.

**Most useful Timer** Up to 12 on/off per 24 hours is what you can get from the Vanner time switch if you fit our adaptor. The shortest on/off time is one hour but you can use any combinations of on/off to make up the 24 hours. An obvious use for this is to control immersion heaters. These are real current consumers and even though the thermostats are working properly economies can be quite considerable if a time switch is used. Our Vanners are all capable of 20 amp switching. There are of course many other applications for the time switch, which you will remember in its basic form follows the sun switching on at dusk and off at dawn. Price £3.24 plus 50p post for switch with adaptor, extra for plastic case £1.08 or metal case £2.16 + 16p.

**Safe Soilstat** For growers who use soil heating on benches, economies can be made by using a thermostat but if mains voltage equipment is used then the thermostat must be enclosed in a waterproof and earthable container. We can now supply this price £3.78 + 28p. This container will accept the normal immersion heater type thermostat but for soil heating you want one which covers 50 deg. Fahrenheit and upwards, we can supply these at £3.20.

**Motivised Light Flasher** We can offer two motorised units both capable of 2,000W of light. Our second flasher changes every 1/2 second and the 2 second flasher changes every 2 seconds. Either type £6.40.

## BUSH "PARTY AMP"

This very attractive unit is a complete mono amplifier originally designed as the second channel BUSH record players. All solid state, the case houses good quality speaker, power supply, pre-amp and controls. Standard DIN socket input accepts ceramic cartridge direct, 240v operation. Brand new and boxed complete and screened DIN to DIN connection lead and instruction leaflet. Many uses include baby alarm, guitar practice amp, booster amp for transistor radios, etc. etc.

Two types available:  
Type 1 2-3 watts output with volume and tone control £7.50  
Type 2 4 watts output with volume, treble, bass, treble, volume controls and tape output £9.50 + 50p, PP £1.  
\*NOTE For use as baby alarm and guitar practice amp it may be necessary to use our phono preamplifier module (BML).

## 6 DIGIT COUNTER

One pulse at mains voltage moves 1 digit—not resettable—real bargain @ 80p.

## MAINS BLOWER

The Torrini—quiet but powerful outlet size 2 1/2 x 1 1/2 for cooling equipment etc. will extract if outlet is blowing outwards price £5.50.  
Other models from £2.00.

# The latest kit innovation!

from **Sparkrite**



the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

#### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing.

Electronics Design Associates, Dept. EE 5  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Electronics Design Associates, Dept. EE 6  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name .....

Address .....

Phone your order with Access or Barclaycard

Send SAE if brochure only required.

Inc. V.A.T. and P.P. (U.K. only.)

QUANTITY REQ'D.

I enclose cheque/PO's for

X4 KIT **£16.65**

TACHO PULSE  
SLAVE UNIT **£3.85**

£  
Cheque No.

PLEASE STATE POLARITY POS OR NEG EARTH.

Access or Barclaycard No. ....

GIVE YOUR

# LABCENTRE

THE CASE IT DESERVES

SENLAG SYSTEMS' super durable suede finish cases are plush lined, strong and yet easily adapted to suit custom needs.

Approx. internal clear dimensions  
18" wide × 13½" front to rear × 3" depth.  
450mm × 340mm × 75mm

Brief case style with locks & handle on 18" edge.

**ONLY £5.67 incl. VAT. P/P**

Full refund guarantee if returned unused within  
14 days of receipt.

Telephone for further details (callers welcome by appointment only) or send £5.67 by cheque or P/O's payable to

**SENLAG SYSTEMS [E & E] LTD.,**  
14 Dorset Square, London NW1 6QB  
Telephone (01) 894 3413



## ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.  
Bound in stiff linen. Cover size 8½in x 5in.  
Price £7.50 per set (we pay the postage).

- Book 1. Introducing Electronics    Book 4. Meters/Voltage-dividers  
Book 2. Resistors/Capacitors    Book 5. Transistor Project Circuitry  
Book 3. Inductors/Diodes

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Whailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm.

Order now:  
Selray Book Company  
60 Hayes Hill  
Bromley  
BR2 7HP

**OUR 100% GUARANTEE**  
Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £

Name: .....


Address: .....

EE17



Newnes

# constructors projects

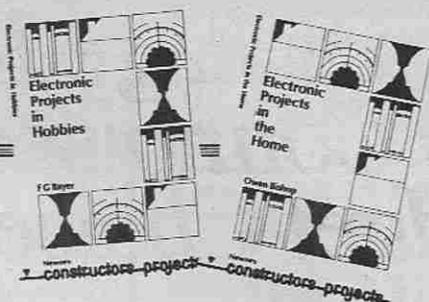

★ This new series has been specially compiled for the electronics enthusiast.

Each book contains a collection of constructional projects, giving details of how the circuit works, how it may be assembled and how setting-up and trouble-shooting problems may be solved. The skilful use of colour in the text helps to clarify circuit operation, and circuit board layouts are suggested. Shopping lists of components are drawn up for each project.

★ The first four titles are available now at £2.25 each (US \$5.25)

Electronic Projects in Audio *R. A. Penfold*  
Electronic Projects in Hobbies *F.G. Rayer*

Electronic Projects in the Home *Owen Bishop*  
Projects in Radio and Electronics *Ian R. Sinclair*

★ Also available six Constructors Guides:

Electronic Diagrams £1.80 US \$4.25  
Electronic Components £1.80 US \$4.25  
Simple Circuit Building £1.90 US \$4.50

Printed Circuit Assembly £1.80 US \$4.25  
Project Planning and Building £1.90 US \$4.50  
Practical Electronic Project Building £1.90 US \$4.50

Write for a free colour brochure about all our hobby books to


**Newnes Technical Books**

Borough Green, Sevenoaks, Kent TN15 8PH



# ALCON

BRING YOU THE NEW CHINAGLIA

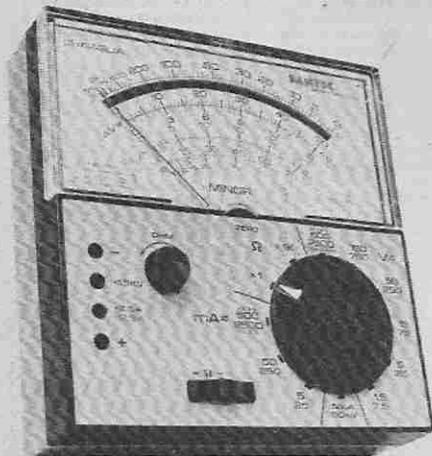

**MINOR  
POCKET  
MULTIMETER  
THE  
PROFESSIONAL  
SOLUTION  
TO  
GENERAL  
MEASUREMENT  
PROBLEMS**

£32.50 inc. VAT.

The best instrument for the workshop, school, toolbox, T.V. shop and anywhere accurate information is needed quickly and simply


**IT OFFERS:**

- ★ Single-knob range selection
- ★ 110° Full-view mirror scale and fine line pointer
- ★ Clear unambiguous scales
- ★ A well-damped cylindrical magnet movement with resilient bearings
- ★ 31 ranges providing coverage from 150mV to 1.5kV d.c.; 7.5V to 1.5kV a.c. 50μA to 2.5A d.c.; 25mA to 12.5A a.c.; 10kΩ and 10MΩ resistance and six signal level ranges.
- ★ Accuracy ± 2.5% d.c., ± 3% a.c. and 2% resistance.

For details of this and other exciting Alcon instruments please write or phone:—

**ALCON** Instruments Ltd.

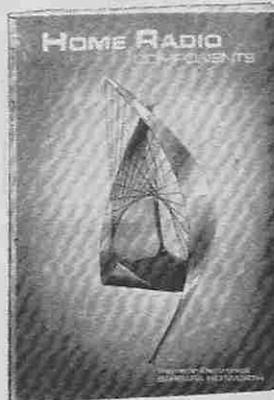19 MULBERRY WALK, LONDON SW3 6DZ. TEL: 01352 1897



## EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.25 with a free bargain list. Send your cheque or postal order now.

**HOME RADIO COMPONENTS LTD.**  
Dept. EE, 234 London Road  
Mitcham, Surrey CR4 3HD



**ACE MAILTRONIX LTD**  
Dept. EE Tootal Street  
Wakefield, W. Yorkshire WF1 5JR

## TOPS THE PACK!

- COMPONENTS** — Now over 1,000 types in stock!
- KITS** — See the new range of low-cost 'ELEKITS'.
- SERVICE QUALITY** — 1st Class same day despatch.
- PRICES** — All guaranteed products.
- MAGAZINE PROJECTS** — Many reductions!
- Trouble-free!

S.A.E. for list of EE projects

I enclose 30p\*, please send catalogue.

Name \_\_\_\_\_  
Address \_\_\_\_\_

\*Refundable with future orders over £5.00.


# BD1 Package Kit- The Connoisseur's Budget Choice

Connoisseur now offer their famous BD1 Kit in a package deal.

The package consists of the BD1 Kit, SAU2 pick-up arm, plinth with anti-vibration feet, acrylic cover complete with hinges and friction lid stays, a pick-up mounting board, and all necessary screws, washers, etc. The plinth, cover and pick-up mounting board are all pre-drilled and ready for assembly.

The illustration shows the package with the BD1 Kit partially assembled.

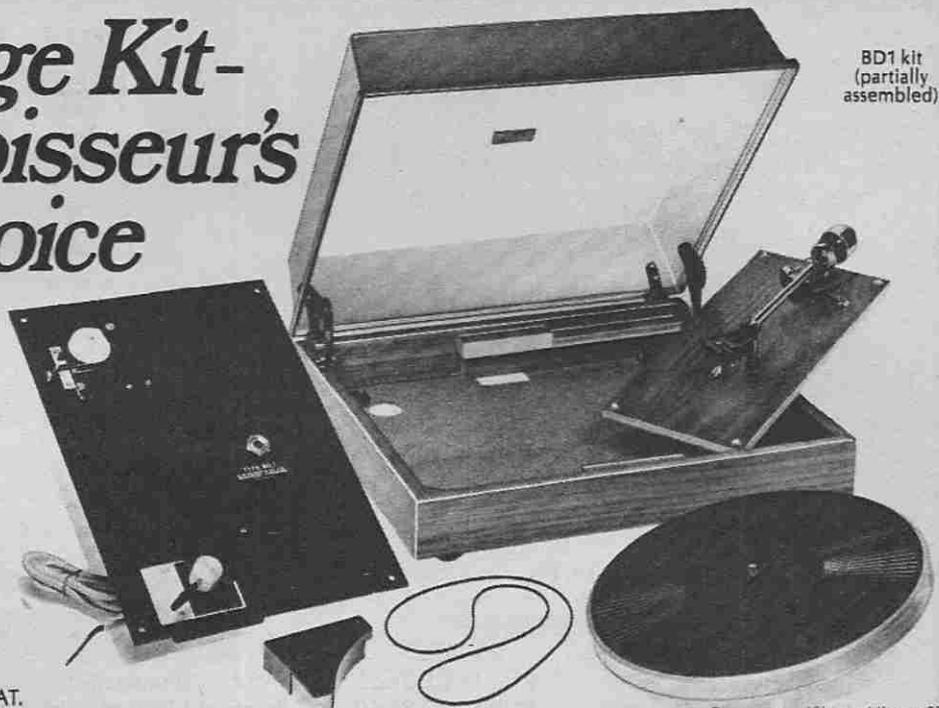Suggested Selling Price around £54.00, plus VAT.



BD1 kit (partially assembled)

Dimensions: 16 1/2in x 14 1/2in x 5 1/2in

# Connoisseur

Write for further details to:  
A. R. Sugden & Co. (Engineers) Ltd.  
Manufacturers of Connoisseur Sound Equipment, Connoisseur Works, Atlas Mill Road, Brighouse, West Yorkshire HD6 1ES  
Telephone: Brighouse (0484) 712 142, Telex: 517144 Sugden G,  
Telegrams & Cables: Connoisseur Brighouse.


## TRUE AS AN *Arrow*



Professional Wire and Cable Fasteners for all installation requirements.

TELEPHONE - ELECTRONICS  
COMMUNICATIONS  
ALARM SYSTEMS, ETC.

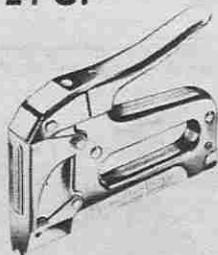4 Precision made models.  
12 different staple sizes.  
Rugged all steel construction in chrome finish.  
Grooved guide.  
Grooved driving blade.  
Tapered striking edge.  
Jam-proof mechanism (patented).  
Short span easy compression handle.



Some of the features that make an Arrow cable fastener the outstanding tool for all installation engineers.

Illustrated literature and details of staple sizes available from:

### SPECIAL PRODUCTS DISTRIBUTORS LTD.

81 PICCADILLY, LONDON W1V 0HL  
TEL. 01-629 9554. Telex 265200 (A/B RACEN)

Cables: Speciproduct London W1

# ELECTROVALUE

Your leading direct suppliers for  
**CAPACITORS**

Ceramics, all types, TANTALUM BEAD, SILVER MICA, POLYESTERS, VARIABLES, ETC. ETC.

Including			
<b>POLYSTYRENE,</b>			
B31110 160V	1-0	100	12p
5, 7, 10, 12pF	2-2	25	12p
15, 22, 27, 33pF	8p	2-2	63
39pF	8p	2-2	100
47, 56, 68, 82pF	7p	4-7	15
100, 120, 150pF	7p	4-7	40
180, 180, 220pF	7p	4-7	63
270 330 390pF	7p	4-7	100
470 560pF	7p	10	6-3
	7p	10	25
	10	40	12p
	10	63	14p
	10	100	15p
<b>POLYSTYRENE,</b>			
31310, 160V	5p	22	10
560, 680, 820pF	5p	22	25
1000, 1500pF	5p	22	40
2200, 3300pF	8p	22	63
1200, 1800pF	8p	22	100
2700, 3900pF	8p	22	100
4700, 5600pF	8p	22	100
8800, 8200pF	8p	47	3
10,000pF	8p	47	10
12,000, 15,000pF	12p	47	25
18,000, 22,000pF	12p	47	40
	12p	47	63
	12p	47	16p

ELECTROLYTIC CAPS			
Daily, sleeved			
1000/25	20p		
2200/50	75p		
6000/25	75p		
4700/100	2-75		
<b>ELECTROLYTIC,</b>			
axial lead			
Siemens B41313/			
B41283/B41010			
µF volts			
0-47 63	21p	150	18p
0-47 100	12p	220	20p
1-0 40	21p	330	20p

SILVERED MICA, 350V  
1% (or 1pF)  
R611, 12-7 x 8mm  
All in pF.  
2-2, 3-3, 5  
6-8, 10, 15  
18, 20, 22, 25  
27, 30, 33  
35, 47, 50  
55, 68 each  
100  
150  
220  
330

Hundreds of other values stocked—see pages 11 to 16, Catalogue 9.  
VAT—Add 8% to quoted prices, except for items marked \* to which 12% must be added. Prices subject to alteration without prior notice discounts non-allowable on Access or Barclaycard.

## ELECTROVALUE LTD

Dept E.E.6, 24 St. Judes Rd, Englefield Green, Egham, Surrey TW20 0HB.  
Phone Egham 3603. Telex 264475.  
Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

● We pay postage

In U.K. on C.W.O. orders list value £5 and over. If under, add 27p handling charge.

● We give discounts

on C.W.O. orders only  
3% on orders list value £10 or more  
10% on orders list value £25 or more

● We stabilise prices

by keeping to our printed price lists which appear but three or four times a year.

● We guarantee

all products brand new, clean and to makers' specs. No seconds, no surplus.

● WE WILL SEND OUR 120 PAGE CATALOGUE No. 9 FREE ON REQUEST

Comprehensive, informative, well produced. Write, phone or call for your copy together with latest price list


**THE NEW**

# EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-coil system and built in safety guard. Only £6.80 inc. VAT & P.P.

**THE UNIQUE**

# EUROBREADBOARD

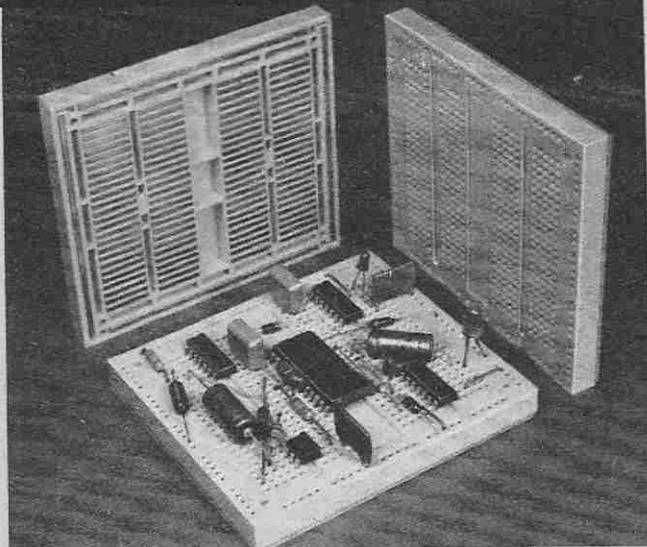

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (<10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF



David George Sales  
r/o 74 Crayford High Street,  
Crayford, Kent, DA1 4EF.

EE 6/79

Please send me  1 EuroSolderSucker @ £6.80  Please  
or  1 EuroBreadBoard @ £5.80  Tick  
or  2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).

Name .....

Company .....

Address .....

Tel. No. ....

Please make cheque/P.O.'s payable to David George Sales.

## BUILD A SYNTHESISER!

**NO SPECIAL SKILLS REQUIRED  
SPECIAL EQUIPMENT**



Using **Dewtron** (Reg'd)  
**PROFESSIONAL MODULES**

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

**D.E.W. LTD.**

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR

## Clef Kits

Designer approved quality kits for Electronic Musical Instrument Construction.


### JOANNA 72 & 88 PIANOS

Six and 7 1/2 Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. A new physical layout has been adopted to simplify construction.

### P.E. STRING ENSEMBLE

The only kit available to the proven A. J. Boothman Design for this versatile String Machine.

Sent S.A.E. to:

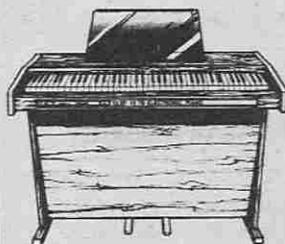

**Clef Products (Dept E.E.)**  
16 Mayfield Road, Bramhall, Cheshire SK7 1JU.

## QUALITY REEL TO REEL & CASSETTE TAPE HEADS

MONOLITH	SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS		
B12-01 MONO PLAYBACK . . . . .	£1.84	E12-09 MONO/STEREO ERASE . . . . .	£1.80
B12-02 MONO RECORD/PLAYBACK . . . . .	£3.92	B22-02 TWIN HALF TRACK RECORD/PLBK	£5.82
B24-01 STEREO PLAYBACK . . . . .	£3.22	C44RP502 QUAD QUARTER TRACK REC/PLBK	£9.14
B24-02 STEREO RECORD/PLAYBACK . . . . .	£6.50	C22E502 TWIN HALF TRACK ERASE . . . . .	£4.60
B24-RP STEREO GLASS FERRITE REC/PLBK	£11.32	MAGNETIC TAPE HEADS CATALOGUE 25 PENCE	

AUDIO AND HI-FI CATALOGUE 180 PAGE FULL COLOUR! 50 PENCE

**MONOLITH**  
THE MONOLITH ELECTRONICS CO. LTD.  
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0450) 74321

PLEASE ENCLOSE 25p P&P WITH ORDER  
ALL PRICES INCLUDE VAT

# LOOK!

## Here's how you master electronics.

.... the **practical** way.


This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

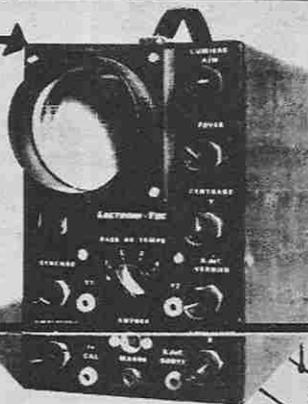
### 1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


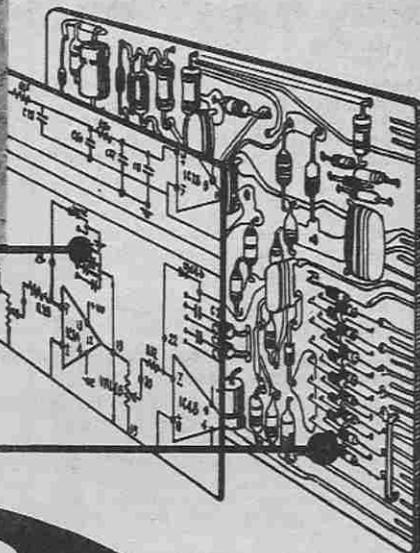
### 2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



### 3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

### 4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

# FREE

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**


P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

EEB/6/79

Block caps please

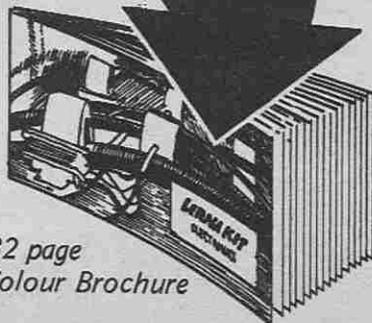

32 page  
Colour Brochure



### NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### Receivers and Components

**DISCOVER ELECTRONICS.** Build forty easy projects including: Metal Detector; Wireless Transmitter; Breathalyser; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms, etc. Circuits, plans all for £1.29 including FREE circuit board. Mail only. RIDLEY PHOTO/ELECTRONICS, Box 62, 111 Rockspark Road, Uckfield, Sussex.

### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-25 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4-50 plus 25p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P.

LOTS MORE! Send 25p for lists.

Prices include VAT.

### BOFFIN PROJECTS

4 CUNLIFFE ROAD, STONELEIGH  
EWELL, SURREY. (E.E.)

**ELECTRONIC COMPONENTS** and E.E. project kits 1973-now. Catalogue SAE, plus 30p. Jadebond Ltd. Middridge Drift Ind. Est., Middridge, Shildon, Co. Durham. Tel: Shildon (038 884) 3845.

**71b ASSORTED COMPONENTS** £3.60. 3 1/2 lb £2-10. Small Audio Amplifiers. 3 Transistors equivalent to AC128, OC72, with circuit, 3 for £1. 300 small components, Transistors, Diodes £1.50. Wire ended Neon's, 20 for £1. Panel with 40 74 series ICs, £1.50. No postage. List 15p, refundable. Insurance add 15p. J.W.B. RADIO, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

**TIRRO's** new mail order price list of electronic components now available on receipt of SAE. TIRRO Electronics, Grenfell Place, Maidenhead, Berks.

## SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £4.40 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

**COMPONENTS.** 32 Leds (12R, 10G, 10Y) £3, 10 packs £25; LM741 15p, 10 for £1.40; NE555 22p, 10 for £2; LM3900 40p, 10 for £3.50; LM380 65p, 10 for £6; CPU's Z80 £10, 6800 £7, 8080 £6, Z80A £14, TMS2708 £6.50 all micros include socket; 2102-1 (450n) 80p; TRANS. 2N2222A 13p. RESISTORS 1/2p any mix; CERAMIC DISC 27pF to 8m2 1p any mix. P&P 12p. CMOS, TTL, MICROS. Free list. Tel: (0506 632337). R. Machnik, 13 Hopefield Place, Blackburn, West Lothian.

**ELECTRONIC CAR BATTERY VOLTMETER,** IC, PCB, full instructions, £2.75 inc. SAE for details. Tritch Electronics, 190 Roding Road, Loughton, Essex.

**CONSTRUCTOR PARCELS,** over 200 parts, 44 lists. SAE. Sole, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

**GUARANTEED ICs.** 7400/10p 7447/55p 7473/24p 74121/24p 4000/15p 4011/15p 4017/55p 4027/32p 709/22p 741/22p 78C5/60p NE555/25p. Many more! SAE full list CP ICs 22 Oakfield Road, Croydon, Surrey.

### Service Sheets

**SERVICE SHEETS** for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

**BELL'S TELEVISION SERVICE** for service sheets of Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

### Books and Publications

**ALL SERVICE SHEETS** and manuals supplied—enquiries welcome—SAE please. Repair any TV easily, full, individual instructions any set for £5 (circuit £1 extra). Send details of set to TIS (EE), 76 Church Street, Larkhall, Lanarks ML9 1HE.

### RADIO BOOK SERVICE

WORLD RADIO-TV HANDBOOK 1978 Edition	£9-28
Radio Stations Guide	£1-35
Long Distance Television Reception for the Enthusiast	£1-35
Popular Electronic Projects	£1-35
Electronic Projects for Beginners	£1-35
Public Discophone Handbook	£1-35
Radio Circuits using ICs	£1-35
Projects in Cavity Electronics	£1-35
How to make Walkie-Talkies	£1-35
Radio Amateur's H'book for Long Distance Reception	£2-95
How to build your own Metal & Treasure Locators	£1-35
How to build Advanced Short Wave Receivers	£1-35
Solid State Short Wave Receivers for Beginners	£1-35
PRICES INCLUDE POSTAGE & PACKING... S.A.E. FOR FULL LIST	
4 CHELSEA COURT, WICKHAM RD, BECKENHAM KENT BR3 2JW	

**INTRODUCTION TO MICROPROCESSORS** and Computing. 50 pages of diagrams and explanation to get you started. Price £2-30 plus 45p postage. EDUCATIONAL DATA AND TECHNICAL SERVICES, 59 Station Road, Cogenhoe, Northampton NN7 1LU.

### CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.

2. The publishers reserve the right to refuse or withdraw any advertisement.

3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

### Record Accessories

**STYLL CARTRIDGES FOR MUSIC CENTRES** &c. FREE List No. 29. For S.A.E. includes Leads, Mikes, Phones, etc. FELSTEAD ELECTRONICS (EE), LONGLEY LANE, GATLEY, CHEADLE, CHES SK8 4EE.

### For Sale

**NEW BACK ISSUES** of "EVERYDAY ELECTRONICS". Available 60p each Post Free, open PO/Cheque returned if not in stock. BELL'S TELEVISION SERVICES 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

### Miscellaneous

### THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4.  
Reg. Office, 22 Coningsby Gardens.

#### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10-19	2-85	1-45	75	60
20-29	2-85	1-65	90	70
30-34	3-05	1-75	1-00	75
35-40	3-40	1-95	1-15	84
41-43	4-55	2-55	1-95	1-30
44-46	4-05	3-05	2-15	1-70
47	8-00	5-00	3-00	1-80
48	15-00	9-00	6-00	3-30

#### SILVER PLATED COPPER WIRE

14, 16, 18	4-50	2-25	1-44	90
20 & 22	5-00	2-85	1-74	1-08
24 & 26	5-70	3-31	2-00	1-22
28 & 30	6-67	3-86	2-35	1-44

Prices include P & P and VAT.  
SAE brings list of copper & resistance Wires.  
Dealer enquiries invited.

**TUNBRIDGE WELLS COMPONENTS,** BALLARD'S, 108 Camden Road, Tunbridge Wells, Phone 31803. No lists, enquiries S.A.E.

### AERIAL BOOSTERS

Improves weak VHF radio & television reception.

B45-UHF TV, B11-VHF RADIO.

For next to the set fitting.

PRICE £5. S.A.E. FOR LEAFLETS.

**ELECTRONIC MAILORDER LTD.**  
Ramsbottom, Bury, Lancs, BLO 9AG.

### RECHARGEABLE BATTERIES

#### TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus catalogue. Write or call, Sandwell Plant Ltd, 2 Union Drive, Boldmers, Sutton Coldfield, West Midlands. 021-354 9784. Or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

**UK502-U  
M.W./L.W. RADIO  
RECEIVER**

This is a simple circuit using two transistors with earphone output. This unit can be connected to an amplifier giving good reception of all local stations.  
Supply 9V D.C.  
Current drain = 700µA  
Transistors 2 x BC109-B  
£5.31 inc. VAT. Post & packing 75p.



LTD  
ELECTRONIC KITS

**UK108  
F.M.  
MICROTRANSMITTER**

This simple and efficient transmitter has many diverse uses, amongst which: as a radio microphone, baby alarm etc. The range is approx. 500 metres max. Complete with high sensitivity dynamic microphone and telescopic antenna.  
Supply 9V D.C.  
Frequency range = 88-108MHz  
Transistors = BC208-B-2N708  
Size = 92 x 80 x 38mm  
Weight = 130GM  
£7.58 inc. VAT. Post & packing 75p  
Not licencable in the UK export only



**UK405  
PORTABLE  
SIGNAL TRACER**

This is a very useful instrument for tracing faults in radio's, television's & audio amplifier's. This device has a R.F. Probe & low frequency input.  
Frequency range = 100HZ - 500MHZ  
R.F. Probe Sensitivity = 10mV  
A.F. Sensitivity = 3mV-3V  
Transistors = 2 x BC209-B  
Integrated Circuit = TAA611  
Diode = AA119  
P.E.T. = 2N3619  
Powered from internal 9V D.C. battery  
£20.75 inc. VAT. Post & packing 75p.




**UK677  
VARIABLE  
STABILIZED POWER  
SUPPLY**

0-20V D.C. at 2.5 amps  
With current limiting control  
Short circuit proof  
Metering for voltage & current  
Mains Voltage 115-220-250V  
AC 50-50HZ  
Load Regulation = 0-15%  
Max Ripple < 1mV  
Transistors = 2N3055-BD138-BC180-BC307B  
Diodes = 5 x IN5401  
Zener Diodes = BZY88 C8V2  
Integrated Circuit = LN723-C  
Dimensions = 235 x 90 x 190mm  
£39.67 inc. VAT. Post & packing £1.00



**UK823  
CAR BURGLAR  
ALARM**

This device provides protection for the vehicle & its accessories. The system is effective against any kind of break-in since it reacts to opening of doors, engine or storage compartments and to the attempted removal of accessories or starting of the engine.  
Supply 12V D.C. negative earth  
Stand by Current Drain = 14mA  
Transistors = 2 x BC108-B-1 x BC301  
Diodes = 7 x IN4001  
Zener Diodes = BZY88 C7V5  
Peak switching current = 8 amp  
£10.64 inc. VAT. Post & packing 75p.

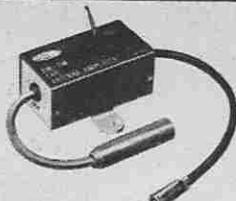

**UK233  
AUTOMOBILE  
ANTENNA  
AMPLIFIER**

This unit very much increases the sensitivity of any car radio and improves stereo reception on VHF. It also compensates for mismatching due to extra capacitance in a long antenna cable.  
Supply 12V D.C. negative earth  
Gain = L.W. = 11-12db M.W. S.W. = 15-18db VHF = 88-108MHz 14-15db  
Current Drain = 6mA  
Transistor BF273  
Kit £5.32 inc. VAT  
Wired & tested £5.75 inc. VAT. Post & packing 50p.



**UK232  
AM-FM ANTENNA  
AMPLIFIER**

This unit increases the sensitivity of any radio over a wide range of frequencies, including amplitude and frequency modulation broadcast. In a simple and economical way using a compact unit that is easy to install.  
Supply 12V D.C.  
Gain = AM (LM/MW/SW) 25db  
FM 88-108 MHz 75 ohm 15db  
Current Drain = 6mA  
Transistor BF273  
Kit £4.84 inc. VAT.  
Wired & tested £5.32 inc. VAT. Post & packing 50p.

FOR CATALOGUE OF COMPLETE RANGE OF KITS AND METAL CABINETS PLEASE SEND S.A.E. TRADE AND EXPORT ENQUIRIES WELCOMED

**For your Guidance  
Value Added Tax**

Unless otherwise shown, all prices in advertisements are inclusive of VAT.

Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

Export orders are not subject to the addition of Value Added Tax.

**MAINS INTERCOM**



**NO BATTERIES NO WIRES**

The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1/2-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom between office and warehouse in surgery and in homes. P. & P. 99p.

ONLY **£32.99** PER PAIR + VAT £4.13

**NEW! AMERICAN TYPE CRADLE  
TELEPHONE AMPLIFIER**



Latest improved transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increases efficiency in the office, shop and surgery. Perfect for "conference" calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control. Conversation recording model at £19.95 + VAT £1.60. P. & P. 99p.

ONLY **£17.95**

+ V.A.T. 8% £1.44

10-day price refund guarantee on all items.  
WEST LONDON DIRECT SUPPLIES (EELS) 169 KENSINGTON HIGH STREET, LONDON, W8 6ER. 01-897 5545

**a digitizer adds another dimension**

The Bit Pad computer digitizer converts graphic information into digital form for direct entry into a computer. By touching a pen like stylus or a cursor, to any position on a drawing, diagram, photograph, or other graphic presentation, the position co-ordinates are converted to digital equivalents.


- Bit Pad interfaces with almost any micro computer.
- Bit Pad consists of a 15" sq. digitizer tablet (11" sq. active area), a stylus, and a controller cabinet.
- Bit Pad costs only £450 (excluding VAT). Fill in the coupon and we will send you full information and details.

Terminal Display Systems Ltd., Hillside, Whitebirk Industrial Estate, Blackburn BBI 5SM, Lancs, England

Send to: Department CPED, Terminal Display Systems Ltd., Hillside, Whitebirk Industrial Estate Blackburn BBI 5SM, Lancs, England.

Name .....

Address .....

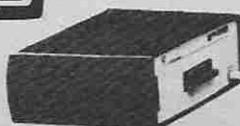

Microcomputer Network Architecture  
Structural Mechanical  
Construction  
Exam marking  
Teaching  
International research  
Measuring  
Management Military  
Menus Market research  
Geographical  
Cartographic Archaeological  
Town Planning  
Orthodontics Design Geographical Statistics Traffic  
Radiology Microscopy Art  
Architecture  
Structural Civil Mechanical  
Process Control  
Teaching Games  
Measuring Biological  
Menus Market research  
Archeological  
Design Geological

# TAMTRONIK LTD (DEPT EE)

217, Toll End Road, TIPTON, West Midlands DY4 0HW TEL: 021-557-9144

## Printed Circuit Boards & KITS for EE projects

Mag Issue	PROJECT	KIT Ref	PRICES		KIT CONTENTS (see key)
			P.C.B.	KIT	
Jan 78	Audio Visual Metronome	E001	+ 85	6-40	B.E.H.L.
	Touch Switch	E002	+1 00	2-35	B.E.
	Rapid Diode Check	E004	+ 85	2-30	B.E.H.L.
Feb	Car Alarm	E005	+1 15	6-45	B.E.G.H.L.
	Lead Tester	E006	80	5-10	B.E.H.L.
	Chaser Light Display	E007	2-70	23-95	B.E.H.L.
	A.C. Meter Converter	E008	+1-05	6-70	B.E.H.L.
Mar	Audio Test (2 x Pcb's)	E009	+2-65	18-75	B.F.G.J.
	C.R. Substitution Box	E010	—	9-95	B.E.H.L.
	Catch-a-Light	E011	+1-40	10-00	B.E.H.L.
	Weird Sound	E012	+1-00	6-45	B.E.H.L.
Apr	Roof Rack Alarm	E013	+1-00	—	—
	Mains Delay Switch	E014	+1-25	14-25	B.E.J.L.L.
	Pocket Timer	E015	+ 95	4-40	B.E.H.L.
May	Flash Meter	E016	+1-10	13-20	B.E.H.L.
	Mains Tester	E17	+ 85	1-90	B.E.H.
	Teach In—Power Amp	E18	—	1-95	—
	Power Pack	E19	+1-20	7-10	B.E.H.L.
Jun	Tele-Bell	E20	+1-35	12-80	B.E.H.L.
	In Situ Transistor Tester	E21	+ 95	6-15	B.E.G.H.L.
	Teach In S.W. Receiver	E22	—	3-30	E.
	Power Slave	E23	2-45	—	—
	Visual Continuity Tester	E24	—	4-95	E.H.L.
July	Auto Night Light	E025	+1-30	11-25	B.E.G.H.L.
	Short Wave Radio	E026	—	10-25	E.J.
	Quagmire	E027	+1-95	8-80	B.E.G.H.
	Logic Probe	E028	+ 80	3-45	B.E.G.H.L.
Aug	Slave Flash	E029	+ 90	8-55	B.E.
	M.W.	E30	+ 80	6-35	B.E.J.L.L.
	Audio Freq. Signal Generator	E031	+1-45	14-85	B.E.H.L.
	Chronostop	E032	+2-95	33-95	C.E.G.K.M.P.
Sept	R.F. Signal Generator	E033	—	18-25	E.H.
	Sound to Light	E034	—	6-20	E.H.L.
	Guitar Tone Booster	E035	1-05	5-00	B.E.H.L.
	Car Battery State Indicator	E036	90	2-20	B.E.
Oct	C.M.O.S. Radio	E037	+1-85	12-75	B.E.G.H.L.
	Fuzz Checker	E038	—	2-15	E.H.L.
	Treasure Hunter	E039	1-80	18-20	B.E.G.H.L.
	TTL Test Bed	E040	—	24-00	N.
	TTL—1st 6 parts complete	E041	—	4-50	N.
Nov	Audio Effects Oscillator	E042	—	3-05	E.H.L.
Dec	Water Level Alert	E043	+ 90	4-65	B.E.G.H.L.
	Subscribers Tele-Tel. Meter	E044	+3-50	24-50	C.E.G.K.M.P.
	Subs. Tele Tel.—3rd Digit	E044A	—	3-50	—
	Combination Lock (2 Pcb's)	E045	+3-45	24-95	B.E.H.L.
	Hotline Game	E046	+1-00	5-50	B.E.H.
Oct	Mini Module—Passive Mixer	E047	—	3-10	E.H.
Dec	Audible Flasher	E048	—	3-00	E.H.
	Fuzz Box	E049	+1-00	6-25	B.E.H.L.
	Vehicle Immobiliser	E050	1-25	5-50	B.E.H.L.
	Mini Module—Microphone Amp	E051	—	3-10	D.E.H.
Jan 79	Mini Module Continuity Tester	E052	+1-05	4-65	B.E.H.
	Lights Reminder	E053	+1-15	6-90	B.E.G.H.L.
	I'm First	E054	—	2-20	E.H.
	Roulette (2 p.c.b.'s)	E055	+4-10	20-45	B.E.H.
	Headphone Enhance	E056	—	2-60	E.H.C.
Dec 78	EE 2020 Tuner Amp A (inc. R. unit)	E057	9-65	58-95	B.E.G.H.
To	EE 2020 Tuner Amp B	E058	3-80	25-95	B.E.H.
Feb 79	EE 2020 Tuner Amp C	E059	1-45	4-70	B.E.H.
	EE 2020 Tuner Amp D	E060	2-30	18-45	B.E.H.
	EE 2020 Tuner Amp E	E061	1-40	24-95	B.E.G.H.
	EE2020 Hardware & wire	E062	—	13-50	K.
	EE 2020 Kit excl. Case	E063	10-90	135-00	B.E.G.K.
	Long Wave Converter	E064	+1-20	7-40	B.E.H.L.
Feb	Mini Module Audio Modulator	E065	—	2-00	E.H.
	Power Supply	E066	+1-00	25-45	B.E.H.
	Thyristor Tester	E067	+ 80	4-85	B.E.H.L.
	Sound Adaptor	E068	+1-20	6-95	B.F.H.
Mar	Car Direction Indicator (Neg. 12v)	E069	+1-25	8-45	B.E.G.H.L.
	Time Delay Indicator	E070	+ 90	4-05	B.E.H.L.
	ONE Transistor Radio (incl. Amp)	E071A	+1-00	8-50	B.E.H.L.
	ONE Transistor Radio (excl. Amp)	E071B	+ 85	7-35	B.E.H.
	Mini Module—Versatile Power Supply	E072	—	5-35	E.H.L.
Apr	Shaver Inverter	E073	+1-00	12-75	B.E.H.L.
	Touch Bleep	E074	+1-15	4-70	B.E.H.L.
Mar	Lab Centre	E075	—	TBA	—
Apr	Lab Centre	E076	—	TBA	—
	Mini Module Transistor Test	E077	+ 95	4-25	B.E.H.
	Choke Warning	E078	+1-00	9-00	B.E.G.H.
May	Electronic Dice	E079	—	—	—

Kits can be supplied excluding P.C.B.'s and/or case. Send SAE for details naming kit and kit reference and free catalogue.

TRADE & EDUCATIONAL ENQUIRIES WELCOME

PRICES INCLUDE VAT & P & P

### KEY TO KIT CONTENTS

- A Vero-board(s)
- B Printed Circuit Board(s)
- C With screen printed component layout
- D Tag strip
- E ALL Resistors, potentiometers, capacitors, Semi-conductors
- F As E but with exclusions—Please ask for details
- G Diode and/or transistor sockets and/or soldercon pins
- H Hardware includes Switches, Knobs, Lamps & Holders, Fuses & Holders, Plugs & Sockets, Microphones, Transformers, Speakers, Meters, Relays, Terminal Blocks, Battery Connectors, etc. BUT excludes nuts, bolts, washers, connecting wire, Batteries and special miscellaneous items.
- J As H but with exclusions—Please ask for details
- K As H but including connecting wire
- L Suitable Case(s)
- M Suitable Case with Screen printed facia
- N Full kit to magazine specified standards
- P Kit with professional finish incorporating all prime features including screen printed PCB and case where appropriate

### Doing-it-Digitally

#### TTL ELECTRONIC TEST BED

Complete kit E040 £24.00

Components for first 6 parts E041 £4.50 (including additional components)

**BOTH KITS (special price) £26.90**

### BARGAIN CORNER

- 100 x 1/4w 1k carbon resistors 30p
- 10 x 1w 5% 1k5 resistors 10p
- 10 x 1w 5% 7k5 resistors 12p
- 10 x 1w 5% 100R resistors 12p
- 10 x 6w 5% 390R wirewound 50p
- 10 x 47u 10v Axial Elec. Caps 25p
- 4 x NE55 Timer £1.00
- Plug in mains PSU
- 3v/5v/9v/12v DC
- 300mA suitable for calculators & T.V. Games £2.99

### TELE-TEL

Nov. 78 Ref. E044

Subscribers phone call charge meter

A kit with a professional finish CASE with screen printed facia similar to magazine photograph but includes provision for 3rd digit.

An aluminium sub-facia panel is also provided with screen printed hole centres to allow access to preset potentiometers.

PCB designed to incorporate 3rd digit facility and is screen printed for ease of assembly.

Basic kit (2 digits) £24.50 (3 digits) £28.00

### CHRONOSTOP

Aug. 78 Ref. E032

SPLIT 6 TAYLOR lap timing modes plus normal start/stop operation.

A kit with a professional finish including CASE with screen printed facia

PCB with screen printed component layout

Full Assembly Instructions

PRICE INC. VAT £33.95

### SOLDERING IRONS & ACCESSORIES

- SRB 18 watt iron inc. No 20 Bit £3.78
- Bit " " " 20 (3mm) " " " 20 (3mm) " " " 21 (4-5mm) " " " 22 (6mm)
- Stand £3.25
- Solder-Savbit 20 inch 52p
- Bit sizes No. 90 (1.5mm) " " " 20 (3mm) " " " 21 (4-5mm) " " " 22 (6mm)
- Ideal for Home Constructor

Tamtronik Ltd. reserves the right to change kit content without notice, where necessary to incorporate current modifications or to make valid substitution for temporarily unavailable components. The majority of the kits we advertise can be supplied from stock or compiled at short notice from component stocks held, but when ordering you should be prepared to allow at least ten days, and up to one month, for us to complete your order.

Telephone or Letter

**VISIT OUR SHOP AT**

32 Market Place, Great Bridge, Tipton, West Midlands.

Buy it with Access

BARCLAYCARD VISA

## INDEX TO ADVERTISERS

Ace Mailtronix	386	George Sales, David	388	Quinton Tool Supplies	380
Alcon Instruments	386	G.M.T. Electronics	326-327	Radio & TV Components	360
Amtron	391	Greenwell	369	Saxon Entertainments	365
Antex	Cover ii	Harvelec	385	Senlac Systems	384
Bi-Pak	375	Heathkit	376	Selray Book Co.	384
Birkett J.	322	Home Radio	386	Special Products	387
B.N.R.E.S.	389	ILP Electronics	370	Stevensons	323
Bull J.	383	Intertext (ICS)	322	Sugden A. R.	387
Clef Projects	388	Magenta Electronics	380	Swanley Electronics	380
Collier McMillan (B.I.E.T.)	380	Maplin Electronic Supplies Ltd.	Cover iv	Tamtronik	392
Crimson Electronics	376	Marshall A.	379	Technomatic	324
C.S.C.	325	Menorcrest	324	Terminal Display Systems	391
Dick Smith	385	Metac	359	Timetron	385
Dewtron	388	Monolith	388	TUAC	369
E.D.A.	384	Newnes-Butterworth	386	Vero Electronics	324
Electroni-Kit	322	Phonosonics	302	Watts Steadman (Gt. British Electronics Bazaar)	Cover iii
Electrovalue	387	Powell T.	369	Watford Electronics	321
				West London Direct Supplies	391

Published approximately the third Friday of each month by IPC Magazines Ltd., Kings Reach Tower, Stamford St., London SE1 9LS. Printed in England by Index Printers Ltd., Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/81a) Ltd. South Africa—Central News Agency Ltd. Subscriptions: Inland £8.50. Overseas £9.50 per annum payable to IPC Services, Oakfield House, Perry Mount Road, Haywards Heath, Sussex. Everyday Electronics is sold subject to the following conditions namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# Come to the Great British Electronics Bazaar

**"ALLY PALLY!"**  
Thursday-Saturday  
28th-30th June.

# FREE!

(AND WAIT TILL YOU SEE OUR SEMINAR PROGRAMME)

## The Great Big 'Bazaar' for the hobbyist, amateur, and small buyer.

There's never been an event like this before.

First, the very scale of the exhibition is huge. Virtually all the companies you're used to hearing about (and buying from) will be there. Companies like Fluke and Gould showing off their low cost multimeters; smaller but important manufacturers like Lektrokit and Chromasonics; and even the R.S.G.B. who will have a station 'on the air' throughout the 'Bazaar.'

Then there are the suppliers of low-cost components and equipment. Plus almost all the journals in the business. Plus, oh, so many more interesting people catering for your needs (including computer kits!).

And you get in FREE if you send an s.a.e. (see alongside).


Our Symbol.  
We think it tells  
you just what the  
Bazaar is all about.


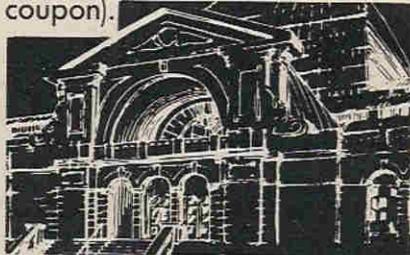
## The Seminars.

If you would like to hear just what the experts have to tell you, a season ticket for three whole days can be yours for only £1.50.

Send an s.a.e. and we'll give you all the information (just use the coupon).



Our home for three days - Alexandra Palace, where it all began. (Our seminars are sited alongside the organ - for those who know this unique hall.)

## SEMINAR TICKETS

£1.50.

I'd like to sit in at your seminars. (And like a free ticket to the exhibition.) Send me full details, please, and I enclose a large-ish s.a.e.

Name: .....

Address: .....

Post to: 'The Bazaar,' 34/36 High Street, Saffron Walden, Essex.

## When?

Between Thursday to Saturday 28th-30th June.

You'll be in very good company; some ten thousand enthusiasts - and over a hundred stands displaying all that you want to see.

## You'll come?

Eyes down for the appropriate coupon.

## ADMISSION FREE

(or 50p on the door).

I'd like to see 'The Bazaar' FREE. I enclose a large-ish s.a.e. and will receive by return a ticket and full information.

Name: .....

Address: .....

Post to: 'The Bazaar,' 34-36 High Street, Saffron Walden, Essex. If you'd rather just pay 50p, go to Wood Green Tube Station and take a bus (every 3 minutes) to Alexandra Palace. We're open 10 am-6 pm daily, Thursday to Saturday, 28th-30th June.




Our catalogue even includes some popular car accessories at marvellous prices.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



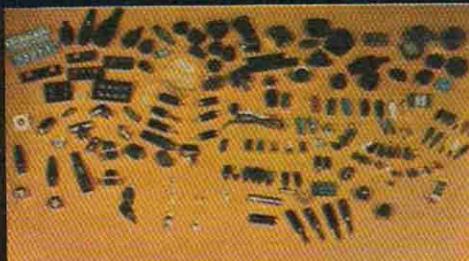Speakers from 1 inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.




61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 186 and 183 to 188 for details.



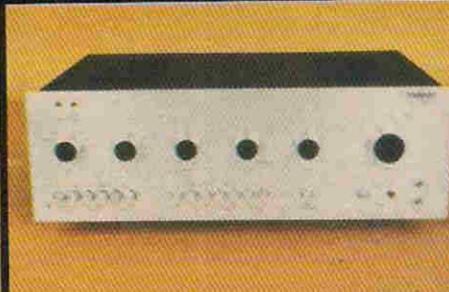A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

# MAPLIN

**ELECTRONIC SUPPLIES LTD**

All mail to:-  
 P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 554155.  
 Shop: 284 London Road,  
 Westcliff-on-Sea, Essex.  
 (Closed on Monday).  
 Telephone: Southend (0702) 554155.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



A 18-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.**  
 Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_