


Easy to build projects for everyone

# Everyday ELECTRONICS

KIOSKS  
McKool

AUG 79  
45p

## WARBLING TIMER

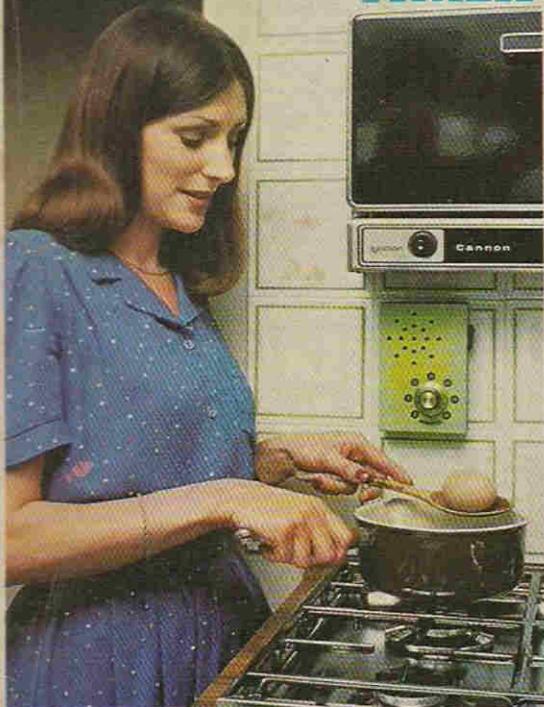


## TRAILER FLASHER UNIT



## ELECTRONIC TUNING FORK



## SQUARE ONE FOR BEGINNERS

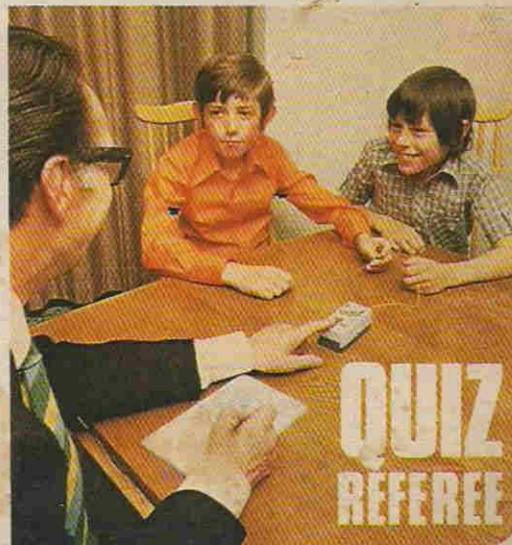

## 9V Power Supply

## QUIZ REFEREE

### QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch. Very slim, only 6mm thick.



M1

### SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins, secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

**£8.65**

Guaranteed same day despatch.



M2

### QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price



M3

**£10.65** Thousands sold! Guaranteed same day despatch.

### QUARTZ LCD ALARM 7 Function

Hours, mins, secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick.

**£12.65**

Guaranteed same day despatch.



M4

### MULTI ALARM 6 Digits 10 Functions

- Hours, mins, secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

**£18.65**



M5

### FRONT-BUTTON Alarm Chrono Dual Time

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs. in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet. Guaranteed same day despatch



**£22.65**  
M6

### SOLAR QUARTZ LCD Chronograph with Alarm Dual Time Zone Facility

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm, 9mm thick. Back-light. Fully adjustable bracelet.



**£27.95**  
M7

### ALARM CHRONO with 9 world time zones

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

**£29.65**



M8

### SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins, secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£12.65**

Guaranteed same day despatch.



M9

### SEIKO Alarm Chrono

LCD, hours, mins, secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDEX glass.

List Price £130.00

METAC PRICE

**£105.00**



M10

### SEIKO MEMORY BANK

Calendar watch M354. Hours, mins, secs. Month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display month, year and all dates for any selected month over 80 year period. Memory bank function. Any desired dates up to 11 can be stored in advanced. 2 year battery life. Water resistant.

List Price £130

Metac Price **£105**



M11

### SEIKO-STYLE Dual time-alarm Chronograph


Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

**£35.00**



M12

### HANIMEX Electronic LED Alarm Clock

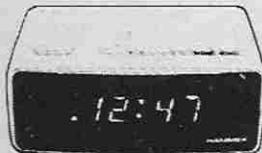

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9 minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 111mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

**£9.65** Thousands sold!

Mains operated.

Guaranteed same day despatch.

M13

### HANIMEX portable LCD clock radio



- Time set & alarm controls.
- Snooze & sleep controls.
- Wake to music or alarm.
- AM/PM indicator.
- Battery operated. No plug required.
- Receives all standard AM radio broadcasts.
- Drawstring carrying case included.
- Back-light.
- Batteries supplied free.
- Quartz crystal controlled.

**£17.95**  
M14

#### HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd. 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME  
Shops open 9.30 - 6.00.

### QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£9.95**

Guaranteed same day despatch.



M15

### Price breakthrough only £18.95



#### OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- **CALENDAR FUNCTIONS** include the date and day in each time zone.
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
- On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch. **M16**

# Metac

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753



# The latest kit innovation!

from **Sparkrite**

*Sparkrite was featured by Shaw Taylor in "DRIVE IN"*



the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

#### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £4.25 inc. VAT, post & packing.

Electronics Design Associates, Dept. EE 5  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Electronics Design Associates, Dept. EE 8  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name .....  
Address .....

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P. (U.K. only.) QUANTITY REQ'D. Send SAE if brochure only required.

I enclose cheque/PO's for

£

PLEASE STATE POLARITY POS OR NEG EARTH.

Access or Barclaycard No. ....

Access or Barclaycard No. ....


- 50 OC 71 TRANSISTORS untested for 75p.
- 50 BC107-8-9 TRANSISTORS assorted, untested @ 57p.
- MINIATURE CERAMIC TRIMMERS 2 to 6pf, 3 to 10pf, 4-7 to 20pf. All at 15p each.
- COIL FORMERS 1/2" Dia. with core, 6 for 25p.
- VHF SOLDER-IN TUBULAR TRIMMERS 6pf @ 16p each.
- ERIE MINIATURE CERAMIC .01uf 100v.w. CAPACITORS @ 5p each.
- 1 AMP TRIACS 400 PIV at 3 for £1.
- MOTOROLA OP-AMPS MC 1438G at 35p, 3 for £1.
- NON-POLARISED CAPACITORS 1uf 63v.w., @ 5p, 4-7uf 63v.w., @ 10p, 10uf 63v.w., @ 15p.
- 25 5 AMP S.C.R.'s Stud Mounting untested @ 75p.
- 50 1 AMP S.C.R.'s TO5 Package untested @ £1.
- SPECIAL VARIABLE CAPACITOR WITH S.M. DRIVE 250 + 250 + 20 + 20 + 20pf @ 75p.
- PLASTIC BRIDGES 100 PIV 1 amp @ 20p, 200 PIV 4 amp @ 80p.
- MULLARD POLYESTER CAPACITORS .1uf 160v.w. at 20p doz.
- MINIATURE LOUDSPEAKERS 1 1/2" Dia. 8 ohm at 75p.
- 100 MULLARD C230 CAPACITORS assorted for 57p.
- MINIATURE DISC CERAMICS .01uf 50v.w. @ 20p doz.
- MULLARD TRANSISTORS BC 545 or BC 545 at 8 for 50p.
- PLASTIC BC 108 TRANSISTORS with House Numbers at 10 for 80p.
- VARIABLE CAPACITORS Direct Drive. 5pf @ 75p, 10pf @ 75p, 30pf @ 85p, 125 + 125pf @ 55p, 100 + 200pf @ 55p, 200 + 200 + 17 + 17pf @ 55p. With S.M. Drive 500 + 500 + 25 + 25pf @ 55p, 250 + 250 + 20 + 20 + 20pf @ 75p, Sub-Miniature 25 + 25 + 25pf @ £1.
- R.F. TRANSISTORS AF 239 @ 50p, MPS 6514 @ 15p, 2N 5180 @ 50p, 2N 5179 @ 50p, BF 90 @ 50p, BF 224 @ 16p, BF 362 @ 25p.
- VHF FETS 2N 3819 @ 20p, J310 @ 20p, MF 131 @ 30p, BF 256 @ 25p, E111 @ 12p, E112 @ 10p. DUAL GATE TYPE 40673 @ 35p.
- 400mW UNMARKED GOOD ZENERS 3-8v, 6-8v, 10, 11, 12, 13, 16, 18, 24, 30, 35, 36 volt. All at 10 for 40p.
- ELECTROLYTIC CAPACITOR 5000 + 5000uf 25v.w., @ 75p.
- PLESSEY 44 WAY PLUG AND SOCKET at £1 per pair.
- IRON CORED CHOKE 2 MH at 4 amp for 50p (P&P 20p).
- CLOSE TOLERANCE CAPACITORS 1288pf @ 5p, 1670pf @ 5p, 5979 @ 5p, 19600pf @ 5p. All 1%, .01uf 2% @ 8p, .1uf 1% @ 8p.
- MULLARD POLYSTYRENE TYPE 424-41193 .011uf 63v.w., 5% @ 20p doz.
- BYXB19 MINIATURE SILICON DIODES like OA 202, 10 for 25p.
- 10 ASSORTED PUSH BUTTON BANKS (less knobs for £1-90).
- MIDGET 20pf AIR SPACED TRIMMERS for 10p each.
- 100 ASSORTED DISC CERAMIC CAPACITORS @ 57p.
- 200 1/2 watt RESISTORS assorted for 75p.
- 10 SLIDER POTENTIOMETERS assorted for £1.
- 5 WATT NPN DARLINGTON TRANSISTORS TO5 case @ 3 for 50p.
- 10 ASSORTED PHONO SOCKETS 2, 3, 4 way for 50p.
- 20 PHOTO TRANSISTORS AND DARLINGTONS assorted untested @ £1.
- SILICON SOLAR CELLS .5 volt 5mA @ 35p each.
- 50 VARI-CAP DIODES like BA 102, untested @ 57p.
- 30 ASSORTED 10XAJ CRYSTALS @ £1-10, 20 ASSORTED FT 241 CRYSTALS @ £1-10, 20 ASSORTED FT 243 CRYSTALS @ £1-30, 25 10X CRYSTALS @ £1-50.

Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas postage at cost.

**J. BIRKETT**

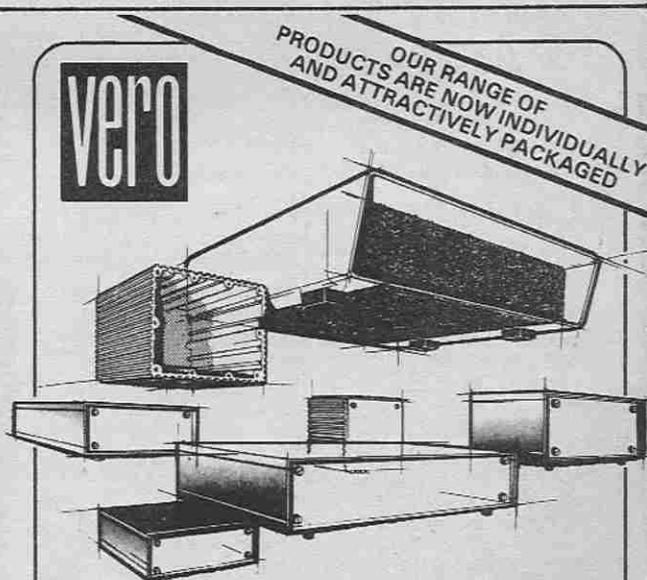**RADIO COMPONENT SUPPLIERS**

25 The Strait, Lincoln LN2 1JF Tel. 20767



Our new catalogue lists a whole range of metal cases to house all your projects. And we've got circuit boards, accessories, module systems, and plastic boxes - everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

**VERO ELECTRONICS LTD. RETAIL DEPT.**  
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR  
Telephone Chandlers Ford (04215) 2956

# LOOK! Here's how you master electronics.

.... the **practical** way.


This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.
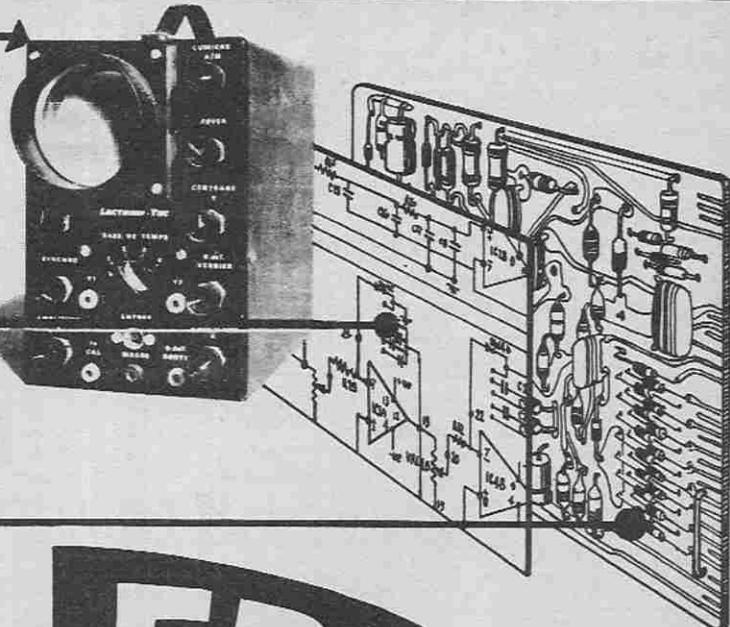
## 1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



## 2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

## 3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

## 4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

# FREE

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO &  
ELECTRONICS SCHOOL**


P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

EEB/8/79

Block caps please

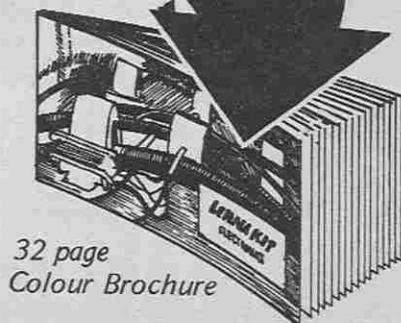

32 page  
Colour Brochure

# KITS FOR SOUND EFFECTS AND OTHER PROJECTS

## PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

### FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit  
Component set (incl. PCB) £2-05

### P.E. TUNING FORK (P.E. Nov. 75)

Produces 34 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.  
Main component set (incl. PCB) £14-95  
Power supply set (incl. PCB) £8-28

### SYNTHESIZER TUNING INDICATOR

(P.E. July 77)  
A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of the P.E. Tuning Fork is not required.  
Component and PCB (but excl. sw.) £7-45

### DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.  
Component set (incl. PCB) £4-58

### CONSTANT DISPLAY FREQUENCY

METER (P.E. Aug. 78)  
A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.  
Component set £24-05  
Printed circuit board £3-05

### MANY MORE KITS

for Synthesizers, Rhythm Generators, Electronic Pianos and other projects, big, small, simple or complex, are available, plus a range of keyboards, separate components and accessories. Details in our lists.

**PHOTOGRAPHS** in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

**EXPORT ORDERS ARE WELCOME** but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list—Europe send 20p, other countries send 50p. **PRICES ARE CORRECT AT TIME OF PRESS. E.&O.E. DELIVERY SUBJECT TO AVAILABILITY.**

### GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.  
Component set with special foot operated switches £7-89  
Alternative component set with panel switches £5-05  
Printed circuit board £1-43

### GUITAR FREQUENCY DOUBLER

(P.E. Aug. 77)  
A modified and extended version of the circuit published.  
Component set and PCB £4-52

### GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.  
Component set using dual rotary pot £6-89  
Printed circuit board £1-62

### GUITAR SUSTAIN (P.E. Oct. 77)

Maintains the natural attack whilst extending note duration.  
Component set, PCB and foot switches £5-13  
Component set, PCB and panel switches £3-71

### WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.  
Component set (incl. PCB) £4-26

**COMPONENTS SETS** include all necessary resistors, capacitors, semi-conductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately.

Fuller details of kits, PCBs and parts are shown in our lists.  
**CIRCUIT AND LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

**PHOTOGRAPHS** of texts for most of the kits are available—prices in our lists.  
**LIST**—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

**10% DISCOUNT VOUCHER (E694)**  
TERMS: Goods in current adverts & lists over £50 goods value (incl. P&P & VAT). Correctly coded. C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of E.E.

**ADD: POST & HANDLING**  
U.K. orders—Keyboards add £2-00 each plus VAT. Other goods: under £15 add 25p plus VAT, over £15 add 50p plus VAT. Recommended: optional insurance against postal mishaps, add 50p for cover up to £50, £1-00 for £200 cover, etc. pro-rata.  
N.B. Eire, C.I., S.F.P.O. and other countries are subject to higher export postage rates.

**ADD 15% VAT**  
(or current rate if changed).  
Must be added to full total of goods. Discount, post & handling, on all U.K. orders. Does not apply to Exports.

PHONOSONICS · DEPT. EE98 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL: 01-332 8184)

MAIL ORDER DEPT.

## CRESCENT RADIO LTD.


1, ST. MICHAELS TERRACE, WOOD GREEN, LONDON, N22. 4SJ.  
PHONE 01-888 3206



### "FLIP"

Push button heads or tails. Complete kit and full instructions supplied. A pocket game. Easy to build and great to play. Kit price—£5-25 + 8% VAT. Post free.

### 4 OHM DOOR MOUNTING CAR LOUSPEAKERS

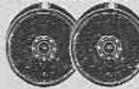

High performance, door mounting. 5 1/2 inch units with smart front grill. 10 oz magnet, 12 watts, 4 ohms. In attractive see-through carton. £12-60 + 12 1/2% VAT. per pair.

### HEAVY DUTY XOVER 2 WAY 8 OHM

A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100 watt. Fitted with screw terminals for input and a three position "HF LEVEL" switch which selects either Flat, -3dB or -6dB. ONLY £3-00 + 8% VAT

**A CRESCENT "SUPERBUY"**  
Goodmans 5" 8 ohm long throw H/D loudspeaker. Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5 1/2" (diagonally). ONLY £5-00 + 12 1/2% VAT



'P&P' ORDERS UP TO £5, Add 30p  
ORDERS £5-£10, Add 50p  
All orders over £10 post free!  
Please add VAT as shown.  
S.A.E. with all enquiries please




Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N13.  
ALSO, 13 SOUTH MALL, EDMONTON GREEN, EDMONTON.

**M.E.C.A.**  
14 HOPETON STREET  
BATHGATE  
WEST LOTHIAN  
Tel: Bathgate 632337

TERMS: C.W.O. No Min. 12p P & P  
ACCESS AND BARCLAYCARD ACCEPTED  
Min. £5 Post & Packing 25p.  
GOVERNMENT, SCHOOLS, COLLEGES  
ORDERS ACCEPTED  
Send or Phone for Catalogue.

CMOS	4522	70p	7472	N LSN	REGULATORS	MICROS.
4000	4528	70p	7473	78L	78L	21P
4001	4529	70p	7474	28p	78M	28p
4002	MC14409	99p	7475	25p	78P	28p
4004	MC14419	295p	7476	26p	78Q	28p
4006	74C151	80p	7477	30p	78R	28p
4007	All prices include		7478	35p	78S	28p
4008	VAT.		7479	40p	78T	28p
4009			7480	45p	78U	28p
4010	BUFFERED		7481	50p	78V	28p
4011	types on request		7482	55p	78W	28p
4012	according to our		7483	60p	78X	28p
4013	stock position.		7484	65p	78Y	28p
4014			7485	70p	78Z	28p
4015			7486	75p	78AA	28p
4016			7487	80p	78AB	28p
4017			7488	85p	78AC	28p
4018			7489	90p	78AD	28p
4019			7490	95p	78AE	28p
4020			7491	100p	78AF	28p
4021			7492	105p	78AG	28p
4022			7493	110p	78AH	28p
4023			7494	115p	78AI	28p
4024			7495	120p	78AJ	28p
4025			7496	125p	78AK	28p
4026			7497	130p	78AL	28p
4027			7498	135p	78AM	28p
4028			7499	140p	78AN	28p
4029			7500	145p	78AO	28p
4030			7501	150p	78AP	28p
4031			7502	155p	78AQ	28p
4032			7503	160p	78AR	28p
4033			7504	165p	78AS	28p
4034			7505	170p	78AT	28p
4035			7506	175p	78AU	28p
4036			7507	180p	78AV	28p
4037			7508	185p	78AW	28p
4040			7509	190p	78AX	28p
4041			7510	195p	78AY	28p
4042			7511	200p	78AZ	28p
4043			7512	205p	78BA	28p
4044			7513	210p	78BB	28p
4045			7514	215p	78BC	28p
4046			7515	220p	78BD	28p
4047			7516	225p	78BE	28p
4048			7517	230p	78BF	28p
4049			7518	235p	78BG	28p
4050			7519	240p	78BH	28p
4051			7520	245p	78BI	28p
4052			7521	250p	78BJ	28p
4053			7522	255p	78BK	28p
4054			7523	260p	78BL	28p
4055			7524	265p	78BM	28p
4056			7525	270p	78BN	28p
4057			7526	275p	78BO	28p
4058			7527	280p	78BP	28p
4059			7528	285p	78BQ	28p
4060			7529	290p	78BR	28p
4061			7530	295p	78BS	28p
4062			7531	300p	78BT	28p
4063			7532	305p	78BU	28p
4064			7533	310p	78BV	28p
4065			7534	315p	78BW	28p
4066			7535	320p	78BX	28p
4067			7536	325p	78BY	28p
4068			7537	330p	78BZ	28p
4069			7538	335p	78CA	28p
4070			7539	340p	78CB	28p
4071			7540	345p	78CC	28p
4072			7541	350p	78CD	28p
4073			7542	355p	78CE	28p
4074			7543	360p	78CF	28p
4075			7544	365p	78CG	28p
4076			7545	370p	78CH	28p
4077			7546	375p	78CI	28p
4078			7547	380p	78CJ	28p
4079			7548	385p	78CK	28p
4080			7549	390p	78CL	28p
4081			7550	395p	78CM	28p
4082			7551	400p	78CN	28p
4083			7552	405p	78CO	28p
4084			7553	410p	78CP	28p
4085			7554	415p	78CQ	28p
4086			7555	420p	78CR	28p
4087			7556	425p	78CS	28p
4088			7557	430p	78CT	28p
4089			7558	435p	78CU	28p
4090			7559	440p	78CV	28p
4091			7560	445p	78CW	28p
4092			7561	450p	78CX	28p
4093			7562	455p	78CY	28p
4094			7563	460p	78CZ	28p
4095			7564	465p	78DA	28p
4096			7565	470p	78DB	28p
4097			7566	475p	78DC	28p
4098			7567	480p	78DD	28p
4099			7568	485p	78DE	28p
4100			7569	490p	78DF	28p
4101			7570	495p	78DG	28p
4102			7571	500p	78DH	28p
4103			7572	505p	78DI	28p
4104			7573	510p	78DJ	28p
4105			7574	515p	78DK	28p
4106			7575	520p	78DL	28p
4107			7576	525p	78DM	28p
4108			7577	530p	78DN	28p
4109			7578	535p	78DO	28p
4110			7579	540p	78DP	28p
4111			7580	545p	78DQ	28p
4112			7581	550p	78DR	28p
4113			7582	555p	78DS	28p
4114			7583	560p	78DT	28p
4115			7584	565p	78DU	28p
4116			7585	570p	78DV	28p
4117			7586	575p	78DW	28p
4118			7587	580p	78DX	28p
4119			7588	585p	78DY	28p
4120			7589	590p	78DZ	28p
4121			7590	595p	78EA	28p
4122			7591	600p	78EB	28p
4123			7592	605p	78EC	28p
4124			7593	610p	78ED	28p
4125			7594	615p	78EE	28p
4126			7595	620p	78EF	28p
4127			7596	625p	78EG	28p
4128			7597	630p	78EH	28p
4129			7598	635p	78EI	28p
4130			7599	640p	78EJ	28p
4131			7600			

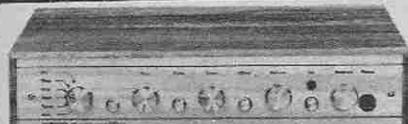

**20 x 20 WATT STEREO AMPLIFIER**  
Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia. red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.

**£29.90**  
£2.50 p&p

**30x30 WATT AMPLIFIER IN KIT FORM**  
For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4, 15 ohms speakers.

+ p&p  
**£29.00** £2.50

**SPECIAL OFFER**  
**30 x 30 WATT AMPLIFIER KIT** with BSR P200 belt drive deck and Shure M75 cartridge.

**£55.00**  
+ p&p £5.00

**EMI SPEAKER BARGAIN**  
Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround. 2 1/2" approx. Audaux tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance.

**£14.95**  
Per stereo pair  
£3.40 p&p

**BSR P200**  
Belt drive chassis turntable unit semi automatic, cueing device.

**£24.95**  
p&p £2.55

A.D.C. OLM 30 Mk III Magnetic Cartridge to suit. **£7.75**

**BSR** Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use.

OUR PRICE **£10.95** £2.55

**GARRARD DECK MODEL CC 10A**  
Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

**£7.95** p&p £2.00 Size 12" x 8 1/2"

**SANYO** Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/4" x 1 1/4" x 2" approx.

**£7.50** p&p £1.50p

**BARGAIN FOR PERSONAL SHOPPERS ONLY**  
**Altone UA4 Stereo System**  
Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones complete with speakers.

**£34.95**

**Micro Cassette Recorder**  
Pocket size—home or office use or when travelling.

**£13.95**

**Battery operated fluorescent camping lamp.**  
Runs off 8 U2 batteries.

**£4.50**

# Mullard

**AUDIO MODULES IN BARGAIN PACKS**  
**CURRENT CATALOGUE**

**PRICE £ AT OVER 25 PER PACK**

**SEE OUR PRICES**


**1** PACK 1. 2 x LP1173 10w. RMS output power audio amp modules. + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.  
OUR PRICE **£4.95**  
p+p £1.00

**2** PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.  
OUR PRICE **£7.45**  
p+p £1.00

**illus. £7.45**  
p+p £1.00

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT.

**10 + 10 AMPLIFIER KIT**  
An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.  
Size approximately 9 1/4" x 8 1/4" x 4"  
p&p £2.05 **£11.95**

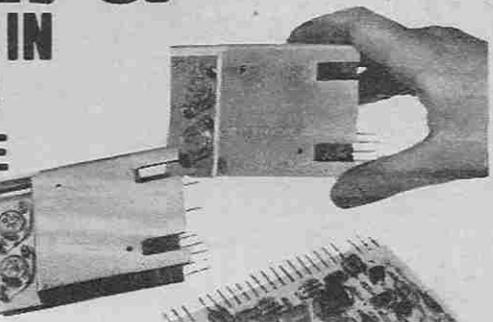

**ACCESSORIES**

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£2.90** plus £1.50 p&p

**Two Way Speaker Kit**  
Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£3.95** per stereo pair plus £1.50 p&p



**BARGAINS FOR PERSONAL SHOPPERS**

LED 5 function men's digital watch stainless steel finish **£5.95**  
LCD 5 function men's digital watch stainless steel finish **£6.95**  
LCD 8 Function **CHRONOGRAPH** men's digital watch, stainless steel finish **£12.95**  
**POCKET CALCULATOR.** With LED display, memory and percentage key **£2.95**  
**AM/FM DIGITAL CLOCK RADIO** Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer **£11.95**

125 Watt Power Amp Module **£13.95**  
Mains power supply for above unit **£3.50**  
MULLARD Built power supply **£1.50**  
DECCA 20w Stereo speaker kit comprising 2.8" approx. bass units + 2.3" approx. tweeter inc. crossovers **£20.00**  
"VIDEOMASTER" Super Score TV Game with pistol mains operation **£14.95**

**PORTABLE RADIO/CASSETTE RECORDER, AM/FM** with clock LW, MW, SW, VHF mains/battery operation. **£41.95**  
**VIDEOMASTER COLOUR SHOT TV GAME**  
Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED. **OPPORTUNITY AT £9.95 ONLY**

**50 WATT MONO DISCO AMP**  
**£29.95**  
P&P £2.50  
Size approx. 13 3/8" x 5 1/4" x 6 1/4"  
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

**70 & 100 WATT MONO DISCO AMP**  
Size approx. 14" x 4" x 10 1/4"  
Brushed aluminium fascia and rotary controls  
Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level.  
Output 100 watts RMS 200 watts peak.

70 watt **£57**  
140 watt peak p&p £4.00  
100 watt **£65**

**FOR PERSONAL SHOPPERS ONLY**  
**DUO II SPEAKERS**  
Attractive teak finish, modern design, incorporating 2 speaker units—8" approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz impedance 8 ohms. Power 15 watts RMS. 20 watts max. Per stereo pair **£17.00**

**FOR PERSONAL SHOPPERS ONLY**  
**STEREO RADIOGRAM CABINET**  
Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**  
Size approximately 47" x 15 1/2" x 15"




323 EDGWARE ROAD, LONDON W2  
21 A. HIGH STREET, ACTON W3 6NG  
ACTON: Mail Order only. No callers  
ALL PRICES INCLUDE VAT AT 12 1/2%  
All items subject to availability. Price correct at 4/4/79 and subject to change without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK

## 24 TUNE DOOR CHIMES
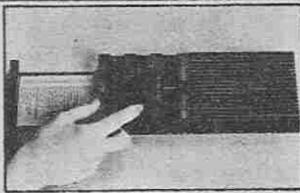
### DOOR TUNES £16.44 + VAT.

Waddington's Videomaster announces a doorbell that doesn't go Brrring, Ding-Dong or Bzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



## T.V. GAMES

### PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to expand your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/right/left) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



### EXTRA CARTRIDGES:

**ROAD RACE** - £8.87 + VAT.  
Grand Prix motor racing with gear changes, crash noises  
**SUPER WIPEOUT** - £8.17 + VAT.  
10 different games of blasting obstacles off the screen  
**STUNT RIDER** - £12.16 + VAT.  
Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.  
**NON-PROGRAMMABLE TV GAMES**

6 Game - COLOURSCORE II - £13.50 + VAT.  
10 Game COLOUR SPORTSWORLD £22.50 + VAT.

## CHESS COMPUTERS

### STAR CHESS - £56.00 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.




### CHESS CHALLENGER 7 - £85.05 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Castling, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.
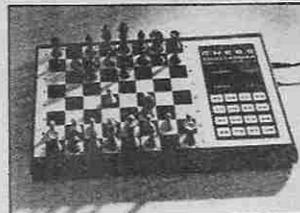
### OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

**CHESS CHAMPION** - 6 LEVELS £92.07 + VAT.  
**CHESS CHALLENGER** - 10 LEVELS - £143.00 + VAT.  
**BORIS** - MULTI-LEVEL TALKING DISPLAY £195.20 + VAT.



ELECTRONIC CHESS BOARD TUTOR £19.75 inc. VAT.

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 7 master games.

## DRAUGHTS COMPUTERS

### CHECKER CHALLENGER 2 LEVELS £43.98 + VAT. 4 LEVELS £90.09 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

### PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER.



## FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on. Calls welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm Mon-Sat (9am-1pm Wed). To order by telephone please quote your name, address and Access/Barclaycard number. Postage and Packing FREE.

**AJD DIRECT SUPPLIES LIMITED**, Dept. EE5, 102 Bellegrave Road, Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)

# ELECTROVALUE

Your leading direct suppliers for



**NASCOM MICROCOMPUTERS  
AND FULL SUPPORTING RANGE  
OF ITEMS TO ENABLE YOU TO  
WORK AT PROPER  
PROFESSIONAL LEVELS**

- ★ At newest reduced prices.
- ★ Widest possible range stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

**Appointed distributors for the  
fine products of:**

**SIEMENS, ISKRA, RADIOHM,  
VERO AND MANY OTHER  
FAMOUS MANUFACTURERS**

It's a good deal better from

## ELECTROVALUE LTD

Dept. EE8, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.  
Phone: Egham 3603. Telex 264475.  
Northern Branch (Personal shoppers only), 680 Burnage Lane,  
Burnage, Manchester M19 1NA. Phone (061) 432 4945.

### ● We pay postage

in U.K. on orders list value £5 or over. If under, add 30p handling charge.

### ● We give discounts

on C.W.O. orders, except for a few items marked Net or N in our catalogues.

5% on orders, list value £10 or more

10% on orders list value £25 or more.

Not on Access or Barclay card purchase orders.

### ● We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

### ● We guarantee

all products brand new, clean and to maker's spec. No seconds, no surplus.

### ● WE WILL SEND YOU OUR 120-PAGE CATALOGUE No. 9 FREE ON REQUEST.

Comprehensive, informative, very well produced. Write, phone or call for your free copy, together with latest current price list.

# GREENWELD

443D MILLBROOK ROAD, SOUTHAMPTON SO1 0HX  
All prices include VAT—just add 25p post



### PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resistant pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.50

## COMPONENT GABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors diodes and I.C.'s. All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts!

All parts contained in clearly marked bags in a plastic storage cabinet. 292 x 121 x 165mm with 9 drawers into which all parts can be neatly located.

If bought individually parts plus case would cost over £45 but we are offering this for ONLY £29.95 + £3 p & p. Simply send a cheque or P/O for £30.95 for immediate despatch.

### CONTENTS:

200 ½ watt resistors  
20 Wire wound resistors  
70 Ceramic Capacitors  
70 Mylar Capacitors  
50 Polyester Capacitors  
58 Electrolytic Capacitors  
61 Transistors  
12 I.C.'s  
20 L.E.D.'s  
95 Diodes and rectifiers

Altogether 614 components.

Price includes current catalogue and Greenweld pen for reordering supplies. Plus free surprise gift.

## THE NEW 1978-9 GREENWELD CATALOGUE

### FEATURES INCLUDE:

- 50p Discount Vouchers
  - Quantity prices for bulk buyers
  - Bargain List Supplement
  - Reply Paid Envelope
  - Priority Order Form
  - VAT inclusive prices
- PRICE 30p + 15p POST

## KITS OF BITS FOR EE PROJECTS

We supply parts for nearly all EE projects—for a detailed components list of this month's, and previous articles, please send SAE.

Examples from earlier issues:

**MW MINI** £2.50  
**SOUND TO LIGHT UNIT** £1.85  
**AIR FRESHENER** £7.95  
**FUZZ BOX** £4.00  
**TRANSISTOR TESTER** £2.85  
**TREMELO UNIT** £6.95  
**LOW COST METAL LOCATOR** £3.25  
**ELECTRONIC CANARY** £3-15 inc Box  
**DOING IT DIGITALLY** £23-25

Largest range of quality components in the U.K.—over 8,000 types stocked

# Marshall's

Head office and mail order to DEPT EE  
A. Marshall (London) Ltd.  
Kingsgate House, Kingsgate Place, London NW6 4TA  
Tel: 01-624-0805 Telex 21492

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 also 325 Edgware Road, W2. Tel: 01-723 4242.  
Glasgow: 85 West Regent Street, G2 2QD Tel: 041-332 4133 and Bristol: 108A Stoke's Croft, Bristol. Tel: 0272 426801/2.

### LEDS + OPTO BY SIEMENS

Displays 7 seg	LEDS	Red	Gr	Yell
Com anode or cath	5mm	18	19	20
Red	Large 5mm	20	20	20
14mm HT	£1.50 Extra			
10mm HT	£1.45 Bright	40	40	40
8mm HT	£1.57 Red LDZ71	£0.55		
18mm HT	£1.85 IR receiver	£1.45		
	Opto coupler	£1.55		

Full range + data in our '79 catalogue

### RAACO STORAGE BOXES

Strong durable high impact polystyrene boxes with brass hinge pins.

B3	£1-62	B13	£1-78
----	-------	-----	-------

### LINEAR (See catalogue for full range)

LM339N	0-80	LM1828N	1-90	CA3266	0-70
LM340T-5	0-80	LM1830N	1-90	CA3268A	0-90
LM340T-12	0-80	LM1848N	1-50	CA3268B	1-25
LM340T-15	0-88	LM1848N	1-98	CA3269	0-70
LM340T-24	0-88	LM1850N	1-90	CA3269A	0-90
LM341P-5	0-56	LM1889N	2-50	CA3300	1-50
LM341P-12	0-56	LM1890N P.O.A.	CA3300A	2-30	
LM341P-15	0-56	LM2907N-8	0-80	CA3303	3-70
LM341P-24	0-56	LM3011N-1	1-10	CA3304	2-75
LM343K	0-97	LM3301N	1-60	CA3305	3-00
LM348N	0-95	LM3302N	0-55	CA3306	1-21
LM350K	0-50	LM3401N	0-55	CA3308	2-20
LM358N	0-60	LM3900N	0-68	CA3308A	4-10
LM360N	3-00	LM3905N	1-15	CA3309	0-70
LM370N	3-30	LM3909N	0-78	CA3340	3-75
LM371H	2-25	LM3911N	1-10	CA3341	1-65
LM373H	3-35	LM3913N P.O.A.	CA3342	1-85	
LM374N	3-35	LM3914N	2-70	CA3343	2-20
LM377N	1-80	LM4250CN	1-30	CA3345	1-55
LM378N	2-40	LM78L05CH	0-85	CA3346	0-77
LM378S	4-25	LM78L12CH	0-85	CA3347	2-45
LM380N-8	0-98	LM78L15CH	0-85	CA3347A	3-10
LM380N-14	2-00	LM78L24CH	0-85	CA3348	1-98
LM381AN	1-70	LM7805KC	1-56	CA3349	1-98
LM381N	1-69	LM7812KC	1-56	CA3350	2-66
LM382N	1-32	LM7815KC	1-56	CA3351	1-82
LM384N	1-55	LM7824KC	1-56	CA3352	1-77
LM385N	1-10	LM78L05CZ	0-30	CA3353	0-70
LM387N	1-10	LM78L12CZ	0-30	CA3354	2-10
LM388N	1-00	LM78L15CZ	0-30	CA3355	2-18
LM388N	1-00	LM78L24CZ	0-30	CA3360	2-50
LM392N	0-87	MC667P	2-75	CA3362	3-75
LM7018	2-99	MC671P	1-75	CA3364	1-10
LM701C	2-99	MC672P	1-75	CA3365	1-80
LM702C	0-81	MC724P	2-10	CA3368	1-90
LM703LN	1-15	MC739P	1-80	CA3370	1-90
LM709CH	0-70	MC790P	1-10	CA3371	1-90
LM709-8	0-50	MC798P	2-20	CA3372	1-90
LM709-14	0-49	MC799P	2-20	CA3375	1-70
LM710CH	0-87	MC832P	0-70	CA3376	2-12
LM710-14	0-48	MC833P	0-70	CA3380	0-85
LM711CN	0-48	MC838P	0-82	CA3380A	0-80
LM715	1-00	MC837P	0-82	CA3386	0-50
LM723CH	0-62	MC838P	2-35	CA3388F	1-87
LM723C-14	0-45	MC840P	1-65	CA3389E	2-90
LM741CH	0-30	MC844P	0-70	CA3390Q	4-40
LM741C-8	0-30	MC845P	0-70	CA3130	1-60
LM741C-14	0-30	MC846P	0-70	CA3140	1-04
LM747CN	0-78	MC849P	0-70	LD3T1	2-25
LM748-8	0-50	MC857P	0-85	LF355N	0-80
LM748-14	0-50	MC861P	0-85	LF356N	0-80
LM900	0-50	MC1035P	1-90	LF357N	0-80
LM911	0-50	CA3300	3-30	LF13201N	3-00
LM921	0-50	CA3301	4-25	LF13331N	3-00
LM923	0-50	CA3302	2-30	FI3300A	3-00
LM1303N	1-15	CA3306	4-00	LF13741N	0-38
LM1304N	1-52	CA3307	4-15	LM114H	2-75
LM1305N	1-02	CA3308	2-55	LM301AH	0-40
LM1307N	1-22	CA3312	1-65	LM301-B	0-30
LM1310N	2-10	CA3313	1-85	LM304H	1-50
LM1331N	1-20	CA3314	2-20	LM307N	0-50
LM1453N	0-45	CA3018	0-75	LM308H	0-50
LM1496N	0-97	CA3018A	1-10	LM308N	0-55
LM1800N	1-94	CA3020	2-20	LM309KC	1-55
LM1801N	2-25	CA3020A	2-50	LM317K	3-35
LM1808N	2-10	CA3021	2-40	LM317MP	1-35
LM1812N	0-20	CA3022	2-20	LM317T	2-20
LM1820N	1-16	CA3023	2-20	LM318N	2-45

### MEMORIES (see catalogue for full range)

MM2708Q	0-00	MM88C30N	2-00	TMS4043-2N1	2-58	TMS9903N	13-74
MM2804Q	0-00	MM5311AN	4-47	TMS4044-20N18	8-5	TMS9904	P.O.A.
MM5303N	0-63	MM57105N	10-43	TMS4045-20N18	8-5	TMS9905	P.O.A.
MM5307AA/N13	0-65	MM57109N	13-41	TMS4050-2N1	8-48	ADC0817CCN	
MM5314	4-69	MM57160N	6-71	TMS4051-2N1	8-46		15-63
MM5316	4-60	MM57161N	6-71	TMS4060-2N1	8-48	ADC3511CCN	8-30
MM5330	4-25	TMS7165JL	19-50	TMS4116-25JL		ADC3711CCN	9-35
MM80C95N	0-58	TMS4027-25N1			26-00	ADD3501CCN	8-30
MM80C96N	0-56		6-10	TMS4164N	P.O.A.	ADD3701CCN	9-35
MM80C97N	0-56	TMS4033N1	1-75	TMS6011NC	5-36	AY2513	8-75
MM80C98N	0-66	TMS4036-2N1	3-28	TMS9900JL	44-41	AY-8500	12-58
MM82C19N	2-90	TMS4039-2N1	2-78	TMS9901N1	10-66	AY-8710	12-75
MM82C29N	2-08	TMS4042-2N1	2-90	TMS9902N1	9-16	SFF7301A	8-85
						SFF96364	16-00

### CMOS (see catalogue for full range)

74C00N	0-24	74C48N	1-38	74C85N	1-04	CD4000	0-20	CD4013B	0-52
74C02N	0-24	74C73N	0-54	74C107N	1-22	CD4001	0-20	CD4014	1-00
74C04N	0-24	74C74N	0-56	74C150N	4-14	CD4002	0-18	CD4015	0-75
74C08N	0-24	74C76N	0-54	74C151N	2-47	CD4003	1-25	CD4016	0-52
74C10N	0-24	74C83N	1-30	74C154N	3-68	CD4007	0-18	CD4017B	1-05
74C14N	0-24	74C85N	1-30	74C157N	2-20	CD4008B	0-98	CD4919B	1-05
74C20N	0-24	74C88N	0-84	74C160N	1-11	CD4009	0-58	CD4019B	0-52
74C30N	0-24	74C89N	4-39	74C161N	1-11	CD4010	0-58	CD4020B	1-15
74C32N	0-24	74C90N	0-85	74C162N	1-11	CD4011B	0-20	CD4021	1-05
74C42N	0-24	74C93N	0-85	74C163N	1-11	CD4012	0-20	CD4022B	1-00

### NEW 1979 CATALOGUE

48 page catalogue—new enlarged micro section—largest range of quality components from franchised suppliers available in UK. All VAT inclusive prices. Over 8,000 line items plus lots more. 45p post paid or 35p to callers at any of our four branches.

### ★ MAIL ORDER ★

Quick service on all orders—please add 40p for p/p to all orders. Telephone orders on credit cards £10.00 minimum.



Credit cards welcome

## Get a great deal from Marshall's

### 3 1/2 DIGIT LCD AND LED PANEL METER KITS

Low-cost, easy-to-assemble kits using the new Intersil 7106/7 A/D converters

Intersil's 7106 is the first single-chip CMOS A/D for driving LCD displays — including backplane — directly. The 7107 is the first single-chip CMOS A/D for driving instrument-size LED displays directly without buffering. Each provides parallel seven segment outputs, ideal for DVMS, DPMs and anywhere modern digital displays are needed. Both have internal reference and clock, and both are CMOS so you get low noise (12 to 15µV) comparable with the finest bipolar devices, and low power (10 mW max. @ 10V).

Kits provide all materials... including PC board, for a functioning panel meter. Assembly time is only 1 hour.

ICL 7106B (LED)	£26.99	SPECIAL OFFER	£19.90
ICL 7107E (LED)	£21.99	SPECIAL OFFER	£15.90
Chip alone - ICL 7106B		SPECIAL OFFER	£7.90

### L200 - 5 Terminal Adjustable Voltage and Current Regulator

The L200 is a silicon monolithic integrated circuit for voltage and current programmable regulation.

- ADJUSTABLE OUTPUT CURRENT UP TO 2A
  - ADJUSTABLE OUTPUT VOLTAGE DOWN TO 2.85V
- REDUCED PRICE NOW ONLY £1.95 each.

### TRIACS

POWER PRICES AT UNBEATABLE PRICES	TYPE	RATING	CASE	PRICE
TIC206D	Plastic TO66	400v	4A	£0.60
TIC225D	Plastic TO66	400v	6A	£0.70
TIC226D	Plastic TO66	400v	8A	£0.70
TIC266D	Plastic TO66	400v	12A	£1.00
TIC246D	Plastic TO66	400v	16A	£1.21
TIC253D	Plastic TO3	400v	20A	£1.87
TIC263D	Plastic TO3	400v	25A	£2.20
40576				£2.20
40665				£1.30
40444				£2.25
40444				£1.95

### THYRISTORS

TYPE	RATING	CASE	PRICE
TIC44T	0-6A 30v	TO18	£0.30
TIC46T	0-8A 100v	TO18	£0.50
TIC47T	0-6A 200v	TO18	£0.68
2N5060	0-5A 25v	TO18	£0.32
2N5061	0-5A 50v	TO18	£0.33
2N5062	0-5A 100v	TO18	£0.40
2N5063	0-5A 150v	TO18	£0.43
2N5064	0-5A 200v	TO18	£0.45
Bst180246	4-7A 700v	Plastic	£1.48
BY106		Stud Mounting	£1.10
BT121 (XK3139/3158/3132)			£1.10
BT121 (XK3134)			£1.10

### TTL (see catalogue for full range)

SN74H05N	0-80	74LS63N	1-25	74LS183N	2-70
SN74H10N	0-56	74LS73N	0-42	74LS189N	3-74
SN74H11N	0-55	74LS74N	0-42	74LS190N	1-00
SN74H12N	0-55	74LS76N	0-42	74LS191N	1-00
SN74H13N	0-55	74LS78N	0-42	74LS192N	0-95
SN74H14N	0-55	74LS83AN	0-90	74LS194N	0-70
SN74H51N	0-55	74LS85N	0-95	74LS195N	0-70
SN74H53N	0-55	74LS88N	0-64	74LS196N	0-80
SN74H55N	0-55	74LS90N	0-64	74LS197N	0-80
SN74H60N	0-55	74LS92N	0-70	74LS240N	1-50
SN74H62N	0-55	74LS93N	0-64	74LS241N	1-50
SN74L00N	0-55	74LS95AN	0-90	74LS242N	1-25
SN74L02N	0-56	74LS96N	1-35	74LS243N	1-25
SN74L04N	0-60	74LS107N	0-42	74LS244N	1-60
SN74L07N	0-50	74LS109N	0-42	74LS245N	1-55
SN74L14N	0-90	74LS112N	0-42	74LS247N	1-00
SN74L18N	2-62	74LS113N	0-42	74LS248N	1-00
SN74L32N	2-30	74LS114N	0-42	74LS249N	1-09
74LS00N	0-20	74LS122N	0-62	74LS251N	1-00
74LS01N	0-26	74LS123N	0-62	74LS253N	1-00
74LS02N	0-26	74LS124N	1-70	74LS259N	1-00
74LS04N	0-26	74LS125N	0-60	74LS260N	1-00
74LS05N	0-29	74LS126N	0-50	74LS269N	1-55
74LS06N	0-26	74LS132N	0-85	74LS261N	3-25
74LS09N	0-26	74LS136N	0-42	74LS266N	0-44
74LS10N	0-26	74LS138N	0-65	74LS273N	1-30
74LS11N	0-26	74LS139N	0-65	74LS275N	3-20
74LS12N	0-26	74LS145N	1-30	74LS278N	0-58
74LS13N	0-26	74LS147N	1-65	74LS280N	1-00

**EDITOR**

F. E. BENNETT

**ASSISTANT EDITOR**

B. W. TERRELL B.Sc.

**PRODUCTION EDITOR**

D. G. BARRINGTON

**TECHNICAL SUB-EDITOR**

T. J. JOHNSON G8MG5

**ART EDITOR**

R. F. PALMER

**ASSISTANT ART EDITOR**

P. A. LOATES

**TECHNICAL ILLUSTRATOR**

D. J. GOODING

**EDITORIAL OFFICES**

Kings Reach Tower,  
Stamford Street,  
London SE1 9LS  
Phone: 01-261 6873

**ADVERTISEMENT MANAGER**

R. SMITH  
Phone: 01-261 6671

**REPRESENTATIVE**

N. BELLWOOD  
Phone: 01-261 6865

**CLASSIFIED MANAGER**

C. R. BROWN  
Phone: 01-261 5762

**MAKE-UP AND COPY DEPARTMENT**

Phone 01-261 6618

**ADVERTISEMENT OFFICES**

Kings Reach Tower  
Stamford Street,  
London SE1 9LS

# Projects... Theory... and Popular Features ...

Every household needs an electronics constructor.

Without such an enthusiast in the house, the family is in serious danger of missing out on an awful lot. A home may be replete with expensive electronic consumer products like audio centres, TV, radio and recorders; it may even boast a microwave oven, a home computer, and a video recorder, yet be without some very desirable additional services and facilities that electronics can provide quite cheaply.

Why such an oversight?

Well these kind of electronic devices are not always available in the shops; or if they are do not receive the lavish promotion in the glossy Sunday Supplements and other media that is bestowed upon the more prestigious and expensive products. So the public by and large is ignorant of a whole range of interesting and useful electronic devices, instruments, or gadgets, that can help the smooth running of the home and add to personal pleasure and comfort in countless unexpected ways.

This underlines the importance to the community of the electronics constructor. One role he or she performs is filling-in deficiencies that the commercial market cannot or will not cover.

Electronics provides something special in the way of creative pastimes, the pursuer of this hobby is kept in touch with developments in the most exciting technology of our

times, and the permanent spin-off from his or her efforts can be of lasting value to the whole family.

Look at this month's projects. Is there a single household that could not make use of one if not more of these designs? Strictly functional devices for the kitchen, the bedroom, the front porch and even for the holiday-home-on-wheels, are complemented by some that come into the amusement category: an electronic quiz master, a tuning aid for the guitarist, and a Swanee Whistler! Finally, less glamorous but indispensable in the constructor's workshop, there is a mains operated power unit.

Just as every householder needs an electronics constructor, so every electronics constructor needs EVERYDAY ELECTRONICS. With selections of designs such as these every month the enthusiast is in clover—and the only possible regret will concern the shortness of time at his or her disposal for this exciting and worthwhile pastime.

If you are a newcomer to electronics, please note it's never too late to start. Study *Square One* regularly and stand by for our new 12 Part Series *Teach In 80*, commencing in our October issue. We have the right method for home study—as will be confirmed by former "graduates" of 72, 74, 76 and 78 *Teach In's*.



Our September issue will be published on Friday, August 17. See page 495 for details.

**Readers' Enquiries**


We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

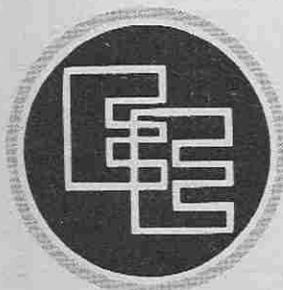**Component Supplies**

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



# Everyday ELECTRONICS

VOL. 8 NO. 8

AUGUST 1979

## CONSTRUCTIONAL PROJECTS

- WARBLING TIMER** Versatile, variable timing range by O. N. Bishop 474  
**9V POWER SUPPLY** Variable supply for the workshop by S. V. Essex 479  
**MINI MODULE: 10—SWANEE WHISTLER** Novel sound effects by George Hylton 482  
**ELECTRONIC TUNING FORK** Audio and visual tuning aid for guitars by R. A. Penfold 490  
**TRAILER FLASHER** Direction indicators for towed vehicle by J. Bloxham 500  
**TOUCH-ON PILOT LIGHT** For short-term low level illumination by F. G. Rayer 510  
**LIGHT PLUS BELL** Economical 2-way signalling circuit by S. Vaughan 515  
**QUIZ REFEREE** Precedence detector with time-up indicator by A. P. Donleavy 516

## GENERAL FEATURES

- EDITORIAL** 472  
**CROSSWORD NO. 18** by D. P. Newton 478  
**DOING IT DIGITALLY** Part 10: Binary addition and subtraction by O. N. Bishop 484  
**BRIGHT IDEAS** Readers hints and tips 489, 495  
**READERS LETTERS** Your news and views 494  
**VIDEO REVOLUTION** Developments in TV home recording by Adrian Hope 496  
**SHOP TALK** Retail news, products and component buying by Dave Barrington 499  
**COUNTER INTELLIGENCE** A retailer comments by Paul Young 503  
**SQUARE ONE** Beginners Page. Photo guide to soldering 504  
**EVERYDAY NEWS** What's happening in the world of electronics 506  
**RADIO WORLD** A commentary by Pat Hawker 508  
**WORKSHOP MATTERS** Metal working by Harry T. Kitchen 512  
**MICROPROCESSOR BASICS** Part 6: Programming a microprocessor (cont.) by R. W. Coles 521  
**JACK PLUG AND FAMILY** Cartoon by Doug Baker 522  
**RUMMAGING AROUND** Money saving ideas for the constructor by Keith Cadbury 524  
**PROFESSOR ERNEST EVERSURE** The Extraordinary Experiments of. by Anthony J. Bassett 525  
**PLEASE TAKE NOTE** Metal Locator, Pocket Radio 526

### Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price 70p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

### Binders

Binders to hold one volume (12 issues) are available from the above address for £2.85 (U.K.), £3.45 (overseas) inclusive of postage and packing. Please state which Volume.

### Subscriptions

Annual subscription for delivery direct to any address in the UK: £8.50, overseas: £9.50. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613 Kings Reach Tower, Stamford Street, London SE1 9LS.

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

**OUR  
REGULAR  
FEATURE  
FOR  
BEGINNERS**

Is on page 504

SQUARE  
**one**

# Warbling TIMER

By O. N. Bishop

**T**HIS device emits a warbling tone at the end of a pre-set period of time. The tone is loud and distinctive, yet reasonably melodious, so the timer is suitable for many applications in the home. It can time periods of a few minutes duration or periods as long as two or three hours.

## TIMING CIRCUIT

The timing circuit consists of a field effect transistor TR1 and a low-value capacitor C1 together

with a resistor R1 connected as in Fig. 1. The source-drain resistance of the f.e.t. is high when the circuit is first switched on; it immediately begins to decrease rapidly but later decreases more slowly. The effect of the change of resistance is to produce a change in the potential-divider. As the resistance of the f.e.t. decreases, the potential at A rises. (If you connect these three components together as shown in Fig. 1, using a patch-board or wires with crocodile clips, you can use a voltmeter to observe

what happens.) After the circuit is switched on, the potential rises rapidly during the first second. Next it continues to rise but much more slowly, over a period lasting several minutes, Fig. 2. It eventually becomes steady at around 5.75V (assuming a 9V supply).

Typical values are:

C1 (pF)	Rapid limited rise to	Time to reach 5.75V
120	2.5V	1.5 minutes
6800	1.2V	2 hours

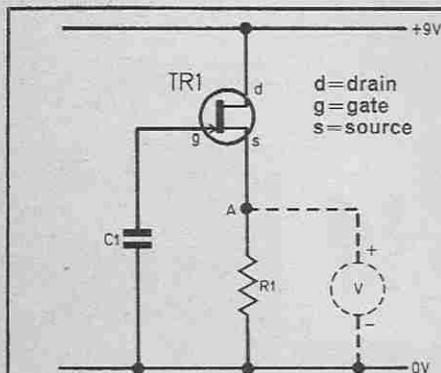


Fig. 1. The timing circuit. Changes of potential at point A may be examined by a voltmeter as shown.

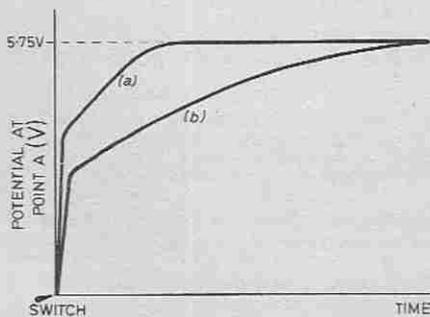


Fig. 2. Rise in potential at point A: (a) with low value capacitor (b) with capacitor of greater value.

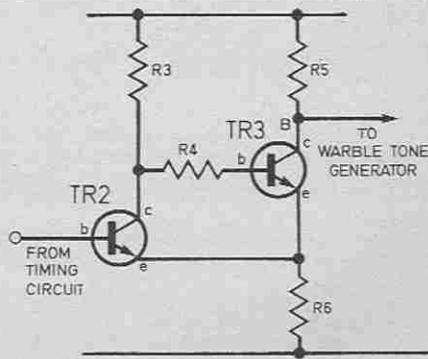


Fig. 3. The trigger circuit: b=base, c=collector, e=emitter.

Thus the operating period of the timer is partly determined by the value chosen for C1. For periods up to 1.5 minutes, C1 can be 120pF. For longer periods (up to about 45 minutes) C1 should have a greater value, say 1500pF. For periods of 2-3 hours, C1 should be 6800pF.

## TRIGGER CIRCUIT

The trigger circuit consists of two transistors TR2, TR3 and their associated resistors R3-R6 as shown in Fig. 3. When the potential at the base of TR2 exceeds a certain triggering level, a base current flows so switching TR2 on. The potential at the collector of TR2 falls and the base current to TR3 is thus reduced. TR3 is switched off. Since it is no longer conducting, the potential at its collector (point B) rises to almost 9V. Current then flows to the integrated circuit that generates the warbling tone.

The trigger circuit comes into action when the potential at the base of TR2 rises above 2.7V. VR1 and R2 (Fig. 4) form a potential divider. As the potential at A rises to 5.75V, the potential at the wiper rises to a lesser value. If the wiper is set at the end of VR1 nearer to A, the potential at the wiper exceeds 2.7V relatively quickly and timed periods are short.

To increase the length of timed periods, the wiper is set round the end of VR1 nearest to R2. If set too

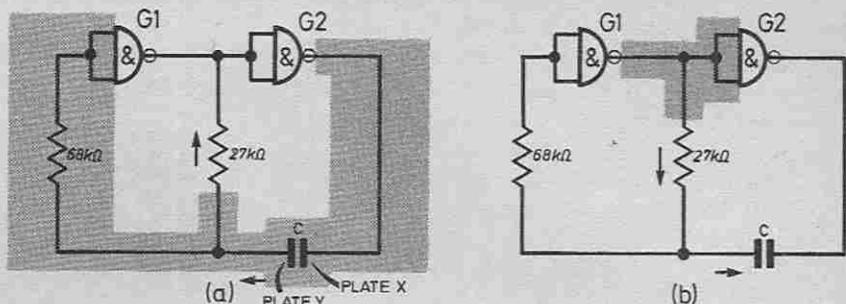


Fig. 5. The two states of an astable multivibrator, as used in the warble-tone generator. Parts of the circuit shaded are at "high" potential; other parts are at "low" potential.

close to the R2 end, the potential may never reach 2.7V.

## WARBLE TONE GENERATOR

The tone generator consists of two multivibrators, each built from two NAND gates.

The four gates are contained in a single CMOS integrated circuit IC1, type CD4011. In this circuit the two inputs of each gate are connected so that each gate acts as an inverter. When both gate inputs are "high" (9V), its output goes "low" (0V) and vice versa.

## MULTIVIBRATOR ACTION

The action of a single multivibrator is shown in Fig. 5. In (a) the output of gate 1 has just gone 'low', making the input to gate 2 'low' also. This causes the output of gate 2 to go high, so raising the potential of all parts of the circuit that are shaded in Fig. 5a.

Current flows from plate Y of the capacitor through the 27 kilohm

resistor to the part of the circuit that is at "low" potential, as indicated by the arrows. As the circuit current flows, the potential of this part of the circuit rises giving a steadily increasing input potential at gate 2. The rate at which potential rises depend on the values of the resistor and capacitor.

When the input potential becomes high enough to count as a "high" input the gate begins to change state. Its output potential begins to fall, giving a low input to gate 1, which then produces a "high" output.

We have now arrived at the state shown in Fig. 5b. Now the reverse conditions apply and the current begins to flow through the resistor in the reverse direction and charges plate X. The input potential of gate 2 gradually falls. When it has fallen to a sufficiently low value, the gate changes state again and the astable returns to the original state shown in Fig. 5a. Thus this arrangement of 2 gates changes state regularly at a rate

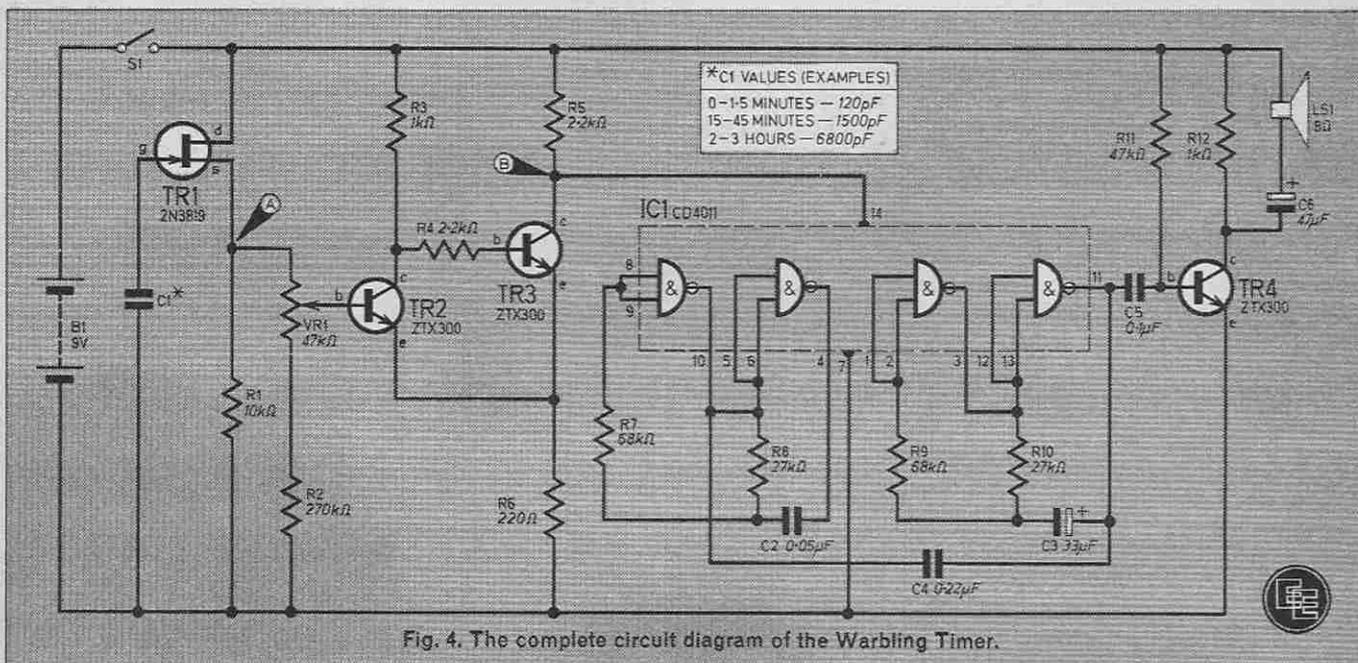


Fig. 4. The complete circuit diagram of the Warbling Timer.

dependent on the value of the capacitor and resistor.

## TWO ASTABLES

In the warble-tone generator we have two such astables, one with a  $0.05\mu\text{F}$  capacitor oscillating at a few hundred hertz to give an audible tone, the other with a  $33\mu\text{F}$  oscillating at about  $0.5\text{Hz}$  to produce the warbling effect. The two astables are coupled by capacitors C4 so that each astable has an effect on the action of the other. The result is not a simple combination of the two frequencies but a complex warbling tone that is very suited to this application. The combined output is fed through C5 to the final stage of the timer, the amplifier. This consists of a single transistor TR4 which drives the loudspeaker LS1.




## COMPONENT BOARD

The unit is built on a single piece of stripboard (Fig. 7). Begin by constructing the timing circuit (TR1, C1, R1). If you have a Testmeter set it to a suitable voltage range and connect it between the ground rail (battery negative, strip B) and the source terminal of TR1. Switch on and observe the potential rise (Fig. 2).

Depending on the applications you have in mind for the timer, you may decide at this stage to use a capacitor of higher or lower value. Alternatively, if you need just a *slight* increase in the timing period, you can connect a second capacitor between strips L and T—in parallel with C1.

(When two or more capacitors are connected *in parallel*, their total capacitance is the sum of their individual capacitances. For example, if your C1 has a capacitance of  $1000\text{pF}$  and the potential rises to  $5.75\text{V}$  in only 25 minutes, but you would like to be able to time up to 30 minutes, you can either use a capacitor value of  $1200\text{pF}$ , or add a capacitor of value,  $200\text{pF}$  in parallel with C1,

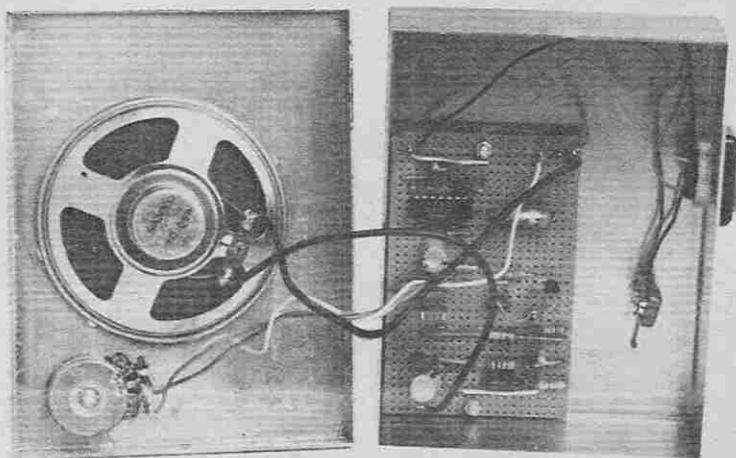

The finished Warbling Timer showing positioning of board and components mounted on the front panel.

whichever is more convenient.)

Next build the trigger circuit (TR2, TR3, R3-R6) and the potential-dividing network (VR1, R2). Test the output of this circuit by increasing the voltage at the collector of TR3 (S31). At switch-on this should remain low (a fraction of a volt) but rise sharply to almost  $9\text{V}$  at the end of the timing period.

Altering the setting of VR1 varies the length of this period. The nearer the wiper of VR1 is set to the "R2" end of VR1, the longer the period. Note that if it is set *too* near this end, the wiper potential may never reach  $2.7\text{V}$  and the circuit will not be triggered. For initial testing, it is best to set it at the end nearest point A (Fig. 4), so that it is triggered after the shortest possible time.

The amplifier section is best built next, including C5. To test roughly, switch on and then join the free terminal of C5 (G23) alternately to battery positive and negative. Loud clicks should result.


## INTEGRATED CIRCUIT

IC1 is a CMOS device and needs special handling precautions. It is better to solder most of the other components in position first (C2-C4, R7-R10 and the various wire links) before soldering the i.c. Note that pins 3 and 12 and also pin 5 and 10 are to be joined by the copper strips beneath the board, so the strips should NOT be cut away at G9 and E9.

Keep the i.c. in its original pack-

ing until you are ready to solder it in place. Then spread a rectangle of kitchen foil on your workbench and connect this by wire to earth (for example, a cold water pipe). Alternatively use an earthed "tin" lid (unpainted) such as the lid of a biscuit tin.

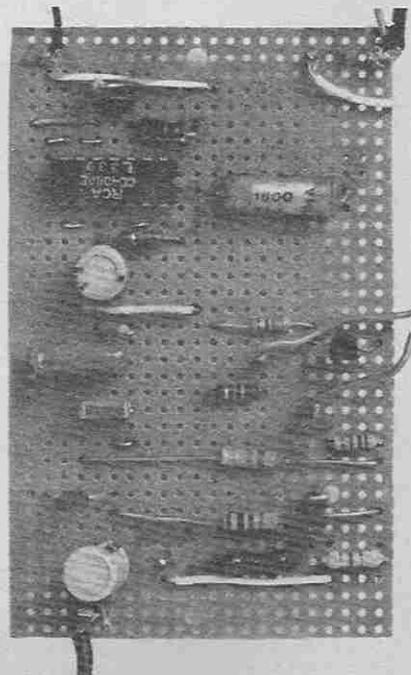Place the circuit board on the metal sheet. Roll up your sleeves if you are wearing clothing made of nylon or other man-made fibre. Touch your fingers against the earthed sheets before unwrapping the i.c. or removing it from the black conduction foam in which



The completed circuit board.

# Warbling TIMER


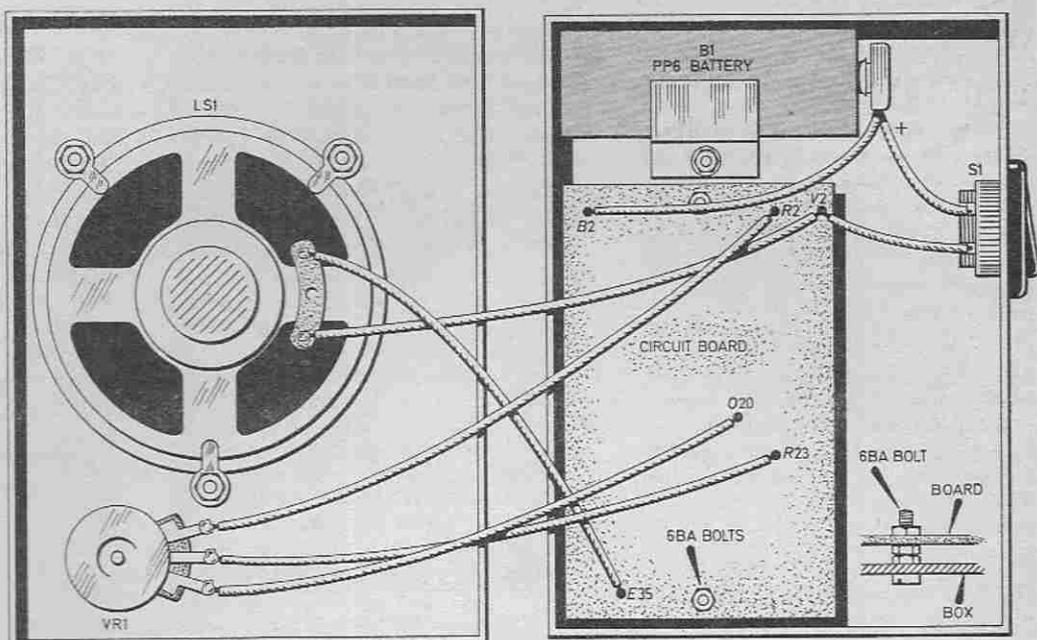


Fig. 6. The complete assembly with inter-wiring between the circuit board and the other components mounted directly onto the aluminium box.

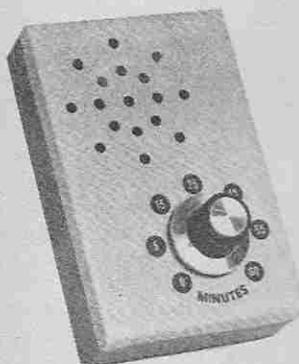

## COMPONENTS

### Resistors

R1	10k $\Omega$
R2	270k $\Omega$
R3	1k $\Omega$
R4	2.2k $\Omega$
R5	2.2k $\Omega$
R6	220 $\Omega$
R7	68k $\Omega$
R8	27k $\Omega$
R9	68k $\Omega$
R10	27k $\Omega$
R11	47k $\Omega$
R12	1k $\Omega$

All  $\frac{1}{4}$  W carbon  $\pm 5\%$

### Potentiometer

VR1 47k $\Omega$  carbon linear

### Capacitors

C1	1500pF (see text)
C2	0.05 $\mu$ F disc ceramic
C3	33 $\mu$ F 25V elect.
C4	0.22 $\mu$ F polyester type C280
C5	0.1 $\mu$ F polyester
C6	47 $\mu$ F 25V elect.

### Semiconductors

TR1	2N3819 <i>n</i> -channel f.e.t.
TR2	ZTX300 silicon <i>n</i> pn
TR3	ZTX300 silicon <i>n</i> pn
TR4	ZTX300 silicon <i>n</i> pn
IC1	CD4011AE Quad 2-input NAND gate, 14-pin d.i.l.

See  
**Shop  
Talk**  
page 499

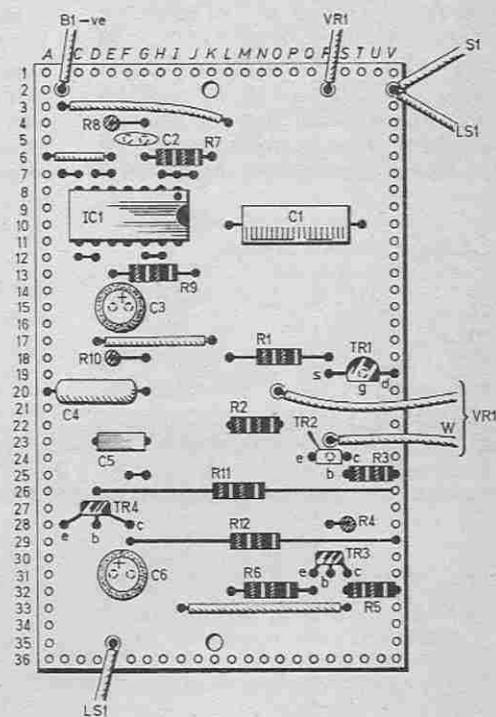
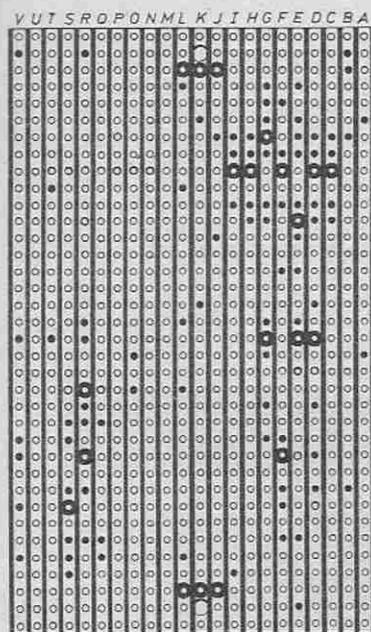


Fig. 7. Underside and top view of the stripboard. Note the breaks required in the copper strips, also the wire links.


### Miscellaneous

B1	9V battery PP6
S1	toggle switch, s.p.s.t.
LS1	3 inch dia., 8 $\Omega$ speaker
	Piece stripboard, 0.1 inch matrix, 22 by 36 holes; battery connector; metal box $5\frac{1}{4} \times 4 \times 1\frac{1}{2}$ inch approx; 6BA screws and nuts; knob for VR1; connecting wire.

**COMPONENTS**  
approximate  
cost  
**£4**

you received it. Handle the i.c. as little as possible. Before each soldering operation, touch the tip of the soldering iron briefly against the metal sheet.

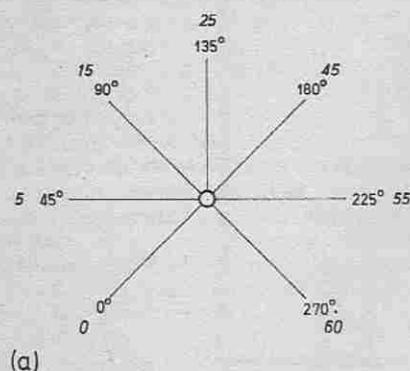
If you solder all 14 pins in rapid succession, the i.c. will become unduly hot. Solder two or three pins at a time and allow a period for cooling-off. Note that there are



(a)

begins and continues until the device is switched off.

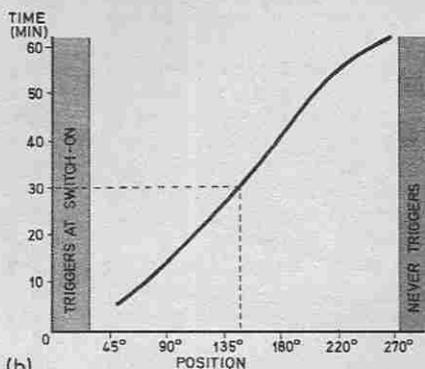Before enclosing the board in its case experiments can be made with different values of C2 and C3 to vary the warbling sound. Reduction in the value of C2 give tones of higher pitch. Reduction in the value of C3 gives a more rapidly modulated warble.



(b)

Fig. 8. (a) Positions of the knob of VR1, during calibration. (b) Calibration graph (see text) For 30 min setting the knob should be set to 140°.

several wire links to be soldered between adjacent copper strips, so as to connect pairs of pins (1 to 2, 5 to 6, 8 to 9 and 12 to 13). Finally solder R7 and R9 in position, and thereafter there is no further need for the precautions described above.

## TESTING

The circuit is now complete. After switching on, the speaker should be silent during the timing period. Then the warbling note

If the sound is not loud enough, it is worth altering the value of R11 which supplies the bias current to TR4. Changing the value of this to say 39 kilohm or 56 kilohm alters the volume and may also alter the quality of the note providing a harsher or a more gentle tone, as required.

## CASE AND BATTERIES

The board, loudspeaker, switch and VR1 may be mounted in a simple aluminium box, as shown

in Fig. 6. There is space for a PP6 battery which may be held in position by a double-sided adhesive "Sticky Fixer". Such a battery is suitable for operating the timer for periods in the 10-20 minute range.

If it is intended to run the timer frequently for periods exceeding 1 hour, it is advisable to use a bigger case to allow a larger battery to be accommodated. For example: two 4.5V heavy duty batteries, such as are used for electric bell systems; a single 6V bell battery; or a battery holder containing four HP2 cells.

For use in the workshop one could dispense with batteries and mount two terminals on the front panel instead. These could be connected to the workshop d.c. supply (6V to 9V) such as a low voltage power pack.

## CALIBRATION

The final operation is to calibrate the setting of VR1. The quickest procedure is to set the knob to the seven positions shown in Fig. 8a and measure the time taken for each position. Find the positions which give the shortest and the longest useful timing periods. For these positions and for the positions between plot a graph, Fig. 8b. You can then use this to read the exact position for any derived time and mark out a scale (calibrated in minutes) on the instrument case.

# EE CROSSWORD No 18

BY D. P. NEWTON

### ACROSS

- 1 Deliberate decaying of an oscillation.
- 4 Together with 27 Across, undesirable elastic property on making contact.
- 7 Wire attire.
- 9 Designator of operative conditions on  $I_c - V_c$  characteristic (4, 4).
- 10 Grief.
- 11 Referring to ourselves in wave.
- 13 A conveyance characteristic of a transistor.
- 14 Module assembly with a purpose.
- 17 Compensating op-amp null pin.
- 20 Characteristic electronic reveille? (4, 4).
- 22 Knock off the end of an electron.
- 23 Drilling tools.
- 24 Aerial element of managerial status.
- 25 Standard twin emission reproducing extra orchestration.


- 27 See 4 Across.

- 28 Device with axe-like properties for converting a slowly changing waveform to a high frequency one.
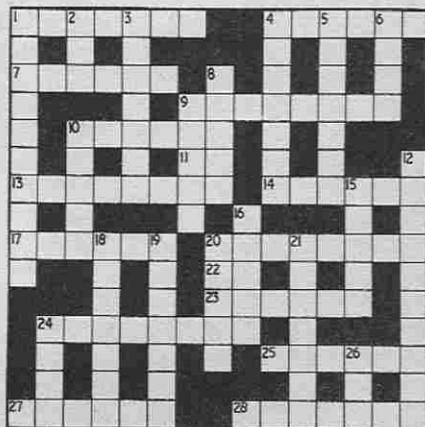
### DOWN

- 1 Lack of clarity often resulting from overloaded input.
- 2 Imperial honour.
- 3 In virtually all cases, this process turns signals over.
- 4 Areas of poor u.h.f. reception owing to material obstruction.
- 5 Renders a molecule charged.
- 6 Resistors, for example, have such a specialised language.
- 8 Square voltage on the top and resistance underneath.
- 10 Pole to aid walking.
- 12 Battery measure (6, 4).
- 15 Gates, but for some vehicles rather than for electronic purposes.
- 16 One of the smaller current carriers?

- 18 Circuit contraction of low resistance.
- 19 Charge at a slow rate.
- 20 Automaton.
- 21 Common prefix in this hobby.
- 24 Nothing is so dead.
- 26 About par for a blow.



Solution on page 526

# 9V POWER SUPPLY

By S. V. Essex

ONE OF THE first pieces of equipment a beginner to the hobby of electronics finds a need for, is a power supply. What is usually required is not an elaborate bench type supply with a high specification, but merely a battery substitute. To maximise the utility of the unit, it would be an advantage if it could be used to power a radio, cassette recorder or calculator when it is not being used for experimental purposes.

The power supply described in this article enables this to be done by simply using an ordinary phono socket as the output connection—by making

up several different leads which will all plug into this socket, connections to different pieces of equipment can be changed readily and quickly. The number of different connectors that can be used on the ends of the leads is quite large; battery connectors (to connect in place of batteries), jack power plugs, ordinary connecting plugs or crocodile clips for use when experimenting, and so on. This enormously increases the versatility of the unit.

The circuit provides a continuously variable output from 0 to 9 volts at a maximum current of about 400mA. The power supply is fully protected against an accidental short circuit applied across the output—an essential requirement for use when experimenting. It can be built into quite a small box, and will therefore take up little space on the experimenters crowded workbench.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the unit is shown in Fig. 1.

As can be seen, this is entirely conventional. A transformer, T1, has its two 12V secondary windings connected in parallel to provide 12V r.m.s. This is then rectified by the bridge rectifier consisting of diodes D1 to D4, and the resultant d.c. is smoothed by reservoir capacitor C1.

The output voltage is regulated by transistors TR2 and TR3; they are connected as a Darlington pair emitter follower, and are controlled by the voltage applied to TR2 base. This voltage is derived from the Zener diode D5, across which an almost constant voltage is developed, via a potentiometer VR1 which is used to alter the output voltage.

Bias for D5 is provided by resistors R2 and R3, hum and ripple being reduced to a minimal level by C2 and C3.

Output short circuit protection is provided by TR1. When the output current rises above about 400mA, the

voltage developed across R1 (about 0.6V) turns on TR1.

The collector of this transistor is connected to the base of TR2, so this action results in a drop in output voltage to counteract the increase in output current. This ensures that even when the output is completely short circuited, the current is limited to a safe value (about 430mA), protecting the power supply from damage.

Resistor R5 is included between the slider of VR1 and the base of TR2 to isolate the action of the overload protection circuit from C3. If this resistor were not present, operation of the protection circuit would mean that TR1 has to discharge C3 before any change in output voltage occurred. Not only would this lead to an increase in the reaction time of the circuit, but it entails TR1 having to pass a relatively heavy discharge current, which leads to unreliability, hence inclusion of R5.

Resistor R6 is included to stabilise the circuit at low output currents.


## COMPONENTS

All components are readily available, but one or two points require noting.

The transformer used in the prototype featured two separate 12V, 0.25A secondary windings, which were connected in parallel to provide 12V, 0.5A but in reality any transformer capable of providing 12V at 0.5A with a single secondary can be used. Note that it would be wise to obtain the transformer before obtaining the box into which it is to be built, if any doubt exists over its dimensions, especially if the constructor intends to follow the prototype layout described here.

The bridge rectifier can either be bought as one encapsulated unit as used in the prototype, or four discrete diodes can be used. For the former, any bridge rectifier rated at 50V, 0.5A or more can be used—a BY164 is suitable. If four separate diodes are used, 1N4001's would be suitable.

Fig. 1. Complete circuit diagram for the Nine Volt Power Supply.

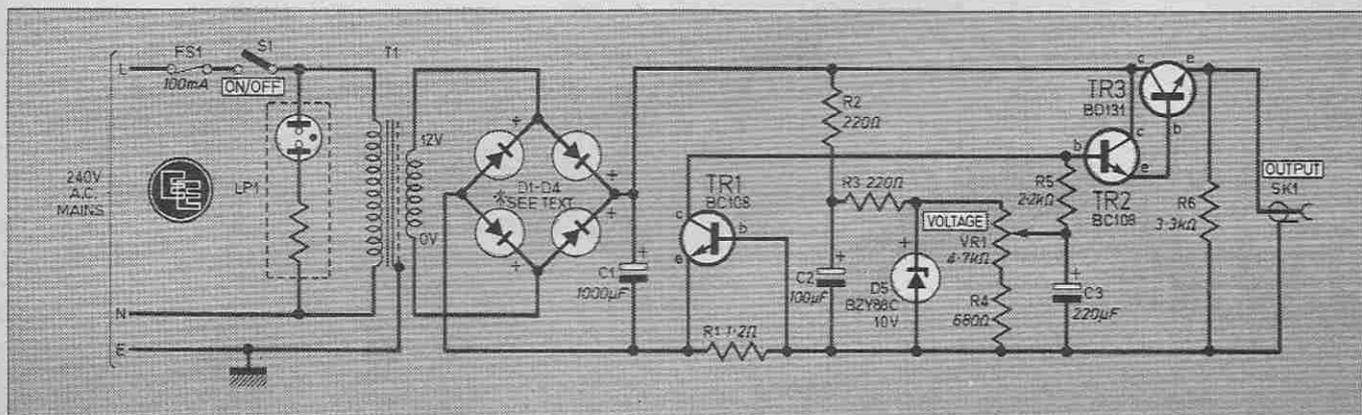

# COMPONENTS

approximate  
cost




£6.50  
excluding  
p.c.b.
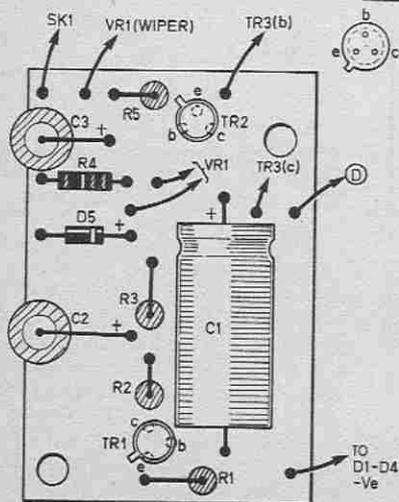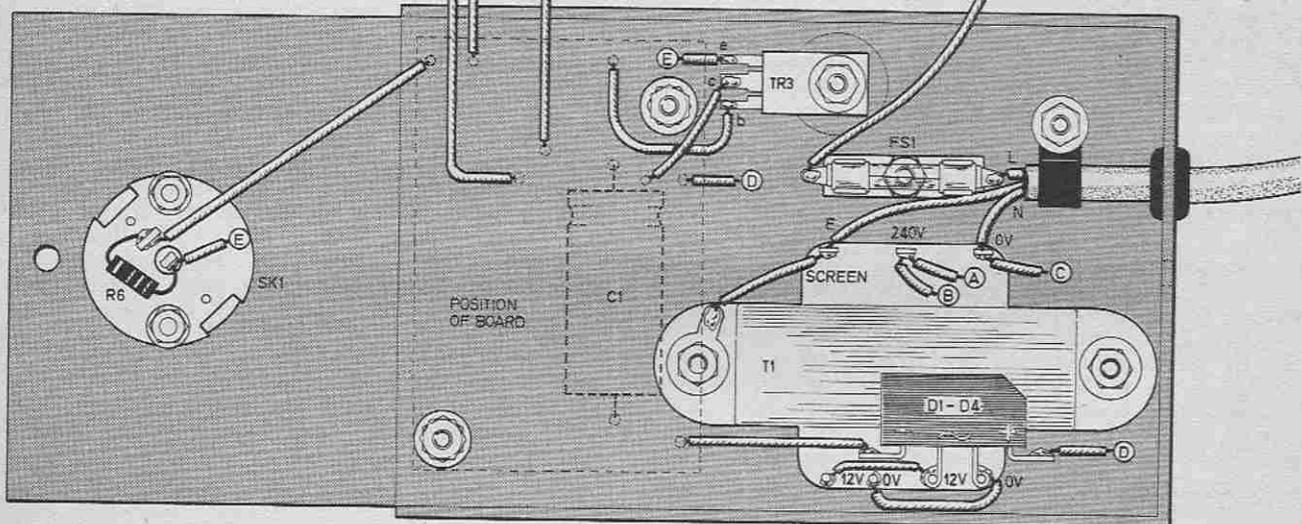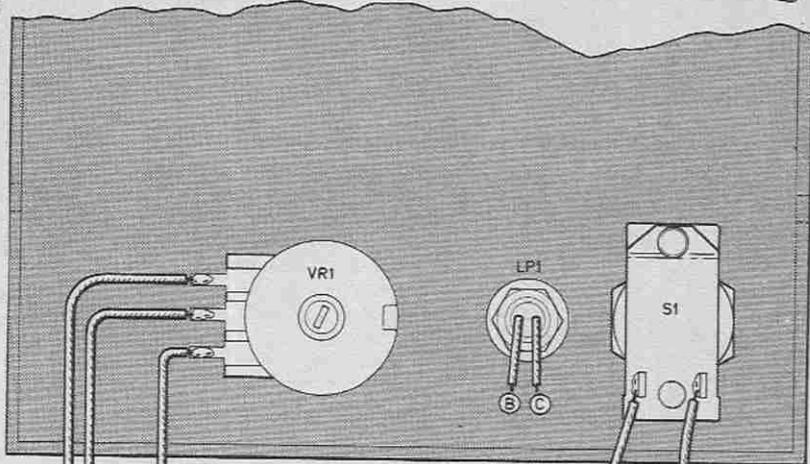
# 9V POWER SUPPLY


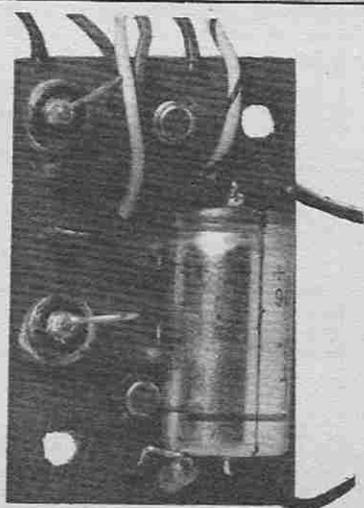


Fig. 2. (Right). Complete wiring details for the power supply. The case has been opened out for clarity. Note that TR3 is mounted with its metal face down towards the panel. Insure that the p.c.b. is mounted on short spacers (5mm) otherwise there is a risk of shorting out to the earth tag on the transformer. Careful positioning of the transformer and switch is also important.

Fig. 3. (Below). Printed circuit board as used in the prototype, also showing the component layout. This is shown full size and may be traced.

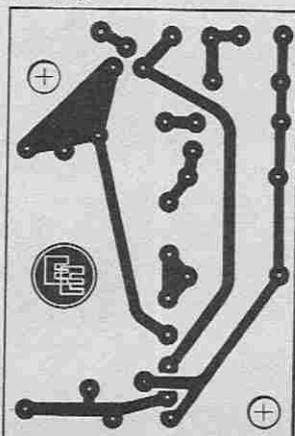

b  
c  
e  
UNDERSIDE  
VIEW OF TR1,2



# CONSTRUCTION starts here


The prototype was built in an aluminium box, type AB5, size 100 x 63 x 50mm, with the on/off switch, neon indicator (LP1), and output voltage control (VR1) mounted on the lid. The output socket was mounted on one side of the box.

The drawing of Fig. 2 shows the internal layout adopted. As can be seen, a printed circuit board was used to support the majority of the components, with the exception of the mains input components, the bridge rectifier, which was mounted directly onto the secondary transformer tags, and R6, which was soldered directly onto the output socket.

Layout is not critical and other methods of construction, for example stripboard, can be used if desired. The printed circuit layout used in the prototype is shown in Fig. 3.

Transistor TR3, because it has to dissipate a reasonable amount of heat, should be firmly mounted to the box

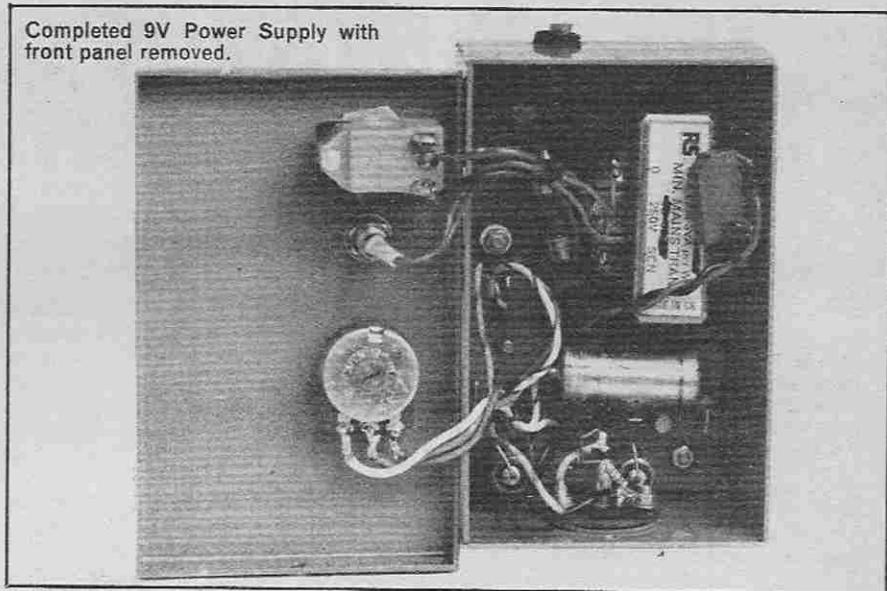Completed 9V Power Supply with front panel removed.



using a mica washer insulation kit and silicon grease. It will be found that the box will get quite warm if the output is left short-circuited for any length of time, and if the temperature of the box is thought to be excessive it can be painted matt black to allow it to dissipate the heat more readily.

The mounting hole for TR3 should be clean and free from burrs, to avoid puncturing the mica washer and to ensure good thermal contact.

For obvious safety reasons, the metal box must be reliably earthed and all components on the low voltage side of the circuit must be kept well clear of those carrying mains voltage. It will be found advantageous to leave the output electrically floating, i.e. with neither side of the output earthed, so insulation of all components, especially the output socket, should be ensured.

If the transformer is fitted with a screen this should be connected to earth.

## COMPONENTS

### Resistors

R1	1.2 $\Omega$	R4	680 $\Omega$
R2	220 $\Omega$	R5	2.2k $\Omega$
R3	220 $\Omega$	R6	3.3k $\Omega$

All  $\frac{1}{4}$ W carbon  $\pm 10\%$

### Potentiometer

VR1 4.7k $\Omega$  carbon lin.

### Capacitors

C1 1000 $\mu$ F 25V elect.  
C2 100 $\mu$ F 10V elect.  
C3 220 $\mu$ F 10V elect.

### Semiconductors

TR1 BC108 *npn* silicon  
TR2 BC108 *npn* silicon  
TR3 BD131 *npn* silicon  
D1-D4 BY164 bridge or 1N4001 silicon diodes (4 off)  
D5 BZV88C10V 10V 400mW Zener diode

### Miscellaneous

T1 mains primary, 0-12, 0-12V 250mA secondaries  
S1 single pole on/off toggle  
LP1 panel mounting mains neon  
FS1 100mA 20mm with chassis mounting holder  
SK1 single insulated phono socket  
Aluminium case type AB5, 100 x 63 x 50mm or similar; printed circuit board; insulating kit for TR3; one small round knob; four rubber feet; 6BA hardware;  $\frac{1}{4}$  inch grommet; length of mains cable as required; connecting wire.



See  
**Shop  
Talk**  
page 499

## TESTING

The simplicity of the circuit means that there is very little to go wrong, but the following points are worth mentioning.

If, during testing, it is discovered that the input voltage to the bridge rectifier is almost zero then this, assuming the use of a transformer with two 12V secondaries will be due to them being connected in anti-phase, so that the voltage in each opposes the other. Changing the connections to one of the windings is the answer.

One common error is to connect the Zener diode into the circuit the wrong way—the voltage across it is then about 0.6V and the fault is easily detected using a multimeter.

A test of the short-circuit protection circuit can be done by connecting an ammeter on its 1A range directly across the output for a few seconds, if the current exceeds about 500mA, the circuit is not functioning correctly and a careful check should be made of TR1 and its associated components.

If all the tests perform satisfactorily, and there are no faults the unit can then be put into use. After a period of use you will wonder how you ever managed without a power supply—except of course the saving on the cost of numerous batteries!  $\square$



# MINI-MODULES By George Hylton

Handy "Beginner" projects based on simple circuits and featuring a variety of building methods.

# 10

## SWANEE WHISTLER

**T**HIS month's Mini Module can serve either as a simple musical instrument or as a variable frequency audio oscillator for sound effects. Musical readers will be familiar with the Swanee Whistle. This is a simple wind instrument on the lines of a penny whistle, but instead of placing the fingers over stop holes to change the note you do so by moving a piston in the barrel of the instrument. This shortens or lengthens the pipe and so adjusts the note.

The Swanee Whistler does the same sort of thing but note adjustment is by moving a slider potentiometer. The output power is only a few milliwatts but is quite sufficient to produce an audible note in a high-impedance loud-speaker.

### LOUDSPEAKER

A speaker of more than about 50 ohms impedance may be connected directly to the output. Speakers of lower impedances require a matching transformer for maximising the output, though no harm will come to the circuit from connecting a low-impedance speaker direct.

A transformer which converts the speaker impedance to 500 ohms will receive about 20mW. The d.c. through the primary is only about 5mA. These figures show that it should be possible to salvage a push-pull output transformer from an old pocket portable and connect to the Swanee Whistler using the pocket portable original speaker of 3-8 ohms impedance.

Any kind of high-impedance ear-phone may be connected.

If the output is used to drive an amplifier, several volts are available. If the amplifier input circuit has no d.c. blocking capacitor it will be necessary to add one: 0.1 $\mu$ F should be suitable.

### THE CIRCUIT

Readers who have been following this series may have noticed that the Swanee Whistler circuit (Fig. 1) bears a close resemblance to the circuit of

the Continuity Tester which formed Number 4 of the series. This is no accident. While developing the Continuity Tester I realised that essentially the same basic arrangement could be used as an audio source, and here it is.

The two transistors TR1, TR2 form an amplifier. This is turned into an unstable amplifier by applying positive feedback from the emitter of TR2 to the emitter of TR1 via R4.

### FEEDBACK

By itself this (d.c.) feedback would merely turn TR1 hard off while allowing TR2 to be turned hard on by current through R1. However there is also some negative feedback via VR1 and R3. This tries to stabilise the circuit but its action is delayed by C1, which takes time to charge or discharge. The result is that the circuit first flips into one state because of the positive feedback then, after a while, the negative feedback catches up and resets it.

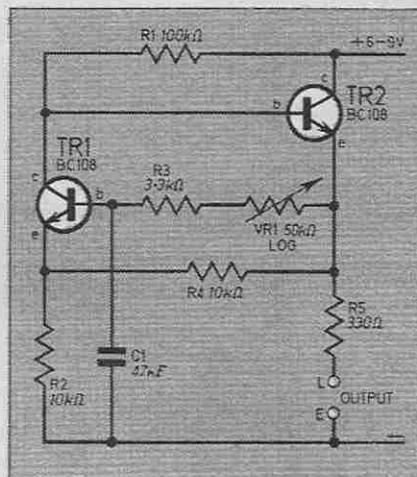


Fig. 1. Swanee Whistler circuit diagram.

The process continues, the negative feedback always lagging behind. TR2 is periodically turned on for a time then off and the current through it comes in pulses. Changing VR1 adjusts the rate at which C1 charges and this controls the frequency.

Quite large frequency sweeps can be obtained but the wider the coverage the harder it is to hit the right pitch by adjusting the slider pot VR1. So R3 is included to limit the frequency range at the high end. With the values shown the range is about 400-4,000Hz when a 100 ohm load is connected, falling to 300-1,000Hz when the load is of very high impedance.

### EFFECTS

For sound effects use it may be preferable to dispense with R3 and connect the left-hand end of the potentiometer straight to C1 and TR1 base. This will enable the frequency to shoot up to infinity (or more likely to go high then stop) with VR1 set to zero resistance.

Battery drain is less than 100 $\mu$ A when no load is connected and rises to about 5mA with a low-resistance load.

### COMPONENTS

#### Resistors

- R1 100k $\Omega$
  - R2 10k $\Omega$
  - R3 3-3k $\Omega$
  - R4 10k $\Omega$
  - R5 330 $\Omega$
- All carbon film  $\pm 5\%$ ,  $\frac{1}{4}$ W

#### Potentiometers

- VR1 47k $\Omega$  or 50k $\Omega$   
slider potentiometer log law

#### Capacitors

- C1 47nF (0.047 $\mu$ F) polyester

#### Transistors

- TR1, TR2 BC107, BC108 or BC109 (2 off)

#### Miscellaneous

- Knob for slider pot. Case (twin-switch box). Formica for panel. Pins. Hardboard, 8BA nuts, solder tags, and 5/8 inch bolts. (4 of each). 4BA bolts (4).

## CONSTRUCTION

The circuit board used in the prototype is designed for economy. A copy of the component layout diagram (Fig. 2) is laid over a suitably-sized piece of hardboard and pins inserted at each junction point to serve as solder tags for the components and wiring.

I used ordinary domestic pins one inch long then cut off the heads but domestic pins are easily bent and it may be preferable to substitute bright new half-inch panel pins which are much stiffer.

The four lead-outs are  $\frac{5}{8}$ -inch 8BA bolts, with a solder tag for connections on the inside and a nut on the outside.

end and break out the slot material carefully with the tip of a screwdriver.

The case for the prototype is a metal twin-switch box of the deeper kind as used for mounting the older sorts of light switches in the wall. Any other kind of case will serve and it need not be made of metal.

## USING THE SWANEE WHISTLER

The circuit as it stands will enable you, with the addition of a suitable speaker, to make enough noise indoors to amuse yourself or drive the family mad: continuous sounds are very penetrating even at low volume.

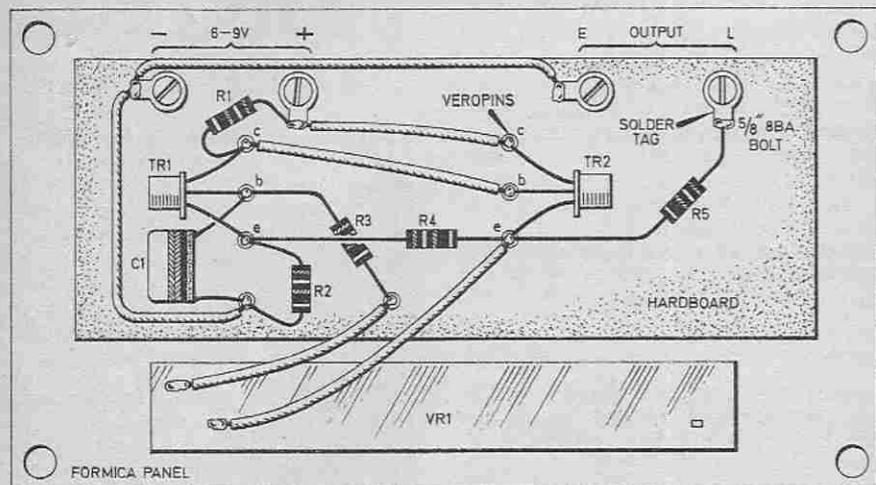


Fig. 2. Component layout on hardboard base. This is secured to the Formica panel by the four 8BA bolts.

They can then serve to fix the board to the panel as well.

The panel is a piece of Formica. Cutting the slot for the slider control can be done either by drilling a straight row of small holes, close together, then breaking down the divisions and finally tidying up with a nail file, or by using a Stanley scoring knife to cut through the Formica from the decorative side.

This second method is neater but requires patience. When the cut has gone almost through to the back of the board drill a small hole at each

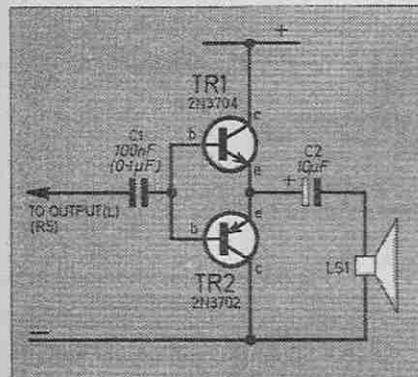


Fig. 3. An optional add-on amplifier stage.

If however it is desired to make serious musical use of the circuit some additions are desirable. First, a power amplifier to increase the volume. A low-power battery operated amplifier will be described later in this series, but it is possible to add-on a very simple low-power stage in the form of a complementary pair of transistors, Fig. 3.

Since we are dealing with square pulses and distortion is unimportant the transistors may be operated unbiased. If desired a volume control in the form of a 10 kilohm log law pot can be interposed between the Whistler output and the power amplifier. It can conveniently include an on-off switch.

If a separate tuning adjustment is needed it can be provided by substituting for R2 a linear pot of 22 kilohms or thereabouts, connected as a simple variable resistance.

## CORRECTION

Mini Module 8 (June). Formula second line 355 should read:

$$R4 \text{ (new)} = 100 \text{ kilohms}/(A-1).$$

Next Month: Mini Amplifier.

For  
Beginners

TEACH-IN 80

Continuing  
a Great  
Everyday  
Electronics  
Tradition

TEACH-IN 80

Starting  
Oct. 79  
issue

# DOING IT DIGITALLY



## PART 11

By O. N. Bishop

Table 11.1. Binary addition

Inputs (the numbers to be added together)		Outputs (the result of addition)		Equivalent equations (in binary form)
A	B	Carry C	Sum S	
0	0	0	0	0+0=0
0	1	0	1	0+1=1
1	0	0	1	1+0=1
1	1	1	1	1+1=10 (or 0, carry 1.)

**S**OLVING Jack Plug's Problem (Part 9) and adding two and two to get four have one thing in common—they are both logical operations. That being so, TTL can deal with arithmetic as well as the more perplexing problems that beset the Plug family. Since TTL has only two kinds of input and output, high (=1) and low (=0), it operates on numbers in binary form. This presents no difficulty, for it is easy to arrange a coding circuit (such as the keyboard coder described in Part 5) to turn decimal numbers into binary form, and a decoding circuit (such as the 7447 i.c.s of the Test-Bed display system) to convert the binary numbers back to decimal when the calculations are completed.

### BINARY ADDITION

Since a digit can have only one of two values in binary arithmetic, a short truth table, Table 11.1, covers all the possible addition operations.

The equation for the last line of the table would be  $1+1=2$ , if written in decimal form. The carry digit (C) is added to the next column of figures to the left when you are adding two numbers each consisting of more than one digit. If we look for logical relationships in the truth table, we find that the carry column (C) is the AND of A and B. The sum column (S) is the exclusive-OR of A and B. Exclusive-OR is a little different from the ordinary OR operation we met earlier. In exclusive-OR the output is high if one or the other but not both of the two inputs are high. In Fig. 11.1 we obtain the exclusive-OR function by using five NAND gates. If you ever need this function in other applications, this is the way to obtain it, but if you need several exclusive-OR circuits use the 7486 i.c., which has four two-input exclusive OR gates on one chip.

In Fig. 11.1 we obtain AND, by inverting NAND, so constructing the entire half-adder with NAND gates. With two 7400 i.c.s on the Test-Bed you can assemble the half-adder and carry out all the basic binary additions listed in the truth table.

The circuit is called a *half-adder* because it has no input for accepting

a carry from a previous stage of addition. For example, to add binary 11 and 1, we set out the addition like this:

$$\begin{array}{r} 11 \\ + 1 \\ \hline \end{array}$$

Answer

The half-adder can perform the first stage, adding the "units" column (or least significant digits), and giving the outputs  $S=0$ ,  $C=1$ . The "units" digit of the answer is 0, and we carry 1 to the next most significant digit, the "twos" column. Here the half-adder

could accept the 1 and 0 (not actually written but implied), but there is no way to tell it that there is a 1 carried over from the previous operation. We need a *full-adder* circuit that can accept this carry and work out that  $1+0+1$  (carried over)=0, carry 1.

A third operation is required to work out the "fours" column (most significant digit), for which a full-adder would give  $0+0+1$  (carried over)=1, carry 0. This gives us the final answer,  $11+1=100$ . In decimal, the equivalent operation is written  $3+1=4$ .

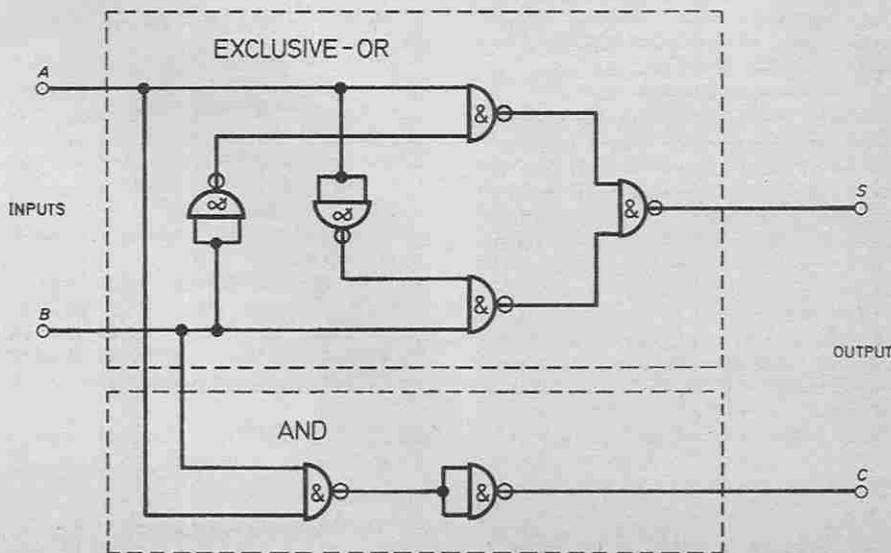


Fig. 11.1. Half-adder made from exclusive-OR and AND sub-units.

## FULL ADDER I.C.

To assemble a full-adder we need several more gates, but fortunately we can buy a complete full-adder in a single i.c., the 7480 pinning details in Fig. 11.2. This contains a full-adder circuit which adds together two input digits ( $A$  and  $B$ ) and the carry-in digit. The input gating allows us to vary the way we use the adder. The rules for inputs at the "A" set of pins are listed below.

(1) If  $A_0$  is low, the input to the adder circuit is high (=1) whatever the state of the other  $A$  inputs. Normally we wire  $A_0$  to  $V_{cc}$ , to allow the other inputs to function as in rules (2) and (3) or for short-periods use we leave it disconnected, effectively high.

(2) If  $A^*$  is high, the input to the adder is the AND of  $A_1$  and  $A_2$ .

(3) If  $A^*$  is low, the input to the adder is the NAND of  $A_1$  and  $A_2$ .

The same rules apply to the  $B$  inputs. In the circuit and Test-Bed layout shown in Figs. 11.3a and b, we make  $A_0$  and  $B_0$  high, we leave  $A_2$ ,  $A^*$ ,  $B_2$  and  $B^*$  disconnected (=high), and use  $A_1$  and  $B_1$  to input the digits to be added. If  $A_1$  is high, the adder receives the AND of  $A_1$  (=high) and  $A_2$  (=high), which is high. If  $A_1$  is low, the adder receives low. The inputs to the adder are thus identical with those applied at  $A_1$  and  $B_1$ , and their sum  $S$  is obtained from IC1 pin 5, with the carry digit appearing inverted, at pin 4. If we require a carry-in, this can be applied to pin 3 ( $C_n$ ), so for the first stage of an addition we always make  $C_n$  low.

## SERIAL AND PARALLEL ADDITION

The 7480 can add only one pair of digits and the carry-in at a time. To add numbers with more than one digit, we can work in one of two ways:

(1) SERIAL. Add the columns one at a time, working from right (least significant digit) to left (most significant digit), just as we do when working with pencil and paper.

(2) PARALLEL. Add all columns simultaneously, taking carries into account. For parallel adding we need a row of 7480's, one for each column to be added, with the carry from one i.c. fed to the i.c. dealing with the next most significant digit. Serial addition requires fewer i.c.s, for we simply present the pairs of digits to the i.c., one pair at a time in order from l.s.d. to m.s.d., and arrange for a memory unit to retain the carry digit until the next stage of addition. In this month's adding circuit we use serial addition.

## SHIFT REGISTER

Before we can put the 7480 to work we must have some means of registering the numbers we wish to add, and

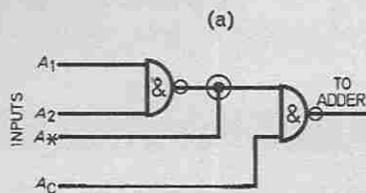
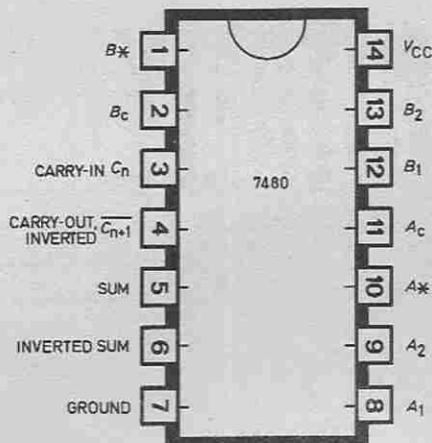


Fig. 11.2a Pinout details for the 7480 Full-adder i.c. and (b) gating on  $A$  inputs ( $B$  input gating is identical).

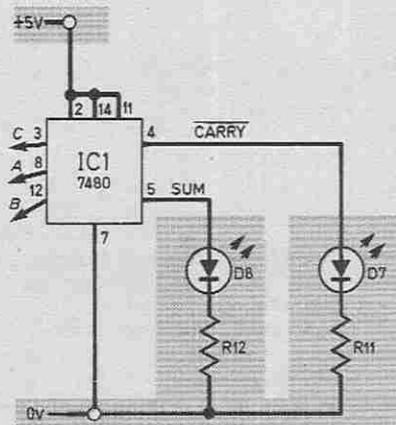


Fig. 11.3a. Circuit diagram for a Full-adder using the 7480.

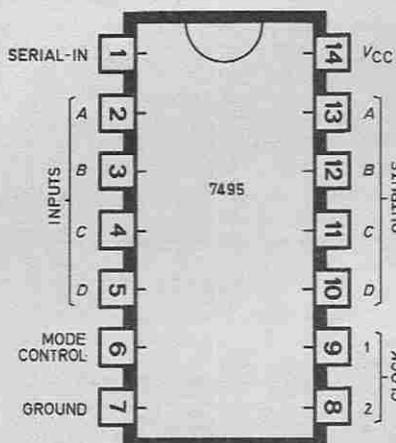


Fig. 11.4. Pinning details for the 7495 shift register.

presenting them to the adder, digit by digit, in order. In the previous series of *Doing It Digitally* we punched a paper tape to represent the rows of digits and fed this through a special home-made tape-reader. In this series we store the numbers electronically in a device called a shift register.

Many types of shift register are available, a suitable one being the 7495, see Fig. 11.4. It contains four flip-flops  $A$ ,  $B$ ,  $C$ , and  $D$ , each of which can be set (output=1) or reset (output=0) when one of the clock inputs changes from high to low.

## MODE CONTROL

To load the flip-flops we make the mode control input high, make the inputs  $A$  to  $D$  high or low (depending

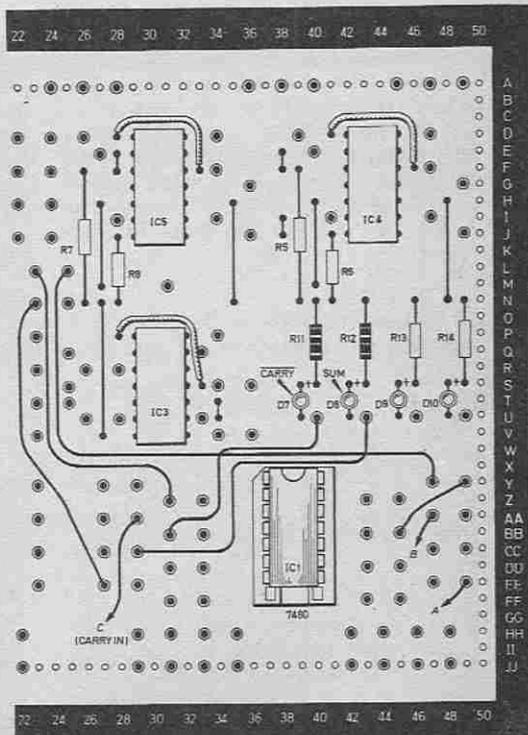


Fig. 11.3b. The circuit of Fig. 11.3a wired on the Test-Bed for testing the 7480 Full-adder.

on what number we wish to store) and wait for the clock to change from high to low. At that instant the data at the inputs is transferred to the flip-flops, and their outputs become identical with their inputs. Once the clock has gone low, the data is stored (or loaded) and changing the inputs does not alter the outputs (until the next time the clock goes low).

If the mode control is made low, data is shifted the next time the clock goes low. At that instant the content of flip-flop  $A$  is transferred to flip-flop  $B$  (all inputs  $A$  to  $D$  are ignored), the content of  $B$  is transferred to  $C$ , the content of  $C$  is transferred to  $D$ , and the content of  $D$  is lost. What

happens to flip-flop A depends upon the state of the "serial in" input (pin 1). Whatever is applied to this input, is transferred to flip-flop A when shifting occurs.

In Fig. 11.5a, serial A is grounded, so flip-flop A goes low when shift occurs. The i.c. has two clock inputs. Clock 1 input is used during shifting, and clock 2 input during loading, so that the two functions can, if required, be clocked independently. Here we clock both functions from the same clocking sequence by joining the pins together.

The easiest way of applying data to the register is to use the keyboard decoder described in Part 5 (February 1979). Note that corrections to the keyboard appeared last month. One of the spare keys is used to apply mode control. We use the lower left-hand spare key; join the drawing-pin to ground by inserting a wire link from BB24 to I24, and cut the copper strip at BB23; solder a soldercon socket at AA28, to provide a connection to mode control, and cut the strip at AA29. We call this the SHIFT key, for when the key is pressed, mode control is grounded and shifting occurs. The four l.e.d.s display the state of each register.

#### KEYBOARD SHIFT REGISTER ANNOTATION

There is some unavoidable confusion over the lettering on the keyboard diagram and that on the 7495. The keyboard (and also the outputs of the in-built counters IC4 and IC5, and the inputs to the Test-Bed display system) are labelled so that the l.s.d. is called A and the m.s.d. is called D. When using the shift register, we use flip-flop A to store the m.s.d., and flip-flop D to store the l.s.d. The l.e.d.s are lettered according to the shift registers so that they display a number just as it is written on paper, with the l.s.d. on the right. It is very helpful to know the state of the clock output and for this purpose a clock l.e.d. is incorporated.

To load a number, press one of the number keys while the clock output is high; hold the key until the clock goes low, when the binary version of the number should appear on the l.e.d.s A to D. Unless you continue to hold the number key down, the number is cleared when the clock next goes low, for the input will have become 0000 if the key is released. However, if (while the clock is high) you press and hold the SHIFT key, the number shifts one place to the right each time the clock goes low. Since "serial in" is grounded, the display is cleared digit by digit from the left.

Try entering various numbers and shifting them, to gain experience at keeping your key-pressing in time with the clock, see Fig. 11.5b.

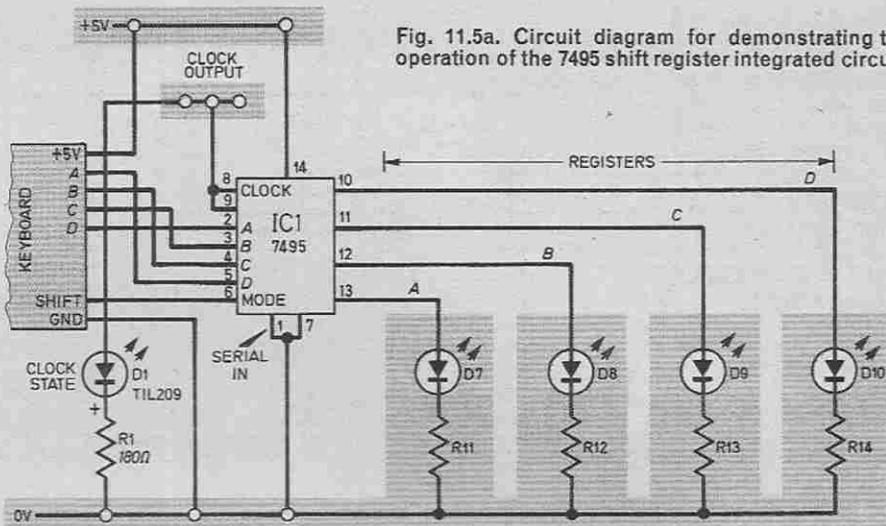


Fig. 11.5a. Circuit diagram for demonstrating the operation of the 7495 shift register integrated circuit.

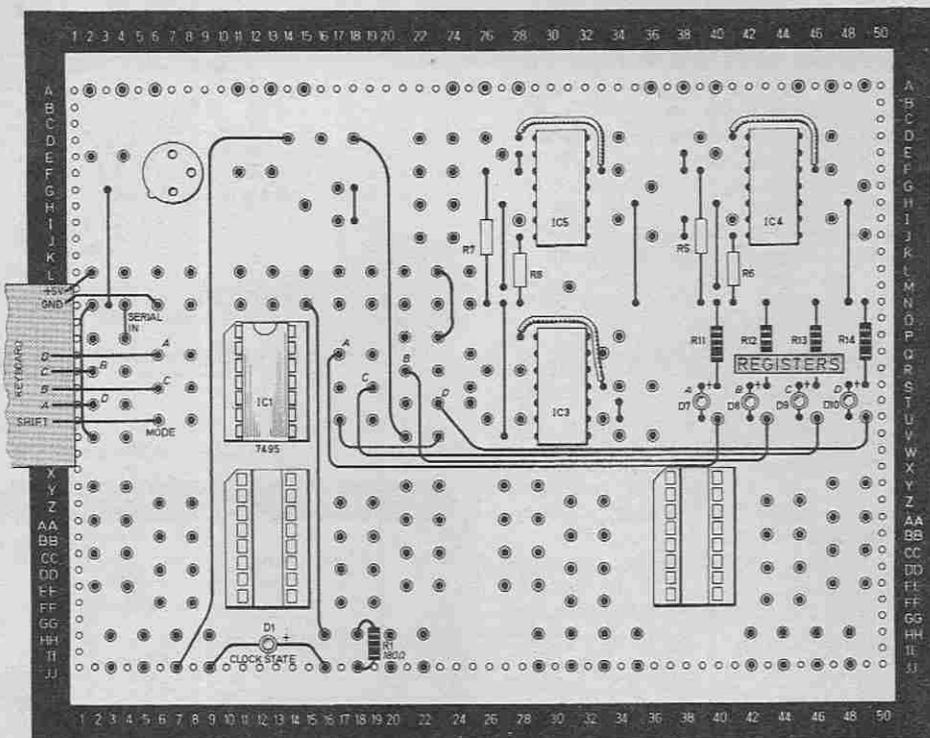



Fig. 11.5b. The circuit of Fig. 11.5a wired on the Test-Bed for testing the 7495.

#### A SIMPLE CALCULATOR

Now we are ready to combine two shift registers and an adder to make a calculator, but let us get it clear that this is in no way a substitute for your pocket calculator. The most it can do is add 7 plus 7.

The main purpose of setting it up—as with almost all the other projects set up on the Test-Bed—is to give you some insight into how logic circuits work. With only three i.c. sockets available, the Test-Bed can never carry any really complex logical circuit. Its purpose is simply to try out simple combinations of i.c.s which, once understood, can be built into a permanently wired unit.

This simple calculator is particularly valuable as it is a good example of a sequential logical circuit. This is a circuit in which the output is not decided simply by its present inputs, but partly by inputs at earlier stages. The circuit (Fig. 11.6a) is designed to add together two three-digit binary numbers, which we shall represent by XYZ and LMN. We first load XYZ into shift register 1, then shift it serially in shift register 2; as it leaves register 1, we enter LMN in register 1. The digits are then shifted out of the D flip-flops of both registers and into the adder, which sums Z with N, Y with M, and X with L, making any carries that are necessary.

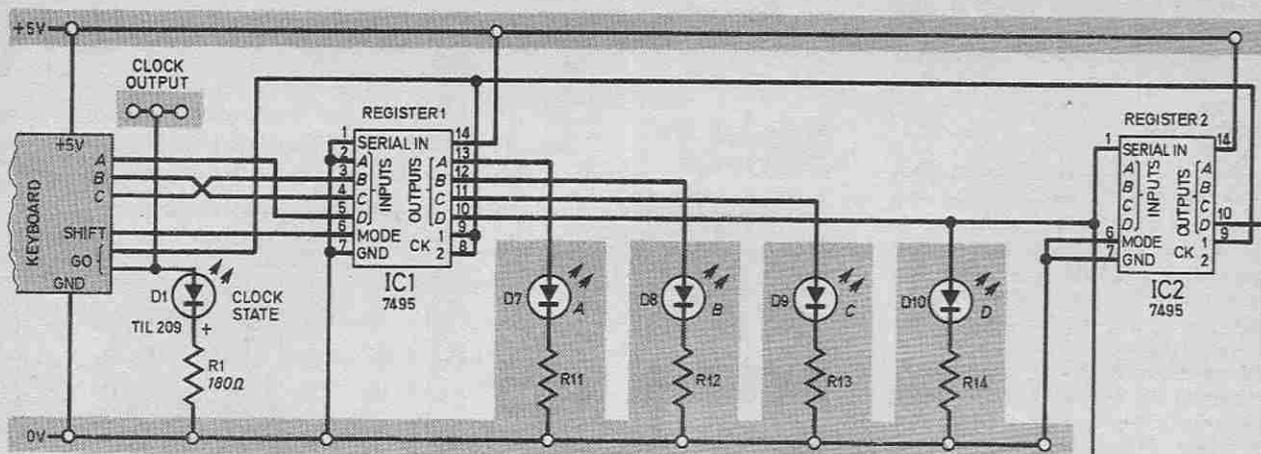

## TEST-BED CALCULATOR

The layout on the Test-Bed is shown in Fig. 11.6b, but for the moment we will simplify matters by omitting the carry-over facility, and therefore ground the carry input of the 7480. To make the circuit easier to handle, a switch is included between the clock output and the registers. For this go key, we use another of the spare keys on the keyboard, the bottom right-hand key. To make this suitable cut the copper strip at BB29, and insert soldercon pins at AA34 and BB34.

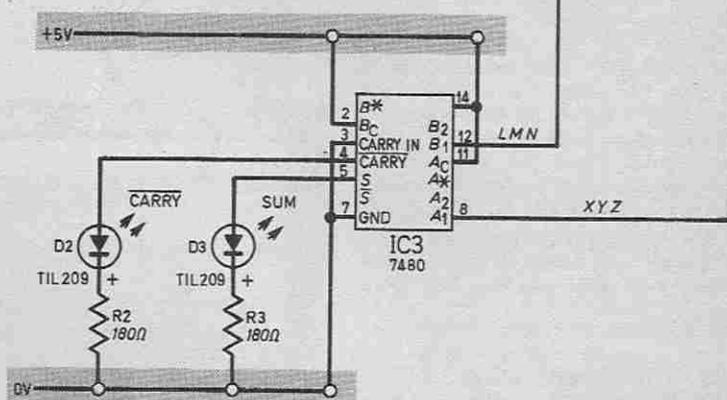


Fig. 11.6a. Circuit diagram for a simple calculator (without carry facility).

Fig. 11.6b. The circuit of Fig. 11.6a wired on the Test-Bed.


## SHIFT SEQUENCE

Since Register 2 has simply to receive number XYZ shifted from Register 1, its mode control is permanently grounded and only the clock 1 input is required. The output from flip-flop D, Register 1, is shifted direct to flip-flop A, Register 2 by way of the serial-in pin.

The addition sequence, reading from top to bottom is illustrated in Fig. 11.7. Remember that loading and shifting occur as the clock goes from low to high. To feed in the clock pulses, the go key must be pressed and held all the time. To halt the sequence, release go when the clock is high; to resume the sequence press go when the clock is high. If go is pressed when the clock is low, this may cause multiple low pulses which will shift the data one or even more places along. You will probably need to watch the clock state i.e.d. and count out aloud as you run through the stages of calculation.
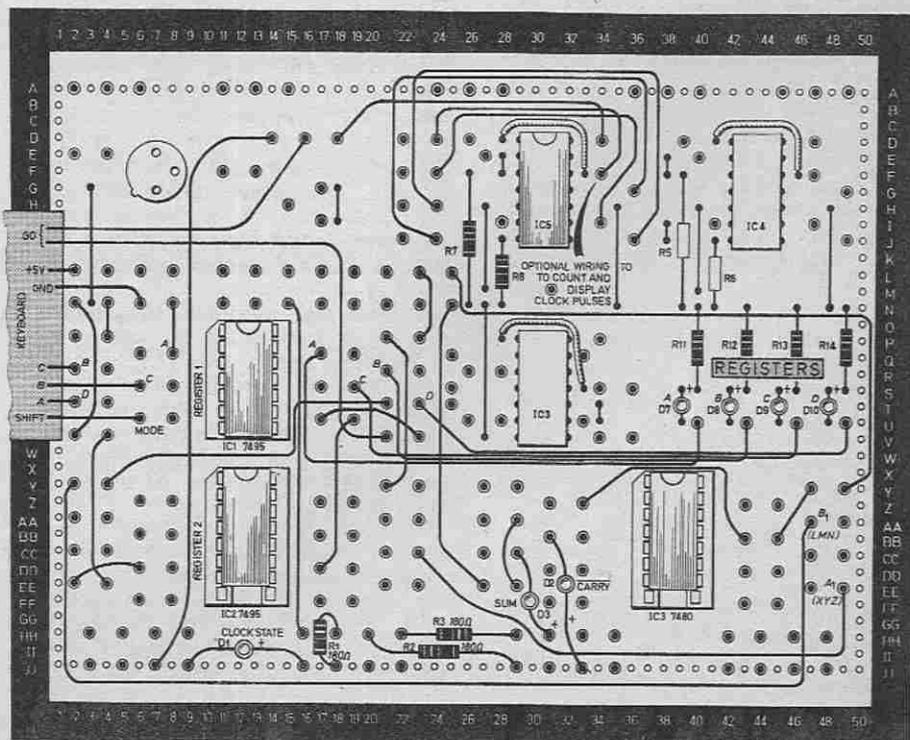
## CLOCK SPEED

If the clock runs too fast for you to keep up with it, try feeding the clock output into IC4 (pin D47) and use the output from pin F47 as a clock running at half frequency (or even pins J47, J49, or G49 for lower frequencies). You may find it easier to keep count if you wire up IC5 as a



counter, connecting its output to the right-hand 7-segment display. The display changes each time the clock goes low.

## OPERATION

In Fig. 11.7 it can be seen that the answers appear on the SUM and CARRY i.e.d.s immediately after counts 5 to 8. The l.s.d. comes first. You will have noticed that this calculator has only a 3-digit input, input A of Register 1 being wired to ground. This is necessary because a blank space is needed between X and N to make room for the final carry after X and L have been added.

Since this circuit has no provision for carry, use it only with additions in which no carry is required, for example, 1+10, 101+10, 1000+101.

When you have tried out a few additions you will begin to realise how much easier it would be if there could be additional control circuits to make shifting take place at exactly the right stages, and to record the serial output from the adder. It is possible (and not really difficult) to shift the answer digits back into Register 1 and display a four-digit answer, but there is just no room on the Test-Bed to mount both the calculator circuit and the few control circuits that are needed. Perhaps the reader may be motivated to design and build a slightly more sophisticated calculator incorporating these refinements.

## CARRY

The carry function can be performed manually by disconnecting the carry input from ground at each step of the calculation when the *previous* step has produced a low output at CARRY. With so many other things to think about at the same time, manual carrying taxes the patience of the most cool-headed, and an automatic carry is almost essential. Fortunately it can just be fitted on to the Test-Bed, making use of the remaining built-in circuits.

## CIRCUIT DESCRIPTION

The complete carry circuit is shown in Fig. 11.8a. The bistable changes state when a low pulse appears on lines P or Q, depending upon which state it is in already; P and Q cannot both go low at the same time, and neither can go low while the clock is high. The bistable can change state only during the second half of a clocking period, that is to say the time leading up to a "count" when loading or shifting occur.

During the first half of a time period, immediately after a count, the two digits presented to the adder are added and CARRY becomes high (= carry 0) or low (= carry 1). This has

OPERATION	CLOCK OUTPUT	COUNT	DIRECTION OF SHIFT →									
			OUTPUTS REGISTER 1				OUTPUTS REGISTER 2				OUTPUTS OF ADDER	
			A	B	C	D	A	B	C	D		
	LOW	START	0	0	0	0	0	0	0	0	0	IGNORE
PRESS KEY FOR XYZ	HIGH	1	0	X	Y	Z	0	0	0	0	Z	
XYZ LOADED	LOW	2	0	0	X	Y	Z	0	0	0	Y	
	HIGH	3	0	0	0	X	Y	Z	0	0	X	
	LOW	4	0	0	0	0	X	Y	Z	0	0	READ ADDER OUTPUTS IN ORDER AND RECORD RIGHT TO LEFT
	HIGH	5	0	0	0	0	X	Y	Z	0	Z+N (L.s.d.)	
PRESS KEY FOR LMN	LOW	6	0	L	M	N	0	X	Y	Z	Y+M	
	HIGH	7	0	0	L	M	N	0	X	Y	X+L	
	LOW	8	0	0	0	L	M	N	0	X	FINAL CARRY (m.s.d.)	
	HIGH	FINISH	0	0	0	0	L	M	N	0		

Fig. 11.7. The sequence of operations for adding two binary numbers XYZ and LMN.

no immediate effect on the bistable, but CARRY remains high and when clock next goes high, P goes low. This triggers the bistable to change state (if the bistable is not already in that state) giving a low output to the carry-in terminal of the adder.

When the clock goes low again, at the next count of the calculation sequence, there is no change in state of the bistable. Its output remains low, giving low carry-in to the next stage of the calculation. Thus the low carry from one stage gets added in with the new pair of digits of the next stage. Suppose that this addition results in CARRY going low (= carry 1). There is no immediate effect on the bistable, but when the clock goes high Q goes low and it changes state. This gives a high input to carry-in and this is retained ready for the next stage of addition. Note that when the clock goes high and there is a change of state of the bistable the *new* carry-in is being fed to the adder, which may then give a different output. This does not affect the carry-over operation but may affect the SUM display. This display should therefore be read immediately after each count, while the clock is still low.

## USING DISCRETES

To make this carry circuit we use in-built IC3 to provide the bistable, the INVERT gate and one of the NAND gates. The other NAND is made from discrete components. This is a useful reminder that although we use i.c.s. most of the time, there are occasions

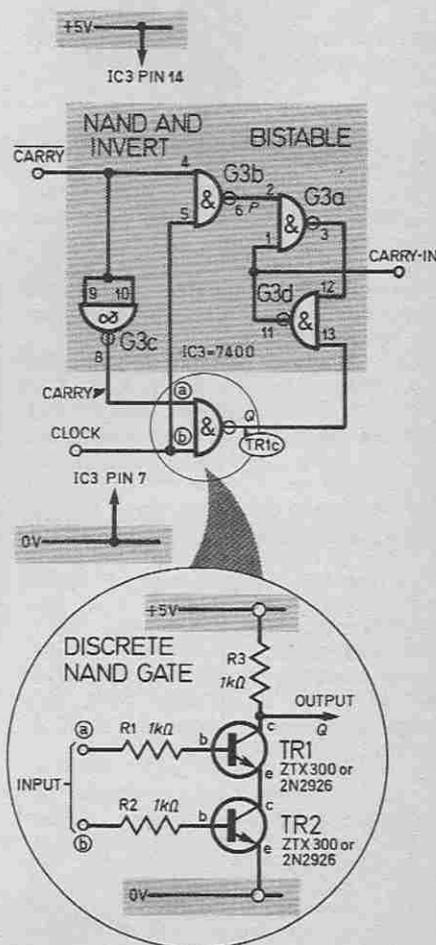


Fig. 11.8a. Circuit diagram for carry function and circuit of a discrete NAND gate.

when it is more convenient to go back to first principles and build a gate from a few transistors and resistors.

From Fig. 11.8a it can be seen that the output is high unless both transistors are switched on. When both are switched on, by applying high inputs to both bases, the output is effectively connected to ground, and becomes low. Almost any npn transistor can be used to build this gate. The additional wiring for the carry circuit is shown in Fig. 11.8b. The link from AA29 to EE29 (Fig. 11.6b) is removed, and the CARRY l.e.d. is no longer required.

When the carry circuit has been connected, try calculations involving carrying, such as 1+11, 1111+1111, 110+110.

## SUBTRACTION

The Test-Bed is looking more like a bird's nest than ever before, but there is still one more improvement to make.

Luckily, binary subtraction can be carried out by a process involving addition. The rule is simple; for example, to subtract 110 from 1000, we first find the complement of 110. We do this by replacing all the 1's by 0's and all the 0's by 1's, so the complement of 110 is 001. We then add the 001 to 1000 and finally add 1 to the total:

$$\begin{array}{r} 1000 \\ + \text{complement of } 110 \quad 001 \\ + 1 \\ \hline \text{equivalent to } 1000 - 110 = 10 \end{array}$$

Ignore the first 1 in the answer, arriving at 010, which is the difference required.

In our calculator we can find (XYZ-LMN) by loading XYZ in the normal way, but when LMN is being fed to the adder at input A<sub>i</sub> we make A\* low, so that the inverse of each digit it presented to the adding circuit of the 7480. We can use a third spare key on the keyboard to ground A\* when it is pressed.

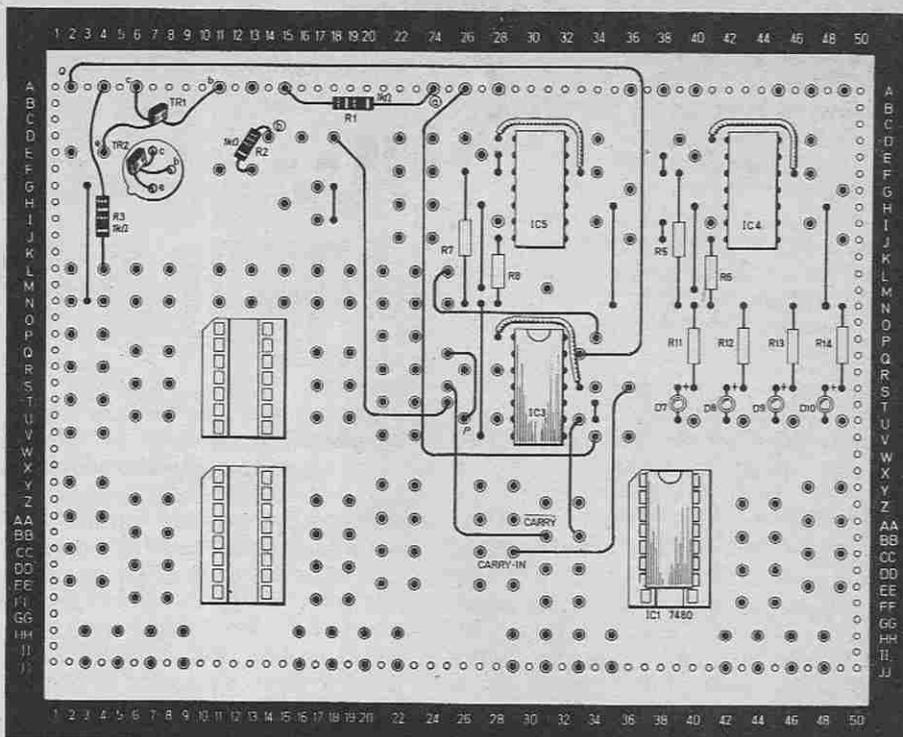


Fig. 11.8b. The circuit of Fig. 11.8a wired on the Test Bed.

The top left key is used, by soldering a wire link between N29 and I29, inserting a soldercon socket at R24 and cutting the strip at R28. Call this the COMPLEMENT key.

To add in the extra 1, we make the carry-in high at the first stage of addition. This can be done by grounding the CARRY output briefly when clock is high, just before the first count of the subtraction sequence. The top right-hand key (ADD ONE) can be used for this; the connection to ground is already wired in; solder a socket at R34 to connect to CARRY. The sequence for subtraction is as follows:

Load and shift XYZ, as in counts 1 to 4 of Fig. 11.7.

Just before count 5, press the ADD ONE key briefly, then press the number key for LMN.

After count 5, release the number key, but press COMPLEMENT key down for the rest of the sequence.

Press and hold SHIFT key as in Fig. 11.8.

The answer to the subtraction is found by reading the digits obtained after counts 5, 6, 7, and 8. the digit at count 9 is normally 1, and should be ignored when writing down the answer.

### Problem

What happens when you take 1001 from 1000, or 111 from 1? What does it mean when the digit at count 9 is 0?

To be continued


# BRIGHT IDEAS

## COMPONENT HOLDER

When constructing a circuit it is usual to have the components in front of you. I normally use plastic bags and small boxes. This has not really been suitable, due to the time involved sorting out the right component. I then decided to use a piece of foam plastic. The components, resistors, capacitors etc, are simply pushed in the foam.

Using this method I find it easier to pick out the required components. Also when they are accidentally knocked on to the floor, as with boxes the components go everywhere, but with foam they stay put.

L. Privett, Barking, Essex.

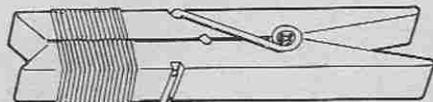


WIRE WRAPPED TIGHTLY AROUND EACH END.

## THIRD HAND HEATSINK

To allow a free hand when soldering I have developed a simple peg heatsink to protect components against excessive heat.

All that is necessary is two 200mm lengths of 1.5mm dia. copper wire and a wooden clothes peg, see diagram. The peg can easily be clipped onto the lead being soldered and will remain there without being handheld.

D. G. Taylor, Merseyside.

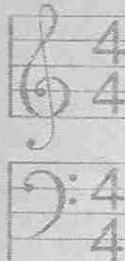

# ELECTRONIC TUNING FORK

**T**HIS DEVICE is primarily intended to permit quick and easy tuning of a guitar, but it has also been used successfully with a violin and could no doubt be employed with other musical instruments of this general type. Like an ordinary tuning fork the unit has an audible output against which the unit can be tuned by ear. Each of the six guitar notes can be selected by means of a front panel switch.

## BEAT NOTE

An additional and very useful feature of the unit is the ability to compare the frequency of the guitar with the internal reference oscillator, and produce an output note which is equal to the difference in the two frequencies,

normally termed the beat note. The beat note can be heard in the earphone as a sort of phasing effect due to the interaction between the two input signals. The note itself is usually too low to be audible as such.

A light emitting diode has therefore been incorporated in the unit, and this flashes on and off at a rate equal to the beat frequency. This gives a clear indication of the tuning error, and facilitates accurate and easy tuning merely by adjusting the guitar for the lowest attainable flashing rate. In this way it is very easy to bring the guitar to within 1Hz of the reference oscillator's frequency, which is far more accurate than most people can achieve by usual means.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the Electronic Tuning Fork is shown in Fig. 1.

With an acoustic guitar the input signal to the unit must be obtained via a microphone, but an electrical signal can obviously be taken direct from an electric instrument. In either case only

a fairly low signal level will be obtained, particularly in view of the fact that the output from a guitar quickly decays to only a small fraction of its initial peak level. This makes it necessary to considerably amplify the input signal to bring it up to a suitable level to drive the next stage of the unit.


This amplification is provided by TR1 and TR2, both of which are connected as high gain common emitter amplifiers. Less than 1mV. is needed at the input in order to drive TR2 beyond the clipping threshold. This is adequate to give good results if the unit is fed direct from an electric instrument, or driven from an acoustic guitar via a low impedance dynamic (cassette type) microphone. An electret microphone having an internal preamplifier should also be suitable, but a crystal type is unlikely to prove satisfactory due to the fairly low input impedance of the circuit.

## REFERENCE OSCILLATOR

The reference oscillator uses an NE555V device, IC1 in the astable mode. The six preset resistors, VR1

**COMPONENTS**  
 approximate  
 cost **£7.50**  
 excluding  
 microphone

Fig. 1. Complete circuit diagram of the Electronic Tuning Fork.

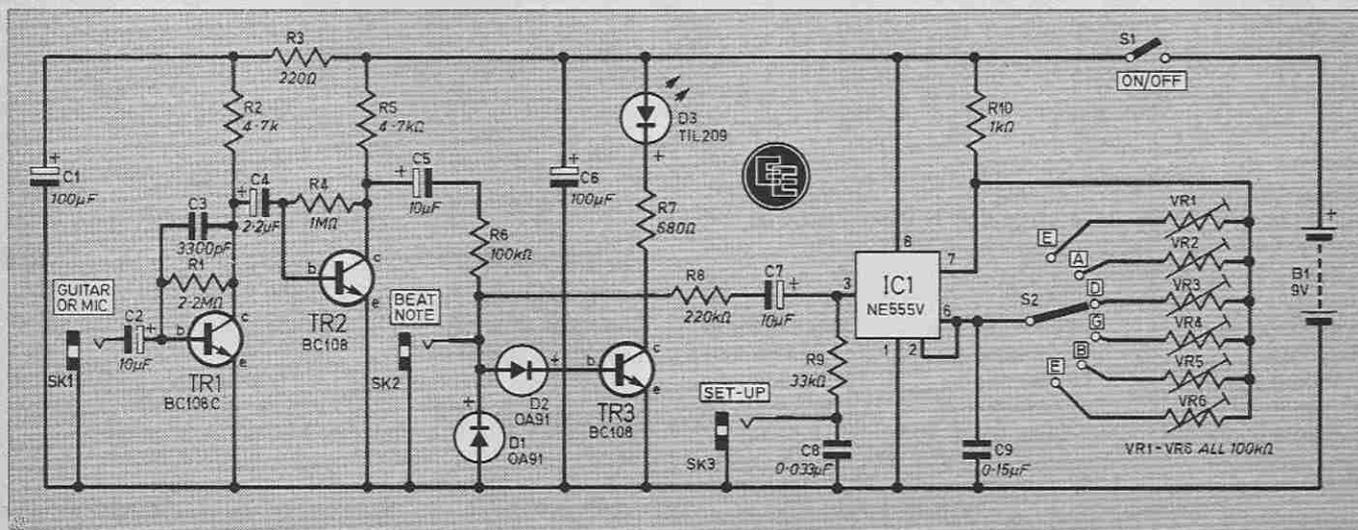



to VR6, are each tuned to a different open string guitar note, with the desired preset and note being selected using S2. A rough square-wave output is obtained at pin 3 of IC1, and this is fed to an earphone socket by way of a simple top cut filter comprised of R9 and C8. The purpose of the filtering is to attenuate the harmonics on the output which are otherwise excessive, and tend to drown the fundamental frequency.

Some of the output from IC1 is coupled by C7 to one input of a passive mixer formed by R8 and R6. The output of TR2 is coupled to the other input by C3.

## MIXING

If the two signals are at the same frequency the mixing will either result in the two signals adding together if they are in phase (if they rise and fall precisely in step and are of the same polarity), or cancelling one another out if they are out of phase (if they rise and fall in step but are of opposite polarity to one another). This results in either a rapid stream of pulses being fed to TR3 base via the rectifier circuit consisting of D1 and D2, or no signal at all being fed to TR3.

Transistor TR3 has l.e.d. indicator D3 and current limiting resistor R7 as its collector load, and the positive pulses to TR3 base will result in D3 glowing brightly. If the signals are out of phase and there is no input to TR3, D3 will switch off. The important thing is, that, the l.e.d. indicator remains in the same state and does not switch on and off. Of course, the two input signals may not be perfectly in or out of phase as has been assumed above, but may be somewhere in between these two extremes. This causes the two

signals to either partially add together or cancel one another out, producing an intermediate but steady level of illumination from D3.

## PHASE EFFECT

If the two input signals are at slightly different frequencies they will not have a fixed phase relationship, but will alternate between the in phase and out of phase states. This results in the signals first adding together and switching on D3, and then cancelling out and switching off D3. This happens continuously with D3 flashing on and off in consequence. The greater the difference in the

two input frequencies the quicker the changes in phase relationship, and the faster the flashing rate of D3. In fact D3 switches on and off at a rate equal to the difference in the two input frequencies.


The mixing process produces an audible phasing effect at the junction of R6 and R8, and this can be heard using a crystal earpiece plugged into SK2. Note that only a crystal earphone is suitable for use with this unit, and magnetic types are unsuitable.

On/off switching is provided by S1. The current consumption of the unit from a 9 volt supply is approximately 18mA, and this is provided by a PP6 size battery which gives many hours of operation.



Most of the components are assembled on a 0.1inch matrix stripboard which measures 13 copper strips by 37 holes. This


## HOW IT WORKS

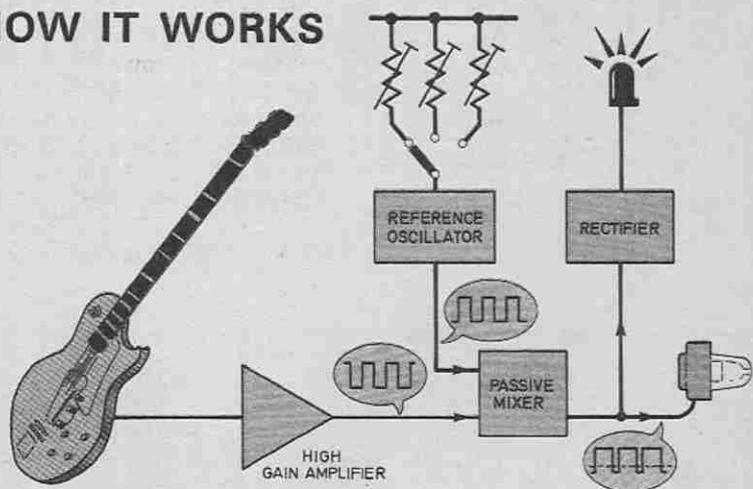


A note from either an acoustic or electric guitar is applied to a *high gain amplifier* which turns the very low input from the guitar into a much larger signal which is sufficient to be applied to one input of a *mixer*. The other input is connected to a stable *reference oscillator* having six switched frequencies which correspond to the six notes of a guitar.

The output from the *mixer* is equal to the difference between the two input frequencies. The guitar is then tuned for minimum output frequency (zero beat) so that it is brought to the same pitch as the reference oscillator. Both audible and visual indication is provided, the latter being useful for fine tuning.

# ELECTRONIC TUNING FORK

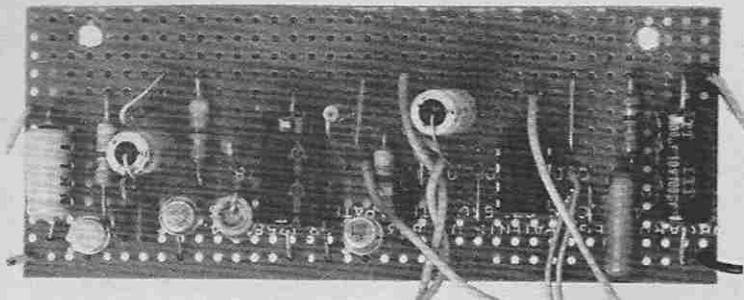

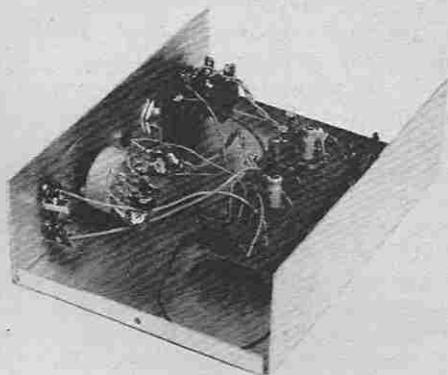The completed circuit board for the Electronic Tuning Fork.



The finished unit showing how the preset potentiometers are mounted on the tuning switch.

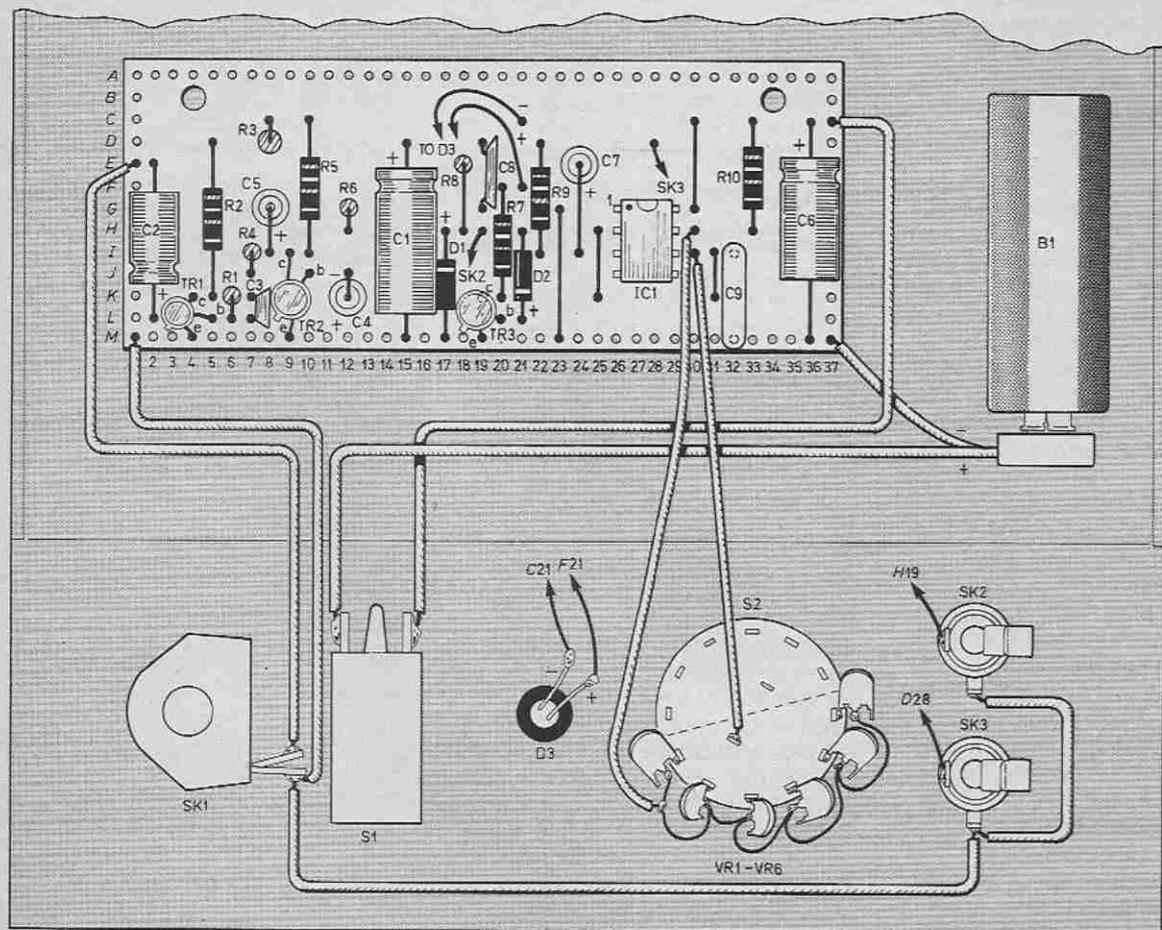
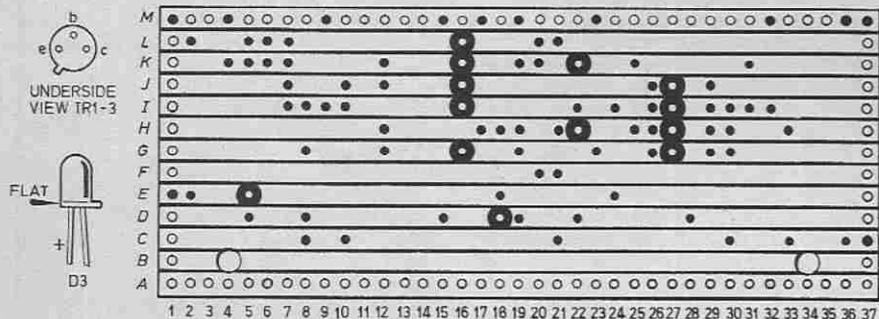


Fig. 2. Complete wiring details for the unit also showing the stripboard layout and breaks to be made. All the tuning presets are mounted on the switch to save space on the board. It is not necessary to use screened wire when wiring to the sockets, as the metal case provides sufficient screening.

must be cut down from a larger board using a hacksaw, and any rough edges are then filed smooth. Next the two 3.3mm diameter mounting holes and the breaks in the strips are made at the points indicated in the component panel layout diagram of Fig. 2.

The components are then soldered into place with the semiconductor devices being left until the end. D1 and D2 are germanium diodes, and these are more easily damaged by overheating than the other devices. Either a heatshunt should be used on each of their leadout wires as it is soldered into place, or the leads should be connected fairly swiftly so that there is no chance for the diodes to overheat. Be careful not to omit the four link wires around IC1.

## CASE

A metal instrument case having approximate outside dimensions of 152 x 120 x 51mm was used as the case for the prototype, and any similar case should provide a suitable housing. It is recommended that a metal case should be used as this will screen the sensitive amplifier circuitry from possible sources of electrical interference.

The general layout of the unit can be seen from the photographs, but is not critical and any sensible layout can be used.

Many low impedance dynamic microphones have a 2.5mm jack plug as well as the 3.5mm one which carries the output signal, and it is quite common for the two plugs to be contained in a single moulding. If a microphone of this type is to be used with the unit it will be necessary to mount a 2.5mm jack on the front panel to accommodate the unused 2.5mm plug. Alternatively an ordinary 3.5mm plug can be fitted to the microphone in place of the original.

In order to minimise the amount of wiring between the component panel and the controls, VR1 to VR6 are mounted on S2 rather than on the component panel. The component panel is mounted using 6BA screws about 12mm or so long, and spacers are used to ensure that the connections on the underside of the panel are kept well clear of the metal case.

The small amount of point to point wiring must be completed before the panel can finally be bolted into position.

## COMPONENTS

### Resistors

R1 2.2M $\Omega$	R6 100k $\Omega$
R2 4.7k $\Omega$	R7 680 $\Omega$
R3 220 $\Omega$	R8 220k $\Omega$
R4 1M $\Omega$	R9 33k $\Omega$
R5 4.7k $\Omega$	R10 1k $\Omega$

All  $\frac{1}{4}$ W carbon  $\pm 5\%$

### Potentiometers

VR1-6 100k $\Omega$  miniature vertical presets (6 off)

### Semiconductors

TR1 BC108C *npn* silicon  
 TR2 BC108 *npn* silicon  
 TR3 BC108 *npn* silicon  
 D1,2 OA91 germanium (2 off)  
 D3 TIL209 red light emitting diode  
 IC1 NE555V timer

### Miscellaneous

SK1  $\frac{1}{4}$  inch mono jack socket  
 SK2, 3 3.5mm jack socket (2 off)  
 S1 standard single pole toggle  
 S2 2-pole 6-way rotary switch (only one pole used)  
 B1 9V PP6 battery

Stripboard, 0.1 inch matrix 13 strips by 37 holes, metal case 152 x 120 x 51mm or similar; PP3 type battery connector for B1; small round control knob; mounting clip for D3; extra 2.5mm jack socket if required —see text; 8 pin i.c. socket if required; low impedance dynamic microphone (200 ohm cassette type); connecting wire; crystal earpiece with 3.5mm plug.

### Capacitors

C1 100 $\mu$ F 10V elect.  
 C2 10 $\mu$ F 10V elect.  
 C3 3300pF ceramic plate  
 C4 2.2 $\mu$ F 10V elect.  
 C5 10 $\mu$ F 10V elect.  
 C6 100 $\mu$ F 10V elect.  
 C7 10 $\mu$ F 10V elect.  
 C8 0.033 $\mu$ F ceramic plate  
 C9 0.15 $\mu$ F polyester

See  
**Shop  
 Talk**  
 page 499

## ADJUSTMENTS

Initially VR1 to VR6 should all be set for about half maximum resistance. With an earphone connected to SK3 and the unit switched on, a fairly low audio tone should be produced with S2 set to any of its positions. If this does not happen, switch off at once and check the wiring for errors.

The presets are adjusted by ear against a piano, pitch pipes, or other such source, to give the six open string notes of a guitar at the six settings of S2. This should obviously be done as accurately as possible. Once set, the unit should not need any readjustment for a considerable period of time as the reference oscillator is very stable, and is not, for instance, significantly affected by variations in the battery voltage.

## IN USE

In use, each guitar string must be brought fairly close to the correct pitch before D3 will flash on and off at a rate which is slow

enough to be perceived. The unit must therefore be used as a conventional tuning fork when making the initial adjustments to an instrument which is badly out of tune. With the earphone connected to SK2, an audible beat note will often be heard before the indicator light flashes at a slow enough rate to be perceived, but once the tuning is almost correct, the flashing light will probably give a clearer indication of the beat note.

It should be borne in mind that harmonics of the two input signals to the mixer can interact to produce beat notes even when the guitar is well off tune. However, this is not really too much of a problem as these spurious results only occur when the tuning is so far out that it should be obvious that it is an erroneous response.

Also, the flashing of D3 is far less pronounced at these secondary responses, with only minor fluctuations in its brightness occurring. At the main response it will vary from full brightness to no output whatever.  $\square$

# LETTERS

## Subjective Response

Having just read Adrian Hope's article (*For Your Entertainment*) in the June issue of *Everyday Electronics* I feel it necessary to reply to that part subtitled "Sound off".

Sound level meters measure sound pressure and not energy. These meters generally incorporate an "A" weighted network which closely relates to the subjective response of the normal human ear to sound. In the field of acoustics the "A" weighting is accepted as the best descriptor of human perception to sound.

The difference between subjective response to a shout and speech recorded at identical energy levels lies in the frequency content of the sounds rather than the energy output. Since the ear is sensitive to frequency changes these differences are readily noticeable.

A great deal of work has been done by persons such as Stevens, Zwicker and Beranek to establish equal loudness contours and their results are remarkably similar, from large but differing samples of people. Modern microtechnology has made the incorporation of these equal loudness contours into a sound level meter a real possibility although of limited use to the acoustician.

Finally, I should like to offer a possible solution to the mystery of the differing maximum frequency sensitivity between the sexes. In young children the threshold of audibility of 4kHz can be as low as -2dB. This alters with age and more important noise exposure. Men are generally subjected to greater noise exposure than women. This exposure leads to a shift in the maximum frequency sensitivity from around 4kHz to 3kHz or less. This shift is characteristic of noise induced hearing loss both temporary and permanent.

R. N. Lovett  
Dunstable

## Matter of "Sferics"

I find your *Counter Intelligence* articles very interesting and informative. In the May issue you query the usefulness of static electricity and I wonder if my memory of an article in the magazine "Scientific American" back about 1956 would be of help.

It was on the use of old radio material rewired to measure the "crackles" that in some cases was due to static and the suggestion for using the machine was to predict the nearness of lightning. If I can find the copy I will send it to you for passing on to Mr. Young, as I feel the task would be helped by your colleagues upgrading the apparatus to modern terms and it might even be of use.

I am hesitant about mentioning this as it was quite a time ago but I know most libraries can obtain this publication and its unusual in that it gives good scientific reports and practical schemes in esoteric fields. I mention this before saying

that the static should be measured in units called "sferics", but I think it really was a serious article (I once was told by a technical officer that they would make the apparatus if I got a research grant of about £50! I am afraid I never tried).

I hope this is of interest and you can make something of it as this might be the time when technology has the means to discover what static can be used for, rather than shocking us in our synthetic world.

D. S. Mayne,  
Armagh.

## Suitable definition

In reply to Mr. Young's question concerning static electricity (*Counter Intelligence*, May 1979 issue), first a suitable definition must be found; for this I have decided upon—an electric charge which is at rest—i.e., a charge which remains on an object without change.

This reveals the basic difference between static electricity and "... the ordinary sort..." since the latter must travel to produce an effect. Coincidentally this movement is due to attempts, by the electrons, to produce an equilibrium of potential, i.e. to become static electricity.

By definition static electricity is therefore unable to do anything useful except to attract and repel an electron beam, i.e. move the dot on an oscilloscope.

David R. Clarke (aged 15)  
Rugby.

## Static Charge

As regards to Mr. Young's query about static electricity (*Counter Intelligence*, May 1979 issue), I hope the following information might be useful.

As we all know, "electricity" is due to the fact that charged particles (electrons) move from one point to another, e.g. down a wire, their movement being caused by a difference in potential at the two ends of the wire. Now static electricity is due to the build up of charges on an object.

The charges that have built up do not "move" and so there is no current flow. If, however, the charges are allowed to leak away by contact with something at earth potential, there is an associated current, which is the result of the much lower potential to which charges tend to flow.

So, electricity is the flow of charge whereas static charge is the result of the build up of charge on an area; giving the same effects when they move as do electric currents due to a battery for example. However, in electrostatics we are usually dealing with a small charge (few micro-coulombs) and several kV; in current electricity the opposite is usually the case.

Well, what use is static charge? Today's modern technology has put electrostatics into some quite useful situations.

Coal-fired power stations, steel, cement and chemical industries use electrostatic precipitation in order to contain flue gas outputs which would otherwise be discharged into the atmosphere. The flue gases pass through some positively and some negatively charged grids. The gas particles pick up the charge from one of the grids and are thus attracted by the other, causing collection of the particles on the grids.

Electrostatic spraying of paints is possible; electrostatic loudspeakers and microphones are in common use as are electrostatic copying machines. In nuclear physics electrostatic generators are used to produce static which then generates several million volts and is used to accelerate atomic particles for research.

A knowledge of static electricity is also needed to combat situations where the static could produce disastrous results. Static charges build up on wings of aircraft in flight and on plastics in industry creating potential explosion hazards if not combated; lightning conductors are used to protect buildings.

Nearer home ground, static charges come into play when a capacitor is fully charged and no more charge flows from one plate to the other.

But as we can appreciate, most of the functions described need "current" electricity to produce the charged surface in the first place, but we can consider functions such as employed using Van de Graff generators (e.g. nuclear physics) as being static electricity on its own performing useful functions.


George Kesic  
Leeds

## Measuring A.C. Current

Many multimeters currently on the market do not have a high a.c. current range for measuring mains current for example. You can easily adapt a meter by using a simple bridge rectifier. The circuit is shown in the diagram. A full wave bridge, rated at about 5 amps is used, and a meter set to a d.c. current range which has a f.s.d. equal to the peak a.c. current to be measured.

As the meter will indicate only the peak value of the current, a shunt can be made up and connected across the meter so that it will indicate true r.m.s. instead of peak current.

R. H. Marco,  
London SW10

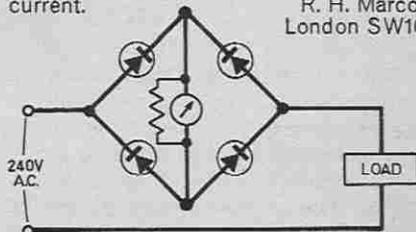

# BRIGHT IDEAS

## STORAGE

I have found a simple and cheap method of storing components. Components are placed into plastic bags of the press to seal variety about 150mm x 100mm. A hole is punched through the unused plastic above the seal in the centre. The bags are then hung on a length of string, fastened between any two points.


A simple hook is made from stiff wire 55mm long which provides an easy method of removal when required. A system of this kind I think compares favourably with commercial storage bins etc.

J. Fleming, London E7.

## CROCODILE CLIPS

Needing a few additional crocodile clips (when the shops were closed) I made up suitable alternatives, using just an ordinary clothes peg and thin insulated wire. The clothes pegs can be shaped to a point similar to that on pliers. The leads are then stripped for about 150mm and then wound round the ends as shown in the diagram.

S. Moss, Bath.

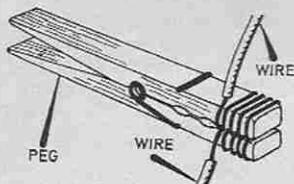


## COMPONENT BREADBOARDING

As a devoted electronics enthusiast, I construct projects purely for the fun of it. As such I very rarely keep the projects so constructed. Therefore I have found it wise to mount certain components on a board. A size of 25cm x 15cm seems about right.

The component, for example a speaker, is mounted on one side of the board, plywood for instance and nails driven through from the other side. When the component is to be used I just connect it up using crocodile clips.

A. White, Burbage, Leicestershire.

## TOOTHPASTE TERMINALS

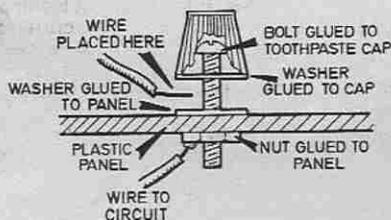

When constructing test equipment etc. the cost of terminals can be quite high, and is often cheaper for the constructor to make his own. My idea is to use an old toothpaste cap. The drawing above shows how this is made.

Thus the external wire can then be gripped firmly between the two washers when the terminal is screwed down.

P. Baily, Rutherglen, Scotland.



A psychedelic light show for discos, parties and pop groups. Has three modes of flashing—two chase patterns and a strobe effect. Total output power 750 watts per channel.

## VARICAP POCKET RECEIVER

A unique feature of this receiver is the unusual use of a varicap diode in tuning a ZN414 t.r.f. radio i.c.


## REFLEX LOUDSPEAKER

An advanced top quality system, incorporating three drive units in a 62 litre (3cu ft) enclosure. 50-70 watts handling capacity.

... and much, much more besides!

SEPTEMBER ISSUE ON SALE AUGUST 17

# THE VIDEO REVOLUTION

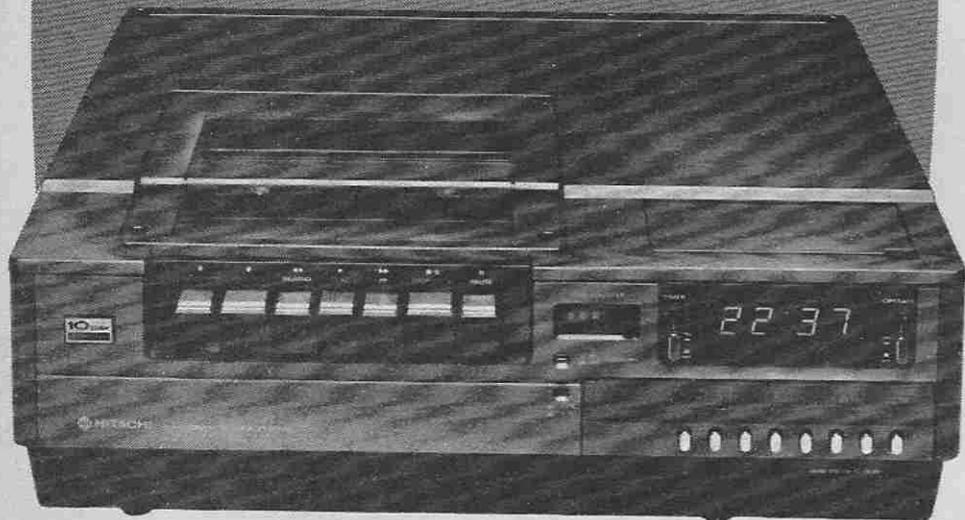

BY ADRIAN HOPE

**S**UDDENLY video is happening. There are two reasons why the long awaited video revolution has now finally arrived. Most people who can afford a hi fi system already have at least one and are "in the market" for another electronic gadget; and the new generation of video cassette recorders, which are now selling from a wide variety of UK shops, offer greatly increased playing time and drastically reduced "feeding" cost.

This latter phrase neatly sums up the cost in blank cassette tape of using a video recorder.

Until a year or so ago feeding costs were high enough to be a marked deterrent for all but the very well-heeled. Now they are at a very low level, £5.00 an hour or less.

## FIRST GENERATION

The first generation of domestic video recorders (the N1500 series)

came from Philips of Eindhoven in 1974, the result of research and development work carried out by a Philips team in Austria.

It costs around £25 an hour to record television programmes off-air using one of the original N1500 series Philips video recorders. This was fine if you re-used the same cassette over and over again but not so fine if you wished to store a programme. Also the cassette had a maximum playing time of one hour.


Everyone recognised that tape cost must be reduced and playing time per cassette increased. The break-through came from Japan with announcement by JVC of the VHS system and by Sony of Betamax. Although VHS and Betamax are very similar they are not the same and are not compatible, that is to say a cassette recorded on the VHS machine will not replay on a Betamax machine and vice-versa.

## LONGER PLAY

Both VHS and Betamax machines are now available in the UK and both have in common a much increased playing time, around three hours per cassette, and a greatly reduced feeding cost, less than £5.00 an hour. This is achieved by a very low tape speed which enables a lengthy recording to be made on a relatively short tape.

In response to the Japanese competition, Philips launched a Long Play version of their original N1500 series machines, the N1700 series. Grundig then launched SVR a Super Long Play version of the long-play Philips format. It is only necessary to compare tape speeds over the years to get some idea of the astonishing rate at which video technology has moved. All domestic machines use tape which is  $\frac{1}{2}$  inch wide.

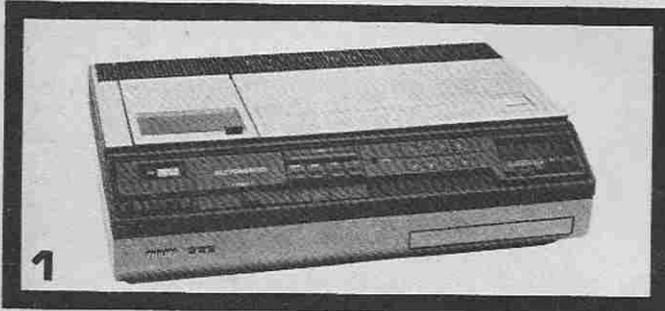
The original Philips N1500 recorders ran the tape past the recording heads at 14.29cm per second. To enable the tape to hold a bandwidth of 3MHz (which is necessary for recording colour television) the recording heads spin round very rapidly indeed laying a series of



1



3

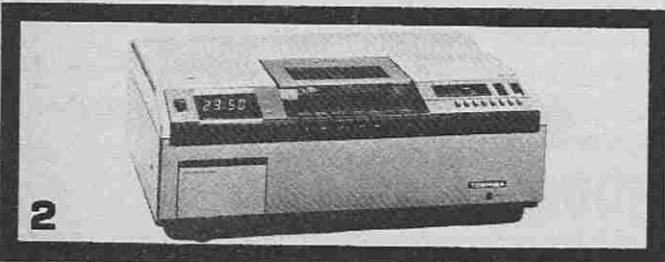

2

1—Philips N1702 video recorder (VRC).

2—Toshiba Betavideo V5250B (Beta).

3—Ferguson Videostar 3V00 (VHS).

closely packed helical strips across the slowly moving tape. Hence the term "helical scan recorder".

All domestic video recorders work on the helical scan principle, the heads rotating up to 20 miles an hour to "write" the necessary video information onto the tape.

## TAPE SPEED

The Philips Long Play video cassette recorder (N1700) uses the same video cassettes as the original N1500 but the tape speed is reduced to 6.56cm per second. But even this is a much higher tape speed than the two Japanese systems and the German Grundig modification.

The VHS system as marketed in this country for instance by JVC, Akai and Ferguson (most VHS machines are actually made by JVC) relies on the almost unbelievably low tape speed of 2.34cm per second.

Think about that figure: 3MHz bandwidth on half-inch wide tape moving at 2.3cm per second. Just a few years ago anyone who dared to suggest that this might be possible would have been publicly mocked.

But Betamax recorders suitable for use in the UK run at an even lower tape speed—just 1.9cm per second. And in an "anything you can do we can do slower" confrontation the Beta and VHS designers in Japan have recently announced even slower tape speeds to offer up to nine hours recording from a single cassette.

Initially Philips also responded to the commercial challenge of lower feeding costs from Japan by slashing the price of blank cassettes by as much as 40 per cent. Although the price of Philips format blank cassettes in the shops varies widely, depending on where you shop, it is now possible to buy a Philips format LVC 150 that runs for 2½ hours on an N1700 machine for as little as £15.00.

## PRICE CUTTING

But video cassettes are expensive to make and price cuts such as these

must have left the tape manufacturers with a very tight profit margin.

Usually firms tend to sell hardware (such as cameras and recorders) cheaply and then make their money on the software (blank tape and raw film). Doubtless this is one reason why Grundig chose the different approach of launching SVR. This uses what at first appears to be a standard Philips format video cassette and a tape running speed of 3.95cm per second. (ITT incidentally are selling the German-made Grundig SVR recorder under their own name.)

Although the SVR machine appears to take standard Philips-format cassettes it is in fact designed to take only Philips-format cassettes which have been modified by the addition of a special lug. Grundig say that the very low tape speed on which the machine relies necessitates the use of especially good tape and precision cassette construction and that Philips format cassettes with the extra lug and labelled SVC can be relied on in this respect.

Inevitably this has created some confusion in the shops. Also it initially created some pretty bad will because the price of special lugged Philips-format SVC video cassettes was at first higher than the cost of apparently, but not actually, identical Philips-format cassettes without lug. Now the situation has improved because some tape firms, like BASF, are simply selling only SVC lugged Philips-format video cassettes which can be used on either Philips N1700 series or Grundig SVR machines.

## FIVE STANDARDS

But the trade and public is still confronted with a choice between five video standards—two generations of the Philips-format, the Grundig modification of the Philips-format plus VHS plus Betamax. And that is by no means all. At the Berlin Radio Show in August it is almost certain that some new formats will be launched.

It is almost certain, for instance, that BASF will introduce its Linear

Video Recording System. In LVR a length of tape shuttles very fast backwards and forwards past a fixed recording head which switches position at each pass of the tape, rather like the heads of a car cartridge player.

Moreover, although Grundig's new video factory in Nuremberg is producing 500 SVR machines a day, and although Philips has launched the N1702, a slightly improved version of the basic Long Play N1700, it is expected that Philips and Grundig will very soon make a joint announcement about their future plans for a new format.

Meanwhile the overall uncertainty caused by such rumours has created a drastic fall in video recorder prices. You can now buy a brand new machine for under £500, instead of the £700 or £800 it cost just a few months ago.



## VIDEO DISCS

As explained, a helical scan video tape recorder captures the wide bandwidth colour television signal (around 3MHz) by spinning the record heads fast past slowly moving tape. A video disc player adopts a more obvious approach, although the technology involved is equally daunting. All video discs systems, and many have been proposed, work by spinning the disc very fast under a stationary pick-up head.

The first video disc was made by John Logie Baird in 1928 who used an old, ordinary 78r.p.m. disc to capture the low bandwidth signals necessary to generate a muzzy picture on his mechanical TV system. Some discs were actually sold for seven shillings each at Selfridges in the mid 1930's. Video discs then virtually died for forty years.
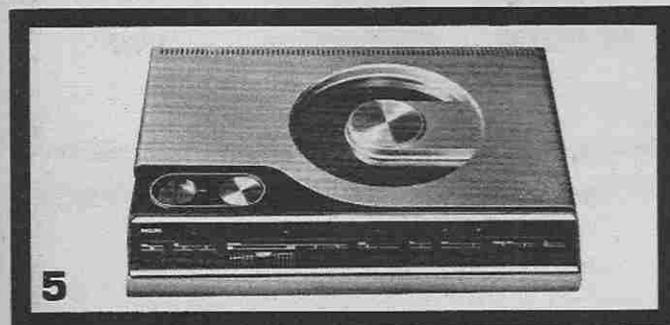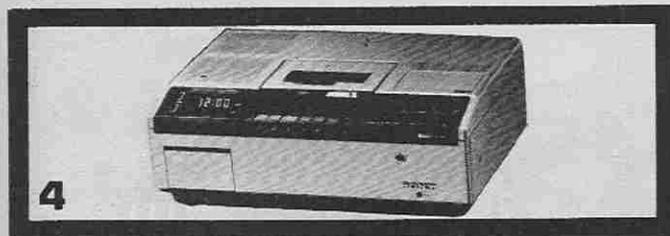
## INSTANT REPLAY TV

Many television companies now use a computer-style magnetic disc which rotates very fast to capture short TV picture sequences. This is how freeze-



4—Sony Betamax (Beta).

5—An early Philips/MCA videodisc player.

6—The Philips Compact Disc player.

frame and instant replay pictures are presented on TV. The transmitted signal is continually recorded onto the magnetic video disc. The disc has around half-a-minute recording ability. Thus at any moment the broadcaster can instantly replay up to half a minute of the programme just transmitted, slowing down or speeding up or freezing the picture, for instance to highlight a goal in a football match.

### A SERIOUS LIMITATION

On the domestic market many systems have been developed but none yet commercially marketed in the UK. All systems so far are for replay, that is, they do not enable the user to make recordings of his own. This is one reason why video discs have not yet succeeded commercially.

No one yet seems quite sure what kind of material the public will be prepared to buy on a pre-recorded video disc. After all, very few television programmes or feature films bear watching once, let alone several times! And there is an unsolved problem over royalties for the performers.

### TELDEC SYSTEM

The first domestic video disc system to be announced was the Teledec system developed by Telefunken (of Germany) and Decca. The Teldec system was first publicly shown in Berlin in 1971 and by 1975 Teldec discs and players were actually being sold in some Continental countries.

A Teldec disc is not really a disc at all. It is a thin flexible sheet of plastics foil with the video information encoded in a spiral groove superficially similar to that of an ordinary gramophone record. But the video information is encoded by frequency modulation and the groove is cut in vertical or hill and dale fashion.

The Teldec disc rotates at 1,500-r.p.m. and is tracked by a special diamond stylus and piezo transducer. Each disc holds up to ten minutes of colour video. But the system has never succeeded commercially or met with much enthusiasm from engineers.

### RCA DISC SYSTEM

RCA in the USA has meanwhile developed a video disc with a groove in which the video information is encoded as capacitance variations. These are sensed by a pick-up serving as an electrode. Very few people have seen the RCA system in action and no one seems to know when or whether it will ever be launched. But recently when I was in New York I was given a very professional demonstration of the newest prototype RCA player, which is mechanically very simple and performed well.

### OPTICAL SYSTEMS

Most people still regard the optical system developed by Philips in Europe and MCA in the States (with a similar system independently developed by Thomson in France and Sony in Japan) as the front-runner.

According to the Philips system the video information is encoded as variations in reflection on the surface of a rapidly rotating shiny disc. A tiny laser beams a narrow pencil of light down onto the surface where minute pits vary the strength of the beam reflected up again onto a sensor. (The French Thomson system uses a transparent disc with variation in light transmission.)

For several years Philips and MCA annually promised to launch their system "next year" but it never quite seemed to happen. But just before Christmas 1978 the Philips subsidiary Magnovox started marketing Philips disc players and discs in Atlanta Georgia and the company demonstrated the system in the UK.

Performance of the Philips player is beyond reproach; the reproduced pictures are of broadcast standard.

### VISC SYSTEM

The Japanese company Matsushita have developed the Visc system which is in many respects a modern version of Teldec. Visc looks like an ordinary vinyl audio disc. In fact it is an ordinary vinyl disc except that the

groove is of very fine pitch and (like Teldec) contains video information of around 3MHz bandwidth recorded as frequency modulation in hill and dale fashion. But whereas Teldec only provides 10 minutes of colour video on one side of the flimsy foil disc, a Visc can carry over an hour of colour video and stereo sound on each side.



Visc was first demonstrated in 1978 and has subsequently been modified to squeeze longer playing time from smaller disc sizes. But now the future of Visc is in doubt because Matsushita has signed a deal with the sister company JVC, who had developed a completely different system. This relies on capacitance, like the RCA disc, but has no grooves. The electrode stylus tracks across the smooth disc surface under electronic servo control.

Although Sony is "flexible" over standardisation the company has so far shown most enthusiasm for an optical system, like the Philips disc. Other Japanese companies, including Pioneer, have made similar moves. So it seems likely that in the future the main battle will be between Sony, Philips, Pioneer and a few others on the one hand and Matsushita and JVC on the other, with RCA in the middle.
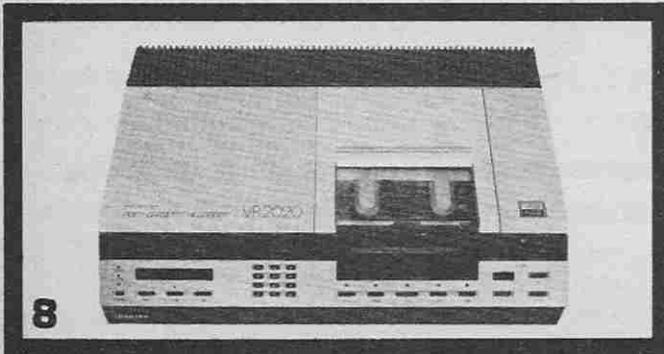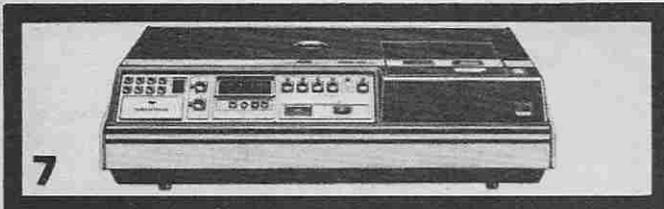
### FUTURE SYSTEMS

It remains to be seen now what further video disc systems are launched by other companies prompted into disclosing their researches by the USA marketing moves by Philips. Companies like RCA and JVC will not lightly ditch their own systems in favour of that of a rival. But while there is rivalry and no standardisation, no system will succeed. There is even the added problem that video discs tailored for the USA or Japan will be incompatible with European TV.

Although video discs may seem an irrelevancy to anyone who has no desire to buy a pre-recorded TV programme or feature film, they do have massive potential for education. Also they happen, by a happy coincidence, to be the ideal medium on which to record digital sound.



7—Grundig SVR4004 with 10 day timer (SVR).  
8—Latest Philips VR2020 uses paper-back size cassettes.  
9—Hitachi VKC500 colour video camera for use with the VT5000E 10 day recorder shown in our heading pic.



By Dave Barrington

**T**HIS month we have some new products which should be of particular interest to the constructor and should prove useful acquisitions.

### PCB Etcher


For the person keen on making his own printed circuit boards, a new bubble etcher aimed at both the hobbyist and professional has just been marketed by Mega Electronics.

Designated the type PLBE-1210 bubble etcher this new p.c. production ancillary has a fluid capacity of 5 litres, and accepts printed circuit boards up to 305 x 254mm. Extra capacity in the tank has been achieved by positioning the heating element so that it does not protrude into the tank.

The average etching time for both single-sided and double-sided boards is claimed to be 4 to 5 minutes. Other features include full thermostatic control of the fluid temperature and protection against evaporation and splashing.

The PLBE-1210 bubble etcher is priced at £55 including VAT and further details can be obtained from

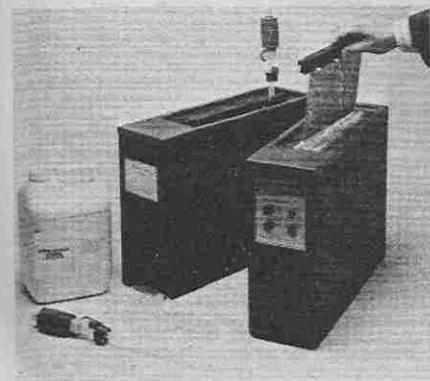The PLBE-1210 bubble etcher from Mega Electronics.



Mega Electronics Ltd., Dept EE, 9 Radwinter Road, Saffron Walden, Essex, CB11 3HU.


### Mini Stripper

Anyone who has tried stripping and using the very fine gauge wire now commonly used for interwiring multipin devices will welcome the latest offering from OK Machine & Tool (UK) Ltd.

The CAS-130 "Clip and Strip" is claimed to cut and strip without nicking 0.025mm wire and is ideal for Kynar wire-wrapping wire. Shaped similar to a miniature paper fastener, the stripper is held between thumb and finger and the wire placed in the jaws which are squeezed together to clip and strip a 25mm length of wire.

Produced primarily for the hobby market and selling for £1.52 (excluding packaging and VAT), the CAS-130 wire stripper could prove equally useful for the prototype wireman in industry.

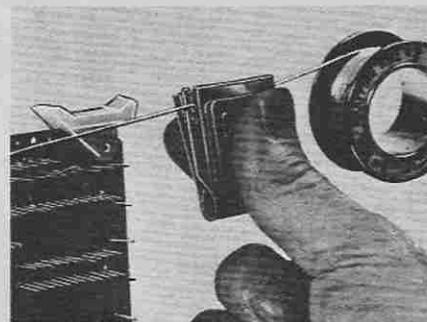Further information and addresses of nearest stockists can be obtained from OK Machine & Tool (UK) Ltd., Dept EE, 48a The Avenue, Southampton, Hants, SO1 2SY.



The OK CAS-130 wire stripper.

## CONSTRUCTIONAL PROJECTS

Although we have a bumper number of constructional projects this month no buying problems are envisaged as components are available from a number of sources.

### Trailer Flasher Unit

It is most important that first grade components are used for the *Trailer Flasher* project, the 2N3055 transistors must be new types. Also particular care must be taken when mounting the mica washer to ensure it is not punctured during mounting.

This is usually caused by insufficient cleaning of the metal work after drilling to accept the power transistors. When the drilling is completed for the power transistors it is a good idea to clean the surface with a damp rag and some household cleaning powder to remove any surplus swarf.


### 9V Power Supply

Any transformer with a 12V at 0.5A secondary will be suitable for the *9V Power Supply*. The only limitation is the physical size of the component and the one used in our prototype used two secondaries of 12V at 250mA wired in parallel.
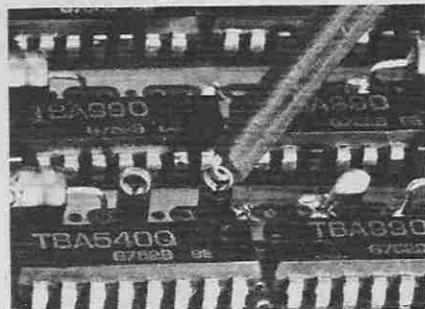
### Mini Module

Although this month's *Mini Module, Swanee Whistler* calls for a slider type potentiometer there is no reason why a normal rotary potentiometer should not be used. These are approximately 50 per cent cheaper and more likely to be to hand in the spares box.

Apart from the above comments, readers should have no difficulty in obtaining components for the rest of our projects this month as they are listed in most advertisers catalogues.



Miniature terminal assemblies from Vero Electronics.

### Terminal Posts

Designed as terminal posts for test points on circuit boards for clipping test probes such as multimeter or oscilloscope leads, we are sure readers will find many applications for the new terminal assemblies from Vero Electronics.

The sprung metal "split" pin is surrounded by a sintered glass bead which allows the eye of the pin to stand proud from the board for easy access and will remain in place when the board is reversed for soldering.

Intended for "through-hole-plated" printed circuit boards, we found that the terminals made ideal mounting posts for components on 0.15in plain perforated board. The interwiring is easily soldered on the underside of the board between the protruding pins.

Details of prices and nearest stockists can be obtained from Vero Electronics Ltd., Dept EE, Industrial Estate, Chandler's Ford, Eastleigh, Hants, SO5 3ZR.

## VAT

Due to recent change of VAT rates at time of going to press, readers are advised to check prices in advertisements before ordering any components.

# TRAILER FLASHER

CAMPING and caravanning have enjoyed a considerable growth in popularity in recent years and many D.I.Y. motorists will be tackling the job of wiring up a trailer socket so as to connect the motor car lighting circuits to a trailer or caravan. In the case of the tail lights and brake lights these are usually straightforward d.c. connections. However complications arise in the connection of the flashing indicator lights.

## OPERATING FREQUENCY

Nearly all car flasher systems are affected by the number of bulbs in circuit, and connecting extra lamps will usually upset the flasher frequency, often causing the lights to flash much too fast, or, perhaps, not at all.

To be legally correct the flasher system must operate between 60 and 120 times per minute, and also, when the trailer is connected,

there must be some means of indicating the failure of the trailer flasher lamps to the driver.

The purpose of the unit described here is to drive the trailer flashers correctly and to monitor their operation.

## CIRCUIT PRINCIPAL

Fig. 1 is a simple illustration of the basic circuit. A 21 watt flasher bulb (LP2) has a much lower resistance than a 2 watt panel lamp (LP1), so that if the two are connected in series as shown and connected across a 12 volt car battery nearly all the 12 volts appears across LP1. LP1 lights up therefore, there being insufficient voltage across LP2 to illuminate it. LP1 remains lit as long as the filament of LP2 is intact, and therefore acts as a monitor.

If switch S1 is now closed LP1 is shorted out and the full 12 volts appears across LP2, causing it to

light. If S1 is made to operate in unison with the car flasher system then both LP1 and LP2 would flash, alternatively but at the correct speed.

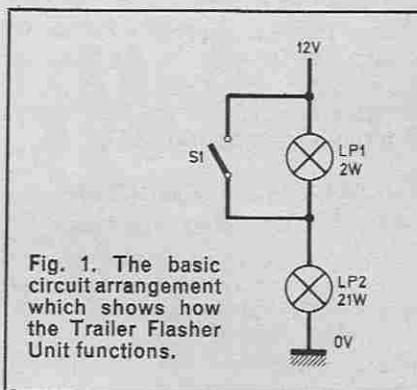


Fig. 1. The basic circuit arrangement which shows how the Trailer Flasher Unit functions.

## FULL CIRCUIT

Fig. 2 shows the full circuit of the trailer flasher unit connected to the motor car circuits. The dotted line encloses the additional components comprising the unit.

It will be seen that a 12 volt feed, via a 4 amp fuse FS1, supplies two parallel circuits—one for each trailer lamp. The panel lamp LP1 is in series with the trailer right rear lamp via the 7-pin trailer socket, likewise LP2 is in series with the trailer left rear lamp.


## SWITCHING

Instead of mechanical switches two *npn* power transistors are connected across the panel lamp, with their emitters connected to the trailer lamps. Each transistor base is connected via a 10 ohm 1 watt resistor and series diode to the left and right flasher feeds from the car direction indicator switch. When the flashers are not working there are no base voltages for the transistors and they are therefore virtually open circuit. This means that the panel lamps remain lit, showing that the trailer lamps are intact.

If S1 is moved, say, to the right, the right hand flasher lamps are energised via the car flasher unit, which causes them to flash as usual. 12 volt pulses are fed via D1 and R1 to the base of TR1,



# UNIT

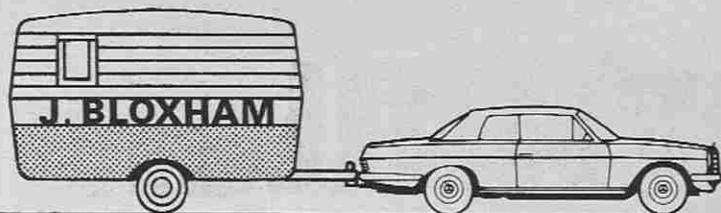

causing it to turn hard on, shorting out LP1 and switching on LP3. Thus both LP1 and LP3 flash (alternately) in time with the car circuit, which only has to provide a few milliamps base current for TR1—a negligible loading. Virtually all the current for LP3 comes via FS1 and TR1. A similar sequence occurs when S1 is moved to the left, to operate LP4.

## CONSTANT REMINDER

It will be seen that when the trailer plug is disconnected from the socket there is no connection to chassis and the unit is effectively switched off. Inserting the trailer plug completes the circuits and causes both panel lamps to come on—providing the trailer lamps are intact of course. The twin lights give a constant reminder that the trailer is connected—some small camping trailers are invisible through the driving mirror!

The base resistors R1, R2 are of a low value (10 ohms) to give some limit to the base current yet ensure that the transistors turn fully

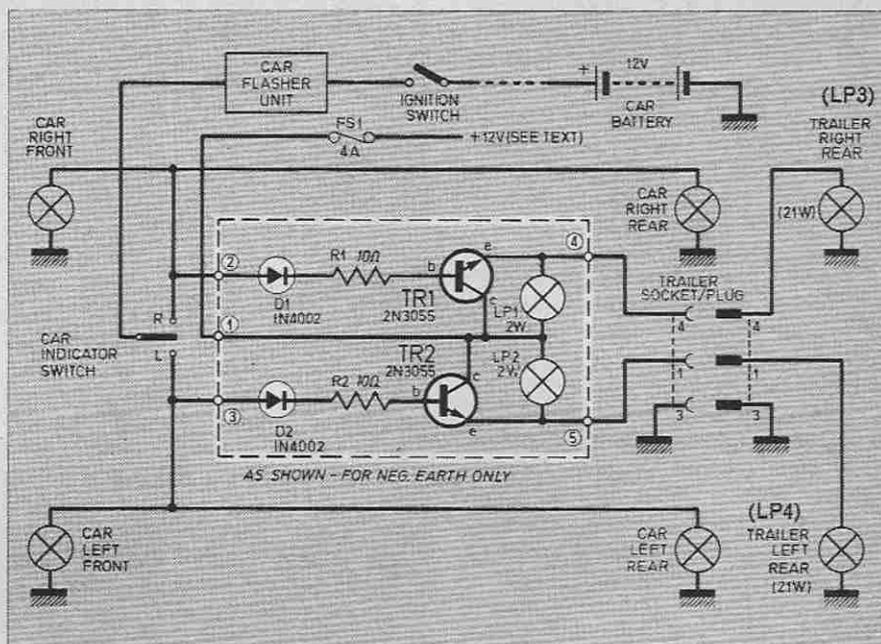


Fig. 2. Full circuit diagram of the Trailer Flasher Unit (within broken line) shown connected to the car circuits and, via trailer socket, to the trailer or caravan circuits. For positive earth TR1 and TR2 must be replaced by *pnp* types.

on. The diodes D1, D2 have no effect on circuit operation, but they were found necessary in the prototype to prevent reverse leakage through the base/emitter junctions of TR1 and TR2. This caused LP1 and LP2 to glow slightly when the trailer plug was disconnected.

The circuit shown is for negative earth vehicles. For positive earth operation the transistors must be *pnp* types and the diodes D1, D2 reversed.

## COMPONENTS

Almost any type of power transistors may be used, providing they have a current rating of at least two amps, and some suitable types are shown in the components list. Nondescript surplus transistors should not be used. One should bear in mind that the failure of a cheap transistor when on the road might bring all sorts of unpleasant consequences.

The 2 watt panel lamps are standard plastic types which are usually a push fit into a 12.5mm hole. These are readily available from motor shops and will

probably have spade-type push-on terminals, to which connecting wires may be soldered directly. It is important that the lamps are isolated from their mountings if they are to be fixed into a metal panel.

The five-way terminal strip is cut from a mains connector block as sold in Woolworths.

The wiring of the unit and its connections to the car circuits should be of reasonably stout insulated wire. Motor shops do sell proper automobile type connecting wire, but wire stripped from 13 amp mains cable is just as good and somewhat cheaper. The four amp fuse FS1 should be mounted in an in-line fuseholder as used for car radios.

**COMPONENTS**  
approximate  
cost £2.80

## COMPONENTS

### Resistors

- R1 10 $\Omega$
- R2 10 $\Omega$
- All 1W carbon  $\pm 10\%$

### Diodes

- D1 1N4002
- D2 1N4002

See  
**Shop  
Talk**  
page 499

### Transistors

- TR1, TR2
- NEG. EARTH
- 2N3055, 2N3054,
- AD2161, BD130,
- TIP33A etc.

- POS. EARTH
- AD162, AD143,
- AD149, BD132
- OC36 etc.

### Miscellaneous

- FS1 4 amp fuse.
- LP1,2 12.5mm plastic panel lamp 12V 2W (2 off)
- Five-way terminal strip.
- Fuseholder. "Scotch-loc" connectors.
- Sheet aluminium.

# CONSTRUCTION starts here

The constructional layout is not important and will depend to a great extent on the layout of the motor car and the materials to hand. The panel lamps may be mounted in the dashboard proper, if space permits, and remotely connected to the other components which may be mounted anywhere convenient.

The transistors do not really need heatsinking in this application as they are being operated as switches, that means fully on or fully off, and so generate little heat. However, it is by far the simplest method to bolt up the transistors in the normal way, one arrangement is shown in Fig. 3.

## CHASSIS

Here the complete unit is built on a simple chassis made up from aluminium sheet about 60mm x 180mm, and is intended to be mounted under the dashboard or parcel shelf. The panel should be drilled before being folded up. No

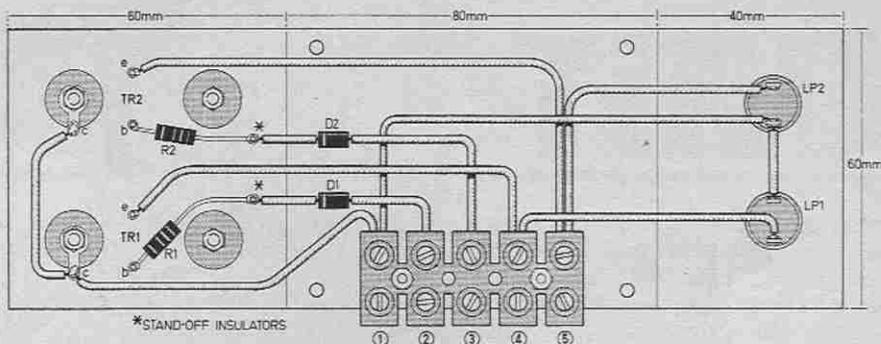


Fig. 3. The complete Flasher Unit shown "opened up" for clarity. The chassis is made from a single piece of 18 or 20 s.w.g. aluminium, with two bends as indicated. All drilling should be carried out before bending. See text for further details.

dimensions are given as these will vary with the devices used. The transistors must be isolated from the metal panel with the usual mica washer which may, with care, be used as a template for making the holes.

Fig. 3 shows the wiring connections with the chassis opened out for clarity but in fact the connections should be fairly short and rigid. When connecting wires into the terminal block ensure that the screws bite firmly onto the wire and not the insulation. Plastic sleeving should be used on any bare component leads.

## INSTALLATION

The unit may be mounted under the dashboard or parcel shelf with

PIN	CIRCUIT
1	L.H. FLASHER
2	SPARE
3	EARTH (CHASSIS)
4	R.H. FLASHER
5	R.H. REAR AND NUMBER PLATE
6	BRAKE LIGHTS
7	L.H. REAR

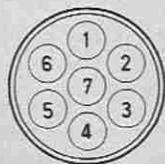


Fig. 4. Pin connections to Trailer Socket. The pin numbers are usually marked on the socket.

small bolts or self-tapping screws, using spacers if necessary. Wires may then be run from the car circuits to the terminal block. The five numbered terminals in Fig. 3 correspond with the circled numbers in Fig. 2.


Connections 2 and 3 are probably best made to the wiring loom alongside the steering column. The car wiring diagram will show the correct wires to tap into if the connections to the indicator switch are not visible.

Sound insulated connections are required and the simplest method is to use "Scotchloc" connectors, also available from motor shops.


The two wires to the trailer socket from the unit should be tucked out of the way under the carpet or behind the trim, taking care that they are not likely to chafe on sharp metal edges. Fig. 4 shows the internationally agreed pin connections for the trailer socket and it should be wired accordingly.
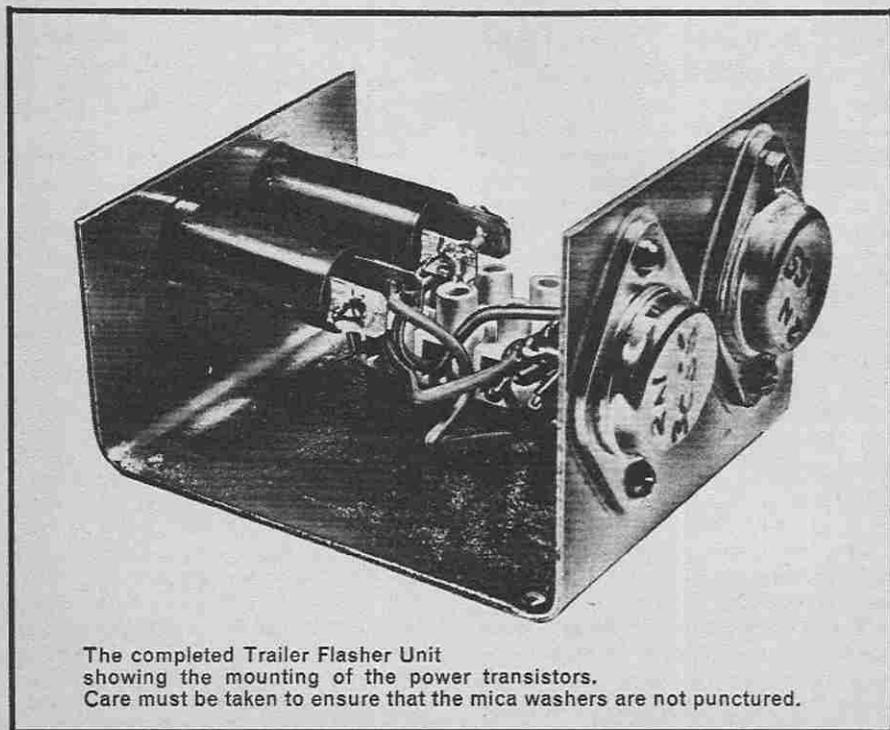
## HAZARD SYSTEM

The 12 volt feed via FS1 should be connected to the car fuse box, or perhaps to the ignition switch directly, so that the supply is live only when the ignition is turned on. If there is a spare fuse position in the fuse box it may be used instead of an in-line fuse holder.



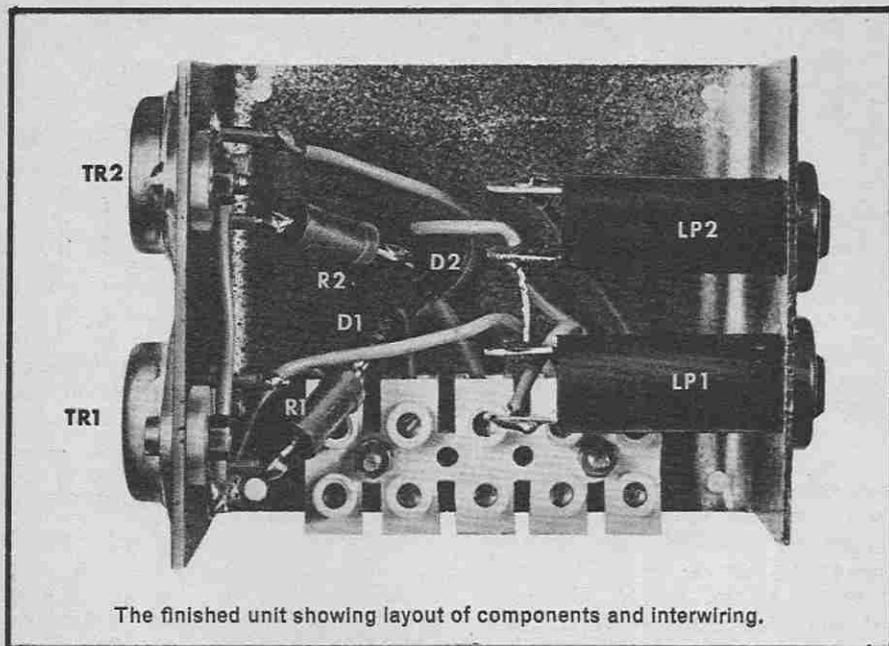The completed Trailer Flasher Unit showing the mounting of the power transistors. Care must be taken to ensure that the mica washers are not punctured.



The finished unit showing layout of components and interwiring.

The reason for this arrangement is that most modern cars are fitted with a "hazard" flasher system which causes all four flashers to light, to give warning of a breakdown etc. If the trailer is connected and the Trailer Flasher Unit in use this would cause both trailer lamps to flash as well—a useful feature.

However, six flasher bulbs means a load in excess of 120 watts, which could drain the car battery if left on for a lengthy period. Providing the engine is kept running, and therefore the charging system working, there is not likely to be any difficulty.

If the unit is wired to an ignition-controlled source as described, then switching off the engine will extinguish the trailer lamps and limit the hazard system load to the four lamps on the car. ☐



do not deal with it, but I will get my colleague who does to contact you".

The very next morning a parcel arrived in the post containing one P10 charger and to date I have had no bill! With all the tales one hears of poor service, it is nice to discover there is another side to the coin!

### Static reply

I was pleased to receive letters from readers on my static query. In particular I would like to thank David Mayne, David Clarke and George Kesic for their helpful suggestions and I would ask them to accept my apologies for not sending individual replies. I can honestly claim pressure of business. Some of these letters are reproduced in this issue.

If I sum up the answers correctly the consensus is that static and ordinary electricity are basically the same thing, but with static we are dealing with a very high voltage and very low current and with the more familiar sort, the voltages are usually lower and the current correspondingly higher.

Readers also reminded me of the innumerable uses to which static is put, from moving the spot on your television screen, to photocopying and even the plating of plastics. One even mentioned the uses to which the piezo electric phenomena is put, but I have the feeling that this is something different again.

Of course, what I had in my mind was static being used to power some kind of electric motor, perhaps with enough urge to drive a car! That really would be something. Here is a chance for you inventors!

### Electronic wizards

I am sure that one of these days some of my readers are going to tick me off for my predilection for poking fun at computers. The truth is, I think, we all have a certain animosity towards these electronic wizards and I believe the reason for it is this, we feel that they are getting too smart for us.

They can beat us at any game from noughts and crosses to chess, solve arithmetical problems that are far beyond our mental capacity and there are now pocket translators that can handle any language including Japanese. In short they tend to give us a massive inferiority complex.

Consequently when one falls flat on its nose (perhaps they do not have noses, so perhaps I had better rephrase it and say falls flat on its software) our mirth is not only uncontrollable but understandable because it has re-established our self esteem. What we must never lose sight of is the fact it was the human brain that conceived and built the computer in the first place.

To redress the balance I will say something in their favour. About seven years ago we bought an electronic calculator, that would do any calculation and give a print-out. It was a splendid machine but it measured about eighteen inches by eighteen inches by six inches and weighed about forty pounds. To-day we have replaced it with a Cannon P10 which does the same job, only measures about four inches by six inches by three inches and weighs a few ounces. It is completely portable and operates from a rechargeable cell.

### Poste Haste

In this connection I would like to give a pat on the back to the suppliers "Poste Haste". Every calculator is supplied complete with a charger, so when one of my staff said "We want some new batteries in the P10" looking very superior I said "not at all, you simply plug in the charger; here, let me show you." Do you think I could find the charger? I could not!

So I telephoned "Poste Haste" and explained my predicament. The girl who answered the phone said "I

# SQUARE one

## FOR BEGINNERS

lead composition.

### STAGE 2

Tinning the bit. The tip is "tinned" with a thin coat of solder. Do not allow the solder to run down the main body of the bit.

### STAGE 3

An essential part of soldering is clean components. Use a piece of fine sandpaper and then tin the lead.

### STAGE 4

A tidy looking board is a pleasure to see, so don't insert components as on the right! Be neat.

### STAGE 5

The joint is now ready to be soldered. This shows the correct position of iron. Note that it is in contact with both lead and copper strip.

### STAGE 6

An even flow of solder is necessary to produce a sound, bright looking

joint as the one on the left. Bad workmanship produces dry joints (centre) and bridges, etc (right).

### STAGE 7

Stranded wires should always be tinned. Here we show how this is done, and the final result if you are unlucky (far right).

### STAGE 8

The correct way to solder a wire to say, a Veropin. The wire on the right is obviously wrong, the loose wires could cause a short circuit.

### STAGE 9

As in the previous photo, a good mechanical joint is essential when wiring up to tagged components. Do not let the wire "hang" in the tag.

### STAGE 10

Although nothing to do with good soldered joints, the use of a heat shunt on heat sensitive component leads is a "must".


### STAGE 11

One tricky operation is the soldering of an i.c. Here we show the correct angle for the iron bit and solder.

**S**OLDERING is the most important aspect of project building. Unless you are competent in this "art" your projects are more than likely to fail. The importance of good, neat, clean soldering cannot be overstressed. As with most things a good soldering technique comes with practice.
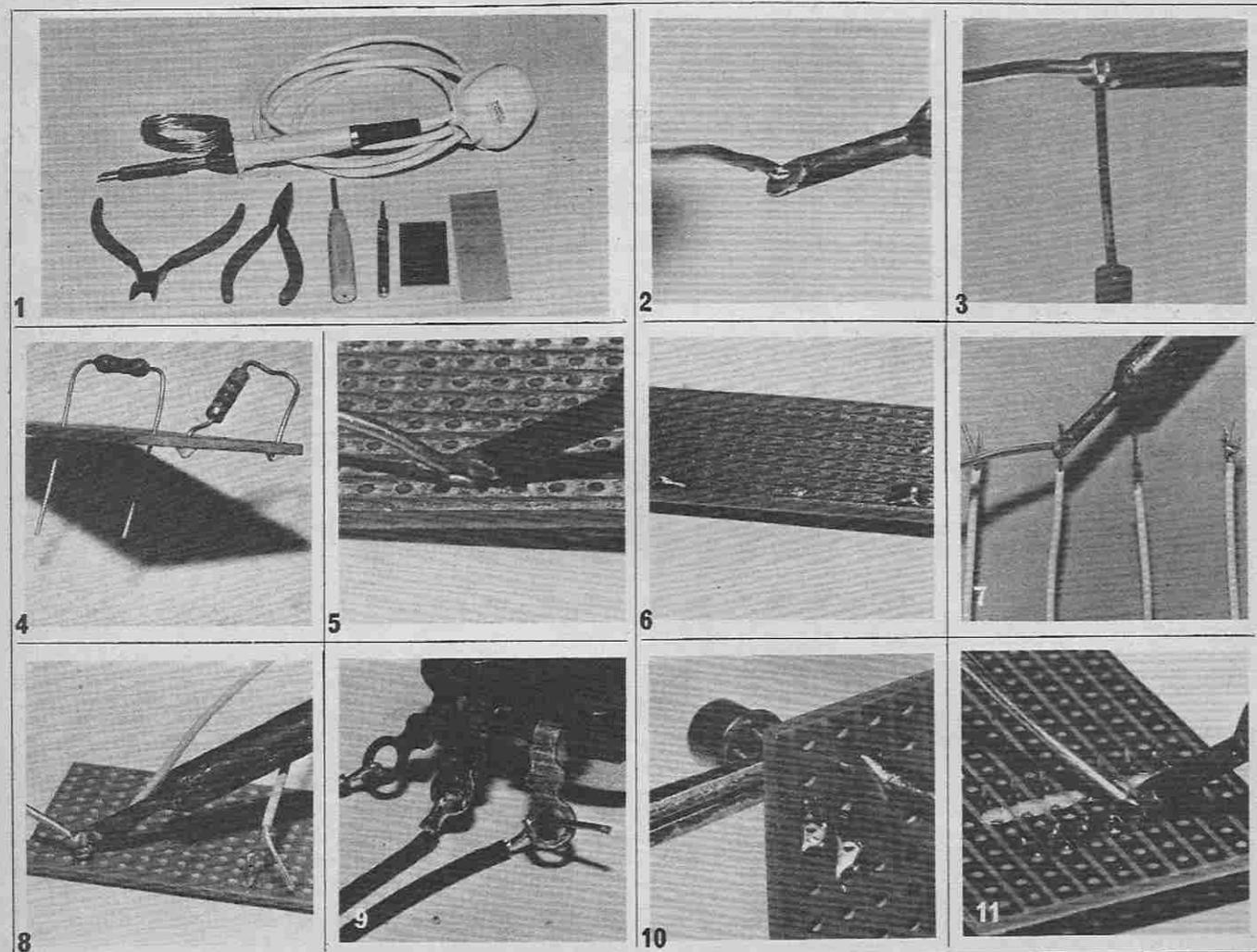
### STAGE 1

The tools required are few and simple. Choose an iron with a bit size appropriate to the job in hand. Always use a resin-cored solder of 60/40 tin/





# Everyday News

## SATELLITES AND SUPERTITLES

At a recent open day at the Independent Broadcasting Authority (IBA) Engineering Centre at Crawley Court, some of the many areas of activity were demonstrated. Of particular interest are the use of space Satellites for broadcasting and the work being carried out to help the deaf and hard of hearing to receive subtitles on normal television programmes.

### Satellites


Studies are at present underway using a transportable trailer-mounted 2.5 metre dish antenna transmitting at 14GHz to a geostationary Orbital Test Satellite (OTS) situated 22,300 miles above the Earth. Transmissions from the satellite are received on a 3.5 metre parabolic dish antenna part of a compact satellite receiving terminal located at Crawley Court.

This set-up provides temporary links from remote places (reached by truck and trailer) allowing "live" news and other programmes

to be received. This could eventually lead to direct-broadcasting satellites providing programmes direct to the home.

The IBA's prime concern is to secure suitably frequency allocations for mobile satellite operations and provided suitable terminals can be made available, it would be possible to set up a temporary outside broadcast link via a satellite very quickly, with a minimum of forward planning.

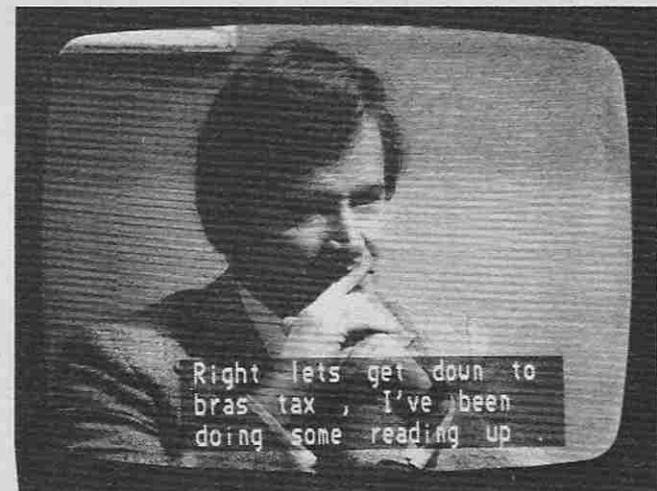Theoretically, with a smaller dish, a roving reporter in a news car could make use of the satellite.



### Supertitles

Optional subtitles on television programmes, or "Supertitles" as the IBA have named them, for persons with impaired hearing are being researched and developed by the IBA and the ITCA in conjunction with a team led by Dr. Alan Newell at Southampton University.

The idea is to make use of the Oracle teletext system which incidentally has not been as enthusiastically received by the general public as all concerned had expected. The reception of Supertitles requires the use of a t.v. capable of teletext reception.

The main concern has been the time and cost involved in the preparation of the subtitles requiring man-hours in the order of 20 to 30 times the programme running time for perfect subtitling. This makes subtitling of "live" programmes impossible.

In an effort to overcome this, a system is being explored that uses a Palantype shorthand machine linked to an electronic processor. In

basic form the subtitles require some experience and training on the part of the viewer, phonetic spellings being one problem.

Subtitled test programmes are being shown to deaf and hard of hearing viewers for their reactions and comments. Later a number of experimental transmissions will be made through the Oracle service.

---

The UK-developed micro-processor chip used in the Chromatronics 24-tune door chime is now available as a component for home constructors.

---

Officials of the EEC are keeping a watch on Japanese TV and other electronic goods companies seeking to set up manufacturing units in Spain.

They see the current Japanese interest in Spain as a back-door entry into the EEC by the Japanese in advance of Spain becoming an EEC member by the mid-1980s.



## Electronic White Sticks

An experimental guidance system for the blind is in use in a Swedish shopping centre. It uses an underground cable and a portable receiver.

An unsighted person can follow a prescribed route by listening to a signal which changes tone if deviation takes place. A further development suggested for the blind is a stick fitted with laser-beam equipment which will allow detection of obstacles up to six feet away. Again the user is warned by an audible signal.



## ANALYSIS

### HOPPING MAD!

Superficially, radio communications and radio broadcasting appear to be the same thing. Yet there is a major difference. Communication is person-to-person or organisation to organisation and is essentially private in character. In contrast, broadcasting, as the name implies, is something for everybody to hear.

Technically, however, they are the same thing. Once a radio transmitter goes on the air everyone within range who has appropriate receiving equipment can listen equally well to the transmission whether it be a radio communications link (private) or a broadcast (public). The general rule is that if one inadvertently hears a transmission not intended for public reception then it should be ignored, and if not ignored then the message content should certainly not be passed on to a third party or in any way made public.

As well as amateur listeners there are professional listeners, mainly government and defence services. They constantly monitor diplomatic radio links of friendly as well as potentially enemy powers and also listen in to military networks. They want to know what's going on and it goes under the name of communications intelligence (COMINT), a branch of electronics warfare and an esoteric form of spying.

The traditional way of keeping such communications private is by enciphering the messages so that they are meaningless unless the recipient has the key to the cipher. The trouble is that modern code-breaking by electronic computer is now so powerful that nobody can really be sure that even the most complex cipher cannot be broken by the key being discovered in a matter of hours.

One solution is to make unauthorised reception more difficult for casual or, more important, intentional listeners. And one way of doing this is by frequency hopping. Imagine you are sitting down in front of your radio and the signal you are trying to listen to is hopping from one spot on the dial to another and then to a third and so on. It would be hard to keep up.

Imagine the frequency hops are at the rate of hundreds of hops per second, each new frequency at which the signal settles appearing to be completely random with no detectable sequence. This is now being achieved.

In fact radio system designers are now hopping mad! The frequency synthesizer, broad-band r.f. circuits which need no tuning, microprocessor control and large scale integration are the new tools which make frequency hopping possible in even military manpack sets.

The pattern of the hopping sequence is determined in a similar way to modern electronically generated ciphers so that if you haven't got the key there is no way of telling where the next hop will be. The technical problem of making the receiver tuning hop in exact synchronism with the transmitter has been overcome, at least in the laboratory, and the first UK-designed frequency hopping tactical field radio will be demonstrated later this year.

Apart from communications security, frequency hopping in the battlefield has another advantage. If several radio nets are all operating and all hopping about at the same time it would be immensely more difficult for an enemy direction finding station to detect their individual locations.

Needless to say, while one bunch of radio buffs are slaving away perfecting frequency hopping radio, another bunch are spending sleepless nights solving the problem of perfecting the broadband receivers and hopping analysers which may be able to follow the hops and so allow COMINT to continue unchecked.

Brian G. Peck

The National Television Rental Association is one of the bodies leading the campaign to popularise the Prestel TV-based information service among the UK's 20 million TV viewers.

The rental companies, members of NTRA, expect rental charges of Prestel-equipped receivers to be about £24 a month.

### FLY-BY-TOUCH

The Royal Aircraft Establishment is evaluating the Digilux "touch mask" developed by Marconi Radar for use in the cockpits of combat aircraft. The "touch mask" enables a large number of controls and functions to be centralised on a single panel on which the pilot can exercise command by merely placing a finger at the appropriate point instead of operating conventional switches and knobs.

The "touch mask" is already in use in air traffic control functions and this is the first time it has been tried in aircraft cockpits with the intention of easing the pilot's work load.

### Underground Computer

Military mainframe computers are generally well fortified, even underground, to protect them from nuclear attack. Now the first civilian computer has been built in an underground bunker.

Not from military threat by a foreign power but against internal terrorists and vandalism. It has happened in Italy which has experienced over two dozen attacks on computer installations in the last three years.

### SOLAR WITCHCRAFT

Mass production of solar cells on a continuous strip is now a fact in the United States. Dr Paul Maycock of the US Department of Energy states that four years ago this technology looked like witchcraft and today it is a viable solar alternative.

He believes that such techniques will so lower costs of direct conversion of sunlight to energy that solar energy will become economically viable in the USA by the mid-1980s rather than earlier forecasts of the year 2000.

The new Eurovision Control Centre in Brussels is now in operation. Crow of Reading supplied the monitoring and control system which provides push-button routing for 30 audio and video channels.

The equipment was built in the UK and shipped to Brussels in a single 12-ton consignment.

### Speed of light

The IBM Company is working on solid state devices with switching speeds more than 10 times faster than the fastest transistor logic circuits. The technique is called current injection logic and to obtain a switching speed as little as 7 picoseconds the circuits need to operate at extremely low temperatures.

Total switching time is 15 picoseconds because it takes 6 picoseconds for the signal to move from one circuit to the next. And if you wonder what a picosecond is—it is a trillionth of a second.

## SHOWING THE WAY AHEAD

For the first time ever, the British telecommunication industry is joining forces to present a co-ordinated display of its systems, equipment and capability to the world.

Five leading firms are joining with the Post Office to show their products and services at Telecom '79—the world telecommunications exhibition and conference to be held in Geneva from September 20 to 26. The companies are: GEC Telecommunications, Plessey Telecommunications, Standard Telephones and Cables, Marconi Communication Systems and Pye TMC.

The six co-ordinated exhibits will form, with a working model of System X, Britain's all-electronic telephone exchange system for the 80s and beyond. This will include the full range of services, systems and marketing skills available to meet the needs of overseas telecommunications administrations.

# RADIO WORLD

By Pat Hawker, G3VA

## The whispering gallery

ALMOST all standard textbooks tell us that short-wave (h.f.) signals travel round the world in a series of "hops" each having a maximum range of about 5000km. The signals, so we are told, travel up to the F layer of the ionosphere, then down again to the surface of the earth, up again to the F layer and so on. Well yes; there is plenty of evidence that this is what happens with powerful signals at frequencies significantly below the maximum usable frequency (i.e. at what is often called the optimum "working frequency").

But over the past 20 years or so there has been convincing evidence that this is *not* the path that allows radio amateurs and short-wave listeners to work or listen to low-power stations at very long distances. For example signals arriving from Australia and New Zealand around dawn and dusk are often at strengths that do not stand up to conventional "path-loss" calculations that assume a 6dB loss at each intermediate ground reflection point.

## Chordal Hop

It has in fact become increasingly clear that these stronger-than-expected signals are virtually always propagated by what is called "chordal hop" or sometimes the "whispering gallery" mode (from the effect that can be observed with speech in the gallery of St Pauls Cathedral, London), and which are close to or even a little above the "maximum usable frequency" for the route. The signals are trapped between different layers of the ionosphere or skim along the under surface of a layer, often being launched into or out of this mode by ionospheric "tilts". In fact such signals may not return to Earth anywhere between the transmitter and the receiver.

It was a German radio amateur, Hans Albrecht, working in Australia, who first showed that the amateur radio signals he could receive from Europe just did not tie up with the conventional ideas about h.f. propagation and linked this with the investigations in the USA with "round-the-world echoes". It was one of the important new discoveries in an era when it had been thought that most of the mysteries of radio propagation had been solved. But most textbooks have still not caught up with the new concept.

## Helping travellers

The BBC is due shortly to begin field trials of CARFAX, the time-multiplexed area-broadcasting system intended to provide local traffic information over an interlocking network of transmitters sharing a single channel at the low-frequency end of the medium-wave band.

While technically the system now seems promising (although the original proposals ran into the problem of poor definition of areas and had to be modified) I still find it difficult to believe that motorists really need or want a 24-hour information system.

However in the USA, with its vastly greater geographical area, the Federal Highway Administration has commissioned a research organisation to conduct a systems analysis and provide guidelines for a chain of "Highway Advisory Radio Stations" designed to provide a "travellers information service". These will be low-power, short-range stations operating on 530 or 1610kHz (i.e. both ends of the present a.m. broadcast band). Stations may also be set up by city authorities.

In some cases, apart from announcements about traffic conditions, detours, emergencies and weather news, the broadcasts will draw attention to historic sites and local recreational areas. Road signs will tell the motorist when he is coming into range of one of these stations, and no special form of decoder or automatic switching will be needed.

## Crackles and buzzes

Certainly in the London area, and I suspect elsewhere, the levels of man-made electrical interference (r.f.i.) continue to rise over most of the l.f. m.f. h.f. and v.h.f. bands. Thermostats and small motors and hundreds of other sources continue to clobber or mask weak signals, while the Russian "Woodpecker" radar, broadcast jammers and military pseudo-noise spread spectrum systems all go to show that Governments are among the worst offenders. We really do need a society for the preservation of the ionosphere and the elimination of pollution!

Among the latest noises are those coming from "home computers" (and even pocket calculators) and in the United States the Federal Communications Commission have begun a special enquiry into this new source of r.f.i. Part of the troubles are faulty

modulators used to connect into the TV sets (a problem also with video-games) but there is also interference from the pulses surging around in the logic circuitry. This problem of digital techniques seems to be often overlooked by those who believe that conventional analogue techniques are now becoming obsolete.

With the Post Office looking ahead to an all-digital telephone network (System X etc) one wonders how much thought has been given to the question of radiation from telephone circuits (at least until we all use optical fibres to carry the signals in the form of light). Is this why the P.O. keep promoting that confounded bird "Buzby"?

And there is trouble coming in the kitchens. Sir Bernard Lovell has recently drawn attention to the way microwave ovens can play havoc with weak radio astronomy signals. He claims that poorly constructed ovens can interfere with his radiotelescopes at distances of several miles.

It has also been suggested that microwave ovens may present a problem when it comes to direct-broadcast satellites working on 12GHz—a sort of TV/dinner confrontation?

## Cow and pig power

The search for alternative, small-is-beautiful technology that would free us from dependence on electricity supply mains is being taken seriously by some radio amateurs. Quite a lot has been written about harnessing wind, water, sunshine and even muscle power (an energetic man with a pedal generator can deliver about 100 watts of electric power for a short time).

At least two radio amateurs, Tim Hutchinson, 5Z4DV in Kenya and Lars-Erik Johansson, SM4AQL in Sweden, have found a practical way of obtaining power not only for their amateur radio equipment but also for their domestic and farm appliances. Both use "output" from farm animals to obtain a regular supply of methane gas which can then be used to generate electricity.

Tim Hutchinson began using a cow and pig powered transmitter as long ago as 1955, using a modified 2HP paraffin engine to charge a 32-volt bank of large NiFe cells. This engine has clocked up over 60,000 hours running on "biogas" (methane/carbon-dioxide mixture) produced from cow and pig manure, coffee skins, grass etc, roughly the equivalent of 10 gallons of fuel a day, and providing him also with a rich organic fertiliser for his coffee crop.

The Swedish amateur has an even more impressive installation, using a 22,000 gallon methane-digester which produces 70 cubic metres of methane gas from the "throughput" of 50 Friesian cows and 40 heifers and again ending up as non-smell fertiliser.

# STEVENSON

## Electronic Components

### REGULATORS


78L05 30p	7805 60p	79L05 70p	7912 80p
78L12 30p	7812 60p	79L12 70p	7915 80p
78L15 30p	7815 60p	7905 80p	LM723 35p

### HARDWARE
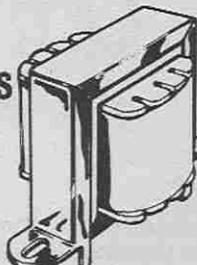
#### MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.  
Available with secondaries of:  
6-0-6, 9-0-9 and  
12-0-12. 92p. each.



#### LOUDSPEAKERS

56mm dia. 8 ohms	70p
64mm dia. 8 ohms	75p
64mm dia. 64 ohms	75p
70mm dia. 8 ohms	100p
70mm dia. 80 ohms	110p



#### TERMINALS

Rated at 10A. Accepts 4mm plug, black, blue, green, brown and red . . . 22p

#### SWITCHES

Subminiature toggle. Rated at 3A 250V.  
SPDT 70p SPDT centre off 75p  
DPDT 80p DPDT centre off 95p



Standard toggle


SPST 34p DPDT 48p

Wavechange switches.

1P12W, 2P6W, 3P4W or 4P3W all 43p ea.

Miniature switches (non-locking)

Push to make 15p Push to break 20p

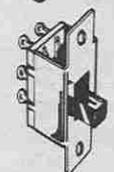

Slide switches (DPDT)

Miniature 14p Standard 15p

#### CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p




WHY NOT VISIT OUR
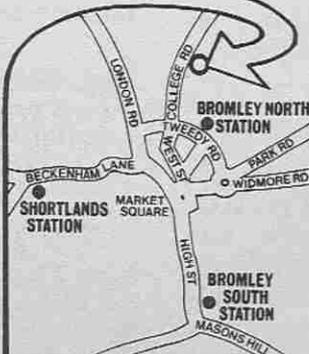
## NEW SHOP

We welcome callers at our new premises at the address below (5 mins. from High St.) We are open Mon - Sat, 9am-6pm. Special offers available.

Express telephone order service. Orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Tel: 01-464 2951/5770.



ORDERS  
DESPATCHED  
BY RETURN  
POST

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980.

Official orders welcome.

BARCLAYCARD  
& ACCESS WELCOME.



### TRANSISTORS

AC127 17p	BCY71 14p	ZTX109 14p
AC128 16p	BCY72 14p	ZTX300 16p
AC176 18p	BD131 35p	2N697 12p
AD161 38p	BD132 35p	3N1302 38p
AD162 38p	BD135 38p	2N2905 22p
BC107 8p	BD139 35p	2N2907 22p
BC108 8p	BD140 35p	2N3053 18p
BC109 8p	BF244B 36p	2N3055 50p
BC147 7p	BFY50 15p	2N3442 135p
BC148 7p	BFY51 15p	2N3702 8p
BC149 8p	BFY52 15p	2N3704 8p
BC148 9p	MJ2955 98p	2N3705 9p
BC177 14p	MPSA06 20p	2N3706 9p
BC178 14p	MPSA56 20p	2N3707 9p
BC179 14p	TIP29C 60p	2N3708 8p
BC182 10p	TIP30C 70p	2N3819 22p
BC182L 10p	TIP31C 65p	2N3904 8p
BC184 10p	TIP32C 80p	2N3905 8p
BC184L 10p	ZTX107 14p	2N3906 8p
BC212 10p	ZTX108 14p	2N3908 8p
BC212L 10p		2N3904 8p
BC214 10p		2N3905 8p
BC214L 10p		2N3906 8p
BC477 19p		2N3908 8p
BC478 19p		2N3904 8p
BC479 19p		2N3905 8p
BC548 10p		2N3906 8p
BCY70 14p		2N3908 8p

### DIODES

1N914 3p	1N5401 13p
1N4001 4p	BZY88ser. 8p
Full spec. product.	
1N4148	£1.40/100, £11/1000

### LINEAR

CA3140 38p	NE555 21p
LM301AN 28p	NE566 50p
LM318N 85p	NE565 85p
LM324 45p	NE567 170p
LM339 45p	SN76003 200p
709 28p	LM380 75p
741 16p	LM382 120p
747 40p	LM1830 150p
748 30p	LM3900 50p
CA3046 55p	LM3909 65p
CA3080 70p	MC1496 60p
CA3130 90p	MC1458 32p
	SN76013 140p
	SN76023 140p
	SN76033 200p
	SN76477 220p
	TBA800 70p
	TDA1022 650p
	ZN414 75p

### CAPACITORS

<b>TANTALUM BEAD</b>		each
0.1, 0.15, 0.22, 0.33, 0.47, 0.68,		
1 & 2.2uF @ 35V		8p
4.7, 6.8, 10uF @ 25V		13p
22 @ 16V, 47 @ 5V, 100 @ 3V		16p
<b>MYLAR FILM</b>		
0.001, 0.01, 0.022, 0.033, 0.047		3p
0.068, 0.1		4p
<b>POLYESTER</b>		
Mullard C280 series		
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1		5p
0.15, 0.22		7p
0.33, 0.47		10p
0.68		14p
1.0uF		17p
<b>CERAMIC</b>		
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF		2p
<b>RADIAL LEAD ELECTROLYTIC</b>		
63V 0.47 1.0 2.2 4.7 10		5p
	22 33 47	7p
		13p
	220	20p
25V 10 22 33 47		5p
		8p
	220	10p
	470	15p
		23p

### CONNECTORS

<b>JACK PLUGS AND SOCKETS</b>			
	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p
<b>DIN PLUGS AND SOCKETS</b>			
	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p
<b>1mm PLUGS AND SOCKETS</b>			
Suitable for low voltage circuits, Red & black.			
Plugs: 6p each Sockets: 7p each.			
<b>4mm PLUGS AND SOCKETS</b>			
Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each			
<b>PHONO PLUGS AND SOCKETS</b>			
Insulated plug in red or black . . . . . 9p			
Screened plug . . . . . 13p			
Single socket . . . . . 7p Double socket . . . . . 10p			

### VERO

Size in.	0.1in.	0.15in.	Veropins—
2.5 x 1	14p	13p	single sided
2.5 x 3.75	42p	40p	per 100
2.5 x 5	52p	50p	0.1in 35p
3.75 x 5	60p	60p	0.15in 40p
3.75 x 17	195p	180p	

### BOXES



Aluminium boxes with lid and screws

	Length	width	height	
AL1	3	2	1	48p
AL2	4	3	1½	58p
AL3	4	3	2	65p
AL4	6	4	2	70p
AL5	6	4	3	85p
AL6	8	6	2	116p

### THYRISTORS

Plastic-cased Thyristors: Texas

100V	4A	8A	12A
200V	36p	45p	62p
400V	42p	53p	68p
	51p	66p	86p

### TRIACS

Plastic cased Triacs. Texas. All rated at 400V.

4A	70p	42A	90p	20A	185p
8A	80p	16A	95p	25A	215p


### CMOS

4001 12p	4018 55p	4050 25p
4002 12p	4023 12p	4066 35p
4007 12p	4024 40p	4068 18p
4011 12p	4026 90p	4069 12p
4012 12p	4027 30p	4071 12p
4013 28p	4028 48p	4081 13p
4014 12p	4029 50p	4093 45p
4015 50p	4040 60p	4510 65p
4016 30p	4042 50p	4511 65p
4017 48p	4046 90p	4518 65p
	4049 25p	4520 60p

FULL DETAILS IN CATALOGUE!

### SKTS

Low profile by Texas

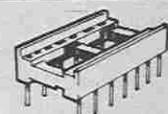

8 pin	8p	16 pin	11p	28 pin	22p
14 pin	10p	24 pin	18p	40 pin	32p
Soldercon pins: 100:50p. 1000:370p					

### OPTO

LED's	0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p	8p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		

### DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

### RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:			
0.25W	each	100+	1000+
0.5W	1p	0.9p	0.8p
	1.5p	1.2p	1p
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.			
<b>METAL FILM RESISTORS</b>			
Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix:			
0.25W	each	100+	1000+
	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER OVER 2500 STOCK ITEMS.




Mail orders to: STEVENSON (Dept EE)

# 76 College Road, Bromley, Kent, England

# TOUCH-ON PILOT LIGHT

By F. G. Rayer

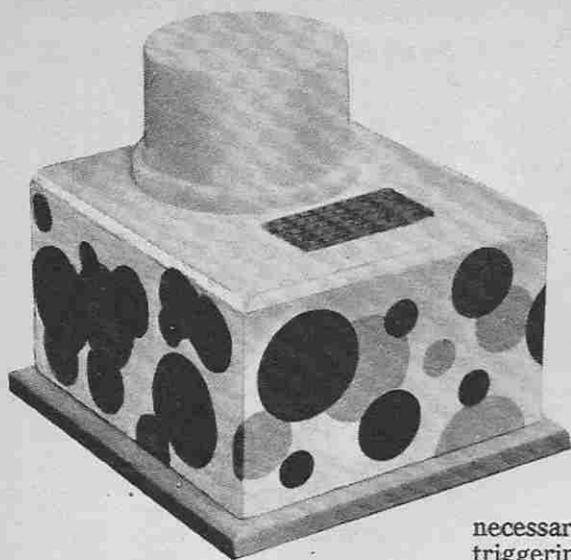

**T**HE SIMPLE project described here operates from a 4.5V dry battery and so is completely safe. It is not necessary to locate and operate a switch in darkness, as the light is put on by light finger contact with a touch pad. The lamp remains on until extinguished by a switch fitted on the unit.

## CIRCUIT DESCRIPTION

The circuit of the unit is shown in Fig. 1. The lamp receives current through the silicon controlled rectifier CSR1. As CSR1 is normally in a non-conducting state, the lamp is extinguished. Push switch S1 is normally closed.

The touch pad has no circuit from TR1 collector to base, so there is no base current for TR1. As a result, no collector current flows and the emitter cannot provide gate current for CSR1.

When a finger is placed on the touch pad, base current flows and the emitter of TR1 moves positive since TR1 is now turned on. As gate *g* of CSR1 is connected to the emitter, it is triggered into conduction. Current through CSR1 then lights the lamp. It now remains in the conducting state once triggered, even though gate current is no longer available when the finger is withdrawn from the touch pad.

When the light is no longer required, S1 is pressed. This breaks the anode supply to CSR1, so that it reverts to its non-conducting state.

A 3.5V 0.3A bulb is used, but a 6.3V 0.15A bulb can be substituted if only a relatively weak light is needed, as for seeing the time. Capacitor, C1 was found

necessary to avoid occasional triggering of a sensitive thyristor when S1 closes. The value is not critical.



Most of the components are mounted on a piece of 0.15 inch matrix stripboard, 5 strips by 16 holes. This is shown in Fig. 2. Only one break is required and can be made with a sharp drill or cutter.

Pass the component wires through the holes shown, and solder them below. Snip off unwanted wires. External wires, of thin flex, are then soldered on as required.

## CASE

It is clear that any insulated box large enough for the battery and board will be suitable. However, the case shown was made from plywood and looked quite presentable.

Two pieces 90 x 50mm and two pieces 100 x 50mm form the sides. The top is 100 x 90mm. Fit these together with panel pins and wood-working adhesive, and glasspaper the joints later.

The bottom is about 3mm larger all round, and is fixed with four small screws. The whole box can then be painted or varnished.

## TOUCH PAD

A piece of 0.15 inch stripboard, 5 strips by 10 holes is used as the

touch pad. Short wires are soldered to alternate strips and pass down through holes in the top as shown in Fig. 3. The stripboard is cemented to the box, foils upwards, and the leads are joined as shown, and taken to the circuit board.

The circuit board is fixed with two screws, with nuts or other spacers underneath it.

The "lens" is quite simply a white aerosol can top. Choose one which is fairly opaque so as to let the most amount of light through.

Three small cheese head screws are placed equally around a circle corresponding to the internal diameter of the aerosol top. The top can then be simply pushed into place, whereby the screws should hold the top fairly well. It is not advisable to glue the top into place, as changing of the bulb would be difficult at a later date.

Depending on its height the lamp holder can either be mounted on top of the case, or, as in the prototype on the underside, with just the bulb projecting through.

## IN USE

A 4.5V 1289 type flat battery fits in the case. Make tinfoil clips for its contacts, or solder positive and negative leads directly to it. Polarity must be correct.

Light finger contact anywhere on the pad should bring the bulb on. Pressing S1 resets it to off. The pad should be clean, and connections to it properly insulated, or the bulb may come on too easily. Sensitivity can be reduced by placing a 2.2 megohm resistor connected between TR1 base and the negative line, but this was found to be unnecessary with the prototype. □

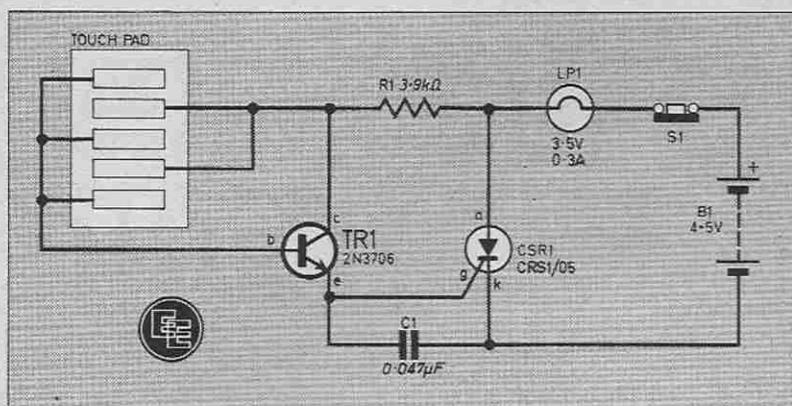


Fig. 1. Complete circuit diagram for the Touch-on Pilot Light.

**COMPONENTS**  
**approximate**  
**cost**                    **£2**

**Resistor**

R1 3.9kΩ ¼W carbon ±10%

**Capacitor**

C1 0.047μF polyester

**Semiconductors**

TR1 2N3706 silicon npn

CSR1, CRS1/05 or similar 50V  
1A thyristor

**Miscellaneous**

LP1 3.5V 0.3A (or 6.3V

0.15A, see text)

MES bulb

S1 single pole push-to-break  
switch

B1 4.5V, type 1289 battery

Stripboard 0.15 inch matrix,  
5 strips × 16 holes, and 5

strips × 10 holes (one off  
each); MES type batten holder

for LP1; white aerosol can  
cap; material for case or ready

made type as required; con-  
necting wire.



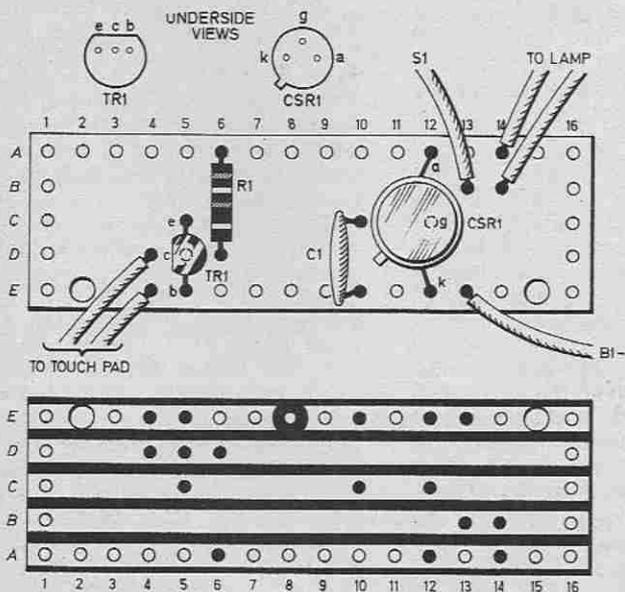


Fig. 2. Stripboard layout. Only one break is required. Insure that the thyristor and transistor are inserted correctly. If a metal case is used then it is necessary to isolate the mounting holes by means of breaks either side of the holes.

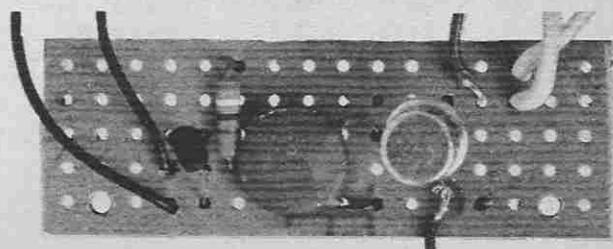

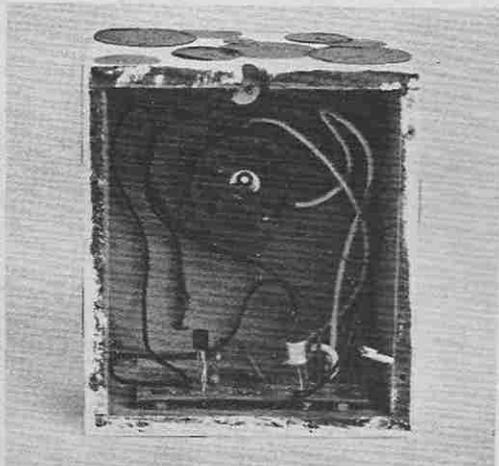The completed circuit board for the Touch-on Pilot Light.



The completed Touch-on Pilot Light showing positioning of components and circuit board.

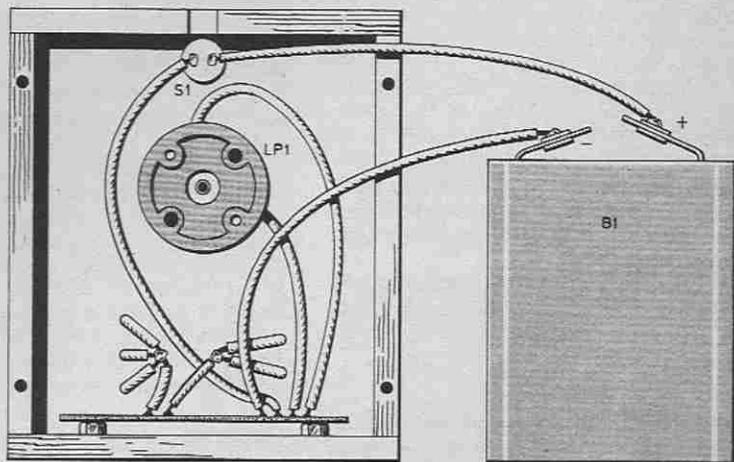


Fig. 3. The remainder of the wiring is completed as shown here. The holder for the bulb is simply glued into place.

# WORKSHOP MATTERS

By Harry T. Kitchen

## Metal Working

The art and science of "chassis bashing" disappeared with the advent of semiconductors. This is in many ways a great pity. "What," you may well ask "has this to do with modern electronics?". A great deal, I do assure you. Chassis bashing required a variety of skills, skills that can be usefully incorporated into "cabinet bashing" to coin a phrase.

Equipment, ancient or modern, requires cabinets, and commercially available cabinets are both expensive and rarely suit the project in hand; rather the project has to be tailored to suit the cabinet available, and thus there is considerable incentive to make your own cabinets.

What do we require, where do we start? Let us consider tools first, then techniques.

## Marking Out

Cabinets vary in size and in shape, they have a number of holes, probably of varying size. The project will determine the size of the cabinet, and will require the holes to be in specific positions, sometimes to a high degree of accuracy.

We can, of course, use an ordinary rule for marking out our piece of virgin aluminium sheet, but a better method is to use a proper combination square. This enables a rule to be fixed at a precise position with respect to the frame, and thus repetitive accuracy, if required, is assured. It also enables marking-off at right angles to the edge of the aluminium to be effected automatically, and most also provide for a fixed 45 degree angle.

An ordinary rule can slide about on the aluminium sheet; the combination square will not since the frame is in contact with the edge of the aluminium sheet. For more involved work, a fully adjustable combination square is available, but this is of course much more expensive.

If the combination square does not incorporate a scribe—most do—then you will need to buy one.

## Cutting Tools

However you buy your aluminium sheets, sooner or later you will need to cut them, into smaller sizes say. Basically you can use a hacksaw or a pair of tin snips. Which do you buy?

Ideally both, and both come in various shapes and sizes. So let us look at hacksaws first.

The most common saw is the 12 inch; most of these will also accept 10 inch blades by adjusting the frame. Most will also allow the blade to be rotated through 90 degrees permitting long lengths of metal to be cut, but the width is limited by the distance between the frame and the blade.

Then we have the little 6 inch saw, sometimes called the "junior" saw. This is a handy little tool since it can be used where space precludes the use of the larger saw.

## Hacksaw Blades

Hacksaw blades do not, in my experience, get the attention they deserve from amateurs. Essential, when selecting a blade, is to discover the number of teeth per inch and the metal from which it is made.

The number of teeth per inch, or per 2.54cm for our metricated friends, must be chosen to suit the application; the thinner the metal, the more teeth you require per unit of length. A reasonable compromise is a blade having around 20 teeth per inch.

Blade material is selected by the manufacturer to suit different applications. Looking at the Eclipse catalogue, three types stand out for amateur use. These are the *HiCut* blades, claimed to be unbreakable under normal use, as are the *Flexible* blades. For use on soft materials, such as our aluminium sheets, are the *Low Alloy* blades.

Before leaving hacksaws, let us look at a most useful adjunct to these, the pad saw handle. This permits odd lengths of broken blades to be used, and is almost indispensable when cutting out straight-sided holes in sheets of metal once a hole has been started the length of the blade.

We can now look, briefly, at tin snips. Large or small, straight or curved? Four basic choices. Personally I prefer the straight snips, and whilst a large and a small snips may occasionally prove useful for coarse and fine work say, the large snips will prove adequate for most of the work.

## Drilling

An electric drill on a stand, preferably, or on its own, is a useful aid to drilling holes. On the other hand a good

quality hand drill will prove to be capable of coping easily with much of our work.

The drill should be one having machine-cut gears as these mesh better and run much more smoothly than cheap cast gears. An idler gear, opposite to the driving gear, assists greatly in reducing the sort of excessive slop that makes precision drilling difficult.

Most such drills have a chuck that will accept drill bits with a maximum shank diameter of  $\frac{1}{2}$  inch, and this is perfectly adequate as larger holes can be filed or cut out as necessary. If the drill is to be used for very fine drill bits, for p.c.b. drilling say, then it is essential that the chuck will close sufficiently; many do not.

## Drill Bits

Drill bits come in several sizes, denoted in four ways: letter, number, fractional, metric. Letter drills cover from A=0.234 inch to Z=0.413 inch; Number drills cover from No: 1=0.228 inch to No: 80=0.0135 inch; Fractional drills cover from  $\frac{1}{16}$  to  $\frac{1}{2}$  inch in  $\frac{1}{16}$ th inch increments; Metric drills cover from 0.5mm to 25mm.

The problem resolves into selecting any particular system—if you are starting from scratch. Undoubtedly metric will win the day, and this is perhaps, the way to go. Top quality drills, of any denomination, are expensive, but looked after they will give years of service.

If you are into p.c.b. work to any appreciable extent, then it will pay you to investigate one of the little electric drills and stands that are specifically marketed for this application. The motors are generally 12 volts d.c. working and can be run from a battery or from a power pack, and most of us have one of those lying around. If the power pack has a variable voltage output, this can be used to control drill speed, but of course the drill should not be operated above its rated voltage.



"Wouldn't you think they'd have a quicker method of smoothing the grass."

# THREE FOR FREE FROM CSC


ELECTRONICS BY NUMBERS  
FREE PROJECTS  
No 1, No 2,  
& No 3.

## ELECTRONICS BY NUMBERS
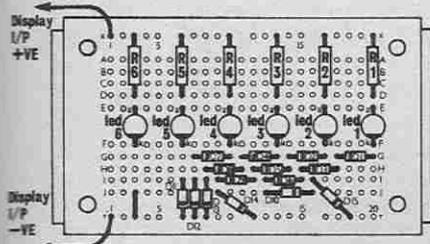
### LED BAR GRAPH UNIVERSAL INDICATOR

Now using **EXPERIMENTOR BREADBOARDS** and following the instructions in "Electronics by numbers" ANYBODY can build electronic projects.

Look at the diagram and select R1, this is a resistor with a value between 120 to 270 ohm. Plug it into holes X20 and D20, now take LED 1 and plug it into holes E20 and F20. Do the same with the Diodes e.g. plug D7 into holes G7 and G10.



## YOU WILL NEED

### EXP- ANY EXPERIMENTOR BREADBOARD

D1 to D15 - Silicon Diodes (such as 1N914)  
R1 to R6 - From 120-270 ohm resistors 1/4 watt.

LED1 to LED6 - Light emitting diodes.

**LED BAR GRAPHS** are replacing analogue meters as voltage-level indicators in many instances.

This circuit uses the forward voltage drop of diodes to determine how many LEDs light up. Any type of diode can be used but you must use all the same type. For full working details of this circuit fill in the coupon.

If you have already built the Two-transistor Radio and the Fish'n'cliks projects you will find that you can reuse the components from these projects to build other projects in the series.


**FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE FULL COPIES OF "ELECTRONICS BY NUMBERS" PROJECTS No 1, No 2 and No 3.**

## EXPERIMENTOR BREADBOARDS.


No soldering modular breadboards, simply plug components in-and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


**EXP.325.** The ideal breadboard for 1 chip circuits.  
Accepts 8,14,16 and up to 22 pin IC's.  
**ONLY £1.60.**

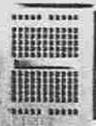

**EXP.350. £3.15.**  
270 contact points with two 20-point bus-bars.

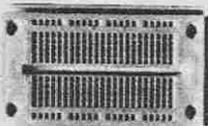

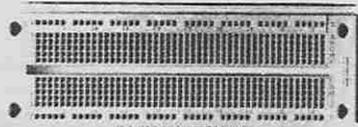**EXP. 300.**  
550 contacts with two 40-point bus-bars.  
**£5.75.**



**EXP. 650** for Micro-processors. **£3.60.**




**EXP 4B.**  
More bus-bars.  
**£2.30.**



ALL EXP.300 Breadboards mix and match with 600 series.

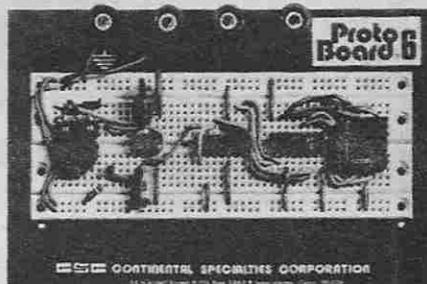
## PROTO-BOARDS.

THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST. TWO EASILY ASSEMBLED KITS.



PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

**PROTO-BOARD 6 KIT. £9.20.**

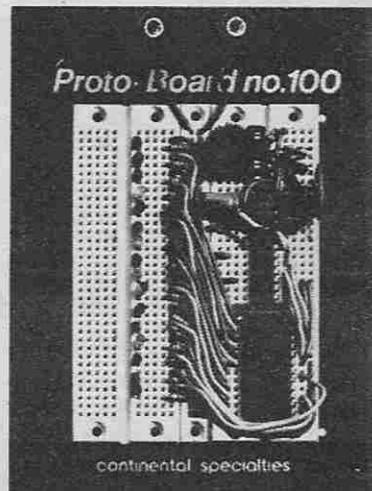

PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

**PROTO-BOARD 100 KIT £11.80.**

## HOW TO ORDER AND RECEIVE FREE COPY OF TWO-TRANSISTOR RADIO PROJECT, FISH'N'CLIKS AND LED BAR GRAPH.

**CSC UK LTD.** Dept 4T2, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T. 15%
EXP. 325	130	1	£ 2.70
EXP. 350	270	3	£ 4.48
EXP. 300	550	6	£ 7.76
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.99
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.51
TEST CLIPS			
PC. 16.			£ 4.03
PC.16-18.			£ 8.05
PC. 16-18 Dual Clip.			£12.94
PROTO-BOARDS.			
PB. 6.	630	6	£11.73
PB. 100.	760	10	£14.72

NAME .....

ADDRESS .....

DEPT. 4T2

## PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



PC - 16 pin. £2.75.

PC - 16 pin with cable. £6.00.

PC - 16 with cable and 16 pin clips at both ends. £10.25.

CONTINENTAL SPECIALTIES CORPORATION



Europe, Africa, Mid-East: CSC UK LTD.  
Dept 4T2, Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: SAFFRON WALDEN 21682.  
Telex: 817477.

FILL IN COUPON & RECEIVE FREE COPY OF  
ELECTRONICS BY NUMBERS PROJECTS No 1, 2 AND 3

## ELECTRONIC BOOKS

Ref. No.	Title	Price
126	Boys Book of Crystal Sets	25p
138	How to Make Aerials for TV (Band 1-2-3)	25p
160	Coil Design and Construction Manual	75p
196	AF-RF Reactance-Frequency Chart for Constructors	15p
200	Handbook of Practical Electronic Musical Novelties	50p
201	Practical Transistorised Novelties for Hi-Fi Enthusiasts	35p
202	Handbook of Integrated Circuits (IC's) Equivalents and Substitutes	1.00p
203	IC's and Transistor Gadgets Construction Handbook	60p
205	First Book on Hi-Fi Loudspeaker Enclosures	75p
206	Practical Transistor Circuits for Modern Test Equipment	60p
207	Practical Electronic Science Projects	75p
208	Practical Stereo and Quadrophony Handbook	75p
210	The Complete Car Radio Manual	1.00p
211	First Book of Diode Characteristics Equivalents and Substitutes	95p
213	Electronic Circuits for Model Railways (Reprinting)	1.00p
214	Audio Enthusiasts Handbook	85p
215	Shortwave Circuits and Gear for Experimenters and Radio Hams	85p
216	Electronic Gadgets and Games	1.00p
217	Solid State Power Supply Handbook	85p
218	Build Your Own Electronic Experimenters Laboratory	85p
219	Solid State Novelty Projects	85p
220	Build Your Own Solid State Hi-Fi and Audio Accessories	85p
221	28 Tested Transistor Projects	95p
222	Solid State Short Wave Receivers for Beginners	95p
223	50 Projects Using IC CA 3130	95p
224	50 CMOS IC Projects	95p
225	A Practical Introduction to Digital IC's	95p
226	How to Build Advanced Short Wave Receivers	1.20p
227	Beginners Guide to Building Electronic Projects	1.25p
228	Essential Theory for the Electronics Hobbyist	1.25p
RCC	Resistor Colour Code Disc Calculator	10p
BP1	First Book of Transistor Equivalents and Substitutes	50p
BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60p
BP6	Engineers and Machinists Reference Tables	50p
BP7	Radio and Electronic Colour Codes and Data Chart (Reprinting)	25p
BP11	Practical Transistor Novelty Circuits	40p
BP14	Second Book of Transistor Equivalents and Substitutes	1.10p
BP22	79 Electronic Novelty Circuits	75p
BP23	First Book of Practical Electronic Projects	75p
BP24	52 Projects Using IC741	95p
BP25	How to Build Your Own Electronic and Quartz Controlled Watches & Clocks	85p
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p
BP28	Resistor Selection Handbook (International Edition)	60p
BP29	Major Solid State Audio Hi-Fi Construction Projects	85p
BP30	Two Transistor Electronic Projects	85p
BP31	Practical Electrical Re-Wiring and Repairs	85p
BP32	How to Build Your Own Metal and Treasure Locators	1.00p
BP33	Electronic Calculator Users Handbook	95p
BP34	Practical Repair and Renovation of Colour TVs (Reprinting)	95p
BP35	Handbook of IC Audio Pre-amplifier and Power Amplifier Construction (Reprinting)	95p
BP36	50 Circuits Using Germanium Silicon and Zener Diodes	75p
BP37	50 Projects Using Relays, SCR's and TRIACS	1.10p
BP38	Fun and Games with your Electronic Calculator	75p
BP39	50 (FET) Field Effect Transistor Projects	1.25p
BP40	Digital IC Equivalents and Pin Connections	2.50p
BP41	Linear IC Equivalents and Pin Connections	2.75p
BP42	50 Simple L.E.D. Circuits	75p
BP43	How to Make Walkie-Talkies	1.25p
BP44	IC555 Projects	1.45p
BP45	Project in Opto-Electronics	1.25p
BP46	Radio Circuits Using IC's	1.35p
BP47	Mobile Discotheque Handbook	1.35p
BP48	Electronic Projects for Beginners	1.35p
BP49	Popular Electronic Projects	1.45p
BP50	IC LM3900 Projects	1.35p
BP51	Electronic Music and Creative Tape Recording	1.25p
BP52	Long Distance Television Reception (TV-DX) For The Enthusiast	1.45p
BP53	Practical Electronic Calculations and Formulae	2.25p
BP54	Your Electronic Calculator and Your Money	1.35p
BP55	Radio Stations Guide	1.45p


Please add 20p p. & p. per book  
Send SAE for our large range of Components

## TECHNOMATIC LTD

17 BURNLEY ROAD, LONDON NW10 1ED  
(2 minutes from Dollis Hill Tube station)

(Ample parking space)


Telephone: 01-452 1500  
Telex: 922800

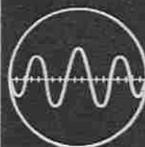

# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING CONTROL SYSTEMS

## NEW FROM TUAC

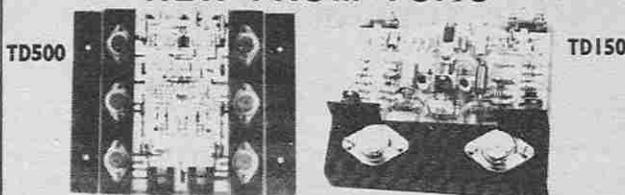

### 7" x 9" x 1 3/4" ULTRA QUALITY HIGH POWER 5" x 5" x 2" New D.C. Coupled Design AMPLIFIERS

**Featuring**—Electronic Short Open and Thermal Overload Protection.  
**Brief Spec.**—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms.  
Frequency Response 20 Hz - 20 KHz T.H.D. at full power 0-1%  
Hum and Noise—100 dB Relative full output.

**T.D. 500** 300W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms..... **£45-00**  
Power supply P.S.300..... **£30-00**

**T.D. 150** 150W into 4 Ohms. 100W into 8 Ohms..... **£26-25**  
Power supply P.S. 150..... **£19-75**

**T.D. 150** 60 Version 60W into 8 Ohms. 40W into 15 Ohms..... **£19-75**  
Power supply P.S.60..... **£15-50**

Note—P.S. 300 will drive 2 T.D. 150 amplifiers  
All output ratings are R.M.S. continuous sine wave output.

#### TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD., or quote Access/Barclay Card No. (We accept holders phone orders 01-672 9080).

Post to—

TUAC LTD., 121 CHARLMONT ROAD, LONDON SW 17 9AB.

Send stamp for our free 36 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.



## Wilmslow Audio

**THE firm for speakers!**

**SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.**

AUDAX ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GOODMAN'S ● HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● TANNOY ● VIDEOTONE ● WHARFEDALE

## WILMSLOW AUDIO (Dept. EE)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street  
Speakers, Mail Order & Export 0625 529599 HI-FI 0625 526213

# LIGHT PLUS BELL

By E. Vaughan

## ECONOMICAL 2-WAY SIGNALLING CIRCUIT

**T**HE SIMPLE project described here came about due to a situation which arose at the author's home. It was suggested that it would be a good idea to have a small light over the front door number, but without the trouble of another pair of wires running around the house. At the same time, it was decided not to use batteries.

Although originally intended for this purpose, the idea of sending two sets of conditions down a single pair of wires could have other possibilities.

### CIRCUIT DESCRIPTION

The circuit for the device appears in Fig. 1. It was decided to use the only pair of wires available, and these were in fact for an electric bell. Many of the components in the circuit, will probably already exist. Components such as T1, WD1 and S1 will form the normal front door bell set-up.

Assume for the moment that diodes D1, D3 and the bell WD1 are not in circuit. A circuit therefore exists via LP1/LP2, D4 and D2, thus the bulb illuminates but only on negative portions of the a.c. produced by the transformer. Now with the other components,

a circuit exists when S1 is pressed, but will only work on positive portions of the a.c. waveform. In effect, the diodes are being used in pairs, to *steer* both positive and negative voltages in the required directions.

Think of it another way. Assume that the a.c. waveform has gone positive, D1 conducts and passes this current via WD1 to the junction of D3 and D4. The current cannot go via D4, as this diode will be reverse biased. The only route for the current is via D3.

### COMPONENTS

#### Semiconductors

D1-D4 IN4002 rectifiers (4 off)


#### Miscellaneous

T1  
WD1  
S1

Part of the existing electric bell system

LP1, LP2 Type depends on the secondary voltage of T1 and size and shape required.

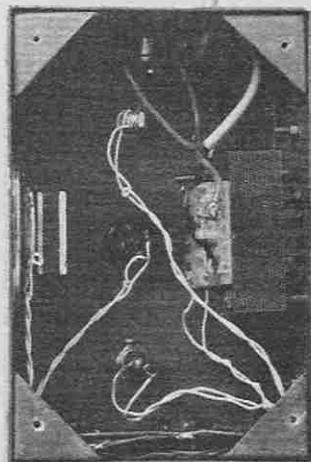Approx cost £1.25 Guidance only excluding bell circuit and case



The prototype unit used to prove the circuit.

A similar situation arises when the a.c. goes negative; D2 conducts, D3 is reverse biased and the current passes via D4 to light the bulbs.

Lamps LP1 and LP2 are the additional lamps fitted over the front door number.


### CONSTRUCTION

It is left to the reader to decide how best to wire the circuit. The diodes at the transformer end can easily be fitted somewhere inside the transformer. Those at the bell-push could even be wired inside the switch itself. The only extra wires that are required, are from the bell-push to the lamps.

The photograph shows the author's prototype demonstration unit, which was used to prove the circuit. It is not therefore necessary to construct the unit exactly as per the photograph.

Once constructed the circuit will prove to be trouble-free in operation, and will have solved quite a common problem; that is, getting four down two!

Fig. 1. Circuit diagram of the two-way signalling circuit.

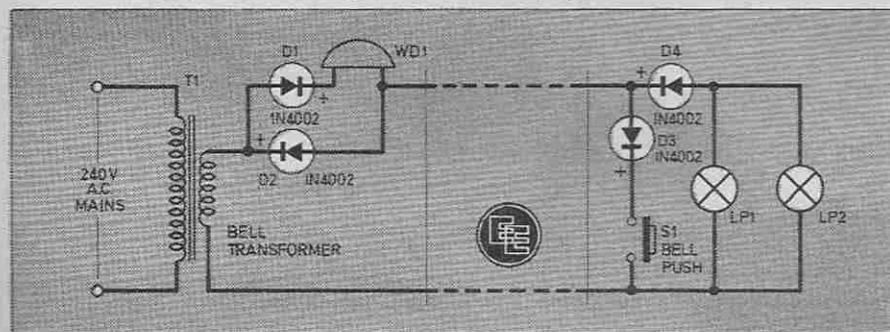

THE FIRST MAN ON THE MOON WHO WAS  
 AMERICA? THE FIRST PERSON  
 HOW WAS HE KILLED IF HALF  
 ROBIN? THE TITANIC  
 K MINISTER? WHEN T  
 TITLE OF WATERLOO? A FURLONG? WHY DO THE

# Quiz

## referee

By A. P. Donleavy

**T**HE UNIT to be described here can be used by a quiz-master to referee more fairly a contest between two individual players or two teams. Each team is provided with a button or buttons to press when an answer to a question has been found. By means of two light emitting diodes the unit displays whichever team has answered first.

A timer is incorporated which allows a preset time in which the answer must be offered. If no replies have been given during this time, the unit will automatically prevent any further pressing of the buttons from illuminating the l.e.d.s.

The unit is very easy to build and should be ideal for the beginner.

### CIRCUIT DESCRIPTION

The complete circuit for the Quiz Referee is shown in Fig. 1 and can be conveniently split into two sections: a timer and flip-flop.

#### Timer

The timer part of the circuit is formed by gates G1a and G1b of IC1. Together they form a monostable multivibrator, the timing interval being dependent on the values of VR1 and C1. With the values given, a maximum time of about 40 seconds is obtained.

To set the multivibrator in operation a momentary depression of S1 applies the positive supply to one input of G1a. This is quite sufficient to start the circuit. When

it is desired to stop the multivibrator a short depression of S2 inhibits the charging action of C1 thus stopping the multivibrator.


Gate G1c is used merely to invert the signal applied to IC2. During the timing period, the light emitting diode D1 is extinguished. At the end of the time it illuminates, thus alerting the user that "time is up".

#### Flip-Flop

The flip-flop part of the circuit is IC2 and associated components. There is in fact two separate flip-flops in this i.c., one for each player or team. Consider just one, Flip Flop 1.

During the timing period, the input to the SET terminal, pin 6

Fig. 1. Complete circuit diagram for the Quiz Referee.

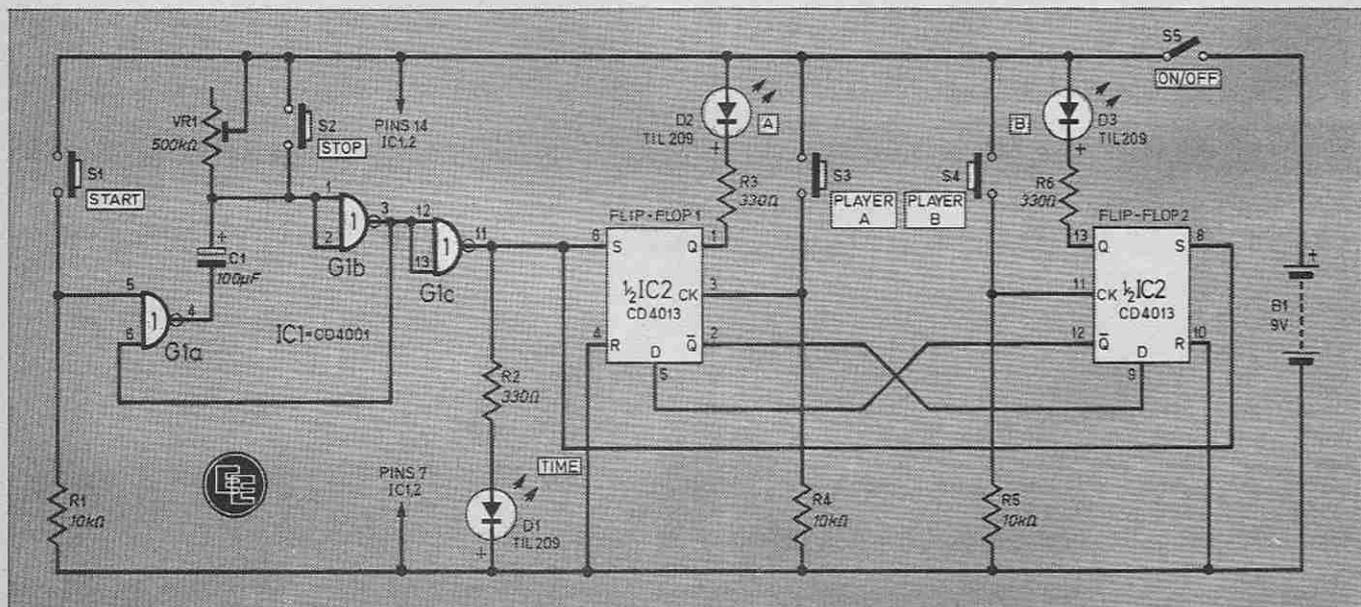

is normally low. When S3 is pressed, a pulse is applied to the clock terminal, pin 3. This causes the flip-flop to change state, producing a low output at pin 1 and a high output at pin 2. The low at pin 1 illuminates D2 thus indicating that player A has answered the question first. At the same time the high condition at pin 2 is applied to pin 9 of Flip Flop 2 preventing it from changing state if player B presses his button.

Precisely the same happens if player B presses his button first, this time however it is Flip Flop 2 which changes state and Flip Flop 1 which is inhibited. The circuit is quite precise at recognising which button is pressed first, a time difference of less than a micro-second is average.

At the end of the timing period the inputs to pins 6 and 8 of IC2 go high turning off whichever l.e.d. is on, and also prevents either flip-flop from changing state with further depressions of S3 or S4. If a further question is to be asked before the end of the timing period, the stop switch is pressed thus ending the timing and resetting the flip-flops.

Although S3 is shown as a single switch it may be paralleled with as many as required depending on the number in each team. The same applies to S4.

## CIRCUIT OPTIONS

If the timing section of the unit is not required then all the components to the left and including D1/R2 may be omitted. If this is done the flip-flop part of the circuit


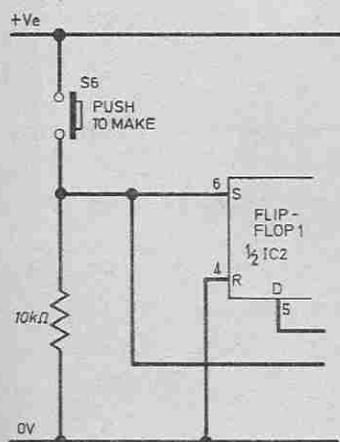


Fig. 2. Modification required to the circuit of Fig. 1 if the timing period option is not required.

## HOW IT WORKS

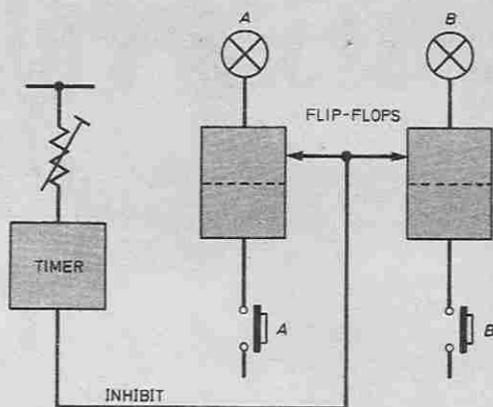

The unit consists of two flip flops, one for each player or teams. A flip flop is an electronic circuit which has two stable states; a short clock pulse applied to the input will cause the device to change state. In this circuit, if player A presses his button the flip flop will change state and illuminate the light. At the same time a second output from the flip flop will inhibit player B's flip flop.

Thus the circuit detects who was first in pressing his own button. At no time however will both lights be on, due to this "cross coupling" between flip flops. A further refinement to the circuit is a timer which only allows the flip flop to operate during a certain preset time, after which they are inhibited.

will require a reset switch. The circuit of Fig. 2 shows how this is done. The remainder of the circuit remains the same as in Fig. 1.

In the prototype, VR1 was a small preset mounted on the circuit board. This could easily be replaced by a standard potentiometer mounted on the case. If it is fitted with a pointer knob, a scale can be drawn and be directly calibrated in seconds.

## COMPONENTS

Although the two l.e.d.s D2 and D3 are both coloured red, it may be an advantage if different colours were used. The push switches as used on the prototype were miniature types, although larger types such as bell pushes will be more suitable. The unit is powered by a 9V battery, although the circuit will work with any voltage in the range 3 to 15V. If different voltages are used then it may be necessary to adjust the values of R3 and R6 to compensate for the varying brightness in the l.e.d.s.

Both i.c.s are of the CMOS type and as such must be handled with care. The use of sockets is recommended although they were not used on the prototype.

**COMPONENTS**  
approximate  
cost £5



# Quiz referee

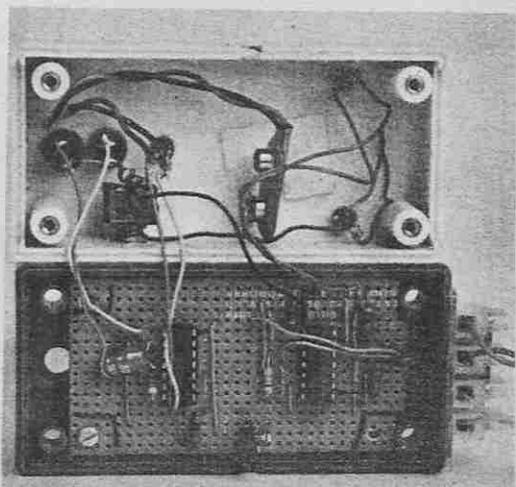
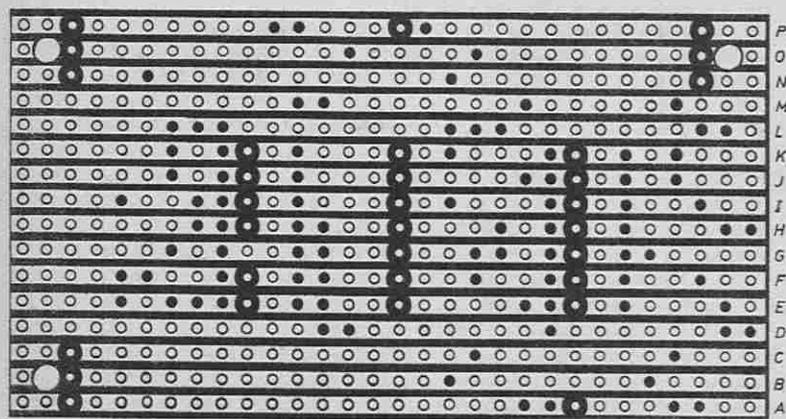
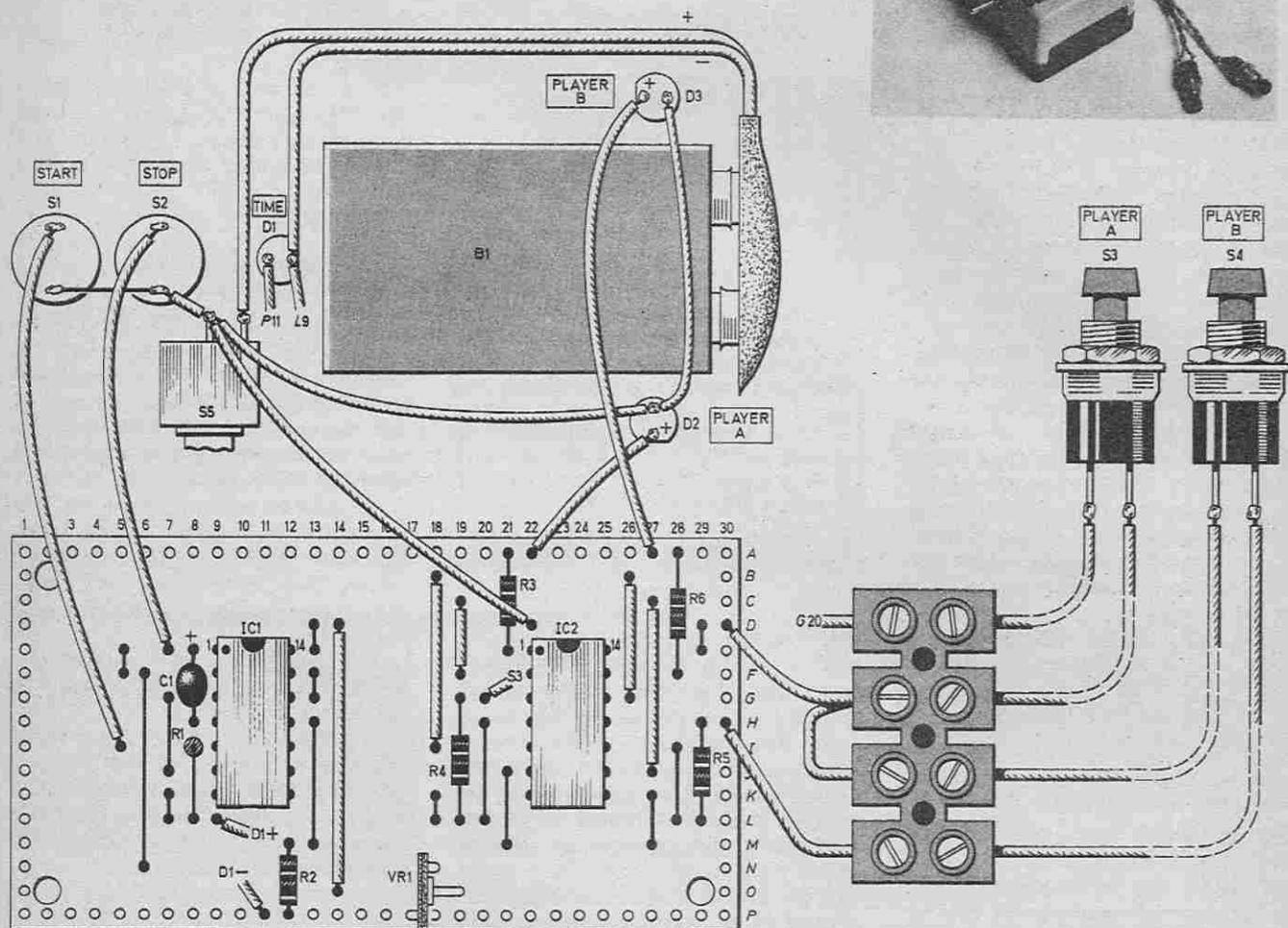


Fig. 3. Complete wiring details for the unit, also showing the stripboard and breaks to be made. There is nothing critical about the layout and can be varied if required.

The prototype Quiz Referee with lid removed showing the mounting of the component board.

# CONSTRUCTION starts here

Most of the components are mounted on a piece of 0.1 inch matrix stripboard having 16 strips by 30 holes, the layout of which is shown in Fig. 3. This drawing also shows the remainder of the wiring to the switches and l.e.d.s.

## CASE

The case used in the prototype was a small Verobox type 65-2516G, having overall dimensions of 100 x 50 x 40mm, although any similar size can be used. However it must not be significantly smaller as the components might not fit in.

The l.e.d.s can be simply a tight push fit into their respective holes or standard mounting clips can be used. The battery is fitted to the lid using double sided sticky tape. A small plastic connecting block is screwed to one end of the case facilitating connection to the push switches.

Lettering can be applied using Letraset or similar and finally given a thin coat of protective clear varnish. Ordinary twin bell wire can be used to connect the push switches to the unit. Be sure to identify which is player A and

## COMPONENTS

### Resistors

- R1 10k $\Omega$
- R2 330 $\Omega$
- R3 330 $\Omega$
- R4 10k $\Omega$
- R5 10k $\Omega$
- R6 330 $\Omega$

All  $\frac{1}{4}$ W carbon  $\pm 10\%$

### Potentiometers

- VR1 500k $\Omega$  vertical preset

### Capacitor

- C1 100 $\mu$ F 10V tantalum

### Semiconductors

- IC1 CD4001 quad 2-input NAND gate
- IC2 CD4013 dual "D" flip flop
- D1, 2, 3 TIL209 red light emitting diode (3 off)

### Miscellaneous

- S1-4 miniature push-to-make release-to-break (4 off)
- S5 miniature single pole toggle
- B1 9V PP3 battery
- Stripboard 0.1 inch matrix, 16 strips by 30 holes; Verobox type 65 2516G, 100 x 50 x 40mm or similar; PP3 battery connector; 14 pin i.c. sockets (2 off); 4-way plastic connecting block; 8 metres thin bell wire; connecting wire.

See  
**Shop  
Talk**

page 499

which is player B! Depending on the situation in which it is to be used a length of four metres for each set of switches seems reasonable.

## IN USE

Before finally screwing the lid into place, VR1 will have to be adjusted for the time period required (assuming that a preset is used). Do this by switching on the unit whereupon D1 will light. Press S1 and D1 will go out for the duration of the timing period. Adjust VR1 by trial and error until you obtain the required time interval.

If a panel mounting potentiometer is used then the above process is carried out, but after each time period, a mark is made on a scale around VR1.

After the unit has been calibrated it is ready for use. Switch on by means of S5 and press the START button. The TIME l.e.d. will go out indicating that the timing period is running. If now either S3 or S4 is pressed, the appropriate l.e.d. will light, and will go out at the end of the timing period, whereupon the TIME l.e.d. will come on once more.

If another question is to be asked before the end of the time, the STOP switch is pressed terminating that period, and the START switch pressed to start a new timing period.

If an answer is given after the end of time, no l.e.d.s will come on, indicating to the players that they have failed. The unit is then reset and a new timing period started.

If the timing part of the circuit is not used then the unit becomes a simple precedence detector with a reset switch, S6.  $\square$

### Subscription Rates

## Everyday ELECTRONICS

U.K., Isle of Man,  
Channel Islands  
and the Irish Republic. £8.50

U.S.A. & Canada (\$19.00) £9.50

Other Countries £9.50

Money Orders, etc., should be made payable to IPC Magazines Ltd.

Subscription Applications must be accompanied by payment.

IPC Magazines Ltd., Regd. Office:  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Regd. No. 53626  
England.  
A subsidiary of  
Reed International Ltd.

## MAGAZINE SUBSCRIPTIONS MAKE IDEAL GIFTS

You can order magazines covering a wide range of interests for friends or relatives at Home or Abroad.

Tick this box   
and we will send you details of all IPC Magazines available by Postal Subscription.

## Everyday ELECTRONICS

### SUBSCRIPTION APPLICATION FORM

Please send EVERYDAY ELECTRONICS by post for 1 year to the address below:

Name..... Please print

Address.....

I enclose payment of £..... Signed:.....

Send this application form, with payment, to:  
Room 2613 King's Reach Tower, Stamford Street, London SE1 9LS.  
Allow 4 weeks for processing.

Newnes

# constructors projects



- ☆ More books in our series for the electronics enthusiast.
- ☆ There are now eight titles available at £2.25 each (US \$5.25)

Electronic Projects in the Workshop *R.A. Penfold*

Electronic Projects in the Car *M. George*

Electronic Projects in Music *A.J. Flind*

Electronic Game Projects *F.G. Rayer*

Electronic Projects in Audio *R.A. Penfold*

Electronic Projects in the Home *Owen Bishop*

Electronic Projects in Hobbies *F.G. Rayer*

Projects in Radio and Electronics *Ian R. Sinclair*

Each book contains a collection of constructional projects, giving details of how the circuit works, how it may be assembled and how setting-up and trouble-shooting problems may be solved. The skilful use of colour in the text helps to clarify circuit operation, and circuit board layouts are suggested. Shopping lists of components are included.

Write for a free colour brochure about all our hobby books to

## Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH



### New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

### New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.


Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself - computers, oscilloscopes, transceivers etc. . . . Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451). Registered in England, No. 606177.

Soldering iron offer FREE

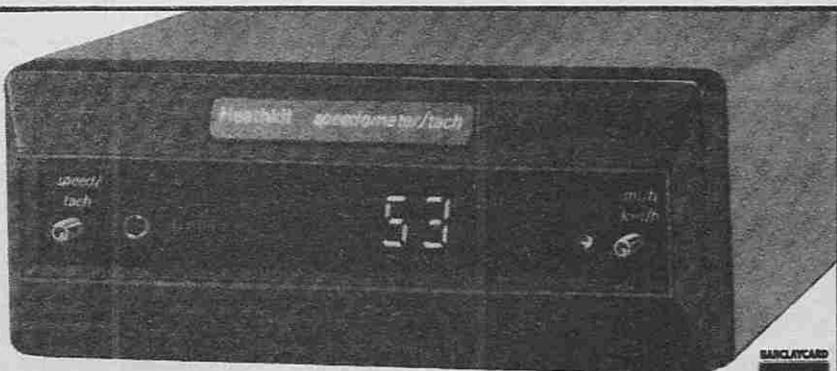

### New Heathkit CI 1265 Digital Tach/Speedometer.

Push-button digital readout. Displays engine speed/rpm. Accurate to 1 mph or rpm variations of 100.



To: Heath (Gloucester) Limited, Dept. EE8/79 Bristol Road, Gloucester, GL2 6EE.  
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.

Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name \_\_\_\_\_

Address \_\_\_\_\_

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

When you receive your catalogue you will get details of this free offer.



# HEATHKIT

HEATH  
Schlumberger

# MICROPROCESSOR BASICS

By R. W. Coles

THIS month we complete our look at Instruction Types, and then discuss Addressing Modes.

## TRANSFER OF CONTROL GROUP

Most programs are written in the form of "loops". This means that instead of starting at the beginning, working through to the end, and then "dropping-off", at some point control is transferred back to near the start of the program so that the program operations are repeated. Programs also contain many "minor" loops which make more efficient use of program memory than would be possible with in-line code.

Have a look at Fig. 6.1. This is a very simple program to demonstrate the action of loops. It does not do anything useful as it stands, but it is typical of the structure of other programs which are useful.

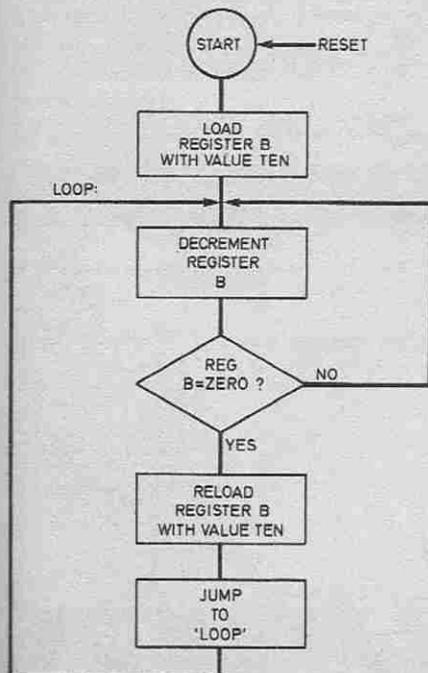


Fig. 6.1. Example of conditional and unconditional jump instructions.

The program is shown in "flow-chart" form. This is a useful way to sketch out programs before finally coding them for entry into a micro' system, and is a big help in visualising program operation. This program does nothing more complicated than count down from 9 to 0 in a register I have called register B.

After reset, register B is loaded with the value 9 (decimal) which is 9 (hexadecimal) and 00001001 (binary). After this we enter the main loop and start by decrementing (counting down by one) register B. After the first decrement, register B will contain the value 8, and so on.

**Conditioned-jump.** Now we come to the important bit, the transfer of control operation, and in this case we have what is known as a "conditional-jump" instruction. When this instruction is carried out, program flow can continue from one of two points depending on the contents of register B.

If register B contains zero then the next instruction in sequence is carried out, but if it contains a number other than zero, then control is transferred back to the location known as LOOP.

In this way, microprocessors can be programmed to take decisions on the basis of data supplied to them, and this is a very important ability indeed. An SC/MP instruction which could be used in this program is:

**JNZ (Jump if not zero).** Add to the contents of the program counter the data following this instruction if the accumulator does not contain zero. (The data can be negative.)

**Unconditioned-jump.** On nine occasions out of 10, our program will loop. On the tenth pass, the contents of register B will reach zero and when this happens we reload register B with 9 (decimal).

Since the program must continue to run, we now need to get back to the start of the loop once more, and so we use an instruction which performs an "unconditional-jump" or in other words "jump-always." An SC/MP instruction to do this is:

**JMP** Add to the contents of the program counter the data following this instruction. (The data can be negative.)

Notice that the program of Fig. 6.1 will not stop until the "Reset" button is pressed or power is removed. Many control programs operate in this way.

**Jump to subroutine.** Another very important transfer of control operation which is unfortunately not available on the SC/MP chip is the "jump to subroutine". This is very useful where we have a small program segment, let's say a multiplication routine, which has to be used in several places in our main program. Rather than repeat it each time we need it, the multiplication routine can be entered once and accessed from anywhere in the main program using a "jump to subroutine" instruction.

If you have a look back at the action of the two jumps from the SC/MP instruction set you will see that in each case the contents of the program counter are modified by new data. The old contents are destroyed by this replacement, but not when a "jump to subroutine" is carried out. In this case the previous contents are saved in a special register or RAM area called "the stack", so that they can be retrieved later when required.

**Return from subroutine.** To complete the picture we need another instruction often called a "return from subroutine", which has the effect of restoring the original program counter contents after the "multiply" has been performed.

The return from subroutine does not cause a jump to a specific address, but to the address which was saved on the stack, whatever it was. This means that our "multiply" can be called from several points in a program, and control will always be passed back to the area from which the call was made.

**Nesting.** Taking this a stage further, most microprocessors allow subroutines themselves to call other subroutines and so on. This requires a multiple entry "stack" so that control can be passed back from one subroutine to the next until a proper return to the main program is made. This is known as subroutine "nesting", a very powerful and efficient technique.

## MISCELLANEOUS GROUP

After removing the instructions which fall neatly into the other groups, there will always be some left over. Since those remaining form a rather rag-tag bunch, it's easiest to call them the "miscellaneous group"! Examples from SC/MP include:

**CCL** Clear the carry flip-flop to zero.

**NOP** Don't do anything at all.

**DLY** Don't proceed until a given delay count has been decremented to zero.

## ADDRESSING MODES

Many instructions need access to data in memory. This is not only

true of data transfer instructions such as LD, but also of others such as OR and ADD. To provide flexibility, many microprocessors allow a variety of memory addressing formats to be used, in some cases ten or more memory reference modes are available. It is possible to write successful programs using only a few of the available modes, and some of the more exotic combinations certainly won't appear to have obvious applications until you are adept at the programming art!

To make the whole business a bit less complicated I have decided to look only at the more basic modes. Such goodies as "indirect-indexed-addressing" (used by the 6502 microprocessor), can wait until later!

**Immediate Addressing.** This is easy, the data is stored immediately after the instruction itself. This mode is useful for loading constants.

**Direct Addressing.** Still easy, the data can be found at the address given after the instruction. For an eight-bit microprocessor direct addressing will usually mean a three-byte instruction, one opcode byte and two address bytes. Any address in memory can be specified, and this mode is ideal for access to variables. This mode is not available with the SC/MP chip.

**Indirect Addressing.** A bit tricky, the address following the instruction points to a location where the address of the data can be found.

The location holding the data address can be in RAM or it can be an on-chip register. This mode is useful for stepping through tables of data in memory, and for "looking up" an entry in a table.

One particular variation on the indirect-addressing theme is that of indexing. In this case special registers called Index Registers are used to hold all or part of the data address, and microprocessors with these facilities are capable of very fast data transfers from one area of memory to another. The SC/MP pointer registers can be used for indexing if required.

**Relative Addressing.** This mode of addressing is used with transfer of control instructions only. The destination of a jump is specified as a displacement from the current program counter value. This is like the jumps we looked at earlier because what happens is that a displacement value (usually one byte) is added or subtracted from the current program counter-value. The resultant jump is therefore "forwards *n* bytes" or "backwards *n* bytes", rather than to an absolute address.


## THAT'S IT

Well, that's all there is to it. All you have to do now is to put the theory into practice by writing some programs of your own. If you really *do* feel inclined to try it, there are a few practical hints on how to set about the job in last month's *Microprofile* feature.

To be continued

## JACK PLUG & FAMILY...

BY DOUG BAKER

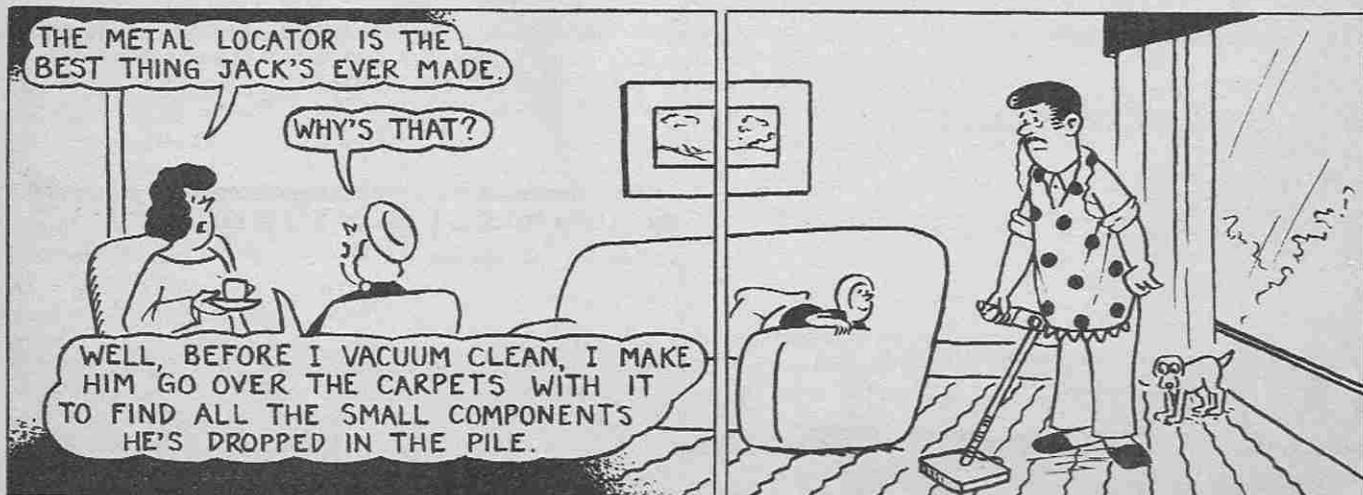

# Simply ahead!

HIGH PERFORMANCE MODULAR UNITS  
BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE

30 WATTS R.M.S.  
INTO 8 OHMS

I.L.P POWER AMP  
MODEL HY50

PROFESSIONAL  
FINISH

ENCAPSULATED FOR  
OPTIMUM THERMAL  
STABILITY

EXTRA RUGGED  
CONSTRUCTION

SHORT/OPEN  
PROTECTION

ONLY 5 SIMPLE  
CONNECTIONS

NO EXTRA HEAT  
SINK NECESSARY



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build or up-grade a hi-fi system, run a small high quality P.A. system, amplify a musical instrument (say for practise or small range use) or use it for lab work. Its useful 30 watts RMS output into 8ohms, its rugged construction and freedom from heatsink worries make HY50 the ideal all-purpose quality power amp—and it is unconditionally guaranteed for five years. Ten of thousands are in use throughout the world

... and a spec that means what it says!

Encapsulated power amp with integral full-rated heatsink. Input—500mV.  
Output 30 watts RMS/8Ω.  
Load Impedance—4 to 16Ω.  
Distortion—0.04% from 100mW to 25 watts at 1KHz/8Ω.  
Supply Voltage ±25V. Size 105 × 50 × 25mm.  
Inc. V.A.T. and postage in U.K. £8.15

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensures world leadership for I.L.P. Now we have up-graded output ratings and down-graded prices to bring I.L.P. within easier reach of all who want the best.

New production techniques enable us to reduce prices by an average of 20%, making I.L.P. a better buy than ever.  
**USE OUR FREE POST SERVICE** for sending your orders, requests for information sheets etc. Simply address envelope. No stamps required.

**ILP**  
ELECTRONICS LTD.


FREEPOST 3

Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP  
Phone (0227) 54778

Everyday Electronics, August 1979

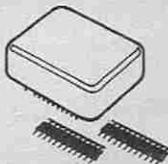
## OTHER UNITS IN THE RANGE

OTHER UNITS IN THE RANGE  
All prices inc. V.A.T. & Postage in the U.K.


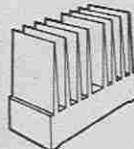
### HY5 PRE-AMPLIFIER


Compatible with all I.L.P. power amps and P.S.U.'s in a single pack, needs external pots and switches. Multi-function equalization. 5 inputs. High overload margin. Active tone controls, 500mV out. Distortion at 1 KHz—0.01%. Two connect easily for stereo. £5.22


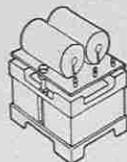
### THE POWER AMPS

With heatsinks, full load line and thermal protection. Distortion typically 0.05% at 1 KHz.

HY120 60 Watts RMS/8Ω 114 × 50 × 85mm £16.42  
HY200 120 Watts RMS/8Ω 114 × 50 × 85mm £18.92  
HY400 240 Watts RMS/4Ω 114 × 100 × 85mm £29.89



### THE POWER SUPPLY UNITS

(Split line outputs to suit I.L.P. power amps and HY5)

PSU50 for 1 or 2 × HY50 £9.11  
PSU70 for 1 or 2 × HY120 £14.70  
PSU90 for one HY200 £14.70  
PSU180 for one HY400 or 2 × HY200s £24.80

★ NOW-PRICES DOWN BY 20%

Please supply .....  
Total Purchase Price.....  
I Enclose Cheque  Postal Orders  Money Order   
Please debit my Access account/Barclaycard Account number.....  
Name .....  
Address .....  
Signature.....  
FP3/7.....  
Reg. Bus No. 1032630 Eng.



# RUMMAGING AROUND

with Keith Cadbury

**M**MUCH has been written in this magazine and its contemporaries concerning the production of printed circuit boards. It occurs to me that the reason we so often read how easy it is to make our own "one-off" p.c.b.s, is that so many beginners are hesitant to try for themselves. Such was certainly true in my case: over a year elapsed before I ventured to make my first p.c.b. in spite of a well-known lack of reticence!

Those among us who have delayed attempting p.c.b.-making by reason of limitations imposed by a strict budget may find encouragement from various cost-cutting ruses that have helped me.

The basic "ingredients" you will need are: a method of laying an etch-resistant image on to the copper-clad board; etching solution a tray or dish to hold the board and solution; a suitable piece of copper-clad board and something to clean it with; and (for finally preparing the board when etching is complete) a method of drilling 1mm holes in the p.c.b.

Maybe I am biased, having been using Letraset-type of products for graphic design since the days when it involved a gauze frame and water, but I have found that the rub-down transfer method of producing an etch-resistant image by far the best.

A set of suitable transfers can be purchased for about £2, or an extra economy would be to purchase a sheet of various pads, corners, etc., plus a sheet of straight lines.

Graphic designers do not usually use a ball-pen to transfer the image, as a nylon or polythene rubbing-tool is available for a few pence from any decent art shop that stocks rub-down lettering. If you cannot locate such a device (and I do not know of any mail-order electronics supplier that offers it), then use a ball-pen as the only alternative. But to avoid getting the sheet in an awful mess, use an old pen that has run-out of ink.

You will of course have cleaned the copper side of the board thoroughly before laying the image—a sheet of fine abrasive paper, such as "flour-paper" is an easy way.

I have tried producing the circuit image completely freehand, with an etch-resistant pen, and also using rub-down pads and the pen for lines only. Neither to my mind was as satisfactory as the exclusive use of rub-down transfers—the pen lines may be a lot quicker to apply, but are never so clear-cut and well-defined, and I have found that the pen lines are inclined to spread just enough to make checking the finished boards of "tight" circuits a drudge.

Large areas of board that require to remain copper-clad can be covered with plastic tape.

If you are a photographer who makes his own photographic prints, you will own dishes suitable for holding the etching solution, if not, the cost of developing trays from a photographic shop will hasten the selection of an alternative.

A plastic carton from the freezer is ideal—failing which, treat the family to two litres of ice-cream, at a cost of about £1. If you are impatient to use the plastic carton and the family will not oblige by consuming vast amounts of the stuff immediately, I suppose you could transfer it to other suitable receptacles, like jam jars.

I have never attempted to mix etching fluid from anhydrous ferric chloride crystals and water, indeed, my local electronics shop does not stock it. The etching fluid available ready-mixed, in plastic bottles of about a half-pint has sufficed to date, and I hear from

some other enthusiasts that mixing the crystals and water is a messy and time-consuming operation.

I have calculated that I etched about 200 square inches of board with one bottle of etching fluid, at which rate it is quite viable to forgo one's own mixing.


If you feel the need for tongs of some sort, to remove the p.c.b. from the fluid, do not of course use metal ones. Plastic tongs can be made by cutting a plastic bottle, of the type often used to hold indigestion preparations. See diagram.

The satisfaction derived from producing your own p.c.b.s, rather than buying a board from a manufacturer (in the case of a published project) is not the only reason for attempting your own etching. The board layout can easily be adapted from the drawings published, to use alternative components, or to incorporate additional circuits.

If your design doesn't work you have got a problem, but checking your diagram against the p.c.b. can be an absorbing past-time—it is when things go wrong that my young children learn new words with which to impress the vicar and his wife.

I have not yet found a make of rub-down lettering that is not etch-resistant, so for the cost of a suitable sheet of small lettering, you can also etch your initials, or a name or some other circuit recognition, to make the finished board more professional-looking.

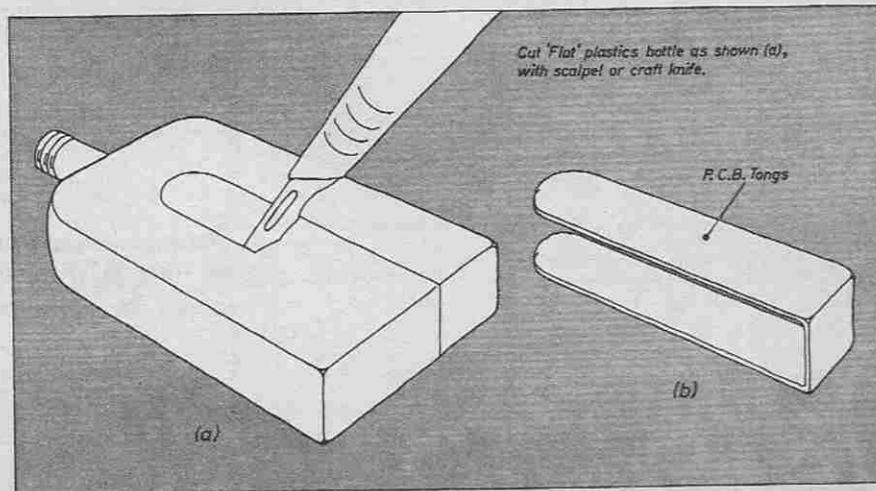It only remains to drill the p.c.b. before inserting the components, and if you have to date used a hand-drill, or the normal do-it-yourselfer's electric drill, next months RA could be written especially for you.




Cut "flat" plastic bottle as shown (a), with scalpel or craft knife.

P.C.B. Tongs

(a)

(b)
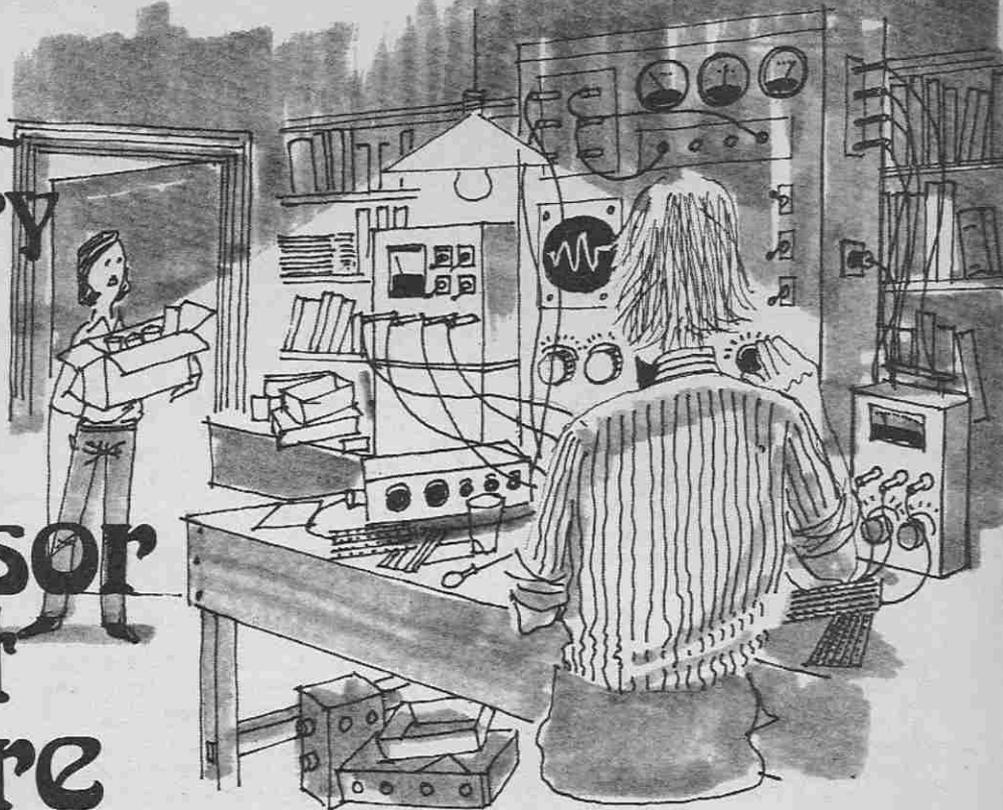
# The Extraordinary Experiments of Professor Ernest Eversure



by Anthony John Bassett

**B**OB AND the Prof. have been discussing the various aspects of energy carrying beams. Just at that moment a warning bleep sounded inside the helmet of the Prof's spacesuit, and a message appeared on a nearby computer viewscreen.

"Time to renew our life-support system, Bob, and as the display indicates that we are expecting visitors, perhaps we'd better take off the space suits and let the robots recharge them."

## VISITORS

So it happened that the visitors, Tom and Maurice, were just in time to see Bob and the Prof. stepping out of the airlock of the vacuum chamber still dressed in their amazing space suits. The Prof's experimental robots helped them out of the suits, as Bob's friends Tom and Maurice watched astounded, the robots whisked the suits away for recharging.

"Prof.," whispered Tom, gradually recovering from his surprise, "were those real robots and real spacesuits, or were we dreaming?"

"They were real, Tom," the Prof. assured him, "Bob and I have just been doing some experiments with energy beams in a simulated space environment."

## SPACE AGE ROCK

"That's great, Prof.," Maurice broke in, "Tom and I are forming a Space Age Rock Band and the members of the band want to dress up as robots and spacemen and to have all sorts of electronic equipment, amplifiers, sound effects, synthesisers, electronic drums and percussion."

"Yes!" said Tom, "a real show-band offering comprehensive entertainment with as many weird and unusual musical instruments and effects as possible, unusual lightshows, strange sounds, anything we can manage to get on stage, almost to give an image of modern and futuristic technology along with the basic instruments and equipment to produce good music!"

"Trouble is," said Maurice, "we've got much more enthusiasm than 'know how' and we're starting almost from scratch. Also as we'll be playing mainly for charities, with only a few paid bookings, we can't afford anything expensive. Some of our friends in more well-to-do bands have let us have their old equipment, but most of it is in need of repairs."

"We're hoping that your knowledge of real robots, spacesuits and gadgets can be brought to a more

down-to-earth use and that you will be able to help us with some technical advice on equipment for the Band!"

"I see," said the Prof., "it seems that you would like me to advise and help you with almost all the technical aspects of the equipment of a band, right from the beginning! Rather interesting, as your band seems to have some special requirements."

## WAH WAH

"I'm keen to help with this too," Bob remarked, "It will be good practice for me and I'd like to learn a lot more about Band equipment and electronics! By putting in some work on repairs, and construction of new equipment, I'll gain experience, and by saving the band some money, this will help the charities they work for!"

Maurice dug into his huge duffle-bag and brought out a variety of small items of band equipment, a fuzz box, wah wah, reverberation unit, microphones, and amplifier.

"Your duffle bag seems bottomless!" the Prof. was amazed at the quantity and variety of bits and pieces which Maurice was in the habit of carrying around.

"These are some of the things we got as the result of a charity



## IT'S FREE

Our Monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—It's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

### EX GPO TELEPHONES

Normal black desk instrument with dial and internal bell, latest type £2-85 each, preceding type £4-05 each.

### TELEPHONE SWITCHES

Desk mounting. These are the older, winking eye type almost becoming museum pieces. Prices depend on condition starting at £15 + £1-20 plus carriage at cost.

### BLOWER BARGAIN

Smith's Industries—mains operated blower/fan—a real air mover that takes up very little space as it's balanced four pole motor is let into the air turbine—overall size approx 7" diameter by 2 1/2" thick. Suitable for drying—blowing extraction, air circulating etc etc only £4.

### THREE MORE TRANSFORMERS

TM54 This is an upright mounting—varnish impregnated, it has a main secondary of 200v/500mA and another of 6.3v 1amp price £4-50 + 34p post £1.  
TM55 Again upright mounting and impregnated, this one has two secondary windings, both 12v 5amp so it can be used as 12v 10amp—24v 5amp or 12-0-12 @ 5amp, price £4-95 + 40p post £1.25.  
TM56 One secondary of 4v 2amp—this is quite a small transformer and could also be used as a 80-1 matching transformer for microphone etc, price £1-50 + 12p

### TANGENTIAL BLOWER

Metal blades—mains powered super silent unit with dozens of applications, cooker hoods—fume extractor—blower heater—fresh air impeller etc. Air outlet is rectangular size approx 10 1/2" x 2 1/2" £3-95.

### WANT LOW VOLTAGE MAINS AND ISOLATION

A 10 watt £2-10, 35 watt at £4. Larger sizes on request.

### MODEL MOTORS

We have at least 150,000 small battery operated motors in stock, mostly Japanese made and good quality, all will work on 3 volts upwards, some will work from single 1 1/2 volts cell, some are very small and the smallest requires no on/off switch as it won't start until it is spun and when it stops it will get into a no current position if possible. The largest is powerful enough to operate a hand drill. We have a leaflet which briefly describes these but if you're contemplating making a toy or a novelty needing a motor then send £2-50 for our assortment of 8 motors—find the right one for your project—we will supply this at a special quantity discount.

### NOW SOME BIGGER 12 VOLT MOTORS

12V MOTOR BY CROUZET—a powerful motor virtually impossible to stop by hand, size approx 1 1/2" long and 2 1/2" dia, this is a permanent magnet field type so is reversible simply by changing polarity and has a relatively constant speed with or without load. Fitted with a splined shaft which could directly engage a toothed gear wheel or to which a pulley could be attached. Ideal for large models, or small machines etc. Price £4-25.

### 12 VOLT MOTOR BY SMITHS INDUSTRIAL

Made for use in cars these are series wound and become more powerful as load increases—they will in fact burn themselves out if over loaded to stopping point—reversible by rewiring. Being series wound they will also work off a.c. mains through a step down transformer and if you use a variable voltage type then the motor speed can be varied by the voltage.

Size approx 3 1/2" long by 3" dia these have a good length of 1" dia spindle—price £3 + 24p. Ditto but double ended £3-95.

### MAINS OPERATED LOW SPEED MOTORS

Type as fitted into time switches etc—we have a good selection and can offer the following final speeds:  
1 r 24 hrs—1 r 8 hrs—1 r 4 h—1 r 2 h—r h—4 r h—12 r h—30 r h—30 r min—2 r min—4 r min—8 r min—15 r min—25 r min—30 r min—200 r min all at £2-95 each.

### SPIT MOTORS

These are powerful mains operated induction motors with gear box attached. Shaft is a 3/8" rod with square hole, final speed is approx 3 revs per min, price £5-25—similar motor but with final speed 110 rpm £5-15, 80 rpm same price.

### SUB MINI MICROPHONE

Size only 1/2" x 3/4" x 3/8" so small enough for a bugging device ex hearing aids but guaranteed. Price £1-50.

### SUB MINI MICRO SWITCH

American make size approx 1 1/2" x 3/4" x 3/8" changeover contacts—three types in stock, button operated 35p, lever 40p + 3p.

### MEDIUM AND LARGE MICRO SWITCHES

We have over 100,000 of them in stock at prices from 10p each—may we have your enquiries please with a sample if possible.

### DP DT TOGGLE SWITCH

Normal size, normal fixing bright plated toggle and fixing nuts—by NSF. 3amp 250v price 49p each. £35 + £2-40 per 100.

### SP DT TOGGLE SWITCH

15amp at 250v—bakelite body flat toggle—bright plated fixing nut 35p. £22 per hundred.

### WAVE CHANGE SWITCHES

We have mini types @ 40p + 5p available in the following combinations 4 pole 3 way, 3 pole 4 way, 2 pole 6 way and 1 pole 12 way.

### STANDARD TYPES

1 1/2" wafer made to your specification at £1 + 12p per wafer plus 50p + 8p for clicker mechanism and spindle. Wafers stock are 1 pole 12 way, 1 pole 10 way, 2 pole 9 way, 2 pole 8 way, 2 pole 6 way, 3 pole 5 way, 4 pole 4 way, 6 pole 3 way, and 8 pole 2 way. We can stack up to 10 wafers so could make say 10 pole 12 way or 80 pole.

### INSTRUMENT SWITCHES

These use a smaller moulded wafer size approx 1 1/4" dia—available in some combinations as standard switches price £1-50 + 19p for each wafer and 75p + 5p for clicker and spindle.

### WALL MOUNTING THERMOSTAT

By Danfoss in a really pretty two tone grey case with scale and dial. Setting temperature from 0-30c—13amp 250v contacts. Price £4-32.

### UP TO 5 MINUTE TIMER

Mains motorised, the dial of this is calibrated in 1/10th of a minute up to 5 minutes—slipping clutch motor takes preset time to travel to its stop, then it slips until switched off. Fitted micro switch operates at the stop. Micro switch could be used to make the timer repeat, switch off etc. American made—ex equipment—believed unused. Price £3-25.

### MAINS STEP-ER

Is a 24 way stud switch controlled by two solenoids. One ratchets the switch arm round one stud per impulse—the second solenoid returns the switch arm on a metal chassis size approx 4 1/2" x 3" £4-85.

### MINIATURE MAGNETIC CIRCUIT BREAKERS

will trip faster than a fuse can blow, use to control your service bench etc will save you the trouble of renewing fuses, or replace your fuse box with a line of these. Available as follows: 1amp—2amp—5amp—10amp—15amp—25amp. All same price £2-25 each.

### CASSETTE MECHANISMS

with record and playback heads, all electronics, switches and speakers. Price £8-95 (Surely this must be the bargain of the year). Stereo with heads but not electronics £14-95.

### JUNCTION BOXES

Ideal for ring main or lighting installations. Brown bakelite base and cover, 25p each or box of 12 for £2.



## 24 HOUR TIMERS VENNOR

As illustrated with sun correction made for G.P.O. phone boxes used perfect £2-95. 20 amp switching contacts.

## SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 10, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1-94—crystal earphone 55p including VAT and postage.




## 12v SIREN/BLEEPER

Makes a sound very similar to the Black & Decker smoke alarm. 6-12ac or 12-14v a.c. Ideal for fire and smoke alarm, anti-mugging device, car or motor anti-theft. American made, compact about the size of an egg. £1-35. Order Delta Bleeper. A large quantity in stock so we will be glad to quote special price for quantity user.




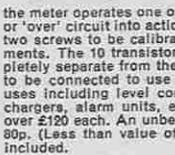
## ELECTRONIC VOLTMETER/SENSITIVE RELAY

Consists of a large, extremely readable, 4 1/2" square drop through panel volt meter, 0-0-1 'sd. Built into the front of the meter are two screw adjusters which move two separate pointers one red and one green, up and down the scale, the purpose being to set a minimum and maximum level so that when the needle falls below or rises above the preset levels a unique 'under' and 'over' circuit inside the meter operates one of two red relays to bring an 'under' or 'over' circuit into action. The scale plate is detachable via two screws to be calibrated to your own individual requirements. The 10 transistor 'under' and 'over' circuit is completely separate from the meter movement so does not have to be connected to use this as a standard 0-1 meter. Many uses including level controls, light controls, auto battery chargers, alarm units, etc. etc. Manufacturers list price of over £120 each. An unbelievable snip at £7-75 + 62p, p & p 80p. (Less than value of the meter alone). Circuit diagram included.



## BURGLAR ALARM ITEMS

- |                               |                |
|-------------------------------|----------------|
| (Circuit free on application) |                |
| Trigger mats 24in x 18in      | £2-45          |
| 13in x 10in                   | £1-95          |
| Relay 24 volt                 | 95p            |
| 9-12 volt                     | 95p            |
| Alarm Bell 24 volt            | £7-50          |
| 9-12 volt                     | £2-25          |
| Mains                         | on application |
| Reset switch, ordinary        | 45p            |
| Secret type with key          | 95p            |
| Wire—100 metres               | £1-50          |
| 24v Power unit mains operated | £5-35          |

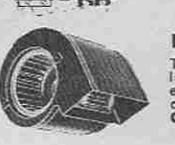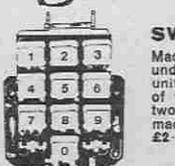

## DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3-45.

## SWITCH PAD

Made for the GPO for incorporation, we understand, in push-button dialling units, this has the usual 10 digits, each of which when depressed operates a two pole switch. Really beautifully made, size approx 4" square. Price £2-95.

## MAINS BLOWER

The Torrini—quiet but powerful outlet size 2 1/2" x 1 1/2" for cooling equipment etc. will extract if outlet is blowing outwards price £5-50. Other models from £2-00.

## 6 DIGIT COUNTER

One pulse at mains voltage moves 1 digit—not resettable—real bargain @ 80p.

TERMS: Cash with order—but orders under £6 must add 50p to offset packing etc  
BULK ENQUIRIES INVITED PHONE 01-888 1833  
ACCESS & BARCLAYCARD ACCEPTED

**J. BULL (ELECTRICAL) LTD**  
(Dept. E. E.), 103 TAMWORTH RD.,  
CROYDON CR8 1SG

## BUS BARS FOR PUSH ON TAGS Type 1

as used in cookers etc is a panel approx 3" x 2" with two hefty cable trap terminals, marked N & L and bus bars will take 12 push on tags each—useful on work bench or would help in construction of most electrical heaters etc. Price 44p. Type 2

## CONNECTOR STRIPS

Normal 12 screw down in polythene base, 3-5 amp 10 for £2, 15amp 10 for £3, 25 amp 10 for £4.

## NUMBERED CONNECTION STRIP

For 25amp cables this is very compact only 3 1/2" long, 3/4" wide. The body is not polythene but a harder material probably nylon. The contacts are numbered 1-12, useful for intercom, and similar installations. Price 10 for £4-50.

## PLUG-IN-ABLE CONNECTOR STRIP

Female usual screw downs on one side, but sprung holes on other. Male pins screw down one side and plugs on the other. The plugs are tightly gripped by the sprung holes. Female portion is available in strips of 3 connectors 16p or 12 connectors 50p. Male portion only in strips of 3 connectors price 25p. 600 OHM WIRE WOUND RESISTOR 15 Watt type, 10 for £1.

## SPRING FIXINGS FOR 15 WATT RESISTORS

Specialty shaped spring clip pushes into resistor, 20 for £1.

## FUSE HOLDERS

For 20mm fuse. Chassis mounting, polythene base with hole for fixing. Strips of 10. Price 54p.

## THYRISTOR TRIGGER MODULE

By Mullard their MY5001, brand new in maker's sealed packing. Price £5-50.

## NOVEL 50HZ FREQUENCY CHECKER

For checking frequency of invertors etc, is a frequency controlled motor with reduction gear box—simply fit a cardboard disc to spindle, connect direct to the unknown supply—if 200-250v if not use a transformer—if the disc revolves at 16 r.p.m. then supply is correct frequency if less than 16 r.p.m. it is slow, if more than it is fast. Price £1-50 + 12p.

## SERVICEMAN'S LEAD ASSORTMENT

More and more appliances, we have tags and to quickly hook these up you need lead. We offer an assortment of twenty leads ending with push on connectors, all for £1-08 will save their cost in no time.

## KETTLE LEAD AND PLUG

Fits all normal kettles: a robust plug with a good length of heavy duty three core lead. Price 85p, 10 for £8.

## HEAVY DUTY RELAY

With twin 20amp changeover contacts, coil voltage is 24 volts D.C. or 50 volts A.C. Four of these with coils in series could be used to switch lighting etc. Price 88p.

## MAINS OPERATED CONTACTOR

Beautifully made in West Germany, this has 3 poles switching on, and a fourth pole with changeover, all contacts look big and strong for 15-20amp and the closing coil is mains operated. Normal bakelite upright mounting, size approx 3" x 2 1/2" x 3 1/2" high. Price £4-50.

## 6 VOLT RELAY

Standard open single screw fixing with 3 pairs 10amp C/O contacts. Price £1-68.

## MAINS SOLENOID WATER VALVES

Made by Asco. Two models available both suitable for water and non corrosive liquids, both for normal mains operation. Ref. V for 1/2" pipes and low pressure operation, V2 is for 1" pipe and high pressure operation. Only £4-32 either type.

## MINIATURE 24 HOUR TIME SWITCHES

Superb piece of precision engineering: measures only 2" x 2" x 2". Standard mains operation, with provision for up to 36 independent on/off's, massive 16amp contacts enable many switching applications. Brand new with one set of on/off triggers at £7-25. Additional on/off triggers £1 a pair.

## INTEL 400

4 bit MPU, this is the forerunner of the 8008 MPU chip and is ideal for breadboarding etc. to control keyboards, CRT's, memories etc. etc. supplied with complete data showing 40+ instruction set and as there is a great amount of established software available this is a tremendous offer at only £3-47 + 28p.

## SPERRY-UNIVAC

Servo Driven Tape Cassette System. This superb unit consists of an attractive desk standing console with twin servo driven cassette drives and all TTL electronics. Facilities such as "block transfer", "data transfer", "electronic LED tape position locator" are inbuilt. No data is presently available for these units but they seem to be selling very fast. As we only have a few left we must restrict this snip to callers only. Price £75. Standard 240 volt operation.

## SPERRY UNIVAC UNISCOP 30

As described in our previous newsletter we still have a few left of these VDU, Keyboard, PSU controller systems available. They are not in as good a condition as previously mentioned, therefore warrant a reduced price of £75 "as seen". Callers only.

## TAPE READERS AND PUNCHES

The cheapest way of non volatile memory-programmes is via mag. tape or paper tape. We have a few Viatron tape decks, £12 each for also Burroughs high speed optical tape readers £50 and High speed tape punches £45. Still available 8 bit NCR tape punch at £18-50.

## RAPAL C10 SUPERGRADE CASSETTES

Supergrade 10 minute cassettes complete with library cases, top quality made for data storage, 2 for £1, 10 for £4-50. Self adhesive die cut labels 20 for £1.

## VERBATIM MINI DISCS

Soft Sectors, ideal for Tandy TRS 80 Disc System etc. £3-50 each or 10 for £35. FREE LIBRARY CASE INCLUDED ON PURCHASE OF 10.

## PHILIPS 9 TRACK DIGITAL TAPEDECKS

Just arrived for personal callers are these small 9 track tape decks, measuring only 15" x 12" x 12" they are complete with all T.T.L. controllers and P.S.U. 110 volt operation, auto transformers available £35 each.

## PHILIPS QUERTY KEYBOARDS

Uncoded keyboards with standard typewriter keyboard, mounted on PCB, complete with cover and inbuilt 8 bit optical tape reader £25-00.

## MINIATURE UNISELECTOR

12 pole 8 way, this has 4 wiper arms coming out so it could be used for continuous motoring, the speed of which can be varied by using our time delay module and a pot. Made for the GPO, these are new and unused, very compact all the connections coming out of the bottom. Thousands of switching combinations are possible. Price £8-50.

## IMPULSE CLOCKS

10" dia, white face and a large clear hands. Require two impulses per min to give correct time but they are also useful educationally as they can be set to any time very quickly. Really beautiful clock, price only £5-50.

## REGULATED POWER SUPPLIES

Precision built on stout metal chassis using only top class components, normal mains input. Six different models are available. Simply order by output specification.

- |                 |                    |
|-----------------|--------------------|
| 100v—250mA      | } all £13-00 each. |
| 150v—200mA      |                    |
| 200v—200mA      |                    |
| 175v+225v—150mA |                    |
| 225v+275v—150mA |                    |

**ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED**

CAPACITORS				Electrolytic Axial Leads				Order Code				Cap 015 + $\mu$ F + V.d.c.			
$\mu$ F	V.d.c.	16	25	40	63	8	8	8	8	8	8	8	8	8	
1.0															
1.5															
2.2															
3.3															
4.7															
6.8															
10															
15		7			8	10									
22		7	7		12										
33		7			8										
47		7	7		10	12									
68		8	7		10										
100		8	8	12											
150		8	9		29										
220		12		24	34										
330				28	37										
470			21	30	44										
680		19	28	38	50										
1000		23	28	35											
1500		32	36												
2200		39													

Electrolytic Can Type				Order Code			
High Ripple, TEC Grade 1, Low E.S.R.	Cap HR + $\mu$ F + Volts						
Supplier complete with Vertical Fixing Clip	Ripple 1A @ 85°C	1.4A @ 50°C	166				
2200 $\mu$ F 18V	2.8A	3.6A	184				
4700 $\mu$ F 18V	3.8A	5.1A	222				
10000 $\mu$ F 18V	9.8A	13.7A	348				
22000 $\mu$ F 18V	13.8A	18.8A	175				
47000 $\mu$ F 25V	4.8A	6.4A	201				
100000 $\mu$ F 25V	8.0A	11.2A	264				
220000 $\mu$ F 25V	12.8A	17.9A	438				
1000 $\mu$ F 40V	0.9A	1.2A	168				
2200 $\mu$ F 40V	2.4A	3.2A	188				
4700 $\mu$ F 40V	5.6A	7.8A	231				
10000 $\mu$ F 40V	9.2A	12.8A	367				
1000 $\mu$ F 70V	1.8A	2.5A	190				
2200 $\mu$ F 70V	4.0A	5.6A	235				
4700 $\mu$ F 70V	7.5A	10.5A	376				
10000 $\mu$ F 100V	4.0A	5.6A	232				
2200 $\mu$ F 100V	7.8A	10.9A	348				

Electrolytic Radial Leads				Order Code			
-10% to +50% Tol.	Cap 034 + $\mu$ F + Volts						
$\mu$ F	V.d.c.	10	16	25	35	40	50
47							6
88							6
1.0							6
1.5							6
2.2							6
3.3							6
4.7							6
6.8							6
10							6
15							6
22							6
33							6
47							6
68							6
100							6
150							6
220							6

Tantalum Bead				Order Code			
20% Tol.	Cap PR + $\mu$ F + Volts						
$\mu$ F	V.d.c.	3.15	6.3	10	16	25	35
0.1							9
0.15							9
0.22							9
0.33							9
0.47							9
0.68							9
1							9
1.5							9
2.2							9
3.3							9
4.7							9
6.8							9
10							9
15							9
22							9
33							9
47							9
68							9
100							9

Trimmers				Order Code			
260V D.C. Wkg. Film Dielectric, Miniature	500V D.C. Wkg. C004 EA Tubular Type						
1.4 - 4.1pF	Cap 808 A	3 - 3.8pF	48	Cap 802 J			
2 - 8pF	Cap 808 B	3 - 6.8pF	48	Cap 802 K			
2 - 20pF	Cap 808 C	1 - 13pF	61	Cap 802 L			
5.5 - 59.5pF	Cap 808 D	1.7 - 19.7	62	Cap 802 M			

Polyester Radial Leads				Order Code			
Dipped Type, +20% Tol., > 250V D.C. Wkg. C280/352 Style	Moulded Type, +10% Tol., > 100V D.C. Wkg. 10.2mm Pitch Centres	Moulded Type, +10% Tol., > 100V D.C. Wkg. 7.8mm Pitch Centres					
$\mu$ F	352	360	PHE280	$\mu$ F	352	360	PHE280
.001	5	6	5	5	6	8	9
.0015	5	6	5	15	7	9	
.0022	5	6	5	22	8	10	
.0033	5	6	5	33	10		
.0047	5	6	5	47	12		
.0068	5	6	5	68	15		
.01	5	6	5	1.0	19		
.015	5	6	5	1.5	27		
.022	5	6	5	2.2	32		
.033	5	6	5	3.3	32		
.047	5	6	5	4.7	32		
.068	5	6	5	6.8	32		

### CASES

**Small Desk Console - Boss Industrial Mouldings**  
Slope Front Console, Recessed Top  
ABS Base, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel Finished Grey

Order Code  
W181 D96, H39 (57) 186 Case B1M1005 OR  
W215 D130, H47 (73) 268 Case B1M1006 OR

**Plastic Boxes - Boss Industrial Mouldings**  
Moulded Box and Clear Fitting Flanged Lid  
ABS Box, C/W Brass Bushes, and Lid In Orange

Order Code  
L112 W82 D31 87 Case B1M2003 OR  
L160 W80 D50 115 Case B1M2005 OR  
L190 W110 D60 195 Case B1M2006 OR

**Instrument Case - Boss Industrial Mouldings**  
Covers Manufactured from 14SWG Aluminium  
Chassis Manufactured from 18SWG Mild Steel  
Covers Finished Orange  
Chassis Finished Matt Black

Order Code  
W250 D167.5 H 68.5 (Chassis 153mm Deep) 1480 Case B1M3000 OR

**Plastic Boxes with Metal Lids - Boss Industrial Mouldings**  
Recessed Top Box  
ABS Base, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel Finished Grey

Order Code  
L85 W56 D29 97 Case B1M4003 OR  
L111 W71 D42 130 Case B1M4004 OR  
L161 W96 D53 182 Case B1M4005 OR

**Diecast Boxes - Boss Industrial Mouldings**  
Diecast Box and Flanged Lid  
Aluminium Box and Lid in Natural Finish

Order Code  
L112 W83 D31 104 Case B1M5003 NA  
L152 W83 D50 181 Case B1M5005 NA  
L192 W113 D61 290 Case B1M5006 NA

### VERO ELECTRONICS PRODUCTS

2.5" x 5.1" pitch Veroboard 59 VERO 21099J  
3.75" x 5.1" pitch Veroboard 66 VERO 21072D  
2.5" x 1.1" pitch Veroboard (S) 70/Pack VERO 21076C  
3.75" x 1.1" pitch Plain Board 56 VERO 21078E  
8.82" x 2.9" 1" pitch V.G. DIP Board 111 VERO 21084E  
Spot Face Cutter 89 VERO 21013A  
Pin Insertion Tool for .040 type pin 122 VERO 21015F  
DS Pins .040 (100) 38/Pack VERO 21087G  
59 Pins .040 (100) 38/Pack VERO 21017B  
6mm Board Standoff (100) 181/Pack VERO 21321K  
15mm Board Standoff (100) 215/Pack VERO 21322G  
19mm Board Standoff (100) 226/Pack VERO 21323D  
Verovinc Kit (1-pair, 2-wire, 25-comb) 375/Kit VERO 21341D  
Verovinc Comb (100) 407/Pack VERO 21339F  
Verovinc Wire (4) 228/Pack VERO 21340G  
Flip Top Box, Small, Black 192 VERO 21317D  
Flip Top Box, Large, Black 250 VERO 21319J

**Small Desk Consoles - Boss Industrial Mouldings**  
Slope Front Console, Recessed Top  
ABS Base, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel Finished Grey  
Ventilation Slots In Base

Order Code  
W106 D143 X32 (56) 206 Case B1M6006 OR  
W170 D143 X32 (56) 271 Case B1M6006 OR  
W170 D214 X32 (82) 375 Case B1M6007 OR

**All Metal Desk Consoles - Boss Industrial Mouldings**  
Slope Front Console, Recessed Top  
Two Piece All Aluminium Construction  
Ventilation Slots In Rear and Base  
Choice of 15° or 30° Sloping Front  
Off White Top Panel, Blue Base

Order Code  
W102 D140 H28 (51) 15° slope 1018 Case B1M7151A  
W165 D211 H33 (76) 15° slope 1350 Case B1M7154A  
W254 D287 H33 (76) 15° slope 1572 Case B1M7156A  
W255 D207 H33 (76) 15° slope 1823 Case B1M7158A  
W102 D140 H28 (78) 30° slope 1018 Case B1M7301A  
W165 D183 H28 (102) 30° slope 1202 Case B1M7303A  
W254 D289 H28 (102) 30° slope 1572 Case B1M7306A  
W256 D259 H28 (102) 30° slope 1823 Case B1M7308A

**European Size Desk Console - Boss Industrial Mouldings**  
Slope Front Console  
ABS Case, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel, Finished Grey

Order Code  
W169 D127 H45 (70) 375 Case B1M8006 OR

### HARDWARE

**D.I.L. Sockets**

8 Pin Low Profile Socket Tin 11 DIL SKT 8  
14 Pin Low Profile Socket Tin 13 DIL SKT 14  
16 Pin Low Profile Socket Tin 14 DIL SKT 16  
24 Pin Low Profile Socket Gold 86 DIL SKT 24  
28 Pin Low Profile Socket Gold 78 DIL SKT 28  
40 Pin Low Profile Socket Gold 127 DIL SKT 40

**Heatinks**

Individual Type for 1 x T05 50°C/W 10 Sink 5F  
Individual Type for 1 x T06 10.5°C/W 26 Sink TV2  
Individual Type for 1 x T03 7.2°C/W 24 Sink TV3  
Individual Type for 1 x T012 17°C/W 23 Sink TV4  
Individual Type for 1 x T022 17°C/W 23 Sink TV5

**P.C.B. Components**

Delco Pen, Blue Ink, Slow Drying 52 Pen 33PC

**Fuseholders**

Suit 20mm x 5mm fuses

P.C.B. Mounting, Open Type 8 Fuse/H208  
Chassis Mounting, Open Type 17 Fuse/H20C  
Panel Mounting, Screwdriver Slot 77 Fuse/H20PT  
Panel Mounting, Finger Release 56 Fuse/H20P

**Fuses**

20mm x 5mm Glass

Quick Blow, Range 100mA-5A 8 Fuse 20  
Slow Blow, Range 250mA-5A 135 A/S Fuse 20  
- Rating

**Lampholders, Panel Mounting**

Similar in Style to Fuse/H 20P  
Low Voltage Type Suits LES and M/P Bulbs.

Low Voltage, Red, Amber or Green 75 Lamp LV  
Internal Nech 200/240V Red or Amber 95 Lamp N  
+ Colour

**Bulbs, Low Voltage, L.E.S.**

6V, 0.36W, 6.5V, 1W, 14V, 0.75W 22 Bulb LES  
+ Voltage

RESISTORS				Order Code			
<b>Carbon Film, Fixed</b>							
0.25W, E24 Values IRO-10M, 5% Tol.	1.5 ea.	80p/100 (Mult 10/Value)	£7.90/1000 (Mult 100/Value)	Res RD4			
0.5W, E12 Values IRO-4M7, 10% Tol.	2 ea.	1.25p/100 (Mult 10/Value)	£10.10/1000 (Mult 100/Value)	Res RD4			
+ Value							
<b>Metal Film, Fixed</b>							
0.5W, E24 Values SR-1M, 2% Tol.	8 ea.	3.80/100 (Mult 10/Value)	£32.40/1000 (Mult 100/Value)	Res MR30			
2.5W, E12 Values IOR-27K, 5% Tol.	10 ea.	7.90/100 (Mult 10/Value)		Res PR52			
+ Value							
<b>Metal Glaze, Fixed</b>							
0.5W, E24 Values IM-33M, 5% Tol.	10 ea.	5.40/100 (Mult 10/Value)		Res VR37			
+ Value							

Skeleton Presets, Miniature				Order Code			
0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting			7				
0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting			7				
Skeleton Presets, Standard							
0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting			10				
0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting			10				
Potentiometer, Rotary							
0.5W, E3 Values, 1K-2M2 Lin.			34				
0.25W, E3 Values, 4K7-2M2 Log			34				
+ Value							

- ACCESS
- BARCLAYCARD
- CASH
- CHEQUE

**FREEPOST ON ORDERS** **GMT ELECTRONICS**  
**VAT INCLUSIVE PRICES** **Freepost**  
**ADD 30p P&P** **Birmingham B19 1BR**  
**24 HR TELEPHONE ANSWERING SERVICE** TEL ORDERS WELCOME

**DIGITAL INTEGRATED CIRCUITS**

4000 Buffered C-MOS - High Speed  
 5-15V 'B' Series, Up to 20MHz

7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.			
HEF4001	14	HEF4046	100	HEF4514	250	N7400N	9	N74122N	39	N74190N	60	N74LS28N	32	N74LS138N	85	N74LS253N	105
HEF4002	14	HEF4047	87	HEF4515	299	N7401N	11	N74123N	37	N74194N	80	N74LS30N	16	N74LS139N	86	N74LS254N	104
HEF4006	95	HEF4049	28	HEF4516	90	N7402N	11	N74124N	62	N74195N	79	N74LS32N	24	N74LS140N	76	N74LS255N	107
HEF4007	14	HEF4050	28	HEF4517	382	N7403N	11	N74125N	51	N74196N	32	N74LS33N	32	N74LS141N	122	N74LS256N	200
HEF4008	80	HEF4051	69	HEF4518	69	N7404N	12	N74126N	44	N74197N	74	N74LS37N	24	N74LS142N	80	N74LS257N	36
HEF4011	14	HEF4052	72	HEF4519	55	N7405N	12	N74127N	13	N74200N	46	N74LS38N	24	N74LS143N	80	N74LS258N	40
HEF4012	14	HEF4053	72	HEF4520	85	N7406N	25	N74128N	13	N74201N	80	N74LS39N	22	N74LS144N	54	N74LS259N	130
HEF4013	32	HEF4054	37	HEF4521	168	N7407N	27	N74129N	15	N74202N	126	N74LS40N	22	N74LS145N	60	N74LS260N	118
HEF4014	84	HEF4055	300	HEF4522	99	N7408N	13	N74130N	15	N74203N	126	N74LS42N	53	N74LS146N	120	N74LS261N	90
HEF4015	60	HEF4056	14	HEF4523	120	N7409N	13	N74131N	13	N74204N	83	N74LS44N	150	N74LS147N	78	N74LS262N	100
HEF4016	35	HEF4057	14	HEF4524	510	N7410N	11	N74132N	26	N74205N	46	N74LS45N	120	N74LS148N	130	N74LS263N	100
HEF4017	35	HEF4058	14	HEF4525	110	N7411N	18	N74133N	22	N74206N	55	N74LS46N	29	N74LS149N	78	N74LS264N	170
HEF4018	58	HEF4059	14	HEF4526	155	N7412N	17	N74134N	23	N74207N	98	N74LS47N	40	N74LS150N	90	N74LS265N	105
HEF4019	46	HEF4060	18	HEF4527	78	N7413N	29	N74135N	22	N74208N	53	N74LS48N	33	N74LS151N	91	N74LS266N	105
HEF4020	88	HEF4061	16	HEF4528	78	N7414N	46	N74136N	28	N74209N	49	N74LS49N	33	N74LS152N	100	N74LS267N	105
HEF4021	86	HEF4062	85	HEF4529	398	N7415N	22	N74137N	23	N74210N	43	N74LS50N	15	N74LS153N	100	N74LS268N	105
HEF4022	82	HEF4063	14	HEF4530	87	N7416N	23	N74138N	24	N74211N	54	N74LS51N	16	N74LS154N	100	N74LS269N	160
HEF4023	14	HEF4064	16	HEF4531	731	N7417N	21	N74139N	21	N74212N	74	N74LS52N	16	N74LS155N	100	N74LS270N	100
HEF4024	85	HEF4065	16	HEF4532	90	N7418N	28	N74140N	65	N74213N	74	N74LS53N	16	N74LS156N	91	N74LS271N	100
HEF4025	14	HEF4066	16	HEF4533	73	N7419N	27	N74141N	63	N74214N	74	N74LS54N	16	N74LS157N	95	N74LS272N	160
HEF4027	32	HEF4067	64	HEF4534	62	N7420N	22	N74142N	74	N74215N	74	N74LS55N	23	N74LS158N	128	N74LS273N	35
HEF4028	52	HEF4068	64	HEF4535	119	N7421N	22	N74143N	60	N74216N	65	N74LS56N	23	N74LS159N	130	N74LS274N	170
HEF4029	60	HEF4069	64	HEF4536	119	N7422N	30	N74144N	33	N74217N	65	N74LS57N	118	N74LS160N	150	N74LS275N	170
HEF4030	80	HEF4070	50	HEF4537	115	N7423N	30	N74145N	31	N74218N	64	N74LS58N	118	N74LS161N	150	N74LS276N	170
HEF4031	200	HEF4071	16	HEF4538	178	N7424N	21	N74146N	74	N74219N	64	N74LS59N	22	N74LS162N	150	N74LS277N	100
HEF4035	110	HEF4072	91	HEF4539	119	N7425N	21	N74147N	74	N74220N	63	N74LS60N	22	N74LS163N	110	N74LS278N	100
HEF4040	78	HEF4073	16	HEF4540	119	N7426N	30	N74148N	46	N74221N	63	N74LS61N	38	N74LS164N	160	N74LS279N	100
HEF4041	85	HEF4074	16	HEF4541	140	N7427N	80	N74149N	28	N74222N	82	N74LS62N	24	N74LS165N	160	N74LS280N	100
HEF4042	84	HEF4075	10	HEF4542	140	N7428N	80	N74150N	25	N74223N	82	N74LS63N	24	N74LS166N	160	N74LS281N	100
HEF4043	73	HEF4076	110	HEF4543	117	N7429N	40	N74151N	148	N74224N	69	N74LS64N	22	N74LS167N	160	N74LS282N	100
HEF4044	84	HEF4077	98	HEF4544	98	N7430N	78	N74152N	23	N74225N	62	N74LS65N	27	N74LS168N	160	N74LS283N	100

**LINEAR INTEGRATED CIRCUITS**

CA3011	92	NE592K	162
CA3018	75	RC4136	130
CA3020	191	TBA1205	79
CA3028A	86	TCA580	348
CA3046	78	TCA730	450
CA3048	245	TCA740	450
CA3080E	70	TDA1008	326
CA3089E	263	TDA1022	648
CA3130E	90	TDA1028	338
CA3140E	38	TDA1029	338
CA3189E	266	TDA1034B	217
LM301AN	30	TDA2581	266
LM308N	85	TDA2640	292
LM312N	200	TL081CP	75
LM318N	218	TL084CN	140
LM324N	70	UA703CT	45
LM339N	71	UA705CN	40
LM381N	110	UA710CN	41
LM381AN	180	UA711CN	85
LM382	120	UA714CT	47
		UA747CN	50
		UA748CN	35

**Voltage Regulators**

MC1458N	35	LM3090A (K)	108
MC1496N	97	LM723CN	38
NE531	119	UA785CU	36
NE536T	216	UA781CU	65
NE540	225	UA7815CU	65
NE555N	25	UA7905CU	86
NE558N	80	UA7912CU	86
NE560N	38	UA7915CU	86
NE561N	427	UA7915CU	86
NE562N	461	UA7915CU	86
NE568N	150	UA7915CU	86
NE569N	125	UA7915CU	86
NE571N	170	UA7915CU	86
NE570N	405	UA78L12CS	32
NE571N	469	UA78L15CS	32

**OPTO ELECTRONICS**

Light Emitting Diodes, Individual	Order Code
.125" (3mm) Red	14 CQY54
Green	17 CQY95
Yellow	19 CQY97
Panel Mounting Clip to suit.	3 LED3 Clip
2" (5mm) Red	15 CQY24A
Green	17 CQY94
Yellow	19 CQY96
Panel Mounting Clip to suit.	5 LED5 Clip

**Light Emitting Diodes - 7 Segment Display**

3" (7.6mm) C. Anode R.H. Decimal Pt. Red	160 XAN3061
C. Anode R.H. Decimal Pt. Green	199 XAN3051
C. Cathode R.H. Decimal Pt. Red, Low current drain	150 XAN3074

**Phototransistors**

ORP12	90	ORP12
ORP61	90	ORP61

**Photocouplers**

OCF71	180	OCF71
BPX25	175	BPX25
FC0820	150	FC0820

**SWITCHES**

Miniature Toggle - Honeywell	Order Code
SPDT C/O/H	2A/250V A.C., 5A/28V D.C.
SPDT Double Bias To Centre	58 SW 8A1011
SPDT Single Bias To Centre	67 SW 8A1021
SPDT Bias	75 SW 8A1041
DPDT	70 SW 8A1051
DPDT	70 SW 8A1061
DPDT	86 SW 8A2011
DPDT	92 SW 8A2021
DPDT Double Bias To Centre	102 SW 8A2041
DPDT Single Bias To Centre	102 SW 8A2051
DPDT Bias	96 SW 8A2061

**Miniature Push - C & K**

SP Push To Make, Momentary	0.5A/250V A.C., 1A/28V D.C.
SP Push To Break, Momentary	54 SW 8531
SP	54 SW 8533

**Slide - Switchcraft**

DPDT Standard Actuator	36 SW 46206
DPDT Slot Actuator, Voltage Change, Marked 110/240	43 SW 46206F

**SEMICONDUCTORS**

Diodes	Order Code						
IN827	193	IN4006	7	BB110G	61	OA202	9
IN914	4	IN4007	8	BY127	15		
IN916	5	IN4148	3	BY208	34		
IN4001	4	IN5402	15	BYX10	19		
IN4002	4	IN5404	16	OA67	0		
IN4003	6	SAX13	5	OA90	7	BAW950	1091
IN4004	6	BAY38	27	OA91	7	CL8960	2292
IN4005	7	8B106(4)	122	OA200	9	CX111C	1280

**Zener Diodes**

400mW CV17-C33	1.3W CV75-C75
BZV68/BZV75 + Voltage	BZK61 + Voltage

**SEMICONDUCTORS**

Rectifier Bridges	Order Code
1A 400V S.L.L.	93 BY179
1.4A 80V S.L.L.	84 BY164
1.5A 100V D.I.L.	33 VM18
1.5A 100V D.I.L.	39 VM48
1.5A 100V	45 W01
1.5A 400V	32 W04
2A 100V	89 VS148
2A 400V	109 VS448
8A 100V	143 VJ148
8A 400V	163 VJ448
10A 100V	172 VJ148
10A 400V	201 VJ448
15A 100V	215 VL148
15A 400V	226 VL448
30A 100V	242 VK148
30A 400V	260 VK448

**S.C.R.'s**

4A 400V	54 C106D
12A 400V	108 TIC128D

**Triacs**

10A 500V	124 BT138-500
15A 500V	177 BT139-500
23A 500V	492 BTW41-500

**MAINS TRANSFORMERS**

Order Code			
Secondaries may be connected in series or parallel to give wide voltage range			
Primary: 0-220, 240V			
6VA - Clamp Type Construction			
Approx. 18% Regulation, F.C. 54, H36, W35			
0-4.5V, 0-4.5V Secondaries	220	Trans 6VA	45
0.5V, 0.6V			80
0-12V, 0-12V			120
0-15V, 0-15V			150
0-20V, 0-20V			200
20VA - Clamp Type Construction			
Approx. 16% Regulation F.C. 70, H48, W46			
0-4.5V, 0-4.5V Secondaries	335	Trans 20VA	45
0.6V, 0.6V			80
0-12V, 0-12V			120
0-15V, 0-15V			150
0-17.5V, 0-17.5V			175
0-20V, 0-20V			200
55VA - Clamp Type Construction			
Approx. 10% Regulation F.C. 82, H64, W57			
0.6V, 0.6V Secondaries	540	Trans 55VA	80
0-12V, 0-12V			120
0-15V, 0-15V			150
0-20V, 0-20V			200
0-30V, 0-30V			300
100VA - Frame Type Construction			
Approx. 8% Regulation H87, W74, D84			
0-25V, 0-25V Secondaries	825	Trans 100VA	250
0-40V, 0-40V			400

**COMMUNICATIONS INTEGRATED CIRCUITS - PLESSEY**


SL390C	242	SL841C	384
SL392C	302	SL850C	855
SL510	230	SL851C	786
SL811C	230	SL852C	329
SL812C	230	SL895C	230

# TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

—WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS—

## STEREO PRE-AMPLIFIER

## POWER AMPLIFIER

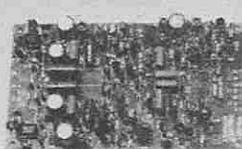

CPR



### CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slew rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 10B; signal to noise ratio is 70dB relative to 3.5mV; distortion < 0.05% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc., up to power amp. signal levels. Signal to noise ratio 85dB; slew-rate 3V/μs; T.H.D. 20Hz–20kHz < 0.05% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 × 90 × 20mm. Supply to be ± 15 volts.

### MC 1—PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

### REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

### POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc., who have been using CRIMSON amps, satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types; they all have the same specification: T.H.D. typically 0.1% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz–35kHz, —8dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 × 80 × 25mm.

### POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120–240 primary and single bolt fixing (includes capacitors/bridge rectifier).
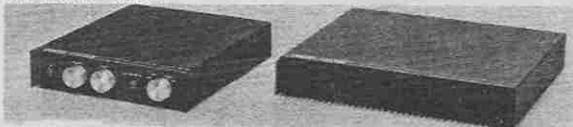
### POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



### PRE-AMPLIFIER KIT

This includes all metalwork, pots, knobs, etc., to make a complete pre-amp with the CPR 1(S) module and the MC 1(S) if required.

### ACTIVE CROSSOVERS

XO2 ..... £14.95 XO3 ..... £23.95  
**POWER AMPLIFIER MODULES**  
 CE 608 60W/8 ohms 35-0-35v £18.33  
 CE 1004 100W/4 ohms 35-0-35v £21.62  
 CE 1008 100W/8 ohms 45-0-45v £24.38  
 CE 1704 170W/4 ohms 45-0-45v £29.12  
 CE 1708 170W/8 ohms 60-0-60v £31.90

### TOROIDAL POWER SUPPLIES

CP52 for 2 × CE 608 or 1 × CE 1004 £15.55  
 CP52 for 2 × CE 1004 or 2/4 × CE 608 ..... £17.66  
 CP53 for 2 × CE 1008 or 1 × CE 1704 ..... £18.54  
 CP54 for 1 × CE 1008 ..... £18.08  
 CP53 for 1 × CE 1708 ..... £22.58  
 CP58 for 2 × CE 1704 or 2 × CE CE 1708 ..... £23.96

### HEATSINKS

Light duty, 50mm, 2°C/W ..... £1.35  
 Medium power, 100mm, 1-4°C/W ..... £2.20  
 Disco/group, 150mm, 1-1°C/W £2.85  
 Fan, 80mm, state 120 or 240v ..... £18.50  
 Fan mounted on two drilled 100mm heatsinks, 2 × 4°C/W, 65°C max. with two 170W modules ..... £29.16  
**THERMAL CUT-OUT, 70C.** £1.45

### POWER AMP KIT

PRE-AMPS: £32.90

RESISTORS: £30.95

CPRI ..... £30.95

CPRIIS ..... £30.95

MCI ..... £20.81

MCIS ..... £22.44

Pre-amp kit £37.24

### POWER SUPPLY

REG1 ..... £5.75

TR6 ..... £1.92

### BRIDGE DRIVER, BDI

Obtain up to 340W using 2 × 170W amps and this module BDI £5.40

### CRIMSON ELEKTRIK

1E STAMFORD STREET,  
 LEICESTER, LE1 6NL  
 Tel: (0533) 553568

All prices shown are UK only and include VAT and post. COD 90p extra. £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

### Distributors—

**BADGER SOUND SERVICES LTD.**  
 46 WOOD STREET,  
 LYTHAM ST. ANNES,  
 LANCASHIRE, FY8 1QG  
**"MINIC TELEPRODUKTER"**  
 BOX 49033; S-750 12  
 UPPSALA 12, SWEDEN"

TRAIN AT HOME

## Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future.

Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course—or, refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

Courses in  
 C & G Elect. Technicians  
 C & G Elect. Installations  
 Telecomms. Technicians Exams  
 Television Servicing  
 Radio Maint. & Repairs (BIET)  
 Pract. Radio & Electronics  
 Plus over 60 other home study courses.

### POST COUPON FOR FREE 44 PAGE GUIDE

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept. TEE 46 Reading RG7 4PF.

NAME (Block capitals please) \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

Other Subjects \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by CACC Member of ABCC

**SINCLAIR PRODUCTS** New 10MHz scope pos. PFM200 £49.48, case £3.19, adaptor £3.19, connector kit £10.58. Microvision TV UK model £89.95, mains adaptor £6.73. PDM35 £27.95, mains adaptor £3.19, case £3.19. DM350 £67.45, DM450 £95.95, DM235 £49.45, rechargeable batts £7.50, mains adaptor £3.70, case £2.45. Enterprise prog. calculator with accessories £21.95.  
**COMPUTER GAMES** Star chess £58.45. Chess champion 6 £88.50. Chess challenger 7 £95. Chess challenger 10 £153.50. Voice challenger pos. Checker challenger 2 £24. Atari video computer £138, cartridges £13.45.  
**COMPONENTS** 1N4148 1-4p. 1N4002 2-8p. 741 17p. bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 5p. Resistors 1/8W 5% E12 10R to 10M 1p, 0-8p for 50+ of one value. 16V electrolytics. 5/12/5/10/22uf 5p, 100uf 6p, 1000uf 10p. 11b FeCl £1.13. Dalo pen 79p. 40 9c int. pcb 90p. Polystyrene capacitors E12 63V 10 to 1000pf 3p. 1n2 to 10n 4p. Ceramic capacitors 50V E6 22pf to 47n 2p. Zeners 400mW E24 2v7 to 33v 7p. Preset pots submin 0-1W 100 to 4M7 6-8p.  
**TV GAMES** AY-3-8500 + kit £28.95. Rifle kit £24.95. AY-3-8810 + kit £15.70. Stunt cycle chip + kit £15.70. AY-3-8803 chip

£8-90.  
**TRANSFORMERS** 6-0-6V 100ma 74p. 1 1/2 £2.35. 6-3V 1 1/2 £1.89. 9-0-9V 75ma 74p. 1a £2.2a £2.60. 12-0-12V 100ma 90p. 1a £2.49.  
**IC AUDIO AMPS** with pcb. JC12 6W £1.95. JC20 10W £2.95.  
**BATTERY ELIMINATORS** 3-way type 6/7/9v 300 ma £2.95. 100ma radio type with press-studs 9V £3.35. 9V+9V £4.50. Car converter 12v input, output 4/6/7/9v 800 ma £2.50.  
**BATTERY ELIMINATOR KITS** 100ma radio type with press-studs 4/9V £1.40, 6V £1.40, 9V £1.40, 4.5V+4.5V £1.80, 6-9V £1.80, 9-9V £1.80. Stabilized 8-way types 3/4/6/7/9/12/15/18v 100ma £2.80, 1 Amp £6.40. Stabilized power kits 2-18V 100ma £2.80, 2-30v 1A £6.95, 2-30v 2A £10.95. 12v car converter 6/7/9v 1A £1.35.  
**T-DEC AND CSC BREADBOARDS** s-dec £3.80, 1-dec £4.02, u-dec £4.40, u-dec £5.73, 16 oil adaptor £2.17 exp4B £2.48, exp300 £6.21, exp350 £3.40.

**SWANLEY ELECTRONICS**  
 Dept. EE, 32 Goldsrd Rd., Swanley, Kent.

Post 30p extra. Prices include VAT. Official and overseas orders welcome. Lists 20p post free.



## EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.25 with a free bargain list. Send your cheque or postal order now.

**HOME RADIO COMPONENTS LTD.**  
 Dept. EE, 234 London Road  
 Mitcham, Surrey CR4 3HD

# RST VALVE MAIL ORDER CO. (EE 6)

## CLIMAX HOUSE, FALLSBROOK ROAD, LONDON SW16 6ED

### SPECIAL EXPRESS MAIL ORDER SERVICE

#### SEMICONDUCTORS

AA119 0-11	ASZ26 0-43	BC159 0-11	BCY72 0-14	BF194 0-10	BZK61 0-19	OA70 0-32	OC82 0-70	ZS271 0-26	2N697 0-27	2N3055 0-76
AA30 0-29	ASZ27 0-43	BC167 0-11	BCZ11 1-82	BF195 0-10	Series	OA79 0-32	OC83 0-70	ZS278 0-64	2N698 0-32	2N3440 0-86
AA32 0-45	ASZ15 1-35	BC170 0-12	BD115 0-49	BF196 0-11	BZ88 0-14	OA81 0-32	OC84 0-70	ZTX107 0-12	2N705 1-30	2N3441 0-86
AA213 0-19	ASZ16 1-35	BC171 0-11	BD121 1-30	BF197 0-14	CRS/140 0-65	OA85 0-32	OC122 1-82	ZTX108 0-11	2N706 0-16	2N3442 1-19
AA215 0-37	ASZ17 1-35	BC172 0-11	BD123 1-30	BF200 0-29	CRS/340 0-81	OA90 0-09	OC123 1-89	ZTX109 0-14	2N708 0-22	
AA217 0-29	ASZ20 1-62	BC173 0-13	BD124 1-40	BF224 0-23	CRS/360 0-97	OA91 0-09	OC139 2-43	ZTX300 0-14	2N830 0-22	
AC107 0-65	ASZ21 2-18	BC177 0-16	BD131 0-38	BF257 0-26	GEF95 1-62	OA95 0-09	OC140 2-87	ZTX301 0-18	2N1131 0-28	2N3702 0-12
AC125 0-22	AU110 1-84	BC178 0-15	BD132 0-38	BF258 0-26	GEK54 1-88	OA200 0-10	OC141 3-81	ZTX302 0-17	2N1132 0-28	2N3703 0-15
AC126 0-22	AU113 1-84	BC179 0-17	BD135 0-37	BF259 0-35	GJ3M 0-81	OA202 0-10	OC170 1-08	ZTX303 0-19	2N1302 0-38	2N3704 0-15
AC127 0-22	AU114 1-84	BC182 0-12	BD136 0-37	BF259 0-35	GJ3M 0-81	OA211 1-08	OC171 1-08	ZTX304 0-21	2N1303 0-38	2N3705 0-15
AC128 0-22	BA145 0-15	BC183 0-11	BD137 0-38	BF335 0-32	GM0378A1-99	OA220 1-08	OC200 1-82	ZTX311 0-14	2N1304 0-48	2N3706 0-15
AC141 0-27	BA148 0-15	BC184 0-12	BD138 0-43	BF337 0-32	MJE370 1-26	OA220 1-08	OC201 1-89	ZTX314 0-23	2N1305 0-48	2N3707 0-15
AC141K 0-38	BA154 0-10	BC185 0-11	BD139 0-48	BF337 0-32	MJE371 0-66	OA220 1-08	OC202 1-89	ZTX500 0-15	2N1306 2-84	2N3708 0-11
AC142 0-22	BA155 0-11	BC186 0-11	BD140 0-48	BF338 0-33	MS100A 0-51	OA220 1-08	OC203 1-89	ZTX501 0-18	2N1307 0-54	2N3709 0-15
AC142K 0-32	BA156 0-10	BC187 0-11	BD141 0-48	BF338 0-33	MJE370 1-26	OA220 1-08	OC204 2-70	ZTX502 0-16	2N1308 0-59	2N3710 0-11
AC176 0-22	BAW62 0-08	BC188 0-12	BD142 0-48	BF338 0-33	MJE371 0-66	OA220 1-08	OC205 2-70	ZTX503 0-19	2N1309 0-59	2N3711 0-11
AC187 0-22	BAX13 0-07	BC189 0-11	BD143 0-48	BF338 0-33	MJE371 0-66	OA220 1-08	OC206 2-70	ZTX504 0-23	2N1613 0-27	2N3712 1-87
AC188 0-22	BAX16 0-10	BC190 0-12	BD144 2-16	BF338 0-33	MJE520 0-86	OC22 2-97	OC207 1-89	ZTX531 0-23	2N1871 1-62	2N3772 2-16
ACV17 0-82	BC107 0-13	BC191 0-11	BD145 2-16	BF338 0-33	MJE521 0-89	OC23 2-97	OC208 2-70	ZTX532 0-23	2N1893 0-27	2N3773 3-24
ACV18 0-86	BC108 0-13	BC192 0-11	BD146 2-16	BF338 0-33	MJE521 0-89	OC24 3-24	OC209 2-70	ZTX533 0-23	2N1914 0-86	2N3819 0-41
ACV19 0-81	BC109 0-14	BC193 0-11	BD147 2-16	BF338 0-33	MJE521 0-89	OC25 0-97	OC210 2-70	ZTX534 0-23	2N1915 0-86	2N3820 0-81
ACV20 0-76	BC110 0-14	BC194 0-11	BD148 2-16	BF338 0-33	MJE521 0-89	OC26 0-97	OC211 2-70	ZTX535 0-23	2N1916 0-86	2N3821 0-81
ACV21 0-81	BC111 0-14	BC195 0-11	BD149 2-16	BF338 0-33	MJE521 0-89	OC27 0-97	OC212 2-70	ZTX536 0-23	2N1917 1-62	2N3822 0-81
ACV22 0-81	BC112 0-14	BC196 0-11	BD150 2-16	BF338 0-33	MJE521 0-89	OC28 2-16	OC213 2-70	ZTX537 0-23	2N1918 0-86	2N3823 0-81
ACV23 0-81	BC113 0-14	BC197 0-11	BD151 2-16	BF338 0-33	MJE521 0-89	OC29 2-16	OC214 2-70	ZTX538 0-23	2N1919 0-86	2N3824 0-81
AD139 1-82	BC114 0-14	BC198 0-11	BD152 2-16	BF338 0-33	MJE521 0-89	OC30 1-62	OC215 2-70	ZTX539 0-23	2N1920 0-86	2N3825 0-81
AD149 0-76	BC115 0-15	BC199 0-11	BD153 2-16	BF338 0-33	MJE521 0-89	OC31 1-62	OC216 2-70	ZTX540 0-23	2N1921 0-86	2N3826 0-81
AD159 0-76	BC116 0-17	BC200 0-11	BD154 2-16	BF338 0-33	MJE521 0-89	OC32 1-62	OC217 2-70	ZTX541 0-23	2N1922 0-86	2N3827 0-81
AD161 0-49	BC117 0-19	BC201 0-11	BD155 2-16	BF338 0-33	MJE521 0-89	OC33 1-62	OC218 2-70	ZTX542 0-23	2N1923 0-86	2N3828 0-81
AD162 0-49	BC118 0-19	BC202 0-11	BD156 2-16	BF338 0-33	MJE521 0-89	OC34 1-62	OC219 2-70	ZTX543 0-23	2N1924 0-86	2N3829 0-81
AF106 0-49	BC119 0-19	BC203 0-11	BD157 2-16	BF338 0-33	MJE521 0-89	OC35 1-62	OC220 2-70	ZTX544 0-23	2N1925 0-86	2N3830 0-81
AF114 0-81	BC120 0-23	BC204 0-11	BD158 2-16	BF338 0-33	MJE521 0-89	OC36 1-62	OC221 2-70	ZTX545 0-23	2N1926 0-86	2N3831 0-81
AF115 0-81	BC121 0-23	BC205 0-11	BD159 2-16	BF338 0-33	MJE521 0-89	OC37 1-62	OC222 2-70	ZTX546 0-23	2N1927 0-86	2N3832 0-81
AF116 0-81	BC122 0-23	BC206 0-11	BD160 2-16	BF338 0-33	MJE521 0-89	OC38 1-62	OC223 2-70	ZTX547 0-23	2N1928 0-86	2N3833 0-81
AF117 0-81	BC123 0-23	BC207 0-11	BD161 2-16	BF338 0-33	MJE521 0-89	OC39 1-62	OC224 2-70	ZTX548 0-23	2N1929 0-86	2N3834 0-81
AF139 0-43	BC124 0-23	BC208 0-11	BD162 2-16	BF338 0-33	MJE521 0-89	OC40 1-62	OC225 2-70	ZTX549 0-23	2N1930 0-86	2N3835 0-81
AF186 1-30	BC125 0-23	BC209 0-11	BD163 2-16	BF338 0-33	MJE521 0-89	OC41 0-86	OC226 2-70	ZTX550 0-23	2N1931 0-86	2N3836 0-81
AF239 0-49	BC126 0-23	BC210 0-11	BD164 2-16	BF338 0-33	MJE521 0-89	OC42 0-81	OC227 2-70	ZTX551 0-23	2N1932 0-86	2N3837 0-81
AF211 2-87	BC127 0-23	BC211 0-11	BD165 2-16	BF338 0-33	MJE521 0-89	OC43 0-81	OC228 2-70	ZTX552 0-23	2N1933 0-86	2N3838 0-81
AF212 2-87	BC128 0-23	BC212 0-11	BD166 2-16	BF338 0-33	MJE521 0-89	OC44 0-81	OC229 2-70	ZTX553 0-23	2N1934 0-86	2N3839 0-81
	BC129 0-23	BC213 0-11	BD167 2-16	BF338 0-33	MJE521 0-89	OC45 0-81	OC230 2-70	ZTX554 0-23	2N1935 0-86	2N3840 0-81
	BC130 0-23	BC214 0-11	BD168 2-16	BF338 0-33	MJE521 0-89	OC46 0-81	OC231 2-70	ZTX555 0-23	2N1936 0-86	2N3841 0-81
	BC131 0-23	BC215 0-11	BD169 2-16	BF338 0-33	MJE521 0-89	OC47 0-81	OC232 2-70	ZTX556 0-23	2N1937 0-86	2N3842 0-81
	BC132 0-23	BC216 0-11	BD170 2-16	BF338 0-33	MJE521 0-89	OC48 0-81	OC233 2-70	ZTX557 0-23	2N1938 0-86	2N3843 0-81
	BC133 0-23	BC217 0-11	BD171 2-16	BF338 0-33	MJE521 0-89	OC49 0-81	OC234 2-70	ZTX558 0-23	2N1939 0-86	2N3844 0-81
	BC134 0-23	BC218 0-11	BD172 2-16	BF338 0-33	MJE521 0-89	OC50 0-81	OC235 2-70	ZTX559 0-23	2N1940 0-86	2N3845 0-81
	BC135 0-23	BC219 0-11	BD173 2-16	BF338 0-33	MJE521 0-89	OC51 0-81	OC236 2-70	ZTX560 0-23	2N1941 0-86	2N3846 0-81
	BC136 0-23	BC220 0-11	BD174 2-16	BF338 0-33	MJE521 0-89	OC52 0-81	OC237 2-70	ZTX561 0-23	2N1942 0-86	2N3847 0-81
	BC137 0-23	BC221 0-11	BD175 2-16	BF338 0-33	MJE521 0-89	OC53 0-81	OC238 2-70	ZTX562 0-23	2N1943 0-86	2N3848 0-81
	BC138 0-23	BC222 0-11	BD176 2-16	BF338 0-33	MJE521 0-89	OC54 0-81	OC239 2-70	ZTX563 0-23	2N1944 0-86	2N3849 0-81
	BC139 0-23	BC223 0-11	BD177 2-16	BF338 0-33	MJE521 0-89	OC55 0-81	OC240 2-70	ZTX564 0-23	2N1945 0-86	2N3850 0-81
	BC140 0-23	BC224 0-11	BD178 2-16	BF338 0-33	MJE521 0-89	OC56 0-81	OC241 2-70	ZTX565 0-23	2N1946 0-86	2N3851 0-81
	BC141 0-23	BC225 0-11	BD179 2-16	BF338 0-33	MJE521 0-89	OC57 0-81	OC242 2-70	ZTX566 0-23	2N1947 0-86	2N3852 0-81
	BC142 0-23	BC226 0-11	BD180 2-16	BF338 0-33	MJE521 0-89	OC58 0-81	OC243 2-70	ZTX567 0-23	2N1948 0-86	2N3853 0-81
	BC143 0-23	BC227 0-11	BD181 2-16	BF338 0-33	MJE521 0-89	OC59 0-81	OC244 2-70	ZTX568 0-23	2N1949 0-86	2N3854 0-81
	BC144 0-23	BC228 0-11	BD182 2-16	BF338 0-33	MJE521 0-89	OC60 0-81	OC245 2-70	ZTX569 0-23	2N1950 0-86	2N3855 0-81
	BC145 0-23	BC229 0-11	BD183 2-16	BF338 0-33	MJE521 0-89	OC61 0-81	OC246 2-70	ZTX570 0-23	2N1951 0-86	2N3856 0-81
	BC146 0-23	BC230 0-11	BD184 2-16	BF338 0-33	MJE521 0-89	OC62 0-81	OC247 2-70	ZTX571 0-23	2N1952 0-86	2N3857 0-81
	BC147 0-23	BC231 0-11	BD185 2-16	BF338 0-33	MJE521 0-89	OC63 0-81	OC248 2-70	ZTX572 0-23	2N1953 0-86	2N3858 0-81
	BC148 0-23	BC232 0-11	BD186 2-16	BF338 0-33	MJE521 0-89	OC64 0-81	OC249 2-70	ZTX573 0-23	2N1954 0-86	2N3859 0-81
	BC149 0-23	BC233 0-11	BD187 2-16	BF338 0-33	MJE521 0-89	OC65 0-81	OC250 2-70	ZTX574 0-23	2N1955 0-86	2N3860 0-81
	BC150 0-23	BC234 0-11	BD188 2-16	BF338 0-33	MJE521 0-89	OC66 0-81	OC251 2-70	ZTX575 0-23	2N1956 0-86	2N3861 0-81
	BC151 0-23	BC235 0-11	BD189 2-16	BF338 0-33	MJE521 0-89	OC67 0-81	OC252 2-70	ZTX576 0-23	2N1957 0-86	2N3862 0-81
	BC152 0-23	BC236 0-11	BD190 2-16	BF338 0-33	MJE521 0-89	OC68 0-81	OC253 2-70	ZTX577 0-23	2N1958 0-86	2N3863 0-81
	BC153 0-23	BC237 0-11	BD191 2-16	BF338 0-33	MJE521 0-89	OC69 0-81	OC254 2-70	ZTX578 0-23	2N1959 0-86	2N3864 0-81
	BC154 0-23	BC238 0-11	BD192 2-16	BF338 0-33	MJE521 0-89	OC70 0-81	OC255 2-70	ZTX579 0-23	2N1960 0-86	2N3865 0-81
	BC155 0-23	BC239 0-11	BD193 2-16	BF338 0-33	MJE521 0-89	OC71 0-81	OC256 2-70	ZTX580 0-23	2N1961 0-86	2N3866 0-81
	BC156 0-23	BC240 0-11	BD194 2-16	BF338 0-33	MJE521 0-89	OC72 0-81	OC257 2-70	ZTX581 0-23	2N1962 0-86	2N3867 0-81
	BC157 0-23	BC241 0-11	BD195 2-16	BF338 0-33	MJE521 0-89	OC73 0-81	OC258 2-70	ZTX582 0-23	2N1963 0-86	2N3868 0-81
	BC158 0-23	BC242 0-11	BD196 2-16	BF338 0-33	MJE521 0-89	OC74 0-81	OC259 2-70	ZTX583 0-23	2N1964 0-86	2N3869 0-81
	BC159 0-23	BC243 0-11	BD197 2-16	BF338 0-33	MJE521 0-89	OC75 0-81	OC260 2-70	ZTX584 0-23	2N1965 0-86	2N3870 0-81
	BC160 0-23	BC244 0-11	BD198 2-16	BF338 0-33	MJE521 0-89	OC76 0-81	OC261 2-70	ZTX585 0-23		

# MAGENTA ELECTRONICS LTD.

## E.E. PROJECT KITS

Make us YOUR No. 1 SUPPLIER of KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Appropriate hardware—nuts, screws, I.C. sockets are included. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply—You construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. "PROJECT INSTRUCTIONS ONLY SUPPLIED AS EXTRA 39p EACH".

**TREMOLO UNIT.** June 79. £10.87.  
**ELECTRONIC CANARY.** June 79. £4.50.  
**LOW COST METAL LOCATOR.** June 79. £5.14.  
 Handle & coil former parts extra £4.75.  
**METER AMPLIFIER.** June 79. £3.64.  
**QUAD SIMULATOR.** June 79. £6.07.  
**INTRUDER ALARM.** May 1979. £15.02.  
 Less Ext. Buzzer & Lamp and Loop Components.  
**SHORT WAVE CONVERTER.** May 79. £14.28 inc. cases.  
**THERMOSTAT. 'PHOTO' SOLUTIONS.** May 79. £14.03. Less socket, tube and grease.  
**SHAVY INVERTER.** April 79. £12.36.  
**TRANSISTOR TESTER.** April 79. £3.50.  
**TOUCH BLEEPER.** April 79. £3.29.  
**ONE TRANSISTOR RADIO.** Mar. 79. with Amplifier & Headset. Less case. £8.43.  
**TIME DELAY INDICATOR.** Mar. 79. £4.49.  
**VERSATILE POWER SUPPLY.** Mar. 79. £8.10.  
**CHOCKE WARNING DEVICE.** Apr. 79. £8.86 case 75p.  
**AUDIO MODULATOR.** Feb. 79. £1.58 less case and pins.  
**LC CONVERTER.** Feb. 79. £6.02.  
**THYRISTOR TESTER.** Feb. 79. £3.28.  
**ADJUSTABLE PSU.** Feb. 79. £23.70. Case (horizontal layout) £3.39 extra.  
**I'M FIRST.** Jan. 79. £3.37 less cases.  
**LIGHTS REMINDER.** Jan. 79. £4.58.  
**CONTINUITY TESTER.** Jan. 79. £3.20 less case.  
**FUZZ BOX.** Dec. 78. £4.98.  
**VEHICLE IMMOBILISER.** Inc. PCB. Dec. 78. £4.15.  
**WATER LEVEL ALERT.** Nov. 78. £5.30.  
**'HOT LINE' GAME.** Nov. 78. £4.65 less case & rod.  
**AUDIO EFFECTS OSCILLATOR.** Nov. 78. £3.03 inc. board.  
**SUBSCRIBERS TELE TEL METER.** Nov. 78. £17.55 case extra £4.13.  
**FUSE CHECKER.** Oct. 78. £1.66.  
**C.MOS RADIO.** Oct. 78. £3.57.  
**TREASURE HUNTER.** Oct. 78. £16.98 less handle & coil former.  
**GUITAR TONE BOOSTER.** Sept. 78. £4.78 inc. p.c.b.

**SOUND TO LIGHT.** Sept. 78. £6.58.  
**FILTER.** £1.38  
**SLAVE FLASH.** Aug. 78. £2.92 less SK1.  
**LOGIC PROBE.** July 78. £2.52.  
**IN SITU TRANSISTOR TESTER.** June 78. £5.20.  
**VISUAL CONTINUITY CHECKER.** June 78. £3.26 inc. probes.  
**FLASHMETER.** May 78. £12.42 less calc and diffuser.  
**POCKET TIMER.** April 78. £3.10.  
**WEIRD SOUND EFFECTS GENERATOR.** Mar. 78. £4.96.  
**CHASER LIGHT DISPLAY.** Feb. 78. £21.78 inc. p.c.b. case extra £3.90.  
**AUDIO VISUAL METRONOME.** Jan. 78. £4.64.  
**RAPID DIODE CHECK.** Jan. 78. £2.17.  
**AUTOMATIC PHASE BOX.** Dec. 77. £10.58 inc. p.c.b.  
**'HF RADIO.** Nov. 77. £12.60.  
**ULTRASONIC REMOTE CONTROL.** Nov./Dec. 77. £15.13.  
**TREASURE LOCATOR.** Oct. 77. £9.65 case extra £2.55. Less handle, etc.  
**ELECTRONIC DICE.** March 77. £4.67.  
**SOIL MOISTURE INDICATOR.** June 77. £3.40 inc. probe.  
**PHONE/DOORBELL REPEATER.** July 77. £5.80.  
**SHORT WAVE RECEIVER.** Aug. 77. £12.09 case extra £1.64.  
**CAR BATTERY STATE INDICATOR.** Sept. 78. £1.89 less case inc. PCB.  
**R.F. SIGNAL GENERATOR.** Sept. 78. £16.83 less case.  
**TRANSISTOR TESTER.** Oct. 77. £6.98 case extra £3.90.  
**ELECTRONIC TOUCH SWITCH.** Jan. 78. £1.19.  
**ADD-ON CAPACITANCE UNIT.** Sept. 77. £4.91.  
**A.F. SIGNAL GENERATOR.** Aug. 78 less dial. £12.10.  
**QUAGMIRE.** July 78. £8.28 less case pins & counters.  
**CATCH-A-LIGHT.** Mar. 78. £7.42.  
**CAR SYSTEM ALARM.** Feb. 78. £5.21.  
**HEADPHONE ENHANCER.** Jan. 79. £2.47.  
**PASSIVE MIXER.** Oct. 78. £2.90.  
**MIC AMP.** Dec. 78. £2.41.  
**AUDIBLE FLASHER.** Dec. 78. £1.19.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

## 1979 ELECTRONICS CONSTRUCTORS CATALOGUE

MAGENTA'S CATALOGUE HAS BEEN CAREFULLY DESIGNED FOR E.E. READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR THE CONSTRUCTOR. CATALOGUE INCLUDES CIRCUIT IDEAS FOR YOU TO BUILD.

NO MINIMUM ORDER—ALL PRODUCTS ARE STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE! WRITE TODAY ENCLOSED 4 x 9p STAMPS.

MAGENTA gives you FAST DELIVERY BY FIRST CLASS POST OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

### LOW COST

#### METAL LOCATOR

E.E. JUNE 79.

WE HAVE MADE UP A COMPLETE HARDWARE KIT FOR THIS PROJECT. WITH TUBULAR PLASTIC COLLAPSIBLE HANDLE, HAND GRIP, COIL FORMER, AND ALL SCREWS, NUTS, CLIPS, TAPE, FOIL SPACERS etc.

Everything you need for the project including electronics and case £9.89

Or separately:  
 Electronics & Case £5.14  
 Hardware Kit £4.75

**MULTIMETER TYPE 1.** 1,000 o.p.v. with probes. 2" x 3 1/2" x 1". £6.78.  
**MULTIMETER TYPE 2.** 20,000 o.p.v. with case and probes. 5" x 3 1/2" x 1 1/2". £14.25.  
**ANTEX X25 SOLDERING IRON 25W.** Ideal for electronics. £4.45.

**SOLDERING IRON STAND.** Antex ST3. £2.03.

**SPARE BITS.** 2-3mm, 3mm, 4-7mm. 65p.

**DESOLDER BRAID.** 60p.

**HEAT SINK TWEEDERS.** 45p.

**DESOLDER PUMP.** Easy to use. £6.58.

**F.M. INDOOR AERIAL.** 57p.

**TELESCOPIC AERIAL.** 120 c.m. £2.08.

**TELEPHONE PICK-UP COIL.** 72p.

**CRYSTAL MICROPHONE INSERT.** 63p.

**SPEAKERS MINIATURE.** 8 ohm 87p.

64 ohm 89p, 80 ohm £1.28

**PILLOW SPEAKER.** 8 ohm £1.08p.

**6" ROUND SPEAKER.** 8 ohm, 5W. £2.18.

**CABINET SPEAKER.** 8 ohm, 5W. 5" speaker. Cabinet 10" x 7" x 4". £7.43

**RE-ENTRANT HORN SPEAKER.** 8 ohm S.W. Horn dia. 5 1/2". £5.27.

**EARTHPIECES.** Crystal 48p. Magnetic 18p.

**STETHOSCOPE ATTACHMENT.** Fits our earpieces 69p.

**BUZZER.** 6V 82p, 12V 85p.

**MONO HEADPHONES.** 2K. Padded. Superior. Sensitive. £3.28.

**STEREO HEADPHONES.** 8 ohm. Padded. £4.24.

**INTERCOM.** 2 Station. Desk. £7.10.

**MICROPHONE DYNAMIC.** 600 ohm. Cassette type. £1.38.

**DENTISTS MIRROR.** Adjustable. £2.37.

**JEWELLERS EYEGLASS.** £1.08p

**TRIPLE MAGNIFIER.** £1.63.

**HAND MAGNIFIER.** 3" Lens. £3.28.

### DOING IT DIGITALLY

Complete kit IN STOCK NOW for FAST DELIVERY by FIRST CLASS POST. All top quality components as specified by EVERYDAY ELECTRONICS. Our kit comes complete with FREE TTL & COMPONENT IDENTIFICATION SHEETS. £25.25 for the TTL TEST BED. £4.13 for ADDITIONAL COMPONENTS for first 6 months.

NEXT 6 MONTHS PARTS:—BPX25, £1.42. ORP12, 76p. 555, 49p. 80 ohm, speaker, £1.28. 2N2926, 12p. 0.1µF. 6 1/2p. Resistors, 1 1/2p. 100µF 10V, 9 1/2p. 7404, 30p. 7408, 30p. 7410, 29p. 7413, 51p. 7430, 29p. 7447, £1.21. 7454, 40p. 7490, 55p. 7492, 75p.

**SPECTACLE MAGNIFIER.** Clips on to spectacle frame. £4.38

**ILLUMINATED MAGNIFIERS.** 1 1/2" lens £1.09. 3" lens £3.07.

**SIGNAL INJECTOR.** £5.48.

**POCKET TOOL SET.** 20 piece. £4.09.

**SCREWDRIVER SET.** Six piece. £2.18.

**Q MAX PUNCH.** 1" £2.14. 1/2" £2.39.

1/4" £2.41. 1/8" £2.50.

**DRILL 12V.** Hand or stand use. £11.42.

**STANDER 27.57.**

**CAPACITANCE SUBSTITUTION BOX.** Nine values, 100pF—0.22µF. £3.03.

**QUICKTEST.** Mains connector. £5.83.

**PLUG IN POWER SUPPLY.** 6, 7.5-9V d.c. 300mA. £4.95.

**SPRINGS—SMALL.** 100 Ass'd, £1.08.

**CROC CLIP TEST LEAD SET.** 10 leads with 20 clips. £1.95.

**DIMMER SWITCH.** 240V. 800W. £4.13

**TRADITIONAL STYLE BELL.** 3-8V. 70mm chrome gong. £1.68.

**UNDERMOUNT BELL.** 4-10V. Smart. Dia. 70mm. £1.97.

**TOWERS INTERNATIONAL TRANSISTOR SELECTOR.** New edition. £6.22.

**F.M. TUNER CHASSIS.** 88-108MHz. 9V d.c. £9.19.

**MORSE KEY.** High speed. £3.83.

**PANEL METERS.** 60 x 45mm. Modern style. 50µA, 100µA, 1mA, 1A, 25V d.c. £8.33.

**NIGHT LIGHT.** Plug type. £1.08.

**CONNECTING WIRE PACK.** 5 x 5yd coils. 55p.

**VERO SPOT FACE CUTTER.** £1.06.

**VERO PIN INSERTION TOOL.** 0-1" £1.46. 0-15" £1.45

**RESISTOR COLOUR CODE CALCULATOR.** 21p.

### TEACH-IN-78

COMPLETE KIT £16.48

INCLUDES FREE COMPONENT IDENTIFICATION CHART. TEACH-IN REPRINTS EXTRA 39p EACH PART. ALL 12 PARTS AVAILABLE.

### EVERYDAY ELECTRONICS FEB 79

G.P. POWER SUPPLY VARIABLE 0-20V 0-1A

WITH CALIBRATED VOLTMETER AND AMMETER ALL COMPONENTS AND HARDWARE £23.76. CASE (Horizontal Layout) £3.69 EXTRA.

## MAGENTA ELECTRONICS LTD.

EH7, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI.

OFFICIAL ORDERS FROM SCHOOLS, UNIVERSITIES ETC. WELCOME. MAIL ORDER ONLY.

ALL PRICES INCLUDE 15% VAT AND FIRST CLASS POST. ADD 30p TO ORDERS UNDER £10 ENQUIRIES MUST INCLUDE S.A.E.

# TOPS THE PACK!

ACE MAILTRONIX LTD  
 Dept. EE Toolkit Street  
 Wakefield, W. Yorkshire WF1 5JR

<b>COMPONENTS</b>	— Now over 1,000 types in stock!
<b>KITS</b>	— See the new range of low-cost 'ELEKITS'.
<b>SERVICE</b>	— 1st Class same day despatch.
<b>QUALITY</b>	— All guaranteed products.
<b>PRICES</b>	— Many reductions!
<b>MAGAZINE PROJECTS</b>	— Trouble-free!
S.A.E. for list of EE projects	

I enclose 30p\*, please send catalogue.

Name \_\_\_\_\_  
 Address \_\_\_\_\_

\*Refundable with future orders over £5.00.

**QUALITY REEL TO REEL & CASSETTE TAPE HEADS**

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01	MONO PLAYBACK . . . . .	£1.89	E12-09	MONO/STEREO ERASE . . . . .	£1.85
B12-02	MONO RECORD/PLAYBACK . . . . .	£4.02	B22-02	TWIN HALF TRACK RECORD/PLBK	£5.97
B24-01	STEREO PLAYBACK . . . . .	£3.30	C4ARP502	QUAD QUARTER TRACK REC/PLBK	£9.37
B24-02	STEREO RECORD/PLAYBACK . . . . .		C22E502	TWIN HALF TRACK ERASE . . . . .	£4.72
B24-RP	STEREO GLASS FERRITE REC/PLBK	£1.60		MAGNETIC TAPE HEADS CATALOGUE 25 PENCE	

AUDIO AND HI-FI CATALOGUE (80 PAGE FULL COLOUR) 50 PENCE

## MONOLITH

THE MONOLITH ELECTRONICS CO. LTD.  
 57 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER  
 ALL PRICES INCLUDE VAT

## BUILD A SYNTHESISER!

**NO SPECIAL SKILLS  
SPECIAL EQUIPMENT REQUIRED**



Using **Dewtron** (Reg'd)  
**PROFESSIONAL MODULES**

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

**D.E.W. LTD.**

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR

## TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

**City and Guilds Certificates:**  
Telecommunications Technicians  
Radio, TV, Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
MPT Radio Communications Certificate

**Diploma Courses:**  
Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV, Audio Engineering and Servicing  
Electrical Engineering, Installation  
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

**ICS** To: International Correspondence  
Schools

Dept K268 Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest .....  
Name .....  
Address .....  
Tel: ..... Age: .....


**THE NEW**

## EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £6.80 inc. VAT & P.P.

**THE UNIQUE**

## EUROBREADBOARD

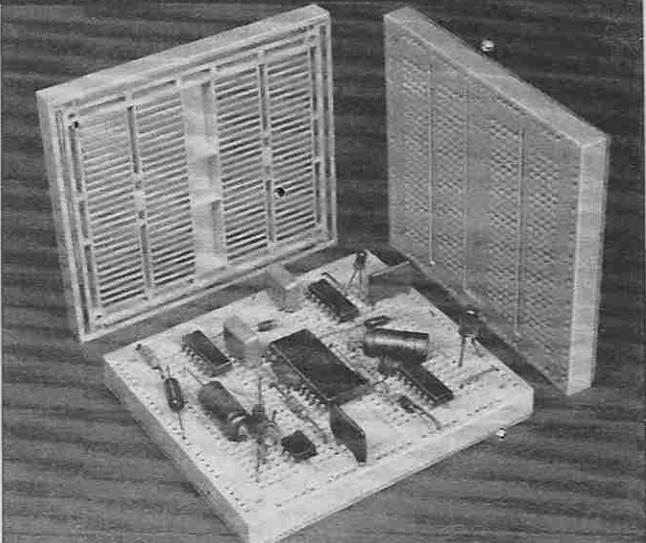

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

**All connection rows and columns are now numbered or lettered enabling exact location indexing.**

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF

David George Sales  
r/o 74 Crayford High Street,  
Crayford, Kent, DA1 4EF.

EE 8/79

Please send me 1 EuroSolderSucker @ £6.80  Please  
or 1 EuroBreadBoard @ £5.80  Tick  
or 2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).

Name: .....

Company: .....

Address: .....

Tel. No. ....

Please make cheque/P.O.'s payable to David George Sales



### NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### For Sale

**NEW BACK ISSUES** of "EVERYDAY ELECTRONICS". Available 60p each Post Free, open PO/Cheque returned if not in stock. **BELL'S TELEVISION SERVICES** 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

**E.E. BACK ISSUES.** Volume 1 issue 1 to date. Complete Volumes 1 to 7 in self-binders with indexes, £25 ono plus carriage. Lanfear, 53 College Street, Camborne, Cornwall.

**4600 MUSIC SYNTHESIZER** complete with construction manual. Small faults on three individual modules, hence £350 ono. Kinghorn, Fife. Telephone 890342.

**PHILLIPS X40 and X40A** (amplifier) kits, complete. £20 pair ono. Back issues E.E. Jan. '79 to present; offers. 59 Bay Road, Wormit, Newport-on-Tay, DD6 8LW.

## SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £4.40 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

### CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

### Service Sheets

**SERVICE SHEETS** for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

**BELL'S TELEVISION SERVICE** for service sheets of Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

### Miscellaneous

**TUNBRIDGE WELLS COMPONENTS, BALLARD'S**, 108 Camden Road, Tunbridge Wells, Phone 31803. No lists, enquiries S.A.E.

### RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus catalogue. Write or call, Sandwell Plant Ltd, 2 Union Drive, Boldmere, Sutton Coldfield, West Midlands. 021-354 9764. Or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

**AUDIO OSCILLATOR** Sine—Square—R.I.A.A. outputs: 15Hz to 200KHz in four ranges. Thermistor stabilised. Assembled PCB ready to use. 9V supply required. SAE data. £16.50 inclusive. Quantec, 40 Aln Court, Ellington, Morpeth, Northumberland. Morpeth 860101.

**PRINTED CIRCUIT BOARDS** from your tape or film masters, prototypes or short runs. Photographic masters from your layout. SAE for details. Dia-Dim Audio Visual, 21 Brammay Drive, Tottington, Bury BL8 3HS.

### AERIAL BOOSTERS

Improves weak VHF radio & television reception.

B45-UHF TV, B11-VHF RADIO. For next to the set fitting.

PRICE £5. S.A.E. FOR LEAFLETS.

**ELECTRONIC MAILORDER LTD.**  
Ramsbottom, Bury, Lancs, BLO 9AG.

**BUILD 25 PROJECTS** with our Multi-purpose kits, details supplied. Send £19.00 to Major Oak Services, 33 Lillian Avenue, London, W3.

### THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4.  
Reg. Office, 22 Coningsby Gardens.

#### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10-19	2.65	1.45	.75	.80
20-29	2.85	1.65	.90	.70
30-34	3.05	1.75	1.00	.75
35-40	3.40	1.95	1.15	.84
41-43	4.55	2.55	1.95	1.30
44-46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

#### SILVER PLATED COPPER WIRE

	4.50	2.25	1.44	.80
14, 16, 18	4.50	2.25	1.44	.80
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT.  
SAE brings list of copper & resistance Wires.  
Dealer enquiries invited.

### Receivers and Components

**AF/RF SIGNAL INJECTORS** £2.50, with instructions. SAE for list, Bobker, 29 Chaderton Drive, Unsworth, Bury, Lancs.

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Everyday Electronics for ..... insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)


NAME .....

ADDRESS .....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager

**EVERYDAY ELECTRONICS**

GMG, Classified Advertisements Dept., Room 2337, King's Reach Tower, Stamford Street, London SE1 9LS. Telephone 01-261 5942

Rate:

18p per word, minimum 12 words. Box No. 60p extra.

## Receivers and Components

**SALE.** Everything must go most at half price. Transistors, general purpose BC109, etc. 6p; power from 20p; triacs from 30p; jack plugs and sockets sub-min DPDT 50p. Send your list and SAE for quotation. J.A.I. ELECTRONICS, 30 Balvernie Grove, SW18 5RR.

## NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-25 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4-50 plus 25p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P.

LOTS MORE! Send 25p for lists.

Prices include VAT.

## BOFFIN PROJECTS

4 CUNLIFFE ROAD, STONELEIGH  
EWELL, SURREY. (E.E.)

**NEW AND UNUSED COMPONENTS.** Surplus to teaching experiments. Die cast boxes 6 $\frac{1}{2}$  in x 4 $\frac{1}{2}$  x 4, £1.60; mains transformers 9-0-9 at lamp, £1.60; capacitors electrolytic wire ended 10,000/40V 50p; 1,500/16V, 20p; 470/25V, 10p; polyester pcb type 1-0, 0-68, 0-47, 0-22, 0-1, 0-047, 0-01, £7 per 100 any mix and quantity. Add 15% P&P. **INEXPENSIVE ELECTRONIC LOGIC EXPERIMENT KIT**—send large SAE for details. S. E. Warren, 15 Moorland Terrace, Skipton, North Yorkshire, Tel: 3270.

**TIRRO's** new mail order price list of electronic components now available on receipt of SAE. TIRRO Electronics, Grenfell Place, Maidenhead, Berks.

**TURN YOUR SURPLUS** capacitors, transistors, etc., into cash. Contact COLESHARDING & CO, 105 South Brink, Wisbech, Cambs, 0945 4188. Immediate settlement.

200 COMPONENTS £4 10 L.E.D.s 0-125 90p. Lists 15p. Sole (E. E.), 37 Stanley Street, Ormskirk, Lancs L39 2DH.

**DISCOVER ELECTRONICS.** Build forty easy projects including: Metal Detector; Wireless Transmitter; Breathalyser; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms, etc. Circuits, plans all for £1-29 including FREE circuit board. Mail only. RIDLEY PHOTO/ELECTRONICS, Box 62, 111 Rockspark Road, Uckfield, Sussex.

**SMALL AUDIO AMPLIFIERS.** 3 transistors equivalent to AC128, OC72 with circuit 3 for £1. 300 small components, transistors, diodes, £1-60. Wire ended neons, 20 for £1. Panel with 40 74 series ICs, £1-50. 100 assorted C280 polyester capacitors £1-20 no Postage. List 15p refundable. Insurance add 15p. J.W.B. RADIO, 2 Barnfield Crescent Sale, Cheshire M33 1NL.

**ELECTRONIC COMPONENTS.** Send SAE for list. Special offers monthly. Radnor Supplies, 23 Arbury Road, Nuneaton, Warks.

**ELECTRONIC COMPONENTS** and E.E. project kits 1973-now. Catalogue SAE, plus 50p Jadebond Ltd., Middridge Drift Ind. Est., Middridge, Shildon, Co. Durham. Tel: Shildon (038 884) 3845.

**C.P. ICs.** 74 series 00/9p 01/11p 02/11p 03/11p 04/11p 06/24p 08/15p 09/12p 10/12p 11/15p 12/15p 13/24p 14/50p 16/23p 20/12p 30/12p 37/22p 40/20p 45/65p 47/65p 70/25p 72/24p 73/24p 74/24p 75/30p 76/28p 85/60p 86/24p 89/135p 90/32p 92/35p 93/33p 95/50p 121/24p 122/33p 123/40p 125/35p 132/48p 141/58p 164/65p 190/72p 191/72p 192/60p  
CMOS 4000/15p 01/15p 02/15p 11/15p 12/15p 13/30p 15/57p 17/55p 18/60p 20/60p 23/15p 24/45p 25/15p 27/32p 28/50p 29/80p 30/35p 35/60p 40/65p 42/50p 46/100p 49/30p 50/30p 66/40p 71/16p 81/20p. Linears and Regs 555/25p 741/16p 747/40p 1458/40p 7805/60p 7812/60p 7815/60p 7818/60p 7824/60p 78L05/45p 78L12/45p 78L15/45p 7905/90p 7912/90p 7924/90p. Many more. SAE list 25p P&P. 22 Oakfield Road, Croydon, Surrey.

## Record Accessories

**STYLII, CARTRIDGES FOR MUSIC CENTRES** &c. FREE List No. 29. For S.A.E. includes Leads, Mikes, Phones, etc. FELSTEAD ELECTRONICS (EE), LONGLEY LANE, GATLEY, CHEADLE, CHES SK8 4EE.

## Kits

**CONSTRUCT YOUR OWN VHF TRANSMITTER** (not licensable in UK), hand-held, range 500 yds. Complete kit £5-25. **NEW SERVICE**—PCB's produced from your exact drawing 17p sq in. WEBB ELECTRONICS, 41 Winwick Street, Warrington.

## Books and Publications

**INTRODUCTION TO MICROPROCESSORS** and Computing. 50 pages of diagrams and explanation to get you started. Price £2-30 plus 45p postage. **EDUCATIONAL DATA AND TECHNICAL SERVICES**, 59 Station Road, Cogenhoe, Northampton NN7 1LU.

Complete repair information any requested T.V. £5 (with diagrams £5-50). Any requested service sheet for £1 plus SAE. SAE brings newsletter & special offers—service sheets from 50p, bargain vouchers, unique publications

## AUS (EE)

76 Church St., Larkhall, Lanarkshire.

## SPECIAL 1/2 PRICE OFFER !!!

"RIGHT FROM THE START"

The only PRACTICAL Home Study Course for you! Projects and experiments introducing Audio, Radio, Logic and Measurement techniques. A progressive practical MINIMUM MATHS course at a SPECIAL SUMMER OFFER price of only £17-50 covering all necessary components, including printed circuit type solder boards. The profusely illustrated MANUAL, especially written for the beginner, may also be purchased separately for ONLY £5-00.

Prices include P. & P., etc. C.W.O. to:

**MANTEC** 7 Dellisome Lane, Welham Green, HATFIELD, HERTS.

## MAINS INTERCOM



**NO BATTERIES  
NO WIRES**

**ONLY  
£32-99  
PER PAIR**

VAT 15% = £4-95

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1/2 mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. P. & P. 89p.

## 4-STATION INTERCOM



**£27-95**

VAT 15% = £4-19

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs) in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 65ft. A Battery and other accessories. P. & P. 99p.

## NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



**£17-95**

VAT 15% = £2-69

Latest transistorised Telephone Amplifier with detached plug-in speaker. Flipping the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £19-95 + VAT 15% = £2-99. P. & P. 90p.

## DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch locks), mains power unit, cable (8-way), 50 ft. and wiring diagrams. Price £24-95 + VAT £3-24 + P. & P. £1-25. Kit with two Telephones £24-95 + VAT £9-74 + P. & P. £1-50.

10-day price refund guarantee on all items.

WEST LONDON DIRECT SUPPLIES (EES)  
169 KENSINGTON HIGH STREET, LONDON, W8

## MAIL ORDER PROTECTION SCHEME

The Publishers of Everyday Electronics are members of the Periodical Publishers Association which gives an undertaking to the Director General of Fair Trading to refund moneys sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund moneys owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with Everyday Electronics within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:— 'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered. 'Classified and catalogue mail order advertising are excluded.

# TAMTRONIK LTD (DEPT EE)

217, Toll End Road, TIPTON, West Midlands DY4 0HW TEL: 021-557-9144

# Printed Circuit Boards & KITS for EE projects

Mag Issue	PROJECT	KIT Ref	PRICES		KIT CONTENTS (See key)
			P.C.B.	KIT	
Jan 78	Audio Visual Metronome	E001	+ 85	6-40	B.E.H.L.
	Touch Switch	E002	+1-00	2-35	B.E.
	Rapid Diode Check	E004	+ 85	2-80	B.E.H.L.
Feb	Car Alarm	E005	+1-15	5-55	B.E.G.H.L.
	Chaser Light Display	E007	2-70	23-95	B.E.H.L.
Mar	Weird Sound	E012	+1-00	6-45	B.E.H.L.
Apr	Pocket Timer	E015	+ 95	4-40	B.E.H.L.
May	Flash Meter	E016	+1-10	13-20	B.E.H.L.
	Mains Tester	E17	+ 85	1-90	B.E.H.
	Power Pack	E19	+1-20	7-10	B.E.H.L.
Jun	Tele-Ball	E20	+1-35	12-60	B.E.H.L.
	Insitu-Transistor Tester	E21	+ 95	6-15	B.E.G.H.L.
	Teach In S.W. Receiver	E22	—	3-30	E.
July	Power Slave	E23	2-45	—	—
	Visual Continuity Tester	E24	—	4-95	E.H.L.
	Auto Night Light	E025	+1-30	11-25	B.E.G.H.L.
Aug	Short Wave Radio	E026	—	10-25	E.J.
	Quagmire	E027	+1-95	8-80	B.E.G.H.
	Logic Probe	E028	+ 80	3-45	B.E.G.H.L.
Sept	Slave Flash	E029	+ 80	3-55	B.E.H.L.
	I.M.W.	E30	+ 80	6-35	B.E.J.L.
	Audio Freq. Signal Generator	E031	+1-45	14-85	B.E.J.L.
Oct	Chronosop	E032	+2-95	33-95	C.E.G.K.M.P.
	R.F. Signal Generator	E033	—	18-25	E.H.
	Sound to Light	E034	—	6-20	E.H.L.
Nov	Guitar Tone Booster	E035	1-05	5-00	B.E.H.L.
	Car Battery State Indicator	E036	90	2-20	B.E.
	C.M.O.S. Radio	E037	+1-85	12-75	B.E.G.H.L.
Dec	Fuse Checker	E038	—	2-15	B.E.H.L.
	Treasure Hunter	E039	1-80	18-20	B.E.G.H.L.
	Audio Effects Oscillator	E042	—	3-05	E.H.L.
Jan 79	Water Level Alert	E043	+ 90	4-65	B.E.G.H.L.
	Subscribers Tele-Tel. Meter	E044	+3-50	24-50	C.E.G.K.M.P.
	Subs. Tele Tel—3rd Digit	E044A	—	3-50	E.
Feb	Combination Lock (2 Pcb's)	E045	+3-45	24-95	B.E.H.L.
	Hotline Game	E046	+1-00	5-50	B.E.H.
	Fuzz Box	E049	+1-00	6-25	B.E.H.L.
Mar	Vehicle Immobiliser	E050	1-25	5-50	B.E.H.L.
	Mini Module—Microphone Amp	E051	—	3-10	D.E.H.
	Mini Module—Continuity Tester	E052	+1-05	4-65	B.E.H.
Apr	Light Reminder	E053	+1-15	6-90	B.E.G.H.L.
	I'm First	E054	—	2-20	E.H.
	Roulette (2 p.c.b.'s)	E055	+4-10	20-45	B.E.H.
May	Headphone Enhance	E056	—	2-60	E.H.C.
	EE 2020 Tuner Amp A (Inc. R. unit)	E057	3-65	58-95	B.E.G.H.
	EE 2020 Tuner Amp B	E058	3-60	25-95	B.E.H.
June	EE 2020 Tuner Amp C	E059	1-45	4-70	B.E.H.
	EE 2020 Tuner Amp D	E060	2-30	18-45	B.E.H.
	EE 2020 Tuner Amp E	E061	1-40	24-95	B.E.G.H.
July	EE2020 Hardware & wire	E062	—	13-50	K.
	EE 2020 Kit excl. Case	E063	10-90	135-00	B.E.G.K.
	Long Wave Converter	E064	+1-20	7-40	B.E.H.L.
Aug	Mini Module Audio Modulator	E065	—	2-00	E.H.
	Power Supply	E066	+1-00	25-45	B.E.H.
	Thyristor Tester	E067	+ 80	4-85	B.E.H.L.
Sept	Sound Adaptor	E068	+1-20	6-95	B.F.H.
	Car Direction Indicator (Neg. 12v)	E069	+1-25	8-45	B.E.G.H.L.
	Time Delay Indicator	E070	+ 80	4-05	B.E.J.L.
Oct	ONE Transistor Radio (inc. Amp)	E071A	+1-00	8-50	B.E.H.
	ONE Transistor Radio (excl. Amp)	E071B	+ 85	7-35	B.E.H.
	Mini Module—Versatile Power Supply	E072	—	5-35	E.H.L.
Nov	Shaver Inverter	E073	+1-00	12-75	B.E.H.L.
	Touch Bleep	E074	+1-15	4-70	B.E.H.L.
	Mini Module Transistor Test	E076	+ 95	4-25	B.E.H.
Dec	Choke Warning	E077	+1-00	9-00	B.E.G.H.
	Intruder Alarm	E078	+1-35	25-45	B.E.H.L.
	Electronic Dice	E079	2-15	14-45	B.E.H.L.
Jan 80	Shortwave Converter	E080	—	17-95	B.E.L.
	Thermostat	E081	+1-25	12-65	E.J.L.
	Tremolo Unit	E082	—	11-00	A.E.K.L.
Feb	Electronic Canary	E083	—	4-38	A.E.U.L.
	Low Cost Metal Locator (Electronic Unit)	E084	—	6-07	A.E.U.L.
	Mini Module Meter Amplifier	E085	—	2-00	E.
Mar	Pocket Radio	E086	+ 85	12-85	B.E.G.H.L.
	Quad Simulator	E087	—	5-83	D.E.H.L.
	+ P.c.b.'s designed by Tamtronik to EE circuit specifications				

### KEY TO KIT CONTENTS

A Vero-board(s)  
 B Printed Circuit Board(s)  
 C With screen printed component layout  
 D Tag strip  
 E ALL Resistors, potentiometers, capacitors, Semi-conductors  
 F As E but with exclusions—Please ask for details  
 G DIL and/or transistor sockets and/or soldercon pins  
 H Hardware includes Switches, Knobs, Lamps & Holders, Fuses & Holders, Plugs & Sockets, Microphones, Transformers, Speakers, Meters, Relays, Terminal Blocks, Battery Connectors, etc. BUT excludes nuts, bolts, washers, connecting wire, Batteries and special miscellaneous items.  
 J As H but with exclusions—Please ask for details  
 K As H but including connecting wire  
 L Suitable Case(s)  
 M Suitable Case with Screen printed fascia.  
 N Full kit to magazine specified standards  
 P Full kit with professional finish incorporating all prime features including screen printed PCB and case where appropriate

### Doing-it-Digitally

#### TTL ELECTRONIC TEST BED

Complete kit E040  
**£26-40**

Components for first 6 parts E041 **£4-95** (including additional components)

### BARGAIN CORNER

100 x 1/4w 1k carbon resistors 30p  
 10 x 1w 5% 1k5 resistors 10p  
 10 x 1w 5% 7k5 resistors 12p  
 10 x 1w 5% 100R resistors 12p  
 10 x 6w 5% 390R wirewound 50p  
 10 x 47u 10v Axial Elec. Caps 25p  
 4 x NE55 Timer **£1-00**

Plug in mains PSU  
 3v/6v/9v/12v DC  
 300mA suitable for calculators & T.V. Games **£2-90**

### TELE-TEL

Nov. 78 Ref. E044

Subscribers phone call charge meter

A kit with a professional finish CASE with screen printed fascia similar to magazine photograph but includes provision for 3rd digit.

An aluminium sub-facia panel is also provided with screen printed hole centres to allow access to preset potentiometers.

PCB designed to incorporate 3rd digit facility and is screen printed for ease of assembly.

Basic kit (2 digits) **£24-50**  
 (3 digits) **£28-00**

### CHRONOSTOP

Aug. 78 Ref. E032

SPLIT & TAYLOR lap timing modes plus normal start/stop operation.

A kit with a professional finish including CASE with screen printed fascia

PCB with a screen component layout

Full Assembly Instructions

**PRICE INC. VAT £33-95**

### SOLDERING IRONS & ACCESSORIES

SRB 18 watt iron inc. No 20 **£3-78**  
 Bit **£3-25**  
 Stand **£3-25**  
 Solder-Savbit 20 inch **52p**

Bit sizes No. 9 (1-5mm)  
 " " " 20 (3mm)  
 " " " 21 (4-5mm)  
 " " " 22 (6mm)

Ideal for Home Constructor

Tamtronik Ltd. reserves the right to change kit content without notice, where necessary to incorporate current modifications or to make valid substitution for temporarily unavailable components. The majority of the kits we advertise can be supplied from stock or compiled at short notice from component stocks held, but when ordering you should be prepared to allow at least ten days, and up to one month, for us to complete your order.

Kits can be supplied excluding P.C.B.'s and/or case. Send SAE for details naming kit and kit reference and free catalogue.

TRADE & EDUCATIONAL ENQUIRIES WELCOME

MINIMUM ORDER **£3**

PRICES INCLUDE P & P. VAT ONLY 7% ADD PLEASE

VISIT OUR SHOP AT Telephone or Letter

32 Market Place, Great Bridge, Tipton, West Midlands.

Buy it with Access

BARCLAYCARD VISA

### INDEX TO ADVERTISERS

Ace Maitronix	532	E.D.A.	466	Newnes-Butterworth	520
A.J.D.	470	Electrovalue	470	Phonosonics	468
Bi-Pak	505	George Sales, David	533	R.S.T.	531
Birkett J.	466	G.M.T. Electronics	528, 529	Radio & TV Components	469
B.N.R.E.S.	467	Greenwell	470	Swanley	530
Bull J.	527	Heathkit	520	Tamtronik	536
Collier McMillan (B.I.E.T.)	530	Home Radio	530	Technomatic	514
Colour Print Express	cover iii	I.L.P. Electronics	523	TUAC	514
C. N. Stevenson	509	Intertext (ICS)	533	Vero Electronics	466
Crescent Radio	468	Magenta Electronics	532	Watford Electronics	465
Crimson Electronics	530	Maplin Electronic Supplies Ltd.	cover iv	West London Direct Supplies	535
C.S.C.	513	Marshall A.	471	Wilmslow Audio	514
Dewtron	533	M.E.C.A.	468		
		Metac	cover ii		
		Monolith	532		

Published approximately the third Friday of each month by IPC Magazines Ltd., Kings Reach Tower, Stamford St., London SE1 9LS. Printed in England by Index Printers Ltd., Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/Sia) Ltd. South Africa—Central News Agency Ltd. Subscriptions: Inland £8.50, Overseas £9.50 per annum payable to IPC Services, Oakfield House, Perry-mount Road, Hayward Heath, Sussex. Everyday Electronics is sold subject to the following conditions namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# Why buy colour films?

When you get a Kodak colour film

# FREE

for every one you send in for processing by the Everyday Electronics Colour Print Service!



#### Send no money

But don't send any money until you see the colour of your prints. We're so confident in the reliability of the service and the quality of our prints, every one of which is checked by professionals at our laboratories.

#### Luxury colour prints

You'll be amazed at the crisp, sharp, high-definition sheen finish of the prints we supply . . . borderless to give you maximum picture area. And coming with the prints will be your FREE Kodak colour film, worth around £1, the same size as the one you sent us for processing.

#### Unbeatable value

What about prices? Ours are certainly much less than those you would pay in most shops—quite apart from the free film you get every time we develop and print for you.

Our Colour Print Service charges you only 15p for each print, plus 85p towards developing, postage and packing. The minimum charge is 85p inc. VAT (that is, if no prints can be made). The offer is limited to the UK, Eire, CI and BFPO.

#### Reliability at less cost

Photography can cost you a lot less these days. If you know how to go about it. Like the hundreds of thousands of magazine readers who are

delighted with this reliable Colour Print Service—and the replacement films that come FREE to every customer! So why don't you give it a try? Here's what you do. Send us any make of colour print film inside the envelope enclosed in this issue. Or fill in the coupon below and send it with your film in a strong envelope to: The Everyday Electronics Colour Print Service, Freepost, Teddington, Middlesex, TW11 8BR. No stamp is required.

#### More benefits to you

You benefit in two additional ways. Firstly, you enjoy a personal service with every care taken over each individual order. And secondly, you pay only for what you get—with no credit vouchers as with many other companies. An invoice comes with your prints so it's a straight business transaction.

Use this label if you haven't got an envelope, or pass it to a friend who might like to take advantage of our offer. It is used to send your prints and free film.

(Offer Excl. Minolta & Sub-miniature. Roll Film 10p surcharge 400 ASA 20p surcharge).

From: Everyday Electronics Colour Print Service, Freepost, Teddington, Middlesex TW11 8BR

Mr/Ms \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_



A quality range of British made electrical accessories plus a 'How to...' book. Do your own home electrical work with complete confidence. See cat. pages 129 to 134.



This superb organ—build the first working section for just over £100. Full specification in our catalogue.




A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!




Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.



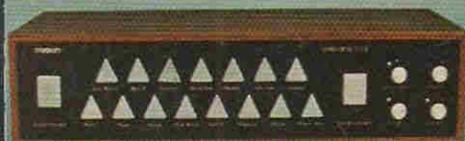A pulse width trim controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



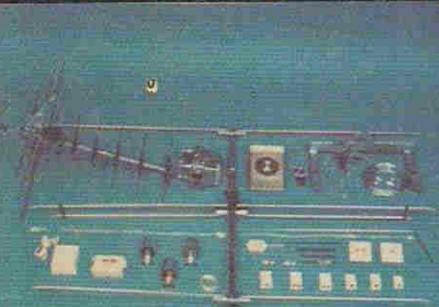Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.

# MAPLIN

**ELECTRONIC SUPPLIES LTD**

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road,  
Westcliff-on-Sea, Essex.

(Closed on Monday).

Telephone: Southend (0702) 554155.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £13.88 (incl. V.A.T. & p & p) MA1023 module only £8.42 (incl. V.A.T.).



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages—some in full colour—it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.**

Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_