

Easy to build projects for everyone

DEC. 79

45p

Everyday ELECTRONICS



**TWINKLING STAR
PEG-A-HOLE GAME
EVERLASTING CANDLE**

*Some simple presents
for you to build*

**CHECKING YOUR
CHRISTMAS LIGHTS**

plus

*Other bright ideas for
seasonal decoration*

The perfect kit
for miniature work!

ANTEX TCSU1 or 2 with CTC

NEW
TCSU2
with visual
temperature
guide



Model TCSU1

Micro-Soldering Station

Model CTC - 24volts. Priced at **£9.75** (1.87)



Model XTC - 24volts. Priced at **£9.75** (1.87)



Accurate pin point temperature control between 65° and 400°C. Heating element and sensor built in tip of the iron for fast response. Interchangeable slide-on-bits from 4.7mm (3/16") down to 0.5mm. Zero voltage switching, no spikes. No magnetic field, no leakage. Supplied with miniature CTC (35-40watt) iron or XTC (50watt). TCSU1 soldering station with XTC or CTC iron **£36** (6.44) Nett to Industry.

Model TCSU2—
Specification as TCSU1
except temperature
range 200°-400°C.
Visual temperature
indicators by square
LED at 270, 300, 330
and 360°C. Priced at
£42.50 (7.50)
Nett to Industry.

270	300	330	360°C

Model CX 17watts - 230 volts



A miniature iron with the element enclosed first in a ceramic shaft, then in stainless steel. Virtually leak-free. Only 7½" long. Fitted with a 3/32" bit. **£4.20** (.98)
Range of 5 other bits available from ¼" down to 3/64". Also available for 24volts.



Spare element Model CX230E

Model X25 25 watts - 230volts



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at **£4.20** (.98)
Range of 4 other bits available. Also available in 24volts.



Spare element Model X25/240E

Model SK3 Kit

Model SK4 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at **£5.70** (1.49)
It makes an excellent present for the radio amateur or hobbyist.



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at **£5.70** (1.49)

Model SK1

Model MLX 12volts

ST3 Stand.



This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet. 'How to Solder'. Priced at **£5.95** (1.53)




The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price **£4.55** (1.14)



A strong chromium plated, steel spring screwed into a plastic base of high grade insulating material provides a safe and handy receptacle for all ANTEX models soldering irons. Priced at **£1.50** (.57)

V.A.T. + P&P as shown in brackets ()

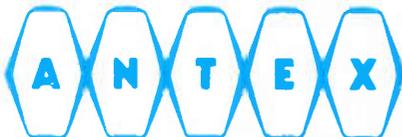

Stocked by many wholesalers and retailers or direct from us if you are desperate.

Please send me the Antex colour brochure I enclose cheque/P.O./Giro No.258 1000

Please send the following.....

Name

Address

Antex Ltd., Freepost, Plymouth PL1 1BR Tel. 0752 67377



LE12

MAGENTA ELECTRONICS LTD.

E.E. PROJECT KITS

Make us YOUR No. 1 SUPPLIER OF KITS AND COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Project kits include ALL THE ELECTRONICS AND HARDWARE NEEDED—we have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply—you construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. IF YOU DO NOT HAVE THE ISSUE OF E.E. WHICH CONTAINS THE PROJECT—YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA—39p. each.

ONE ARMED BANDIT. Oct. 79. £18-28. case extra £3-99.
HIGH IMPEDANCE VOLTMETER. Oct. 79. £18-22.
LIGHTS ON REMINDER. Oct. 79. £4-43.
SIGNAL LEVEL INDICATOR. Oct. 79. £4-81 (stereo).
UNIVERSAL OSCILLATOR. Oct. 79. £3-89.
CHASER LIGHTS. Sept. 79. £18-95.
VARIAC M.W. RADIO. Sept. 79. £5-85.
SIMPLE TRANSISTOR TESTER. Sept. 79. £5-58.
ELECTRONIC TUNING FORK. Aug. 79. £3-21. Suitble microphone & plug £1-61 extra.
WARBLING TIMER. Aug. 79. £5-99.
9V POWER SUPPLY. Aug. 79. £8-87 inc. pcb.
SWANEE WHISTLER. Aug. 79. £2-89.
TOUCH ON PILOT LIGHT. Aug. 79. £2-92.
QUIZ REFEREE. Aug. 79. £5-88.
SOLDERING IRON BIT SAVER. July 79. £7-25.
VOLTAGE SPLITTER. July 79. £3-22.
DOLLS LIGHTS ECONOMISER. July 79. £4-38 no case.
DARKROOM TIMER. July 79. £2-55.
WATER LEVEL INDICATOR. July 79. £4-92.
CONFERENCE TIMER. July 79. £39-21 inc 1 extension unit.
TREMULO UNIT. June 79. £10-87.
ELECTRONIC CANARY. June 79. £4-50.
LOW COST METAL LOCATOR. June 79. £2-14.
 Handle & coil former parts extra £4-75.
METER AMPLIFIER. June 79. £3-64.
QUAD SIMULATOR. June 79. £8-07.
INTRUDER ALARM. May 1978. £18-92. Less Ext. Buzzer & Lamp and Loop Components.
SHORT WAVE CONVERTER. May 79. £14-28 inc. cases.
THERMOSTAT. 'PHOTO' SOLUTIONS. May 79. £14-93. Less socket, tube and grease.
SHAVER INVERTER. April 79. £12-36.
TRANSISTOR TESTER. April 79. £3-59.
TOUCH BLEEPER. April 79. £3-29.
ONE TRANSISTOR RADIO. Mar. 79. with Amplifier & Headset. Less case. £4-43.
TIME DELAY INDICATOR. Mar. 79. £4-49.
VERSATILE POWER SUPPLY. Mar. 79. £9-19.
CHOKE WARNING DEVICE. Apr. 79. £3-96 case 78p.
AUDIO MODULATOR. Feb. 79. £1-58 less case and pins.
LW CONVERTER. Feb. 79. £8-82.
THYRISTOR TESTER. Feb. 79. £3-22.
ADJUSTABLE PSU. Feb. 79. £23-70. Case (horizontal layout) £3-89 extra.
I'M FIRST. Jan. 79. £3-37 less case.
LIGHTS REMINDER. Jan. 79. £4-58.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

3 BAND SHORT WAVE RADIO

Simple trf design covering 1.2-24MHz. Covers most amateur bands and short wave broadcast bands. Five controls—bandset, bandspread, reaction, wavechange and attenuator. Uses an internal 9v battery—very low current consumption. The 3 coils are all mounted on the pcb—selection is by a wavechange switch. Use with headphones or a crystal earpiece. Kit contains all the components required including the pcb and case. Instructions are included with this kit. Headphones are not included—we recommend our high impedance mono headphones.

KIT £18-97

HEADPHONES EXTRA £3-28.

1980 ELECTRONICS CATALOGUE

MAGENTA'S CATALOGUE HAS BEEN CAREFULLY DESIGNED FOR E.E. READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR THE CONSTRUCTOR. CATALOGUE INCLUDES CIRCUIT IDEAS FOR YOU TO BUILD.

NO MINIMUM ORDER—ALL PRODUCTS ARE STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE! WRITE TODAY ENCLOSING 5 x 10p STAMPS.

MAGENTA ELECTRONICS LTD.

EM11, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI.

OFFICIAL ORDERS FROM SCHOOLS, UNIVERSITIES ETC. WELCOME. MAIL ORDER ONLY.

ALL PRICES INCLUDE 15% VAT AND FIRST CLASS POST. ADD 30p TO ORDERS UNDER £10 ENQUIRIES MUST INCLUDE S.A.E.

MAGENTA gives you FAST DELIVERY BY FIRST CLASS POST OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

ONE-ARMED BANDIT

Oct 79
 Complete with 0-2" LED's and all components. £18-28.
 Case extra £3-99

CHASER LIGHTS

Sept 79
 Complete kit — with Case, plugs and sockets etc. £18-95

G. P. POWER SUPPLY

Feb 79
 0-20V 0-1A. Variable with calibrated VOLTMETER and AMMETER
 All components and Hardware £25-17.
 Case (horizontal & layout) £4-98 extra.

DOING IT DIGITALLY

Complete kit of top quality components as specified by EVERYDAY ELECTRONICS. Kit comes complete with free component identification sheets.
TTL TEST BED £28-84.
FIRST 6 months COMPONENTS £4-96.
COMPONENTS FOR PARTS 7, 8, 9 & 10 £19-98 includes: photocells I.C.'s, Resistors, Capacitors, thermistors, microphone, speaker, preatts etc.
PART 11 £2-73. PART 12 £3-19.
 Reprints:—Part 1—78p others 39p each.

LOW COST METAL LOCATOR

E.E. June 79
 WE HAVE MADE UP A COMPLETE HARDWARE KIT FOR THIS PROJECT, WITH HANDLE, COIL FORMER and SCREWS etc. Everything you need for the project, including electronics and case £9-99.
 Or separately:
 Electronics & Case £5-14.
 Hardware Kit £4-75.

TEACH IN 80

NEW SERIES—ALL COMPONENTS IN STOCK NOW FOR FAST DELIVERY. All top quality components as specified by Everyday Electronics. Out kit comes complete with FREE COMPONENT IDENTIFICATION SHEET. Follow this educational series and learn about electronics—Start today! SEND £22-95 for the TUTOR DECK and ADDITIONAL COMPONENTS parts 1-6. All orders sent by FIRST CLASS POST. Out kit contains all these parts:—

TUTOR DECK: METER, BREADBOARD, TRANSFORMER, LEADS, POTENTIOMETERS, SWITCHES, SPEAKER, PLUGS, SOCKETS, BATTERY CLIPS, WIRE, CABLE, FUSES, FUSE-HOLDERS, KNOBS. ADDITIONAL COMPONENTS. PARTS 1-6, RESISTORS, PHOTOCCELL, DIODES, CAPACITORS.

CASE WOODWORK KIT £4-98 extra. Complete kit for tutor deck woodwork, contains all the softwood, hardboard, ramin, panel pins, adhesive, screws, feet, strap-handle, and fixings. Cut to size and ready to assemble.

IDEAL SOLDERING EQUIPMENT FOR THE TEACH IN AND ELECTRONICS

ANTEX X25 SOLDERING IRON 25W £4-98
 SOLDERING IRON STAND £2-03
 SPARE BITS. Small, Standard, Large. 65p each.
 SOLDER. Handy size 75p.

DESOLDER BRAID 69p
 HOW TO SOLDER BOOKLET 12p
 HEAT SINK TWEEZERS 15p.
 SOLDER BOBBIN 30p
 DESOLDER PUMP £8-98

SWING STORAGE DRAWERS £5-98.
 MULTIMETER TYPE 3 100,000 o.p.v. with transistor tester ranges £39-95.
 WIRELESS INTERCOM 2 STATION £4-95.
 SIREN. 12V £5-95.
 P.C.B. ASSEMBLY JIG. £11-96.
 P.C.B. ETCHING KIT. £4-98.
 A.M.-P.M. AIRCRAFT BAND PORTABLE RADIO £18-95.
 WIRE STRIPPERS & CUTTERS £2-21.
 ULTRASONIC TRANSDUCERS. £5-50 pair.
 P.A. MICROPHONE coiled lead & switch £4-88.
 STEREO MICROPHONE PAIR £10-95.
 MULTIMETER TYPE 1, 1,000 o.p.v. with probes. 2" x 3 1/2" x 1 1/2" £6-78.
 MULTIMETER TYPE 2, 20,000 o.p.v. with case and probes. 5" x 3 1/2" x 1 1/2". £14-25.
 F.M. INDOOR AERIAL. 57p.
 TELESCOPIC AERIAL. 120 c.m. £2-86.
 TELEPHONE PICK-UP COIL. 72p.
 CRYSTAL MICROPHONE INSERT. 93p.
 SPEAKERS MINIATURE. 8 ohm 87p. 64 ohm 98p. 80 ohm £1-28.
 PILLOW SPEAKER. 8 ohm £1-68p.
 6" ROUND SPEAKER. 8 ohm, 5W. £2-18.
 CABINET SPEAKER. 8 ohm, 5W, 5" speaker. Cabinet 10" x 7" x 4". £7-43.
 RE-ENTRANT HORN SPEAKER. 8 ohm S.W. Horn dia. 9 1/2". £5-27.
 EARPIECES. Crystal 48p. Magnetic 18p.
 STETHOSCOPE ATTACHMENT. Fits our earpieces 98p.
 BUZZER. 6V 82p. 12V 85p.
 BONO HEADPHONES. 2K. Padded. Superior. Sensitive. £3-28.
 STEREO HEADPHONES. 8 ohm. Padded. £4-24.
 INTERCOM. 2 Station, Desk. £7-18.
 MICROPHONE DYNAMIC. 600 ohm. Cassette type. £1-38.
 DENTISTS MIRROR. Adjustable. £2-44.
 JEWELLERS EYEGLASS. £1-88p.
 TRIPLE MAGNIFIER. £5-82.
 HAND MAGNIFIER. 3" Lens. £3-43.
 SPECTACLE MAGNIFIER. Clips on to spectacle frame. £4-65.
 ILLUMINATED MAGNIFIERS. 1 1/2" lens £1-98. 3" lens £3-87.
 SIGNAL INJECTOR. £5-68.
 POCKET TOOL SET. 20 pieces. £4-99.
 SCREWDRIVER SET. Six pieces. £2-18.
 Q MAX PUNCH. 1" £2-14. 1 1/2" £2-30. 1 3/4" £2-41. 1 3/8" £2-50.
 DRILL 12V. Hand or stand use. £19-95. Stand £8-98.
 CAPACITANCE SUBSTITUTION BOX. Nine values. 100pF—0.22uF. £2-88.
 QUICKTEST. Mains connector. £6-41.
 PLUG IN POWER SUPPLY. 6, 7.5-9V d.c. 300mA. £4-85.
 SPRINGS—SMALL. 100 Asstd. £1-68.
 CROC CLIP TEST LEAD SET. 10 leads with 20 clips. £1-98.
 DIMMER SWITCH. 240V. 800W. £4-48.
 TRADITIONAL STYLE BELL. 3-5V. 70mm chrome gong. £1-80.
 UNDERDOME BELL. 4-10V. Smart. Dia. 70mm. £2-27.
 TOWERS INTERNATIONAL TRANSISTOR SELECTOR. New edition. £9-22.
 F.M. TUNER CHASSIS. 88-108MHz. 9V d.c. £9-10.
 MORSE KEY. High speed. £3-83.
 PANEL METERS. 60 x 45mm. Modern style. 50uA, 100uA, 1mA, 1A, 25V d.c. £6-33.
 NIGHT LIGHT. Plug type. £1-98.
 CONNECTING WIRE PACK. 5 x 5yd. coils. 35p.
 VERO SPOT FACE CUTTER. £1-06.
 VERO PIN INSERTION TOOL. 0-1" £1-48. 0-15" £1-45.
 RESISTOR COLOUR CODE CALCULATOR. 21p.

SEIKO MEMORY BANK

Calendar watch M354
Hours, mins., secs.
Month, day, date in
12 or 24 hour format
all indicated continuously.
Monthly calendar display
month, year and all dates
for any selected month over
80 year period.
Memory bank function.
Any desired dates up to 11
can be stored in advanced.
2 year battery life.
Water resistant.
Metac Price



£79.50

M11

SEIKO Alarm Chronograph

With WEEKLY Alarm.
Hours, mins, secs, month,
date, day, am/pm.
Weekly alarm - can be set
for every day at designated
time e.g. 6.30 am on Mon,
Wed and Friday.
Alarm set time displayed
above time of day.
Full stopwatch functions,
laptime, split etc.



£89.95

M10

SEIKO Melody Alarm Chronograph

Chiming Alarm,
plus chrono.
Hours, mins, secs, date,
day, 24 hour alarm, 12
hour chronograph, 1/10th
secs, Laptime, Back light.
Stainless steel, mineral
glass.



METAC PRICE

£92.95

M19

SEIKO Calculator Watch

Full specification
calculator with
memory, plus multi
function watch.
Hours, mins, secs,
day, date, backlight,
Automatic calendar.
Long life battery.



£99.95

M27

CASIO CHRONO 95QS-3LB

Stainless steel case
water resistant to 66 feet.
Hours, mins, secs, am/pm,
year, month, date, day.
Auto-calendar
pre-programmed
until the year 2029.
12/24 hour. Stopwatch
function.
Range 7 hours, 1/100 sec.
(Mode) Net time/lap-time/
1st-2nd place times.
Dual time function.
Accuracy 15 secs per month.
Battery life approx 4 years.



£22.95

M22

CASIO LADIES 86CL-23B-1

Elegant slim line.
Stainless steel bracelet,
fully adjustable.
Hour, mins, 10 sec symbol
second by flash, am/pm.
Month, date, day.
Auto-calendar preprogrammed
for 28th day in Feb.
Accuracy per month 15 secs.
Battery life approx 15 months.



£29.95

M23

CASIO F-200 Sports Chrono

Attractive Mens watch
in black resin with
mineral glass.
Hours, mins, secs, am/pm.
Month, date,
alpha-numeric day.
Auto-calendar set
28th Feb.
Stopwatch working
range 1 hour,
units 1/100 sec. Mode.
Net Time/lap/time/
1st-2nd place times.
Accuracy approx 15 secs
per month.
Battery 12 months.



£14.95

M24

CASIO ALARM CHRONO 81CS-36B

Hours, mins, secs, day,
and also day, month and year
perpetual automatic calendar.
100th sec chronograph to
7 hours.
Net time/lap/time/1st
and 2nd place times. User
optional 12/24 hr display. 24
Alarm. User optional,
hourly chime.
Backlight, mineral glass,
stainless steel.
Water resistant to
100ft.
Battery life approx 4 years.



£34.95

M25

BELTIME Chronograph

(9-Functions)
Hours, mins, secs,
date, day, month,
interchange feature,
automatic calendar,
backlight, Net
time/lap/time.
Stainless steel bracelet.
Battery life 1 year.



£14.95

M34

BELTIME Multi Alarm

29 Functions
Hours, mins, secs,
date, day.
Alarm, chronograph,
Light.
Watch 8 functions,
Alarm 4 functions,
chronograph 17
functions.
Stainless steel
bracelet.



£29.95

M35

CASIO F-8C 3 Year Battery life.

Hours, mins, secs,
am/pm, date, day.
Auto calendar set
28th Feb.
Stopwatch function.
Accuracy 15 secs per
month. Battery life
approx 3 years.



£9.95

M36

CASIO CALENDAR 200

47CS-23B-1 Black. Stainless steel.

Hours, mins, 10 second
symbol, second (by flash),
am/pm. Month, day, date.
Auto-calendar set from
1901 to 2009.
Full month calendar display.
Dual time function.
Accuracy 10 secs per
month. Battery life
approx 15 months.



£59.95 M37

MELODY Multi Alarm Chronograph

Hours, mins, secs,
Day, Date, Count-
down alarm,
Dual time zone,
1/100th sec
stopwatch.
Lap/split time,
1st and 2nd place
times, Melody test
function.



£26.95

M30

DUAL TIME-ALARM CHRONOGRAPH

Incorporating module
of world famous
Japanese watch
manufacture.
Hours, mins, secs,
days of week, month,
day and date,
24 hour alarm,
12 hour chronograph,
1/10th secs,
lap time, Back light,
stainless steel case
and bracelet,
Mineral glass,
Battery hatch,
long life battery.



£35.00

M12

PICOQUARTZ Microprocessor Alarm Chronograph

Multilanguage-day of
the week can be set
to English, French,
German, Italian or
Spanish.
Chime - every full
hour combined with a
response signal,
beeping at every
pressing of the
functions.
Can be switched off.
12-24 hour format.
Backlight.
Chrono - 1, full scale
chrono with lap,
counting hours upto
24 hrs. Mins, secs.
1/100th secs.
Two Alarm systems.
Two time zones.



£37.95

M32

SEIKO CHRONOGRAPH

Hours, mins, secs
and day of the week.
Month date and
day of the week.
Stopwatch display -
Hours, mins, secs
up to 12 hours
(mins, secs, 1/100 secs
up to 20 minutes).
Lap timing,
Continuous time
measurement of two
competitors.
Stainless steel,
mineral glass.



£56.00

M33

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch. Very slim, only 6mm thick.



M1

SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins, secs., day. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

QUARTZ LCD 11 Function. SLIM CHRONO

6 digit, 11 functions. Hours, mins, secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold! Guaranteed same day despatch.



M3

QUARTZ LCD ALARM 7 Function

Hours, mins., secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

MULTI ALARM 6 Digits 10 Functions

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual zone.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

£18.65

M5



FRONT-BUTTON Alarm Chrono Dual Time

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Qual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet. Guaranteed same day despatch

£22.65

M6



SOLAR QUARTZ LCD Chronograph with Alarm Dual Time Zone Facility

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec., steps. Split and lap timing modes. Qual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

£27.95

M7



ALARM CHRONO with 9 world time zones

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

£29.65

M8



SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins, secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£13.65

Guaranteed same day despatch.

M9



QUARTZ LCD Ladies Day Watch

Only 25 x 20mm and 6mm thick. Hours, minutes, seconds, day, date, backlight and auto calendar. Elegant metal bracelet in silver or gold fully adjustable to suit very slim wrists. State colour preference.

£9.95

Guaranteed same day despatch.

M15



QUARTZ LCD Ladies Fashion Watch

Elegant bracelet in bronze/gold finish or silver colour. Hours, mins, secs, day, date, backlight and auto calendar. Adjustable for the slimmest of wrists. State colour preference.

£14.95

Guaranteed same day despatch

M17



QUARTZ LCD Ladies Cocktail Watch

Highly functional watch which also suits those special occasions. Beautifully designed with a very thin bracelet which retains strength as well as elegance. Hours, mins, secs, day, date, backlight and autocalendar. Bracelet fully adjustable to suit slim wrists. State gold or silver finish.

£19.95

Guaranteed same day despatch

M18



HANIMEX Electronic LED Alarm Clock



Features and Specification
Hour minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9 minute snooze. Display bright dim modes control. Size: 5 15" x 3 93" x 2 36" (131mm x 113mm x 60mm)
Weight: 1.43 lbs (0.65 kg) AC power 220V.

£10.20 Thousands sold!

Mains operated.

Guaranteed same day despatch

M13

EXECUTIVE ALARM WATCH

6 Functions plus Alarm: Conference signal, 5 minute snooze alarm. Conference signal sounds 4 secs., before main alarm to give advance warning and an option to cancel. Snooze sounds 5 mins., after main alarm and is always preceded by the conference signal.

£14.95

M60



MACY QUARTZ ANALOGUE

Automatic Calendar Day and Date infinite bracelet. This mans watch has elegance as well as the robust appearance provided by a watch with traditional features. Accuracy is provided by a quartz crystal powered by a long life miniature battery.

£24.95

M21



Metac price breakthrough for an Alarm Chronograph with Qual Time only

£18.95



OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
 - **CALENDAR FUNCTIONS** include the date and day in each time zone.
 - **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
 - On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
 - **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!
- Guaranteed same day despatch. **M16**

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and order details clearly, enclose 40 pence per single item for post and packing or the amount stated in the advert. All products carry 1 year written guarantee and full money-back 10 day reassurance. Battery fitting and electronic calibration service is available to customers at any Metac shop. All prices include VAT currently at 15%.

Metac Wholesale:

Trade enquiries - send for a complete list of prices for all the goods advertised plus many more not shown also minimum order details.

Telephone orders: Credit card customers can telephone orders direct to Oavertry (03272) 76545 or Edgware Rd. 01-723 4753 24 hours a day.



Service Enquiries 03272-77659

CALLERS WELCOME Shops open 9-30am-6.00

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753


THE NEW

EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £7.25 inc. VAT & P.P.

THE UNIQUE

EUROBREADBOARD

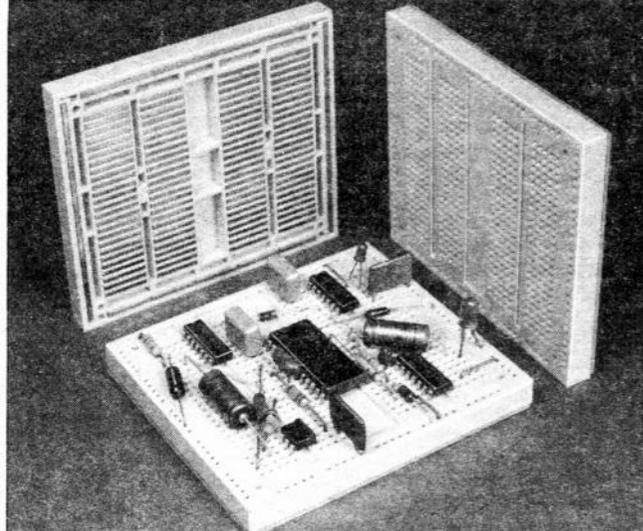

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m, ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £6.20 each or £11.70 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

EE 10/79

Please send me 1 EuroSolderSucker @ £7.25 Please
or 1 EuroBreadBoard @ Tick
or 2 EuroBreadBoards @ £11.70

All prices are applicable from July 1st 1979 and include VAT + P.P. but add 15% for overseas orders.

Name.....

Company.....

Address.....

Tel. No.....

Please make cheque/P.O.'s payable to David George Sales

TUNE IN!

Build the World Famous CHROMA-CHIME



Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built ABS cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

ONLY £9.95
+ 75p p&p
UK ONLY

* Save pounds on normal retail price by building yourself.

TMS 1000N - MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.



New low price only **£4.95** inc. p&p

R/C MODELLERS - LISTEN FOR THE C.B. MENACE GET A 27MHZ MONITOR

- * Audibly confirm your channel's clear.
- * Tunes over whole 27mhz model band. (CB)
- * Receives normal broadcast AM/FM bands as well.
- * Sensitive with telescopic aerial.
- * Totally portable.
- * Runs on standard batteries.

This neat three band Superhet receiver not only provides an invaluable service, checking your channel and TX, but gives normal broadcast reception when you need it as well. Costing less than a decent Servo, you'll find it cheap and reassuring insurance!

ONLY £17.95
INC. V.A.T.
AND P. & P.



ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME _____

ADDRESS _____

I enclose cheque/PO value £ _____

or debit my ACCESS/BARCLAYCARD account no.

Signature _____

CHROMATRONICS

Everyday Electronics, December 1979

Technowledgey for sale.

The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT

With Hyperfi Series modules £185.00 + £23.12



ALL TUNER KITS £3 carriage

Features of the system:

- * Precision construction & design of all parts
- * Time/frequency display
- * State of the art performance with facilities for updates, using modular plug in systems.
- * Deviation level calibrator for recording
- * All usual tuner features

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gang) tuned FET tunerhead, with ceramic IF filters and interstation mute; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.95 VAT
Complete with digital frequency readout/clock-timer hardware £99.00 + £14.85 VAT
Complete with MA1023 clock/timer module with dial scale £66.00 + £9.90 VAT
Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

LW/MW/FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RF! - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV. Complete kit £19.50 + £2.93 VAT, built and tested module £27.00 + £4.05VAT
part two of the catalogue contains details of the MSM5523/4/5/6 range, and the versatile MSL2318 divide by ten or hundred prescaler IC. The DFM1 combined counter for AM, FM SW and direct/clock/stopwatch/timers - details available, but SAE please!



PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00+£5.55vat

VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design but using standard (funde9) crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 +£3.90vat

MICROMARKET

6800P	650P	8212	230P	2102	170P
6820P	600P	8216	195P	2112	340P
6850P	275P	8224	350P	2513	754P
6810	400P	8228	470P	4027	578P
6852	365P	8251	625P	2114	1000P
8080	630P	8255	540P	+15% VAT	

OSTS: Remember all OSTS stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering.

TTL Standard AND LP Schottky

All prices listed in pence x

LSV		NSV		LSV		NSV		
N	LSV	N	NSV	N	LSV	N	NSV	
7400	13	20	7472	28	74142	265	74257	108
7401	13	20	7473	32	74143	312	74260	153
7402	14	20	7474	27	74144	312	74273	124
7403	14	20	7475	38	74145	65	74283	120
7404	14	20	7476	37	74146	97	74293	95
7405	18	26	7478	38	74147	175	74303	95
7406	38	48	7480	48	74148	109	74365	49
7407	38	48	7481	86	74149	191	74366	49
7409	17	24	7481	86	74150	99	74367	43
7410	15	24	7482	69	74151	64	74368	49
7411	20	24	7485	104	74152	64	74373	7
7412	17	24	7486	40	74153	64	74374	7
7413	30	36	7486	20	74154	96	74377	124
7414	51	7490	33	90	74155	110	74379	130
7415	24	7490	33	90	74156	60	74393	140
7416	30	7492	38	78	74157	210		
7417	30	7493	32	78	74158	82		
7420	16	24	7494	78	74159	210		
7421	20	24	7495	65	74160	82		
7422	27	36	7495	65	74161	78		
7423	27	36	7496	58	74162	130		
7425	27	36	7497	185	74163	98		
7426	27	36	7498	185	74164	104		
7427	27	36	7499	185	74165	105		
7428	35	39	7410X series		74166	105		
7429	35	39	74107	32	74167	20		
7430	17	24	74108	63	74168	200		
7431	17	24	74110	54	74169	200		
7432	25	24	74111	68	74170	230		
7433	25	24	74112	68	74171	230		
7434	33	24	74113	38	74172	625		
7435	33	24	74114	38	74173	67		
7436	33	24	74115	38	74174	67		
7437	33	24	74116	38	74175	67		
7438	33	24	74117	38	74176	75		
7439	33	24	74118	38	74177	75		
7440	17	24	74119	38	74178	110		
7441	74	74	74120	115	74179	110		
7442	70	99	74121	25	74180	165		
7443	115	115	74122	46	74181	165		
7444	112	115	74123	46	74182	210		
7445	94	74	74124	46	74183	135		
7446	94	74	74125	46	74184	135		
7447	82	89	74126	46	74185	134		
7448	56	99	74127	46	74186	175		
7449	56	99	74128	137	74187	92		
7450	56	99	74129	137	74188	105		
7451	17	24	74130	38	74189	105		
7452	17	24	74131	38	74190	99		
7453	17	24	74132	73	74191	99		
7454	17	24	74133	73	74192	105		
7455	17	24	74134	73	74193	105		
7456	17	24	74135	60	74194	105		
7457	17	24	74136	60	74195	99		
7458	17	24	74137	60	74196	99		
7459	17	24	74138	60	74197	110		
7460	17	24	74139	60	74198	150		
7461	17	24	74140	60	74199	160		
7462	17	24	74141	56	74200	90		
7463	17	24	74142	56	74201	90		
7464	17	24	74143	56	74202	90		
7465	17	24	74144	56	74203	90		
7466	17	24	74145	56	74204	90		
7467	17	24	74146	56	74205	90		
7468	17	24	74147	56	74206	90		
7469	17	24	74148	56	74207	90		
7470	17	24	74149	56	74208	90		
7471	17	24	74150	56	74209	90		
7472	17	24	74151	56	74210	90		
7473	17	24	74152	56	74211	90		
7474	17	24	74153	56	74212	90		
7475	17	24	74154	56	74213	90		
7476	17	24	74155	56	74214	90		
7477	17	24	74156	56	74215	90		
7478	17	24	74157	56	74216	90		
7479	17	24	74158	56	74217	90		
7480	17	24	74159	56	74218	90		
7481	17	24	74160	56	74219	90		
7482	17	24	74161	56	74220	90		
7483	17	24	74162	56	74221	90		
7484	17	24	74163	56	74222	90		
7485	17	24	74164	56	74223	90		
7486	17	24	74165	56	74224	90		
7487	17	24	74166	56	74225	90		
7488	17	24	74167	56	74226	90		
7489	17	24	74168	56	74227	90		
7490	17	24	74169	56	74228	90		
7491	17	24	74170	56	74229	90		
7492	17	24	74171	56	74230	90		
7493	17	24	74172	56	74231	90		
7494	17	24	74173	56	74232	90		
7495	17	24	74174	56	74233	90		
7496	17	24	74175	56	74234	90		
7497	17	24	74176	56	74235	90		
7498	17	24	74177	56	74236	90		
7499	17	24	74178	56	74237	90		
7500	17	24	74179	56	74238	90		

Current news: A PCB for the Mullard DC tone and volume control system is now available £3 + 0.45 VAT. HMOS PA modules for 60-100W - kit £14 + £2.10VAT, heatsink £4.10+0.61. FM radio control system crystals £3.75 pair inc VAT (Sept on). MK50366N: static drive clock/timer IC £3.78 + 0.57 VAT. 12kHz channel spacing 8 pole 10.7MHz XTAL filter by TOYO type HA4002 £15.50 + £2.32VAT. A further updated price list is now available, and we would like to remind you that enquiries can only be answered if accompanied either by an official business letterhead, or an SAE. STOP PRESS: TOKO's new split-apart triple AM tuning diodes are in stock £2.45 + 37p VAT, (KV1215). S BL1 diode D100 - £4.25+0.64p. Terms: CWO please. Account facilities for commercial customers O/A. Postage 25p per order. Minimum credit invoice for account customers £10.00. Please follow instructions on VAT, which is usually shown as a separate amount. Overseas customers welcome - please allow for postage etc according to desired shipping method. Access facilities for credit purchases. Catalogues: Ambit. Part 1 45p. Part 2 50p 90p pair. TOKO Euro shortform 20p. Micrometals toroid cores 40p. All inc PP etc. Full data service described in price list supplements. Hours/phone: We are open from 9am-7pm for phone calls. Callers from 10am to 7pm. Administrative enquiries 9am to 4.30pm please (not Saturdays). Saturday service 10am to 6pm.

RADIO AND AUDIO MODULES: Consistently the most advanced FOR FM

EF5801-3-4 series: 6 stage varicap tuning, all with oscillator output
5801 Dual gate MOSFET RF stages, bipolar mixer £17.45 + 2.61VAT
5803 Dual gate RF/mixer stages, amplified LO out £19.75 + 2.96VAT
5804 'Hyperfi' series, with internal PIN diode apc, and ultra wide range tuning system £24.95 + 3.74VAT
EF5402 4 stage varicap tuner with TDA1052 and LO output. Uses FET/IC input. PIN apc £10.75 + 1.61VAT

FOR 30-200MHz

The EF series are available on special order to cover bands (usually approx 20% of the centre frequency) in the range described. Details in our price list.
FOR FM IFs at 10.7MHz
7030 single 6 pole linear phase filter IF with HA1137E10.95 + 1.64VAT
7130 two 6 pole linear phase filter IF with CA3189E16.25 + 2.44VAT
7230 Hyperfi IF, switched bandwidth, AGC IF preamp, linear phase ceramic filters with diode switched narrow filter £24.95+3.74VAT

DECODERS FOR MPX (STEREO)

Various types, guaranteed the world's biggest and best ranges
LARSHOLT FM TUNERSSETS
7252 MOSFET front end combined with CA3089 IF £26.50 + 3.97VAT
7252 JFET front end, combined with IF and decoder £26.50 + 3.97VAT
FM/AM tuning synthesiser, see details elsewhere in this advertisement

COMPONENTS FOR RADIO/COMMUNICATIONS/AUDIO/TV etc.

As usual, Ambit brings you the latest and best, a small selection of which is shown in this advertisement. The Ambit catalogues contain information on most of the devices mentioned here - and an order for the new part three will ensure you stay up with latest developments. Data photocopying service described in price list info.
RADIO ICs for FM varicap £16.00 series
CA3089E 1.94 29 SL1610 1.60 24 LM381N 1.81 27
CA3189E 2.45 37 SL1611 1.60 24 LM382N 1.65 25
HA1137W 2.20 33 SL1612 1.60 24 KB4436 2.53 38
HA11275 2.20 33 SL1613 1.89 28 KB4438 2.22 33
SN7660N 0.75 11 SL1620 2.17 33 TDA1028 3.50 51
RADIO ICs for AM/FM SL1621 2.17 33 TDA1029 3.50 53
TDA1090 3.35 50 SL1623 2.44 37 TDA1074 3.75 56
TDA1083 1.95 29 SL 624 3.28 49 Audio power
TDA1220 1.40 21 SL1625 2.17 33 TB8A20M 0.75 11
IF AMPLIFIERS SL1626 2.44 37 TB8A10AS 1.09 16
LM380N 1.00 15
K84406 0.50 07 SL1630 1.62 24 ULN28B3 1.00 15
MC1350 1.20 18 SL1641 1.89 28 TDA2002 1.95 29
see comms lcs also SL1642 1.89 28 HA1370 2.99 45
COMMUNICATIONS SL6640 2.75 41 TDA2020 2.99 45
K84412 2.55 38 MC3357 3.12 47 FETs, MOSFETs, bipolars
K84413 2.75 41 MC1496 1.25 19 and various others: see PL
S06000 3.75 56 NE544 1.70 25

MORE FROM THE GENERAL AMBIT CATALOGUE RANGES:

1.9v AM tuning (C: 15:1) from TOKO
KV1211 double matched 175p 26p vat
KV1210 triple matched 245p 37p vat
KV1215 triple snap-attach 245p 37p vat
MVAM115 single 15v 105p 16p vat
MVAM125 single 25v 105p 16p vat
MVAM2 double 25v 148p 22p vat
BB204/104 double FM 40p 6p vat
BA102 single AFC etc 30p 4p vat
BA121/IT10 single etc 30p 4p vat
BB105B single UHF 40p 6p vat
PIN DIODES, 8ANDSWITCH types
BA479 PIN attenuator 35p 5p vat
TD1061P pin atten. 95p 14p vat
BA182 Bandswitch 21p 3p vat
All RF semiconductor stocks in depth. Please ask for quantity pricing details.

TOP GRADE LEDS by AEG. PRICES ARE EXC. VAT (add 15%)

SIZE	Red	Green	Yellow	Orange	Quantity discount
5mm	14p	16p	15p	20p	10 per type - less 10%
3mm	13p	15p	18p	19p	100 per type - less 30%
2x5x15	17p	20p	20p	24p	100 mix in 10s - less 25%

FUTABA FLUORESCENT VACUUM DISPLAYS FOR CLOCK etc

5LT02 clock display (static drive) with AM/PM flags £9 + 1.35
5LT03 DFM display for MSM5525 LSI counter £9.45 + 1.42 vat
6LT06 5 digit DFM display (GI AY58100) mpxed £9.75 + 1.46 vat

TOKO COILS, FILTERS, CHOKES, etc for AM/FM/TV comms -

TYPE	Size: 5mm	7mm	10mm	(please add VAT @15%)

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume. Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200/250V. PRICE \pounds 18-40, P. & P. \pounds 21-20

HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 30 watts music power. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12 1/2in wide \times 5in high \times 7 1/2in deep. Special introductory price \pounds 29-00 + \pounds 2-50 carriage and packing.



MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV r.m.s. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w \times 4" h \times 9 1/4" d approx.

LIMITED NUMBER ONLY at \pounds 29-00 + \pounds 1-50 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylish finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 50p + SAE (Free with parts). All parts sold separately ONLY \pounds 18-40, P. & P. \pounds 1-40. Also available ready built and tested \pounds 22-50, P. & P. \pounds 1-40.

STEREO DECODER MK.II.

SIZE 1 1/2" \times 2 5/16" \times 1 1/2" ready built. Pre-aligned and tested for 10-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions supplied. \pounds 7-00 plus 20p. P. & P. Stereo beacon light if required \pounds 40 extra.

SPECIAL OFFERS

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coil speakers, telescopic aerial and internal ferrite aerial. Earpiece socket for personal listening. Finished in attractive simulated leatherette. Size 7" H \times 9 1/4" W \times 4" D approx. Fully guaranteed. Bargain price of only \pounds 10-25 + \pounds 1-30 p. & p. Mullard LP1159 RF-IF module 470KHz \pounds 2-50 + P. & P. 20p. Specification and connection details supplied. Fye VHF FM Tuner Head covering 88-108MHz 10-7 MHz I.F. output. 7-8V + earth. Supplied pre-aligned, with full circuit diagram with precision-ganged F.M. gang and 323PF + 323PF A.M. Tuning gang only \pounds 3-40 + P. & P. 35p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2" \times 1 1/4" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only \pounds 8-80 each + p. & p. (one 90p, two \pounds 1-10). Now available in 8" round version. 10 watts RMS 60Hz 20KHz \pounds 6-30. P. & P. (one 65p, two 75p).

STEREO MAGNETIC RPE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. 1dB from 20Hz to 20KHz. Input impedance 47K. Size 10" \times 20" \times 50H. \pounds 3-20 + 20p P. & P.

All prices and specifications correct at time of press and subject to alteration without notice. PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

HARVERSON SURPLUS CO. LTD. (Dept. E.E.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station. Open 930-530 Mon. to Fri. 930-5 Sat. Closed Wed.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speaker from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω ; Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp. Overall Size 12" w \times 8" d \times 2 1/2h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT \pounds 14-95 P. & P. 80p (Magnetic input components 33p extra).
POWER PACK KTI \pounds 6-20 P. & P. 95p
CABINET \pounds 6-20 P. & P. 95p

SPECIAL OFFER—only \pounds 25-80 if all 3 items ordered at one time plus \pounds 1-25 p. & p.

Full after sales service
Also avail. ready built and tested \pounds 32-20, P. & P. \pounds 1-50.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" \times 11" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only \pounds 10-40 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at \pounds 2-15 + 40p P. & P. if required. Full connection details supplied.

VYNAIR & REXINE SPEAKERS & CABINET FABRIC app. 54 in. wide. Our price \pounds 2-30 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

S. & R. BREWSTER LIMITED

WHY PAY MORE?

for Miniature Soldering Irons & Accessories		PRICE EACH	P & P Extra EACH
S.R.B. 18 watt Soldering Iron available in 12, 110 & 240 Volts, fitted with No 20 bit		\pounds 4-43	+ 24p
SPARE BITS	No 19 size 1.5mm or No 20 size 3mm or No 21 size 4.5mm or No 22 size 6mm	52p	—
	No 78 1C Desoldering Bit	\pounds 1-04	+10p
	No. 1920L Long Life Bit	\pounds 1-12	70p
SAFETY STAND		\pounds 4-23	+ 10p
SOLDER	Savbit 20	61p	+ 9p
	Savbit 10	32p	+ 5p
	Lowmelt 10	76p	+10p

INDUSTRIAL/RETAIL ENQUIRIES WELCOME FOR THE ABOVE

We also Offer & Recommend for Mail Order & Personal Callers Only

	PRICES EACH including V.A.T. and P. & P.
Oryx 50 Temperature Controlled Soldering Iron	\pounds 11 75
Spare tips for above	\pounds 1 39
Isotip quick charge rechargeable Soldering Iron	\pounds 24 60
Spare tips for above	\pounds 3 42
Cable 7/0.2 11 Colours 100 meter reel	\pounds 2 40
0.1 Veroboard 3 1/2" \times 11 1/2"	\pounds 2 00
0.1 Veroboard 4 1/4" \times 18"	\pounds 4 50
Copper Clad board single sided	75p
Watchmakers Side Cutters	\pounds 5 85
Watchmakers Pliers	\pounds 4 75
Transformer 100VA 2 \times 12V 4.1A	\pounds 11-20

OTHER ITEMS ALSO AVAILABLE ASK FOR LIST S.A.E.

MAIL ORDER DEPT.
86-88 Union Street, Plymouth
PL1 3HG Tel:(0752)65011

THE MIGHTY MIDGETS

Please Quote your Number when ordering

ELECTROVALUE

Your leading direct suppliers for



NASCOM MICROCOMPUTERS AND FULL SUPPORTING RANGE OF ITEMS TO ENABLE YOU TO WORK AT PROPER PROFESSIONAL LEVELS

- ★ At newest reduced prices.
- ★ Widest possible range stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

Appointed distributors for the fine products of:

SIEMENS, ISKRA, RADIOHM, VERO AND MANY OTHER FAMOUS MANUFACTURERS

It's a good deal better from

ELECTROVALUE LTD

Dept. EE12, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 9HB.
Phone: EHAM 33603. (London, dial 87 first; STD 0784). Telex 264475.
Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

BE AMONG THE VERY FIRST TO RECEIVE YOUR FREE CATALOGUE 10 (ready shortly) BY SENDING YOUR NAME AND ADDRESS NOW (124 pages-packed with items, illustrations, etc.)

- We pay postage in U.K. on orders list value \pounds 5 or over. If under, add 30p handling charge.
- We give discounts on C.W.O. orders, except for a few items marked Net or N in our catalogues. on orders, list value 5% \pounds 10 or more on orders list value 10% \pounds 25 or more. Not on Access or Barclay card purchase orders.
- We stabilise prices. by keeping to our printed price lists which appear but three or four times a year.
- We guarantee all products brand new, clean and to maker's spec. No seconds, no surplus.



How to make a hobby

The opportunities in electronics, today, and for the future are limitless – throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics – especially for the servicing of radio, TV and all associated equipment – can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.

We give modern training courses in all fields of electronics – practical D.I.Y. courses – courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.


All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.

and a career.


COURSES AVAILABLE

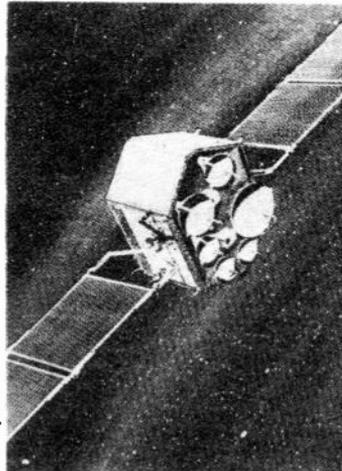- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free 32 page Colour Booklet.

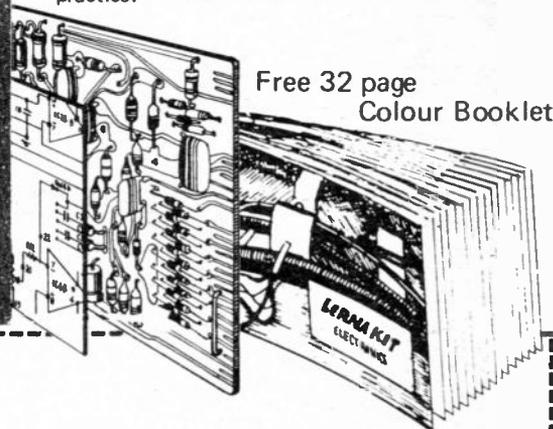

WE ARE AN INTERNATIONAL SCHOOL SPECIALISING IN ELECTRONICS TRAINING ONLY AND HAVE OVER 40 YEARS EXPERIENCE IN THIS SUBJECT.

EE/A/1/80

NAME.....
 ADDRESS

Block Caps Please

Post now, without obligation, to:-

BRITISH NATIONAL RADIO and ELECTRONICS SCHOOL
 P.O. Box 156, Jersey, Channel Islands.

BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	£0 50
BP14	2nd Book Transistor Equivs. & Subs.	£1 10
BP24	52 Projects Using IC741 (or Equiv)	£0 95
BP26	Radio Antenna Book Long Distance Reception & Transmission	£0 85
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	£0 60
BP32	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	£1 00
BP35	50 Ccts use Germ/Sil/Zener Diodes	£1 25
BP36	50 Field Effect Trans Projects	£0 75
BP39	Digital IC Equivs & Pin Connection	£1 25
BP40	Linear IC Equivs & Pin Connection	£2 50
BP41	50 Simple LED Circuits	£2 75
BP42	How to make Walkie Talkies	£0 75
BP43	Projects on Opto-electronics	£1 25
BP44	Radio Circuits Using IC's	£1 25
BP45	Mobile Discotheque Handbook	£1 35
BP46	Electronics Projects for Beginners	£1 35
BP47	Popular Electronic Projects	£1 45
BP48	IC LM3900 Projects	£1 35
BP49	Radio Stations Guide	£1 45
BP50	Cold Design & Consequence Manual	£0 75
BP51	Handbook of Integrated Circuits	£1 35
BP202	Equivalent & Substitutes	£1 00
BP205	1st Book of Hi-Fi Speaker Enclosures	£0 75
BP213	Circuits for Model Railways	£1 00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	£0 85
BP217	Solid State Power Supply Handbook	£0 85
BP221	28 Test and Transistor Projects	£1 25
BP222	Short-wave Receivers for Beginners	£0 95
BP223	50 Projects using IC CA3130	£0 95
BP224	50 CMOS IC Projects	£0 95
BP225	A Practical Intro to Digital IC's	£0 95
BP226	Build Advanced Short-wave Receivers	£1 20
BP227	Beginners Guide to Building Electronic Projects	£1 25

NEWNES BOOKS

216	Transistors 3rd Ed.	£1 00
217	Integrated Circuits	£1 00
218	Radio & Television	£1 25
219	Electronics	£1 15
220	Colour TV 2nd Ed.	£1 15
221	Hi-Fi	£1 15
222	20 Solid State Proj. for Car	£1 95
223	20 Solid State Proj. for Home	£1 95
224	110 Int. Circ. Proj. for Home	£2 95
225	110 Thyristor Projects	£2 50
226	Operational Amp Proj. for Home	£2 50
228	Electricity	£1 15
229	Beginners Guide to Electronics	£2 25
230	Beginners Guide to Television	£2 25
231	Beginners Guide to Transistors	£2 25
232	Beginners Guide to Electric Wiring	£2 25
233	Beginners Guide to Radio	£2 75
234	Guide to Colour TV	£2 25
235	Electronic Diagrams	£1 80
236	Electronic Components	£1 80
237	Printed Circuit Assembly	£1 80
238	Transistor Pocket Book	£3 90
239	50 Photoelectric Circuits	£1 80
240	Semiconductor Handbook Part 1	£5 25
241	Semiconductor Handbook Part 2	£4 28
242	Electronics Pocket Book	£3 30
244	Beginners Guide to Integrated Circuits	£2 75
209	BI-PAK TTL Data Book	50p
	BI-PAK CMOS Data Book	50p

SWITCHES

Description	No.	Price
DDT miniature slide	1975	£0 16
DPDT standard slide	1973	£0 17
Toggle switch SPST 1/2 amp 250V ac	1970	£0 38
Toggle switch DPDT 1 amp 250V ac	1976	£0 48
Rotary on-off mains switch	1977	£0 58
Push switch — Push to make	1978	£0 16
Push switch — Push to break	1979	£0 21

Colour	No.	Price
RED	1980	£0 35
BLACK	1981	£0 35
WHITE	1982	£0 35
BLUE	1983	£0 35
YELLOW	1984	£0 35
LUMINOUS	1985	£0 35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0 81
Miniature SPST toggle 2 amp 250V ac	1959	£0 86
Miniature DPDT toggle 2 amp 250V ac	1980	£0 91
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1 07
Push-button SPST 2 amp 250V ac	1962	£1 04
Push-button SPST 2 amp 250V ac	1963	£1 09
Push-button DPDT 2 amp 250V ac	1964	£1 34

Description	No.	Price
1 pole 12 way	1965	£0 55
2 pole 6 way	1966	£0 55
3 pole 4 way	1967	£0 55
4 pole 3 way	1968	£0 55

Description	No.	Price
Plastic button givess simple 1 pole change over action		
Rating 10 amp 250V ac	1970	£0 29

OPTOELECTRONICS

NEW INCREASED RANGE—ALL 1st QUALITY LED's (diffused)

O/no.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (125)	RED	£0 12
1502	MIL332 (TIL211)	3mm (125)	GREEN	£0 22
1503	MIL3331 (OP212A)	3mm (125)	YELLOW	£0 22
1504	ARL4850 (FLV117)	5mm (2)	RED	£0 12
1505	MIL 5251 (TIL222)	5mm (2)	GREEN	£0 22
1506	MIL5351 (MV5353)	5mm (2)	YELLOW	£0 22
1509	FLV111	5mm (2)	CLEAR (IIR Red)	£0 13

SUPER 'HL-Brite' Type

O/no.	Type	Size	Colour	Price
1521	MIL32	3mm (125)	RED	£0 12
1522	MIL32	5mm (2)	RED	£0 12
1514	ORP12	Light dependent resistor		£0 63
1520	OC711	Photo transistor		£0 40

LED CLIPS

1508/125	pack of 5	125 clips	£0 17
1508/2	pack of 5	2 clips	£0 21

DISPLAYS:

Description	Common Anode o/no.	Price
DL703 7 segment D.P. left (30" height)	1523	£0 85
RED Single Digit		
DL707 7 segment D.P. left (30" height)	1512	£0 92
RED Single Digit		
DL527 7 segment D.P. left (50" height)	1524	£2 08
RED Two-Digit Reflector		
DL727 7 segment D.P. right (510" height)	1512	£2 07
RED Single Digit Light Pipe		
DL747 7 segment D.P. left (630" height)	1511	£1 73
RED Single Digit Light Pipe		

OPTO-ISOLATORS

Isolation Breakdown—Voltage 1500—continuous fwd current 100mA CIL74, Single-Channel 5 pin DIP standard type—optically coupled pair with Infra-red LED Emitter and NPN Silicon Photo Transistor

CILD74	Multi-Channel 8 pin DIP Two Isolated Channels	o/no. 1497	£0 61
CILQ74	Multi-Channel 16 pin DIP Four Isolated Channels	o/no. 1498	£1 22

MEL 11 (TIL81) NPN Light Detector

Silicon Photo Darlington Amplifier—VCBO 30v VECO 10v IC 100mA Ptot 300mW ILM In 0.5 Typ. 2mA ID 100mA nA £0 29

FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0 18
11mm x 5mm chassis mounting	507	£0 14
1 1/2in car inline type	508	£0 18
Panel mounting 20mm	509	£0 23
Panel mounting 1 1/2in	510	£0 37

QUICK BLOW 20mm

Type	No.	Type	No.	Type	No.
150mA 611 7p 1A	615	6p	3A	619	6p
250mA 612 6p 1.5A	616	7p	4A	620	10p
550mA 613 6p 2A	617	6p	5A	621	6p
800mA 614 8p 2.5A	618	7p			

ANTI-SURGE 20mm

Type	No.	Type	No.
100mA 622 1A	625	2.5A	628
250mA 623 2A	626	3.15A	629
500mA 624 1.6A	627	5A	630

All 8p each

QUICK-BLOW 1 1/2in.

Type	No.	Type	No.
250mA 631 500mA	632	800mA	634

All 8p each

Type	No.	Type	No.
1A 635 2.5A	638	4A	641
2A 637 3A	639	5A	642

All 8p each

NUTS AND BOLTS

BA BOLTS—packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
1in 0BA 839	£1 38	1in 4BA 846	£2 37		
1in 0BA 840	£0 76	1in 4BA 847	£0 29		
1in 2BA 842	£0 75	1in 6BA 848	£0 46		
1in 2BA 843	£0 52	1in 6BA 849	£0 24		
1in 2BA 844	£0 60	1in 6BA 850	£0 29		
1in 4BA 845	£0 51				

BA NUTS—packs of cadmium plated full nuts in multiples of 50

Type	No.	Price	Type	No.	Price
0BA 850	£0 83	4BA 857	£0 25		
2BA 856	£0 55	6BA 858	£0 28		

BA WASHERS—flat cadmium plated plain stamped washers supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
0BA 859	£0 16	4BA 861	£0 14		
2BA 860	£0 14	6BA 862	£0 14		

SOLDER TAGS—Hot tinned supplied in multiples of 50

Type	No.	Price	Type	No.	Price
0BA 851	£0 46	4BA 853	£0 25		
2BA 852	£0 32	6BA 854	£0 25		

TANTALUM

Type	No.	Price	Type	No.	Price
3137 1MFD 35V	£0 13	3142 4.4MFD 35V	£0 21		
3138 22MFD 35V	£0 13	3157 3.3MFD 25V	£0 21		
3139 47MFD 35V	£0 13	3143 10MFD 35V	£0 25		
3140 1.0MFD 35V	£0 13	3144 22MFD 16V	£0 25		
3141 2.2MFD 35V	£0 14	3156 33MFD 35V	£0 13		

CAPACITORS

AUDIO LEADS

No.	Type	Price
107	FM indoor Ribbon Aerial	£0 69
113	3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m	£0 86
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m.	£0 98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m.	£0 98
116	Car aerial extension. Screened insulated lead fitted plug and socket	£1 44
117	AC mains connecting lead for cassette recorders and radios 2 metres	£0 78
118	5 pin DIN phono plug to stereo headphone Jack socket	£1 21
119	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones	£1 04
120	Car Stereo connector. Variable geometry plug to fit most car cassettes, 8-track cartridge and combination units. Supplied with inlined fuse power lead and instructions	£0 69
123	6.5m Coiled Guitar Lead Mono Jack plug to Mono Jack plug Black	£1 72
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0 85
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0 85
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0 85
127	5 pin DIN plug to 4 Phono Plugs.	
	All colour coded. Length 1.5m.	£1 49
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0 92
129	5 pin DIN plug to 5 pin DIN plug mirror image	£1 21
130	2 pin DIN plug to 2 pin DIN inline socket	£0 78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5	£0 95
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1 13
133	5 pin DIN plug to Phono plugs	£0 86
134	5 pin DIN plug to 2 Phono sockets	£1 75
135	5 pin DIN socket to 2 Phono plugs	£0 78
	Connected pins 3 & 5. Length 23cm	£0 78
136	Coiled stereo headphone extension lead	£2 01
178	Block, length 6m	£2 01
	AC mains lead for calculators etc	£0 52

CASES AND BOXES

INSTRUMENT CASES. In two sections, vinyl covered top and sides aluminum bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1 73
156	11in	6in	3in	£2 92
157	11in	4 1/2in	1 1/2in	£1 75
158	9in	5 1/2in	2 1/2in	£2 43

ALUMINIUM BOXES. Made from bright a.l., folded construction each box complete with half-inch-deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0 85
160	4in	1 1/2in	1 1/2in	£0 85
161	4in	2 1/2in	1 1/2in	£0 85
162	5 1/2in	4in	1 1/2in	£0 97
163	4in	2 1/2in	2in	£0 87
164	3in	2in	1 1/2in	£0 60
165	7in	5in	2 1/2in	£1 43
166	8in	6in	3in	£1 82
167	6in	4in	2in	£0 18

TRANSFORMERS

Send your orders to:
DEPT. EE11, PO BOX 6, WARE, HERTS. Tel: 0920-3182
 Visit our **NEW shop: 3 BALDOCK ST., WARE, HERTS. Telex: 81786**


EXPERIEMTOR BREAD BOARDS FROM



No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size. All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP-4B.


EXP.3W5. The ideal breadboard for 1 chip circuits.
 Accepts 8, 14, 16 and up to 22 pin IC's.

ONLY £1.71.

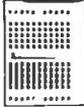

EXP.350. £3.62.


270 contact points with two 40-point bus-bars.

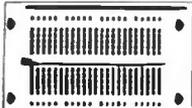

EXP.300.


550 contacts with two 40-point bus-bars

£6.61.

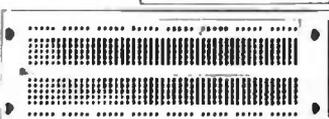

EXP.650 for Micro-processors

£4-14.

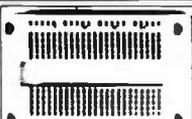

EXP.4B.

More bus-bars
£2.65.



ALL EXP. 300 Breadboards mix and match with 600 series.

POTENTIOMETERS

CARBON POTS (Linear Track)
 Single gang with wire end terminations. 6mm x 50mm plastic shaft 10mm bushes supplied with shake proof washer and nut. Tolerance 20% of resistance.

1831 1k ohms	1837 100k ohms
1832 2k2 ohms	1838 220k ohms
1833 4k7 ohms	1839 470k ohms
1834 10k ohms	1840 1 Meg
1835 22k ohms	1841 2M2
1836 47k ohms	All at 30p each

CARBON POTS (Log Track)

1842 4k7 ohms	1847 220k ohms
1843 10k ohms	1848 470k ohms
1844 22k ohms	1849 1 Meg
1845 47k ohms	1850 2 M2
1846 100k ohms	All at 30p each

Designed to fit 2.54mm pitch board. All tracks are linear law.

VC7

1816 100 ohms	1824 47k ohms
1817 220 ohms	1825 100k ohms
1818 470 ohms	1826 220k ohms
1819 1k ohms	1827 470k ohms
1820 2k2 ohms	1828 1 Meg ohms
1821 4k7 ohms	1829 2M2 ohms
1822 10k ohms	1830 4M7 ohms
1823 22k ohms	All at 10p each

DUAL CARBON POTS (Log Law)

1860 4k7 ohms	1865 220k ohms
1861 10k ohms	1866 470k ohms
1862 22k ohms	1867 1 Meg
1863 47k ohms	1868 2M2
1864 100k ohms	All at 99p each

SINGLE GANG SWITCHED (Lin Law)
 These potentiometers are fitted with double pole on-off switches. The switch is incorporated within the rotary action of the pot. Specification of pot is as VC1 Switch rating 1.5 amps at 250V AC.

1870 4k7 ohms	1875 220k ohms
1871 10k ohms	1876 470k ohms
1872 22k ohms	1877 1 Meg
1873 47k ohms	1878 2M2
1874 100k ohms	All at 75p each

DUAL GANG LONG-ANTI-LOG POT
 1888 Track specification as dual gang pots VC3, but tracks moulded to log-anti-log action 100k ohms **£0.86.**

SPECIAL VOLUME CONTROLS
 A miniature 16mm type replacement volume control incorporating single pole on-off switch. Resistance value 5k ohms. Tolerance +20% 1/8 watt rating.

MINIATURE ROTARY VOLUME CONTROL
 5k ohms log law with on-off switch, 20mm grooved spindle. Tag connections 17mm dia. Supplied with fixing nut. Used mainly for replacement.

WIRE WOUND POTS
 A range of wire wound single gang pots with linear tracks of 1 watt rating fitted with 10mm bush and supplied with shake-proof washer and nut.

1891 10 ohms	1896 470 ohms
1892 22 ohms	1897 1k ohms
1893 47 ohms	1898 2k2 ohms
1894 20 ohms	1899 4k7 ohms
1895 220 ohms	All at 92p each

SWITCHED POT (Log Track)
 Specification as VC2 but track having (log) law.

1879 4k7 ohms	1884 220k ohms
1880 10k ohms	1885 470k ohms
1881 22k ohms	1886 1 Meg
1882 47k ohms	1887 2M2
1883 100k ohms	All at 75p each

PRE-SET POTS HORIZONTAL MOUNTING
 Miniature type for transistor circuits. The wiper of the preset is provided with a slot for screw adjustment. The tags of the preset will fit printed wiring boards with a pitch of 2.54mm. All tracks are linear law.

1801 100 ohms	1809 47k ohms
1802 220 ohms	1810 100k ohms
1803 470 ohms	1811 220k ohms
1804 1k ohms	1812 470k ohms
1805 2k2 ohms	1813 1 M ohms
1806 4k7 ohms	1814 2M2 ohms
1807 10k ohms	1815 4M7 ohms
1808 22k ohms	All at 10p each

PRE-SET POTS VERTICAL MOUNTING
 Miniature type for transistor circuits. Wiper adjustment is made by a screw driver slot.

SILICON RECTIFIERS

200mA	£0.07
IS920 50v	£0.07
IS921 100v	£0.08
IS922 150v	£0.09
IS923 200v	£0.10
IS924 300v	£0.12
1 Amp	
IN4001 50v	£0.05
IN4002 100v	£0.06
IN4003 200v	£0.07
IN4004 400v	£0.08
IN4005 600v	£0.09
IN4006 800v	£0.10
IN4007 1000v	£0.12
1.5 Amp	
IS015 50v	£0.10
IS020 100v	£0.12
IS021 200v	£0.13
IS023 400v	£0.15
IS025 600v	£0.16
IS027 800v	£0.18
IS029 1000v	£0.23
IS031 1200v	£0.29
3 Amp	
IN5400 50v	£0.16
IN5401 100v	£0.17
IN5402 200v	£0.18
IN5405 400v	£0.22
IN5406 600v	£0.24
IN5407 800v	£0.28
IN5408 1000v	£0.35
10 Amp	
IS10/50 50v	£0.22
IS10/100 100v	£0.24
IS10/200 200v	£0.26
IS10/400 400v	£0.40
IS10/600 600v	£0.48
IS10/800 800v	£0.59
IS10/1000 1000v	£0.69
IS10/1200 1200v	£0.79
30 Amp	
IS30/50 50v	£0.64
IS30/100 100v	£0.79
IS30/200 200v	£1.07
IS30/400 400v	£1.44
IS30/600 600v	£2.02
IS30/800 800v	£2.23
IS30/1000 1000v	£2.51
IS30/1200 1200v	£3.16
70 Amp	
IS70/50 50v	£0.86
IS70/100 100v	£0.97
IS70/200 200v	£1.38
IS70/400 400v	£2.01
IS70/600 600v	£2.59
IS70/800 800v	£2.88
IS70/1000 1000v	£3.45
IS70/1200 1200v	£4.97
BYX38/300 6A 300v	£0.52
BYX38/600 6A 600v	£0.69
BYX38/300 9V 6A 300v	£0.52
BYX38/600 9V 6A 600v	£0.69

ZENER

400 mw (Bzy88) D007 Glass encapsulated range of voltages available 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v.

No. Z4 9p each
 1w-1.5w. Plastic and metal encapsulated Range of voltages available 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

No. Z13 17p each
 10w Metal stud type S010 case Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

No. Z10 40p each

ANTEX IRONS

1943 15 watt high quality soldering iron totally enclosed element in a ceramic shaft fitted with 3/32" bit. **£4.83**

1947 Replacement element for 1943 iron. **£2.19**

1944 iron coated bit 3/32" for 1943 iron **£0.53**

1945 iron coated bit 1/4" for 1943 iron. **£0.53**

1946 iron coated bit 3/16" for 1943 iron. **£0.53**

1948 General purpose 18 watt iron fitted with iron coated bit. **£4.54**

1952 Replacement element for 1948 iron **£2.19**

1949 Iron coated bit 3/32" for 1948 iron. **£0.53**

1950 Iron coated bit 1/4" for 1948 iron. **£0.53**

1951 Iron coated bit 3/16" for 1948 iron. **£0.53**

1931 Highly popular x25 25 watt quality soldering iron ceramic shafts to provide near perfect insulation breakdown voltage.

of 1500 volts AC and a leakage current of only 3.5uA and another shaft of stainless steel to ensure strength. **£4.83**

1935 Replacement element for 1931 iron. **£1.84**

1932 iron coated bit 1/4" for 1931 iron. **£0.58**

1933 iron coated bit 2/16" for 1931 iron. **£0.58**

1934 iron coated bit 3/32" for 1931 iron. **£0.58**

1953 SK1 soldering kit—This kit contains 15 watt soldering iron fitted with a 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to solder'. In presentation display box. **£6.38**

1939 ST3 soldering iron stand. Stand made from high grade bakelite material, chromium plated strong steel spring, suitable for all models, includes accommodation for six spare bits and two sponges which serve to keep the soldering iron bits clean. **£1.75**

AUDIO MODULES

Amplifiers

AL20 5 watt amplifier module	£3.73
AL30A 7-10 watt amplifier module	£4.35
AL60 15-25 watt amp. module	£5.39
AL80 35 watt amplifier module	£8.44
AL120 50 watt amplifier module	£13.74
AL250 125 watt amplifier module	£19.24

Pre-amplifiers

PA12 Stereo pre-amp. module	£8.94
PA100 Stereo pre-amp. module	£18.45
PA2000 Stereo pre-amp. module	£19.07
MM100 Mono pre-amplifier	£13.00
MM100G Mono guitar pre-amp.	£13.00

Power Supplies

PS12 Power supply (24 volts DC)	£1.72
SPM80 Stabilized power supply (33V)	£5.96
SPM120/45 Stabilized power supply (45V)	£6.67
SPM120/55 Stabilized power supply (55V)	£6.67
SPM120/65 Stabilized power supply (65V)	£6.67
SG30 Power supply for equaliser	£4.37

Miscellaneous

MPA30 Stereo magnetic cartridge pre-amp	£4.42
S450 Stereo tuner	£26.72
Stereo 30 Complete 7 watt 4 stereo amplifier board	£22.66
BP124 Siren alarm module 5 watts	£4.02
GE100MK11 10 channel monographic equaliser	£23.00

SPECIAL OFFERS

MINIDRILL 12v hand held battery-operated mini drill 7,500 r.p.m. Collet chuck ideal for drilling printed circuits or model, marking No. 1402. **£7.79**

TRANSFORMER 240v Primary 0-20V .. 2A Secondary. By removing 5 turns for each volt from the secondary winding winding any voltage up to 20v .. 2A is obtainable ideal for the experimenter No. 2042. **£1.50+86p P & P**

ANTEX MLX soldering iron. Sturdy 25 watt iron complete with 4 metres of 2-core. Works off a 12 volt battery. Ideal for car. Boat. Caravan No 1724 **£5.29**

Access and Barclaycard accepted. Giro Account No. 388 7006.

All prices include VAT. Add 35p post per order.



EDITOR

F. E. BENNETT

ASSISTANT EDITOR

B. W. TERRELL B.Sc.

PRODUCTION EDITOR

D. G. BARRINGTON

ART EDITOR

R. F. PALMER

ASSISTANT ART EDITOR

P. A. LOATES

TECHNICAL ILLUSTRATOR

D. J. GOODING

EDITORIAL OFFICES

Kings Reach Tower,
Stamford Street,
London SE1 9LS
Phone: 01-261 6873

ADVERTISEMENT MANAGER

R. SMITH
Phone: 01-261 6671

REPRESENTATIVE

N. BELLWOOD
Phone: 01-261 6865

CLASSIFIED MANAGER

C. R. BROWN
Phone: 01-261 5762

MAKE-UP AND COPY DEPARTMENT

Phone 01-261 6615

ADVERTISEMENT OFFICES

Kings Reach Tower
Stamford Street,
London SE1 9LS

Projects... Theory...

and Popular Features ...

These last few weeks before Christmas are hectic ones for the typical household and this has been borne in mind in planning this month's issue.

One of the many extra chores that have to be organised is the setting up of decorative lights, but this is not always a simple and trouble-free operation.

Anyone who has had experience in handling strings of miniature electric light bulbs knows only too well the trouble that can be caused by just a single defective bulb. This is always a possibility, especially in the case of lights that have been in one's possession for a number of years and are brought out of storage annually to provide another brief but scintillating performance.

Anything that helps the harassed householder to pin-point the fault quickly will be welcome at this time. Such helpful practical guidance is offered this month in our special feature *Xmas Lights Without Tears*. The same article also gives ideas for improving the overall reliability of decorative lights.


Dealing with a closely related theme is *Xmas Bright Ideas* which provides a few novel circuit ideas for electronically controlling decorative lights. These can be put to imaginative use by our readers to enhance the overall effects of such illuminations.

Coming now to fully detailed projects, time is short we realise but constructors should be able to complete at least one of our three simple novelties before Christmas.

That perennial problem of seeking out unusual and interesting small gifts for children could be solved with our *Everlasting Candle* or the *Peg-A-Hole* game; while the *Twinkling Star* will add further lustre to any Christmas Tree, or fit into other decorative arrangements.

All three are easy to build, need but a few circuit components and make use of commonplace materials and items found around the home.

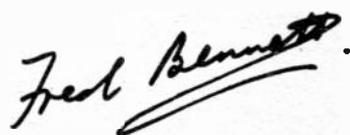From among the other projects this month we make special mention of the *Lightcall*, principally because this simple device could be of great service to the hard-of-hearing. Its construction and installation would be a worth-while task (during the Christmas vacation?) for any enthusiast who knows of a neighbour or relative who would appreciate a visual back-up for the doorbell or chimes.



Our January issue will be published on Friday, December 14. See page 817 for details.

Readers' Enquiries


We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in **EVERYDAY ELECTRONICS**, but these requirements can be met by our advertisers.

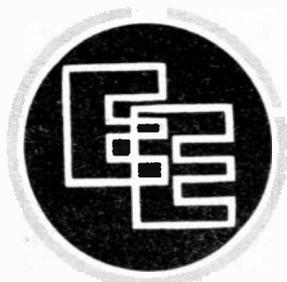All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



Everyday ELECTRONICS

VOL. 8 NO. 12

DECEMBER 1979

CONSTRUCTIONAL PROJECTS

PEG-A-HOLE GAME An exciting party game by F. G. Rayer	784
EVERLASTING CANDLE A novel nightlight by A. Sproston	786
TWINKLING STAR Add sparkle to your decorations by E. M. Lyndsell	788
LIGHTCALL Visual back-up for your doorbell by T. R. de Vaux-Balbirnie	799
MODULATED TONE GENERATOR Sound unit for alarms or timers by R. A. Penfold	803
EE RADIO CONTROL SYSTEM Part 2: Constructing the Transmitter and Field Strength Meter by L. Armstrong, H. Dickinson and W. Wilkinson	806
UNIBOARDS 2—BURGLAR ALARM Warning sounds when a "loop" is broken by A. R. Winstanley	824

GENERAL FEATURES

EDITORIAL	778
XMAS LIGHTS WITHOUT TEARS Tracing faulty bulbs and other hints by T. R. de Vaux-Balbirnie	780
XMAS BRIGHT IDEAS Santa's Eyes, Flashing Tree Lights, Bell Lights and Xmas Sound-to-Light by E. M. Lyndsell	782
FOR YOUR ENTERTAINMENT Choosing a video game by Adrian Hope	790
SQUARE ONE Beginners Page: Circuit Symbols	793
CROSSWORD NO. 23 by D. P. Newton	793
TEACH-IN 80 Part 3: Calculating currents in different resistive networks by S. R. Lewis B.Sc.	794
SHOP TALK Retail news, products and component buying by Dave Barrington	798
JACK PLUG AND FAMILY Cartoon by Doug Baker	798
COUNTER INTELLIGENCE A retailer comments by Paul Young	802
EVERYDAY NEWS What's happening in the world of electronics	812
RADIO WORLD A commentary by Pat Hawker	814
PROFESSOR ERNEST EVERSURE The Extraordinary Experiments of. by Anthony J. Bassett	818
WORKSHOP MATTERS Finishing off by Harry T. Kitchen	822
THE ADVENTURES OF TANTY BEAD Cartoon by Matthew Read	826
INDEX FOR VOLUME 8	829

Part 2 of Synthesisers Explained will appear next month.

Back Issues

Certain back issues* of EVERYDAY ELECTRONICS are available worldwide price 70p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

* Not available: October 1978 to July 1979.

Binders

Binders to hold one volume (12 issues) are available from the above address for £3.75 (home and overseas) inclusive of postage and packing. Please state which Volume.

Subscriptions

Annual subscription for delivery direct to any address in the UK: £8.50, overseas: £9.50. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613 Kings Reach Tower, Stamford Street, London SE1 9LS.


© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

SEE YOU AT BREADBOARD 79

STANDS J6 & J7

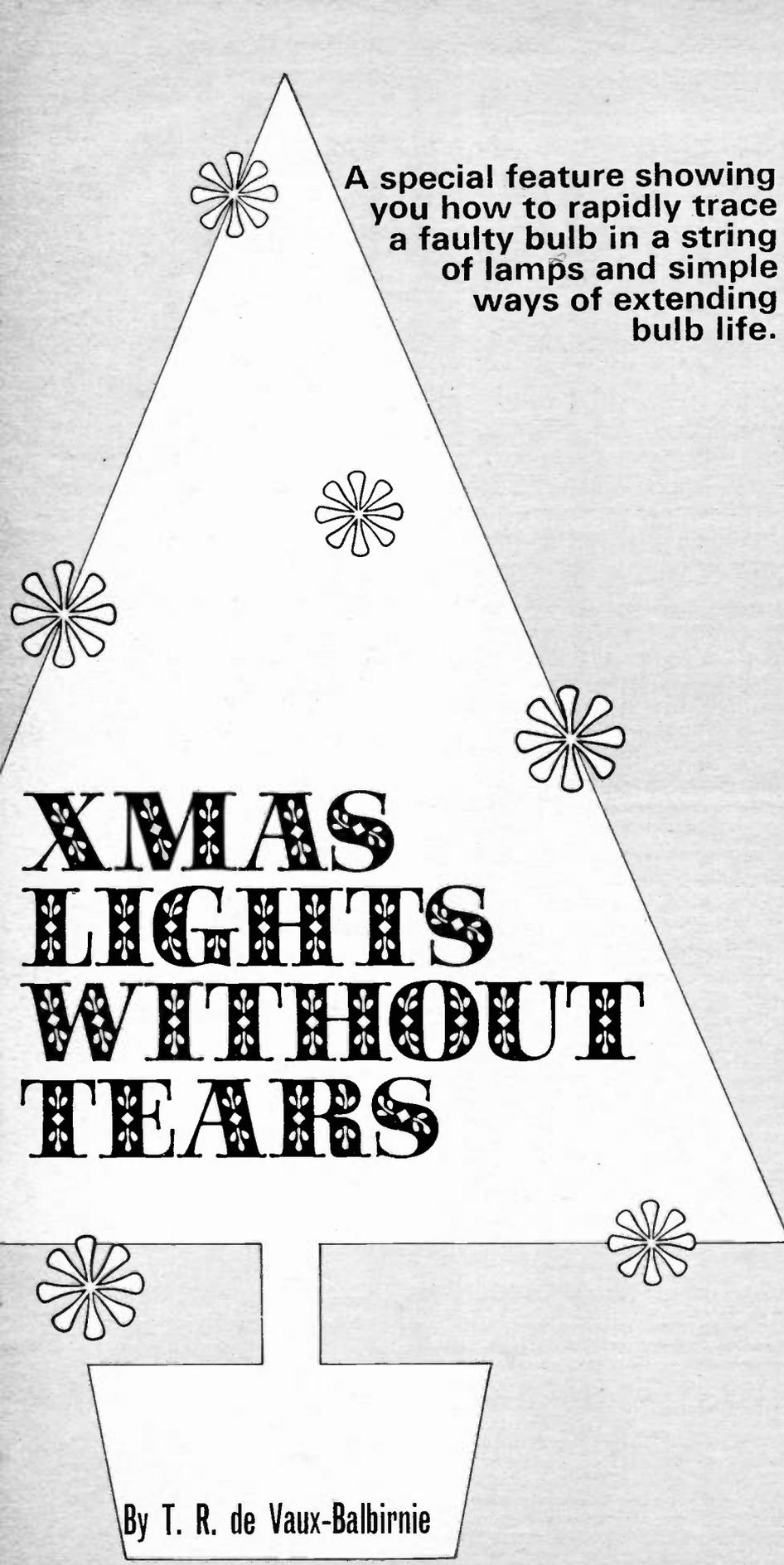ROYAL HORTICULTURAL HALLS
ELVERTON ST. WESTMINSTER
LONDON SW1 DEC. 4-8th 1979





**A special feature showing
you how to rapidly trace
a faulty bulb in a string
of lamps and simple
ways of extending
bulb life.**

XMAS LIGHTS WITHOUT TEARS

By T. R. de Vaux-Balbirnie

IN the author's house, Christmas starts by standing on a chair and reaching into the loft to recover a rather old cardboard carton. Labelled "Christmas Box" in felt tip pen, it contains all the usual decorations including a 40 lamp set of lights for the Christmas tree.

When the lights are plugged in they never work first time even though they were in good condition the previous year. Perhaps the fairies "pop" a bulb or two on their annual visit to the Christmas Box in the summer. More likely, a lamp on its last legs fails under the vibration of packing the lights away.

It seems that there are two problems associated with these lights and the author has attempted to solve, or at least to alleviate, both. The first problem is the inherent short life of the bulbs and the second is finding which bulb has "blown" in the event of failure.

BULBS ARE SERIES CONNECTED

Christmas tree light sets have all the bulbs connected in series, i.e. in a chain, see Fig. 1. This has the disadvantage that failure of one bulb causes them all to go out.

Due to the large number of lamps in the set and the short life of the bulbs this is a grave problem. It is true that certain types of bulbs are designed to short circuit themselves internally when the filament blows so preserving continuity in the circuit. It is then an easy matter to spot which lamp has failed as it is the only one not glowing. Unfortunately, from experience, they are not very reliable and the self-shorting mechanism does not always work.

Another problem is that the "shorted" lamp causes all the other lamps in the chain to be overloaded so that other bulbs near the end of their lives will fail more quickly. A chain reaction could occur resulting in failure of all the bulbs unless a special "fuse bulb" is included in the circuit. This will blow if the current rises excessively.

Lamps connected in series are never a good idea but it would be difficult and expensive to make mains voltage bulbs of the small size required. As it is, the bulbs share the mains voltage equally so that in a 40 lamp set, for instance, the voltage rating for each lamp will be 6 volts (240/40). In a set of 20 lamps it will be 12 volts and so on. Such bulbs may be manufactured relatively cheaply (although a packet of 6 cost 39p in 1978 and gave little service.)

EXTENDING BULB LIFE

In an effort to extend the life of the bulbs, several ways of dimming them slightly have been explored. Such dim-

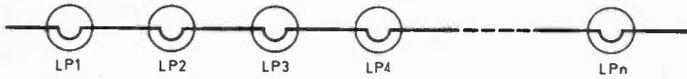


Fig. 1. Lamps in Christmas Lights are connected as shown above—in series.

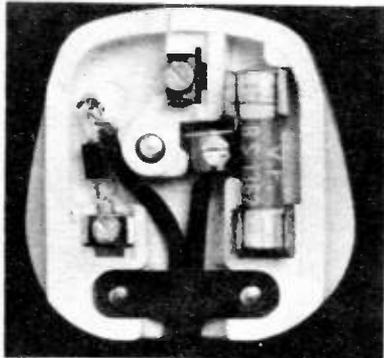


Fig. 2. Simple and convenient means of connecting a diode in series with the Christmas Lights. See text for details.

ming of filament lamps has a dramatic effect in increasing the life. It is thought that these lights are too bright anyway—the pinpricks of brilliant light can be very distracting. There seems to be a definite case for introducing a slight dimming.

A cheap and extremely simple way of achieving this is to connect a suitable diode in series with the chain of lights. This rectifies the mains supply so that current only flows on one of the half cycles. A small diode may be chosen which will fit inside the mains plug as shown in Fig. 2.

The diode may be connected (either way round) in the neutral lead using a hooked connection for the lead out of the plug. This connection must be soldered. The cable clamp on the plug must be tight so that a trial tug on the wire cannot dislodge the wire from the diode. As virtually no heat is generated in the diode it will be quite safe in position.

DIODE RATING

The diode must be capable of withstanding the current required for the lights and also must have a voltage rating at least equal to the peak voltage of the mains supply. For a 240 volt mains it will be necessary to choose a diode with at least 340 volts working. The type 1N4004 is ideal.

Experiments yielded no noticeable flickering as might be expected from such an arrangement (the current is turned off for half the wave cycle and the filaments in the bulbs have a chance to cool down a little before the next current pulse arrives).

As a general rule, the resistance of a metallic conductor rises with increased temperature. When a lamp is under-run it will operate at a lower temperature than normal so its resistance will be lower. This means that a higher average current will flow in the lamp than theory predicts. This

ultimately means that the dimming effect is not as great as might be imagined but it is still significant.

Obviously a transformer could be used to reduce the voltage applied to the lights. This idea was ruled out on the grounds of cost and size.

BULB ACTS AS RESISTOR

Another way to achieve dimming is to connect a suitable resistor in series with the lights. The disadvantage of a resistor is that it dissipates heat and could be dangerous for this reason. The advantage over the diode idea is that the effect may be controlled by suitable selection of the value of the resistor. This idea was almost ruled out on safety grounds until experiments with *mains lamps as resistors* were investigated. Here the heat is far less likely to be a problem and there is no difficulty with the housing or connections.

In operation the mains lamp will probably glow a little. The light may be used to illuminate a Christmas scene or just hidden out of the way. A standard bayonet lampholder is used in series with the chain. In the author's case, the correct effect was obtained with a 60 watt lamp but there is room for experiment here. As mains voltage exists along the chain it is essential to make proper connections to the lampholder.

Beware of calculations based on the resistance of the lamp—once more, the temperature effect of resistance makes such figures misleading. For instance, the calculated value of the resistance of a 60 watt lamp is about 1 kilohm. However, a multimeter indicates a resistance of only 80 ohms! Under working conditions, the resistance of the lamp will be somewhere between these extremes.

USING A CAPACITOR

An excellent, if unconventional, way to dim the lights was found. This was to connect a *capacitor* in series with the chain. A capacitor allows an a.c. current to flow but not d.c. In a way, a capacitor behaves as a resistor as far as a.c. is concerned but there is one important difference. A capacitor produces no heat and wastes no energy.

A good effect was obtained with a $1\mu\text{F}$ capacitor but a brighter operation was obtained with $2.2\mu\text{F}$ (or two $1\mu\text{F}$ capacitors wired in parallel) When

buying a capacitor it must be a good quality component with a working voltage of at least 340 volts. On no account must it be an electrolytic capacitor. These are polarised and must not be used in a.c. work of this kind.

Another idea is to connect a few more bulbs of the same type in series with the chain. An old, discarded set of lights would be ideal for the purpose. Care must be taken over the quality of the joints. Trial and error will soon reveal the best number of additional lamps.

It would be possible to replace all the 6 volt bulbs in a 40 lamp set with the 12 volt variety designed for 20 lamp sets. It is likely that the final effect would be too dim, however. Unless lamps have the same current rating, it is important not to mix lamps of different voltages.

TRACING FAULTY BULB

So much for extending the lives of bulbs. Now for the other problem—that of finding which bulb has blown when failure occurs. The most obvious way is to replace the lamps one by one with a lamp known to be good. Alternatively, each lamp may be tested with a battery. This is a tedious job especially when the blown bulb is

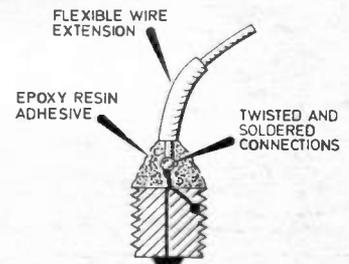


Fig. 3. Construction details for making a test lamp.

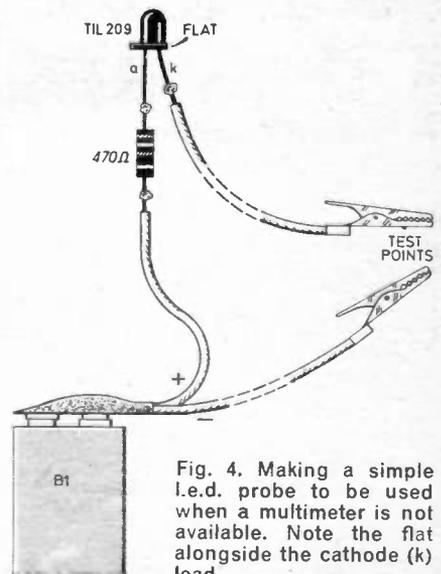


Fig. 4. Making a simple i.e.d. probe to be used when a multimeter is not available. Note the flat alongside the cathode (k) lead.

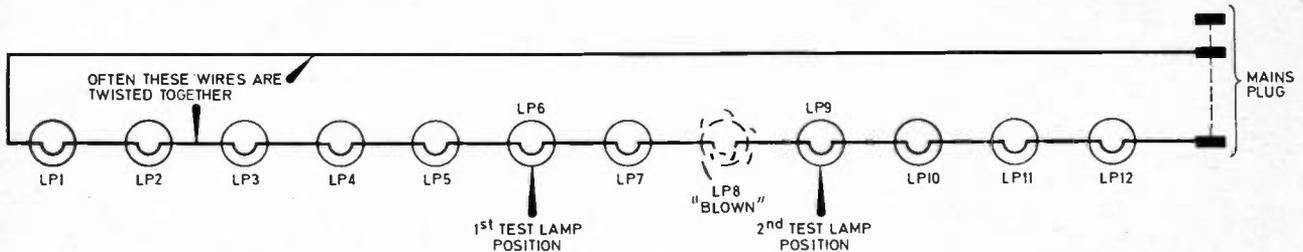


Fig. 5. Procedure for tracing a faulty bulb in a string of twelve series connected bulbs.

the last one in the chain to be tested! Another problem is that when the bulbs are on the tree it is easy to miss one. Although the following method sounds complicated at first it greatly reduces the time required to locate the faulty lamp.

TEST LAMPS

Three "test lamps" are made in the following way. Old "blown" (non-functioning) bulbs have the glass broken and carefully removed. The wires leading to the filament are then gently twisted together and a short length of wire soldered to them as seen in Fig. 3. The whole joint is protected with a little quick setting epoxy resin adhesive.

As well as these test lamps, a multimeter will be required. If none is available, a suitable alternative is an l.e.d. connected in series with a 470 ohm resistor and a 9 volt battery (as shown in Fig. 4). When using l.e.d.s it should be remembered that they will only work one way round with the battery. For all the following the plug is disconnected from the mains.

EXAMPLE

For simplicity of description, imagine a set of only 12 lamps with number 8 blown, Fig. 5. A lamp near the centre of the chain (say LP6) is replaced with a test lamp. Checks are then made with the multimeter set to ohms or with the l.e.d. between the wire end on the test lamp and the Live and Neutral pins on the mains plug in turn.

In this example, a low ohms reading (or l.e.d. on) will be indicated between the test lamp and the Neutral but a high ohms value (or l.e.d. off) between this and the Live pin. This shows that the fault lies in the latter half of the chain. In this way the fault has been narrowed to one half of the chain. Naturally, if a low reading is indicated in both of these tests, then the faulty lamp is the one which has been replaced with the test lamp i.e. LP6. A high reading in both tests will indicate a faulty bulb in each half.

Having established which is the faulty half, another test lamp is connected about half way along that section (say LP9). Checks are then

made as above between the test lamp just inserted and that already in LP6 and the live pin of the plug in turn. In the example, a high reading will be indicated between LP6 and LP9. This locates the faulty quarter of the chain.

FURTHER CHECKS

A similar check will narrow the location of the bulb still further but when it has been found to within two or three bulbs it is simpler to check by substitution than to pursue the above method any further.

With a 40 lamp set, one operation will find which "20" the fault lies in. The next operation will find which "10" and the third operation will locate which "5". Another test may be used to find which "2" or "3", then substitution used.

One day someone may invent very reliable l.e.d. Christmas tree light sets—there are some very good colours these days. Until that time the foregoing may help to avoid unnecessary aggro during the festive season.

XMAS BRIGHT IDEAS

By E. M. Lyndsell

SANTA'S EYES

AMONG the many decorations used at Christmas time is a cardboard face of Santa Claus. By use of the circuit in Fig. 1 Santa's eyes can be made to wink (or flash) at you.

The circuit uses a 555 timer i.c. wired as an astable multivibrator. The flashing rate is set by the values of R1, R2, VR1 and C1. The output at pin 3 alternately switches at this rate between 0V and +9V. Thus for

pin 3 at 0V, D1 is lit with D2 off; for pin 3 at +9V, D2 is lit and D1 off.

If the l.e.d.s are fitted in the eye positions on the "Santa card", he will appear to be winking at you. A red knob on VR1 placed at Santa's nose will add to the effect and allow the flashing rate to be altered to suit. Lots of fun for the children.

Alternatively, a single l.e.d. could be used on a cardboard replica of "Rudolph" at his nose position.

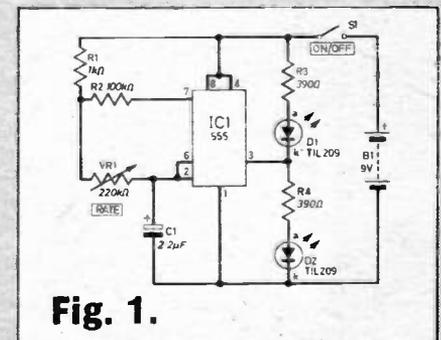


Fig. 1.

FLASHING TREE LIGHTS

The Christmas tree lights can be caused to repeatedly flash on and off by the application of the circuit in Fig. 2. Once again, a single 555 timer i.c. is used in the astable mode with its output feeding a relay coil.

The relay contacts are wired to act as a switch in series with the string of lamps. The contacts need to be of the normally closed (n.c.) variety to allow the lamps to be on (no flashing) when the unit is switched off. The contact rating must be 240V a.c. at a current to suit the total bulb load.

Resistor R1 is made small in relation to R2 to obtain an almost 1:1 mark/space ratio; R2 and C1 control the operation rate which has been arranged to flash at 0.5Hz.

When the output at pin 3 is low (0V), the relay coil is not activated and the contacts are closed and the lamps are lit. When pin 3 goes high (+9V) the coil is energised and the contacts open and the lights are switched off. Thus under running conditions, the lamps are alternately switched on and off at 0.5Hz producing a low-rate flashing effect.

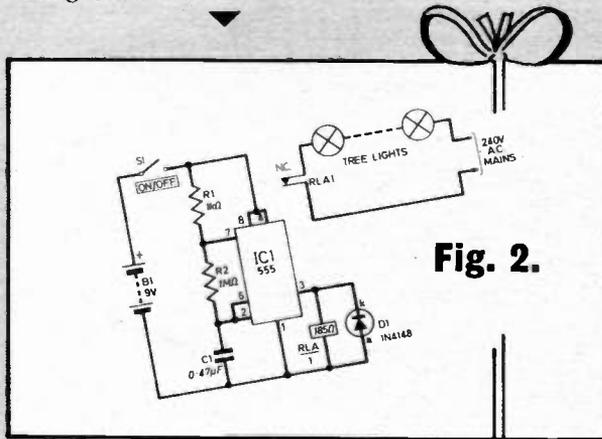


Fig. 2.

XMAS SOUND-TO-LIGHT

For the teenage fraternity the circuit of Fig. 4 is included. This converts the sound picked up by a microphone into a flashing light pattern—the lights being a string on a Xmas tree.

Almost any microphone can be used and is placed close to a source of music such as that from a loudspeaker of a record player for example. The signals are first amplified (or attenuated) by a variable gain amplifier, IC1 and then isolated and boosted by the action of T1. The resultant signal on the secondary of the "step-up" transformer is connected to the gate terminal of a mains thyristor loaded with the string of lights.

The lamps flash in time with the amplitude peaks of the music heard in the loudspeaker. The threshold of triggering is variable by means of VR1. The i.c. amplifier is battery powered—two PP3 batteries are suitable.

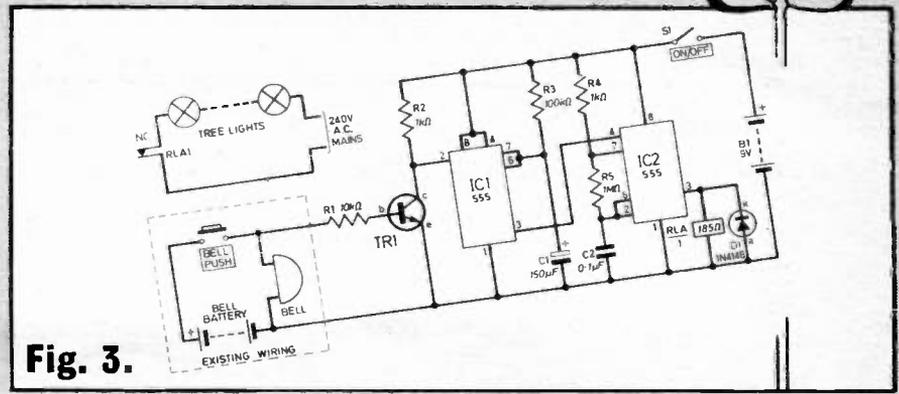


Fig. 3.

BELL-LIGHTS

With the party in full swing it is sometimes difficult to hear the doorbell when it rings. The circuit of Fig. 3 will announce the arrival of a caller by flashing the lights on the Christmas tree (or elsewhere) for a period of about 15 seconds when the bell-push is operated. After this time the lights return to their constant illumination condition.

Here two 555 timers are employed, one wired as an astable with the other as a monostable.

The reset terminal, pin 4 of IC2 (astable configuration) is linked to the output of IC1 which is at 0V in the untriggered condition. This inhibits the operation of IC2.

Integrated circuit IC1 is switched on for a time governed by the values of R3 and C1 when a low voltage (less than 3V) is received on pin 2, the trigger input. This happens when the bell push is operated via TR1 functioning as an inverter. IC1, pin 3, goes high allowing IC2 to oscillate and cause the relay contacts to open and close as described for Fig. 2. Contacts must be capable of handling mains voltages.

The astable here runs at a faster rate than the previous astable to produce a more startling effect.

The lights will flash for each successive operation of the bell-push after the expiration of the monostable "on" time for each push. □

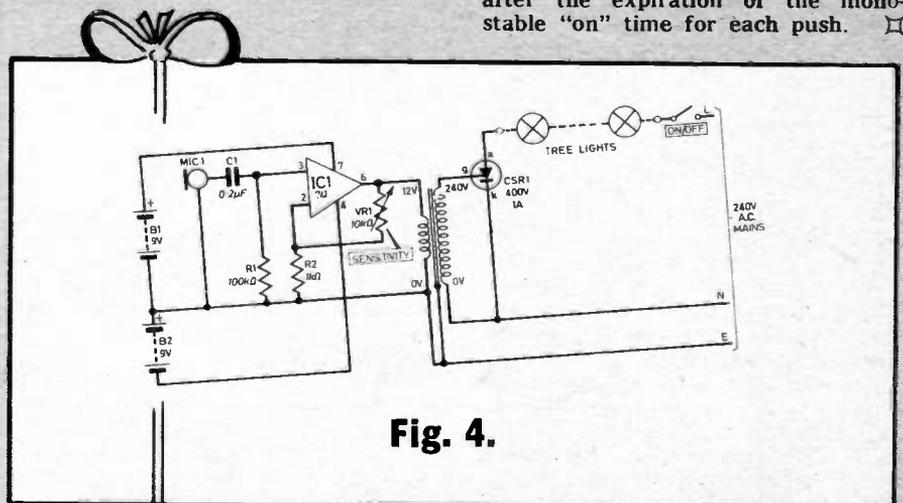


Fig. 4.

PEG-A-HOLE GAME

By F. G. Rayer

THIS game is suitable for one or more players, and can be of any grade of difficulty, from the very easy to almost impossible. In play, shaped metal plates with holes drilled at their centres are placed one by one on a metal peg using a "stick" fitted with a crocodile clip. As the size of the hole becomes smaller and smaller, so does the successful placing of the piece on the peg become more and more difficult. An additional "hazard" is the releasing of the plate from the crocodile clip. This device can therefore be used to measure co-ordination and a steady hand.

RULES OF PLAY

A single player can find how small a hole he can successfully peg, or can place the metal pieces while timing himself. Two players can take it in turns to place the pieces, until one (the loser) fails, or they can compete individually while timing the successful placing of a certain number of plates.

The game can be made more interesting for two players (or teams) by using say 10 pieces and numbering them 1 to 10, these being the points scored for successfully placing the piece on the peg. The point value is to be inversely proportional to the hole size i.e. the smallest hole—10 pts, the largest hole—1 pt.

The players take turns and are allowed to choose any piece to try and peg. If successful they score its point value. If they fail, that player's score so far is reduced by the point value of that piece but that piece remains on the peg. The winner is the player with the highest score after all ten pieces have been played.

CIRCUIT OPERATION

The complete circuit diagram of the Peg-a-Hole game is seen in Fig. 1.

The circuit uses a thyristor, CSR1. This device exhibits an open circuit between anode and cathode until a positive voltage is received at its gate terminal. The lamp LP1 is normally off. The "peg" is wired to the gate terminal.

The crocodile clip which is used for gripping the actual playing pieces is connected via R1 to the positive supply rail. Thus when a gripped metal

plate touches the peg, with S1 closed, a positive voltage appears on the gate terminal and causes CSR1 to turn on, (anode effectively shorted to cathode) resulting in LP1 being lit. The lamp remains on even if the contact to the peg is broken, and can only be turned off by means of S1.

A 6.3V 150mA bulb is fitted, but a 3.5V 300mA bulb could be used instead. A three-cell 4.5 volt battery is adequate, but 6V could be used, with a bulb to suit.

ASSEMBLY ON BASE

The game is constructed on a board about 200×150mm and 12 to 18mm or so thick as seen in Fig. 2.

The metal peg used in the prototype was a 76mm long nail, driven through from the bottom. Recess the wood for the head, or drive it flat with the surface. Solder on a wire and bring it up through a hole near to where the tagstrip is to be positioned. This is the gate (g) connection to the thyristor.

Screw the batten mounting lamp-holder and the tagstrip to the board and solder the components to the strip and wire the latter to the holder. A strip of aluminium, about 115mm long and 20mm wide should be shaped to secure the battery to the board, and fitted by means of two screws.

Switch S1 consists of a strip of metal, bearing on a round-headed screw. It is simply lifted with one's finger to break circuit. And may be rotated to one side to leave the game permanently off. A conventional switch, or push-for-off switch could be used instead.

Convenient and economical battery connectors for the 1289 battery can be made from paper clips soldered to lengths of p.v.c. covered wire.

A sheet of cardboard glued to the underside will protect the wiring and the playing area. Four rubber feet fitted to the underside will afford the same protection and enhance the appearance.

PLAYING PIECES


The "gripper" for the playing pieces is made by feeding about 50cm of flexible p.v.c. covered wire, fitted with a crocodile clip at one end, through an old Biro pen case. The clip should be a tight push fit into the end, otherwise it will need to be glued. The free end is then soldered to the tag strip.

The metal playing pieces used by the author were rectangular in shape and cut from stout scrap aluminium sheet (16 s.w.g.). Any shape could be used e.g. triangular, circular, hexagonal, etc., or a combination of different shapes for the sake of appearance, with a range of different sized holes drilled at each plate centre.

PLAY

Several different ideas for playing have been discussed earlier, and no doubt constructors will devise their own rules for the game.

Beside its obvious amusement value, this unit has a more serious application in testing a person's co-ordination and could be used in this connection with children, the hole sizes probably being enlarged. ☐

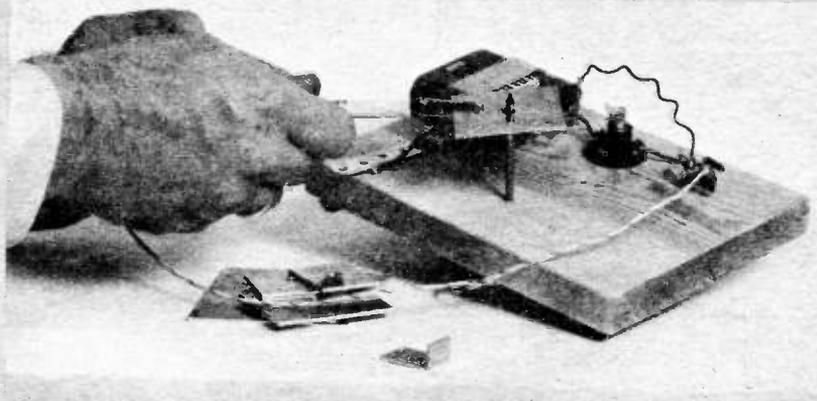


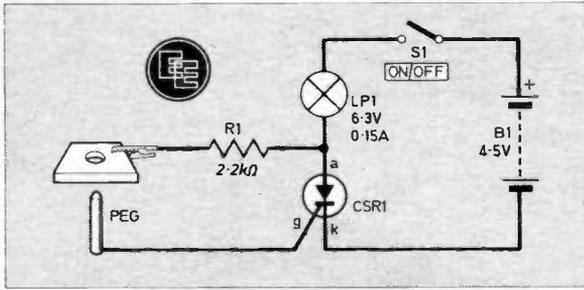


Fig. 1. Circuit diagram of the Peg-a-Hole game.

COMPONENTS

- R1 2.2kΩ ½W carbon ±5%
- CSR1 CSR1/05 or other type to accommodate LP1 current
- LP1 6.3V 150mA m.e.s. bulb
- B1 4.5V type 1289
- S1 single-pole on/off (home-made type used in prototype)

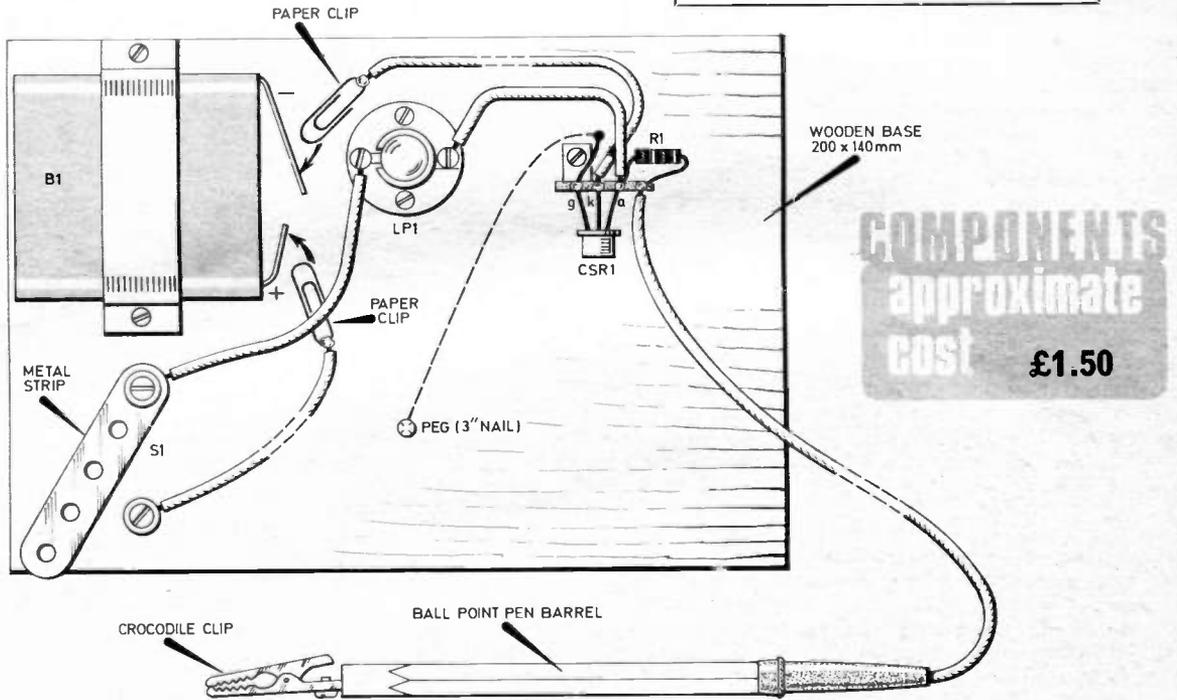Batten mounting m.e.s. bulb holder; standard crocodile clip; 4-way tag strip with support; aluminium plate; woodscrews (7 off); pen case; flexible wire; wood for base; rubber feet; 76mm long wire nail; paper clips (2 off)



COMPONENTS
approximate
cost **£1.50**


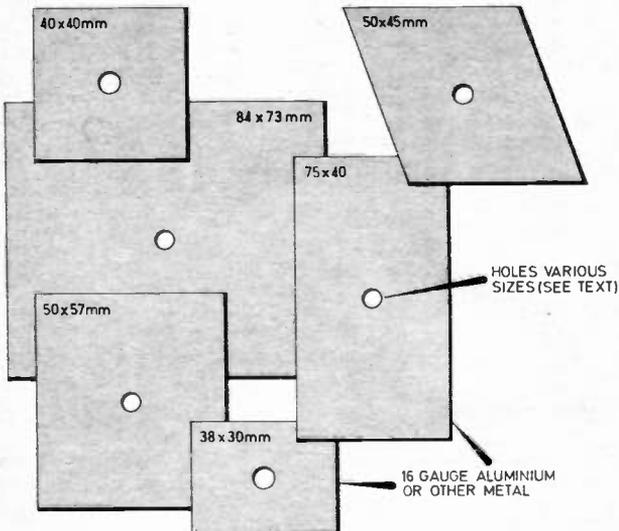


Fig. 2. Completed game showing interwiring and suggested dimensions for the metal pieces.

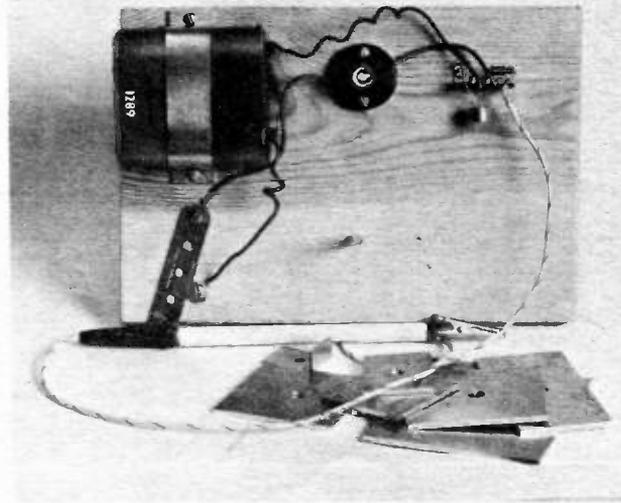

The complete game showing stick and metal pieces.

EVERLASTING CANDLE

By A. Sproxton

THE purpose of this useful gadget is to provide a convenient portable form of light for the odd nocturnal visit to the bathroom. It also has the added advantages that it will never fail because of a used-up battery, and it is easy to find in the dark because of the tiny glow from the incorporated light emitting diode.

CIRCUIT DESCRIPTION

The circuit diagram is shown in Fig. 1. It consists of a 1.25V m.e.s. bulb and rechargeable battery wired in parallel with the transformer secondary and an l.e.d.

With the candle in position on the charger board, S2 opens turning off the lamp, and S1 closes completing the circuit from the secondary of the transformer. The light emitting diode D1 acts as a rectifier and the battery is supplied with a charging current.

When the candle is removed, S2 closes turning on the light, and S1 opens switching off the battery charging circuit. The resistor R1 is used to reduce the charging voltage to a suitable value. Besides acting as a rectifier, D1 also serves to show when charging is taking place.

CHARGER BOARD

It is best to start construction with the board for the charger. This consists of a piece of plywood 150mm x 100mm x 15mm. To determine the positions of S1 and magnet B, take the ceiling rose and remove the terminal block. This can easily be done using a hot soldering iron and some ingenuity.

Place the rose on the board about 10mm from one end, draw round it and mark the position of the terminal block and lower knock out panel. Recesses can now be cut in the board so that reed switch S1 and magnet B can be mounted flush with the surface as shown in Fig. 2a. Note that magnet B is offset. This is because the contacts in S2 are at one end of the glass envelope and not in the centre.

Two holes should now be drilled through the board to take the leads from S1, which can now be mounted and secured in position by bending its wires carefully with pliers. Glue magnet B in place.

CANDLE

Construction of the candle itself can start next. The switch S2 consists of part of a single-pole changeover reed switch. The unwanted "normally open" contact wire should be cut off carefully about 5mm from the glass. This switch can now be glued with Araldite onto the base of the ceiling rose in the recess where the terminal block used to be, see Fig. 3, making sure that the contacts of the switch are on the right hand side. Magnet A can then be glued down over the lower knock-out panel.

ROSE GUIDES AND CONTACTS

At this stage the ceiling rose base should be placed on the charger board to make sure that S1 and S2 are aligned properly and are working. The top of the charger board can then be covered with Formica or similar laminate.

The rose guides can be mounted next. These are positioned by placing the ceiling rose base in the correct operating position on the charger board, drawing round it and spacing out the rose guides about 5mm outside this circle.

Next the charger contacts are fixed in position. These are made of large brass drawing pins with 24 s.w.g. tinned copper wire attached to them and are located in the following way. Place the rose base on the charger board and mark the position of the mounting screw holes. A small hole is then drilled through the board at these points to take the contact wires and then the contacts themselves are secured (glued) in position.

Finally the transformer and associated components can be mounted and wired up as shown in Fig. 2b and c. The underside of the board should be finished with a protective covering e.g. hardboard, and a small ventilated plastic box fitted over the transformer for safety reasons.

The contacts on the underside of the ceiling rose can be fitted next. These consist of short 2BA bolts with solder tags mounted on the inside, see Fig. 3. These should be countersunk so they lie flush with the rest of the underside. Replace the cover on the rose and place it in its correct operating position on the charger board. Mark the desired location of the l.e.d. and carrying handle, drill suitable size holes and fit these components.

Assembly of the candle unit can now be completed. Take one of the end caps, cut it down to about 15mm in length and drill a hole in the centre just big enough to fit over the hole in the top of the ceiling rose. Glue this on to the ceiling rose cover. The other end cap should be similarly treated so that it can take lamp LP1.

COMPLETING ASSEMBLY

Wires are then soldered onto the battery and lamp according to Fig. 3 and the two solder tags fitted to the ceiling rose cover. Complete the wiring and slot the unit together. Care should be taken to wire the l.e.d. in the way shown or the battery will not charge and may be damaged.

As a finishing touch some form of location marks can be put on the board and candle to ensure that it is always set down in the right position. ☆

COMPONENTS

- R1 220Ω ¼W carbon ± 10%
- T1 mains primary/6V 100mA secondary transformer
- D1 TIL209 l.e.d. red or green
- B1 1.5V type U11 rechargeable battery
- LP1 1.25V 0.25A m.e.s. lamp
- S1 s.p.s.t. normally open reed switch including magnet
- S2 s.p.d.t. reed switch including magnet

m.e.s. bulb holder; mains cable; connecting wire; ceiling rose; piece of plastic tubing with end caps to fit; cable clip for handle; piece of plywood 150mm x 100mm; covering for charger board; 2BA countersunk bolts, nuts and solder tags (2 off each); 4BA nuts, bolts and solder tags (2 off each); brass drawing pins (2 off); rubber feet (4 off); nuts and bolts for handle.

See
**Shop
Talk**
page 798


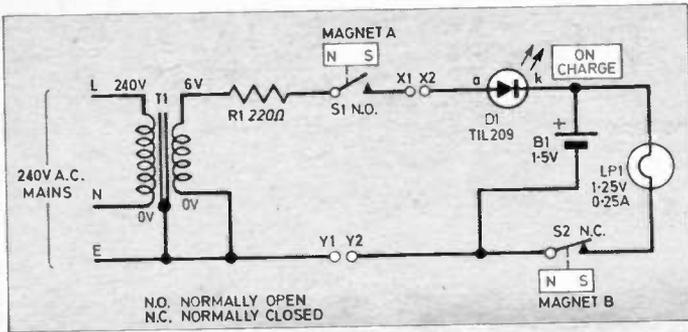


Fig. 1. Complete circuit diagram of the Everlasting Candle.

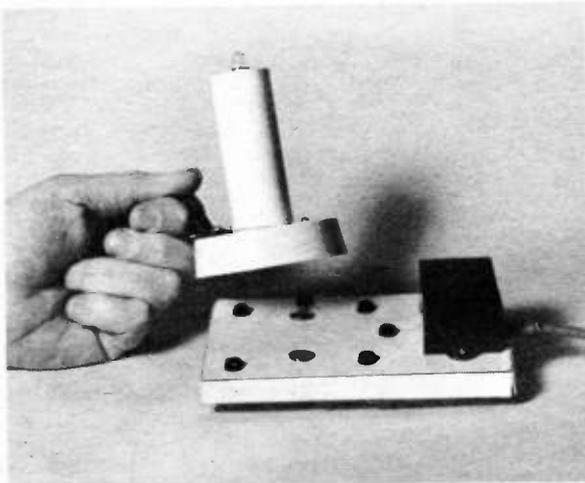

The "candle" being removed from the charger base. For safety reasons a plastic cover **must** be placed over the mains transformer.

COMPONENTS
approximate
cost
£8

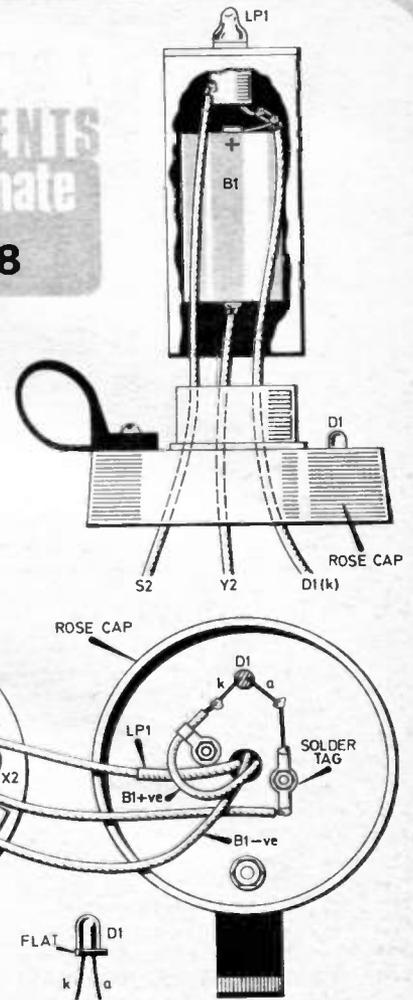


Fig. 3. Component layout of the candle unit.

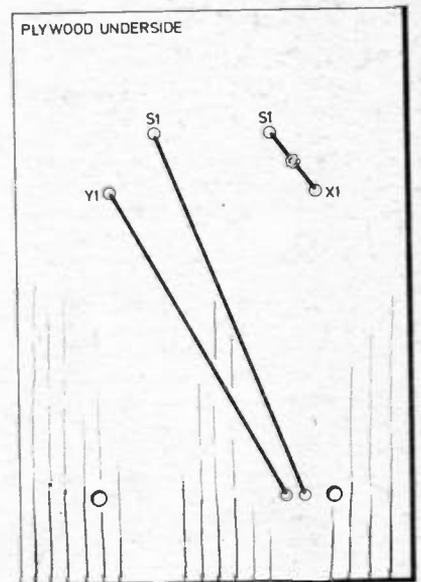
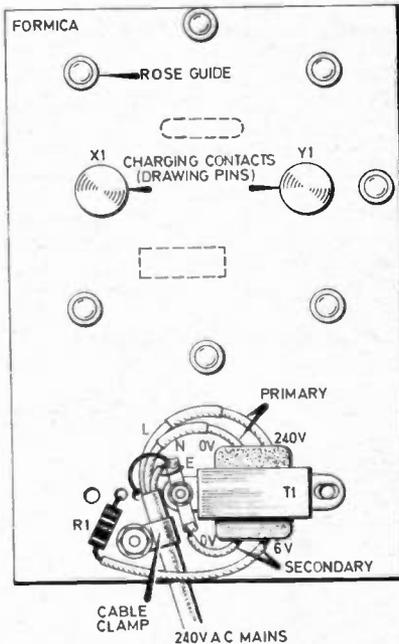
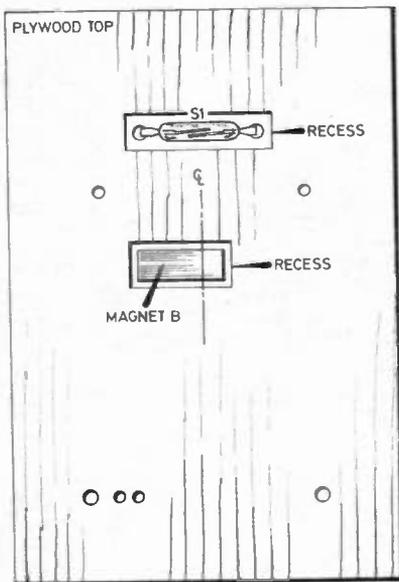


Fig. 2. Component layout of charger board showing (a) top side before covering with Formica, (b) top side after covering, (c) the underside.

TWINKLING STAR

By E. M. Lyndsell

CHRISTMAS will be with us again soon and homes will be adorned with decorations of many sorts. The Twinkling Star described here is intended to be such a decoration and was originally designed to hang on the Christmas tree but could also be used to decorate a wall or window.

Construction is quite straightforward and uses easily obtainable components allowing it to be built in good time for the festive season.

The unit consumes an average of 400mA and for this reason a mains derived power supply is incorporated. For those with a 9 volt battery eliminator capable of supplying this current, D1, T1, C1 and S1 can be omitted from the shopping list.

CIRCUIT DESCRIPTION

The complete circuit diagram of the unit is shown in Fig. 1. Use is made of the versatile 555 timer i.c. Two devices are used here, IC1, 2 both wired as astable multivibrators. Output from the 555 is at pin 3, and the

number of times per second (frequency) that it switches between the 0V and positive supply rails is determined by the values of C2 and C3 and their series resistors.

The frequency of IC1 is equal to $1/[(R1 + 2R2) \times C2] = 2.3\text{Hz}$, and for IC2 the frequency is 1.5Hz.

The exact values of frequency are not too important, but their ratio is, as this determines the flashing rate and brightness of LP3. A frequency ratio of 2:3 was found most suitable. This can be experimented with by changing the values of R4 and/or R2.

When power is applied to the circuit lamp pair LP1 and LP2 will flash alternatively at 2.3Hz as will pair LP4 and LP5 at 1.5Hz. Lamp LP3 will only be on (bright) when IC1 pin 3 is high and IC2 pin 3 is low and vice versa. The centre lamp LP6 is on all the time as it is connected directly across the supply lines.

The total effect is to simulate a twinkling star.

The wattage of LP6 is less than all the other lamps in an attempt to produce an even illumination from all lamps. The other lamps will appear less bright than their rating due to being constantly turned on and off.

The lamps are over-run to increase brightness i.e. 6V lamps operated from a 9V power supply. This has the effect of reducing the bulb life but is of little consequence in this application.

POWER SUPPLY SECTION

Mains voltage is placed across the primary of T1 via S1 resulting in 6V a.c. appearing across T1 secondary. This is half-wave rectified by D1 to produce pulsed d.c. to reservoir capacitor C1 which results in a fairly smooth d.c. level of about 9 volts at C1 positive terminal.

STAR

The construction is in two distinct parts, the encased circuit board/transformer and the star lamp wiring. Four wires interconnect the two.

The prototype five-pointed star was made from hardboard and covered with aluminium cooking foil and edged with tinsel. The star was drawn inside a 30cm diameter circle. This dimension is not critical and can be altered to suit application.


With the hardboard cut to shape drill the six lampholder mounting holes. The size will vary according to holders obtained. Secure the plastic four-way terminal block in place using countersunk bolts. Crinkled foil (or other covering) can now be lightly glued or folded over the edges to hold in place followed by the fixing of the lampholders which can then be interconnected according to Fig. 2.

CIRCUIT BOARD

The remainder of the components with the exception of the transformer were mounted on a small piece of 0.1 inch matrix stripboard size 19 strips x 22 holes with breaks made on the underside as seen in Fig. 3.

Assemble the components as shown in Fig. 3 including the flying leads and then fix this and the transformer to the base of the case. The four wires from the board reach the externally mounted screw terminal block via a small hole drilled in the case. The mains cable enters the case, near the transformer, via a cable strain relief bush or other means of securing cable.

Insert the bulbs in their holders and interconnect the two sections and plug into the mains. A twinkling star should be seen, which should add sparkle to your festive decorations. □

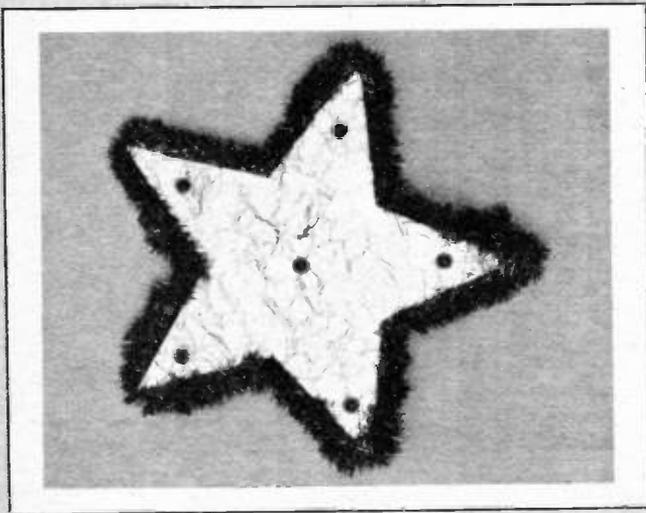

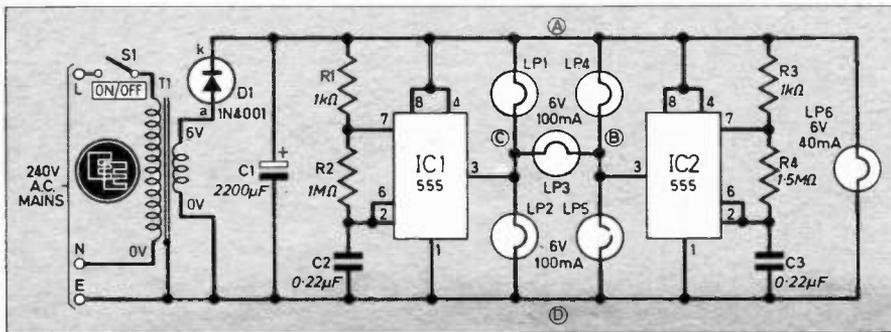


Fig. 1. The complete circuit diagram of the Twinkling Star including an integral power supply unit. Alternately, a battery eliminator can be employed, see text.

COMPONENTS

Resistors

- R1 1kΩ
- R2 1MΩ
- R3 1kΩ
- R4 1.5MΩ
- All ½W carbon ± 5%

Capacitors

- C1 1000µF 10V elect.
- C2, 3 0.22µF plastic (2 off)

Semiconductors

- D1 1N4001 or other 1A silicon diode
- IC1, 2 555 timer i.c. (2 off)

Miscellaneous

- LP1-LP5 6V 100mA m.e.s. bulbs (5 off)
- LP6 6V 40mA m.e.s. bulb
- T1 mains primary/6V 500mA secondary
- S1 mains on/off toggle
- Stripboard: 0.1 inch matrix 19 strips × 22 holes; m.e.s. lamp-holders (6 off); 4-way plastic screw terminal block (2 off); p.v.c. covered wire; materials for star; case; 6BA fixings; solder tag; mains cable.

COMPONENTS
approximate
cost

£4.20
excluding case

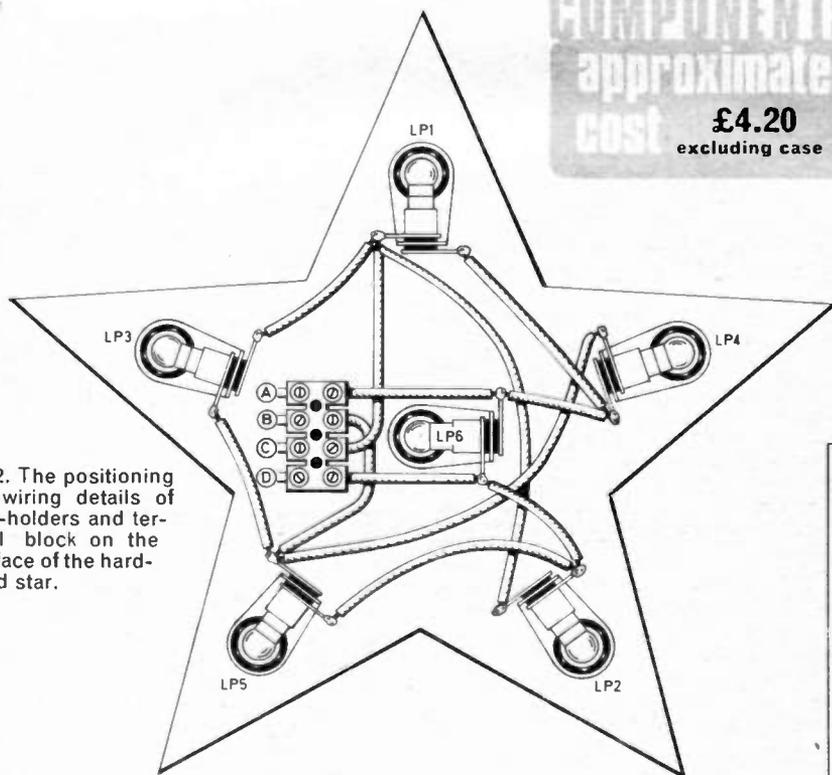


Fig. 2. The positioning and wiring details of lamp-holders and terminal block on the rear face of the hard-board star.



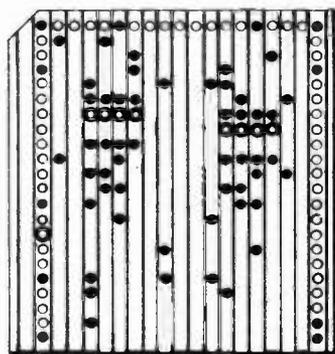


Fig. 3. (Above and right). Shows the layout of the components on the topside of the board (and breaks to be made on the underside) fitted in the case with complete interwiring details.

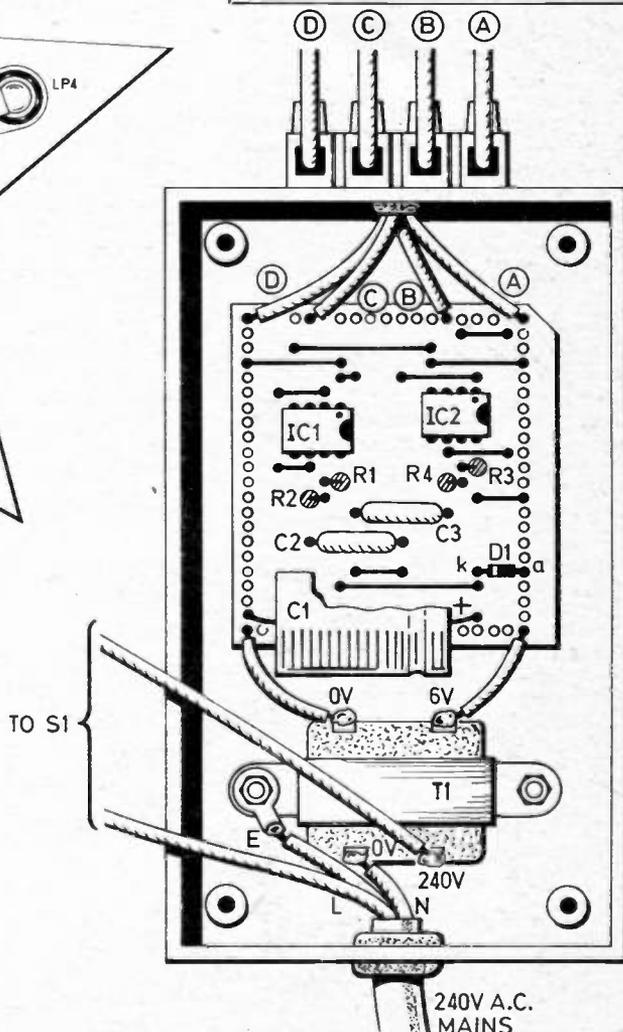

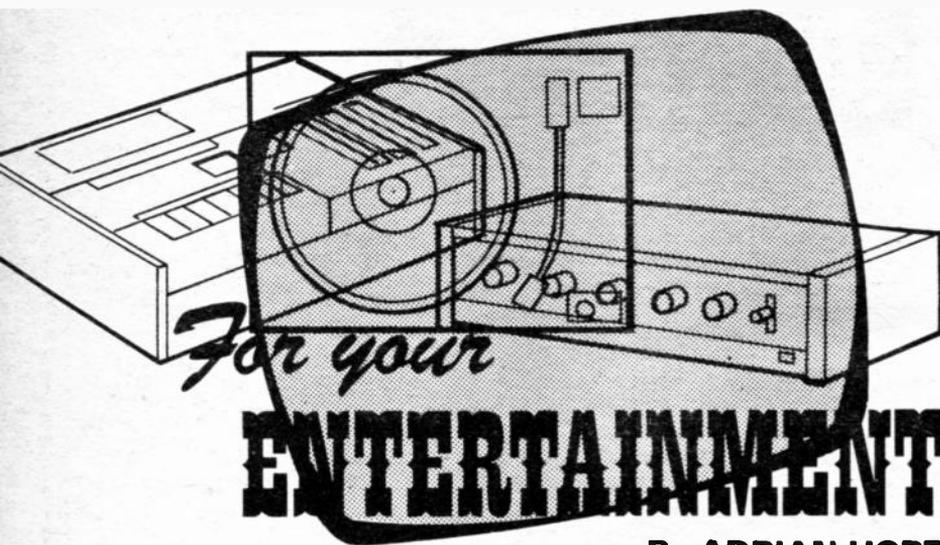

By **ADRIAN HOPE**

Choosing Your Game

The world of video games is now moving so fast that almost anything written about specific brand name products and their price is likely to be out of date before it's published. Here then are some more general guidelines which could help anyone thinking of buying a game for themselves or their children.

First and foremost the word "game" is now a misnomer; many video games or toys could equally well be called "educational aids". But advertising men know full well that the word "education" is the kiss of death to large sales.

So microprocessor-based fully programmable systems which can be used for education will often be sold under the generic label "TV Game". Children and adults who would normally run a mile at any suggestion that they should take up home computing, can be hooked on the idea while thinking that they are simply playing games with a toy.

It's fascinating for instance to watch children in a modern amusement arcade striving to beat the ever more sophisticated computer games that are appearing. Without realising it they are learning to interface with a computer display screen and thereby learning skills that will be of real value to them in this modern age.

In the beginning, which in this fast moving field of technology is only about five years ago, all TV games were built up from literally dozens of discrete chips and transistors. After 1976, when GI produced a single i.c. (integrated circuit) offering six games, the price fell significantly.

Dedicated Game

But all those early games, whether based on discrete circuitry or the single chip, were "dedicated" i.e. completely inflexible over the choice of game. To extend the choice of games, and to make the games more complicated, required the provision of more digital memory to store more game instructions.

One early idea was to store the game instructions on a cassette tape and this approach was patented by Sanders Associates. This is the American research firm who invented and patented the

original concept of TV games, but subsequently sold the licensing rights to Magnavox (the North American subsidiary of Philips).

Brain Power

The idea of taped game instructions didn't catch on and designers came up with the idea of a semi-programmable game. The basic game circuit contains very little memory and is thus like a body without a brain.

The brain power comes in cartridges, each with enough ROM (or Read Only Memory) to instruct the game body how to play one or more specific games. The more complicated the games and thus the more instructions needed, the fewer the games that can be stored in a single cartridge.

Semi-programmable games of this type tend to be fairly cheap, currently as low as £30 for the game body and around £10 a time for each cartridge of brain power. A major disadvantage is the lack of long term flexibility.

Fully Programmable

A fully programmable game costs more because the body contains a microprocessor and is thus really a mini-computer. One of the cheapest is the Philips Videopac G7000 which is made by Magnavox in the USA and sold here for around £150.

Fully programmable games are very flexible and thus of greater long term value to the owner.

The microprocessor has a Random Access Memory or RAM. The instructions necessary for programming the micro to play a TV game are stored in a ROM contained in a cartridge superficially similar to that used for a semi-programmable game.

When the cartridge is plugged into the game, its ROM dumps programming instructions for the game into the micro RAM.

In the Philips-Magnavox game the microprocessor has an 8K bit ROM of its own which permanently offers enough basic memory to generate characters and graphics on the screen under the control of whatever game instructions are fed into

the microprocessor RAM by the cartridge ROM. The micro RAM has a capacity of 2K bits and the cartridge ROM has a 16K bit capacity.

The instructions are grouped in 8 bit words and transferred from the cartridge ROM to the micro RAM at a rate of around 5 Megabits per second. So although the cartridge is programming the micro-processor like a human operator, it's far, far faster than any human could ever hope to be.

In practice it takes an eight man team at Magnavox around a month to write the programme for each new game and the cartridge ROM dumps them into the micro RAM in well under a second!

Because the cartridge ROM has a greater capacity than the micro RAM, each cartridge can contain several different games, for instance several versions of car racing and moon landing, or one much more complex, multi-stage game like golf or baseball which is continually scanned by the micro while the game is played. With a fully programmable game it is theoretically possible to use something other than a cartridge ROM to supply the micro RAM with instructions.

Cable Games

One idea currently gaining support in the USA is for cable TV stations to pipe not just TV entertainment into the home, but a choice of TV game programmes. Several of the British TV companies are working on the idea of transmitting game programmes over the air.

A special interface cartridge links the micro RAM to the cable TV outlet or TV receiver and in a split second the micro is programmed to play a completely new game. And of course the game needn't be a game. If the unit has a typewriter style keyboard, as well as ordinary joystick game controls, it can be used in the manner of a budget computer and even used as a video film titling machine.

You type out a phrase on the keyboard and connect the system output to the input of a video recorder; the phrase is then "written" directly onto video tape. There's also the possibility of interface with an ordinary audio cassette recorder, to enable information typed into the keyboard to be stored as a digital recording on an audio cassette.


Making a Choice

Indeed, the possibilities with a fully programmable video games system are virtually limitless. But how does a customer know whether a game is fully- or only semi-programmable?

Obviously prices are one indication. At current levels a games unit costing around £30 will almost certainly be only semi-programmable. But how to tell whether a unit costing around £150 is a good-value for money fully-programmable unit or an overpriced semi-programmable?

Unfortunately, there's no really fool-proof rule of thumb. The best guide is availability or otherwise of a keyboard. If the unit either has a built in alpha-numeric (i.e. typewriter style) keyboard, or if such a keyboard can be used as an optional extra, then it will be fully programmable.

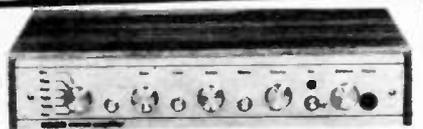If there is no keyboard facility possible, and the game has just fader or joystick controls, it's an odds on certainty that it's only semi-programmable.



20 x 20 WATT STEREO AMPLIFIER
Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS. 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/4" x 3" x 10" approx. **NEW** feature—units now includes a built in four channel stereo sound facility.

£31.90
£3.00 p&p

30x30 WATT AMPLIFIER IN KIT FORM
For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output, 60x60 watts peak. For use with 4 to 15 ohms speakers.

£31.50 p&p
£3.00

SPECIAL OFFER
30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge.

£57.00
+ p&p £6.00

EMI SPEAKER BARGAIN
Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£18.25
Per stereo pair
£3.65 p&p

BSR P200
Belt drive chassis turntable unit semi-automatic, cueing device. AOC OLM 30 Mk III Magnetic Cartridge to suit.

£25.50 p&p £2.60
£7.95

BSR Manual single play record deck with auto return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use.

OUR PRICE £11.25 £2.75

GARRARD DECK MODEL CC 10A
Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£8.15 p&p £2.05 Size 12" x 8 1/2"

UNIT AUDIO STAND
Can be used with TV foot. Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors.

£3.95 £2.25 p&p
24" x 12 1/2" x 11 1/2" approx.

BARGAIN FOR PERSONAL SHOPPERS ONLY
Altone UA4 Stereo System
Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones.

complete with speakers £35.75

Micro Cassette Recorder
Pocket size—home or office use or when travelling.

£14.25

Battery operated fluorescent camping lamp.
Runs off 8 U2 batteries.

£4.80

Mullard


AUDIO MODULES IN BARGAIN PACKS
CURRENT CATALOGUE

PRICE £ AT OVER 25 PER PACK

SEE OUR PRICES

- 1** PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.
OUR PRICE £5.00
p&p £1.00
- 2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.
OUR PRICE £7.65
p&p £1.00

illus. £7.65

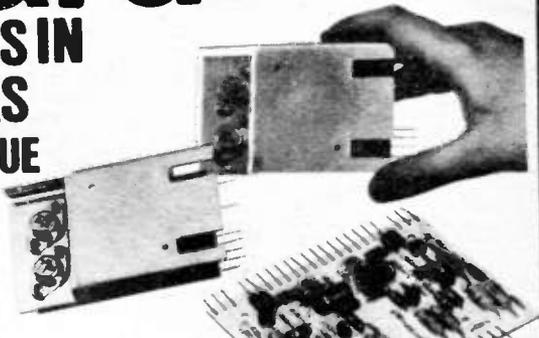

Two Way Speaker Kit


ACCESSORIES
Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance.
£3.00 plus £1.50 p&p

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors.
£4.05 per stereo pair plus £1.55 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.
Size approximately 9 1/2" x 8 1/2" x 4"
p&p £2.25

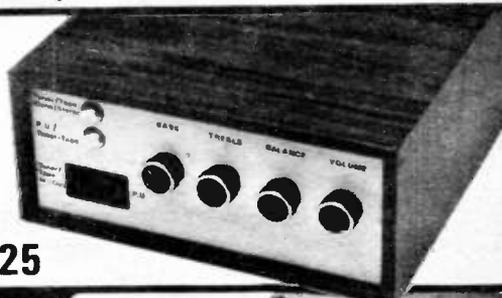

£12.25


BARGAINS FOR PERSONAL SHOPPERS

- LCD Solar 5 function with backlite stainless steel finish case and strap £7.40
- LCD Solar Chrono 9 function with backlite stainless steel finish case and strap £9.55
- Chrono stop watch 9 function with back lite stainless steel finish case and strap £8.95
- Solar Alarm LCD stainless steel case and strap. £21.95
- AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer £12.20
- 100 Watt Power Amp Module £14.25
Mains power supply for above unit £3.60
- DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3 1/2" approx tweeter inc crossovers £20.45
- VIDEOMASTER Super Score TV Game with pistol mains operation £15.95
- PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation £42.90
- ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop. £24.50


100 WATT MONO DISCO AMP
Size approx 14" x 6" x 10 1/2"
Brushed aluminium fascia and rotary controls.
Five vertical slide controls, master volume, tape level, mic level, deck level.
PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2 or vice versa Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.
p&p £4.05 £66.45



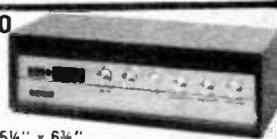50 WATT MONO DISCO AMP
£30.60 p&p £2.70
Size approx. 13 1/2" x 5 1/4" x 6 1/2"
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



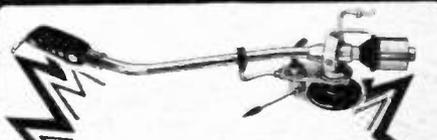Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00.
P & P £2.50
OUR PRICE £11.95



323 EDGWARE ROAD, LONDON W2
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Prices correct at 1.10.79 and subject to change without notice.
NOTE: Persons under 16 years not served without parent's authorization.

A new edition from **Newnes Technical Books**

Questions and Answers Integrated Circuits

Second Edition

R. G. Hibberd

Covers in easy-to-follow Q & A format, all main types of integrated circuits. A new chapter on microprocessors and their application has been added for this new edition.

1979

108 pages

£1.55

(US \$3.50)

In the same series

Q & A Electronics, Clement Brown

Q & A Hi-Fi, Clement Brown

Q & A Radio Repair, Les Lawry-Johns

Q & A Radio and Television — Fourth

Edition, H. W. Hellyer and I. R. Sinclair

£1.55 each (US \$3.50)


For further information please send for a free colour brochure describing these and many other publications



Newnes-Butterworths

Borough Green, Sevenoaks, Kent TN15 8PH. Tel: (0732) 884567

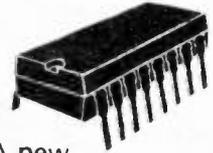Butterworths have companies in Australia, Canada, New Zealand, South Africa and the USA, where local prices apply



What's new from Heathkit?



IM 2212 — Auto Ranging DMM



IO 4105 — Single Beam 5 MHz Oscilloscope



IM 5217 — Portable Multimeter

Plus

* GD 1290 — VLF Metal Locator

* HX 1681 — CW Transmitter

* IR 5201 — XY Recorder

* CI 1525 — Car Temperature Indicator

These brand new self-assembly kits are designed to the highest specification.

The step-by-step instructions make them easy to build at your leisure in your own home.

And first class quality makes them excellent value for money.

Details of the full Heathkit range are available in the Heathkit catalogue. Send for your copy now.



IM 2215 — Hand-held DMM

To: Heath (Gloucester) Limited, Dept. (EE12), Bristol Road, Gloucester, GL2 6EE.

Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.

Name _____

Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

Soldering
Iron offer
FREE

When you receive your catalogue you will get details of this free offer.




There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451).

HEATHKIT



SQUARE One

This month we show some of the circuit symbols and circuit references used in E.E. circuit diagrams to represent components and their interconnections.

CAPACITORS

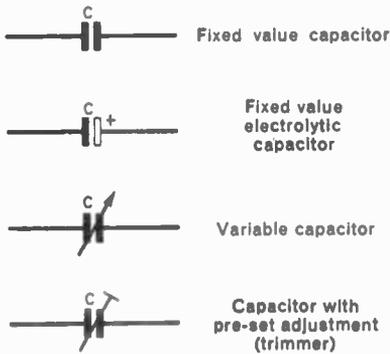

MISCELLANEOUS

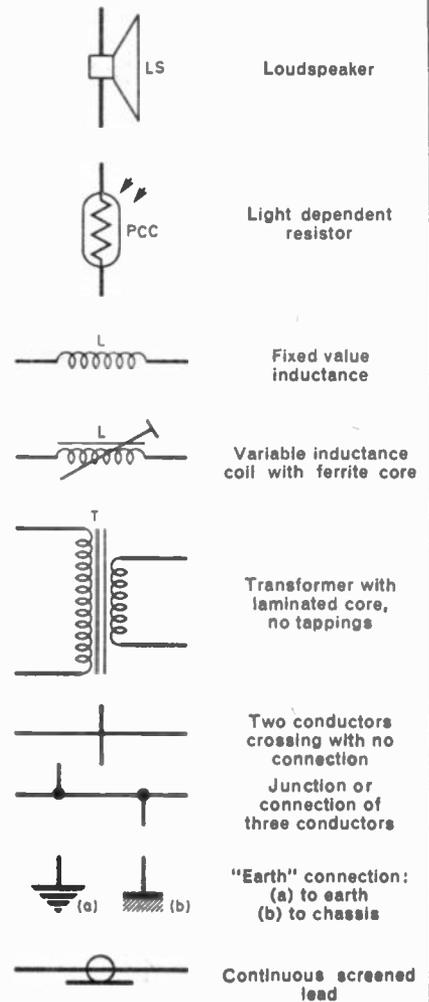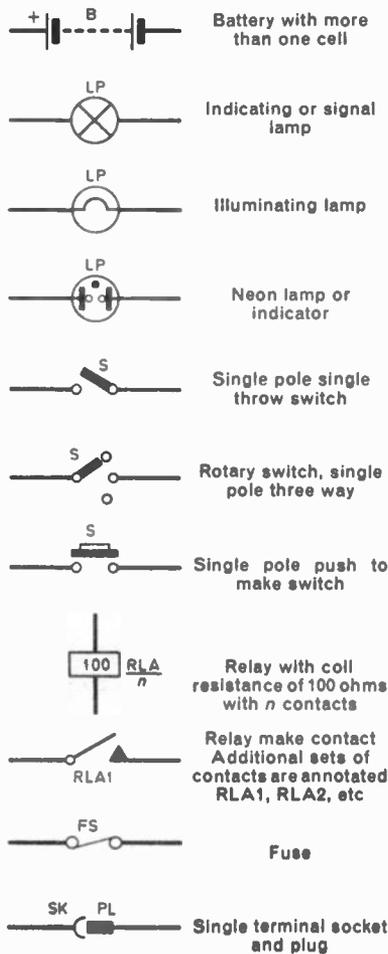

EE CROSSWORD No 22 BY D. P. NEWTON

ACROSS


- 1 & 5 Means of preventing alternative circuits (10, 4).
- 7 Random electrical discharge produces sound action in such a manner.
- 9 Personal induction.
- 10 To oppose electrically.
- 12 Coulombs per volt.
- 14 Use X-rays for creative activity.
- 16 Roof cover.
- 18 Vegetative vehicle decay basically caused by electrolytic action.
- 19 Specialises in entertainment by means of electronic display.
- 20 Descriptive of one who is rather rude and basic.
- 22 Valve interior, possibly needed for 14 across unless you are 20 across.
- 25 To run lazily.
- 26 I moan Ma, about a gas (Anag.).

27 100db?

28 (5, 5).


DOWN

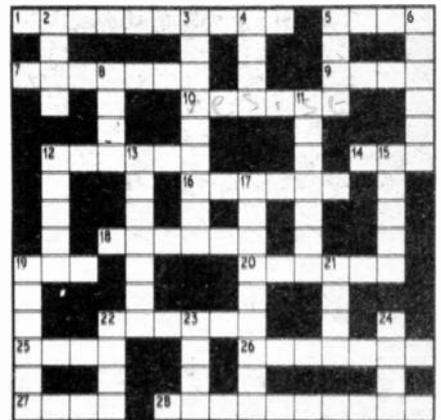- 2 Discharge tube shows a red light.
- 3
- 4 Volts per amp.
- 5 Examination intended to indicate a fault, even, perhaps, a soaking.
- 6 The output end of lines of force?
- 8 Equine goad of circuit extension.
- 11 Creator of electrical embarrassment, possibly by 20 across.
- 12 1dB?
- 13 Galvo which is never ecstatic.



Solution on page 730

- 15 & 24 Communications satellite which got the worm? (5, 4).
- 17 Selection of one and then the other by means of a.c?
- 19 Element designed to respond to waves.
- 21 The triode provides an entertaining group.
- 22 Small unit of plant life.
- 23 Relaxation, but not a circuit.

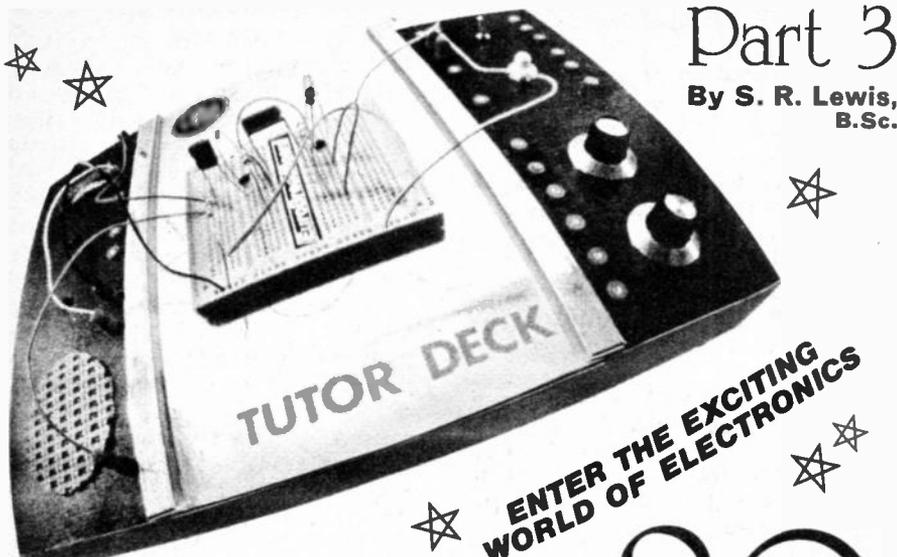

Part 3

By S. R. Lewis,
B.Sc.

ENTER THE EXCITING
WORLD OF ELECTRONICS

TEACH-IN 80

IN THE first part of this series, the simplest electric circuit was described. This consisted of a piece of wire connected to a battery. We saw how the electromotive force of the battery supplied electric charge to maintain the field across the wire.

In real life, it would be unwise to connect a wire directly across a battery, since either the wire or the battery would be damaged by the large current which would flow.

Electric current has already been defined as the rate of flow of charge. Since the wire across the battery caused too much current to flow, let us instead consider a resistor placed across the battery terminals (Fig. 3.1). The resistor/battery combination forms a closed loop and since we know that charge cannot build up in one place, an imaginary cross-section taken anywhere in the loop would show the same number of electrons crossing it per second.

The actual rate of flow of charge (current) can be calculated as we know both the voltage across the resistor and the value of the resistor. The resistance in the loop due to the connecting leads and the battery itself we will ignore for the moment.

From Ohm's Law the current is found to be V divided by R , where V is the battery voltage and R is the resistance. If the units were

measure in are volts and ohms respectively then the current will be in amperes.

We now have a complete description of the circuit—all currents and voltages have been specified.

TWO RESISTOR CIRCUIT

Let us add one step of complication to the circuit by connecting another resistor in the circuit as shown in Fig. 3.2.

Again we have a simple loop so we must again deduce that the current in any part of the circuit

must be the same. Hence the current in resistor R_A is the same as that in R_B . If we call the current I we should be able to calculate it from a knowledge of the values of the two resistors and the battery voltage.

The electromotive force of the battery V must be exactly equal to the sum of the potentials across the two resistors. Mathematically we can state this as

$$V = V_A + V_B$$

But for any resistor the potential difference between its ends is equal to the current flowing through it multiplied by the resistance. So

$$V_A = I \times R_A \text{ and } V_B = I \times R_B$$

Combining these three equations we get

$$V = (I \times R_A) + (I \times R_B)$$

or $V = I \times (R_A + R_B)$

To get I we simply divide both sides of the equation by $(R_A + R_B)$ obtaining

$$I = V / (R_A + R_B)$$

Stated in words this equation indicates that the current in this circuit is exactly the same as that which would flow if a resistor whose value was equal to that of the values of the two resistors added together was used in their place.

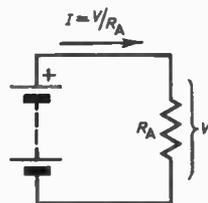


Fig. 3.1. (left) In this simple circuit all the voltages and currents are defined by application of Ohm's Law. An imaginary cut at any point in the circuit would show the same number of electrons crossing per second i.e. the same current.

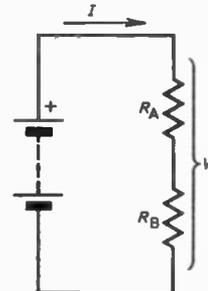


Fig. 3.2. This circuit shows two resistors in series with the battery.

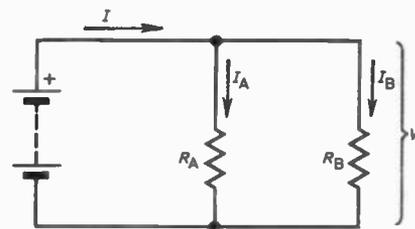


Fig. 3.3. The two resistors in the circuit shown here are in parallel.

When the same current flows through two (or more) circuit components we say that the two components are in **series**.

We can use the same sort of reasoning as used above to derive the result that if any number of resistors are placed in series then their overall resistance is equal to the sum of all the individual resistances.

TWO LOOP CIRCUIT

There is an alternative way of connecting a second resistor in the circuit and this is shown in Fig. 3.3.

Here we have a new situation as we have departed from the simple single-loop circuit. The current from the battery now divides into two paths, some of it flowing in resistor R_A and some in resistor R_B ; but how much in each?

Since charge cannot accumulate in any part of the circuit the current measured at the battery terminals must be equal to that flowing in the two resistors. Mathematically,

$$I = I_A + I_B$$

Both resistors have the same voltage across them so each of the currents can be simply derived.

$$I_A = V/R_A \text{ and } I_B = V/R_B$$

Combining these two equations we get

$$I = V/R_A + V/R_B$$

or
$$I = V \left(\frac{1}{R_A} + \frac{1}{R_B} \right)$$

We call the reciprocal of resistance (one divided by the resistance) the **conductance** of a resistor. The equation we have obtained can thus be stated in words by saying that the total current flowing in the circuit is the same as that which would flow if a resistor whose conductance is the sum of the two individual conductances is used in their place.

When two (or more) components have the same potential across them we say that they are in **parallel**.

For the case of two resistors in parallel we can find the value of the single resistor which could replace them. Its conductance ($1/R$) must be equal to the sum of the two conductances.

So:

$$1/R = 1/R_A + 1/R_B$$

But
$$1/R_A + 1/R_B = \frac{R_A + R_B}{R_A \times R_B}$$

Thus
$$\frac{1}{R} = \frac{R_A + R_B}{R_A \times R_B}$$

Inverting both sides gives the required value of the equivalent resistance:

$$R = \frac{R_A \times R_B}{R_A + R_B}$$

When there are more than two resistors in parallel, it is not so simple to find the equivalent single resistance. It is necessary to take the reciprocal of each of the resistors, add them together and then take the reciprocal of the sum.

MORE COMPLEX CIRCUITS

It is worthwhile studying the results obtained above since the concepts of series and parallel elements are very useful in understanding how electronic circuits operate. Very often one will come across a fairly complex looking circuit but on inspection it appears to be simply a combination of series and parallel connections.

It should be noted that not all circuits are capable of being analysed into series and parallel units but it is unusual to find a circuit with no components or groups of components in one or other of these arrangements.

Let us look at a circuit which, while appearing complex at first sight, in fact breaks down into easily studied sub-units.

The circuit is shown in Fig. 3.4 and consists of four resistors connected to a battery. We want to find the current flowing from the battery.

Inspection shows that resistors R_C and R_D must be in series since they both have the same current flowing through them. They could therefore be replaced with a single resistor of value $(R_C + R_D)$, see Fig. 3.4b.

Let us call this new resistor (or imaginary resistor) R_E . It now becomes apparent that resistors R_B and R_E are in parallel, the value of the equivalent resistor being $(R_B \times R_E)/(R_B + R_E)$.

Let us redraw Fig. 3.4b inserting a new resistor R_F in the place of the parallel combination, see Fig. 3.4c. Now R_F is in series with R_A , the equivalent resistance being $R_A + R_F$. We can now find the battery current by simply dividing the battery voltage by $R_A + R_F$.

Let us insert some values into the circuit to see how the calculation goes.


$$R_E = 100 + 200 = 300 \text{ ohms}$$

$$R_F = \frac{300 \times 300}{300 + 300} = 150 \text{ ohms}$$


$$R_F + R_A = 150 + 750 = 900 \text{ ohms}$$

$$I = 9/900 = 0.01 \text{ A or } 10 \text{ mA}$$

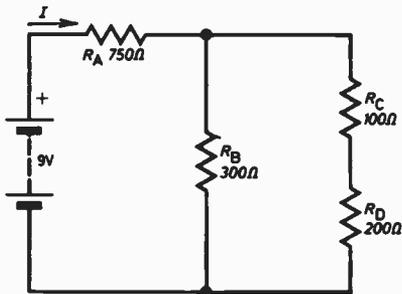
Knowing the battery current we can now work backwards and calculate all the voltages and currents in the circuit. We know the current in R_A is 10mA so the potential difference across it must be 750×0.01 volts, that is 7.5V. The voltage across R_F must therefore be $9 - 7.5 = 1.5 \text{ V}$.



(a)

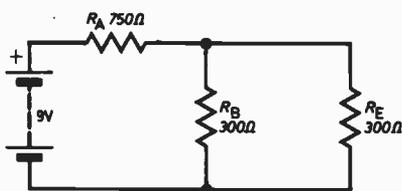

(b)

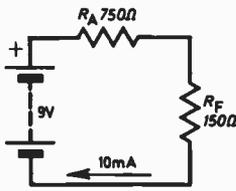

(c)

Fig. 3.4. (a) shows the circuit to be analysed (b) the series resistors replaced by a single resistor and (c) the parallel combination eliminated to give the required single loop.

The current through R_B is $5/300=5\text{mA}$ and the same current must flow through (R_C+R_D) . The voltage across R_C is therefore $100 \times 0.05=0.5\text{V}$ and that across R_D must be $200 \times 0.05=1\text{V}$.

BRIDGE CIRCUITS

Take a look at the circuit in Fig. 3.5. It consists merely of four resistors connected to a battery with a meter placed across the junctions of the two pairs of resistors. At first sight one would not think this a very useful circuit but it is one that turns up a great deal in electronics.

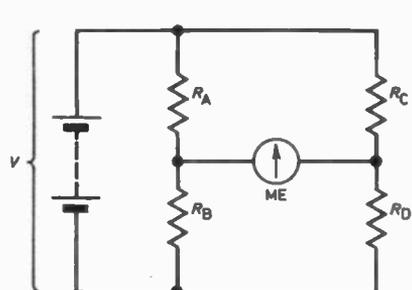


Fig. 3.5. A simple Wheatstone bridge circuit.

Let us make a few calculations so that we know exactly what is going on in the circuit. We will assume that the meter can measure voltage without any current passing through it. This may seem unrealistic but as long as

we make the currents flowing in the rest of the circuit large as compared to the current in the meter then the error caused by neglecting the meter will be minimal.

If no current flows in the meter then it is effectively an open circuit. The circuit is thus reduced to a parallel arrangement of two sets of resistors in series.

The current flowing in the left-hand arm is given by $V/(R_A+R_B)$. The voltage at the junction of R_A and R_B is therefore given by

$$V_A = R_B \times I_B = R_B \times \frac{V}{(R_A + R_B)}$$

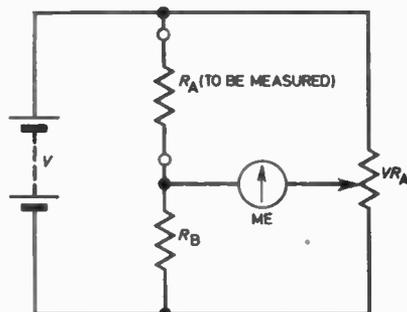


Fig. 3.6. The simple bridge can be converted into an ohmmeter by using a potentiometer and fixing R_B .

Similarly the current through the right-hand arm is $V/(R_C+R_D)$ and the voltage at the junction of R_C and R_D is

$$V_D = R_D \times I_D = R_D \times \frac{V}{(R_C + R_D)}$$

The voltage measured by the meter is $V_A - V_B$ which is

$$\frac{V \times R_B}{R_A + R_B} - \frac{V \times R_D}{R_C + R_D}$$

or $V \times \left(\frac{R_B}{R_A + R_B} - \frac{R_D}{R_C + R_D} \right)$

An interesting situation occurs when $V_A = V_B$ for we obtain

$$\frac{V \times R_B}{R_A + R_B} = \frac{V \times R_D}{R_C + R_D}$$

Now since V appears on both sides of the equation we can cancel it out, finally arriving at

$$\frac{R_B}{R_A + R_B} = \frac{R_D}{R_C + R_D}$$

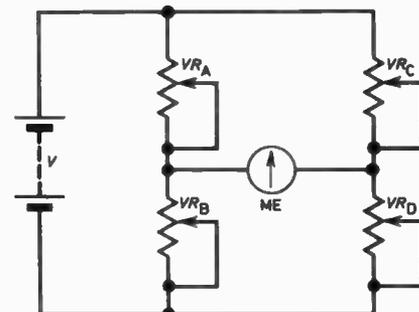


Fig. 3.7. A simple electronic slide-rule can be achieved using four variable resistors (or potentiometers connected as variable resistors).

Cross multiplying gives

$$(R_C \times R_B) + (R_D \times R_B) = (R_D \times R_A) + (R_D \times R_B)$$

Cancelling $R_D \times R_B$ gives

$$R_D \times R_A = R_B \times R_C$$

or $\frac{R_A}{R_B} = \frac{R_C}{R_D}$

The circuit we have been looking at is known as a **Wheatstone bridge circuit**; "Wheatstone" after its inventor and "bridge" from the appearance of the meter as a "bridge" between the two sides of the circuit. When the meter is made to read zero we say that the bridge is balanced. The important fact to note is that when the ratio of the four resistors is chosen so as to balance the circuit it does not matter what the battery voltage is, the meter will still read zero.

What use is the circuit? First let us fix the value of R_B and instead of two resistors let us replace R_C and R_D by a potentiometer. We now have a way of

PART 3 QUESTIONS

3.1. To reduce the current in a resistor should another resistor be placed:

- (a) in parallel
- (b) in series
- (c) either
- (d) neither

3.2. The following are sets of values for R_A , R_B , R_C and R_D in the bridge circuit of Fig. 3.3. Which will form a balanced circuit:

- (a) 1000, 2000, 2000, 4000
- (b) 1000, 2000, 3000, 4000
- (c) 1000, 2000, 1, 2
- (d) 100, 1, 100, 100

3.3. What resistance could be used in place of 80, 100 and 400 ohms in parallel:

- (a) 580
- (b) 40
- (c) 80
- (d) 32

3.4. What value must be placed in parallel with 100 ohms to give an equivalent resistance of 90 ohms:

- (a) 10
- (b) 100
- (c) 900
- (d) 9000

PART 2 ANSWERS

2.1 a) 2.2 b) 2.3 b) 2.4 b) 2.5 a)

EXPERIMENT 3.1: SERIES AND PARALLEL

Components required: 10kΩ resistors (4 off), 100kΩ resistor

Connect the circuit as shown in Fig. 3.8a, the component layout being shown in Fig. 3.8b. Resistors R3 and R4 should not be inserted at this stage.

Adjust the setting of VR1 until the meter reads zero. The reading on the scale of VR1 should be very close to "5". Next insert the resistor marked R3 into the circuit and again adjust the potentiometer until the meter reads zero. Note the new reading. Remove R3 and fit R4. Adjust the potentiometer and note this third reading. Finally insert both R3 and R4 and again find the new balance point.

ADDITIONAL CONNECTIONS FOR BOTH EXPERIMENTS

On right hand panel of Tutor Deck:
link S1(a) to B1 +9V


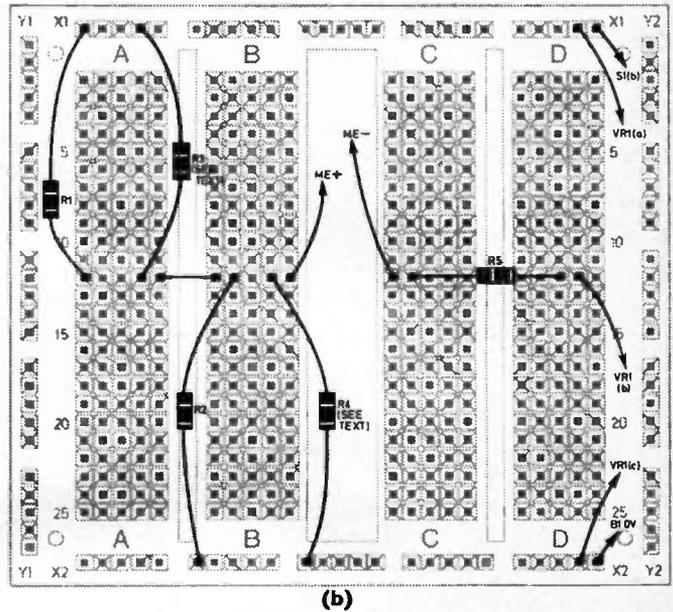
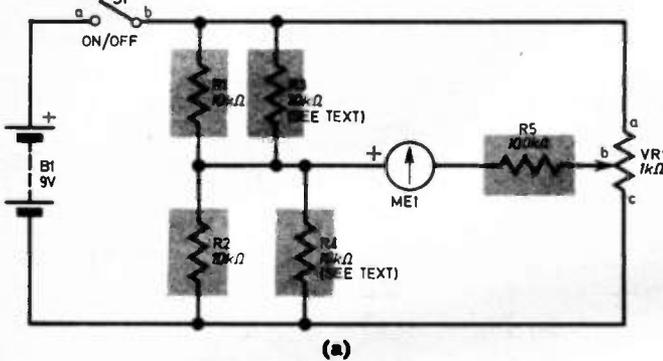


Fig. 3.8. (a) Circuit diagram of the experiment for investigating series and parallel connections. (b) layout of the components on the Tutor Deck.

EXPERIMENT 3.2: SIMPLE OHMMETER

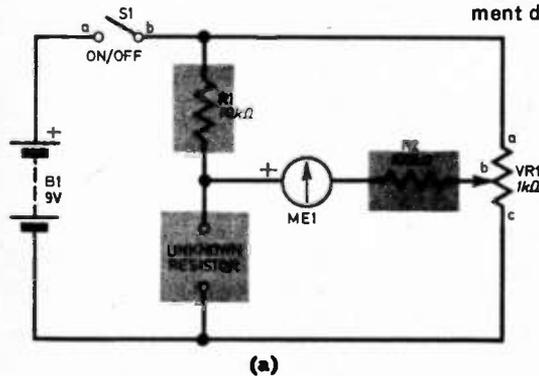Components required: 10kΩ resistor, 100kΩ resistor



The circuit of a simple ohmmeter is shown in Fig. 3.9a with the component layout on The Tutor Deck in Fig. 3.9b.

This ohmmeter can measure resistances from about 1kΩ to 100kΩ. Outside this range the potentiometer will be very near the end of the track making measurement difficult.

The unknown resistor should be placed in the deck and the potentiometer adjusted until

the meter reads zero. The value of the unknown resistor will then be given by

$$R = \frac{S}{10 - S} \times 10k\Omega$$

where S is the scale reading of the potentiometer.

Alternatively, the scale of the potentiometer can be marked so that it reads resistance directly, see Fig. 3.9c.


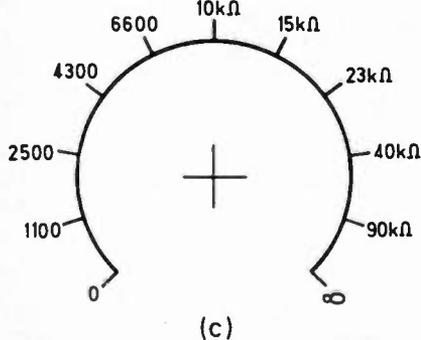


Fig. 3.9. (a) Circuit diagram of the simple ohmmeter (b) Layout of the components on the Tutor Deck. (c) Scaling for the potentiometer so that resistance can be measured directly.

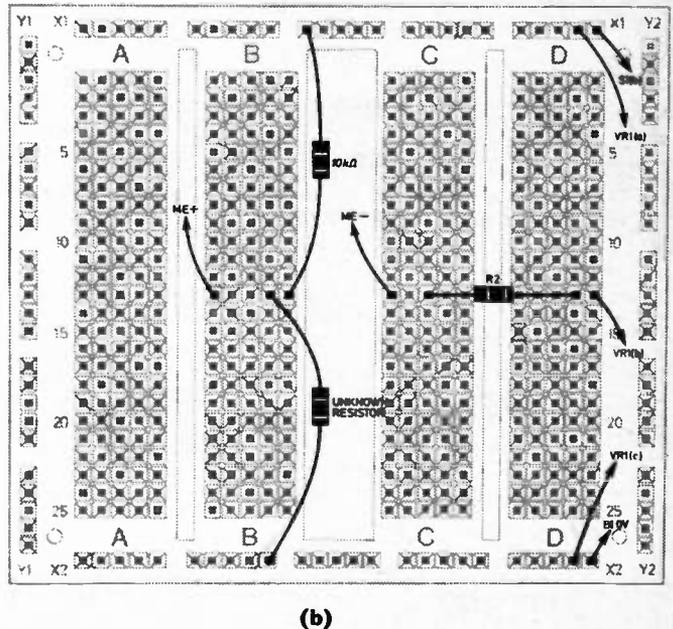

varying the ratio R_C/R_D since R_C is now the resistance from the wiper to the top of the potentiometer and R_D is the resistance from the wiper to the bottom of the potentiometer—both varying as the wiper is moved. Imagine the scale of this potentiometer calibrated so that the ratio R_C/R_D can be read directly. We have now built a simple ohmmeter.

The unknown resistor is simply placed in the position of R_A and the potentiometer adjusted until the meter reads zero. By reading the potentiometer scale and knowing the resistance R_B it is a simple matter to calculate R_A .

$$R_A = R_B \times \frac{R_C}{R_D}$$

SIMPLE SLIDE-RULE

Another use of the Wheatstone bridge is as a simple electronic slide-rule for doing simple multiplications and divisions. All four of the resistors in the bridge circuit are now replaced with variable resistors whose scales are calibrated from zero to 10. To do division we set variable resistor R_B to "1". The divisor is set on R_D and the dividend on R_C . The variable resistor R_A is then adjusted to make the meter read zero, its scale then showing the answer.

To do multiplication, R_A is set to "1" and the two numbers to be multiplied are set on R_B and R_C . R_D is then adjusted to make the meter read zero when its scale

should indicate the answer. Of course, this "computer" is really only of limited use since it is restricted to positive numbers below ten.

Many pieces of test equipment have been produced using the principle of the Wheatstone bridge. Some use fluctuating voltages to power the bridge with a speaker or earphone to monitor the balance of the bridge. It does not matter that the voltage is fluctuating since when the bridge is balanced the current in the balance monitor, be it meter or earphone, will be zero.

Next month we will meet the simplest semiconductor device, the diode.

The TK Electronics catalogue consists of 28 pages and contains a useful selection of integrated circuits. Also, there are some interesting circuit diagrams with suggested applications.

Copies of the TK Electronics catalogue are available free of charge from TK Electronics, Dept EE, 106 Studley Grange Road, London, W7 2LX. A 230 x 152mm stamped addressed envelope is required.

Only 7 pages make up the Ace Mailtronix catalogue, but most components called for in our projects are listed. They are also prepared to obtain some of the more difficult components.

Cost of the catalogue is 30p which is redeemable with orders over £5.

CONSTRUCTIONAL PROJECTS

Looking through the components list, we do not envisage any component buying problems for our special Christmas projects, *Peg-A-Hole*, *Everlasting Candle* and *Twinkling Star*.

Most readers will, no doubt, use their own ingenuity for the housing of the *Everlasting Candle* (an old torch perhaps?), however Home Radio are able to supply a complete kit, including ceiling rose and plastic tubing.

All the "specials" for the *EE Radio Control System* were covered last month. The additional components, including crystals, listed this month should be available from most advertisers.

The only item likely to be difficult in our *Uniboard Burglar Alarm* project, is the thyristor MCR102. This would appear to be only available from Maplin. However, the 2N5060, 2N5061 or 2N5062 could be used.

The components for the *Modulated Tone Generator* should present no buying problems. The power transistor specified can be substituted by many other power types, for example the common 2N3055. Plastic types are not essential since TO-3 and TO-66 cased versions can easily be mounted "off-board" on heatsinks (required for higher power outputs) and connected by leads to the board positions.

Any type of miniature or sub-miniature relay capable of operating at 9V, with a coil resistance of approximately 185 ohm, should be suitable for the *Lightcall* project. However, the relay contacts must be rated at 240V current as required.

The relay used in our prototype model was the RS Components 12V 185Ω, stock No. 348 980.



By Dave Barrington

Two small mail order catalogues have been received this month from TK Electronics and Ace Mailtronix.





LIGHTCALL

visual back-up for your doorbell

By T. R. de Vaux-Balbirnie

THIS PROJECT was designed to give a visual indication when a caller operated the doorbell. It was originally intended to enable someone working in the garden to be aware of a caller and this was achieved by operating a bright bulb in a prominent position.

The author quickly realised that the same system could benefit deaf people or could be used in any situation where either, distance or extraneous noise prevented the bell or chimes from being heard.

FEATURES

The Lightcall has the following features.

First, it is an add-on unit with its own power supply. Only two simple connections are made to the existing doorbell circuit, the operation of which is quite unaffected. Secondly, the circuit is designed to switch on one or more *mains* voltage bulbs. Small bulbs operated by a battery are not really bright enough to attract attention. Thirdly, there is a variable time delay element which switches the bulb, or bulbs on for a preset interval. This is quite independent of the length of time the bell push is operated.

TIME DELAY

The prototype gives delays as short as two or three seconds and as long as one minute. If a longer time interval is required this is easily obtained by increasing the value of C1. A push button switch on the unit, or indeed elsewhere may be used to cancel the light at

any time. Finally, it does not matter what type of bell or chimes are used. They may be battery or mains operated.

If desired, the Lightcall may be built complete but without the mains wiring. An electrician may be called in to do this work and the wires simply connected to the terminal block on the unit. This might be the best plan where several lamps are to be run in different locations or where weatherproof housings are required for outside use.

CIRCUIT DESCRIPTION

The full circuit of the unit appears in Fig. 1. When the bell push at the door is pressed, current flows momentarily through a current-limiting resistor, R1, and diode D1. It then flows to the electrolytic capacitor C1. This charges rapidly and cannot discharge


through the bell because of the action of D1. Current may "bleed" from this charged capacitor by two paths.

First, it may pass through the high value preset variable resistor VR2 to the pair of transistors TR1 and TR2. These transistors are therefore held on as long as C1 can supply the necessary current.

DARLINGTON PAIR

Two transistors connected together directly in this way are called a Darlington pair. They behave as one transistor with very high current gain so that a very small base current in the first transistor will turn or hold the second one on. If only one transistor were used, C1 would not be able to keep up the necessary current for long. As it is, C1 can supply the current for one minute or so. When the transistors are on

Fig. 1. Circuit diagram of the Sight and Sound Doorbell.

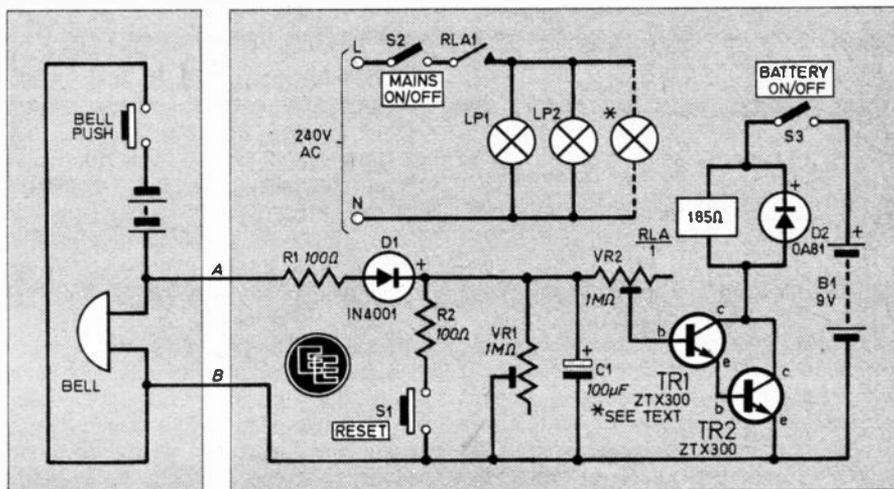

valuable aid for the hard-of hearing

COMPONENTS
approximate
cost £2.50 (excluding bulbs)

necessary for the prototype. It is not a good idea to use the copper strips for mains connections and all relay connections are made direct. To avoid possible trouble, the copper strips should be broken in the vicinity of the relay connections.

COMPONENTS

The relay deserves special mention. This must operate reliably from a 9 volt supply. Many relays sold as 6/12 volt types are suitable but if in doubt the manufacturer's specification should be checked. It is essential that the relay should have at least one set of normally open contacts. The current handling capacity should be at least one amp at mains voltage for up to 240 watts of load—say 4 off—60 watt bulbs. If a greater load is anticipated then contacts with a greater current capacity will be needed, 3 amps for up to 720 watts, etc. There is no harm, of course, in the relay having contacts with a current rating greater than that required. The important point is that the contacts must be suitable for *mains* use.

The resistance of the coil of the relay used in the prototype was 185 ohms but this is not thought to be particularly critical. The purpose of diode D2 is to prevent back e.m.f. as the magnetic field collapses in the relay. Without it there is a possibility of damage to the transistors. The author left D2 out originally without damage but it is certainly advisable to include it. Note the way in which D2 is connected—not in the direction of battery current but *against* it.

EXTERNAL CONNECTIONS

External connections are made to two miniature terminal blocks Fig. 2. It was thought best to use a separate 2-way block for the mains connections and a 3-way for the other connections. This was to avoid as far as possible any mains connections being made wrongly. This could prove disastrous.

Although a small self contained battery could give reasonable service, it was decided to use a larger 9V battery outside the case. During periods of non-use the battery drain is exceptionally low, but of course there is a drain each time the relay operates in the course of service. For periods of absence, a toggle switch, S3, is provided in

the battery positive line. When switched off the device is totally inoperative. A mains switch S2 should also be provided to give isolation from the mains when required to do so. This will not normally be used but it would be bad practice to omit it.

It would also be possible to use one double-pole mains switch to fulfil both functions but possible confusion over connections makes this an unattractive idea. Two separate switches are definitely advised. The two switches just mentioned together with the cancelling switch, S1, will be mounted on the front panel of the unit. As mentioned previously, S1, could be placed elsewhere or even several switches in parallel could be used. This would mean that the unit could be cancelled from various locations. A small plastic box was used to house the circuit in the prototype.

When connecting C1 it is essential to observe polarity. In other words, its positive and negative connections must be made the correct way round. This is because C1 is an electrolytic capacitor and damage results if these are incorrectly connected. The polarity is indicated on the body of the capacitor. Any voltage rating over about 12 volts will be satisfactory.

TESTING

After construction, the unit should be tested in the following way.

For a start, no mains connections should be made, only the battery leads. Presets, VR1 and VR2 should be initially set to about mid position. The battery positive terminal should then be connected temporarily to connection A on the terminal block. A distinct click should be heard from the relay. Some time will elapse before it clicks back again. Some variation of VR2 may be needed for proper operation, whilst VR1 will alter the time interval.

the relay, RLA is energised and a pair of normally open contacts switch on the mains bulbs. There is a second discharge path for C1. This is through the variable resistor VR1. This gives the variable time setting.

The cancelling switch, S1 is of the push to make type and allows for rapid discharge of C1 through the current limiting resistor R2.


If it is anticipated that longer timing periods will be required then a higher value for C1 should be used from the outset. A value of 470 or even 1000 microfarads will greatly increase the maximum times available. Short periods will become very tricky, however.

CONSTRUCTION
starts here

CIRCUIT BOARD

Construction is very straightforward and is based on 0.1 inch matrix stripboard. A suggested layout is given in Fig. 2 but it is not critical. The copper strips must be cut in the places indicated on the diagram and care must be taken to avoid bridging between the strips during the soldering stage.

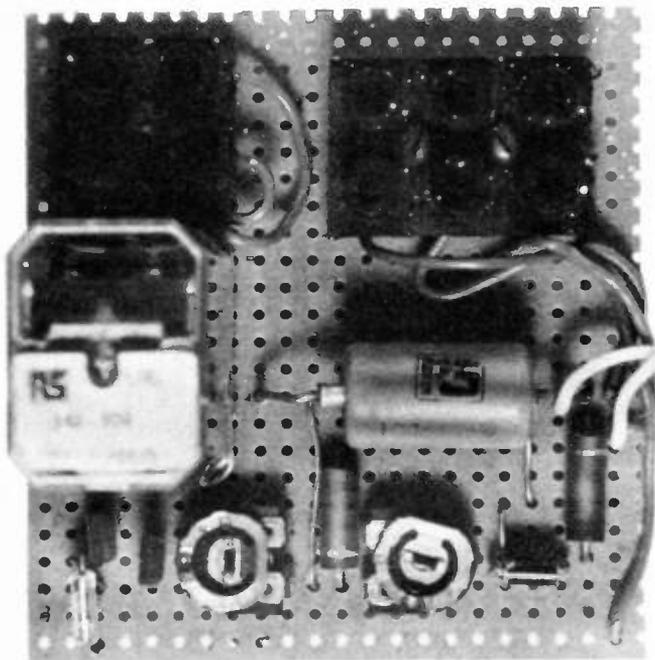In the prototype a square hole was cut in the stripboard to allow all the terminals of the relay to pass through. This will depend to a large extent on the relay used. A relay socket may be used if desired but this was not considered



The complete circuit board for the Lightcall showing the layout of components and mounting of the terminal strips.

COMPONENTS

Resistors

R1, 2 100Ω (2 off)
Both 1/4W carbon ± 5%

Potentiometers

VR1, 2 1MΩ miniature horizontal
preset (2 off)

Capacitor

C1 100μF 12V elect.

Semiconductors

TR1, 2 ZTX300 silicon *npn* (2 off)
D1 1N4001 silicon
D2 OA81 germanium

Miscellaneous

S1 push to make press switch
S2, 3 standard single pole toggle
RLA 9V relay, 185Ω coil with one
make contact
LP1, 2 240V 60W bulbs as required
B1 PP6 9V battery
Stripboard: 0.1 inch matrix 23 strips
× 22 holes; small plastic terminal
blocks, 1 off 3 way, 1 off 2 way;
battery connector for B1; small
plastic case, size as required; con-
necting wire.

See
**Shop
Talk**
page 798


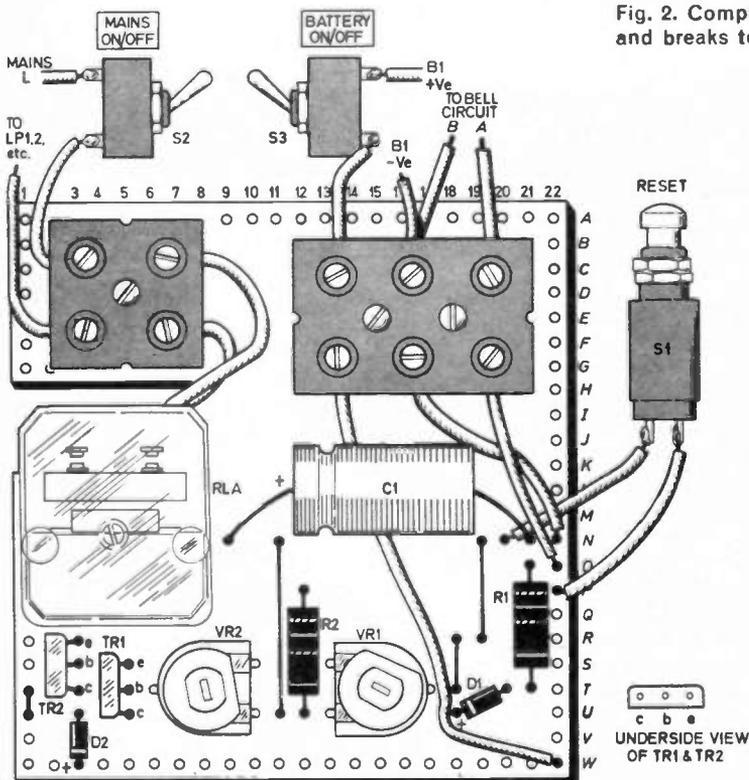


Fig. 2. Complete wiring details for the unit, also showing the stripboard and breaks to be made.

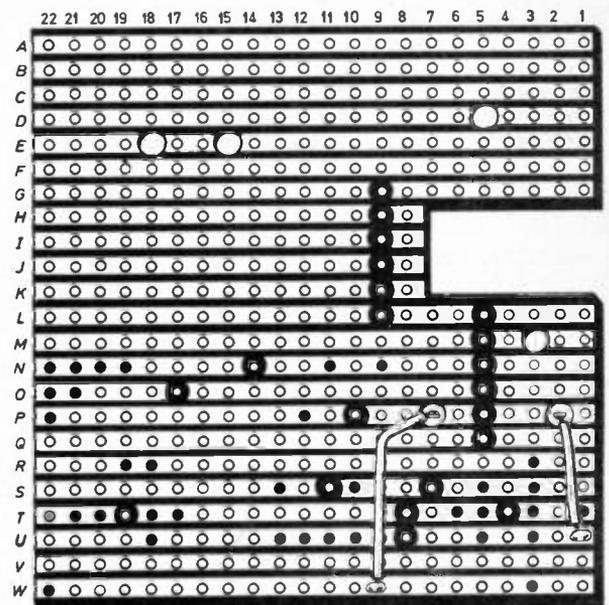

It will be noted that the setting of VR2 has some effect on the time interval as well as VR1 as this controls the current flowing to the transistors. It is important, whilst experimenting with the settings of VR1 and VR2, not to set VR2 to too low a value i.e. on anti-clockwise rotation of VR2 a small margin must always be left before the end of the track. If this is not done, damage may occur to the transistors due to excessive base current flowing.

IN USE

Assuming all is well, the leads A and B are connected to the doorbell. If the doorbell is battery operated it is necessary to connect lead A to the positive terminal. It is not harmful to do the opposite but the project will not work as current will not then flow through D1. If uncertain about the polarity,

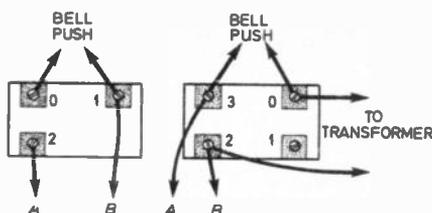


Fig. 3. Typical connections to two of the most popular types of bell systems. These connections are for guidance only and will not necessarily be correct in all cases.

then the best plan is to connect A and B by trial and error. If the doorbell is transformer operated it does not matter which way round A and B are connected as the diode D1 will conduct on the positive half cycles of the alternating current.

There are many types of doorbells and chimes in use today so specific details of the connections cannot be given. It is largely a matter of common sense finding

the connections which are directly across the bell. In an effort to help some readers, connections for two popular units are illustrated in Fig. 3.

If the circuit functions correctly it is suggested that a simple battery and bulb circuit should be used to check the action of the relay contacts. If this works correctly, the mains part may then be completed. It is important to remember that the mains circuit should be protected with a fuse according to the current requirements of the bulbs. This far is not shown in the circuit diagram, but should be wired in the live lead of the mains. Alternatively connection to the mains could be made via a fused plug.

This little device lets you know visually when a caller is there. You may heed it or ignore it as you please.

✧



New ideas

IN SPITE of my gentle leg pulling, I am all for new ideas, and I think it is only right and proper, that us chaps who sell the electronic hardware for, what is after all, the most advanced science, in the world, should be. I certainly have never shirked my duty in this respect or even put personal safety first.

I must have bought the first pressure cooker ever offered for sale. I bought it, and let my wife try it, while I stood outside the house with my fingers in my ears. Well after all you cannot be too careful!

I rushed out and bought one of the first quick heat soldering irons. "Heats Up In Ten Seconds" said the makers and so it did. Unfortunately, I was building a Quality Amplifier at the time and only when I was half way through, did the truth dawn on me, that if you have to wait ten seconds before you can make each joint, a conventional iron is ten times faster!

I think I must have had the first turntable for playing long playing records and one of the first stereo "out-fits".

Even so I have occasionally had my doubts, a case in point being digital presentation instead of analogue, par-

ticularly for watches and test gear, and in this respect it looks as though time is proving me right. It seems that even the power station engineers get dizzy seeing numbers flash before their eyes instead of a large black pointer making a leisurely sweep, to the right or left and in America the conventional watch face is making a come back.

It is strange how the human eye or the mind, prefers the analogue view. The reason for it, may be just this, we have been looking at analogue presentation for over 5000 years. I am thinking of course of sundials.

Another recent invention I am not happy about, is the Microwave cooker. For a start I am always suspicious of loud proclamations made by Government Departments or powerful manufacturers and if either of them tell me something is perfectly safe, I immediately assume it isn't!! There have been cases of radiation leakage with these cookers and the consequences can be very serious.

While we are being told they are perfectly safe, I now see special depots are being set up to check them, and someone is even offering for sale a pocket radiation leakage tester, so you can test your own! Nuff said!

Don't suffer in silence

I am sure half our troubles today are caused by lack of communication. This aspect is particularly applicable to the home constructor who so often relies on mail order for the supply of his bits and pieces.

Every firm makes mistakes, but I know of none, who would not go to great lengths to put them right, once they know, and this is the operative phrase. I am bound to admit that the post today leaves a lot to be desired and this does not help the situation, but as my dear old medico used to tell me, "Don't suffer in silence".

In other words if something has gone wrong write or telephone your supplier, tell him concisely what your complaint is and he will put it right as quick as he can. Most of you I know are very good in this respect, although, a very small minority regard the postal service as perfect and accuse us of making it a scapegoat for any delays.

Try and remember (I am sure you do) that most of us are short staffed and time is precious, so short letters are our favourites. Above all do not put technical queries in with orders or complaints, and if it is about a project, do not send it to us at all, but to the appropriate source.

Sometimes, but fortunately only about once or twice a year, I get a customer who seems to have all the time in the world on his hands, as a result, if he gets one incorrect item in his parcel he sends me a four page letter. I had one recently, and I wrote a letter simply asking him how much we owed him on the postage for returning the wrong part and what did he want us to send him.

Back comes another four page letter telling me how superior all my competitors are and how wicked I was for trying to blame the PO for the delays. This time in desperation I wrote and told him that during the War, Churchill made an agreement with Russia on half a sheet of notepaper, would he please be a good fellow and follow his example!

MODULATED TONE GENERATOR

by R.A. PENFOLD

THIS UNIT provides a very effective audible alarm signal which consists of an audio tone of rapidly changing pitch. The output power of the unit depends upon the supply voltage and speaker impedance selected, and varies from about 112mW with a 6 volt supply and 80 ohm speaker to approximately 4.5W with a 12 volt supply and 8 ohm impedance speaker.

The alarm is therefore suitable for use in fairly high power applications such as burglar alarm systems, as well as in lower power circuits such as timers.

In order to aid the selection of a suitable supply voltage and speaker impedance, Table 1 is provided. Apart from giving the nominal r.m.s. output powers for various speaker impedance and supply voltage combinations, it also gives the approximate mean current consumption.

The circuit has a gating input which can, if required, be used to electronically control the alarm, rather than simply switching it on and off by means of the power source. This enables the unit to be

easily controlled by many circuits without the need for a relay or other form of driver circuit.

It should be possible to use it as an add-on alarm, perhaps for a circuit which already has an alarm, but one which proves to be ineffective for some reason.

THE CIRCUIT

The complete circuit diagram of the Modulated Tone Generator appears in Fig. 1. This is based on two oscillators: one to generate an audio tone, and the other to frequency modulate the tone generator. This gives a much more noticeable sound than that given by a single tone.

Both oscillators are based on the same integrated circuit, which is a CMOS Quad 2-input NOR gate (IC1). Two gates are used in each oscillator. Although this device is not specifically designed for use in oscillator circuits, it lends itself well to such applications and is often used in this mode.

The output of a NOR gate assumes the high logic state (vir-

tually equal to the positive supply rail voltage) unless one of the inputs is taken to the high state. The output then goes to the low logic state (virtually equal to the negative supply potential).

In this case, one input of each gate is taken to the control input, and if this input is high, the output of each gate must be low and the other four inputs will have no effect on the circuit. With the outputs low, TR1 and TR2, which are connected as a Darlington pair, will be cut off and no significant current will be supplied to the speaker. The circuit will be blocked and only small leakage currents of about 1 μ A in total will be drawn from the supply lines.

With the control input at the low state, the output state of each gate will depend upon the logic state of its second input. If this input is low, the output will go high, and if it is high, the output will go low. In other words, there is a simple inverter action between the input and output.


INVERTERS AS OSCILLATORS

Now CMOS inverters are easily made to function as oscillators by adding two stages in series, biasing the first stage with a resistor connected between its input and output, and using a capacitor to provide a positive feedback path between the output of the second stage and the input of the first stage. This configuration is used for both oscillators in this circuit.

Inverters G1c and G1d are used in the tone generator oscillator, and the specified values for R3 and C3 give a nominal operating frequency of about 800Hz. A square-wave is produced at inverter G1d output, and on positive excursions TR1 and TR2 are switched hard on

Table 1. Table showing r.m.s. output power and mean current consumption for various speaker impedances and supply voltage options.

LOUDSPEAKER IMPEDANCE (Ω)	SUPPLY VOLTAGE (V)		
	6	9	12
8	1.125W 375mA	2.53W 562mA	4.5W 750mA
16	562mW 187mA	1.27W 281mA	2.25W 325mA
25	360mW 120mA	810mW 180mA	1.344W 240mA
40	250mW 75mA	506mW 112mA	1W 150mA
80	112mW 37.5mA	253mW 56mA	500mW 75mA

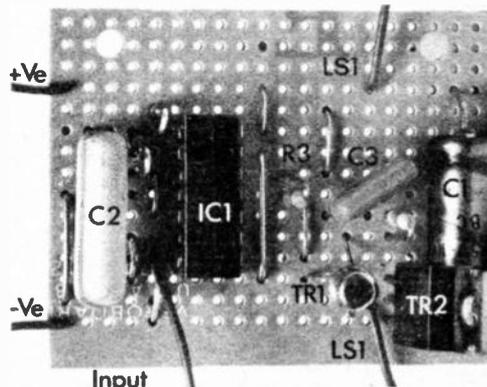

The completed prototype board.

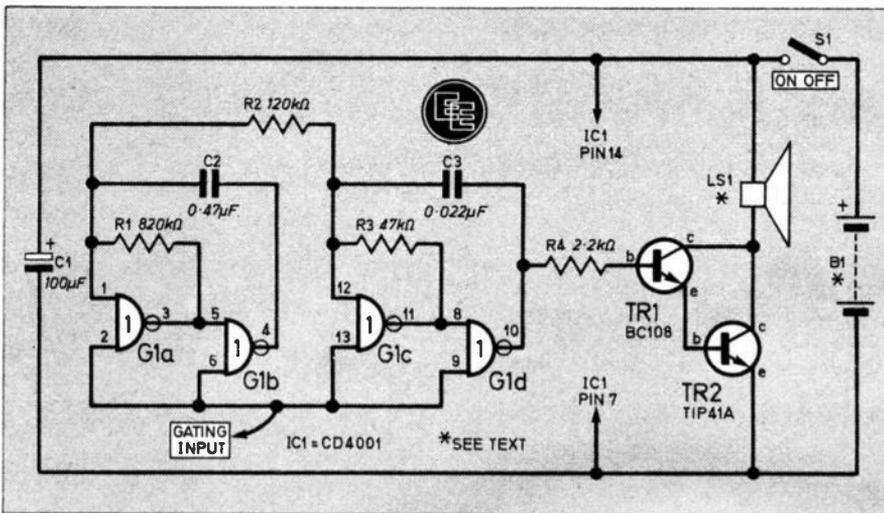


Fig. 1. The complete circuit diagram of the Modulated Tone Generator.

by the base current they receive via R4. This causes a series of pulses to be fed to the speaker and an audio tone to be generated.

The modulating oscillator uses inverters G1a and G1b. The bias resistor (R1) and feedback capacitor (C2) have much higher values than their equivalents in the tone generator circuit, and this gives a much lower operating frequency of only about 1 to 2Hz.

The waveform at pin 1 of G1a is a form of sawtooth signal, and it is this that is used to modulate the tone generator. The necessary coupling between the two oscillators is provided by R2.

As the modulating signal's voltage rises and falls, the current flowing through R2 alters the timing of the tone generator circuitry, and sweeps the output tone up and down in frequency.

Capacitor C1 is merely a supply decoupling capacitor.

If the gating facility is not required, the gating input is permanently wired to the negative supply rail so that the unit always operates when the power is switched on.



The unit is assembled on a piece of 0.01inch matrix stripboard, 15 strips by 20 holes. The component layout is shown in Fig. 2. There are eight breaks in the copper strips, as detailed in the diagram, and it is advisable to make these before soldering in the various

components. If the appropriate tool is not available, they can be made using a hand held twist drill of about 4mm in diameter, or using a sharp modelling knife.

The components and link wires are then soldered into position, the integrated circuit being left until last. This is a CMOS device which can be damaged by high static voltages. It should be supplied in some form of protective packaging, and should be left in this until it is to be soldered into position. It should then be handled as little as possible and soldered in place using a soldering iron having an earthed bit.

An i.c. socket could be used for this component, of course, but the CD 4001 is such an inexpensive device that this is probably not worthwhile.

COMPONENTS

Resistors

- R1 820kΩ
- R2 120kΩ
- R3 47kΩ
- R4 47kΩ
- R5 2.2kΩ
- All ¼ Watt carbon ±5%.

Capacitors

- C1 100μF 12V elect.
- C2 0.47μF polyester (C280)
- C3 0.022μF polyester (C280)

Semiconductors

- IC1 CD4001BE Quad 2-input NOR gate
- TR1 BC108 silicon *nnp*
- TR2 TIP41A silicon *nnp*

Miscellaneous

- LS1 8Ω to 80Ω loudspeaker (see text)
- B1 6V to 12V (see text)
- Stripboard: 0.1 inch matrix 15 strips × 20 holes; connecting wire.


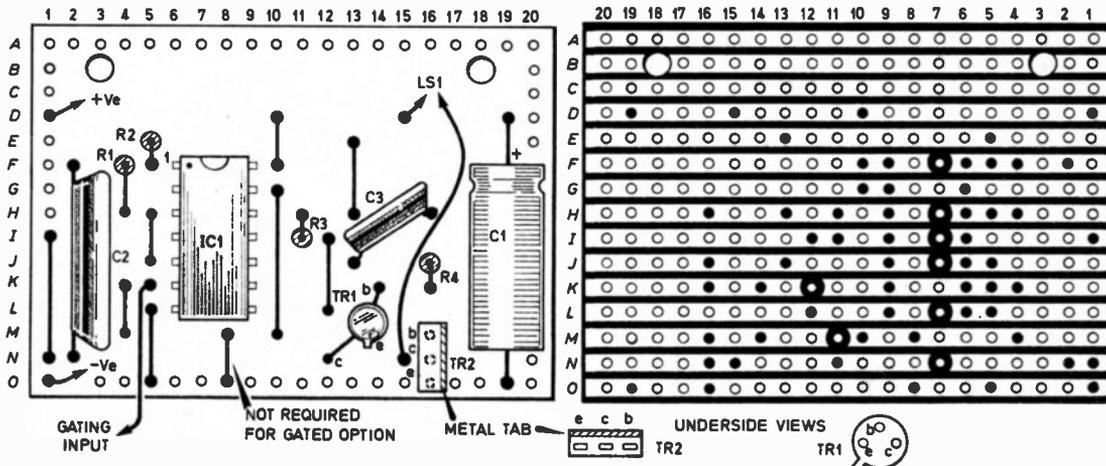


Fig. 2. The layout of the components on the topside of the stripboard and the breaks to be made on the underside.

COMPONENTS

approximate cost £2

HOW IT WORKS

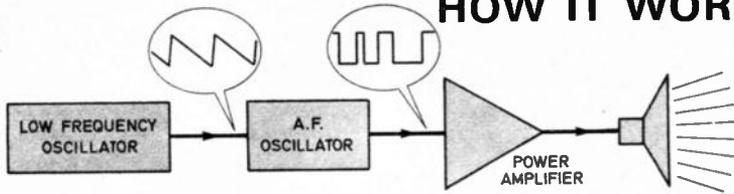

The circuit utilizes two oscillators; one to produce an audio tone, and the other to automatically vary the pitch of this tone. The modulating oscillator operates at a frequency of about 1 to 2Hz, and its output therefore causes the pitch of the tone oscillator to rise and fall about once or twice per second. This rapidly varying of the output note produces a very noticeable and effective alarm signal.

Only a low power signal is generated by the oscillators, and this is considerably amplified to produce a very loud tone via a loudspeaker.

less than one third of the supply voltage, and the high state means more than $\frac{2}{3}$ of the supply potential.

This unit is compatible with the popular NE555V timer i.c. and many other devices and circuits.

If the alarm is supplying an output power of more than about 2 watts it is advisable to fit TR2 with a small finned heatsink, as it might otherwise overheat and be destroyed.

The frequencies of the modulator and tone oscillators can, if desired, be altered by changing the values of C2 and C3 respectively. Decreasing the value proportionately increases the frequency of operation, and vice versa.

No case fixing details are supplied as it is likely that this device will be added to existing units. ☐

USING THE UNIT

It is important to ensure that the loudspeaker employed with the alarm has a suitable power rating, although slightly exceeding this rating is unlikely to have any detrimental effects in this particular application. If the highest possible volume is required it is advisable to use a fairly large speaker since

these generally have higher efficiencies than smaller types.

If the alarm is being controlled by the gating input, it must be borne in mind that the alarm is switched on when this input is low, and turned off when it is high. If the opposite of this is required, it will be necessary to add an inverter stage at the input. Incidentally, in this case the low logic state means

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

R.C.S. LOUSPEAKER BARGAINS

3ohm, 6 x 4in. £1.50, 7 x 4in. £1.50, 6 x 5in. £2.50, 6 1/2in. £1.80, 8in. £2.80, 10in. £3.12in. £4.
6 ohm, 2 1/2in. £1.50, 3in. £1.50, 5in. £1.50, 10in. £3.12in. £4.
16 ohm, 6 x 4in. £1.50, 7 x 4in. £1.50, 8in. £1.50, 8in. £2.80, 10in. £3.12in. £4. 10 x 6in. £3.50.

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 19p.
500mF 12V 17p; 25V 29p; 50V 39p;
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 79p.
5000mF 6V 25p; 25V 43p; 400mF/500V £1.30.
2500mF 50V £2; 3000mF 25V 47p; 50V 85p.
300mF 100V £1.40, 4700mF 63V £1.20, 2700mF/76V £1.
5000mF 6V 25p; 12V 43p; 35V 85p, 5000mF/76V £1.75.

HIGH VOLTAGE ELECTROLYTICS

8/350V 22p 8+8/450V 59p 50+ 50/300V 99p
16/350V 39p 8+16/450V 59p 32+32/450V 75p
32/500V 75p 16+16/450V 99p 100+100/275V 85p
50/500V £1.20 32+32/350V 99p 150+200/275V 79p

MANY OTHER ELECTROLYTICS IN STOCK

SHORT WAVE 100pf air spaced gangable tuner, 95p.
TRIMMERS 100pf, 30pf, 50pf, 100pf, 150pf, 15p.
CERAMIC, 1pf to 0.01mf, 5p, Silver Mica 2 to 5000pf, 5p.
PAPER 350V-0.1 7p; 0.5 13p; 1mf 150V 29p; 2mf 150V 29p; 500V-0.001 to 0.05 12p; 0.1 15p; 0.25 25p; 0.47 35p.
MICRO SWITCH SINGLE POLE CHANGEOVER 29p.
SUB-MIN MICRO SWITCH, 25p. Single pole change over.
TWIN GANGS, 100 to 10M, 1W, 1W, 20% 2p; 2W, 19p.
HIGH STABILITY, 1W 2% 10 ohms to 1 meg., 12p.
Ditto 5%, Preferred values 10 ohms to 10 meg., 5p.
RELAYS, 12V DC 95p, 6V DC 85p, 240V AC 95p.
BLANK ALUMINIUM CHASSIS, 6 x 4-95p; 8 x 6-£1.40; 10 x 7-£1.50; 12 x 9-£1.70; 14 x 9-£1.90; 16 x 6-£1.85; 18 x 10-£2.20, ANGLE ALL 8 x 3 1/2in-99p.
ALUMINIUM PANELS, 6 x 4-24p; 8 x 6-39p; 14 x 3-49p; 10 x 7-64p; 12 x 8-79p; 12 x 5-44p; 16 x 9-79p; 14 x 9-94p; 12 x 12-£1; 16 x 10-£1.16.
PLASTIC AND ALI BOXES IN STOCK. MANY SIZES
VARICAP FM TUNER HEAD with circuit & connections.
Some technical knowledge required £4.95.
TAG STRIP 28-way 12p.
TAPE OSCILLATOR COIL, Valve type, 35p.
BRIDGE RECTIFIER 200V PIV 1/2 amp 59p, 5 amp £2.90.
TOGGLE SWITCHES SP 39p, DPST 49p, DPDT 59p.
MANY OTHER TOGGLE IN STOCK. Please enquire.
PICK-UP CARTRIDGES ACOS, GP91 £2.99, GP94 £2.99.
SONOTONE STAHM Diamond £2.78, Magnetic £2.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 19p.
CASSETTE MOTOR, 6 volt £1.90.

BAKER 50 WATT AMPLIFIER £65 Post £1



Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue working on black cabinet.

BAKER 150 Watt AMPLIFIER 4 inputs £85. DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Post 35p £3.25

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. Post 35p £2.95

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200mV to 100 watts signal source. Suitable for home Hi-Fi and all Disco Amplifiers. £18
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4. Or 12 for £7.50.

MAINS TRANSFORMERS Post 75p

250-0-250V 70mA, 6-5V, 2A	£3.45
250-0-250V 80mA, 6-3V 3-5A, 6-3V 1A	£4.90
300-0-300V 100mA, 6-3V 3A	£5.90
300-0-300V 120mA, 2 x 6-3V 2A C.T., 5V 2A	£10.90
220V 45mA, 6-3V 2A	£2.75
HEATER TRANSFORMER, 6-3V 1amp £1.90, 3 amp £2.20	£2.20
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs	
2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£4.00
1 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60	£4.00
2 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60	£5.90
3 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60	£12.90
5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60	£16.00
12V, 100mA	£1.30
12V, 750mA	£1.90
10-0-10V 2amp	£3.00
30V, 5 amp and	
17V-0-17V, 2 amp	£4.00
0.5, 8, 10, 16V, 1/2 amp	£2.90
9V, 3 amp	£3.90
25-0-25V 2 amp	£4.90
30V, 2 amp	£3.90
30V, 1 1/2 amp	£3.20
20V, 40V, 60V, 1 amp	£4.00
10V, 3 amp	£3.90
10V, 30V, 40V, 2 amp	£3.90
40V, 2 amp	£3.90
20V, 1 amp	£2.00
20V-0-20V, 1 amp	£3.90
30V-0-30V, 2 amp	£3.90
2 of 16V, 6 amp, each	£11.00
12-0-12V, 2 amp	£3.90
9V, 1/2 amp	£1.90
28 + 28V 1A	£11.00
32-0-32V 6-5A	£11.00

BAKER SPEAKERS "BIG SOUND" Post £1 ea.

Robustly constructed to stand up to long periods of electronic power. Useful response 30-16,000 cps. Bass resonance 55 cps.

GROUP 45-12 £15

12in. 45 watt 4, 8 or 16 ohms.

GROUP 75-12 £24


12in. 75W professional model, 4, 8 or 16 ohms

Response 30 - 16,000 cps. With aluminium presence dome.

GROUP 100-15 £35

15in. 100 watt 8 or 16 ohms

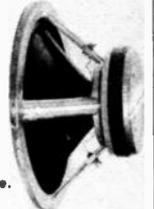Send for leaflets on Disco, P.A. and Group Gear.



E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. 10W, 3 or 8 ohm. £8.95 Post 75p

15W model £10.95 Post 75p

8 ohms Bass unit only. £8.95 Post 75p

GOODMANS 20 Watt Woofer

Size 12 x 10in. 4 ohms. Rubber cone surround. £8.95 Post £1.00


Hi-Fi Bass unit. £8.95 Post 75p

GOODMANS TWIN AXIOM 8

8in. 8 ohm Hi-Fi Twin Cone Special unit £8.95 Post 50p



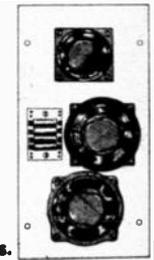R.C.S. MINI MODULE HI-FI KIT 15 x 8 1/2in 3-way Loudspeaker System, EMI 5in, Bass 5in, Middle 3in. Tweeter with 3-way Crossover and Ready Cut Baffle. Full assembly instructions supplied. Response = 60 to 20,000 cps 12 watt RMS. 8 ohm. £10.95 per kit. Postage £1. One or two kits.



RADIO COMPONENT SPECIALISTS

Minimum post 39p.

Components List 39p.

Access & Barclaycard by Phone

337 WHITEHORSE ROAD, CROYDON

Open 9-6 Sat. 9-5 (Closed all day Wednesday)

Tel. 01-884 1005



By L. ARMSTRONG • H. DICKINSON • W. WILKINSON

EE RADIO CONTROL SYSTEM

TRANSMITTER CONSTRUCTION & FIELD STRENGTH METER

PART TWO

AS EXPLAINED in Part 1, the first major concern before starting construction is to decide how many channels you are going to have; remember you can have any number up to seven. Having decided, there is one more option to decide upon: that is the plug-in channel facility which requires the 3-pin plugs and sockets.

HARDWARE

As was mentioned in the Introduction last month the whole of this R.C. system has been based where possible on commercially available parts, this is especially so in the case of the transmitter where the sticks, case and plugs and sockets and other sundry items are manufactured by S.L.M. (Model) Engineers Ltd. of Cheltenham. It is strongly recommended that these identical parts (especially the case) are used in order to have a neat and tidy system as an end-product.

We will describe the construction from the point of view of using these parts. However, should you decide to

make your own case, purchase the sticks, meter, switch, etc., before drilling and bending so that their position can be chosen to enable the p.c.b. to be mounted on the back of the sticks.

The S.L.M. case as specified comes ready bent with plastic sides and holes punched for a pair of open gimble sticks, so if you require more than four channels then extra holes and slots will have to be cut where required. However, the case does have holes cut for the aerial socket, meter, Noble switch and charger socket.

PRINTED CIRCUIT BOARD

Most of the transmitter circuit is built on a printed circuit board. A full-size pattern of the p.c.b. is given in Fig. 2.1 and the top view of the board showing the disposition of the components appears in Fig. 2.2.

Assembly of parts on to the p.c.b. should commence with the stick socket(s) SK1.

In the case of the full system this means the 7-way block, and for less

than seven channels the single 3-pin sockets are used. Channel 1 is at the top and Channel 7 at the bottom of the board, so if only three channels are going to be used then the sockets should be inserted into the top three positions.

If you are not having the channel reverse option, that is no sockets, then leave the necessary spaces for the wires to be soldered directly to the board at a later date (Fig. 2.2). Unused channels will have wired in their place fixed resistors Ra and Rb as in Fig. 2.3a. These are positioned on the p.c.b. as in Fig. 2.3b in place of the sockets or wires.

Resistors R4 to R10 can now be inserted between the block and IC1. When inserting these resistors stand them up in the hole nearest IC1 then pass the other lead through either of the holes in the island next to the block then loop under and solder to the centre pin of the block and to the island itself (Fig. 2.4).

Where the Ra and Rb resistors are used then the lead is cut off at the island as per Fig. 2.3b.

CRYSTAL SOCKET

The crystal socket SK3 can be inserted next by locating its two plastic lugs in the p.c.b. holes and melting them into place on the copper side using the side of your soldering iron bit. Small lengths of tinned copper wire are used to connect from the crystal socket pins to the p.c.b.

Insert the two links and the aerial loop using the same type of wire. Something in the region of 20 s.w.g. wire is best for these connections and links; however, if you do not already possess something suitable then use the chopped-off resistor leads.

CARE WITH ICS

The remaining components can now be inserted in any order providing the CMOS i.c.s IC1 and IC2 are left until last, as these can be damaged by static electricity.

For those constructors not familiar with CMOS there are two precautions to take that virtually eliminate any possibility of damage. The first of these is to ensure that your soldering iron is earthed correctly and the second is to keep the i.c.s in their black conductive foam until you are ready to insert them into the board and then to do so as quickly as possible with the least amount of handling; try to avoid touching the leads.

POTENTIOMETER CONNECTIONS

Having now completed the insertion of the components the connecting wires to the pots can be attached for

ADDITIONAL COMPONENTS REQUIRED FOR LESS THAN 7 CHANNELS

Resistors

Ra, Rb 2.7k Ω (one pair for each unused channel)
 $\frac{1}{4}$ W $\pm 10\%$ carbon

Plugs and Sockets

3-pin plug and socket (one pair for each channel used—instead of 7-way block for full system)

Sticks

Single-axis sticks (for less than 4 channels—see Table 1.1)

CRYSTALS

X1, 2 pair of 27MHz band crystals with 455kHz spacing (one for transmitter and one for the receiver—see text)

NOTE — CIRCUIT DIAGRAM

Fig. 1.3

Transpose SK2 pin numbers 1 and 3 to agree with Fig. 2.6.

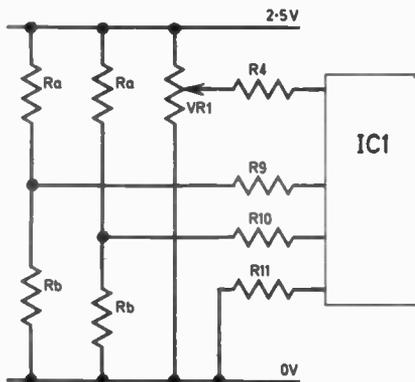


Fig. 2.3. (a) Part of channel switching circuit (see Fig. 1.3) showing additional resistors Ra and Rb fitted to unused channels.

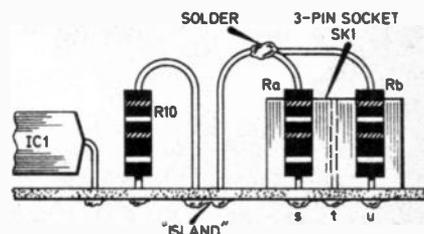


Fig. 2.3. (b) Edge-on view of p.c.b. showing how the additional resistors are mounted in place of the 7-way socket block. (Individual 3-pin sockets are installed for each channel used).

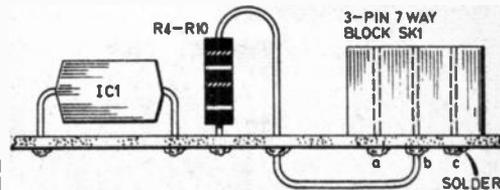


Fig. 2.4. Edge-on view of p.c.b. showing resistors R4 to R10 and their connection to the 7-way socket block.

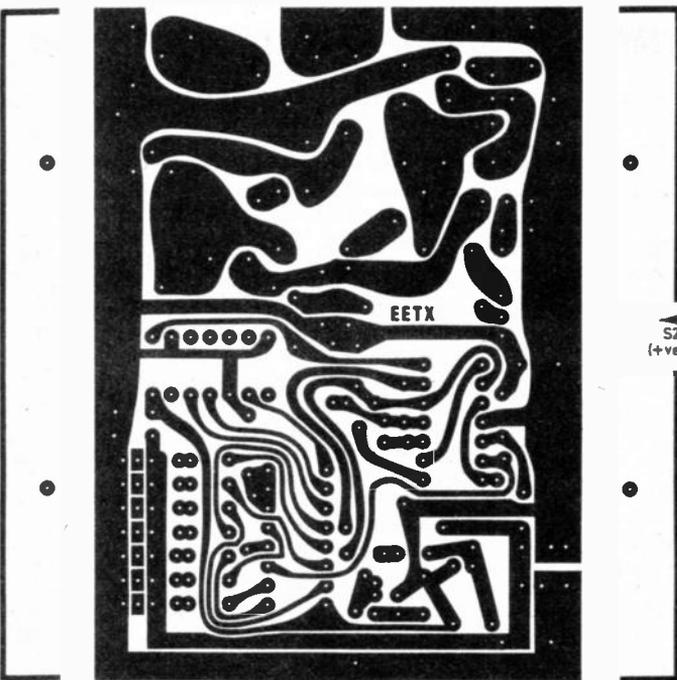


Fig. 2.1. Printed circuit board for the EE Radio Control Transmitter. This is actual size. Note the fixing holes on the outer "plain" or completely etched areas.

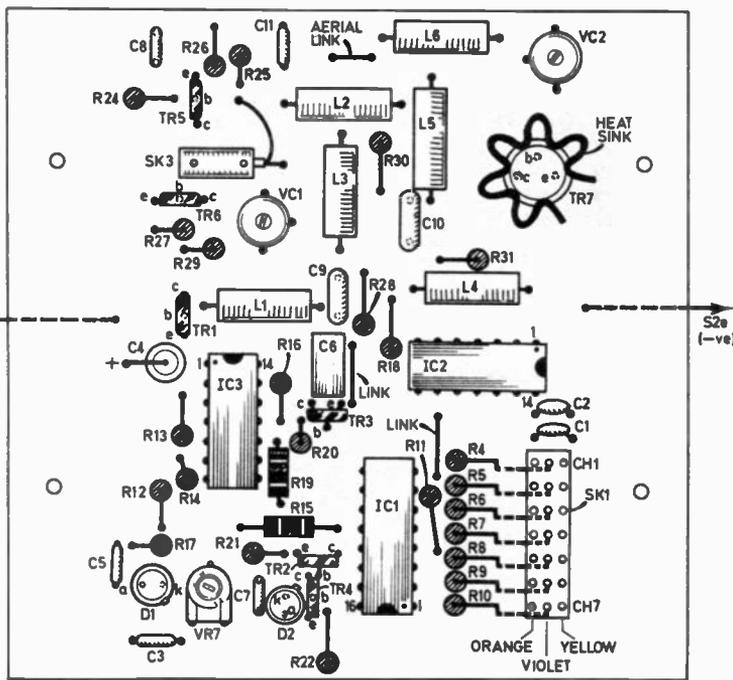


Fig. 2.2. Top view of the printed circuit board with all components in situ (full 7-channel version).


COST TO BUILD

Approximate cost for different-sized systems.

Two-channel version	£75
Four-channel version	£110
Seven-channel version	£170

The cost for each version includes all units specified in Part 1.

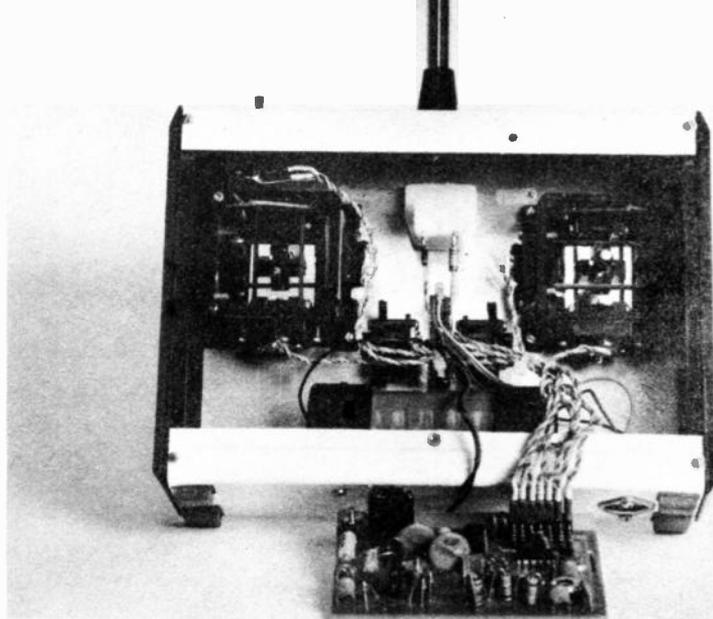The EE Radio Control System is fully capable of expansion from two channels to seven channels at anytime, simply by fitting additional sticks and servos.



those constructors not using the sockets. Fig. 2.2 shows the points to connect to. For tidiness sake the wires should be twisted together to form a trio; 6in lengths should be sufficient to attach to the board for now, final trimming to length can be performed at a later date when the board is inserted into the case.

If you are using the sockets, then these 6in lengths of wire should be attached to a 3-pin plug as shown in Fig. 2.5a. The sleeving over these connections should be of the heat-shrink type to grip the wire securely, but should not exceed $\frac{1}{4}$ in in length as it is possible to foul the back of the case when inserted into the socket on the board.

ASSEMBLY WITHIN CASE

Start assembly with the smallest parts (such as the switch and meter) first, as once the open-gimble sticks are in place there is not much room left for tightening nuts and screws.

Before the channel switch S1 is mounted it is best to solder on to this switch the resistors R1, R2 and R3 as in Fig. 2.5.

CASE DRILLING

As already explained the case which comes from S.L.M. requires the extra holes to be cut for the 5th, 6th and 7th channels. So before construction decide upon the positions of these functions. See Fig. 2.5.

Fig. 2.7 shows the positioning of the two auxiliary function sticks on the front panel as used in the prototype. The 7th channel was a switch on the top panel positioned such that it was in easy reach of the right index finger. This requires a $\frac{1}{4}$ in hole.

The only other drilling required is for the battery pack mounts which consist of two plastic end-caps for the button-type Nicad battery. These mounts require four 3mm dia. holes as in Fig. 2.5.

POTENTIOMETER ADJUSTMENT

Before the sticks can be inserted the pots need to be secured in the stick assemblies and for this you will require to have a multimeter to hand.

The pots are fitted in place with their fixing screws loose enough so the pot body can just be rotated; then, with the stick in the neutral position (don't forget the trim on the main sticks) the pot is rotated until the wiper of the pot is in the centre.

To do this set your multimeter to the resistance range and connect one lead to the pot wiper connection then take a reading of the resistance to each end of the pot and move the pot in the required direction until both readings are the same, then tighten the securing screws.

With the screws now tightened check the readings again to make sure that there was no movement during tightening. If there was then you will have to set up the pot again. **It is most important that the pot wiper is in the centre to ensure that all channels have the same neutral pulse width and to also ensure there is no offset when the plug is turned round for channel reversing.**

FIXING ARRANGEMENTS

All the parts except the meter are secured to the case with small screws. The meter requires to be glued in position, using either an epoxy or contact adhesive. When using the glue ensure that none comes into

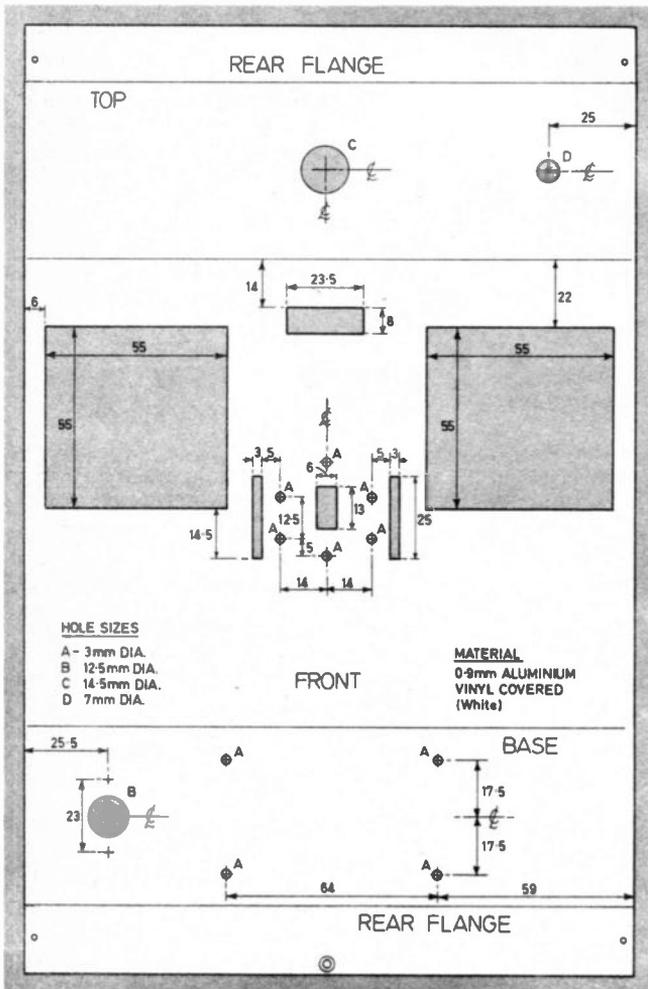


Fig. 2.5. Transmitter case panel opened out flat. Cut-out and drilling details to accommodate controls for seven channels.

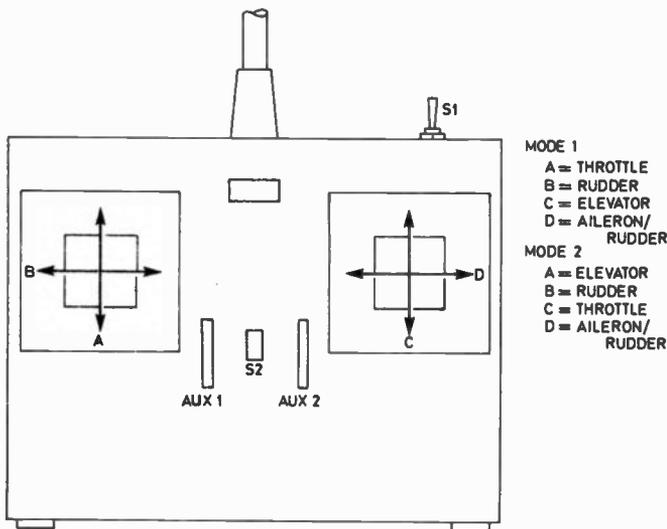


Fig. 2.7. Stick modes. Note: Throttle is usually a ratchet and all other functions are self-centering.

contact with the actual meter face as this will mar its appearance. All glueing should be done on its hidden face.

The aerial base should be bolted in place with a 6 B.A. nut and bolt of sufficient length such that it acts as the aerial locating screw as well. Position a solder tag on the bolt end, pointing out to the rear of the case so that it can be folded back down

on to the loop of wire on the top of the p.c.b. when the board is in place.

With all the items now secured into the case the wiring-up can now proceed. Start with the supply connections as shown in Fig. 2.7. The voltage offset components D3 and R23 provide the connection between the meter and switch and their leads should be kept as short and as close to the case front as possible to avoid

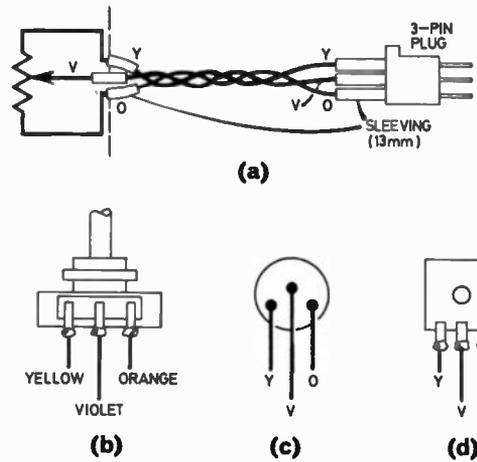


Fig. 2.8. Stick Potentiometers (a) connections to 3-pin plug (b) standard pot (c) cermet or plastic film pot (d) carbon film pot.

them coming into contact with the rear of the p.c.b.

Note that there is a central point for the ground leads on the switch S2, with the case earthed at the DIN socket SK2.

Now attach the wires to the stick pots. These wires were originally left at a length of 6in. These can be trimmed to suit each stick such that they do not flop around and yet are not so short that they are a struggle to fit into the socket. A good idea, which was used on the prototype, is to use Ty-rap clips to hold the cables in one bunch to aid tidiness.

If you are not using the plugs and sockets then you should already have the wires connected to the p.c.b. so this should aid you to adjust the length correctly.

CHANNEL FUNCTIONS

An ideal order for the channels is to have the most used functions first as follows: (1) Aileron/Rudder, (2) Elevator, (3) Rudder, (4) Throttle, (5) Aux. 1, (6) Aux. 2, (7) Switch. Fig. 2.7 shows where these functions will appear on the sticks.

There are two basic modes used in radio control and there are advantages and disadvantages to both, however, the guide here is to find out from local modellers which system they use and then set up your system accordingly as this makes things easier when you ask them to test your model for you.

POTENTIOMETER VARIETIES

The stick assemblies available today come with several types of pot. Fig. 2.8 shows these different types and how to connect to them. If your stick assembly uses a standard pot then Fig. 2.8b is the wiring configuration, Fig. 2.8c is for the cermet or plastic film pot. Fig. 2.8d is another type of film pot available.


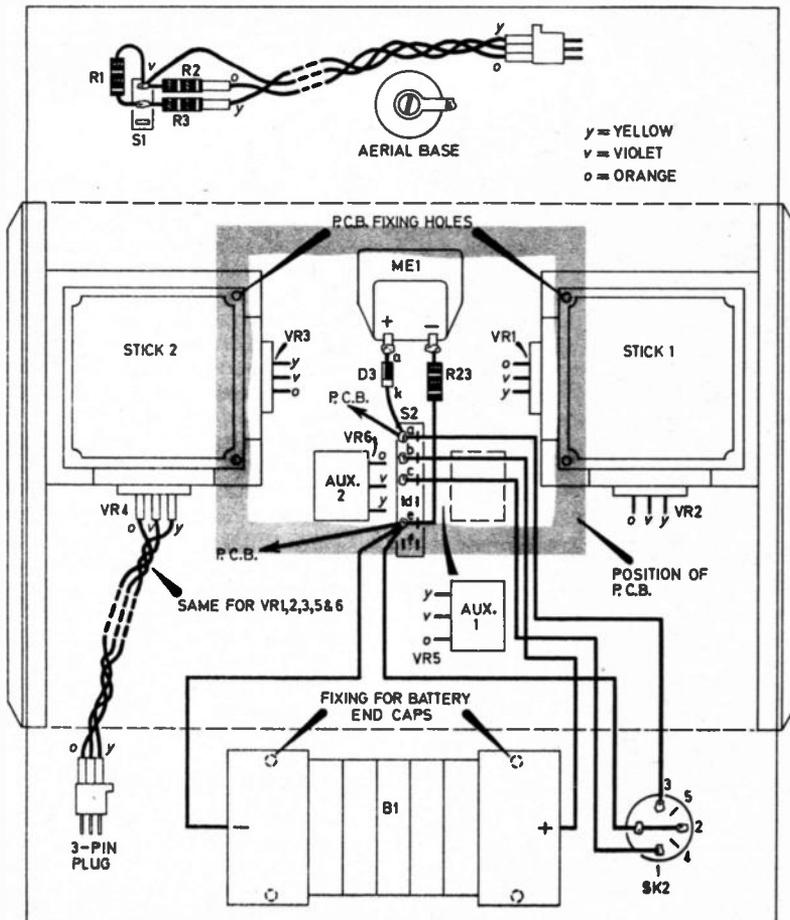


Fig. 2.6. Wiring within the case, to be completed before fitting the p.c.b.

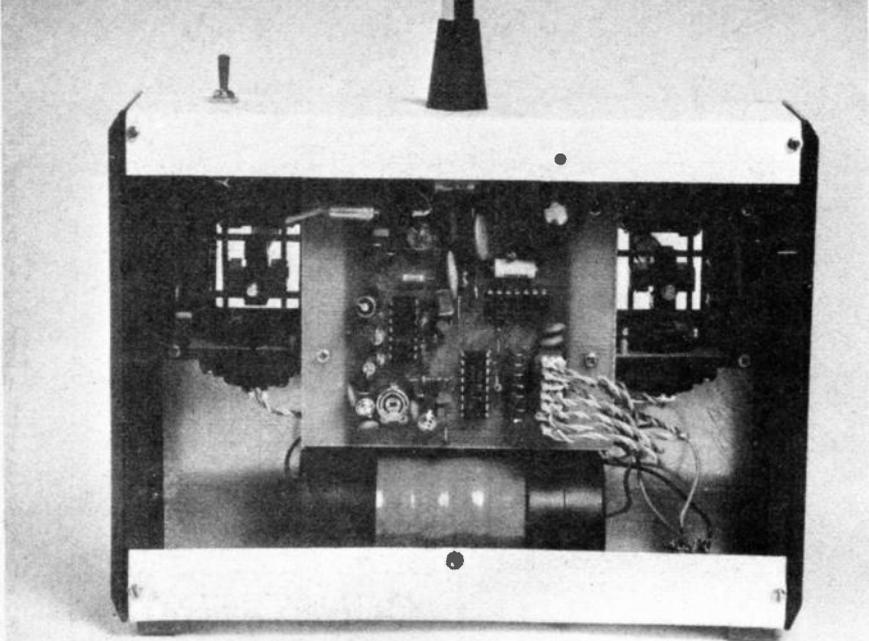

CRYSTALS

Two 27MHz band crystals are required, one for the transmitter and one for the receiver.

The pair of crystals should have a difference of 455kHz between the values stamped on them, and it is the higher frequency of the two that is used in the transmitter. For example: 27.045 transmitter and 26.590: receiver.

Within the R.C. band there are 13 spot frequencies, each indicated by coloured pennants as in Table 2.1. You should always display the appropriate pennant on your aerial when using your transmitter to enable other modellers to recognise which frequency you are operating on.

TABLE 2.1
THE R.C. BAND SPOT
FREQUENCIES

Transmitter Frequency (MHz)	Colour	Receiver Frequency (MHz)
26.970	Black	26.515
26.995	Brown	26.540
27.025	Brown/Red	26.570
27.045	Red	26.690
27.075	Red/Orange	26.620
27.095	Orange	26.640
27.125	Orange/Yellow	26.670
27.145	Yellow	26.690
27.175	Yellow/Green	26.720
27.195	Green	26.740
27.225	Green/Blue	26.770
27.245	Blue	26.790
27.275	White	26.820


FIXING THE P.C.B.

The p.c.b. should now be ready for mounting. First ensure the switch S2 is off (switch knob down) then solder the two supply leads to the underside of the board.

To mount the board the two screws on each stick assembly nearest to the centre of the case require to be removed, then the p.c.b. can be placed components side to the rear of the case and located over the sticks such

that the mounting holes coincide with the screw holes on the rear of the sticks. These screws can now be replaced and tightened so the p.c.b. is firmly mounted between the sticks.

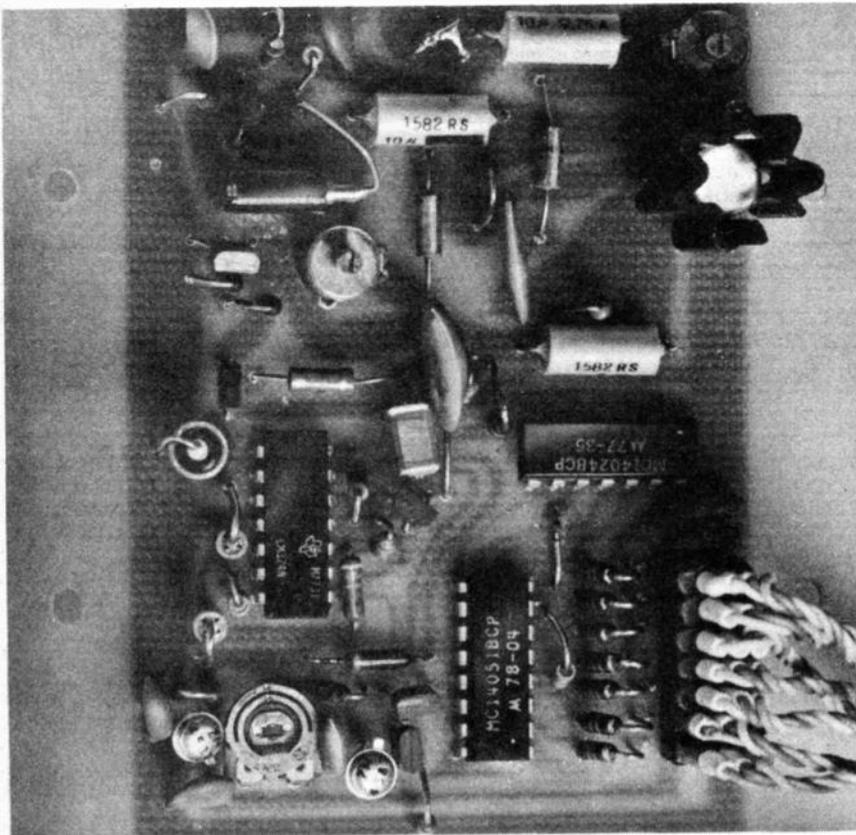The aerial is connected by folding the solder tag down on to the wire link at the top of the board and soldering well in place. The stick leads can now be plugged in the socket block on the board leaving only the crystal to be inserted to complete the transmitter.



TRANSMITTER SET-UP

The transmitter is tuned by adjusting the two variable capacitors VC1 and VC2. To help this operation we require to build the "tune-up" tuned circuit shown in Fig. 2.9. If an oscilloscope is available it could be used with advantage during the following setting-up operations.

The circuit in Fig. 2.9 is a simple tuned circuit which we will use to monitor the field strength of the transmitter output. (Full constructional details for this Field Strength Meter are given below.)

R.F. TUNING

With your multimeter set to d.c. volts (10V range) and connected to the output of the tuned circuit place the circuit with its aerial close to the fully extended transmitter aerial ready for switch on.

To adjust the variable capacitors you will require a small plastic blade trimming screwdriver, so with everything now to hand and having given the p.c.b. and wiring one last check through, switch the transmitter on and check that the battery voltage meter ME1 shows full scale.

FIELD STRENGTH METER

The Field Strength Meter circuit is built on a piece of 0.1in matrix stripboard. Two take-off points are provided for the meter. The coils L1 and L2 are wound round a 1in former, L1 first with L2 wound on top. VC1 will have to be adjusted for maximum reading on the meter during the transmitter tuning-up process.

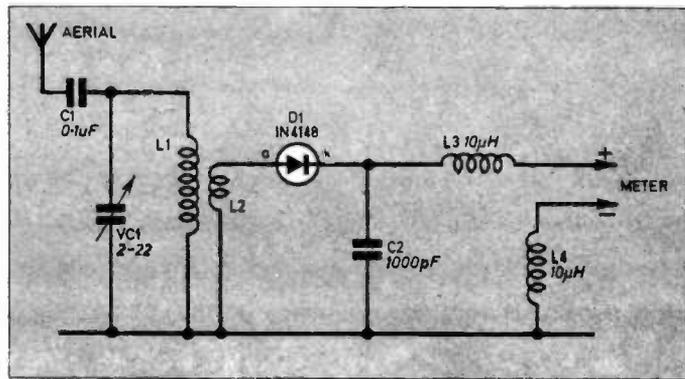


Fig. 2.9. Circuit diagram of the simple Field Strength Meter.

COMPONENTS

- C1 0.1µF disc ceramic
- C2 1,000µF polyester
- VC1 2-22pF miniature polypropylene trimmer
- D1 IN4148 diode
- L1 6½ turns 22 s.w.g.
- L2 2½ turns 22 s.w.g.
- L3 10µH r.f. choke
- L4 10µH r.f. choke

Aerial 36 inch length of wire

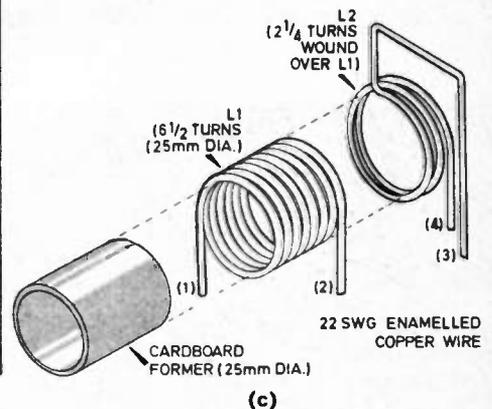
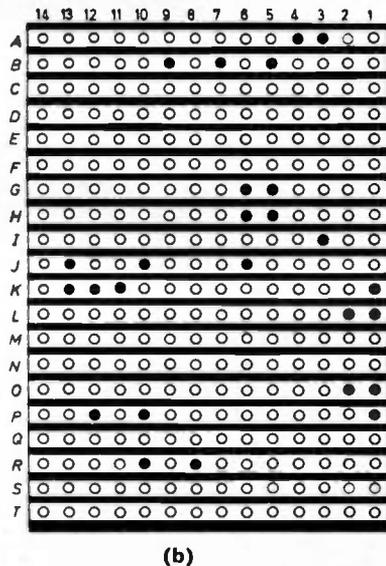
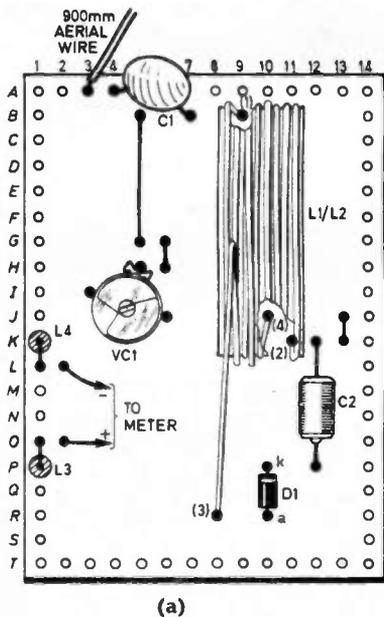


Fig. 2.10. Construction of the Field Strength Meter (a) top view of stripboard (b) underside of stripboard (c) details of coil construction.

With good batteries installed in the transmitter see if there is any reading on the multimeter, if not switch to a more sensitive range. If there is still no reading on the multimeter on its most sensitive range then the crystal oscillator is not running so you will have to turn VC1 until it does. Once you have a reading VC1 requires to be adjusted carefully until a peak is reached. If your multimeter goes to full scale reduce the sensitivity and adjust VC1 again for maximum reading.

Turn your attention now to VC2 and adjust this for maximum reading on your multimeter; again, you may have to reduce the sensitivity of your multimeter. With VC2 now adjusted

go back and check VC1 and then come back to VC2 again for its last adjustment and you should now have a correctly tuned-up r.f. stage. As a further check remove the crystal and your multimeter should show zero; if not, then the circuit is oscillating on its own so go back and check the wiring on the p.c.b.

PULSE WIDTH ADJUSTMENT

The other adjustment to be made on the transmitter is to set up the pulse widths, this is done with VR7. If you have access to an oscilloscope then look at pin 14 on IC3 and you should see the inverse of the waveform shown in Fig. 1.5 (Part 1).

You now require to set the stick on the first channel to its neutral position and then to set-up the first pulse width to 1.5mS using VR7. Moving the stick on the first channel to its extremes should change the pulse width from a minimum of approximately 1mS to a maximum of 2mS.

If you have no access to any equipment other than your multimeter it is suggested that the pot VR7 is left in the centre position and any final setting up its left until the receiver and servos have been made and then the whole system can be set up correctly together.

Next Month: The receiver.

Everyday News

A ROYAL REWARD FOR THE YOUNG

The highlight for winning competitors in this year's finals of the "Young Engineer for Britain 1979" and the Design Council GEC Schools Design Prize "Tomorrows Designers" was to receive their prizes and diplomas from HRH The Prince of Wales and HRH The Duke of Edinburgh.

HRH The Prince of Wales presented the awards to find the "Young Engineer for Britain 1979" at a ceremony held in the Wembley Conference Centre, London, October 25.

A record entry of over 300 youngsters with some 180 projects joined the trail to become Young Engineer for Britain 1979. Amongst the class winners was a project for an electronic pelican crossing and a proximity alarm.


HRH the Duke of Edinburgh presented the young "designers of tomorrow" with their certificates at a ceremony at Buckingham Palace, October 18, and some of the class winners are shown below.

Sense Box

An educational toy primarily to entertain mentally-handicapped children was produced by five girls, Sharon Scandrett, Tracey

Ellis, Beth Hall, Andrea Clark, Helen Taylor and three boys, Julian Mitchell, Adrian Taylor and Scott Kenney from Thomas Easterly Community College.

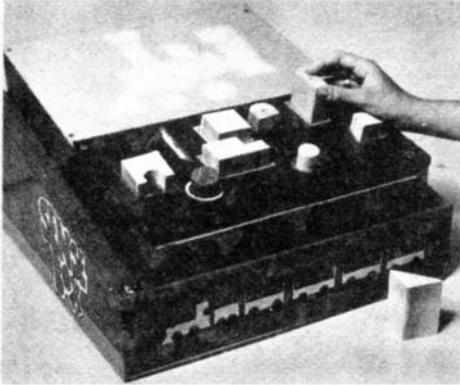The Sense Box consists of a series of differently shaped holes into which corresponding wooden blocks have to be "posted". When a block is in place, its weight triggers a switch which lights a similar shape.



Dosimeter Recharger

Three students from St Austell College, Ian Grainger-Allen, Alan Varco and Philip Dover won a prize for their design of a re-charging unit for a dosimeter—an instrument which measures the amount of atomic radiation in the air.

The Students' prize-winning idea was easy to use, effective, and ergonomically designed. For their charging agent they used a piezoelectric crystal, taken from a cigarette lighter, and designed a pistol-shaped casing to contain it. The dosimeter fits on top, along the "barrel", and the user holds the unit up to his eye in order to read the scale which tells him when re-charging has been successfully completed.

Steam Engine Simulator

An interest in electronics rather than model trains brought a commission for Jonathan Stewart, Ampleforth College, to design a system which puts the "chuff" into a model railway steam engine.

Basing the sequence of

sounds on a full scale steam engine, Jonathan's design also produces the noise of a feedwater pump, the safety valve and the air pumps. The effect of the "chuff" is obtained from bursts of white noise repeated at a rate dependent on the velocity of the engine. The sound is regulated by a switching device on the train's wheel breaking the contact at regular intervals.

The idea of a model steam engine making a sound is not new, but Jonathan's design has two major innovations. One is that the unit is designed to be housed in the locomotive rather than beside the track, with the speaker in the engine tender. Secondly, the sounds are automatically controlled according to speed and load so that all the sounds, including starting and stopping, are realistic.

Although the design is currently only at the prototype stage with a large box containing the circuitry, the likelihood is that if it is taken up for production by a firm it can be incorporated into a micro-chip.



Space sell-out

The first 38 flights of the US Space Shuttle have been sold out reports John Yardley, director of the space transportation system at NASA.

First flight is now scheduled for mid-1980. The 38 flights will carry 62 individual payloads, many of them directly concerned with electronics such as satellites, or experiments in orbiting laboratories.

SPY RADIO

A new form of spy radio has been developed by Racal. It fits in an executive briefcase, is battery powered and self-tuning.

The message is converted into data and transmitted in a high-speed burst of code to avoid detection. Short messages can be sent in one or two seconds. A message of 204 five-figure groups only takes 20 seconds to transmit.

Micro Aid Cuts

Government spending economies have resulted in cut-backs in aid in the British microelectronics industry promotion programmes. Under the revised arrangements the Microprocessor Industry Support Programme will now receive £55 million and the Microprocessor Applications Project £25 million.

The Inmos microelectronics production project still goes ahead with £25 million of basic capital investment with a second tranche of £25 million currently under review.

On the plus side some £6 million is being made available from the EEC to promote the technology in Europe, a sum regarded as derisory by many industry commentators.

ANALYSIS

THE WIRED COMMUNITY

Latterly there has been a huge expansion in information services. People can use the telephone for the latest test match scores, stock exchange index, today's food recipe and so on. With suitably equipped TV sets there is now access to data banks, constantly updated. And through merging the home telephone with radio, individuals are able to participate from their homes in live phone-in radio programmes.

Now the Japanese have taken community communications a whole stage forward by putting all such services into a single package which they call Hi-OVIS (Highly Interactive Optical Visual information System). It took over two years in design and construction and came into service in July 1978. It is the prototype of the wired city of the future.

Technically it is of greatest interest through the exclusive use of fibre-optic communication lines rather than co-axial cable. Operationally its greatest feature is that all the homes linked into the system not only have a keyboard terminal for calling up the services required but also a monochrome TV camera and microphone through which they can participate in community discussions on live TV without visiting a studio.

The choice of optical fibre cables was based on large transmission capacity, low loss, freedom from electrical interference and economy. The cable is strung overhead using existing telephone and power line poles. Total length of cable connecting the present 158 "subscribers" to the Hi-Ovis centre is 350km.

Needless to say the whole system is computer-controlled from two sets of minicomputers which normally share the tasks involved in dealing with requests from subscribers. If one set breaks down the other carries on with all tasks so providing a fail-soft facility. Apart from responding to the requests of subscribers for national TV, local TV, films, data, weather and traffic news, shopping guide and dozens of other services, the computing system also generates statistics on the type and number of requests from the subscribers.

In fact Hi-Ovis is more a social than a technological experiment. The technology is available today and has been implemented, even though on a fairly small scale, in the Higashi-Ikoma District. But it is a modular system capable of easy expansion in sub-centre blocks of 168 home terminals.

The big question is whether people really need such comprehensive facilities for entertainment, information and two-way communication and how will it affect their lives— for good or for ill?

So the social consequences are being studied and analysed in depth and on an international scale. Well over 4,000 people from many countries and organisations have visited Higashi-Ikoma to see Hi-OVIS in action. Whatever the final outcome we should be grateful to the residents of the area for offering themselves as guinea-pigs in a live social experiment which may one day transform our style of living.

Brian G. Peck.

Energetic waves

The systems engineering and consultancy company EASAMS Ltd., has been awarded a contract from the Department of Energy to assess the viability of wave energy devices.

In the UK the most energetic wave fields are off the west coast of Scotland where it has been estimated that a wave power station 1000km long could yield 70 million megawatt-hours/year, about one third of the present UK demand for electricity.

MPUs in action

Of 66 equipments on show at the Racal Group's private exhibition Racalex 79 in London, 45 of them incorporated MPUs.

Among the new items was the first ever working demonstration of frequency-hopping v.h.f. military tactical radio which, by changing frequency several times a second, allows communications to continue successfully during heavy enemy jamming.

Videodiscs

Philips/MCA system videodiscs will be pressed at Mullard's plant at Blackburn. It will be the first plant outside the USA to make videodiscs and will employ about 200 people in the process.

The Philips/MCA videodisc system is to be launched in Europe in 1981. The videodisc players are being made at the Philips plant at Hasselt in Belgium.

British businessmen can now dial direct to Peking for sending telex messages, a big advantage now that trade with the People's Republic is increasing fast. China is the 129th country to which Britain's 80,000 telex users can directly dial.



A bubble memory module with a data capacity of 1,048,576 bits (128k bytes) has been introduced by Intel. Texas Instruments, however, also has a megabit memory which claims to have a faster access time. Other manufacturers are tooling up for the megabit market.

EARTH TERMINAL

A new Plessey company, Plessey Satellite Communications, got away to a good start with a £1.4 million order for an earth terminal for Western Samoa.

The earth terminal business world-wide is currently estimated at £100 million a year. Plessey hopes to secure a 10 per cent market share by 1985.

The Independent Broadcasting Authority aims to have 30 main high-power transmitting stations for the new Fourth Channel colour television network completed and ready for simultaneous launch in all ITV regions (except Channel Islands) by November 1982.

From the outset the Fourth Channel will be available to over 80 per cent of the population of the United Kingdom, more than 40 million potential viewers. An additional 18 high-power main stations will then join the network as they are completed at the rate of one a month during 1983-84.

Priority for Wales

Priority is being given to Wales in two ways. All six main high-power stations serving Wales are included among the first 30 stations on which the Fourth Channel will be launched. These are Wenvoe, Llanddona, Carmel, Presely, Blaen-Plwyf and Moel-y-Parc.

Additionally, it is planned to equip some 80 local relay stations in Wales before November 1982. The population coverage in Wales, from the start, should be in excess of 90 per cent.

Contracts and Employment

The IBA has already awarded contracts totalling more than £16 million to Marconi Communication Systems Ltd, of Chelmsford and Pye TVT Ltd, of Cambridge for the supply and installation of the 48 sets of high-power transmitters. These contracts, for the latest generation of u.h.f. transmitters, are the most valuable ever placed by the Authority.

The new high-power transmitters will comprise the first major television network to be based on the latest generation of high-efficiency klystron amplifiers. Also, they will feature a novel microprocessor-based programmable transmitter control system which, in conjunction with control units to be supplied by the IBA, will provide automatic operation of the transmitters, together with external status indications and remote and supervisory functions at the IBA's new Regional Operations Centres around which the entire network will be built.

In placing these large orders, the first time all main transmitters for a large television network have been ordered at the same time, the IBA will not only simplify its own planning and building operations but will also help the British manufacturers to plan their production on a long-term basis, creating and ensuring steady employment.

Viewers sets

The Fourth Channel will be the first programme service in the history of British television for which the vast majority of viewers will already have suitable receivers and aerials at the time of the launching. While viewers will need to ensure that their sets are correctly tuned to the new channel, and some may need to have their aerials re-adjusted to achieve good balance of signals over all four channels, for many it will just be a matter of pushing their presently unused channel-selection button.

MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current: 0-150 mA. Resistance: 0-100,000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges. $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE



£6.95

6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Req. 9V battery. 22-351. REG. PRICE



£79.95

MULTITESTER


Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a, 0-3-30-300 milliamp. Resistance 0-30-300-3k-301k-1 megaohm, 0-100-1k-10 10k-100k-3 megaohms. Req. 9V battery. 22-209.



REG. PRICE
£29.95

TRANSISTORIZED SIGNAL TRACER

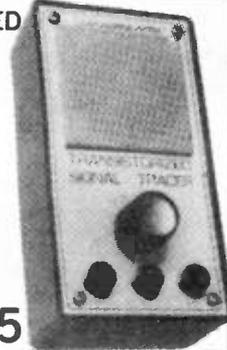Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.



REG. PRICE **£9.95**

DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.



REG. PRICE **£19.95**

SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.



REG. PRICE **£2.79**

AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**

REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.

REG. PRICE **£229.95**



DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.



REG. PRICE
£9.95

VARIABLE POWER SUPPLY

Power project boards. IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**



You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

TANDY



TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access. Barclaycard and Trustcard welcome. Prices may vary at individual stores.

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.

Everyday Electronics, December 1979

All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

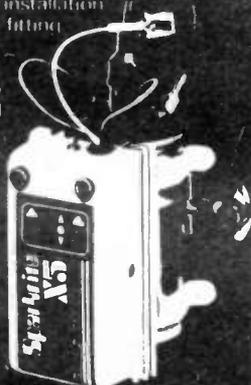There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built-in static timing light, systems function light, and security changeover switch. Will work all rev counters.



Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED. Die-cast case, Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. EE1179
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X5 KIT £16.95

£


Cheque No. _____

ACCESS OR BARCLAY CARD No. _____

Send SAE if brochure only required

ELECTRONI-KIT

DENSHI KITS— SPECIAL OFFER

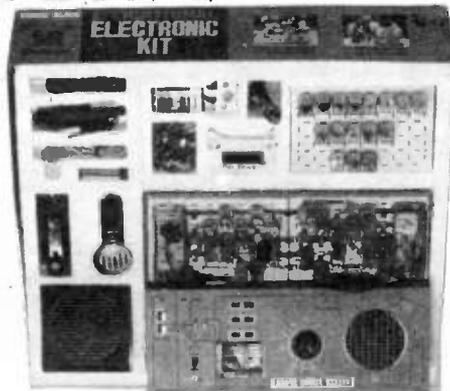

"... fun and entertainment as well as education"—
(EVERYDAY ELECTRONICS mag.)

The SR-3A kit (over 100 circuits) and the SR-3A de luxe kit (over 105 circuits) are available again, at little more than their 1977 prices

Circuits are constructed by plugging the encapsulated components into the boards provided, following the instruction manual. Technical details are also given concerning each project. The components are used over and over again and you can design your own circuits too, or use the kit as a useful testing board.

No previous experience of electronics is required but you learn as you build—and have a lot of fun too. The kits are safe for anyone.

SR-3A KIT £29.95
(16½ × 10 × 2½")

Build over 100 projects including 3-TR reflex radio receiver, 3-TR radio receiver with RF amplifier, 2-TR reflex radio receiver, 3-TR amplifier for crystal mike, 3-TR amplifier for speaker/mike, 3-TR signal tracer, Morse Code trainer, 2-TR electronic organ, electronic metronome, electronic bird, electronic cat, electronic siren, electronic gun, 2-TR sleeping aid, high voltage generator, discontinuity warning device, water supply warning device, photoelectric alarming device, 3-TR burglar alarm, 3-TR water supply warning device, 3-TR water level warning device, 3-TR photoelectric alarming device, Morse Code trainer with sound & light, discontinuity warning device with sound & light, water level warning device with sound & light, electronic metronome with sound & light, buzzer with sound & light, wireless mike, wireless telegraph set, wireless discontinuity warning device, wireless water level warning device, wireless water supply warning device, wireless photoelectric warning device etc. etc.

SR-3A de luxe KIT £39.95
(illustrated 16 × 14 × 3½")

Similar to SR-3A, more components including solar cell and additional Speaker unit plus sophisticated control panel.

All kits are guaranteed and supplied complete with extensive construction manuals PLUS Hamlyn's "All colour" 160 page book "Electronics" (free of charge whilst stocks last).

Prices include batteries, educational manuals, free book, VAT, p&p (in the UK), free introduction to the British Amateur Electronics Club.

Cheque/P.O./Access/Barclaycard (or 16p. for illustrated literature) to DEPT. EE.

ELECTRONI-KIT LTD.
RECTORY COURT, CHALVINGTON,
E.SUSSEX, BN27 3TD (032 183 579)

DON'T LET THIS BE A
WINTER OF DISCONTENT

GET ALOFT

AND INSTALL THE EE
EARLY WARNING
SYSTEM

This provides instant warning of water leakage, overflow and approaching freezing conditions in the loft.

- ★ Independent visual indicator for each channel
- ★ Master warning light
- ★ Audible alarm with presettable on-time
- ★ Facility for extension alarm to meet domestic environment needs
- ★ Battery operated



EXTENDED RANGE TIMER

A versatile unit that will generate time delays of up to twelve hours, in one hour increments. Suitable for switching mains appliances on or off.

REVERBERATION UNIT

An effects unit for use with electronic musical instruments and microphone. Ideal for the pop musician and vocalist. An easy to build project employing a springline.

UNIBOARD No. 3
9 VOLT POWER SUPPLY

AND ALL THE REGULAR FEATURES


Everyday ELECTRONICS

JANUARY 1980

ISSUE ON SALE
FRIDAY, DECEMBER 14
Price 45p

The Extraordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett

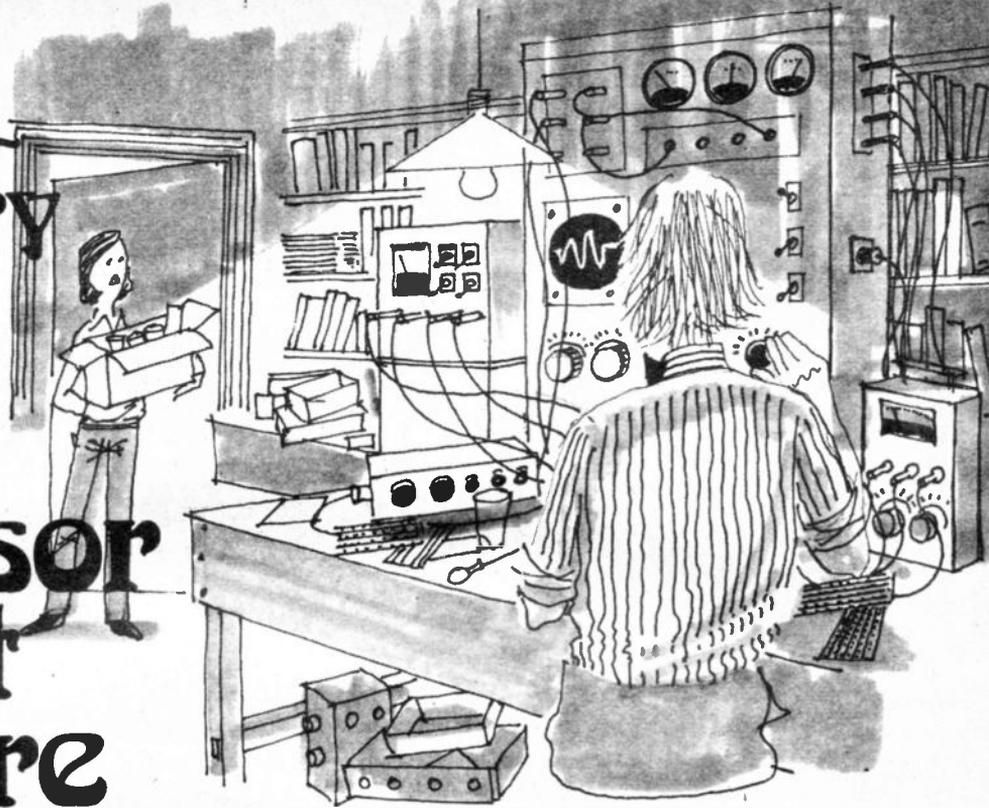

MAURICE dug deeply into his amazingly capacious duffel bag and eventually produced a couple of dishevelled fuzz boxes, part of the electronic equipment for the "Space Age Rock Band" which he and Tom are forming to play in support of various local charities.

WHAT'S ALL THIS FUZZ?

"These old fuzz boxes have been given to us and we wonder whether they're worth mending, also there are a few things we don't understand about fuzz boxes, and we would be very grateful if you could explain something of their principles."

"Yes, Prof.," Tom joined in, "One of the things that puzzle me most about fuzz boxes is that they all seem to sound different from one another."


"Although there are a few designs which sound nearly the same as each other and are probably almost identical copies inside, it seems to me that there are big ones, small ones, simple ones, complicated ones, expensive ones and cheap ones, some of which sound better than the expensive ones. When I plug my guitar in and try a few different fuzz boxes, the

sounds I hear from some are so radically different from others, it has puzzled me for a long time how these mysterious electronic boxes can, magically it seems, alter the sound of my guitar in so many ways!"

"A very interesting question, Tom," The Prof. began to explain: "It's all to do with sound waves, which are represented inside

audio equipment by changing voltage patterns which we can consider graphically as waveforms.

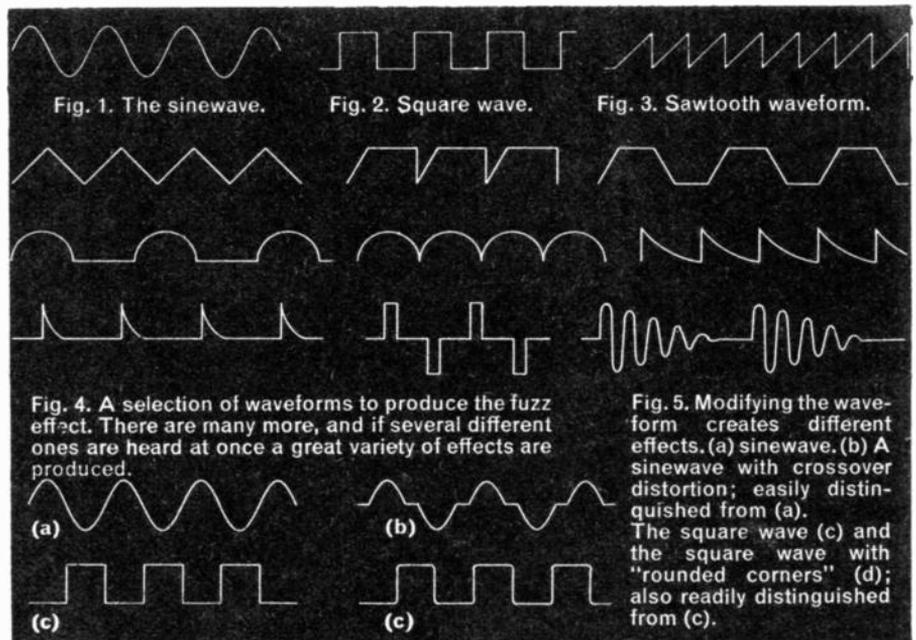"I think we all know a little already about audio waveforms: the sinewave, Fig. 1, which sounds somewhat flute-like; square wave (Fig. 2) with a reedier sound; sawtooth waves (Fig. 3) which sound a little like violins, but without the rich resonance of a good instru-



OK MACHINE & TOOL (U.K.) LTD. HARDWARE SUPPLIES

ALL PRICES IN PENCE UNLESS STATED OTHERWISE

FOR FURTHER INFORMATION RING FOR DETAILS.

NOTE: PRICES INCLUDE P&P & V.A.T.

DIP SOCKETS WIRE WRAP MIN. ORDER 5 OFF SOLDER

C81-08-04	.30	C83-08-02	.13
C81-14-04	.39	C83-14-02	.15
C81-16-04	.43	C83-16-02	.17
C81-18-04	.49	C83-18-02	.20
C81-20-04	.63	C83-20-02	.24
C81-22-04	.66	C83-22-02	.26
C81-24-04	.69	C83-24-02	.31
C81-28-04	.77	C83-28-02	.34
C81-36-04	1.24	C83-36-02	.40
C81-40-04	1.26	C83-40-02	.46

EUROPEAN STANDARD CARDFRAME SYSTEM

(3U x 160MM) NO. 420-000 17.25
(6U x 160MM) NO. 420-068K 24.80


GUIDES FOR ABOVE

426-008 52 PR.

TWO PART DIN41612 CONNECTORS

MALE 64 WAY FEMALE 64 WAY
064-08-03317 2.41 564-08-04347 (SOLDER) 4.00
(ANGLE SOLDER PIN) 164-08-04317 (WIRE WRAP) 3.28

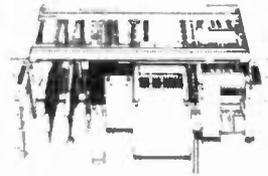FRONT PANELS AND MODULES AVAILABLE ON REQUEST.



NEW ALL PURPOSE VOLT CHECKERS AC, DC

HOBBY CHECK 110V, 220V, 380V (+ & -)	4.48
VOLT CHECK 0-380V	3.44
POWER CHECK 110V, 220V, 380V ~ AC 150V, 300V, 500V - DC	3.11
MASTER CHECK 6, 12, 24, 50, 110, 220, 380V =	8.24

MIN 'D' RS232 CONNECTORS SOLDER BUCKET

15 WAY MALE	.96
15 WAY FEMALE	1.11
25 WAY MALE	1.42
25 WAY FEMALE	1.62
50 WAY MALE	2.48
50 WAY FEMALE	2.96

EURO OK BOARDS 100 x 160MM FIBREGLASS 0.1" MAT 0.042" HOLES

PC-01 TERMINAL BOARD PLAIN	2.62
PC-02 PCB INSULATED CU PADS	3.26
PC-03 PCB SINGLE SIDED CV STRIP	3.26
PC-04 PCB HORIZONTAL & VERTICAL CU STRIPS	3.54

NEW LATEST DEVELOPMENT IN LOGIC PROBES 1000's OF HAPPY USERS

CMOS TTL NOS. SENSITIVE 10MS.
150MS STRETCH ALL LOGIC 4-15V
NO. PRB-1 29.89



PCB TERMINAL STRIPS

SCREW CLAMPING	
TS-4 POLE	1.18
TS-8 POLE	1.84
TS-12 POLE	2.52

NEW MODULAR BREADBOARDS CIRCUIT MOUNT

C100 PROTOTYPE BOARD 10.20 CONTACTS	18.23
C200 PROTOTYPE BOARD 6.30 CONTACTS	11.56
C300 PROTOTYPE BOARD 5.90 CONTACTS	6.99
C400 PROTOTYPE BOARD .80 CONTACTS	1.71
C500 BUS STRIP 1.00 CONTACTS	1.64

DIP PLUG RIBBON CABLE ASSEMBLIES

14 PIN		16 PIN	
DE 14-2"	2.63	DE 16-2"	2.92
DE 14-4"	2.71	DE 16-4"	2.98
DE 14-8"	2.77	DE 16-8"	3.06
DE 14-24"	2.92	DE 16-24"	3.20

DIP PLUG WITH COVER (2 PER PACK)

14 PIN		16 PIN	
14 PLG	1.22	16 PLG	1.34

TERMINALS WIRE WRAP GOLD PLATED 0.025" SQ. POST

WWT- SLOTTED	2.62	1
WWT- SINGLE SIDED	1.57	2
WWT- IC SOCKET	2.62	3
WWT- DOUBLE SIDED	1.04	4

WIRE DISPENSERS 30AWG INC. WIRE

WD-30B BLUE	3.32	WD-TRI-30	
WD-30Y YELLOW	3.32	3 COLOURS	5.01
WD-30W WHITE	3.32		
WD-30R RED	3.32		
REFILLS AVAILABLE			

PLIERS & CUTTERS BOX JOINTED HIGH QUALITY

304 140MM LONG FLAT NOSE	4.83	3136 CUT ANYTHING	4.43
306 140MM LONG CHAIN NOSE	4.83	CT01 CRIMPING TOOL	3.19
301 115MM FLAT MICRO	4.74	SP01 SELF ADJUSTING	
303 115MM CHAIN MICRO	4.74	STRIPPER	19.59
311 110MM CUTTER DIAGONAL	5.46	SAF01 SAFETY SHEAR	2.50
751 160MM WIRE STRIPPING PLIERS ADJUSTABLE	4.14		

SCREWDRIVERS STEADFAST

SUPERDRIVE		FLAT BLADE	
BP0/100	1.13	3205/3 60MM	.12
BP1/075	1.08	3205/5 100MM	.26
BP2/100	1.25	3205/7 150MM	.52
		3205/9 200MM	.81

WIRE WRAPPING CENTRE THE ORIGINAL AND BEST

WSM30 3 IN 1 WRAPPER, STRIPPER, UNWRAPPER	5.59
NEW	
JW-1 DAISYCHAIN JUST WRAP, NEW INVENTION (INCLUDES WIRE BLUE, RED, YELLOW, WHITE)	12.61
BW630K BATTERY TOOL KIT (POWER TOOL, NICAD BATTERY CHARGER)	48.42
CAS130 CLIP & STRIP 1" OF 30AWG	1.67

NEW UNIVERSAL VACUUM VICE

VV5 5.85
STRONG GRIPPING
2 JAW SIZES



NEW ELECTRONIC VACUUM VICE

VV1 2.94

CMOS IC INSERTORS

MOS 1416	6.69
MOS 2428	6.69
MOS 40	6.69
DIP EXTRACTOR	11.80



ELECTRONIC ENCLOSURES FOR THE PROFESSIONAL HOBBYIST AS USED BY LEADING U.S.A. & BRITISH INSTRUMENT MANUFACTURERS

	WIDTH	DEPTH	HEIGHT	
C23K	8.5"	9.25"	2.44-3.69"	12.07
CH23K	AS ABOVE	WITH HANDLE		14.15
CL45K	12.5"	11.63"	4.5-5.76"	18.18
CM5425K	5.08"	5.25"	1.5"	5.67
CM6-300K	6.06"	6.25"	3.25"	6.51
HP	3.60"	5.75"	1.12"	2.40
BLACK, BEIGE, BLUE & GREY.				

OK Machine & Tool U.K. Limited

Dutton Lane, Eastleigh SO5 4AA Telephone Eastleigh (0703) 610944/5

Telex 477222 Cablegram OKMACH

ment, and there are a good many more different waveforms (Fig. 4), and all of them sound different. Our hearing can be so sensitive that a healthy human being can easily distinguish between waveforms which may appear to be only very slightly different from one another (Figs. 5a, b, c, d).

SAWMILL FUZZ

"A fuzz box will change the waveform of the electrical output from the pickups of your guitar. With some types of fuzz box the change may be quite subtle, but with our sensitive hearing, quite noticeable and often pleasant and interesting to listen to. Others produce a drastic change and may even cause a guitar which usually sounds mellow, to produce a harsh buzz like a sawmill!!

"Obviously a fuzz box which causes a guitar to sound like a sawmill will have processed the waveform in a manner quite different from that of one of the gentler types and this is why some guitarists have more than one fuzz box. One kind for use in ballads and quiet numbers, and another to really wake up their audience in heavy rock numbers.

FUZZY WRINKLES

"It is interesting to consider how fuzz effects have developed over a number of years. For instance, most modern fuzz boxes plug in between the guitar and the input of the amplifier. Some of the earlier ones did not connect like this at all, but went in between the amplifier speaker output and the loudspeakers."

The Prof. drew a few sketches of early fuzz circuits which connect to the speaker (Figs 6a, b, c, d).

"This one, Fig. 6a, gives an effect on the waveform similar to Fig. 5a, b which resembles crossover distortion, whilst Fig. 6b gives a smoother sound. In each of these circuits, different capacitor values may be tried for individually preferred effects; also the two circuits may be combined together.

"In Fig. 6c the signal from the amplifier is split between two speakers. The positive half of the waveform goes to one speaker and the negative half to another. Although one may well disapprove of the ultimate effects on the

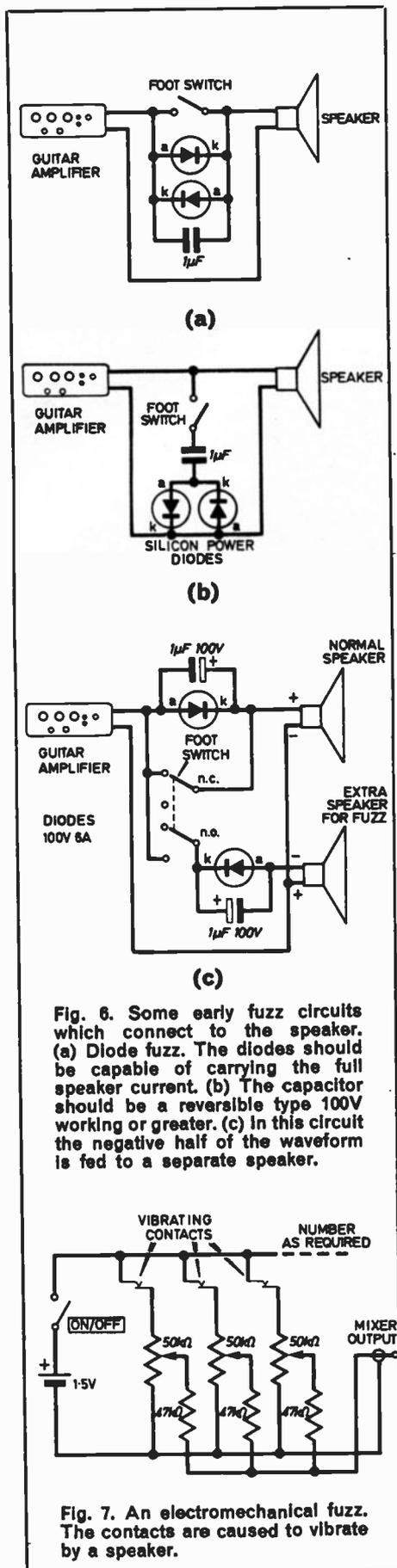


Fig. 6. Some early fuzz circuits which connect to the speaker. (a) Diode fuzz. The diodes should be capable of carrying the full speaker current. (b) The capacitor should be a reversible type 100V working or greater. (c) In this circuit the negative half of the waveform is fed to a separate speaker.

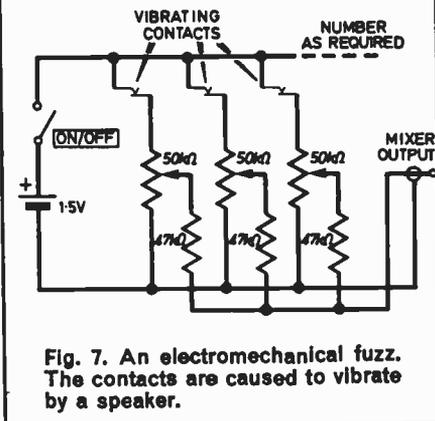


Fig. 7. An electromechanical fuzz. The contacts are caused to vibrate by a speaker.

speakers, apparently some users of fuzz effects consider this worthwhile.

MECHANICAL FUZZ

"Before we go on to consider a number of more modern fuzz boxes using transistors and integrated circuits, it is worth briefly mentioning mechanical fuzz and electromechanical fuzz; methods where the fuzz effects are mechanically produced and the only electronics being the amplifier!

"Perhaps the simplest 'mechanical fuzz' consists of a modification to a loudspeaker, the cone of which is pierced with a number of small holes. Through each small hole a split-pin or else a bifurcated rivet is threaded, and the tangs bent so that although it cannot come out, it will rattle freely when the speaker cone vibrates, rather like the rivets in a drummer's rivet cymbal. The holes in the speaker cone should be strengthened using metal or plastic eyelets or washers.

"I'll leave you to imagine what this might sound like, or else to try it if you've got a spare speaker to risk!

ELECTROMECHANICAL

An electromechanical method which does not involve such drastic alterations to the fabric of a loudspeaker cone involves a number of vibrating contacts, which are caused to vibrate by means of a diaphragm stretched over a hole in a speaker cabinet.

"A small additional amplifier and speaker are used to vibrate the contacts, and are fed with the signal from the guitar. Each contact pair is carefully adjusted so that any slight vibration of the speaker cone causes it to make and break. The contacts are mounted on springs of different lengths so that their natural frequencies are not identical and are connected through a passive mixer network of resistors and potentiometers to the input of the main amplifier (Fig. 7).

"There is a lot of scope for experiments on mechanical and electromechanical fuzz; using vibrating particles, carbon rods, and many other ingenious ideas, some of which have been tried—and some of which you could be the first to discover!"

To be continued.

GMT
ELECTRONICS

**Freepost
Birmingham
B19 1BR
021-233-2400**


- ACCESS
- VISA
- CASH
- CHEQUE

See
at us

**FREE
BOARD
1979**

4th - 8th
December
Royal Horticultural
Halls, London

FULL SPEC KIT TELETEXT DECODER

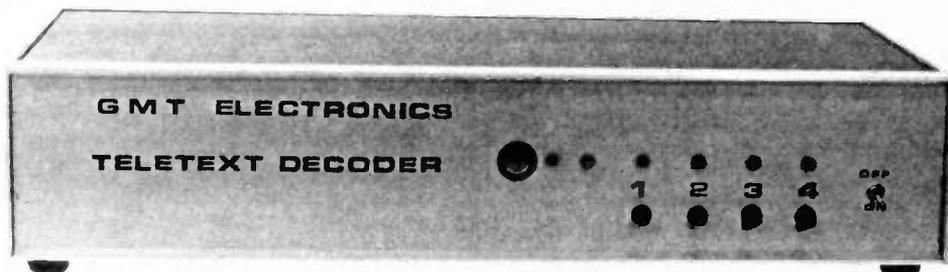

- STATE OF THE ART L.S.I. CIRCUITS
- DOUBLE HEIGHT CHARACTER SELECTABLE FOR LEGIBILITY
- CHARACTER ROUNDING - EFFECTIVELY DOUBLES DEFINITION
- ULTRASONIC REMOTE CONTROL
- HIGH QUALITY THROUGH PLATED P.C.B.
- ALL I.C. MOUNTED ON SOCKETS
- PREALIGNED UHF/IF MODULES
- NEEDS NO INTERNAL CONNECTION TO THE TELEVISION SET
- SIZE 430mm x 90mm x 220mm
- SUPPLY 240v 50Hz 35w
- *NEW *TOUCH CONTROL KEYPAD* NEW*


INCLUDES TUNER, P.S.U., DECODER, REMOTE KEYBOARD, P.A.L. ENCODER, U.H.F. MODULATOR CASE WITH SCREENED AND PUNCHED FRONT PANEL.

— £189.90 inc VAT. P & P £3.00.

FULL TELETEXT MANUAL IF BOUGHT SEPARATELY — £2.50 P & P £0.50.


P.C.B.'S AND L.S.I. I.C.'S NOT SOLD SEPARATE FROM KITS.

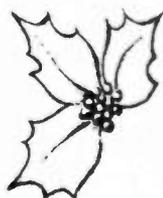P & P INCLUDES CARRIAGE, PACKING AND INSURANCE



GMT HAS

Ideas for Christmas

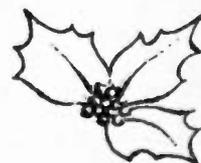

SEND FOR OUR FREE LEAFLET

Enclosing an S.A.E.

* KITS, TOOLS & OTHER GOODIES *

WORKSHOP MATTERS

By Harry T. Kitchen

Fastenings

We have now arrived at the situation where we have a number of sheets of aluminium cut, drilled and bent, ready to form our cabinet. How do we secure them together? Well, as amateurs, we have three basic methods, all with advantages and disadvantages. We can use "pop" rivets, self tapping screws, and nuts with bolts.

Pop rivets are fine for fixing things that do not need to be taken apart easily, as the rivet has to be drilled out. Self tapping screws cut their own threads into any metal hole, and thus have a limited life if continual dismantling is involved. Nuts with bolts are fine where accessibility is reasonable.

My personal preference is for nuts and bolts for fixings of a semi-permanent nature, with self tapping screws for fixing the front panel. Many years' experience has taught me that, with care, self tapping screws can be used in the same hole being inserted and withdrawn many times without damaging the thread it has cut in the metal.

To take the case of our cabinet as an example, I would use nuts and bolts for securing the rear panel of the cabinet to the upper and lower halves—I make much use of two "U" shaped pieces for these as this simplifies construction—with self tapping screws being used for securing the front panel as this may require periodic removal for servicing, rebuilding etc.

Finishing

Now that we have our finished cabinet, do we leave it bare shining aluminium or do we paint it, or otherwise alter the finish? Personally, I have settled for a crackle black cabinet with a "brushed" aluminium front panel, a combination that looks very smart indeed, and assures continuity of appearance.

The black crackle paint is applied onto the aluminium, which is lightly sanded to provide a "key" or "tooth" for the paint. This preparation is essential if the cabinet is not to shower flakes of paint every time it is knocked.

One possible objection to the crackle finish paint is that it does provide lodging for dust; the better the crackle effect, the greater the amount of dust. An alternative which is free from this defect is the hammer finish paint.

If you do not like paint, you can cover your cabinets with materials such as Fablon, and this is available in various finishes; as such it is more suitable for equipment destined for the living room or lounge rather than the work shop. You are your own master here, and can choose the finish you like best, but be prepared to carry out some experiments to achieve optimum results.

Brushed aluminium

The brushed aluminium effect is simple to obtain, and requires nothing more elaborate than steel wool and elbow grease, aided by a little light oil, such as 3 in 1. One of the advantages of this finish is that it can delete careless markings on the panel provided these are not too deep.

To commence, put a few spots of oil on the panel then take a ball of steel wool and draw it across the length of the panel in as straight a line as you can. Repeat, a little further along, say equal to half the width of the ball of steel wool.

Continue doing so, turning the ball of steel wool so that fresh wool is always presented to the panel. You will probably have to repeat the whole operation a number of times. Eventually you should obtain the effect you want.

At this point you will have to wash off the oil and general aluminium/steel wool debris in which the panel is covered by a liberal application of washing up liquid and hot water. The panel must be really free from oil if the following processes are to succeed. Care is the watch word at all times.

Labelling

If our panel is at all complex, then it is well worth labelling all the controls to denote their functions; this not only provides instant recognition, but gives a more professional appearance.

Probably the simplest way of labelling the panel is by using transfers. These are available in various sizes and styles, and most good art shops sell sheets not only of lettering but also of words and symbols, so that you can, with care and discrimination, end up with a panel of distinction.

The letters are transferred onto the metal panel by rubbing the reverse of the sheet with a smooth rounded object; many ball point pens have caps

that are ideally suited for this application. Having completed the lettering of the panel, it is now essential to protect the relatively fragile transfers.

There are essentially two ways of protecting the transfers. You can spray on a lacquer that, when dried thoroughly, gives a fair degree of protection, or you can use a clear Perspex cover. This is in essence another panel, since all the piercings in the panel have to be repeated here, so that it can fit over the panel proper. This is the more expensive and time consuming method, but it gives complete protection to the transfers.

Stencils

An intermediate method that I have occasionally used is to stencil the appropriate wording, using a suitable stencil and pen with black Indian ink, onto a sheet of white card. This is then sandwiched between the panel and the Perspex, and of course hides any scars appearing on the panel.

If you use the hints and tips contained in this short series on panel bashing, with care and patience you should be able to produce cabinets to be proud of. And you will have saved a great deal of money. Try it and I'm sure you will agree.

Bind it

It's so easy and tidy with the Easibind to file your copies away. Each binder is designed to hold approximately 12 issues and is bound and blocked with the Everyday Electronics logo. Gold lettraset supplied for self blocking of volume numbers and years.

Price £3.75 including postage, packing and V.A.T., Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd, Post Sales Dept, Lavington House, 25 Lavington St, London SE1 0PF



it's easy with **EASIBIND**

Order Form

Everyday ELECTRONICS

I enclose p.o./cheque value
for binders. Years required

(BLOCK LETTERS PLEASE)

Name

Address

Date

Britain's Best Breadboard Buy at Breadboard '79

**FREE
ENTRY TICKET
WORTH £1.00
WITH EVERY PURCHASE**

All over Britain, hobbyists are discovering Britain's Best Breadboard Buys. At the London Breadboard exhibition '79 on Stand Nos. F1, F2 and G1, G2, CSC will be exhibiting their full range of breadboards.

Here is your chance to obtain a special ticket for Breadboard '79 worth £1.00 absolutely FREE.

Cut out the coupon below and take it along to one of our listed dealers, and make a purchase of any of our breadboards and receive your special FREE ticket — see you at Breadboard '79.

Take the coupon to any of these main dealers:

LONDON
Rastra Electronics Ltd., 279-281 King Street, Hammersmith, London W6

Cubegate Ltd., Audio Electronics, 301 Edgware Road, London W2 1BN

Technomatic Ltd., 17 Burnley Road, London NW10 1ED
Precision Instrument Labs., Instrument House, 727 Old Kent Road, London SE15

MANCHESTER
Shudehill Supply Co., 53 Shudehill, Manchester M4 4AW

BUCKINGHAMSHIRE
West Hyde Development, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET

Best Electronics (Slough) Ltd., Unit 4 Farnburn Ave., Slough, Bucks SL1 4XU

KENT
Lawtronics, 13a High Street, Edenbridge, Kent TN8 5AX

NEWCASTLE
Aitken Bros., 35 High Bridge, Newcastle upon Tyne

SCOTLAND
Marshalls, 85 West Regent Street, Glasgow G2
F. Brown & Co., 45 George IV Bridge, Edinburgh EH1 1E3


LEEDS
Leeds Amateur Radio Club, Cookridge Street, Leeds 1

HERTFORDSHIRE
81-PAK, 3 Baldock Street, Ware, Herts.

CONTINENTAL SPECIALTIES CORPORATION



CSC UK LTD. EUROPE, AFRICA, MIDEAST
Dept 4CC2 Shire Hill Industrial Estate Units 1 and 2, Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682. Telex: 817477

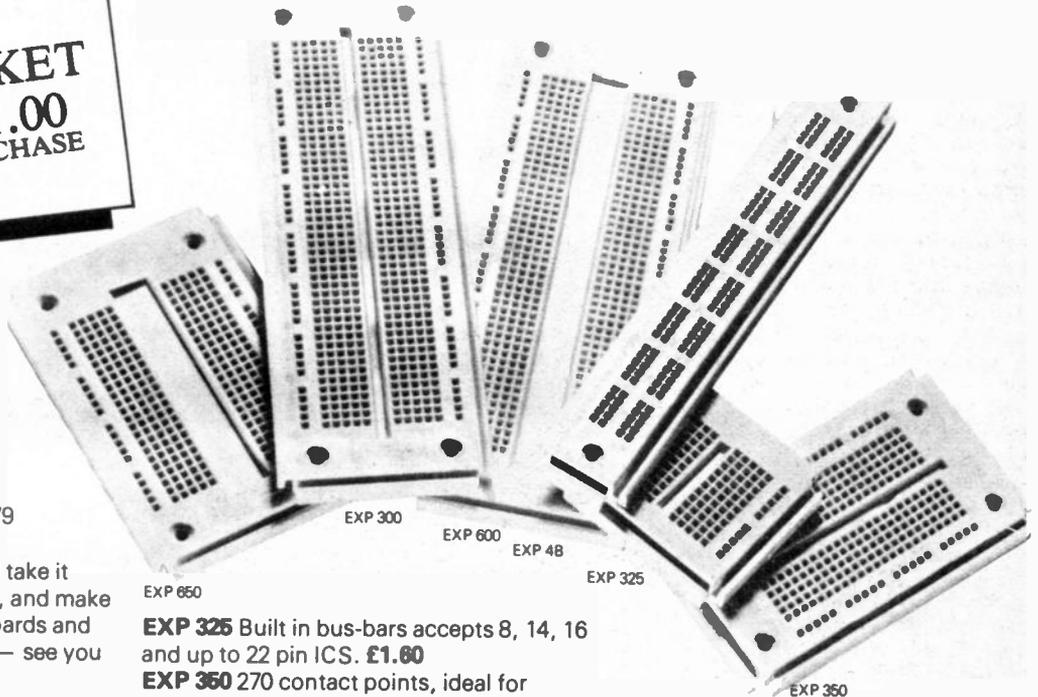

EXP 650

EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. **£1.60**

EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**

EXP 650 For microprocessor chips. **£3.60**
EXP 4B An extra 4 bus-bars in one unit. **£2.30**

EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**

EXP 600 6" centre channel makes this the Microprocessor Breadboard. **£6.30**

PB6 Professional breadboard in easily assembled kit form. **£9.20**

PB100 Kit form breadboard recommended for students and educational uses. **£11.80**

The above prices do not include P&P and 15% VAT

The Experimentor System

4 ways to order Experimentor Systems

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB — £1.32
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads — £1.68
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard — £8.60
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad — £9.30

This coupon entitles the holder to a free ticket worth £1.00 to Breadboard '79, with the purchase of any listed breadboards

1. EXP 325	Qty. Req'd.	2. EXP 350	Qty. Req'd.
£2.70		£4.40	
3. EXP 650	Qty. Req'd.	4. EXP 4B	Qty. Req'd.
£5.00		£2.30	
5. EXP 300	Qty. Req'd.	6. EXP 600	Qty. Req'd.
£7.75		£6.30	
7. PB6	Qty. Req'd.	8. PB 100	Qty. Req'd.
£11.75		£14.72	

Experimentor System

1. EXP 300PC	Qty. Req'd.	2. EXP 302	Qty. Req'd.
£1.32		£2.70	
3. EXP 303	Qty. Req'd.	4. EXP 304	Qty. Req'd.
£8.60		£9.30	

Boxed prices include P&P and 15% VAT

If no dealer in your area contact CSC direct.

Continental Specialties Corporation, (U.K.) Limited, Dept 4CC2
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex Tel: (0799) 21682

NAME

ADDRESS

FREE catalogue tick box

I enclose cheque/PO for £
or debit my Barclaycard, Access, American Express card

No. Exp. date
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

UNIBOARDS

SIMPLE TRANSISTOR DESIGNS

By A.R. Winstanley

2

BURGLAR ALARM

MANY designs have been published for burglar alarms which give comprehensive protection against intruders. Quite often, however, all that one may require is a very simple system such as the Burglar Alarm Module described here.

This device incorporates one n.c. (normally closed) and one n.o. (normally open) loop for the detection arrangement. Several switches could be placed in series or parallel—depending on the loop used—so that more than one potential break-in point could be monitored with just one loop, see later.

The system described operates from a 9V PP3 battery and as such is not intended for heavy use, although the circuit has been designed to draw as small a quiescent current as possible (50 microamps). Battery life is therefore quite good, but if the module is to be used regularly, then it is advised that a mains derived power pack is used thereby obviating battery replacements.

CIRCUIT DESCRIPTION

The circuit diagram of the alarm is shown in Fig. 1. Resistors R1 and R2, being of equal value, form a potential divider clamping the base of TR1 to half the supply rail, i.e. 4.5V. The emitter TR1, therefore, will be 0.6V less than this—3.9V. The normally-closed loop is connected between TR1 base and 0V, so the base is normally grounded and TR1 is off, the emitter being low.

When the n.c. loop is broken, the base rises immediately to 4.5V and the emitter "follows" this, rising to 3.9V. This signal is transmitted

through R4 and D1 to the gate of CSR1, thereby triggering this thyristor. The thyristor then completes the circuit to WD1 and R6, D2 and so WD1 sounds and D2 illuminates.

The alarm, WD1, is a miniature electronic audible warning device consuming only about 15mA when operating. Conventional electro-mechanical buzzers cannot be used because they can easily draw in excess of 500mA, the maximum forward current allowable in the thyristor. If a heavier alarm load needs to be switched, then WD1 could be substituted by a 9V relay with contacts rated to suit one's needs.

Light emitting diode, D2, indicates that the alarm is operating, but it also provides a minimum holding current for the thyristor, thereby preventing it from resetting undesirably.

The n.o. loop is connected between the positive rail and R5, a current limiting resistor for the gate of CSR1.

When the loop is closed, even for a tiny fraction of a second, then CSR1 will trigger and operate the alarm. Diode D1 isolates the n.o. loop from R4 and R3. If it were not present then if the n.o. loop were closed, R5, R4 and R3 would form a potential divider holding the gate of CSR1 at exactly 0.5V—not enough to trigger the thyristor.

Capacitor C1 prevents the thyristor from triggering on initial power switch on. This particular design seemed prone to do this. Whilst it will slow down the response time of the circuit, this is not noticeable and the circuit still operates very fast.

Finally, S1 is a normally-closed switch incorporated into the n.c. loop but this switch is mounted in the module. When it is pressed it will cause the warning device to operate. The switch therefore provides an alarm/battery test facility, and enables a rough check on the battery condition to be made.


CONSTRUCTION starts here

CIRCUIT BOARD

The module is built into a plastic box type PB1, of dimensions 114×76×38mm. The circuit itself is built onto a piece of 0.1 inch stripboard measuring 24 holes×10 strips, see Fig. 2.

Construction is quite straightforward. Drill two holes as shown to take two 6BA mounting screws. Make all of the breaks in the copper strip using either a spot face cutter or a hand held twist drill, then proceed to solder in the components followed by suitable lengths of lead to reach the case mounted components.

Fig. 1. The circuit diagram of the Burglar Alarm with integrated battery supply.

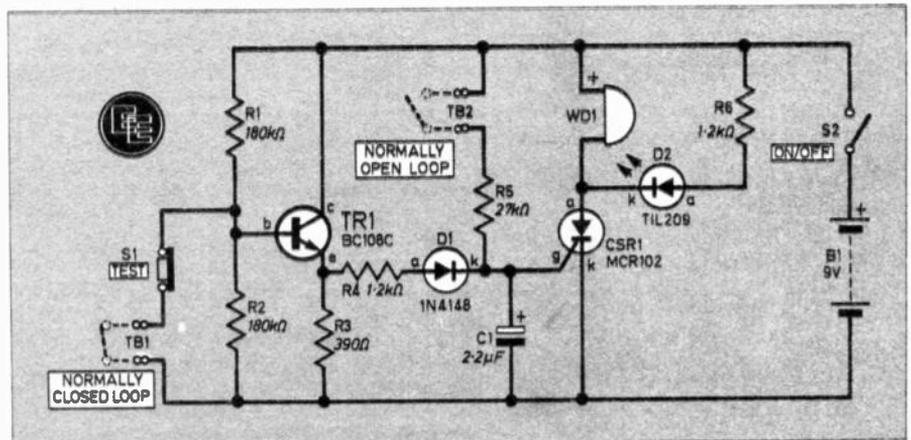



Components mounted on the circuit board.



The finished Burglar Alarm module. The base of the case becomes the "front panel" and components are mounted as shown, including the warning buzzer. Small terminal strips are mounted on the side of the case to take the closed and open loop wiring.

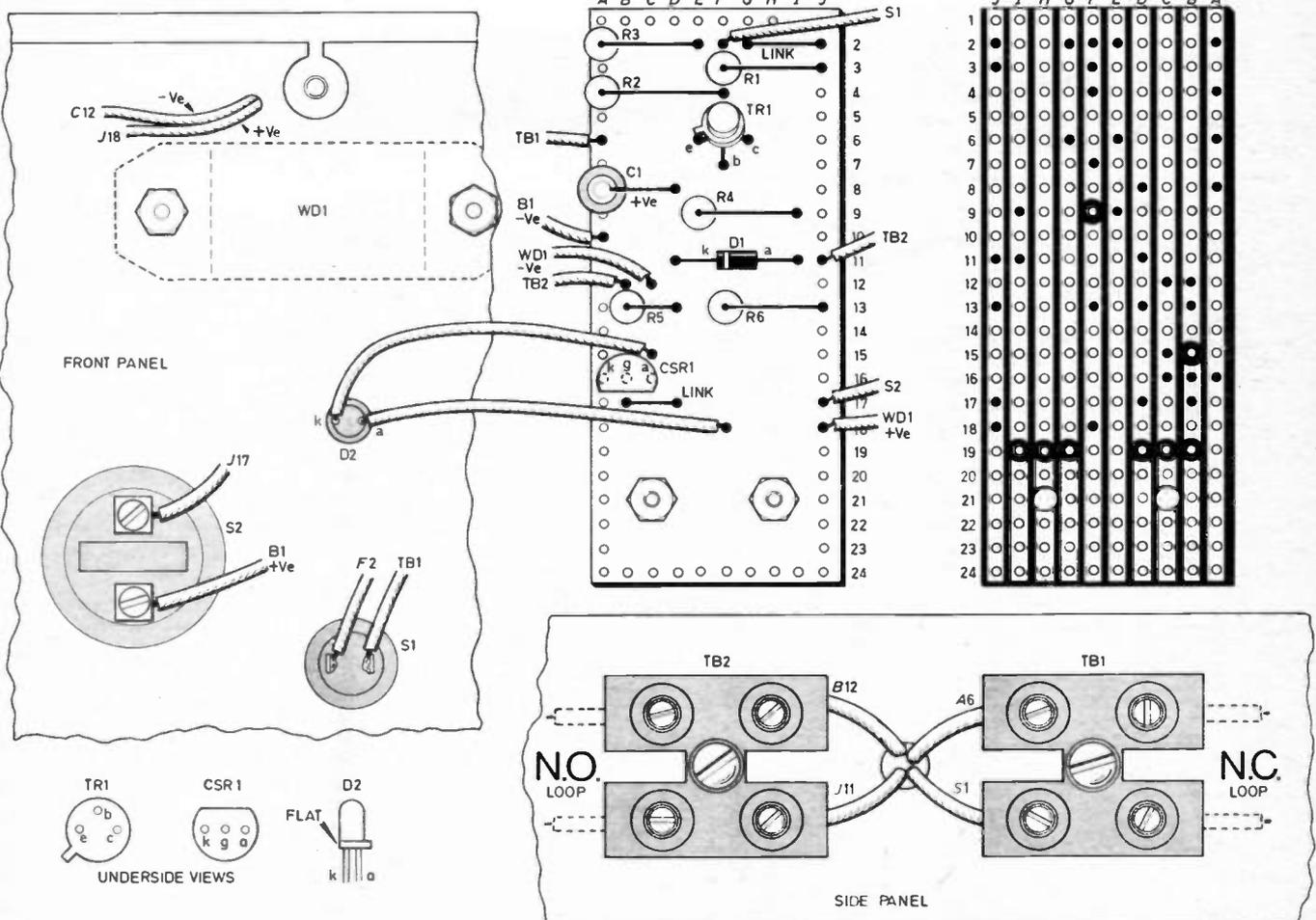


Fig. 2. Complete construction details showing interwiring between board and case mounted components, and layout of the components on the top side of the stripboard.

COMPONENTS

Resistors

R1 180k Ω	R4 1.2k Ω
R2 180k Ω	R5 27k Ω
R3 390 Ω	R6 1.2k Ω
All $\frac{1}{4}$ W carbon $\pm 5\%$	

Capacitors

C1 2.2 μ F 10V elect.

Semiconductors

TR1 BC108 <i>n</i> p <i>n</i> silicon
D1 IN4148 or similar silicon diode
D2 TIL209 or similar red l.e.d.
CSR1 MCR102

Miscellaneous

S1 s.p.s.t. push-to-break, release-to-make
S2 s.p.s.t. rocker
B1 9 volt PP3 (preferably Duracell)
WD1 miniature 9V audible warning device

Stripboard: 0.1 inch matrix, 10 strips \times 24 holes; 4-way 2 Amp terminal block; PP3 connector; retaining clip for D2; case type PB1, approximately 110 \times 73 \times 35mm; 6BA nuts (8 off) bolts (6 off); washers (10 off), spacers (2 off); wire and switches for loops.

Approx. cost **£4.00** Guidance only
excluding loop components


The usual rules regarding soldering apply. Do not overheat any semiconductors and take care not to bridge adjacent copper strips with whiskers of solder, etc.

Prepare the case to accept the case mounted components and fix these in position and wire up to the board as shown in Fig. 2.

In the prototype, the board was fitted to the case by two 18mm long 6BA nuts and bolts and 12mm long spacers.

The audible warning device (WD1) is mounted on the front of the box using two 8BA bolts. A small hole is

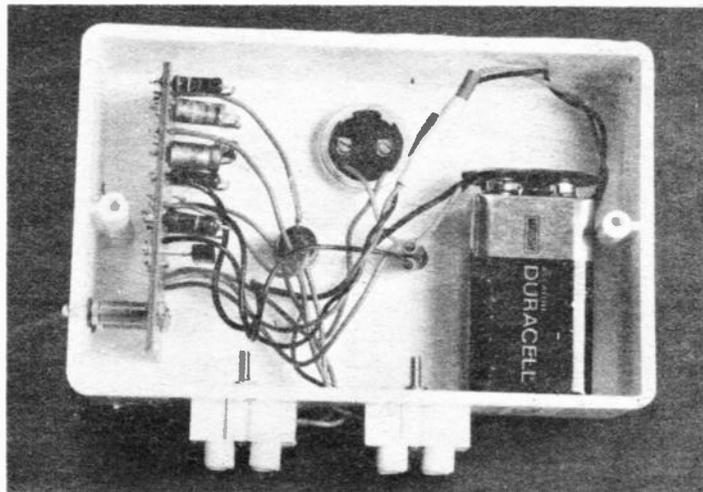Positioning of components, battery and circuit board within the case. The circuit board should be mounted on two small spacers. The battery can alternatively be held in place by glueing some sponge to the lid which when fitted, the sponge will compress and hold the battery in position.



drilled nearby to take the leadouts from the buzzer to the circuit board.

The two "loops" are connected to the circuitry by means of terminal blocks mounted on the side of the case. The interior layout can be arranged to suit one's requirements but enough room must of course be left to take the battery which, incidentally, can be stuck down using a small piece of doublesided foam strip.

Complete the construction of the module and check the wiring carefully. If satisfactory, the panel mounted controls can then be lettered as required to indicate their functions.

TESTING

Short out the n.c. terminal block connector with a short piece of wire, clip on the battery and switch on. Press S1; this will cause the buzzer to operate and D2 should also illuminate. Reset the circuit at S2 and short the n.o. loop connector—this again should also operate the alarm. The device is then complete and ready to be connected to the "loops".

If the device is to be used with the 9V Power Pack (to be described later in this series) then the battery clip will be omitted and a suitable con-

ductor used instead (e.g. a 3.5mm jack socket). However with a quiescent current of only 50 microamps, it might pay to try battery operation before building the power pack, to see if the battery power is feasible.

LOOPS AND SWITCHES

The alarm offers double loop protection but only a single loop can be used if desired. If the normally open version is chosen alone, then a permanent shorting link across TB2 is necessary.

The switches in the n.c. loop must have normally closed contacts and all be wired in series. In the n.o. loop, all the switches must have normally open contacts and be wired in parallel.

The constructor will have his own ideas regarding the type of switch to use but can be either miniature push-button, microswitch, reed/magnet, a pressure mat or home-made from brass strip or conductive tape.

For security reasons the switches and wires should be concealed. The framework between the hinges is a safe place to site the switches for doors and windows.

Next Month: 9V Power Supply.

The Adventures of Tanty Bead

By Matthew Reed




CMOS			
4001	13p	4020	50p
4002	13p	4022	50p
4007	13p	4023	13p
4009	30p	4024	40p
4011	13p	4026	90p
4012	13p	4027	28p
4013	28p	4028	45p
4015	50p	4029	50p
4016	28p	4030	45p
4017	47p	4040	55p
4018	55p	4041	55p
		4042	55p
		4043	50p
		4046	90p
		4049	25p
		4050	25p
		4060	30p
		4066	30p
		4068	13p
		4069	13p
		4070	13p
		4071	13p
		4072	13p
		4081	13p
		4093	36p
		4510	60p
		4511	60p
		4518	65p
		4520	60p
		4528	60p

FULL DETAILS IN CATALOGUE!

TTL			
7400	10p	7473	20p
7401	10p	7474	22p
7402	10p	7475	25p
7404	12p	7476	20p
7406	22p	7478	55p
7408	12p	7485	20p
7410	10p	7486	20p
7413	22p	7489	135p
7414	39p	7490	25p
7420	12p	7491	30p
7427	20p	7492	25p
7432	18p	7493	25p
7438	18p	7494	45p
7442	38p	7495	35p
7447	45p	7496	35p
7454	12p	7497	35p
		7498	50p
		7499	90p
		74141	55p
		74145	55p
		74148	90p
		74150	55p
		74151	40p
		74154	65p
		74157	40p
		74164	55p
		74170	100p
		74174	55p
		74177	50p
		74190	50p
		74191	50p
		74192	50p
		74193	50p
		74196	50p
		74197	50p
		74199	90p

OPTO			
LED's	0.125in.	0.2in	each 100+
Red	TIL209	TIL220	9p 7.5p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips	3p	3p	
DISPLAYS			
DL704	0.3 in CC		130p 120p
DL707	0.3 in CA		130p 120p
FND500	0.5 in CC		100p 80p

SKTS

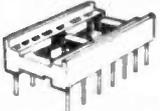

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

3 lead TO18 or TO5 socket. 10p each
Soldercon pins: 100:50p 1000:370p

PCBS			
Size in	0.1in	0.15in.	Vero
25 x 1	14p	14p	Cutter 80p.
2.5 x 3.75	45p	45p	
2.5 x 5	54p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 17	205p	185p	
Single sided pins per 100	40p	40p	
Top quality fibre glass copper board Single sided Size 203 x 95mm. 60p each			
'Data' pins 75p each			
Five mixed sheets of Alfac. 145p per pack			

RESISTORS			
Carbon film resistors. High stability, low noise 5%.			
E12 series. 4.7 ohms to 10M. Any mix:			
	each	100+	1000+
0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg. ohm (650 res) 0.5W £7.50 0.25W £5.70.			
METAL FILM RESISTORS			
Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix.			
	each	100+	1000+
0.25W	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.

LINEAR				
THIS IS ONLY A SELECTIDNI	LF356	80p	NE531	98p
	LM301AN	26p	NE555	23p
	LM308	60p	NE556	60p
	LM318N	75p	NE567	100p
	LM324	45p	RC4136	100p
709	35p	LM339	45p	SN76477
741	16p	LM378	230p	T8A800
747	45p	LM379S	410p	T8A810S
748	30p	LM380	75p	TDA1022
7106	850p	LM3900	50p	TL081
7107	900p	LM3909	65p	TL084
CA3046	55p	LM3911	100p	ZN414
CA3080	70p	MC1458	32p	ZN425E
CA3130	90p	MM57160	590p	ZN1034E

TRANSISTORS			
AC127	17p	8CY72	14p
AC128	16p	BD131	35p
AC176	18p	BD132	35p
AD161	38p	BD139	35p
AD162	38p	8D140	35p
BC107	8p	8FY50	15p
BC108	8p	8FY51	15p
BC108C	8p	8FY52	15p
BC109	8p	MJ2955	98p
BC109C	10p	MPSA06	20p
BC147	7p	MPSA56	20p
BC148	7p	TIP29C	60p
BC177	14p	TIP30C	70p
BC178	14p	TIP31C	65p
BC179	14p	TIP32C	80p
BC182	10p	TIP2955	65p
BC182L	10p	ZTX107	14p
BC184	10p	ZTX108	14p
BC184L	10p	ZTX300	16p
BC212	10p		
BC212L	10p		
BC214	10p		
BC214L	10p		
BC477	19p	1N914	3p
BC478	19p	1N4001	4p
BC548	10p	1N4002	4p
BCY70	14p	ITT Full spec product.	
BCY71	14p	1N4148	-£1.40/100 £11/1000
		1N4006	6p
		1N5401	13p
		8ZY88 ser.	8p

CAPACITORS			
TANTALUM BEAD			
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V			each
4.7, 6.8, 10uF @ 25V			8p
22 @ 16V, 47 @ 6V, 100 @ 3V			13p
			16p
MYLAR FILM			
0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1			3p
			4p
POLYESTER			
Multifar C280 series			
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1.0uF			5p
			7p
			10p
			14p
			17p
CERAMIC			
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF			
RADIAL LEAD ELECTROLYTIC			
63V 0.47 1.0 2.2 4.7 10			5p
		22 33 47	7p
			13p
		220	20p
25V 10 22 33 47			5p
		100	8p
		220	10p
		470	15p
		1000	23p

CONNECTORS			
JACK PLUGS AND SOCKETS			
	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p
DIN PLUGS AND SOCKETS			
	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p
1mm PLUGS AND SOCKETS			
Suitable for low voltage circuits, Red & black. Plugs 6p each Sockets 7p each			
4mm PLUGS AND SOCKETS			
Available in blue, black, green, brown, red, white and yellow Plugs 11p each Sockets 12p each			
PHONO PLUGS AND SOCKETS			
Insulated plug in red or black			9p
Screened plug			13p
Single socket			7p
Double socket			10p

STEVENSON

Electronic Components

SOLDERING IRONS


ANTEX X25 (25W) or ANTEX CX (17W) 390p each
Reel of solder (39.6M) 240p each

LOUDSPEAKERS

56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p
64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p
Magnetic earpiece including 2.5 or 3.5mm plug. 15p each
Crstal earpiece including 3.5mm plug. 30p each

SWITCHES

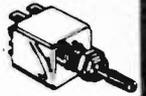Subminiature toggle. SPDT 70p. DPDT 80p.
Standard toggle. SPST 34p. DPDT 48p.



Slide switches (DPDT) miniature or standard 15p.
Push to make switch. 15p. Push to break switch. 20p.

Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow & black. 14p.



MISCELLANEOUS

Connection cable available in single or stranded packs of eight colours.

	Single	Stranded
8 metre pack	18p	18p
40 metre pack	85p	80p


BATTERY CLIPS

Battery clips for PP3 with lead. 6p each.
Battery clips for PP9 with lead. 10p each.
Miniature crocodile clips in red or black. 8p each.
Red or black probe clips. 20p each.



Murata Ultrasonic Transducers. 180p each. 350p pair.

PANEL METERS

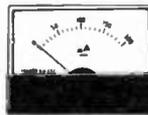

High quality 2" wide view meters.
Zero adjustment. Back illumination wiring.
Available in 50 uA, 100 uA, 500 uA, 1 mA, 100 mA, 500 mA, 1 A. £4.75 ea.
VU meter similar style. £1.40 ea.

SLIDE POTENTIOMETERS

Good quality 60mm travel slider with 80mm fixing centres.
Available from 5k - 500k in log and linear. 55p each.
Suitable black knobs 6p ea. Coloured knobs 10p ea.



We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



BARCLAYCARD & ACCESS WELCOME



Mail orders to: STEVENSON (Dept EE)

76 College Road, Bromley, Kent BR1 1DE.



ALL PRICES INCLUDE 15% V.A.T.

Everyday ELECTRONICS

VOLUME 8 INDEX

JANUARY 1979 TO DECEMBER 1979

Pages	Issue	Pages	Issue
1-64	January	393-464	July
65-128	February	465-536	August
129-192	March	537-608	September
193-256	April	609-688	October
257-320	May	689-768	November
321-392	June	769-848	December

CONSTRUCTIONAL FEATURES

ALARM, BABY	735	8—Meter Amplifier	354
ALARM, BURGLAR	824	9—Voltage Splitter	410
ALARM, INTRUDER	266	10—Swanee Whistler	482
ALARM, LIGHTS REMINDER	48, 626	11—Low Power Audio Amplifier	556
ALARM, OPTO	712	12—Universal Oscillator	654
ALARM, TOUCH BLEEPER	206	MODEL CONTROL	724
AMPLIFIER, EE2020 TUNER	35, 100, 164, 238, 306, 493	MODULATED TONE GENERATOR by R. A. Penfold	803
AMPLIFIER, LOW POWER AUDIO	556	MW & LW RADIO TUNER by F. G. Rayer	707
AMPLIFIER, METER	354		
		NICKEL CADMIUM BATTERY MONITOR by A. J. Adamson	586, 730
BABY ALARM by E. M. Lyndsell	735	NIGHTLIGHT	786
BATTERY MONITOR, NICKEL CADMIUM	586, 730		
BELL, LIGHT PLUS	515	ONE ARMED BANDIT by K. A. Hutchin	620
BIT SAVER, SOLDERING IRON	414	ONE TRANSISTOR RADIO by F. G. Rayer	716
BLEEPER, TOUCH	206	OPTO LARM	142
BURGLAR ALARM	824		
		PEG-A-HOLE GAME by F. G. Rayer	784
CANARY, ELECTRONIC	334	PHOTOGRAPHIC SOLUTIONS THERMOSTAT	294
CANDLE, EVERLASTING	786	PILOT LIGHT, TOUCH-ON	510
CAR CHOKE WARNING DEVICE	233	POCKET RADIO by J. Herron	366, 526
CAR DIRECTION INDICATOR by B. Hamill	138	POWER SUPPLY, GENERAL PURPOSE	93
CAR LIGHTS REMINDER	48, 626	POWER SUPPLY, VERSATILE	157
CAR SHAVAR INVERTER	202	POWER SUPPLY, 9V	479
CAR TRAILER FLASHER	500		
CHASER LIGHTS by J. R. W. Barnes	572	QUAD SIMULATOR by B. York	371
CHOKE WARNING DEVICE by T. R. de Vaux-Balbirnie	233	QUIZ REFEREE by A. P. Donleavy	516
CONFERENCE TIMER by A. J. Bassett	404		
CONTINUITY TESTER	24	RADIO CONTROL SYSTEM, EE	
CONVERTOR, LONG WAVE	74	by L. Armstrong, H. Dickinson, W. Wilkinson	724, 806
		RADIO, LONG WAVE CONVERTOR	74
DARKROOM TIMER by A. R. Winstanley	422	RADIO, ONE TRANSISTOR	146
DICE, ELECTRONIC	272, 439	RADIO, POCKET	366, 526
DOLLS HOUSE LIGHTS ECONOMISER by H. Clough	424	RADIO, SHORT WAVE CONVERTOR	288
DOORBELL, MICROCHIME	77	RADIO TUNER, MW & LW	707
		RADIO, VARICAP MW	548
ELECTRONIC CANARY by F. G. Rayer	334	REFEREE, QUIZ	516
ELECTRONIC DICE by P. Leah	272, 439	ROULETTE	10, 107
ELECTRONIC TUNING FORK by R. A. Penfold	490		
EVERLASTING CANDLE by A. Sproston	786	SHAVAR INVERTER by D. S. Gibbs & I. M. Shaw	202
		SHORT WAVE CONVERTOR by R. A. Penfold	288
FLASHER, TRAILER	500	SIGNAL LEVEL INDICATOR by P. W. Bond	646
		SIMPLE TRANSISTOR TESTER by D. J. Edwards	553
GENERAL PURPOSE POWER SUPPLY by F. G. Rayer	93	SINE WAVE GENERATOR	700
GENERATOR, MODULATED TONE	803	SNAP	18
GENERATOR, 3-FUNCTION	700	SOLDERING IRON BIT SAVER by R. A. Penfold	414
GUITAR TREMOLO UNIT	330	SOLID STATE ROULETTE by E. M. Lyndsell	10, 107
		SOUND ADAPTOR, TREASURE HUNTER	113
HEADPHONE ENHANCER by R. A. Penfold	43	SQUARE WAVE GENERATOR	700
HIGH IMPEDANCE VOLTMETER by R. A. Penfold	642	STAR, TWINKLING	788
I'M FIRST by F. G. Rayer	18	THERMOSTAT for PHOTOGRAPHIC SOLUTIONS	
INDICATOR, CAR DIRECTION	138	by R. A. Penfold	294
INDICATOR, SIGNAL LEVEL	646	THYRISTOR TESTER by P. C. O'Neil	108
INDICATOR, TIME DELAY	143	TIME DELAY INDICATOR by A. R. Winstanley	143
INDICATOR, WATER LEVEL	442	TIMER, CONFERENCE	404
INTRUDER ALARM by F. G. Rayer	266	TIMER, DARKROOM	422
INVERTER, SHAVAR	202	TIMER, WARBLING	474
		TOUCH BLEEPER by T. J. Herklots	206
LABCENTRE, EE by R. W. Coles & B. Cullen	151, 215, 280, 344	TOUCH-ON PILOT LIGHT by F. G. Rayer	510
LIGHTCALL by T. R. de Vaux-Balbirnie	797	TRAILER FLASHER by J. Boxham	500
LIGHT, CHASER	572	TRANSISTOR TESTER	220, 553
LIGHT PLUS BELL by S. Vaughan	515	TRANSMITTER, EE RADIO CONTROL	724, 806
LIGHT, TOUCH-ON PILOT	510	TREASURE HUNTER SOUND ADAPTOR by N. Hunter	113
LIGHTS ECONOMISER, DOLLS HOUSE	424	TREMOLO UNIT by E. M. Lyndsell	330
LIGHTS-ON REMINDER by T. R. de Vaux-Balbirnie	626	TRIANGLE WAVE GENERATOR	700
LIGHTS REMINDER by P. J. Tyrrell	48	TUNER AMPLIFIER, EE2020	35, 100, 164, 238, 306, 439
LONG WAVE CONVERTOR FOR 4 by F. G. Rayer	74	TUNER, MW & LW RADIO	707
LOUDSPEAKER, EE20, EE70 by R. F. Stephens	427, 563	TUNING FORK, ELECTRONIC	490
LOW COST METAL LOCATOR by R. A. Penfold	348, 526	TUTOR DECK, EE by S. Lewis, B.Sc.	631
LW & MW RADIO TUNER	707	TWINKLING STAR, by E. M. Lyndsell	788
METAL LOCATOR, LOW COST	348, 526	UNIBOARDS by A. F. Winstanley	712, 824
MICROCHIME, EE by Robin Palmer	77	1—Opto Alarm	712
MINI-MODULES by George Hylton	24, 86, 157, 220, 354, 410, 482, 556, 654	2—Burglar Alarm	824
		VARICAP MW RADIO by R. A. Penfold	548
4—Continuity Tester	24	VOLTAGE SPLITTER	410
5—Audio Modulators	86	VOLTMETER, HIGH IMPEDANCE	642
6—Versatile Power Supply	157		
7—Transistor Tester	220		

WARBLING TIMER by O. N. Bishop	474	3-FUNCTION GENERATOR by F. C. Judd	700
WATER LEVEL INDICATOR		9V POWER SUPPLY by S. V. Essex	479
by H. W. Gleaves & S. F. Gregory	442	24-TUNE DOORBELL	77
WHISTLER, SWANEE	482	2020 TUNER AMPLIFIER, EE by E. A. Rule	35, 100, 164, 238, 306, 439

GENERAL FEATURES

BOOK REVIEWS	117, 184, 270	Low Cost Metal Locator June 1979	526
BREADBOARD '78 REVIEW Terry Johnson	89	Nickel Cadmium Battery Monitor September 1979	730
BRIGHT IDEAS 46, 107, 116, 489, 495, 650, 710, 738, 782		Pocket Radio June 1979	526
Button Stop	738	Solid State Roulette January 1979	107
Component Breadboarding	495	Treasure Hunter October 1978	46
Component Holder	489		
Crocodile Clips	495	RADIO WORLD by Pat Hawker	53, 104, 177, 245, 312, 361, 434, 508, 585, 665, 740, 749, 814
Heatsink	46	Older by the year, No waves in ESP, Paying for TV	
I.C. Socket	710	Next Steps, Australian novices	53
PCB Alternative	107	Air traffic control, Broadcast receivers, Hair-pins and h.f. radio, Sunspots and weather	104
PCB Holder	650	Stereo on medium waves, URP's abound, Packet switching	177
Photodetector	738	Balanced level, Exorcising TV ghosts, Amateurs in space, World at their Fingertips	245
Plastic Circuit Cover	116	Losing the lead, Not so easy, Working the stars	312
Plug and Socket	46	One station listening, Saturday's private army, Contacts	361
Rawplug Post	116	Broadcasting and s.w., H.F. stations, amateur stations	434
Scales from Scratch	650	Whispering gallery, Carfax, Cow and Pig Power	508
Spacer and Holder	107	CB band-wagon, Geneva plan, Super sets, Coloured sounds	585
Storage Bags	495	WARC 1979, Morse and the novice, CB and amateurs	665
Third Hand Heatsink	489	Amateur news service, Radiation non-hazards, Why so slow	749
Toothpaste Terminals	495	Safety first, h.f. receivers, examinations	814
Track Cleaner	107		
Wine Cork Knob	116		
CB for UK? by F. C. Judd	593		
COMPETITION RESULTS	184, 555		
CROSSWORD by D. P. Newton 41, 107, 150, 230, 287, 336, 444, 478, 594, 625, 706, 793		RUMMAGING AROUND by Keith Cadbury	310, 364, 446, 524, 582, 658, 745
COUNTER INTELLIGENCE by Paul Young 45, 92, 142, 230, 282, 342, 453, 503, 571, 675, 723, 802		READERS LETTERS	494, 599, 666, 730
DIGITAL RECORDING by Adrain Hope	671	SHOP TALK by Dave Barrington	34, 92, 144, 236, 287, 333, 426, 499, 590, 630, 742
EDITORIAL	8, 72, 136, 200, 264, 328, 402, 472, 546, 618, 698, 778	SPECIAL REPORT	174, 377
EVERYDAY NEWS	32, 98, 172, 228, 292, 362, 432, 506, 580, 652, 732, 812	Denshi-Gakken Kits	174
JACK PLUG AND FAMILY by Doug Baker	34, 97, 163, 212, 279, 373, 431, 522, 587, 730, 798	Connoisseur Package Deal	377
MAKING PRINTED CIRCUIT BOARDS by E. M. Lyndsell	82	TANTY BEAD by Matthew Reed	710, 826
MINI MODULES IN COMBINATION by George Hylton	353	VIDEO REVOLUTION by Adrian Hope	496
PLEASE TAKE NOTE	46, 107, 439, 526, 730	XMAS BRIGHT IDEAS by E. M. Lyndsell	782
EE2020 Tuner Amplifier December to May 1979	439	XMAS LIGHTS WITHOUT TEARS by T. R. de Vaux-Balbirnie	780
Electronic Dice May 1979	439		

SPECIAL SERIES

DOING IT DIGITALLY by O. N. Bishop	20, 82, 180, 208, 276, 338, 418, 484, 558	PROFESSOR ERNEST EVERSURE by A. J. Bassett	54, 118, 246, 302, 381, 450, 525, 597, 673, 818
4—Counting with flip-flops	20	Valve amplifier output stages	54
5—Counting and the binary system (7490)	82	In-circuit valve tester	118
6—Digital counting and displays	180	Vacuum chamber	246
7—Modules and systems	208	Vacuum chamber experiments	302
8—Timing systems with the 555	276	Electron beam	381
9—Problem solving and games with TTL	338	Properties of energy beams	450
10—Interfacing to alarm systems	418	Wah Wah	525
11—Binary addition and subtraction	484	Spring line reverb	597, 673
12—Parallel addition and analogue/digital sensing	558	Fuzz Circuits	818
DOWN TO EARTH by George Hylton	120, 159	SQUARE ONE	26, 88, 145, 222, 283, 378, 449, 504, 588, 660, 711
Pot's Law—logarithmic and linear	120	Resistors and Capacitors	26
Sidebands and carriers	159	Electrolytic and Tantalum Capacitors	88
FOR YOUR ENTERTAINMENT by Adrian Hope	17, 85, 213, 271, 337, 412, 578, 662, 746, 790	Using Stripboard	145
Digital Sound and Curious Sensation	17	Resistor and Capacitor Codes	222
Computers	85	The Transistor	283
Radio Dentist, Teletext and Prestel	178	Component Coding	378
Keys of the Future	213	Guide to Circuit Symbols	449
Audio Reviewing	271	Soldering	504
Sound, Speech and Translating	337	Putting together a project	588
Armstrong's Radio Patents	412	Stripboard	660
Bugging, Double Exposure and Off the Record	578	Diodes	711
Interference, power and time piece	662	SYNTHESISERS EXPLAINED by B. H. Bailly	720
Wireless Act, Take-away Radio, War on CB	746	1—Introduction	720
Choosing a Video Game	790	TEACH-IN 80 by S. Lewis, B.Sc.	637, 714, 794
MICROPROCESSOR BASICS by R. W. Coles & B. Cullen	160, 223, 284, 356, 436, 521, 568	1—Introduction	637
1—Introduction	160	2—Conductors, insulators and resistors	714
2—Microprocessor chip	223	3—Calculating currents in resistive networks	794
3—ROMS, PROMS, EPROMS, and RAMS	284	WORKSHOP MATTERS by Harry T. Kitchen	374, 441, 512, 669, 751
4—ROMS, UART and Build Your Own ROM	356	Organising the workshop and component buying	374
5—Programming a microprocessor chip	436	Choosing a Multimeter	441
6—Programming a microprocessor chip cont.	521	Metal Working	512, 669
7—Guide to choosing a home computer	568	Marking out, cutting and bending	751
		Finishing off	822


SPECIAL INSERTS AND OFFERS

STRIPBOARD	March 1979	CONSTRUCTORS DATA 24 page booklet	October 1979
ANTEX SOLDERING COMPETITION	April 1979	SOLAR POWERED DIGITAL WRISTWATCH (Special Offer)	November 1979
SCREWDRIVER	May 1979		



TUAC

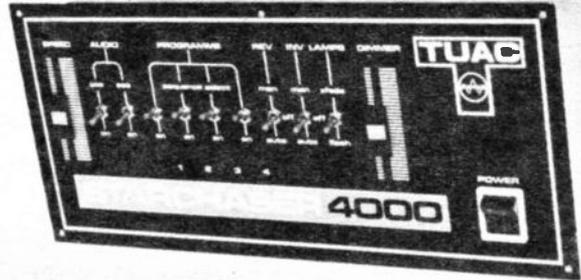TRANSISTOR UNIVERSAL
AMPLIFICATION CO LTD
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY
AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS



HERE ARE JUST A FEW OF THE 1000 REASONS

which makes the Starchaser 4000 the finest 4 channel lighting unit available anywhere. *4 channels 750W each *over 1000 different sequence patterns and effects *3 alternative sound triggers *A.G.C. *simulated strobing *zero reference triac firing *superb TUAC quality and reliability..... **£99.00 inc. VAT.** Move into the 80's today by sending for further details to: TUAC Ltd., 119 Charlmont Road, S.W.17. Tel: 01-672 3137/9080.

TUAC Main Distributors (Callers Only)


A1 Music, 88 Oxford Street, Manchester (Tel: 236 0340). Cookies Disco Centre, 126/128 West Street, Crewe (Tel: 4739). Electra Centre, 58 Lancaster Road, Preston (Tel: 58488). Electrosure, Fore Street, Exeter (Tel: 56687). Garland Bros., Deptford Broadway, London (Tel: 01-692 4412). George Matthews, 85/87 Hurst Street, Birmingham (Tel: 622 1941). Luton Disco Centre, 88 Wellington Street, Luton (Tel: 411733). Memhouse, 82 St. Mary Street, Southampton (Tel: 28028). Salscoglen, 43 Borough Road, Middlesborough (Tel: 242851). Socodi, 9 The Friars, Canterbury (Tel: 60948). Session Music, 163 Mitcham Road, Tooting, London (01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE

Electronics Make a job~or hobby~of it.....

The opportunities in electronics, today, and for the future are limitless - throughout the world - jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics - especially for the servicing of radio, T.V. and all associated equipment - can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on the world market.

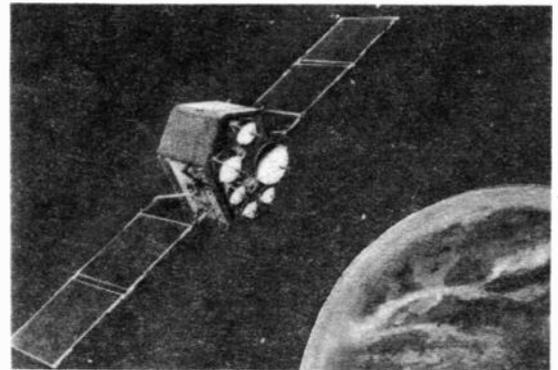We give modern training courses in all fields of electronics - practical D.I.Y. courses - courses for City and Guild exams, the Radio Amateur Licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years of experience in the subject. - Details sent without any obligation from . . .



Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

EEB/1/80 Block caps please

Hand held COMPUTER GAMES

We have selected the best available
It's you against the computer!

GRANDSTAND 4-in-1
Calculator/Auto Race/Code
Breaker (as Mastermind)/
Blackjack.
Convenience—skill—
brainpower—luck
£22.50



UFO MASTER BLASTER STATION
More sophisticated than Destroyer. Guide
missiles to destroy UFO's which may change
course or disappear!
£22.50

AMAZE-A-TRON
Over 1 million mazes to defeat! 1 or 2 players.
Electronic sound effects.
£17.25

GRANDSTAND DESTROYER
Protect your convoy from torpedoes.
£14.75

GRANDSTAND SOLITAIRE
Absorbing and challenging.
£14.75

DIGITS (As Mastermind)
Deduce four random numbers
£13.95

MICROPROCESSORS

FAIRCHILD GRANDSTAND
Video Entertainment Computer
£74.95



19 plug-in pre-programmed memory cart-
ridges now available. **Each £12.50**

NEW SCIENTIFICS With non-volatile memory



CASIO FX-2600
Ultra slim—
5/32 inch
6 + 2 digits LC Display.
43 sci functions. Auto
power off with memory
retention. 6 level (.)
SD, R to P, P to R, Eng.,
FIX, SCI, RND and
Random number keys.
5/32 x 2 1/4 x 4 1/4 in.
£19.95



CASIO FX-3200
10 digit version.
£21.95

CASIO FX-310
Similar to FX-2600 but
50 sci funct. 1/4 x 2 1/4 x 5 1/4
£17.95

CASIO FX-510
10 digit version.
£19.95

FROM CASIO — THE NEXT STEP FORWARD IN TIME

Casio's new Lithium battery lasting 5 years, totally eclipses most Solar watches
Have a fabulous time this Christmas—from TEMPUS

From CASIO's New Collection we present
some of the most sophisticated executive
watches available today.

ALARM CHRONOGRAPHS

Displaying hours, minutes, seconds, date,
am/pm; or hours, minutes, alpha day, date,
am/pm. With automatic 28, 30, 31 day
calendar.

83QS-27B
4 YEAR BATTERY.

1/10 second chrono to
12 hrs., measuring net,
lap and 1st & 2nd place
times. 24 hour alarm.
Hourly chimes. Backlight.
Mineral glass. Stainless steel
encased. Water resistant
to 66 feet.
(£31.95)
£27.95



Displaying hours, minutes, seconds with
day, date, month and year automatic calendar.



81QS-33B
(Available soon)
5 YEAR BATTERY
Chrome plated case
WR to 66 feet
(£31.95)
£27.95

1/100 second chrono
to 7 hours.
Net, lap and 1st
& 2nd place.
Selectable 12 or
24 hour display.

24 hour alarm.
Selectable hourly chime
facility. Backlight.
Mineral glass face.



81CS-36B
As above but:
Stainless steel case,
WR to 100 feet
(£39.95)
£35.95

HONG KONG WATCHES

Most low cost digital watches come from
Hong Kong. In our experience these are
proving unreliable, particularly those with
multi-function modules, with very high
failure rates. Repairs can take as long as
three months and replacement parts are
not always available, even replacement
plastic glasses!
Compare this with Casio, Citizen and Seiko,
whose failure rate is typically under 1%.
Casio's service time of 2-3 weeks and com-
prehensive stock of spares and we ask you:

**ISN'T IT WORTH PAYING A LITTLE
MORE FOR QUALITY AND
RELIABILITY?**

Fully guaranteed for 12 months

Most CASIO products available from
stock. Send 25p for illustrated brochures
and membership of our CHRISTMAS
CLUB. EXTRA DISCOUNTS on many
items.

CASIO CHRONOGRAPHS

Constant LC Display of hours, minutes,
seconds, am/pm and day, (12 or 24 hour).
Dual time (12 or 24 hour). Automatic day,
date, month and year calendar. Chronograph
measures net, lap and 1st, 2nd place times
from 1/100 second to 7 hours. Backlight
Mineral glass face. Guaranteed water re-
sistant to 66 or 100 feet.

NEW MODEL
95QS-32B

4 YEAR BATTERY
Superbly styled brass
case heavily chrome
plated. Water Resistant
to 66 feet.
(RRP £27.95)
£23.95



95QS-31B (left)
4 YR BATTERY
S/Steel jacket
WR to 66 feet
(£27.95)
£23.95



95CS-31B (right)
5 YR BATTERY
Solid S/S case
WR to 100 feet
(£34.95)
£29.95

F-200 SPORTS CHRONO

Hours, minutes, seconds,
am/pm. Day, date, month.
1/100 sec. chrono to 1 hr.
Net, lap and 1st and 2nd
place times. Backlight.
Resin case/strap. Mineral
glass. WR to 66 feet.
Silver oxide battery.
(£17.95)
£15.95



F-8C Time/date
3 YEAR BATTERY
Hours, minutes, seconds,
date, day, am/pm. Auto
28, 30, 31 day calendar
Backlight. Resin case/
strap. Mineral glass
WR to 66ft (£12.95)
£10.95

LADIES MODELS (Others available)

Hours, mins, 10 seconds, am/pm. Automatic
calendar. Stainless steel, mineral glass,
WR to 100 feet.



£26.50

£31.95


£37.25

Price includes VAT, P&P. Send your
cheque, P.O. or phone your ACCESS or
B*CARD number to:—

TEMPUS

Dept. EE, Beaumont Centre, 164-167 East
Rd., Cambridge CB1 1DB. Tel. 0223 312866

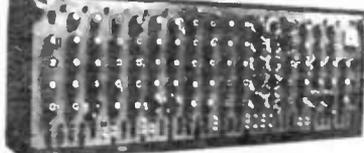KITS FOR SOUND EFFECTS AND OTHER PROJECTS



PHONOSONICS

DEPT EE9D, 22 HIGH STREET,
SIDCUP, KENT DA14 6EH



MAIL ORDER SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND COMPONENTS TO
A WORLD-WIDE MARKET.

P.E. GUITAR EFFECTS PEDAL

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls. Basic parts with foot switches KIT 42-1 £8-45
Basic parts with panel switches KIT 42-2 £5-55
PCB & layout chart PCB 42A £1-57
Text photocopy £28

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit including variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Can be used with other electronic instruments. Set of basic components KIT 56-1 £7-57
PCB & layout chart PCB 56A £1-78
Text photocopy £68

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit. Set of basic components, PCB & chart KIT 74-1 £4-97
Text photocopy £39

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration. Basic comps, foot switches, PCB & chart KIT 75-1 £5-64
Basic comps, panel switches, PCB & chart KIT 75-2 £4-08
Text photocopy £38

P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control. Set of basic components, PCB & chart KIT 51-1 £3-99

P.E. AUTO-WAH UNIT

Automatically Wah or Swell sounds with each note played. Basic comps, foot switches, PCB & chart KIT 58-1 £8-43
Basic comps, panel switches, PCB & chart KIT 58-2 £5-31
Text photocopy £58

P.E. THREE-CHANNEL SOUND-TO-LIGHT

A simple sound-to-light controller. Set of basic components, PCB & chart KIT 52-1 £14-16
Text photocopy £24

P.E. PHASER

An automatic 6-stage phasing unit with integrator/oscillator. Set of basic comps, PCB & chart KIT 88-1 £10-14
Text photocopy £58

ELECKOR PHASING & VIBRATO UNIT

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage. Set of basic components KIT 70-1 £19-11
PCB & layout chart KIT 70A £2-56
Text photocopy £67

P.E. PHASING UNIT

A simple but effective manually controlled phasing unit. Set of basic comps PCB & chart KIT 25-1 £3-52
Text photocopy £28

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses. Set of basic components, PCB & chart KIT 89-1 £3-82
Text photocopy £78

P.E. SMOOTH FUZZ

Set of basic components, PCB & chart KIT 91-1 £5-01

TREMOLO UNIT

A slightly modified version of the simple P.E. unit. Set of basic components, PCB & chart KIT 54-1 £3-23

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit. Set of basic components, PCB & chart KIT 28-1 £4-68
Text photocopy £28

P.E. MICROPHONE PRE-AMP

Includes preset gain-control to match most microphones. base roll-off, treble lift, master gain control. Set of basic components, PCB & chart KIT 61-1 £4-20

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments. Set of basic comps, PCB & chart KIT 46-1 £16-42
Power Supply comps, PCB & chart KIT 46-2 £6-90
Text photocopy £97

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesizers and other Instruments where the full versatility of KIT 46 is not required. Basic comps, PCB & chart, but excl sw. KIT 69-1 £8-19
Text photocopy £58

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels. Set of basic components, PCB & chart KIT 62-1 £5-03

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 5-digit counter for 1Hz to 99KHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking. Set of basic components KIT 79-1 £26-45
PCB (as published) PCB 79A £3-33
Text photocopy £78

TAPE NOISE LIMITER

Effectively reduces tape-recording hiss. Set of basic components, PCB & chart KIT 6-3 £4-13
Power Supply comps, PCB & chart KIT 6-2 £5-15
Text photocopy £19

P.E. DISCOSTROBE

4-channel sound-to-light controller also giving sequential, random or strobe modes of control. Set of basic components KIT 57-1 £20-00
PCB & layout chart PCB 57A £3-79
Text photocopy £78

MANY MORE KITS

for synthesizers, Rhythm Generators, Electronic Pianos and other projects, big, small, simple or complex, are available, plus a range of keyboards, separate components and accessories. Details in our lists.

COMPONENT SETS Incl all necessary res, caps, s/cs, pots, t/ormers. Hardware such as cases, skts, knobs, kbds, etc, are not incl, but most can be bought separately. Fuller details in lists.

ADD: POST & HANDLING
U.K. orders; under £5 add 25p, under £20 add 50p, over £20 add 75p. Recommended insurances against postal mishaps; add

50p for cover up to £50, £1 for £100 cover, etc., pro-rata, must be added to credit card orders. N.B. Eire, C.L., B.F.P.O. and other countries are subject to higher rates.

ADD 15% VAT
(or current rate if changed). Must be added to full total of goods, post & handling on all U.K. orders. Does not apply to exports.

LIST: Send stamped addressed envelope

with all U.K. requests for free list giving fuller details of our goods. Europe send 25p, other countries send 50p, or equivalent in international reply coupons

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT
(TEL: 01-302 8184)



TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course—or refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

- Courses in
- C & G Elect. Technicians
 - C & G Elect. Installations
 - Telecomms. Technicians Exams
 - Television Servicing
 - Radio Maint. & Repairs (BIET)
 - Pract. Radio & Electronics
 - Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY


Aldermaston Court, Dept. TEE50 Reading RG7 4PF.

NAME (Block capitals please) _____
ADDRESS _____
POSTCODE _____

Other Subjects _____ AGE _____
Accredited by ACC Member of ABCC

AT BREADBOARD '79 ALCON PRESENT THE BIGGEST RANGE OF MULTIMETERS

and the new AMAZING MINI 20

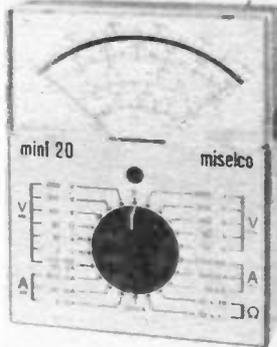

a complete pocket
multimeter at
only £27.37 incl VAT.

PLUS MANY OTHER INCREDIBLE BARGAINS!!
SEE YOU AT STAND C8

For details of this and other exciting Alcon instruments please write or phone:

ALCON Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL. 01-352 1897 · TELE X. 918867

7 HUGHENDEN ROAD, HASTINGS, SUSSEX. TN34 3TG

Telephone: HASTINGS (0424) 436004



**UK567
LOGIC CIRCUIT
TEST PROBE**

A very handy device for checking the state of Logic Circuits, red & green state indicators.
Power supply = 5 V.D.C.
O/C Current = 10 M/A
Under Load Current = 80 M/A
Dia. = 25mm 100mm
Price £5.57 inc. VAT. P & P 50p.



ELECTRONIC KITS



**UK108
F.M.**


MICROTRANSMITTER

This simple and efficient transmitter has many diverse uses, amongst which: as a radio microphone, baby alarm etc. The range is approx. 300 metres max. Complete with high sensitivity dynamic microphone and telescopic antenna.
Supply 9V D.C.
Frequency range = 88-108MHz
Transistors = BC208-B-2N708
Size = 92 x 60 x 35mm
Weight = 130GM
£10.05 inc. VAT. Post & packing 50p
Not licencable in the UK export only



**UK406
PORTABLE
SIGNAL TRACER**

This is a very useful instrument for tracing faults in radio's, television's & audio amplifiers. This device has a R.F. Probe & low frequency input.
Frequency range = 100HZ = 500MHz
R. F. Probe Sensitivity = 10mV
A. F. Sensitivity = 3mV-3V
Transistors = 2 x BC209-B
Integrated Circuit = TAA611
Diode = AA119
FET = 2N3619
Powered from internal 9V D.C. battery
£25.62 inc. VAT. Post & packing 75p.

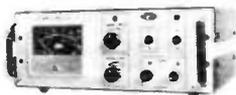

**UK677
VARIABLE
STABILIZED POWER
SUPPLY**

0-20V D.C. at 2.5 amps
With current limiting control
Short circuit proof
Metering for voltage & current
Mains Voltage 115-220-250V
AC 50-60HZ
Load Regulation = 0.15%
Max Ripple < 1mV
Transistors = 2N3055-BD138-BC160-BC307B
Diodes = 5 x 1N5401
Zener Diodes = BZY88 C8V2
Integrated Circuit = LN723-C
Dimensions = 235 x 90 x 190mm
£44.54 inc. VAT. Post & packing £1.00



**UK562
TRANSISTOR &
DIODE TESTER**

This handy device allows a quick and easily read check of the condition of diodes and NPN & PNP transistors.
Powered by internal 4.5V battery
Base current = 10-100 UA
Parameter measured = B (Beta)
Dimensions = 85 x 145 x 55mm
Price £17.16 inc. VAT. P & P 75p



**UK233
AUTOMOBILE
ANTENNA
AMPLIFIER**

This unit very much increases the sensitivity of any car radio and improves stereo reception on VHF. It also compensates for mismatching due to extra capacitance in a long antenna cable.
Supply 12V D.C. negative earth
Gain = L.W. = 11-12db M.W.
S.W. = 15-18db VHF = 88-108MHz 14-15dB
Current Drain = 6mA
Transistor BF273
Kit £6.47 inc. VAT
Wired & tested £7.38 inc. VAT.
Post & packing 50p.



**UK232
AM-FM ANTENNA
AMPLIFIER**

This unit increases the sensitivity of any radio over a wide range of frequencies. Including amplitude and frequency modulation broadcast. In a simple and economical way using a compact unit that is easy to install.
Supply 12V D.C.
Gain = AM (LM/MW/SW) 25dB
FM 88-108 MHz 75 ohm 15dB
Current Drain = 6mA
Transistor BF273
Kit £5.69 inc. VAT.
Wired & tested £6.96 inc. VAT.
Post & packing 50p.

FOR CATALOGUE OF COMPLETE RANGE OF KITS AND METAL CABINETS PLEASE SEND S.A.E. TRADE AND EXPORT ENQUIRIES WELCOMED

DO YOU EVER WISH YOU HAD A FEW MORE HANDS?

YOU KNOW WHAT ITS LIKE WHEN YOU'RE ABOUT TO START THAT NEW PROJECT - ARMED WITH A NICELY HOT SOLDERING IRON IN ONE HAND, THE SOLDER IN THE OTHER, YOU SUDDENLY FIND YOU'VE NO HANDS LEFT TO HOLD THE CIRCUIT BOARD AND COMPONENT, LET ALONE THE HEAT SINK.




Experience a new freedom with

THE MINIBENCH*

A twist of the clamping control nut and the Board is held securely. The jaws can then be flipped across so that either side of the board is accessible at will. Flexible arms terminating in crocodile clips hold components and in addition an arm can be provided to hold a magnifying lens to reduce the strain on those valuable eyes of yours.
Provision is made for the fitting of up to four flexible arms if required.

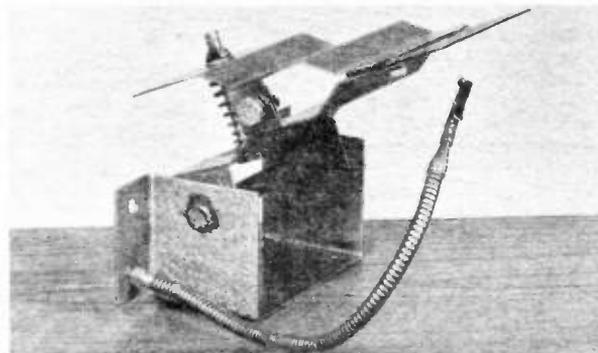ALL DESIGNED TO ENABLE YOU TO DERIVE GREATER PLEASURE FROM YOUR HOBBY.



* Trade Mark

Patent Applied For

- Please supplyMinibench @ £12.95 each
- Flexible Arms with clips..... @ £ 3.75 each
- Flexible Arms with Lens..... @ £ 5.25 each
- Postage and Packing £ 1.00


Cheque/Postal Order enclosed for £.....

POST COUPON TODAY TO-
Messrs. ABSONGLEN LIMITED, THE FORGE.
STAPLOW COTTAGE, STAPLOW,
LEDBURY, HEREFORDSHIRE HR8 1NP

Name.....
Address.....
.....
.....
Postal Code.....

Simply ahead . .

ILP'S NEW GENERATION OF HIGH

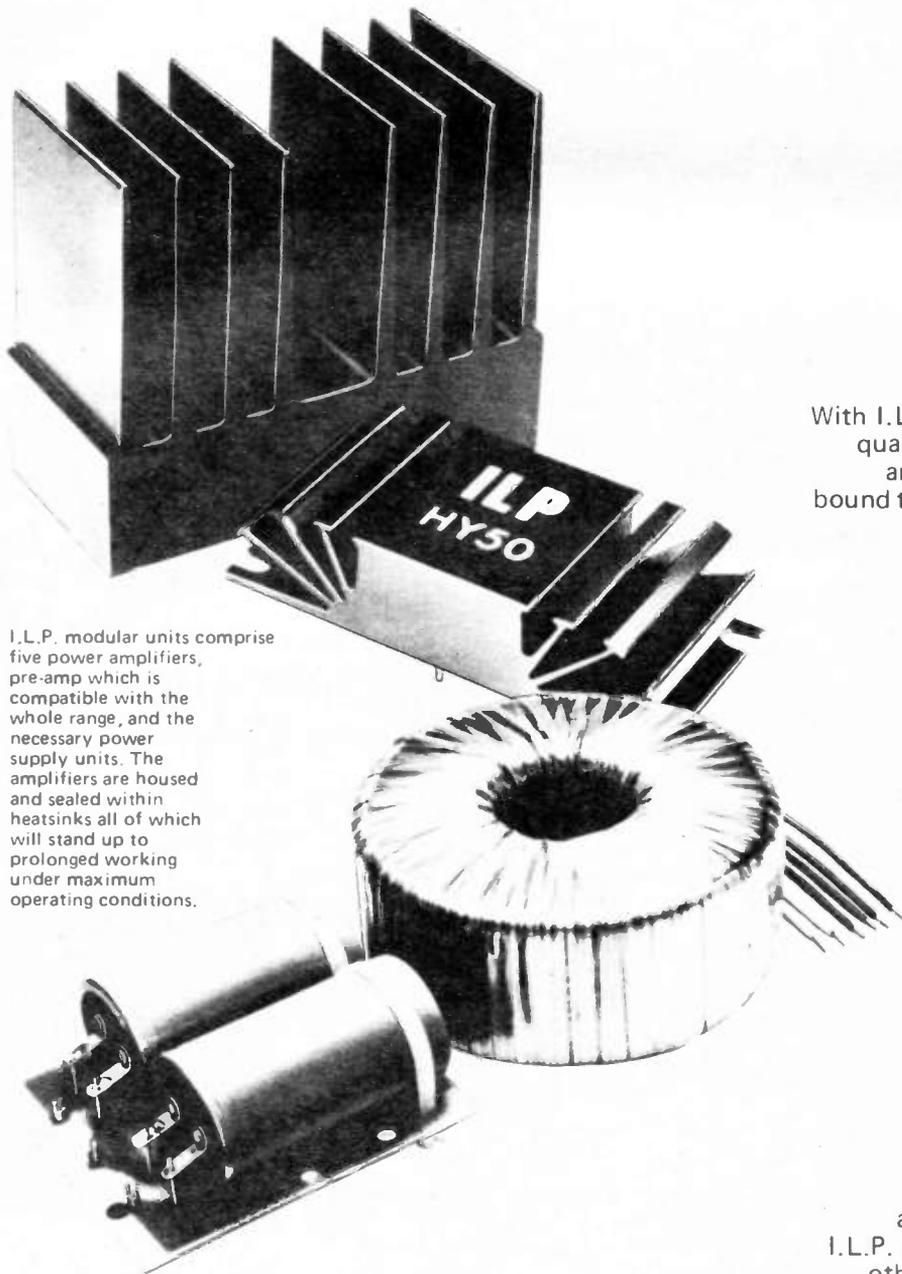

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.



With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance — and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain — the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.

**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

and staying there

PERFORMANCE MODULAR UNITS


HY5 PRE-AMPLIFIER

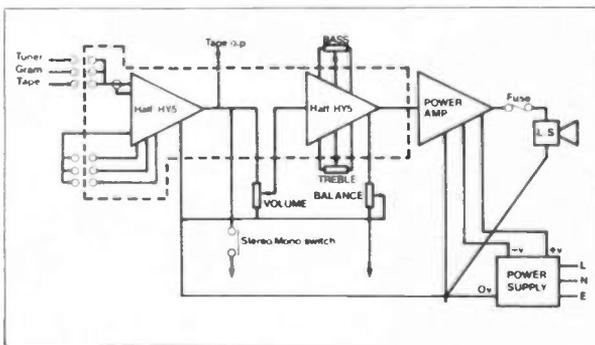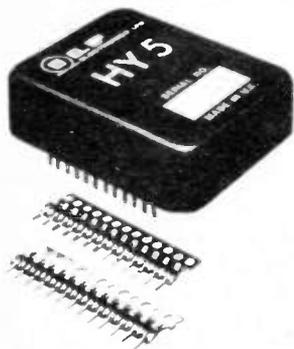

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm. and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz—0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

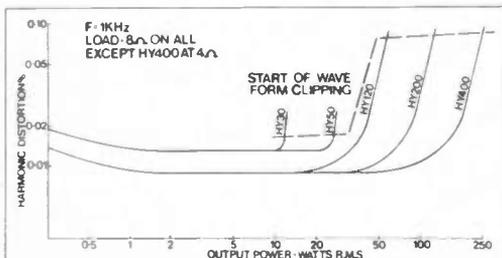

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/ Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0 +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0 +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0 +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0 +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0 +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance — all models 4 - 16 Ω
 Input sensitivity — all models 500 mV
 Input impedance — all models 100 KΩ
 Frequency response — all models 10Hz - 45KHz - 3dB

THE POWER SUPPLY UNITS

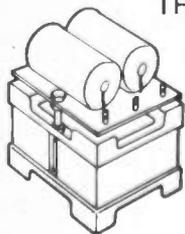

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms—one with circuit panel mounted on conventionally styled transformer the other with toroidal transformer having half the weight and height of its conventional laminated types.

PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT
PSU 30	± 15V at 100ma to drive up to five HY5 pre-amps	£4.50 + 68p VAT

**NO QUIBBLE
 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 BUILT-IN PROTECTIVE CIRCUITRY
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE
 — see below**

ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope — we pay postage on all letters sent to us by readers of this journal.



I.L.P.

ELECTRONICS LTD.

FREEPOST 3 Graham Bell House, Roper Close,
 Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 Telex 905780

Please supply

..... Total purchase price £.....

I enclose Cheque Postal Orders International Money Order

Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature

ELECTRONIC BOOKS

Ref.	Title	Price
126	BOYS BOOK OF CRYSTAL SETS	25p
900	HAND BOOK OF PRACTICAL ELECTRONIC MUSICAL NOVELTIES	50p
202	HANDBOOK OF IC EQUIVALENTS AND SUBSTITUTES	100p
207	PRACTICAL ELECTRONIC SCIENCE PROJECTS	75p
208	PRACTICAL STEREO AND QUADROPHONY HANDBOOK	75p
218	BUILD YOUR OWN ELECTRONIC EXPERIMENTERS LABORATORY	65p
221	26 TESTED TRANSISTOR PROJECTS	65p
222	SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS	65p
224	50 CMOS IC PROJECTS	65p
225	A PRACTICAL INTRODUCTION TO DIGITAL ICs	65p
226	HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS	120p
227	BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS	125p
RCC	RESISTOR COLOUR CODE DISC CALCULATOR	20p
BP1	FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES	60p
BP7	RADIO AND ELECTRONIC COLOUR CODES AND DATA CHARTS	25p
BP14	SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES	110p
BP25	HOW TO BUILD YOUR OWN ELECTRONIC WATCHES AND QUARTZ CONTROLLED CLOCKS	85p
BP32	HOW TO BUILD YOUR METAL AND TREASURE LOCATORS	95p
BP43	HOW TO MAKE WALKIE-TALKIES	125p
BP48	ELECTRONIC PROJECTS FOR BEGINNERS	125p
BP56	ELECTRONIC SECURITY DEVICES	150p
BP57	HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE	150p
BP58	50 CIRCUITS USING 7400 SERIES ICs	135p
BP59	SECOND BOOK OF CMOS ICs PROJECTS	150p
BP61	BEGINNERS GUIDE TO DIGITAL TECHNIQUES	95p

Please add 20p p & p per book. No VAT on books. Send SAE for full list of Babani Books

DIL SOCKETS		ANTEX SOLDERING IRONS	VERO-BOARDS
8 pin	10p	C-15W	20p
14 pin	11p	CCN-15W	400p
16 pin	12p	CX-17W	400p
18 pin	24p	X25	400p
		C-15W Kit	570p
		Spare Bits	50p
		Stand	160p
			0.1 Copperclad
			2 1/2 x 5
			3 1/2 x 2 1/2
			3 1/2 x 5
			3 1/2 x 3 1/2
			3 1/2 x 1 1/2
			V-O Board for ICs
			No track cutting
			Pkt. of 100 pins
			Insertion Tool
			S.F. Cutter

IC INSERTION/EXTRACTION TOOL	TRANSISTORS	LINEAR ICs	TTL/CMOS	VOLTAGE REGULATORS
50p	AC125/7	CA3046	7400	1 Amp +ve
	AC128	CA3090E	7401	Plastic
	AC176	CA3098E	7402	1 Amp +ve
	AD149	CA3090	7403	5V
	AD101/2	CA3140E	7404	8V
	BC107/8	ICL8038	7408	12V
	BC109	LF555P	7410	15V
	BC177/8	LM301A	7413	18V
	BC178	LM309K	7414	24V
	BC182/3	LM311	7416	1 Amp -ve
	AC184	LM324	7420	5V
	BC212/3	LM339	7427	12V
	BC214	LM348	7430	15V
	BC548	LM337	7432	18V
	BCY71/2	LM380	7440	24V
	BC131/2	LM381AN	7447A	5V
	MPSA12	LM710	7448	12V
	TIP31A	LM741	7450	15V
	TIP32A	LM748	7470	4502
	TIP33A	LM3900	7473	4503
	TIP34A	LM3909	7474	4511
	TIP41A	LM3911	7475	4516
	TIP42A	LM4136	7476	4520
	ZTX108	MC1310P	7483	4528
	2N219A	MC1458	7488	4584
	2N2222A	MC3340P	7490	
	2N2369A	MC3360P	7489	
	2N2646	NE531	7492A	
	2N2926	NE555	7493	
	2N3053	NE556	74107	
	2N3055	NE567	74121	
	2N3442	SN76003N	74123	
	2N3773	SN76013N	74141	
	2N3819	SN76013ND	74154	
	2N3702/2	SN76023ND	74157	
	2N4123	SN76033N	74160	
	2N4401	TBA4181B11	74181	
	2N5191	TBA800	74184	
	2N5194	TBA810S	74198	
	2N5245	TCA940E	74198	
	2N5401	TDA1022		
	2N5457/8	TL072		
	2N5459	TL074		
	2N6107	TL081		
	2N6254	TL084		
	2N6247	TL082		
	2N6290	ZN414		
	40873	ZN425E		
	40871/2	ZN1034E		

OPTO-ELECTRONICS		MULTIMETERS	
Red LEDs	Displays	Pocket Multimeter	5-00
0.125" 13p	DL707 180p	LT22 (20K/V)	12-00
0.2" 14p	DL747 240p	Microtest 80R	10-00 P & P 0-75
Green	FND500 110p	Supertester 680R	33-50 P & P 1-00
0.125" 10p	FND507 110p		
0.2" 20p	ORP12 80p		
Clips	2N5777 45p		

EXPERIMENTOR BREADBOARDS
No soldering suitable for DIL ICs
EXP325 (1 IC up to 22 pin) 170p
EXP 300 (up to 5 x 14 pin) 575p
EXP600 (up to 7 x 14 pin) 630p
EXP350 (up to 2 x 14 pin) 3-15

PROTO BOARDS SOLDERLESS
Socket Strips/Bus Strips/Binding Posts mounted on sturdy base plate
PB 6 6 x 14 pin DIL ICs 9-20
PB 100 10 x 14 pin DIL ICs 11-80
PB 102 12 x 14 pin DIL ICs 22-95
PB 103 24 x 14 pin DIL ICs 35-45
PB 104 32 x 14 pin DIL ICs 45-95
(The above boards are suitable for all DIL ICs)

LOGIC PROBES
ULTRASONIC TRANSDUCERS Rx & Tx 3-45 pr.
LOGIC PROBE £18-00
LOGIC PROBE KIT £15-75
SUBMINIATURE SWITCHES (Toggle) SPST 60p SPDT 85p DPDT 78p Push to Make 15p Push to Break 22p Slide DPDT 10p

LOUDSPEAKERS
2 1/2" 8R 85p
1 1/2" 8R 80p

TECHNOMATIC LTD
17 BURNLEY ROAD, LONDON NW10
(2 minutes from Dollis Hill Tube)
Tel. 01-452 1500 Tlx. 922800

VAT Rate. Please add 15% to your total. Please send SAE for full list. CALLERS WELCOME MON-FRI 9.30-5.30 SAT 10.30-4.30 Add 30p p & p (75p p & p for official orders)

MULLARD POLYESTER CAPACITORS .1uf 180v.w., @ 20p doz.
COMPRESSION TRIMMERS 10pf, 30pf, 50pf, 1000pf All 10p ea.
TEXAS BRIDGES 100 PIV 1 amp @ 30p, 200 PIV 4 amp @ 60p.
300 TO 75 OHM BALUN TRANSFORMERS at 20p each.
VARIABLE CAPACITORS 5pf @ 75p, 10pf @ 75p, 50+50pf @ £1, 125+125pf @ 60p, 100+200pf @ 60p, 200+300pf @ 60p, 250+250+20+20+20pf @ 75p, 25+25+25pf @ 75p.
12 VOLT MINIATURE 2 POLE CHANGE OVER RELAY @ 60p.
LED's 0.2" Red @ 15p, Green @ 10p, TL 209 @ 15p.
OP-TO ISOLATOR 1L-74 with data @ 50p.
R. F. TRANSISTORS AF 239, 2N 5179, 2N 5180, BFY 90. All at 50p, 2N 918 @ 25p.
MULLARD STRIPLINE BF 302 @ 25p.
TRANSMITTING VARIABLE CAPACITOR 30+30pf @ £2-20.
VHF-UHF FETS 800 MHz Type BF 256C @ 4 for 75p.
5 ASSORTED PIECES OF BLOB BOARD for £1-50.
MINIATURE 12 WAY CERAMIC TAG STRIPS for 15p.
POLYESTER CAPACITORS 1uf 63v.w., @ 5p, 4-7uf 63v.w., @ 10p, 10uf 63v.w. @ 15p.
DAU TRIMMERS 2 To 9pf, 7 To 35pf, 6 To 45pf, 8 To 125pf, 8 To 140pf, All at 15p.
CERAMIC TRIMMERS 2-5 To 6pf, 3 To 10pf, 4-7 To 20pf, All at 15p.
5 WATT NPN DARLINGTON TRANSISTOR at 3 for 50p.
10 ASSORTED PUSH BUTTON BANKS less knobs for £1-30.
10 SLIDER POTENTIOMETERS Assorted 60mm, 50mm in length @ £1.
E84 VHF-UHF FET at 4 for £1.
400mW ZENERS unmarked Good. 3-0v, 6-8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36 volt. All at 10 for 40p.
3/16" Dia. COIL FORMERS with core at 6 for 25p.
50. PLASTIC NPN TRANSISTORS BC 107-9 series untested @ 60p.
50. PLASTIC PNP TRANSISTORS untested @ 60p.
50. ASSORTED 2 WATT ZENERS untested @ 60p.
50. 1 AMP S.C.R.'s T05 case untested @ £1.
25. 5 AMP S.C.R.'s Stud Mounting untested @ 75p.
10. 20 AMP STUD MOUNTING DIODES untested @ 60p.
20. 10 AMP STUD MOUNTING DIODES untested @ 60p.
1000pf 0 K.V.W. DISC CERAMICS at 6 for 20p.
HIGH SPEED CMOS HEF4518 @ 5p, 5 for £2.
50. OC71 TRANSISTORS untested for 75p.
WIRE WOUND POTENTIOMETERS 2K, 10K, 2 watt, 5K, 100K, 4 watt all 30p.
VERNITRON FM 4 10-7 MHz FILTERS at 50p, 3 for £1.
250 VOLT 10 AMP TOGGLE SWITCHES 2 Pole Make @ 50p each.
MAINS TRANSFORMERS 240 Volt Input. Type 1. 24 volt tapped at 14 volt 1 Amp @ £1-30 (P&P 25p), Type 2. 30-0-30 Volt 500 mA @ £1-30 (P&P 25p), Type 3. 45 volt, 6 amp @ £4-50 (P&P 95p), Type 4. 20 volt lamp Twice, 10 volt 1 amp wice @ £4-50 (P&P 95p), Type 5. 45 volt 2 AMP, 45 volt 500mA @ £3-50 (P&P 85p), Type 6. 10 volt 2 amp @ £1-50 (P&P 25p), Type 8. 30 volt 1 amp @ £1-50 (P&P 25p).
3 PIN PLUG AND SOCKET like R.S. European Type with 2 metres of Cable @ 75p.
T85 NPN 100 VOLT 800 mA TRANSISTORS 2N 657 @ 25p each.
2 GHz STRIPLINE NPN TRANSISTORS @ £1 each.
Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas postage charged at cost.

J. BIRKETT
RADIO COMPONENT SUPPLIERS
25 The Strait, Lincoln LN2 1JF Tel. 20767



FIRST and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation second to none for our catalogue—and for the service that backs it up. Experience both for yourself. Just send £1-30 with the coupon and a catalogue will come by return of post.

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.
Dept. EE., 234-240 London Road, Mitcham, Surrey CR4 3HD
01-845 8422

POST THIS COUPON
with cheque or P.O. for £1-30

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD. Dept. EE
234-240 London Road, Mitcham, Surrey CR4 3HD (Regn. No London 912966)



The hobby that grows

What you see above is a kit of parts that builds into a fully working oscilloscope. No toy, this vital piece of functional equipment can be found in any professional electronics workshop. It is a valuable instrument of true professional quality.

By building the oscilloscope you will be taking the first steps to a rewarding hobby that knows no bounds. Each constructional stage is a complete lesson

in the basics of electronics practice and carefully designed to be understood by those with no previous knowledge. Once built, this instrument can be used to complete a course of practical study and experimentation that will reveal the secrets of printed circuitry, testing and servicing of T.V. and radio and the vast majority of electronic equipment. Invaluable knowledge that pays big dividends. Send today for the free colour brochure and start growing a new hobby.

and grows.

1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2. Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.


We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

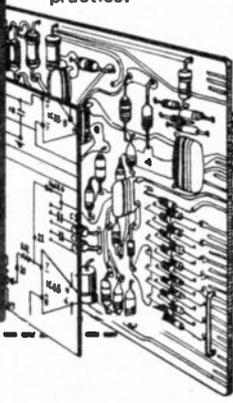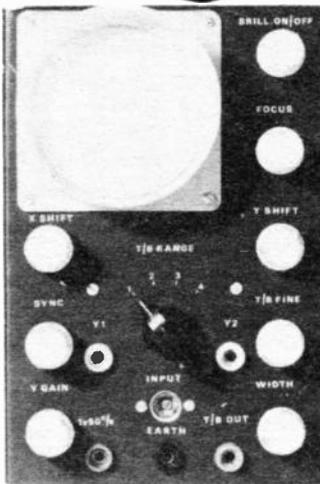4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



Free 32 page Colour Booklet.

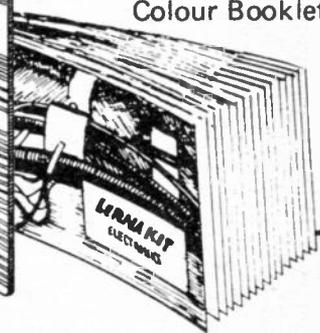

EEA/12/79


NAME.....
 ADDRESS.....

Block Caps Please

Post now, without obligation, to:-
BRITISH NATIONAL RADIO and ELECTRONICS SCHOOL
 P.O. Box 156, Jersey, Channel Islands.

GREENWELD

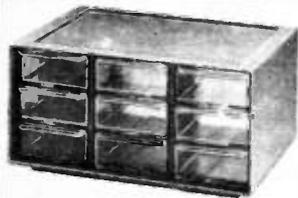443D MILLBROOK ROAD, SOUTHAMPTON SO1 0HX
All prices include VAT—just add 30p post. Tel (0703) 772501



COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors, diodes and I.C.'s. All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts!

All parts contained in clearly marked bags in a plastic storage cabinet 232 x 121 x 185mm with 9 drawers into which all parts can be neatly located.

If bought individually parts plus case would cost over £47 but we are offering this for ONLY £31.95 + £1 p & p. Simply send a cheque or P/O for £32.95 for immediate despatch.

CONTENTS:

- 200 ½ watt resistors
- 20 Wire wound resistors
- 70 Ceramic Capacitors
- 70 Mylar Capacitors
- 50 Polyester Capacitors
- 56 Electrolytic Capacitors
- 61 Transistors
- 12 I.C.'s
- 20 L.E.D.'s
- 55 Diodes and rectifiers

Altogether 614 components.

Price includes current catalogue and Greenweld pen for reordering supplies. Plus FREE surprise gift.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resistant pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.10

KITS OF BITS FOR EE PROJECTS

We supply parts for nearly all EE projects—for a detailed components list of this month's, and previous articles, please send SAE.



VEROBLOC BREADBOARD

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC. Blocs and be joined together. Bus strips on X & Y axis—total 360 connexion points for just £3.70.

VU METERS

V002 Twin type, 2 meters 40 x 40mm and driver board, supplied with circuit and connexion data, £3.50.
V003 New type, just in. Twin type moulded in one piece. 80 x 40mm (no driver board but suitable circuit supplied). £2.50.

THE AMAZING GREENWELD CATALOGUE

FEATURES INCLUDE:


- 50p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

3W Amp Module

Ready built and tested, this handy amplifier will prove very useful around the workshop. Just requires 17V ac source (and 8R spkr) as bridge rect and smoothing cap are mounted on the PCB. The 4 transistor circuit provides enough sensitivity for most applications. Supplied complete with circuit diagram and wiring details.

Only £1.75. Suitable transformer £2.20.

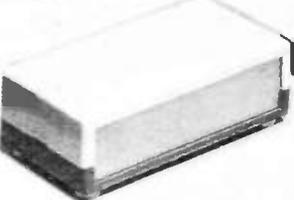

VEROCASE SALE!!

Four popular sizes of Verocase at drastically reduced prices—these were part of their standard range (75-1411 etc.) but are in GREEN and have been discontinued by Vero. We have purchased their entire stock and offer them as below:

Type No	Size	Price
21050	205 x 140 x 75mm	£2.70
21051	180 x 120 x 65mm	£2.20
21052	154 x 85 x 60mm	£1.70
21053	125 x 65 x 40mm	£1.40

1A 400V RECTIFIERS

Plastic, like 1N4004, type 388F these diodes have preformed leads for horizontal mntg (15mm FC). Supersaver price—100 for £2.30; 500/£10 1000/£18

BUZZERS & MOTORS

Z401 Powerful 6V DC, all metal construction 50mm dia x 20mm 70p.
Z402 Miniature type, 3-9V, only 22x15x16mm. Very neat. 65p.
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only £1.
Z451 12V high torque motor 30mm dia x 40mm high, with 10mm spindle. 65p.
Z452 6V DC motor with gearbox giving final shaft speed 700rpm. Spindle is threaded OBA. Ex-equip £1.
Z453 As above, but 300rpm and un-threaded spindle. £1.

TEACH IN 80

We are again supplying all parts required for this major series which started in October. The price for all the Tutor Deck parts is £19.50. Also supplied without breadboard for £13.50. The price for the additional components required for Parts 1-6 is £2.00. All prices include VAT and Postage. Reprints of Oct & Nov parts 30p ea.



Wilmslow Audio

THE firm for speakers!

SEND 30P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER ● MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNOY ● VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. EE)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

QUALITY REEL TO

REEL & CASSETTE TAPE HEADS

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01	MONO PLAYBACK	£1.89	E12-09	MONO/STEREO ERASE	£1.85
B12-02	MONO RECORD/PLAYBACK	£4.02	B22-02	TWIN HALF TRACK RECORD/PLBK	£5.97
B24-01	STEREO PLAYBACK	£3.30	C44RPS02	QUAD QUARTER TRACK REC/PLBK	£9.37
B24-02	STEREO RECORD/PLAYBACK	£6.56	C22ES02	TWIN HALF TRACK ERASE	£4.72
B24-RP	STEREO GLASS FERRITE REC/PLBK	£11.60	MAGNETIC TAPE HEADS CATALOGUE 25 PENCE		
AUDIO AND HI-FI CATALOGUE 180 PAGE FULL COLOUR! 50 PENCE					

MONOLITH

THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER

ALL PRICES INCLUDE VAT

FITS ALL 12 VOLT SYSTEMS

ELECTRONIC CAR ELECTRICS

2 YEAR G'TEE

Here is an instrument the size of a matchbox that mounts on or under your dash in just a few minutes. It will display the condition of your battery, and monitor your charge rate. The display shows red and yellow stripes when all is well. Faults are shown as red only or yellow only, and our unique fault finding guide helps you track them down.

TRY THE C-MORE ON YOUR CAR

We'll despatch it by return, and if you don't like—

- THE HIGH BRIGHTNESS LED DISPLAY
- THE EASE OF INSTALLATION
- OUR UNIQUE FAULT FINDING GUIDE


or anything else. Send it back within 10 days for a refund of the purchase price.

Please send C-Mores at £8.35 each (inc. VAT) (+ 27p U.K. p & p, 50p Airmail export), please.

To:

Cheque/P.O./M.O. value:

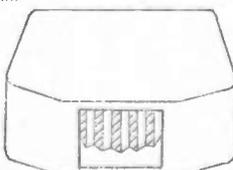To: HARVELEC (Dept. EE), 1 Formby Ave., St. Helens, Merseyside WA10 3NW.
Regd. in U.K. No: 2395248



All this for lower cost than conventional instruments that offer less.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY BY RETURN OF P & P ADD 30P TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

VAT Export orders no V.A.T. Applicable to U.K. Customers only. Unless stated otherwise all prices are exclusive of V.A.T. Please add 15% to total cost including P & P.

We stock many more items. If you wish to visit us, we are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am-6.00 pm. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in μ F)
400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 22n, 33n, 47n, 68n, 100n, 150n, 220n, 330n, 470n, 680n, 1000n; 1 μ F 640, 2 μ F 820, 5 μ F 1000, 10 μ F 1500, 22 μ F 2200, 47 μ F 3300, 100 μ F 4700, 220 μ F 6800, 470 μ F 10000, 1000 μ F 15000; 250V: 100n, 150n, 220n, 330n, 470n, 680n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 10000n; 100V: 10nF, 15n, 20n, 22n, 25n, 30n, 33n, 39n, 47n, 56n, 68n, 82n, 100n, 150n, 220n, 330n, 470n, 680n, 1000n; 50V: 10nF, 15n, 20n, 22n, 25n, 30n, 33n, 39n, 47n, 56n, 68n, 82n, 100n, 150n, 220n, 330n, 470n, 680n, 1000n.

POLYESTER RADIAL LEAD CAPACITORS (250V)
10nF, 15n, 22n, 27n, 50n, 33n, 47n, 68n, 100n, 150n, 220n, 330n, 470n, 680n, 1000n; 1 μ F 22p, 1 μ S 30p, 2 μ S 34p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F)
250V: 100 85p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22 8p; 47, 32, 50 12p; 83, 100 27p; 50V: 50, 100, 220 25p; 47, 32, 33p; 1000 50p; 40V: 22, 33, 47, 56, 68, 82, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000; 25V: 10, 22, 47, 68, 80, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000; 10V: 10, 22, 47, 68, 80, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000; 5V: 10, 22, 47, 68, 80, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000.

TANTALUM BEAD CAPACITORS: 35V: 0.1 μ F, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2 μ F, 3.3, 4.7, 6.8 25V: 1.5, 10, 20V: 1.5 18V: 10 μ F 13p each 47, 100, 40V: 10 μ F, 22 μ F, 33 20V: 47, 68, 100, 30p 3V: 68, 100 μ F, 20p

MYLAR FILM CAPACITORS
0.01V: 0.001, 0.002, 0.005, 0.01 μ F 7p
0.05V: 0.02, 0.04, 0.05, 0.056 μ F 7p
0.1 μ F, 0.2 9p 50V: 0.47 12p

MINIATURE TYPE TRIMMERS
2.5-5pF, 3-10pF, 10-40pF 22p
5-25pF, 5-45pF, 60pF, 85pF 30p

COMPRESSION TRIMMERS
3-40pF, 10-80pF 30p; 25-190pF 33p
100 500pF 45p 125p 50p 58p.

POLYSTYRENE CAPACITORS
10pF to 1nF 6p; 1.5nF to 10nF 10p

SILVER MICA (Values in pF) 3-3, 4, 7, 8, 10, 12, 18, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 180 8p each 220, 250, 300, 330, 360, 390, 600, 820 16p each 1000, 1200, 1800, 2000 20p each

CERAMIC CAPACITORS: 50V 0.5pF to 10nF 4p; 22n to 100n 6p.

EURO BREADBOARD £5-30

VOLTAGE REGULATORS*
1A TO3 +5V -5V 7905 220p
5V 7805 145p 7905 220p
12V 7812 145p 7912 220p
15V 7815 145p
18V 7818 145p

1A TO220 Plastic Casing
5V 7805 65p 7905 75p
12V 7812 65p 7912 75p
15V 7815 65p 7915 75p
18V 7818 65p 7918 75p
24V 7824 65p 7924 75p

100mA TO92 Plastic Casing
5V 78L05 30p 79L05 65p
6V 78L02 30p
8V 78L02 30p
12V 78L12 30p 79L12 65p
15V 78L15 30p 79L15 65p

CA3085 95 LM323K 625 MVR5 150
LM300H 170 LM325N 240 MVR12 150
LM305H 140 LM326N 240 TA A550 50
LM309K 135 LM327N 270 TDA625B 95
LM317K 350 LM723 39 TDA1412 150

JACKSONS VARIABLE CAPACITORS
Dielectric 0.2 365pF with slow motion
100/300pF 175p Drive 1028/176 325p
500pF 205p Drive 208/176 285p
1.6 Ball Drive motion drive 125p
4511/DAF 125p motion drive 325p
Dial Drive 4103 C804-5pF 135p
8/136 1 850p 25.50 pF 175p
Rum 54mm 40p 100, 150pF 275p
0.1-365pF 245p 'L' 3 x 310pF 530p
0.02-365pF 275p 3.0 x 2.5pF 450p

DENCO COILS RDT2 88p
'BP' VALVE TYPE RFC5 5 chokes 88p
Range 1 to 5 Bl., RFC7 (19mH) 102p
Rd., Yl. Wht. 92p 1 FT 13, 14, 15;
6-7 B.Y.R. 85p 16; 17, 92p
1-5 Green 95p 1 FT 18/18 104p
1 FT to 5 Bl., Yl., 1 FT 18/465 92p
Rd., Wht. 1-05p TOC 92p
B9A Valve Holder MW/SFR 112p
28p MW/LW 5FR 120p

VEROBOARD 0-1 0-15 0-15
2x 3 3 (copper clad) (plain)
2x 5 5 55p 50p 31p
3x 3 3 55p 50p -
3x 5 5 62p 67p 43p
3x 17 169p 135p 92p
3x 17 218p 180p 120p
4x 17 280p 218p 180p
Pkt of 35 pins
Spot face cutter
Pin insertion tool

DIODES
AA119 25 Range 2V7 to 3V
AA129 20 39V 400mW
BA100 10 8p each
BY126 12 Range 3V3 to 33V, 1-3W
BY127 12 15p each
CRO33 148
OA9 7
OA47 12
OA70 12
OA79 10
OA81 15
OA85 14
OA90 7
OA91 6
OA95 8
OA200 8
OA202 8
IN814 4
IN815 5
IN4001/2 5
IN4003 6
IN4004/5 6
IN4006/7 6
IN4148 4
3A/100V 18
3A/400V 20
3A/600V 27
3A/1000V 30

ZENERS
Range 2V7 to 39V 400mW
8p each
Range 3V3 to 33V, 1-3W
15p each
5A300V 35
5A600V 43
8A500V 58
8A800V 85
12A300V 25
12A500V 92
15A/700V 195p
2N4444 140p
BT106 150
C1068 38
C1069 38
TIC45 45

SCRs Thyristors
0-8A/200V 30p
0-8A/100V 30p
0-8A/200A 35p
1A/600V 70
5A300V 35
5A600V 43
8A500V 58
8A800V 85
12A300V 25
12A500V 92
15A/700V 195p
2N4444 140p
BT106 150
C1068 38
C1069 38
TIC45 45

TRIACS
3A100V 48
3A200V 48
3A400V 48
8A100V 54
8A200V 64
8A400V 72
12A100V 60
12A200V 60
12A400V 70
12A800V 130p
16A100V 95
16A500V 150
25A800V 295
25A1000V 480p
27B800V 120

BRIDGE RECTIFIERS
(plastic case)
15A/700V 195p
2N4444 140p
BT106 150
C1068 38
C1069 38
TIC45 45

WIDE SELECTION OF Electronic Books and Magazines

EE TEACH-IN Complete kit of parts now available £20-95.

SWITCHES Miniature Non-Locking Push to Make 15p
ROCKER: SPST on/off 10A 250V 23p
ROCKER: Illuminated (white) Lights when on: 3A 240V 70p
ROTARY: (ADJUSTABLE STOP) 1 pole/2-12 way 2p/2-6W, 3p/2-4W, 4p/2-3W. 41p
ROTARY: Mains 250V AC, 4 Amp 45p

DIL SOCKETS (Low Profile - Texas) 8 pin 10p; 14 pin 12p; 16 pin 13p; 18 pin 16p; 20 pin 22p; 24 pin 25p; 28 pin 39p; 40 pin 50p.

TRANSISTORS AC125 20 BC171 11 BF179 30 MPSU56 56 ZTX302 20 ZTX307 11 AC126 20 BC172 11 BF194 12 OC28 150 ZTX304 24 ZTX309 11 AC127 20 BC177 18 BF195 12 OC28 170 ZTX310 24 ZTX311 16 AC128 20 BC178 16 BF196 12 OC28 170 ZTX311 24 ZTX312 16 AC141 24 BC182 11 BF197 12 OC28 170 ZTX312 24 BC182 11 BF200 30 OC42 48 ZTX501 15 ZTX313 21 AC188 24 BC183 6 BF224A 11 OC43 55 ZTX502 18 ZTX314 16 AC189 11 BF224 30 OC44 31 ZTX503 25 ZTX315 21 AC197 35 BC184 9 BF225 30 OC45 60 ZTX504 25 ZTX316 21 AC198 40 BC185 11 BF227 30 OC46 28 ZTX505 25 ZTX317 21 AC199 40 BC187 28 BF228 30 OC70 28 ZTX506 25 ZTX318 21 AC201 35 BC212 11 BF259 30 OC71 28 ZTX507 25 ZTX319 21 AC202 40 BC213 10 BF259 38 OC72 42 ZTX508 25 ZTX320 18 AC203 30 BC214 11 BF259 38 OC73 36 ZTX509 25 ZTX321 16 AC204 30 BC215 11 BF259 38 OC74 36 ZTX510 25 ZTX322 16 AC205 30 BC216 11 BF259 38 OC75 36 ZTX511 25 ZTX323 16 AC206 30 BC217 11 BF259 38 OC76 36 ZTX512 25 ZTX324 16 AC337 30 BC348 11 BF259 38 OC207 36 ZTX643 25 ZTX455 16



GIVE US SPACE

YES WE'VE DONE IT AGAIN—ANOTHER HUGE PURCHASE OF COMPONENTS HAS ARRIVED AND OUR STORES ARE OVERFLOWING WITH BARGAINS. SO HERE'S YOUR CHANCE—**CUT OUT WHOLE COUPON—ADD MONEY, MARK NUMBER OF PACKS REQUIRED IN BOX**

- | | | |
|--|-------|--------------------------|
| 1. TELEVISION GAMES CHIP (colour) AY3-8800 by General Instruments—ball & paddle, tennis, hockey, soccer, squash, practice, grid ball, basket ball. Includes data | £1.00 | <input type="checkbox"/> |
| 2. TELEVISION GAMES CHIP (colour) AY3-8850 ball & paddle, tennis, soccer, squash. Includes data | £1.00 | <input type="checkbox"/> |
| 3. ZENER DIODE PACK—15 assorted high & low wattage zeners—mixed voltages | £1.00 | <input type="checkbox"/> |
| 4. 20 ASSORTED TRANSISTORS—no junk—all working branded—plastic and metal cans | £1.00 | <input type="checkbox"/> |
| 5. DIODES—20 assorted. May include signal, planar germanium rectifiers | £1.00 | <input type="checkbox"/> |
| 6. RESISTORS—our giant pack, minimum quarter kilo, of assorted resistors—all types | £1.00 | <input type="checkbox"/> |
| 7. TERRIFIC VALUE—our capacitor packs (100 approx.) may include discs, mylara, electrolytics, polyester | £1.00 | <input type="checkbox"/> |
| 8. 8 ASSORTED POTENTIOMETERS AND PRESETS—carbon, wirewound, rectilinear, etc | £1.00 | <input type="checkbox"/> |
| 9. 70 WATT AMPLIFIER KITS by famous maker includes PCB, heatsink, all components instructions fraction of original price, to clear | £6.50 | <input type="checkbox"/> |
| 10. PRE-AMPLIFIER KIT (suite above or W.H.Y.) with all metalwork excellent appearance. Sacrifice @ | £3.00 | <input type="checkbox"/> |
| 11. GUITAR PRE-AMP KIT (suite 70W amp or W.H.Y.) all metalwork, etc, Sacrifice @ | £5.50 | <input type="checkbox"/> |
| FREE All orders over £10 get a free junk box filler pack. Lots of useful bits | FREE | <input type="checkbox"/> |
- (my order is over £10)

ONLY PACKS 1-5 INCLUSIVE AVAILABLE FOR EXPORT. Prices include V.A.T. POSTAGE 46p but free if you order £5 or over.

To: (Your name and address)

.....

.....

Please print clearly and give your postcode. Cut out whole advertisement and post with cheque, postal order or cash to:

ARROW ELECTRONICS LTD

LEADER HOUSE, COPTFOLD ROAD, BRENTWOOD, ESSEX CM14 4BN
OR you may collect at our shop (open 9-5 Mon.-Sat. Closed PM Thursday)

KITS FOR E.E. PROJECTS

VARICAP RADIO (ZB 1)	Sept 79	£8.50
TRANSISTOR TESTER (ZB 2)	Sept 79	£5.00
LOW POWER AUDIO AMPLIFIER WITHOUT CASE (ZB 3)	Sept 79	£2.70
SEE LIST (ZB 33)		
WARBLING TIMER (ZB 5)	Aug 79	£5.80
POWER SUPPLY 9V (ZB 6)	Aug 79	£8.25
ELECTRONIC TUNING FORK (ZB 7)	Aug 79	£8.80
SWANEE WHISTLER (ZB 8)	Aug 79	£3.50
TRAILER FLASHER UNIT (ZB 9)	Aug 79	£3.00
TOUCH-ON PILOT LIGHT LESS CASE (ZB 10)	Aug 79	£1.70
SEE LIST (ZB 34)		
QUIZ REFERENCE (ZB 12)	Aug 79	£4.50
SOLDERING IRON BIT SAVER (ZB 13)	July 79	£7.00
CONFERENCE TIMER INCLUDES 1 EXT UNIT (ZB 14)	July 79	£38.00
VOLTAGE SPLITTER (ZB 15)	July 79	£3.25
SEE LIST (ZB 35)		
DARKROOM TIMER (ZB 17)	July 79	£2.50
TREMOLO UNIT (ZB 18)	June 79	£10.00
ELECTRONIC CANARY (ZB 19)	June 79	£4.50
METAL LOCATOR (ZB 20)	June 79	£10.00
METER AMPLIFIER (ZB 21)	June 79	£3.50
QUAD SIMULATOR (ZB 22)	June 79	£8.00
INTRUDER ALARM (ZB 23)	May 79	£23.00
ELECTRONIC DICE (ZB 24)	May 79	£13.50
SHORT WAVE CONVERTER (ZB 25)	May 79	£13.75
SHAVY INVERTER (ZB 26)	April 79	£12.00
TOUCH BLEEPER (ZB 27)	April 79	£3.25
CHOKE WARNING DEVICE (ZB 28)	April 79	£7.50
SEE LIST (ZB 36)		
POWER SUPPLY (ZB 30)	Feb 79	£27.00
SEE LIST (ZB 37)		
LIGHTS REMINDER FOR CAR (ZB 32)	Jan 79	£4.50

All above kits include parts as described in article, i.e. vero/board or p.c. board, i.e. sockets, connecting wire etc.

TEACH-IN '80

New to electronics, then start at the beginning. All electronic components for construction of Tutor Deck and Teach-in experiments during the first six parts of the series. Lists A and B £18.50.

ALL PRICES INCLUDE V.A.T.
BARCLAY/VISA/ACCESS CARDS ACCEPTED.
MINIMUM TELEPHONE ORDERS £5.00.

T. POWELL

306 ST. PAUL'S ROAD, LONDON N.1

01-226-1499

SHOP HOURS: MON-FRI 9 a.m.-5.30 p.m., SATURDAY 9 a.m.-4.30 p.m.



ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages. Bound in stiff linen. Cover size 8 1/2 x 5 1/2 in. Price £8.00 per set (we pay the postage).

- | | |
|---------------------------------|--------------------------------------|
| Book 1. Introducing Electronics | Book 4. Meters/Voltage-dividers |
| Book 2. Resistors/Capacitors | Book 5. Transistor Project Circuitry |
| Book 3. Inductors/Diodes | |

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order now:
Selray Book Company
60 Hayes Hill
Bromley
BR2 7HP

OUR 100% GUARANTEE

Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £

Name:

Address:

EE17

IT'S FREE

This newsletter brings advance information of new lines, special snips and "too few to advertise" items. We call it "Advance Advertising News". Whenever you want a copy just send a S.A.E. or the subscription rate of £1.50 for 12 issues, which is just about what it costs us to address the envelope and post them second class.

SPECIAL NOTES: The "A" sign after the amount shows the amount of V.A.T. The postage is based upon the amount in the article cost in the same article forms part of a larger parcel. Would your order be less than £6.00 however, you must send an additional 50p to offset packing and other expenses.

IMPORTANT NOTES:

1. Our July/Aug newsletter we announced a standby heater kit. The heading for this should have read: 5000 watts not 500 watts, and don't forget you can save yourself over £4 by ordering this during September.
2. In some advertisements the Delta siren/bleeper was specified as suitable for A.C. only, it will however work from 6-12 volts D.C. or 12-24 volts A.C.

12v SUBMERSIBLE PUMP

Just join it to your car battery, drop it into the liquid to be moved and up it comes, no messing about, no priming, etc. Suitable for water, paraffin and any non-explosive, non-corrosive liquid. One use if you are a camper, make yourself a sewer. Price £28 + 8pp. A free gift, first 100 purchasers will get tap with built-in switch and length of plastic tubing.

PRECISION RESISTORS

A fortunate purchase enables us to offer almost a complete range of Mullard metal film precision resistors, 1% tolerance. Values start at 5 and go right through to 976 k. Most values are available in 1 watt and 3 watt ratings. Price 25p + 3pp each in small quantities, or 30p + 3pp each where supplied not less than 10 of a value, 15p + 2pp each not less than 100 of a value.

THIS MONTH'S ELECTRICAL SNIP

Parcel of M.E.M. White flush 13 amp sockets, switches, etc. Total retail value over £55 + vat for only £28 + £4.29. You get 10 double 13 amp sockets and 6 single 13 amp S sockets with neons, 14 power (20 amp dpt switches and spurs some with neons), 20 single ganged one-way, two-way and intermediate switches, and super free gift (worth £3). If not collecting please add £2.

M.E.M. WHITE SOCKETS, ETC.

We have picked out the popular items for the snip parcel described above but a list of the other parts available is as follows (makers list Nos.): 220, 224, 240, 242, 244, 711, 712, 813, 1000, 1005, 1010, 1011, 1020, 1021, 1022, 1024, 1025, 1033, 1400, 1400 WH, 1401 WH, 1402, 1402 WH, 1403, 1403 WH, 1404, 1404 WH, 1405, 1405 WH, 1407, 2025, 7092. Electricians and Contractors using these accessories should send for our M.E.M. Electrical List where prices and quantity discounts will be quoted.

VARI-CAP T.V. PUSH BUTTON TUNER

W. German make but fitted to several popular colour T.V.'s, makers Ref. No. 2357 0078. This has 6 push buttons, each of which is in effect a multi turn pot. Total resistance is 15k. The buttons are black with chrome metal tops. Price £1 + 15p, post 25p. Good quantity available at usual discount rates.

MULTI TURN POT WITH KNOB

10mm dia, 20 turn used in many T.V. receivers, makers ref. 7802 412-00051. Suitable for fine control of resistance in general circuitry. Price 40p + 6p.

T.V. DIPLEXER

On plastic moulding size 2 1/2" x 1 1/2". We are able to offer these at such a low price that they can be used as T.V. aerial sockets only. Price 10 for £1 + 15p.

TRANSUCERS

As used remote control T.V. receivers. Price £1.50 + 22p.

BURGLAR ALARM

Mains operated new circuit available, this is simple to install and trouble free. Price list and diagram free on request.

ARMY 40 BATTERIES

As made for and used in the Second World War, we have a few of these in mint condition, complete with carrying satchels, headphones, throat mikes and instruction cards. In unopened boxes. Price £30 + £4.50. Post £2.

MUSIC CENTRE COVER

Size 20" x 13 1/2". Clear plastic £3.50 + 52p, carriage and special packing £2.

25 AMP D.C. METERS

Flush panel mounting, wide angle, extra long, 320° scale made for G.P.O. Really beautiful instrument, brand new in original cartons. Limited quantity only so no discounts. Price £4 + £1.20. (Less than half maker's price.)

BIG BLOWER

Driven by 1/10 H.P. mains motor but compact and quiet running. This is ideal for air conditioning, fume extraction, pressurizing and many other applications. Overall size 10 1/2" x 10 1/2" dia. Outlet size 10 1/2" x 4 1/2". Price £15 + £2.25. Carriage £3. Note that this is the largest of 3 "small" shaped blowers, we have smaller ones right down to 1 watt tubes with outlets as small as 2" x 2", in fact we can cover almost any application and welcome your enquiries. Prices are from £3 complete with motor.

COILS HOUSE SWITCH

Time is fast moving when you may be thinking of making toys. Small surface mounting switches are often a pip and this is why we are now offering this plastic bodied rotary switch suitable for low voltage applications. Price 10 for £1.50 + 22p.

CASSETTE STORAGE CASE

With dust cover, holds 5 cassettes and comes complete with clip for joining to another, so you can make up in lengths to suit yourself. Price 50p + 7pp + 50p post or ten for £4 + 90p, post £1.50.

TELEPHONE ANSWERING MACHINES

Grade 2 machines are in stock ready for immediate despatch or collection (if coming specially to collect please telephone first). For the benefit of new readers we supply these machines on the understanding they are broken up or at least not used for their original purpose. The machines are secondhand but so far as we can see they are complete and quite possibly in good working order. We do not test them but guarantee to replace any part of the machine should it be missing or faulty, providing we are notified within 7 days of receipt. Prices for the machines are as follows: Grade 2 that is in very good condition £15.50 + £2.25, and Grade 1 which are top grade machines and are our very best almost perfect £28 + £3 each, but there is likely to be one month's wait. To these prices must be added £2.50 for cover carriage. Mains Power Pack in Plastic Case for Telephone Answering Machine. Price £4.50 + 63p. Post 50p.

POT CORES

We now have good stocks of Ferrite pot cores. These are ex unused equipment and contain the bobbin and have been opened ready for use.

	Diameter	Thickness	Price
FX 2243	4.5 cm	3.0 cm	75p + 12p
FX 2242	3.5 cm	2.3 cm	60p + 9p
FX 2240	2.5 cm	1.8 cm	50p + 7p

per pair

CASES AND BOARD 40

Again from unused equipment, major items on these are two power silicon transistors, Motor Roia Ref. S1 5433, mounted on a heat sink with mica insulators, also behind the panel are two power rectifiers ST NS 100B. Price 90p + 6p.

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of speakers this should sell at about £30—but due to a special bulk-buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.




SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 10, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £2.30—crystal earphone 65p including VAT and postage.



RADIO STETHOSCOPE

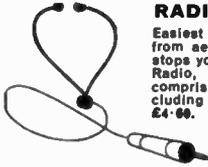Easiest way to fault find, traces, signal from aerial to a speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set £4.60.



WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make £4.25.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.75.

SOUND TO LIGHT UNIT

Will prove circuit flashes up to 750 watts of lamps. Complete kit includes S.C.P. mains input leads, all parts and very neat plastic case £4.95.

CASSETTE OUTFITS

Complete mechanisms with record/playback and erase heads—all electronics and speaker £3.75 post and V.A.T. paid. Note these are all cased up ready to use but case may be slightly incomplete, cracked or broken.

VARICAP POCKET RECEIVER CHASER DISPLAY

To quickly receive parts for these and other E.E. projects, send the approximate cost as shown. Any cash adjustment can be made later.



MINI-MULTI TESTER

Amazing, deluxe pocket size precision moving coil instrument jewelled bearings—1000 opv—mirrored scale. 11 instant ranges measure:—DC volts 10, 50, 250, 1000 AC volts 10, 50, 250, 1000 DC amps 0-1mA and 0-100 mA. Continuity and resistance 0-150K ohms. Complete with insulated probes, leads, battery, circuit diagram and instructions.

Unbelievable value only £5.50 + 50p post and insurance. FREE Amps ranges kit enable you to read DC current from 0-100mA, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one send £1.50.

TERMS: Cash with order—but orders under £6 must add 50p to offset packing, etc.
BULK ENQUIRIES INVITED. PHONE: 01-688 1833.
ACCESS & BARCLAYCARD ACCEPTED

J. BULL (ELECTRAL) LTD
(Dept. E.E.), 103 TAMWORTH RD.,
CROYDON CR8 1SG

HEAVY DUTY 3 CORE APPLIANCES LEAD

15 amp wire, 6ft. long, conventional yellow, green, brown and blue cores, grey PVC outer, prepared ends, this flex normally sells at 30p per metre. 10 leads for £2.50 + 40p. Post £1.50.

E.H.T. MAINS TRANSFORMER

Output voltage 4-5kv 3mA. These transformers are ex unused P.S.U.'s. Price £25 + 30p, post 40p.

LOUD SPEAKER GRILL

Good quality rigid plastic. Ideal for use in car or home extension speakers. Two sizes available: 12" x 12", price 75p + 15p, 18" x 18" £1.50 + 22p.

DIGIT COUNTER-RESETTABLE

Coin voltage 45 D.C. or 115v A.C., current 100mA approx. Price £1.95 + 30p.

10 DIGIT SWITCH PAD

Made we believe for G.P.O. push button telephones, each button operates 2 pole switch which returns automatically, panel size 2 1/2" x 3 1/2" x 1 1/2". Push buttons with clear plastic protected digits 0-9. Price £1.95 + 30p.

MAINS BLOWER

Real bargain this month is a blower made by Smiths, the mains motor is let right into the turbulator and takes up the minimum of space. Overall size of the blower is 7" dia. x 2 1/2" and the outlet is 1 1/2" x 2 1/2". Price only £2.50 + 30p + p & 50p.

DIGIT INDICATOR

As used in tool making and other precision measuring operations, the famous John Bull accurately shows differences of 0.01mm. A beautifully made precision instrument, price in most tool shops would be £12-15. Price £8 + £1.20.

WATERPROOF SWITCH

Ideal for use in house or outdoor, plastic body. Price 60p + 9p.

CAR SPEAKER

Elliptical size 7 1/2" x 5", 4 ohm. Price £1.50 + 12p, post 20p + 2p.

7 SEGMENT DIGITAL DISPLAY

TIL 302, i.e.d. com. anode—character size 4" approx. Price £3.15 + 16p.

USEFUL BREAKDOWN UNIT

We do not normally offer second hand equipment for breaking down but this particular item contains so many useful pieces that we have decided to break our rule. The unit is in fact a pocket "bleeper" in a most useful case, size about 2 1/2" wide by 3 1/2" high by 5 1/2" deep, ideal size to fit into the top jacket pocket. Case comes apart by undoing two screws, inside is printed circuit board upon which are mounted a miniature loud speaker, three rechargeable nicada disc type 150-4 ferrite potted coils, three of which are tunable, 4" ferrite rod. Mercury tilt switch on when case is upright, 4 electrolytic condensers, one micro switch, 8 transistors all with usable length leads, 4 polystyrene capacitors, 2 pin plug for charging batteries without uncasing and approximately 4 diodes and approximately 30 various capacitors and resistors, most of the resistors being 1 watt type, truly a very useful unit although secondhand, still in reasonable condition. Price £1.50 + 22p.

25 WATT SPEAKERS

Comprising 8" woofer and 3" tweeter with crossover and terminal connection panel, all mounted in good quality non-resonant cabinet. These are extremely good quality units comparable with those selling at twice the price. Cabinet size approx. 20" high, 10 1/2" wide and 8 1/2" deep, heavy cabinet made of thick blockboard. Price £25 + £3.75 the pair, well worth your coming to collect, but if you cannot collect they are still worth this £5 extra for carriage.

TWIN PADDED FLEX

5 amp ideal for some electric irons and appliances that require very flexible lead, 10 metre lengths. Price £1 + 15p. Post 40p.

ROD THERMOSTAT

Suitable for high temperatures up to 550°F. This is adjustable either at the head or remotely by a length of flexible drive. Price £2.50 + 30p.

DRY FILM LUBRICANT

In easy application and for putting lubricant into places where the normal oil-can cannot reach. Offered at about half the original list price. 50p + 7p per can (8 oz) or 12 cans for £4 + 60p, post £1.50. The lubricant is I.C.I. Fluon L169.

1/2 MICROSWITCH

Popular switch with 10 amp 250 volt changeover contacts. Price £15 per 100, or £140 per 1000 + V.A.T. Ditto with 15 amp changeover contacts £20 per 100 or £190 per 1000.

ASSORTED MICROSWITCHES

10 different small, medium and large sizes to suit most projects and repair jobs. Price £1.50 + 22p. If this pack does not contain the one you want, give us a ring, we may have it.

PUSH SWITCHES

That really stand out, its large dished knob also makes this extra easy to operate, sprung to return to normal when pressure is removed. 10 amp 250 volt changeover contacts. Type 1, 1 c/o 40p + 6p. Type 2, 2 c/o 60p + 9p. Type 3, 3 c/o 80p + 12p.

HFV KIT

Light Tracer and Strobe for disco's or parties. 2 running light patterns and a strobe. Was described with full constructional details in September Everyday Electronics. Our price for complete kit including case £14 + £2.10.

SPRING LOADED ROCKER SWITCH

Made originally for car dash. This is a simple on/off for up to 10 amps. Price 25p + 4p.

DP PANEL SWITCH

Arco made. This is a handsome switch, it has a long flanged toggle, black and chrome finish. Rated 2 amps at 250 volts and double-pole on/off. Price 40p + 6p.

PUSH BUTTON SWITCH

Suitable mains, audio or RF. Each switch rated at 250 volts 15 amps. 1st (black push button) closes 2 circuits; 2nd (white push button) operates one changeover; 3rd (white push button) operates one changeover; 4th (white push button) opens one circuit. Note: All depressed buttons remain down until released by the 5th (red button). Further note: It is a relatively easy job to alter the position of the tags, thus making the switches suit your circuit. Fitted with 3 white, 1 red and 1 black button. Price 75p + 11p.

COMBINATION SWITCH

This comprises 12 miniature changeover micro switches joined in a block of 3 and mounted on frame with four digital numbered thumb wheels and a removable lever for locking the thumb wheel, the thumb wheel operates 3 banks. Over 4,000 combinations are possible, by re-wiring the switch connections underneath thousands more variations are possible. If you are making equipment which should not be switched on accidentally or without authority, then this is a switch to consider. It can be used as a coding switch for many other operations. Very neat and compact, measuring approx. 4" x 1 1/2" and 1 1/2" deep. Price £1.75 + 26p.

BALANCE ARMATURE INSERTS

600 ohm impedance, used as either speaker or mike. Price 50p + 7p.

1/40 TRANSISTOR

First class maker, will respond to light or infra-red. 5 for £1 + 15p. 100 for £15 + £2.20. 1000 for £125 + £8.75.

CONTACT STAT

This is a skeleton thermostat with control knob calibrated 90°F-190°F. Put it into a box and you have calibrated wall stat on base in close contact with the item to be controlled, for instance, bolt it to the casing of an electric motor, heat sink of semi conductor or other device which must not be allowed to overheat or strap it to a water tank, etc., etc. The switch will make and break 15 amps at normal mains voltage. Price £1.90 + 22p.

DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

DL1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. £14.60

DLZ1000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. £8.00
Optional Opto Input (DLAI) 60p



DL1000K



DLZ1000K

LIGHTING CONTROL KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touchplates. Easy to follow instructions.

TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. £6.50

TDE/K Extension kit for TD300K for 2-way switching etc. £1.50

TSD300K—TOUCHSWITCH & DIMMER. Single touchplate, small knob controls brightness. £5.50

TS300K—ON/OFF TOUCHSWITCH. Two touchplates. £4.30

TSA300K—AUTOMATIC. Single touchplate. Time delay variable 2 secs. to 3½ mins. £4.30

LD300K—LIGHTDIMMER KIT. £2.90

LEDS

0.1" Red 9p
0.2" Red 9p
Green 12p
Yellow 12p
Square Red 5 x 2.5 x 9mm 20p

SPECIAL OFFER

25 off 0.2" LEDS
Red £1.50
Green £2.00
Yellow £2.00

RESISTORS

½W 22 ohm 10M E12 Series
Pack of 10 (one value) 10p
10 Packs 80p

DISPLAYS

DL727 0.5" 2-digit CA £1.25
DL304/307 (pin compatible with DL704/707) 0.3" CC Red 70p
DL847 CA/DL850 (pin compatible with DL747/750) 0.8" CA/CC £1.80

LIQUID CRYSTAL DISPLAY

3½ digit 40 pin dill £8.10


SPECIAL IL74 Opto Isolator 45p.

SPECIAL OFFERS

2N3819—Set 20p
T15 43—VJT 25p
TIC 106 4A/400B 30p
EC4 182L 10 for 50p

TRIACS

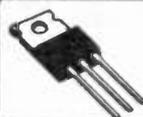400V Plastic Case (Texas)
3A 49p 16A 90p
8A 57p 20A 165p
12A 70p 25A 190p
6A with trigger 80p
8A isolated tab 82p
Diac 18p



24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC 0.5" LED display, mains supply, display drivers, switches, LEDS, triac, PCBs & full instructions.

CT 1000K Basic Kit £14.90
CT 1000KB with white box (56 x 131 x 71mm) £17.40
Ready built £12.50

INTEGRATED CIRCUITS



555 Timer 21p
741 Op. Amp 18p
AY-5-1224 Clock £2.60
AY-5-1230 Clock/Timer £4.50
AY-5-1232 Clock/Timer £4.50
ICL7106 D.V.M. (LCD Drive) £7.50
TDA1024 Zero Voltage Switch £1.20
LM10C Op. Amp. 1-1V27U £2.99
LM3911 Thermometer £1.00
LM3914 Dot/bar Driver £2.60
MM57160 (stac) Timer £5.95
S566B Touchdimmer £2.60
S9263 Touchswitch £4.85
ZN1034E Timer £1.80
All ICs supplied with data and circuit.

DIGITAL VOLTMETER/THERMOMETER KIT

Based on the ICL7106. This Kit contains a PCB resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display.



Components are also included to enable the basic DV kit to be modified to a Digital Thermometer, using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery) £20.75.

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 30p P&P. MAIL ORDER—CALLERS WELCOME BY APPOINTMENT.



TK Electronics (EE)

106 STUDLEY GRANGE ROAD
LONDON W7 2LX. TEL. 01-579 9794



TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City and Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept P268 Interhex House, London SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Tel:

Age:

Random Electronic


EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box and descriptive instructions.

Complete
or
Kit



PCB
Layout

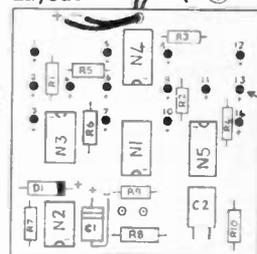

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

- a *Self Assemble Dice £3.95
b *Ready built Dice £4.75 (INCL. P+P)

Order now from **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk O473-210151

Amount enclosed £

Name

Address

please state amount required in appropriate box a b



For Sale

MULLARD LP1164 AM/FM I.F. Modules guaranteed unused £1.50. P.P. C.W.O. S.A.E. Lists. Tennex Limited, Stock Road Industrial Estate, Southend, Essex.

NEW BACK ISSUES of "EVERYDAY ELECTRONICS". Available 65p each Post Free, open PO/Cheque returned if not in stock. **BELL'S TELEVISION SERVICES** 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

OFFERS FOR "EVERYDAY ELECTRONICS". Issues Dec '71; Jan '72; All issues Mar '72 to Dec '75. Newport I.O.W. 527864.

Books and Publications

FREE. World-famous manufacturer's convenient, pocket-sized electronic construction guide (nearly 200 full-colour illustrations). Limited period offer. Send SAE now to **TECHNOCENTRE**, 54, Adcote Road, Middlesbrough.

Business Opportunities

IN VIEW of current Government moves towards free enterprise in the sale of telephones and their installation we may be presented with the largest instant growth industry opportunity of the decade.

We are the largest reproduction telephone manufacturers and importers in the U.K. We wish to grasp these opportunities.

You are interested in handling sales and/or installation of a wide variety of decorative telephones. You wish to grasp these opportunities.

Please write for details, enclosing 2 x 10p stamps for a brochure of our telephones if required, and enclosing relevant details about yourself which will be held in strict confidence. **Conversation Pieces**, 55 Swindon Road, Cheltenham, Glos. Cheltenham 35707.

Service Sheets

SERVICE SHEETS from 50p and SAE. Catalogue 25p and SAE. **Hamilton Radio**, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICE for service sheets of Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to **BTS**, 190 King's Rd, Harrogate, N. Yorkshire. Tel: 0423 55885.

Situations Vacant

MONEY FROM YOUR HOBBY!

We are a small colour photographic processing laboratory and require a part-time engineer/enthusiast to maintain, service, modify and improve our electronic and electromechanical processing equipment. Would suit amateur or part-qualified enthusiast (preferably local and with interest in photography). Flexible hours and negotiable terms. Write or phone for a friendly chat **Keith Lyons**, 'Round the Clock Colour Prints Ltd., 16 Blenheim Terrace, London N.W.8. Telephone 024 2244 or 285 8283.

SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £5.00 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to **Everyday Electronics** and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, **Everyday Electronics**, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

Record Accessories

STYLI, CARTRIDGES FOR MUSIC CENTRES &c. **FREE** List No. 29. For S.A.E. includes Leads, Mikes, Phones, etc. **FELSTEAD ELECTRONICS (EE)**, **LONGLEY LANE, GATLEY, CHEADLE, CHES SK8 4EE.**

Receivers and Components

COMPONENTS AT SILLY PRICES. 1,000 mixed resistors £3.60. SAE lists. W.V.E.2, **Craig Farm, Tintern, Gwent.**

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-70 plus 25p P. & P.

'Brain-Freeze' 'em with a **MINI-STROBE** Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4-50 plus 25p P. & P. Experiment with a psychedelic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P.

LOTS MORE! Send 25p for lists.

Prices include VAT.

BOFFIN PROJECTS

4 **CUNLIFF ROAD, STONELEIGH**
EWELL, SURREY. (E.E.)

P.C.B.s Paxolin 10 1/2" x 4 1/2" £1.30. 12" x 9 1/2" 85p. 16" x 11 1/2" £1.40. D.S. 10" x 9 1/2" 85p. Fibreglass 12" x 7 1/2" £1.00. 14" x 6" £1.90. D.S. 10 1/2" x 7" £1.35. 8" x 7" £1.15. Panel with 40 assorted 74 series I.C.s £1.00. 20 wire ended Neons £1.20. Small 3 Transistor Audio Amps 3-£1.20. 300 Small Components, Trans, Diodes £1.00. 71bs Assorted Components £3.75. List 15p. refundable. Post 20p. Insurance add 15p.

J.W.B. RADIO

2 **Barnfield Crescent, Sale, Cheshire M33 1NL**

QUALITY ELECTRONIC COMPONENTS AT LOW PRICES

Write or telephone for free pamphlet to:

HARRISON BROS. DEPT E.E.

P.O. Box 55, Westcliff-on-Sea, Essex. SSO 7LQ.
Tel: Southend-on-Sea 32338

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO**, 103 South Brink, Wisbech, Cambs, 0945 4188. Immediate settlement.

100 ASSORTED COMPONENTS 115p, 100 resistors 75p, 10 mains neons 50p, 20 micro-switches 150p, 50 reed switches 200p. Add 25p p&p. **DURRANTS**, 9 St. Mary's Street, Shrewsbury, Salop.

DISCOVER ELECTRONICS. Build forty easy projects including: Metal Detector; Breathalyzer; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms, etc. Circuits, plans all for £1.29 including **FREE** circuit board. Mail only. **RIDLEY PHOTO/ELECTRONICS**, Box 62, 111 Rockspark Road, Uckfield, Sussex.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

200 COMPONENTS £4 10. Red L.E.D.s 0-125 90p. Lists 15p. Sole (E. E.), 37 Stanley Street, Ormskirk, Lancs L39 2DH.

Miscellaneous

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! **Golden Fotolak** Light Sensitive Lacquer—now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/packing 60p. **WHITE HOUSE ELECTRONICS**, P.O. Box 19, Castle Drive, Penzance, Cornwall.

NORTHERN IRELAND. Build your own Computer. **Nascom-1** Microcomputer kits. From **P & O Computers (N.I)**, 81 Dublin Rd, Belfast BT2 7HF. Tel: 22010 evenings. Donaghmore 312. Belfast 621706.

AERIAL BOOSTERS

Improves weak VHF radio & television reception. **B45-UHF TV, B11-VHF RADIO. B11 A-2** metres.

For next to the set fitting.

PRICE £8. S.A.E. FOR LEAFLETS.

ELECTRONIC MAILORDER LTD.

82 Bridge Street
Ramsbottom, Bury, Lancs, BLO 9AG.

THE SCIENTIFIC WIRE COMPANY

PO Box 20, London E.4.
Reg. Office, 22 Coningsby Gardens.

ENAMELLED COPPER WIRE

SWG	1 lb	4 oz	2 oz
10-10	2-85	1-45	0-75
20-20	2-85	1-65	0-90
30-34	3-05	1-75	1-00
35-40	3-40	1-95	1-15
41-43	4-85	2-55	1-95
44-48	5-05	3-05	2-15
47	8-00	5-00	3-00
48	15-00	9-00	6-00

SILVER PLATED COPPER WIRE

14, 16, 18	4-50	2-25	1-44
20 & 22	5-00	2-85	1-74
24 & 26	5-70	3-31	2-00
28 & 30	6-67	3-86	2-35

Prices include P & P and VAT.
SAE brings list of copper & resistance Wires.
Dealer enquiries invited.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus catalogue. Write or call, **Sandwell Plant Ltd**, 2 Union Drive, Boldmere, Sutton Coldfield, West Midlands. 021-354 9764. Or see them at **TLC**, 32 Craven Street, Charing Cross, London WC2.

BUILD 25 PROJECTS with our multi-purpose kits, details supplied. Send £15.00 to **Major Oak Services**, 33 Lillian Avenue, London W3.


TUNBRIDGE WELLS COMPONENTS, **BALLARD'S**, 108 Camden Road, Tunbridge Wells, Phone 31803. No lists, enquiries S.A.E.

Road Runner

The NEW logic/
microprocessor prototype
wire threading system

- ★ Versatile, suitable for all types of circuit board.
- ★ Fast, economical and efficient in use.
- ★ Accepted and approved by leading industrial, research and educational establishments.
- ★ Compact, high quality, low profile finished results.
- ★ Ideal for microprocessor development.
- ★ Designed for all prototype and pre-release applications.

DRAMATICALLY REDUCES
DEVELOPMENT COSTS

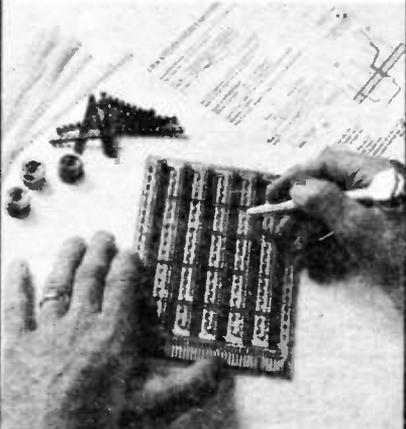

Roadrunner Wire Threading System

Introkit	£9.88
Pencil	2.44
6" Glue Strips (pkt 20) ..	2.80
2" Press Strips (pkt 20) ..	2.92
Bobbins, 4 of 1 col./pkt. Green, Blue, Gold, Pink ..	2.12
DIL Breadboard	2.65

Prices include P & P. Please add 15% VAT.

Come and see us at
Breadboard
on Stand F10

For further information please write to:

T. J. BRINE ASSOCIATES
116 Blackdown Rural Industries,
Haste Hill, Haslemere, Surrey.

MAINS INTERCOM



NO
BATTERIES
NO WIRES
ONLY
£32.99
PER PAIR
+ VAT £4.95

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. P. & P. £1.25.

4-STATION INTERCOM **£27.95**
+ VAT £4.19

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs) in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. A Battery and other accessories. P. & P. £1.95.

NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£17.95
+VAT £2.70
+ P & P 99p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £19.95 + VAT £3.00. P. & P. 99p.

DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for surface mortise reversible latch locks) mains power unit, cable (8-wire) 50 ft and wiring diagram. Price £49.95 + VAT £7.50 + P. & P. £1.50. Kit with two Telephones £59.95 + VAT £9.00 + P. & P. £1.75.
10-day price refund guarantee on all items.

WEST LONDON DIRECT SUPPLIES (EE12)
169 KENSINGTON HIGH STREET, LONDON W8



Please
mention

*Everyday
Electronics*

when
replying
to
advertisements



IT's COMING!

PROFESSIONAL
ELECTRONICS

'The Ultimate
in Quality'

A
Phenomenal
NEW

Mail
Order
Company
the likes
of which
YOU'VE
NEVER
SEEN
BEFORE

Providing the
most
PROFESSIONAL

Electronics
Equipment
on the market
for

YOU!

M.E.C.A.

14 HOPETOUN STR.,
BATHGATE,
WEST LOTHIAN
Tel: Bathgate 631371

FREE 4 RECTIFIER DIODES

in 4003 or 4005 ON ALL ORDERS
dated before 1.1.1980

TERMS: C.W.O. No Min. 15p P & P.
ACCESS & BARCLAYCARD ACCEPTED
Min. £5 Post & Packing 25p.
GOVERNMENT, SCHOOLS, COLLEGES
ORDERS ACCEPTED
Send or Phone for Catalogue.

CMOS		N LSN		N LSN		N LSN		N LSN		AUDIO		100+ Less 20%		CAPACITORS:—	
4000	8p	4049	26p	7411	15p	18p	7490	29p	40p	74198	95p	60p	1K Less 25%	ELECTROLYTIC. RADIAL	
4001	11p	4052	45p	7412	15p		7491	49p		74221	99p	190p	D.L.747	£1.50	LEAD
4002	12p	4053	45p	7413	15p	30p	7492	29p		74367	99p	130p			Values
4004	25p	4066	30p	7414	45p	65p	7493	28p	40p	REGULATORS		130p	1N4148	1.3p	16V
4006	70p	4089	20p	7416	16p		7494	69p		78L	25p	190p	100	£1	40V
4007	12p	4071	15p	7417	24p		7495	45p	62p	723	25p	70p	1N4002	3p	63V
4008	45p	4081	16p	7420	10p	16p	7496	48p		78M	40p	90p	1N4003	3.5p	Values
4009	25p	4082	17p	7426	15p		74100	79p		7805	50p	80p	1N4005	4p	1uF
4010	26p	4507	48p	7427	15p		74107	19p	32p	7812	50p	600p	1N4007	5p	2.2uF
4011	12p	4511	55p	7430	10p	16p	74121	22p		7815	55p		1N5402	10p	3.3uF
4012	12p	4512	65p	7432	12p	18p	74122	35p		7824	55p				4.7uF
4013	26p	4515	195p	7437	12p	20p	74123	35p	55p	LM309	90p				10uF
4014	55p	4519	42p	7438	13p	25p	74125	30p	40p	LM323	375p				22uF
4015	50p	4522	70p	7440	12p	22p	74126	29p	40p	LM340K	75p				33uF
4016	21p	4526	70p	7441	52p		74132	44p	60p	79	75p				47uF
4017	45p	4528	70p	7442	26p	45p	74141	49p		MICROS.					68uF
4018	45p	4529	70p	7443	42p		74150	53p		CPU's					100uF
4019	25p	MC14409	999p	7444	42p		74151	39p	49p	Z80	£9				150uF
4020	50p	MC14419	295p	7445	42p		74153	45p	49p	Z80A	£11				220uF
4021	50p	74C151	80p	7446	42p		74154	65p	120p	6800	£7				330uF
4022	45p	All prices		7447	42p	68p	74156	39p	78p	8080	£4				470uF
4023	12p	include V.A.T.		7448	42p	48p	74157	39p	45p	280P10	£6.75				680uF
4024	45p	BUFFERED		7450	13p		74161	49p	75p	MEMORIES:					1000uF
4025	12p	types on request		7451	13p	20p	74163	49p	79p	2102L	£1				2200uF
4026	95p	according to our		7453	13p		74164	55p	75p	2114L	£4.75				
4027	25p	stock position.		7454	13p	16p	74165	59p		2122L	£4.75				
4028	45p			7460	13p		74166	60p		4044	£6				
4029	60p	TTL:—		7470	26p		74175	55p	58p	4116	£6.50				
4030	20p	N LSN		7472	24p		74176	49p		PROMS					
4033	80p	7400	7p	14p	7473	16p	74178	60p		1702A	£4				
4034	150p	7401	9p	14p	7474	19p	74180	60p		2708	£5.75				
4035	50p	7402	9p	14p	7475	26p	74181	125p		2716	£18				
4037	90p	7403	9p	14p	7476	25p	74182	45p		2758 5V	£15				
4040	50p	7404	7p	14p	7480	35p	74188	45p		CHARACTER					
4041	45p	7405	13p	18p	7481	60p	74190	60p	78p	GENERATORS					
4042	40p	7406	15p		7482	45p	74191	60p	90p	2513	£5				
4043	30p	7407	24p		7483	45p	74192	55p	69p	UARTS					
4044	50p	7408	9p	14p	7485	60p	74193	55p	65p	TR16028	£3				
4046	75p	7409	9p	18p	7486	20p	74194	55p		LEDS 8.2"					
4048	50p	7410	9p	14p	7489	99p	74195	49p	60p	Red	8p				
							74196	49p	78p	Green	10p				
							74197	49p	POA	Yellow	10p				
										10+	Less 10%				

INDEX TO ADVERTISERS

Absonglen Ltd.	835	Electrovalue	774	O.K. Machine & Tool	819
A.J.D.	845	Electroni-Kit	816	Phonosonics	834
Alcon	834	Elverston Electronics	847	Powell, T.	842
Ambit	773	Fringewood Electronics	844				
Amtron	835					R.S.T.	831
Antex	Cover ii	George Sales, David	772	Radio Components Specialties	805
Arrow Electronics	842	G.M.T. Electronics	821	Radio & Television Components	791
				Greenweld	840				
Bi-Pak	767, 777					Selray Book Co.	842
Birkett, J.	838	Harvelec	840	Stevenson, C. N.	827
B.N.R.E.S.	775, 832, 839	Harversons	774	Swanley Electronics	845
Brewster, S. & R.	774	Heathkit	792				
Brine, T. J.	847	Home Radio	838	Tandy	815
Bull, J.	843					Technomatic	838
Butterworths	824	I.L.P. Electronics	836, 837	Tempus	833
				Intertext (ICS)	844	T.K. Electronics	844
Chromasonics	845					TUAC	832
Chromatronics	772	Magenta Electronics	769				
Collier McMillan (B.I.E.T.)	808	Maplin Electronic Supplies Ltd.	Cover iv	Videotime Products	828
Comp Shop	Cover iii	Marshall, A.	828	Watford Electronics	841
Continental Specialities Corporation	827	Meca	848	West London Direct Supplies	847
				Metac	770, 771	Wilmslow Audio	840
E.D.A.	816	Monolith...	840				



GRANDSTAND

VIDEO ENTERTAINMENT COMPUTER

SIMPLY PLUGS INTO YOUR TV

Beautifully simple to link to any 625-line UHF Television. Connects to the mains and just plugs into the TV aerial socket and ... you're off! Plays in colour on colour TVs and gives a sparkling black and white picture with B & W televisions, and broadcasts realistic sound effects to add to the excitement.

Space-age computer technology brings an amazing variety of games which you play in the comfort of your own armchair stadium at home. Get in with the action without getting out! Fun for all the family, it plays the generation game with live TV action to suit all ages. Once you've been in control of the TV, normal service might never be resumed again!

It's so excitingly different ... great for parties and to make the evening when visitors call.

CARTRIDGES AVAILABLE AT £11.99



Videocart-1: 1-player games—

"Noughts and Crosses," "Shooting Gallery," "Doodle" and "Quadroodle"

Videocart-2: 2-player "Desert Fox" and 1-player "Shooting Gallery"

Videocart-3:

1 and 2-player "Video Blackjack"

Videocart-4: 1 and

2-player "Spitfire"

Videocart-5: 2-player

"Space War"

Videocart-6: 1-player "Math Quiz 1" (addition-subtraction)

Videocart-8: 1-player

"Mind Reader"

Videocart-9: 2-player

"Drag Strip"

Videocart-10: 1 and 2-player

"Maze" and "Cat & Mouse"

Videocart-11: 2-player

"Backgammon" and

"Acey-Ducey"

Videocart-12: 2-player

"Baseball"

Videocart-13: 1 and 2-player

"Torpedo Alley" and

"Robot War"

Videocart-14: 1 and 2-player

"Sonar Search"

Videocart-15: 1 and 2-player

"Memory Match"

Videocart-16: 1 and 2-player

"Dodge It"

Videocart-17: 1 and 2-player

"Pinball Challenge"

Videocart-18: 1 and 2-player

"Hangman"

Videocart-20: 1 and 2-player

"Video Whizball"

Videocart-21: 1 and 2-player

"Bowling"

HITACHI PROFESSIONAL MONITORS



9" — £129 + VAT
12" — £199 + VAT

● **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability.

● **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved at picture center.

● **Stable picture** Even played back pictures of VTR can be displayed without jittering.

● **Looping video input** Video input can be looped through with built-in termination switch.

● **External sync operation** (available as option for U and C types) ● **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

Break the language barrier £138 ONLY + VAT



At a price equivalent to learning one language, LEXICON offers you, English, Spanish, French, German, Italian and Greek. The LK3000 comes to you with the person to person module which contains 6 languages, de-luxe carrying case and a charger adaptor using its own power source which will give you 4 - 5 hours continuous use, and can easily be re-charged from the mains supply.

wherever you may be in the world. Every additional module carries a concise and understandable instruction book. Your deluxe carrying case has room for two additional modules.

UNIVERSAL POWER SUPPLY

Suitable for Nascom I, Nascom II, Superboard and all computers requiring these specifications.

+5V @ 3 amps +12V @ 1 amp -5V @ 500 mills -12v @ 500 mills

Easy to construct — complete with transformer. Our price £24.90

ETI TV PINBALL FEATURING BREAKOUT

CHIP & PCB
£14.90

ALL OTHER PARTS
ALSO EX-STOCK

THE ATARI VIDEO COMPUTER SYSTEM £138 + VAT



Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges!

Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous.

You'll have thrill after thrill, whether you're in the thick of a dogfight, screaming around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on color TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

Cartridges now available All at £13.90 each + VAT

Basic Maths, Airsea Battle, Black Jack Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score, Space War, Sky Diver, Air Sea Battle Codebreaker, Miniature Golf

Extra Paddle Controllers—£14.90 + VAT

*Keyboard Controllers—£16.90 + VAT

SPECIAL OFFER WHILE STOCKS LAST:

Free extra cartridge of your choice, please state 1st, 2nd and 3rd preference.

MODULATORS UHF Channel 36

Standard 6 meg band width £2.25

High Quality 8 meg band width £4.90 EX-STOCK

SHORT C12 CASSETTES FOR COMPUTER PROGRAMMES 10 for £4.00

video 100

12" BLACK & WHITE
LOW COST VIDEO
MONITOR

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum in Central 80% of CRT; 550 Lines Minimum beyond central 80%.



Only **£79 + VAT**



Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMP SHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CARD or AMERICAN EXPRESS number. CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G
Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday

NOW OPEN ALL DAY SUNDAY — For Shop Sales Only

Close to New Barnet BR Station — Moorgate Lane.



COMP COMPUTER COMPONENTS
(Part of the Compshop Ltd. Group)



MAPLIN



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.

Breadboard 1979 is even bigger and better than last year. It's the one show no one should miss!

These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.



Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.

A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £750. Full specification in our catalogue.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £18.38 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).

MAPLIN

ELECTRONIC SUPPLIES LTD


Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____

ADDRESS _____

E.E. 12/79

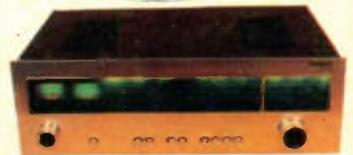

A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.

Maplin will be there in force with all our projects on permanent demonstration. There will be plenty to see and many of our interesting lines will be on sale.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000.