

Easy to build projects for everyone

FEB. 80
50p

Everyday ELECTRONICS



**MICRO
MUSIC BOX**

SLIDE/TAPE SYNCRONISER



**SIMPLE S.W. RECEIVER
MORSE PRACTICE OSCILLATOR**

**SPECIAL OFFER
Mini 20 MULTIMETER**



MAGENTA ELECTRONICS LTD.

E.E. PROJECT KITS

Make us **YOUR No. 1 SUPPLIER OF KITS AND COMPONENTS** for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Project kits include **ALL THE ELECTRONICS AND HARDWARE NEEDED**—we have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own **FREE COMPONENT IDENTIFICATION SHEET**. We supply—you construct. **PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. IF YOU DO NOT HAVE THE ISSUE OF E.E. WHICH CONTAINS THE PROJECT—YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA—39p. each.**

UNIBAND BURGLAR ALARM. Dec. 79. £4.75.
LIGHTS CALL. Dec. 79. £5-13.
BABY ALARM. Nov. 79. £2-20.
OPTO ALARM. Nov. 79. £5-36 inc. optional parts.
MW/LW RADIO TUNER. Nov. 79. £15-50 less dial.
3 FUNCTION GENERATOR. Nov. 79. £18-44 less pointer, case extra £7-18.
ONE ARMED BANDIT. Oct. 79. £18-39, case extra £3-98.
HIGH IMPEDANCE VOLTMETER. Oct. 79. £16-22.
LIGHTS ON REMINDER. Oct. 79. £4-62.
SIGNAL LEVEL INDICATOR. Oct. 79. £4-81 (stereo).
UNIVERSAL OSCILLATOR. Oct. 79. £3-89.
CHASER LIGHTS. Sept. 79. £18-95.
VARICAP M.W. RADIO. Sept. 79. £8-98.
SIMPLE TRANSISTOR TESTER. Sept. 79. £6-26.
ELECTRONIC TUNING FORK. Aug. 79. £3-94. Suitable microphone + plug £1-59 extra.
WARBLING TIMER. Aug. 79. £6-25.
9V POWER SUPPLY. Aug. 79. £9-94 inc. pcb.
SWANE WHISTLER. Aug. 79. £3-19.
TOUCH ON PILOT LIGHT. Aug. 79. £3-06.
QUIZ REFEREE. Aug. 79. £5-81.
SOLDERING IRON BIT SAVER. July 79. £10-19.
VOLTAGE SPLITTER. July 79. £3-37.
DARKROOM TIMER. July 79. £2-41.
WATER LEVEL INDICATOR. July 79. £4-60.
TREMOLO UNIT. June 79. £10-99.
ELECTRONIC CANARY. June 79. £4-99.
LOW COST METAL LOCATOR. June 79. £5-44.
 Handle & coil former parts extra £4-95.
METER AMPLIFIER. June 79. £4-19.
QUAD SIMULATOR. June 79. £9-26.
INTRUDER ALARM. May 1979. £16-44. Less Ext. Buzzer & Lamp and Loop Components.
SHORT WAVE CONVERTER. May 79. £15-36 inc. cases.
THERMOSTAT 'PHOTO' SOLUTIONS. May 79. £15-75. Less socket, tube and grease.
SHAVER INVERTER. April 79. £13-68.
TRANSISTOR TESTER. April 79. £3-83.
TOUCH BLEEPER. April 79. £3-30.
ONE TRANSISTOR RADIO. Mar. 79. with Amplifier & Headset. Less case. £6-84.
TIME DELAY INDICATOR. Mar. 79. £3-95.
VERSATILE POWER SUPPLY. Mar. 79. £8-99.
CHOKE WARNING DEVICE. Apr. 79. £7-79.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

3 BAND SHORT WAVE RADIO

Simple trf design covering 1.2-24MHz. Covers most amateur bands and short wave broadcast bands. Five controls—bandset, bandspread, reaction, wavechange and attenuator. Uses an internal 9v battery—very low current consumption. The 3 coils are all mounted on the pcb—selection is by a wavechange switch. Use with headphones or a crystal earpiece. **Kit contains all the components required including the pcb and case.** Instructions are included with this kit. Headphones are not included—we recommend our high impedance mono headphones.

KIT £18-97

HEADPHONES EXTRA £3-28.

1980 ELECTRONICS CATALOGUE

MAGENTA'S CATALOGUE HAS BEEN CAREFULLY DESIGNED FOR E.E. READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR THE CONSTRUCTOR. CATALOGUE INCLUDES CIRCUIT IDEAS FOR YOU TO BUILD.

NO MINIMUM ORDER—ALL PRODUCTS ARE STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE! WRITE TODAY ENCLOSING 5 x 10p STAMPS.

MAGENTA ELECTRONICS LTD.

EO13, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI.

OFFICIAL ORDERS FROM SCHOOLS, UNIVERSITIES ETC. WELCOME. ALL PRICES INCLUDE 15% VAT AND FIRST CLASS POST. ADD 30p TO ORDERS UNDER £10 ENQUIRIES MUST INCLUDE S.A.E. MAIL ORDER ONLY.

MAGENTA gives you **FAST DELIVERY BY FIRST CLASS POST OF QUALITY COMPONENTS & KITS.** All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—**HAVE YOU TRIED US?**

ONE-ARMED BANDIT

Oct 79
 Complete with 0-2" LED's and all components. **£18-39.**
 Case extra £3-98

CHASER LIGHTS

Sept 79
 Complete kit — with Case, plugs and sockets etc. **£18-95**

G. P. POWER SUPPLY

Feb 79
0-20V 0-1A. Variable with calibrated VOLTMETER and AMMETER
 All components and Hardware **£25-17.**
 Case (horizontal & layout) **£5-21 extra.**

DOING IT DIGITALLY

Complete kit of top quality components as specified by EVERYDAY ELECTRONICS. Kit comes complete with free component identification sheets.
TTL TEST BED £28-84.
FIRST 6 months COMPONENTS £4-98.
COMPONENTS FOR PARTS 7, 8, 9 & 10 £10-98 includes: photocells, I.C.'s, Resistors, Capacitors, thermistors, microphone, speaker, presets etc.
PART 11 £2-73. PART 12 £3-19.
 Reprints:—Part 1—78p others 39p each.

LOW COST METAL LOCATOR

E.E. June 79
WE HAVE MADE UP A COMPLETE HARDWARE KIT FOR THIS PROJECT, WITH HANDLE, COIL FORMER and SCREWS etc. Everything you need for the project, including electronics and case **£10-39.**
 Or separately:
 Electronics & Case **£5-14.**
 Hardware Kit **£4-95.**

TEACH IN 80

NEW SERIES—ALL COMPONENTS IN STOCK NOW FOR FAST DELIVERY. All top quality components as specified by Everyday Electronics. Out kit comes complete with **FREE COMPONENT IDENTIFICATION SHEET.** Follow this educational series and learn about electronics—Start today! **SEND £22-95 for the TUTOR DECK and ADDITIONAL COMPONENTS parts 1-6.** All orders sent by **FIRST CLASS POST.** Out kit contains all these parts:—

TUTOR DECK: METER, BREADBOARD, TRANSFORMER LEDS, POTENTIOMETERS, SWITCHES, SPEAKER, PLUGS, SOCKETS, BATTERY CLIPS, WIRE, CABLE, FUSES, FUSE-HOLDERS, KNOBS. ADDITIONAL COMPONENTS. PARTS 1-6, RESISTORS, PHOTOCELL, DIODES, CAPACITORS.

CASE WOODWORK KIT £4-98 extra. Complete kit for tutor desk woodwork, contains all the softwood, hardboard, ramin, panel pins, adhesive, screws, feet, strap-handle, and fixings. Cut to size and ready to assemble.

IDEAL SOLDERING EQUIPMENT FOR THE TEACH IN AND ELECTRONICS

ANTEX X25 SOLDERING IRON 25W £4-98
SOLDERING IRON STAND £2-03
SPARE BITS. Small. Standard, Large. 65p each.
SOLDER. Handy size 78p.

DESOLDER BRAID 69p
HOW TO SOLDER BOOKLET 12p
HEAT SINK TWEEZERS 15p.
SOLDER BOBBIN 30p
DESOLDER PUMP £6-98

SWING STORAGE DRAWERS £5-98.
MULTIMETER TYPE 3 100,000 o.p.v. with transistor tester ranges £39-95.
WIRELESS INTERCOM 2 STATION £42-85
SIREN. 12V £5-95.
P.C.B. ASSEMBLY JIG. £11-98.
P.C.B. ETCHING KIT. £4-98.
A.M.F.M. AIRCRAFT BAND PORTABLE RADIO £10-95.
WIRE STRIPPERS & CUTTERS £2-21.
ULTRASONIC TRANSDUCERS. £5-50 pair.
P.A. MICROPHONE coiled lead & switch **£4-68.**
STEREO MICROPHONE PAIR £10-95.
MULTIMETER TYPE 1, 1,000 o.p.v. with probes. 2" x 3 1/2" x 1 1/2". £6-98.
MULTIMETER TYPE 2, 20,000 o.p.v. with case and probes. 5" x 3 1/2" x 1 1/2". £14-25.
F.M. INDOOR AERIAL. 57p.
TELESCOPE AERIAL. 120 c.m. £2-08.
TELEPHONE PICK-UP COIL. 72p.
CRYSTAL MICROPHONE INSERT. 59p.
SPEAKERS MINIATURE. 8 ohm 87p. 64 ohm 88p. 80 ohm £1-28.
PILLOW SPEAKER. 8 ohm 98p.
6" ROUND SPEAKER. 8 ohm, 5W. £2-28.
CABINET SPEAKER. 8 ohm, 5W. 5" speaker. Cabinet 10" x 7" x 4". £6-75.
RE-ENTRANT HORN SPEAKER. 8 ohm S.W. Horn dia. 5 1/2". £5-27.
EARPIECES. Crystal 48p. Magnetic 18p.
STETHOSCOPE ATTACHMENT. Fits our earpieces 69p.
BUZZER. 6V 82p. 12V 85p.
MONO HEADPHONES. 2K. Padded. Superior. Sensitive. £3-28.
STEREO HEADPHONES. 8 ohm. Padded. £4-35.
INTERCOM. 2 Station. Desk. £7-48.
MICROPHONE DYNAMIC. 600 ohm. Cassette type. £1-38.
DENTISTS MIRROR. Adjustable. £2-44
JEWELLERS EYEGLASS. £1-08p
TRIPLE MAGNIFIER. £1-63.
HAND MAGNIFIER. 3" Lens. £3-43.
SPECTACLE MAGNIFIER. Clips on to spectacle frame. £4-65
ILLUMINATED MAGNIFIERS. 1 1/2" lens £1-10. 3" lens £2-98.
POCKET TOOL SET. 20 piece. £4-09.
SCREWDRIVER SET. Six piece. £2-18.
Q. MAX PUNCH. 1" £2-14. 1 1/2" £2-39. 1 3/4" £2-41. 1 3/8" £2-50.
DRILL 12V. Hand or stand use. £10-95. Stand £6-88.
CAPACITANCE SUBSTITUTION BOX. Nine values, 100pF—0.22uF. £2-98.
QUICKEST. Mains connector. £6-41.
PLUG IN POWER SUPPLY. 6, 7.5-9V d.c. 300mA. £4-05.
SPRINGS—SMALL. 10 Ass'd. £1-08.
CROC CLIP TEST LEAD SET. 10 leads with 20 clips. £1-06.
DIMMER SWITCH. 240V. 800W. £4-48.
TRADITIONAL STYLE BELL. 3-8V. 70mm chrome gong. £1.60.
UNDERDOME BELL. 4-10V. Smart. Dia. 70mm. £2-27.
TOWERS INTERNATIONAL TRANSISTOR SELECTOR. New edition. £6-54.
F.M. TUNER CHASSIS. 88-108MHz. 9V d.c. £9-49.
MORSE KEY. High speed. £3-83.
PANEL METERS. 60 x 45mm. Modern style. 50uA, 100uA, 1mA, 1A, 25V d.c. £6-48.
NIGHT LIGHT. Plug type. £1-08.
CONNECTING WIRE PACK. 5 x 5yd. coils. 55p.
VERO SPOT FACE CUTTER. £1-09.
VERO PIN INSERTION TOOL. 0-1" £1-48. 0-15" £1-49.
RESISTOR COLOUR CODE CALCULATOR. 21p.

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D I Y world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R P M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light systems function light and security changeover switch. Will work all rev counters.

Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISE EVERYTHING NEEDED

Die pressed case. Ready drilled aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.

Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."



Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Assoc.
82 Bath Street, Walsall WS1 3DE

Electronics Design Associates, Dept. EE2/80
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X5KIT £16.95

£

ACCESS OR BARCLAY CARD No.


Cheque No.

Send SAE if brochure only required.

24 TUNE DOOR CHIMES

DOOR TUNES £17.13 + VAT.

Waddington's Videomaster announce a doorbell that doesn't go Brrringg, Ding Dong or Bzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.

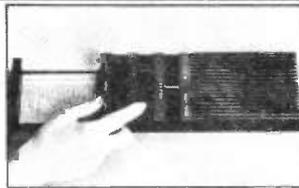

T.V. GAMES

PROGRAMMABLE £29.50 + VAT.
COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/left/right) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



EXTRA CARTRIDGES:

ROAD RACE - £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises

SUPER WIPEOUT - £9.17 + VAT.

10 different games of blasting obstacles off the screen

STUNT RIDER - £12.16 + VAT.

Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.

NON PROGRAMMABLE TV GAMES

6 Game - COLOURSCORE II - £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

CHESS COMPUTERS

STAR CHESS - £55.09 + VAT.
PLAY CHESS AGAINST YOUR PARTNER.

using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess it adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 - £85.65 + VAT.
PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passent, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black and white and against itself and comes complete with a mains adaptor and 12 months guarantee.


OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

CHESS CHAMPION - 6 LEVELS £47.39 + VAT.

CHESS CHALLENGER - 10 LEVELS £138.70 + VAT.

BORIS - MULTI-LEVEL TALKING DISPLAY

£163.04 + VAT.

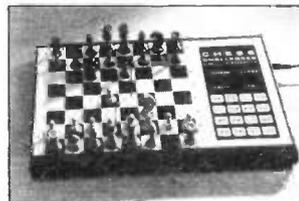

ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT.


A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £17.17 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

DRAUGHTS COMPUTERS

CHECKER 2 LEVELS £43.00 + VAT.
CHALLENGER 4 LEVELS £80.00 + VAT.

PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

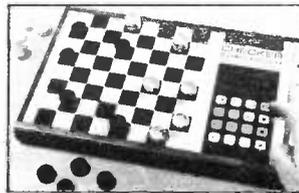

FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm Mon-Sat 9am-1pm Wed.

To order by telephone please quote your name, address and Access/Barclaycard number.

Postage and Packing FREE.

AJD DIRECT SUPPLIES LIMITED, Dept. EE2 102 Bellegrave Road,
Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)

THREE FOR FREE FROM CSC

NEW PROJECTS

Electronics by Numbers
Projects No 4, No 5, No 6

Available from selected stockists
ELECTRONICS BY NUMBERS

RAIN ALARM

You need never be caught out by the weather again. The rain alarm will emit a warning sound whenever there's rain or moisture in the atmosphere. The current drawn from the battery is negligible so it can be left switched on for up to a year!

WOBBLY WIRE GAME


All the fun of the fair, in your own home! Test your skill at building and playing this version of the popular game, where a 'wand' has to be moved from one end of a wire to the other, without the loop at the end of the wand ever touching the wire.

HIGH QUALITY CONTINUITY TESTER

An invaluable piece of test gear for testing and fault finding circuits and wiring. Pure continuity checks can be carried out without being affected by adjoining circuitry.

Want to get started on building exciting projects but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instruction in our FREE "Electronics by Numbers" leaflets, ANYBODY can build electronic projects.

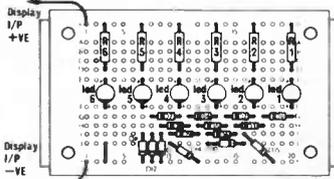Look at the diagram, select R1, plug it in to the letter numbered holes on the EXPERIMENTOR BREADBOARD, do the same with the other components, connect to battery and ANYBODY can build a perfect working project.



YOU WILL NEED

- e.g. LED Bar Graph (a previous project) components EXP300 or EXP350
- D1 to D15 — Silicon Diodes
- R1 to R6 Resistors
- LED 1 to LED 6 Light emitting diodes

For the full detailed instructions, including "Electronics by Numbers" circuit diagrams, simply

take the coupon to your nearest CSC stockist or send direct to us and you will receive "THREE FREE PROJECTS FROM CSC".

If you missed Free project No's 1, 2 and 3, please tick the appropriate box in the coupon.


PROTO-BOARDS

The ultimate in breadboards for the minimum of cost. Two easily assembled kits.



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

PROTO-BOARD 6 KIT £9.20

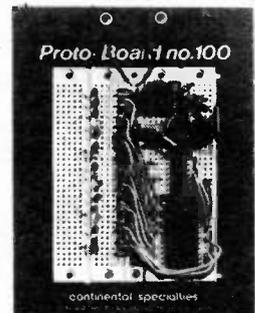

PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

PROTO-BOARD 100 KIT £11.80

EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP 4B.

EXP 325 £1.60 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.



EXP 350 £3.15 Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.



EXP 300 £5.75 The most widely bought bread-board in the UK. With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS.




EXP 600 £6.30 Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600



EXP 650 £3.60 Has .6" centre spacing so is perfect for MICROPROCESSOR applications.



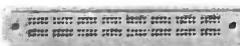EXP 4B £2.30 Four more bus-bars in "snap-on" unit.



The above prices are exclusive of P&P and 15% VAT.

THE CSC 24 HOUR SERVICE TELEPHONE (0799) 21682

With your Access, American Express, Barclaycard number and your order will be in the post immediately

CONTINENTAL SPECIALTIES CORPORATION



CSC (UK) LTD. EUROPE, AFRICA, MIDEAST
Dept 4EE Shire Hill Industrial Estate Units 1 and 2
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682. Telex: 817477

IT'S EASY WITH C.S.C.

TO RECEIVE YOUR FREE COPY OF PROJECTS 4, 5 and 6.

Just clip the coupon

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate box(es) the breadboard(s) you require.

For immediate action

The C.S.C. 24 hour, 5 day a week service. Telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post immediately

EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN DIP	UNIT PRICE INC P&P @ 15% VAT	Qty req.
EXP 325	130	1	£ 2.70	
EXP 350	270	3	£ 4.48	
EXP 300	550	6	£ 7.78	
EXP 600			£ 8.39	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus-Bar	£ 5.00	
EXP 4B	Four 40 Point Bus-Bars		£ 3.50	

PROTO-BOARDS	CONTACT	IC CAPACITY 14 PIN DIP	UNIT PRICE INC P&P @ 15% VAT	Qty req.
PB6	630	6	£11.73	
PB100	760	10	£14.72	

NAME

ADDRESS

.....

.....

I enclose cheque/P.O. for £

Debit my Barclaycard, Access, American Express card No.

..... Expiry date

If you missed project No's 1, 2 and 3. Project 1: Two-Transistor Radio. Project 2: Fish'n'Clicks. Project 3: Led Bar Graph tick box

For Free catalogue tick box

C.S.C.(UK)LTD. Dept 4EE Shire Hill Industrial Estate Units 1 and 2 Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682. Telex: 817477

Great 1980 Sale

SPECIAL OFFER!
COMPONENT PAKS

SUPER SOUND SAVING!
DINDY LOW NOISE CASSETTES

SJ30	10 C30	15 min per side	£2.00
SJ55	10 C46	23 min per side (LP)	£2.50
SJ31	10 C90	45 min per side	£3.50
SJ32	10 C120	40 min per side	£4.50

ALL REDUCED!
CAPACITOR PAKS

16201	18 electrolytics	4.7uf-10uf	
16202	18 electrolytics	10uf-100uf	
16203	18 electrolytics	100uf-680uf	
ALL 3 at SPECIAL PRICE of £1.30			
16160	24 ceramic caps	22pf-82pf	
16161	24 ceramic caps	100pf-390pf	
16162	24 ceramic caps	470pf-3300pf	
16163	24 ceramic caps	4700pf-0.047pf	
ALL 4 at SPECIAL PRICE of £1.80			

RESISTOR PAKS

16213	60 1/2w resistors	100ohm-820ohm	
16214	60 1/2w resistors	1K-8.2K	
16215	60 1/2w resistors	10K-82K	
16216	60 1/2w resistors	100K-820K	
ALL 4 at SPECIAL PRICE of £1.80			
16217	40 1/2w resistors	100ohm-820ohm	
16218	40 1/2w resistors	1K-8.2K	
16219	40 1/2w resistors	10K-82K	
16220	40 1/2w resistors	100K-820K	
ALL 4 at SPECIAL PRICE of £1.80			

IC SOCKET PAKS

SJ36	14	8 pin	2N3819	£0.17
SJ37	12	14 pin	2N5458	£0.18
SJ38	11	16 pin	2N4220	£0.28
SJ39	8	18 pin	2N4860	£0.25
SJ40	7	20 pin		
SJ41	6	22 pin		
SJ42	5	24 pin		
SJ43	4	28 pin		
SJ44	3	40 pin	2N6027	£0.25
ALL at ONLY £1.00 each				

F.E.T.'s

uA7805	£0.65	uA7905	£0.70
uA7812	£0.65	uA7912	£0.70
uA7815	£0.65	uA7915	£0.70
uA7818	£0.65	uA7918	£0.70
uA7824	£0.65	uA7924	£0.70
UA723 14 pin DIL	£0.35		
LM309K T03	£1.10		

VOLTAGE REGULATORS

Positive	Case T0220	Negative	
uA7805	£0.65	uA7905	£0.70
uA7812	£0.65	uA7912	£0.70
uA7815	£0.65	uA7915	£0.70
uA7818	£0.65	uA7918	£0.70
uA7824	£0.65	uA7924	£0.70
UA723 14 pin DIL	£0.35		
LM309K T03	£1.10		

OPTOELECTRONICS
OISPLAYS

1510	707 LED Display	Price each	£0.70
1511	747 LED Display	Price each	£1.50
1512	727 LED Display	Price each (dual)	£1.55

L.E.D.'s

SJ78	125 LED Diffused	RED	£0.08
SJ79	2 LED Diffused	RED	£0.08
SJ20	125 LED Bright	RED	£0.09
SJ21	2 LED Bright	RED	£0.09
1502	125 LED Diffused	GREEN	£0.11
1505	2 LED Diffused	GREEN	£0.11
1503	125 LED Diffused	YELLOW	£0.11
1506	2 LED Diffused	YELLOW	£0.11
SJ80	2 LED Bright	YELLOW	£0.14
SJ82	2 LED Clear illuminating	RED	£0.10
SJ83	125 LED Clear illuminating	RED	£0.10

2nd QUALITY LED PAKS

1507	10 assorted	colours & size	£0.65
S122	10 .125	RED	£0.50
S123	10 .2	RED	£0.50

LED CLIPS

1508/125	125	5 for £0.10
1508/2	2	5 for £0.12

SJ81	1	Infra RED emitter - Fairchild FP100	£0.25
SJ98	5	Photo Detector MEL11 + Data	£1.00
ORP12		NORP12 Cad Cell	£0.45
SJ99	4	ITT 5B70 ST Nixie Tubes	£1.00

SJ29	Texas NPN silicon transistors 2S503=8C108 T0-18 metal can - perfect & coded	50 off £2.50 - 100 off £4.00 - 1000 off £35.00
------	---	--

SPECIAL OFFER

SJ100	12v Electric Drill 7,500 RPM for all your PCB drilling complete with 2 drills - 1 & .75	
-------	---	--

SUPER DUPER COMPONENT BOX

Min. 3 lbs in weight consisting of a fantastic assortment of Electronic Components - Pots, Resistors, Condensers, Switches, Relays.
Board Semiconductors, wire, hardware, etc. etc. etc.
This is a large box and is sent separate to your order
\$140 £2.50 including p&p

CALCULATOR CHIP

GOM2-C500	24 pin MOS	£0.50
-----------	------------	-------

IC INSERTION/EXTRACTION TOOL

2015		£0.35 each
------	--	------------

TRANSISTORS

Type	Price	Type	Price	Type	Price
AC107	£0.20	8C441	£0.25	TIP30A	£0.30
AC126	£0.17	8C460	£0.28	TIP30B	£0.32
AC127	£0.16	8C461	£0.28	TIP30C	£0.32
AC128	£0.15	8C477	£0.15	TIP31	£0.30
AC128K	£0.24	8C478	£0.15	TIP31A	£0.30
AC176	£0.16	8C479	£0.15	TIP31B	£0.32
AC171K	£0.24	8C547	£0.08	TIP31C	£0.34
AC187	£0.16	8C548	£0.08	TIP32	£0.30
AC187K	£0.26	8C549	£0.08	TIP32A	£0.30
AC188	£0.16	8C557	£0.10	TIP32B	£0.32
AC188K	£0.26	8C558	£0.09	TIP32C	£0.34
AD161/162MP	£0.85/pr	8C559	£0.10	TIP41	£0.34
AD140	£0.50	8C570	£0.13	TIP41A	£0.34
AD149	£0.53	8C571	£0.13	TIP41B	£0.36
AF239	£0.35	8C572	£0.13	TIP41C	£0.38
BC107	£0.06	8D115	£0.45	TIP42	£0.34
BC107A	£0.06	8D131	£0.30	TIP42A	£0.34
BC107B	£0.07	8D132	£0.30	TIP42B	£0.36
BC107C	£0.09	8D135	£0.28	TIP42C	£0.38
BC108	£0.06	8D136	£0.28	TIP2955	£0.50
BC108A	£0.06	8D239A/		TIP3D55	£0.45
BC108B	£0.07	8D240A/MP		ZTX107	£0.08
BC108C	£0.08		£0.80/pr	ZTX108	£0.08
BC109	£0.06	BF115	£0.20	ZTX109	£0.09
BC109B	£0.07	BF167	£0.20	ZTX300	£0.10
BC109C	£0.07	BF173	£0.20	ZTX301	£0.10
BC113	£0.10	BF195	£0.09	ZTX302	£0.12
BC114	£0.12	BF196	£0.09	ZTX500	£0.10
BC116	£0.16	BF197	£0.10	ZTX501	£0.10
BC118	£0.10	BF257	£0.22	ZTX502	£0.12
BC140	£0.20	BF258	£0.22	2N696	£0.10
BC141	£0.20	BF259	£0.24	2N697	£0.10
BC142	£0.18	BFR39	£0.20	2N706	£0.09
BC147	£0.07	BFR40	£0.20	2N706A	£0.10
BC148	£0.07	BRF79	£0.22	2N708	£0.10
BC149	£0.07	BRF80	£0.22	2N1302	£0.15
BC157	£0.09	BFTR4	£0.20	2N1303	£0.15
BC158	£0.09	BFTR5	£0.20	2N1613	£0.18
BC159	£0.09	BFX29	£0.20	2N1711	£0.18
BC169C	£0.09	BFX84	£0.20	2N1893	£0.25
BC170	£0.06	BFY50	£0.15	2N2218	£0.18
BC171	£0.07	BFY51	£0.15	2N2218A	£0.20
BC172	£0.07	BFY52	£0.15	2N2219	£0.18
BC173	£0.08	BIP19/20MP		2N2219A	£0.20
BC177	£0.13		£0.70/pr	2N2221	£0.18
BC178	£0.13	MJE340	£0.80	2N2221A	£0.20
BC179	£0.13	MJE2955	£0.75	2N2222	£0.18
BC182	£0.07	MJE3055	£0.50	2N2222A	£0.18
BC182L	£0.07	MPSA05	£0.15	2N2369	£0.12
BC183	£0.07	MPSA06	£0.15	2N2904	£0.16
BC183L	£0.07	MPSA55	£0.15	2N2904A	£0.17
BC184	£0.07	MPSA56	£0.15	2N2905	£0.16
BC184L	£0.07	OC25	£0.50	2N2905A	£0.18
BC207	£0.08	OC26	£0.45	2N2906	£0.14
BC208	£0.08	OC28	£0.60	2N2906A	£0.15
BC209	£0.09	OC29	£0.55	2N2907	£0.15
BC212	£0.07	OC35	£0.55	2N2907A	£0.16
BC212L	£0.07	OC36	£0.60	2N2926G	£0.08
BC213	£0.07	OC42	£0.18	2N3053	£0.15
BC213L	£0.07	OC44	£0.20	2N3054	£0.30
BC214	£0.07	OC45	£0.18	2N3055	£0.35
BC214L	£0.07	OC71	£0.12	2N3056	£0.35
BC251	£0.10	OC72	£0.16	2N3702	£0.07
BC251	£0.10	OC75	£0.18	2N3703	£0.07
BC261	£0.14	OC81	£0.20	2N3704	£0.08
BC327	£0.12	TIP29	£0.30	2N3705	£0.06
BC328	£0.12	TIP29A	£0.30	2N3706	£0.07
BC327	£0.12	TIP29B	£0.32	2N3771	£1.00
BC338	£0.12	TIP29C	£0.34	2N3772	£1.10
BC440	£0.25	TIP30	£0.30	2N3773	£1.50

DIODES

Type	Price	Type	Price	Type	Price
AA119	£0.06	0A70	£0.06	IN4004	£0.06
BA100	£0.08	0A79	£0.08	IN4005	£0.07
BA148	£0.13	0A81	£0.08	IN4006	£0.08
BA173	£0.13	0A90	£0.08	IN4007	£0.09
BA1X3	£0.05	0A91	£0.08	IN5400	£0.12
8AX16	£0.06	0A95	£0.08	IN5401	£0.13
0A200	£0.06	IN34	£0.06	IN5402	£0.14
0A202	£0.07	IN60	£0.07	IN5403	£0.15
BY100	£0.18	IN4148	£0.05	IN5406	£0.19
BY126	£0.14	IN4001	£0.04	IN5407	£0.23
8Y127	£0.12	IN4002	£0.04	IN5408	£0.28
0A47	£0.06	IN4003	£0.05	IS44	£0.03

LINEAR

Type	Price	Type	Price	Type	Price
CA270	£0.95	SL414A	£1.75	TBA810	£0.85
CA308B	£1.70	SN761013N	£1.65	TBA820	£0.85
CA3090	£3.00	SN76023N	£1.60	uA703	£0.20
LM380	£0.80	SN76115	£1.60	uA709C	£0.25
LM381	£1.35	TAA550	£0.30	uA710	£0.25
LM3900	£0.50	TAA621A	£1.80	uA711	£0.26
MC1310P	£0.85	TBA120B	£0.60	741P	£0.16
NE555	£0.18	TBA641A	£1.10	TAA661	£1.25
NE556	£0.55	TBA800	£0.75	TAA661B	£1.25

O/NO	Quantity	£	p
SJ1	200 Resistors mixed values	0.50	
SJ2	200 Carbon resistors 1/2 watt preformed	0.50	
SJ3	100 1/2 watt miniature resistors mixed values	0.50	
SJ4	60 1/2 watt resistors mixed values	0.50	
SJ5	50 1/2 watt resistors mixed pot values	0.50	
SJ6	50 Precision resistors 1-2% tol. mixed	0.50	

ELECTROVALUE CATALOGUE 10 READY NOW

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

FREE

(You don't even have to pay postage in U.K.)

IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

• We give discounts

on C.W.O. orders, except for a few items market Net or N in our price lists.

5% on orders, list value £10 or more

10% on orders list value £25 or more.

Not applicable on Access or Barclaycard purchase orders.

• We pay postage

in U.K. on orders list value £5 or over. If under, add 30p handling charge.

• We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

• We guarantee

all products brand new, clean and maker's spec. No seconds, no surplus.

• Appointed distributors for SIEMENS, VERO, ISKRA, NASCOM and many others.

OUR NEW CATALOGUE No 10

Full 128 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

ELECTROVALUE LTD

HEAD OFFICE (Mail Orders)


28(A) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London prefix 87. STD 0784) Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)

680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432 4945.

GREENWELD

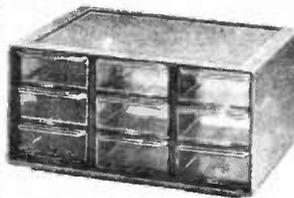443D MILLBROOK ROAD, SOUTHAMPTON SO1 0HX
All prices include VAT—just add 30p post. Tel (0703) 772501



COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors, diodes and I.C.'s. All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts!

All parts contained in clearly marked bags in a plastic storage cabinet 232 x 121 x 185mm with 9 drawers into which all parts can be neatly located. If bought individually parts plus case would cost over £47 but we are offering this for **ONLY £31.95 + £1 p & p**. Simply send a cheque or P/O for **£32.95** for immediate despatch.

CONTENTS:

- 200 ½ watt resistors
- 20 Wire wound resistors
- 70 Ceramic Capacitors
- 70 Mylar Capacitors
- 50 Polyester Capacitors
- 50 Electrolytic Capacitors
- 61 Transistors
- 12 I.C.'s
- 20 L.E.D.'s
- 55 Diodes and rectifiers

Altogether 614 components.


Price includes current catalogue and Greenweld pen for reordering supplies. Plus FREE surprise gift.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.95**

KITS OF BITS FOR EE PROJECTS

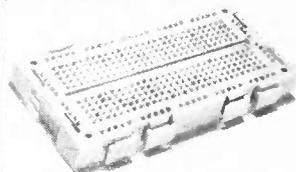We supply parts for nearly all EE projects—for a detailed components list of this month's, and previous articles, please send SAE.



VEROBLOC BREADBOARD

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC. Blocs and be joined together. Bus strips on X & Y axes—total 380 connexion points for just **£3.70**.

VU METERS

V002 Twin type, 2 meters 40 x 40mm and driver board, supplied with circuit and connexion data, **£3.50**.

V003 New type, just in. Twin type moulded in one piece, 80 x 40mm (no driver board but suitable circuit supplied), **£2.50**.

THE NEW 1980 GREENWELD CATALOGUE

FEATURES INCLUDE:

- 60p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 40p + 20p POST


WIRE & FLEX

Solid core—ideal for breadboards etc. 50 x 2m lengths many assorted colours, total 100m for **£1.30**.
Flex packs—5 x 5m lengths of multi-strand thin flex, ideal for wiring up circuits. Only 35p

3W Amp Module

Ready built and tested, this handy amplifier will prove very useful around the workshop. Just requires 17V ac source (and 8R spkr) as bridge rect and smoothing cap are mounted on the PCB. The 4 transistor circuit provides enough sensitivity for most applications. Supplied complete with circuit diagram and wiring details.

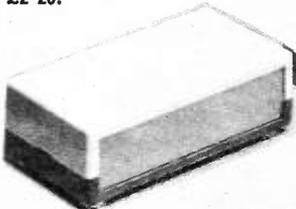Only **£1.75**. Suitable transformer **£2.20**.



VEROCASE SALE!!

3 popular sizes of Verocase at drastically reduced prices—these were part of their standard range (75-1411 etc.) but are in GREEN and have been discontinued by Vero. We have purchased their entire stock and offer them as below:

Type No	Size	Price
21050	205 x 140 x 75mm	£2.70
21052	154 x 85 x 60mm	£1.70
21053	125 x 65 x 40mm	£1.40

1A 400V RECTIFIERS

Plastic, like 1N4004, type 388F these diodes have preformed leads for horizontal mntg (15mm FC). Supersaver price—100 for **£2.30**; 500/£10 1000/£18

BUZZERS & MOTORS & RELAYS

Z401 Powerful 6V DC Buzzer all metal construction 50mm dia x 20mm 70p.
Z402 Miniature type Buzzer 3-9V, only 22 x 15 x 16mm. Very neat 65p.

Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only **£1**.

Z451 12V high torque motor 30mm dia x 40mm high, with 10mm spindle, 85p.

W892 Heavy duty 12V relay, ideal for car use—single 15A make contact. Coil 25R.
W890 DIL reed relay—SPCO 2.4V-10V 200R coil. Only **£2.20**.

TEACH IN 80

We are again supplying all parts required for this major series which started in October. The price for all the Tutor Deck parts is **£19.50**. Also supplied without breadboard for **£13.50**. The price for the additional components required for Parts 1-6 is **£2.00**. All prices include VAT and Postage. Reprints of Oct & Nov parts 30p ea.



20 x 20 WATT STEREO AMPLIFIER
Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS 40 x 40 watts peak for use with 8 to 15 ohm speakers.
Size 14 1/4" x 3" x 10" approx. **NEW** feature—units now includes a built in four channel stereo sound facility.

£31.90
£3.00 p&p



30x30 WATT AMPLIFIER IN KIT FORM
For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4 to 15 ohms speakers.

£31.50 p&p
£3.00

SPECIAL OFFER

30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge.

£57.00
+ p&p £6.00



EMI SPEAKER BARGAIN
Stereo pair 350 kit. System consists of 13" x 8" approx woofer with rolled surround, 2 1/2" approx. Audio tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£18.25
Per stereo pair
£3.65 p&p



BSR P200
Belt drive chassis turntable unit semi-automatic, cueing device.

£25.50
p&p £2.60



SHURE M756 Magnetic Cartridge to suit

£7.95



BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use.

OUR PRICE: £12.25 £2.75



GARRARD DECK MODEL CC 10A
Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£8.15 p&p £2.05 Size 12" x 8 1/2"



UNIT AUDIO STAND
Can be used with TV too! Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors.

£3.95 £2.25 p&p
24" x 12 1/2" x 11 1/2" approx.




BARGAIN FOR PERSONAL SHOPPERS ONLY
Altone UA4 Stereo System
Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones.

complete with speakers. **£35.75**



Micro Cassette Recorder
Pocket size—home or office use or when travelling.

£14.25

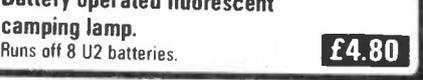

Battery operated fluorescent camping lamp.
Runs off 8 U2 batteries.

£4.80

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE
PRICE & AT OVER 25 PER PACK

SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1184/2 Stereo pre amp for ceramic and auxiliary input.
OUR PRICE p+p £1.00 **£5.00**

2 PACK 2. 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs
OUR PRICE p+p £1.00 **£7.65**

illus. **OUR PRICE p+p £1.00** **£7.65**

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.
Size approximately 9 1/4" x 8 3/4" x 4"
p&p **£2.25** **£12.25**



ACCESSORIES
Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance
£3.00
plus £1.50 p&p

Two Way Speaker Kit
Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors
£4.05
per stereo pair plus £1.55 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

BARGAINS FOR PERSONAL SHOPPERS

LCD Solar 5 function with backlite stainless steel finish case and strap **£7.40**

LCD Solar Chrono 9 function with backlite stainless steel finish case and strap **£9.55**

Chrono stop watch 9 function with back lite stainless steel finish case and strap. **£8.95**

Solar Alarm LCD stainless steel case and strap. **£21.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer **£12.20**



100 Watt Power Amp Module **£14.25**
Mains power supply for above unit **£3.60**

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers **£20.45**

'VIDEOMASTER' Super Score TV Game with pistol mains operation **£15.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation **£42.90**

ISP Radio Cassette-recorder Mains/Battery AM/FM built in mic auto stop. **£24.50**

100 WATT MONO DISCO AMP

Size approx 14" x 4" x 10 1/4"
Brushed aluminium fascia and rotary controls
Five vertical slide controls, master volume, tape level, mic level, deck level PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2 or vice versa Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak
p&p **£4.05** **£66.45**



50 WATT MONO DISCO AMP

£30.60
p&p **£2.70**
Size approx. 13 3/4" x 5 1/4" x 6 3/4"
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



BARGAIN OFFER
Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00.
P & P **£2.50**

OUR PRICE £11.95




323 EDGWARE ROAD, LONDON W2
21A HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Prices correct at 30-11-79 and subject to change without notice
NOTE: Persons under 16 years not served without parent's authorisation.

Simply ahead . .

ILP'S NEW GENERATION OF HIGH

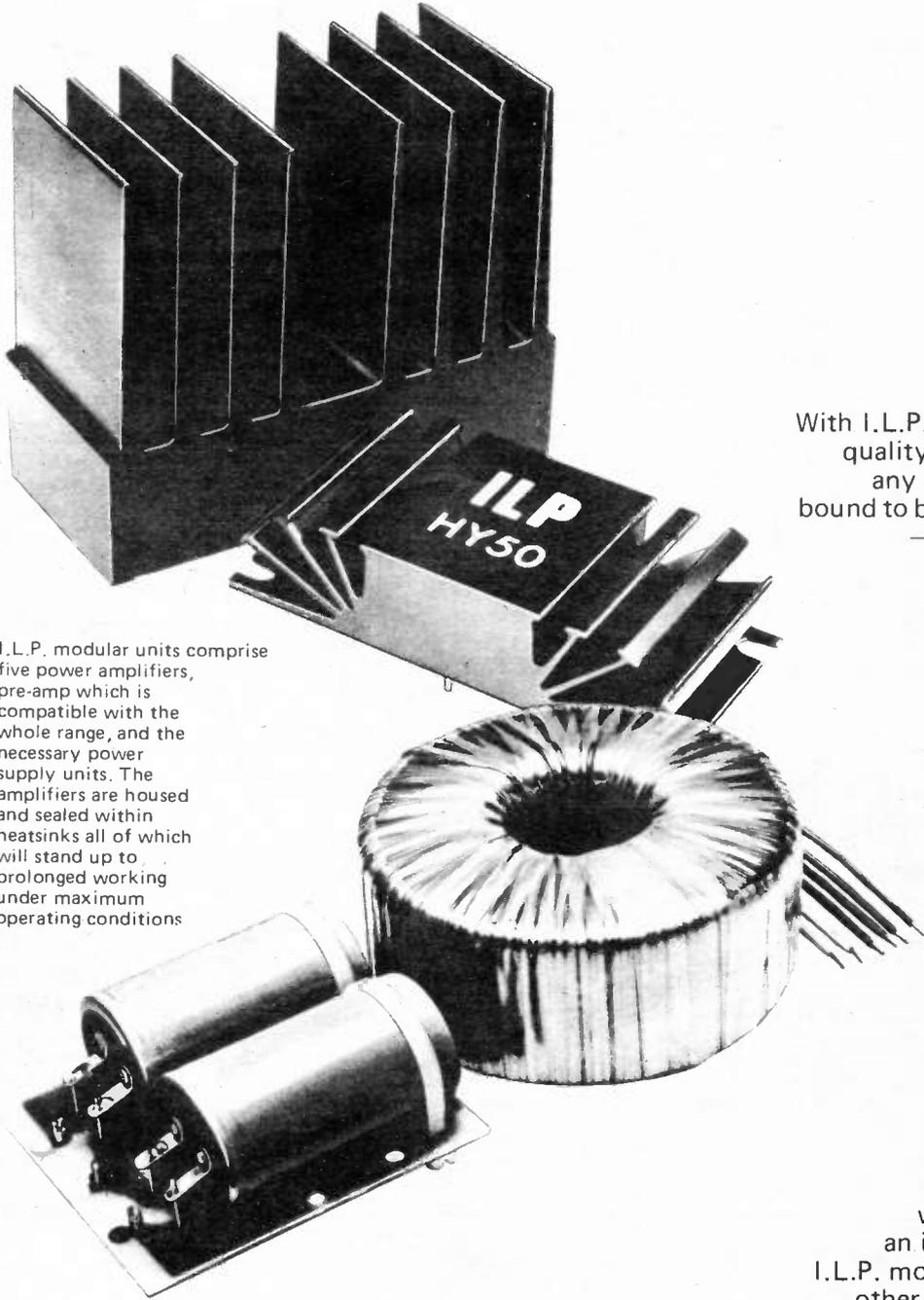

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions

With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance — and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain — the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.



**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

& also available from a number of selected stockists

and staying there

PERFORMANCE MODULAR UNITS


HY5 PRE-AMPLIFIER

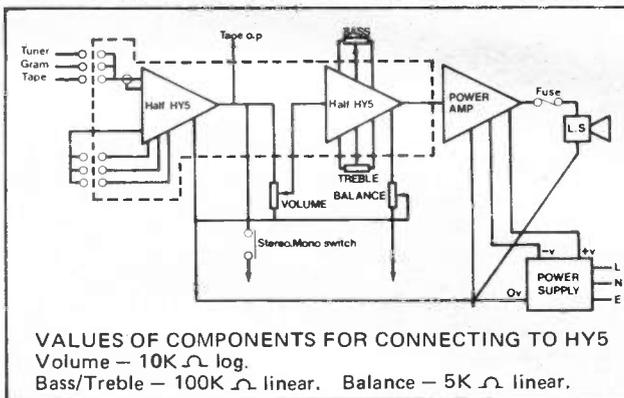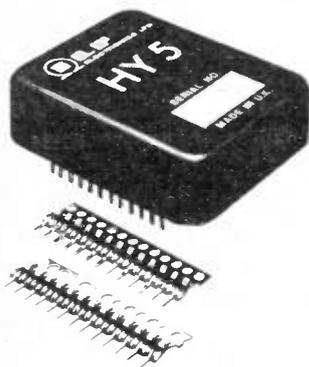


The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm, and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz - 0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT

THE POWER AMPLIFIERS

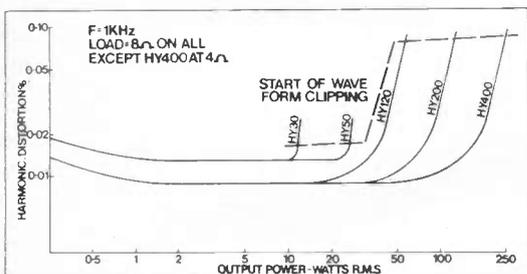


Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/ Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

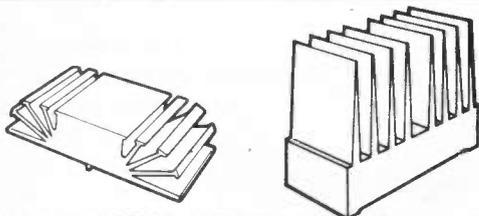

Load impedance - all models 4 - 16 Ω
 Input sensitivity - all models 500 mV
 Input impedance - all models 100K Ω
 Frequency response - all models 10Hz - 45Hz - 3dB

THE POWER SUPPLY UNITS

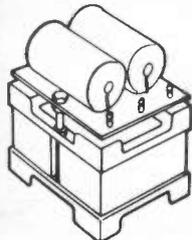

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30	$\pm 15V$ at 100ma to drive up to five HY5 pre-amps	£4.50 + £0.68 VAT
PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT

NO QUIBBLE
5 YEAR GUARANTEE

7-DAY DESPATCH ON ALL ORDERS

INTEGRAL HEATSINKS

BRITISH DESIGN AND MANUFACTURE

FREEPOST SERVICE

-see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope - we pay postage on all letters sent to us by readers of this journal.



I.L.P. ELECTRONICS LTD.

FREEPOST 3 Graham Bell House, Roper Close,
 Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778

Telex 965780

Please supply

..... Total purchase price £

I enclose Cheque Postal Orders International Money Order

Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature

EDITOR

F. E. BENNETT

ASSISTANT EDITOR

B. W. TERRELL B.Sc.

PRODUCTION EDITOR

D. G. BARRINGTON

TECHNICAL SUB-EDITOR

S. E. DOLLIN B.Sc.

ART EDITOR

R. F. PALMER

ASSISTANT ART EDITOR

P. A. LOATES

TECHNICAL ILLUSTRATOR

D. J. GOODING

EDITORIAL OFFICES

Kings Reach Tower,
Stamford Street,
London SE1 9LS
Phone: 01-261 6873

ADVERTISEMENT MANAGER

R. SMITH
Phone: 01-261 6671

REPRESENTATIVE

N. BELLWOOD
Phone: 01-261 6865

CLASSIFIED MANAGER

C. R. BROWN
Phone: 01-261 5762

MAKE-UP AND COPY DEPARTMENT

Phone 01-261 6615

ADVERTISEMENT OFFICES

Kings Reach Tower
Stamford Street,
London SE1 9LS

Projects... Theory...

and Popular Features ...

The seventies could with justice be called the decade of the digit. During the past ten years advances in semiconductor technology greatly favoured the application of digital techniques in the world of electronics.

Speed of circuit operation is the essential ingredient in electronic computing systems. Semiconductor designers and manufacturers have combined this requirement with another very important quality—that of packing a tremendous amount of circuitry inside “chips” of small size. Thus making possible, amongst other things, those personal electronic goods the digital watch and the pocket calculator.

But computing is not all. In the eighties we can expect digital or pulse code modulation (PCM) techniques to make their impact upon the recording field. Digital audio and video discs will bring about another major revolution in the hi-fi and home entertainment area.

Talking of digital techniques . . . the first practical use of electricity was to send messages over wire circuits. Samuel F. B. Morse was the inventor of the electric telegraph and also of the dot-dash code that bears his name. That was around 1838. Today it is worth remembering that the most elementary of all electric signalling methods—opening and closing a switch—is fundamental to


all electronic digital computing systems.

The morse code is still in use. By this means, radio amateurs communicate regularly over thousands of miles, often using very low transmitting power. In difficult reception conditions W/T (or c.w.) nearly always “gets through”, unlike telephony. And there are no language problems.

Thus our *Morse Practice Oscillator* is more than a sentimental gesture to the past. It is a means for acquiring an essential skill for those aspiring to obtain the full Radio Amateur Transmitting Licence.

As a fitting complement we also include in this issue a *Simple Short Wave Receiver*. Searching around the short waves never fails to offer interest, knowledge and frequently excitement as amateur and broadcast transmissions are logged from all over the world.

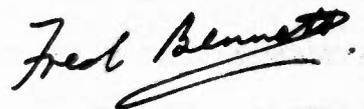And finally something else “digital” but with a difference—a certain microprocessor makes a return appearance in EE this month. This i.c. device and all its associates in circuit are shown off to the best possible advantage in our *Micro Music Box*. All of which is patently clear to see.



Our March issue will be published on Friday, February 15. See page 102 for details.

Readers' Enquiries


We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

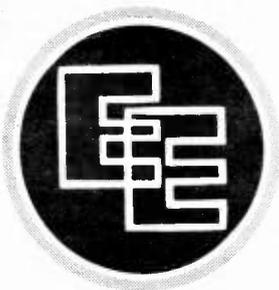All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



Everyday ELECTRONICS

VOL. 9 NO. 2

FEBRUARY 1980

CONSTRUCTIONAL PROJECTS

- SLIDE/TAPE SYNCHRONISER** For perfect accompaniment by G. N. Slee 92
MORSE PRACTICE OSCILLATOR A useful aid for the budding "ham" by S. F. Gregory 96
SIMPLE SHORT WAVE RECEIVER Covers 1.67MHz to 31.5MHz in 3 ranges by R. A. Penfold 98
EE RADIO CONTROL SYSTEM Part 4: Servo Units by L. Armstrong, H. Dickinson and W. Wilkinson 115
MICRO MUSIC BOX A traditional novelty updated by R. D. Palmer B.Sc. 125

GENERAL FEATURES

- EDITORIAL** 90
BREADBOARD 1979 REPORT A review of the constructors own exhibition by Stuart Dollin 104
COUNTER INTELLIGENCE A retailer comments by Paul Young 105
TEACH-IN 80 Part 5: Capacitance and practical capacitors by S. R. Lewis B.Sc. 106
THE ADVENTURES OF TANTY BEAD Cartoon by Matthew Read 111
SQUARE ONE Beginners Page: The art of soldering 112
RUMMAGING AROUND Money-saving ideas for the constructor by Keith Cadbury 113
SHOP TALK Retail news, products and component buying by Dave Barrington 114
CROSSWORD NO. 24 by D. P. Newton 114
BRIGHT IDEAS Reader's hints and tips 119
PLEASE TAKE NOTE Trailer Flasher Unit; Santa's Eyes; Twinkling Star 119
EVERYDAY NEWS What's happening in the world of electronics 120
FOR YOUR ENTERTAINMENT The Post Office and unauthorised telephone gadgetry by Adrian Hope 122
RADIO WORLD A commentary by Pat Hawker 124
BOOK REVIEWS A selection of recent releases 132
JACK PLUG AND FAMILY Cartoon by Doug Baker 132
SYNTHESISERS EXPLAINED—3 Voltage Controlled Amplifier, Envelope Follower and Log. Law by B. H. Baily 134
SPECIAL OFFER Mini 20 Multimeter 103

Back Issues

Certain back issues* of EVERYDAY ELECTRONICS are available worldwide price 70p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

* Not available: October 1978 to May 1979.


Binders

Binders to hold one volume (12 issues) are available from the above address for £3.75 (home and overseas) inclusive of postage and packing. Please state which Volume.

Subscriptions

Annual subscription for delivery direct to any address in the UK: £9.00, overseas: £10.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613 Kings Reach Tower, Stamford Street, London SE1 9LS.

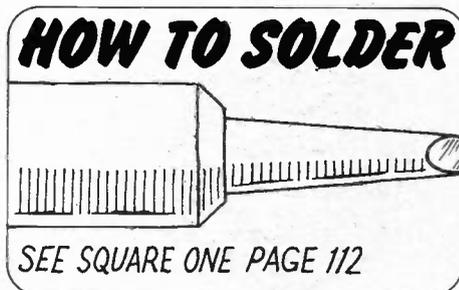© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.





slide/tape synchroniser

BY G. N. SLEE

AFTER looking through many photographic press magazines, the author was surprised to find only one advertisement for a slide/tape synchroniser. This prompted the necessity for this design which is simple, inexpensive and effective.

A slide/tape synchroniser is a must for amateur photographers who wish to give the professional touch to their slide presentation. With such a unit connected to a stereo tape recorder, the tape is programmed to change the slides in conjunction with commentary, music, or both. Any slide projector fitted with a remote control socket, may be used with this unit.

DESIGN

The synchroniser consists of three sections—a tone generator, followed by a rectifier/smoothing section and an electronic switch. When making up a slide/tape programme the unit is used to record a tone pulse on the left-hand channel of the tape at each point where a slide change is required.

Commentary and music are recorded on the right-hand channel. When the tape is played back the pulses on the left-hand channel activate the electronic switch in the synchroniser which activates the slide change mechanism in the projector.

The entire circuit, which consumes only a small standing current, is

powered by a 9V PP3 battery. The unit is sufficiently sensitive to use with the majority of reel or cassette stereo tape recorders.

In the event of the slide programme lagging behind the commentary the SYNC switch can be used as an override button when operating the unit from tape. Commentary and background music can be recorded or played back by connecting a mixer or amplifier to the audio socket.

Standard 5-pin to 5-pin 180 degree DIN recording leads are used for connections to both AMP and TAPE sockets (SK1 and 2), unless external equipment connections are different.

PULSE CIRCUIT

The tone generator stage consists of TR1, TR2, C1, C2, R1, R2, R3 and R4 and associated components wired to make up a multivibrator whose frequency f is determined by the formula.

$$f = \frac{1}{0.7(C1R3 + C2R2)}$$

In this particular circuit the values of C1 and C2 are the same as those of R2 and R3. This means that the formula can be simplified to

$$f = \frac{1}{1.4 RC}$$

where R is R2 or R3 and C is C1 or C2.

The output is then passed through an attenuator network made up of C3, R5 and R6 before going to the SYNC switch S1. This is a momentary action d.p.s.t. type. Capacitor C3 is included to block d.c. and to shape the tone output.

The supply to the tone generator is controlled by S1b, and S1a switches the output. When this is pressed and released it provides a tone burst to the next stage and to the TAPE input/output socket SK1.

Although switch S1b is conventionally placed in the negative supply line, this has proved advantageous in the wiring of the unit.

The output to the tape is taken directly from the other side of S1a to pin one of a 5-pin 180 degree DIN socket SK2.

The next stage is controlled by S1 supplying the pulse when recording, or the tape on playback.

ELECTRONIC SWITCH

On arrival at the base of TR3 the pulse is amplified and then rectified into d.c. by D1 and D2 and smoothed by C6. This voltage applied to the base of TR4 causes the Darlington pair TR4 and TR5 to turn on hard, energising the relay. Diode D3 is included to protect these transistors against any back e.m.f.

The relay chosen has a coil resistance of 185 ohms and an operating range of 5.5V to 17V (nominal 12V). A coil resistance less than this could

The Slide/Tape Synchroniser showing front panel layout and input/output sockets.

damage TR4 although a higher coil resistance could be used. The specified relay should not be used to switch mains loads.


A set of normally open contacts are wired to pins 2 and 3 of the PROJECTOR socket SK3. The other end of the lead into SK3 is terminated in a suitable connector for the projector, normally a 6-pin 240 degree DIN. Two-core lighting flex is suitable for interconnecting the unit to the projector, connections being made from pin 3 to pin 3 and pin 2 to pin 2 respectively. (Check with your handbook.)

To stop relay chatter, a 100 ohm resistor R11 and a 0.1 microfarad capacitor C7 are connected in series across pins 2 and 3 of the synchroniser projector socket forming a contact arc suppressor.


CONSTRUCTION
starts here

The synchroniser is housed in a small module box. This is made of an A.B.S. plastics material with an aluminium lid, and incorporates circuit board guides, which are used to mount the two circuit boards. The tone generator circuit is built on one board (Fig. 2) which is 15 strips by


Fig. 1. The complete circuit diagram of the Slide/Tape Synchroniser showing connections to amplifier, recorder and projector.

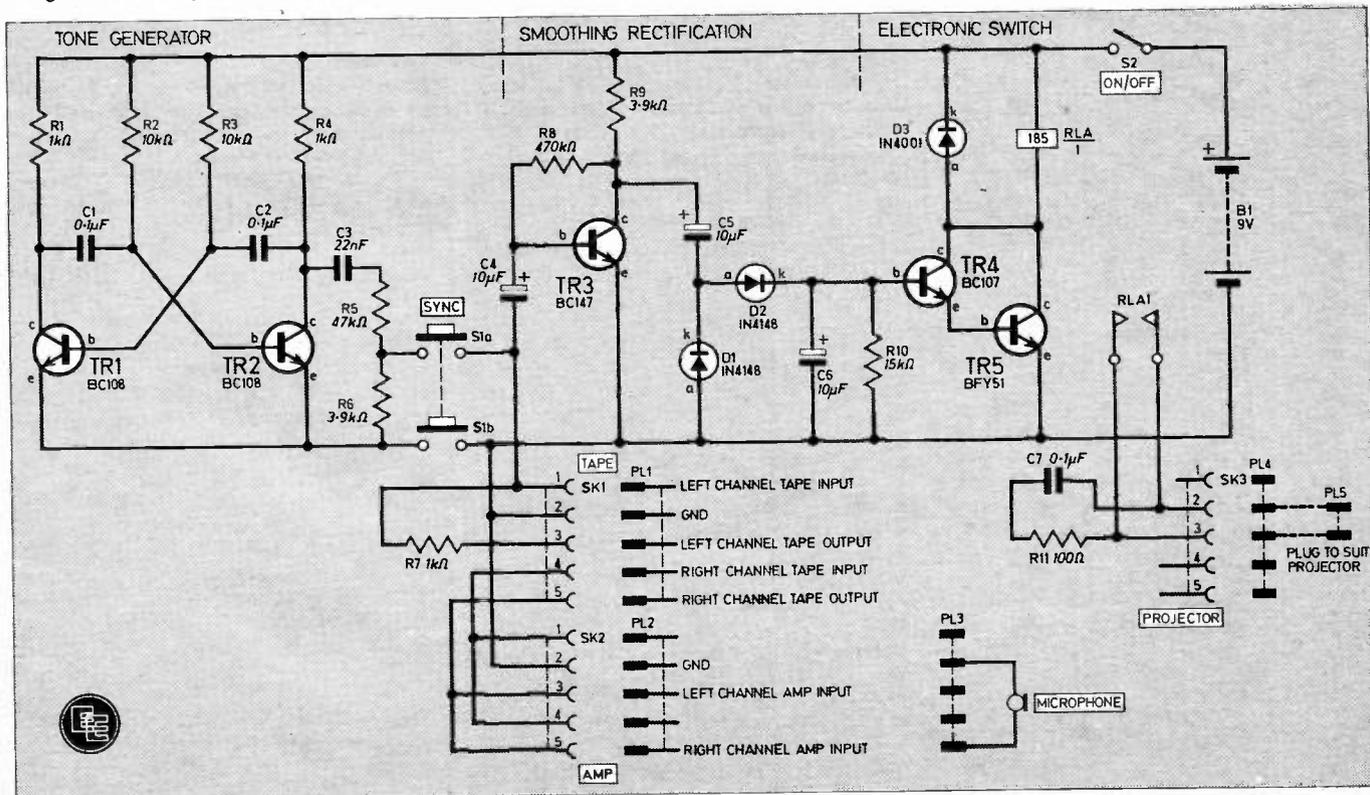


slide/tape synchroniser

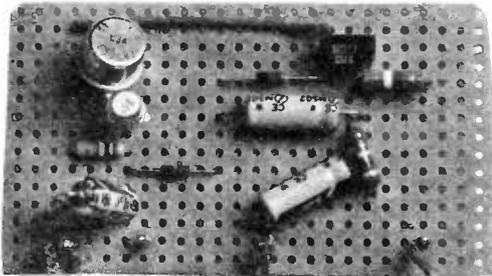



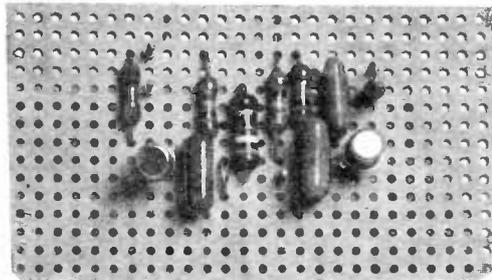
Completed electronic switch circuit board.



Completed tone generator circuit board.

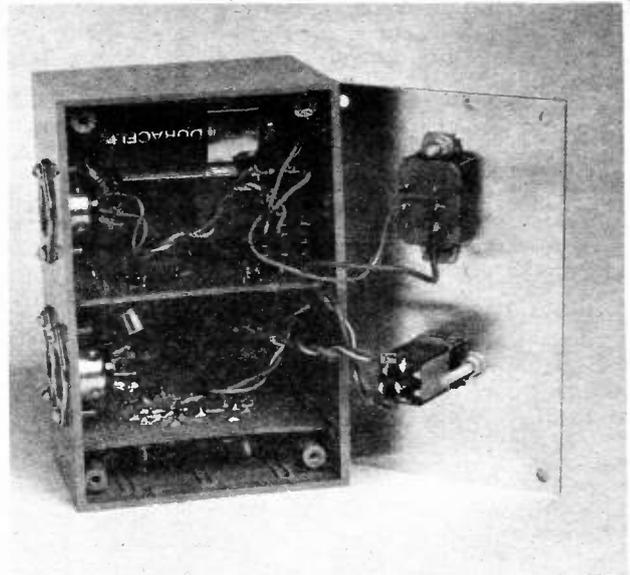

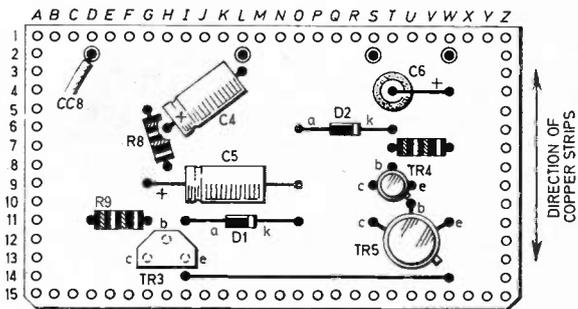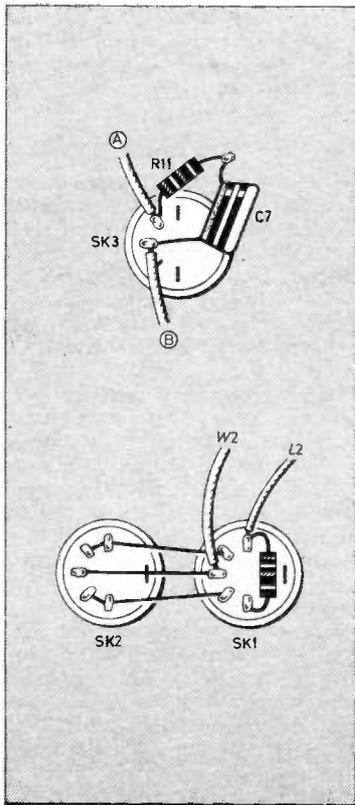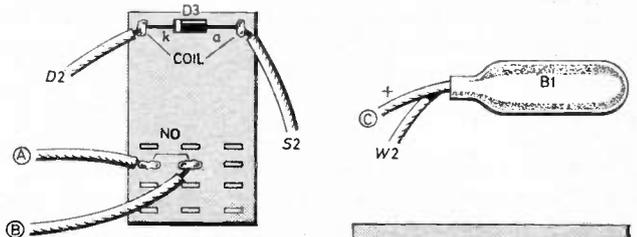Front panel removed showing the circuit boards "sandwiched" in the case.



● = VEROPINS
⊗ = BREAKS IN COPPER STRIP

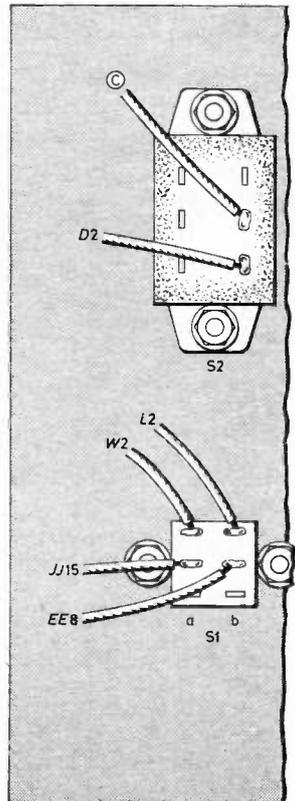
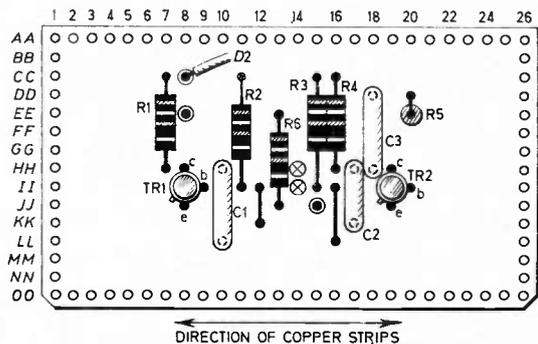


Fig. 2. Internal wiring showing circuit board layouts and interconnections.

26 holes, the sides of which are tapered to fit the guides as shown.


The electronic switch is built on the other board (Fig. 2) which is 26 strips by 15 holes, the sides of which are also tapered. Both boards are 0.1 inch matrix s.r.b.p. stripboard.

The breaks in the strips are made first with either a spot face cutter or a hand-held twist drill (5mm). Double-sided Veropins are recommended for lead-outs from the boards. These are soldered in position first and then the link wires followed by the rest of the components, leaving the transistors until last. Care should be taken to avoid overheating these which could cause damage.

Components should be as close to the board as possible and their physical size should also be as small as possible, especially in the case of the Astable board, otherwise this will not fit in the case.

Before mounting anything in the case, the holes for the DIN sockets are drilled as indicated in Fig. 2. Next the top panel is drilled to suit the switches. Because of the compact proportions of the box it is advisable to wire the sockets before the circuit boards are installed. Thin flexible stranded wire is used for all connections.

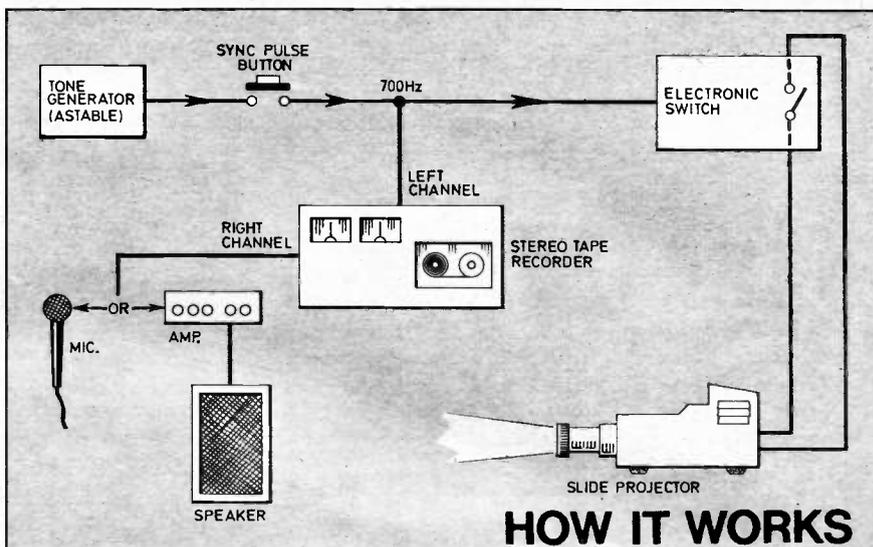The relay is connected upside-down with its connections pointing upwards by means of double-sided sticky pads.



A tone generator provides a tone of frequency 700Hz. When the sync button on the Synchroniser is pressed, the tone is applied to the electronic switch and also to the left hand channel of the tape recorder (set on "record"). The effect of this is to activate the switch which changes the slide and also to record a tone burst on the tape.

Music and commentary are recorded on the right hand channel of the tape at the same time.

When the programme is repeated, the commentary and music are reproduced from the right hand channel of the tape whilst the tone bursts on the left hand channel activate the electronic switch and change the slide at the appropriate time.

COMPONENTS

Resistors

R1 1k Ω	R7 1k Ω
R2 10k Ω	R8 470k Ω
R3 10k Ω	R9 3.9k Ω
R4 1k Ω	R10 15k Ω
R5 47k Ω	R11 100 Ω
R6 3.9k Ω	

All $\frac{1}{4}$ W carbon $\pm 5\%$

Capacitors

C1 0.1 μ F polyester	C5 10 μ F 25V elect.
C2 0.1 μ F polyester	C6 10 μ F 25V elect.
C3 22nF polyester	C7 0.1 μ F polyester
C4 10 μ F 25V elect.	

Semiconductors

TR1 BC108 npn silicon
TR2 BC108 npn silicon
TR3 BC147 npn silicon
TR4 BC107 npn silicon
TR5 BFY51 npn silicon
D1 1N4148 small signal silicon diode
D2 1N4148 small signal silicon diode
D3 1N4001 50V 1A silicon diode

Miscellaneous

S1 d.p.s.t. momentary miniature push button
S2 s.p.s.t. miniature toggle
SK1, SK2 5-pin 180 degree DIN socket (2 off)
SK3 5-pin DIN socket
RLA 12V relay, coil resistance 185 Ω with two sets of changeover contacts
B1 PP3 type 9 volt battery
PL1-4, 5-pin 180 degree DIN plug (4 off)
PL5 To suit projector

0.1 inch matrix strip board, one piece 15 strips by 26 holes, one piece 26 strips by 15 holes; battery clips; Veropins; connecting wire; sticky pads; case (R.S. type 348-908 or similar)

See
**Shop
Talk**
page 114

COMPONENTS
approximate
cost **£7**
excluding case

The battery is placed in position first and the relay is placed tightly against the battery. This forms a kind of battery clip. Make sure of course you are able to remove the battery.

IN USE

The unit is connected to a projector and a stereo recorder or cassette deck. A microphone is connected to the right-hand channel and the left-hand channel is used for the synchroniser. Alternatively a mixer can be connected to the AMP socket of the synchroniser to provide music and commentary.

The unit is then switched on and the recording level is set for the left-hand channel by holding the sync-pulse button down. The slide magazine is now set to the first slide and recording is started. Commentary is given for the first slide and then the sync button is pressed and released. This changes the slide and records a tone on the tape.

The process is repeated until the last slide is reached and then the recording is stopped. When required, the slide magazine is reset to the beginning in the usual manner, the tape rewind, and an amplifier connected to the AMP socket. The tape is started and the recorded programme is replayed automatically with the commentary synchronised to its particular slide. □

MORSE PRACTICE OSCILLATOR

By S. F. Gregory



This simple unit was built for the author's friend who is a keen short wave listener. After being on the receiving end for so long he felt that he would like to be able to transmit so he has decided to attend night school for a year's study and then attempt the Radio Amateurs Examination and the Morse examination.

The Morse exam involves the sending and receiving of Morse code characters at a speed of 12 words per minute for a period of three minutes, and the sending and receiving of 10 groups of 5 figures in each group for 1½ minutes.

To reach this standard a generally agreed figure of about 60 to 65 hours of practice is necessary but this can vary considerably between individuals.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Morse Oscillator is shown in Fig. 1.

It uses two transistors which form a complementary astable multivibrator in conjunction with R1 and C1. When the key S1 is pressed C1 will commence to charge through R1. When it has charged to approximately 0.2V TR2 will conduct. This in turn switches TR2 into conduction but C1 will now be shorted out and it will therefore lose its charge and result in TR1 and TR2 switching "off".

Capacitor C1 will now commence to charge up again, and the above process will repeat itself as long as the key is held down.

Every time TR1 and TR2 conduct, a pulse of current will flow through the loudspeaker and with the capacitor and resistor used, these pulses will be of an audio rate and result in a tone at the loudspeaker.

If it is desired, the audio output can be made variable by connecting a 10kΩ variable potentiometer, VR1 in circuit, and lowering the value of R1 to about 82kΩ. To do this, the connection at point A is broken and VR1 inserted in series.

ASSEMBLY

The oscillator is constructed on a piece of 0.1 inch matrix stripboard size 24 holes × 10 strips. After cutting the board to the required size and drilling the two mounting holes, it is advisable to remove any jagged edges with a small file. The single break can now be made in the copper strip as shown in Fig. 2.

The next step is to insert R1, C1, TR1 and TR2 ensuring that a heat sink is used on the transistor leads as semiconductors are likely to be damaged due to excessive heat.

The unit is mounted in a plastics box size 80 x 115 x 35mm. It should first be prepared by drilling all mounting holes, and the aperture holes for the loudspeaker (see Fig. 2).

When all rough edges have been filed smooth, the loudspeaker can be carefully glued in position and the rest of the components mounted according to Fig. 2.

It is unnecessary to provide an on/off switch for the completed unit, as the key acts as a switch.


A battery holder can be fabricated using a piece of wood or circuit board guide and some pieces of foam. Connections are made using the negative connectors from two sets of PP9 battery connector clips.

During long sessions of practice, it is advisable that the key is secured to a block of heavy wood, or similar heavy object, so as to prevent undesired movements which could result in bad sending in the long run.

LEARNING THE CODE

When a newcomer commences to learn the Morse Code he must think of each individual character in dit dah form and *not* as dots and dashes. The reason for this is that no sense of rhythm is achieved when using dots and dashes and without the sense of rhythm, the recognition of characters when listening on a receiver becomes very difficult.

Fig.1. Full circuit diagram of Morse Practice Oscillator

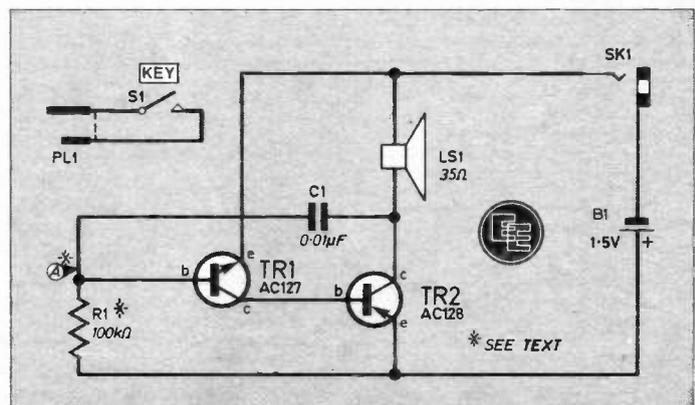


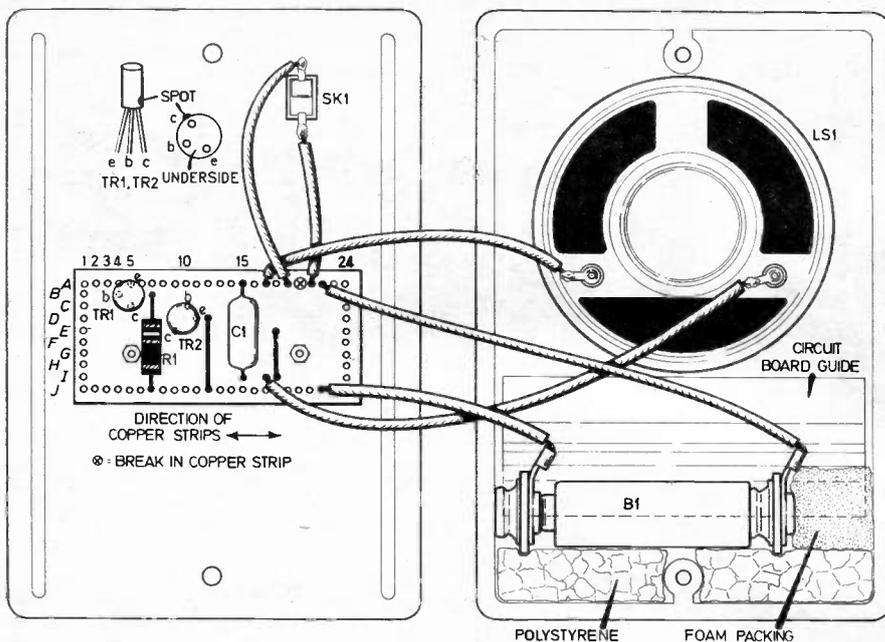


Fig. 2. (above) Assembly and layout details. Note circuit board layout and the position of the one break in the copper strips. (left) Interior layout of oscillator.

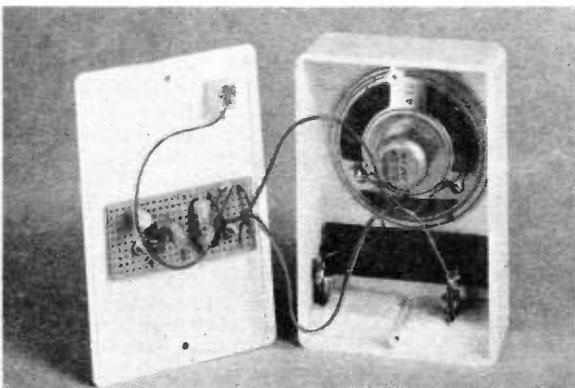

COMPONENTS
 approximate
 cost **£2.50**
 excluding case

COMPONENTS

Resistor

R1 100kΩ (see text)
 Carbon ¼W ± 10%

Capacitor

C1 0.01μF polyester

Semiconductors

TR1 AC127 germanium *npn*
 TR2 AC128 germanium *pnp*

Miscellaneous

B1 1.5V type HP7 or similar
 S1 Morse key with normally open contacts
 LS1 miniature moving coil loud-speaker, 35 to 80 ohms impedance
 SK1 3.5mm miniature jack socket
 PL1 3.5mm miniature jack plug
 Plastics case, 80 × 115 × 35mm;
 0.1 inch matrix stripboard, 24 holes × 10 strips; 6BA nuts and bolts for stripboard mounting; interconnecting wire; battery connectors (see text); foam and circuit board guide or fillet of wood for battery clip.

As soon as the person learning the code is capable of recognising the individual characters in dit dah form he has completed the first stage in learning the Morse Code.

The next stage is to be able to receive at the necessary speed. This will only come about by practising with a person who already knows the Morse code or if such a person is not available it is advisable that he joins a reputable amateur radio club in the area in which he lives.

The address of many amateur radio clubs in your area can be obtained by writing to the R.S.G.B. As soon as your receiving is up to standard learning to send can now be attempted. This is where this month's article comes in use.

It has often been said that a good sender is as good as his key. We therefore stress that a good rugged Morse key is used and not one of the cheap tinny tappers which are on the market at present. A good key can usually be purchased from army surplus stores for a few pounds. ✕

THE INTERNATIONAL MORSE CODE


A di-dah	1 di-dah-dah-dah-dah
B dah-di-di-dit	2 di-di-dah-dah-dah
C dah-di-dah-dit	3 di-di-di-dah-dah
D dah-di-dit	4 di-di-di-di-dah
E dit	5 di-di-di-di-dit
F di-di-dah-dit	6 dah-di-di-di-dit
G dah-dah-dit	7 dah-dah-di-di-dit
H di-di-di-dit	8 dah-dah-dah-di-dit
I di-dit	9 dah-dah-dah-dah-dit
J di-dah-dah-dah	0 dah-dah-dah-dah-dah
K dah-di-dah	
L di-dah-di-dit	
M dah-dah	
N dah-dit	
O dah-dah-dah	
P di-dah-dah-dit	
Q dah-dah-di-dah	
R di-dah-dit	
S di-di-dit	
T dah	
U di-di-dah	
V di-di-di-dah	
W di-dah-dah	
X dah-di-di-dah	
Y dah-di-dah-dah	
Z dah-dah-di-dit	

Note

One "dah" should be equal to three "dits" in length. The space between parts of the same letters should be equal to one "dit".

The space between two letters should be equal to three "dits".

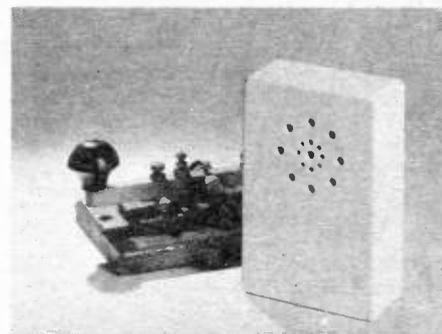The space between two words should be equal to six "dits".





Simple S.W. Receiver

By R. A. Penfold

The receiver is suitable for both Amateur Band and Broadcast Band listening as it is capable of resolving c.w. (Morse) and s.s.b. (single side-band) transmissions, as well as ordinary a.m. (amplitude modulation) transmissions.

A frequency coverage of about 1.67 to 31.5MHz in three ranges can be obtained, and so the set covers the entire s.w. frequency spectrum. The approximate coverage of each range is given below. The Range numbers are those used by the manufacturer of the coils employed in the unit.

Range 3 1.67 to 5.3MHz (180 to 57 metres).

Range 4 5 to 15MHz (60 to 20 metres).

Range 5 10.5 to 31.5MHz (28 to 9.5 metres).

Plug-in band changing is used, the desired band being selected merely by plugging the appropriate coil into the coil holder.

Although a proper outdoor antenna is required in order to obtain optimum results from the receiver, a

large number of stations can be received using a short indoor aerial.

THE CIRCUIT

Only two transistors are used in the receiver, as can be seen by reference to the circuit diagram shown in Fig. 1. The aerial signal is coupled to the primary winding of L1. Normally the aerial is plugged into SK2 so that there is direct coupling here, but with very strong input signals present SK1 can be used instead. Losses through C2 will then prevent overloading.

TR1 is a field effect transistor (f.e.t.), and as such it has an extremely high input impedance. The tuned winding of L1 can therefore be coupled direct to TR1 gate without there being any detrimental effect on performance. The variable capacitors C3 and C4 are both forms of tuning control, and they are termed the "Bandspread" and "Bandset" controls respectively. These terms are fully explained in the section dealing with operation of the set.

Transistor TR1 is used in the common source mode, with R1 acting as the source bias resistor and C3 as its r.f. bypass capacitor. The choke L2 acts as the drain load for TR1, and the amplified gate signal appears at TR1 drain.

REACTION

Some of this signal is coupled back to the input of the circuit via the third winding of L1, and C1, the latter being used to control the amount of feedback. This feedback is usually termed "regeneration", and is also known as "reaction". It has the obvious effect of increasing the gain of the receiver, but it also boosts selectivity.

THE short wave receiver which is described in this article has been designed to combine both simplicity and good performance. A circuit of the t.r.f. (tuned radio frequency) type is used as this avoids the complexities of a superhet circuit, including the need for any complicated alignment of the finished receiver.


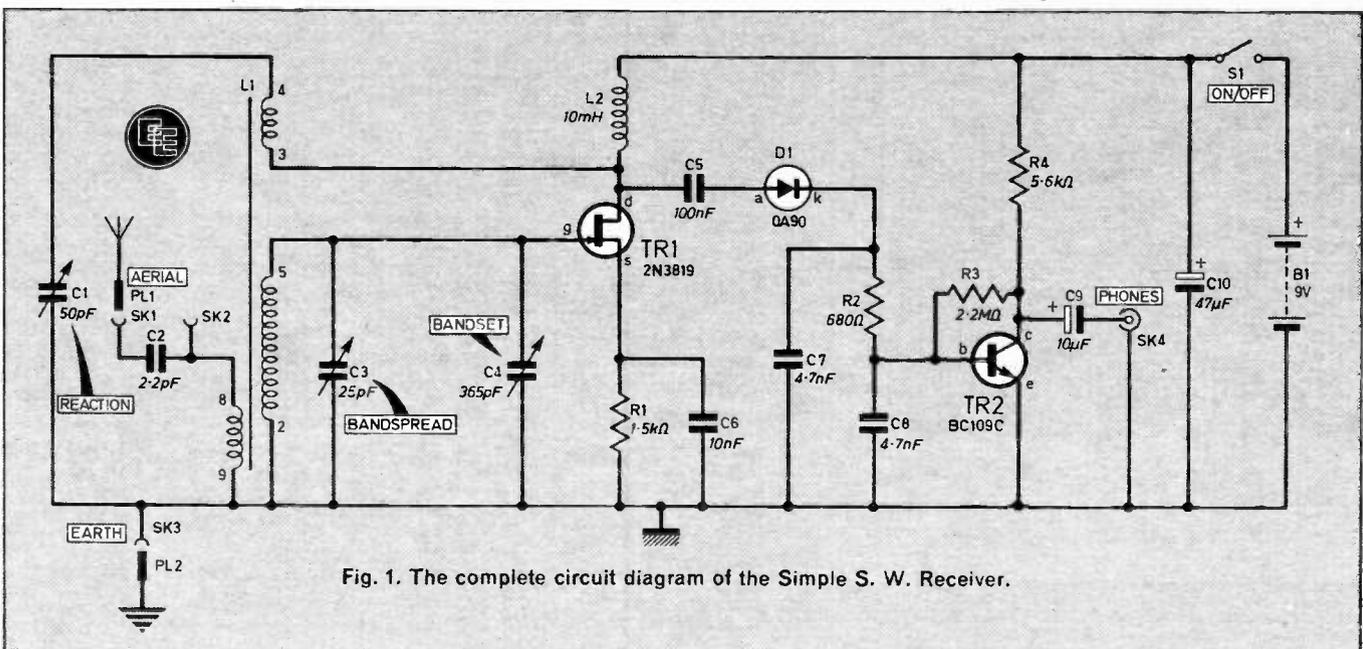


Fig. 1. The complete circuit diagram of the Simple S. W. Receiver.

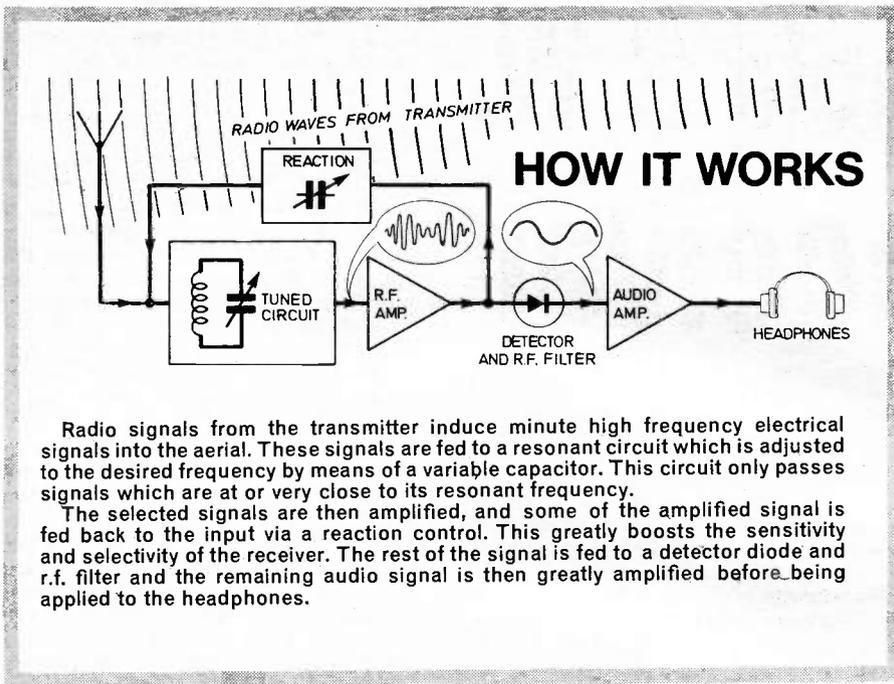

Radio signals from the transmitter induce minute high frequency electrical signals into the aerial. These signals are fed to a resonant circuit which is adjusted to the desired frequency by means of a variable capacitor. This circuit only passes signals which are at or very close to its resonant frequency.

The selected signals are then amplified, and some of the amplified signal is fed back to the input via a reaction control. This greatly boosts the sensitivity and selectivity of the receiver. The rest of the signal is fed to a detector diode and r.f. filter and the remaining audio signal is then greatly amplified before being applied to the headphones.

Layout details of the front and rear panels are shown in the photographs and this is quite straightforward apart from the 19mm diameter cut out in the rear panel. Ideally this should be made using a chassis punch, but in the absence of a suitable punch, it can be made using a miniature round file or a fretsaw.

Variable capacitor C4 is mounted by means of a 12mm long 4BA bolt. A 4mm diameter mounting hole is drilled for this in the base panel of the case, 18mm back from the front panel, and in line behind the hole for the spindle of C4. Spacers must be used over the mounting bolt to hold the capacitor 8mm clear of the bottom of the case. The author used a couple of 2BA full nuts here.

Note that the mounting bolt should not be more than about 12mm long, as there is otherwise a risk that it will penetrate too far into the capacitor and cause damage to the sets of metal vanes. The mounting bolt fits into a ready-made 4BA threaded hole in the underside of C4.

Selectivity is the ability of a receiver to pick up just one of several closely spaced transmissions. Good selectivity is extremely important in a s.w. receiver as the s.w. bands are extremely crowded.

Reaction improves selectivity as it provides the greatest boost in gain towards the centre of the receiver's passband where the set will be most sensitive to the feedback, just as it would be to any other signal.

There is a limit to the useful amount of reaction which can be applied to the circuit, as exceeding this limit will cause TR1 to oscillate. The reaction level is adjusted to just below the threshold of oscillation for a.m. reception, and just beyond this threshold for c.w. and s.s.b. reception.

DETECTOR AND AMPLIFIER

The output from TR1 is coupled to an ordinary diode detector by way of d.c. blocking capacitor C5. Components C7, R2, and C8 provide r.f. filtering at the detector output, and the remaining audio signal is fed straight into the base of TR2.

TR2 is used as a high gain common emitter amplifier, and it feeds a pair of high impedance headphones via d.c. blocking capacitor C9.

Despite its simplicity the circuit provides excellent results. The use of high gain low noise transistors plus reaction results in good sensitivity and selectivity. Unlike some t.r.f. designs this set also has a very low background noise level, this being aided by the use of a separate diode detector rather than the more usual regenerative detector.



CHASSIS

The case is actually a 203×63.5×152mm 18 s.w.g. aluminium chassis with baseplate. This is used upside down, so that the baseplate becomes the lid. The lid can be held in place by four self-tapping screws which fasten it to the corner pieces of the chassis, but this was not necessary on the prototype where the lid was a tight fit and simply clipped into position.


COIL MOUNTING BRACKET

The coil units have a 9-pin base which fits into a standard B9A valveholder. This enables a B9A valveholder to be used as a coil holder, with the desired range being selected by merely plugging in the appropriate coil unit.

However, the receiver has to be arranged so that there is easy access to the coil holder in order to facilitate easy band changing. In this case the coil holder is mounted vertically behind a cutout in the rear panel. It is mounted on an 18 s.w.g. aluminium bracket, and details of this are provided in Fig. 2. The positions of the two small mounting holes for the coil holder are found using the holder as a template.

Mount the coil holder so that pins 1 and 9 are uppermost. This makes it easy to give the coil the correct orientation when it is plugged in.

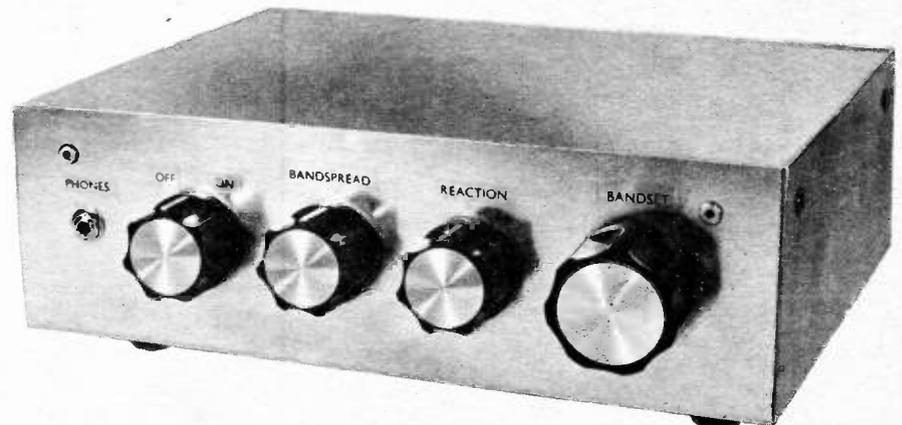The bracket is positioned so that the top of the coil holder is about



COMPONENTS



Resistors

- R1 1.5k Ω
- R2 680 Ω
- R3 2.2M Ω
- R4 5.6k Ω
- All $\frac{1}{4}$ W carbon $\pm 5\%$

See
**Shop
Talk**
page 114

Capacitors

- C1 50pF air spaced variable (Jackson type C804)
- C2 2.2pF ceramic or plastic
- C3 25pF air spaced variable (Jackson type C804)
- C4 365pF air spaced variable (Jackson type 0)
- C5 100nF polyester
- C6 10nF plastic foil
- C7 4.7nF polystyrene
- C8 4.7nF polystyrene
- C9 10 μ F 10V elect.
- C10 47 μ F 10V elect.

COMPONENTS
approximate
cost **£15**
including three coils

Semiconductors

- TR1 2N3819 *n*-channel f.e.t.
- TR2 BC109C *n*p*n* silicon
- D1 OA90 germanium small signal diode

Inductors


- L1 Derico Green dual purpose coil, ranges 3, 4 and 5
- L2 10mH r.f. choke Repanco type CH4

Miscellaneous


- SK1, SK2 4mm sockets, red (2 off)
- SK3 4mm socket, black
- SK4 3.5mm jack socket
- PL1, 2.4mm plugs (one red, one black)
- B1 9V PP3 type
- S1 s.p.s.t. rotary type

Aluminium chassis 203 x 64 x 153mm with baseplate; stripboard: 0.15 inch matrix 13 strips by 9 holes; B9A valve-holder for coil; control knobs, 3 small, 1 large; PP3 battery connector; 18 s.w.g. aluminium for coil mounting bracket; interconnecting wire; 4BA nuts and bolts (4 off); 4BA spacing collars for circuit board mounting (2 off).

Simple S.W. Receiver

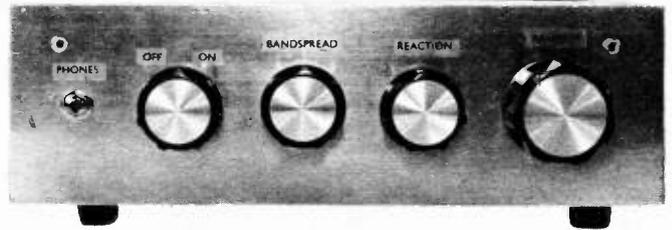

Front view of completed S.W. Receiver.

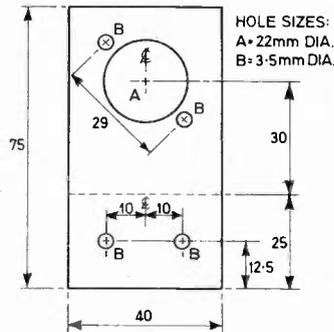

ALL DIMENSIONS IN mm.

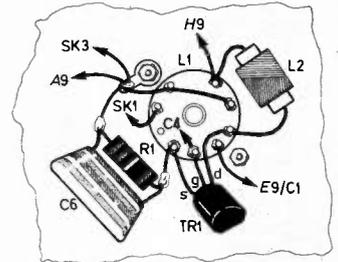


Fig. 3. Wiring of the r.f. components on the coil holder.

Fig. 2. Drilling details for the coil holder bracket.


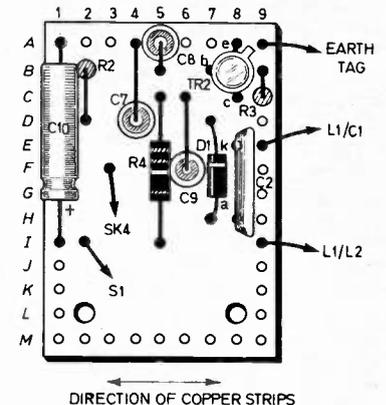
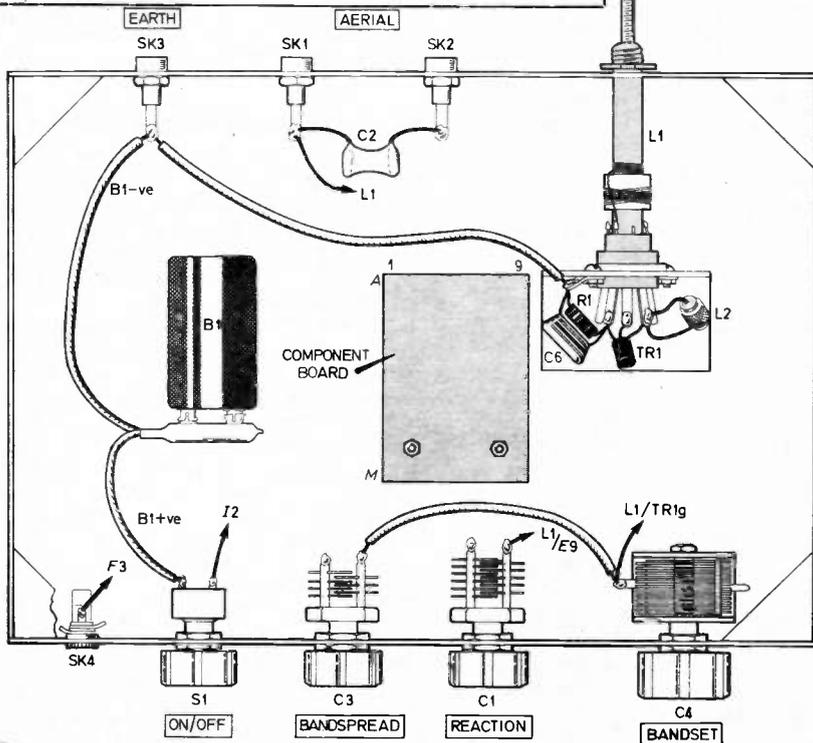
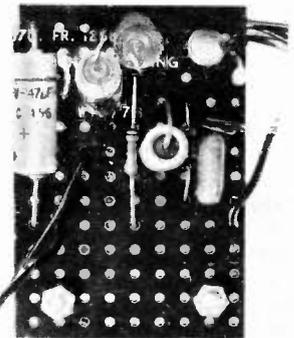


Fig. 4 (left). Interior of the receiver showing point to point wiring of the components. Fig. 5 (above). Close up view of the top of the circuit board. Note that there are no breaks in the copper strips.

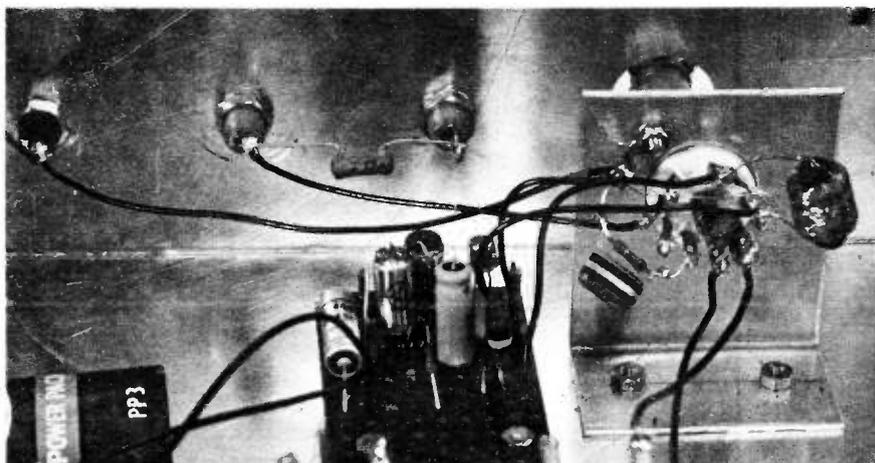

View of the inside of the receiver showing the circuit board, coil holder bracket, and rear panel.

27 to 30mm back from the rear panel of the case, and immediately behind the cutout in the rear panel. It is secured using a couple of short M3 or 6BA bolts. The coil holder is mounted on its bracket in the same way, and a soldertag is secured on the mounting bolt nearest to pins 1 and 9 of the holder.

WIRING

The audio and detector components are wired up on a piece of 0.15in matrix stripboard 13 strips by 9 holes. Details of this panel are provided in Fig. 5. The other wiring of the receiver can be seen in Fig. 4. This is all of the point-to-point type.

Construction of the panel commences with the two 3.2mm diameter mounting holes being drilled, and then the components are soldered into position.

The completed board is then wired up to the rest of the unit before it is mounted on the base of the case just to the left of L1. Spacers are used to hold the panel about 10mm or so clear of the case.

The remaining wiring can then be completed. Try to keep the r.f. wiring reasonably short and direct (see Fig. 3). The ends of component lead-out wires, tags, etc., should all be generously tinned with solder prior to making a joint. There should then be no problems with dry joints.

AERIAL AND EARTH

The set is designed for use with an ordinary long-wire antenna. If possible, this should consist of about 10 to 40 metres of aerial wire mounted outside, as high as possible, and preferably clear of buildings or similar obstructions.

As mentioned earlier, a fairly short indoor aerial will provide quite good results, although reception will obviously not be as good as when using a long outdoor aerial. An

indoor aerial can consist of a few metres of aerial wire fixed along a wall close to the ceiling.

An earth connection is by no means essential, and is likely to be of little or no benefit except on Range 3. An earth connection usually consists of an insulated lead connected to a metal spike or piece of thin pipe which is driven into the ground. Do not use a water pipe, gas pipe, or mains earth.

USING THE RECEIVER

Ideally the receiver should be used with a pair of good quality high impedance headphones, but inexpensive high impedance phones are also suitable, and even a crystal earpiece can be used.

Under normal circumstances the aerial should be plugged into SK2, but if this causes overloading the aerial should be connected to SK1 instead. Overloading will be made evident by an abnormally high background noise level and an apparent worsening of the selectivity.

Switch S1 is an ordinary on/off device.

The variable capacitor C1 should not be regarded as an ordinary volume control though, and it is not used in the same way. With C1 backed right off (the two sets of vanes unmeshed) very few (if any) stations will be received. As it is advanced, the sensitivity and selectivity of the set will considerably increase.

However, advancing this control too far will cause the r.f. amplifier to break into oscillation. This will be accompanied by an increase in the background noise level, and a varying tone will be heard as the set is tuned across an a.m. station. It is impossible to correctly resolve a.m. signals with the set in this condition.

For optimum results on a.m. signals the receiver should be adjusted to just below the point at which oscillation occurs. This is somewhat

harder than it might at first appear as C1 will need slight readjustment each time the tuning is significantly altered. A certain amount of skill has to be acquired before the operator will obtain the best from the receiver.

Amplitude modulation (a.m.) is the mode of transmission used on the s.w. broadcast bands, and most of the popular broadcast bands fall within the coverage of the Range 4 coil (the 49, 41, 31 and 25 metre bands).

AMATEUR BANDS

The main transmission modes used on the amateur bands these days are c.w. and s.s.b. and these can be resolved by adjusting C1 slightly beyond the threshold of oscillation. Do not advance C1 any further than is necessary to cause oscillation as this will result in a loss of sensitivity.

The exception to this is when an extremely strong s.s.b. signal is being received. Such signals can overload the set unless C1 is advanced slightly more than normal.

When receiving c.w. signals the tuning controls are adjusted to produce an audio note of the desired pitch. When resolving an s.s.b. signal the tuning controls must be adjusted to produce an audio output of a realistic pitch.

The amateur bands which will provide the most interesting results are the 80 and 20 metre bands. The 80 metre band appears at the high frequency end of Range 3 (C4 adjusted almost fully anticlockwise) and the 20 metre band can best be received at about the middle of Range 5 (it also appears at the high frequency end of Range 4).

BANDSET AND BANDSPREAD

Variable capacitor C4 is the main tuning or "Bandset" control, but tuning will be difficult using this, especially on Range 5, and when tuning c.w. and s.s.b. signals. For this reason the "Bandspread" control C3 is included in the circuit.

Tuning is very cramped using C4 as it covers such a wide range of frequencies. This is not the case with C3 which has a much lower value, and therefore only covers a limited range of frequencies. Tuning is best accomplished by setting C4 to the part of the range which is to be scanned for signals, and then actually searching for signals using C3.

Finally, the coils have an adjustable core which affects the frequency coverage. As supplied, this core is fully screwed down for packing purposes. In use the core should be unscrewed slightly so that roughly 10mm of metal screwthread protrudes from the top of the coil. ☐

NEXT MONTH

PROJECTS AROUND THE HOME

CABLE AND PIPE LOCATOR

An essential tool for the handyman. For detecting the presence and tracing the route of metallic pipes and cables buried under plaster or under floorboards, for example.

DOOR BELL REGISTER

Records that someone has called during absence of occupant. Operation of doorbell causes l.e.d. to light and remain on until cancelled manually.

KITCHEN TIMER

Operating periods available: from 1 minute to 2 hours in 1 minute stages. Audio alarm.

STEREO HEADPHONE AMPLIFIER

Ideal for personal listening and it solves the space problem at the same time. Can be used with a magnetic, crystal or ceramic pick-up, tape deck, or tuner. Battery operated.



PLACE A REGULAR ORDER NOW

Everyday ELECTRONICS

MARCH 1980
ISSUE ON SALE
FRIDAY, FEBRUARY 15
Price 50p


SUPER OFFER

to
Everyday Electronics
Readers

mini 20 multimeter

only £18.50

INCLUSIVE OF POST & PACKAGE AND
V.A.T.

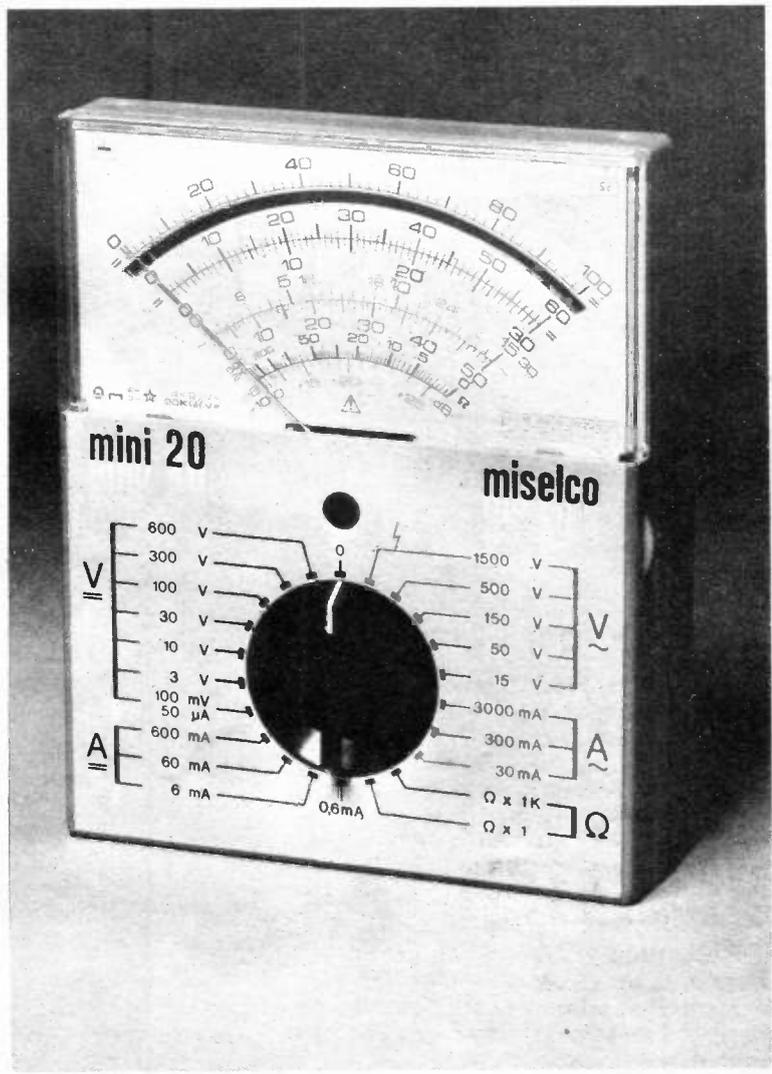

The Mini 20 Multimeter is an ideal instrument for the constructor.

In particular, to those just taking up electronics, this Special Offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10 on the normal retail price.

The 21 ranges cover all likely requirements. Operation is straight-forward, just turn the 22-position selection switch to the required range.

Sensitivity 20kΩ/V d.c. 4kΩ/V a.c.

Ranges extend from

- | | |
|--------------------|-----------------|
| 100mV to 600V d.c. | 30mA to 3A a.c. |
| 15V to 1,500V a.c. | 0 to 2kΩ |
| 50µA to 600mA d.c. | 0 to 2MΩ |

Movement protected by internal diode and fuse.

The instrument is supplied complete with case, leads and instructions.

Please complete both parts of the coupon in
BLOCK CAPITALS.

To: Alcon Instruments Ltd., 19 Mulberry Walk,
London SW3 6DZ.

Mail Order Only

Please send me at *£18.50 each.
I enclose P.O./Cheque No..... value

Name.....

Address

.....

* Including VAT, postage and packing.

Please allow 21 days (maximum) for delivery
(more for overseas orders).

OFFER CLOSES—MARCH 18

From: Alcon Instruments Ltd., (E.E. Offer),
19 Mulberry Walk, London SW3 6DZ.

Name.....


Address

.....

.....

BREAD BOARD

1979

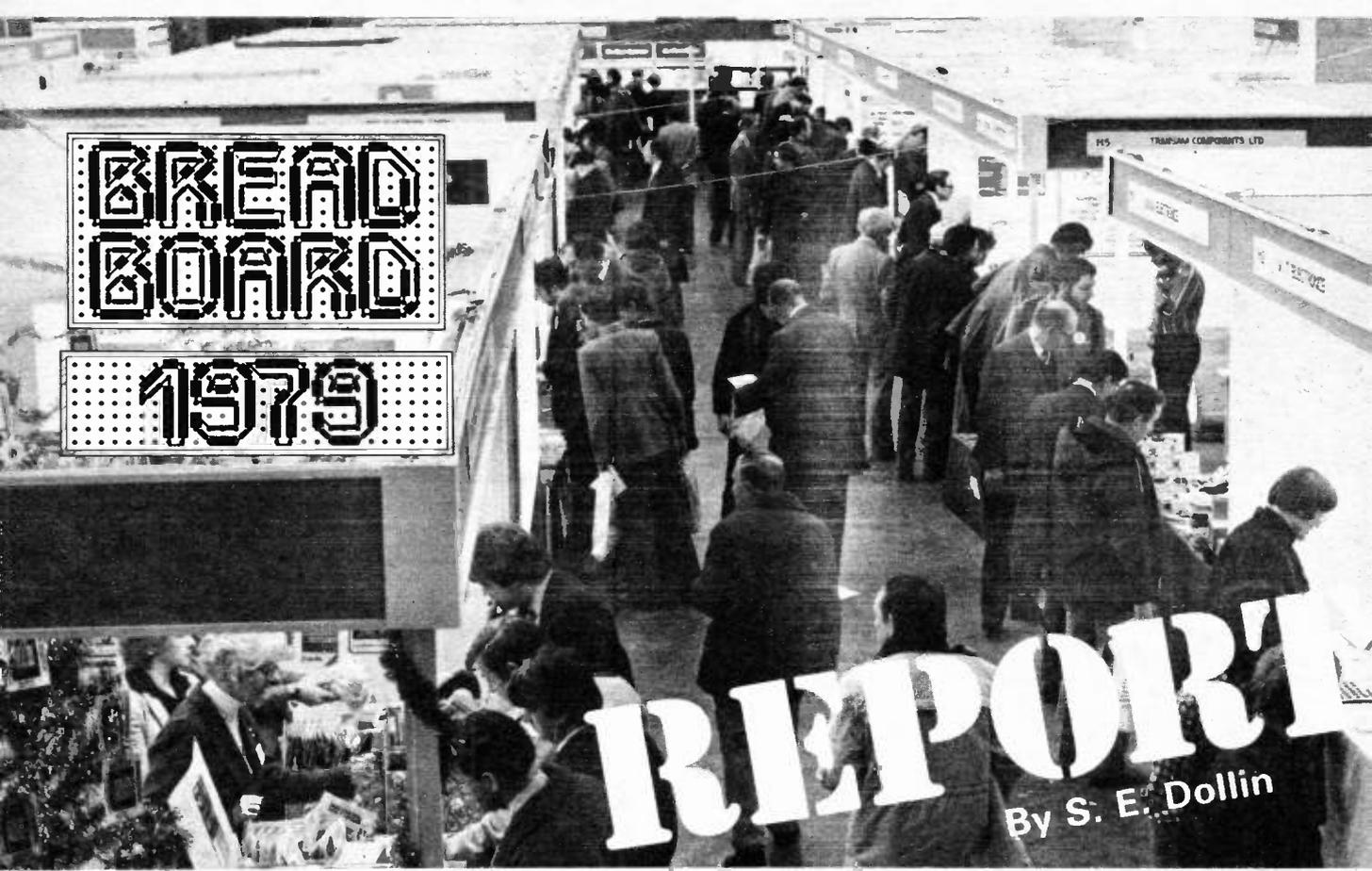

ANYONE visiting the Breadboard 79 exhibition at the Royal Horticultural Halls, London, early in December last, would have at once been overwhelmed by the plethora of sound as he or she came through the door. Indeed the visitor could be forgiven for thinking that he was attending some futuristic music fair, although a quick glance round would soon belie this initial impression.

In fact there seemed to be exhibitors from just about all sectors of the electronics hobby field including most of the major component suppliers, one or two computer specialists and several magazines (including your very own EVERYDAY ELECTRONICS of course).

BOXES AND BREADBOARDS

Of the larger industrial concerns, Vero Electronics had the most interesting stand with a full display of all their products including a new breadboard with the trade name Verobloc and a range of electronics kits called Hobbikits. Apparently the first batch of kits was only completed the day before the show opened. However Vero boast that these are the only kits to be put together and packaged in the U.K. and that they live up to the company's usual high standards.

Certainly they are well presented with full circuit descriptions and assembly details and also a separate

book on such essentials as how to solder, resistor colour codes and the like. Prices range from about £6 to £18 and full details can be obtained from the company.

Although Vero seem to have a large market in factory built cases for the home constructor, Boss Industrial Mouldings were also showing an impressive range of boxes and breadboards.

Continental Specialities Corporation seemed to be pushing their own solderless breadboards, especially the new TM system, and they also had a fascinating range of test equipment for digital circuits.

MICRO COMPUTING

Microcomputers featured quite strongly this year with several specialist computer concerns taking stands as well as a predominance of computer products amongst general component suppliers and magazines.

Newbear had one of the biggest spreads with a comprehensive selection of computer hardware, including the new Sharp microcomputer, backed up by an equally comprehensive selection of books. Microdigital of Liverpool were also out to make an impact with their wide range of products and books, although of the manufacturers, only Commodore and Acorn were actually represented and neither of these had anything particularly new to see.

COMPONENTS AND THE LIKE


Of course no show would be complete without working models and of these there were plenty. In fact virtually every component supplier had brought along something that would at least flash a light if not make an incalculable volume of sound. Tuac were the chief culprits here having a large part of their range of disco equipment available for demonstration.



The new Hobbikit range from Vero Electronics.

However the biggest display of working models came from Maplin Electronic Supplies who had taken the best, not to mention most expansive, exhibition space and set up two large demonstration tents, one for the new 5600S synthesiser and the other for the MES50 electronic organ. The space around these was filled up with all manner of different products, nearly all in an operational state.

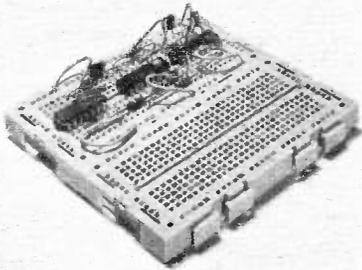Watford Electronics were sticking more exclusively to computer products to catch the public's eye although they did feature their new laser project as well as a fairly large range of stock. Marshalls on the other hand preferred to stick to a more limited range of products—some at a discounted price. Bi-Pak were out



Verobloc breadboarding system showing two boards clipped together.

to make an impression with their large stand and the Bi-Kit range of high quality audio modules.

The centre-piece of T. Powell's stand was a very neat version of the E.E. Tutor Deck (like many other component suppliers, they were offering a complete kit of parts for the Teach-In 80 series). In fact, taking into account the number of smaller component shops represented, constructors should have been able to find virtually any component imaginable somewhere in the place.

AMATEUR CLUBS

It was heartening to see that a couple of amateur clubs were able to be present at the exhibition. The British Amateur Electronics Club founded in 1966 had a small display, mainly of books and pamphlets designed to attract new members.

The Electronic Organ Constructors Society were much more ambitious having several organs on display built by their own members including a certain model with the resplendent title "The Mini Minor Moveable Mk 2".

MAGAZINES

Turning to the press, most of the usual hobby magazines were represented, each with its own set of demonstrations adding to the general



The Sharp MZ80K microcomputer.

cacophony. EVERYDAY ELECTRONICS was featuring various musical sound effects (some published, some yet to be seen in print) which proved very popular, and also the Loft Alert as well as a static display of several other projects "in the flesh" as one youngster put it. These included the Radio-Control System and the Tutor Deck, both of which aroused considerable interest.

So was it all worth it? There was certainly "something for everyone" as the saying goes. The attraction for many people, it seems, lay in the fact that everything was there under the one roof, both magazines and suppliers, and where better to see that unit you were going to build or buy that transistor you couldn't find deep in furthest Ipswich? ☞



Electronic Translation

The latest marvel to catch my eye is the electronic translator. It is pocket size, and you merely spell out the word in English, press the button and "hey presto", there is the equivalent word in French, German, Italian or whatever language you have selected.

I am not knocking the idea which is a brilliant piece of technology, but it will cost you around £150 and I am wondering if I could not do just as well with a dictionary costing a pound or so. The trouble is, that without a working knowledge of the language concerned, it is impossible to write a letter with a dictionary.

This was forcibly brought home to me a few years ago by a letter I received from the third world, Benin City to be precise. I always remember one phrase in the middle of the letter which ran "Never let failure be the result" which raised a smile and if any of my staff were in difficulty over anything someone was bound to quote it to them.

I know when I am in a strange country I shall fall back on my usual technique of pointing to my mouth when I am hungry, putting my two hands together and laying my head on them when I am tired.

All Electric

Several years ago, I decided that as my business was electronics everything in my house should be electric. I even had an electric fire lighter and very good it was too. It was about this time that I decided we ought to have central heating and it coincided with the invention of the storage heaters.

Now as I understand it, and I hope my electrical friends will correct me if I am wrong, the theory behind the storage heaters was this. At night when most of the load on the power stations is switched off, the engineers are faced with a problem.

Their machines must always run at constant speed otherwise the frequency would change with devastating results. So when the load is taken off it must be

replaced with an artificial load. In other words lots of kilowatts are wasted.

Along comes a bright lad, and suggests using them to warm up fire bricks in a container and these would continue to give out heat all next day. Thus the storage heater was born.


The Electricity Authority could afford to sell this night supply at a cheap rate, because in the past they had received nothing for it at all. Storage heaters had little to recommend them, they were big, heavy, ugly, and practically uncontrollable but they were cheap to run.

This was the situation up to about three years ago when some luminary on the Board decided he would put up the cost of the night supply. The results were disastrous.

Faced with astronomical bills people had to change to an alternative system overnight. Factories making storage heaters closed down, and work on two power stations was halted because of the sudden drop in demand. Added to that, the Electricity Authority were back to square one, getting nothing for their surplus which has to be shunted off as before.

Apparently even after this calamity became apparent, no one could reverse the decision and put it right. Instead the Electricity Board's remedy is to waste public money on a vast advertising campaign to try and persuade people to have a storage heater, saying that "We can supply you with one for £99!".

Pardon me while I give a hollow laugh. I have been trying to give my storage heaters away for months and I am just about to bury them in my garden and I am not joking!

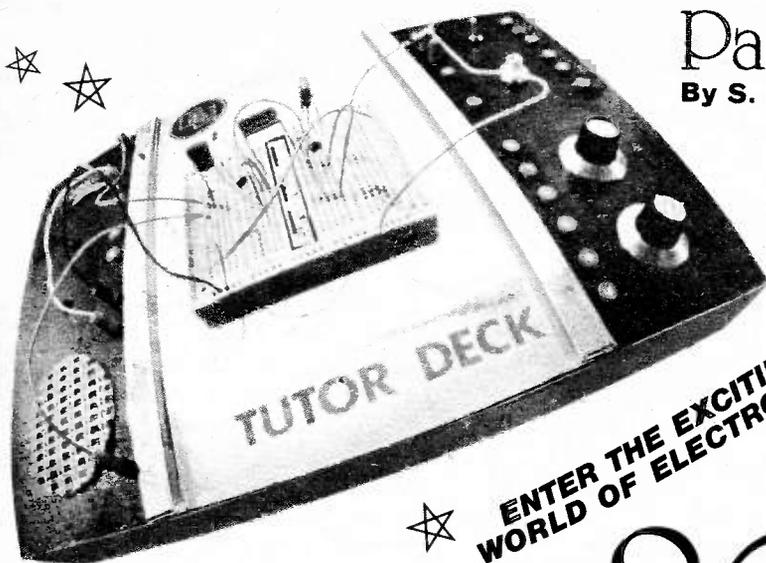

Part 5

By S. R. Lewis,
B.Sc.

ENTER THE EXCITING
WORLD OF ELECTRONICS

TEACH-IN 80

IN ALL the electronic circuits which we have looked at in previous parts of this series, the variables in which we have been interested (current and voltage) have been invariant with time; it did not matter when the measurements were made, providing the connections were the same then the variables would be the same.

We are now about to look at **capacitors** and we must now concern ourselves with a new dimension—that of **time**. It is now no longer a matter of measuring voltages and currents, we must now take the timing of the measurements into consideration.

Before looking at capacitors (as physical circuit components) we will take a look at the property which capacitors are designed to exploit: **capacitance**.

CAPACITANCE

Resistance is a property of all components: every material through which current passes produces some resistance to that flow. Capacitance is another property which all components exhibit although, like resistance, there are a large number of situations where it is so small as to be negligible.

Resistance is a property which is fairly easily visualised in terms of everyday systems. It is sometimes thought of as like a thin pipe opposing the flow of water or a

narrow passage through which lots of people are trying to pass. Analogies of this sort, with all their limitations help us to comprehend in part at least a rather abstract concept.

When it comes to capacitance we have to resort to rather more complicated visual models and thus capacitance is a more difficult concept to grasp.

Capacitance arises because of the charge on a body and the field in which it exists. When a charge moves in an electric field, energy is either absorbed or released. It is similar to raising a weight in the gravitational field (which absorbs energy) or dropping a weight (which releases the stored energy).

Each charge has a potential, in other words a stored amount of energy. To go back to the analogy of gravity, the potential of the weight would depend on its distance above the object on which it was to be dropped.

Table 5.1

UNITS OF CAPACITANCE

Submultiple	Symbol
10^{-6} micro	μF
10^{-9} nano	nF
10^{-12} pico	pF
10^{-12} micro micro	$\mu\mu\text{F}$

It will be observed that pF and $\mu\mu\text{F}$ are alternative ways of expressing the same thing; the first (pF) is more commonly used nowadays.

The potential of a charged body (of any sort) is proportional to its charge. The ratio of charge (Q) to potential (V) we call capacitance (C).

$$\text{Thus } C = Q/V.$$

THE FARAD

The charge of a body (Q) is measured in coulombs (C) and the potential of the body (V) is measured in volts. A body with a charge of one coulomb and a potential of one volt is said to have a capacitance of one **farad**. This unit is named after Michael Faraday.

One farad is rather a large unit for normal, practical electronic circuits so submultiples of the farad, such as the **microfarad** (equal to one millionth of a farad) and the **picrofarad** (one millionth-millionth of a farad) are the units commonly used.

Symbols for these submultiples of the farad are given in Table 5.1.

The capacitance of a body depends on the nature of the body (its physical shape, size, etc) and the field in which it exists.

CAPACITORS

All charged bodies can be said to possess capacitance but unless the body is carefully designed and constructed it will be low.

Since capacitance is charge divided by potential, we can increase the capacitance of a given body by increasing the charge which it can hold whilst reducing the potential. This can be done by concentrating the region over which the electric field extends. Capacitors can therefore be described as components for concentrating electric field energy.

Most modern capacitors are designed around the simple **parallel plate** principle. They are constructed of two parallel metal plates with as large an area as is necessary to achieve the required capacitance, separated by a very thin insulating layer called the **dielectric**.

The dielectric is a material specially chosen to be able to support a high concentration of field energy—it must therefore be a very good insulator. The sort of materials that are used in modern capacitors for the dielectrics are **polyester**, **polycarbonate** and **polystyrene**. Older capacitors had **paper** or **mica** dielectrics.

CONSTRUCTION

The construction of a typical polystyrene capacitor is shown in Fig. 5.2. The metal plates are thin sheets of aluminium placed on either side of a thin sheet of polystyrene. The whole arrangement is then rolled very tightly, making sure that the two plates do not touch.

At each end of the capacitor electrical connection is made to one of the plates. The whole assembly is then covered with a coating of plastic, and the finished component looks like that shown in Fig. 5.3a.

Capacitors of this type tend to become extremely large when values over a few microfarad are required. The problem is that the distance between the plates is governed by the thickness of the dielectric. Since this can only be made as small as manufacturing processes allow, the plate area (and hence the size of the capacitor) has to be kept large to compensate.

ELECTROLYTIC CAPACITORS

It is possible to produce capacitors with high values in a small volume but the dielectric must be

produced in a new way. Instead of a dry insulating material between the plates of the capacitor, a special liquid, or, more usually a liquid impregnated paper, is used. The liquid is an **electrolyte** which has the property of allowing current to pass through it. This liquid dielectric gives this type of capacitor its name: **electrolytic**.

The way that electrolytic capacitors work is that a steady (d.c.) current through the electrolyte causes a very thin film of oxide to form on one of the plates. This layer is an almost perfect dielectric as it is very thin but can withstand quite high voltages across it.

Sometimes the plates are treated in a special way to make them rougher ("corrugated") and hence increase the effective surface area of the plates.

SOME DRAWBACKS

Whilst they produce very high capacitance in a small volume, electrolytic capacitors have quite a few drawbacks.

First, there must be a d.c. current through the capacitor in order to maintain the dielectric.

Secondly, the so-called **polarising current** must be in the correct direction. If the voltage across electrolytic capacitors is acciden-

tally reversed then the dielectric layer may be destroyed.

Some electrolytics are called **reversible** but this does not mean that they can be used in the same way as non-electrolytics as the "reversing" may not be able to take place as fast as the voltage across the capacitor is changing.

The other drawback is that electrolytics cannot work in as harsh an environment as non-electrolytics since the electrolyte requires a rather narrow range of operating temperatures.

TANTALUM CAPACITOR

Another type of capacitor which is now quite widely used is the **tantalum** capacitor. Again these capacitors need a polarising current in a specific direction in order to maintain the dielectric layer.

The dielectric layer in this type is even thinner than that in electrolytics, but the voltage that it can withstand is lower. Thus while tantalum capacitors have very high values in small volumes, the working voltage (that is the maximum voltage that can be safely placed across them) is only in the order of a few tens of volts.

Three typical types of capacitor are illustrated in Fig. 5.3.

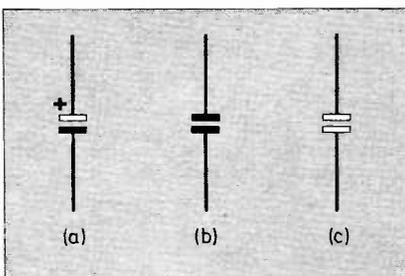


Fig. 5.1. Circuit symbols for three types of capacitor. (a) polarised or electrolytic type (b) non-electrolytic (c) reversible electrolytic.

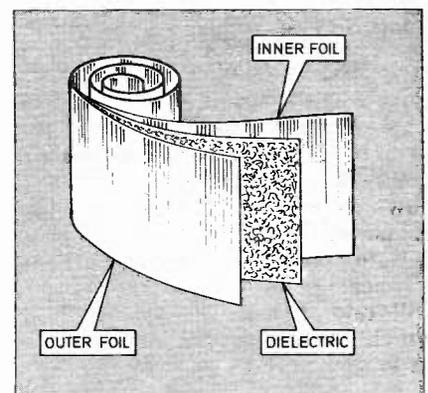


Fig. 5.2. Construction of a typical non-electrolytic capacitor.


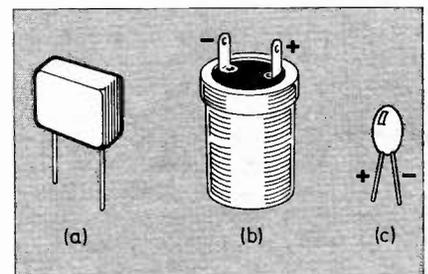


Fig. 5.3. Three different types of capacitor. (a) polyester (non-electrolytic) (b) metal can type electrolytic (c) tantalum.

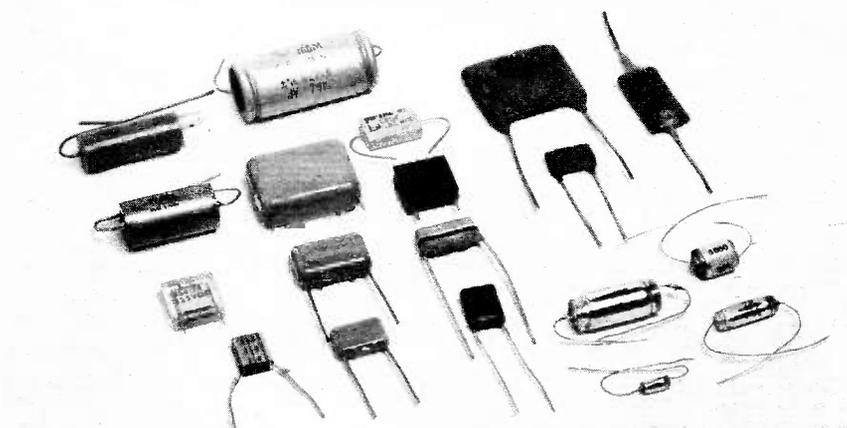

A selection of commonly used small-value types of capacitors. Dielectrics include mica, paper and polyester film. Aluminium cans, moulded plastic cases and dipped encapsulation are all included in this group.

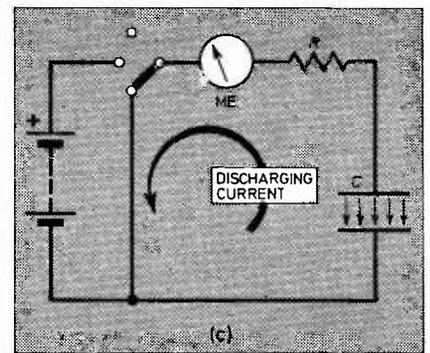
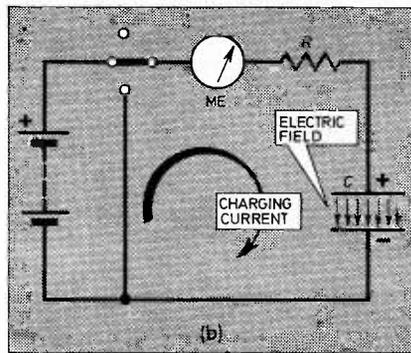
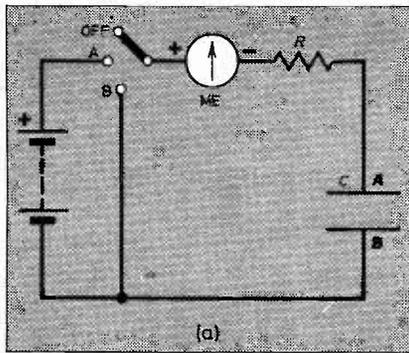


Fig. 5.4. Charging and discharging a capacitor from a battery through a resistor. (a) Switch open—no charge on the capacitor, no current through the meter. (b) Switch closed—charge accumulates on the capacitor and current flows in the meter, slowly decaying to zero. (c) Short circuit—field on capacitor drives current in opposite direction. Meter indicates flow in reverse direction.

CAPACITOR SPECIFICATIONS

When capacitors are specified for constructional projects in this and other magazines they are usually described in terms of three or sometimes four parameters: **capacitance**; **dielectric type**; **working voltage** and, sometimes, **tolerance**.

Capacitors in general tend to have much wider tolerances than resistors. It is not uncommon to use non-electrolytic types with tolerances of ± 20 per cent and electrolytics with tolerances of -50 to $+100$ per cent! This is not to say that close tolerance capacitors are not sometimes used but, on the whole, it is rare to find a circuit which relies on close tolerance capacitors.

The reason for this is that the two components (resistors and capacitors) are used for different reasons. Resistors tend to be used for setting voltage and current levels within a circuit, whilst capacitors are used for such things as d.c. isolation, smoothing pulsating voltages and decoupling power supplies (these terms will be explained later).

In short, one could say that resistors are used in a **quantitative** manner whilst capacitors are used in a **qualitative manner**.

The type of dielectric is specified since the properties of the capacitor depend on the dielectric. Certain dielectrics work better in high frequency circuits whilst others are good for use in timing circuits where one requires very low leakage current through the capacitor.

In most cases the type of dielectric is not critical and the cheapest type (usually paper or polyester) can be used.

CHARGING AND DISCHARGING A CAPACITOR

To see how a capacitor behaves in a circuit we will look at what is perhaps the most fundamental circuit containing a capacitor.

A battery, switch, meter, resistor and capacitor are connected in series as shown in Fig. 5.4. The switch is initially open and therefore no current can flow in the circuit. When the switch is closed an interesting thing occurs.

The meter swings nearly to full scale at the instant that the switch is closed but gradually the reading on the meter falls until eventually it reaches zero.

If the meter is again reading zero then no current can be flowing and thus the voltage across the resistor must be zero. The only way that this can happen is if the voltage across the capacitor is exactly the same as that of the battery.

We can understand what has happened by considering electron flow around the circuit.

As soon as the switch is closed there is a brief rush of electrons from plate A which is connected to the positive terminal of the battery through the battery to plate B where they accumulate. The meter will be showing maximum deflection at this time.

Current will keep flowing until the potential difference between the plates is equal to the voltage of the battery.

As plate B gathers more and more electrons it becomes harder for any more to arrive because of like charges repelling. Similarly, at plate A as more electrons are lost it becomes increasingly harder to lose further electrons because

of the attraction of opposite charges.

Thus, as the charge on the plates increases it becomes harder and harder for the current to flow.

The two oppositely charged plates produce a field in the dielectric separating them. If the switch is now opened each plate is left charged with a certain quantity of electricity, A with a positive charge and B with a negative charge.

The sum of the charges is zero so when one sees a reference to the "charge on a capacitor" one should understand that it is in fact the charge on *one* of the plates.

ENERGY STORE

If the battery is now removed and replaced with a short circuit (direct connection) and the switch is again closed we see another interesting feature of capacitors: they act as stores of energy.

The field which was created by the charge from the battery flowing into the capacitor now sees no opposition since the battery is not in circuit. The electrons therefore rush back along the paths through which they arrived until the charge is evenly distributed throughout the circuit.

If we look at the meter when this is happening we see that the flow is in the opposite direction as we would expect and like the charging current it begins at a maximum and slowly decays to zero. This is because as the charge from the plates distributes itself in the circuit, the force generated by the charge on the plates becomes less and less until, when there is even distribution of charge, the current is zero.

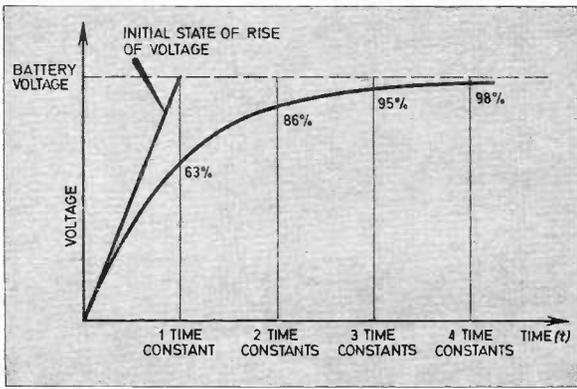


Fig. 5.5. Voltage on a charging capacitor plotted against time. It takes about 0.69 time constants for the voltage to reach 50 per cent of the battery voltage.

To use an analogy, the capacitor is like a spring which stores the energy which was used to stretch it. This energy can be released by releasing the force on the spring.

CHARGING RATE

We have said that the current through the meter starts off large and reduces to zero but we have not said anything about the *size* of the current or the *time* that it takes to reach zero.

When the capacitor is fully discharged, that is there is no potential difference between its plates, and the switch is closed the capacitor appears simply as a short circuit. The current that flows is therefore solely determined by the battery voltage divided by the value of the resistance—Ohm's Law.

Say we imagine this current flowing for a short time t . The charge which will have accumulated on the plates will be $I \times t$ (where I is battery voltage divided by resistance R). Now this charge will produce a voltage across the capacitor in an opposite sense to the battery voltage and of magnitude $(I \times t)/C$ where C is the value of the capacitor.

The current which now flows in the circuit must be less by an amount equal to the voltage on the capacitor. Therefore, in the next time period t the charge accumulated on the capacitor will be slightly smaller.

We can thus plot the voltage on the capacitor against time as series of short straight lines to obtain a graph like that of Fig. 5.5. Providing the time interval has been made small enough then the graph will be a pretty true representation of the actual voltage.

EXPONENTIAL RISE

The shape of the curve is known to mathematicians as an "exponential rise" and it can be described very accurately using calculus.

A couple of interesting features of the graph should be noted. First, the voltage on the capacitor never theoretically reaches the

voltage on the battery. This is because the more charge on the plates the more difficult it is for any more charge to be added.

In a real situation, however, we need to have some way of relating the shape of the curve with the value of the circuit components. We therefore look at the angle which the initial part of the curve makes with the time axis.

TIME CONSTANT

The rate of rise of voltage is simple given by V/CR . Now since this is **rate of rise of voltage** the units of $C \times R$ must be units of time. We call the value of the capacitance multiplied by the resistance the **time constant** of the circuit.

In one time constant the voltage on the capacitor will have reached 63 per cent of the battery voltage.

In two time constants the voltage will be 86 per cent of the battery voltage. The figures for three, four and five time constants are 95, 98 and 99 per cent, respectively.

CAPACITORS IN PARALLEL

If we place two capacitors in parallel and again charge them up through the battery and resistor circuit, then we would end up with each capacitor having the same charge that the single capacitor had. If we call the charge on the single capacitor Q then the total charge on the two capacitors will be $2 \times Q$.

Since the voltage across the capacitors is still equal to the battery voltage the total capacitance in the circuit (total charge divided by total voltage) will be $2 \times Q/V$.

Since Q/V is the capacitance of the single capacitor we can deduce that two capacitors in parallel are equivalent to the sum of the capacitances of the individual components.

CAPACITORS IN SERIES

If two equal capacitances are placed in series and charged by the battery through the resistance as before, then clearly the voltage on each of them must be half the battery voltage. The total charge is still the same so that the total capacitance is $V/2 \times Q$ or $\frac{1}{2} \times Q/V$. Thus the total capacitance is half that of a single capacitor of the same value.

PART 5 QUESTIONS

5.1. To increase the capacitance for a given plate area should the plates be moved:

- a) nearer
- b) further apart

5.2. A $0.1\mu\text{F}$ and a $0.47\mu\text{F}$ capacitor in parallel have a capacitance of:

- a) $0.57\mu\text{F}$
- b) $0.37\mu\text{F}$
- c) $0.08\mu\text{F}$

5.3. Two $0.22\mu\text{F}$ capacitors in series have a capacitance of:

- a) $0.44\mu\text{F}$
- b) $0.11\mu\text{F}$
- c) $0.22\mu\text{F}$

5.4. How long will it take a $10\mu\text{F}$ capacitor to charge to 99 volts from a 100V battery through 470kilohms:

- a) 23.5 seconds
- b) 2.35 seconds
- c) 4.7 seconds

5.5. A $10\mu\text{F}$ and a $5\mu\text{F}$ capacitor in series are charged to 15V. What is the voltage on the $5\mu\text{F}$ capacitor:

- a) 10V
- b) 5V
- c) 7.5V

PART 4 ANSWERS

4.1. b) 4.2. b) 4.3. b) 4.4. a) 4.5. b)

EXPERIMENT 5.1: CHARGING AND DISCHARGING

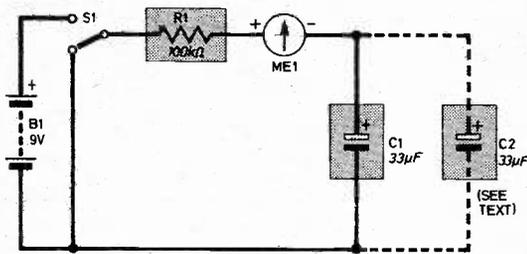


Fig. 5.7. Charging and discharging a capacitor are illustrated with this circuit. (a) shows the circuit diagram and (b) the Tutor Deck layout. Note these additional connections on right hand panel of Tutor Deck: link S1(a) to B2 +9V.

Components needed: 100kΩ resistor, 33μF tantalum capacitors (2 off)

The circuit of this experiment is quite simple consisting of a battery, switch, meter, a resistor and a capacitor in series. The capacitor used is of the tantalum type and the polarity markings must be observed on the body and made to match the orientation shown in the diagram Fig. 5.7.

The meter is measuring current flow, not voltage on the capacitor. When the switch is operated so that the battery is connected to the circuit the meter will


swing full scale and then return to zero, rapidly at first but much more slowly as time progresses.

When the switch is placed in the other position there is again a swing to almost full scale followed by a "decay" back to zero, but now the current flow is in the reverse direction.

Note the time that the meter takes to go back to half scale and verify that it takes the same time whether the capacitor is charging or discharging.

Now put another 33μF capacitor in parallel with the first and again record the time for the meter to reach half scale. This should be twice the original time.

Fig. 5.7b

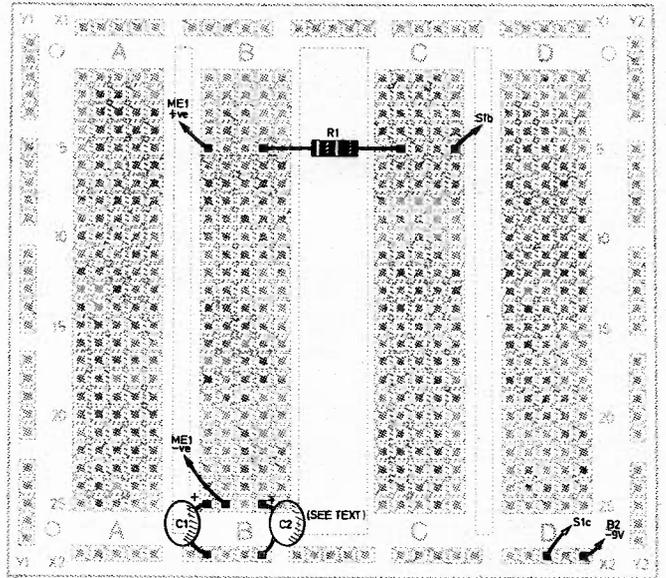

For identification of Tutor Deck components and their associated sockets refer to Fig. 2.8.

EXPERIMENT 5.2: CAPACITOR BRIDGE

Components needed: 100kΩ resistor, diodes (4 off), 10kΩ resistor, 0.47μF capacitor, capacitors to test.

This circuit makes use of the calibrated scale as described in Part 2 of this series, but this time it is used with VR1.

The reference capacitor is a 0.47μF type so capacitance values from about 0.05μF to 5μF can be measured using the circuit.

Note that the voltage across the bridge is now a.c. so the meter does not give a true reading of current. However since it is simply used to null the bridge, this does not matter.

The potentiometer is simply used to adjust the meter reading until the bridge is balanced. The capacitance is then given by

$$C = (0.47 \times R) \mu\text{F}$$

where R is the reading on VR1 scale (0 to 10).

Note that the meter will only swing in the positive direction since the diode bridge will only produce current in one direction through it. The null is thus when the meter reading is a minimum.

Fig. 5.8b


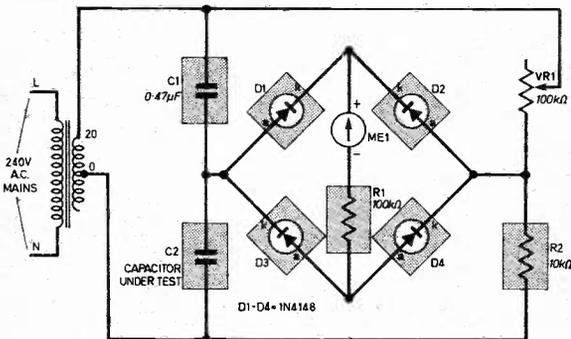


Fig. 5.8. A capacitor bridge to measure unknown capacitance between 0.05 and 5μF. (a) shows the circuit diagram and (b) the layout of the components on the Tutor Deck.

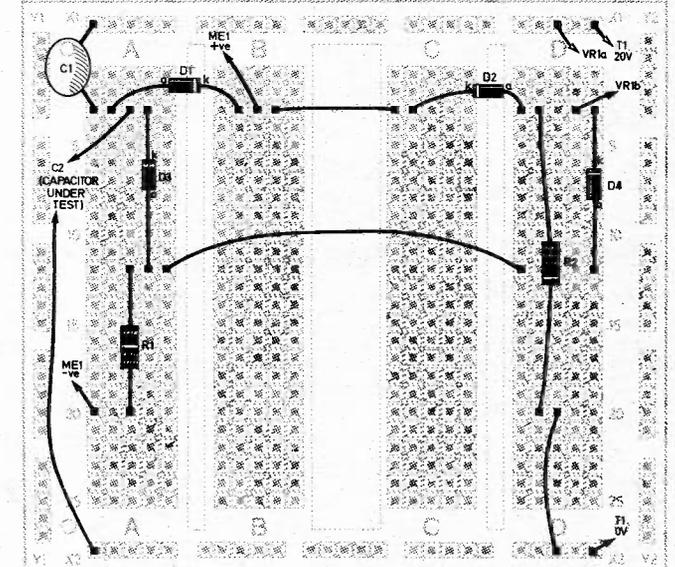

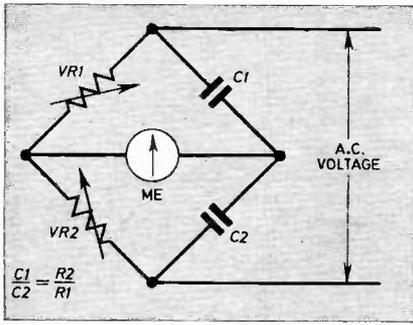


Fig. 5.6. Capacitor bridge circuit. The meter is assumed to be able to read a.c. current. The unknown capacitor can be deduced from knowledge of the resistor ratio and the known capacitor.

To generalise: the total capacitance of any number of capacitors in parallel is given by the sum of the capacitors. For capacitors in series the total capacitance is equal to the reciprocal of the sum of the reciprocals of the individual capacitors.

Parallel: $C_T = C_1 + C_2 + C_3 + \dots$

Series: $C_T = \frac{1}{1/C_1 + 1/C_2 + 1/C_3 + \dots}$

CAPACITORS IN A.C. CIRCUITS

When we were looking at the charging of a capacitor one deduction that could have been made is that the current flowing in the circuit was a maximum when the rate of change of voltage across the capacitor was also at a maximum. In fact there is a direct relationship between the current flow into a capacitor and the rate of change of potential. The relating factor is again the capacitance.

The relationship states that the current through a capacitor is directly proportional to the rate of change of voltage across it.

This relationship is all-important when it comes to a.c. circuits for here we are dealing only with voltages that are constantly changing. The higher the frequency of a signal the greater is its rate of change of voltage and so we can deduce that the higher the frequency of an a.c. voltage applied to a capacitor, the greater will be the a.c. current through that capacitor.

To more fully appreciate how capacitors, and indeed those other components **inductors**, act in an a.c. circuit we will have to look at a.c. circuits in more detail.

CAPACITOR BRIDGE

When looking at circuits containing only resistance we looked at the way a "bridge" circuit could be used to identify unknown resistors by using a calibrated potentiometer and a meter to balance the current through the known and the unknown halves of the bridge.

A bridge circuit can also be constructed using a capacitor to replace one of the resistors. The unknown component now becomes a capacitor rather than a resistor. The circuit is shown in Fig. 5.6.

We have seen that a direct voltage flowing through a resistor will simply cause the capacitor to charge up until the force created by the field in the capacitor exactly balances the electromotive force of the battery.

To measure the unknown capa-

CORRECTION!
We are sorry for these small errors which occurred in previous parts of this series. Please mark your copies as follows:
Part 2 page 716
Second column 17th line should read: "just over 0.1 A (100mA)".
Part 3 page 796
First paragraph, lines 5 and 6, should read:
"100 × 0.005 = 0.5V and that . . . must be 200 × 0.005 = 1V."
Question 3.2. Bridge circuit referred to should read: "Fig. 3.5".
Answer to Question 2.3 should read: "a".

capacitor using direct voltage would therefore require the measurements to be made only during the charging period, for this is the only time that appreciable current flows. In order to keep current flowing in the circuit we use an alternating voltage to drive the bridge.

Because the voltage is alternating and the meter is only designed to read direct current we must have some way of converting the rapidly changing current into a direct current. We do this using a diode bridge since this will only conduct in one direction, the current flow in the reverse direction being negligible.


Because the voltage across the capacitors is constantly reversing this circuit can only be used with non-electrolytic capacitors.

Notice that with capacitors in series (as they are in the bridge) the larger the capacitor, the smaller the voltage which will be developed across it.

Next month we will look at inductance and a.c. circuits.

The Adventures of Tanty Bead

By Matthew Reed

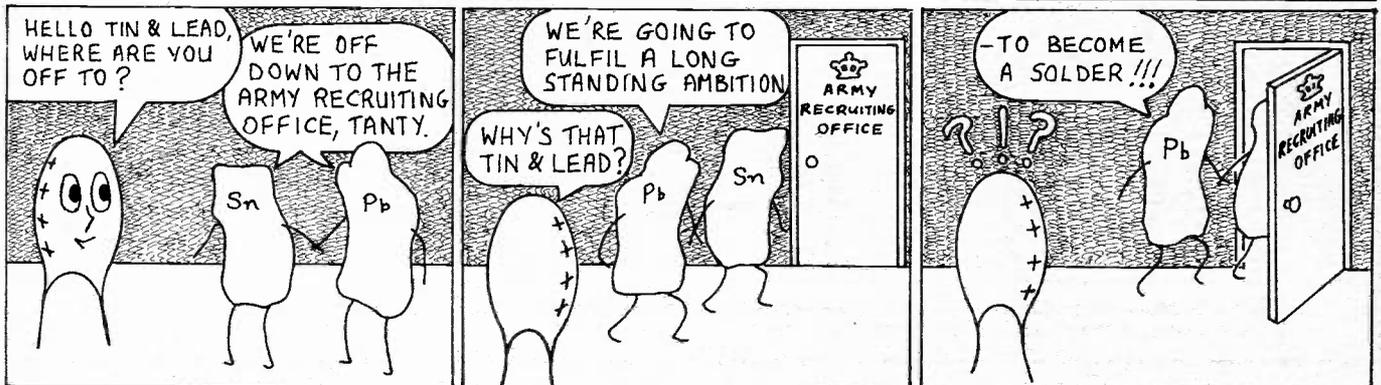



FOR BEGINNERS

SOLDERING

COMPONENTS forming an electronic circuit are bonded together using "solder". This is an alloy of lead and tin, a very good conductor. The soldered joint thus provides continuity between components and produces a joint of considerable strength.

Solder is silvery in colour and wire-like in appearance, being very pliable. It is obtainable in a range of different sizes (gauges). Throughout its length are a number of cores filled with a resinous flux to "clean" the joint as it is being made.

To make a soldered joint in electronic circuits an electric soldering iron is required. This is a special tool to heat up the joint to a sufficient temperature to cause the applied solder to melt. Basically the "iron" consists of a coil of resistive wire (similar to the bar on an electric fire) which is in contact with a solid shaped metal rod called the "bit". Current through the coil causes the bit temperature to rise.

Soldering is extremely important.

Every joint must be good to enable successful operation of the unit being built. If you have never carried out any soldering before it is wise to practice on scraps of circuit board and components before attempting to construct a project.

For the majority of projects published in E.E. an electric soldering iron rated between 15 and 25 watts will be most suitable. A selection of bit sizes will be useful and most jobs can be accommodated with a 1/16 in, 1/8 in, and a 3/16 in bits or their metric equivalents. On no account use an iron that is heated in a flame or electric furnace.

Use the resinous-flux-incorporated solder as described above. Never use unfluxed solder or separate flux or acid to clean joints: 18 s.w.g. or 22 s.w.g. "Multicore" solder is ideal for E.E. projects.

The bits of new soldering irons may contain a protective layer of light oil which should be removed before the iron is heated. Methylated spirit or similar solvent will remove this.

TINNING

For best results and ease of soldering the bit should be "tinned" immediately before use. This means coating the tip of the bit with a thin layer of solder. Merely melt some solder on the tip and see it flow over a clean tip.


It is a good idea to have a piece of damp sponge foam available to occasionally "wipe" the bit clean from the oxide that accumulates.

Component leads in general do not require to be tinned before connection since this is carried out by the manufacturer. In some cases the leads may be gold plated for ease of connection. However, if they appear to be dirty, emery paper or steel wool can be used to clean the wires, and then preferably tinned.

With copper clad circuit boards, such as stripboard, the surface may need to be cleaned with emery paper/steel wool to remove any oxide or grease that would impair the making of a good bond.

The two items to be joined must be in good contact before soldering, preferably a "mechanical" or "semi-mechanical" connection, see below.

The solder should *not* be melted onto the iron. Instead, the iron is used to heat the two surfaces and the solder melted onto and around the contact area. When the solder is seen to flow evenly over the joint, remove the solder followed by the iron and allow to cool. A shiny, smooth globular appearance will indicate a good joint. If the joint is disturbed during cooling or insufficient heat is applied, or the surfaces are dirty in any way, a "dry joint" may result. This will be indicated by a dull ragged looking joint. Such a joint could have a high resistance or even be open circuit—components not electrically connected.

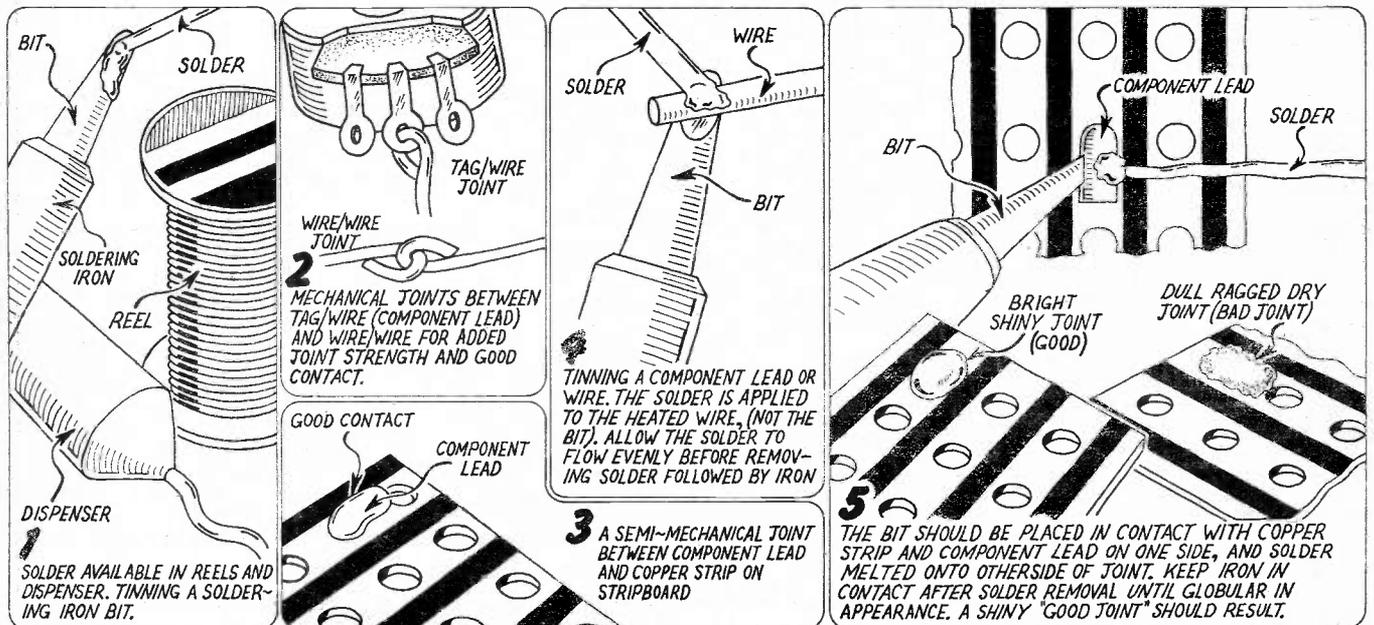



RUMMAGING AROUND

with Keith Cadbury

WAR GAMES

FIFTEEN years ago your humble scribe was a documentary film cameraman, employed by various companies contracted to the Air Ministry to make films concerned with aspects of RAF procedure and modern warfare. The work was exciting and very, very interesting, but the very nature of film making gave the camera crew periods, sometimes quite lengthy, of inactivity.

One particular film was concerned with electronic warfare, and we were "on location" in an underground radar base, somewhere on the east coast of Britain. The camera was set ready to film a radar screen in a room just off the main operations centre.

While we waited for a Squadron Leader to come back from tea, or something, Cadbury (documentary's answer to Cecil B. de Mille) did not desert his camera. The various controls around the radar console were fun to play with, and there were no RAF personnel in the room to rap naughty fingers.

Scanning hundreds of miles across the North Sea, the screen displayed "blips" that represented all aircraft in the sector. A "joystick" control could be manoeuvred, guiding a small circle across the screen. When an aircraft was thus encircled, a switch could be thrown and after a short pause, digital displays would inform height and distance of the selected aircraft.

INQUISITIVE CAMERAMAN

This electronic miracle (fifteen years ago, remember) was possible by way of the great computer, air-conditioned and temperamental, that occupied an area the size of a tennis court. An even greater aspect of the miracle was discovered by this in-

quisitive cameraman, as the Squadron Leader continued to stay absent, and new knobs and switches were found.

Under a hinged glass box was a large illuminated press-switch that bore the inscription "Identify." If this switch was depressed, the blip that was ringed could be identified as an aircraft that was friendly or presumably (although I never found one) as enemy.

Before the confirmation of the aeroplane's friendly intentions came through, another blip was seen to home-in on the selected blip. Presumably some other aspect of the device that I had not yet fathomed.

Over a period of about three-quarters of an hour, several aircraft blips were encircled and subsequently identified in this way. It was only after I got bored with playing with just one radar screen and thought of an interesting variation that things started to get out of hand.

I discovered that when a blip was being homed-in for identification, I could move to the next radar console and pick-out the "homing" blip, depress the appropriate controls, and another blip would be seen to enter the area also. The third console in the room seemed to be out of action, or I could have sent yet another blip

scudding into the scene.

An officer with God knows how many rings round his sleeves came into the room and asked me to desist—"If you wouldn't mind, old chap, as there seems to be a bit of a flap on."

It turned out that every time I pressed the "Identify" button, I was "scrambling" a Lightning jet fighter to fly up and carry out the identification!

ON THE BLINK?

At first, the fighter stations concerned thought that all the sudden activity was merely an unannounced exercise, but when aircraft were being scrambled to "buzz" aircraft from the same base, doubts were voiced. Someone from Fighter Command had telephoned the radar station to enquire "If the computer thingy is on the blink again, what?"

The RAF "brass" never discovered, as far as I know, that the entire "flap" was my doing. I didn't find out how many thousands of pounds of the RAF's, or NATO's, or the taxpayers' money I used up that afternoon, but I consoled myself with the thought that it was jolly good practice, to keep the chaps on their toes, what?

BLOWN FUSE INDICATOR

I was recently approached by a friend who runs a sophisticated discotheque, incorporating many different circuits for a variety of purposes. Several high-power amplifiers, many different lighting effects and various other devices are banked behind the DJ's control desk, and the problem my friend had was that he needed an indication of when a fuse has blown.


With some of the combinations of sounds and lights, he had found it a long, laborious business to locate a couple of blown fuses. Perhaps some simple indication of the state of the fuses would be possible?

He had sketched out various electronic circuits that would do the job, but they all seemed to be quite complicated, and wondered if I knew of any simpler circuits.

What I worked out appeared at first sight to be dangerous, but when we checked it against each and every one of his circuit diagrams, and then tried out, it has proved adequate, and I thus pass on the thought to you.

All the fuses were mains, so we simply put a neon indicator across each fuse, thus the neon remains "off" until the fuse blows. Once the fuse blows, the neon illuminates.

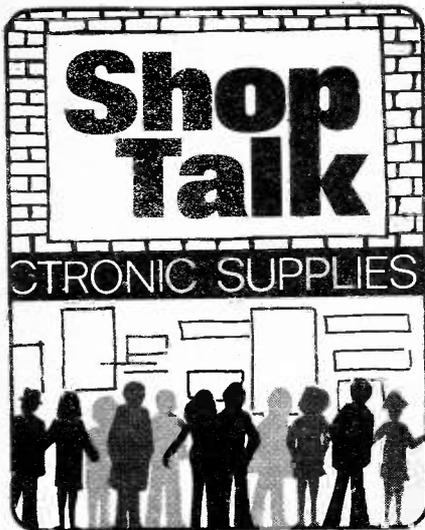All the circuits I have considered would not be damaged by the neon, so long as the mains is switched-off before replacing the fuse, and it is borne in mind that the neon gives no indication as to why the fuse has blown. Electronics purists may well shudder at my solution to the problem, but then they would at other of my devices no doubt!



By Dave Barrington

Catalogues

A new computer products catalogue containing details of their products and specialist services offered to micro computer users has just been published by Transam Components.

Of special interest is their range of integrated circuits, memory devices and a complete range of p.c.b. and cable connectors suitable for microprocessor applications. They also offer a specialist EPROM programming service to customers and users of their own Triton Personal Computer.

Copies of the catalogue can be obtained from Transam Components Ltd., Dept EE, 12 Chapel St., London, NW1 5DH.

Just in time for their move to bigger premises comes news of the publication of Ambit International's Part Three Components Catalogue.

If you are looking for i.c.d. clock/timer modules, communications equipment, radio integrated circuits or radio

control parts, there all to be found in this latest edition.

Also, the already extensive range of v.h.f. tunerheads stocked by Ambit has been extended with the introduction of the EF5804. This has been designed with synthesised control in mind and tunes over the f.m. Band II (88-108MHz) with only 2V to 8V bias.

Since the complete range of tunerheads are made in the UK by Ambit, they are able to offer a custom versions to special order.

Copies of the new Ambit International components catalogue are available from 200 North Service Road, Brentwood, Essex.

Wire and Wire Tidy

A new range of wire packs and a wire bin from OK Machine Co. will help to alleviate the frustration of trying to find suitable wire lengths and gauge when in the middle of a project.

The wire bin, wire-Tidy WB-16, consists of sixteen plastics tubes mounted in front and back end "cheeks". The front panel being numbered so that the user can easily compile an identification system for selecting suitable wires.

The wire storage tubes have adjustable depth stops to take wire lengths from 25mm to 350mm. Each wire bin can store up to 10,000 wires and can be grouped together to extend the storage capabilities.

Amongst the many wire packs and reels from OK are Kynar-insulated wire for wire-wrapping and various packs of general purpose wire with stripped ends.

For more information write to OK Machine & Tool (UK) Ltd., Dept EE, Dutton Lane, Eastleigh, Hants S05 4AA.

Storage Boxes

Although intended specially for printed circuit boards, the storage and handling boxes from Adcola Products make ideal storage cabinets for all the numerous forms of circuit boards usually found laying around the workshop.

Available in two sizes, 450 x 250 x 158mm and 450 x 250 x 82mm, the boxes

are made from tough corrugated cardboard with plastics grooved liners. Similar in concept to slide-film holders, the dividers hold the boards apart one from the other and can be supplied in short and long lengths to enable several "compartments" to be made up.

The boxes are supplied with either a p.v.c. or corrugated self-stacking lid and cost approximately £5 each. Further particulars and stockists can be obtained from Adcola Products Ltd., Dept EE, Adcola House, Gauden Road, London, SW4 6LH.

Constructional Projects

The majority of components required to build this month's projects should be readily available from many sources. In the *Micro Music Box* the i.c. type TMS 1000N MP0027A is only available from Chromatronics, Coachworks House, River Way, Harlow, Essex. The cost is £4.95 inclusive of post and packing.

The *Morse Practice Oscillator* calls up a Morse key. These can be obtained from Watford Electronics, Maplin and Home Radio.

Coils and variable capacitors often cause supply problems for the constructor. Both are used in the *Short Wave Receiver*. The Denco coils can be obtained direct from the manufacturers Denco (Clacton) Ltd; 357/9 Old Road, Clacton-on-Sea, Essex (Tel: 22807). Jackson variable capacitors are specified and are listed in the catalogues of the three firms mentioned above.

The relay is the only component likely to cause concern in the *Tape/Slide Synchroniser*. The relay contacts should be rated to suit the projector being used. Constructors are advised to consult their handbook before ordering. The coil impedance specified should be regarded as the minimum value for the circuit. Higher values may be used that will operate from a 9V supply.

Suppliers for the more unusual components required for the *Radio Control* project are mentioned in the article.


EE CROSSWORD No 24 BY D. P. NEWTON

ACROSS

- 1 Comfort and control unit (7).
 4  as forbidden meats (6).
 7 Event concluding meeting with referee (4,3).
 10 Not so much a lag, more a droop (3).
 11 The Mother of all at ground level (5).
 12 Part of the alarm gives warm currents (7).
 13 Commonly found in electrical backwaters (4).
 15 Noise associated with pulse through loudspeaker (5).
 16 Found at end of travel (4).
 20 Rejection needed to keep things going in the home (7).
 21 Electrical arena associated with the agrarian revolution (5).
 22 Decays from rotor (3).
 23 To oppose with a mathematical recording device (7).
 26 Very short wave aerials but never need washing (6).
 27 Mauve followed by two black rings (7).


DOWN

- 1 Small tape unit (8).
 2 Rare gas gives us the red light (4).
 3 Gold found on trees? (4).
 5 Forceful verbal objection (6).
 6 Pulsed in the power supply (6).
 8 Unclean (5).
 9 Working at the utmost capacity (4,4).
 10 Meter by-pass (5).
 11 Operated by wired energy (8).
 14 To wander as the electron (5).
 16 Rejection from the addition to house wiring (5).
 17 Antipodean electrical property (8).

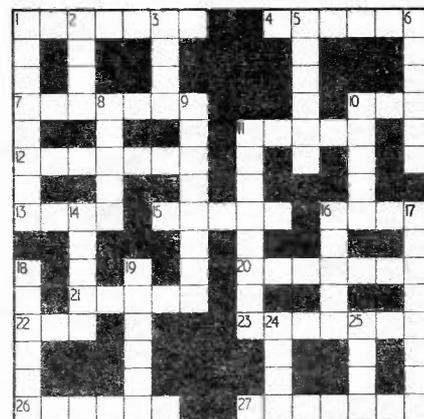

- 18 Wiry London street (6).
 19 Often found with 23 across, to replace both hands (6).
 24 Singular occurrence (4).
 25 Wafer-like (4).

Solution on page 137

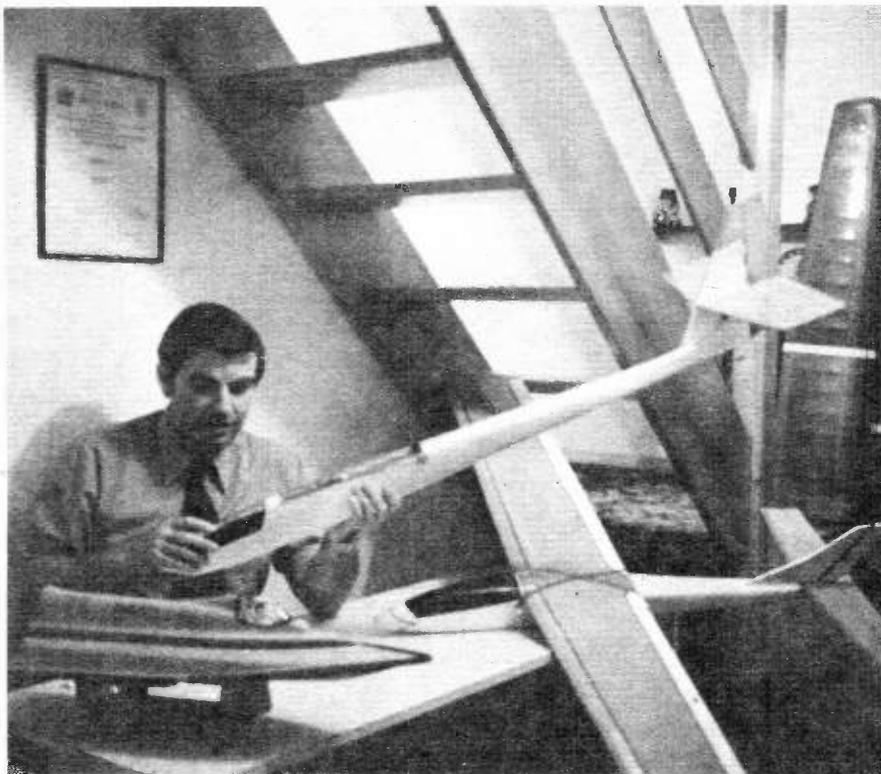

By L. ARMSTRONG • H. DICKINSON • W. WILKINSON

PART FOUR

EE RADIO CONTROL SYSTEM

SERVO UNIT DESCRIPTION AND CONSTRUCTION

IN THE first part of this series we discussed and described how we make use of radio frequencies as a means of transmitting information from one place to another: in this case the movement of a stick into pulses of a width dependent upon that stick position. The final process in this system is that of converting the electrical signal back into some form of mechanical movement (servo) or into movement of an electric powered vehicle (speed controller).

This article provides full information on the servo. The proportional speed controller will be covered next month.

SERVO DESCRIPTION

The purpose of the servo is to convert the decoded electrical signal from the receiver back into a mechanical movement which corresponds to the stick position of that particular channel. A typical servo therefore consists of some form of amplifier to convert the input signal into a signal

suitable to drive a motor.

This motor is connected to a gear-box to generate sufficient power to drive an output arm, which will be connected to some control function. Also connected to this output arm is the feedback device, usually a variable resistor, which is connected back to the amplifier. A schematic of this system is shown in Fig. 4.1.

I.C. AMPLIFIER

There are several amplifiers available on the market these days, all in the form of integrated circuits. Some of these are in small TO5 cans,

others are in 12-pin d.i.s. However, the one chosen in this particular instance is the ZN419CE Precision Servo I.C. manufactured by Ferranti but also available as the SRC419P as marketed by Skyleader Radio Control Ltd. This device comes in a shortened 14-pin d.i.l. to enable it to fit into most mechanics available today.

The ZN419CE was chosen because of its good performance over other makes in terms of linearity and output drive. The output drive is attained by making use of two "on-chip" npn transistors and two external pnp transistors to form a bridge drive.

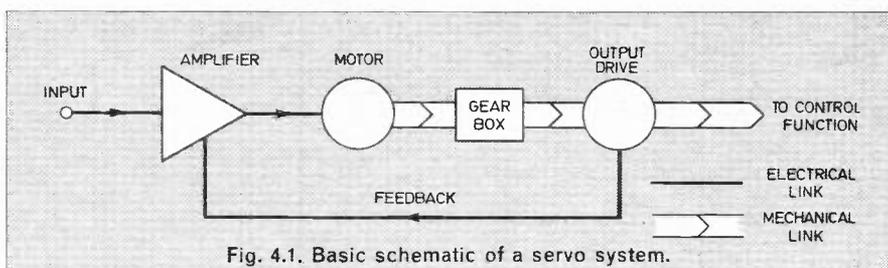


Fig. 4.1. Basic schematic of a servo system.

The use of external *pnps* gives far better saturation voltages and therefore more power under stall conditions than the equivalent i.c.s with the *pnps* "on-chip". The latter are always of a poorer quality due to the difficulty in fabricating them in most integrated circuit semiconductor processes.

FEEDBACK POTENTIAL DIVIDER

The ZN419CE also has the advantage of using the feedback pot in the potential divider mode, thus reducing the effect of pot noise to which the amplifiers using the pot as a variable resistor become prone.

SERVO CIRCUIT

The circuit diagram for the servo appears in Fig. 4.2.

The servo input from the receiver is in the form of a positive-going pulse which as explained in previous parts of this series, varies in width dependent upon the stick position.

The capacitor C1 is in the input circuit to avoid the servo "locking-up" should a permanent high level be presented to the servo from the receiver when going out of range of the transmitter; thus—in the case of aircraft—avoiding a disastrous crash.

The input signal is compared with a signal from the feedback potentiometer VR1 which produces an error signal related to the difference in position of the output arm and position of the stick on the transmitter. This error signal is then expanded to form a pulse to drive the motor in the required direction.

Depending upon the size of the error the amplifier will in turn provide an appropriate size of drive signal; that is if there is a large error the signal to the motor will be 100 per cent drive, if however, the error is small then the drive is reduced accordingly down to 20 per cent drive.

ERROR AND DRIVE RELATIONSHIP

Fig. 4.3 shows the relationship between error and output drive. As can be seen, above a certain error there will always be 100 per cent drive to set the servo arm to its approximate position as quickly as possible, then, as that position is approached, the drive will smoothly drop off. The quick drop off from 20 per cent is there so that the servo is given one last "kick" into its final position, therefore avoiding "creeping" with the servo buzzing and taking unnecessary supply current.

DEADBAND

The amount of error that is required before drive is given is called

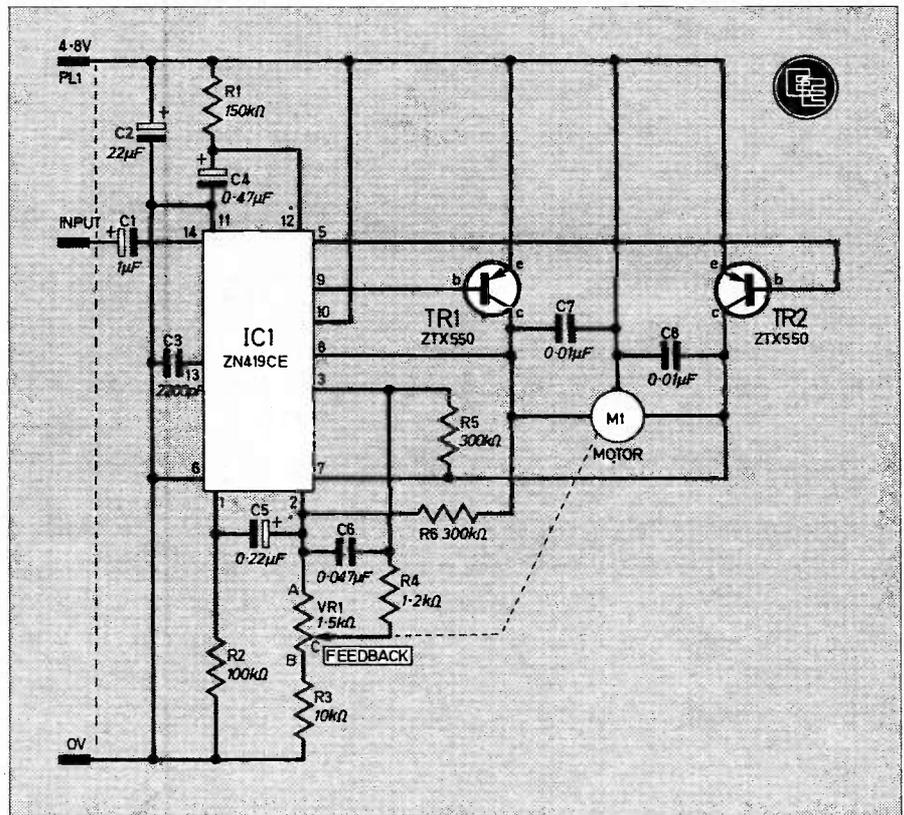


Fig. 4.2. Circuit of the EE Radio Control System Servo Unit.

the "deadband" and is set by the capacitor C3. The value is chosen such that the servo will respond to very small stick movements but not so small that the servo is responding to jitter in the input pulse. The other components in that network R1 and C4 are the pulse expansion components and determine the point at which 100 per cent drive is reached.

The resistor R2 and capacitor C5 are the timing components and are

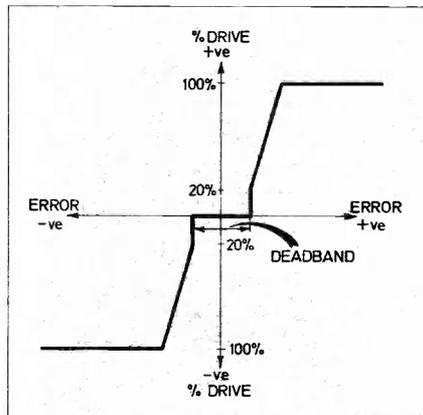


Fig. 4.3. Servo error and output drive relationship.

EE RADIO CONTROL SYSTEM COST TO BUILD

Approximate cost for different-sized systems.

Two-channel version	£75
Four-channel version	£110
Seven-channel version	£170

The cost for each version includes all units specified in Part 1.

The EE Radio Control System is fully capable of expansion from two-channels to seven-channels at anytime, simply by fitting additional sticks and servos.

chosen for a pulse input of 1.5 millisecond centre. R3 in turn sets the overall throw of the servo arm.

DECOUPLING CAPACITORS

The capacitors C2, C6, C7 and C8 are purely decoupling components. C2 is across the supply, C5 is to stop r.f. affecting the servo operation when one is stood over a model with the aerial fully extended; C7 and C8 are to stop motor noise being radiated.

EE RADIO CONTROL SERVO



Fig. 4.4. Printed circuit board for the EE Radio Control System Servo Unit, actual size.

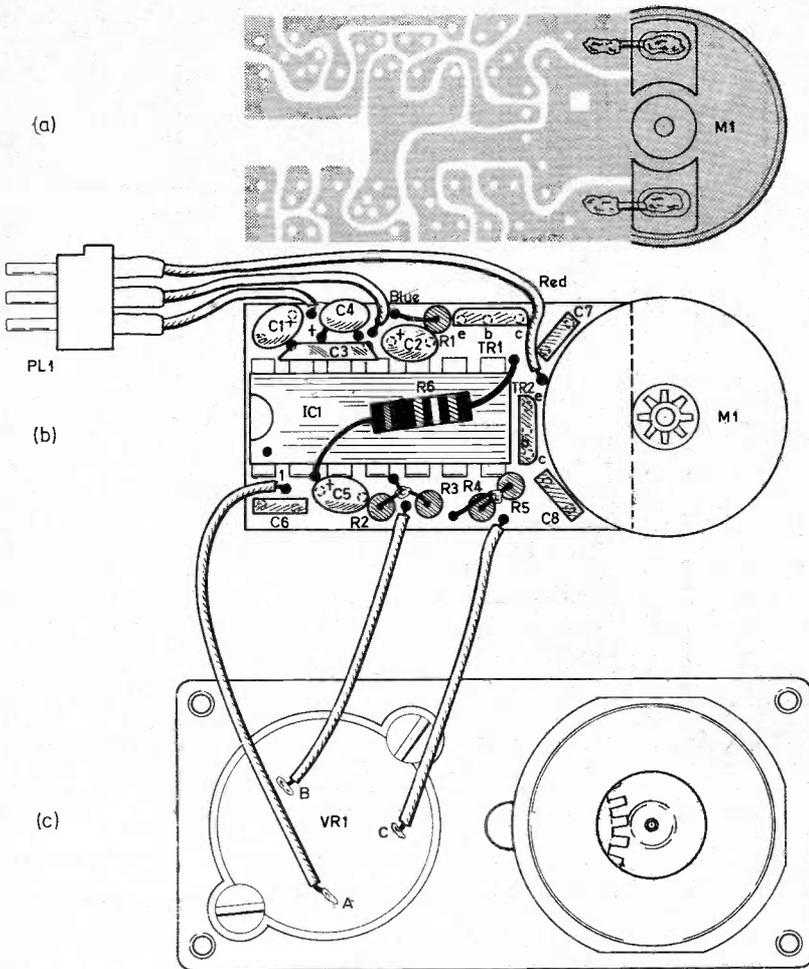


Fig. 4.5. The completed Servo unit (a) Underside view of p.c.b. showing how this is secured to the motor M1 by means of two soldered link wires. (b) Top view of p.c.b. (twice actual size) with all components in situ, and showing external wiring. (c) Underside of servo mechanics showing connections to the feedback pot VR1.

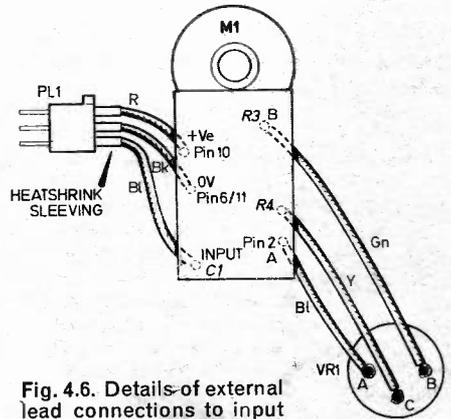


Fig. 4.6. Details of external lead connections to input plug PL1 and to feedback pot VR1.

COMPONENTS

SERVO

Resistors

- R1 150k Ω
- R2 100k Ω
- R3 10k Ω
- R4 1.2k Ω
- R5 300k Ω
- R6 300k Ω
- All $\frac{1}{8}$ W carbon $\pm 5\%$
- VR1 1.5k Ω plastic film potentiometer*

Capacitors

- C1 1 μ F tantalum bead 10V
- C2 22 μ F tantalum bead 6.3V
- C3 2,200pF ceramic
- C4 0.47 μ F tantalum bead 10V
- C5 0.22 μ F tantalum bead 35V
- C6 0.047 μ F ceramic disc
- C7 0.01 μ F ceramic
- C8 0.01 μ F ceramic


Semiconductors

- TR1,2 ZTX550 or ZTX750 (Ferranti)
(2 off)
- IC1 ZN419CE or SRC419P

Miscellaneous

- M1 Motor, 11 Ω *
- PL1 3-pin plug (SLM)
- Printed circuit board. Wire for leads. Heat shrinkable, plastic sleeving.

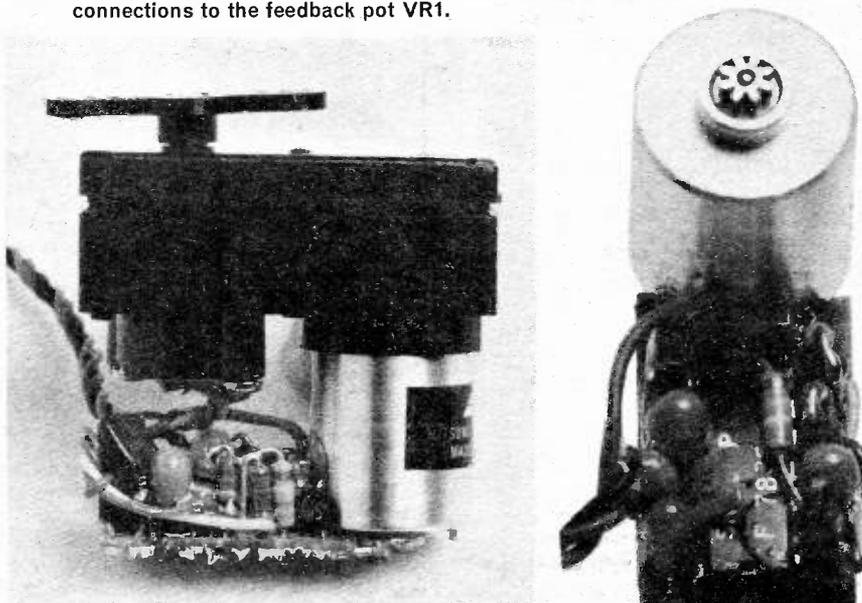*Part of Servo mechanism, type FB1 or FB2, available SLM Model Engineers.



Side and plan views of the servo unit.

FEEDBACK RESISTORS

The resistors R5 and R6 are the feedback resistors which stop any tendency of the servo to overshoot its final position. The values of 300kilohm are chosen for servo mechanics which are fairly fast in the movement where overshoot tendencies are highest, whereas if the user intends to use a slow servo (such as a SLM FB3) then this value can be raised to 360kilohm or even 390kilohm.

The variable feedback pot VR1 is of 1.5kilohm in value and is usually supplied as a plastic film pot with the servo mechanics. The 11ohm motor M1 also comes with the mechanics.

It is strongly recommended that the transistors TR1 and TR2 are of the ZTX550 type as these have an exceptionally low saturation voltage thus enabling more power to be transmitted to the motor.



The servo electronics are assembled on a small p.c.b. and this is finally attached to the servo motor.

The motor and the feedback pot are integral parts of the servo mechanism unit.


If you thought the soldering for the transmitter and receiver was tricky then you may have difficulty with the servo amp. However, the building of these units should have given you enough practice and confidence to attempt the servo amp and produce a working and reliable servo.

The p.c.b. pattern is given in Fig. 4.4 and the component layout in Fig. 4.5. The smallness of this board and the close packing of the components on its upper (plain) side demand a high order of skill and dexterity on the part of the constructor. **This is obviously NOT a task to be undertaken by the inexperienced.**

ASSEMBLY OF COMPONENTS

Assembly on the p.c.b. should start with the mounting of IC1, followed by the two components C3 and R6 which sit on top of it.

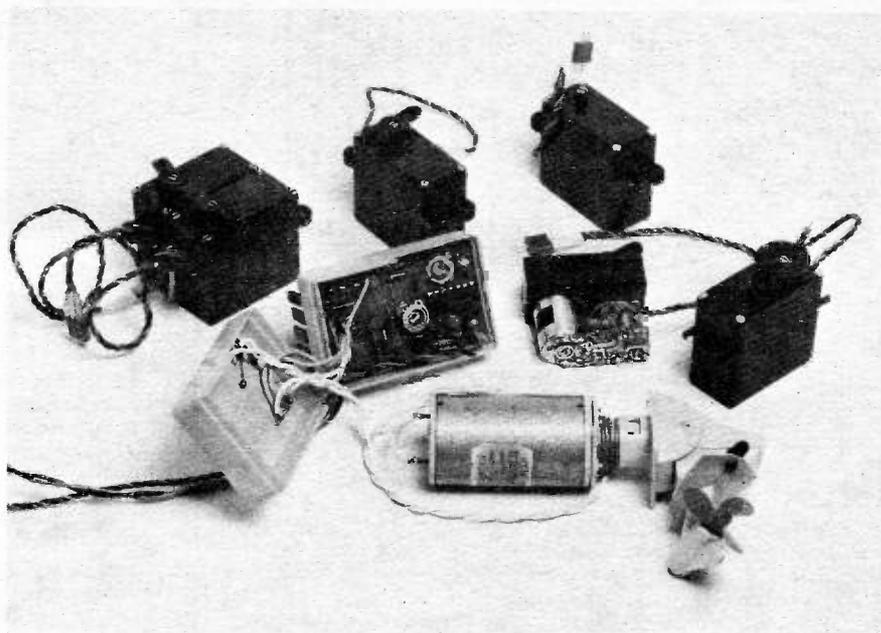The resistors R2 and R4 are fitted next, before the resistors R3 and R5 which require to be fitted in by soldering to the top lead of the former, respectively, as in Fig 4.5(b).



A group of five typical servo units, and (centre) the proportional speed controller and drive motor with propeller/rudder attachment.

In all cases where a wire is to be soldered into the same "land" on the p.c.b. as a component lead it is best to leave the soldering of the component until you are ready to fit the wire in then solder in both at once.

The remaining components can be fitted in in any order.

WARNING: When you purchase a ZN419CE you may get an old type in the full length package. On these packages it is possible for a small bit of metal to protrude from the pin 7, 8 end of the package and short to the base of TR2, so you may have to insulate accordingly. On the shortened package this is not possible as the metal is ground down flush with the plastic, also there is plenty of clearance with the pack and TR2.

EXTERNAL LEADS

To connect to the feedback pot VR1 you will require three lengths of thin insulated wire (the R.S. "miniature" wire is suitable). Lengths of 2 inches should be sufficient. For the input leads, 6 inch lengths of the same wire will be required. The input leads will require to be twisted together for neatness and connected to the plug as was done with the transmitter pot leads and the receiver output leads. See Fig. 4.5 and Fig. 4.6.

FITTING TO MOTOR

The amplifier is finally secured to the motor by the two tinned copper wire leads and the motor case tag. Again, cut-off resistor leads are suitable as the links. Fig. 4.5 shows the connections to be made to the amplifier.

The input leads will require to have a suitable plug attached, which in the case of a new constructor is the 3-pin SLM plug as mentioned in the receiver section (Part 3). Fig. 4.5 shows the connections to it. Three $\frac{1}{4}$ inch lengths of heat shrink sleeving will be required over the connector soldered joints, and for the pot joints.

TESTING

The completed servo should be thoroughly checked for any shorts between tracks—which on this p.c.b. are particularly close. If in doubt check with the p.c.b. artwork.


Providing that everything is connected the correct way round there is little else that can be wrong so connect to the receiver and switch on both the transmitter (first) and then the receiver. The servo should rotate to some position, and then follow the relevant stick on the transmitter.

If the servo continuously rotates or hunts around a certain position then the likely fault is that pot connections require to be reversed. This is done by removing from the pot the two end connections A and B on Fig. 4.5 and swapping them around. Reconnect the servo and switch on again and the servo should now follow the stick correctly.

Should problems still be present, recheck everything especially the transmitter and receiver if this is first time they have been tried with a servo.

A comprehensive fault finding chart will be given at the end of this series.

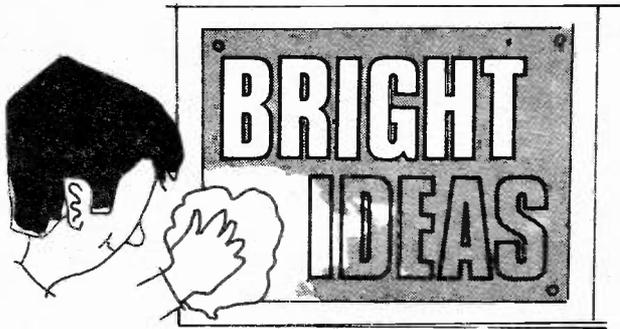Next Month: Proportional speed controller.




Readers' Bright Ideas; any idea that is published will be awarded payment according to its merit. The ideas have not been proved by us.

LETTER BELL

Nearly all houses have doorbells for visitors to attract our attention. The same idea could be used on a letter box. It would tell us when the post arrived.

A microswitch fixed on the letter box could be in parallel with the doorbell switch as shown. If a separate alarm is wanted the circuit could still run off the same batteries as shown below.


Robin Hudson,
Bracknell, Berks.

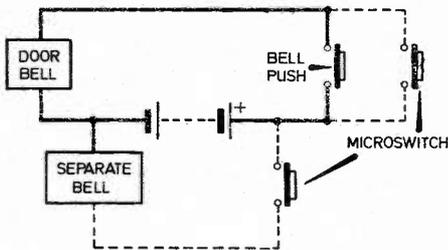

BATTERY HOLDER

If a circuit requires a 1.5V supply, an effective holder can be made from a vitamin tablets container normally available to expectant and nursing mothers from clinics.

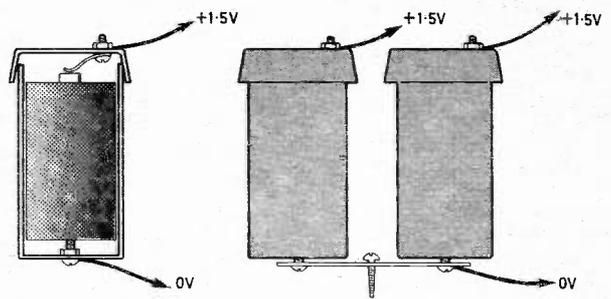The container is made of plastic with a snap-fit lid, which produces a leak-proof holder. The centres of the



lid and base are drilled and a bent-over solder tag bolted to the inside of the lid (orange/red conveniently to indicate positive terminal) and a pointed screw through the base. When the lid is clicked into position, a good connection is made. The holders can then be fixed with confidence inside a small project box, alongside the circuit board.

K Croft,
Broadstairs, Kent.

SIGNAL TRACER

I have evolved a simple method of tracing audio signals in a circuit. A crystal earpiece is used, but the plastic jack plug is replaced with a 3.5mm metal barrelled jack plug.

Whilst holding the metal barrel, the tip of the jack plug is touched against the various audio points in the circuit and a signal should be heard in the earpiece.

One point to notice is that apparently a complete circuit is not made; but this is not usually necessary due to stray capacitance.

Kevin Hadfield (aged 15),
Clifton, Nottingham.

NOVEL CASES

I have found that by looking around the most unlikely objects can make novel and interesting cases.

A tape cassette box is ideal for "mini" projects if some sort of clip is used to hold the sides together. A plastic lunch box of the type which has two sections the same size makes a very professional looking case.

Holes for potentiometers, switches etc, can be made with twist drills. The cases can, of course, be painted if desired.

J. Murphy (aged 15),
Waterfall, Ireland.

PLEASE TAKE NOTE


Twinkling Star—December 1979

A discrepancy exists between the value of C1 in the circuit diagram and the components list. Either value can be used. A 2200µF was used in the prototype.

Trailer Flasher Unit—August 1979

An important factor regarding the extension of the brake lights has recently been brought to our attention.

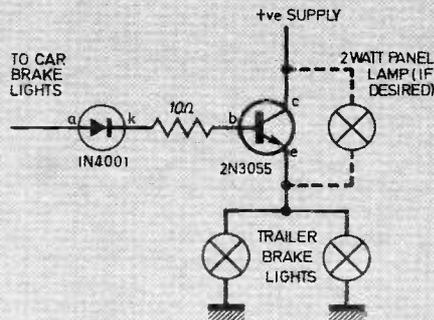The Lucas hydraulics—pressure brake—light switch fitted to some




cars cannot be used to additionally power the trailer lights as simply as was suggested, since the switch was designed to handle only 50 watts. Exceeding this rating could cause rupture of the diaphragm in the switch, resulting in a loss of brake fluid. For cars fitted with such a switch a "third channel" is required as shown above.

Xmas Bright Ideas—

December 1979

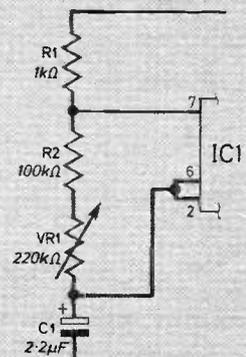In the Santa's Eyes circuit, Fig. 1 page 782, resistor R2 has been misplaced. The circuit diagram should be amended as shown below.



Everyday News

POST OFFICE VIEWDATA GETS TOP AWARD

Britain's premier engineering award, The MacRobert Award, has been won, this year, by a consultant engineer, Mr. Sam Fedida, and Post Office Telecommunications for the invention and development of the Prestel viewdata software system.

HRH The Duke of Edinburgh, Founder President of the Council of Engineering Institutions, made the presentation of the MacRobert Medal and £25,000 to Mr. Fedida for the invention of the viewdata concept and the MacRobert Gold Medal to Mr. Peter Benton, Managing Director of Post Office Telecommunications, at Buckingham Palace.

The MacRobert Award, made annually by the Council of Engineering Institutions on behalf of the MacRobert Trustees, is presented in recognition of an outstanding contribution to innovation in engineering and physical technologies, or in the application of physical sciences, which has enhanced the prestige and prosperity of the United Kingdom. The rules allow the prize to be made to a team of no more than five people or to an individual.

The concept of viewdata was invented by Mr Fedida whilst working at the Post Office Research Establishment, Dollis Hill, in the 1960s. Prestel is the Post Office's electronic information service which combines a modified TV, telephone line and computer and is claimed to put Britain years ahead in the mass marketing of electronic information.

The Post Office launched Prestel last year as the first public viewdata service in the world. A push-button, remote-control panel calls up

a "page" of the information required by a subscriber on to a television screen using a telephone line link routed into a computer data bank.

There are currently 1,750 Prestel sets linked to the system and some quarter of a million "pages" of information in the storage bank provided by 800 British and international organisations. The growth potential of Prestel is such that it will eventually be within the grasp of every telephone user in the country.



The service, now centred in London, will be extended to other centres during the year. Prestel is a joint project in which the Post Office has co-operated with the country's electronics indus-

tries and information providers.

The Post Office has already sold Prestel technology to telecommunications authorities in West Germany, Holland, Switzerland, Hong Kong and the USA.

Swiss Time Olympics

This year's Olympic Games in Moscow will be officially timed throughout by Swiss electronic equipment.

This prestige appointment reinstates Switzerland as world leaders in time-keeping and in their traditional role in the Olympics. The Japanese took over only when the Games were staged in Japan.

CB Hit By Cuts

On Monday night 26 November, Mr. Timothy Raison Minister of State Home Office told the all Party Committee on CB that a good deal of work had been done in examining the possibility of introducing a CB Service in the United Kingdom, but it was too early for any firm decision to be reached.

Mr. Raison told the Committee that there was no question of having a CB Service on 27MHz; the main problem was that of providing staff to undertake regulatory duties on alternative frequencies at a time when the Government was committed to reducing the size of the Civil Service.

TRIP OF A LIFETIME

A week in Japan with all expenses paid is the first prize to be announced for the "Young Engineer for Britain 1980" competition.

The award, a new one sponsored by "The Engineer", will be made for the best individual electronics project. The trip will enable the winner to see some of the many electronics applications in Japan. An alternative to the trip is £500 in cash.

Honour for CPU Work

One of the United States' most coveted awards for scientific and technical achievements, The Franklin Institute "Stuart Balantine Medal", has been won by Dr Marcian E. (Ted) Hoff, of the Intel Corporation, for his development of the Microprocessor.

In addition to his work on digital microprocessors he contributed to the development of the first high-density memory devices for both mainframe computers and microcomputers and more recently the first analogue microprocessor.

In 1969 he proposed the microprocessor architecture, the first microprocessor, leading to the production of Intel 4004, in 1971.

An electronic device which emits a loud tone if a "this-way-up" packing crate departs substantially from its correct upright position has been designed by Auto-systems Development, Huddersfield.

Called Topsy-Turvy, it should help protect fragile products or delicate scientific equipment from careless handling while in transit.



ANALYSIS

SURVIVING WITH LSI

Large scale integration (l.s.i.), has been overshadowed in the headlines by more pressing problems of the Ayattollah, the energy crisis and the continuing debate on the economy. L.S.I. and its consequences have not, however, gone away, nor has the debate.

Let's take the simple everyday example of the wristwatch, once universally regarded as the highest level of precision engineering and a miracle of mechanical ingenuity and craftsmanship. Today's digital watch of chronometer accuracy has only five components or assemblies; the display, the l.s.i. chip, the quartz crystal, the case and the battery. It can be assembled by anyone with nimble fingers without years of apprenticeship and experience in the watchmaker's art.

The threat is that all old-style watchmakers are to lose their jobs, as many clearly have. The promise is that everyone is now able to afford a wristwatch of chronometer accuracy. In its cheaper forms it is already a throw-away item, not worth the cost of repairing, and so it can be argued that even the watch repairer will suffer damage to, if not the complete destruction, of his traditional business.

This, and other examples feature in a report issued by the European Trade Union Institute which was discussed in Oslo last December. For instance in a well-known make of sewing machine 350 mechanical parts are replaced by one MPU. A new German telex terminal goes even better with the MPU throwing out 936 mechanical parts. The electronic office is also prominent with Bradford Council quoted as an example where the typing staff has been reduced from 39 people to 19 for the same volume of work.

Wherever we look we find electronics making work easier and cutting costs. L.S.I., by slashing assembly costs compared with that of discrete solid state, let alone the older valved sets, has more than stabilised the cost of colour TV sets. They are much cheaper relative to income as well as of better quality and more reliable than they were in 1970. In fact electronics is the only commodity which gets cheaper every year.

Naturally trade union leaders are concerned that their members' employment is under threat in a great number of occupations. But they only too easily forget that while many traditional skills are being phased out new skills are needed for the new technology. Put a stop to electronic data processing and whole armies of equipment and component assemblers as well as programmers would finish up in social security queues.

My own view is that, on balance, electronics has proved beneficial rather than harmful. And that we shall all adapt to changing circumstances as mankind has always done in the past. Imagine the screams of protest from stage-coach drivers when the railways came. Not all that different, one imagines, from postal workers today confronted with the prospect of electronic mail.

Brian G. Peck.

Heath Carries On

The supplier of the popular Heathkit home construction electronic kits Heath (Gloucester) Ltd, has changed its name to Heath Electronics (UK) Ltd. This follows the sale by former parent company Schlumberger to Zenith Radio Corp.

All electronic kits will still be sold under the Heathkit

brand name. MPUs and peripherals are to be marketed as Zenith Data Systems and education courses as Heath Education Products.

When the activities of the British Post Office are separated by Act of Parliament into two separate businesses the new name for the telephone business will be **British Telecommunications.**

Teletext

A low-cost system for adding Ceefax, Oracle and Prestel services to TV sets has been developed by General Instrument Microelectronics.

It uses only three MOS-LSI chips and a few peripheral components and can be built on a PCB only 15x10cm. The chips will be made available to TV set manufacturers.

NEW TECHNOLOGY IN INDUSTRY

A report entitled "Impact of Microprocessors on British Industry" published recently by the NCC states that Britain has no choice but to go forward with micro-electronics technology or "go out of business". The significance of this particular publication lies in the fact that it represents a consensus of opinion between several disparate groups—management, trade unions, academics, etc, and its importance was summed up at a recent press conference by the author Francis Kinsman when he said, "We must manage a change and not let it manage us".

On a more sinister note when asked whether a "Clockwork Orange" situation of disaffected youth running amok amongst society could develop, it was said that there was always such a danger if the new technology was mishandled and educational possibilities were not taken up although the micro-processor should not be made a scapegoat for societies ills.

In effect most aspects of the applications of micro-technology to industry are covered in the report which can be obtained from the National Computing Centre, Oxford Road, Manchester, at a cost of £5.50.

BREADBOARD '79 SECOND SUCCESSFUL YEAR


Over 11,000 electronics enthusiasts and dealers from all over the UK flocked to Breadboard '79 during its successful five-day run at the Royal Horticultural Halls, London, last December.

A capacity crowd on the last day necessitated the closing of the show for part of the morning in order that numbers could be controlled.

"Breadboard '79 has now firmly established itself as the major public exhibition for the home electronics enthusiast" say the organisers Trident International Exhibitions Ltd. A statement firmly endorsed by the delighted exhibitors.

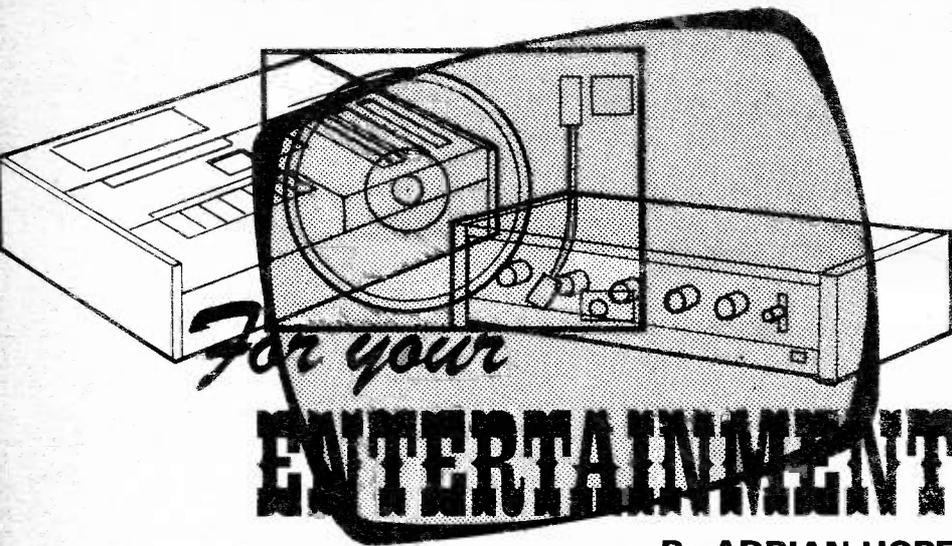The Everyday Electronics stand at Breadboard '79





By ADRIAN HOPE

Call for Freedom

Everybody loves to hate the British Post Office. On the whole they do a pretty good job, but like all government backed monopolies, can be infuriatingly insular.

Currently, until the new laws regarding telephones take effect, the Post Office monopoly on telephones is still total. But in the USA the phone company's monopoly now stops at the telephone users front door. Here's how it's happened.

Up to five years ago any USA subscriber who wanted to use his own telephone or telephone gadget had to pay the phone company for the installation of a "protective device" to isolate it from the telephone system. He then had to cough up a monthly rental of between 2 and 4 dollars.

Nationwide cries of extortion, finally prompted the Federal Communications Commission (the FCC is equivalent to the British Post Office and Home Office rolled into one) to rule in 1975 that subscribers needn't use a phone company protector as long as the equipment used was registered. Then in the Winter of 1977, after two years of court battles, the US Supreme Court completely broke the phone company's monopoly. The Court ruled that private equipment could be hooked up to the telephone system provided it was compatible with the network and of a make approved by the FCC.

With this ruling a market for 125 million home telephones was created overnight and sales have quadrupled every year since then. In the USA phones are now big business. They are sold already fitted with a tiny plug that fits into a wall jack socket. In theory the phone company should install this socket, but in practice it is often installed by the user or an independent contractor.

Choice of Equipment

You can now buy an extraordinary range of plug-in telephone gadgetry in the USA. Push button telephones are all the rage and many of these have memory circuits which enable the subscriber to call the same number over and over again without re-keying it.

On some telephones this "last number recall" is commanded by the push of a button. But on more exotic phones a

number can be automatically recalled over and over again, until connection is made.

This can be very useful if you are trying to dial overseas or long distance over lines that are continually "engaged, please try again later." It could also be useful if you are dialling a telephone that is in heavy use and thus often engaged.

There is gadgetry to divert calls automatically from one telephone number to another, there is gadgetry to patch in several phones at one and the same time and there are memory and calculator phones on which you can do sums, and in which you can store dozens of numbers for auto-dialling at the push of a button.

Voice analysers are available and these are supposed to detect stress in the speech of a caller. There are countless answering and message machines based on simple tape recorders.

One Californian hospital had a cardiograph permanently hooked to a telephone line so that patients can call in to the hospital, feed the sound of their heart beat down the line and receive instant diagnosis of any problems.

Because CB radio is legal in the USA there are now any number of cordless telephones which rely on a radio link. A mains powered CB transceiver base station is hooked up instead of the phone and this links with a hand set with a built in battery powered transceiver which the user can carry around the house or into the garden. Calls can be made or received from anywhere within a hundred yards of the base station.

Exotic Memory

Until recently the British Post Office showed little or no interest in telephone gadgetry, other than to remind subscribers that they were forbidden to use anything other than authorized and rented PO equipment on PO lines. But you can now buy exotic phone gadgetry in England, mainly thanks to enterprising importers who bring it in from abroad. Also many people holidaying overseas now bring a telephone or two home with them. The Post Office has countered by offering British subscribers more variety.

In theory at least, British subscribers in some parts of the country can now rent a push button memory telephone from the Post Office. But it's not cheap,

connection charge is £5.00 and rental is an extra £7.00 a quarter plus VAT, which makes it almost twice as expensive as an ordinary telephone.

As memory recall phones of this type are on open outright sale in the USA for £50 upwards, and on open sale in some British shops for around twice that figure, it's hardly surprising that more and more British subscribers are crossing their fingers and buying their own phones for unauthorised installation. What's more although authorised memory phones are advertised as available from the Post Office, in practice they seem to be in pretty short supply.

Installation Problems

Anyone tempted by the idea of unauthorised installation of an exotic phone should bear a few technical and legal facts in mind.

In the USA there are two quite different types of telephone. One, the so-called MF type, switches a matrix of passive components across the line as you dial or key in the number.

This produces a series of different musical tones which the exchange equipment recognizes as a dialling instruction. The advantage of this type of phone is that it can be made and sold very cheaply, because very little circuitry need be incorporated in the user's equipment.

In the distant future the UK system will be capable of handling MF telephones, but so far it isn't. So anyone travelling abroad and bringing back an MF telephone to the UK will find it utterly useless.

The other type of phone generates a stream of pulses either from a dial or keyboard. All UK exchanges use the pulse system but a pulse phone bought abroad may or may not work in the UK. It all depends on the rate of the pulses. If they are too rapid the British telephone exchange will simply ignore them.

Contrary to public opinion, it is not illegal to connect an unauthorised phone in the UK. You won't be arrested and charged if you are caught. But, perhaps more important, the Post Office can cut off your line.

When you apply to the Post Office for a telephone line you sign an agreement not to connect "anything not provided by the Post Office". The Post Office Telecommunications Scheme, which legally reinforces the Post Office monopoly, makes it quite clear that anyone with an unauthorised attachment can be asked to disconnect it. If they refuse the Post Office is entitled simply to disconnect their phone line at the exchange.

The Best

The British phone system is one of the best in the world and growing by more than a million more customers each year. It risks being degraded if subscribers hang unauthorised gadgetry on the line, often introducing faults through their ignorance of subtleties such as ringer resistance and the need to wire multi-phone installations in a series-parallel combination.

Moreover the amateur connection of mains powered gadgetry risks feeding potentially lethal voltages onto the lines. If a wide range of approved gadgetry were readily available for outright purchase at reasonable price, there would be a positive disincentive for subscribers to act irresponsibly.

RADIO WORLD

By Pat Hawker, G3VA

WARC—Uneasy Outcome

Those who have been closely involved with the recent World Administrative Radio Conference in Geneva seem agreed that by no stretch of the imagination can it be said that the ten or so weeks spent solidly talking about the division of the radio spectrum among its many users have produced a significantly mored orderly or more workable International Table of Frequency Allocations. The highest praise seems to be that conceivably (and at one time likely) the outcome could have been worse.

It has been suggested to me that only two groups of spectrum users have any cause to be moderately pleased with the results: the radio astronomers (who need protected bands primarily for reception only); and the radio amateurs who at least succeeded in their quest for three completely new (although very narrow) h.f. bands: 10-100 to 10-150MHz (29.6 metres); 18-068 to 18-168MHz (16.5 metres); and 24-890 to 24-990MHz (12 metres).

However, even the amateurs are not jumping for joy. The main worry is that it is very difficult at this stage to assess just what effect the many new "footnotes" and "resolutions" will have on existing and future services: very few frequencies are likely to be available on a world-wide "exclusive" basis and much depends on the extent to which the various reservations and footnotes are actually used.

Amateur enthusiasts should have every reason to be grateful for the work of their national and international organisations, particularly the Radio Society of Great Britain and the International Amateur Radio Union. British amateurs seem unlikely to lose any of their existing frequencies although many of these have to be shared with other services.

Broadcasting

Broadcasters and short-wave listeners concerned with international services have gained a good deal less than they originally hoped. It became clear that many of the developing countries still regard point-to-point h.f. communications as more important than broadcasting and are not yet ready to agree to transfer services to space satellites; yet at the same time these countries wish to ensure that when they are ready to use satellite systems there will still be geostationary orbital positions available for them.

For U.K. domestic listeners the most important result would seem to be that the Band II v.h.f./f.m. broadcasting band will eventually extend up to 108MHz rather than 100MHz. It should be noted that it is by no means certain that all of the 100 to 108MHz sector will necessarily be available to broadcasters in the United Kingdom, even after 1995. Nevertheless, it seems likely that some extra Band II frequencies will be available here within a few years.

A new footnote makes provision for traffic information services such as Carfax at the low-frequency end of the medium wave band. And again, a footnote will facilitate the use of mobile (transportable) earth stations to allow space satellites to be used for relaying news and sports events on television, as pioneered during the past year or so by the IBA.

Much more doubtful is the future of direct-satellite sound broadcasting in a band somewhere about 1GHz and 2.5GHz; although a number of countries urged that such a facility should be reflected in the frequency table, there was an argument about which band would be technically most suitable. In the end the decision was deferred, coupled with a resolution that experimental work should be undertaken. Indeed, many questions relating to broadcasting have been deferred to a whole series of planning conferences due to be held over the next few years.

Meanwhile it looks as though we shall be burdened with a rather tattered International Table with something approaching three times the number of "footnotes" (virtually agreements to disagree) than before, plus a large number of "resolutions" that may or may not be taken up by national administrations. For most spectrum users the decisive power governing what they can and cannot do will rest firmly with their own national administrations. Just as a British "Citizen's Band" appears once again to have been shelved for an indefinite period, so must all radio spectrum users depend on what the Home Office Radio Regulatory Department ordains.

Radio and the Fastnet tragedy

Recently the "Observer Magazine" commenting on the tragedy that overtook the 1979 Fastnet yacht race questioned whether it should be mandatory for all yachts in such events to carry two-way radio equipment. At present the rules of the Royal Ocean Racing Club require only the yachts must carry a radio receiver capable of picking up weather forecasts. If all boats had carried radio communications equipment "panicking crews on small boats could have been advised and reassured".

Certainly the need for effective communications in such circumstances may seem an obvious and necessary precaution. But there is a counter argument put forward by the Observer's writers that if all the yachts in trouble had been equipped for VHF Channel 16 (the marine emergency channel for v.h.d. radiotelephones) "nobody would have been able to pick up anything... old hands were complaining about very irregular radio procedure and such a density of traffic that it was difficult to make out

just what was going on. If boats in the Fastnet are going to be required to carry a two-way radio then it will also be necessary to demand proof that somebody on board is trained to operate it."

The fact that equipment is only part of any successful communications link and that the human operator still occupies a key role is something, I feel, that too often gets overlooked in these days of "intelligent" hardware. Perhaps part of the trouble is the way that in films and television plays, the users of two-way radios never seem to have any troubles.

All the actors seem to know exactly how to use their equipment and to pass messages clearly and without ambiguity. None of those confusing "send three-and-four-pence we're going to a dance" messages that turn out to be "send reinforcements we are going to advance"—or the tangles that can take place when there are a number of unskilled operators all trying to use the same channel.

Although the classic Tony Hancock disc "The Radio Ham" tends to be resented by some amateurs as totally unfaithful to the hobby, his hapless attempts to deal with the "Mayday" message from the sinking yacht "Billet Doux" 300 miles off the African coast is not only extremely funny but contains more than a hint of all the things that can in real life go wrong with emergency radio communications: broken pencils, radio interference, complaining neighbours, the electric meter running out, the mix up between latitude and longitude and the valves that go *phut* at the critical moment.

Although it would be an unfortunate sailor whose distress messages were subject to all these mishaps at the same time, not even the most skilled operators could claim that things never go awry.

The Cocktail Party Effect

One scientist who fully recognised the importance of the human being as an element of a communications system was Professor Colin Cherry of Imperial College, London whose death was reported recently.

It was Professor Cherry who first raised public interest in the curious "Cocktail Party effect". He showed that in a crowded room, with a number of people split into small groups and with each group talking simultaneously, it is usually still possible for a listener to concentrate on, and follow, the words being spoken in his particular group, even under conditions of such poor signal-to-noise ratio that one would expect the messages to become unintelligible.

This effect depends upon the very complex and still imperfectly understood directional characteristics of the auditory system and the ear/brain interface. It is these mechanisms that have been so successfully exploited in stereophonic sound systems and other sound processing techniques.

For instance, a few years ago it was my privilege to describe for the first time in print, how F. J. Charman, G6CJ had proved by deliberately simulating the "Cocktail Party" effect on incoming speech and Morse radio signals, by introducing an electronic delay line on part of the signal, it is possible to make intelligible signals that would otherwise be lost in the background noise.



micro MUSIC BOX

By R. D. Palmer B.Sc.

IN THIS article we show you how to make a replacement for the traditional musical box mechanism using the Chromatronics TMS 1000N MP 0027A musical microcomputer chip. This musical box is able to automatically sequence the tune each time it is played. Out of a total repertoire of 24 tunes it plays eight tunes in rotation. Alternative banks of eight tunes are selected by means of a three-way selector switch or link.

TUNE GENERATION

In a traditional type of mechanical musical box the tune is "stored" by means of the position of little brass pegs set into a barrel. The read only memory fabricated as an integral part of the microcomputer chip is virtually

an analogue of the mechanical system. This 1,024 word \times 8 bit device has all its data put in as part of the manufacturing process, and is therefore as permanent as the metal pins.

In the method of tone generation there is no comparison between the old type mechanical music box and this contemporary counterpart. Instead of plucking a set of metal reeds the TMS 1000N MP 0027A produces its notes by a complicated mathematical process which basically counts machine cycles (derived from the master oscillator) to produce the correct timing intervals for the precise frequencies needed for musical output.

An output from the chip oscillates at audio frequencies and drives a loudspeaker via an audio amplifier and processing network.

SYSTEM ARRANGEMENT

The functional areas of the music box are shown in the block diagram, Fig. 1.

The whole system is triggered by means of a touch plate which can either be fixed to the sides or the top of the music box. This is much easier to make than a switch which would be closed once the lid of the box was opened. The touch plate is much more adaptable and of course much more novel!

Once the plate is touched a minute amount of current is fed to the trigger input of the monostable which fires producing a pulse of approximately 60mS. This turns on the micro computer chip which within a few milliseconds activates the electronic power switch to maintain its own power supply.

It then starts to scan eight of its outputs R_0 to R_7 by turning each one on sequentially. It would continue to do this indefinitely if the three selector inputs K_1 , K_2 and K_4 stayed at a low logic level. However, one of the selector gates is arranged to be turned on by the divide-by-8 counter. Thus one of the R outputs activates one of the K inputs and the micro computer senses this and jumps to a new subroutine to play the tune associated with the particular R and K connections linked.

A raw audio frequency square wave is derived from the O_7 , O_6 , O_1 outputs from the chip and fed to an envelope generator. At the beginning of each note the envelope generator is triggered so that the square wave is shaped with an exponential decay. This makes a sound very similar to that of a chime or dulcimer.

The resulting waveform is fed to a simple audio amplifier in order to drive the output loudspeaker.

The tempo at which the microcomputer plays the tune being played is controlled by means of an external timer; for each note which is generated the processor produces a number of trigger pulses at its R_9 output. These initiate a simple RC timer which is sensed by its K_8 input. The number of timing cycles used for each note depends on the length required i.e. crotchet, quaver, semi-quaver etc.

When the system reaches the end of the tune the output controlling the power switch R_{10} goes low, causing the supply to be cut off to

COMPONENTS
 approximate
 cost **£10**
 excluding case

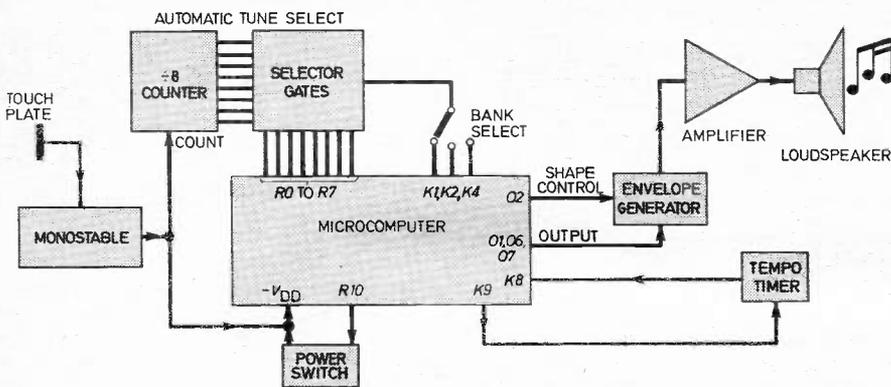


Fig. 1. Block diagram of the Micro Music Box.

the chip. Obviously this causes a complete halt of further activity. However, at this instant the divide-by-8 counter is clocked, thus enabling a new tune to be played the next time the touch plate is activated.

CIRCUIT DESCRIPTION

The complete circuit diagram shown in Fig. 2 should be regarded such that the positive $+V_{SS}$ rail is the common. This is because the TMS 1000N is a p-channel device and therefore powered from a negative supply. However, this should not provide any undue difficulty. It is not recommended to stand on one's head whilst comprehending the circuit diagram, nor indeed, inverting the magazine!

Power for the system is provided by two PP3 9-volt batteries in series, B1 and B2, making a total supply voltage of 18 volts. The three CMOS chips IC2, IC3 and IC4 used in conjunction with IC1 are permanently connected to the battery. This is possible due to the very low current drain of CMOS devices when not actually switching i.e. their quiescent current. The actual supply current for the musical box when it is not playing is less than 1 microamp.

TOUCH INPUT

A simple monostable is formed around an AND gate ($\frac{1}{4}$ IC3) by means of R2 and C1. The second input to the AND gate at pin 12 provides the trigger function. This is normally held logically high by R1 via R3.

When the touch plates are touched, current is diverted through the skin connecting the plates from the input therefore the level at pin 12 goes low, triggering the monostable for a time set by C1 and R2 which is approximately 60 milliseconds. However, if the touch input persists longer than this period then the output from the monostable will remain low until the input stimulus is removed. This would mean the musical box will play continuously provided the touch plate is kept touched.

Resistor R19 is designed to protect the delicate CMOS input device against possible static electricity damage discharged onto the touch plate. The value is kept as high as possible to minimise the peak current in this event.

The sensitivity of the touch input is controlled by R1. The lower the value of this resistor the more current which has to be diverted through the touch plates to activate the monostable. With R1 equal to 10 megohms the input is extremely sensitive and might be troublesome should condensation or sticky fingers contaminate the touch plate. If this is likely to be a problem then R1 could be 2.2 megohms or even 1 megohm.

POWER CONTROL

The output from the monostable going low applies the negative supply $-V_{DD}$ to IC1 via D1. Within a short

period of activation the processor turns on its output at R10 (pin 3) which is arranged to turn on switch transistor TR2 via R3. This transistor then holds on the negative power supply from the battery. Resistor R5 simply makes sure that leakage does not effect TR2 and also ensures a fast turn-off. At the end of a tune sequence, the R10 output turns off causing TR2 to turn off thereby removing $-V_{DD}$ from IC1.

TEMPO CONTROL

The tempo is timed by means of the RC network comprising C2 and R6 and VR1 in series. At the start of each note the processor turns on its output line at R9 (pin 2) momentarily. This turns on TR1 in order to discharge C2 completely. The timing capacitor C2 is then charged via the tempo control potentiometer VR1 and R6 until its voltage reaches about -3 volts with respect to $+V_{SS}$. At this point the K8 input (pin 8) senses a logical low and R9 is turned on once again to discharge C2.

This timer operation may repeat a number of variable cycles depending on the length of the note being played. The setting of VR1 can be arbitrarily set at any position according to taste.

The master clock timing components R8 and C3 set its frequency at approximately 400kHz. This only affects the overall pitch of the music, not the tempo.

TUNE SELECTION

Each time IC1 "shuts down" ($-V_{DD}$ line removed) the selection counter IC4 is clocked via its input, pin 14. This device is a Johnson decade counter which turns on each of its outputs sequentially on receipt of a clock pulse. All outputs of IC4, except one, are low (at logic 0). The position of the "high" output depends on the number of clock pulses received. Hence on the rising clock edge the "high" moves on to the next output.

The outputs are arranged to turn on sequentially each of seven and

CHOICE OF REPERTOIRE



LINK TO K1

Oh Come All Ye Faithful
Oranges and Lemons
Westminster Chimes
Sailor's Hornpipe
Land of Hope and Glory
Rule Britannia
God Save the Queen
Greensleeves


LINK TO K2

Soldiers Chorus (Faust)
Twinkle Twinkle Little Star
Great Gate of Kiev
Red Flag/Maryland/Tannenbaum
William Tell Overture
Beethoven's Ode to Joy (9th)
The Star Spangled Banner
Cook House Door

LINK TO K4

Mozart
Colonel Bogie
Wedding March (Mendelssohn)
The Lorelei
Tocatta in D Minor (Bach)
Deutschland Uber Alles
The Marseillaise
Beethoven's "Fate Knocking"

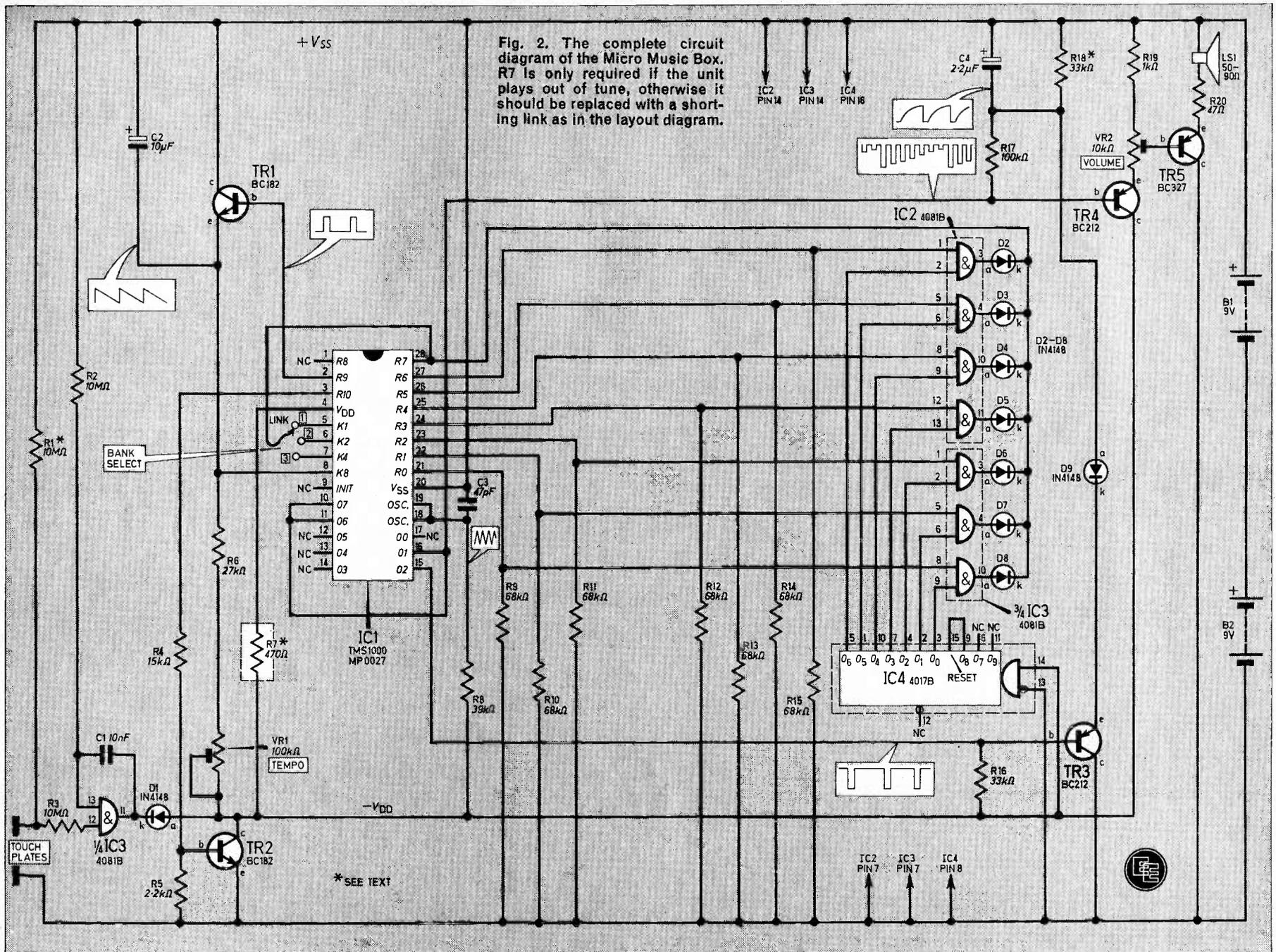The selection of the tune repertoire is made by the positioning of the K link (or switch if fitted)



* SEE TEXT

gates (IC2 and IC3), forming a 7-to-1 multiplexer. The connection of output pin 0_s (pin 9 IC4) to MR (pin 15) forces a reset on each eighth clock input.

When the processor first receives power it steps through its R0 to R7 outputs sequentially turning each one on for approximately 100µS.

Thus when an R output matches to the counter output in one of the selector AND gates its output goes high, ored by one of the diodes D2 to D8. This signal is linked to one of the K inputs K1, K2 or K4.

Output R7 does not need to be multiplexed by an AND gate in the same way as the others since it is the last one to be strobed. Resistors R9 to R15 merely provide a pull-down function for the R outputs to establish a proper logical low for the inputs of the AND gates.

If only one set of eight tunes is required then "Link 1" bank-select may be wired permanently. Otherwise a single-pole three-way switch can be simply installed so that all 24 tunes in the repertoire of the micro-computer can be played.

OUTPUT CIRCUITRY

All the microcomputer's outputs are open-drain types. This means they all need pull-down resistors of one sort or another to establish their output amplitudes. This facility makes it very easy to control the envelope of the audio output coming from 06/07/01 in combination.

Basically resistor R17 is the pull-down for these outputs, the voltage on C4 controlling the actual audio amplitude. As C4 effectively discharges through R17 and R18 (if fitted) then an exponential decay is applied to each note.

At the beginning of each note the output at 02 (pin 15, IC1) turns on TR3 momentarily charging C4 via D9. Thus peak amplitude occurs at the beginning of the note and gradually decays away.

The decay rate can be shortened by introducing R18, a typical value for this would be about 33 kilohm and would tend to make the sound more like a plucked pizzicato string rather than a chime sound.

Audio amplification is provided by TR4 and TR5 operating as a modified Darlington pair. This amplifier only needs to be fairly crude as the audio signal has a pulse format and is unaffected by additional clipping. Resistor R20 is used to limit the maximum current into the loudspeaker in order to prevent overheating of TR5. This value may be larger than 47 ohms if very loud volume is not required.

If an 8 ohm speaker is used then the volume will be quite low and R20 must be 68 ohms ½ watt or larger in value.



The prototype Micro Music Box was built on a piece of 0.1 inch matrix stripboard. All integrated circuits were mounted in sockets, IC1 using soldercon pins so that the unit could be safely assembled without the risk of static electricity damage etc. The i.c.s can then be plugged into their respective sockets only when the unit is complete and ready for testing.

An i.c. socket may be used instead of soldercon pins for mounting IC1, but will be more expensive. When soldercon pin sockets are used never remove the connecting strip until the board is absolutely ready and complete with the i.c.s pushed into position.

ASSEMBLY

Most of the components are mounted on a piece of 0.1 inch matrix

stripboard size 26 strips×46 holes. The layout of the components on the board is shown in two stages, for clarity, in Figs. 3a and 3b, the latter showing the wire links to be made after component assembly.

Begin by making the breaks along the copper strips on the underside according to Fig. 3c.

In the prototype the board was secured to the case by means of self-adhesive foam pads. If the board is to be held by bolts, the necessary mounting holes and isolating breaks around them should be made at this stage.

Assemble and solder in place the i.c. sockets and Veropins (or soldercon pins). These will then aid component positioning.

At this stage, it should be decided whether or not any of the controls, TEMPO, VOLUME, are to be adjustable by control knobs on the outside of the case. If so, flying leads should be attached to the board in place of the preset potentiometers.

Also, the bank select link may be made externally switchable by using a single-pole three way switch wired to the four Veropins near IC1.

Continue assembly by positioning and soldering in the resistors, capacitors, presets (if applicable), transistors, diodes and bare link wires,

COMPONENTS

Resistors

R1	10MΩ, see text	R11	68kΩ
R2	10MΩ	R12	68kΩ
R3	10MΩ	R13	68kΩ
R4	15kΩ	R14	68kΩ
R5	2.2kΩ	R15	68kΩ
R6	27kΩ	R16	33kΩ
R7	470Ω, see text	R17	100kΩ
R8	39kΩ	R18	33kΩ, see text
R9	68kΩ	R19	1kΩ
R10	68kΩ	R20	47Ω ½ W

All ½ W carbon ±5% except where stated otherwise

Potentiometers

- VR1 100kΩ horizontal skeleton preset or shafted type as required, see text
- VR2 10kΩ horizontal skeleton preset or shafted type as required, see text

Capacitors

- C1 10nF ± 20% ceramic or polyester
- C2 10µF 25V elect.
- C3 47pF ±5% ceramic or polystyrene
- C4 2.2µF 25V elect.

Semiconductors



- D1 to D9 1N4148 or other general purpose silicon diode (9 off)
- TR1,2 BC182 or other general purpose 30V *nnp* silicon (2 off)
- TR3,4 BC212 or other general purpose 30V *pnnp* silicon (2 off)
- TR5 BC327 or other general purpose medium power 500mW 30V *pnnp* silicon
- IC1 TMS 1000N MP0027A (CS107-01) microcomputer (Chromatronics)
- IC2,3 CD4081B CMOS Quad dual-input AND gates (2 off)
- IC4 CD4017B CMOS decade counter/divider

Miscellaneous

- LS1 miniature moving coil loudspeaker 50 to 90 ohms, see text
- B1, B2 9V type PP3 (2 off)

Stripboard: 0.1 inch matrix size 26 strips × 46 holes; battery connectors for B1, B2 (2 pair); d.i.l. sockets for i.c.s: 28 pin (1 off), 16 pin (1 off), 14 pin (2 off), or soldercon pins; case, minimum internal dimensions 75 × 200 × 38mm or Perspex sheet to build case; self-adhesive foam pads; self-adhesive rubber feet (4 off).

See
**Shop
Talk**
page 114

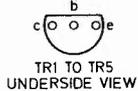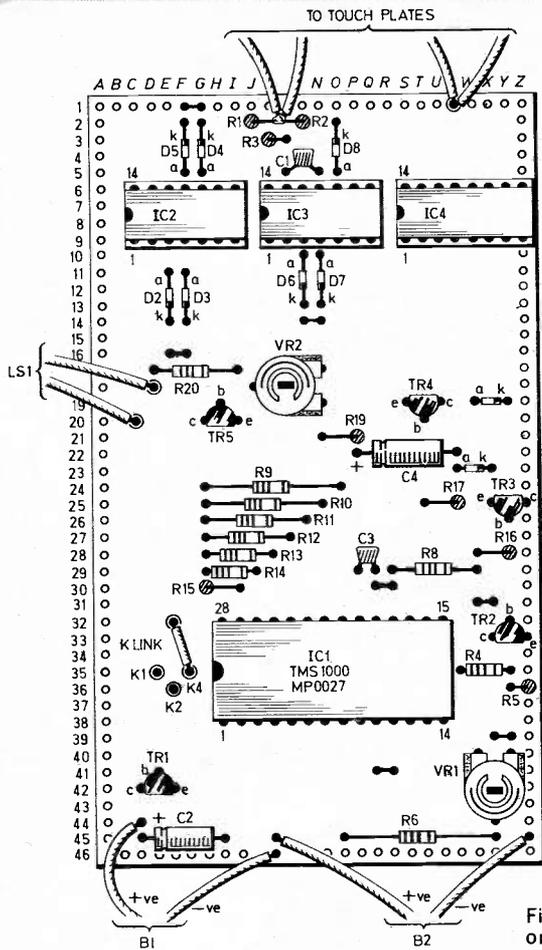

● = VEROPINS

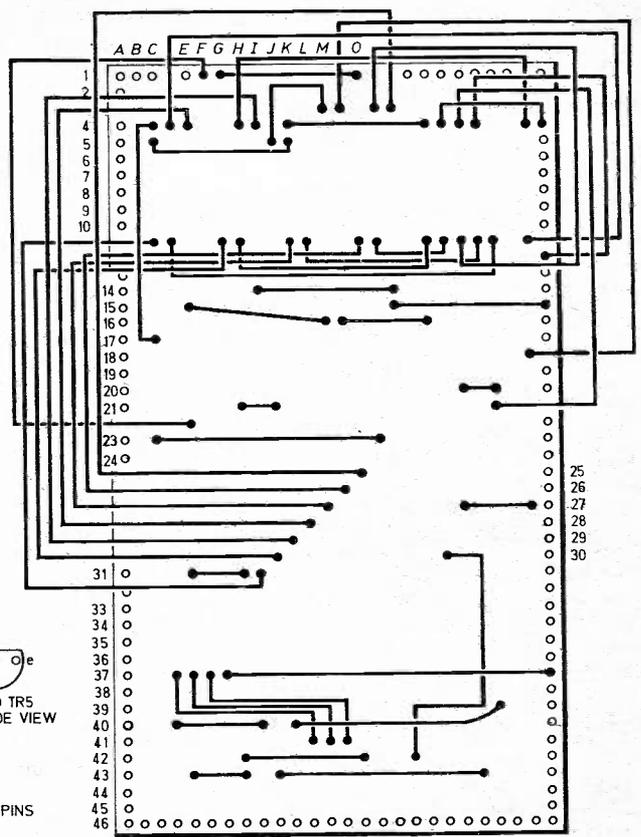


Fig. 3(a) (top left). The layout of the components and bare link wires on the topside of the circuit board; (b) (above right) Shows the remaining board interlinks to be made using lightweight p.v.c. covered wire.


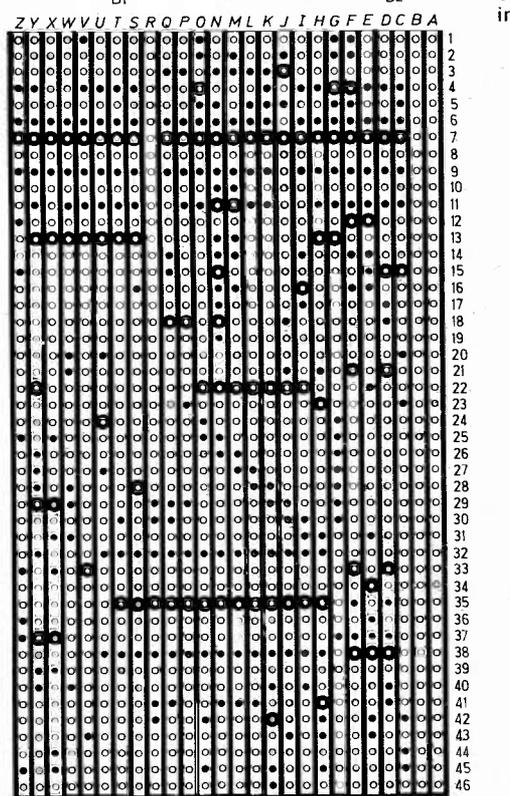



Fig. 3c. The underside of the circuit board showing the breaks to be made along the copper strips and all the soldered connections.


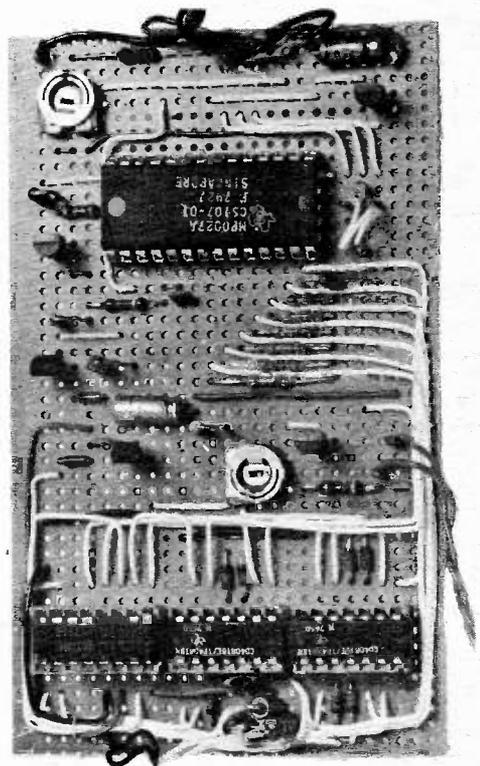


Prototype circuit board.

micro MUSIC BOX

Fig. 4. Shows the construction of the Perspex case used in the prototype together with the full-size printed circuit board pattern for the touch plates. The case panels shown shaded were colour tinted in the prototype. Three alternative touch plate ideas are shown at the foot of the page.

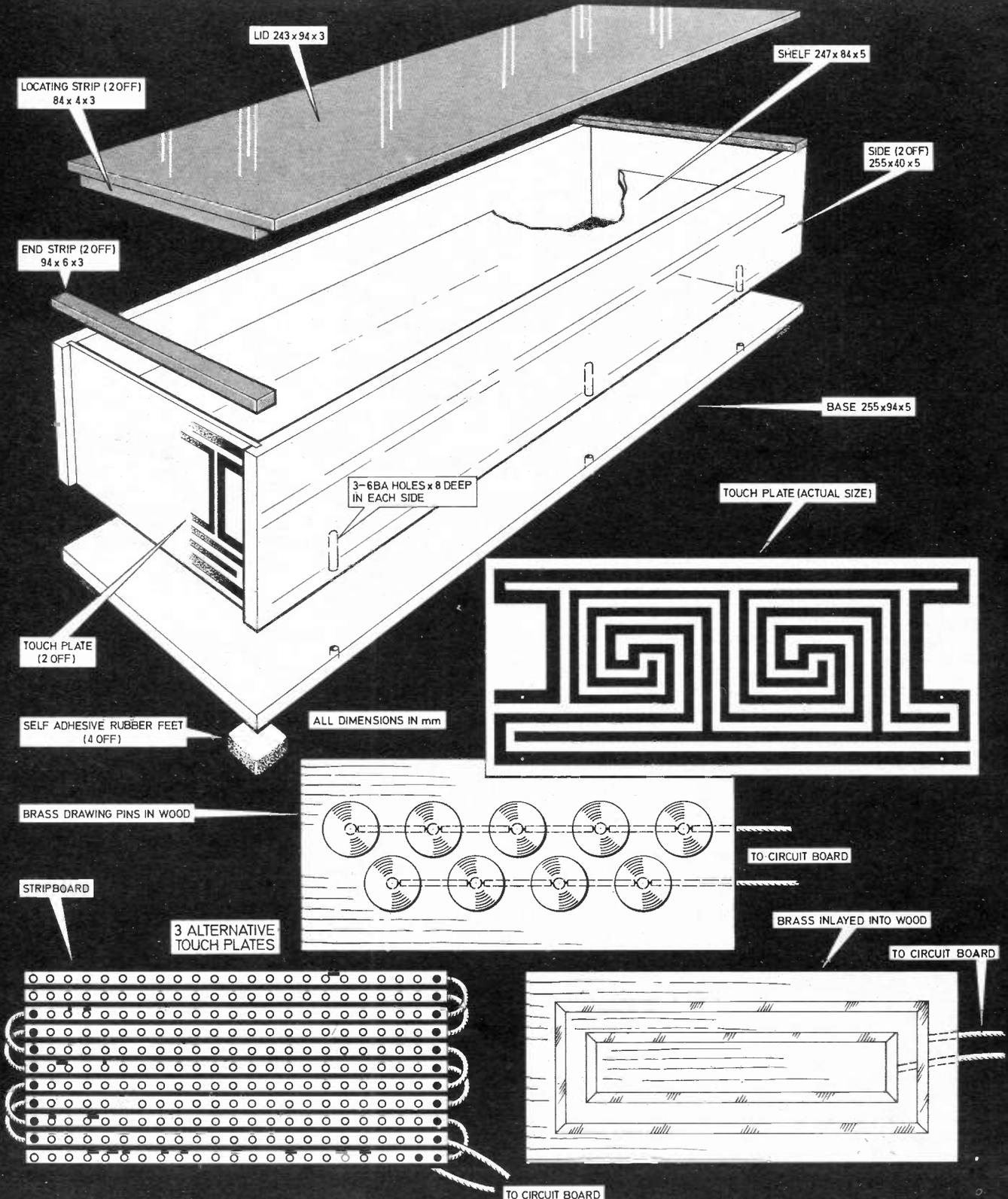

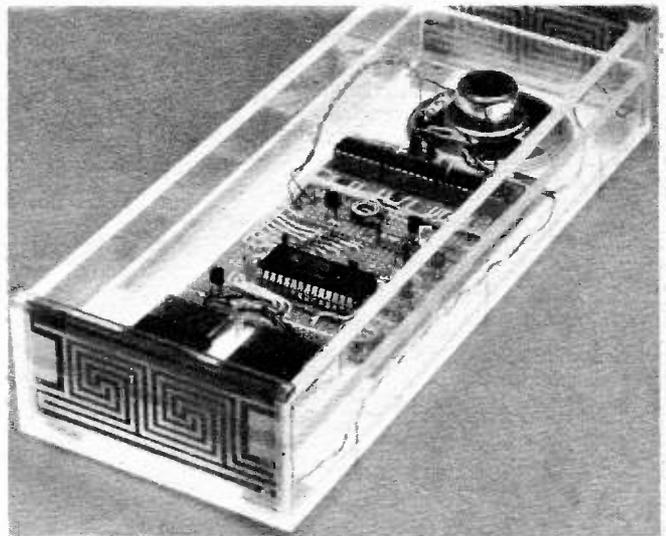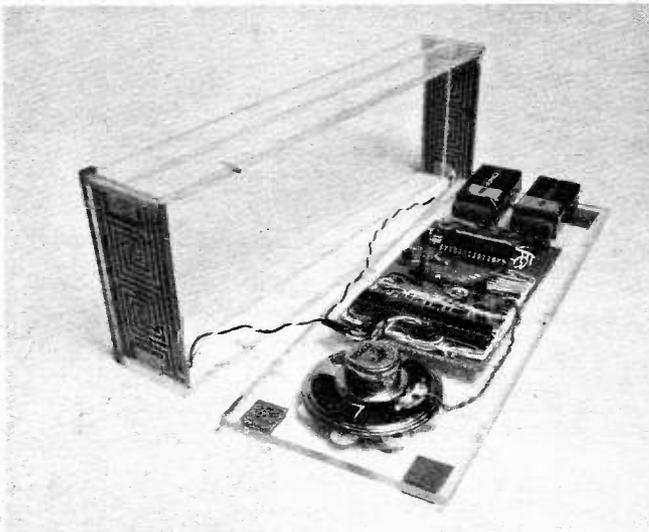

Now referring to Fig. 3b, begin connecting all the p.v.c. covered link wires.

Connect the speaker, battery and touch plate leads and then thoroughly check over your construction and read the following before inserting the integrated circuits.

HANDLING THE I.C.s.

Do not handle the integrated circuits unnecessarily prior to insertion in the sockets. All these devices are susceptible to static electricity damage and should only ever be handled by their plastic bodies. Check that the pins are true and straight. If not they may be carefully bent with long-nose pliers.

The rows of pins are usually splayed out very slightly wider than the mounting holes in the i.c. sockets. If this is so gently push the i.c. down edgewise on the flat of the pins onto a hard surface such as wood or Formica worktop. Make sure all the devices are inserted the correct way round and into their sockets as shown.

It may be slightly confusing at first to identify which end of the TMS 1000N MP 0027A is which! However, if you look carefully you will see that the top end i.e. that with pin 1 on the left hand side, has an indentation with flat sides to it whereas the opposite end sometimes has a small circular depression left by the moulding process.

If soldercon pins have been used, then once the i.c.s have been inserted the bridging strip can now be snapped off.

TESTING

On connecting the batteries, if all is well a tune will be heard in the loudspeaker—without touching the touchplate. Briefly placing a finger on the touch plate will cause another dif-

ferent tune to be played. If this is repeated at the end of each tune, the full eight tunes will be heard in sequence which will repeat in order for further operations.

The tempo can be varied by means of VR1, and the volume set by VR2.

If the unit does not operate as outlined, the following fault finding section should be consulted.

FAULT FINDING

If you have a multimeter then check the quiescent current when the batteries are connected is less than $10\mu\text{A}$. Playing out of tune usually means a low voltage spec TMS1000N. This is cured by the insertion of R7 (470 ohms) to drop the voltage to the V_{DD} pin. Normal supply current when playing is approximately 30 to 70mA.

If the unit should fail to operate properly then a multimeter on a voltage range between 20 to 30 volts d.c. may be used as a logic level detector. The positive lead of the multimeter is connected to the $+V_{SS}$ line and the negative lead used to probe various parts of the circuitry as follows:

1. When the touch plates are touched the voltage at pin 11 of IC3 should go from 0 to full battery volts.
2. When the touch plates are touched the voltage on the $-V_{DD}$ line should go from 0 to full battery volts and stay there after the touch is removed.
3. Check the voltage at the junction C2 with TR1 collector for 1.5 volts (approx.).
4. Check that one of the outputs on either pin 2, 3, 4, 5, 6, 7 or 10 of IC4 is low, all the others should be high. The low one should step round each time the unit is activated (plate touched).
5. The measured voltage on C4 at the junction of R15 should be 3 volts minimum.
6. The operation of the master clock that appears at pins 18 and 19 of IC1

can only be checked using an oscilloscope using a $\times 10$ probe. This will be normally 300 to 400kHz at a few volts peak to peak.

CASE CONSTRUCTION

The electronics for the Micro Music Box are small enough to be fitted into a variety of commercially made boxes of various sorts. One could even use an old cedar wood cigar box!

When selecting a box one must bear in mind that access is needed for the replacement of batteries and that the touch plate contacts be conveniently mounted somewhere on the exterior of the box. In addition it is important that the loudspeaker can be mounted in such a position to "baffle" it and let the sound out.

For the prototype it was decided to make a box from sheet Perspex with printed circuit board touch panels. This makes the box even more interesting being of transparent material which enables admirers to see the marvellous technological electronic miracle that you have built!

A fully dimensioned drawing showing the construction of the case, and a master p.c.b. pattern for the touch panels are shown in Fig. 4. Also shown are three alternative touch plate ideas that could be used instead. These are not drawn to the same scale as the p.c.b. pattern.

By fitting the loudspeaker into the base of the box and fitting feet to raise it a little above the table to let the sound out, the top of the box will be totally unencumbered with wires etc.

For symmetry two touch plates, one at either end of the unit are connected together in parallel. However this is not entirely necessary and one small touch plate would do quite nicely or even two large drawing pins side by side could be used where one doesn't want to spoil the exterior of a wooden box. □

BOOK REVIEWS

TELETEXT AND VIEWDATA

Author Steve A. Money
Price £5.50
Size 223 × 140mm 151 pages
Publisher Newnes Technical Books
ISBN 0 408 00378 2

WITH the growth in the number of TV sets equipped with teletext decoding and display equipment and the imminent general introduction of the GPO's Prestel system, the publication of a book explaining the principles of operation of this system is welcome.

This particular publication covers the ground from the basic system concept to circuit principles and ends with a look at the future. Although the book is well written and presented it seems to suffer from a general fault that whereas some sections are explained using full circuit diagrams others are left at the block diagram stage.

Some knowledge of electronics is assumed and students, engineers and particularly electronics enthusiasts should find the book stimulating and interesting. Separate chapters are devoted to an explanation of basic logic devices, data acquisition, memory, graphics and Teletext production. The various types of decoder are considered and the fitting of these into a standard colour TV receiver is discussed.

The book is not particularly cheap at £5.50 but it does present a worthwhile introduction to this expanding field of data communication. S.E.D.

ADVENTURES WITH MICROELECTRONICS

Author Tom Duncan
Price £3.25
Size 254 × 193mm 64 pages
Publisher John Murray
ISBN 0 7195 3672 3

AN interesting and appealing title which is not let down by the contents inside. Clear diagrams, bold type and

two-colour printing make this book an obvious choice for the inexperienced constructor wanting to familiarise himself with some of the more common i.c. chips.

One feature that is not made clear in the title is the fact that all the projects are built up on a proprietary breadboard. In fact this is a great help to constructors as it eliminates the need for messy interwiring and soldering although you would have to translate the layouts onto some other form of board if you didn't wish to pay out the £4 or £5 for a special breadboard.

The book opens with a brief explanation of the more common components including the breadboard and also mentions the resistor colour code before launching into the circuits proper. These are preceded by an in-depth examination of most (although one wonders why not all) of the i.c.s used and one or two preliminary experiments are given to show their operating features.

The projects featured cover a wide range of gadgets and each one is complete with a "how it works" section and suggestions for circuit modifications. The last idea is especially useful if the reader is looking for a deeper understanding of the circuit. S.E.D.

ADVENTURES WITH PHYSICS

Author Tom Duncan
Price £2.95
Size 254 × 193mm 58 pages
Publisher John Murray
ISBN 0 7195 3643 X

WITH a front cover strongly reminiscent of the latest kid's comic this book cannot fail to catch the eye of the younger reader. However, despite an abundance of two-colour illustrations, it is debatable whether our younger reader would persevere past the first half dozen or so pages.

The layout and style of the book is very similar to the Exploring Physics series of "O" level text books by the same author. Unfortunately this approach does not work quite so well for a general interest book and it is a pity that the cartoon style of the front cover could not have been carried on through the book.

This apart there are a great number of interesting experiments to try, none of which need special apparatus, followed by some fourteen models although a gas burner is required for some of these. All the major areas of physics are covered including mechanics, optics and electricity. S.E.D.

JACK PLUG & FAMILY...

BY DOUG BAKER




Now, the complete MK 14 micro-computer system from Science of Cambridge

VDU MODULE. £33.75


(£26.85 without character generator) inc. p & p.

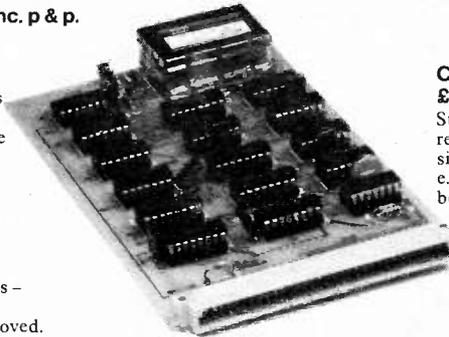Display up to ½K memory (32 lines x 16 chars, with character generator; or 4096 spot positions in graphics mode) on UHF domestic TV. Eurocard-sized module includes UHF modulator, runs on single 5 V supply. Complete ascii upper-case character set can be mixed with graphics.





CASSETTE INTERFACE MODULE. £7.25, inc. p & p.

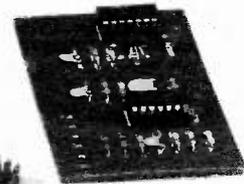Store and retrieve programs on any cassette recorder. Use for serial transmission down single line at up to 110 baud (teletype speed), e.g. over telephone line, and to communicate between two or more MK 14s.



POWER SUPPLY. £6.10 inc. p & p.

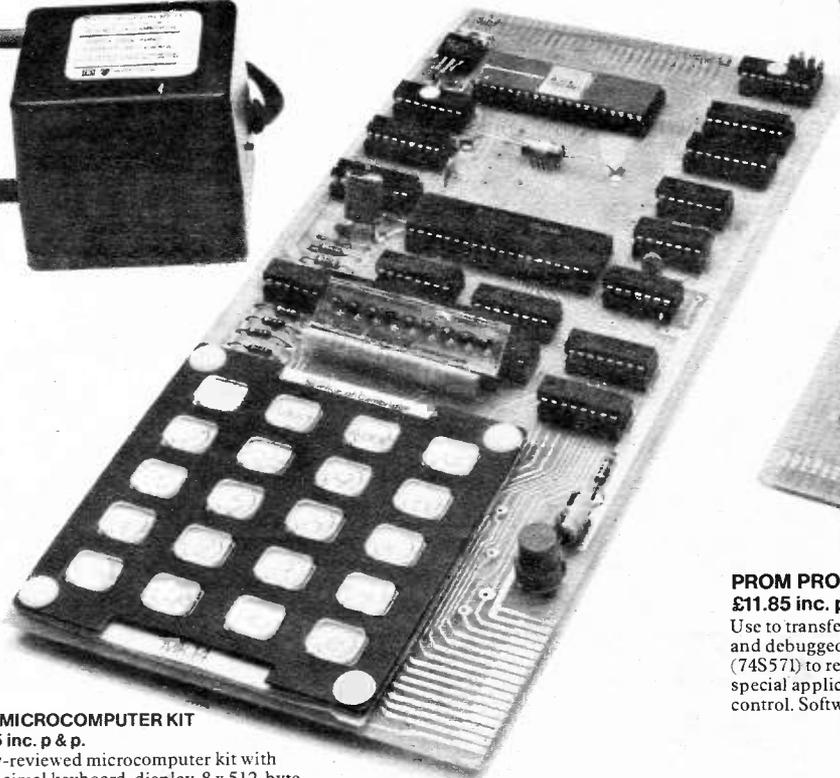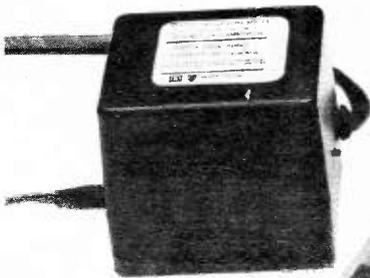Delivers 8 V at 600 mA from 220/240 V mains – sufficient to drive all modules shown here simultaneously. Sealed plastic case, BS-approved.



MK 14 MICROCOMPUTER KIT

£46.55 inc. p & p.


Widely-reviewed microcomputer kit with hexadecimal keyboard, display, 8 x 512-byte PROM, 256-byte RAM, and optional 16-lines I/O plus further 128 bytes of RAM.

Supplied with free manual to cover operations of all types – from games to basic maths to electronics design. Manual contains programs plus instructions for creating valuable personal programs. Also a superb education and training aid – an ideal introduction to computer technology.

Designed for fast, easy assembly; supplied with step-by-step instructions.

PROM PROGRAMMER. £11.85 inc. p & p.

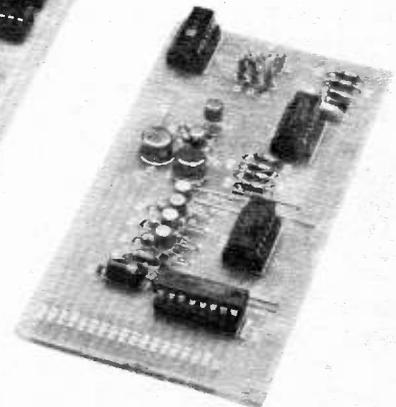Use to transfer your own program developed and debugged on the MK 14 RAM to PROM (74S571) to replace SCI0S monitor for special applications, e.g. model railway control. Software allows editing and verifying.



To order, complete coupon and post to Science of Cambridge
Return as received within 14 days for full money refund if not completely satisfied.

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me:

- MK 14 standard kit @ £46.55.
- Extra RAM @ £4.14 per pair.
- RAM I/O device @ £8.97.
- VDU module including character generator @ £33.75.
- VDU module without character generator @ £26.85.

- Cassette interface module @ £7.25.
- PROM programmer @ £11.85.
- Power supply @ £6.10.
- Full technical details of the MK 14 System, with order form.

All prices include p+p and VAT.

I enclose cheque/MO/PO for £ _____ (total).


Name _____

Address (please print) _____

Science of Cambridge Ltd

6 Kings Parade, Cambridge, CAMBS., CB2 1SN.
Tel: 0223 311488.

EE/2/80

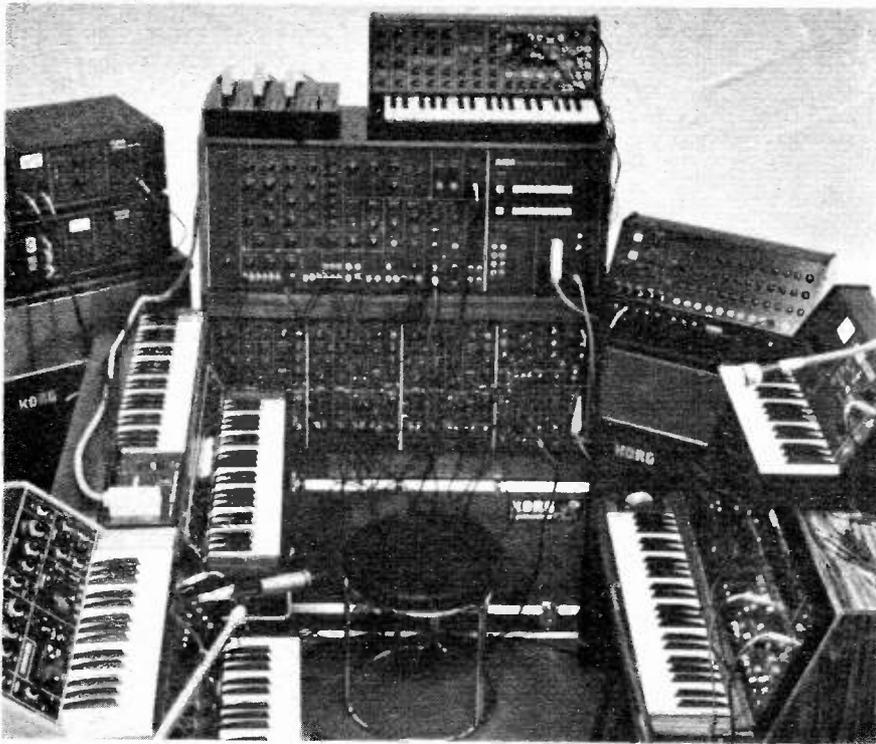

By B. H. Baily

Synthesizers

EXPLAINED

PART 3

THE circuits and functions described in the preceding articles form the basic heart of a synthesiser, and they are the blocks concerned mainly with the production of tone in conjunction with the keyboard switching. We shall now take a look at some other circuit blocks and discuss their uses and the way in which they function.

VOLTAGE CONTROLLED AMPLIFIER

The *Voltage Controlled Amplifier* (v.c.a.) is just what one would expect it to be. It is an amplifier, the degree of amplification of which is controlled by the value of a voltage applied on its voltage control line. The function of the voltage control is akin to the volume control in a conventional amplifier.

If the synthesiser output signal is applied to the v.c.a. input, the level of this signal at its output will depend on the voltage applied at the voltage control line input. Thus, if a varying voltage is applied to the voltage control input, the signal level at

the output will vary up and down in sympathy with the varying voltage control input.

An interesting use of v.c.a.s is to incorporate one in each channel of a stereo system, and connect them such that when the gain of one is increased by a varying voltage on its control input, the gain of the other is decreased simultaneously. The effect on the stereo signal is a *panning* or gradual changeover of sound positioning from one speaker to the other.

Another use of the v.c.a. is to produce an identical envelope for a second signal, from the envelope shaper handling the first signal. This can be done by controlling the voltage control line of the v.c.a. from the trapezoid output of the envelope shaper.

ENVELOPE FOLLOWER

Another circuit concerned with envelopes is the *Envelope Follower*. This has its primary use in conjunction with signals produced outside the synthesiser, the envelopes of which is required to be used inside the syn-

thesiser to control other signals. It operates by accepting an audio signal and producing a d.c. level, the voltage of which is proportional to the amplitude of the incoming signal.

Hence, when for example a guitar signal is fed into the envelope follower, the plucking of the string results in a high-amplitude signal at the envelope follower circuit input, and produces a high-level output, say, for example, 6 volts. As the signal from the guitar string decays, the output voltage of 6 volts drops in unison, so that the output traces the shape of the envelope of the guitar signal, see Fig. 3.1. This d.c. output can be applied to a v.c.a. to create an envelope for a signal in the synthesiser, or it can be used to control a voltage controlled filter, or of course, another voltage controlled circuit.

PHASING

The popular phasing circuit appears as a built-in facility on some synthesisers. The effect itself is familiar to all who listen to modern music of the pop variety, and is easily recognised

Three great miniature power drills with a complete range of accessories

P1
£9.95
pp 40p



P2
£17.55
pp 92p



P3
universal
chuck
£17.55
pp 92p



JIGSAW
attachment
for P2 drill
£11.50
pp 40p




TRANSFORMER
vari-speed
£14.00
pp 92p



For full details write to;


DRILLS

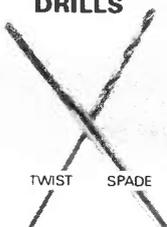

TWIST SPADE

GRINDING STONES

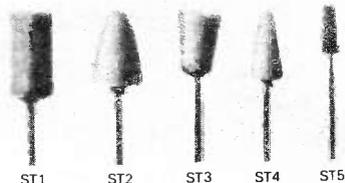
Fine Grade for Metal, Wood, Plastic, Glass



ST1 ST2 ST3 ST4 ST5

GRINDING WHEELS

22mm Dia You need Arbor A1

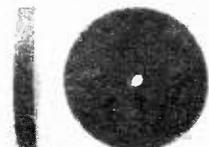


G1 Coarse G2 Medium G3 Fine

SAW BLADES for Wood, Plastic

SB1 2mm SB2 19mm SB3 16mm SB4 12mm


BURRS

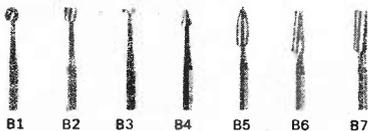For Milling and Grouting. No arbor needed.



B1 B2 B3 B4 B5 B6 B7

WIRE BRUSHES

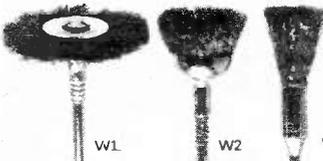


W1 W2 W3

CARBORUNDUM DISC C1 22mm WHEEL C2



POLISHERS

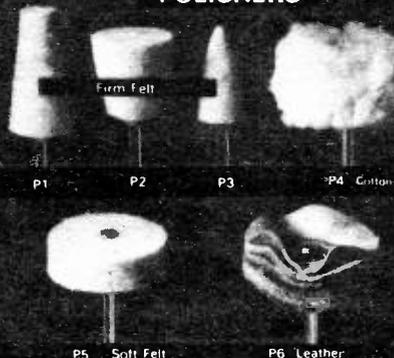

P1 P2 P3 P4 Cotton
P5 Soft Felt P6 Leather


CARBORUNDUM CYLINDER

C3 Also in Rubber B3
Arbor A3 needed

ORDER FORM

DRILLS 40p each	
SIZE	TWIST SPADE
0.1mm	SD1
0.2mm	SD2
0.3mm	TD3 SD3
0.4mm	TD4 SD4
0.5mm	TD5 SD5
0.6mm	TD6 SD6
0.7mm	TD7 SD7
0.8mm	TD8 SD8
0.9mm	TD9 SD9
1.0mm	TD10 SD10
1.1mm	TD11 SD11
1.2mm	TD12 SD12
1.3mm	TD13 SD13
1.4mm	TD14 SD14
1.5mm	TD15 SD15
1.6mm	TD16 SD16
1.7mm	TD17 SD17
1.8mm	TD18 SD18
1.9mm	TD19 SD19
2.0mm	TD20 SD20
2.1mm	TD21 SD21
2.2mm	TD22 SD22
2.3mm	TD23 SD23
2.4mm	TD24 SD24
2.5mm	TD25 SD25

ARBORS

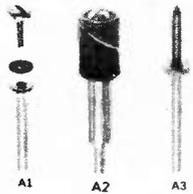

A1 for Saws, Wheels, Discs
A2 Expanding with Band
A3 for Cylinder

CHUCK


with 3 collets



H1

COLLETS

For P2 Drill

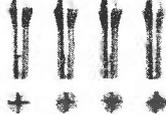

L1/2 L2/2 L3 2 L4 2

For P1 Drill
L1 1 L2 1 L3 1

To: PRECISION PETITE LTD.
119A HIGH ST., TEDDINGTON, MIDDX TW11 8HG.
Please send me the items I have circled.
Enclosed is cheque, postal order in payment.

All prices inc. VAT

ST1 ST2 ST3 ST4 ST5	40p each
G1 G2 G3	"
P1 P2 P3 P4 P5 P6	"
B1 B2 B3 B4 B5 B6 B7	"
TUNGSTEN BURRS	
TB1 TB2 TB3 TB6 TB7	£1.75 each
W1 W2 W3	40p each
A1 A3	"
A2 (expanding) 1/4" £1.07 3/8" £1.41	
C1 C2 C3	40p each
L1/2 L2/2 L3/2 L4/2 (for P2 drill)	53p each
L1/1 L2/1 L3/1 (for P1 drill)	53p each
H1 (chuck with 3 collets)	£3
SB1 SB2 SB3 SB4	75p each
SET OF SAW BLADES SB1/2/3/4 & Arbor	£3
FLEXIBLE DRIVE SHAFT	£4.95
JIG SAW ATTACHMENT	£11.50 pp 40p
EMERY BANDS	10 for 86p

P + P any quantity 25p unless otherwise stated

NAME

ADDRESS

If you do not want to cut your book - list items on separate sheet of paper.

EE



PRECISION PETITE LIMITED

119a HIGH STREET TEDDINGTON MIDDLESEX TW11 8HG TEL: 01-977 0878

by its "sky-riding" quality. This is accomplished by altering the phase of a signal, basically by slightly altering its timing, and mixing this altered signal with the original signal. Depending on how much the timing is affected, so certain frequencies will be affected such that the altered and unaltered signals cancel one another out, and a particular frequency will be conspicuous by its absence! But the change is made gradually, so that a whole spectrum of frequencies is affected, i.e. the sweep of cancelling covers the spectrum.

Various degrees of cancelling are passed through, and at certain points some frequencies are boosted by the effect. When this is done by a voltage controlled circuit, it becomes very versatile, and, as with the voltage controlled filter, can be controlled in a variety of ways, depending on what voltage control source is used to control it.

RING MODULATOR

One of the most novel in its effects, and most interesting in its function, is the circuit called the *Ring Modulator*. It is used for a variety of effects, one of which is well known as the Dalek voice of the well-known serial "Dr Who," and television advertisements depicting the voices of outer-space beings. It has also varied uses in the production of electronic music and sound effects.

The circuit normally functions with two different frequency inputs by intermodulating the two signals such that neither is present at the output. Instead, the output comprises the sum of the input frequencies, and the difference of the two inputs see Fig. 3.2. In simple mathematical terms this may be expressed: $Output = (f_1 + f_2)$ and $(f_1 - f_2)$ where f_1 and f_2 are the two input frequencies.

The Dalek voice is produced by applying a low-frequency signal to one of the inputs, and applying a normal voice signal from a microphone to the other input. Thus, when normal speech is applied via the microphone, a modulated complex signal is produced at the output, with the characteristic Dalek-like quality.

OCTAVE LIFTING

An unusual and interesting use of the ring modulator is that of frequency-doubling, or octave-lifting. If a single signal (it is better to use a sine wave for this) is applied simultaneously to the two inputs, a signal of one octave higher is generated at the output.

Looking back to the simple equation above, it can be seen why this is so. Because the two inputs are in fact the same signal, then f_1 must equal f_2 . So $(f_1 - f_2)$ must cancel out,

so will not be present at the output, and $(f_1 + f_2)$ must equal $2 \times f_1$, which in words is twice f_1 . Twice a frequency is in music one octave higher!

Unfortunately, the ring modulator is fussy about the shape of waveforms it will frequency-double, and really only works properly in this particular function with pure sine-wave input. However, its other functions are not limited to sinewaves, and some very interesting effects are created by using a wide range of waveshapes as inputs.

The two signals f_1 and f_2 are applied at the respective inputs, see Fig. 3.2. Notice the form which the output takes. It comprises a higher frequency, $(f_1 + f_2)$, which is "modulated" by the lower frequency $(f_1 - f_2)$. Apart from these two component frequencies the output contains no other components.

In practice, a very small amount of the two input frequencies sometimes breaks through into the output, but where this occurs the breakthrough is very small indeed and does not impair the main function of the circuit.

Although the ring modulator can be used in various ways in a synthesiser, a favourite way is to use it to modulate together the outputs of two voltage controlled oscillators, both of which take their scaling, or pitch control from the keyboard. In order

to bring the modulating function to the fore, the two oscillators are offset from one another to produce a harmonious chord, e.g. root and fifth, or, in easier terms, one is set to "doh" of the tonic solfa, and the other to "soh". The result, without going into the mathematics of the analysis, is a pleasant sound which, if given suitable attack and decay has a curiously pleasant bell-like quality to it.

PATCHING

We have thus far covered a fair number of modules in isolation. In practical synthesisers there must be a way of arranging for the various circuits required at any one time to be brought into use. Some synthesisers use rotary switches to select their various functions, but this system can only be used to a limited degree. Where greater versatility is required a system of "patching" is used, and this can take more than one form.

One system may be likened to a manually operated telephone switchboard, where a large number of cords with plugs on their ends can be connected to a similarly large number of sockets. This system is very unwieldy and a system often used is one in which a matrix of sockets are laid out in rows and columns in a rectangular area.

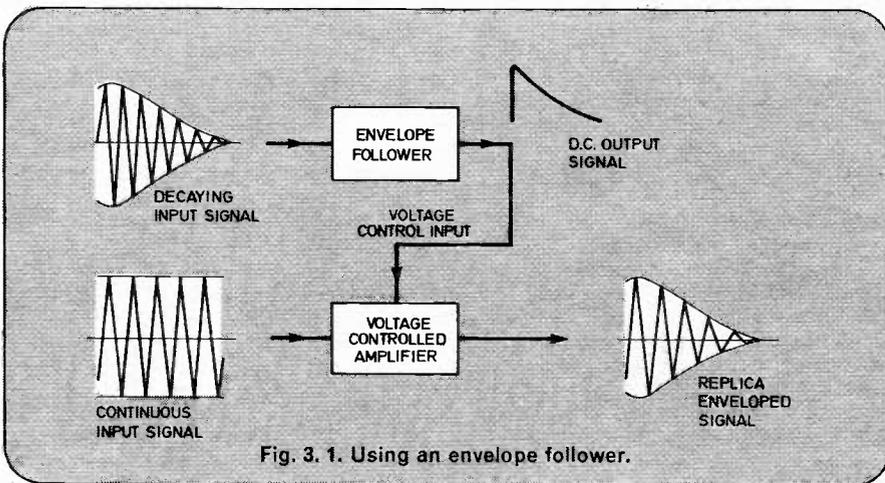


Fig. 3. 1. Using an envelope follower.

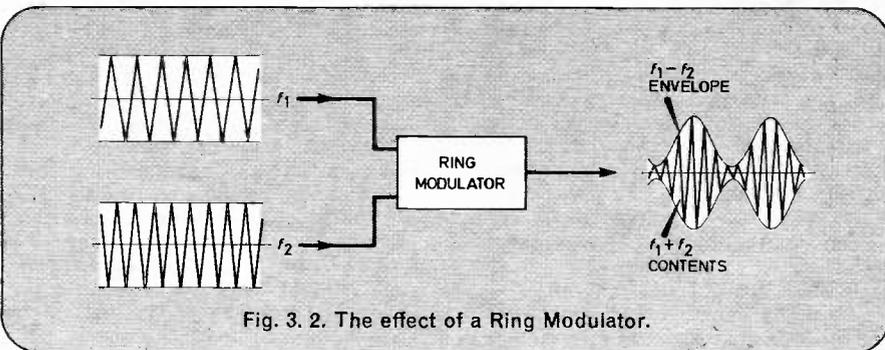


Fig. 3. 2. The effect of a Ring Modulator.

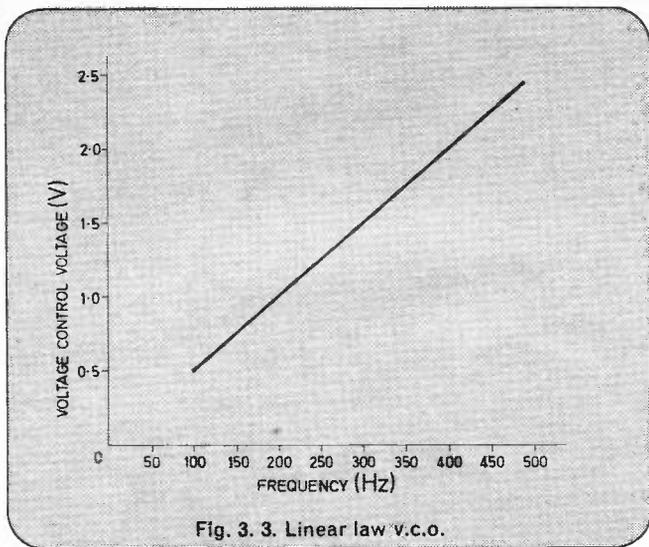


Fig. 3. 3. Linear law v.c.o.

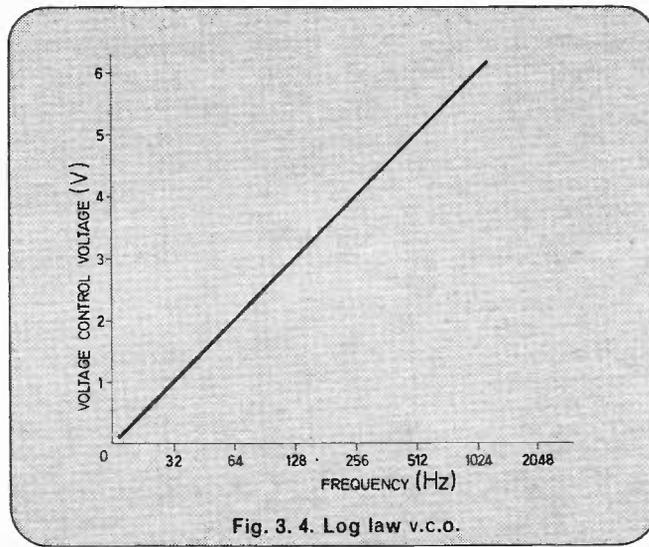


Fig. 3. 4. Log law v.c.o.

The horizontal rows are each labelled as outputs from the various circuits, and the vertical columns are labelled inputs to the same circuits. When it is required to connect the output of a particular circuit to the input of another, a plug is placed in the socket which is located at the intersection of the two circuits concerned, and electrical continuity is made via the inserted plug.

By placing a number of plugs in the correct sockets it is possible to route the v.c.o. output signals through, say, filter, phaser, envelope shaper and any other circuitry required for a given set of effects. In a similar way, the voltage control routing can be patched to give the required results.

LOG-LAW AND ITS PURPOSE

Of all the circuits discussed in this series of articles, it will have become evident that the heart of any synthesiser is surely the circuit which produces the basic tone, that is the voltage controlled oscillator. As such, it is felt that it deserves perhaps a deeper treatment than the other circuits, and indeed its actual circuitry and design is certainly very special.

A simple v.c.o. can be produced fairly easily, and there are various integrated circuits ("chips") which can be obtained which form a complete oscillator in a single package these days. However, a simple v.c.o. is not suited to synthesiser use as its electrical characteristics have to be rather special to make it really versatile in this application.

In a simple v.c.o. the frequency produced at the output is directly proportional to the voltage applied at its voltage control input, as was stated earlier. This means that if we want to double the output frequency (i.e. raise it by one octave) we must double the voltage control voltage. When this is applied practically, it is

found that to raise the frequency by steps of one note at a time, the voltage change per step varies over the range of the keyboard.

CHANGING THE LAW

In some synthesisers this is not found to be too important, but in most designs steps are taken to remedy the situation, and change the "law" of the oscillator voltage control so that each successive note requires the same change in voltage to attain a one note interval. This, in turn, means that the resistance ladder for the keyboard voltage selection can be built up of a series of equal-value resistors.

One small advantage of this is that vibrato can be applied to the voltage control lines of the v.c.o.s and the same variation in musical pitch will result, no matter what note is being produced.

The change in law of each oscillator used is produced by a special circuit, nowadays forming part of the v.c.o. circuitry. The circuit changes the linear voltage-to-frequency law to what is termed a *log-law*.

Instead of having to double the input voltage to raise frequency one octave, log-law makes the circuit require a constant change in voltage to raise frequency one octave. For instance, a linear law circuit would require say one volt change to raise its frequency by one hundred cycles, whereas in a log-law circuit the change of one volt would give a frequency change of one octave. Some circuits may be 0.5V.

The two laws are shown in graphical form in Fig. 3.3 and 3.4. Note that both lines in the graphs are straight, but that the frequency axis of the second graph has been altered from a linear representation to a log representation, i.e. it is shown in terms of octave points.

Had the linear form of frequency

been repeated in Fig. 3.4 the graph would have become very cumbersome, as can be seen by comparison with that in Fig. 3.3. Had linear representation been possible, then the graph trace would have appeared curved.

CONCLUSION

In this short series of articles the basic principles of electronic organs and monophonic synthesisers have been described. As previously stated, there are now obtainable polyphonic synthesisers, and these use principles used in both the simple synthesisers described, and also organ techniques.

The way developments are going today, we have many surprises to come in the field of electronic sound synthesis. If the last decade's progress is to be maintained, let alone overtaken, some of those surprises are likely to be almost unimaginable at present, like the phaser effect was some years ago.

Already, light and music are being combined in discos. Could smell be the next sensation to be exploited? The mind fairly boggles!

Crossword No. 24—Solution

1	C	2	N	S	O	3	L	E	4	J	5	O	I	N	T	6	S												
A	E												U				U												
S	O												T				R												
7	S	E	N	8	D	O	F	9	F				C		10	S	R	G											
E										11	E	R	X	T	H			E											
12	T	H	E	R	M	A	R	L					L	Y				D											
																			N										
13	E	D	14	D	Y					15	C	L	I	C	K	16	S	T	O	17	P								
																						O							
18	S									19	D	A				20	R	E	F	U	S	A	L						
T										21	F	I	E	L	D								A						
22	R	O	T													23		24	U	N	25	E	R						
A																							I						
N																							T						
26	I	S	H	E	S																		27	E	V	E	N	T	Y

SEIKO MEMORY BANK

Calendar watch M354
Hours, mins., secs.
Month, day, date in
12 or 24 hour format
all indicated continuously.
Monthly calendar display
month, year and all dates
for any selected month over
80 year period.
Memory bank function.
Any desired dates up to 11
can be stored in advanced.
2 year battery life.
Water resistant.
Metac Price



£79.50

M11

SEIKO Alarm Chronograph

With WEEKLY Alarm.
Hours, mins, secs, month,
date, day, am/pm.
Weekly alarm - can be set
for every day at designated
time e.g. 6.30 am on Mon,
Wed and Friday.
Alarm set time displayed
above time of day.
Full stopwatch functions,
laptime, split etc.



£89.95

M10

SEIKO Melody Alarm Chronograph

Chiming Alarm,
plus chrono.
Hours, mins, secs, date,
day, 24 hour alarm, 12
hour chronograph, 1/10th
secs, Laptime, Back light,
Stainless steel, mineral
glass.



METAC PRICE

£92.95

M19

SEIKO Calculator Watch

Full specification
calculator with
memory, plus multi
function watch.
Hours, mins, secs,
day, date, backlight,
Automatic calendar.
Long life battery.



£99.95

M27

CASIO CHRONO 95QS-3LB

Stainless steel case,
water resistant to 66 feet.
Hours, mins, secs, am/pm,
year, month, date, day.
Auto-calendar
pre-programmed
until the year 2029.
12/24 hour: Stopwatch
function.
Range 7 hours. 1/100 sec.
(Mode) Net time/lap-time/
1st-2nd place times.
Dual time function.
Accuracy 15 secs per month.
Battery life approx 4 years.



£22.95

M22

CASIO LADIES 86CL-23B-1

Elegant slim line.
Stainless steel bracelet,
fully adjustable.
Hour, mins, 10 sec symbol
second by flash, am/pm.
Month, date, day.
Auto-calendar preprogrammed
for 28th day in Feb.
Accuracy per month 15 secs.
Battery life approx 15 months.



£29.95

M23

CASIO F-200 Sports Chrono

Attractive Mans watch
in black resin with
mineral glass.
Hours, mins, secs, am/pm.
Month, date,
alpha-numeric day.
Auto-calendar set
28th Feb.
Stopwatch working
range 1 hour,
units 1/100 sec. Mode.
Net Time/lap/time/
1st-2nd place times.
Accuracy approx 15 secs
per month.
Battery 12 months.



£14.95

M24

CASIO ALARM CHRONO 81CS-36B

Hours, mins, secs, day,
and also day, month and year
perpetual automatic calendar.
100th sec chronograph to
7 hours.
Net time/lap/time/1st
and 2nd place times. User
optional 12/24 hr display. 24
Alarm. User optional,
hourly chime.
Backlight, mineral glass,
stainless steel.
Water resistant to
100ft.
Battery life approx 4 years.



£34.95

M25

BELTIME Chronograph

(9-Functions)
Hours, mins, secs,
day, date, month,
interchange feature,
automatic calendar,
backlight, Net
time/lap/time.
Stainless steel bracelet.
Battery life 1 year.



£14.95

M34

BELTIME Multi Alarm

29 Functions
Hours, mins, secs,
date, day.
Alarm, chronograph,
Light.
Watch 8 functions,
Alarm 4 functions,
chronograph 17
functions.
Stainless steel
bracelet.



£29.95

M35

CASIO F-8C 3 Year Battery life.

Hours, mins, secs,
am/pm, date, day.
Auto calendar set
28th Feb.
Stopwatch function.
Accuracy 15 secs per
month. Battery life
approx 3 years.



£9.95

M36

CASIO CALENDAR 200

47CS-23B-1 Black.
Stainless steel.
Hours, mins, 10 second
symbol, second (by flash),
am/pm, Month, day, date.
Auto-calendar set from
1901 to 2009.
Full month calendar display,
Dual time function.
Accuracy 10 secs per
month. Battery life
approx 15 months.



£59.95 M37

MELODY Multi Alarm Chronograph

Hours, mins, secs,
Day, Date, Count-
down alarm,
Dual time zone,
1/100th sec
stopwatch.
Lap/split time,
1st and 2nd place
times, Melody test
function.



£26.95

M30

DUAL TIME-ALARM CHRONOGRAPH

Incorporating module
of world famous
Japanese watch
manufacture.
Hours, mins, secs,
days of week, month,
day and date,
24 hour alarm,
12 hour chronograph,
1/10th secs,
lap time, Back light,
stainless steel case
and bracelet,
Mineral glass,
Battery hatch,
long life battery.



£35.00

M12

PICOQUARTZ Microprocessor Alarm Chronograph

Multilanguage-day of
the week can be set
to English, French,
German, Italian or
Spanish.
Chime - every full
hour combined with a
response signal,
beeping at every
pressing of the
functions.
Can be switched off.
12-24 hour format.
Backlight.
Chrono - 1, full scale
chrono with lap,
counting hours up to
24 hrs. Mins, secs,
1/100th secs.
Two Alarm systems.
Two time zones.



£37.95

M32

SEIKO CHRONOGRAPH

Hours, mins, secs
and day of the week.
Month date and
day of the week.
Stopwatch display -
Hours, mins, secs
up to 12 hours
(mins, secs, 1/100 secs
up to 20 minutes).
Lap timing.
Continuous time
measurement of two
competitors.
Stainless steel,
mineral glass.



£56.00

M33

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

**QUARTZ LCD
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch. Very slim, only 6mm thick.



M1

**SOLAR QUARTZ
LCD 5 Function**

Genuine solar panel with battery back-up. Hours, mins., secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

**QUARTZ LCD
11 Function** SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins., Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold! Guaranteed same day despatch.



M3

**QUARTZ LCD
ALARM 7 Function**

Hours, mins., secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

**MULTI ALARM
6 Digits 10
Functions**

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

£18.65



M5

**FRONT-BUTTON
Alarm Chrono
Dual Time**

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet. Guaranteed same day despatch



£22.65
M6

**SOLAR QUARTZ LCD
Chronograph with
Alarm
Dual Time Zone
Facility**

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec., steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.



£27.95
M7

**ALARM CHRONO
with 9 world
time zones**

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

£29.65



M8

**SOLAR QUARTZ LCD
Chronograph**

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£13.65

Guaranteed same day despatch.



M9

**QUARTZ LCD
Ladies Day Watch**

Only 25 x 20mm and 6mm thick. Hours, minutes, seconds, day, date, backlight and auto calendar. Elegant metal bracelet in silver or gold fully adjustable to suit very slim wrists. State colour preference.

£9.95

Guaranteed same day despatch.



M15

**QUARTZ LCD
Ladies Fashion Watch**

Elegant bracelet in bronze/gold finish or silver colour. Hours, mins, secs, day, date, backlight and auto calendar. Adjustable for the slimmest of wrists. State colour preference.

£14.95

Guaranteed same day despatch



M17

**QUARTZ LCD
Ladies Cocktail Watch**

Highly functional watch which also suits those special occasions. Beautifully designed with a very thin bracelet which retains strength as well as elegance. Hours, mins, secs, day, date, backlight and autocalendar. Bracelet fully adjustable to suit slim wrists. State gold or silver finish.

£19.95

Guaranteed same day despatch



M18

**HANIMEX
Electronic
LED Alarm Clock**



Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 111mm x 60mm) Weight: 1.43 lbs (0.65 kg). AC power 220V.

£10.20 Thousands sold!

Mains operated.

Guaranteed same day despatch.

M13

**EXECUTIVE ALARM
WATCH**

6 Functions plus Alarm: Conference signal, 5 minute snooze alarm. Conference signal sounds 4 secs., before main alarm to give advance warning and an option to cancel. Snooze sounds 5 mins., after main alarm and is always preceded by the conference signal.

£14.95

M60



**MACY QUARTZ
ANALOGUE**

Automatic Calendar Day and Date infinite bracelet. This mans watch has elegance as well as the robust appearance provided by a watch with traditional features. Accuracy is provided by a quartz crystal powered by a long life miniature battery.

£24.95

M21



Metac price breakthrough for an Alarm Chronograph with Dual Time only

£18.95



OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- **CALENDAR FUNCTIONS** include the date and day in each time zone.
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
- On command, stopwatch display freezes to show **intermediate (split/lap) time** while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch. **M16**

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and order details clearly, enclose 40 pence per single item for post and packing or the amount stated in the advert. All products carry 1 year written guarantee and full money-back 10 day reassurance. Battery fitting and electronic calibration service is available to customers at any Metac shop. All prices include VAT currently at 15%.

Metac Wholesale:

Trade enquiries - send for a complete list of prices for all the goods advertised plus many more not shown also minimum order details. Telephone orders: Credit card customers can telephone orders direct to Daventry (03272) 76545 or Edgware Rd. 01-723 4753 24 hours a day.



Service Enquiries 03272-77659
CALLERS WELCOME Shops open 9-30am-6.00


Metac

**ELECTRONICS
& TIME CENTRES**

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

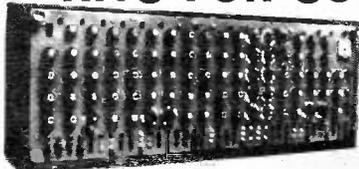KITS FOR SOUND EFFECTS AND OTHER PROJECTS



P.E. GUITAR EFFECTS PEDAL

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls. Basic parts with foot switches KIT 42-1 £8.45
Basic parts with panel switches KIT 42-2 £5.55
PCB & layout chart PCB 42A £1.57
Text photocopy .28

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit including variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Can be used with other electronic instruments. Set of basic components KIT 56-1 £7.57
PCB & layout chart PCB 56A £1.78
Text photocopy .68

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit. Set of basic components, PCB & chart KIT 74-1 £4.97
Text photocopy .39

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration. Basic comps, foot switches, PCB & chart KIT 75-1 £5.64
Basic comps, panel switches, PCB & chart KIT 75-2 £4.08
Text photocopy .38

P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control. Set of basic components, PCB & chart KIT 51-1 £3.99

P.E. AUTO-WAH UNIT

Automatically Wah or Swell sounds with each note played. Basic comps, panel switches, PCB & chart KIT 58-2 £5.31
Text photocopy .58

P.E. THREE-CHANNEL SOUND-TO-LIGHT

A simple sound-to-light controller. Set of basic components, PCB & chart KIT 52-1 £14.16
Text photocopy .24

COMPONENT SETS incl all necessary res, caps, s/cs, pots, t/formers. Hardware such as cases, skts, knobs, kbds, etc, are not incl, but most can be bought separately. Fuller details in lists.

ADD: POST & HANDLING
U.K. orders; under £5 add 25p, under £20 add 50p, over £20 add 75p. Recommended insurances against postal mishaps: add

50p for cover up to £50, £1 for £100 cover, etc., pro-rata, must be added to credit card orders. N.B. Eire, C.L., B.F.P.O. and other countries are subject to higher rates.

ADD 15% VAT
(or current rate if changed). Must be added to full total of goods, post & handling on all U.K. orders. Does not apply to exports.

LIST: Send stamped addressed envelope

with all U.K. requests for free list giving fuller details of our goods. Europe send 25p, other countries send 50p, or equivalent in international reply coupons

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT
(TEL: 01-302 6184)



PHONOSONICS

DEPT EE9D, 22 HIGH STREET,
SIDCUP, KENT DA14 6EH

MAIL ORDER SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND COMPONENTS TO
A WORLD-WIDE MARKET.

P.E. PHASER

An automatic 6-stage phasing unit with integral oscillator. Set of basic comps, PCB & chart KIT 88-1 £10.14
Text photocopy .68

ELEKOR PHASING & VIBRATO UNIT

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage. Set of basic components KIT 70-1 £19.11
PCB & layout chart KIT 70A £2.56
Text photocopy .67

P.E. PHASING UNIT

A simple but effective manually controlled phasing unit. Set of basic comps PCB & chart KIT 25-1 £3.52
Text photocopy .28

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses. Set of basic components, PCB & chart KIT 89-1 £3.82
Text photocopy .78

P.E. SMOOTH FUZZ

Set of basic components, PCB & chart KIT 91-1 £5.01

TREMOLO UNIT

A slightly modified version of the simple P.E. unit. Set of basic components, PCB & chart KIT 54-1 £3.23

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit. Set of basic components, PCB & chart KIT 28-1 £4.68
Text photocopy .28

P.E. MICROPHONE PRE-AMP

Includes preset gain-control to match most microphones, bass roll-off, treble lift, master gain control. Set of basic components, PCB & chart KIT 61-1 £4.20

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments. Set of basic comps, PCB & chart KIT 46-1 £16.42
Power Supply comps, PCB & chart KIT 46-2 £6.90
Text photocopy .97

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of KIT 46 is not required. Basic comps, PCB & chart, but excl sw. KIT 69-1 £8.19
Text photocopy .58

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels. Set of basic components, PCB & chart KIT 62-1 £5.03

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 5-digit counter for 1Hz to 99KHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking. Set of basic components KIT 79-1 £26.45
PCB (as published) PCB 79A £3.33
Text photocopy .78

TAPE NOISE LIMITER

Effectively reduces tape-recording hiss. Set of basic components, PCB & chart KIT 6-3 £4.13
Power Supply comps, PCB & chart KIT 6-2 £5.15
Text photocopy .19

P.E. DISCOSTROBE

4-channel sound-to-light controller also giving sequential, random or strobe modes of control. Set of basic components KIT 57-1 £20.00
PCB & layout chart PCB 57A £3.79
Text photocopy .78

MANY MORE KITS


for synthesizers, Rhythm Generators, Electronic Pianos and other projects, big, small, simple or complex, are available, plus a range of keyboards, separate components and accessories. Details in our lists.

Electronics

Make a job~or hobby~of it.....

The opportunities in electronics, today, and for the future are limitless - throughout the world - jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics - especially for the servicing of radio, T.V. and all associated equipment - can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on the world market.

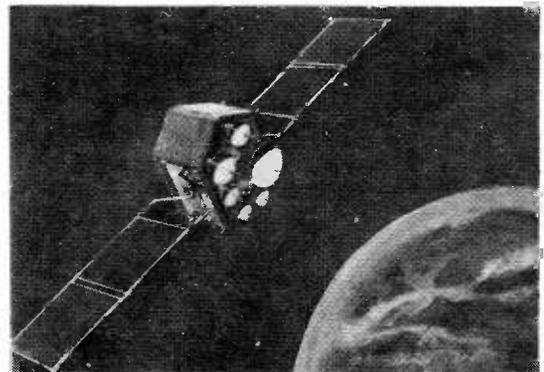We give modern training courses in all fields of electronics - practical D.I.Y. courses - courses for City and Guild exams, the Radio Amateur Licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years of experience in the subject. - Details sent without any obligation from . . .



Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

EEB/2/80 Block caps please

Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.



ELECTRONICS



Build your own oscilloscope.

Learn to draw and understand circuits.

Carry out over 40 experiments.

DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.



COMPUTER TECHNOLOGY


Learn to operate and programme your own home computer.



FREE BROCHURES



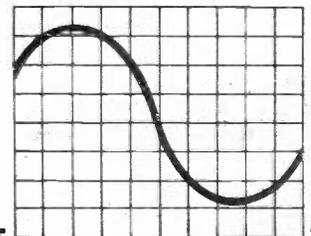No previous knowledge is necessary.
— Just clip the coupon for a brochure



TUTORCOURSE ELECTRONICS

Please rush me details of your
ELECTRONICS COURSE

Name _____

Address _____

Block Caps. Please


Post now, without obligation to:

**British National Radio
& Electronics School.**

P.O. Box 156, Jersey, Channel Isles

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full waverectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume. Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 $\frac{1}{2}$ " deep. AC 200/250V. PRICE \pounds 18.40, P. & P. \pounds 1.35.

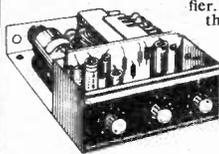

HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 30 watts music power. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200-240 volts. Size approx. 12 $\frac{1}{2}$ in wide \times 5in high \times 7 $\frac{1}{2}$ in deep. Special introductory price \pounds 29.00 + \pounds 2.75 carriage and packing.



"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 $\frac{1}{2}$ " \times 14 $\frac{1}{2}$ " \times 1 $\frac{1}{2}$ " deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only \pounds 8.80 each + p. & p. (one \pounds 1.00, two \pounds 1.25). Now available in 3" round version. 10 watts RMS 60Hz-20KHz \pounds 6.30. P. & P. (one 72p, two 82p).

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 $\frac{1}{2}$ " \times 2 $\frac{1}{2}$ " \times $\frac{1}{8}$ " H. \pounds 3.20 + 22p P. & P.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State FM/AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz.

Built-in Ferrite rod aerial or M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 $\frac{1}{2}$ "w \times 4" h \times 9 $\frac{1}{2}$ "d approx.

LIMITED NUMBER ONLY at \pounds 29.00 + \pounds 1.65 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished mono-aural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet. 50p + SAE (Free with parts). All parts sold separately. ONLY \pounds 18.40, P. & P. \pounds 1.55. Also available ready built and tested \pounds 22.50, P. & P. \pounds 1.55.

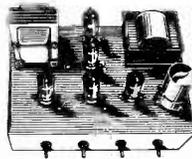

STEREO DECODER MK.II

SIZE 1 $\frac{1}{2}$ " \times 2 $\frac{1}{2}$ " \times $\frac{1}{2}$ " ready built. Pre-aligned and tested for 10-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions supplied. \pounds 7.00 plus 22p. P. & P. Stereo beacon light if required 40p extra.

Mullard LP1159 RF-IF module 470KHz \pounds 2.50 + P. & P. 22p. Full specification and connection details supplied.

Pye VH FFM Tuner Head covering 88-108MHz, 10.7-MHz I.F. output. 7-8V + earth. Supplied pre-aligned, with full circuit diagram with precision geared F.M. gang and 323PF + 323PF A.M. Tuning gang only \pounds 3.40 + P. & P. 40p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price \pounds 2.30 yd. length. P. & P. 55p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000Hz Sensitivity: better than 80mV into 1M Ω ; Full power bandwidth: \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35V, at 1.0 amp. Overall Size 12" w. \times 8" d. \times 2 $\frac{1}{2}$ " h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT \pounds 14.95 P. & P. 88p

(Magnetic input components 33p extra)

POWER PACK KIT \pounds 6.20 P. & P. \pounds 1.05

CABINET \pounds 6.20 P. & P. \pounds 1.05

SPECIAL OFFER—only \pounds 25.80 if all 3 items

ordered at one time plus \pounds 1.40 p. & p.

Full after sales service

Also avail. ready built and tested \pounds 32.20, P. & P. \pounds 1.65.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 $\frac{1}{2}$ " \times 2 $\frac{1}{2}$ " \times 1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only \pounds 10.40 plus 55p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at \pounds 2.15 + 44p P. & P. if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

HARVERSON SURPLUS CO. LTD.

(Dept. E.E.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station. Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.



All you need for listening!

Every month

PRACTICAL HI-FI

Listen with the complete hi-fi magazine

ELECTRONIC BOOKS

Ref.	Title	Price
126	BOYS BOOK OF CRYSTAL SETS	25p
200	HAND BOOK OF PRACTICAL ELECTRONIC MUSICAL NOVELTIES	50p
202	HANDBOOK OF IC EQUIVALENTS AND SUBSTITUTES	100p
207	PRACTICAL ELECTRONIC SCIENCE PROJECTS	75p
208	PRACTICAL STEREO AND QUADROPHONY HANDBOOK	75p
218	BUILD YOUR OWN ELECTRONIC EXPERIMENTERS LABORATORY	85p
221	28 TESTED TRANSISTOR PROJECTS	85p
222	SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS	95p
224	50 CMOS IC PROJECTS	95p
225	A PRACTICAL INTRODUCTION TO DIGITAL ICs	95p
226	HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS	120p
227	BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS	125p
RCC	RESISTOR COLOUR CODE DISC CALCULATOR	20p
BP1	FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES	60p
BP7	RADIO AND ELECTRONIC COLOUR CODES AND DATA CHARTS	25p
BP14	SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES	110p
BP25	HOW TO BUILD YOUR OWN ELECTRONIC WATCHES AND QUARTZ CONTROLLED CLOCKS	85p
BP32	HOW TO BUILD YOUR METAL AND TREASURE LOCATORS	95p
BP43	HOW TO MAKE WALKIE-TALKIES	125p
BP48	ELECTRONIC PROJECTS FOR BEGINNERS	135p
BP56	ELECTRONIC SECURITY DEVICES	150p
BP57	HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE	150p
BP58	50 CIRCUITS USING 7400 SERIES ICs	135p
BP59	SECOND BOOK OF CMOS ICs PROJECTS	150p
BP61	BEGINNERS GUIDE TO DIGITAL TECHNIQUES	95p

Please add 20p p & p per book. No VAT on books. Send SAE for full list of Babani Books

DIL SOCKETS		ANTEX SOLDERING IRONS		VERO-BOARDS	
8 pin	10p	C-15W	380p	0.1 Copperclad	55p
14 pin	11p	CCN-15W	400p	3/32 x 5	48p
16 pin	12p	CX-17W	400p	3/32 x 5	62p
18 pin	24p	X25	400p	3/32 x 3/32	56p
		C-15W Kit	570p	3/32 x 17	222p
		Spare Bits	50p	V.O. Board for ICs	105p
		Stand	160p	No track cutting	55p
				Pkt. of 100 pins	100p
				Insertion Tool	100p
				S.F. Cutter	85p

IC INSERTION/EXTRACTION TOOL		TRANSISTORS		TTL/CMOS	
	50p	AC126/7	20p	4016	45p
		AC128	20p	7400	4017
		AC176	20p	CA3080E	72p
		AD149	70p	CA3089E	225p
		AD161/2	45p	CA3300	375p
		BC107/8	11p	CA3140E	50p
		BC109	12p	ICL8038	340p
		BC177/8	17p	LM309	7410
		BC178	18p	LM301A	36p
		BC182/3	11p	LM309K	135p
		AC184	11p	LM311	7416
		BC212/3	11p	LM324	70p
		BC214	12p	LM339	75p
		BC548	16p	LM348	95p
		BCY11/2	22p	LM377	175p
		BC131/2	50p	LM380	90p
		MPSA12	50p	LM381AN	150p
		TIP31A	50p	LM710	50p
		TIP32A	68p	LM741	20p
		TIP33A	90p	LM748	35p
		TIP41A	115p	LM3900	70p
		TIP42A	70p	LM3909	100p
		ZT1X08	12p	LM3911	130p
		2N2219A	22p	LM4136	120p
		2N2222A	20p	MC1310P	150p
		2N2369A	20p	MC1458	55p
		2N2646	50p	MC3340P	120p
		2N2926	25p	MC3350P	120p
		2N3053	8p	NE531	140p
		2N3055	48p	NE555	22p
		2N3442	140p	NE556	70p
		2N3773	30p	NE567	175p
		2N3819	25p	SN76003N	175p
		2N3702/2	12p	SN76013ND	120p
		2N4123	27p	SN76023ND	120p
		2N4401	21p	SN76033N	175p
		2N5191	85p	TBA641B11	225p
		2N5194	90p	TBA805	100p
		2N5245	40p	TB4310S	110p
		2N5401	50p	TCA940E	175p
		2N5457/8	40p	TDA1022	600p
		2N5459	40p	TL072	90p
		2N6107	130p	TL074	150p
		2N6254	130p	TL081	48p
		2N6247	130p	TL084	130p
		2N6290	65p	TL082	90p
		40673	75p	ZN414	100p
		40871/2	90p	ZN425E	400p
				ZN1034E	200p

OPTO-ELECTRONICS		MULTIMETERS	
Red LEDs	Displays	Pocket Multimeter	5-00
0.125"	13p	LT22 (20K/V)	12-00
0.2"	14p	Microtest 80R	16-00 P & P 0.75
Green	FND507 110p	Supertester 680R	33-50 P & P 1.00
0.125"	16p		
0.2"	20p		
Clips	3p		

EXPERIMENTOR BREADBOARDS		STABILISED POWER SUPPLY	
No soldering suitable for DIL ICs		400mA 3V 6V 7.5V 9V	5-10
EXP325 (1 IC up to 22 pin)	170p		
EXP 300 (up to 5 x 14 pin)	575p		
EXP600 (up to 1 x 40 pin)	630p		
EXP350 (up to 2 x 14 pin)	3-15		

PROTO BOARDS SOLDERLESS BOARDS		ULTRASONIC TRANSDUCERS	
Socket Strips/Bus Strips/Binding		Rx & Tx	3-45 pr.
Posts mounted on sturdy base plate			
PB 6 6 x 14 pin DIL ICs	9-20		
PB 100 10 x 14 pin DIL ICs	11-80		
PB 102 12 x 14 pin DIL ICs	22-95		
PB 103 24 x 14 pin DIL ICs	34-45		
PB 104 32 x 14 pin DIL ICs	45-95		
(The above boards are suitable for all DIL ICs)			

VAT Rate. Please add 15% to your total. (75p p & p for official orders)
 Please send SAE for full list.
 CALLERS WELCOME MON-FRI 9.30-5.30
 SAT 10.30-4.30

TECHNOMATIC LTD

17 BURNLEY ROAD, LONDON NW10
 (2 minutes from Dollis Hill Tube)
 Tel. 01-452 1500 Tlx. 922800



Wilmslow Audio

THE firm for speakers!

SEND 30P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER
 BOWERS & WILKINS ● CASTLE
 CELESTION ● CHARTWELL ● COLES
 DALESFORD ● DECCA ● EMI ● EAGLE
 ELAC ● FANE ● GAUSS ● GOODMAN
 I.M.F. ● ISOPHON ● JR ● JORDAN
 WATTS ● KEF ● LEAK ● LOWTHER
 MCKENZIE ● MONITOR AUDIO ● PEEERLESS
 RADFORD ● RAM ● RICHARD ALLAN
 SEAS ● SHACKMAN ● STAG ● TANGENT
 TANNOY ● VIDEOTONE ● WHARFEDALE
 YAMAHA

WILMSLOW AUDIO (Dept. EE)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street

Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

VHF FET's BF 956C @ 4 for 75p, E304 at 30p, 4 for £1.
 STRIPLINE TRANSISTORS NPN BF 362 @ 25p, PNP BF 679 @ 25p.
 STANDARD VHF TRANSISTORS AF 239, BFY 90, 2N 5179, 2N 5180. All at 50p.
 EDDYSTONE TRANSMITTING VARIABLES 30+30pf (60pf) @ £2.20.
 MINIATURE 12 WATT CERAMIC TAG STRIPS @ 15p.
 VHF WIRE ENDED R.F. CHOKES 3 U.H., 10 U.H., 22 U.H., 27 U.H., 60 U.H., 180 U.H., 600 U.H. All at 75p each.
 SPECIAL 5 PIN D & R LINGTON PAIRS in 14 PIN DIL Package HFE 5000, 10 volt, 500 mA with connections @ 50p.
 MIDGET 6 to 12 volt SINGLE POLE C.O. RELAY 5 amp contacts @ 60p.
 SPECIAL CAPACITORS 10uf 370 V.A.C. @ £1.50, 135 UF 290 V.A.C. @ £6.
 OP-AMPS MC 1498G @ 40p, 3 for £1.
 ON-OFF TOGGLE SWITCHES with Long Paddle Dolly @ 35p.
 TTL IC's 7400, 74100, 7430, 7453. All at 10p each, 6 for 50p.
 POLYESTER CAPACITORS 63v.w., 1uf @ 5p, 4-7uf @ 10p, 10uf @ 15p.
 THYRISTORS 10p AMP Type 100 PIV @ 28p, 400 PIV @ 55p, 800 PIV @ 65p.
 12 WATT PLASTIC BARRIER STRIPS 5 amp @ 30p, 4 for £1.
 50 OC 71 TRANSISTORS untested for 75p.
 50 BC 107-8-9 TRANSISTORS assorted untested @ 60p.
 WIRE ENDED DIODES IN 4001 @ 5p, 6 for 25p.
 TANTALUM BEAD CAPACITORS 6 8uf 35v.w., at 12 for 75p.
 SUB-MINIATURE AIRSPACED 10pf TRIMMERS @ 20p each.
 ELECTRET MICROPHONE WITH FET PRE-AMP @ £1.85.
 CLOSE TOLERANCE CAPACITORS 1288pf, 1670pf, 5979pf, 19669pf. All 1% at 5p each, 100,000pf 1% (1uf) at 12p each.
 SUB-MINIATURE LOUDSPEAKERS 1 1/2" Dia. 8 ohm @ 75p.
 400mW ZENERS unmarked Good 3-6v, 6-8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36 volt all at 10 for 40p.
 300 TO 75 ohm BALUN TRANSFORMERS at 20p each.
 COMMON ANODE 7 SEGMENT DISPLAY FND 507 with data @ 70p.
 0.2" LED's Red, Green or Yellow at 15p each.
 WIRE ENDED 70 VOLT NEONS at 10p each, 6 for 50p.
 SOLDER-IN FEED THRU's 6-8pf, 300pf, 1000pf. All 10p doz.
 VERNICRON FM 4 10-7 MHz FILTERS at 50p, 3 for £1.
 50 DISC CERAMICS assorted for 60p.
 VARIABLE CAPACITORS 5pf @ 75p, 10pf @ 75p, 50+50pf @ £1, 125+125pf @ 60p, 100+200pf @ 60p, 200+200+20+20pf @ 75p, 250+250+20+20+20pf @ 75p, 25+25+25pf @ 75p.
 DUAL GATE MOS FETS LIKE 40673 at 33p, 4 for £1.10.
 50 2 WATT ZENER DIODES assorted untested for 60p.
 10 AMP TOGGLE SWITCHES 2 Pole Make @ 50p.
 NEWMARKET TRANSISTORS NKT 274 @ 10p, 6 for 50p.
 DAU TRIMMERS 2 To 9pf, 7 To 35pf, 6 To 45pf, 8 To 125pf, 8 To 140pf, All at 15p each.
 ERIE RED CAP CERAMIC SUB-MINIATURE DISCS 0.1uf 100v.w., @ 5p.
 3/16" COIL FORMERS with core at 6 for 25p.
 200 ASSORTED 1/2, 1/4 watt RESISTORS for 75p.
 HOT CARRIER DIODES 5082-2800 at 40p each.
 OP-TO ISOLATORS IL-74 with data @ 50p each.
 VHF POWER TRANSISTOR RS174 13 volt 10 watt 175 MHz @ £2.50.
 COMPRESSION TRIMMERS 10pf, 30pf, 50pf, 100pf, 1000pf. All 10p each.
 2N 918 VHF TRANSISTORS @ 25p each.
 SUB-MINIATURE SINGLE POLE C.O. TOGGLE SWITCH @ 50p each.
 Please add 20p for post and packing on U.K. orders under £2. Overseas postage charged at cost.

J. BIRKETT

RADIO COMPONENT SUPPLIERS

25 The Strait, Lincoln LN2 1JF Tel. 20767

Amateur or Craftsman

■■■ You're at home with Practical Woodworking. It's *the* magazine for detailed how-to-do-it features on every aspect of working with wood. Exciting traditional and modern furniture designs, regular wood carving and turning projects...indoors or out, everything you need for greatest hobby enjoyment or home improvement.



PRACTICAL
WOOD WORKING
EVERY MONTH

KITS FOR E.E. PROJECTS

VARICAP RADIO (ZB 1)	Sept 79	£8-50
TRANSISTOR TESTER (ZB 2)	Sept 79	£5-00
LOW POWER AUDIO AMPLIFIER WITHOUT CASE (ZB 3)	Sept 79	£2-70
SEE LIST (ZB 33)		
WARBLING TIMER (ZB 5)	Aug 79	£5-80
POWER SUPPLY 9V (ZB 6)	Aug 79	£8-25
ELECTRONIC TUNING FORK (ZB 7)	Aug 79	£8-90
SWANEE WHISTLER (ZB 8)	Aug 79	£3-50
TRAILER FLASHER UNIT (ZB 9)	Aug 79	£3-00
TOUCH-ON PILOT LIGHT LESS CASE (ZB 10)	Aug 79	£1-70
SEE LIST (ZB 34)		
QUIZ REFERENCE (ZB 12)	Aug 79	£4-50
SOLDERING IRON BIT SAVER (ZB 13)	July 79	£7-00
CONFERENCE TIMER INCLUDES 1 EXT UNIT (ZB 14)	July 79	£38-00
VOLTAGE SPLITTER (ZB 15)	July 79	£3-25
SEE LIST (ZB 35)		
DARKROOM TIMER (ZB 17)	July 79	£2-50
TREMLO UNIT (ZB 18)	June 79	£10-00
ELECTRONIC CANARY (ZB 19)	June 79	£4-50
METAL LOCATOR (ZB 20)	June 79	£10-00
METER AMPLIFIER (ZB 21)	June 79	£3-50
QUAD SIMULATOR (ZB 22)	June 79	£6-00
INTRUDER ALARM (ZB 23)	May 79	£23-00
ELECTRONIC DICE (ZB 24)	May 79	£13-50
SHORT WAVE CONVERTER (ZB 25)	May 79	£13-75
SHAVEN INVERTER (ZB 26)	April 79	£12-00
TOUCH BLEEPER (ZB 27)	April 79	£3-25
CHOKE WARNING DEVICE (ZB 28)	April 79	£7-50
SEE LIST (ZB 36)		
POWER SUPPLY (ZB 30)	Feb 79	£27-60
SEE LIST (ZB 37)		
LIGHTS REMINDER FOR CAR (ZB 32)	Jan 79	£4-50

All above kits include parts as described in article, i.e. vero/board or p.c. board, i.c. sockets, connecting wire etc.

TEACH-IN '80

New to electronics, then start at the beginning. All electronic components for construction of Tutor Deck and Teach-in experiments during the first six parts of the series. Lists A and B £18-50.

ALL PRICES INCLUDE V.A.T.
BARCLAY/VISA/ACCESS CARDS ACCEPTED.
MINIMUM TELEPHONE ORDERS £5-00.

T. POWELL

306 ST. PAUL'S ROAD, LONDON N1

01-226-1489

SHOP HOURS: MON-FRI 9 a.m.-5.30 p.m., SATURDAY 9 a.m.-4.30 p.m.



FIRST and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation *second to none* for our catalogue—and for the service that backs it up. Experience both for yourself. Just send £1-30 with the coupon and a catalogue will come by return of post.

**START THE NEW YEAR WELL
with a Home Radio Catalogue**

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatabe offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.
Dept. EE., 234-240 London Road, Mitcham, Surrey CR4 3HD
Phone: 01-648 8422

POST THIS COUPON
with cheque or P.O. for £1-30

Please write your Name and Address in block capitals

NAME

ADDRESS





HOME RADIO (Components) LTD. Dept. EE (Regn. No)
234-240 London Road, Mitcham, Surrey CR4 3HD London 912956

Random Electronic EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box and descriptive instructions.

Complete or Kit

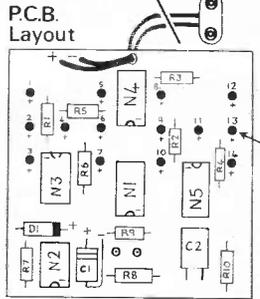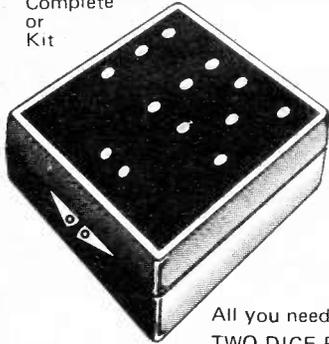


All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

- a *Self Assemble Dice £3.95 + P&P 25p
b *Ready built Dice £4.75 + P&P 25p

Order now from: **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk O473-210151

Amount enclosed £ _____
Name _____
Address _____

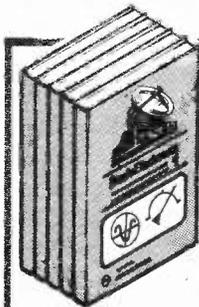please state amount required in appropriate box a b



ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.
Bound in stiff linen. Cover size 8 1/2 in x 5 in.
Price £8.00 per set (we pay the postage).

- Book 1. Introducing Electronics Book 4. Meters/Voltage-dividers
Book 2. Resistors/Capacitors Book 5. Transistor Project Circuitry
Book 3. Inductors/Diodes

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order now:
Selray Book Company
60 Hayes Hill
Bromley
BR2 7HP

OUR 100% GUARANTEE
Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £ _____
Name: _____
Address: _____

EE 18

CAMBRIDGE LEARNING ENTERPRISES

Self
Instruction
Courses

Unit 44, Rivermill Site,
St. Ives, Huntingdon, Cambs.

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC- the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation.

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

Understand Digital Electronics

Written for the student or enthusiast, this course is packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits and finally to an understanding of the design and operation of calculators and computers.



Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems.

Book 2 OR and AND functions; logic gates, NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and ALU's; multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; ROMS and RAMS.

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding.

Book 6 CPU; memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming, assemblers; computers; executive programs; operating systems.

GUARANTEE - No risk to you

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Please send me:-

....**Computer Programming in BASIC (4 books) @ £7.50**

....**Design of Digital Systems (6 books) @ £11.50**

All prices include worldwide surface mailing costs (airmail extra)
IF YOUR ORDER EXCEEDS £15, DEDUCT £2

I enclose a cheque/PO payable to Cambridge Learning Enterprises for £.....


or please charge my Access/Barclaycard account no.....

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers (inc Eire) send a bank draft in sterling drawn on a London bank, or quote credit card and number.

Name

Address

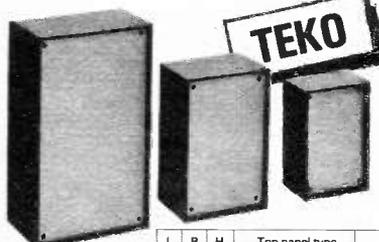Cambridge Learning Enterprises, Unit 44, Rivermill Site,
FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England.



TEKO

WH WEST HYDE

are the sole agents for **TEKO**



*Specify case colour when ordering Nuova: Black or Lobster Red.

L mm	B mm	H mm	Top panel type		TEKO		
			Alu.	Plastic	1 off	10	50
80	50	30	TEK P1A	TEK P1P	0.88	0.58	0.51
105	65	40	TEK P2A	TEK P2P	1.01	0.86	0.76
155	90	50	TEK P3A	TEK P3P	1.49	1.27	1.12
210	125	70	TEK P4A	TEK P4P	2.48	2.11	1.86

A wide range of small and miniature cases in A.B.S. suitable for anything from digital clocks to audio consoles. Low cost


L max mm	L mm	B mm	H mm	Order Code	NUOVA		
					1 off	10	50
86	73	118	46	TEK D12	1.59	1.35	1.19
149	132	135	50	TEK D13	1.91	1.62	1.43
155	135	180	55	TEK D14	2.71	2.30	2.03



W mm	H mm	Order Code	PESO		
			1 off	10	50
58	65	TEK P112	3.40	2.89	2.55
120	65	TEK P122	3.74	3.18	2.81
160	65	TEK P132	4.42	3.76	3.32
220	65	TEK P142	5.12	4.35	3.84
297	65	TEK P152	6.47	5.50	4.85
58	105	TEK P212	3.70	3.15	2.78
120	105	TEK P222	4.08	3.47	3.06
160	105	TEK P232	4.76	4.06	3.57
220	105	TEK P242	5.45	4.63	4.09
297	105	TEK P252	6.81	5.79	5.11

All cases depth 210 mm

with discounts for quantity. **NUOVA** have a transparent red front panel, suitable for L.E.D. displays. **PESO** are solid, substantial cases with either fixed or folding feet. **ARANCIO** have bright orange tops and tin-plated bases. **SCREENED BOXES** are tin-plated steel with loose screen divisions. The very popular **DESKO** and **TEKO** are very widely used in both production and amateur use. **ALBA** are cases with moulded grills top and bottom, for speakers or ventilation.

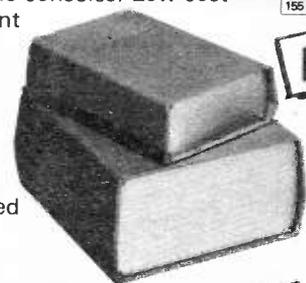

ALBA

B mm	H mm	Order Code*	ALBA		
			1 off	10	50
130	35	TEK K11	2.96	2.52	2.22
130	55	TEK K12	3.18	2.70	2.39
130	70	TEK K22	3.41	2.90	2.56
130	90	TEK K23	3.64	3.09	2.73
130	110	TEK K33	3.87	3.29	2.90
180	35	TEK A11	3.15	2.68	2.36
180	55	TEK A12	3.40	2.88	2.55
180	70	TEK A22	3.60	3.06	2.70
180	90	TEK A23	3.85	3.27	2.89
180	110	TEK A33	4.10	3.48	3.07

*Specify case colour when ordering: Grey, Black or Lobster Red. Cases type K are 173 mm long, type A are 158 mm long.

TRADE ENQUIRIES INVITED

ARANCIO

W mm	H mm	Order Code	ARANCIO		
			1 off	10	50
60	55	TEK CH1	1.09	0.93	0.82
122	55	TEK CH2	1.65	1.40	1.24
162	55	TEK CH3	1.93	1.64	1.45
222	55	TEK CH4	2.24	1.99	1.76
60	90	TEK BC1	1.65	1.40	1.24
120	90	TEK BC2	2.13	1.81	1.60
160	90	TEK BC3	2.46	2.09	1.85
200	90	TEK BC4	2.93	2.49	2.20

All cases depth 120 mm



DESKO

SCREENED

L mm	B mm	H mm	H max mm	Order Code	DESKO		
					1 off	10	50
161	95	60	40	TEK 362	1.65	1.40	1.24
215	130	75	45	TEK 363	2.48	2.11	1.86
311	169	90	50	TEK 364	5.21	4.43	3.91

The West Hyde Catalogue gives full details of these and seven other TEKO ranges—send for your free copy.

L mm	B mm	Order Code	SCREENED BOXES		
			1 off	10	50
53	50	TEK S371	0.86	0.73	0.65
81	50	TEK S372	1.17	0.99	0.88
105	50	TEK S373	1.73	1.47	1.30
160	50	TEK S374	2.04	1.73	1.53

All boxes height 26 mm

All West Hyde cases are available with substantial discounts for quantities. The TEKO ranges have price breaks at 10, 50, 100, 500, and 1,000 off. Prices include post and packing, but not VAT, and are correct at press date. 10% discount is given on the first two price breaks if cases are collected.

WEST HYDE DEVELOPMENTS LIMITED, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks. HP20 1ET. Phone: Aylesbury (0296) 20441. Telex 83570

<p>MEN'S FIVE FUNCTION QUARTZ LCD</p> <p>Hours, mins, secs, month, date, auto calendar. Quality metal bracelet.</p> <p>Same day despatch, £6.95 incl. VAT and P & P. 12 month guarantee.</p> <p>L1</p>	<p>LADY'S 7-FUNCTION ALARM</p> <p>Ladies' 7-function Alarm. Min., sec., hr. Day date, month, backlight.</p> <p>£14.95</p> <p>L2</p>	<p>LADY'S 5-FUNCTION WATCH</p> <p>Hours, mins., sec., day, month, date, backlight.</p> <p>12 month guarantee.</p> <p>£9.95 (inc. VAT, P&P)</p> <p>L3</p>	<p>LADY'S 5-FUNCTION WATCH</p> <p>Hours, mins, sec., day, month, date, backlight.</p> <p>Gold / Silver Colour finish.</p> <p>£12.95 (inc. VAT, P&P) Same day despatch. 12 month guarantee.</p> <p>L4</p>
<p>OTRON SOLAR LCD ALARM CHRONO</p> <p>★ WATER RESISTANT (no vents)</p> <p>★ MINERAL GLASS</p> <p>★ ALL STAINLESS STEEL</p> <p>★ ONLY 7mm THICK</p> <p>24-hr alarm with on/off indication, 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light.</p> <p>12 month guarantee.</p> <p>ONLY £33.95 (inc. VAT, P&P)</p> <p>Same day despatch</p> <p>L5</p>	<p>MEN'S LCD SNOOZE ALARM</p> <p>24-hr Alarm Hours, Mins., Secs., date, month, back-light, auto calendar. Adjustable stainless steel bracelet.</p> <p>12 month guarantee.</p> <p>ONLY £11.95 (inc. VAT, P&P)</p> <p>Same day despatch.</p> <p>L6</p>	<p>MEN'S ALARM CHRONO</p> <p>Hr., min., sec., day, date, 1/10 chronograph, lap time, alarm, 6 digits plus day, 12/24 hour option. Month date/date month option.</p> <p>12 month guarantee.</p> <p>£18.95 (inc. VAT, P&P) Same day despatch.</p> <p>L7</p>	<p>MEN'S 11-FUNCTION</p> <p>6 digit, 11 functions. Hours, mins, secs., day, date, day of week 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.</p> <p>12 month guarantee.</p> <p>£10.95 (inc. VAT, + P&P)</p> <p>L8</p>

LELECTRONICS LTD

12 Little Newport Street
London WC2 7JJ


TEL: 01-437-4910

Payment can be made by sending cheque or postal order. Write your name and address and order details clearly. All products carry one year guarantee and full money back 10-day reassurance. Battery fitting service is available at our shops. All goods are sent by first-class post.

Shop open 7 days per week, 12 noon to 8 p.m.

MONOLITH

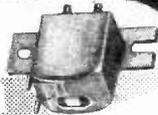QUALITY REEL TO REEL & CASSETTE TAPE HEADS + MECHANISMS



C2000

REMOTE OPERATION TAPE TRANSPORT MECHANISM FOR DIGITAL OR AUDIO.

THIS BRITISH MADE CASSETTE TRANSPORT HAS GIVEN INDUSTRY A GREAT COST SAVINGS OVER COMPARABLE FOREIGN IMPORTS AND IS NOW BEING MADE GENERALLY AVAILABLE.

CAN BE SUPPLIED WITH TAPE FAIL/END DETECTION, SEARCH, AND FAST ERASE. SOLENOID CONTROL PROVIDES FULLY REMOTE OPERATION.

WRITE NOW FOR FULL DETAILS
BASIC PRICE £60.30 INC. VAT.

POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01 Mono Playback.....	£1.89	C42RPH04 Stereo GLASS FERRITE R/P.....	£11.60
B12-02 Mono Record/Playback.....	£4.02	C42RPS18 Stereo TWIN GAP R+P.....	£25.21
B24-01 Stereo Playback.....	£3.30	E12-09 Mono/stereo erase.....	£ 1.85
B24-02 Stereo Record/Plbk.....	£5.66	B22-02 Twin 1/2 track R/P.....	£ 5.97
B24-07 Stereo R/P, (Dolby Stm).....	£7.87	C44RPH03 Quad 1/4 track R/P.....	£13.17
C42RPH20 Stereo SENDUST R/P.....	£9.28	C44RP2ESD1 Quad 1/4 track combined R/P + Erase.....	£26.45
C42RPIESD1 Stereo combined R/P + Erase.....	£10.93	C22ESD2 Twin half track erase.....	£ 4.72

SEND FOR OUR FULL CATALOGUE 25p.

MONOLITH
THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST. CREWKERNE, SOMERSET, ENGLAND. (0450) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER.
ALL PRICES INCLUDE VAT

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success; knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City and Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation and Contracting


POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept R268 Intertext House, London SW8 4UJ or telephone 622 9911

Subject of Interest
Name
Address
Tel: Age:

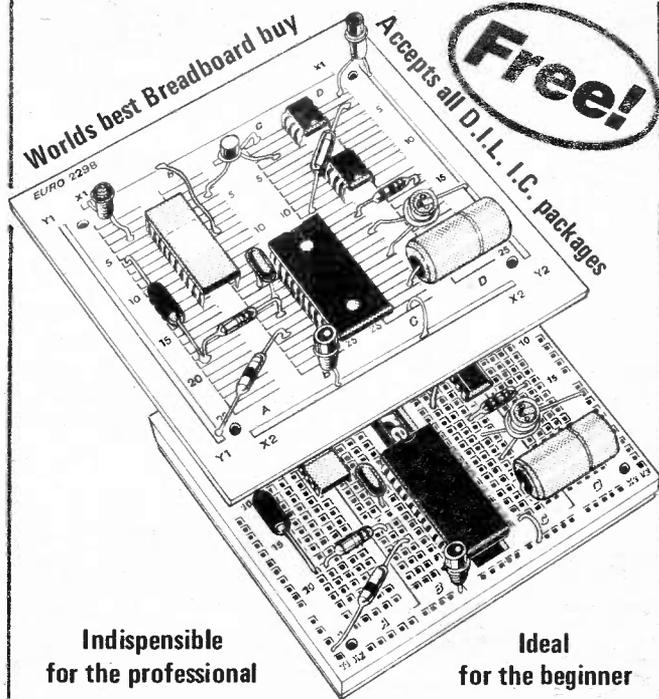First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (< 10m ohms) nickel silver contacts £6.20 each or £11.70 for 2 including 1 or 2 EuroSolderBoards FREE

Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's or FREE with every EuroBreadBoard)

And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.

Please send me:--

- 1 EuroBreadBoard (plus 1 free EuroSolderBoard) @ £ 6.20
- or 2 EuroBreadBoards (plus 2 free EuroSolderBoards) @ £11.70 Please
- or 3 EuroSolderBoards @ £ 2.00 Tick
- or 1 EuroSolderSucker @ £ 7.25

All prices are applicable from Jan. 1st 1980 and include VAT & PP but add 15% for overseas orders.

Name
Company
Address
Tel. No.


Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSM1

- * RCA 8A Triacs
- * 1000W per channel
- * Switched master control for sound operation from 1/2W to 125W
- * Speed control for fixed rate

sequence from 8 per minute to 50 per second

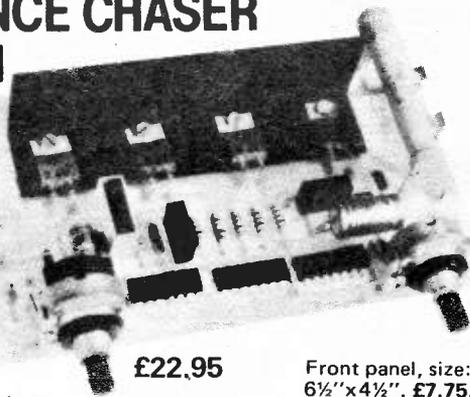- * Full logic integrated circuitry with optical isolation for amplifier protection.



£22.95

Front panel, size: 6 1/2" x 4 1/2", £7.75.




3 CHANNEL AUTO SOUND TO LIGHT - AFL 6

NEW

- * RCA 8 amp Triacs
- * 500W per channel
- * 2 channels flip flop, 1 channel sound to light
- * Fully automatic via built in mic
- * No connection to amp necessary.

£17.50

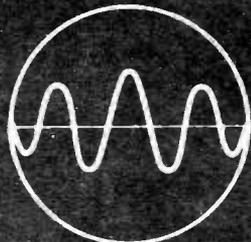SEND FOR OUR FREE 28 PAGE CATALOGUE, PLEASE ENCLOSE A STAMP



TUAC

TUAC Ltd., 121 Charlmont Road, SW17
Tel: 01-672 3137/9080
PRICE INCLUDES VAT. P+P FREE

TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD, 121 Charlmont Road, London SW17 9AB. We accept telephone orders from Access/Barclaycard Holders. Phone 01-672 9080.

TUAC MAIN DISTRIBUTORS (Callers-Only)

- Birmingham**, George Matthews, 85/87 Hurst Street, (Tel: 622 1941).
- Canterbury**, Socoli, 9 The Friars, (Tel: 60948).
- Crews**, Cookies Disco Centre, 126/128 West Street, (Tel: 47397).
- Exeter**, Electrosure, Fore Street, (Tel: 56687).
- London**, Garland Bros., Deptford Broadway, (Tel: 01-692 4412).
- London**, Session Music, 163 Mitcham Road, Tooting, (Tel: 01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.
- Luton**, Luton Disco Centre, 88 Wellington Street, (Tel: 411733).
- Manchester**, A1 Music, 88 Oxford Street, (Tel: 236 0340).
- Middlesborough**, Salscoglen, 43 Borough Road, (Tel: 242851).

TRANSFORMERS Continuous Ratings + VAT 15%

30 VOLT RANGE
Pri 220/240 sec 0-12-15-20-24-30-30V
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V and 15V-0-15V.

Ref	Amps	Price	P & P
112	0-5	2-90	0-90
79	1-0	7-10	1-10
3	2-0	6-35	1-10
20	3-0	6-82	1-31
21	4-0	8-79	1-31
51	5-0	10-86	1-52
117	6-0	12-29	1-67
88	8-0	16-45	1-89
89	10-0	18-98	1-89
90	12-0	21-09	2-24
91	15-0	24-18	2-39
92	2-0	32-40	O.A.

50 VOLT RANGE
Pri 220/240V Sec 0-20-25-33-40-50V
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V and 25V-0-25V.

Ref	Amps	Price	P & P
102	0-5	3-75	0-90
103	1-0	4-57	1-10
104	2-0	7-88	1-31
105	3-0	9-42	1-57
106	4-0	12-82	1-75
107	6-0	16-37	1-99
118	8-0	22-29	2-39
119	10-0	27-48	O.A.
109	12-0	31-79	O.A.

MAINS ISOLATORS (Screened)
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
707	20	4-84	0-91
149	60	7-37	1-10
150	100	8-38	1-31
151	200	12-28	1-31
152	250	14-61	1-73
153	350	18-07	2-12
154	500	22-52	2-47
155	750	O.A.	O.A.
156	1000	40-92	O.A.
157	1500	56-52	O.A.
158	2000	67-99	O.A.
159	3000	95-33	O.A.

*Pri 0-220-240V Sec 115 or 240V.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	6-55	1-04	56W
75	8-50	1-31	64W
150	11-00	1-31	4W
200	12-02	1-67	65W
250	12-55	1-67	69W
500	20-13	1-89	67W
1000	30-67	2-65	84W
1500	42-82	O.A.	93W
2000	54-97	O.A.	95W

SOLID STATE DIGITAL QUARTZ WATCH

12 or 24 hour display
Hour, minute, second, day AM/PM constant display.

Press button for month date, day display, Backlight, lighting by press button, 24, hour mode reading if required (useful for travellers).

Chronograph to 1/10th sec. + lap time + alarm.
1 stainless steel adjustable bracelet
£15.50 inc. VAT 50p P & P.

Ref	12V	24V	Price	P & P
111	0-5	0-25	2-42	0-52
213	1-0	0-5	2-90	0-90
71	2	1	3-86	0-90
18	4	2	4-46	1-10
85	6.5	2-5	6-16	1-10
70	6	3	6-99	1-10
108	8	4	8-16	1-31
72	10	5	8-93	1-31
116	12	6	9-89	1-52
17	16	8	11-79	1-37
115	20	10	15-38	2-39
187	30	15	19-72	2-39
226	60	30	40-41	O.A.

TEST METERS P & P £1-15 15% VAT
AVO 3 MK5 41-50
AVO 71 38-00
AVO 73 50-70
AVO MM5 minor 35-95
Wee Megger 76-25

AUTO TRANSFORMERS

Ref	(Watts)	Step up	Step down	P & P
113	15	0-115-210-240V	2-73	0-81
64	75	0-115-210-240V	4-41	1-10
4	150	0-115-210-240V	5-70	1-10
67	500	0-115-210-240V	12-09	1-91
84	1000		20-64	2-39
93	1500		25-61	O.A.
95	2000		38-31	O.A.
73	3000		65-13	O.A.

ELECTRONIC CONSTRUCTION KIT
Home electronic starter. Start simply and progress to a TRF radio or electronic organ. No soldering. All parts included in presentation box. Instructions. £8-29. P & P 96p, VAT 15%.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8

Nearest Tube Stations: Aldgate & Liverpool St.

MAIL ORDER PROTECTION SCHEME

INTRODUCTION

The Office of Fair Trading have agreed that the notice of the Mail Order Protection Scheme to appear in periodicals carrying mail order advertising should appear as follows:-

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Everyday Electronics will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

(1) You have not received the goods or had your money returned; and (2) You write to the Publisher of Everyday Electronics summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day. Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or Insolvent. This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc, received as a result of answering such advertisements. Classified advertisements are excluded.

OHIO SCIENTIFIC Superboard 2 assembled 50 Hz model, 8K basic 4K ram with free psu and modulator kit £188 + 15% vat post free.

SINCLAIR PRODUCTS New 10MHz scope £145, Pfm200 £51-95, case £3-40, adaptor £3-40, connector kit £11-27. Microvision II £91, adaptor £8-88, Pdm35 £29-76, adaptor £3-40, case £3-40, Dm350 £71-82, dm450 £102-17, dm235 £31-95, rechargeable batts. £7-99, adaptor £3-94, case £9, Enterprise prog. calculator + accessories £19-95.

COMPUTER GAMES chess champion 6 £49-95, Chess challenger 7 £84, Phillips G7000 home computer £149, Videopaks £12-95, Atari videocomputer £147, Carttridges £14-85.

COMPONENTS IN4148 0-9p, IN4002 3-1p, 741 18p, Bc182, bc184, bc212, bc214, bc548 5-5p, Resistors 1W 5% E12 10R to 10M 1p, 0-8p for 50-2, one value, 16V electrolytics 5, 1, 2, 5, 10, 22mf 5p, 100mf 6p, 100mf 10p, 1 1b FeC1 £1-30, Dalo pen 84p, 40 sq ins pcb 45p, Polystyrene capacitors E12 63V 10 to 1000p 3p, 1n2 to 10n 4p, Ceramic capacitors 50V E6 22pf to 47n 2p, Zeners 400mV E24 2v7 to 33v 7p.

TV GAMES AY3-8500 L kit £7-26, Rifle kit £5-27, AY-3-8600 L kit £7-28, Stunt cycle chip + kit £18-66, AY-3-8603 chip £17-63.

TRANSFORMERS 6-0-6V 100ma 76p, 1 1/2 £2-60, 9-0-9V 75ma 76p, 1a £2-22, 2a £3-13, 12-0-12V 100ma 92p, 1a £2-80.

IC AUDIO AMPS with pcb, JC12 6W £2-80, Jc20 10W £3-14.

BATTERY ELIMINATORS 3-way type 6/7 1/2v 300ma £3-14, 100ma radio type with press-studs 9v £3-57, 9+9v £4-79, Car converter 12v input, output 43/6/7 1/2v 300ma £2-66.

BATTERY ELIMINATOR KITS 100ma radio types with press-studs 4 1/2v £1-49, 6v £1-49, 9v £1-49, 4 1/2-4 1/2v £1-82, 6+6v £1-92, 9+9v £1-82, Stabilized 8-way types 3 1/2/6/7 1/2/9/12/15/18v 100ma £2-50, 1 Amp £5-30, Stabilized power kits 2-18v 100ma £2-98, 1-30v 1A £6-20, 1-30v 2A £11-24, 12v car converter 6/7 1/2v 1A £1-35, T-DEC AND CSC BREADBOARDS s-dec £3-79, t-dec £4-59, u-deca £4-69, u-decb £3-76, exp4b £2-64, exp300 £6-61, exp350 £3-62, exp325 £1-84.

BI-PAK AUDIO MODULES s450 £25-06, AL60 £5-06, pa100 £17-33, Spm80 £24-74, Bm180 £6-08, Stereo 30 £21-57, AL30A £4-08, pat2 £8-38, pat2 £1-58.

SWANLEY ELECTRONICS

Dept. EE, 32 Goldsrd Rd., Swanley, Kent. Post 30p extra. Prices include VAT unless stated. Official and overseas orders welcome. Lists 24p post free.

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all . . .

. . . our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.Cs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including I.Cs, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.




Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

What's new from Heathkit?



IM 2212 — Auto Ranging DMM

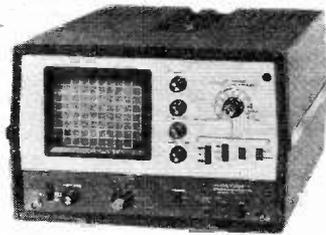

IO 4105 — Single Beam 5MHz Oscilloscope



IM 5217 — Portable Multimeter

Plus

- * GD 1290 — VLF Metal Locator
- * HX 1681 — CW Transmitter
- * IR 5201 — XY Recorder
- * CI 1525 — Car Temperature Indicator

These brand new self-assembly kits are designed to the highest specification.

The step-by-step instructions make them easy to build at your leisure in your own home.

And first class quality makes them excellent value for money.

Details of the full Heathkit range are available in the Heathkit catalogue. Send for your copy now.



IM 2215 — Hand-held DMM

To: Heath (Gloucester) Limited, Dept. EE2 Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.

Name _____

Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

Soldering
Iron offer
FREE

When you receive your catalogue you will get details of this free offer.



There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451).

HEATHKIT



CLASSIFIED

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £5.00 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury

notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

For Sale

NEW BACK ISSUES of "EVERYDAY ELECTRONICS". Available 75p each Post Free, open PO/Cheque returned if not in stock. BELL'S TELEVISION SERVICES 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

BACK ISSUES, November 1971 to February 1976 complete. Also April to September 1976. Offers to: Coventry 87587.

Receivers and Components

COMPONENTS AT SILLY PRICES. 1,000 mixed resistors £3.60. SAE lists. W.V.E.2, Craigo Farm, Tintern, Gwent.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs, 0945 4188. Immediate settlement.

P.C.B.s Paxolin 10 1/2" x 4 1/2" 4-£1.30. 12" x 9 1/2" 85p. 16" x 11 1/2" £1.40. D.S. 10" x 8 1/2" 85p. Fibreglass 12" x 7 1/2" £1.60. 14" x 6" £1.50. D.S. 10 1/2" x 7" £1.35. 8" x 7" £1.45. Panel with 40 assorted 74 series I.C.s £1.60. 20 wire ended Neons £1.20. Small 3 Transistor Audio Amps 3-£1.20. 300 Small Components, Trans, Diodes £1.60. 7lbs Assorted Components £3.75. List 15p. refundable. Post 20p. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

10 MIXED COLOURS, sizes, LEDs £1-15p. Lists 15p. Sole Electronics, EE, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

QUALITY ELECTRONIC COMPONENTS AT LOW PRICES

Write or telephone for free pamphlet to:

HARRISON BROS. DEPT EE.

P.O. Box 55, Westcliff-on-Sea, Essex. SS0 7LQ.
Tel: Southend-on-Sea 32138

DISCOVER ELECTRONICS. Build forty easy projects including: Metal Detector; Breathalyser; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms, etc. Circuits, plans all for £1.29 including FREE circuit board. Mail only. RIDLEY PHOTO/ELECTRONICS, Box 62, 111 Rockspark Road, Uckfield, Sussex.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-70 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4-50 plus 25p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P.

LOTS MORE! Send 25p for lists.

Prices include VAT.

BOFFIN PROJECTS

4 CUNLIFF ROAD, STONELEIGH
EWELL, SURREY. (E.E.)

100 ASSORTED COMPONENTS 115p. 100 assorted resistors 75p. 100 assorted capacitors 150p. P&P 25p. SAE for catalogue. DURRANT, St. Mary's Street, Shrewsbury, Salop.

Educational

COURSES—RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination and obtain your G8 Licence, with an RRC home study course. For details of this, and other courses (GCE, professional examinations etc), write or phone: THE RAPID RESULTS COLLEGE, Dept JRI, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service).

Record Accessories

STYLII CARTRIDGES FOR MUSIC CENTRES &c. FREE List No. 29. For S.A.E. includes Leads, Mikes, Phones, etc. FELSTEAD ELECTRONICS (EE), LONGLEY LANE, GATLEY, CHEADLE, CHES SK8 4EE.

Service Sheets

SERVICE SHEETS from 50p and SAE. Catalogue 25p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. **BELL'S TELEVISION SERVICE** for service sheets on Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Rd, Harrogate, N. Yorkshire. Tel: 0423 55885.

Miscellaneous

LEARN ELECTRONICS THE EASY WAY. Build: amplifiers, oscillators, detectors, testers, flashers, metronomes, etc, more than 25 projects, with our multi-kits, complete instruction manual supplied. Send £15 to: Major Oak Services, 33 Lillian Avenue, London W3.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4.
Reg. Office, 22 Coningsby Gardens.

ENAMELLED COPPER WIRE				
SWG	1 lb	3 oz	4 oz	2 oz
10-19	2.65	1.45	.75	.80
20-29	2.85	1.65	.90	.70
30-34	3.05	1.75	1.00	.75
35-40	3.40	1.95	1.15	.84
41-43	4.55	2.55	1.95	1.30
44-46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30
SILVER PLATED COPPER WIRE				
14, 16, 18	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT.
SAE brings list of copper & resistance Wires.
Dealer enquiries invited.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer—now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/packing 60p. WHITE HOUSE ELECTRONICS, P.O. Box 19, Castle Drive, Penzance, Cornwall.

ELECTROLYTIC CAPACITORS—MODERN MINIATURE TYPE

220uf at 100 V.D.C. (75mm x 35mm) £1.00 ea. inc. p & p. 10+—75p ea. 10+—85p ea. Three channel Sound/light boards 700 w.p.c. £12.00 ea. Complete units £21.50 ea. inc. p & p. Also Sound Chasers, Amps, Sirens, Alien Voice Simulators. Send Large s.a.e. and 10p for lists of range, or Phone, write or call at:

N.J.D. LTD. 3 Marlborough Street, Dunkirk, Nottingham. Phone: Nottingham 703345 (602)

TRADE ENQUIRIES WELCOME—QUANTITY DISCOUNT AVAILABLE

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Phone 31803. No lists, enquiries S.A.E.

E.E. Radio Control System PCB's

Professional quality glassfibre, Fry's solder tinned and drilled.

Dec. 79 Transmitter **£1.47**
Receiver **0.88p**

Postage: Please add 25p postage and packing to complete order.

PHOTO DESIGN

14 Downham Road, Ramsden Heath, Billericay, Essex CM11 1PU Tel: 0268-710722

DON'T

GET ALARMED

ABOUT RISING CAR THEFTS

GET ALARMED

WITH HARVELEC

The new all electronic car alarm. Entry timer—user selectable between 20 and 60 seconds, confuses would be thieves. Exit timer—fixed at 60 seconds, allows leisurely exit. Alarm timer—fixed at 150 seconds, ensures battery is not run down while car is left. Sensitive battery change detector, sets alarm from courtesy light, ignition, radio, etc.

- ★ CAR IMMOBILISATION & EAR SPLITTING ALARM ★
- ★ ACCESSORY PROTECTION ★

Suits all 12-volt -ve. ea. systems. Incredible Introductory price £26.75 inc. VAT and p & p (HORN, CONTROL UNIT & SWITCH)

C-MORE

of your battery condition and charging rate with this fantastic little device.

- ★ EASY DASH MOUNTING ★
- ★ EASY READ RED/YELLOW DISPLAY ★
- ★ FOREWARNS OF EXPENSIVE ELECTRICAL TROUBLE ★

£6.62 inc. VAT & p & p

YOU MAY TRY EITHER DEVICE ON YOUR OWN CAR WITH THE CONFIDENCE OF OUR 10 DAY MONEY BACK ASSURANCE.

HARVELEC (Dept. EE)

1 Formby Avenue, St. Helens, Merseyside, WA10 3NW
Regd. in UK. No. 2395248.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus catalogue. Write or call, Sandwell Plant Ltd, 2 Union Drive, Boldmere, Sutton Coldfield, West Midlands. 021-354 9764. Or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

DIGITAL WATCH BATTERIES. State type or send old battery. 60p each, 2 for £1.20, p.p. 10p. Discount for larger quantities. F. S. Butler, 511 Fulbridge Road, Peterborough PE4 6SB.

AERIAL BOOSTERS

Improves weak VHF Radio and Television reception. B45-UHF TV, B11-VHF Radio. B11A-2 metres. For next to the set fitting. Price £6.

SIGNAL INJECTOR

A complete range of A.F. and R.F. Frequencies up to the UFH Band. Price £5.00. S.A.E. for leaflets—Access.

ELECTRONIC MAILORDER LTD,

62 Bridge Street,
Ramsbottom, Bury, Lancs. BL0 9AG.

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send £7.50 for complete kit and get into a fast growing business. Prompt despatch.



WATCH BATTERY REPLACEMENT CO. (EE 11)
11 Percy Avenue, Ashford, Middx., TW15 2PB

Situations Vacant

TECHNICIAN APPRENTICESHIPS ELECTRONICS

If you read this magazine—it's probably safe to assume you have an interest in electronics! So why not think about making a career for yourself in this field?

Marconi Communication Systems Limited works at the forefront of technology worldwide, developing equipment which includes Mobile Radio Systems, sound and TV Studio Equipment and Space Systems.

Our training is probably second to none, so if you are leaving school in 1980 and hope to obtain either G.C.E. 'O' levels or C.S.E. in Mathematics, Physics and English Language, we would like to hear from you.

Accommodation will be available during your first year of training.

To find out more about the training schemes we can provide and to obtain an application form, write to the Chief Training Officer, Marconi Communication Systems Limited, New Street, Chelmsford, Essex.

MARCONI COMMUNICATION SYSTEMS

A GEC-Marconi Electronics Company

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Everyday Electronics for

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)

NAME

ADDRESS

Send to: Classified Advertisement Manager

EVERYDAY ELECTRONICS
GMC, Classified Advertisements Dept., Room 2337,
King's Reach Tower, Stamford Street, London SE1 9LS.
Telephone 01-261 5942

Rate:
18p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

OPTO



LEDs
 0.1" Red 9p
 0.2" Red 9p
 0.2" Green 12p
 0.2" Yellow 12p
 DL727 0.5" 2-digit CA £1-25
 DL304/307 (pin compatible with DL704/707) 0.3" CC Red 70p
 DL847 CA/DL850 (pin com. with DL747/750) 0.8" CA/CC £1-80
LIQUID CRYSTAL DISPLAY
 3½ digit 40 pin dil £7-50
 *SPECIAL
 IL74 Opto Isolator 45p

INTEGRATED CIRCUITS

555 Timer 21p
 741 Op. Amp 18p
 AY-5-1224 Clock £2-60
 AY-5-1230/2 Clock Timer £4-20
 AY-3-1270 Thermometer £8-20
 ICL7106 DVM (LCD drive) £7-00
 LM377 Dual 2W Amp £1-45
 LM379S Dual 6W Amp £3-50
 LM380 2W Audio Amp 80p
 LM382 Dual low noise pre amp £1-00
 LM386 250mW low voltage amp 75p
 LM1830 Fluid Level Detector £1-50
 LM2907 f-v Converter £1-40
 LM3909 LED Flasher/Oscillator 55p
 LM3911 Thermometer £1-20
 LM3914 Dot/Bar Driver £2-10
 MM57160 (stac) Timer £5-90
 MM74C911 4-digit display controller £6-50
 MM74C915 7-segment-BCD converter 96p
 MM74C926 4-digit counter with 7-seg outputs £4-50
 S566B Touchdimmer £2-50
 S9263 Touchswitch 16-way £4-85
 TBA800 5W Audio Amp 58p
 TBA810AS 7W Audio Amp 85p
 TDA1024 Zero Voltage Switch £1-00
 TDA2020 20W Audio Amp £2-85
 All ICs supplied with data & circuits.
 Data sheets only 5p

LIGHTING CONTROL KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touchplates. Easy to follow instructions.
TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark £6-50
TDE/K Extension kit for TD300K for 2-way switching etc. £1-50
TSD300K—TOUCHSWITCH & DIMMER. Single touchplate, small knob controls brightness £5-50
TSA300K—AUTOMATIC. Single touchplate. Time delay variable 2 secs. to 3½ mins. £4-30
LD300K—LIGHTDIMMER KIT £2-90

DIGITAL VOLTMETER/THERMOMETER KIT

Based on the ICL7106. This Kit contains a PCB resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DV kit to be modified to a Digital Thermometer, using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery) £20-75.



TRIACS



400V Plastic Case (Texas)
 3A 49p 16A 90p
 8A 57p 20A 165p
 12A 70p 25A 190p
 6A with trigger 80p
 8A isolated tab 82p
 Diac 18p

24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT 1000K Basic Kit £14-90
 CT 1000KB with white box (56 x 131 x 71mm) £17-40
 Ready built £22-50

BOXES

Moulded in high impact ABS. Supplied with lids and screws. Black or white.
 PB2 95 x 71 x 35mm 65p
 PB 3 115 x 95 x 37mm 70p

RESISTORS

½W 10 ohm—10M E12 Series
 Pack of 10 (1 value) 10p
 10 Packs (10 values) 80p

CAPACITORS

Polyester 250V

0-01	6p	0-22	12p
0-022	6p	0-33	12p
0-033	7p	0-47	15p
0-047	7p	0-68	18p
0-068	7p	1-0	24p
0-1	7p	1-5	27p
0-15	11p	2-2	31p

Electrolytics
 A = Axial R = Radial

63V 1-0 R	3p	16V 10 R	3p
2-2 R	3p	22 R	3p
4-7 R	4p	33 R	3p
10 R	5p	47 R	4p
47 R	8p	100 R	5p
25V 22	6p	220 R	6p
47 A	6p	470 R	9p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 30p P&P. MAIL ORDER—CALLERS WELCOME BY APPOINTMENT.



TK Electronics (EE)

106 STUDLEY GRANGE ROAD
 LONDON W7 2LX. TEL. 01-579 9794



INDEX TO ADVERTISERS

A.J.D. 82	I.L.P. Electronics 88-89	R. & T. V. Components 87
Ambit Cov iii	Intertext (ICS) 147	Radio Components Specialties 84
Barrie Electronics 148	J.W.B. Radio 150	Science of Cambridge 133
Bi-Pak 85	Leytronics Ltd. 146	Scientific Wire Co. 150
Birkett J. 143	Magenta Electronics 81	Selray Book Co. 145
B.N.R.E.S. 140, 141	Maplin Electronic Supplies Ltd. Cov iv	Stevenson C. N. 123
Boffin Projects 150	Marconi Communication Systems ... 151	Swanley Electronics 148
Cambridge Learning 145	Marshall A. 149	
Continental Specialties Corporation... 83	Meca 84	
E.D.A. 82	Menocrest 145	Technomatic 143
Electronic Mail Order (Bury) Ltd. ... 151	Metac 138-139	T.K. Electronics 152
Electrovalue 86	Monolith... .. 147	TUAC 148
George Sales, David 147	NJD Ltd.... .. 150	
Greenweld 86	Phonosonics 140	Watch Battery Replacement 151
Harrison Bros 150	Powell T. 144	Watford Electronics Cov Ti
Harvelec 150	Precision Petite 135	West Hyde 146
Harversons 142	Proto Design 150	Wilmslow Audio 143
Heathkit 149		
Home Radio 144		


Published approximately the third Friday of each month by IPC Magazines Ltd., Kings Reach Tower, Stamford St., London SE1 9LS. Printed in England by Index Printers Ltd., Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/Sia) Ltd. South Africa—Central News Agency Ltd. Subscriptions: Inland £9.00, Overseas £10.00 per annum payable to IPC Services, Oakfield House, Perry-mount Road, Hayward Heath, Sussex. Everyday Electronics is sold subject to the following conditions namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on cover, excluding Elite where the selling price is subject to V.A.T., and that it shall not be lent, resold, or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

IT'S HAPPENED AGAIN !

THE PART THREE CATALOGUE IS PUBLISHED & WE HAVE MOVED TO BIGGER PREMISES.

Yes, it's here at last - the all new Part Three Catalogue. Fun for all the family, and the usual update on all that is new, worthwhile and exciting in the world of Radio and Communications. A big section on frequency synthesis techniques covering broadcast tuners, to communication quality transmitter systems. More new products than ever - RADIO CONTROL parts, crystal filters, ceramic filters for 455kHz and the new range of TOKO CFSH low temperature coefficient types for 10.7MHz. Details on new radio ICs, including the new HA11225, the CA3189E lookalike with 84dB signal to noise, and adjustable muting threshold. Radio control ICs - and an updated version of the RCM&E 8 channel FM receiver - now with an Ambit designed screened front end, with 27MHz ceramic bandpass filter. LCD panel clock/timer modules - the neatest and best LCD panel DVM yet (only £19.45 each + VAT), the new 5 decade resolution DFM3 for LW/HF/VHF with LCD readout. The DFM6 with fluorescent display to 10kHz resolution on VHF, 1kHz on SW. A 1kHz HF synthesiser with five ICs - the list is endless. Get your copy of the catalogue now. Post publication price is 60p (inc PP etc). The previous two sections are also required for a complete picture: Parts 1 & 2 £1 the pair, All 3 £1.50. And don't miss our spot the gibbon contest, together with a quiz to see if you can spot the differences between a neolithic cave drawing and a circuit diagram of one of our competitor's tuners. (* Yes, we still haven't learnt how to spell.)


FM radio control RX kit

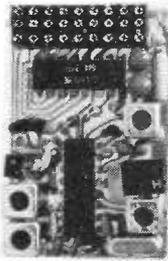

- 8 Channel RC receiver (FM)
- Single IC RF/IF/Detector
- Single IC decoder
- 27MHz ceramic filter input
- FET RF stage with double tuned bandpass filter
- Dual ceramic filter IF
- Best quality SLM servo connector block
- ONLY £16.10 inc VAT (kit) (includes new SLM case)


DOES YOUR ONE GLOW GREEN IN THE DARK ??

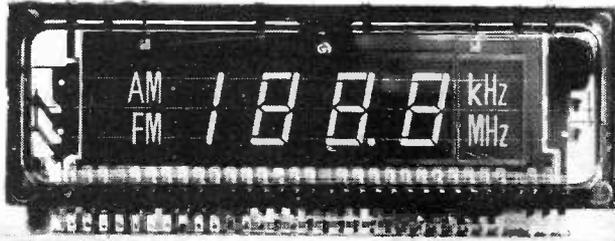Our DFM4 does, since it uses a vacuum fluorescent display for direct readout of MW/LW/FM. Basically the same as the DFM2, (LCD Version). £24.45 kit (inc VAT) Transformer with all necessary windings for DFM4 - £2.50 inc VAT.



Not illustrated here - but also now available is the DFM6. This is a vacuum fluorescent display version of our immensely popular DFM3 (LCD). Resolution is 100Hz to 3.9999MHz, 1kHz to 39.999MHz, and 10kHz to 200.00MHz+; all standard IF offsets (inc. 10.7MHz on shortwave) are available via diode programming.

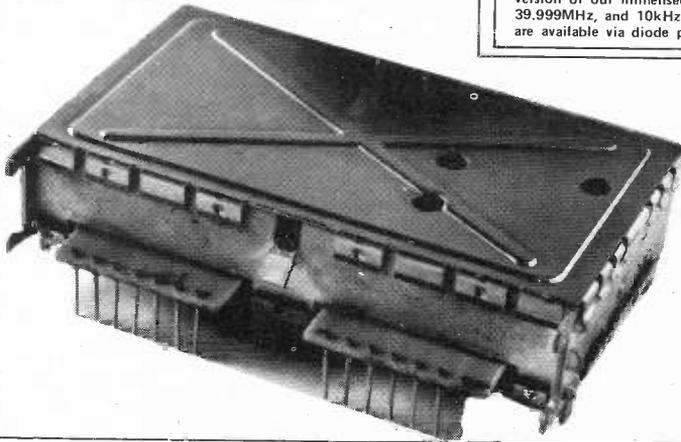New series of radio modules in fully screened cans:



UM1181 VHF band 2 VARICAP TUNERHEAD

5 tuned circuit, with image/spurii better than -80dB, buffered LO output, MOSFET RF stage, FET IF preamp, tunes with only 1½ to 8v, -9dBm 3rd order intercept. 1off price £12.00 inc VAT. (100off) OA)

911225 FM IF strip with all mod cons for the HiFi tuner: All types use 80+dB S/N Hitachi IC, with muting, AFC, AGC, meter outputs for signal level and centre zero. IF preamp stage.

'A' Dual linear phase ceramic filters, with MOSFET (AGC'd) IF preamp and a 3rd narrow filter with OC filter selection. Dual tuned FM detector stage. £23.95 inc VAT (built)
'B' Dual ceramic filters, single tuned detector stage £14.95 inc VAT (All 'A' series units are set up with a spectrum analyzer for best THD)

91072 AM RADIO TUNER MODULES - DC TUNED and DC SWITCHED Available February '80

All include buffered LO output, mechanical IF filter (TOKO CFMG) 1-10v tuning bias, switching by a single pole to earth
A MW/LW (150 to 350kHz LW range) with ferrite rod antenna
B As 'A' but also including SW1 or SW2 (specify.)
SW1 = 1.5 to 4MHz SW2 = 5 to 10MHz
C With both SW ranges

Prices one off inc VAT
'A' £14.43 'B' £15.90 'C' £17.50 (Custom types OA)

FREQUENCY READOUT LSI from OKI, with a one-chip answer to most digital frequency display needs (and various modules).

Crystal and ceramic ladder filters from leading manufacturers, ferrite rods, various ferrite beads and a range of crystals for 'standard' frequencies and both AM and FM radio control at 27MHz. Trimmer capacitors.

METERS - a new range of linear movement types, plus many 'indicator' types for VU, all types of tuning indicators etc.

SOCKETS - a new range that are better quality than Texas low profile, yet better priced.

Modules for AM/FM/STEREO, complete kits for tuners, audio amplifiers from Larsholt.

SWITCHES - complete low cost DIY systems for push button arrays, keyboard switches.

DOUBLE BALANCED MIXERS - MCL SBL1, replacement for MD108 etc. And cheaper.

There is a danger - when advertising in some magazines - that because we do not find space to list everything we sell in every ad., that some readers forget about half the ranges we stock. So to summarize the general ranges:

- TOKO Chokes, coils for AM/FM/SW/MPX, Audio filters etc
Filters: Ceramic for AM/FM, LC for FM, MPX etc.
Polyvaricons
- ICs for radio, clock LSI, radio control, MPX decoders etc
- Micrometals Dust iron cores for toroids for resonant and EMI filters
Toroid mounts
- Hitachi Radio/audio/mpx linear ICs
100W MOSFETs, small signal FETs, MOSFETs and bipolar

And the following groups of products from a broad range of sources:

- Semiconductors - specializing in radio devices, Plessey SL1600, EUROPE's best selection of AM/FM and communications devices. Power MOSFETs, WORLD'S LOWEST NOISE AUDIO small signal transistors, BAR graph LED drivers for linear and log.
- CD4000 series CMOS, TTL/LPSNTTL, standard linears (741, 301, 3080 etc). MPUs, memories.
- Small signal transistors from AEG BC237/8/9 families etc. (1000 off BC239C : 5.2p ea)
- LEDs: AEG 3mm/5mm round, 2.5x5mm flat, red, green, orange, yellow. The best prices you will find for quality products.
- MOSFETs for RF signal processing, including the BF960 UHF device, and 3SK51 for VHF.
- Varicap diodes for 17:1 capacity ratio tuning

OUR LATEST MOVING EXPERIENCE :: At last, we have moved to the address below. There is car parking for customers approaching via North Service Road (an extension of North Road Avenue, entrance opposite the Brentwood Fire Station.) Pedestrian access from the High Street (alongside 117 High Street). The new building is six times bigger than our Gresham Road offices, and we will be installing a much expanded sales counter in the fullness of time. NEW TELEPHONE NUMBER (0277) 230909. TELEX NUMBER (as before) 995194 AMBIT G. See you there !

200 North Service Road, Brentwood, Essex.

MAPLIN



This superb organ—build the first working section for just over £100. Full specification in our catalogue.




Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.




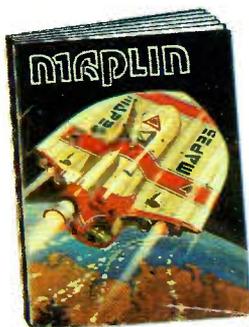61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.

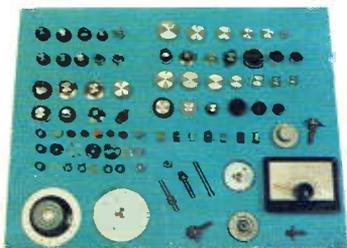A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages—some in full colour—it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Speakers from 1½ inch to 15 inch; megaphone. PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____

ADDRESS _____

EE/2/80



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000.