

198  
Easy to build projects for everyone

# Everyday ELECTRONICS

APRIL 82  
70p

**Secret  
and  
Secure  
with  
our  
MAGNETIC  
LOCK**

**MORE MEMORY**




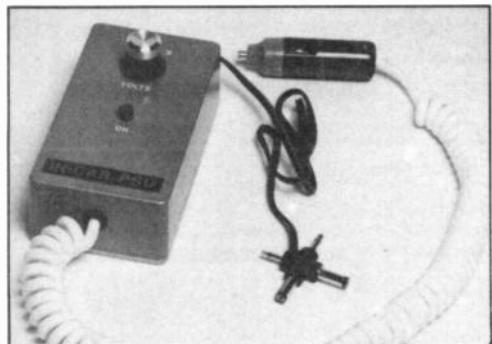**ADD-ON UNIT**





PROJECTS . . . THEORY . . . NEWS . . .  
COMMENT . . . POPULAR FEATURES . . .



ZX81 cover photo—Sinclair Research Ltd.

## SCHOOLS Electronic Design Award COMPETITION

Joint sponsors Mullard Ltd and EVERYDAY ELECTRONICS are delighted with the great response from secondary schools to their challenge. The judges have just completed their examination of entry papers and all participants will be notified directly of the results for Stage 1.

The twelve winning schools are to submit their working models for Stage 2 judging during May. An exhibition of models and presentation of prizes will take place at Mullard House, Torrington Place, London WC1, in June. Further news regarding SEDAC will appear in next month's issue.

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitation in whole or in part are expressly forbidden.

# Everyday ELECTRONICS

## PROJECTS

- |  |            |
|--|------------|
| <b>CAPACITANCE/FREQUENCY METER</b> by A. P. Donleavy | <b>228</b> |
| Dual purpose digital meter for the workshop          |            |
| <b>2K RAM PACK</b> by V. Terrell                     | <b>234</b> |
| Memory expansion for the Sinclair ZX81 Microcomputer |            |
| <b>MAGNETIC LOCK</b> by R. A. Penfold                | <b>244</b> |
| The lock that doesn't betray its presence            |            |
| <b>V.C.O. SOUND EFFECTS UNIT</b> by D. Butler        | <b>257</b> |
| Simple experimental sound generator                  |            |
| <b>IN-CAR P.S.U.</b> by A. R. Winstanley             | <b>260</b> |
| Provides 6V, 7.5V or 9V d.c. from a 12V car battery  |            |
| <b>LIGHT ACTUATED SWITCH</b> by R. A. Penfold        | <b>264</b> |
| Controls equipment by light                          |            |

## SERIES

- |   |            |
|---|------------|
| <b>TEACH-IN 82</b> by O. N. Bishop                    | <b>238</b> |
| Part 7: Amplifiers and the Amplifier Module           |            |
| <b>INTRODUCTION TO LOGIC</b> by J. Crowther           | <b>252</b> |
| Part 12: Final part of this series—flip-flop circuits |            |

## FEATURES

- |   |            |
|---|------------|
| <b>EDITORIAL</b><br>Inconspicuous; Flag Flying  | <b>227</b> |
| <b>SHOP TALK</b> by Dave Barrington<br>Product news and component buying                      | <b>233</b> |
| <b>JACK PLUG AND FAMILY</b> by Doug Baker<br>Cartoon  | <b>237</b> |
| <b>FORMING AN ELECTRONICS CLUB</b><br>by T. R. de Vaux-Balbirnie<br>A school teacher's advice | <b>249</b> |
| <b>EVERYDAY NEWS</b><br>What's happening in the world of electronics                          | <b>254</b> |
| <b>RADIO WORLD</b> by Pat Hawker G3VA<br>Empire Broadcasting, Amateur Satellites              | <b>256</b> |
| <b>READERS LETTERS</b><br>Your news and views   | <b>267</b> |
| <b>DOWN TO EARTH</b> by George Hylton<br>Designing a simple a.m. radio                        | <b>268</b> |
| <b>COUNTER INTELLIGENCE</b> by Paul Young<br>A retailer comments                              | <b>269</b> |
| <b>BRIGHT IDEAS</b><br>Capacitor Measurement  | <b>269</b> |
| <b>FOR YOUR ENTERTAINMENT</b> by Barry Fox<br>A visit to a Japanese semiconductor factory     | <b>270</b> |
| <b>SQUARE ONE</b><br>Beginners' Page: Switches  | <b>272</b> |
| <b>NEW PRODUCTS</b><br>Facts and photos of instruments, equipments and tools                  | <b>273</b> |
| <b>CIRCUIT EXCHANGE</b><br>A forum for readers' ideas   | <b>274</b> |

### DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasant three-note harmonic sequence (not a microprocessor controlled buzz or the same old ding dong) at the touch of a button. This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V DC power. It is built from common parts found in most households. It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 150mW output and draws less than one 1uA from a PP3 battery when the tone ceases. Supply complete with circuit and assembly instructions.

**IDEAL PROJECT FOR BEGINNERS—Only £5**

### REMOTE CONTROL

Published remote control systems tend to be quite complex, requiring difficult to obtain components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infra-red, our KITS range from simple on/off controllers to coded transmitter/receiver with 16 on/off outputs or three channel outputs for use with TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required logic. We sell radio tracs, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices.

We have compiled a booklet on remote control systems containing full data sheets and details of our remote control kits and components. So don't control yourself—SEND US 30p and a stamped addressed envelope for your copy TODAY!

**FAST SERVICE • TOP QUALITY • LOW LOW PRICES**

No circuit is complete without a call to—

**ELECTRONICS**  
11 Boston Road  
London W7 3SJ

ALL PRICES  
EXCLUDE VAT

DEPT. E.E.


Telephone:  
01 579 9794/2842

# KITS & COMPONENTS

### HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TDR300K	Remote Control Dimmer	£14.30
MK6	Transmitter for above	£ 4.20
TD300K	Touchdimmer	£ 7.00
TDE/K	Extension kit for 2-way switching for TD300K	£ 2.00
LD300K	Rotary Controlled Dimmer	£ 3.50

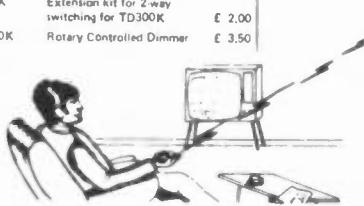

### 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, tracs, PCBs and full instructions.

CT1000K Basic Kit  
CT1000K with white box (56/131 x 71mm). (Ready Built).

### TEACH-IN '82

EE Minilab	£13.50
Parts 1 - 6	£ 7.50
Parts 7 - 12	£ 4.90
Special price for all kits purchased together	£23.50
Woodwork not included	—

The above kits include all the components specified in the Teach-In '82 projects parts 1 - 12 plus sockets for ICs specified.

### DISCO LIGHTING KITS

DL1000K. This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. Only £14.60

DL2100K. A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Only £8.00

Optional opto input DLA1. 60p

Allowing audio ("beat")—light response.

### LEDs

3mm & 5mm Round Red.....09p Green.....12p  
Clips 3mm & 5mm.....03p Yellow.....12p

### [Shaped LEDs]

	Red	Green	Yellow
Rectangular (Gravestone)	16p	16p	16p
Rectangular	15x2.5mm	17p	20p
Square	15x15mm	17p	20p
Triangular	15mm	17p	20p
Arrowhead	12.5x5mm	17p	20p

### [Flashing LEDs]

5mm diameter Red.....39p Flashing/Continuous.....42p

### [Tri Colour LEDs]

5mm round.....30p 5mm Rectangular.....32p




### DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3½ digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (−50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.... Price £15.50


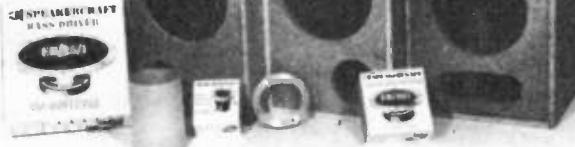
### So you've fancied some WHARFEDALE E90 speakers—

But the bank manager won't co-operate! Don't despair—now there are Wilmslow Audio flat-pack kits for the Wharfedale E50, E70 and E90. A few hours of easy and interesting work will complete your speakers at a very considerable saving on buying 'assembled' E systems.



The kits contain all cabinet components—accurately machined for easy assembly— all drive units, crossover networks, acoustic wadding, reflex port trim, nuts, bolts, terminals, grille fabric, etc. The cabinets can be painted or stained or finished with iron-on veneer. Easy, foolproof assembly instructions are supplied—no electronic or woodworking knowledge necessary.

Prices: £50 kit £182 per pair including VAT, carriage and insurance £ 8  
£70 kit £220 per pair including VAT, carriage and insurance £ 8  
£90 kit £330 per pair including VAT, carriage and insurance £10  
Credit terms available through leading finance house.

Written details on request.



35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!

0625 529599

# MUSIC KITS

ALL WITH PRINTED CIRCUIT BOARDS

128-Note Sequencer	SET76 120 45	Drum-Synthesiser	SET119 50 11
16-Note Sequencer	SET86 54 63	Enlarger/Timer	SET93 39 22
3-Channel Mixer	SET107 21 50	Frequency Doubler	SET98 11 75
3-Microphone Mixer	SET108 12 99	Funny Talker	SET99 15 55
6-Channel Mixer	SET90 96 87	Guitar Effects	SET42 15 22
Analogue Reverb	SET83 45 92	Guitar Multiprocessor	SET85 79 15
Audio Effects	SET105 15 12	Guitar Overdrive	SET56 21 17
Chorusynth	SET100 125 04	Guitar Sustain	SET75 11 77
Compressor	SET120 25 05	Headphone Amplifier	SET104 21 15
Digital Reverb	SET78 75 50	Metronome	SET118 10 58
Disco strobe	SET57 39 78	Microphone Pre-amp	SET61 11 32

### 10% OFF

10% off U.K. CWO. orders over £20. From this advert until end of month. (5% off for credit cards). This coupon must accompany order.

Noise Limiter	SET97 15 96	Split-Phase Tremolo	SET102 29 98
P.E. Minisonic Synth	SET38 181 56	Switched Treble Boost	SET89 12 51
Phaser	SET88 21 08	Synthesiser Interface	SET81 9 49
Phasing & Vibrato	SET70 38 25	Transient Generator	SET63 18 86
Practise Amplifier	SET106 22 15	Tremolo	SET116 13 47
Rhythm Generator	SET103 See Lists	Tuning Fork	SET46 37 04
Signal Tracer	SET109 17 50	Voice Operated Fader	SET30 9 85
Simple Phase Unit	SET25 10 54	Voice-Scrambler	SET117 21 81
Smooth Fuzz	SET91 11 68	Wah-Wah	SET58 14 01
Speech Processor	SET110 12 18	Wind and Rain Unit	SET28 11 39

Sets include PCBs, U.K. P. & P., 15% VAT, Res., Caps., S'C's, Pots, Knobs, SW's, Skts., Wire, Solder, Box, Photocopy of Orig. Text. Fuller details and more great kits in our Free Catalogue.

Prices correct at press. E. & O.E., subject to stock. Delivery frequently by return but please allow 14 days.

# PHONOSONICS

DEPT EE24, 22 HIGH STREET, SIDCUP, KENT, DA14 6EH  
01-302-6184

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED ORDERS  
DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/  
P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL  
INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY  
WELCOME. P&P ADD 50p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS  
POSTAGE AT COST. AIR/SURFACE. (ACCESS orders by telephone welcome).

**VAT** Export orders no V.A.T. Applicable to U.K. Customers only. Unless stated otherwise  
all prices are exclusive of V.A.T. Please add 15% to total cost including P & P.

We stock many more items. It pays to visit us. We are situated behind Watford Football  
Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to  
Saturday 8.00 am - 8.00 pm. Ample Free Car Parking space available.

## POLYESTER CAPACITORS: Axial lead type (Values are in nF)

400V : 1nF, 1n5, 22n, 3n, 4n7, 6n8 11p; 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 16p; 100n, 150n  
20p, 220p 30p; 330n 42p; 470n 52p; 680n 60p; 1uF 8p; 2uF 82p; 4uF 85p;  
160V : 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n 38p; 1uF 42p; 1uF 45p; 2uF  
48p; 4uF 58p.

## POLYESTER RADIAL LEAD CAPACITORS (250V)

10nF, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n,  
470n 17p; 680n 18p; 1uF 23p; 1uF 40p; 2uF 48p.

## ELECTROLYTIC CAPACITORS : (Values are in $\mu$ F) 500V : 10 52p; 47 78p; 63V : 0-47 1-0,

1.5-2.2, 3-3.8p; 4-7 8p; 6-8, 10 10p; 15, 22 12p; 33 15p; 47 12p; 100 19p; 1000 70p; 47 12p;  
68 20p; 220 24p; 470 32p; 2200 90p; 40V : 4-7, 15, 22 16p; 33 20p; 47 20p; 25V : 1-5, 6-8,  
10, 22 8p; 33 9p; 47 8p; 100 11p; 150 12p; 220 15p; 332 22p; 470 25p; 680, 1000 34p; 2200 50p;  
3300 76p; 4700 92p; 16V : 40, 47, 100 19p; 125 22p; 220 33p; 470 20p; 630 34p; 1000 1500 31p;  
2200 34p; 3300 74p; 4700 79p.

## TAG-END TYPE : 70V; 4700, 245p. 64V; 3300 198p; 2200 139. 50V; 3300 154p; 2200 110p.

40V; 4700u 160p, 25V; 4000 82p; 3300 98p; 2500, 2200 90p. 15,000 345p

## TANTALUM Bead Capacitors

35V : 0.1u, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 18p; 2-2, 3-3 18p;  
4-7, 6-8 22p; 10-28 16V : 2-2, 3-3 16p; 4-7, 6-8, 10 18p; 15 30p;  
22 30p; 33 47, 40p; 100 75p;  
16V : 22-24 33p; 33, 47 55p; 100 55p.

## MYLAR FILM CAPACITORS

100V : 1nF, 2n, 4n, 4n7, 10 8p;  
15nF, 22n, 30n, 40n, 47n 7p; 56n,  
100n, 200n 8p. 470n/50V 12p.

## MINIATURE TYPE TRIMMERS

4-8p, 2-10p 22p; 2-25p, 5-65p;  
30p; 10-88p 35p.

## COMPRESSION TRIMMERS

3-40p, 10-80p 20p; 20-250p 28p;  
100-580p 39p; 400-1250p 48p.

## POLYSTYRENE CAPACITORS

10p to 1nF 8p; 1.5n to 12n 10p.

## SILVER MICA : 2pF, 3.3, 4, 7,

8, 8-2, 10, 12, 15, 18, 22, 27, 33,  
39, 47, 50, 56, 68, 75, 82, 85, 100,  
120, 150, 180 15p; 200, 220, 250,  
270, 300, 330, 360, 390, 470, 600,  
800, 820 21p. 1000, 1200, 1800,  
2000 30p. 3300, 4700 60p.

## CERAMIC CAPACITORS : 50V

0.5pF to 10nF 4p; 22n to 100n 7p.

## EURO BREADBOARD £5.20.

## VOLTAGE REGULATORS\*

1A TO3 -4v -ve  
6V 7805 145p 7905 220p  
12V 7812 145p 7912 220p  
15V 7815 145p 7915 220p  
18V 7818 145p

## TO202 Plastic Casing

8V 7805 45p 7905 55p  
12V 7812 50p 7912 55p  
15V 7815 50p 7915 55p  
18V 7818 50p 7918 55p  
24V 7824 50p 7924 55p

## 100mA TO202 Plastic Casing

5V 78L05 30p 79L05 80p  
6V 78L06 30p —  
8V 78L2 30p —  
12V 78L12 30p 79L12 60p  
15V 78L15 30p 79L15 60p

## 723 38 LM317T 125 78H05+5V/5A

CA3085 85 LM323K 500 350  
LM300H 170 TAA50 50 78HG5A +5V  
LM305H 140 TAA50 70 +25V 599  
LM309H 135 TAA50 75 78HG5A -2.25  
LM317H 350 TDA1412 150 10 -24V 785p

## JACKSONS VARIABLE CAPACITORS

Dilicon 0.2 365pF with  
100/300pF 220p slow motion  
500pF 250p Drive 435p  
6.1 Ball Drive 00 208/176 435p  
4511/DAF 185p motion drive 435p  
Dial Drive 4103 185p motion drive 435p  
8/38 1 775p 10 151p  
Drum 54mm 50p 100, 150p 160p  
0.1-365pF 350p 1.3 x 310pF 725p  
00 0.3 x 25pF 575p

## DENCO COILS

RDT2 145p  
'DP' VALVE TYPE RFTC 5 140p  
Range 1 to 5L RFTC 7(19HM) 160p  
Rd, YL, Wht.122p IFT 13: 14; 15;  
6-7 B.Y.R. 1100 16: 17; 180p  
1.5 Green 150p IFT 18/1-6 135p  
'T' 1 to 5 Bl., YL, IFT 18/465 152p  
Rd, Wht., 150p TOC 1 125p  
B9A Valve Holder MW/LWF SFR154p  
42p MW/LWF SFR154p

## VEROBOARDS 1"

COPPER clad plain clad boards  
2x 8" 73p 52p Fibreglass  
2x 5" 83p — 6" 90p  
3x 3" 83p — 6" 12" 150p  
3x 5" 85p 70p S.R.B.P.  
3x 17" 326p 21lp 9.5 x 8 95p  
41x 17" 426p 100 pins 50p  
Pkt. of 100 pins 50p  
Ferric Chloride 1lb.  
Spot Face Cutter 118p  
Pin Insertion Tool 182p  
Dalo Pen 90p

## POTENTIOMETERS : (ROTARY)

Carbon Track, 0.25W Log & 0.5W

Linear Value.

500Ω, 1k & 2k (Lin. only) Single 29p

BK-2 M-Q single gang 26p

BK-2 M-Q single with DP switch 76p

BK-2 M-Q double gang 86p

## SLIDER POTENTIOMETER

0-25W Log and linear values 60mm

8K-500KΩ single gang 70p

10K-500KΩ dual gang 110p

Self Stick Graduated Bezels 40p

## PRESET POTENTIOMETERS

Varietal & Horizontal

0-1W 50Ω 54MΩ Miniature, 7p

0-25W 100Ω-33MΩ Horiz. 10p

0-25W 200Ω-47MΩ Vert 10p

## RESISTORS : Carbon Film, High Stability, Low Noise, Miniature

Tolerance 5%

Range Val. 1-99 100+

1W 202-4M E24 2p 1p

1W 202-4M E12 2p 1p

1W 212-10M E12 5p 4p

2% Metal Film 13Ω-1M 6p 6p

1% Metal Film 5Ω-1M 6p 6p

each value applies to Resistors of

each value not mixed.

## TGS 812 or 813 gas and smoke detector \$75p. Socket for above 40p.

## BLIDE 250V : TOGGLE 2A 250V

SPST 33p 1A DPDT 44p

SPDT 1A DPDT 13p

## PUSH BUTTON

Latching or Momentary

SPST C/Over 9p

DPDT 6tang 75p

DPDT c/oft 88p

DPDT C/Over 145p

## SWITCHES Miniature Non-Locking

Push to Make 16p Push to Break 20p

## ROCKER : SPST On/off 10A 250V

Lights when on: 10A 240V 85p

## ROTARY : (ADJUSTABLE STOP) 1 pole/

2-12 way 2p/2-W, 3p/2-W, 4p/2-W, 45p

## ROTARY : Mains 250V AC, 4 Amp 80p

## DIL SOCKETS (Low Profile - Texas)

8 pin 8p; 14 pin 10p; 16 pin 10p; 18 pin 16p;

20 pin 22p; 24 pin 25p; 28 pin 28p; 40 pin 30p.

## DIODES

## ZENERS

Range 2V to 7V

39V 400W

BY126 12 8p each

BY127 12 Range 3V to 3.3V. 1-3W

CROSS3 250 15 15p each

OAB 40 15p each

OAB47 12 15p each

OAB70 12 15p each

OAB79 15 15p each

OAB81 15 15p each

OAB90 8 15p each

OAB91 8 15p each

OAB95 8 15p each

OAB200 8 15p each

OAB202 8 15p each

OAB204 8 15p each

OAB370 8 15p each

# GREENWELD

443D MILLBROOK ROAD, SOUTHAMPTON SO1 0HX  
All prices include VAT—just add 50p post. Tel (0703) 772501  
Goods normally despatched by return of post

## AMAZING! COMPUTER GAMES PCB's FOR PEANUTS!!

A bulk purchase of PCB's from several well known computer games including Battleship, Simon, Logic 5 and Starbird enables us to offer these at incredibly low prices:

### 'STARBIRD'

Gives realistic engine sounds and flashing laser blasts—accelerating engine noise when module is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt clip. (needs PP3). PCB size 130 x 80mm. Only £1.95

### 'SIMON'

The object of this game is to repeat correctly longer and longer sequence of signals in 3 different games. (Instructions included) PCB contains chips, switches, lampholders and lamps, and is tested working, complete with speaker. Needs 2 x HP11. PCB size 130 x 130mm Only £3.95.

### 'COMPUTER BATTLESHIPS'

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the solid circuit and sell the board for its component value only. (PCB may be chipped or cracked). SN76477 sound IC; TMS1000 u-processor, batt clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra.

### LOGIC 5 PANEL

Tested Logic 5 now sold out—but we have some PCB's with 10 LED's and chip on, but no keyboard. Not tested. 50p.

### 'MICROVISION'

**Cartridges**  
These are a small PCB with a micro-processor chip, designed to plug in to the microvision console. Only snag is, we don't have any consoles!! However, they can be used as an oscillator with 4 different freq. outputs simply by connecting a battery and speaker. Tested and working (and an osc) with pin out data. PCB size 72 x 60 mm. only 25p each!

### RELAY/TRIAC PANEL

Z537 PCB 100 x 75mm containing a wealth of components: 2 x 12V DPCO min. relay, 10 x 47μF 10V tantal. SC1446 10A 500V triac, C122D 8A 400V SCR 555 timer, 10 x 1N4001 diodes, 2N5001 SCR, 2 x 3mm LED's 3 x 9N3704, R's & C's—Amazing value—if bought separately, parts would cost around £81!. Our price for the panel, just £2.95.

### 200 ELECTROLYTICS £4.00

K534 Large variety of values/voltages, mostly croppped leads for PCB mntg. 1-1000μF, 10-63V. All new full spec components, not chuck-outs!! 200 £4.00 £17.50

### COMPONENT PACKS

K503 150 wirewound resistors from 1W to 12W, with a good range of values, £1.75. K505 20 assorted potentiometers, all types including single, ganged, rotary and slider, £1.75.

K511 200 small value poly, mica, ceramic caps from a few pF to .02μF. Excellent variety, £1.25.

K514 100 silver mica caps from 5pF to a few thousand pF. Tolerances from 1% to 10%, £2.00.

K521 Switch pack—20 different, rocker, slide, rotary, toggle, push, micro, etc. Only £2.00.

K521 Heatshrink pack—5 diff. sizes, each 200mm. 30p.

### 1000 RESISTORS £2.50

We've just purchased another 5 million performed resistors, and can make a similar offer to that made two years ago, at the same prices!! K503—1000 mixed + -W 5% carbon film resistors, preformed for PCB mntg. Enormous range of preferred values. 1000 for £2.50; 5000 £16; 20k £36.

### PANELS

Z521 Panel with 1623A (2N3442) on small heat sink, 2N2223 dual transistor, 2 BC108, diodes, caps, resistors, etc. 30p.

Z527 Reed relay panel—contains 2 x 8V reeds, 8 x 250mA or 2520, 8 x 400V rect. & Rs. 30p.

Z528 Pack of ex-computer panels containing 7 series ICs. Lots of different gates and counter logic. All ICs are marked with type no., or code for which an identification sheet is supplied. 20 ICs £1.00; 100 ICs £4.00.

A504 Black case 50 x 50 x 78mm with octal base. PCB inside has 24V red relay, 200V 7A SCR, 4 x 5A 200V rect. etc. 30p.

### SWITCH BARGAIN

Push-on, push-off "table lamp" type, rated 2A 250V ac. 10p each. 15 for £1.00, 50 for £5.

## TEACH-IN 82

Full set of parts as specified by "EE". All new goods, despatched by return of post.

\* All parts for the "MINILAB" only £17.50 + 50p.

\* All components for first 6 parts of "TEACH-IN '82" £7.50 + 50p post.

BUY ALL THREE SETS FOR £29 inc post.

FREE component identification Chart !!

FREE piece of Veroboard !!

Reprints of articles: 30p per part + 30p for Tutor Deck Inc. (only supplied with orders for Teach-in).

### CAPACITOR BARGAINS

2200μF 100V cans 77 x 35mm dia. 75p.

100μF 10V axial 5p; 100 μF 2.2-30.

100μF 10V + 100μF 275V 102 x 44mm dia.

75p; 10 x 10μF 200V 350V, 100 + 100μF 300V can 75 x 44mm dia 40p; 10/£3;

100/£39 100μF 25V Axial £3/100,

0-33μF 50V red, £1.50/100, £12/1000. elec

22μF 50V red £3/100, £24/1000.

### 1W AMP PANELS

A011 Compact audio amp intended for record player on panel 98 x 65mm including vol. control and switch, complete with knobs. Apart from amp circuitry built around LM380A or TBA820M, there is a speed control circuit using 5 transistors. 9V operation, connexion data supplied. ONLY £1.50.

### TOROIDAL TRANSFORMER

110mm dia. x 40mm deep, 110/240V pri., Sec. 18V 4A, 0.3V 1A, 240V 0.3A. Ideal for scopes, monitors, VDU's, etc. Reduced to £1.95.

### OP-AMP PSU KIT

A198 All parts + Instructions to make a 50mA +15, 0, -15V supply from mains input. ONLY £1.95.

### COPPER CLAD BOARD


K522 All pieces too small for our etching kits. Mostly double sided fibreglass. 250gm (approx. 110 sq ins) for just £1.00.

### MIXED LED PACK

All new full spec by Micro, Fairchild, etc. Red, Yellow, Green, Amber, Clear, 3mm & 5mm. Pack of 50 assets £3.95; 250 £15.
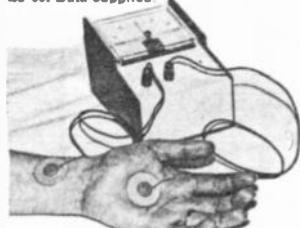
### FILAMENT DISPLAYS

Z563 7 seg display 12.5mm high. Ideal for TTL operation, taking 5V 8mA per seg. Std 14 DIL package. ONLY £1 each. 4 for £3.00. Data supplied.



### LIE DETECTOR

Not a toy, this precision instrument was originally part of an "Open University" course, used to measure a change in emotional balance, or as a lie detector. Full details of how to use it are given, and a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 4V batteries. Overall size 155 x 100 x 100mm. ONLY £7.95—worth that for the case and meter alone!!

### CHEAP CHIPS

76477 Sound IC £1.25.  
2102A RAM 8 for £3.  
MK4027 shift reg. 6 for £6.  
uAT79MG + voltrig £1.00.  
uAT79MG — voltrig £1.20.



### ELECTRO-DIAL

Electrical combination lock—for maximum security—pick proof, 1 million combinations! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid. Overall dia. 65mm x 60mm deep. ONLY £9.95.

Also available without combination—only £3.95.



**METERS: 110 x 82 x 35mm**  
**30μA, 50μA, 100μA. £5.90.**

**Post 50p.**

**METERS: 45 x 50 x 34mm**  
**50μA, 100μA, 1mA, 5mA, 10mA, 25v, 1A, 2A, 5A**

**5A. 25V £2.90. Post 30p.**

**METERS: 60 x 47 x 33mm**  
**50μA, 100μA, 1mA, 5mA, 10mA, 100mA, 1A, 2A, 25v, 50v, 50-0.5μA, 100-0-100μA. £4.76.**

**VU meters. £5.32.**

**Post on above meters 30p.**

**Silicone grease 50g £1.32 Post 14p.**

### MULTI-METER

**7 N 360 T R**  
**20,000 ohm/volt**  
**DC Volts: 0-1, 0-5, 2.5, 10-150—**

**250-1,000v.**  
**AC Volts: 10-50, 250-1,000**

**RESISTANCE RANGES**

**X1, X10, X1K,**

**X10K**

**£14.10**

**P.&P. 87p**



### TRANSFORMERS

**240v Primary**

3-0-3v	100mA	82p
6-0-6v	100mA	87p
6-0-6v	250mA	£1.22

12-0-12v	50mA	92p
12-0-12v	100mA	£1.15

**Post on above transformers 48p.**

9-0-9v	1A	£1.90
12-0-12v	1A	£2.40
15-0-15c	1A	£2.00
6-3v	1½A	£1.90
6-0-6v	1½A	£2.10

**Post on above transformers 87p.**

All above prices include V.A.T. Send 80p for new 1982 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

All goods despatched within 3 days from receipt of the order.

**M. DZIUBAS**  
**158 Bradshawgate, Bolton**  
**Lancs. BL2 1BA**

## TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success; knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

### City and Guilds Certificates:

Telecommunications Technicians

Radio, TV, Electronics Technicians

Technical Communications

Radio Servicing Theory

Radio Amateurs

Electrical Installation Work

MPT Radio Communications Certificate

### Diploma Courses:

Colour TV Servicing

Electronic Engineering and Maintenance

Computer Engineering and Programming

Radio, TV, Audio Engineering and Servicing

Electrical Engineering, Installation

and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

**ICS To: International Correspondence Schools**

Dept 268T Intertex House, London SW8 4UJ or telephone 622 9911

Subject of Interest .....

Name .....

Address .....

Tel: ..... Age: .....

# Rapid Electronics

Tel: 0322 863494  
Hillcroft House  
Station Road  
Eynsford Kent DA4 0EJ



LINEAR	CA3161E	140	LM377	150	LM3900	50	NE566	150	TLO71	45	
	CA3162E	450	★ LM380	65	LM3909	70	★ NE567	100	TLO72	75	
★ 709	25	LM3189E	290	★ LM381	100	LM3911	120	NE571	425	TLO81	30
★ 741	14	ICL7106	790	★ LM382	120	★ LM3914	200	RC4136	90	TLO82	70
748	35	ICL8038	320	★ LM386	65	★ LM3915	200	SN76018	150	TLO83	80
AY-3-1270	840	ICM7555	80	LM387	100	LM13600	120	★ SN76477	250	★ XR2206	300
AY-3-8910	700	★ LF351	40	LM393	100	MC1310	150	TBA800	80	ZN414	100
★ AY-3-8912	625	LF356	85	★ LM709	25	MCS302	150	TBA810	95	ZN423	185
CA3046	64	LM110	395	LM710	50	MC3340	135	TBA820	80	ZN424	135
★ CA3080	65	★ LM301A	25	LM725	350	NE515	270	TA0450	290	ZN425E	390
CA3089	215	LM311	70	LM733	75	NE529	225	TCA940	170	ZN426E	330
CA3090AQ	215	LM318	85	★ LM741	14	NE531	150	TD1004	300	ZN427E	650
CA3130E	375	★ LM339	50	LM747	75	NE544	165	TD1008	320	ZN428E	480
CA3140E	45	LM438	90	LM748	35	★ NE555	16	TD1010	225	ZN1034E	200
CA3160E	100	LM558	100	LM1458	40	NE556	45	TD1022	560		
		LM2917	200	LM2917	120	TD1024	125				

CMOS	★ 4017	43	4035	285	4055	115	4082	20	4502	70	4529	150	
	4000	14	4019	35	4040	295	4059	480	4085	65	4503	95	
★ 4001	12	★ 4020	55	4041	55	4060	85	4086	65	4507	38	4534	495
4002	14	4021	85	4042	55	4066	35	★ 4093	33	4510	65	4543	110
4005	65	4022	70	4043	60	4067	395	4094	14	★ 4511	50	4549	380
4007	17	4023	18	4044	65	★ 4068	15	4095	60	4512	70	4553	295
4008	58	4024	40	4046	70	4069	18	4097	340	4514	180	4555	45
4009	30	4025	18	4047	70	4070	18	4098	65	4515	180	4556	48
4010	35	★ 4026	94	4048	55	4071	18	4099	65	4516	75	4559	390
★ 4011	13	4027	30	★ 4049	28	4072	18	40106	50	★ 4518	45	4560	180
4012	17	4028	55	4050	28	4073	20	40109	60	4520	70	4584	45
★ 4013	22	4029	75	4051	60	4075	20	40183	60	4521	200	4585	99
4014	60	4030	35	4052	70	4076	60	40173	100	4526	80	4724	140
4015	60	4031	170	4053	60	4077	25	40175	100	4527	90		
★ 4016	22	4034	170	4054	110	4081	18	★ 4528	75				

TTL	7413	24	7442	40	7480	45	74107	30	74155	60	74177	75	
	7414	35	7444	85	7482	70	74109	32	74156	60	74179	85	
7400	11	7416	25	7446	60	7483	58	74121	28	74157	43	74180	65
7401	11	7417	25	7447	48	7485	75	74122	45	74160	60	74181	135
7402	12	7420	15	7448	50	7486	25	74123	40	74181	60	74182	75
7403	14	7421	20	7450	16	7489	180	74125	40	74162	60	74190	70
7404	14	7422	20	7451	16	7490	28	74126	40	74163	60	74191	70
7405	17	7427	20	7453	16	7491	45	74132	40	74164	60	74192	70
7406	26	7428	20	7454	16	7492	40	74141	65	74165	60	74193	65
7407	18	7433	25	7472	25	7494	35	74147	100	74170	165	74195	63
7409	18	7433	27	7473	28	7495	50	74148	75	74173	60	74196	63
7410	14	7437	27	7474	25	7496	45	74150	75	74174	65	74197	63
7411	20	7438	27	7475	38	7497	120	74153	45	74175	70	74198	95
7412	20	7440	17	7476	30	74100	80	74154	75	74176	55	74199	95

LS TTL	LS21	15	LS22	20	LS125	30	LS181	42	LS221	60	LS365	38
	LS22	18	LS78	30	LS126	40	LS182	42	LS220	60	LS366	38
LS00	13	LS26	18	LS83	50	LS132	45	LS241	50	LS367	36	
LS01	14	LS27	15	LS85	70	LS138	30	LS164	50	LS368	50	
LS02	14	LS30	18	LS86	25	LS138	35	LS165	60	LS243	50	
LS03	14	LS32	18	LS92	35	LS145	75	LS170	120	LS373	80	
LS04	14	LS37	18	LS93	35	LS147	180	LS172	125	LS375	50	
LS05	18	LS38	18	LS94	35	LS148	180	LS173	70	LS377	90	
LS08	18	LS39	18	LS95	40	LS149	180	LS174	120	LS378	70	
LS09	18	LS40	18	LS96	110	LS150	40	LS175	60	LS387	60	
LS10	16	LS42	18	LS97	45	LS151	45	LS176	60	LS388	75	
LS11	16	LS47	40	LS107	45	LS153	45	LS190	55	LS395	75	
LS12	15	LS48	80	LS109	30	LS154	120	LS191	55	LS399	220	
LS13	25	LS55	30	LS113	50	LS156	45	LS193	60	LS379	90	
LS14	40	LS73	25	LS114	30	LS157	50	LS195	50	LS670	175	
LS15	15	LS74	25	LS122	42	LS158	36	LS196	60	LS823	45	
LS20	15	LS75	25	LS123	55	LS160	60	LS197	60	LS353	100	

TRANSISTORS	BC549	10	BFX29	25	TIP29C	60	VN88AF	95	N20305	23	
	AC125	35	BC17	10	BFX84	25	TIP30A	15	★ VN107	95	
AC126	25	BC158	10	BFX70	19	BFX85	25	TIP30A	8	N20305	55
AC127	25	★ BC158	8	BCY71	16	BFX86	28	TIP30B	10	N20305	50
AC128	22	BC169C	10	BCY72	25	BFX87	25	TIP30C	60	★ VN239	15
AC129	22	BC169C	10	BCY73	25	BFX88	30	TIP31A	16	N20305	10
AC130	22	BC170	8	BCY74	32	BFX89	35	TIP31B	45	★ VN239	15
AC131	22	BC170	8	BCY75	32	BFX90	35	TIP31C	55	N20305	10
AD142	120	BC171	10	BCY76	40	BFX91	35	TIP32A	45	★ VN239	15
AD144	80	BC172	15	BCY77	40	BFX92	35	TIP32B	55	N20305	10
AD161	40	BC177	18	BCY78	40	BFX93	35	TIP32C	60	★ VN239	15
AD162	40	BC178	18	BCY79	40	BFX94	35	TIP33A	60	N20305	10
AD163	40	BC179	18	BCY79	40	BFX95	35	TIP33B	60	★ VN239	15
AD164	22	BC212	10	BCY80	35	BFX96	35	TIP34C	85	★ VN239	15
AD165	22	BC213	10	BCY81	35	BFX97	35	TIP34D	85	★ VN239	15
BC109	9	BC214	12	BCY82	35	BFX98	35	TIP121	90	★ VN2219	25
BC109C	9	★ BC214	8	BCY83	35	BFX99	35	TIP122	90	N20406	10
BC114	22	BC218	10	BCY84	35	BFX100	35	TIP142	100	N20406	10
BC115	22	BC218	10	BCY85	35	BFX101	35	TIP143	100	N20406	10
BC117	22	BC208	15	BCY86	35	BFX102	35	TIP295	110	N20406	10
BC118	22	BC208	15	BCY87	35	BFX103	35	TIP295	110	N20406	10
BC119	15	BC208	15	BCY88	35	BFX104	35	TIP295	110	N20406	10
BC137	40	BC208	14	★ BC4481B	18	BPS55	20	TIS42	40	N20549	30
BC139	40	BC337	14	BC4481B	18	BPS55	20	TIS43	40	N20549	30
BC140	30	BC338	14	BC4481B	18	BPS55	20	TIS44	40	N20549	30
BC141	30	BC477	32	BC4481B	18	BPS56	30	TIS45	40	N20549	30
BC142	25	BC478	32	BC4481B	18	BPS56	30	TIS46	40	N20549	30
BC143	25	BC479	35	BC4481B	18	BPS56	30	TIS47	40	N20549	30
BC144	8	BC517	40	BC4481B	18	BPS57	30	TIS48	40	N20549	30
BC145	8	★ BC547	7	BFR40	23	TIP29A	40	VN46A7	75	N20297	25
BC146	8	★ BC547	10	BFR80	25						

# Into the 80's and beyond

Learn about the op-amp

as an oscillator  
as an inverting and a  
non-inverting amplifier  
make astable, monostable and  
bistable circuits

Learn about the behaviour of a  
transistor

as an amplifier or as a switch or as an  
emitter follower

Learn how to use a milliammeter and  
make voltmeters, electronic  
voltmeters and electronic ohmmeters

Carry out experiments measuring  
the gain of the op-amp and transistor  
and study their characteristics

The Radionic 140 provides the  
perfect introduction to electronics.

A fully illustrated handbook together with  
140 circuit diagrams will guide you from basic  
circuits onto more advanced circuitry.

## The 140 experiments include :

- Light operated switch
- Audible burglar alarm
- Radio receiver with tuning Indicator
- Time delay circuit
- Police car siren
- Electronic voltmeter
- How the transistor can be used in logic circuits
- The charging of a capacitor
- Investigating a square wave generator
- Differential temperature switch

**Radionic 140 . . . . £47.75** Please allow up to 14 days delivery

Price includes VAT and p. and p. order direct from

**Radionic Products Ltd.,  
Waverley Road, Yate, Bristol, BS17 5RB.**

## E.E. PROJECT KITS

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project—you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- CAR OVERHEATING ALARM.** Feb. 82. £8.99.
- M.W. RADIO.** Feb. 82. £25.92.  
Mono headphones extra £2.98.
- CINE INTERVAL TIMER + FRAME COUNTER.** Feb. 82. less remote option £17.61.
- STEREO RECORD PLAYER.** Feb. 82. less deck, cartridge, speakers & cabinets. £20.78.
- SIMPLE STABILISED POWER SUPPLY.** Jan. 82. £22.98.
- MINIEGG TIMER.** Jan. 82. £3.69.
- SIREN MODULE.** Jan. 82. less speaker. £5.21.
- MODEL TRAIN CHUFFER.** Jan. 82. £7.73.
- PEGBOARD GAME.** Dec. 81. less nails. £6.58.
- SQUARE SIX.** Dec. 81. £4.40.
- RACE TRACK SPEEDO.** Dec. 81. £25.40.
- GUITAR ADAPTOR.** Dec. 81. £3.52.
- REACTION METER.** Dec. 81. £18.41.
- HEADS OR TAILS GAME.** Dec. 81. £4.82.
- ELECTRONIC IGNITION.** Nov. 81. £24.33.
- SIMPLE INFRA RED REMOTE CONTROL.** Nov. 81. £15.99.
- LOUDHAILER.** Nov. 81. less handle. £11.93.
- HORN SPEAKER.** £6.75 extra.
- PRESSURE MAT TRIGGER ALARM.** Nov. 81. £5.86 less mats.
- EXPERIMENTER CRYSTAL SET.** Nov. 81. Less aerial. £5.60.  
Headphones. £2.98 extra.
- CAPACITANCE METER.** Oct. 81. £21.98.
- SUSTAIN UNIT.** Oct. 81. £11.93.
- 'POPULAR DESIGNS'.** Oct. 81.
- SNAP INDICATOR.** £3.18.
- DAMP LOCATOR.** £1.51.
- TAPE NOISE LIMITOR.** £4.28.
- HEADS AND TAILS GAME.** £2.36.
- CONTINUITY TESTER.** £3.70.
- PHOTO FLASH SLAVE.** £3.24.
- FUZZ BOX.** £8.82.
- OPTO ALARM.** £6.34.
- SOIL MOISTURE UNIT.** £5.43.
- ICE ALARM.** £7.38.
- MODEL RAILWAY SPEED CONTROLLER.** Sept. 81. £13.46.
- 0-12V POWER SUPPLY.** Sept. 81. £18.84.
- CMOS CAR SECURITY ALARM.** Sept. 81. £8.49.
- CMOS DIE.** Sept. 81. £7.47.
- LED SANDGLASS.** Aug. 81. £7.98.
- WHEEL OF FORTUNE.** Aug. 81. less wire, panel and case. £39.98.
- CMOS METRONOME.** Aug. 81. £7.70.
- COMBINATION LOCK.** July 81. Less case. £18.30.
- BURGLAR ALARM SYSTEM.** June 81. less bell, loop & Mic's. £38.30.
- TAPE AUTO START.** June 81. £11.96.
- TREMOLO.** June 81 less case. £10.48.
- LOOP AERIAL CRYSTAL SET.** June 81. £5.47.
- LIGHTS REMINDER AND IGNITION LOCATOR E.E.** May 81. £5.29.
- SOIL MOISTURE INDICATOR E.E.** May 81. £3.83.
- T.V. INTERFERENCE FILTERS E.E.** May 81. LOW PASS less tinplate £2.88.  
HIGH PASS £1.56.
- GUITAR HEADPHONE AMPLIFIER E.E.** May 81. £3.96.
- PHONE BELL REPEATER / BABY ALARM E.E.** May 81. £5.28.
- DIGITAL RULE (ultrasonic)** April 81. £30.20.
- INTERCOM.** April 81. £20.78.
- SIMPLE TRANSISTOR & DIODE TESTERS.** Mar. 81. Ohmeter version £1.89. Led version £2.56.
- MINI SIREN.** Mar. 81. £7.52.
- LED DICE.** Mar. 81. £7.89.
- LED FLASHER.** Mar. 81. £4.01.
- MODULATED TONE DOORBELL.** Mar. 81. £6.21.
- BENCH POWER SUPPLY.** Mar. 81. £49.98.
- TREBLE BOOST.** Mar. 81. £8.84.
- CAR ACTUATED DRIVEWAY LIGHT.** Feb. 81 less socket. £23.96.
- THREE CHANNEL STEREO MIXER.** Feb. 81. £17.47.
- SIGNAL TRACER.** Feb. 81. £7.64 less probe.
- FOUR BAND RADIO.** Feb. 81. £39.98.
- NI-Cd BATTERY CHARGER.** Feb. 81. £12.72.
- ULTRASONIC INTRUDER DETECTOR.** Jan. 81. less case. £49.98.
- AUTO SLIDE CHANGER.** Jan. 81. £9.28.
- LOGIC PULSE GENERATOR.** Jan. 81. £7.48.
- 2 NOTE DOOR CHIME.** Dec. 80. £8.65.
- LIVE WIRE GAME.** Dec. 80. £10.94.
- GUITAR PRACTICE AMPLIFIER.** Nov. 80. £11.99 less case. Standard case £3.88. High quality case £8.33.
- \_SOUND TO LIGHT.** Nov. 80. 3 channel. £19.95.
- TRANSISTOR TESTER.** Nov. 80. £10.87 inc. test leads.
- AUDIO EFFECTS UNIT FOR WEIRD SOUNDS.** Oct. 80. £12.26.
- PHONE CALL CHARGE JOGGER.** Oct. 80. £6.80.
- BICYCLE ALARM.** Oct. 80. £9.68 less mounting brackets.
- IRON HEAT CONTROL.** Oct. 80. £5.48.
- BEAMING RADIO.** Sept. 80. £17.57.
- TTL LOGIC PROBE.** Sept. 80. £4.85.
- COURTESY LIGHT DELAY.** June 80. £6.89.
- SIGNAL TRACER.** June 80. £5.98.
- ZENER DIODE TESTER.** June 80. £6.23.
- 4 STATION RADIO.** May 80. £15.33 less case.
- LIGHTS WARNING SYSTEM.** May 80. £4.38.
- BATTERY VOLTAGE MONITOR.** May 80. £4.83.
- CABLE & PIPE LOCATOR.** Mar. 80. £3.85 less coil former.
- KITCHEN TIMER.** Mar. 80. £13.70.
- STEREO HEADPHONE AMPLIFIER.** Mar. 80. £16.97.
- MICRO MUSIC BOX.** Feb. 80. £15.20.
- Grey Case £3.99 extra.**
- SIMPLE SHORT WAVE RECEIVER.** Feb. 80. £24.17. Headphones £2.98.
- SLIDE/TAPE SYNCHRONISER.** Feb. 80. £11.30.
- MORSE PRACTICE OSCILLATOR.** Feb. 80. £4.32.
- SPRING LINE REVERB. UNIT.** Jan. 80. £24.17.
- UNIBOARD BURGLAR ALARM.** Dec. 79. £5.64.
- BABY ALARM.** Nov. 79. £8.98.
- ONE ARMED BANDIT.** Oct. 79. £24.80.
- HIGH IMPEDANCE VOLTMETER.** Oct. 79. £17.45.
- CHASER LIGHTS.** Sept. 79. £21.97.
- SIMPLE TRANSISTOR TESTER.** Sept. 79. £6.88.
- ELECTRONIC TUNING FORK.** Aug. 79. £5.99. Suitable microphone & plug £1.79 extra.
- DARKROOM TIMER.** July 79. £2.71.
- ELECTRONIC CANARY.** June 79. £5.48.
- TRANSISTOR TESTER.** April 79. £4.55.
- TOUCH BLEEPER.** April 79. £3.87.
- ONE TRANSISTOR RADIO.** Mar. 79. £2.84 less case £1.62.
- MIC. AMP.** Dec. 78. £3.08.
- AUDIBLE FLASHER.** Dec. 78. £1.33.
- VEHICLE IMMOBILISER.** Inc. PCB. Dec. 78. £8.31.
- FUSE CHECKER.** Oct. 78. £2.18.
- TREASURE HUNTER.** Oct. 78. £19.64 less handle & coil former.
- \_SOUND TO LIGHT.** Sept. 78. £7.67.
- CAR BATTERY STATE INDICATOR.** Sept. 78. Less case. £1.96.
- R.F. SIGNAL GENERATOR.** Sept. 78. £24.90.
- SLAVE FLASH.** Aug. 78. £3.52 less SK1.
- IN SITU TRANSISTOR TESTER.** June 78. £6.33.
- POCKET TIMER.** April 78. £3.27.
- WEIRD SOUND EFFECTS GENERATOR.** Mar. 78. £5.28.
- AUDIO VISUAL METRONOME.** Jan. 78. £5.63.
- ELECTRONIC TOUCH SWITCH.** Jan. 78. £2.54 less case.
- RADIAL DIODE CHECK.** Jan. 78. £2.57.
- AUTOMATIC PHASE BOX.** Dec. 77. £11.50 inc. p.c.b.
- PHONE/DOORBELL REPEATER.** July 77. £6.98.
- ELECTRONIC DICE.** Mar. 77. £5.31.

## GUITAR TUNER—SUPERB PROJECT

Featured by us in E.T.I. Jan. 82. Highly stable internal reference. Microprocessor generates fundamental frequencies. Special synchronous rectifier circuit compares input frequency from guitar pickup or microphone with internally generated pitch. Beat frequency is displayed on a large moving coil panel meter. Also operates with bass guitar, or acoustic instruments via a high impedance microphone.

Complete kit includes smart case, PCBs, panel meter etc. £20.98. Reprint extra 45p. Available separately 45p + 40p p. & p.

I.C.s  
TRANSISTORS  
CAPACITORS

TOOLS  
RESISTORS  
HARDWARE

CASES  
KITS

# MAGENTA ELECTRONICS LTD.

C106D	58p	2N6457	58p	BFY51	24p
TIC46	48p	2N5484	63p	BFY52	23p
OA47	11p	40673	98p	BFX88	32p
OA90	9p	AC128	29p	BRY39	48p
OA202	16p	AC141	38p	MPSA65	1£-18
W/005	33p	AC142	39p	RPY58A	£1-18
W/00	47p	AC176	37p	TIP31A	£1-12
Z5J	£2-92	BC182	11p	TIP32A	83p
IN4001	51p	BC182L	11p	TIP34A	94p
IN4005	6p	BC183	11p	TIP34A	99p
IN4148	5p	BC184	11p	TIP121	£1-12
IN5404	18p	BC184L	11p	TIP2955	69p
IN5408	19p	BC212	11p	TIP3055	69p
BF244	87p	BC212L	11p	TIS43	38p
MPF102	69p	BC213	11p	TPSA13	35p
TIS58A	57p	BC214	11p	SN3053	25p
VN67AF	£1-21	BC214L	11p	2N3055	59p
2N3819	28p	BD131	48p	2N3702	11p
2N3820	78p	BFY50	25p	2N3704	11p

J.W. CARBON FILM RESISTORS  
E12 SERIES. 1R-10M ..... 1p each  
MIN. HORIZ. PRESETS. 100R-4M7 ..... 12p each  
MIDGET POTS. LINEAR. 470R-4M7 ..... 37p each  
LOG. 4K7-2M3 ..... 38p each  
SWITCHED POTS. 4K7-1M. LIN. 75p. LOG 76p

POLYESTER (C280) CAPACITORS. 250V  
10nF; 15nF; 22nF; 33nF; 47nF; 7p each; 68nF;  
100nF 8p; 150nF; 220nF 12p; 330nF 15p; 470nF 20p;  
680nF 28p. 1μF 33p. 1.5μF 49p. 2.2μF 65p.

SUB MINIATURE PLATE CERAMICS. 63V  
Values in pF: 2-2; 3-3; 4-7; 5-6; 6-8; 8-2; 10; 15;  
22; 33; 47 & 56p 7p each. 68pF; 100pF 7p each.  
150pF; 220pF; 330pF 1p each. 390pF; 470pF;  
1000pF 5p each. 2200pF 6p each. 3300pF; 4700pF  
7p each. 10nF 13p. 100nF 22p. 47nF 14p.

ELECTROLYTIC CAPACITORS  
AXIAL Leads: 1μF/18V 11p; 1μF/33V, 1μF/100V  
12p; 2μF/33V, 3-3μF/33V, 4-7μF/33V 12p; 10μF/  
16V 11p; 10μF/25V 10p; 10μF/33V 12p; 22μF/10V 29p/  
25V 12p; 22μF/25V 15p; 33μF/40V 47μF/25V 12p;  
47μF/40V 15p; 47μF/33V 18p; 100μF/16V 12p;  
100μF/25V 15p; 100μF/40V 18p; 100μF/33V 29p;  
220μF/10V 15p; 220μF/25V 19p; 470μF/16V 12p;  
470μF/25V 36p; 470μF/40V 55p; 680μF/16V 32p;  
1000μF/10V 30p; 1000μF/16V 33p; 1000μF/25V 48p;  
1000μF/40V 58p; 1000μF/33V 79p; 2200μF/10V 39p;  
2200μF/25V 64p; 2200μF/33V 1£-10.

SWITCHES  
MIN. TOGGLE spst 59p; spdt 69p; dpdt 79p.

MIN. PUSH ON. 18p. PUSH OFF. 22p.

FOOTSWITCH & ALT. ACTION spco E1-38;

dpcu E1-88.

ROTARY SWITCHES. 1p 12 way, 2p 6w, 3p 4w,

4p 3w, 5p 2w, 6p 1w, 8p 1w, 10p 1w, 12p 1w.

12V 185R DPCU RELAY ..... £2-98

SPEAKERS. Miniature, 8 ohm ..... 87p

84 ohm 88p ..... 75 ohm 88p

CRYSTAL EARPIECE ..... 65p

MONO HEADPHONES ..... £2-94

TELEPHONE PICK-UP COIL ..... 72p

PP3 Clips ..... 10p

VEROBORD 0'1" COPPER STRIPS ..... £1-20 per 5

10 strips 24 holes ..... 89p

24 strips 50 holes ..... 99p

36 strips 50 holes ..... 99p

PANEL METERS

50μA, 100μA, 1mA, 1A, 25V; 100μA-0-100μA. AU £4-98 each. State value.

LINEAR I.C.s	SN76477	£2-59	
555	28p	TL064	£1-64
556	78p	TL071	47p
741	22p	TL082	74p
CA3130E	98p	TL083	£1-52
CA3140E	52p	TL084	£1-54
HA1388	£3-20	TL430	85p
ICL7611	98p	U237B	£1-69
ACM7555	99p	U267B	£2-20
LF351N	58p	ULN2283	£1-57
LF353N	99p	ZN414	98p
CMOS	£1-14	ZN419CE	£2-21
LF356	£1-15	7400	22p
LM301A	38p	7447	£1-14
LM317K	£3-20	7490	55p
LM336Z	£1-16	7495	80p
LM380N	99p	CMOS	
LM386N	92p	4001	20p
LM387N	£1-10	4011	26p
LM389N	£1-10	4013	32p
LM1830	£1-98	4017	62p
LM3909	82p	4020	65p
LM3914	£2-99	4024	60p
LM3915	£3-95	4069	20p
MC3340	£2-15	4081	20p
NE570N	£4-98	4092	38p
NE571N	£4-84	4017A	£1-20
OM335	£8-98	4522	£1-25

OPTO	BPX25	£2-24
2N5777	.....	90p
OPR12	.....	95p
TIL32	.....	81p
TIL78	.....	74p

LEDS WITH CLIPS	3mm. Red 15p. Green 18p. Yellow 20p.
5mm. Red 18p. Green 28p. Yellow 29p.	

FLASHING LED ..... 78p

RECTANGULAR. Red ..... 24p

MAINS PANEL. Neon ..... 32p

ZENER DIODES. 400mW. ZBY88. Range 2V7 to 33V. 12p each.

I.C. SOCKETS

8 pin ..... 18p

14 pin ..... 17p

16 pin ..... 18p

18 pin ..... 22p

24 pin ..... 48p

28 pin ..... 45p

JACKSON

300pF dielcon ..... 2£-36

500pF dielcon ..... 2£-92

C804 Ver. Capac. 10pF £2-28.

25pF £2-48. 50pF £2-48. 100pF £2-82.

150pF £3-48.

200pF £3-88.

250pF £4-28.

300pF £4-68.

350pF £5-08.

400pF £5-48.

450pF £5-88.

500pF £6-28.

550pF £6-68.

600pF £7-08.

650pF £7-48.

700pF £7-88.

750pF £8-28.

800pF £8-68.

850pF £9-08.

900pF £9-48.

950pF £9-88.

1000pF £10-28.

1050pF £10-68.

1100pF £11-08.

1150pF £11-48.

1200pF £11-88.

1250pF £12-28.

1300pF £12-68.

1350pF £13-08.

1400pF £13-48.

1450pF £13-88.

1500pF £14-28.

1550pF £14-68.

1600pF £15-08.

1650pF £15-48.

1700pF £15-88.

1750pF £16-28.

1800pF £16-68.

1850pF £17-08.

1900pF £17-48.

1950pF £17-88.

2000pF £18-28.

2050pF £18-68.

2100pF £19-08.

2150pF £19-48.

2200pF £19-88.

2250pF £20-28.

2300pF £20-68.

2350pF £21-08.

2400pF £21-48.

2450pF £21-88.

2500pF £22-28.

2550pF £22-68.

2600pF £23-08.

2650pF £23-48.

2700pF £23-88.

2750pF £24-28.

2800pF £24-68.

2850pF £25-08.

2900pF £25-48.

2950pF £25-88.

3000pF £26-28.

3050pF £26-68.

3100pF £27-08.

3150pF £27-48.

3200pF £27-88.

3250pF £28-28.

3300pF £28-68.

3350pF £29-08.

3400pF £29-48.

3450pF £29-88.

3500pF £30-28.

3550pF £30-68.

3600pF £31-08.

3650pF £31-48.

3700pF £31-88.

3750pF £32-28.

3800pF £32-68.

3850pF £33-08.

3900pF £33-48.

3950pF £33-88.

4000pF £34-28.

4050pF £34-68.

4100pF £35-08.

4150pF £35-48.

4200pF £35-88.

4250pF £36-28.

4300pF £36-68.

4350pF £37-08.

4400pF £37-48.

4450pF £37-88.

4500pF £38-28.

4550pF £38-68.

4600pF £39-08.

4650pF £39-48.

4700pF £39-88.

4750pF £40-28.

4800pF £40-68.

4850pF £41-08.

4900pF £41-48.

4950pF £41-88.

5000pF £42-28.

5050pF £42-68.

5100pF £43-08.

5150pF £43-48.

5200pF £43-88.

5250pF £44-28.

5300pF £44-68.

5350pF £45-08.

5400pF £45-48.

5450pF £45-88.

5500pF £46-28.

5550pF £46-68.

5600pF £46-88.

5650pF £46-88.

5700pF £47-28.

5750pF £47-6

# ANNOUNCEMENT ENFIELD ELECTRONICS

We are proud to announce the opening of a much needed components shop for the north of London enthusiast.

Over 200,000 components as well as books, kits, service aids and hardware will be stocked.

We invite you to phone:

**01366 1873**


Personal callers welcome.

**208 BAKER STREET,  
ENFIELD, MIDDX.**

Listed below are some of the items stocked

Adaptors	Denco products	Keyboards	Signal injector
Adhesives	Demagnetisers	Keyector	Service aids
Aerials	Desolder broid	Knobs	Silver paint
Alarms	Desolder pump	Lamps	Switchlubricant
Aluminium boxes	Diacs	Lamp holders	Solder mop
A.B.S. boxes	Diodes	Leads	Silicone grease
Amplifiers	Light emitting	Liquid crystal displays	Anti-static spray
Audio leads	photo	LED	Freezit
Audible warning devices	rectifier	LED arrays	Plastic seal
	signal	LED displays	Aero klene
	zener		heat-sink compound
	germanium		Aero duster
Batteries	infra-red	Mains adaptor	Spacers
chargers	Displays	Matrix board	SWR meters
connectors	Drills	Memory I.C.s	Sockets
holders		Meters	Soldering
Bezels	Earpieces	Microphones	Soldering irons
Books	Earphones	Inserts	Sirens
Boxes	Enamelled copper wire	stands	Speakers
Bridge rectifiers	Etch resist products	Microprocessors	Switches
Bulbs		Morse key	Mercury tilt
holders	Filters	Multitesters	Micro
Busbars	Ferric chloride	Neon bulbs	Reed
Buzzers	Ferrite cores	Ni-Cad batteries	Rocker
	Ferrite rods	Ni-Cad chargers	Rotary
Cable	Fixing feet	Opto electronic	Toggle
clips	Fuses	Oscilloscopes	Wafer
ties	Fuse holders	Panels	Slide
markers	Fluorescent displays	Pick-up coils	Push button
sleeving	Flod strength motors	Pliers	Testleads
wrapping	Frequency counter	Pre-sets	Thermistors
stripper	Gas sensor	Potentiometers	Thyristors
Capacitors	Grommets	P.C.B.s	Trance
air spaced	Group panels	P.C.B. transfers	Transformers
trimmer	Grenade	Probes	Mains
suppression		Plugs	Audio
feed through	Headphones	Pressure mats	I.F.
ceramic	Hot sinks	Pre-amps	Transistors
electrolytic	Inspection glasses	Photo electric relays	Transistor tester
polyester	I.C.s	Rocillors	Tape strips
polystyrene	I.C. sockets	Resistors	Threaded copper wire
silver mica	Infra-red source	carbon film	Transducers
tantalum	Infra-red sensor	metal film	Toroids
Cermet pro-sets	Indicators	metal oxide	Terminals
Chokes	Insulating tape	wirewound	Tunning coils
Coilformers		Ring cores	Tunning condensor
Connectors		Regulators	Ultrasonic transmitter
Collie		Relays	Ultrasonic receiver
Continuity testers		Resistance chart	Vero products
Convertors			
Crimp tools			
Crocodile clips			
Crystals			
Jewellers screwdrivers			

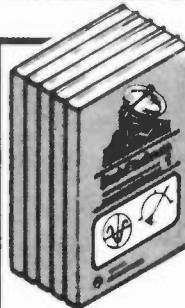We are open from 9 a.m. to 6 p.m., Monday-Saturday



## ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.  
Bound in stiff linen. Cover size 8½in x 5in.  
Price £10.00 per set (we pay the postage).

Book 1. Introducing Electronics Book 4. Meters/Voltage-dividers  
Book 2. Resistors/Capacitors Book 5. Transistor Project Circuity  
Book 3. Inductors/Diodes

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm.

Order now:  
Selby Book Company  
11, Aspen Close,  
Bromley,  
Kent BR1 2NZ.

**OUR 100% GUARANTEE**  
Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Please allow 14 DAYS Delivery

Amount enclosed: £

Name:

Address:

EE 4

## BEFORE AND AFTER SCIENCE

HEY DUMMY! A weekly transfusion of New Musical Express is all it takes to make A REAL PERSON of you. With its scientifically-tested formula — truth and trivia, wit and gibberish — it's the modern music fan's complete life-support system. Every Thursday.

**NME**  
NEW MUSICAL EXPRESS  
The paper for the almost human

*Pic of Kraftwerk dummy by Anton Corbijn.*

# BI-PAK BARGAINS



## 5T31 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes: - 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm. £1.75

## 5T31 NUT DRIVER SET

## 5T41 TOOL SET

## 5T51 WRENCH SET

BUY ALL FOUR SETS: 5T21-5T51 and get HEX KEY SET FREE

HEX KEY SET ON RING.

Sizes: 1.5, 2, 2.5, 3,

4, 5, 5.5 and 6mm.

Made of hardened steel.

HX/1. £1.25



## BI-PAK PCB ETCHANT AND DRILL KIT

Retail Value over £15.00


OUR BI-PAK SPECIAL KIT PRICE £9.75

ORDER NO. SX81



## BI-PAK SOLDER - DESOLDER KIT

OUR SPECIAL KIT PRICE £8.95

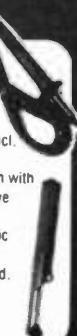

## BRAND NEW LCD DISPLAY MULTITESTER.

Max indication 1999 or -1999

Polarity indication Negative only.

Positive readings appear without + sign.

Input impedance 10 Megohms

Zero adjust Automatic

Sampling time 250 milliseconds

Temperature range -5°C to 50°C

Power Supply 1 x PP3 or equivalent 9V battery

Consumption 20mW

Size 155 x 88 x 31mm

RANGES

DC Voltage 0-200mV

0-2-20-200-1000V. Acc: 0.8%

AC Voltage 0-200-1000V.

Acc. 1.2% DC Current 0-200mA.

0-2-20-200mA 0-10A. Acc: 1.2%

Resistance 0-2-20-200k ohms.

0-2 Megohms. Acc: 1%

BI-PAK VERY LOWEST POSS PRICE

£35.00 each



## SEMICONDUCTORS FROM AROUND THE WORLD

100

A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices.

100

Guaranteed Value over £10 at Normal Retail Price

£4.00

yours  
for  
only  
Data etc.  
in  
every pak.  
Order No. SX66

## EXPERIMENTER BOXES - ALUMINIUM - PLASTIC ALUMINIUM BOXES

SIZE	L	W	H	Order No.	Price
5 ½	2 ½	1 ½	159	83p	
4	2 ½	1 ½	161	83p	
4	2 ½	2	163	83p	
3	2	1	164	57p	
8	6	3	166	£1.68	
6	4	2	167	£1.12	

All measurements for boxes are shown in inches. L = Length. W = Width. H = Height

## Plastic Boxes

SIZE	L	W	H	Order No.	Price
4	2	1	141	£1.00	
4 ¾	2 ½	1 ½	143	£1.30	
6	3 ½	2	144	£1.60	

Plastic as above but with aluminium top panel

SIZE	L	W	H	Order No.	Price
4	2 ½	1	146	£1.40	

Plastic sloping front

SIZE	L	W	H	Order No.	Price
5 ½	4 ¼	2 ¼	slope		

to

SIZE	L	W	H	Order No.	Price
1 ½	148	£2.14			

## The Third and Fourth Hand...

.... you always need but have never got until now This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 ½ diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier Our Price with magnifier as illustrated ORDER NO T402 £5.50 Without magnifier ORDER NO T400 £4.75

.... you always need but have never got until now

This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 ½ diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier Our Price with magnifier as illustrated ORDER NO T402 £5.50

Without magnifier ORDER NO T400 £4.75

.... you always need but have never got until now

This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 ½ diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier Our Price with magnifier as illustrated ORDER NO T402 £5.50

Without magnifier ORDER NO T400 £4.75

.... you always need but have never got until now

This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 ½ diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier Our Price with magnifier as illustrated ORDER NO T402 £5.50

Without magnifier ORDER NO T400 £4.75

.... you always need but have never got until now

This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 ½ diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier Our Price with magnifier as illustrated ORDER NO T402 £5.50


Without magnifier ORDER NO T400 £4.75

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite


## BRANDLEADING ELECTRONICS

### NOW AVAILABLE IN KIT FORM

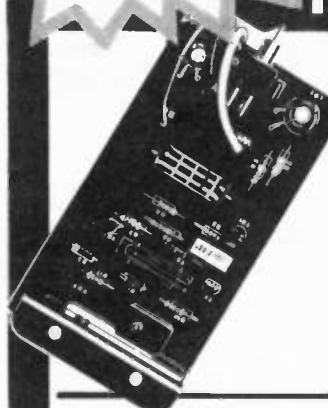
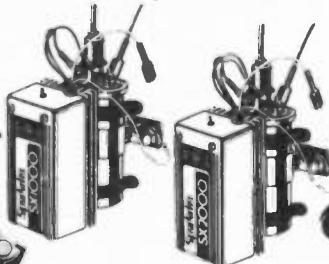
#### SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




#### SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



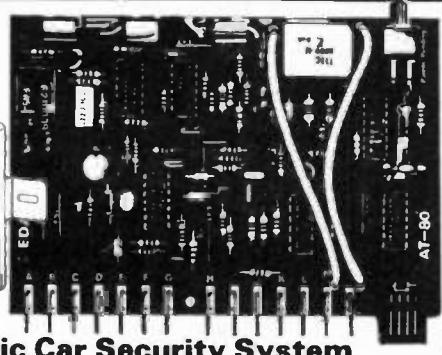
#### AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreensensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble



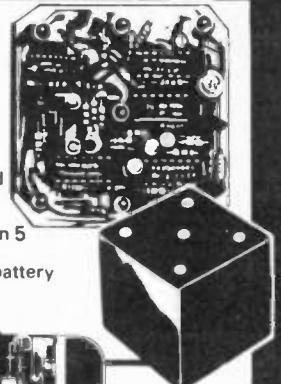
#### MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble




#### TX2002 Electronic Ignition

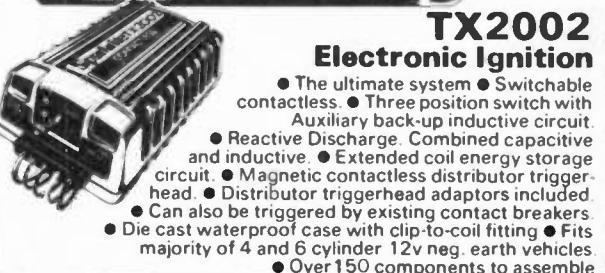
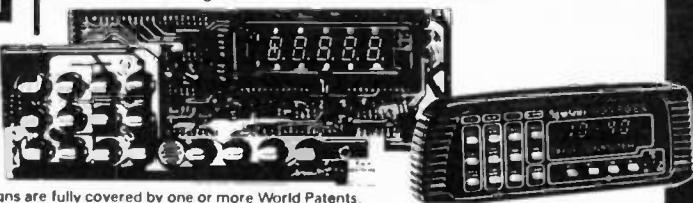
#### VOYAGER Car Drive Computer

- A most sophisticated accessory.
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
- Affords 12 functions centred on Fuel, Speed, Distance and Time.
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on.
- Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity.
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%.
- Large LOG & TRIP memories: 2,000 miles, 180 gallons, 100 hours.
- Full Imperial and Metric calibrations.
- Over 300 components to assemble.
- A real challenge for the electronics enthusiast!



All EOA-SPARKRITE products and designs are fully covered by one or more World Patents.  
**EDA SPARKRITE LIMITED** 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

	SELF ASSEM. KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

Please allow 28 days for delivery

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

££.4.82

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

CHEQUE NO. \_\_\_\_\_ KIT REF. \_\_\_\_\_

24 hr. Answerphone  
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD  
SEND ONLY SAE IF BROCHURE IS REQUIRED



BRANDLEADING BRITISH ELECTRONICS  
CUT OUT THE COUPON NOW!  
Everyday Electronics, April 1982

# Everyday ELECTRONICS

VOL. 11 NO. 4 APRIL 1982

**Editor**  
F. E. BENNETT

**Assistant Editor**  
B. W. TERRELL B.Sc.

**Production Editor**  
D. G. BARRINGTON

**Technical Sub-Editor**  
G. P. HODGSON

**Art Editor**  
R. F. PALMER

**Assistant Art Editor**  
P. A. LOATES

**Technical Illustrator**  
D. J. GOODING Tech. (CEI)

**Secretary**  
JACQUELINE DOIDGE

**Editorial Offices**  
KINGS REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS  
Phone: 01-261 6873

**Advertisement Manager**  
R. SMITH  
Phone: 01-261 6871

**Representative**  
R. WILLETT  
Phone: 01-261 6865

**Classified Supervisor**  
B. BLAKE  
Phone: 01-261 5897

**Make-Up and Copy Department**  
Phone: 01-261 6815

**Advertisement Offices**  
KINGS REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS

## Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

## Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

## INCONSPICUOUS

Doodling with electronic circuits is a form of innocent amusement most of us indulge in from time to time. If one single subject has inspired such abstract designing more than any other, it is likely to be the electronic combination lock. Some years ago, immediately following the introduction of digital integrated circuits, this kind of activity reached well nigh craze proportions we recall. What opportunities for creating tantalising puzzles with labyrinthine circuitry these microchips gave us. That most of these doodles on paper never finally materialised in concrete form is beside the point: more than enough did and there has been no scarcity of practical designs for electronic combination locks to satisfy general needs.

In more recent years the availability of keypads has further helped the development of electronic combination locks as serious functional devices and assured their ready acceptance in a society now well accustomed to the digital keyboard.

One advantage of the combination lock (electronic or otherwise) is that no removable key is involved. But in another respect it is like any conventional lock with a keyhole, in that its presence is advertised by the tell-tale knob or keypad. This is not a serious objection in many cases, such as external doors, for the existence of a lock of some description is a foregone conclusion anyway.

But there could be situations where it might be felt vitally important not to betray the existence of a secured area or compartment—of whatever size. In this strategy the first line of defence is based on concealment and in not attracting attention. The Magnetic Lock meets such a requirement. The particular design described in this issue does require a key—of a special kind—but there is no giveaway keyhole or keypad. Nothing at all need be visible externally to suggest the presence of a locking device. And that is not all. Should the key fall into the hands of some unauthorised person its significance will not be apparent; but even if it were, there remains the problem of just how and exactly where it is used. On that intriguing note we leave the subject, certain that readers will want to learn more from the article itself.

## FLAG FLYING

Good to know of one home-brewed electronic product that is at the top of the charts. Britain's electronic entrepreneur Clive Sinclair is flying high, with over a third of a million ZX81 personal computers sold—some to Japan and the USA.

Owners of the ZX81 will find our plug-in 2K Ram Pak of special interest. This inexpensive project will increase the memory of the standard machine sufficiently for many general needs.

Anytime we can help, Clive!



## Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price 80p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

## Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.

## Subscriptions

Annual subscription for delivery direct to any address in the UK: £11.00. Overseas: £12.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, Kings Reach Tower, Stamford Street, London SE1 9LS.



by the latch/counter circuit, the frequency of oscillation of the clock being adjustable so as to calibrate the display reading. The pulses from the clock oscillator are stored in the latch of the latch/counter and only transferred to the display at the end of the monostable timing pulse. This is achieved by feeding the timing pulse into the latch monostable which is triggered by the negative going edge (also referred to as the "trailing edge"), the resulting latch pulse being very narrow, only about three microseconds long, and it is this pulse which "latches" the stored number of clock pulses into the display.

The negative going edge of the latch pulse also triggers a third monostable, the reset monostable, the purpose of which is to reset the counter and hold it at zero so that pulses from the clock oscillator are not counted during this period. The negative going edge of this reset pulse is also fed back to the timing monostable and the whole sequence restarts. The period of the reset pulse is about one second, although in theory it need only be a few microseconds, but this would give far too many readings per second of the unknown capacitance, hence causing

# Capacitance/Frequency Meter

BY A.P. DONLEAVY

**T**HIS instrument was originally designed exclusively as a capacitance meter, but the addition of a few extra components enables it to function as a frequency meter, with a degree of accuracy sufficient for the needs of most amateur constructors. The scale ranges from approximately 1,000pF to 10 $\mu$ F in the capacitance mode and from 50Hz to 1MHz as a frequency meter. The power is supplied either from a 9V PP3 battery or from a mains calculator adaptor via a 2.5mm jack socket.

## CAPACITANCE METER

Fig. 1 shows the block diagram of the meter, and we shall use this to describe the operation of the circuit.

With S1 in position c as shown, the instrument measures capacitance. A monostable (single shot) multivibrator produces a pulse, the duration of which is proportional to the unknown capacitance ( $C_{ext}$ ) under test, this capacitor forming part of the time constant circuit of the monostable.

During this period, clock pulses from the clock oscillator are counted

the last digit to flicker rapidly and appear as an "8".

So it is in this way that the meter counts a number of clock pulses for a period of time governed by the unknown capacitance and displays this figure as a direct capacitance value.

## DIVIDE-BY-TEN

The divide-by-ten circuit is used to extend the range of the meter by dividing the clock pulse frequency by

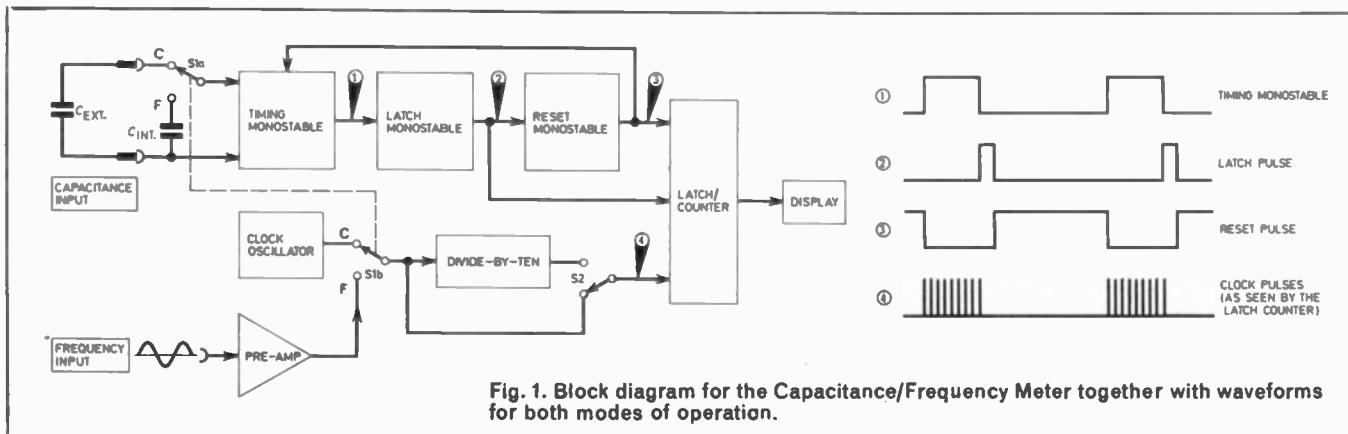


Fig. 1. Block diagram for the Capacitance/Frequency Meter together with waveforms for both modes of operation.

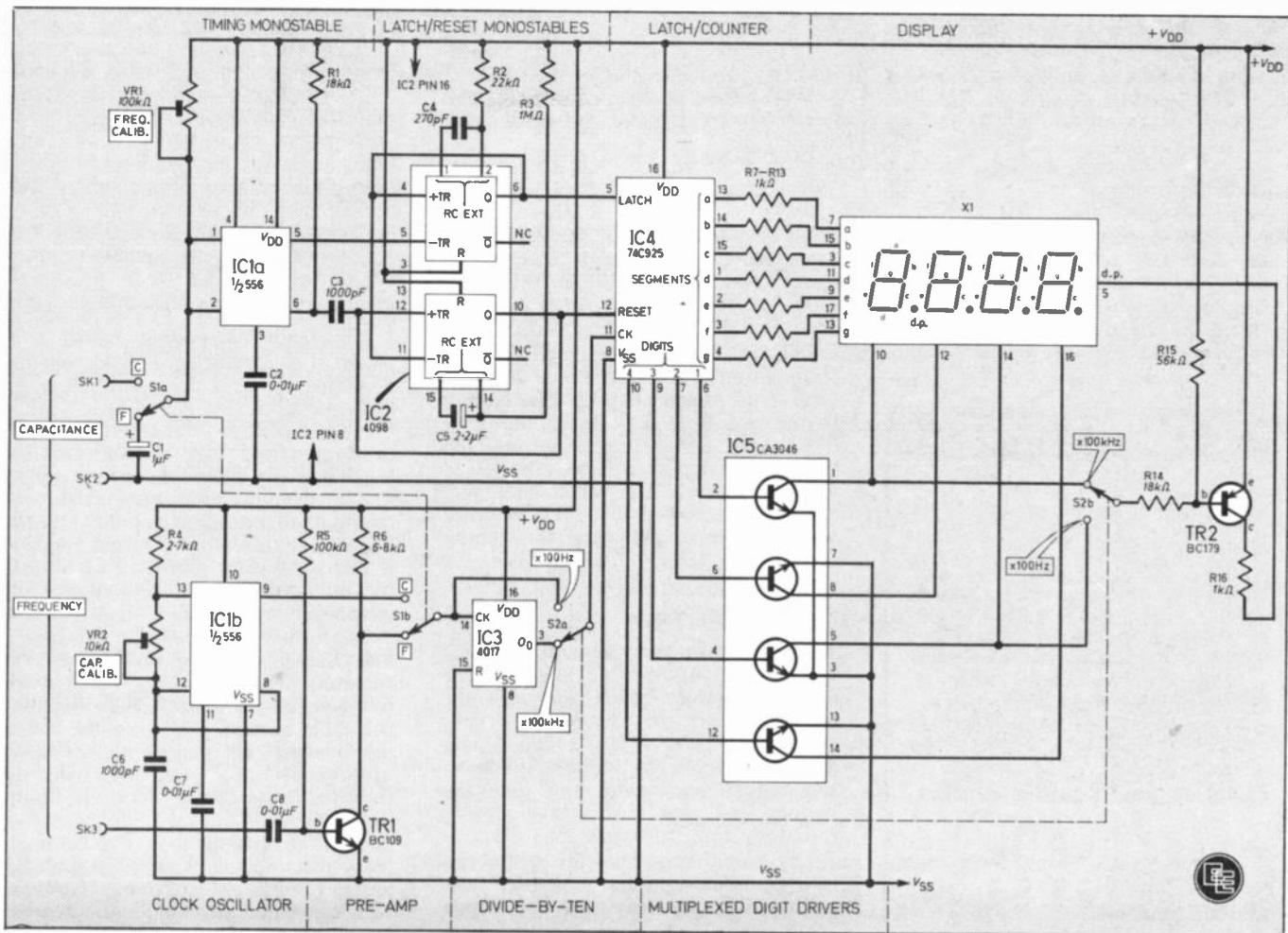


Fig. 2a. Circuit diagram for the Capacitance/Frequency Meter. Note the pin numbers on X1 are for the National Semiconductor display.

ten for evaluating the higher value capacitors. This facility is brought in with S2.

By switching S1 to position F the instrument can now be used for the measurement of frequency.

#### FREQUENCY MEASUREMENT

As a frequency meter, the operation is very similar to above, only a capacitor of known value ( $C_{int}$ ) is used to set a fixed timing monostable pulse width. The unknown input frequency is fed into the meter via a pre-amplifier, either directly or divided by ten (again to extend the range and dependant on the position of S2), to the latch/counter. The display now gives a direct reading of frequency, calibration being achieved by varying a resistive element in the timing monostable time constant circuit.

The waveforms shown in Fig. 1 are present in both modes of operation but note that waveform 4, the clock pulses, are always present but the latch/counter only recognises them when the reset input is at logic 0. Note also that in the frequency mode, these pulses will be the unknown input signal.

#### CIRCUIT DESCRIPTION

The full circuit diagram is shown in Fig. 2. IC1a, half a 556 dual timer i.c., is connected as the timing monostable, with VR1 and C1 forming the time constant components in the frequency mode and VR1 and the unknown capacitor determining this in the capacitance mode.

IC1b, the other half of the 556, is connected as the internal clock oscillator, the frequency of which is adjusted by VR2, this allowing calibration in the capacitance mode. Note that the frequency calibration by means of VR1 must be carried out first, followed by capacitance calibration with VR2, as adjustment of VR1 will affect both modes of operation.

IC2, a CMOS 4098 dual monostable i.c., contains both the latch and reset monostables, the pulse width from each determined by C4/R2 and C5/R3 respectively. The negative edge of the reset pulse from pin 10 of IC2 is coupled back to IC1a via C3 and R1, the reason for these components being that the retriggering pulse must be of a shorter duration than the timing pulse and this would not be so if a direct connection was made.

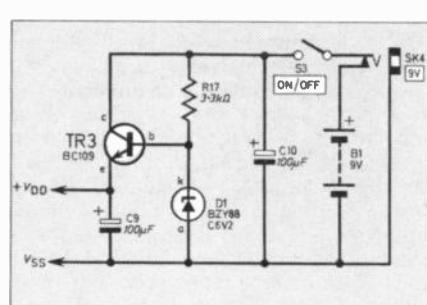


Fig. 2b. Power supply arrangement for the circuit. Insertion of a battery eliminator jack cuts out the internal battery

IC3, a CMOS 4017 decade counter/divider, i.c. is wired as a divide-by-ten and TR1 forms the preamplifier stage for the unknown input signal.

#### MULTIPLEXED DISPLAY

The latch/counter circuit consists of IC4, a 74C925 CMOS four digit counter with multiplexed seven-segment outputs. This i.c. counts the clock pulses at pin 1 when pin 12 (reset) is low and only when pin 5 (latch) goes high will the display give the information contained in the counter. In this circuit, the information in the counter is transferred to

update the display only during the brief period of the latch pulse.

The display is multiplexed and a CA3046 (or the equivalent LM3046, CA3086 etc) is used to drive the four digits. This i.c. contains five individual *npn* transistors, only four of which are used.

The circuitry associated with TR2 drives the decimal point on the display and this is moved accordingly with S2b, S2a being the switch to bring the divide-by-ten circuit.

With S2 in position "X 100kHz", the meter can measure up to 1 mega-

hertz and the display reading must be multiplied by 100,000. The capacitance is given directly in microfarads in the range 0.001μF to 10μF. The decimal point is after the most significant digit.

With S2 in the "X 100Hz" position, the meter measures from 50Hz to 100kHz, this time the display reading must be multiplied by 100. Again the capacitance meter reads directly in microfarads, from 0.1μF to the maximum of 10μF. The decimal point is after the third most significant digit.

The instrument is designed to work from either a 9V battery or a calculator type mains adaptor. The supply to the circuit ( $V_{DD}$ ) should be about 5.5V and although this is not too critical, it should not be allowed to fall much below this value, otherwise the pulse from pin 10 of IC2 may not be sufficient to retrigger the timing monostable, IC1a.

## COMPONENTS

### Resistors

R1, 14	18kΩ (2 off)
R2	22kΩ
R3	1MΩ
R4	2.7kΩ See
R5	100kΩ
R6	6.8kΩ
R7-13, 16	1kΩ (8 off)
R15	56kΩ
R17	3.3kΩ
All	±W carbon ±5%

### Capacitors

C1	1μF 16V electrolytic
C2, 7, 8	0.01μF polyester (3 off)
C3, 6	1000pF polystyrene (2 off)
C4	270pF polystyrene
C5	2.2μF tantalum bead
C9, 10	100μF tantalum bead (2 off)

### Semiconductors

D1	BZY88 6.2V, 400mW Zener diode
TR1, 3	BC109 silicon <i>npn</i> (2 off)
TR2	BC179 silicon <i>pnp</i>
IC1	556 dual timer
IC2	4098 CMOS dual monostable
IC3	4017 CMOS decade counter/divider
IC4	74C925 CMOS 4 digit counter with multiplexed 7-segment output
IC5	CA3046 silicon <i>npn</i> transistor array
X1	Calculator display National NSA 1298 (see text)

### Miscellaneous

S1, 2	d.p.d.t. miniature toggle (2 off)
S3	s.p.s.t. miniature toggle
SK1, 3	4mm socket, red (2 off)
SK2	4mm socket, black
SK4	2.5mm jack socket, switched
VR1	100kΩ multturn preset Spectrol type 43P.
VR2	10kΩ multturn preset Spectrol type 43P.
B1	9V PP3 battery
Stripboard	0.1 inch matrix, 32 strips by 42 holes; aluminium instrument case, 150 × 105 × 45 mm; red display filter approx 50 × 25mm (for X1); battery connector; 16 pin d.i.l. holder (3 off); 14 pin d.i.l. holder (2 off); 7/0.2 p.v.c. sleeved equipment wire; board mounting hardware M2.5 (6BA).

## Shop Talk

page 233

## COMPONENTS

All resistors and capacitors should be as small as possible and for this reason tantalum bead capacitors are used in place of electrolytic types (except for C1). TR1, 2 and 3 can be replaced by any similar specification silicon transistors and potentiometers VR1 and 2 are three-quarter inch long multturn presets.

The display used in the prototype is a common cathode nine digit calculator display, only four of which are used. Individual displays of larger size could be used as indeed could the four digit "bubble" displays in the d.i.l. package, but larger displays will draw more current, and therefore make battery operation less feasible and the size of the box may also need to be increased.

There are several types of calculator display, some with edge connector type mounting, as in the case of the National Semiconductor display used in the prototype model (part No. NSA 1298), and it was for this type that the component board has been laid out and the pin numbers on the circuit diagram refer to. Other types may require modification to the wiring and when purchasing a display, check with the supplier that the pin connection information is available (see Fig. 3).

Generally speaking, calculator displays, often supplied as surplus stock, are cheaper than the alternatives already discussed, their only drawbacks, being the somewhat miniature digits and the need for an additional red filter.

The segment current limiting resistors R7 to 13 and R16 could be of a lower value to increase the display brightness but this would be at the expense of increased current consumption, which on the prototype was about 40mA.

# CONSTRUCTION starts here

## CIRCUIT BOARD

The main component board is a piece of 0.1 inch matrix Veroboard, 32 strips by 42 holes with the plain unpunched copper strips found along the edge of the board left on. It is in these strips that the four mounting holes are drilled as shown in Fig. 4. The original prototype meter was constructed on a special d.i.l. circuit board, but this type of board requires a fairly large number of wire links so the design was transferred to stripboard.

There are 82 breaks in the tracks and the position of these must be carefully checked. The components can now be inserted, proceeding with the d.i.l. holders (this greatly assists in locating the positions of other components) followed by resistors, capacitors, semiconductors and finally links. Small, straight links of no more than 5 holes long can be made from resistor lead croppings but the longer links and particularly those which bend, must be formed from insulated wire. Ideally, the flying leads from the board to the front panel should be soldered to Veropins as this strengthens the joint considerably.

The display can be mounted directly into the board but may require to be soldered onto a row of pins inserted into the board, particularly if a slightly different display is used and any pinout changes can be accommodated at this stage (see note on alternative type of display).

## INSTRUMENT CASE

To mark the board mounting holes in the bottom of the case, use the board itself as a template (prior to any components being assembled on it), placing it in position as shown in Fig. 5.

A drilling guide for the front panel is shown in Fig. 5, and the hole in the rear panel for SK4 must be large enough to clear the mounting bush and nut of the socket. The reason for this being that SK4 is to be isolated from the chassis so it is first mounted on a piece of insulating material (a piece of plain Veroboard for example) and this is then glued behind the back panel, none of the socket's metalwork touching the case.

The board is mounted into the case with long screws (M2.5 or 6BA),

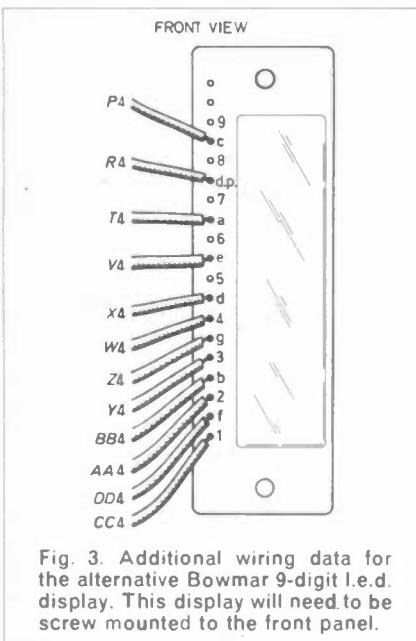


Fig. 3. Additional wiring data for the alternative Bowmar 9-digit i.e.d. display. This display will need to be screw mounted to the front panel.


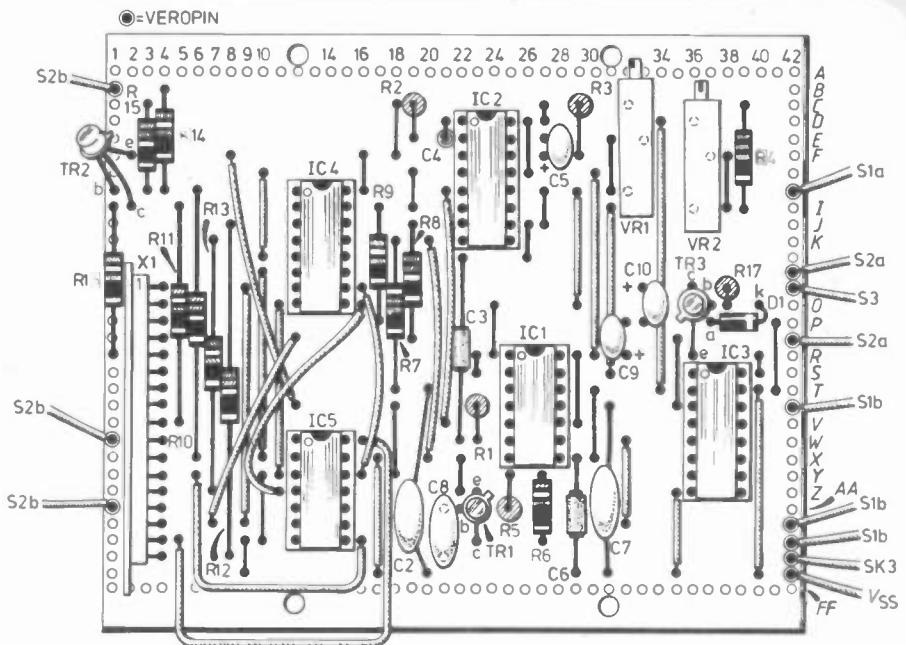


Fig. 4 (right). Component layout on the stripboard together with an underside view showing the cuts to be made in the copper tracks.

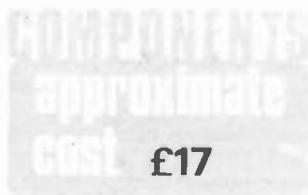Note that there are 82 breaks to be made in the copper tracks and these should be made before inserting the topside components.



£17

Fig. 5 (below). The case has been laid flat to show position of circuit board, switches, sockets and display cutout.




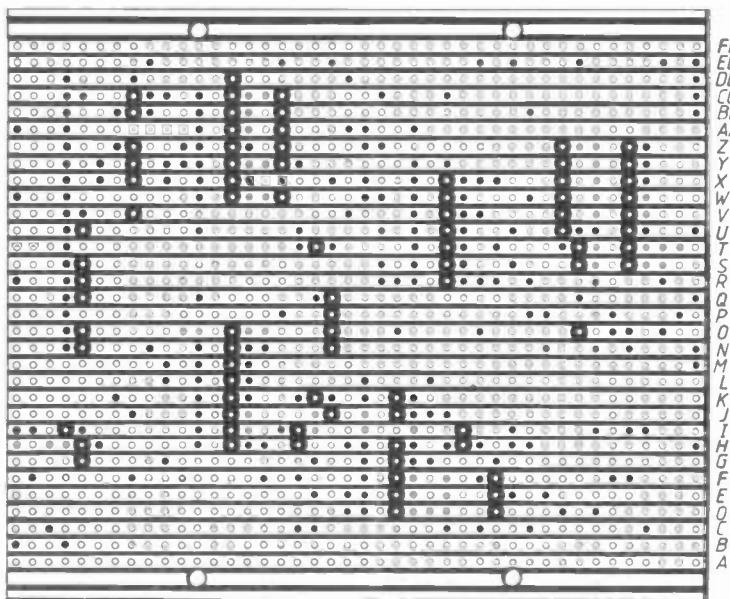


Fig. 5 (below). The case has been laid flat to show position of circuit board, switches, sockets and display cutout.

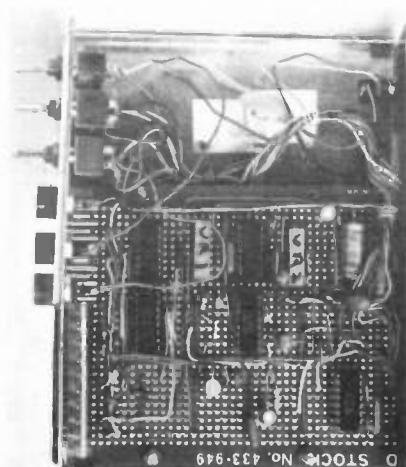

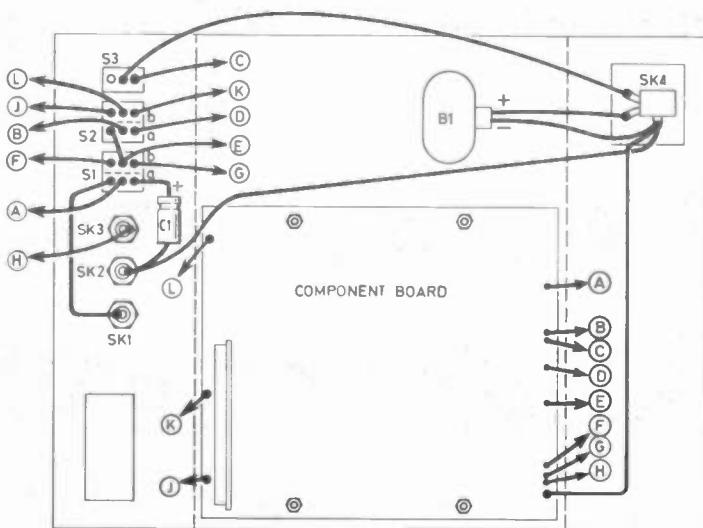

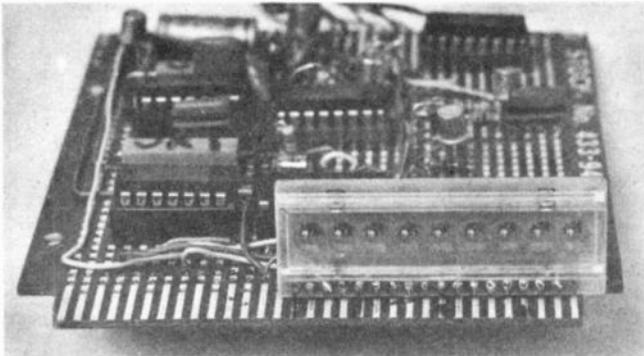Front panel arrangement showing lettering and filter over the display cutout.



Close-up of the display module used on the d.i.l. board prototype.

the reason being that this allows up and down adjustment to get the display accurately behind the window in the front panel, but the board height is typically 12mm meaning the screws must be at least 15 to 20mm long.

Having assembled the case with all switches, sockets and board, wiring can commence.

## FINAL ASSEMBLY

Using Fig. 5 as a guide, all interconnections can be made with flexible, stranded wire. Note the mounting of C1 between SK2 and S1a and that this capacitor is an electrolytic and not a tantalum bead, as the bead would not be robust enough.

Care must be taken when wiring SK4 ensuring that the  $V_{ss}$  lead is soldered to the outer sleeve terminal, the lead from S3 goes to the other contact and the battery positive wire is connected to the switched contact (only connected when no plug is in the socket).

## CALIBRATION

The meter must first be calibrated as a frequency meter, and this is carried out by adjusting VR1 until the display matches a known input frequency. If a signal generator is available then this should be used to set up the instrument, but failing this, a crystal oscillator of known frequency must be built to the circuit given in Fig. 6. Any suitable crystal in the range 100 to 200kHz can be used for X1.

Another, though less satisfactory method of calibration is to take a couple of meters of wire and form it into a loose coil of about 150mm in diameter. Insert the free ends into the input terminals of the meter, and dangle the coil over the back of a turned on television set. The coil will pick up the flyback pulses from the scan coils, the frequency being 15,625Hz for a 625 line system. However, the disadvantage of this method

is the possibility of picking up other frequencies from the set.

Calibration of the capacitance range is performed using a capacitor of known value (as high a tolerance as is available) and adjusting VR2 until the display corresponds with the value. A high value component, for example,  $0.47\mu F$  (not electrolytic or tantalum), is ideal.

If the frequency is recalibrated for any reason, it will also affect the capacitance readings, whereas the capacitance range can be altered without upsetting the frequency calibration.

If a frequency or capacitance is beyond the range of the meter, the display will show an inconsistent result.

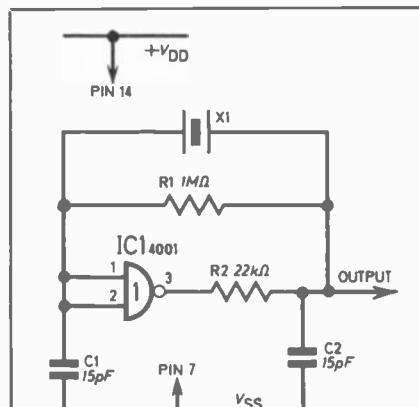


Fig. 6. Crystal oscillator circuit for calibrating the frequency meter mode. See text for X1.

## TROUBLE SHOOTING

The following points may be helpful if the instrument does not work when first turned on.

The display should always show four digits and a decimal point, irrespective of faults elsewhere in the circuit and if it only reads four zeros in the capacitance mode, check that the clock oscillator is working (IC1b) by looking for a signal on pin 9 of IC1. Now check that the timing pulse is being generated by

connecting to the test terminals a high value capacitor (say  $10\mu F$ ) and measuring the voltage across it using a high impedance voltmeter. The voltage should continually rise and then fall, recycling about once every second. If it only rises initially when first turned on, then either IC1 is at fault or more likely, there is no reset pulse coming from IC2 to retrigger the timing pulse.

Attention can then be turned to IC2, this can be easily investigated by removing IC1 from its socket (assuming it has one!) and measuring the voltage at pin 6 of IC2. This should be at 0V. Pin 10 should also be at 0V and whilst these measurements are being taken, pin 5 must be tied to  $+V_{DD}$  via a resistor and this is achieved by inserting the ends of the resistor in pins 5 and 14 of the now empty IC1 socket.

Momentarily short pin 5, IC2 to 0V and pin 10, IC2 should go high (approx  $+V_{DD}$ ) for about one second, then fall to zero volts again.

If this does not happen then either the wiring of this i.c. is incorrect or it is a defective device. If however these measurements are correct but the fault persists when IC1 is replaced, then assuming the wiring is correct, IC1 is faulty.

## IN CONCLUSION

The meter will of course be only as accurate as the standard it is calibrated against and in many instances this will be, in the case of the capacitance range, an off-the-shelf component and for the frequency, a signal generator which may not have seen the calibration engineers test bench for many a year. However, it is felt that for the majority of enthusiasts, it will serve to be a very useful and indeed, accurate enough, tool to have in the workshop.

Its single board construction, dual power supply options and low cost and simplicity make it a very attractive project for the amateur constructor wishing to expand his range of test gear.

# Shop Talk

## Electronic Supplies



**By Dave Barrington**

Two aids that may help the constructor or service engineer to enhance the finished layout of a project and carry out "on-the-spot" running repairs attracted our attention this month.

### Conductive Paint

A new conductive paint-on preparation from Comma Oils & Chemicals intended for the motoring fraternity is an ideal instant printed circuit board "repair kit" in a bottle.

Known as Electrocure 7, its main application is for repairing car rear window heating elements. However, this specially formulated silver based paint makes it easy to make-good broken tracks on p.c.b. boards and even stripboard.



**Comma's Electrocure 7 conductive paint.**

It can also be used for repairing most low voltage equipment where there is a broken connection. A feature of the product is that it has been developed for use on non-solderable surfaces, including glass, plastics, acrylics and ceramic.


Expected to be stocked by most motorising accessory shops, more details of price and addresses of nearest stockists can be obtained from Comma Oils & Chemicals Ltd., Dept. EE, Mark Lane, Gravesend, Kent DA12 2QX.

### Cable Clips

Neat wiring makes it much easier to trace out circuits and locate faults. Apart from wiring spirals, cable retainers and the use of the usual method of tie-cord, any new addition is welcome.

A range of Brandauer self-adhesive cable clips from Stotron provide an inexpensive method of fixing round or ribbon cable to most clean surfaces. The clips can handle round cables from just a few millimetres to 19mm (¾in). Ribbon cables from 13mm (½in) to 75mm (3in) can also be accommodated by a selection of clips with widths in stages of 6mm (¼in).

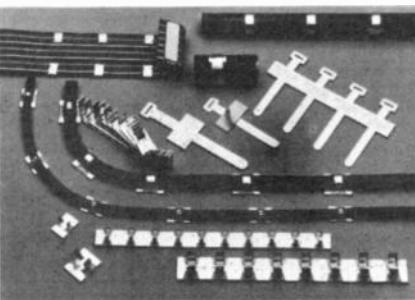For more details of stockists and prices write to Stotron Ltd., Dept EE, Unit 1, Haywood Way, Ivyhouse Lane, Hastings, East Sussex.



**Cable clips from Stotron**


### Case

A range of cases just being marketed by OK Machine & Tool feature a special battery compartment.

Called the HP-BAT-9V, the case has a removable battery "hatch" in its back panel, together with the battery clip and lead. The case is constructed of ABS material, measuring 92mm x 145mm x 28mm, and is ideal for housing all handheld instruments.

Four standard colours are offered, grey, tan, black and blue but special custom colours are available to order.

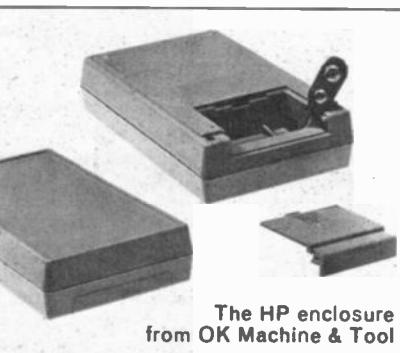The HP-BAT-9V case is available from OK's usual retail outlets, or direct from OK Machine & Tool (UK) Ltd., Dept EE, Dutton Lane, Eastleigh, Hants, SO5 4AA.



**The HP enclosure from OK Machine & Tool**

### Catalogue

The latest catalogue we have received comes from Rheinbergs Science who have been appointed exclusive distributor for the complete range of astronomical and scientific equipment and kits from Edmundson Scientific Products of America.

From lasers and holograms to fibre optics and science kits the Edmundson range consists of over 4,000 items. To promote these, Rheinbergs have equipped a showroom at Tonbridge, Kent, and have issued two catalogues outlining the complete range.

The General Scientific edition consists of 48 pages, in colour, and covers optics,

holography, tools, motors, microscopes and laboratory equipment. The Science Fun kits include electronics, electricity and magnetism, solar energy and a digital electronic computer kit.

Copies of the catalogue can be obtained free from Rheinbergs Sciences Ltd., Dept EE, Sovereign Way, Tonbridge, Kent TN9 1RW.

## CONSTRUCTIONAL PROJECTS

### Capacitance/Frequency Meter

The display used in the prototype model of the Capacitance/Frequency Meter was a nine digit calculator display, only four digits being used.

We have been informed by Bart Trepak of TK Electronics that they have a Bowmar 9-digit display suitable for this project. This is available from TK for the sum of 55p plus VAT. Note, the pinning for this device is different and will have to be "hard-wired" to the board as indicated in the article.

The multturn potentiometers are Spectrol types and stocked by Watford Electronics.

The only source of supply we have been able to locate for the four decade counter/latch i.c., type MM74C925, is Ambit International.

### Magnetic Lock

The only sourcing problems likely to be encountered in the Magnetic Lock is the supply of the Hall Effect devices.

The magnetically-operated TL170C Hall effect i.c. contains an output transistor with open collector for use on voltages up to 30V. This device seems to be only available from Maplin Electronic Supplies, stock number WQ75S (TL170C). They are also suppliers of suitable bar magnets, stock number FX72P.

### Ram Pack

The integrated circuits called up in the 2K Ram Pack should be readily available from most advertisers, but in case of difficulty they are listed by Watford Electronics, Ambit, and Electrovalue.

Readers who are not able to make their own printed circuit for this project may be interested to learn that Proto Design are able to supply one.

The cost for this board is £2.21 including VAT and postage and packing, and can be obtained from Proto Design, Dept EE, 14 Downham Road, Ramsden Heath, Billericay, Essex, CM11 1PU.

The double-sided edge connector used in our model was cut from a 77-pin wire-wrap type to form a 23-pin version. Only a Wirewrap edge connector is suitable for this project and must be used. This is available from Redditch Electronics, Dept EE, 21 Ferney Hill Avenue, Redditch, Worcs, B97 4RU, price £2.95 + 40p p/pkg.

### Light Actuated Switch

There are no unusual components in the Light Actuated Switch although care should be taken when choosing a suitable relay. This must have a 12V coil and mains rated contacts capable of carrying sufficient current for the load being switched. In any case they should not be rated at less than 3A. A suitable type would be the Pigmy Mains Relay available from Electrovalue.

### In-Car P.S.U.

The integrated circuit type LM317T used in the In-Car P.S.U. is available from Tandy stores.

# 2K RAM PACK FOR THE SINCLAIR ZX81

BY V. TERRELL



THE "add on" Ram Pack to be described gives the ZX81 (1K) microcomputer an extra 2K of RAM. It works in conjunction with the ZX81 internal 1K of RAM therefore providing a total of 3K of usable memory. All the necessary voltages and signals are readily available from the p.c.b. dual finger-set at the rear of the ZX81 including its power supply (5V). The unit simply plugs in and is immediately ready for use.

## MEMORY STORE

The 2114 memory chips used in the unit can each store 4-bit wide data at 1024 addresses. Because the ZX81 data bus is 8-bits wide, the four chips in the Ram Pack are wired in

pairs, each pair allowing data to be stored at 1024 addresses 8-bits wide.

## CIRCUIT OPERATION

The complete circuit diagram for the ZX81 Ram Pack is shown in Fig. 1. The address lines A0-A9 are wired in parallel to the two pairs memory

This project has been specially designed to meet the expected memory expansion needs of the ZX81 Personal Computer user who may not immediately require or be able to afford the massive 16K byte Ram Pack from Sinclair at a cost of over £50.

chips, IC1-4. These 10 lines carry information to call up any one of the 1,024 address locations as selected by the computer.

The eight lines D0-D7 carry data which can either be written (stored) into memory when the R/W pin is low, this being controlled by the WR (write) line from the ZX81, or when this line is high, data may be read from the memory and processed by the computer.

The two 1K memory blocks IC1, IC2 and IC3, IC4 are enabled only when their CS pins are low, a high will disable them.

The ZX81 RAM starting address is 16384 and decoding is required to enable the Ram Pack to be positioned 1K beyond this address.

## DECODING

Address decoding for the extra RAM is accomplished using IC5, a three-to-eight line decoder i.c. with tristate outputs. The three inputs A0, A1 and A2 on IC5 form a three-bit binary number (eight decimal numbers). The output corresponding to the binary input goes to a logic low with the remainder at logic high.

The decoding is not unique since an output will go low for the various combinations of 1s and 0s to the inputs, irrespective of the conditions of address lines A12 and A13, but does not need to be taken into account in this 2K system.


The i.c. as stated earlier is a tristate device which means that the outputs can be disabled (effectively disconnected) by suitable control signals to the three enable pins EN1, EN2, EN3 on IC5. The bar indicates that a low is required on EN1 and EN2 and a high on EN3 to "connect" the outputs to the following circuitry.

A logic high on address line A14 means that memory between 16K and 32K has been selected by the processor which is the requirement here. When addressing memory for read or write, the processor generates a low on MREQ at a time when the

Table 1: Decoder truth table.

Inputs				Outputs			Chip Enabled	
	A14	MREQ	A10	A11	Q0	Q1	Q2	
1	0	0	0	0	0	1	1	ZX81 Internal RAM
1	0	1	0	0	1	0	1	IC1, IC2 (First extra 1K)
1	0	0	1	1	1	1	0	IC3, IC4 (Second extra 1K)

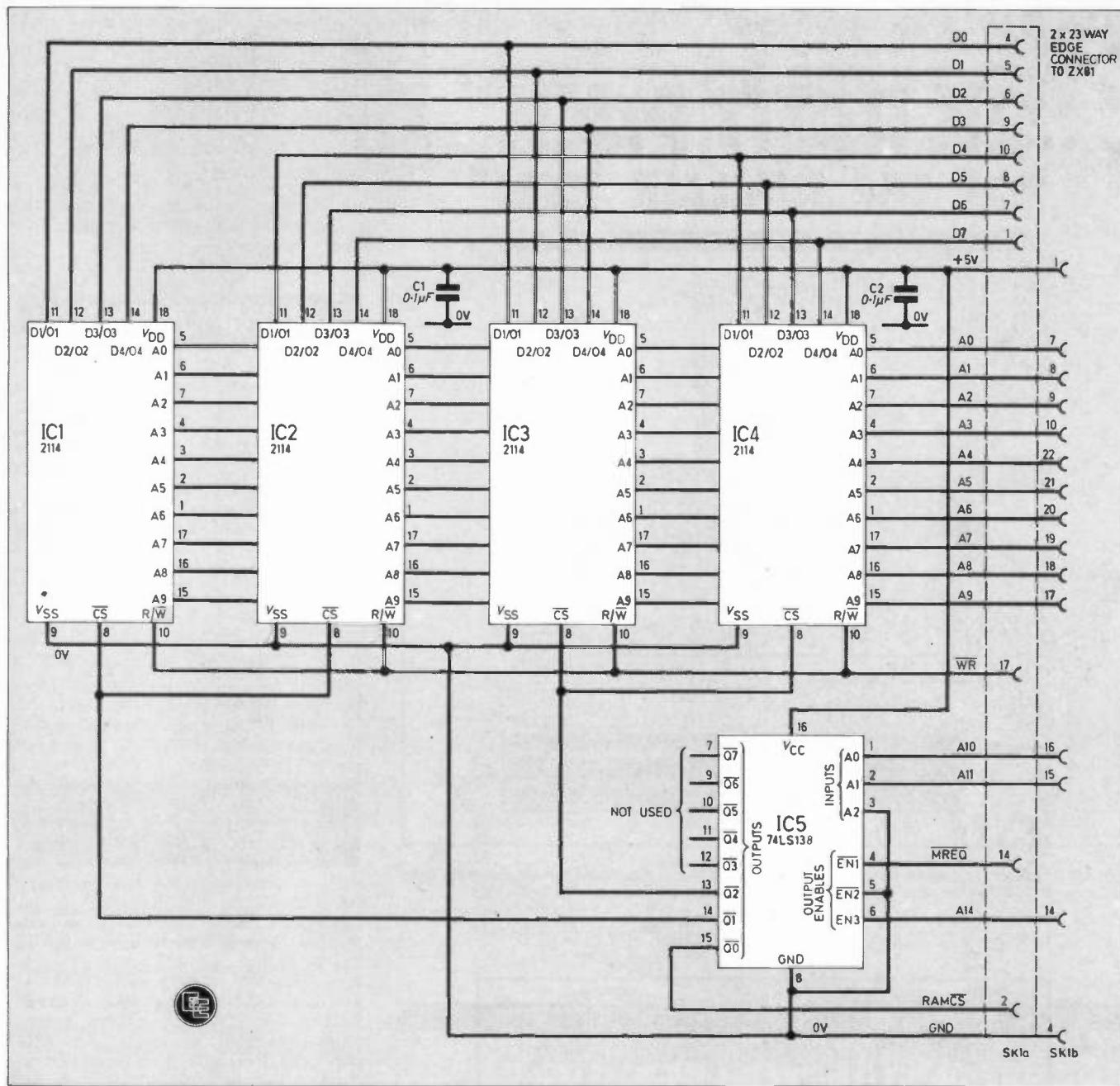If A14 is low or MREQ high, all outputs are high impedance.




address bus is stable. Thus addressing memory above 16K causes one of the outputs  $\overline{Q_0}$  to  $\overline{Q_2}$  to reach the RAM i.c.s. This is summarised in Table 1.  $\overline{Q_3}$  is not used.

#### TRUTH TABLE

The truth table for the decoder (IC5) reads as follows: When  $\overline{Q_0}$  is high the internal 1K RAMCS pin is disabled.  $\overline{Q_1}$  low enables the CS pins of IC1, IC2 selecting the first 1K of memory.  $\overline{Q_2}$  low enables the CS pins of IC3, IC4 selecting the second 1K of memory.


Decoupling capacitors C1 and C2 are required for each RAM pair to filter away any transients that may occur on the supply rail.

Fig. 1. The complete circuit diagram for the 2K Ram Pack for the ZX81.

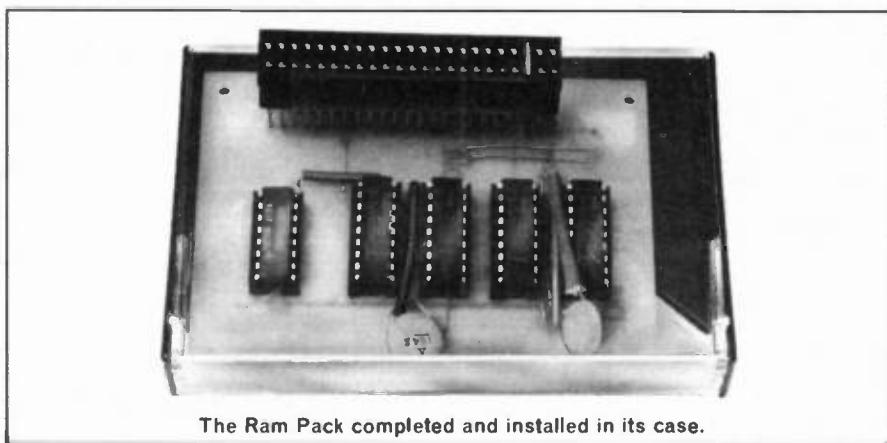

The Ram Pack completed and installed in its case.

# 2K RAM PACK FOR THE SINCLAIR ZX81

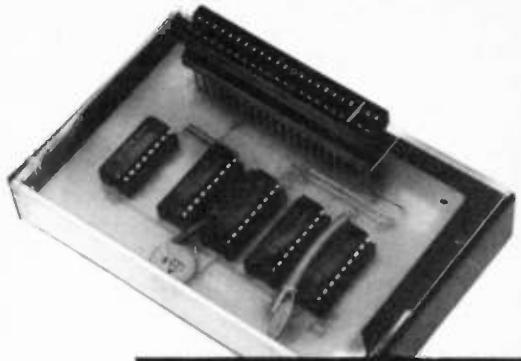

## COMPONENTS

**Capacitors**  
C1, C2 0.1 $\mu$ F disc ceramic (2 off)

**Semiconductors**  
IC1-4 2114-2 4096 bit MOS static RAM i.c. (1K x 4 bit) (4 off)  
IC5 74LS138 TTL tristate 3-to-8 line decoder

**Miscellaneous**  
SK1 0.1 inch pitch 2 x 23 way edge connector, wire wrap type with at least 3cm long pins

Printed circuit board: single sided, size 91 x 65mm; low profile d.i.l. sockets, 18-pin (4 off), 16-pin (1 off); cassette tape case; double sided self adhesive foam pads or strip; tinned copper wire; sleeving; solder.

**Approx. cost  
Guidance only £10**  
See page 233

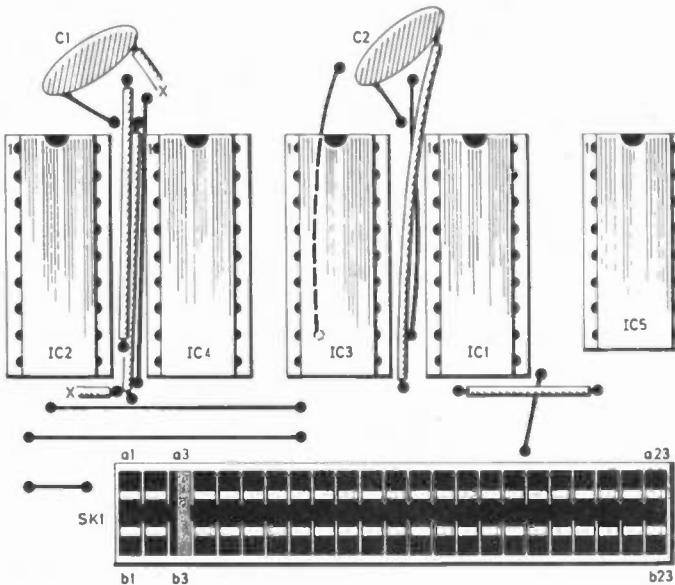


Fig. 3. Layout of the components on the topside of the p.c.b. Note that a link wire runs underneath IC3 socket. It is important to use sleeving on some of the link wires.


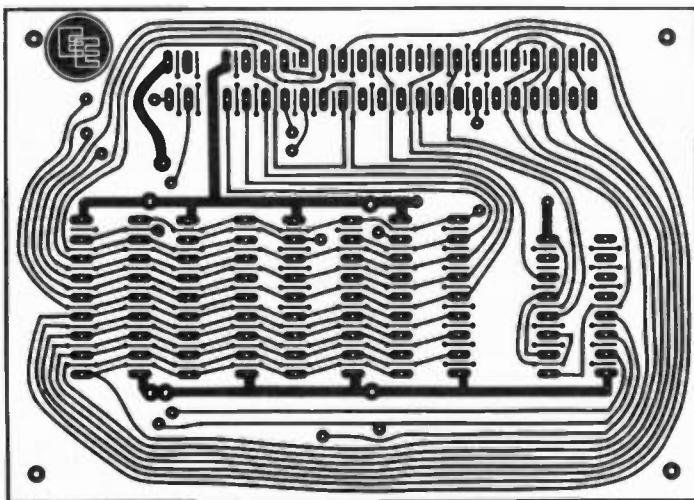


Fig. 2. Full size master of the pattern to be etched on the p.c.b. viewed from the copper side.

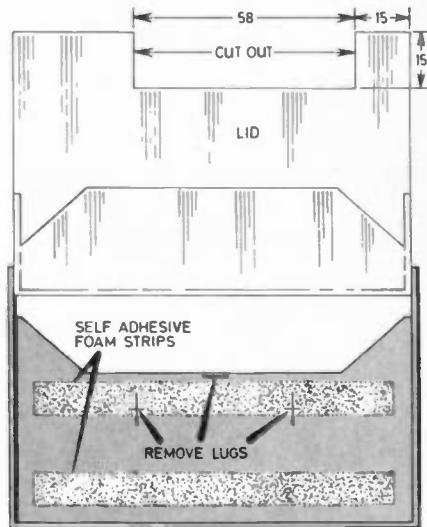

ALL DIMENSIONS IN mm

Fig. 4. Cut-out dimensions in the plastic cassette tape case to allow the edge connector to meet with the ZX81 p.c.b. The foam pads cushion the p.c.b. when the case lid is closed.

# CONSTRUCTION starts here

## EDGE CONNECTOR

The 2×23-way connector may be cut to size from a longer connector and should be of the wire wrap type with pins at least 3cm long. These pins must also be able to be removed to allow a polarising key to be located in the socket across positions 3A and 3B as shown in Fig. 3.

If a "key" is not supplied with the socket it can be cut and shaped from any suitable insulating material of the correct thickness and glued into place.


## PRINTED CIRCUIT BOARD

The circuit is built on a single-sided p.c.b. size 91×65mm. The full-size master of the pattern to be etched is shown in Fig. 2.

The printed circuit board tracks are quite close together so therefore care must be taken when soldering. It is suggested that a fairly small bit be used together with 22 s.w.g. solder.

Start by fitting the ten link wires as shown in Fig. 3. Next solder the five i.c. sockets followed by the two capacitors C1, C2.

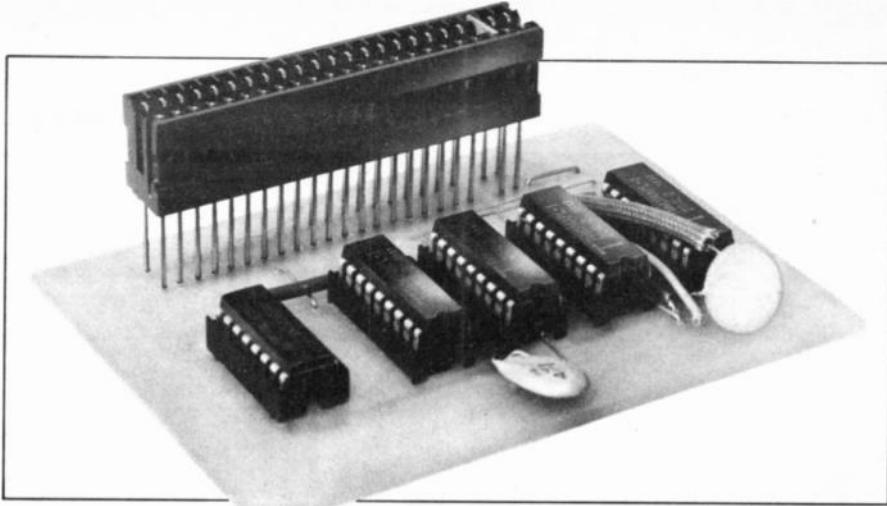Locate and solder the edge connector so that its pins protrude through the board by no more than 2 to 3mm. Before inserting the i.c.s, thoroughly check all soldered joints making sure adjoining tracks are not bridged with solder.



The fully assembled p.c.b. It can be seen that pin 3 on both sides of SK1 has been removed and that a polarising key has been fitted. This key is important and ensures that the connector accurately aligns with the ZX81 finger set.

## CASE

Details for fitting the Ram Pack into the cassette case are shown in Fig. 4. Remove the small plastic lugs in the case with a pair of side-cutters. The cut-out for the edge connector is made by cutting two slots with a junior hacksaw, then scribing between these on both sides with sufficient depth so that the plastic may be broken out.

The two strips of self adhesive foam are positioned as shown to cushion the printed circuit board, the case lid is simply secured down with Sellotape.

## TESTING

The unit can easily be tested by using the ZX81 "ramtop" test. Plug the unit in, then switch the ZX81 on and type in the following:

PRINT PEEK 16388 + 256 \* PEEK 16389 NEW LINE.

You should see 19456 displayed on the screen.

The result 19456 = 16384 + 3K of RAM. This short programme retrieves and displays the contents of locations 16388 and 16389 which contain the least and most significant bits respectively of the address plus 1 of the highest RAM location in circuit.

This information has been "poked" into these locations during the system set-up routine which is initialised at switch-on.

The following is a list of software available on the Sinclair 16K cassettes that were successfully loaded by the author using the 2K Ram Pack.

Cassette No.2 (16K)	Cassette No.4 (16K)
Crash	Substrike
Train	Codebreaker
Division	Twenty One
	Mayday

NOTE. Always make sure the ZX81 is switched off before inserting or removing the Ram Pack. □

## JACK PLUG & FAMILY...

BY DOUG BAKER



# EE TEACH-IN '82

PART 7  
BY O.N. BISHOP



## BASIC ELECTRONIC THEORY WITH EXPERIMENTS

### AMPLIFIERS AND AMPLIFIER MODULE

**I**N Part 5 we saw how a single bipolar transistor can be used to amplify a voltage. In those amplifiers (Figs. 5.9 and 5.11) the input was taken to the base and the output was taken from the collector. The emitter was part of both the input circuit and the output circuit. We say that the transistor is being used in the common-emitter connection. This is the most frequently used way of using a transistor for amplifying.

In Fig. 7.1 input goes to the emitter and output is taken from the collector. The base is common to both circuits, so this is the common-base connection.

The base-emitter current varies according to  $V_{IN}$ . The collector current is  $h_{FE}$  times greater than this. As  $I_C$  varies, the p.d. across  $R_3$  varies in proportion, causing variations in the value of  $V_{OUT}$ . Thus the gain of this amplifier is the same as that of a common-emitter amplifier, but we lose the advantage of the high input impedance of the base. The main use for this amplifier is at very high frequencies.

In a common-emitter amplifier the small capacitance between the emitter and base regions has a relatively large effect (the Miller effect). Voltages cannot change rapidly enough and gain is considerably

reduced at high frequencies. The Miller effect is much smaller in the common-base connection, making this connection specially suitable for high-frequency amplifiers.

The common-collector connection (Fig. 7.2) might seem to have no advantages, since the base-emitter voltage must always be 0.6V (for a silicon transistor) and any increase in base voltage is matched by an equal increase in emitter voltage. Whatever the value of  $h_{FE}$ , the gain of the amplifier is always unity. Such an amplifier is called an emitter-follower, for the voltage at the emitter exactly follows the changes in voltage at the base.

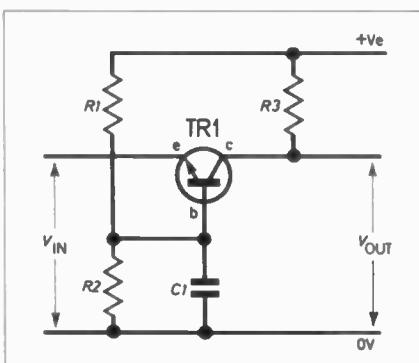


Fig. 7.1. Common base amplifier.

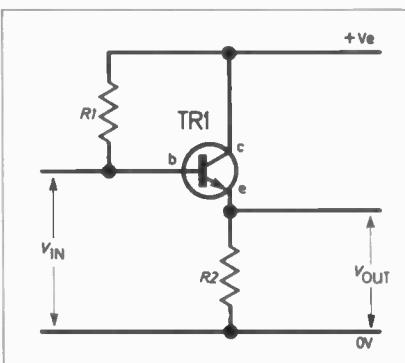


Fig. 7.2. Common collector amplifier (emitter-follower).

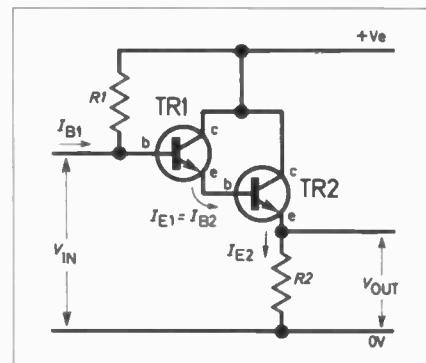


Fig. 7.3. Transistors wired in the Darlington pair configuration.

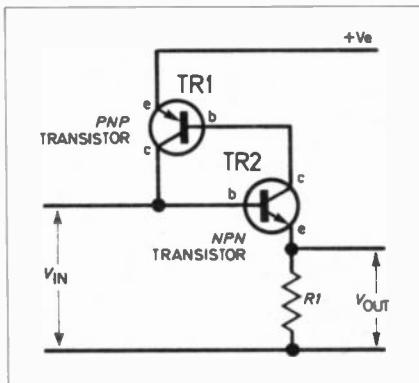


Fig. 7.4. Complementary transistor arrangement (*n-p-n* and *p-n-p*) connected to obtain very high gain.

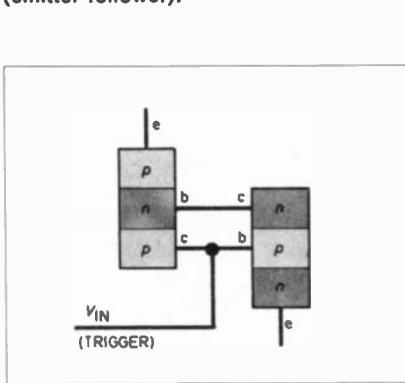


Fig. 7.5. Shows the connected regions of the two transistors of Fig. 7.4.

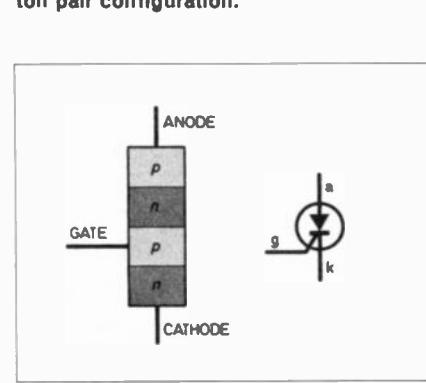


Fig. 7.6. Transistors of Fig. 7.5 combined to make a thyristor.

The advantage of this amplifier is that it has high input impedance (it draws little current on its input side), but has low output impedance (it can provide a lot of current on its output side). It is useful for connecting a high-impedance output to a low-impedance input when we do not need voltage amplification.

## INCREASING GAIN

Fig. 7.3 shows two transistors connected, so that the emitter current from one becomes the base current of the other. If the gain of TR1 is  $h_{FE1}$ , then  $I_{E1} = h_{FE1} \times I_{B1}$ . For TR2,  $I_{E2} = h_{FE2} \times I_{B2}$ . But  $I_{B2} = I_{E1}$ . Therefore  $I_{E2} = h_{FE2} \times h_{FE1} \times I_{B1}$ . The gain of the Darlington pair, as this arrangement is known, is the product of the gains of the two transistors. If they each have a gain of 100, the gain of the pair is 10,000.

We can connect *npn* and *pnp* transistors to form a high-gain pair as in Fig. 7.4.

When power is first applied, TR2 is off, so its collector voltage is high. This makes the base of TR1 high so TR1 is off too. No current can flow to TR2 so it stays off. The transistors hold each other off and no current flows.

If we then supply a very small current to the base of TR2, it begins to turn on. Voltage at its collector falls, drawing current from the base of TR1 (current flows *out* of the base of a *pnp* transistor, not *into* the base as in an *npn* transistor). TR2 begins to turn on, allowing current to flow to the base of TR2 and turning it further on. Its collector voltage falls further, turning TR1 further on. This process continues—even though the original source of current at the input is removed—until both transistors are fully on and a large current is flowing through them. Here we have a circuit which can be turned on by a very small, very short pulse.

Fig. 7.5 shows how the regions of TR1 and TR2 are connected and in Fig. 7.6 we see how to make a single four-layered device which has the same action as the two transistors. Such a device is called a thyristor.

A thyristor is a current-switching device. No current flows through it until a positive pulse has been applied to its *gate*. A small, brief pulse is enough. Then current flows indefinitely from *anode* to *cathode*. If the current is interrupted (for example by turning off the supply) or is reduced below a certain value, conduction stops and another pulse at the gate is required to start it again. Current cannot flow from *cathode* to *anode*, so this device has some of the properties of a diode.

## EXPERIMENT 7.1 Low-noise amplifier

The circuit of Fig. 7.7 can be assembled on *Minilab* as shown in Fig. 7.8. When you have built and tested it you will find that it gives a much louder sound than the one-transistor amplifiers already investigated.

Noise in an amplifier consists of currents caused by the random motion of electrons across the junctions of the transistors. These small randomly-occurring changes in current become amplified. We hear a hissing or rushing sound at the loudspeaker.

If a large amount of noise occurs in the first stages of an amplifier, the noise currents are of the same order of size as the signal current from the microphone. Amplification acts on signal and noise equally, causing a noisy output. It is therefore particularly important to minimise noise in the first stages.

In this circuit we use BC109 transistors which are specially made to have low noise. They also have high gain. Noise is kept to a minimum by making the collector current small in the absence of any signal. Ignoring R8,  $I_C$  is approximately  $12/470,000 = 25\mu A$ .

The fluctuations in  $I_B$  caused by a signal from the microphone cause voltage fluctuations at the R7/TR1 collector junction, and hence at the base of TR2 which acts as a second amplifier. Now that the first stage

of amplification is complete we can allow greater collector current. Hence the low value of R11 compared with R7.

Further amplification by TR2 gives a varying voltage which is coupled by C7 to TR3. The latter is wired as an emitter-follower; no further amplification is required, but the high impedance output of the low-noise amplifier must be matched to the low impedance of the speaker.

Here we do not need a low-noise transistor but prefer instead one which can carry a larger current. Since a ZTX300 can carry up to 500mA, R15 could be reduced to  $18\Omega$  giving an increase of volume. An  $80\Omega$  loudspeaker could be wired in place of R15 and LS1 and would also give greater volume.

Try holding the microphone close in front of the loudspeaker (Fig. 7.9). You should hear a loud high-pitched whistle. Small noises in the room are picked up by the microphone, amplified, and are emitted by the loudspeaker. Now they are louder and are picked up again and amplified again.

## EXPERIMENT 7.1

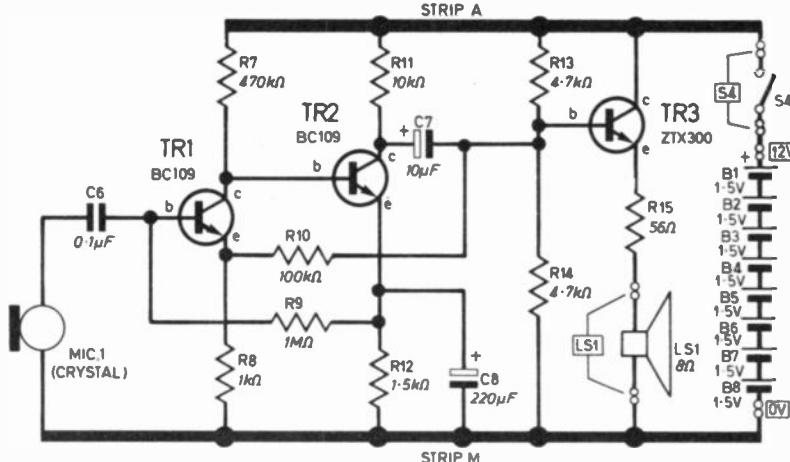


Fig. 7.7. Circuit diagram of a high gain, low noise amplifier with emitter follower (last stage).

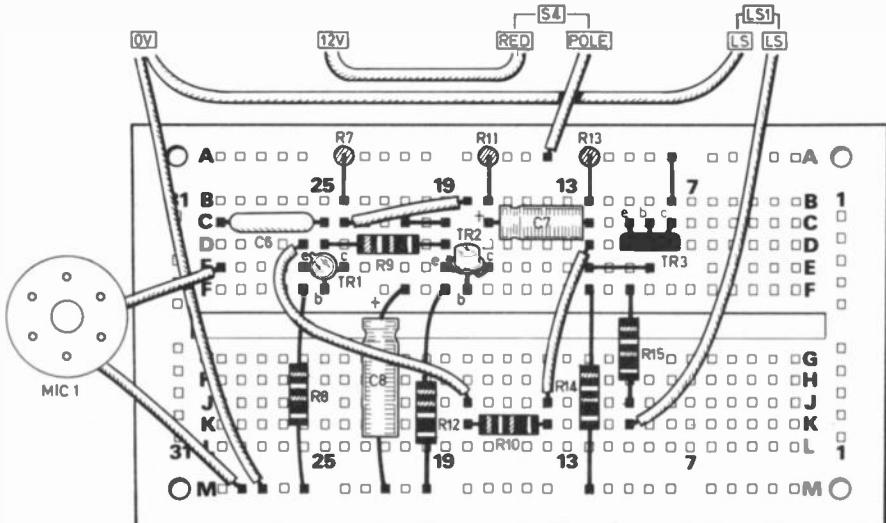


Fig. 7.8. The layout of the components on the Verobloc for the circuit in Fig. 7.7 (Expt. 7.1).

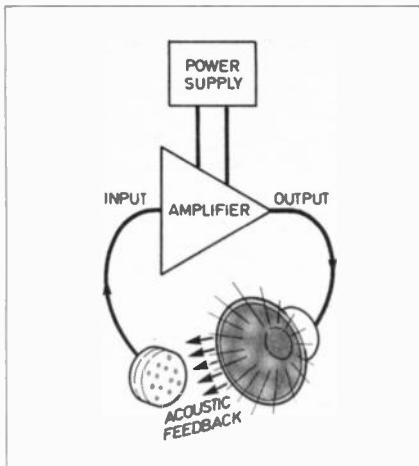


Fig. 7.9. Acoustic feedback (positive feedback).

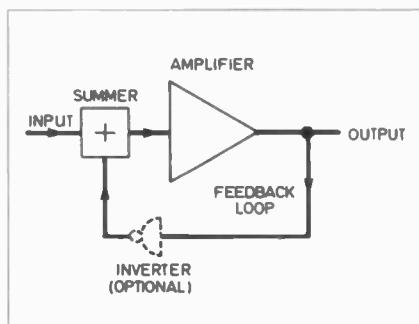


Fig. 7.10. A feedback loop.


This process continues until a very loud sound is being emitted from the speaker. The signal passes round and round a loop. It is amplified each time round. Its power becomes increased, using the power obtainable from the battery.

Most of the added power spreads into the air of the room, but a small fraction is fed back to the microphone. We have feedback. Since the signal fed back acts to produce a further increase in volume, we call this positive feedback.

## FEEDBACK LOOPS

Fig. 7.10 outlines the main stages of feedback. If we include an inverter (a NOT gate for example) in the feedback loop, we have negative feedback. A good example of this is found in the amplifier of Fig. 7.7. The voltage at C7 varies according to the signal. A small fraction of these voltage changes is fed back through R10 to the emitter of TR1.

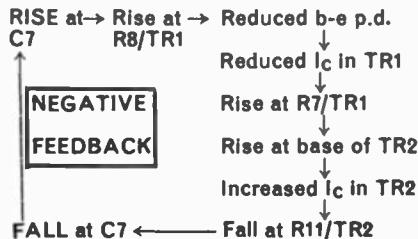How the negative feedback loop in Fig. 7.7 works is illustrated below:




Negative feedback tends to cancel out the rise at C7. The extent to which it does this is determined by the value of R10. The greater the feedback, the greater the effect and the lower the gain of the amplifier.


Although negative feedback reduces the gain of the amplifier, it has the advantage of stabilising its gain, irrespective of the  $h_{FE}$  of each transistor. The gain no longer depends on differences in  $h_{FE}$  due to manufacture, or to variations caused by changes in temperature.

R9 provides feedback of the potential at R12/TR2. It is unaffected by the audio signal, for this is bypassed by C8, as explained last month. The steady d.c. level at R12/TR2 is used to bias TR1. If the  $h_{FE}$  of TR1 happens to be exceptionally large, even a small signal could saturate the transistor, causing distortion. The same could happen if TR2 has extra-high  $h_{FE}$ . Feedback stabilises such conditions.

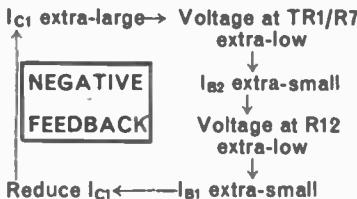If TR1 has extra-high  $h_{FE}$ , then the following chain of events occur:



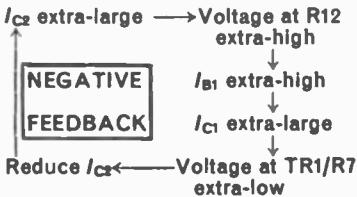If TR2 has extra-high  $h_{FE}$  the following occurs:



The effect of the loop is to stabilise the no-signal conditions of the amplifier.

## AMPLIFIER MODULE

The Amplifier Module to be installed in Minilab is essentially that shown in Fig. 7.7.

but has been re-drawn in Fig. 7.11 in the conventional circuit diagram format and so the component references follow on from the existing permanently wired Minilab components (including the Astable Module). The low-noise amplifier is a handy bench instrument which we shall use in later experiments. It is assembled on Verostrap already fitted to the Minilab and is to reside next to the existing module.

The layout of the components on the board and interwiring to Minilab are shown in Fig. 7.12. To carry out construction the Verostrap must first be removed from the rear panel. It should not be necessary to remove any wiring already connected to this board.

Before replacing the board, thoroughly check over the board, especially on the underside for solder bridges between tracks. Run the blade of a screwdriver between the tracks to dislodge any bridges which may be there.

## TESTING THE MODULE


The module may be tested by wiring up as shown in Fig. 7.13. Switch on at S7. Speak into the microphone to hear your voice reproduced in the loudspeaker.

## OPERATIONAL AMPLIFIERS

Operational amplifiers are very high-gain amplifiers ( $\times 200,000$  for example) which usually come in the form of integrated circuits. They normally work on a dual power-supply, as in Fig. 7.14, where we split the 12V battery supply to provide +6V and -6V.




The amplifier has two inputs. If both inputs are at the same voltage, the output voltage is 0V (relative to the 0V line). If the voltage at the non-inverting (+) input, is higher than that at the inverting (-) input, a positive voltage appears at the output. If the inverting (-) input has the higher voltage, a negative voltage appears at the output. All input voltages must lie between the limits of the power supply (between -6V and +6V in this case).

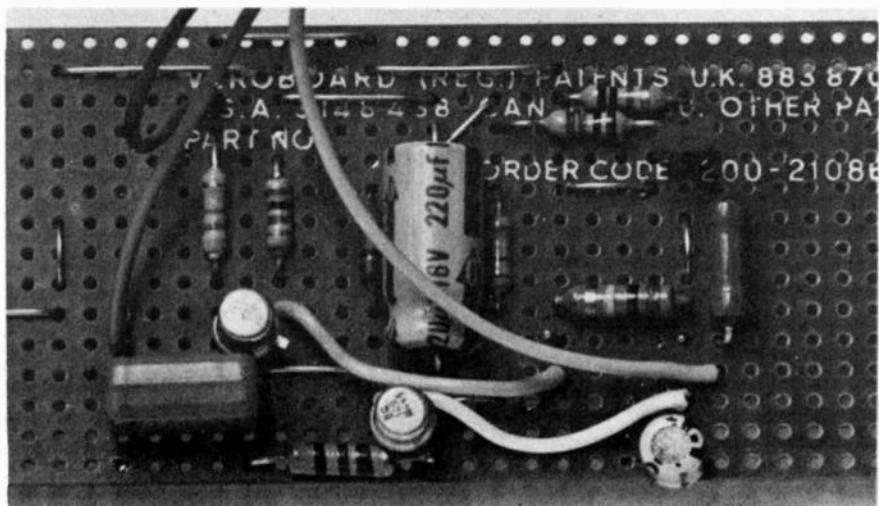Close-up of the Amplifier component layout section on the Verostrap.



## AMPLIFIER MODULE

Fig. 7.11. The complete circuit diagram for the Amplifier Module to be fitted inside the Minilab. Note that the component reference numbers follow on from those already resident in the Minilab.

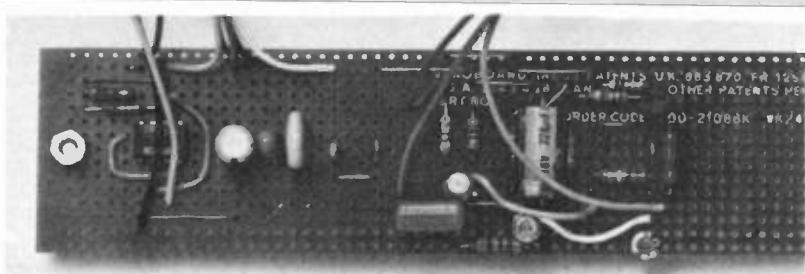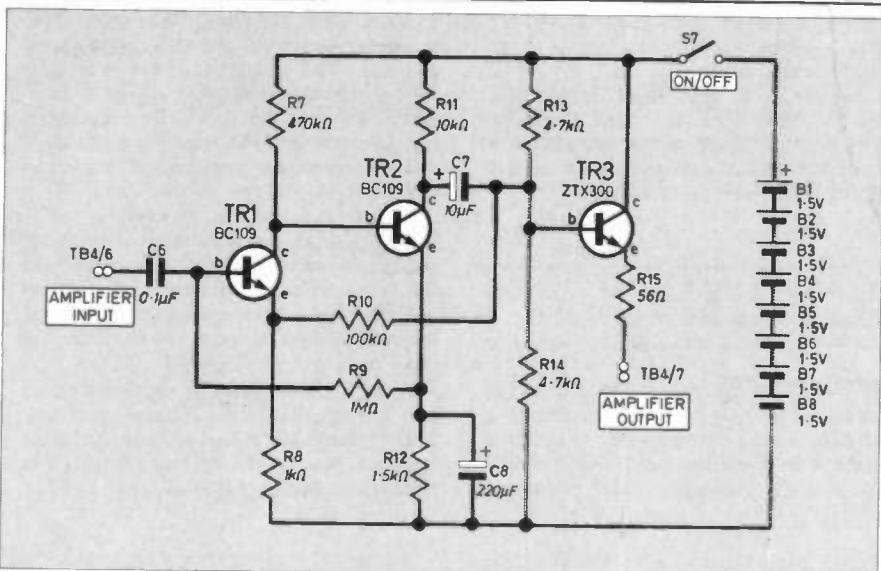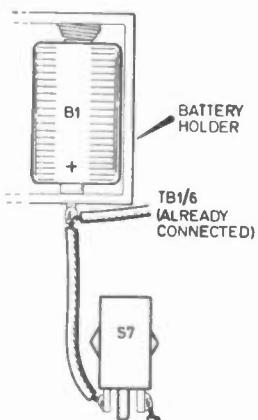

The amplifier components mounted on the Verostrip next to the Astable section.

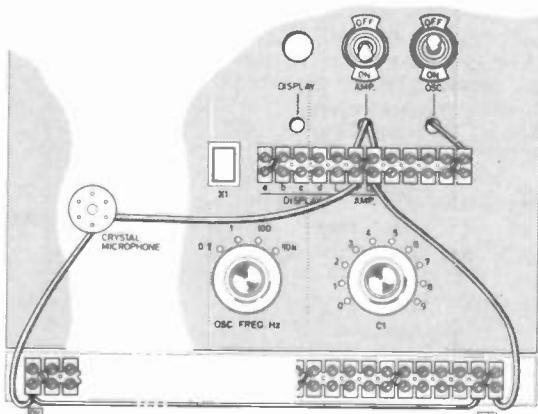
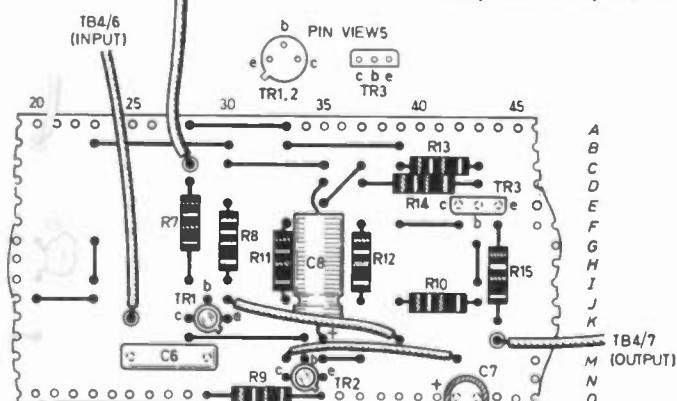


Fig. 7.13. Interwiring to test the installed Amplifier Module

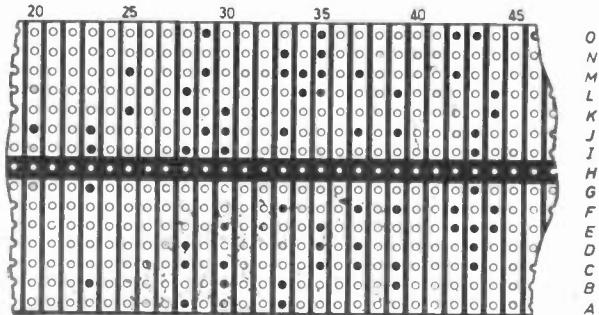


Fig. 7.12. The layout of the components for the Amplifier Module on the Verostrip together with complete interwiring details. The OV line for the amplifier is obtained from the Astable Module.



Minilab from panel showing the amplifier section.

The output voltage of the 741 op-amp cannot swing to the full extent toward  $-6V$  or  $+6V$ , though in other types, such as the CMOS op-amps, voltage can swing freely over the whole range.

Op-amps have high input impedance;  $2M\Omega$  for the 741 and as high as  $10^{11}\Omega$  for CMOS op-amps. Their output impedance is only a few tens of ohms. Now let us see how these amplifiers may be used.

## EXPERIMENT 7.2 Op-amp voltage follower

In Fig. 7.14 the output of IC2 is fed back to the inverting input. VR2 acts as a potential divider to provide a variable voltage source of between 0V and  $+6V$ . The layout for this experiment is shown in

## EXPERIMENT 7.2

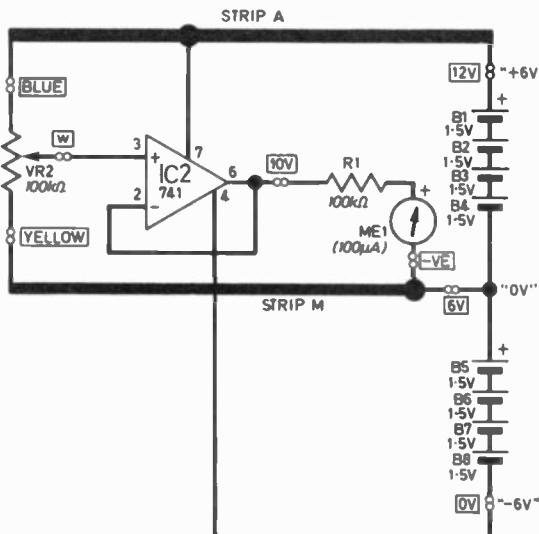


Fig. 7.14. Circuit for investigating the action of an op-amp voltage follower, Expt. 7.2.

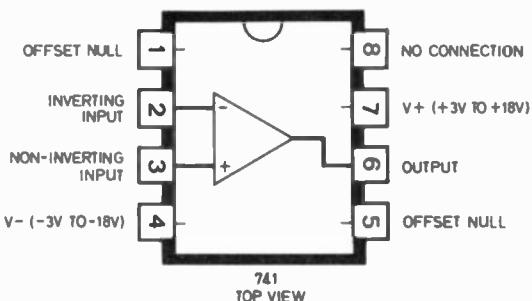


Fig. 7.15b. Pinning details for the i.c. op-amp, 741 used in Expts. 7.2 and 7.3.

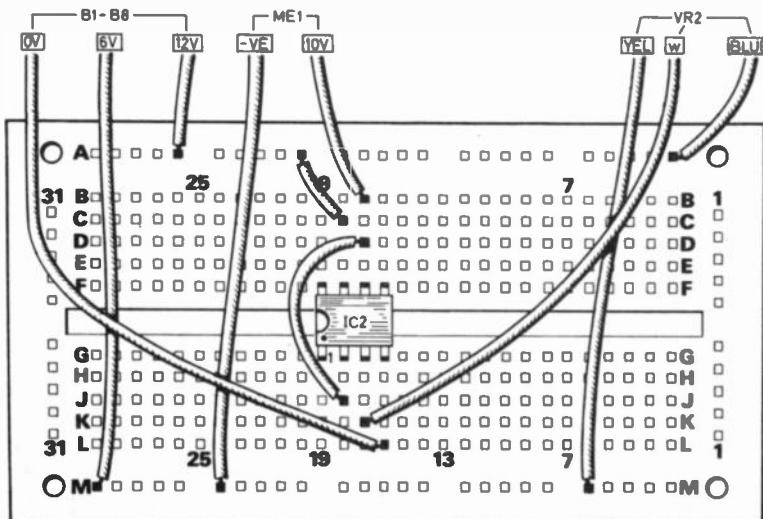


Fig. 7.15a. The layout of the components on the Verobloc for Expt. 7.2.

put changes so as to keep both inputs at equal voltages. If pin 3 is raised to  $+2V$ , pin 3 must be brought to  $+2V$  too. The circuit can be stable only when the output is  $2V$ . As a result, output follows input. The amplifier behaves in a similar way to the emitter-follower circuit (Fig. 7.2). The uses of the circuit are the same too—linking a high output impedance to a low input impedance.

## PART 6 ANSWERS

- 6.1.  $5.7nF$ , or  $5700pF$ .
- 6.2. Storing charge, coupling parts of circuits, passing a.c. signals, smoothing out rapid voltage changes.
- 6.3. 3.3 microcoulombs.
- 6.4. Carbon—it is a conductor.
- 6.5.  $74 \cdot 2Hz$

## EXPERIMENT 7.3

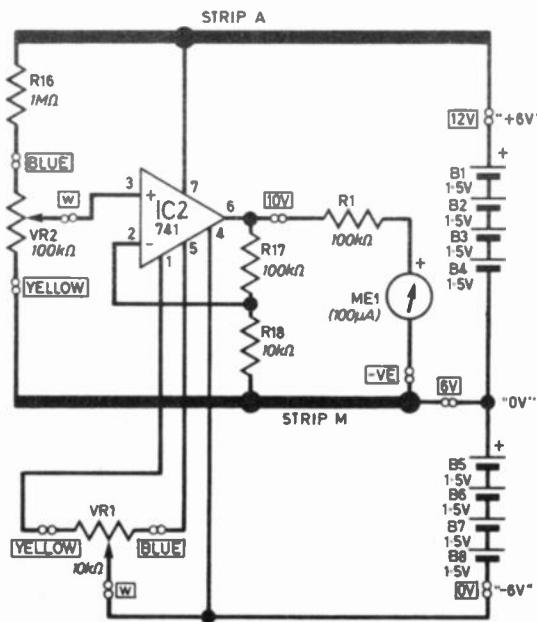


Fig. 7.16. The circuit of a non-inverting op-amp amplifier with fixed gain and offset null control.

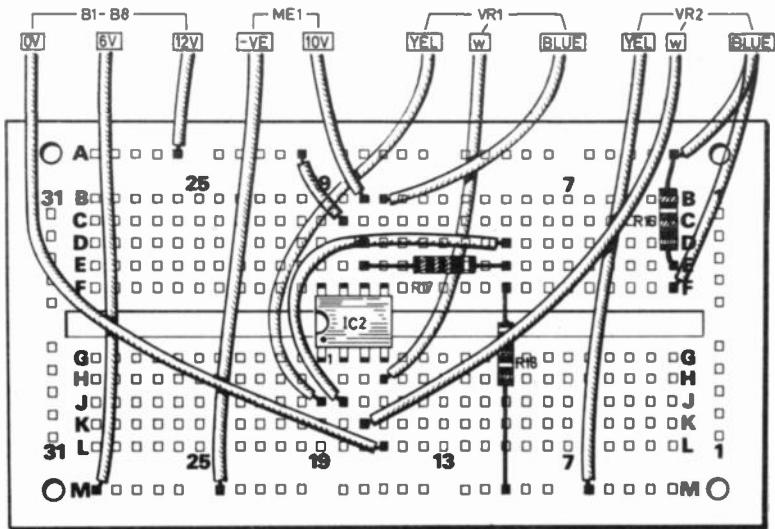


Fig. 7.17. The circuit of Fig. 7.16 wired up on the Verobloc.

### EXPERIMENT 7.3 Non-inverting amplifier

Fig. 7.16 shows feedback being taken from a potential divider (R17/R18), so

#### QUESTION TIME

- 7.1. In the common-collector connection, which terminal of an *n-p-n* transistor is connected directly to the positive rail?
- 7.2. Which type of connection is used to minimise the Miller Effect?
- 7.3. How is the gain of a Darlington pair calculated?
- 7.4. Which capacitors are used for a.c. coupling in Fig. 7.7?
- 7.5. Why are BC109 transistors used for the first stages of amplification in Fig. 7.7?
- 7.6. What type of feedback is used to stabilise the gain of an amplifier?
- 7.7. What is the purpose of the offset null adjustment of an operational amplifier?
- 7.8. If pin 3 (Fig. 7.14) is taken to -3.5V, what will be the output at pin 6?
- 7.9. If pin 3 (Fig. 7.16) is taken to -0.1V, what will be the output at pin 6?
- 7.10. In Fig. 7.16 if  $R_{16} = 1\text{M}\Omega$ ,  $R_{17} = 6.8\text{k}\Omega$ , and the voltage at pin 3 = 0.01V, what will be the output at pin 6?

that only a fraction of the output voltage is fed back. This circuit may be wired up on the Verobloc as shown in Fig. 7.17.

No amplifier is perfect, so the output may not be exactly 0V when both inputs are equal. To begin with, plug the wires from pins 2 and 3 (*J18* and *K17*) directly into the 0V rail (strip *M*). Pins 1 and 5 allow for adjustment of the offset null; to carry out the nulling, you will need to connect the wire from *B17* to *ME1* "100μA" instead of "10V"; turn *VR1* until the meter reads exactly 0V. Do not alter *VR1* after this. Reconnect the wires according to Fig. 7.17.

Resistor *R*<sub>16</sub> forms a potential divider with *VR2*, and sets the maximum possible voltage at *VR2* wiper (fully clockwise) to 0.55 volts approximately.

$$\text{Max. voltage at wiper} = \frac{100\text{k}\Omega}{100\text{k}\Omega + 1\text{M}\Omega} \times 6\text{V} \approx 0.55\text{V}$$

Thus turning *VR2* we obtain a range of voltages from 0V to about 0.55V. Although there may be unevenness in the track of the potentiometer, it is reasonable to assume that the subdivisions of the scale from 0 to 9 correspond to voltages 0, 0.06, 0.12, 0.18, 0.24, 0.30, 0.36, 0.42, 0.49 and 0.55V, respectively. Read the output voltage on *ME1* for each setting (0 to 9) of *VR1*.

At each setting (except possibly the last) the output voltage is 11 times the input voltage. Gain is  $\times 11$ .

$V_{IN}$  is the voltage at pin 3. Pin 2 must be brought to this voltage. When the circuit is stable the voltage at *R*<sub>17</sub>/*R*<sub>18</sub> junction equals  $V_{IN}$ . Since *R*<sub>17</sub> and *R*<sub>18</sub> make a potential divider,

$$\begin{aligned} V_{OUT} &= \frac{R_{17} + R_{18}}{R_{18}} \times V_{IN} \\ &= \frac{100\text{k}\Omega + 10\text{k}\Omega}{10\text{k}\Omega} \times V_{IN} \\ &= 11 \times V_{IN} \end{aligned}$$

By choosing suitable values for *R*<sub>17</sub> and *R*<sub>18</sub>, we can set gain to *any value* within reasonable limits. Try using different values for *R*<sub>17</sub> and *R*<sub>18</sub>, then measure the gain obtained. Check this against the calculated value  $(R_{17} + R_{18})/R_{18}$ .

Also try connecting *R*<sub>16</sub>/*VR2* across the 0V and -6V rails and reversing the connections to *ME1*. Then you can see that the amplifier responds equally well to negative input voltages.

Note that the gain of this circuit is determined solely by the values of *R*<sub>17</sub> and *R*<sub>18</sub>. Variations in the performance of individual i.c.s, or variations due to temperature have no effect on gain.

In Experiment 7.3 we joined pin 6 to pin 2 making *R*<sub>17</sub> = 0. *R*<sub>18</sub> was the value of the load (the meter) connected between pin 6 and the 0V rail. If *R*<sub>17</sub> = 0, then gain =  $R_{18}/R_{18} = 1$ , as found by trial.

There will be more about op-amps in Part 12.

To be continued


# MAGNETIC LOCK

BY R.A. PENFOLD


ELECTRONIC lock designs are by no means a rarity, and published circuits of this type are invariably for combination locks. This design is rather different in that it is opened by a key, and the key is basically just four magnets. However, in order to open the lock the magnets must be in the right position simultaneously, and they must have the correct polarity.

Without the correct key a lock of this type is practically impossible to "crack", even in the case of a very simple design such as the one described here.

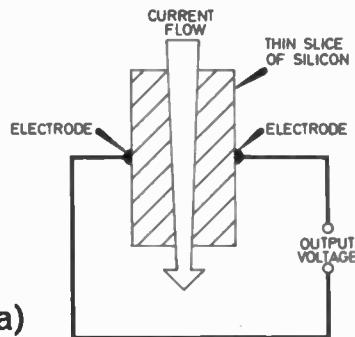The lock is mains powered, and it operates a relay which can in turn be used to operate a solenoid lock mechanism or any other item of electrical equipment. The circuit is built around four Hall Effect switches




(a)

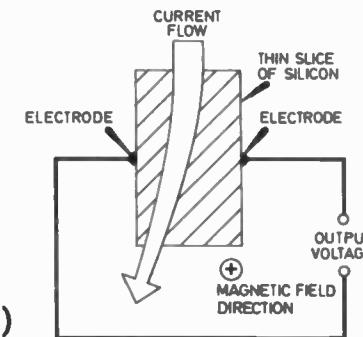

(b)

Fig. 1. Illustrates the basic principle of the Hall Effect sensor (a) in the absence of any magnetic field, output voltage is zero (b) with a magnetic field present (into the page), the current flow is distorted providing a voltage difference between the slice electrodes and consequently a voltage level at the output.

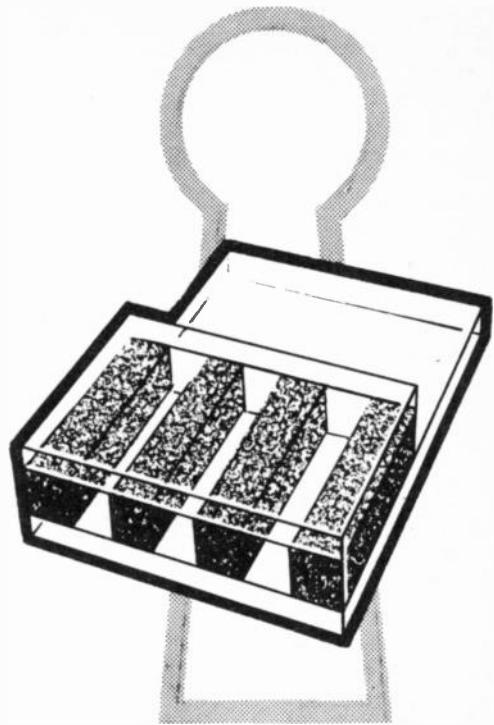

## The Key

to a lock that doesn't betray its presence. Virtually impossible to crack. Ideal for hidden compartments.

which are semiconductor devices that respond to a magnetic field.

### HALL EFFECT SWITCH

A Hall Effect sensor is basically just a thin slice of silicon fitted with two electrodes, as shown in Fig. 1(a). If a current is passed through the slice of silicon a potential gradient will be produced in the silicon. In other words there will be zero volts at the bottom of the slice, steadily rising to the full supply voltage at the top of the slice. There will be about half the supply voltage at each of the electrodes as these are both half way up the slice of silicon. This gives no voltage difference across the two electrodes, and zero output voltage.

A magnetic field has the effect of deflecting the current carriers in the silicon slice, and this is similar to a magnetic field deflecting the electron beam of a cathode ray tube. If the magnetic field is in the direction indicated in Fig. 1(b) then this deflection results in a distortion of the potential

gradient, with a consequent rise in voltage at one electrode and a voltage reduction at the other electrode.

If the magnetic field is reversed there will be an opposite distortion of the potential gradient, giving an identical change in voltage at the electrodes, but of the opposite polarity.

Thus a magnetic field gives an output voltage from the sensor, and the polarity of the output voltage is dependent on the polarity of the magnetic field. The output voltage is also proportional to the strength of the magnetic field incidentally.

A Hall Effect sensor will only respond to a magnetic field in the direction shown in Fig. 1(b), or a field in the opposite direction. A magnetic field at right angles to this direction will give no output voltage at all.

## HALL EFFECT DEVICES

The Hall Effect devices used in this design are all TL170C Hall Effect switches, and the block diagram of Fig. 2 shows in simplified form the arrangement used in the TL170C (which is an integrated circuit and not just a simple Hall Effect sensor).

The output of a Hall Effect sensor is applied to a differential amplifier and provided a suitable magnetic field is applied to the sensor the output of the amplifier will go full positive (high, or logic 1) or fully negative (low, or logic 0), depending on the polarity of the magnetic field.

The output of the differential amplifier is fed to the input of a flip-flop which in turn feeds the base terminal of a common emitter switching transistor. At switch-on the output of the flip-flop goes low and the transistor is switched off.

## MAGNETIC FIELD

If a magnetic field of suitable strength and polarity is applied to the device the output of the differential amplifier will go high and "set" the flip-flop so that its output goes high and switches on the output transistor.

With the magnetic field removed the output of the differential amplifier returns to its quiescent level of about half the supply voltage, and the state of the flip-flop and output transistor remain unchanged. A magnetic field of adequate strength and opposite polarity to the original one sends the output of the differential amplifier low, and this "resets" the flip-flop and switches off the output transistor. Removing the magnetic field results in the output of the differential amplifier returning to its quiescent level of half the supply voltage, and there is no change in the state of the flip-flop or output transistor.

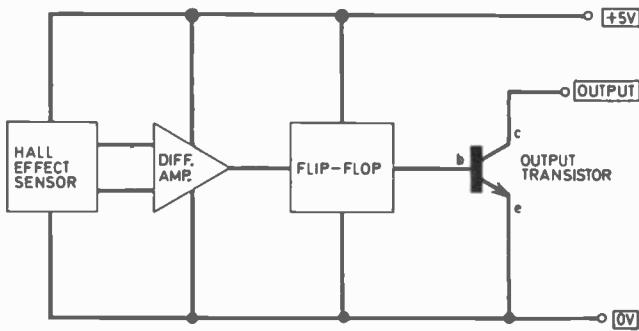


Fig. 2. Block diagram of the Hall Effect switch i.c.

## SWITCHING BY MAGNETIC FIELD

The device can therefore be switched from one state to the other by applying a magnetic field of suitable strength and polarity. In practice this means that applying one pole of a reasonably powerful magnet to one side of the device causes the output transistor to be switched on and to latch in the on state. Applying the other pole of the magnet to the same face of the device causes the output transistor to switch off and latch in the off state.

The device can be switched on and off in the same way if the magnet is applied to the opposite face of the device, but the poles of the magnet will have the opposite effect if this is done. In other words, if the device was previously switched on by a south pole and off by a north pole, applying


the magnet to the opposite face of the device will result in south pole switching it off and a north pole switching it on.

The TL170C is designed to operate from a 5 volt supply, and has an absolute maximum supply voltage rating of 7 volts. However, the output transistor can withstand a collector voltage of up to 30 volts and can handle collector currents of up to 20 millamps.
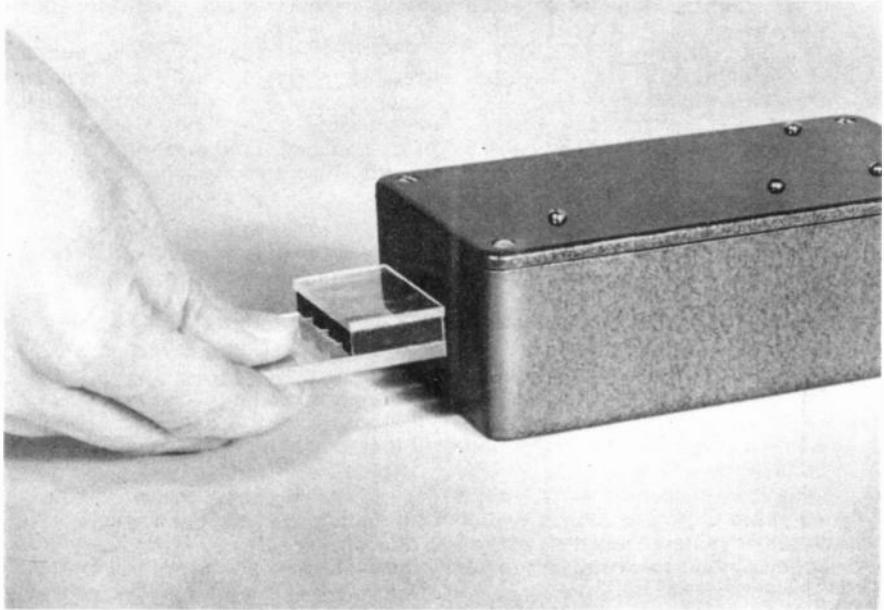
## THE CIRCUIT

Refer to Fig. 3 for the complete circuit diagram of the Magnetic Lock.

The four Hall Effect switches are IC1 to IC4, and these each have a discrete load resistor for the output transistor. The load resistors are R1 to R4. The output of each Hall Effect switch feeds the base of TR1, and a simple OR gate is formed in this part of the circuit by diodes D1 to D4.



The finished prototype being tested before installation and fitting of the terminal blocks.

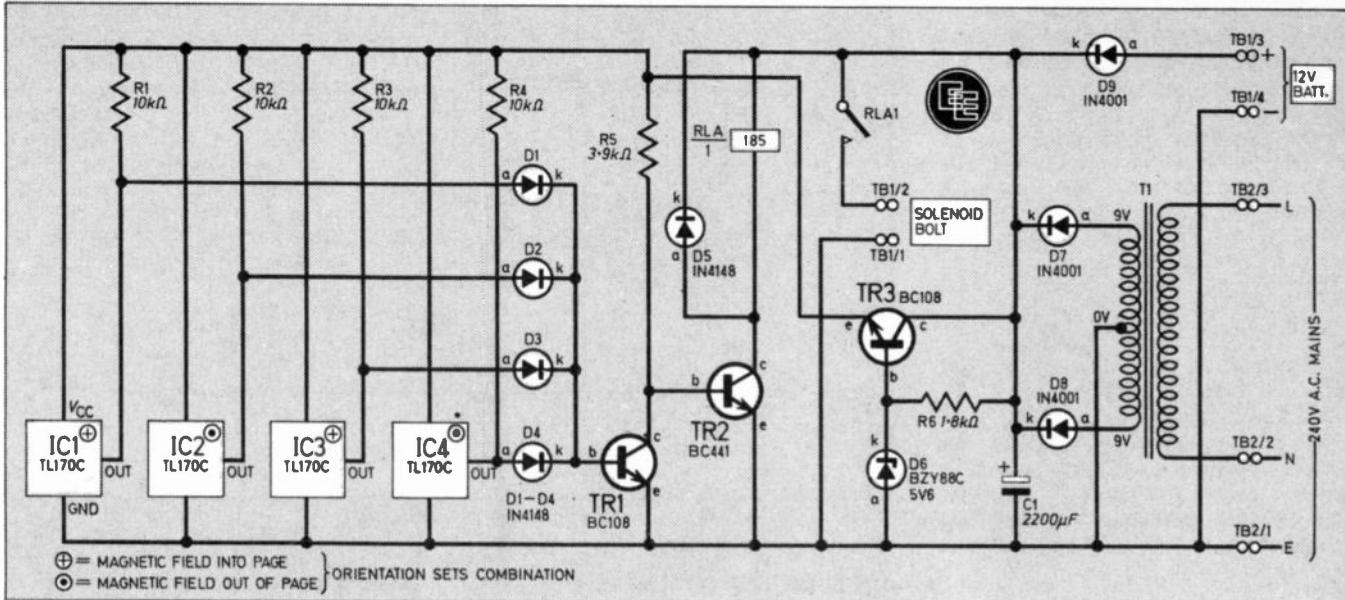


Fig. 3. The complete circuit diagram of the Magnetic Lock. The unit is mains powered but has battery back-up.

If one of the four outputs goes high it will feed a base current to TR1 via one of the gate diodes, and TR1 will be biased hard into conduction. If one of the outputs goes low it will not be able to cut off TR1 since one of the diodes will prevent it from tapping off any of the base current of TR1.

Thus, if any of the outputs are high TR1 will be switched on, and all four must be low in order to switch off TR1.

TR2 is the relay driver transistor, and with TR1 switched off TR2 is biased into conduction by R5 and the relay RLA is activated. If TR1 is switched on, TR2 becomes cut off and the relay is de-energised.

At switch-on the Hall Effect switches all assume the off state and their outputs all go high, switching TR1 on, and TR2 and the relay off. It is essential that the relay should not be activated at switch-on, as otherwise a brief power failure would be sufficient to make the lock open!

#### MAGNETIC KEY

If the magnetic key is used to switch on all four Hall Effect switches the four outputs all go low. TR1 switches off, TR2 switches on, and the relay is operated. Reversing the key switches the Hall Effect devices off again, and the circuit reverts to its original state with the relay switched off.

The key can therefore be used to open and close the lock, and in order to open the lock all four Hall Effect devices must be switched on. It is only necessary to switch off one of these devices in order to close the lock, although for maximum security all four devices should be switched off.


#### MAINS SUPPLY

The mains power supply uses T1, D7, D8, and C1 in a straightforward fullwave circuit which gives a well smoothed but unregulated d.c. output of about 13.5 volts under zero load. The output drops to around 10 volts when the supply is subjected to maximum load.

This unregulated supply is perfectly suitable for the relay driver circuitry, but a lower and more stable supply voltage is needed for the Hall Effect devices. This is derived from a series regulator circuit, comprising TR3, R6, and Zener diode D6.

⊕ = MAGNETIC FIELD INTO PAGE  
⊖ = MAGNETIC FIELD OUT OF PAGE

## HOW IT WORKS

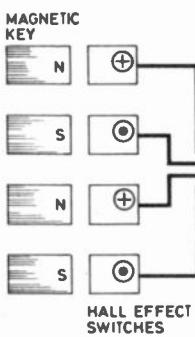

Four Hall Effect switches are operated by a "magnetic key" which is made up from four correctly positioned magnets to have the appropriate pole (north or south) facing their respective Hall Effect devices.

The outputs from the four Hall Effect switches feed a 4-input NOR gate. This gate produces a logic low output only when all four switches are activated, that is, produce a logic high.

The gate output operates a relay via a relay driver circuit. The normally open relay contacts close only when the output of the gate goes low, and these supply power to the solenoid lock mechanism (or other load) to release the bolt.

Thus it is necessary to operate all Hall Effect devices simultaneously to open the lock. The lock is de-activated simply by reversing the key so that the Hall Effect switches are turned off.

The above diagram shows the key in the position for opening the lock.

Although D6 gives a stabilised potential of nominally 5.6 volts, there is a voltage drop of approximately 0.6 volts across the base/emitter junction of TR3, so that a nominal supply potential of 5 volts is available from the output at TR3 emitter.

## BATTERY BACK-UP

A failure of the mains supply would of course immobilise the magnetic lock. To guard against such an eventuality a battery back-up has been incorporated in this design.

A 12 volt battery can be connected to the unit via connector block TB1/3, 4. The diode D9 will isolate the battery so long as the mains power supply circuit is delivering a voltage of 12V or more to the h.t. line. Should this potential fall, D9 will conduct thus bringing the external battery into circuit.

## COMPONENTS

### Resistors

R1 10kΩ  
R2 10kΩ  
R3 10kΩ  
R4 10kΩ  
R5 3.9kΩ  
R6 1.8kΩ  
All 1/3W carbon ±5%

See  
**Shop Talk**  
page 233

### Capacitor

C1 2200μF 16V p.c.b. elect.

### Semiconductors

IC1-4 TL170C Hall-effect switch i.c. (4 off)  
TR1 BC108 silicon *npn* transistor  
TR2 BC441 silicon *npn* transistor  
TR3 BC108 silicon *npn* transistor  
D1-5 1N4148 diode (5 off)  
D6 BZY88C5V6 5.6 volt 400mW Zener diode  
D7, 8, 9 1N4001 diode (3 off)

### Transformer

T1 Standard mains primary, 9V - 0V - 9V secondary rated at 75mA, or more

### Relay

RLA 6/12 volt coil 185 ohms or more, and contacts of the required type and rating (see text).

### Miscellaneous

Case (see text). 0.1in matrix strip-board (36 holes by 21 strips). 4-way connector block (TB1). 3-way (mains) connector block (TB2). Mains lead and mains plug fitted with 3 amp fuse. Four 1in by ½in (25mm by 6.35mm) bar magnets (Maplin or Electrovalue) wire, solder.

# CONSTRUCTION starts here

## CIRCUIT BOARD

With the only exception of the mains transformer T1, the components are all assembled on a 0.1in pitch stripboard. This has 21 copper strips by 36 holes. The component layout is shown in Fig. 4. Construction of the component panel is quite straightforward, and there are only three breaks in the copper strips.


## RELAY

If the relay is a modern miniature type having a plastic casing it can be glued to the board, and two pieces of single strand tinned copper wire can be soldered in place so that they help to hold the relay in position. The relay coil is then wired to the board using a couple of short insulated leads.

With other types of relay it might be necessary to devise some other method of mounting, but any reasonably modern relay should be small enough to fit into the available space on the board (although the board can obviously be made larger if necessary).

Make sure that the relay has contacts of adequate voltage and current rating for whatever load they will control, and also ensure that the relay is a six or 12 volt type having a coil resistance of no less than 185 ohms.

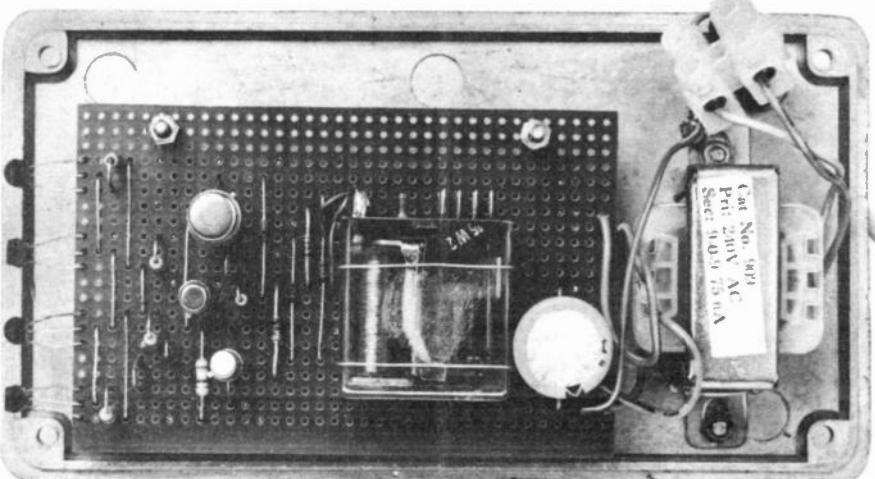
Plan view of the lid containing the assembly. Note that the battery back-up diode has not yet been fitted, and wiring to the terminal blocks is yet to be completed. Also, the relay flying leads are still to be attached.


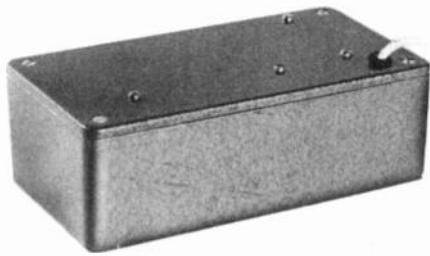
## HOUSING THE UNIT

Mechanically the construction of the unit must be varied to suit the exact application of the lock and the conditions under which it will operate. The case housing the electronics should obviously be a strong metal type and should be installed in such a way that there is no easy way for an unauthorised person to gain access to the circuitry. A diecast aluminium box is probably the best choice.

The key will operate the Hall Effect devices at a maximum range of about 5 or 6mm, and, like most substances, aluminium does not significantly hinder a magnetic force.



The completed unit housed in a robust metal case.

With the component panel mounted so that the Hall Effect devices are next to one side panel of the case, and the leadouts of the Hall Effect devices formed to bring these components against the side of the case if necessary, the key will operate the circuit even through a very thick case provided the key is accurately positioned.

## MAKING THE KEY

The key itself consists of four 25mm x 6.4mm bar magnets glued between two pieces of plastic or plywood, as can be seen in Fig. 5 and the accompanying photograph. The Hall Effect switches are orientated on

# MAGNETIC LOCK

COMPONENTS  
approximate  
cost £14.50



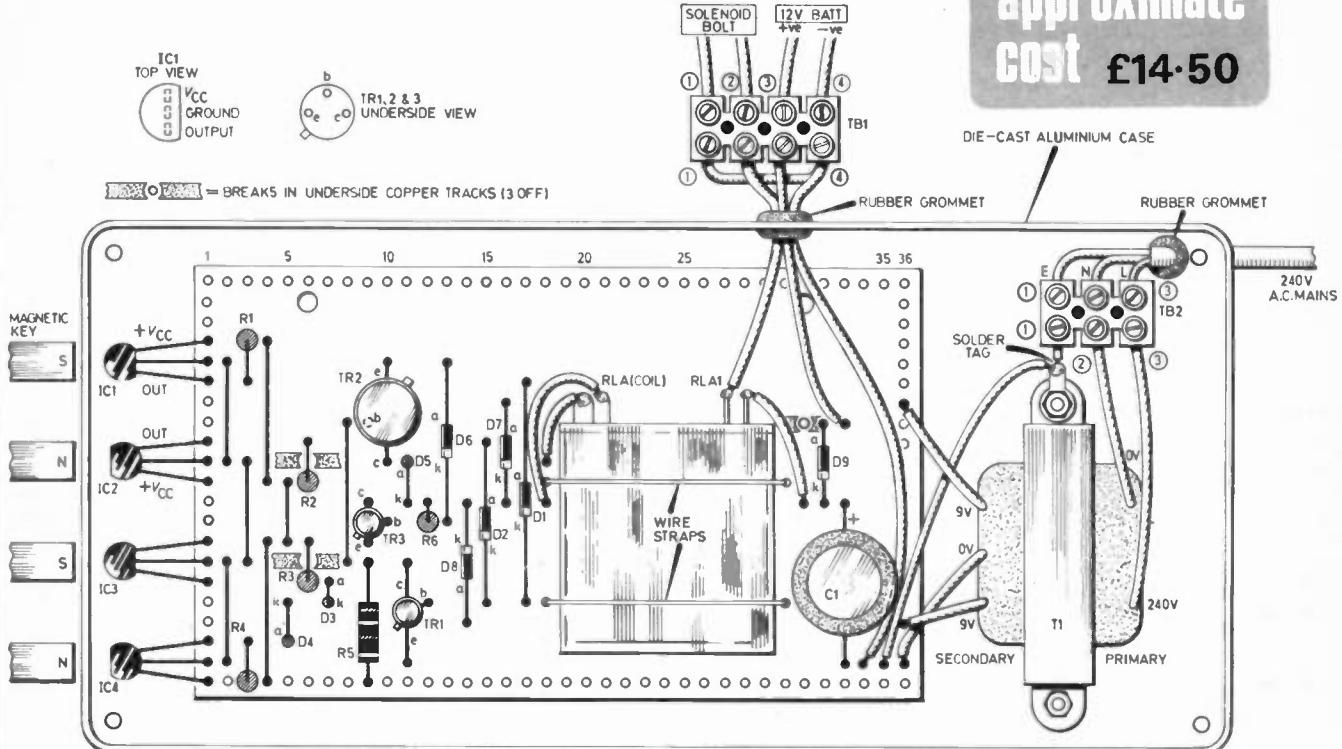


Fig. 4. The layout of the components on the topside of the stripboard and position within the diecast aluminium case. Note the orientation of the sensors to agree with the magnetic key, details below. Note that there are three breaks to be made in the strips on the underside.

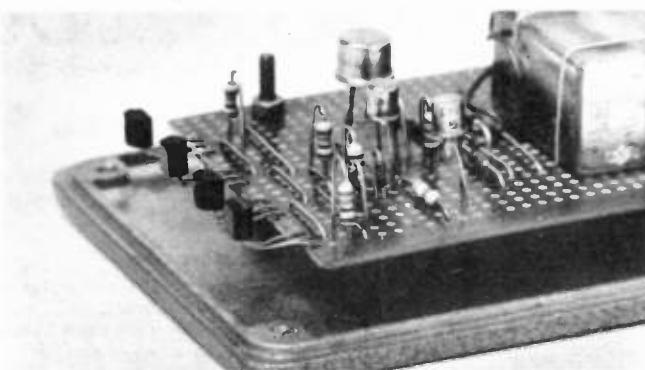

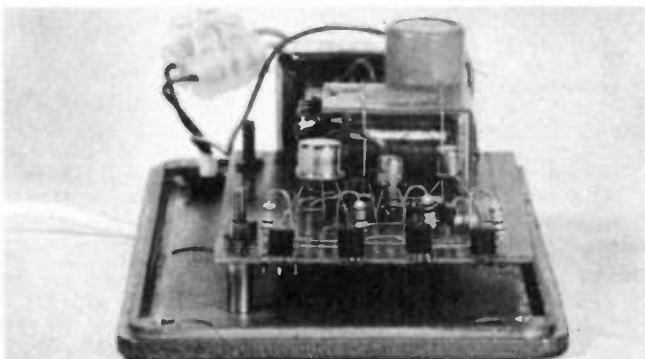Shows the orientation and position of the Hall Effect i.c.s in relation to the board and case.



Shows method of mounting the board to the case; two 10mm long plain spacers are employed.


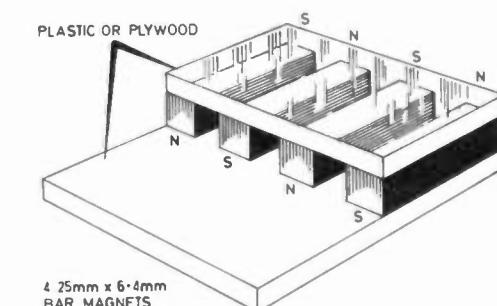


Fig. 5. Construction details for the magnetic key.

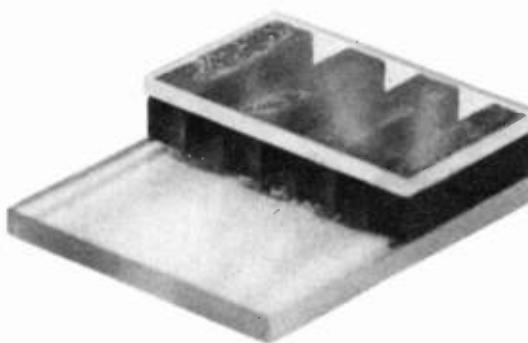


The prototype magnetic key.

the component panel in such a way that the key must present alternate north and south poles to the unit in order to operate it, and the magnets are not lined up with the same polarity.

If the magnets are lined up side by side with alternate polarities they will tend to attract one another and hold together in one lump. If two magnets next to one another have the same polarity they will not hold together and will repel one another slightly. This should eliminate any problems with getting the magnet polarities correct. Of course, the spacing of the magnets must match that of the Hall Effect switches (12.7mm between centres).
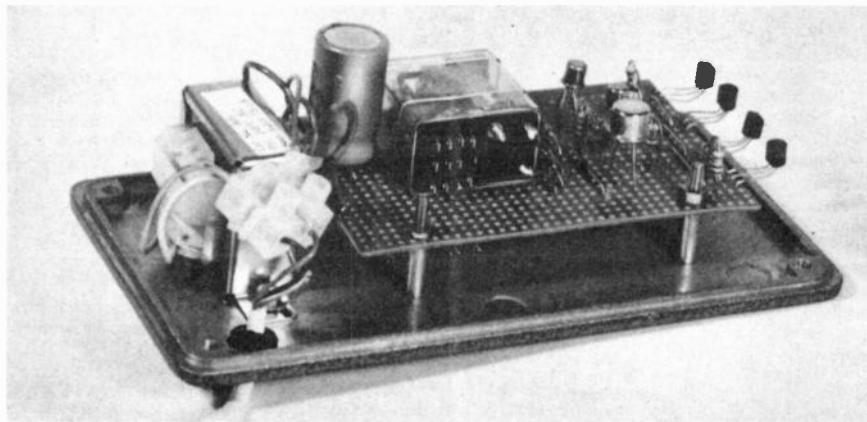
## OPERATION

Applying the key to the unit at the correct point and with the correct orientation will cause the lock to open, and rotating the key through 180 degrees (end-over-end or sideways) will close the lock. Trial and error can be used to find which orientation produces which effect.



The near completed prototype unit. Note that we have used a three-way screw terminal block in preference to the two-way block seen here.

In theory it is possible to open the lock using a single magnet if you know exactly where to apply the magnet, and what pole to apply. In practice this is practically impossible, and there is a tendency to switch off one Hall Effect device when the magnet is positioned to switch on one of the others. The only easy way of

opening and resetting the unit properly is to make up a key.

If preferred, the Hall Effect devices can be mounted off-board, and connected to the board by way of three-way insulated cables. The devices can then be positioned at any desired points on the interior of the case. □



# FORMING AN ELECTRONICS CLUB

By T.R.de Vaux-Balbirnie

*Some words of wisdom for any member of staff thinking of embarking upon an exciting and rewarding enterprise, which will not be without its hazards.*

So you want to form an electronics club! There are things you should know because it is not going to be easy. The actual "electronics" part will probably be the least of your worries. The hardest part will almost certainly be that of finance. In these times of "tight" money, you are unlikely to obtain assistance from local authorities or school funds. Your only recourse will be self-finance and more will be said about this later.

### Club aims

You will need to establish the aims of the club, even though these aims may be rather vague. Is the club to

be educational and used to supplement existing courses? Perhaps it will be organised simply to improve technical skills in circuit building. Is it to have a leaning towards audio and musical work or radio and TV? Is it going to be a "computer" club?

Most likely, it will be a club of general activities where members engage in building their own projects with you acting as adviser.

Will the club be willing to help in related fields like P.A. for sports events or stage lighting for the drama group? In return for a "home" and the use of electricity and perhaps some equipment it will probably be necessary to make yourselves useful in some such activities.

With broad aims defined, it then becomes necessary to

discuss the funding arrangements.

### Funding

Although existing bodies may be unwilling to give money towards the running costs, it is possible that they will grant you a loan. Although loans have the nasty habit of having to be repaid, they can be very useful in getting the club started.

Another idea is to charge an entry fee—non-returnable in cases of "dropping out"—to be used to purchase "communal" components for the club. These jointly-owned components are invaluable for experimental work. It will be understood that where communal components are permanently built into circuits they will have to be paid for.

Even when carefully used, such components will eventually fail—wire ends break off and so on—so a steady flow of cash is needed. Whether or not to fine members who damage components through carelessness is up to you but culprits are not usually easy to find!

### A repair service

Some cash may be raised by taking on basic repair work. The club (hopefully) will soon gain a reputation for speed and efficiency coupled with realistic charges. Since the public think of electronics as an extremely complicated subject, they will see any repairs as near-miracles! If you think that you would be out of your depth taking on this type of work consider the facts.

Semiconductor devices these days are extremely reliable and seldom fail. Likely causes of trouble are in mechanical components such as switches, potentiometers and plugs and sockets. An example is the earphone socket on a radio which silences the internal loudspeaker when the earphone is plugged into it. Components like this are easily and cheaply replaced. Poor quality sound from a tape recorder often indicates that the heads need thorough cleaning.

## Profitable Game

It is better to avoid mains equipment for repair just in case you should become legally involved over a poor job.

A TV game was brought along a few weeks ago with a "jumpy" bat. Most dealers were unwilling to repair it and the few who would quoted high fees and a long wait. It was obvious that the potentiometer in one of the hand controls had failed. Replacement took 10 minutes and cost 40p. The customer had his game back within the week at a charge of £2.50. He was delighted to pay it. Even at today's prices £2.10 will buy quite a lot of components.

Another way to raise money is to sell finished projects—again, avoid those which are mains operated. Projects for cars are popular, as are musical circuits for special effects. You may even run a service to install them!

## Component supply

You will need good suppliers of components. Unless you are lucky in having a properly geared-up dealer in your area, you will need to purchase by mail order. There are many excellent firms advertising in electronics magazines. Some supply free catalogues but often you will be asked to pay about £1. This may seem expensive at first but the possible savings will soon pay for the catalogues.

It will be necessary to shop around to some extent as prices can vary quite a lot. Remember, however, that it is foolish to save a few pence here and there on components only to be faced with extra charges for packing and postage. You must also keep an eye on V.A.T. when comparing prices and remember that V.A.T. is payable on the postage and packing charges also. It sometimes happens that a "nice

letter" from a bona-fide club will bring a free catalogue. Look for the larger advertisements in magazines—these can be almost a catalogue in themselves.

## Club Buyer

It is a good idea to appoint one member of the club to be in charge of purchasing and keeping an up-to-date "shortages list". He or she can work out the best time to place an order and how to do it in the cheapest way.

Although you should always look for special offers and "bargain packs" which often give excellent value, it is not always a good idea to buy untested components. These can waste a lot of time even though the price may seem very attractive.

When members use up communal components by building them into permanent projects, they should enter the item on the shortages list if the stock is run down. They should then pay for the components. Members will be expected to pay a realistic price for components bearing in mind the convenience of the method. This price may be set in an "internal catalogue" at, perhaps, 25 per cent above cost. The profit will restock communal components and go towards the cost of basic equipment.

## Storage

Good storage arrangements for electronic components are essential. Nothing is worse than boxes of assorted components. To begin with, egg boxes, margarine tubs and yoghurt containers may be used, but a more permanent system must be planned. Sets of interlocking plastic drawers are inexpensive and may be added to as the need arises. Large wooden drawers may be divided into compartments using hardboard. In this way, each value of resistor may have its own place. A "Dymo" labelling machine will be found very useful.

## Salvage

Let it be known that you are collecting—sometimes junk can furnish some good components. Unfortunately, some junk is totally useless. It is impossible to specify just what is acceptable and what is not so you will need to accept graciously anything which comes along and make the occasional discreet trip to the local authority refuse dump,

Local electronics industry sometimes helps bona-fide organisations. They will give away their own throw-outs providing you do not sell them. Circuit panels replaced under guarantee can provide a wealth of useful components. It is worth enquiring at your local radio and TV repair shop. Sometimes they will provide you with junk.

## Literature

Magazines are an essential source of ideas. You should subscribe to at least one of them. Enquire about the Everyday Electronics group subscription scheme. This enables educational establishments to obtain copies of the magazine at a special discount rate. As well as current issues, you should collect old magazines. These provide ideas and it often happens that old circuits are easily updated. Someone may be placed in charge of keeping a catalogue of useful articles for future reference.

## Equipment and Tools

You will need some basic equipment but, perhaps, some of it can be borrowed. A few soldering irons and multimeters will certainly be required. An oscilloscope is sometimes useful but is not essential. Certain basic tools like pliers, side cutters, wire strippers, tin snips, screwdrivers and files will be needed.

## Power supplies

Rather than using mains operated power supply units, batteries will be found more convenient. Many circuits use 9 volt supplies and the

physically larger batteries will be found cheaper in the long run than the smaller ones so use PP9s rather than PP3s. An alternative is to tape together two 4.5 volt "bell" batteries connected in series—these provide an excellent power supply capable of delivering fairly high currents. An excellent life may be expected in normal service.

For car circuits, access to a 12 volt battery will be needed for testing. Sometimes you can make do with three off 4.5 volt batteries in series but where high currents are required a car battery or some "Ni-Fe" cells will be needed. When using batteries like these it is essential to provide a line fuse since an accidental short circuit could allow an enormous current to flow.

## Materials

Although much experimental work will be carried out on prototype boards like "S-Decs", plenty of stripboard or Veroboard will be needed for permanent work. Veroboard with a pitch of 0.1 in will be found very convenient. Materials for making printed circuits will be found useful at times.

You will need a ready supply of single core connecting wire as well as the stranded variety. A small stock of sheet aluminium will also be found useful.

Make up plenty of lengths of stranded wire with combinations of crocodile clips, plugs and bare ends. These are invaluable.

Good luck with the club, but beware! It is likely to take you over!



**Everyday  
ELECTRONICS**

The MAY issue brings an Extra  
**8-PAGE SUPPLEMENT**

A Constructors Guide to discrete and  
integrated devices

# **COMPREHENSIVE PUBLIC ADDRESS SYSTEM 50 WATTS OF POWER**

SEVEN INPUTS—Mic (4); Disc; Tape; Auxiliary—FULL MIXING OF ALL INPUTS—VU METER—8 OHM and 166 (line) OUTPUTS—OPERATES FROM EITHER MAINS OR 12V CAR BATTERY—TWO UNIT CONSTRUCTION.



## **TWO-TONE TRAIN HORN**

Another realistic effect for the model railway enthusiast.  
Simulates the sound made by the horn of a diesel or electric train.



## **L.E.D CAR VOLTMETER**

Monitors state of car electrics system under all conditions, by indicating battery voltage in 0.5V steps.

MAY 1982 ISSUE  
ON SALE  
FRIDAY, APRIL 16



## **BIG-NINE INDICATOR**

An extended form of dice, with 0 to 9 randomly indicated on 7-segment display.

# INTRODUCTION TO LOGIC

PART BY J. CROWTHER

## FLIP-FLOPS

There are four main types of flip-flop (bistable multivibrator) used in practice. They are:

- (1) The R.S. or S.R. (set/reset)
- (2) The R.S.T. (set/reset/trigger)
- (3) The J.K. flip-flop (this is the true storage unit)
- (4) The D-type flip-flop (data)

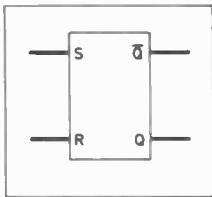


Fig. 12.1. Circuit symbol for an R.S. flip-flop.

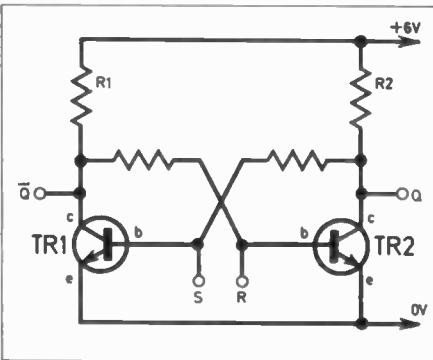


Fig. 12.2. Basic circuit of an R.S. flip-flop.

### (1) The Set/Reset flip-flop

The circuit symbol and basic circuit of an R.S. flip-flop are shown in Figs. 12.1 and 12.2 respectively.

On switching on, one transistor will start to conduct fractionally before the other, and in this case suppose we assume TR2 conducts first. This will cause a voltage drop across R2 and the output at  $Q$  will start to fall making the base of TR1 more negative thus reducing the current through TR1. The effect of this is to reduce the voltage drop across R1, making the output at  $\bar{Q}$  rise and consequently turning TR2 on even more giving a larger voltage drop across R2. The  $\bar{Q}$  output will drop still further and this sequence continues until TR2 is conducting fully and TR1 is cut off resulting the output at  $Q$  falling to nearly zero (logic 0) and output  $\bar{Q}$  rising to 6V (logic 1). This all happens almost instantaneously.

The transistors will stay in this state until a positive pulse is applied to the base of the "off" transistor, input  $S$  for TR1, switching it on. This will cause the voltage across R1 to drop so that output  $\bar{Q}$  falls to zero and the base voltage of TR2 also falls switching it off. This means there will be no voltage drop across R2, causing the output at  $Q$  to rise to 6V.

Once again the transistors will stay in this state until a positive pulse is applied to the base of TR2 at input  $R$ , switching the flip-flop back to the original state.

To summarise, a positive pulse at input  $R$  resets the  $Q$  output to logic zero and a positive pulse at input  $S$  sets the  $Q$  output to logic one. The first pulse will change the output state, the next pulse will change it back to its initial state, and so on.

### (2) The R.S.T. flip-flop

The R.S.T. flip-flop is a development of the R.S. type, requiring only one input terminal to change the output state of the flip-flop, see Fig. 12.3.

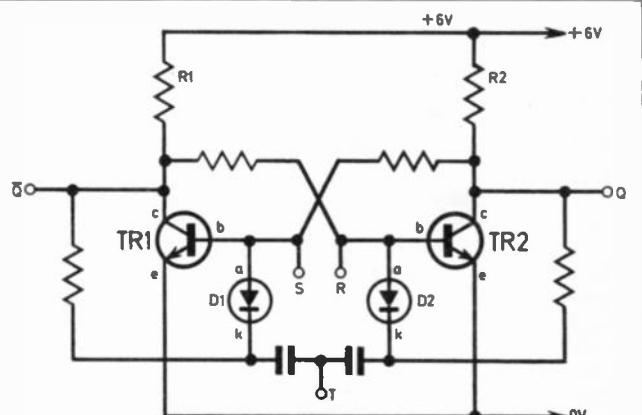


Fig. 12.3. Basic circuit of an R.S.T. flip-flop.

On switching on, suppose that TR2 is conducting and TR1 is cut off, so output  $Q$  will be at logic 0 (approximately 0.25V) and  $\bar{Q}$  at logic 1 (say 5V). Since TR2 is conducting its base will be 0.6V and TR1 base will be at 0V as it is turned off so the potentials on diodes D1 and D2 will be as in Fig. 12.4.

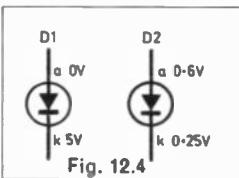


Fig. 12.4

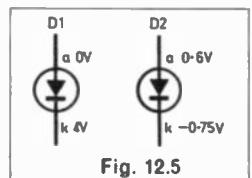


Fig. 12.5

For a diode to conduct, the anode (a) must be 0.6V positive with respect to the cathode (k), so here both diodes are reverse biased and will not be conducting and the two transistors will remain in the same state, that is TR2 on and TR1 off.

If a negative pulse of 1V is now applied to the  $T$  input, the cathode potentials of these two diodes would change, see Fig. 12.5.


Diode D2 is now forward biased and will conduct, and so reduce the base potential of TR2 to below 0.6V, switching it off. Consequently, there will be no voltage drop across R2 and output  $Q$  will rise to logic 1, TR1 will be turned fully-on causing output  $\bar{Q}$  to fall to logic 0.

The flip-flop will stay in this state until it receives another pulse at input  $T$ , upon which it will switch back to the original state, each pulse arriving at  $T$  being steered to the on transistor to switch it off by the diode steering circuit.

Since the pulses are fed to the diodes via capacitors, only a change in voltage level (from high to low) will trigger the flip-flop, so the R.S.T. is triggered by the falling edge of input pulse and not by a logic level as in the case of the R.S. type.

For this reason the R.S.T. flip-flop requires two input pulses to give one output pulse as shown in Fig. 12.6, and this circuit can therefore be used to divide a frequency by two. Cascading

Fig. 12.6. Circuit symbol for R.S.T. flip-flop showing operation. It acts as divider ( $\div 2$ ).

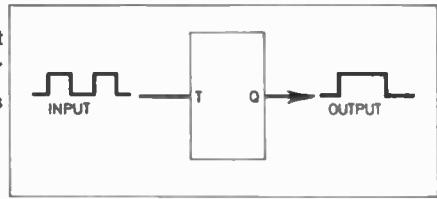

two R.S.T. flip-flops in series so that the output of the first triggers the second would divide by four, three would divide by eight and so on.

The  $R$  and the  $S$  inputs are retained in this circuit, and a logic level on either of these will override the  $T$  input.

Differences between R.S. and R.S.T. circuits:-

- Two inputs for the R.S., and only one for the R.S.T.
- A voltage level triggers the R.S. but a change in voltage level triggers the R.S.T.
- A stream of pulses to a single input of the R.S. (either the  $R$  or  $S$ ) will give no change of state after the first pulse, but a stream of pulses to the  $T$  input of the R.S.T. causes the output to change back and forth.

### (3) The J.K. flip-flop

The J.K. flip-flop is similar to the R.S.T. (see Fig. 12.7) the difference being that the cathodes of diodes D1 and D2 are connected to the  $J$  and  $K$  inputs instead of the  $Q$  and  $\bar{Q}$  outputs. The inputs applied to the  $J$  and  $K$  terminals must be complementary, that is if  $J$  is at logic 1 then  $K$  must be at logic 0, and vice-versa.

Suppose that TR2 is conducting and TR1 is cut-off at switch on, then output  $Q$  will be at logic 0. Now if a logic 1 is applied to the  $J$  input and a logic 0 to the  $K$  input, this would have no effect as the diodes are reverse biased. If a negative pulse of 1V is now applied to terminal  $T$ , D2 will be forward biased and therefore conduct and switch TR2 off, resulting in no volts drop across R2 and the  $Q$  output will be high (logic 1), TR1 turning on to give a logic 0 at  $\bar{Q}$ .

If a second pulse arrives at  $T$  with  $J$  and  $K$  still at 1 and 0 respectively, it will have no effect as it would be steered to the off transistor, therefore a trigger pulse at  $T$  will only change the

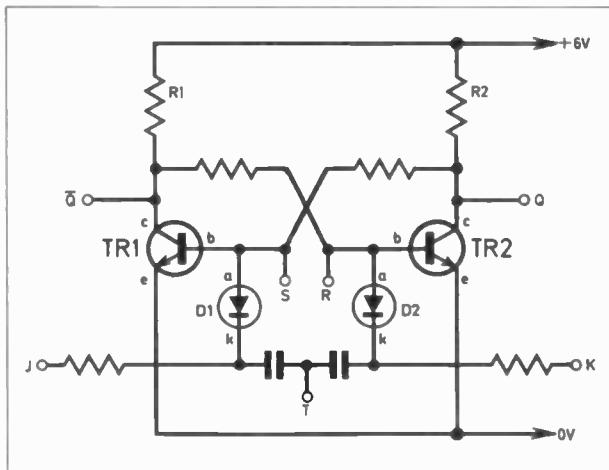


Fig. 12.7. The basic circuit diagram of a J.K. flip-flop.

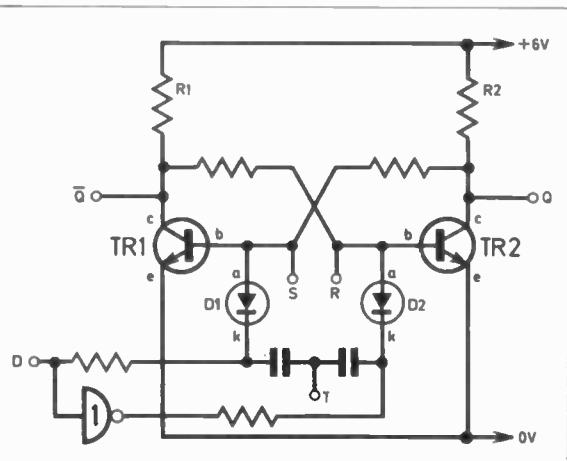


Fig. 12.8. The basic circuit of a D-type flip-flop. Compare with Fig. 12.6.

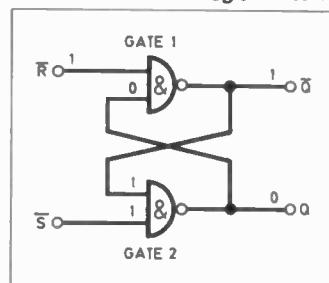


Fig. 12.9. Making an R.S. flip-flop from NAND gates.

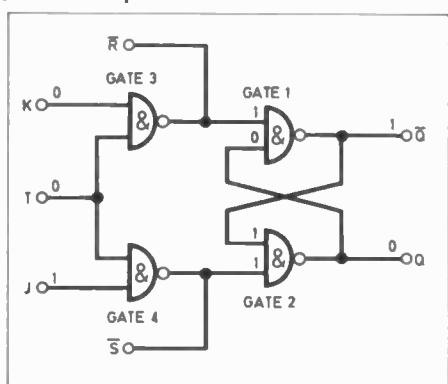


Fig. 12.10. Making a J.K. flip-flop from four NAND gates.

state of the flip-flop if the logic levels of the  $J$  and  $K$  inputs are reversed.

A trigger pulse at  $T$  will only change the state if the logic levels at  $J$  and  $K$  are different, so a logic 1 or 0 can be stored at the  $J$  terminal until a trigger pulse arrives at  $T$ , when the stored level will be released at output  $Q$ .

### (4) The D-type flip-flop

The D-type flip-flop is a modified version of the J.K. flip-flop, the  $J$  and  $K$  inputs being replaced by a single  $D$  (data) input, the complementary input to the  $K$  terminal being achieved by inverting the  $D$  input with a NOT gate whereas the  $D$  input if fed directly to the  $J$  terminal as shown in Fig. 12.8.

## MAKING FLIP FLOPS WITH LOGIC GATES

### (1) The R.S. flip-flop

An R.S. flip-flop can be constructed using two NAND gates, and suppose that on switching on, the  $Q$  output is at 0 and the  $\bar{Q}$  output is at 1 as shown. If both the  $\bar{R}$  and the  $\bar{S}$  inputs are at logic 1, there will be two 1's on the inputs of gate 2 holding its output at 0, and a 1 and 0 on the inputs of gate 1 giving a 1 on the output.

If the  $\bar{S}$  input terminal is changed to a 0, there will now be a 1 and 0 on the inputs of gate 2 resulting in a 1 at the output and this consequently puts two 1's onto the inputs of gate 1 changing its output to a 0.

Changing the  $\bar{S}$  input back to a 1, resulting in a 1 and 0 on the inputs of gate 2 giving a 1 at the output and with the two 1's still on gate 1 inputs, its output remains at 0, therefore the state of the flip-flop has not changed.

To change the flip-flop back to its original state, a logic 0 must be applied to the  $\bar{R}$  input. Therefore a logic 0 on the  $\bar{S}$  input sets the  $Q$  output to logic 1, and a logic 0 on the  $\bar{R}$  input resets the  $Q$  output back to 0.

Note that the transistor R.S. flip-flop requires logic 1's on the inputs to change its state, whereas the NAND gate version requires logic 0's, so the terminals are marked  $\bar{R}$  and  $\bar{S}$  instead of  $R$  and  $S$ , the bar over the letter indicating that a logic 0 changes the state of the flip-flop.

### (2) The J.K. flip-flop

If a logic 1 is applied to the  $J$  input and the  $K$  and  $T$  inputs are at logic 0, then the outputs of gates 3 and 4 will be at logic 1. Now the outputs of gates 3 and 4 are connected to the  $\bar{R}$  and  $\bar{S}$  inputs of an R.S. flip-flop consisting of gates 1 and 2 with the  $Q$  output at 0 and the  $\bar{Q}$  output at 1. If the  $T$  input is pulsed with a logic 1, the output of gate 4 would go low as it now has two 1's on the inputs, and this will change the state of the outputs of the flip-flop ( $Q$  will go to 1 and  $\bar{Q}$  will go to 0). A further pulse on the  $T$  input would return the  $\bar{S}$  terminal to 0 but this will have no effect on the output states of the flip-flop as a logic 0 is required on the  $\bar{R}$  input to change it back to its original state. A pulse on the  $T$  input will only change the output state if the logic states of the  $J$  and  $K$  inputs are reversed.

**THE END**

# Everyday News

## MARCHESA SPEAKS TO THE QUEEN

The Marchesa Maria Cristina Marconi and Princess Elettra Giovanelli, widow and daughter of Guglielmo Marconi, inaugurated the INMARSAT marine communications satellite system in London

WITH the inauguration of the INMARSAT marine communication satellite system in London recently, there unfolded another chapter in the fascinating story of maritime communications—a story which is really only 100 years old, for it was only in 1896 that Guglielmo Marconi managed to establish telegraphic contact between two points some 30 miles apart, so enabling ships at sea to be out of sight of, and yet to be in contact with the land as well as each other.

Elected Lord Rector of St Andrews University shortly before his death in 1937, Marconi entitled his inaugural speech, "The Path of the Inventor". In it he stressed his original intention, as the first developer of radio, to have been to "make the seas safer for seafarers by giving ships a means of communication". This too, is a declared aim of the INMARSAT organisation and it was fitting that the Marchesa Maria Cristina Marconi, his widow, was the guest of honour at the inauguration.

To inaugurate the INMARSAT system, the Marchesa Marconi spoke by satellite to the master of the liner Queen Elizabeth 2, Captain Peter Jackson. The ship was at that time in the South Atlantic, south east of Rio de Janeiro, headed for Cape Town on its world cruise, and the call went via the Southbury coast earth station in the USA.



To inaugurate the INMARSAT system, the Marchesa Marconi spoke by satellite to the master of the liner Queen Elizabeth 2, Captain Peter Jackson. The ship was at that time in the South Atlantic, south east of Rio de Janeiro, headed for Cape Town on its world cruise, and the call went via Southbury coast earth station in the USA. Calls were also made to two other ships—one in the Indian Ocean Region and one in the Pacific Ocean Region. In the first case, INMARSAT's Director General, Mr Olof Lundberg, spoke to the general cargo vessel Wakanami Maru, the call going via Yamaguchi, Japan. He then called the tanker Robert Miller off southern Victoria, Australia, via the new Ibaraki coast earth station in Japan. (Everyday Electronics exclusive photo).

TO: All INMARSAT ship earth stations  
From: All INMARSAT ship earth stations  
Subject: Welcome to INMARSAT

The global maritime satellite system that your vessel is equipped to use is now being run by INMARSAT— the International Maritime Satellite Organization. It gives me great pleasure, 80 years after my late husband pioneered maritime radio communications, to officially inaugurate this new era with a broadcast message to all ships by satellite.

Just as the invention of radio enabled communication for the first time between a ship at sea and land, so satellite communications permit a ship on the high seas to be connected to the worldwide automatic telecommunications networks, allowing rapid communication with virtually anyone in the world having a telephone or telex machine. This will provide the mariner closer contact with his kinfolk and friends on shore, and it will provide the master with the speedy communication necessary for the efficient management of a modern ship.

This reliable form of communication will also ensure that ships can rapidly summon assistance in the event of difficulty, and will lead to improved safety of life and property at sea.

May you find the INMARSAT service an increasingly useful one.

Maria Cristina Marconi


### Milestones

While on the subject of maritime communications, it is perhaps appropriate to reflect on a few milestones: In 1899, the American liner St Paul is believed to have been the first vessel to have "a floating wireless station aboard". In November of 1899, she received a wireless message from the Marconi station on the Isle of Wight.


In 1906, the radio telegraph distress signal SOS, a rhythmic three dots, three dashes, three dots in Morse code, was adopted at a Berlin conference as the international call for help at sea. Some persons interpret SOS as meaning Save Our Ship or Save Our Souls but the letters actually have no intrinsic meaning.



## ... from the World of Electronics

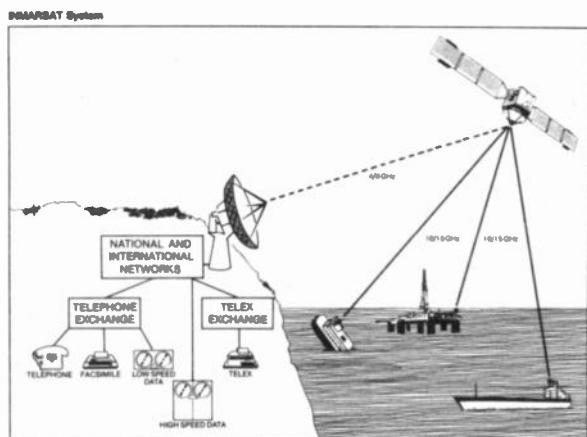

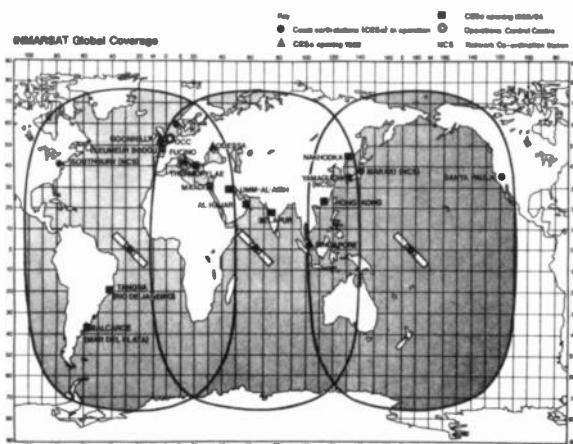Outline of the maritime satellite communications system.



Global coverage of the seas by the Inmarsat satellite system.

Sunday, April 14 in the year 1912 saw the tragedy of the sinking of the luxury liner *Titanic* with the loss of 1503 lives, including her wireless operator, Mr. J. G. Phillips, whose SOS was heard first by the radio officer on the ship *California* at 11.20p.m. The *Titanic* tragedy inspired regulations requiring increased transmitting power and 24-hour manning of radio rooms for passenger-carrying ships.

In 1922, the first ship-to-shore two-way voice communications took place between a station at Deal Beach, New Jersey and the *SS America*, 400 miles at sea.

The word *MAYDAY* was adopted in 1927 as the international distress call for

maritime radio telephone. "Mayday" originated in M'aidez, which is the French for "Help me".

In 1929, high seas radio telephone services became available to the public and technology developed fairly fast from then on. It was 1965 that saw the first commercial communications satellite, *Early Bird*.

The year 1976 saw the launch of the *Marisat* satellites over the Atlantic, Pacific and Indian Oceans. *INMARSAT* (which is where we came in) came into being on July 16 1979. February 1, 1982 saw *Inmarsat* leasing the commercial capacity on all three existing *Marisat* satellites as part of its initial space segment.

## END FOR THE VALVE

The end of an era has come with the production of the last domestic receiving valve by Mullard.

The Mullard name has been synonymous with receiving valves for over 60 years. More than 1,000 million have been produced by the company's Blackburn plant during the last 40-odd years.

It is estimated that it has taken over 80,000 man-years to develop and manufacture the billion or more valves, and that in total they have consumed some two million miles of wire, 25,000 tons of glass and 20,000 million metal parts.

## UK TOP SPOT

A survey of the investment intentions of 500 electronics companies in the USA revealed the UK as the favourite location for setting up overseas operations between now and 1985. West Germany came second and Ireland third.

The criteria included availability of skilled labour, transport, good communica-

tions and labour relations as well as financial incentives, the latter ranking only third in importance. But, warns the poll, the UK position only holds if the UK keeps in the EEC.

**SAFT (UK) Ltd** is spending £0.5 million on a new plant at Hampton, Middlesex, for making lithium oxide cells and batteries.

## ANALYSIS

### ENERGY UPDATE

The energy crisis of recent years has been overshadowed by more pressing anxieties of world trade recession and unemployment. There is even a glut of oil today but the long-term problems of energy supply have not gone away and possible solutions are still being vigorously pursued.

We are now reconciled to higher costs of energy although in fact all energy sources are fundamentally free. In a single week more energy falls on the earth from the sun than is contained in all our fossil fuels deposits built up through the ages. What costs money is its collection and conversion to useable form.

Direct conversion of solar energy into electricity is as yet uneconomic in favourable climates such as California, even more so in the UK where the present alternative energy favourites are harnessing of tidal power in the Severn Estuary, wave power on the Atlantic seaboard, and wind power at a number of proposed sites.

In terms of end-cost to the consumer, efficiency and continuity of supply, wave power could be the "best buy" according to laboratory tests and analysis backed up by small-scale sea trials. But the marine engineering problems are formidable and the final cost of getting electricity ashore on the most optimistic estimates is still much greater than that from land-based oil or coal-fired turbine generators.

Windmills are easier to erect and experimental systems are being built on Orkney and in Carmarthen Bay, initially with some 200kW power to be followed by 3MW units. But even a very large windmill only generates about one thousandth of the power of a conventional power station.

The immediate practical approach is conservation. Here micro-electronics plays a major role in "fine-tuning" of air conditioning systems. New levels of efficiency are being achieved in other areas such as lighting where the 16W 2D lamp from Thorn gives a light output comparable with a standard 100W incandescent bulb.

While the scientists, engineers and technologists are busy on the problem of future energy sources we can all help to conserve existing supplies. Waste not, want not, is an old saying but still a wise one.

Brian G. Peck

# RADIO WORLD

By Pat Hawker, G3VA

## Empire Broadcasting

Several years ago I wrote a short note under the heading "50 years of Empire broadcasting". How come? you may wonder, since it was not until this year that the BBC began holding a series of events in London to commemorate "the fiftieth anniversary of broadcasting to the world" marking the official start of the old "Empire Service" from Daventry in 1931, and inspiring *The Times* to pen a gushing piece on "A service on which the sun still never sets" in praise of Bush House's External Services.

In truth, these were services on which the sun very nearly never rose. For several years the BBC, and in particular its first renowned director-general, Sir John (later Lord) Reith, was firmly opposed to h.f. broadcasting which had been pioneered in the USA in the mid-twenties by Frank Conrad at Pittsburgh under the experimental callsign W8XK (later KDKA).

In fact it was not the BBC but a well-known British amateur radio operator, Gerald Marcuse, G2NM, who launched the first regular service aimed at listeners in all parts of the British Empire. This was in September 1927, some months before the BBC tentatively started experiments

using a Marconi transmitter, G5SW, at Chelmsford.

With Post Office permission, Marcuse broadcast daily, usually in the afternoons, on 32.5 metres from his home at Caterham, Surrey using a "studio" in the home of a friend and neighbour, Percy Valentine. He also (without permission) relayed some BBC medium-wave programmes. He rebroadcast the chimes of Big Ben, heard for the first time across the oceans, from his 100 ft-high aerials and 1.5 kW transmitter.

Occasionally, orchestras and guest soloists and singers were squeezed into the small studio. "Outside broadcasts" included bird songs from his garden and the relay of local church services.

His broadcasts were often relayed by other amateurs overseas, including one in the West Indies. As a result Gerald Marcuse was soon receiving fan mail including a letter from a lady who wrote: "I am enchanted with your voice which I hear every Sunday morning and I have three lovely daughters and a flourishing business. If you would like to come over you can have the pick of the daughters and the business."

Despite such an invitation, Gerry remained in the UK broadcasting regularly until Post Office permission was withdrawn in 1929, so leaving Empire broadcasting to G5SW until the official BBC service began in 1931.

## Amateur Satellites

The Russians certainly have a sense of showmanship. Recently they launched their second series of amateur radio space satellites, satellites that pick up amateur 144MHz transmissions and send them back again to amateurs listening on 29MHz, so permitting long distances to be covered on VHF.

This time, instead of the expected one or two spacecraft they sent up no less than six: RS3 through to RS8 as company for the still working Oscar 8 and UoSAT (UK Oscar 9). Britain's first satellite for amateurs interested in scientific studies, launched in September 1981, and which has been undergoing a long period of checking out.

The Russians have asked amateur operators throughout the world not to use excessive power when working through these satellites. They feel 70 watts effective radiated power, or say a 10-watt transmitter with a reasonably high gain aerial, or under 100 watts with a dipole, is sufficient.

As for the other amateur space satellites, Wednesdays are reserved for planned experimental purposes. The British AMSAT-UK group runs a net on 3780kHz each evening Mondays to Saturdays at 7 p.m. and on Sunday mornings at 10.15 a.m. to discuss and pass on the latest news about the various amateur satellite activities.

of the 20th century. For many years ships not equipped with loops could call-up the 500kHz coast stations who would take cross-bearings and then radio the result to the ship.

The coming of radar, the Decca Navigator and Loran has diminished the importance of d/f but the system is enjoying a new lease of life with its modern extension to VHF. A note from Racal Communications reports the use of their v.h.f. d/f equipment to effect a dramatic rescue of four people on a cabin cruiser during a violent gale in the English Channel.

The cabin cruiser en route from Cherbourg to the Isle of Wight ran into a force ten gale and coastguards found by d/f that it was some 15 miles away from the position estimated by the skipper. The d/f equipment also assisted the coastguards to guide the Poole lifeboat to the distressed craft.

The traditional d/f technique has the advantage that it can be used to locate accurately a craft carrying no other equipment than a standard marine V.H.F. two-way radio telephone. It is thus proving a valuable aid to the safety of shipping in the Channel.

## Silent Room

In my library is a fascinating little wartime booklet published by Pitman at the princely sum of six old pennies: "Wireless Operating Simply Explained". It is full of good advice, rather in the manner of Victorian texts.

I like particularly a little section on "silence", including the following: "A wireless cabin should always be quiet. With faint signals or if atmospheric interference is bad, an operator needs all his hearing unimpeded to read signals.

"Imagine the feelings of the operator on watch when someone bursts into the wireless room whistling the latest popular air, bangs an attache case down, and proceeds to exchange noisy badinage with a colleague . . . The wireless cabin should resemble the consulting room of a Harley Street specialist and not a stag party."

Personally, I can recall radio stations of that era where the only time they resembled a consulting room was when half the night watch was stretched out on the floor asleep! And where the operators had to face the challenge of the station cat suddenly jumping playfully on to their keying arms. Something which I am sure Mr. Crook would have said should be "sternly discouraged". I was reminded of this by the recent High Court case in which radio intercept operators of the Composite Signals Organisation sued the Attorney-General for loss of hearing, after spending decades listening to weak signals in their headphones.

Other recommended "don'ts" included reading papers or books while on watch, working with headphones on your cheeks, placing pork pies, sandwiches etc on the operating bench. I have the impression that Mr. Crook had a good idea of what used to go on in radio stations!

## ON WATCH

Readers who are wireless operators or ex-operators are likely to have some amusing "On Watch" tales to recount.

Why not share them with other readers? Pat will be delighted to hear from you.

## Channel Rescue

For many years the most important radio navigational aid for ships was the simple direction-finding (d/f) loop or alternatively the Bellini Tosi twin loop and radiogoniometer. Both of these systems were developed as early as the first decade



By D. BUTLER

## Simple Sound Box For The Experimenter

THIS project will enable the constructor to take the first tottering steps towards music synthesis with a voltage controlled oscillator (v.c.o.) sound effects unit. The varied and in-

teresting sounds it produces are generated by a circuit, the heart of which is the 4046 CMOS micropower phase locked loop i.c. used here as a v.c.o.

### CIRCUIT DESCRIPTION

The circuit diagram is given in Fig. 1, IC3 being the 4046 CMOS i.c. mentioned above. An external resistor and capacitor, R7 and C4 respectively, govern the operating frequency of this v.c.o. and, with the component values given, is in the order of 1kHz.


The operation of the oscillator is dependent upon a voltage applied at pin 9 and from the circuit diagram it can be seen that there are two sources of this control voltage: (1) directly from a separate clock oscillator consisting of IC1a and IC1b, VR1 and C1; or (2) from IC2, a pseudo-random generator. Switch S2 controls which of these two options is selected.

We shall first examine the former option, whereby two NAND gates, IC1a and IC1b, from a 4011 CMOS i.c. are used as an oscillator, the timing components being potentiometer VR1 and capacitor C1. This gives a minimum operational frequency of approximately 0.5Hz with the potentiometer at its highest resistance.

So with S2 in the DIRECT position the output of this oscillator at pin 4, IC1b is coupled via D4 to the control input of IC3, thus supplying a series of pulses to the v.c.o. Therefore with a positive pulse on pin 9, IC3 will oscillate and when the input drops, it will stop.

Capacitor C3 decouples the v.c.o. input to give a decay effect to the tone generated.

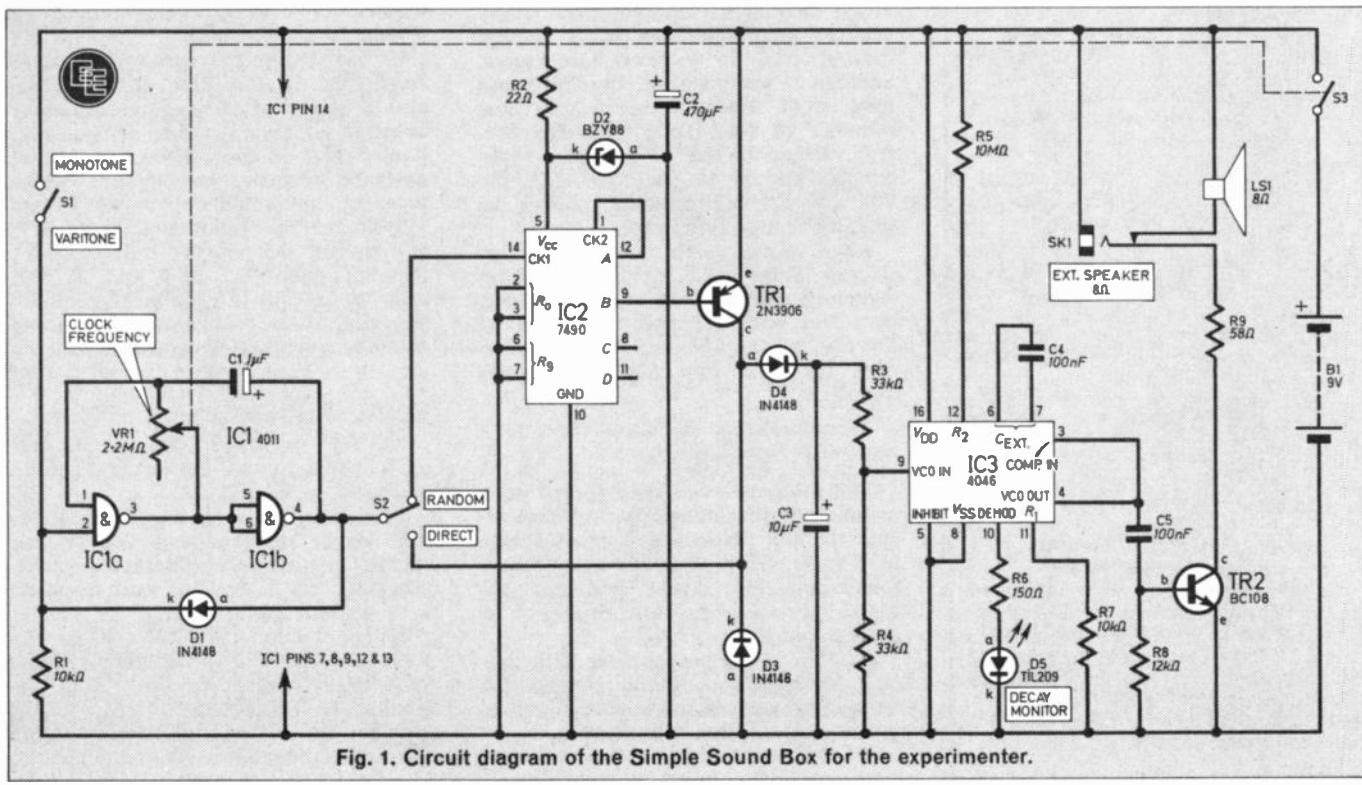All this happens when switch S1 is closed (in the VARITONE position) and



on opening S1 (MONOTONE), a constant note will be generated.

Now to discuss the second option with S2 in the RANDOM position.

## RANDOM

In this case, the output from IC1b is connected to the clock input, pin 14 of IC2, a 7490 TTL decade counter wired as a randomiser.


As the i.c. is a TTL device it requires a 5V power supply, so the 9V battery voltage is regulated with a 5.1V Zener diode, D2, and resistor R2. Note that R2 must be a 1W resistor as it sinks quite a lot of power. C2 is a supply decoupling capacitor.

The output of IC2 at pin 9 is a pseudo-random sequence of pulses so

**COMPONENTS**  
approximate  
cost £8.25

the resulting effect from the v.c.o. cannot be easily predicted.

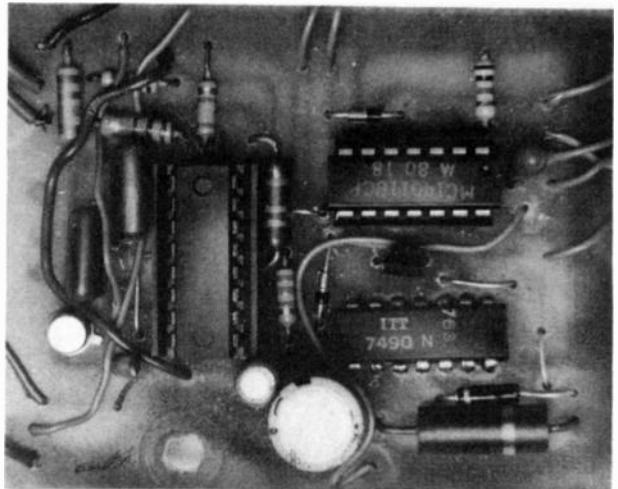Transistor TR1 amplifies the TTL output level to that compatible with the CMOS devices, that is swinging between the nine volt battery supply rails.



Close-up of the prototype circuit board.

## COMPONENTS

### Resistors

R1, 7	10kΩ (2 off)
R2	22Ω 1W
R3, 4	33kΩ (2 off)
R5	10MΩ
R6	150Ω
R8	12kΩ
R9	58Ω

All 1/2W carbon ±5% except where stated

### Capacitors

C1	1μF 10V tantalum bead
C2	470μF 10V elect. radial lead
C3	10μF 10V elect. radial lead
C4, 5	100nF polyester (2 off)

### Semiconductors

D1, 3, 4	1N4148 silicon (3 off)
D2	BZY88 C5V1 400mW 5.1V Zener diode
D5	TIL209 red i.e.d.
TR1	2N3906 pnp silicon
TR2	BC108 or similar npn silicon
IC1	4011 CMOS quad 2-input NAND gate
IC2	7490 TTL decade counter
IC3	4046 CMOS phase locked loop

### Miscellaneous

S1	s.p.s.t. miniature toggle switch
S2	s.p.c.o. miniature toggle switch
S3/VR1	2.2MΩ carbon lin. potentiometer with integral s.p.s.t. switch
LS1	8Ω 0.3W miniature speaker
SK1	3.5mm jack socket, switched contacts

Case 120 x 100 x 45mm; single-sided p.c.b. 70 x 55mm; i.e.d. mounting clip; battery clip; 14 pin d.i.l. i.c. holder; 16 pin d.i.l. i.c. holder; epoxy resin adhesive; 7/0.2 PVC sleeved wire; knob (for VR1); board mounting hardware.

## V.C.O. OUTPUT

The output of IC3 at pins 3 and 4 is coupled via C5 to TR2, a single transistor amplifier, and speaker LS1 provides the audible output, socket SK1 giving the option of an external amplifier and/or speaker.

The i.e.d., D5, is connected internally to the v.c.o. and it monitors the operation of IC3.

Power is supplied to the circuit from a nine volt PP3 battery although a battery eliminator is recommended as the power consumption is around 90mA at the highest frequency level. Switch S3, an integral part of VR1, is the main unit ON/OFF switch.

## CIRCUIT OPTIONS

As the circuit stands, the sound effects available are still rather limited and to expand the range, adding a jack socket to the input (pin 9) of IC3 will enable the constructor to feed an alternative control voltage to the v.c.o. Series resistor R3 should be retained and the voltages applied must of course be of CMOS compatible levels.

Also to vary the operating frequency of the v.c.o. itself, a potentiometer of say 10 kilohm can be added in series with R7 and the value of C4 can be experimented with, however no less than 50pF is recommended.

## CIRCUIT BOARD

The prototype was constructed on a printed circuit board, 70 x 55mm in size, the foil pattern of which is given in Fig. 2. This diagram also shows the component layout and no problems should be encountered in assembling it.

Just the usual precautions with getting the polarity of the electrolytic capacitors and diodes and the orientation of the transistors correct.

All three i.c.s. are shown in holders, however IC2, the TTL device can be

soldered directly to the board if desired with no danger of any damage.

## CASE

Any enclosure of suitable dimensions will be suitable, bearing in mind the size of the potentiometer, switches, speaker and p.c.b. The original prototype uses a plastic box 120 x 100 x 45mm with a screw-on lid.

Four holes are to be made in the lid to accommodate the two switches S1 and S2, the potentiometer VR1 and i.e.d. D5 and these are to be made in the positions shown in the photograph of the finished unit. The potentiometer requires a 10mm diameter hole, the remainder of the lid mounting components needing a 6.4mm diameter hole.

A "grille" for the speaker needs to be drilled in the base of the case, and a series of 3 to 4mm diameter holes in a "star" pattern will suffice. It also adds to the appearance of the unit to slightly countersink these holes on the outside.

Two further holes are necessary, one in the side of the unit for SK1 (6.4mm diameter) and one in the base to accept the mounting pillar for the p.c.b. (diameter of which depends upon screw size used.)


## FINAL ASSEMBLY

Having prepared the case and p.c.b., the unit can be wired together as shown in Fig. 3.

The speaker is to be glued down with epoxy resin adhesive above the "grille" pattern in the base, the p.c.b. mounted on a spacer and secured with a screw and nut.

Wiring to be completed with the p.v.c. sleeved 7/0.2 equipment wire (or similar) and the controls to be labelled as illustrated.

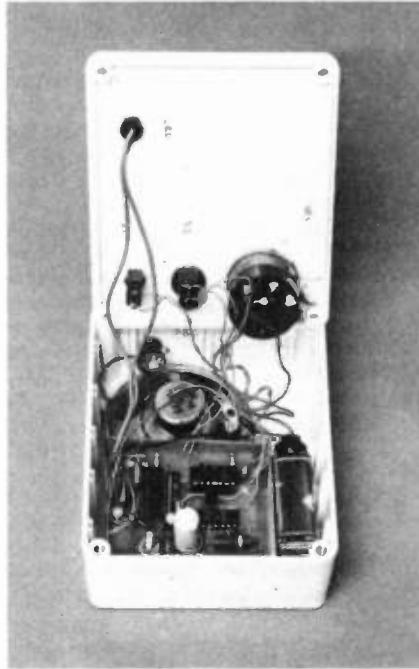Once completed, different sound effects can be created by manipulating S1 and S2 together with VR1. □



Prototype with lid raised showing assembly within the case.

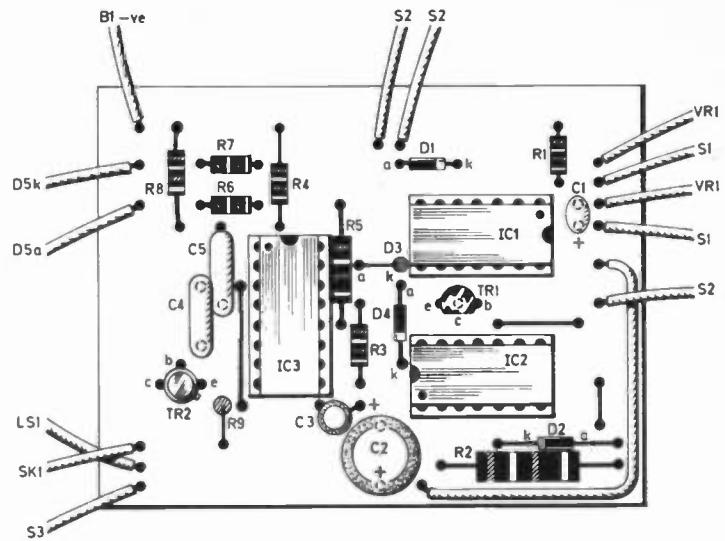


Fig. 3. Layout of the components on the topside of the p.c.b. and wiring details to other components.

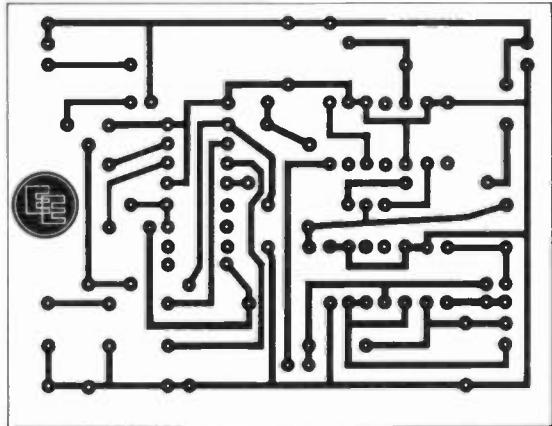


Fig. 2. Full size master for the pattern to be etched on the board. Viewed from copper side.


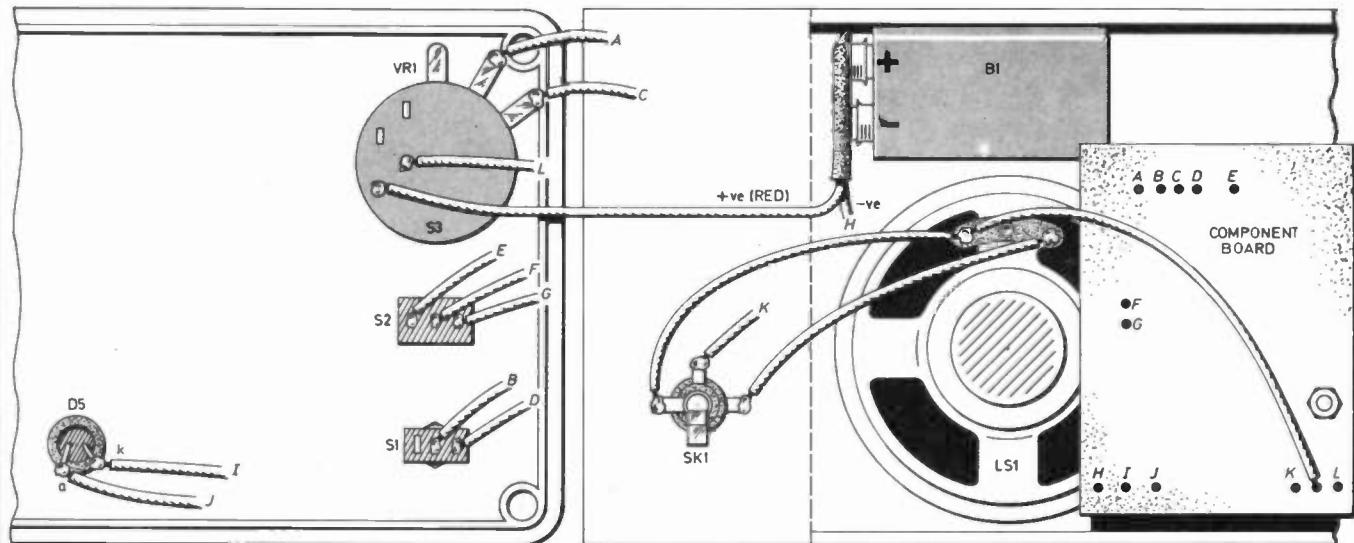


Fig. 3. Position and interwiring of the case mounted components. All flying leads from these components run to the circuit board.

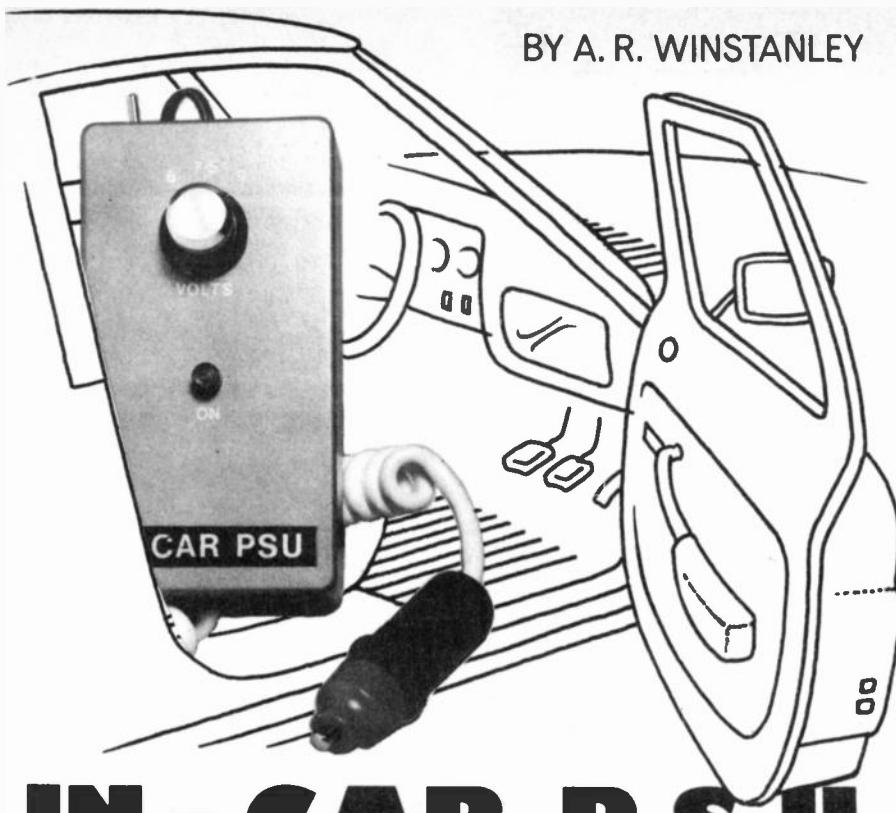

BY A. R. WINSTANLEY

# **IN-CAR P.S.U.**

ONE of the more economical methods of providing music in the car, apart from singing to oneself, is to take along a portable cassette recorder which operates from its own dry batteries. Obviously if a long journey is envisaged then it is often a good idea to carry several spare batteries for the cassette recorder as well!

The main problem of course is that cassette recorders seem to have a voracious appetite for dry cells. It would be more desirable to operate the unit from the car battery, thereby saving the recorder's own batteries for use in and around the house. However, as the car battery is normally rated at 12V, this is not immediately possible. Some sort of adaptor is required which converts the 12V of the car's electrical system to that needed by the cassette recorder. Most cassette recorders operate from either 6V or 7.5V and draw between 400 and 500mA maximum.

The In-Car P.S.U. described here is such an adaptor. Apart from providing 6 or 7.5V, it will also give 9V d.c., the three voltages being available at the touch of a switch. With a maximum current rating of 2.2A (but see later), not only will it operate cassette recorders, but other devices as well — torches, lanterns, battery shavers and radios to mention but a few.

Virtually the only requirement is that the device to be powered from

The circuit itself is quite simple and straightforward. This is because a modern easy-to-use integrated circuit has been used as the basis of the design. The i.c., a three-terminal variable voltage regulator type LM317T, is shown in its basic configuration in Fig. 1.

It can be seen that the three terminals are named *input*, *output* and *adjustment*. A 240 ohm reference resistor is normally placed between output and adjustment, and across this resistor exists a precision 1.2V reference voltage. By varying the value of  $R_x$ , a resistor placed between adjustment and ground, the output voltage may be altered. In fact, using a 240 ohm reference resistor, the value of  $R_x$  is given by the formula

$$R_v = (200 \times V_a) = 240 \text{ ohms}$$

where  $V_o$  is the output voltage in volts. To obtain 6, 7.5 and 9V output voltages therefore we require values of  $R_x$  to be 960, 1260 and 1560 ohms respectively.

The maximum current available is 2·2A, but this will depend on the temperature and power dissipated by the i.c. The device, incorporates thermal overload shutdown and internal current limiting and is available in several packages. It is the TO-220 encapsulation (LM317T) that is employed in this design.


## CIRCUIT DESCRIPTION

The complete circuit diagram is shown in Fig. 2. S1 is a one-pole three-way rotary switch which selects different values of  $R_x$  (Fig. 1) thereby enabling 6, 7.5 or 9V to be obtained. Note that three preset resistors in Fig. 2 replace  $R_x$  in Fig. 1; these are trimmed so that exact output voltages can be obtained. This does mean however that a voltmeter will be required to measure the output voltages during setting up.

D2 is a light-emitting diode which illuminates when the unit is operating. R1 is its associated series resistor which limits the forward current

Fig. 1. The LM317T in basic voltage regulator configuration.

**Fig. 2.** The complete circuit diagram of the In-Car P.S.U.

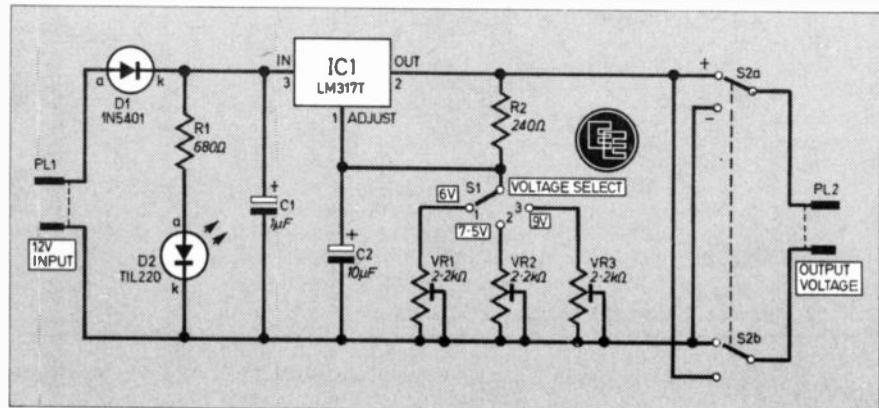

# COMPONENTS

## Resistors

R1 680Ω  
R2 240Ω  
Both  $\pm$ W carbon  $\pm 5\%$

## Capacitors

C1 1μF 16V or greater tantalum bead  
C2 10μF 16V tantalum bead

## Semiconductors

D1 1N5401 3A rectifier  
D2 TIL220 or similar red l.e.d.  
IC1 LM317T adjustable voltage regulator i.c. (TO-220 case)

## Miscellaneous

S1 single-pole three-way rotary  
S2 miniature d.p.d.t. toggle  
VR1-VR3 2·2kΩ miniature carbon preset (3 off)  
PL1 two-pole plug to suit car (for example a plug to suit the car cigar/cigarette lighter socket)  
PL2 two-pole plug to suit equipment (Spider or Universal—see text)  
Printed circuit board, 61 × 27mm; case type BIM 5004/14, diecast aluminium, size 121 × 66 × 40 with p.c.b. guides (see text); lens clip for D2; insulating bush and mica washer for IC1 (TO-220 kit); knob; grommets (2 off); 6BA fixings for IC1.

See  
**Shop Talk**  
page 233

through the l.e.d. to a reasonable level—about 15mA.

C1 is a tantalum bead capacitor placed across the input to eliminate transients and noise which often are present on the car 12V supply rail. C2 bypasses the adjustment terminal to ground to improve the ripple rejection of the i.c. D1 is a heavy-duty rectifier which protects the circuit from accidental reversed polarity.

## CONNECTORS

The 12V input connection to the unit was made, on the prototype, with a twin-core curly lead terminated in a cigar-lighter plug: this enabled the unit to be connected quickly and easily into the car cigar-lighter socket.

The finished unit ready for use in the car. You can see the "universal" or "spider" connector.



The one remaining problem relates to the polarity of the P.S.U. output. The author's radio/cassette recorder requires a 2·1mm power plug with the tip at 0V and the "body" of the plug at +6V. It is likely however that other loads may require a reversed polarity to this, with the tip of the plug positive and the "body" negative.

S2 has been included in the output to switch over the polarity of the spider plug as necessary. This switch needs to have a heavy action on the operating lever to prevent the switch being accidentally knocked over whilst the unit is in operation. A reversed voltage polarity with some devices could have dire results!


**CONSTRUCTION**  
**starts here**

## PRINTED CIRCUIT BOARD

The circuit, with the exception of IC1, is constructed on a glass-fibre printed circuit board measuring 61 × 27mm. The unit is built into a diecast Bimbox type 5004/14 measuring 121 × 40 × 66mm. The dimensions of the p.c.b. are such that it can slide directly into the p.c.b. guides formed on the inside of the specified case, thus eliminating any requirements for p.c.b. mounting pillars.

If another metal case is used then it is necessary that the p.c.b. is mounted in a different manner. Probably 8BA mounting hardware can be used here. A full size master pattern

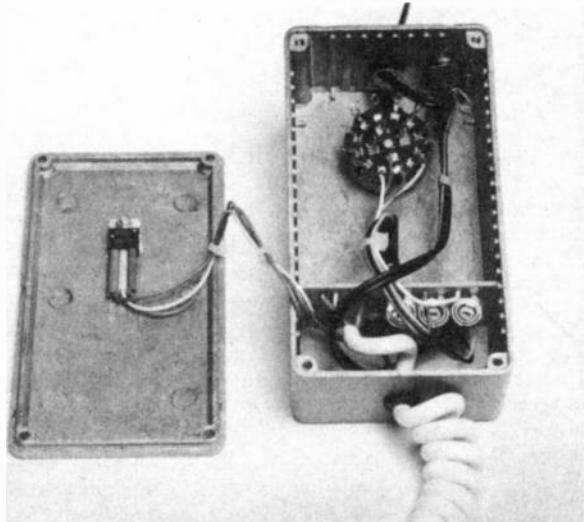In the final stages of assembly, the prototype with lid removed showing in particular the p.c.b. inserted in a slot and the i.c. mounted to the lid.



## IN-CAR P.S.U.

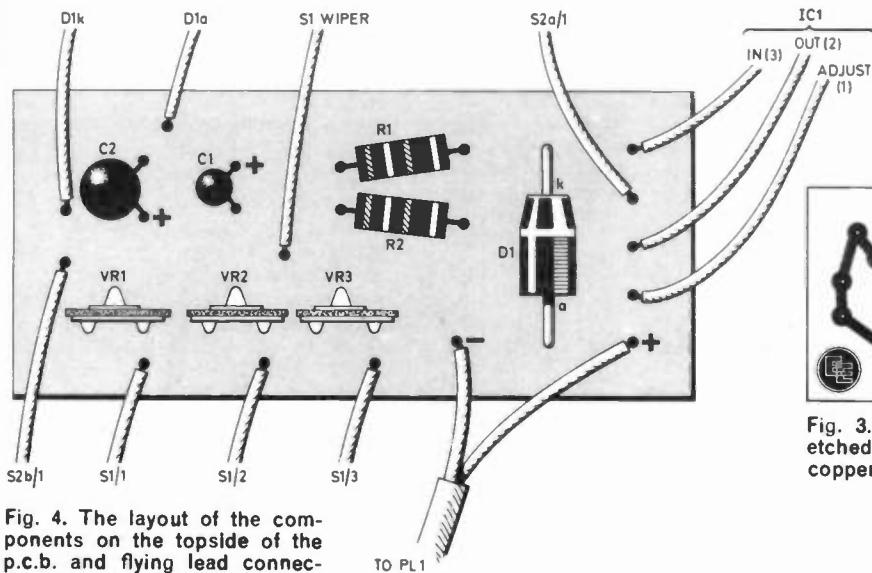


Fig. 4. The layout of the components on the topside of the p.c.b. and flying lead connections to the board.

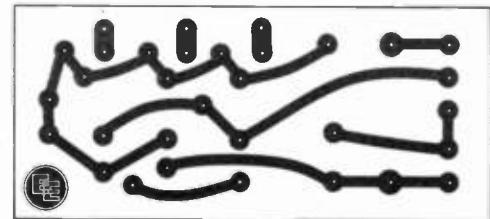


Fig. 3. Full-size master of the pattern to be etched on the board. Black regions denote the copper to remain after etching.

**COMPONENTS**  
approximate  
cost £10·50


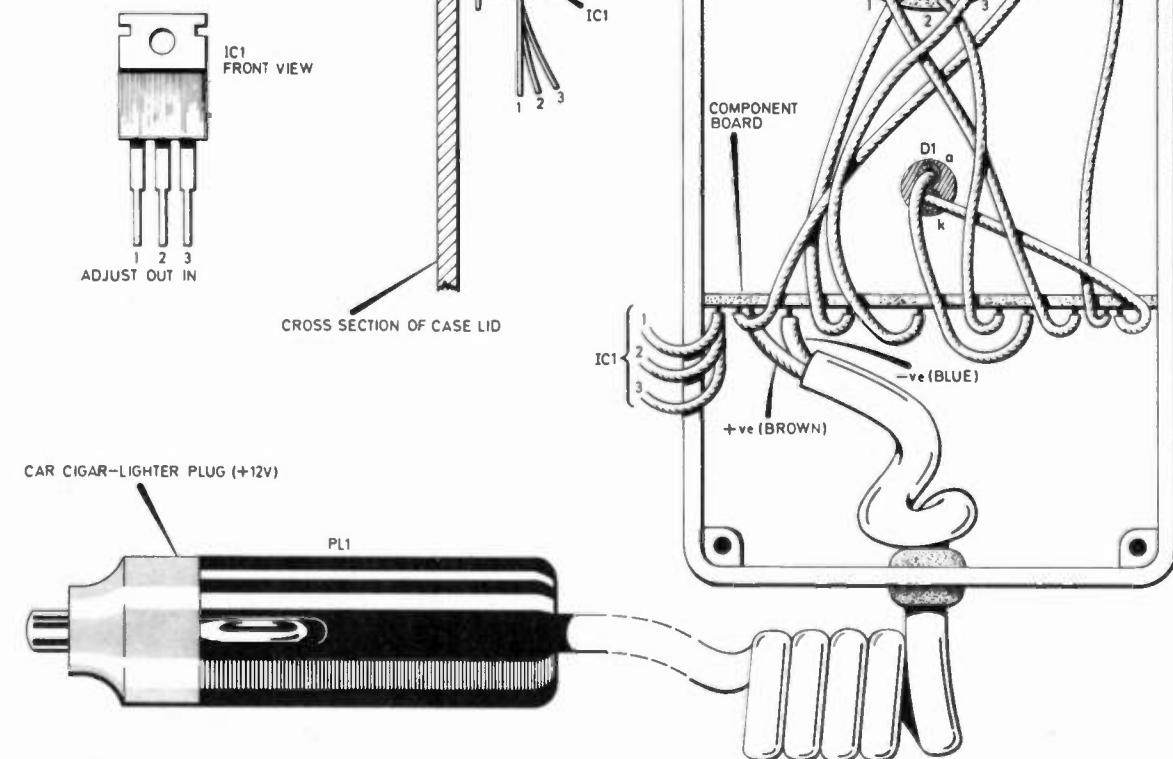


Fig. 5. Position of components and board within the specified case with complete interwiring information. Also shows mounting details for IC1 using mica washer and plastic bush.

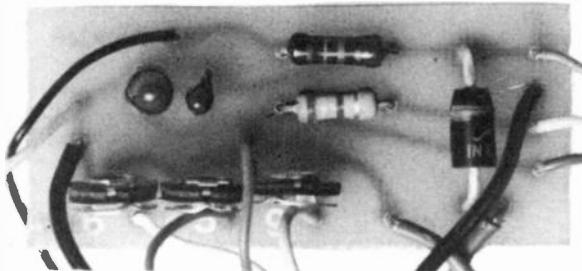

to be etched on the board is given in Fig. 3.

Assembly details of the components on the top side of the p.c.b. are shown in Fig. 4. The polarities of the tantalum capacitors are nearly always marked on the bodies, and it is very important that these components are soldered in the right way round, as is the case with D1 and D2. The latter has a flat alongside its cathode.

The p.c.b. should be completed in accordance with Fig. 4 and then the diecast box can be prepared.

## CASE

The lower section should be drilled to suit the rotary switch, the toggle switch S2, and the l.e.d. Two holes are also needed to enable the 12V input and output leads to pass through and these holes should be fitted with a grommet. It is advisable to fit cable retaining clips to both of these cables.

IC1 is mounted on the removable lid of the box, which acts as a heat-sink—hence the necessity for a metal box to be used. A diecast box has the added advantage that it is very tough and will withstand quite severe knocks.


It was decided that the galvanised finish of the diecast box was somewhat less than aesthetic and so it was resprayed in an attractive shade of gold. If constructors wish to do the same it should be noted that an initial coat of primer may be required. The paint should of course be applied once all the metalworking has been completed.

After the box has been drilled and painted, the lettering can be applied to the case as required. Proprietary rub-down lettering can be used here. Note that clear protective lacquer should not be used over a cellulose paint finish. Experience has shown that the two tend to react unfavourably!
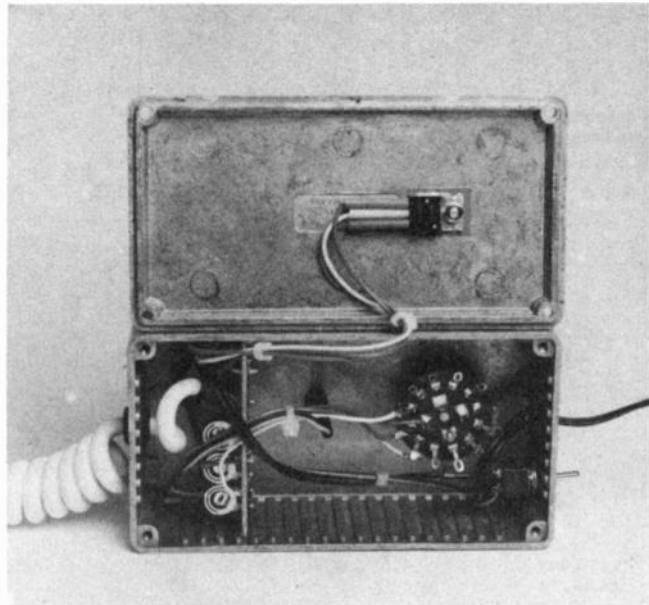
## INTERWIRING

Once the p.c.b. and case have been completed, all interwiring can be carried out, as detailed in Fig. 5. The l.e.d. is mounted using either the usual black plastic bush/clip or alternatively a more attractive, though

Close-up view (above) of the prototype p.c.b. with all components in position.



Plan view of the completed prototype. Note the use of cable ties for the three groups of wiring.

more costly, lens-clip may be employed, as in the prototype. The integrated circuit should be mounted on the lid of the box using a TO-220 insulating kit, so that the metal tab of the device is isolated from the case.

With regard to the rotary switch, a one-pole, three-way switch is required. This is best realised using a four-pole three-way switch. Only one pole is wired up. The remainder of the switch is ignored, as Fig. 5 illustrates.

General-purpose flexible wire, preferably having a minimum rating of 1.5A can be used throughout. All flying leads, plus the input and output leads, can be soldered directly to the p.c.b.; constructors may wish to use Veropins if required.

Check all of the interwiring and set the three presets to midway before proceeding to the setting up stage. This comprises applying 12V to the input, either from the car electrics or a bench power supply unit and then adjusting the appropriate preset until 6V, 7.5V and 9V are measured at the output connected to a 10V d.c. voltmeter for the three settings of S1.

The unit once calibrated in the manner described is then complete and ready for use.

## OUTPUT CURRENT

It was mentioned earlier that the i.c. has built-in current limiting which operates at 2.2A, reducing the current level as necessary if the i.c. temperature increases.


The peak current available from the i.c. therefore is 2.2A. To operate the unit at such current levels for a prolonged period is impracticable.


Whilst short-circuits and very heavy loads will not damage the i.c., as the device is not well heatsinked (the diecast box is not terribly efficient at this), the i.c. temperature can be expected to build up with a consequent reduction of the maximum current available.

Under worst case conditions the i.c. may shut down altogether. In such cases the device will be very hot indeed—probably too hot to touch. When powering cassette units and other devices with a current consumption of about 500mA or less, the i.c. will barely get warm. The maximum recommended current for prolonged use is about 1A. This will ensure that no thermal problems are experienced.

Finally, note that temporary short-circuits will not damage the p.s.u. unit but ensure that the circuit in the car's electrical system will carry the 2A or so which flows under such conditions.

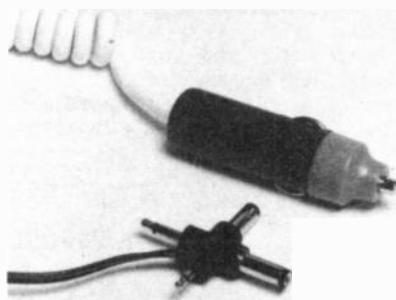The cigar-lighter plug and power supply connector used by the author.



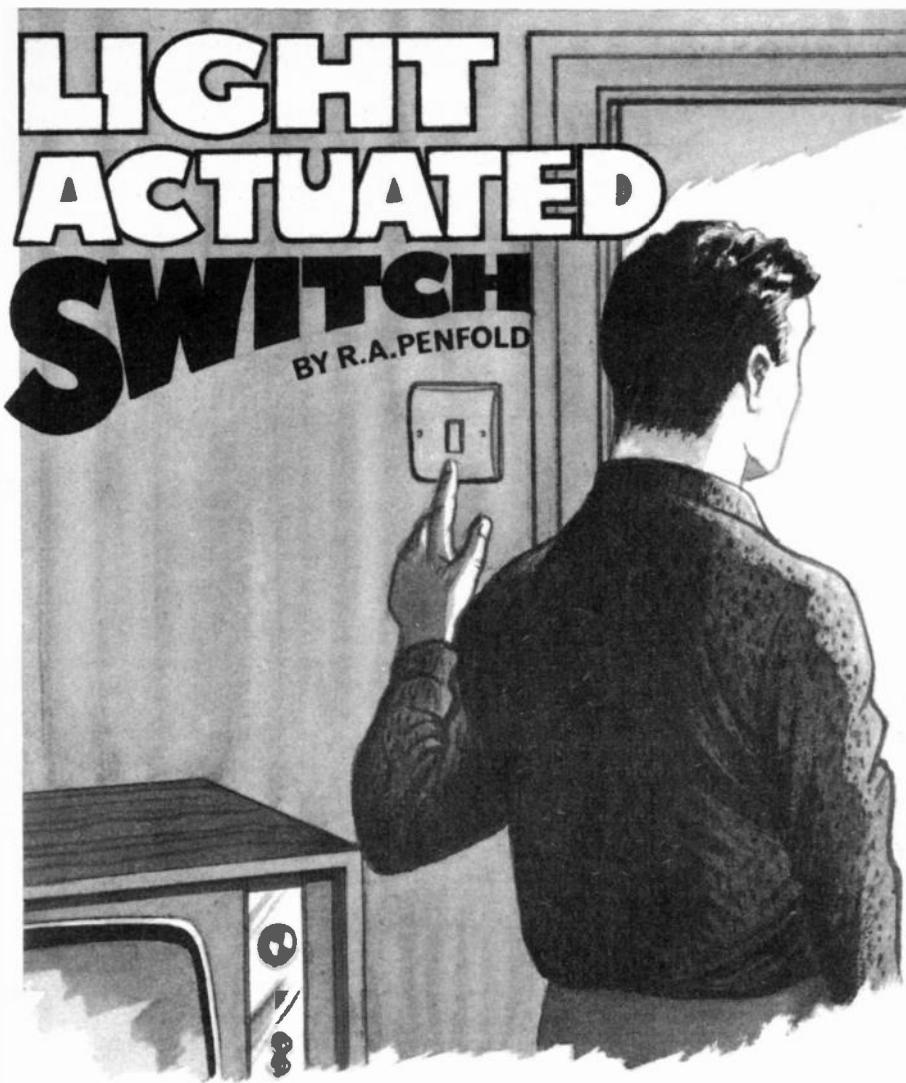

ALTHOUGH a great many light activated switch designs have been published in the past, these have virtually all been circuits which respond to the ambient light level, switching on or off at some predetermined light intensity.

This circuit is different in that it is designed to switch on some item of equipment when an electric light is switched on, and switch it off again when the light is switched off. Apart from this continuous mode of operation, the unit can be used in a single operation mode where it switches off both itself and the controlled equipment when the light is extinguished.

#### FLUCTUATING INTENSITY

For reliable results the unit must be designed to respond to light of rapidly fluctuating intensity, and not to any particular light level. Since mains lighting is run from a 50Hz a.c. supply, the light level increases to a peak and then dies away during the course of each mains half cycle,

producing the rapid variations to which the unit responds. Natural light does not pulsate in this way and is much more consistent in the short term, making the unit almost immune to this type of lighting.

The unit could be used by someone who watches TV in bed, or perhaps by someone who listens to a mains powered radio which cannot easily be conveniently situated.

This light activated switch can be used to automatically switch off the set when the bedroom light is extinguished, obviating the need to get out of bed and switch the set off manually. Another possible application is to ensure that a TV set, hi-fi, or other equipment is not accidentally left switched on overnight.

#### THE CIRCUIT

The complete circuit diagram of the Light Activated Switch is shown in Fig. 1. A simple unregulated supply of about 9 volts is obtained from the straight forward fullwave rectifier circuit which uses T1, D1,

D2, and C1. LP1 is merely the panel neon on/off indicator, and this must be a type having an integral series resistor for normal mains operation.

The heart of the unit is PCC1, a cadmium sulphide photoresistor, and this has a resistance which varies from over 10 megohms in total darkness to only a few tens of ohms in very bright conditions. Together with R2 this forms part of a potential divider, and variations in the light level received by PCC1 cause similar variations in the output from the potential divider.

When PCC1 is subjected to mains lighting, the rapid changes in intensity generate a rapidly alternating output from the potential divider. This is coupled by C3 to a single transistor amplifier. Natural light only produces very slow changes in intensity at a significant amplitude, and these will be blocked by C3, as will the d.c. level produced by the photocell circuit.

Components R1 and C2 considerably smooth and decouple the supply for the photocell circuitry. This is necessary to prevent mains hum from being coupled into the amplifier from the supply lines via R2, which would block the operation of the circuit. This decoupling also prevents instability due to positive feedback through the supply lines.

#### AMPLIFIER

TR1 is used as a conventional common emitter amplifier having collector load resistor R4 and base bias resistor R3. The amplified output from its collector is coupled to a rectifier and smoothing circuit using D3, D4, and C5. In the presence of a suitable input signal this produces a strong positive d.c. bias which switches on TR2, and activates the relay which is connected as its collector load.

Of course, in the absence of 'mains lighting being detected by PCC1, a suitable signal is not present in the circuit, and the relay is not activated. D5 is a protective diode, and this suppresses the high reverse voltage that would otherwise be generated across the relay coil as it switched off. If not suppressed, this voltage spike could damage the semiconductor devices in the circuit.

#### SWITCHING

For continuous operation it is necessary to close S1. Power is then continuously applied to the circuit, and the relay closes whenever PCC1 is subjected to mains light source. When the relay is energised, RLA2 closes and supplies power to the controlled equipment.

If the unit is required to switch itself off when the light is switched

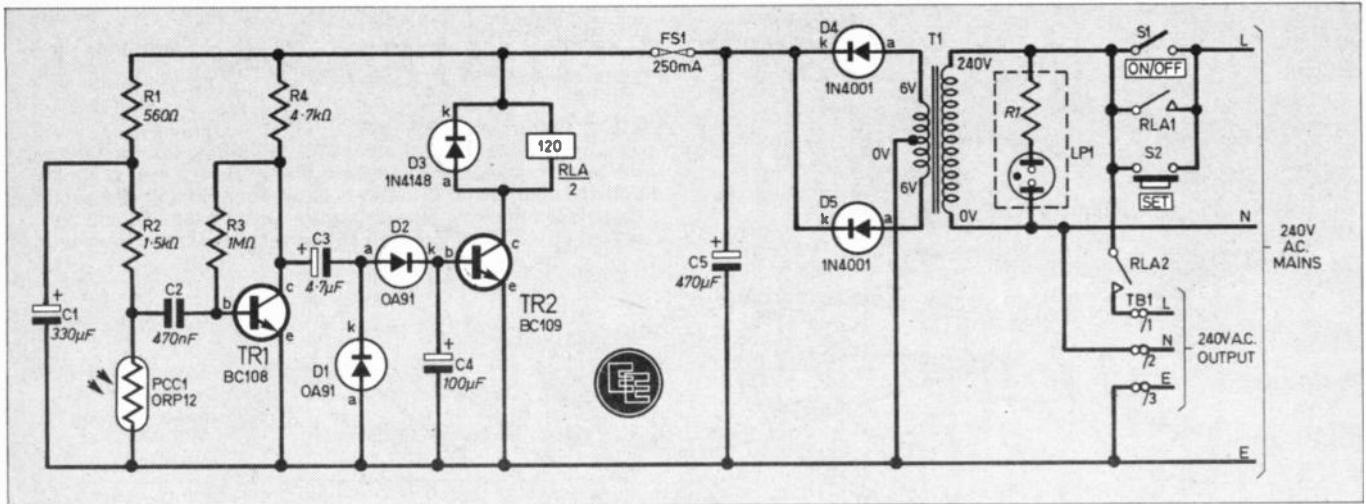


Fig. 1. Full circuit diagram of the Light Actuated Switch.

off, S1 is left in the open position, and push button switch S2 is depressed until the relay is activated (which happens almost immediately). When S2 is released, power will be applied to the unit by way of relay contact RLA1, and to the controlled equipment through both RLA1 and RLA2.

When the light is switched off and the relay contacts open, power will be disconnected from both the controlled equipment and the light switch circuitry. Switching the light on again then obviously has no effect on the unit.

## CONSTRUCTION starts here

### STRIPBOARD

The main circuitry is built on a piece of 0.1 inch matrix stripboard size 18 strips by 23 holes, and the component layout is given in Fig. 2. There is one break in the copper strips, and be careful not to omit the single link wire.

Solder in the resistors and capacitors first, and leave the semiconductor devices until last. Diodes D3 and D4 are germanium devices and they are susceptible to damage by overheating. It is therefore advisable to use a heatsink on each lead of these components when they are being soldered into circuit, or at least make sure that they are quickly soldered into place so they do not overheat.

Finally, the board is completed by connecting the seven insulated flying leads, all of which are about 100mm or so long. These can be trimmed to length when it is time to connect their free ends.


### CASE

The prototype is housed in a metal instrument case which measures approximately 152 × 114 × 51mm, but any case of metallic construction and about these dimensions should also be usable. The general layout of the unit can be seen from the photographs, and is not critical, although neither T1 nor any mains wiring should be positioned close to PCC1 or its wiring.

A soldertag is fixed on one mounting screw of T1 to provide a chassis connection point to which the mains earth can be connected. For reasons of safety it is essential to ensure that the case is properly earthed.

The specified relay can be mounted using a single short 4BA screw which fits into a threaded hole in the base of the relay. It is possible to use an alternative relay if it has suitable ratings, but it may then be necessary to construct a mounting bracket of some kind.

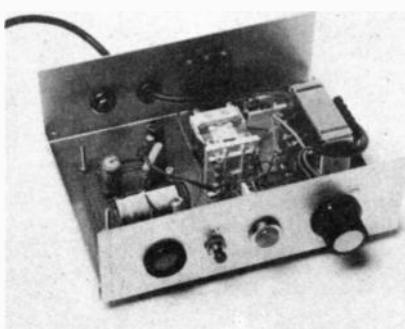The photocell is mounted on the front panel, and if a suitably large grommet can be obtained, this can be used as a sort of panel mounting holder for PCC1. Alternatively it is possible to drill a couple of holes in the panel to accommodate the lead. Interior view of the unit. Note the connector block TB1 on the inside rear panel for connecting up the external equipment.



## COMPONENTS

### Resistors

R1	560Ω	See <b>Shop Talk</b>
R2	1.5kΩ	page 233
R3	1MΩ	
R4	4.7kΩ	
	All 1W carbon ± 5%	

### Capacitors

C1	330μF 10V elect.
C2	470nF polyester type C280
C3	4.7μF 16V elect.
C4	100μF 10V elect.
C5	470μF 16V elect.

### Semiconductors

TR1	BC108 npn silicon
TR2	BC109 npn silicon
D1, 2	OA91 100V, 20mA germanium point contact diode (2 off)
D3	1N4148 small signal silicon diode
D4, 5	1N4001 50V, 1A silicon rectifier diode (2 off)
PCC1	ORP12 cadmium sulphide light dependent resistor

### Miscellaneous

T1	mains primary/6-0-6V 250mA secondary
S1	s.p.s.t. mains rotary
S2	push-to-make, release-to-break mains rated switch
RLA	12V 120 ohm coil with two sets mains rated n.o. contacts, MES 12V power relay or similar.
FS1	250mA 20mm quick-blow cartridge fuse in chassis mounting holder
TB1	three-way 5A screw terminal block
LP1	mains neon indicator with integral series resistor
Case,	152 × 114 × 51mm, Harrison type BC1 or similar; stripboard, 0.1 inch matrix, size 18 strips by 23 holes; knob; interconnecting wire, 6BA mounting hardware for stripboard; 5A three core mains cable; interconnecting wire; grommets (3 off).

Approx. cost  
Guidance only £10

# LIGHT ACTUATED SWITCH




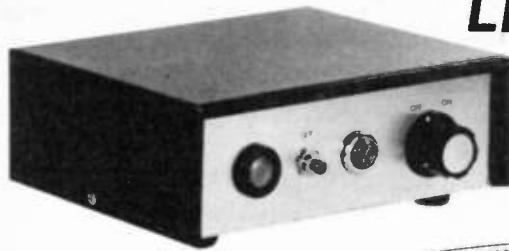


Fig. 2. Circuit board layout and full interconnection diagram. The secondary connections to T1 are below the primary so full transformer connections are shown on the left. A similar detailed diagram for the relay is shown bottom left. The output cable is led into the case through a rubber grommet and connected up via TB1. Photo left shows exterior of completed unit.

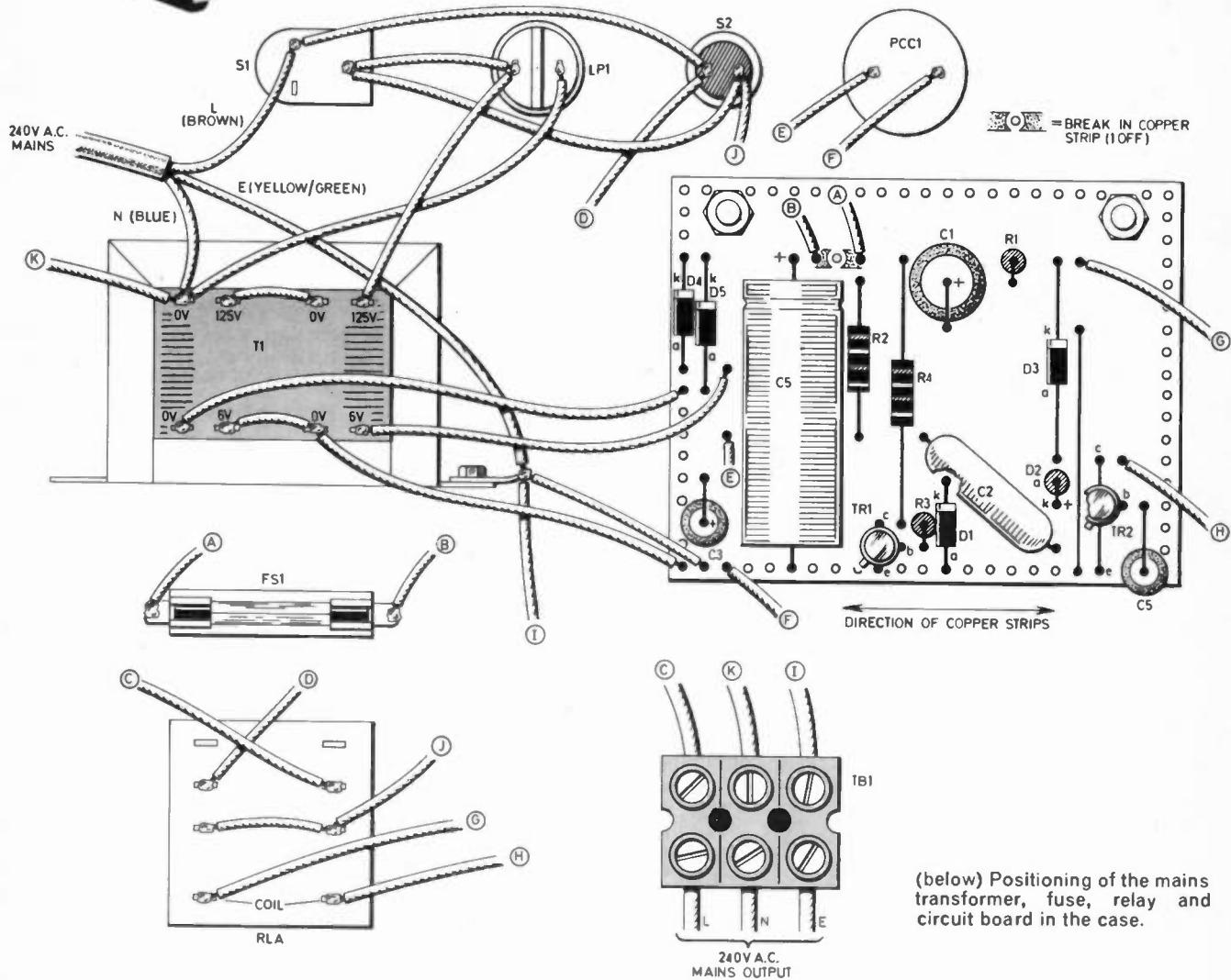

Rear wiring to front panel components.

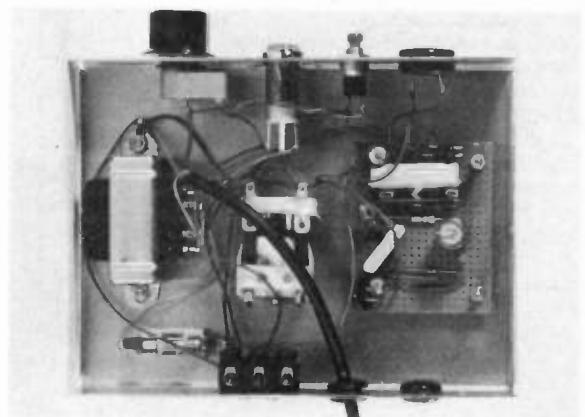

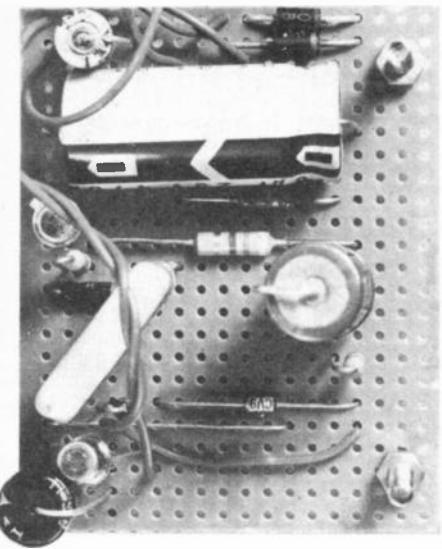

Close up view of the circuit board.

out wires of PCC1 (which protrude from the rear side of the component), and then glue it to the front panel, making quite sure that the leadouts do not short circuit to the metal casing.

The component panel is mounted on the base of the cabinet using two 6BA bolts and fixing nuts. Spacers are used to ensure that the connections on the underside of the board are kept well clear of the metal casing. Two holes are drilled in the rear panel to take the mains input and output leads, and these should be fitted with grommets to protect these cables.

### WIRING

Once all the drilling and component mounting has been completed, the point to point wiring can be undertaken. This is all illustrated in Fig. 2. Be very careful not to make any errors here as much of the wiring is carrying the mains supply, and errors could prove to be expensive or even dangerous. Suitably rated mains cable must be used for wiring that will carry mains power.

The connections to the controlled equipment can be made via a three way terminal block which can be mounted on the rear panel of the case. These blocks are normally sold in twelve way lengths, and a block of the appropriate length is cut from

one of these using a sharp modelling knife.

If preferred, a larger case fitted with a mains outlet socket could be used, and the three output leads would then connect to this socket. However, this would be more complicated and expensive, and is probably not worthwhile unless the unit is to be used with more than one item of equipment.

### TESTING

Before connecting the unit to the mains it is recommended that the wiring should be thoroughly checked over once or twice. It is then just a matter of first checking that with S1 closed, the unit switches on and off in sympathy with any mains light which throws light onto PCC1.

Then S1 should be closed and S2 should be operated so that the single operation mode can be checked. The unit should be quite sensitive, and a shaded 40W light bulb will operate the prototype reliably at a distance of 7 metres or so. However, strong natural light falling on the photocell will inevitably reduce sensitivity somewhat. □

# LETTERS

### Demorgan's Theorem

Readers of the *Introduction to Logic* series by J. Crowther may be interested in the following comprehensive method of converting expressions of even the most complicated kind.

Example. Demorganise: A. B. (C+D)  
Bracket terms not already so:

(A). (B). (C+D)

Complement each bracket:

(A). (B). (C+D)

Complement whole function:

(A). (B). (C+D)

Change signs between brackets for opposite signs (that is, "+" to "-" and "-" to "+");

(A) + (B) + (C+D)

Remove extra brackets:

A + B + (C+D)

The next exercise is slightly more difficult.

Demorganise:

A + B + C + D + E  
(A + B) + (C) + (D) + (E)  
(A + B) + (C) + (D) + (E)  
(A + B) + (C) + (D) + (E)  
(A + B) . (C) + (D) . (E)  
(A + B) . C + D.E

The following three are spot-at-a-glance conversions which can be memorised.

A + B = A.B

A. B = (A + B)

A + B = A.B

H. L. Taylor,  
Old Trafford,  
Manchester.

### The Saga of 'Circuit Sam'

Now 'Circuit Sam' was a whizz-kid bright  
With a knowledge of amps and ohms  
And a store of bits, and half-built kits,  
And esoteric tomes.

His secret scheme and cherished dream  
Was a plan for a robot brain  
And he said, "It's true, if I carry it through,  
That I'll never work again."

"I'll take in problems day by day  
To be solved for a standard fee—  
And my bank account will soon amount  
To £X to the nth degree.

So 'Circuit Sam' took his half-built kits  
To see what he could use  
And from a surplus bench supply  
He took the quick-rise fuse.

His darkroom timer came to hand  
And yielded L.E.D.'s,  
And his signal tracer traced no more  
When he took its F.E.T.'s.

Thus bit by bit, through every kit,  
'C. Sam' a-scrounging came,  
And he acted rash in his headlong dash  
To build that robot brain.

He ravished all his cherished gear  
With a mind too fixed to change  
For he'd promised himself that  
future wealth  
Would replace the entire range.

Then night and day for a month or two  
He worked at his Euroboard  
And the network grew with 'and', 'go-to'.  
Till all human knowledge was stored.

When the data banks, in serried ranks,  
Were 'bursting at the seams'  
Old 'Circuit Sam' gave heartfelt thanks,  
Having realised his dreams.

On the final day, in a mood quite gay,  
Sam pressed the action switch  
And the lights came on and the  
motors whirred  
And the touch pads gave a twitch.

When the current reached its  
working point  
The synthesizer spoke  
And it said, "Dear Sam, for my  
starting plan,  
You're just the very bloke."

"I find your feedback systems work  
With an ease that sets you free  
And I know the thought will not please  
you, but I think  
They'd just suit me."

"So I've searched around in my data banks  
For the skill to set me free  
And I've found it now, and to you  
my thanks—  
It is transplant surgery."

Terence Lee

## Designing A Simple A.M. Radio

A READER enquired recently about designing the tuning circuits for a simple radio. What he had in mind was a type of A.M. radio receiver which is just one step up from a crystal set.

In the days of germanium transistors a very simple circuit (Fig. 1) was often used. Here the transistor TR1 acts as a combined detector and audio amplifier. The circuit works only with strong signals, which means that the user must live close to a transmitter and must attach a long enough aerial to the receiver.

The transistor is operated without bias and to turn it on a peak signal voltage of about 100mV is required. Signals much smaller than this have no effect.

With modern silicon transistors the circuit as it stands is virtually unusable, because the turn-on voltage for silicon is about 500mV and only very strong signals are detectable.

For this reason, when silicon transistors are used in place of germanium the circuit has to be modified to provide enough d.c. bias to turn on the transistor slightly all the time. The arrival of a signal then turns it on more (on positive half cycles

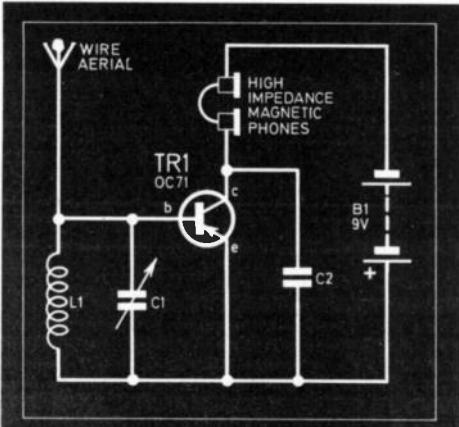


Fig. 1. A simple receiver based on a single germanium transistor.

if it is the usual *npn* silicon type) or less (on the opposite half cycles).

This detects the signal and gives an audio output to the sensitive old-fashioned magnetic earphones, which are of the high-impedance (1 kilohms up) type used with crystal sets. Reception of signals of a few tens of millivolts is then possible.

### Damping

This type of circuit is neither sensitive nor selective. In view of the fact that only one transistor and one tuned circuit are used this may not be surprising. However, the performance is even worse than these limitations imply.

The reason lies in the way in which the transistor reacts upon the tuned circuit. A parallel *LC* circuit like this behaves as an inductance at low frequencies, a capacitance at high frequencies and a resistance at its resonant frequency.

This resistance—called the dynamic resistance to distinguish it from the static resistance of the wire in the coil—can be quite high. For a typical medium-wave

# DOWN TO EARTH

BY GEORGE HYLTON

rising to a sharp peak of 100 kilohms at resonance it climbs gently to a much flattened one of less than 1 kilohm. The *LC* circuit is *damped* by the transistor and selectivity is much reduced. It is further reduced by the long aerial which also has a damping effect.

### Matching

The textbook answer to the damping problem is matching. By using transformer techniques (Fig. 2) energy can be transferred from aerial to tuned circuit and from tuned circuit to transistor with the greatest efficiency. It is just a matter of putting the best number of turns on the coupling windings L2 and L3.

Unfortunately L3 needs a much smaller number of turns than L1, which means that much less signal voltage is applied to the base of the transistor than appears across the tuned winding L1. This step-down in voltage makes for poor detection.

So although Fig. 2 is an advance on Fig. 1 as far as selectivity goes it is not much use from the point of view of sensitivity.


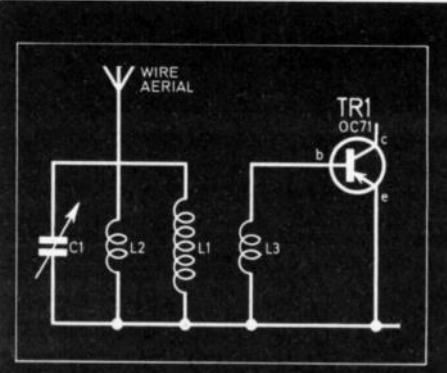


Fig. 2. Matching between aerial and tuned circuit ( $C_1$ ,  $L_1$ ) and between the latter and the transistor is delivered by transformer action. This results in efficient transference of energy.

Fig. 3. A two-stage receiver using silicon transistors. Note the ferrite rod aerial.

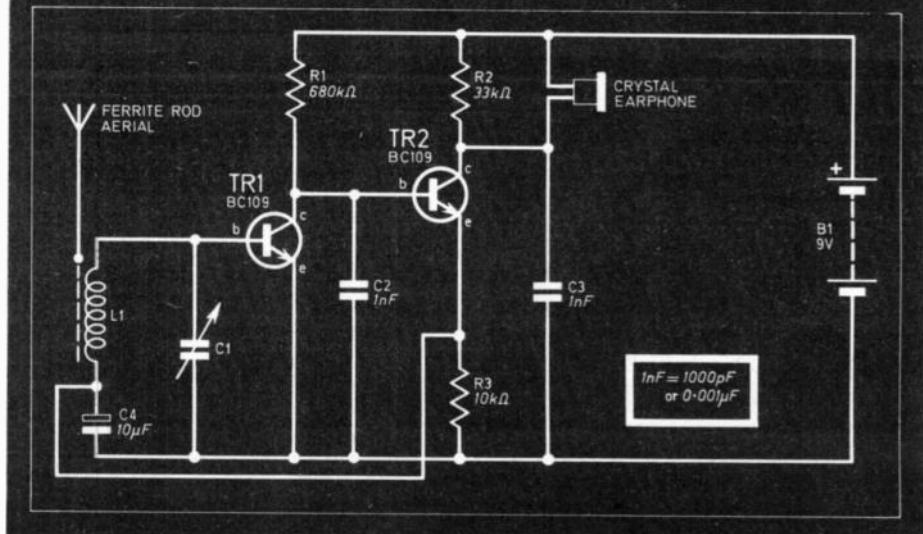

## Transistor Input Impedance

What is needed is some means of applying the maximum possible voltage to the detector transistor (to obtain the best detection efficiency) while at the same time minimising damping.

With modern silicon transistors one option remains. By operating the detector transistor at a very low collector current its input resistance can be raised from the usual few thousand ohms to hundreds of thousands of ohms. The tuned circuit can then be connected directly to the transistor, maximising the signal voltage.

The input resistance in kilohms is roughly equal to 25 times the current amplification (*h<sub>fe</sub>*) divided by the emitter current in microamperes. If a transistor is operated at an emitter current of  $10\mu A$  and at that current has an amplification of 100 at the relevant frequency (say 1MHz) then its input resistance is 250 kilohms, which is satisfactory.

## Practical Circuit

Unfortunately, a transistor operated at  $10\mu A$  can deliver very little audio output

current. So a second stage must be added. Fig. 3 is a convenient arrangement which sets the current in TR1 automatically to the correct value.

## Aerial

In some locations, a ferrite rod carrying L1 will give local-station reception. An outside aerial will certainly pull in more stations but will reveal the limited selectivity of a single tuned circuit. The traditional answer to that problem is to apply positive feedback. But that's a topic for a separate Down to Earth.

fresher and breathing much easier. I have since learned that Barts and other medically establishments find Ionisers very beneficial in cases of asthma, although a friend of mine who is a sufferer, says they do not work in all cases.

## Good Citizens

In my last article, I made a brief mention of Citizen Band Radio and said I thought the idea an excellent one especially for the sick, the old and the bedridden.

I was reminded of this today, when an old friend of mine said that CB radio had been a flop in this country. I expressed my surprise and gave my reasons. He agreed with me; not only had he bought one, but it was the finest investment he had ever made.

I asked him to elaborate, which he did. Jack lost his wife a few months ago and is naturally very lonely. By means of his CB radio he has gained many friends, as there is a wonderful cameraderie sprung up between CB users.

He gave me two specific examples. A few days before Christmas he was chatting to a CB'er who asked him his plans for Christmas day. Jack, with his customary humour, said he would stick a piece of mistletoe into his sausage and consume it in lonely splendour.

"We will soon see about that" said his CB friend. "Be ready at noon, you are having lunch with me and my family." They came and fetched him, gave him a splendid lunch, and later in the day ran him home.

Another time he mentioned that his eye was troubling him, and he had to get to Moorfields Hospital. Fifteen minutes later, a car drew up at his door and another CB friend ran him up to Moorfields, waited an hour while he received treatment, and then returned him safely home.

The marvellous thing was, that all these people were comparative strangers to Jack. The last time I wrote, I gave CB radio a pat on the back. I can see now I underestimated its real value and did not do it justice. This is an attempt to make amends.

## CAPACITOR MEASUREMENT

To measure the value of capacitors greater than about  $1\mu F$  using a standard multimeter, select a high resistance range, apply the leads to the capacitor (for electrolytics the black terminal is positive), and note the pointer's greatest initial swing.

Calibrate with a few known capacitors and either tabulate  $\mu F$  against resistance, or plot a graph. This will be a straight line if "log-log" graph paper is used.

D. Marshall,  
Loughborough,  
Leics



## Off Day

I expect, dear reader, like me, you have your off days. By ten in the morning you are saying, "This is not my Day" and by four in the afternoon, you are saying, "It's a pity I didn't stop in bed all day".

A few weeks ago, in the middle of the cold snap I had such a day. Neither my car nor my wife's car would start and I suspected the battery. I removed it and placed it by the battery charger.

My only excuse for what happened next, is that I was cold and in a hurry. Wait for it! That Electronic Wizard, Paul Young, connected positive to negative, and negative to positive. The result was spectacular!

Although I whipped the leads off in a flash, when I came to assess the damage, I found that I had burnt out the transformer, blown up the rectifier and burnt out the meter. You have to admit, that when old Paul Young blunders, he makes a thorough job of it. Anyway the steel case is still perfect!

Before I am asked why the fuse didn't blow, I will tell you. The fuse was in the battery lead. The battery leads were rather long, and in order to get a better charge I shortened them, and cut out the fusel

range. What I have always wanted to do, is to offer a complimentary kit of fixed capacitors.

This is obviously much more difficult as there are the additional problems of size and voltage. All that is certain, is that in the small values (1 picafarad to 1000 picafarad) you have a choice of, silver mica, polystyrene, or ceramic.

In the middle range (1000 picafarad to 1 microfarad) you have paper, polyester, or mixed dielectric and in the high range you can have electrolytic or tantalum. I am determined to try and produce packs, but I would particularly welcome advice from readers, as to what they think, in their opinion, is required.


Some time ago I mentioned that my wife suffers with stomach pains during thunderstorms, and our readers, helpful as usual, made some useful suggestions. After sifting through all the information, the most likely cause seemed to be that thunderstorms produce an excess of ions in the atmosphere.


I thought the answer might be to make an ioniser to produce negative ions. I purchased a kit from Tom Powell who is a regular advertiser in Everyday Electronics. It was very easy to make and at £16 approximately, shows a considerable saving over the commercially built ones which are nearer £50.

As to the results of my wife, we haven't proved conclusively yet how effective it is, but she did say it made the air seem much
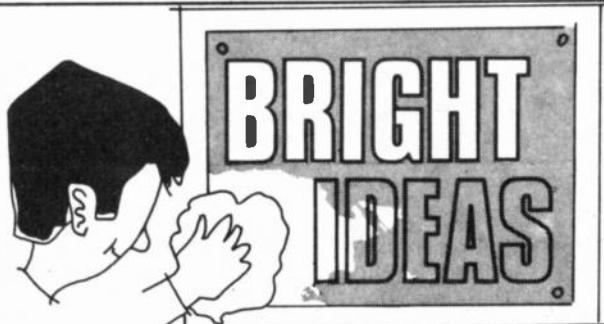
## Capacitor Kit

A few years ago we designed a resistor kit which has proved very popular with constructors, giving them a good selection of preferred values over the whole



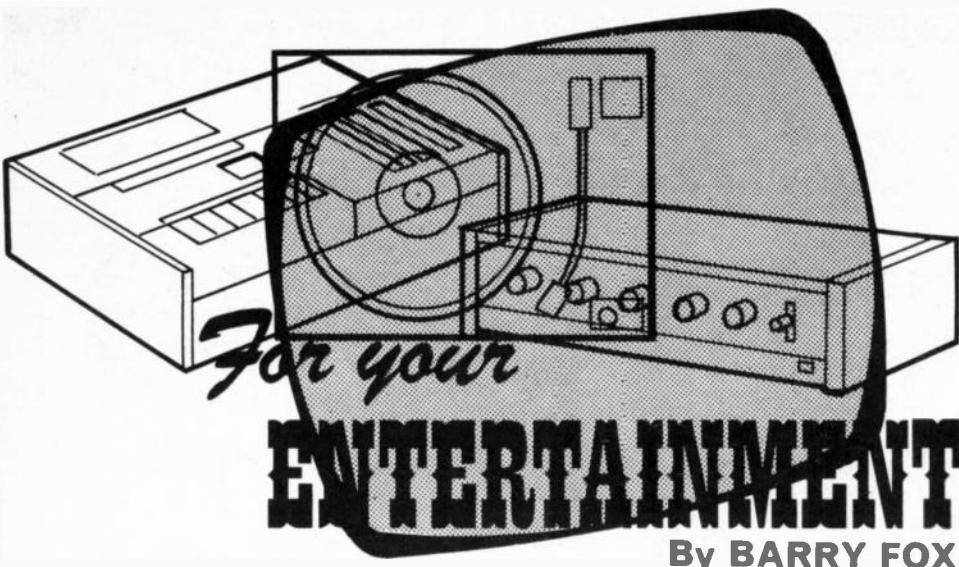

*For your*

# ENTERTAINMENT

By BARRY FOX

## Bond of Honour

Electronics firms, especially in Japan, are very secretive over their semiconductor factories. Although the basic techniques for producing chip circuits are well known, each firm has its own special know-how which is a guarded secret.

The Japanese firm Matsushita, makers of National Panasonic and Technics equipment, has a large semiconductor plant in the Japanese town of Nagaoka. Recently, and for the first time ever, they allowed a party of journalists to look round the production facilities.

Matsushita's interest in semiconductors dates back to 1952 when the company signed a "technical" co-operation agreement with Philips of Eindhoven.

The agreement still stands firm. Philips still sell Matsushita electronic components in Europe under the Philips brand-name and still have a 35 per cent share in the Matsushita Electronics Corporation.

The commercial link between MEC and Philips has often been misinterpreted. "Philips own 35 per cent of Matsushita" was a recent headline. The truth is that although MEC is a large company, it's still just a small part of the vast Matsushita empire, which is now the largest consumer electronics conglomerate in the world.

The Matsushita-Philips link has had far reaching implications in Europe. As part of the original agreement of 30 years ago Matsushita gave an undertaking not to export any raw TV tubes to Europe. So the only way that a Matsushita tube comes to Europe is inside a completed TV set or computer terminal.

This has clearly been a serious commercial handicap to Matsushita who make 5.5 million colour TV tubes a year. It has also been a hidden shield for the European electronics industry. Perhaps most important of all it underlines how seriously the Japanese take a business undertaking; once given, it is always honoured.

## Developments

Although no cameras were allowed inside the Nagaoka plant, and all the work is done in clean atmosphere rooms behind glass windows, it was possible to pick up some valuable information. VLSI products are now routinely made using a

2 or 3 micron rule scale. But two electron beam machines can draw masks to a rule below 1 micron. This is enabling Matsushita to integrate the digital/analog conversion circuitry needed for digital tape and disc recording onto a handful of chips each around 6mm square and each containing the equivalent of 15,000 circuit elements.

They have also developed a gallium-arsenide solid state laser for use in a digital disc player. This has a cost of only a few tens of dollars and a life of 50,000 hours.

## Production Techniques

The Nagaoka factory introduced a new technique for chip production in 1980. The raw silicon slices are loaded by the dozen into a cartridge like a slide magazine. Normally the slices are .4inch diameter wafers, but for test purposes smaller (3 inch) wafers are used. Operators only handle the cartridges, never the wafers.

After the wafers have been coated with photo-resist material they are optically exposed to the image of the solid state circuit to be made. The coating is photographically developed and the wafer put through etching, washing, diffusion and ion-implant processes.

Apart from the manual transport of the cartridges between machines, everything is automatic. The wafers are lifted from the cartridges by robot hands at each process stage.

The completed wafers, with hundreds of individual i.c. circuits spread as a mosaic over the surface, are then 100 per cent tested. Testing is automatic by tiny probes which are pushed down onto the wafer surface to make contact.

## Testing

There are two tests, first a d.c. parameter test and then a dynamic function test where the chip is electrically "inserted" into the actual circuit in which it will finally have to function.

It takes 18 seconds per chip to conduct 34 dynamic test functions. Although lengthy this, totally automated, process ensures that every single circuit is 100 per cent checked. Those circuits on the wafer which are found faulty are marked with a black dot.

The wafers are now passed to another machine which automatically scores lines between the several hundred individual devices on each wafer slice and breaks it into individual chips.

A television microscope shows what is going on at the chip surface. The wire bonder moves so fast that it is almost invisible. It takes only around 5 seconds to bond all the wires and connections to each chip.

Location of the chip with the bonding machine is automatic, using X marks for optical centring. Optical sensing also enables the machine to ignore any chip from the wafer surface which is marked with a black dot, signifying faulty.

To give some idea of the scale of the operation I counted around 200 automatic bonding machines, all in action, spaced along a corridor nearly 100 metres long.

Not surprisingly Matsushita aren't willing to discuss yield and failure rates. They say "yield is high" but add that the fault rate at the edges of each wafer is around 75 per cent whereas the success rate at the centre is around 75 per cent.

The Nagaoka plant has an astonishing output: 6.5 million LSIs a month, 25 million i.c.s, 170 million silicon transistors, 130 million diodes, 35 million l.e.d.s and 6 million silicon power transistors. Remember these are monthly figures!

## Computer Designed

The most astonishing sight is the Computer Aided Design of the masks. Each individual chip circuit (of which there are several hundred on each silicon wafer) starts life as a photographic replica of the circuit which is then etched into physical reality by the photo resist technique.

Clearly it's impractical to make the mask as small as the final circuit. Instead the mask is made large and optically beamed onto the wafer in reduced size, like looking through the wrong end of a telescope.

Until recently MEC were using masks 300 times the size of the final chip circuit, but have now gone to masks 2,400 times the chip size. Up to 14 masks can be used for each chip, one exposed after the other.

This is where Computer Aided Design comes in. As MEC puts it "humans can't cope with the problem". The circuit is "drawn", stage by stage, by keying instructions into a computer terminal.

The terminal screen shows how the components will lie, and simple keyboard commands replace one component with another, alter spacing or alter connections between components and so on. The final circuit can then be automatically drawn, on a giant sheet of tracing paper (2½ metres square), by a robot head which holds four different colour pencils and moves under computer control.

It seems that Matsushita is drawing onto tracing paper only as a visual check. The photo mask is directly created by feeding digital data down a line from the CAD computer and into a mask making machine. Details were secret but presumably the data controls the movement of a laser or electron beam to "draw" the mask onto film.

Bearing in mind it was the first time MEC had allowed outsiders into the Nagaoka factory, it was a revealing experience. As I left I was bothered by a nagging thought. If this is what they are prepared to show me, what is happening in those parts of the factory which aren't on view?

# The Logic Probes

## Spend Less



### LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

**£31.00\***

© Model LP-3 illustrated



### LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits, replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £12.50)

**£18.00\***

© Model LP-3 illustrated

\*price excluding P.P. and 15% VAT

**GLOBAL SPECIALTIES CORPORATION**



G.S.C. (UK) Limited, Dept. 4II  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682.  
Telex: 817477.

*Everyday Electronics, April 1982*

## Test More


### LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz. Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost. LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

**£49.00\***

© Model LP-3 illustrated

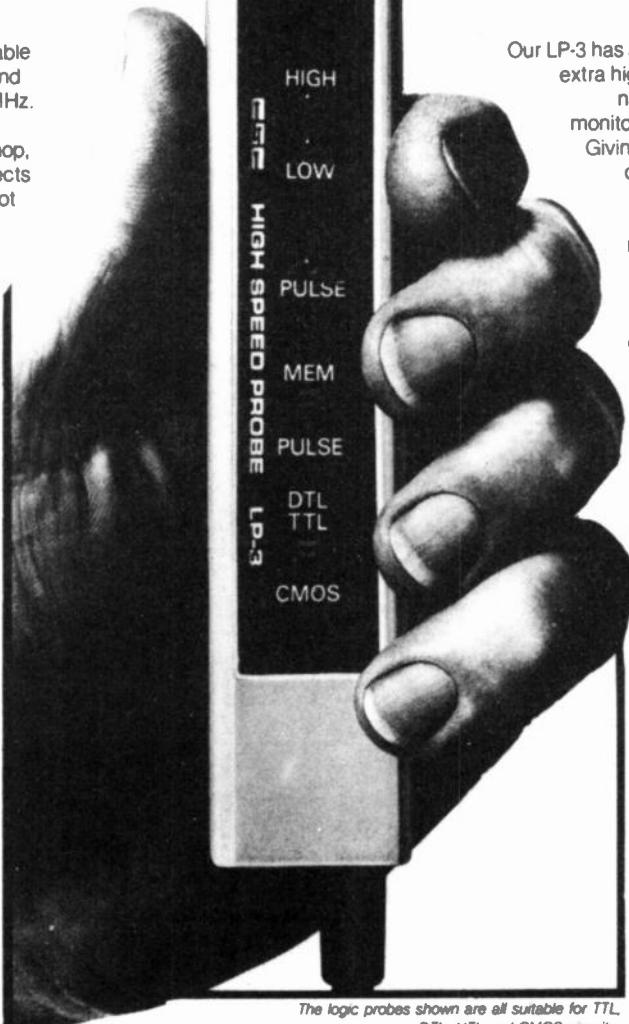

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

### The New Pulser DP-1

The Digital Pulser: another new idea from G.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz. The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

**£51.00\***

© Model LP-3 illustrated

Goods despatched within 48 hours

G.S.C. (UK) Limited, Dept. 4II		Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.												
Prices include P.P. and 15% VAT														
LP-1	£37.38	Qty.	LP-2	£22.14	Qty.	LP-3	£58.08	Qty.	DP-1	£60.38	Qty.	LPK-1	£15.52	Qty.
Name _____ Address _____														
I enclose Cheque/P.O. for £ _____ or debit my Barclaycard/Access/ American Express card no. _____ exp. date _____														
FOR IMMEDIATE ACTION — The G.S.C. 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately.														
For FREE catalogue tick box <input type="checkbox"/>														

# SQUARE One

FOR BEGINNERS

**P**ERHAPS the humble switch is the most basic electronic component of all; a mechanical device for interrupting the flow of an electric current in a circuit. The most obvious example being the on/off switch fitted to almost all domestic appliances, and this simply connects or disconnects the mains to the equipment.

Modern technology has evolved a range of electronic, semiconductor and even magnetic switches but here we shall restrict discussion to the mechanical switch, to make or break the flow of electricity between the contacts.

## SWITCH CONFIGURATIONS

The simplest form of switch is the *Single Pole Single Throw* (abbreviated to s.p.s.t.) and as the name suggests, this type has a single "pole" along with one other terminal, connection being made between the two when the switch is operated.

The next configuration to look at is the *Single Pole Double Throw* switch (abbreviated to s.p.d.t.), and once again this type has only one "pole" but with two other terminals and activating this type will switch the current flowing through the pole from one terminal to the other. For this reason it is also known as a *Single Pole Change-Over* switch.

## DOUBLE POLE SWITCHES

The *Double Pole Single Throw* switch (d.p.s.t.) is really two on/off type switches in the same package and activated simultaneously by the same mechanism. That is, they are mechanically linked but electrically isolated from each other.

In similar fashion, the *Double Pole Double Throw* (d.p.d.t. switch) is in fact two change-over switches mechanically linked and operated by the same mechanism. Once again the two halves of the d.p.d.t. switch are electrically isolated from one another. Also referred to as a *double pole change-over* switch.

## LATCHING ACTION

A latched switch is one which, having been operated, will stay in that state until it is operated again.


However, not all switches are latching, an alternative type being the non-latching or momentary action switch. In this case, the switch will change its state when depressed but return to its original state when the actuating force is removed.

Miniature push-button switches are examples of non-latching switches and can be broken down into a further two categories: the *push-to-make* switch, being off in the natural state and switching on when pressed (also described as having *normally open* contacts); and the *push-to-break* switch, being on in the normal state and switching off when pressed (said to have *normally closed* contacts).
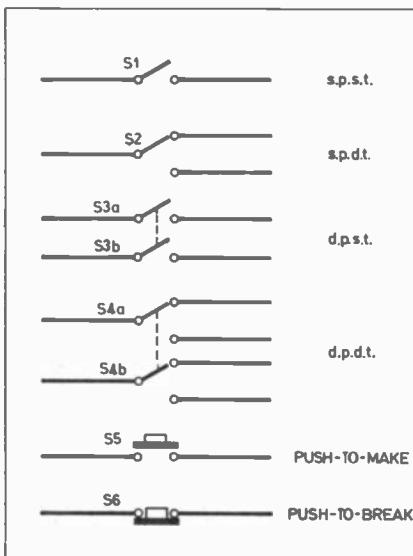
## LEVER SWITCHES

Probably the most familiar switch is the lever or toggle switch which uses a pear shaped metal lever (or "dolly") to activate it and the mechanism is completely enclosed in a black moulded housing with only the solder tags exposed.

Incidentally, the non-latching version of this type is often described as a *biased toggle* switch.



## PUSH BUTTONS

The miniature push-button switch, mentioned previously, is usually a small cylindrical device with a sprung-loaded round button to activate it.

A more complex push-button switch is the latching, modular type that, with the aid of an interlocking bar and mounting bracket, can be made up into a bank of switches like those used for input selection on hi-fi amplifiers, operating so that actuating one switch will cancel any other switch that is actuated at that time. Each switch can have two, four or six sets of change-over contacts and are a little more expensive with the additional cost of the interlocking hardware and the clip-on buttons.


## OTHER SWITCHES

Another modular switch system is the rotary wafer switch, consisting of a rotating switch mechanism onto the spindle of which is placed wafer switch elements, the maximum number of positions usually being twelve. The pole of the switch element is connected to a wiper contact which sweeps around the wafer as the switch is rotated thus making contact with the terminals of the switch. Each position is latched and an adjustable stop enables the switch to be custom designed for any number of "ways".

The microswitch is a useful device to understand, usually being a single pole change-over switch operated by a very small push-button and requiring very little actuating force.

This type of switch is frequently used to indicate the presence of something, for example, an open door operating the switch (ideal for burglar alarms).

Fig.1. (left) The circuit symbols of the four basic switch configurations plus the two types of push-button switch. Photograph (below) showing groups of various types of switch, including: (1) slide switches; (2) rotary switches, including the wafer type; (3) key operated on/off switch; (4) toggle switches ranging from a large d.p.d.t. to a miniature s.p.d.t. and (5) push-button switches, including a microswitch, third from left, and a latching type, extreme right.

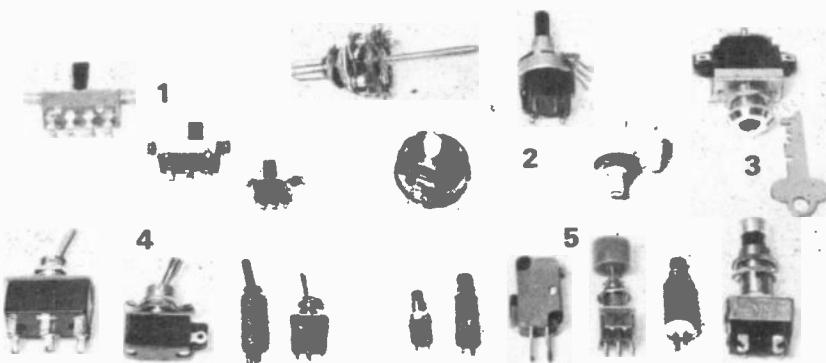

## On the Shelf

The latest Piccolo from Revox is not a new musical instrument, but a new loudspeaker enclosure just introduced to their range of audio equipment.

With a front panel measuring only 220mm x 140mm, the Piccolo is designed for sitting on the bookshelf. The enclosure contains a bass/mid-range driver and a dome tweeter loudspeaker.



With a claimed frequency response of 80Hz to 22kHz ±3dB, the Piccolo will handle up to 35W and retails at £90 plus VAT per pair.

F. W. O. Bauch Ltd, Dept EE, 49 Theobald Street, Boreham Wood, Herts WD6 4RZ.

# NEW • NEW • NEW • NEW PRODUCTS NEW • NEW • NEW • NEW

## DIGITAL THERMOMETER

A hand-held digital thermometer has just recently been launched onto the market by Sinclair Electronics.

Marketed under the brand name of Thandar, the TH301 features a large l.c.d. read-out display and covers a temperature range of -50 to 750°C, with a 1°C resolution. It is claimed that by using the latest technology, over 1,000 hours of battery life is obtainable.

A range of thermocouples are offered as optional extras and include mineral filled, hypodermic, right angle and surface thermocouples.

The Thandar TH301 Digital Thermometer costs £59.50 plus VAT and is supplied with battery and fast response bead thermocouple.



Sinclair Electronics Ltd, Dept EE, London Road, St Ives, Huntingdon, Cambs PE17 4HJ.

## A Good Case

A new range of low profile consoles have recently been marketed by Boss Industrial Mouldings.

The sloping fronts on the BIM 2600 make them ideally suited for applications where meters, keyboards and switches have to be easily visible to the eye.

Ranging in size from 178mm x 261mm with an overall height of 51mm, the cases are of two piece, all aluminium, construction in which the whole unit is held together by screws running through base rubber feet into hank bushes.

The standard colour scheme for the cases is brown base and beige top panels. Alternative colours, together with special vent slots or cutouts, are available at extra cost.

Boss Industrial Mouldings Ltd, Dept EE, James Carter Road, Mildenhall, Suffolk IP28 7DE.



## NEW POWER

As part of a new expansion programme, and to introduce a new range of power supplies, BICC-Vero Electronics have created a new division within the company which will trade under the name of BICC-Vero Distribution, Power Conversion Division.

As such, the Power Conversion Division will become sole UK distributor of the Boschert range of switched power supplies. The company will also act as master supplier to the Boschert distribution network within Europe and Scandinavia.

Based in Silicon Valley, Boschert Inc became a BICC company in 1981. They are an acknowledged leader in switched mode power supply technology, particularly in the field of open frame units. Products range from 25 watts to 400 watts, with accent on reliability.

BICC-Vero Distribution Ltd, Power Conversion Division, Dept EE, Stansted Road, Boyatt Wood Industrial Estate, Eastleigh, Hants.

A pocket microscope, which may be useful for checking for possible "shorts" between copper tracks on p.c.b.s and stripboards, is now being marketed by Stotron.


With a 20 times magnification, the Scope Mark-III is just 125mm long and has a graticule showing linear and angular measurements. Illumination is from standard 1.5V penlight batteries.

## POCKET MICROSCOPE

A micro-stand, with spring clips for sample slides, is available as an option so that the device can be used like a conventional microscope.

The recommended retail price, with stand, is expected to be under £20.

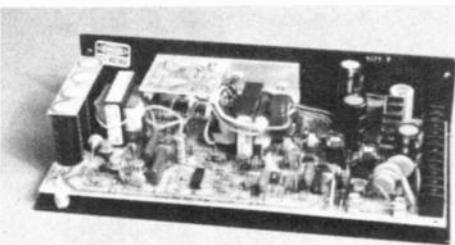Stotron Ltd, Unit 1, Dept EE, Haywood Way, Ivyhouse Lane, Hastings, East Sussex.




## HOOKED

A newly formed company, I & J Products, has taken over the UK franchise for the popular EZ Hook test probes.

The range originated with a single test probe, and has advanced to DIP testers and p.c.b. probes.

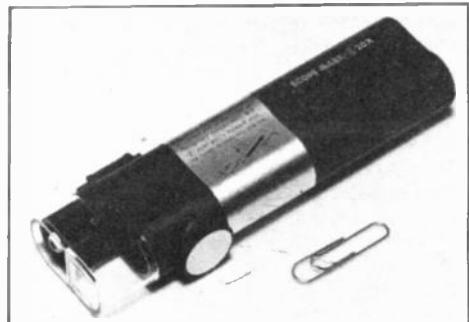I & J Products Ltd, Dept EE, Kingsbury House, 7a Christchurch Road, Ringwood, Hants



# CIRCUIT EXCHANGE

## AUDIBLE HEADS OR TAILS

This circuit was built as a binary decision maker, using the 741 op-amp. It is connected as an astable with an equal mark/space ratio when microswitch S1 is depressed. When S1 is released pin 6 of IC1 goes high or low depending on logic state at the moment of release.


The timer chip, IC2, is connected as an astable multivibrator and with S1 depressed generates a high frequency note in LS1. When S1 is released it will either switch to a low tone or go off altogether.

\* M. Warren,  
Lewes,  
East Sussex.

*This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised.*

*Payment is made for all circuits published in this feature.*

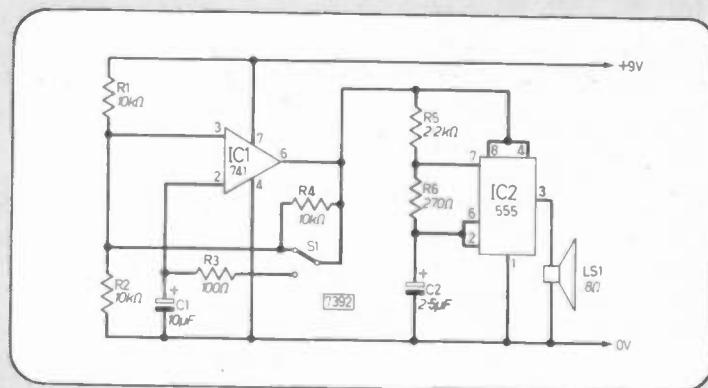*Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.*




\* Please let us have your full address.

## "TWO-SECOND-RULE" TIMER

This simple timer was designed as a safety aid to car drivers. The prototype has been successfully used for some time. It is based on the well-known two-second-rule safety factor.

This method of use is simple, but it may well prove to be a lifesaver. A landmark is chosen, such as a bridge or a motorway signal. As soon as the bonnet of the car in front of you reaches the mark the "go" button is depressed. The tone produced immediately changes. If your car bonnet reaches the mark before the tone reverts to normal you are too close to the car in front and should drop back. When not in use the device produces a continuous tone to remind you to switch it off.

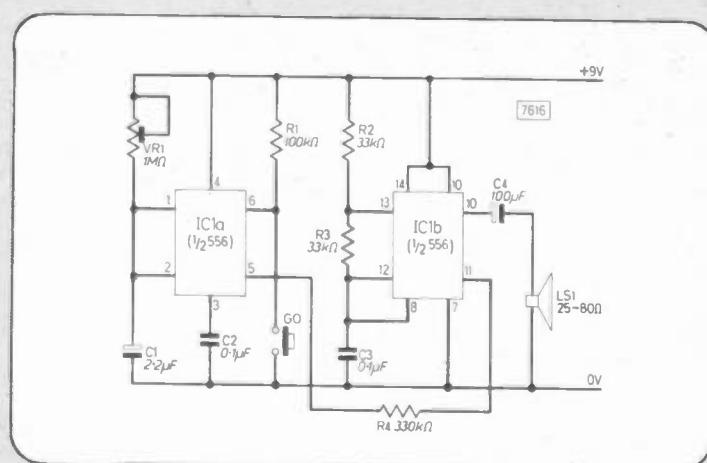Half of a 556 dual timer is used as a monostable while the other half is used as an astable. The frequency



of the astable may be altered by applying a voltage to pin 11. When the "go" button is depressed the monostable produces an output whose

duration is dependent on the value of C1 and VR1. This output modulates the frequency of the astable.


When initially setting the timer, VR1 should be adjusted to give a 2 second tone change when the "go" button is depressed.

Chris Sinclair,  
Hull,  
N. Humberside.

## ELECTRONIC METRONOME

This circuit is for a simple electronic metronome. It is based on a 555 timer i.c. wired as an astable multivibrator. The component values have been chosen to give a set of pulse rates from about 30 to 220 beats per minute. D1 is a l.e.d. and its brightness is controlled by R3. WD1 is a 6V solid state buzzer which can be muted by opening S1. The unit is calibrated with a stopwatch by counting the pulses in one minute.

Andrew White,  
Formby, Liverpool

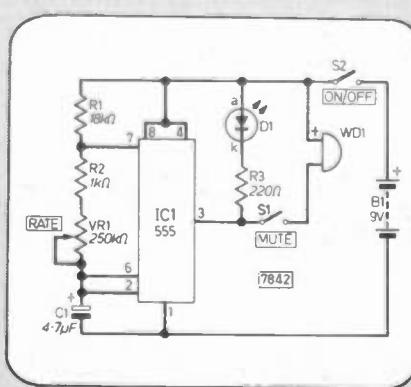

# CIRCUIT EXCHANGE

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

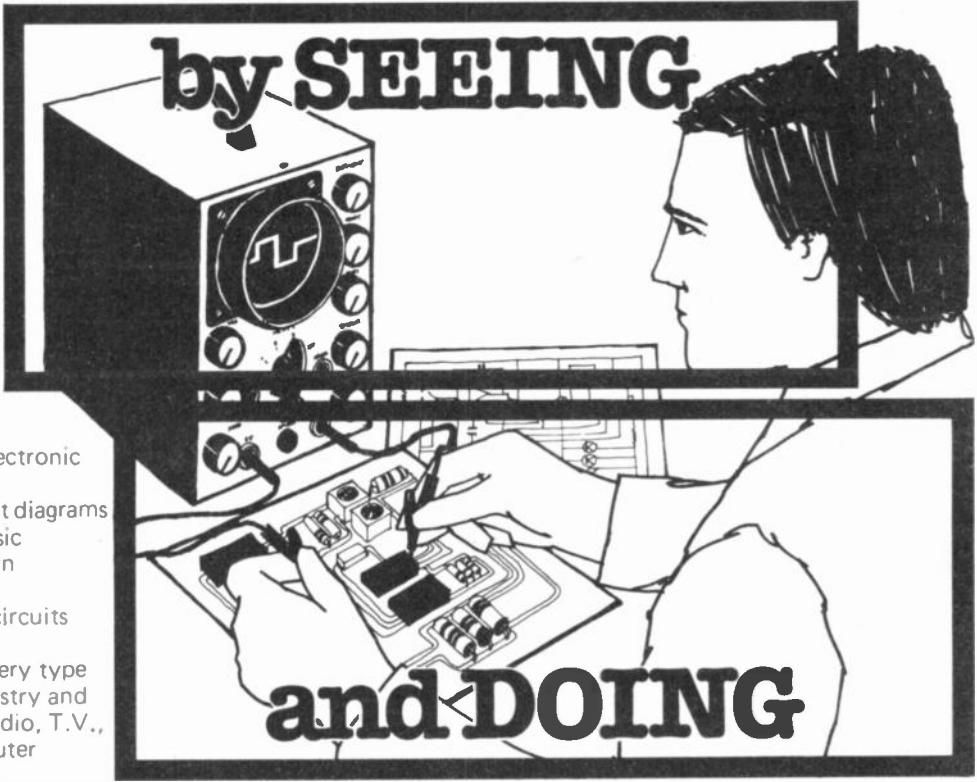

### New Job? New Career? New Hobby? Get into Electronics Now!

**FREE!**  
COLOUR BROCHURE



Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I am interested in:

- COURSE IN ELECTRONICS  
as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

OTHER SUBJECTS \_\_\_\_\_

BLOCK CAPS PLEASE

EE/4/820

British National Radio & Electronics School Reading, Berks. RG1 1BR.

# Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

**Lower price: higher capability**  
With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.

## Kit: £49.95

**Higher specification, lower price – how's it done?**

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

### New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.




## Built: £69.95
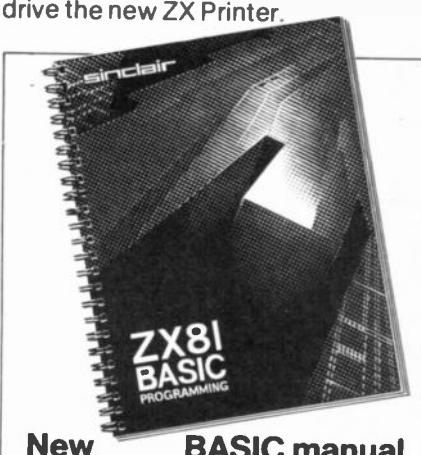
### Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



New BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

# uter-



## Available now- the ZX Printer for only £49.95

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha-numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

### How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.

Order

Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £

\*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £

\*Please charge to my Access/Barclaycard/Trustcard account no.

\*Please delete/complete as applicable.

Please print.

Name: Mr/Mrs/Miss

Address:

FREEPOST - no stamp needed. Offer applies to UK only.

EVE 04

# sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: (0276) 66104 & 21282.

# ELECTROVALUE

## CATALOGUE '82

A MUST FOR ANYONE USING  
A SCREWDRIVER OR  
SOLDERING IRON!



PACKED WITH INFORMATION  
ON MORE THAN 6000 ITEMS  
INCLUDING SIEMENS  
CAPACITORS, FERRITES AND  
SEMI-CONDUCTORS, ALSO  
SOLDER TOOLS, METERS ETC.

FOR YOUR COPY OF  
CATALOGUE '82 please send 70p  
(includes 70p voucher reclaimable  
against orders valued £10.00 or  
over).

### DISCOUNTS

5% on orders over £23.00 (inc.  
VAT). 10% on orders over £57.50  
(inc. VAT) on most catalogue items  
but not for payments by credit  
cards.

**ALL ITEMS BRAND NEW  
AND GUARANTEED  
SPEEDY MAIL ORDER  
SERVICE**

No P/P charges on U.K. C.W.O.  
orders over £5.75 Inc. V.A.T.  
(add 40p handling charge if  
under).

PLEASE ADD 15% V.A.T. TO  
TOTAL VALUE OF ALL  
ORDERS

**NEW PRICE LIST**  
Send S.A.E. for latest issue valid 4  
months. Many reduced prices.


4000BE SERIES	15p	74LS00 SERIES	14p	74LS193	90p
4001BE	18p	74LS02	14p	74LS195	87p
4002BE	18p	74LS04	16p	74LS197	85p
4006BE	89p	74LS05	23p	74LS253	90p
4007BE	18p	74LS08	20p	74LS257	75p
4008BE	65p	74LS10	19p	74LS259	160p
4009BE	54p	74LS11	20p	74LS266	31p
4010BE	45p	74LS14	58p	74LS273	130p
4011BE	18p	74LS20	18p	74LS279	78p
4012BE	19p	74LS30	21p	74LS299	285p
4013BE	38p	74LS32	22p	74LS367	58p
4014BE	96p	74LS37	24p	74LS368	55p
4015BE	114p	74LS38	35p	74LS373	150p
4016BE	38p	74LS42	59p	74LS374	84p
4018BE	68p	74LS51	25p	74LS393	85p
4019BE	44p	74LS73	38p	Computing IC's	
4020BE	90p	74LS74	30p	2114	£1.50
4021BE	88p	74LS75	44p	4116	£1.50
4022BE	70p	74LS76	38p	4116 200nS	£1.50
4023BE	18p	74LS85	89p	4116 250nS	£1.30
4024BE	88p	74LS88	38p	4116 300nS	£1.30
4025BE	55p	74LS90	44p	780A CPU	£6.00
4026BE	58p	74LS93	59p	780A P10	£6.00
4027BE	104p	74LS107	57p	780A CTC	£6.00
4028BE	97p	74LS112	48p	6402 UART	£4.56
4030BE	51p	74LS123	82p	Special Offer	
4041BE	84p	74LS125	45p	25 x 4116 (300nS)	£18.00 only
4042BE	75p	74LS126	42p	REGULATORS	
4043BE	88p	74LS132	60p	7805/12/15/24	65p
4044BE	93p	74LS136	42p	7905/12/15/24	65p
4045BE	128p	74LS137	118p	7805/12/15/24	65p
4049BE	48p	74LS138	45p	7905/12/15/24	65p
4050BE	48p	74LS139	78p	7805/12/15/24	32p
4060BE	133p	74LS145	124p	7905/12/15/24	67p
4069BE	23p	74LS148	165p	723 (14 pin)	36p
4070BE	27p	74LS151	77p	78H05	£5.55
4071BE	19p	74LS153	77p	78MGK	£7.20
4072BE	19p	74LS155	94p	79HKGK	£12.15
4081BE	19p	74LS156	94p	LM317K	£3.21
4082BE	19p	74LS157	60p	Low Profile IC Holders—BICC	
4093BE	45p	74LS161	78p	pins 1 off,	25 off
4510BE	65p	74LS163	90p	8	£1.00
4511BE	60p	74LS164	90p	8	£1.00
4514BE	393p	74LS165	75p	14	£2.40
4516BE	137p	74LS166	185p	16	£2.88
4518BE	50p	74LS173	100p	18	£2.20
4520BE	70p	74LS174	85p	20	£1.80
4543BE	100p	74LS175	94p	22	£4.20
4583BE	195p	74LS191	90p	24	£4.20

SHOP HOURS 9-5.30 p.m. (1 p.m.  
Sat.) Please mention this journal  
when writing or ordering by post.

**ELECTROVALUE**
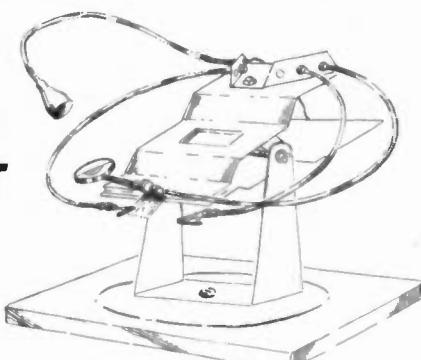
## The MINIBENCH\* System

CAN YOU  
AFFORD  
TO BE  
WITHOUT  
ONE?



\*Trade Mark

Pat App for

For details & price lists see March issue or write:-

**ABSONGLEN LTD**

Dept. EE4

P.O. BOX 13, HEREFORD, HR1 1EA

YOU PUT MORE POWER IN YOUR £  
WHEN YOU BUY FROM US!

### NICADS AND CHARGERS

by Sanyo Cadnic

N1450AA (AA size)

N1800DC (C size)

N1950D (D size)

6N7SP (PP3 size)

CHARGERS:

NC456 (PP3)

NC450S (4 x AA)

NC123 (AA, C,D)

### COMPUTERS

Our computer business is now transferred to:

EV COMPUTING LTD,

700 BURNAGE LANE, BURNAGE,

MANCHESTER M19A 1MA.

Phone 061-432 4945.

- A MICROVALUE FOUNDER

MEMBER & DISTRIBUTOR.

Enquiries and orders may be sent to  
ELECTROVALUE for passing on to EV  
COMPUTING who will deal with you  
promptly and efficiently.

### CAPACITOR PACK

Buy in quantity for best value

CP1: 100 ceramic capacitors from 1p8 to 1μF.

Selection determined by popular demand.

Pack Price £3.50

### RESISTORS IN HANDY PACKS

1W, 5% tolerance, each pack 100 items from one decade.

Selection determined by popularity demanded values.

Pack Price £1.30

### ALUMINIUM BOXES WITH LIDS

Size

Price

AB7 70x133x38

AB8 101x101x38

AB9 101x70x38

AB10 101x133x38

AB11 101x64x51

AB12 76x51x25

AB13 127x89x64

### PANEL METERS

£2.20 each

instead of £2.69

until March 31st

### TYPE MU

FSD 50μA, 100μA, 1mA, 5mA,  
10mA, 50mA, 500mA, 1A.

### SWITCHES AND CONNECTORS IN VERY GREAT VARIETY. VEROBOKES, I.L.P. TOROIDAL TRANSFORMERS.

### SABTRONICS

#### FREQUENCY METER

Model 8000B: 9-digit 1GHz Frequency Meter.  
Professional specification: £100.00

Model 8000B: 9-digit 1GHz Frequency Meter.  
Professional specification: £100.00

Model 8000B: 9-digit 1GHz Frequency Meter.  
Professional specification: £100.00

Model 8000B: 9-digit 1GHz Frequency Meter.  
Professional specification: £100.00
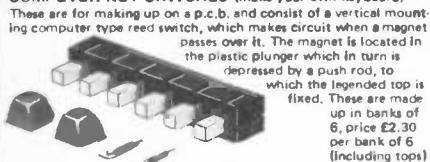
### COMPUTER KEY SWITCHES (make your own keyboard)



**OUR CAR STARTER AND CHARGER KIT** has no doubt saved many motorists from embarrassment in an emergency you can start off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £12.50 + £3.00 post.

**GPO HIGH GAIN AMP/SIGNAL TRACER**. In case measuring only 5x11x3½" x 1½" is not enough, this is an extremely high gain (70dB) solid state amplifier designed for use as a signal tracer on GPO cables, etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4½V battery and has input, output sockets and on/off volume control, mounted flush on the top. Many other uses include general purpose amp, cueing amp, etc. An absolute bargain at only £1.85. Suitable 80mm earpiece £3.95.

### COMPUTER PRINTER FOR ONLY £6.95

Japanese made Epson 310 — has a self-starting, brushless, transistored d.c. motor to drive the print hammers, print drum — tape for forward/reverse and paper feed.

Complete in module form with electronics including Printer Synchro Signal Amplifier & Printer Reset Signal Amplifier. Brand new and with technical data. £6.95 + £1.35 post. Data separately for £1.00.

### SUPER HI-FI SPEAKER CABINETS

Made for an expensive Hi-Fi outfit — will suit any decor. Resonance free. Cut-outs for 6½" woofer and 2½" tweeter. The front material is Dacron. The completed unit is most pleasing. Supplied in pairs, price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.00 the pair.



### GOODMANS SPEAKERS

6½" 8 ohm 25 watt £4.50, 2½" 8 ohm tweeter, £2.50. No extra for postage if ordered with cabinets. Xover £1.50.

### VU METER SNIP

Approximately 1½" square, suitable for use as a recording level meter power output indicator or many similar applications. Full vision front, cover easily removable if you wish to alter the scale. Special snip price £1.00 or 10 for £9.00.




### MOTORISED DISCO SWITCH

With 10 amp change-over switches. Multi-adjustable switches all rated at 10 amps, this would provide a magnificent display. For mains operated 8 switch model £6.25, 10 switch model £6.75, 12 switch model £7.25.
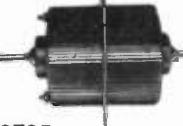
### 12v MOTOR BY SMITHS

Made for use in cars, these are series wound and they become more powerful as load increases. Size 3½" long by 3" dia. These have a good length of ¼" spindle — price £3.45. Ditto, but double ended £4.25.



### EXTRA POWERFUL 12v MOTOR

Made to work battery lawnmower, this probably develops up to ½ h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. £6.80 + £1.35 post.

### THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 - 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our water-proof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

### UNIVAC KEYBOARD BARGAIN

50 keys, together with 5 miniature toggle switches all mounted on a p.c.b. together with 12 i.c.'s, many transistors and other parts. £13.60 + £2.00 post.

This is far less than the value of the switches alone. Diagram of this keyboard is available separately for £1.



### SOLENOID WITH PLUNGER

Mains operated £1.99  
10 - 12 volts DC operated £1.50.

**FREE** OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

# J. BULL (Electrical) Ltd.

(Dept. EE), 34 - 36 AMERICA LANE,  
HAYWARDS HEATH, SUSSEX RH16 3QU.

Established  
30 YEARS

### MULLARD UNILEX

A mains operated 4 + 4 stereo system. Retain one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. It's easy to assemble modular form this should sell at about £30 — but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16.75 including VAT and post. **FREE GIFT** — buy this month and you will receive a pair of Goodman's elliptical 8" x 5" speakers to match this amplifier.



### 3 CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it

is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by ¼" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £14.95 in kit form or £25.00 assembled and tested.

### FIVE UNUSUAL SWITCHES

For inventors, experimenters, service engineers, students or in fact anyone interested in making electrical gadgets. The parcel contains: — delay switch — motor driven switch — two-way and off switch — polarity changing switch — and humidity switch. Our regular price for these switches bought separately is over £10, but this month you can have the 5 for £2.50.

### THIS MONTH'S SNIP

#### IONISER — AIR FRESHENER


Headaches, tiredness and that "Thundery Weather Feeling" — Scientists say are caused by an excess of positive ions, they also say that heaters and other modern aids can cause this ion imbalance. The answer is a negative ion generator or ioniser — this mains operated device will fill your home, office or workshop with a refreshing breeze neg. ions, which you will find both stimulating and invigorating. Complete kit in neat sturdy plastic case. £14.95.

### SPIT MOTORS

These are powerful mains operated induction motors with gear box attached. The final shaft is a ½" rod with square hole, so you have alternative coupling methods — final speed is approx. 5 revs/min, price £5.50. — Similar motors with final speeds of 80, 100, 150 & 200 r.p.m. same price.
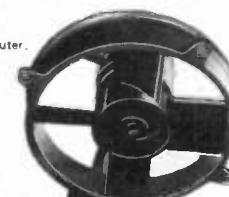
### EXTRACTOR FAN

Mains operated — ex. computer.  
5" Woods extractor £5.95, Post £1.50  
5" Planair extractor £6.50, Post £1.25  
4" x 4" Muffin 115v. £4.50, Post 75p.  
4" x 4" Muffin 230v. £5.75, Post 75p.



### TAPE PUNCH & READER

For controlling machine tools, etc. motorised 8 bit punch with matching tape reader. Ex-computers, believed in good working order, any not so would be exchanged. £17.50 pair. Post £4.00.

**MINI-MULTI TESTER** Deluxe pocket size precision moving coil instrument, jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC Volts 10, 50, 250, 1000, AC Volts 10, 50, 250, 1000, DC Amps 0 - 100 mA.

Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test probes and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

**FREE** Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

**MAIL ORDER TERMS:** Cash, P.O. or cheque with order. Orders under £10, add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclaycard orders phone Haywards Heath (0444) 54563. Bulk Orders: Write for quote. Normal delivery by return.

### TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox — all electronic parts and circuit. £2.30. (not licensable in the U.K.).

### RADIO MIKE

Ideal for disco and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £8.90 comp. kit. (not licensable in the U.K.).

### FM RECEIVER

Made up and working, complete with scale and pointer needs only a headphones, ideal for use with our surveillance transmitter or radio mike. £5.85.

### LEVEL METER

Size approximately ¾" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.



### POCKET AUDIO COMPONENT TESTER

With it you can quickly test diodes, rectifiers, transistors, capacitors, check wiring and p.c. boards for open circuits, find the anode and cathode of a diode or rectifier and whether a transistor is PNP or NPN, which are the base collector and emitter connections. Condensers, if bad, give a continuous signal, but if good, give intermittent signals of varying length depending on their value. The test current very low (20uA) and the voltage only 1.4V, so it is also possible to check MOS devices, as well as sensitive transistors without fear of damaging them. The unit is supplied complete with internal battery, which should last many months. Price £3.45.

### VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs, repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case, but we can supply a plastic base £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/offs per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

### STEREO HEADPHONES

Very good quality, 8 ohm impedance, padded, terminating with standard ¼" jack plug £2.99 post 60p.



### TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs. £2.50.



### DELAY SWITCH

Mains operated — delay can be accurately set with pointers knob for periods of up to 2½ hrs. 2 contacts suitable to switch 10 amps — second contact opens a few minutes after 1st contact. £1.95.

### 6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit includes case materials, six transistors and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy if you have an amplifier to connect it to or a pair of high resistance headphones. Price £11.95.

### MEDIUM & 2 SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 65p. High resistance headphones (give best results) £3.75. Kit includes chassis and front but not case.

### RADIO STETHOSCOPE

Easy to fault find — start at the aerial and work towards the speaker — when signal stops you have found the fault. Complete kit £4.95.

### INTERRUPTED BEAM

This kit enables you to make a switch that will trigger when a steady beam of infra red or ordinary light is broken. Main components — relay, photo transistor, resistors and caps, etc. Circuit diagram but no case. Price £2.30.

### MUGGER DETERRENT

A high-note beeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

### TANGENTIAL BLOW HEATER

2.5 Kw quiet, efficient instant heating from 230/240 volt mains. Kit consists of blower as illustrated, 2.5 Kw element, control switch and data all for £4.95. post £1.50.



### 12V SUBMERSIBLE PUMP

Just join it to your car battery, drop it into the liquid to be moved and up it comes, no messing about, no priming, etc. and you get a very good head. Suitable for water, paraffin and any non-explosive non-corrosive liquid. One use if you are a camper, make yourself a shower. Price: £9.50.

# ALCON

SPECIAL OFFER

20k $\Omega$ /V d.c.  
4k $\Omega$ /V a.c.

## mini 20

The Mini 20 is an ideal instrument for the constructor.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10 on the normal retail price.

The 28 ranges cover all likely requirements. Operation is straight-forward, just turn the selection switch to the required range position.

### RANGES

d.c. V: 100mV, 3V, 10V, 30V, 100V, 300V, 600V.

a.c. V: 15V, 50V, 150V, 500V, 1500V.

d.c. I: 50 $\mu$ A, 600 $\mu$ A, 6mA, 60mA, 600mA.

a.c. I: 30mA, 300mA, 3A.

Ohms: 2k $\Omega$ , 2M $\Omega$ .

Accuracy: 2% d.c. & resistance, 3% a.c.

Dimensions: 105 x 130 x 40mm

**Movement protected by internal diode and fuse.**

For details of this and the many other exciting instruments in the Alcon range, including multimeters, component measuring and electronic instruments please write or telephone:



Supplied complete  
with case, leads and  
instructions.

**only £21.60**

**INCLUSIVE OF POST  
PACKAGE-V.A.T.**

Goods despatched by return of post

**ALCON Instruments Ltd.**

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

Buy British—Buy Douglas Transformers  
Mail Order from TITAN Transformers &  
Components

Central Hall Chambers, Duncombe Street,  
Grimsby, South Humberside DN32 7EG

Prices include 15% V.A.T. Send for our  
Catalogue. Please allow up to 28 days delivery.



12-24V RANGE PRI 220/240V

SEC 115V 230V 240V 250V

0-12V 24V 30V 36V 48V

TYPE AMPS PRICE P/P TYPE AMPS PRICE P/P TYPE VA PRICE P/P

12V 0-50 2.65 0.94 124 1 0.5 3.30 1.57 25 65 3.90 1.20

71 2 1 2.77 1.20 126 2 1 8.36 1.57 64 80 4.82 1.20

18 4 2 3.88 1.87 127 4 2 16.88 2.90 90 140 6.21 1.57

68 3 1.5 3.46 1.87 128 6 3 11.78 2.10 69 250 7.54 1.57

85 5 2.5 6.08 1.57 129 8 4 14.72 2.40 53 350 9.73 2.10

70 6 3 8.67 1.57 130 10 5 17.10 2.40 67 500 11.70 2.40

108 8 4 8.03 1.57 130 12 6 19.44 2.55 83 750 13.51 2.25

116 12 6 9.31 2.10 121 16 8 27.70 2.90 84 1000 18.21 2.55

17 16 8 11.46 2.25 122 20 10 32.05 4.50 95 2KVA 34.38 5.50

187 30 15 19.23 2.50 189 24 12 37.02 5.50 73 3 64.74 5.50

232 40 20 27.01 5.00 101 10 170.08 10.50

30-60V RANGE PRI 120/20/240V

SEC 115V 230V 240V

0-12V 24V 30V 36V 48V

VOLTS OUT 1-25 2-50 3-100 4-200

TYPE AMPS PRICE P/P TYPE AMPS PRICE P/P TYPE VA PRICE P/P

15V 30v 0.50 2.84 1.20 430 1 0.5 4.08 1.57 56W 20 6.60 0.94

70 2 1 3.89 2.00 431 2 1 7.84 1.57 64W 80 8.43 1.57

3 4 2 6.18 1.57 432 4 2 12.94 2.25 4V 150 16.46 1.90

20 6 3 9.19 1.90 433 6 3 14.82 2.40 69W 250 13.17 2.10

21 8 4 8.52 1.90 434 8 4 16.04 2.70 67V 500 20.46 2.40

51 10 5 16.57 2.10 435 10 5 28.75 2.90 67V 500 20.46 2.40

117 12 6 11.94 2.25 436 12 6 36.16 4.50 95W 2000 54.83 5.50

88 16 8 18.14 2.40 437 16 8 39.47 5.50 73W 3000 78.67 7.00

25-50V RANGE PRI 120/220/240V

SEC 115V 230V 240V

0-12V 24V 30V 36V 48V

VOLTS OUT 1-25 2-50 3-100 4-200

TYPE AMPS PRICE P/P TYPE VA PRICE P/P TYPE VA PRICE P/P

24V 50V 0.50 3.29 1.43 149F 60 8.40 1.90 415C 50 2.31 0.94

102 1 0.50 4.09 1.43 150F 100 9.71 1.90 416C 100 3.46 0.94

103 2 1 4.09 1.43 151F 200 13.84 2.25 417C 200 4.00 1.20

104 4 2 1.73 1.73 151F 350 20.77 2.80 418F 500 6.26 1.57

105 6 3 9.68 1.90 152F 250 18.69 2.40 418F 350 6.26 1.57

106 8 4 12.24 1.90 153F 350 20.77 2.80 419F 500 6.74 1.90

107 12 6 18.15 2.20 154F 500 26.03 2.90 420E 750 8.33 2.10

118 16 8 22.46 2.55 155F 750 36.75 5.50 421F 1000 11.64 2.25

119 20 10 37.05 2.55 156F 1000 47.42 6.50

## JOIN UP WITH LITESOLD

Litesold's new 'L' Series soldering iron — now at a bargain price.

Outstanding performance. Lightweight. Easy to maintain.

Elements are enclosed in Stainless Steel shafts. insulated with mica and ceramic. Non-seize

interchangeable bits. choose from

'copper' or 'long life'. A very special

tool at a very special 'direct' price.

Just £5.58 for Iron fitted with 3.2mm

copper bit. Just £2.40 for 3 spare

copper bits (1.6; 2.4; 4.7).

A mere £4.38 for

professional spring

stand! Or buy the

lot for £11.12!

and save 10%.

All prices inc. VAT & P.P.

Please allow 14 days delivery.

Write today. Send Cheque/P.O. to Litesold, 97-99 Gloucester Road, Croydon CR0 2DN or phone 01-689 0874 for Barclaycard/Access sales.



**The ONE catalogue  
you MUST  
have!**



- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.

Send cheque or P.O. for £1.50.

**HOME RADIO Components Ltd**  
Dept. EE P.O. Box 92, Mitcham, Surrey.  
01-643 9866

Send Today 50p (Refundable with First Order) for Catalogue  
**TITAN TRANSFORMERS AND COMPONENTS**  
CENTRAL HALL CHAMBERS GRIMSBY DN32 7EG  
MAIL ORDER ONLY - PRICES INCLUDE 15% VAT EE 4

# WE WILL BEAT BY 5% ANY LOWER PRICE ADVERTISED BY COMPETITORS★

## WATER RESISTANT WATCHES

With Alarm, Hourly Time Signal, Stopwatch and  
Calendar

### 100 METRE WATER RESISTANT



W-100  
Resin  
case/strap  
£19.95



W-150C  
S/S case,  
resin strap  
£21.95



W-150  
All  
S/S  
£24.95

Time and auto calendar. Alarm and hourly chimes. Countdown alarm timer with repeat memory function. Professional 1/100 second stopwatch. Time is always on display, regardless of display mode. Amazing 5 year lithium battery life. Superior to the W-250.

### 50 METRE WATER RESISTANT



W-20  
Resin  
case/strap  
£12.95



W-21  
Resin  
S/S trim  
£14.95



W-30  
All  
S/S  
£19.95

12/24 hour time and auto calendar. Alarm and hourly chimes. Professional 1/100 second stopwatch to 12 hrs. Compact and slim cases, approx. 8mm thick. Lithium.

### OTHER MODELS

**AX-210.** The world's most versatile watch?

Analog Display  
LC Display of hours and minutes

Digital display

★ Local time, 12 or 24 hour  
★ Full calendar display

★ Dual time, 12 or 24 hour

★ Alarm time display

★ Countdown alarm timer with  
memory function

★ Professional 1/100 second stopwatch

Hourly time signal. Daily alarm electronic buzzer or 3 selectable melodies. Rapid forward/back setting. 9.4 x 35.4 x 36mm.

Usual Price £29.95

Lowest price elsewhere

★ £27.95



CA-85  
Resin  
Usually £19.95  
Price elsewhere  
★ £18.95



CA-901  
Chrome  
Usually £29.95  
Price elsewhere  
★ £27.95



J-100  
Resin  
£19.95

**CA 85/901.** Time and auto calendar. Calculator. Alarm and hourly chimes. Stopwatch. Dual time. DIGITAL SPACE INVADER game.

**J-100.** Similar to the CA-85 but without dual time and with a JOGGING COMPUTER instead of the game function.

**GM-10.** Alarm chrono with SPACE INTERCEPTOR game

£19.95

★ Providing the advertiser has stocks and we do not sell at a loss. DELIVERY NORMALLY BY RETURN

Price includes VAT and P&P. Send cheques, PO, or phone your ACCESS, VISA or B'CARD number to:

LEADING CASIO SPECIALISTS

Dept. EE,

38 Burleigh Street, Cambridge CB1 1DG

Telephone: 0223 312866

# TEMPUS

Everyday Electronics, April 1982

## CALCULATORS

### £100 POCKET COMPUTER.

Casio FX-702P. NOW ONLY £99.95

FX-602P. Usual price £74.95. Price elsewhere £71.95

FP-10 Printer £44.95 (elsewhere £41.95)

FA-2 £19.95

### OUR BEST SELLING SCIENTIFIC

### FX-3600P

10 digits, 61 scientific functions including Integrals and Regressional analysis. Up to 38 program steps, 2 programs and 7 memories, all non-volatile. Wallet size. 1,300 hour battery. Usual Price £22.95

Price elsewhere

★ £21.95

### FX-180P. Hand held version without hyperbolics

£19.95

### FX-8100 Scientific with Clock, Alarms and Stopwatch

8 digits, 49 scientific functions. Clock, hourly chimes, alarm.

2 countdown alarm timers. Auto calendar. 1/100 second pro stopwatch. Complete with wallet. Usual Price £19.95

Price elsewhere £23.95 ★

### FX-550

10 digits, 50 scientific functions including hyperbolics, standard deviations, etc. Wallet 2 1/2 x 5 1/2". Wallet. 1,300 hour lithium battery life.

Usual Price £19.95

Price elsewhere ★ £18.95

FX-5 £8.95. FX-7 £10.95. FX-82 £12.95.

FX-100 £16.95.

## CALCULATING ALARM CLOCKS

### FT-7 Fortune Teller and Matchmaker



Clock, alarm, hourly chimes, calendar. Predictions of individual fortunes (health, gambling/investment, business and love), or the compatibility between two persons on any given day. Usual Price £16.95.

Price elsewhere ★ £15.95

**BG-15.** Boxing game, alarm clock, calculator. Usual Price £16.95. Price elsewhere £15.95

ML-75. 12 melody alarms, clock, calculator. £14.95

ML-120. Wallet version of above. £14.95

ML-2000 £22.95. UC-3000 £27.95. UC-300/365 £19.95

## BASIC CALCULATORS

### MG-777 Compendium of Games

A game of chance, a game to test your reactions and a game to tax your intelligence. Plus a very useful clock as well and, of course, a wallet sized calculator.

ONLY £14.95

SL-801 Solar £8.95. HQ-25 Time calculations £9.95.




CATALOGUE ON REQUEST. 15½p STAMP APPRECIATED

## SENSATION

of the Japanese Music Fair
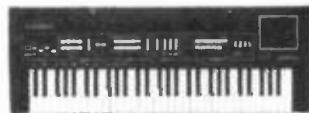
### CASIOTONE 701 COMPUTERISED ORGAN

Fully Programmable, 5 Octave, Polyphonic Keyboard "THE instrument of 1982... probably the best instructive keyboard I have come across. But it is also a top line musical instrument capable of satisfying even the most proficient musician" Keyboards & Music Player.



CT-701 (RRP £555) ONLY £495

Program the 345 melody steps and the 201 chord steps, (max.) with music specially scored in bar code and read by a light pen, or enter your own chords and melody via the keyboard, with full editing and repeat facilities.


3-way replay:—Automatic; One Key Play; Melody Guide. (lights above the keyboard indicate the next note to play). Split keyboard; 20 superb instrument voices; 16 rhythm accompaniments; fingered or auto chords with walking bass and arpeggio; fill-in and effect buttons. 37 1/2 x 13 1/4 x 5". Weight: 12.5kg (27.6lbs).

CT-601. As 701 but without programming functions £395

### COMMON SPECIFICATIONS

All Casiotones (except VL-Tones) are 8-note polyphonic. They all have built-in amplifiers and speakers, with output jacks for headphones and external amplification and a pitch control. CT models are mains only and have volume and sustain pedal jacks.

### CT-403

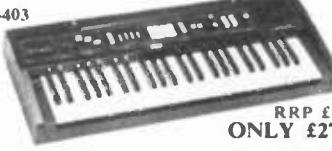

RRP £325.00  
ONLY £275.00

25 instruments over 4 octaves. Four voice memory function with push button selection. Vibrato and sustain switches. 16 rhythm accompaniments with fill-in variation Casio Auto Chord for one finger or auto playing of major, minor and 7th chords with bass. Ten functional controls 4 1/2 x 30 1/2 x 11 1/2. Weight 17.6lbs.

### CT-202



RRP £325  
ONLY £275

"Son of success... The two harpsichords demonstrate the Casiotone's talent for sparkling, crystal clear tones... Even more impressive is the clav..." (Melody Maker).

49 instruments over 4 octaves. 4 voice memory function with push button selection, 3 vibrato settings and sustain 3 1/2 x 34 1/2 x 11 1/2. 16.8lbs.

### CT-101. Similar to 202 but has 25 voices.

ONLY £195

### MT-40



RRP £125

ONLY £99

37 key, 3 octave keyboard plus 15 key bass keyboard with automatic, synchronised bass function. 22 instrument voices; 6 auto rhythms with dual fill-in. Sustain and Vibrato. Battery powered, or optional mains adaptor AD-1E (£5). 23 x 7 x 2 1/2". Weight 4.9lb. VL-TONE. Become an Instant Musician with this amazing programmable Musical Instrument. 10 auto rhythms, five voices + ADSR. 2 extra books worth £5.90 FREE.

£35.95

## CATALOGUE ON REQUEST

15½p stamp appreciated

## LIMITED OFFER!

As an introduction to CRICKLEWOOD ELECTRONICS LTD., (Marshall's Old Shop), 40 Cricklewood Broadway, London NW2 JET tel: 01 452 0161 Whilst stocks last and only if accompanied by this Ad.

### DESOLDERING TOOL



Now every one can afford one of these superb, anodised aluminium high pressure hand desoldering tools at nearly half our normal price. Normal Price £6.50 + VAT with this ad £3.85 + VAT. Spare Teflon screw-in noses 75p + VAT.

**JAPANESE TRANSISTORS** May not be as hard to replace as you think. Phone our equivalent service on 01 452 0161 (everyday except Wednesdays) or write. We have thousands of Transistors, ICs, LEDs in stock, as well as every conceivable type of component—Why not make CRICKLEWOOD ELECTRONICS your personal ELECTRONICS HOBBY CENTRE? We have the goods!

Now you need no longer grope in the dark. For a miniature price you can watch those volts move! See those resistors jump to life!



**THE MIGHTY MINI MULTITESTER** 2,000 ohms per volt. DC & AC Voltage ranges: 10V, 50V, 250V, 1000V. DC current ranges 100mA. Resistance ohms x 10, ohms x 100db from -10db to +22db. Mirror arc scale, overload protected, complete with battery, test leads & instructions. Usual price £8.65 + VAT; with this Ad: £4.95 + VAT.

### ORDER FORM

Name .....

Address .....

Desoldering tools @ £3.85 = £.....  
Spare Teflon noses @ .75 = £.....  
Mighty Mini Testers @ £4.95 = £.....

Postage, packing and Insurance @ 60p per one device 25p for each additional device £.....

Sub total £.....  
Add 15% VAT £.....

I enclose cheque no/P.O. no. ....

Alternatively please credit my VISA/ACCESS no. ....

Signature .....

This offer applies to UK only. Please allow 7-10 days delivery. Overseas customers please do not add VAT but allow enough to cover postage.

TRADE ENQUIRIES WELCOME.


**CRICKLEWOOD ELECTRONICS LTD.**

40 Cricklewood Broadway, London NW2 JET tel 01 452 0161

# THE MEKON IS BACK



## Make the connection with Access

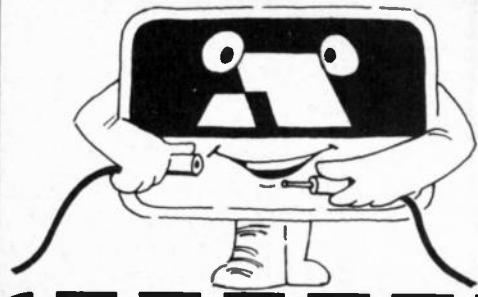

and receive a regular postal delivery of Everyday Electronics. It's easy, it's straightforward and it's quick. Just use the subscription order form to get your Access card account charged with the price of a subscription or order your subscription through Access on the phone: (01) 886 6433. If you pay by cheque or postal order, use the subscription order form in the usual way.

### SUBSCRIPTION ORDER FORM

I wish to become a subscriber to **Everyday Electronics** for one year and enclose cheque/postal order value..... no..... made payable to IPC Magazines Ltd.

Complete this portion if you are using your Access card account. I authorise you to debit my Access card account with the above amount.

My Access no. is

(Block letters please)

Name.....

Address.....

Signature.....

### Subscription Rates:

UK, Isle of Man, Channel Islands and Irish Republic £11

Overseas £12

Unless you are phoning your order, complete and post this order form to:

**Everyday Electronics,**  
2613 King's Reach Tower,  
Stamford Street,  
London SE1 9LS.



# BENNING CROSS ELECTRONICS

67 Vicarage Road, Watford, Herts  
Telephone WATFORD (0923) 36234



All prices subject to VAT at 15% extra  
Export orders welcome  
All deliveries within 7 days.

All devices brand new, full spec. and fully guaranteed. Orders despatched by return of post. Terms of business. PO Cheque/Cash or Bankers Draft with order. Government and educational institutions official orders accepted. Trade and export enquiries welcome. P&P add 50p to all orders under £9 nett. Overseas orders postage at cost.

Polyester capacitors radial lead type—250v

10N, 15N, 22N, 27N 6p; 33N, 47N, 100N 7p; 150N, 220N, 10p; 330N, 470N 14p; 680N, 1uF, 20p; 1.5MF, 2.2uF, 43p.

Tantalum bead capacitors 35V;

0.1uF, 0.22, 0.33, 15p; 0.47, 0.68, 0.1, 1.5, 16p; 2.2, 3, 18p;

4.7, 6, 8, 22p; 10, 28p; 18V, 15N, 22N, 33N, 47N, 100NF, 150NF,

220NF, 8p.

Ceramic capacitors 50V

range 1PF to 10NF 4p;

15N, 22N, 33N, 47N, 100NF, 150NF,

220NF, 8p.

ZENERS

Range, 2V7 to 39V

400mW 7p each.

Range, 3V3 to 33V.

1.3W 14p each

Polypropylene capacitors: 10PF to

100PF, 1.5pF to 12NF 12p.

Minature type trimmers: 2.6PF,

2-10PF, 24p. 10-88PF 34p. 2-25 34p.

Transformers: 606.

Dale Etch

Resin Pln 85

VEROBOARDS S.O. 1"

Clad Plain

1lb bag Anhydrous 19p

COPPER CLAD BOARDS

Fibre Single-

Glass Double-

sided

8p 9p

12p 13p

18p 19p

24p 25p

30p 31p

36p 37p

42p 43p

48p 49p

54p 55p

60p 61p

66p 67p

72p 73p

78p 79p

84p 85p

90p 91p

96p 97p

102p 103p

108p 109p

114p 115p

120p 121p

126p 127p

132p 133p

138p 139p

144p 145p

150p 151p

156p 157p

162p 163p

168p 169p

174p 175p

180p 181p

186p 187p

192p 193p

198p 199p

204p 205p

210p 211p

216p 217p

222p 223p

228p 229p

234p 235p

240p 241p

246p 247p

252p 253p

258p 259p

264p 265p

270p 271p

276p 277p

282p 283p

288p 289p

294p 295p

296p 297p

298p 299p

304p 305p

310p 311p

316p 317p

322p 323p

328p 329p

334p 335p

340p 341p

346p 347p

352p 353p

358p 359p

364p 365p

370p 371p

376p 377p

382p 383p

388p 389p

394p 395p

396p 397p

398p 399p

404p 405p

410p 411p

416p 417p

422p 423p

428p 429p

434p 435p

440p 441p

446p 447p

452p 453p

458p 459p

464p 465p

470p 471p

476p 477p

482p 483p

488p 489p

494p 495p

496p 497p

502p 503p

508p 509p

514p 515p

520p 521p

526p 527p

532p 533p

538p 539p

544p 545p

550p 551p

556p 557p

562p 563p

568p 569p

574p 575p

580p 581p

586p 587p

592p 593p

598p 599p

604p 605p

610p 611p

616p 617p

622p 623p

628p 629p

634p 635p

640p 641p

646p 647p

652p 653p

658p 659p

664p 665p

670p 671p

676p 677p

682p 683p

688p 689p

694p 695p

698p 699p

704p 705p

710p 711p

716p 717p

722p 723p

728p 729p

734p 735p

740p 741p

746p 747p

752p 753p

758p 759p

764p 765p

770p 771p

776p 777p

782p 783p

788p 789p

794p 795p

798p 799p

804p 805p

808p 809p

814p 815p

818p 819p

824p 825p

828p 829p

834p 835p

840p 841p

846p 847p

852p 853p

858p 859p

864p 865p

868p 869p

874p 875p

878p 879p

884p 885p

888p 889p

894p 895p

898p 899p

904p 905p

910p 911p

916p 917p

922p 923p

928p 929p

934p 935p

938p 939p

944p 945p

950p 951p

956p 957p

962p 963p

968p 969p

974p 975p

980p 981p

986p 987p

992p 993p

998p 999p

1004p 1005p

1010p 1011p

1016p 1017p

1022p 1023p

1028p 1029p

1034p 1035p

1040p 1041p

1046p 1047p

1052p 1053p

1058p 1059p

1064p 1065p

1070p 1071p

1076p 1077p

1082p 1083p

1088p 1089p

1094p 1095p

1098p 1099p

1104p 1105p

1110p 1111p

1116p 1117p

1118p 1119p

1124p 1125p

1129p 1130p

1134p 1135p

1138p 1139p

1144p 1145p

1148p 1149p

1154p 1155p

1158p 1159p

1164p 1165p

1170p 1171p

1176p 1177p

1182p 1183p

1188p 1189p

1194p 1195p

1198p 1199p

1204p 1205p

1210p 1211p

1216p 1217p

1222p 1223p

1228p 1229p

1234p 1235p

1238p 1239p

1244p 1245p

1250p 1251p

1256p 1257p

1262p 1263p

1268p 1269p

1274p 1275p

1278p 1279p

1284p 1285p

1290p 1291p

1296p 1297p

# ELECTRONIC IGNITION

Makes a good car  
better



**TOTAL ENERGY DISCHARGE** electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** — higher output voltage under all conditions.

**IMPROVED ECONOMY** — no loss of ignition performance between services.

**FIRESDULDED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

## PLUS

**SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** — full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

## IN KIT FORM

It provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

## AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 issue and EVERYDAY ELECTRONICS December '81 issue

**FITS ALL NEGATIVE EARTH VEHICLES,**  
6 or 12 volt, with or without ballast

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS**  
Some older current impulse types (Smiths pre '74) require an adaptor —  
PRICE £2.95

**STANDARD CAR KIT** £14.85  
**Assembled and Tested** £24.95

**TWIN OUTPUT KIT** £22.95  
For MOTOR CYCLES and CARS with twin ignition systems  
**Assembled and Tested** £34.70

**ELECTRONIZE DESIGN**  
Goods normally despatched within 7 days


Dept. C, Magnus Road, Wilnecote

Tamworth, B77 5BY

Phone (0827) 281000

PLUS  
£1.00  
U.K.  
P. & P.  
Prices  
Include  
VAT.

As seen on television's Tomorrows World

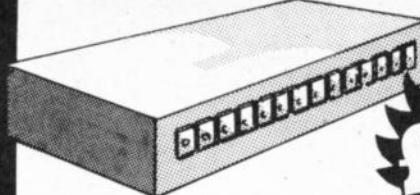

**£98.00**  
Plus p & p £2.00

## The Black Box

home electronics control centre

Utilizing digital circuit techniques, the Black Box centralises the operation of all electrics in your home. This initial unit controls lighting and also provides an effective security alarm system to protect your home against intruders. Additions to the Black Box, offered in the next few months, will provide an infra-red remote control pack, followed by a further facility for controlling the function of switch-on appliances, together with pre-determined time selector controls. The Black Box provides absolute flexibility in command of the electrics in your home, all from the comfort of your armchair. Place your order today, or write for further details.

### Black Box Specification

- Safe, low power control switching, 9v @ 1mA
- No need for dual control switching
- Zero voltage switching increases bulb life
- Two Dimmers
- Visible Bell/Intruder Alarm
- Master on/off Control
- Timer Control
- Eight on/off controls

### ARA Electronics

Burrel Road, Industrial Estate, St. Ives, Cambs  
Telephone: (0480) 65868

## NAMAL ELECTRONICS

No. 1 Claygate Road, Cambridge CB1 4JZ

Tel: 0223 248257 Telex: 817445

MEMORY EXPANSION PACKS AT  
UNBEATABLE PRICES !

<b>3K.</b>	FOR VIC 20	£21.30
<b>8K.</b>	FOR VIC 20 (expandable to 16K)	£35.00
<b>16K.</b>	FOR SINCLAIR ZX 81	£30.00

Please add £1.00 P & P, plus V.A.T.

If you find an ad  
unacceptable,  
don't turn the page:  
turn to us. ✓

The Advertising Standards Authority.  
If an advertisement is wrong, we're here to put it right.  
A.S.A. Ltd, Brook House, Tonbridge Place, London WC1E 7HN.

# LOCK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire.

Self-assembly simulated wood cabinet.

£4.50 + £1.50 p+p.


INTRODUCTORY OFFER - ONLY

**£32.95**

+ £2.75 p+p.

Featured in April issue Practical Electronics, reprint 50p - Free with Kit.

## STEREO AMPLIFIER KIT

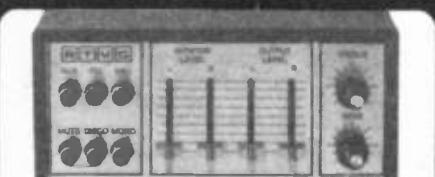

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/4" x 3" (approx).

• 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with kit.

**£16.50**

+ £2.90 p+p.

SPECIFICATIONS: Suitable for 4 to 8 ohm speakers  
Frequency response 40Hz - 20KHz  
Input sensitivity 0.1mV.  
Tone controls Bass ±12db @ 60Hz  
Distortion 0.1% typically @ 8 watts  
Mains supply 220 - 250 volts 50Hz.

8" SPEAKER KIT Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p+p. when purchased with amplifier. Available separately £6.75 & £1.70 p+p.

## PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II



2 WAVE BAND, MW - LW

- Easy to build. • 5 push button tuning. • Modern design. • 6 watt output. • Ready etched and punched PCB. • Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1183 ceramic filter type re-aligned and assembled, and a Bird pre-aligned push button tuning unit. Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.) available as a complete kit. £2.50/pack + £1.50 p+p.

**£12.95**

+ £2.00 p+p.

## BIRD AUDIO STEREO CAR RADIO BOOSTER

To boost your car radio or radio cassette to 15W r.m.s. per channel.

**£9.95**

+ £1.50 p+p.



## P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP
- TAPE COUNTER
- SWITCHABLE E.Q.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

## 125W HIGH POWER AMP MODULE

KIT: **£10.50** BUILT: **£14.25**  
+ £1.15 p+p.

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result in a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Suitable mains power supply kit with transformer: £7.50 plus £1.15 p+p. Suitable LS coupling electrolytic: £1.00 plus 25p p+p.




### SPECIFICATIONS:

Max. output power (RMS): 125W  
Operating voltage (DC): 50 - 80 max.  
Loads: 4 - 16 ohms.  
Frequency response measured @ 100 watts: 25Hz - 20KHz.  
Sensitivity for 100 watts: 400mV @ 47K.  
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.  
Dimensions: 205 x 90 and 190 x 36 mm.
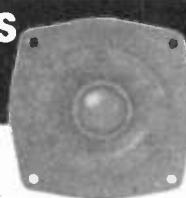
## HI-FI SPEAKERS AT BARGAIN PRICES

GOODMAN'S TWEETERS  
8 ohm soft dome radiator tweeter (3 1/2" sq.) for use in up to 40W systems, with 2 element crossover.  
**£3.50 each (p+p £1) or £5.95 pair (p+p £2).**



## P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale, Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

**£17.95**

Plus £2.50 p+p.

## TV SOUND TUNER KIT

**£11.45**

+ £1.50 p+p.

As featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case.

• Transformer £1.50 + £1.50 p+p (p+p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation. £1.95 + 75p p+p.

## 35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4" app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIFIJSM. Complete with 2 element crossover. Total impedance of system 4 ohms.

**£7.95**

PER SET + £2.70 p+p.



### SPECIAL OFFER! TUNER KIT PLUS:

• Matching I.C. 10 watt per channel Power amp kit. • Mullard LP1183 built pre-amp, suitable for ceramic pick-up and aux. inputs. • Matching power supply kit with transformer. • Matching set of 4 slider controls for bass, treble and volumes. + £21.95

controls for bass, treble and volumes. + £3.80 p+p.

## MONO MIXER AMP

**£39.95**

+ £3.70 p+p.

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.). two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux inputs. Size: 13 1/2" x 6 1/2" x 3 1/2". Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.



### ALL MAIL TO:

21A HIGH STREET, ACTON, W3 6NG.

Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope. All items subject to availability. Prices correct at 31/1/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch.

ALL PRICES INCLUDE VAT AT 15%.

ALL CALLERS TO: 323 Edgware Rd, London W2. Telephone: 01-723 8432.

Open 9.30 - 5.30pm. Closed all day Thursday. RTVC Limited reserve the right to update their products without notice.





## Personal

**CHRISTIAN SINGLES.** Holidays, tours, weekend houseparties. Friendship contacts —CFF Dept/N42, Edenthorpe, Doncaster.

## Wanted

**WANTED,** Teach in kits, basic tools, equipment. PRICE, 15 Colbourne Road, Tipton, West Midlands DY4 8RU.

## For Sale

**HEATHKIT SELF INSTRUCTION PROGRAMMES** plus trainer as new. £150. Reigate 47304 evenings.

**NEW BACK ISSUES OF "EVERYDAY ELECTRONICS".** Available 85p each Post Free, cheque or uncrossed PO returned if not in stock. **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

## Miscellaneous

**LEARN ELECTRONICS WITHOUT SOLDER**

Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec. Send cheque or P.O. to: Roden Products, Dept EE, High March, Daventry, Northants, NN11 4OE.

**£3.85** plus 40p p&p each

## EVERYDAY ELECTRONICS P.C.B's Drilled 1.5mm Glassfibre Fry's Roller Tinned

SEP 81	Model train control £1.50
	CMOS dice £1.13
NOV 81	Electronic ignition £1.00
APR 82	2K RAM for ZX81 £1.00
For full list and current PCB's send SAE. CWO Please. Postage. Add 35p postage and packing.	
PROTO DESIGN, 14 DOWNHAM RD., RAMSDEN HEATH, BILLERICAY, ESSEX, CM11 1PU Telephone 0268-710722	

**CENTURION BURGLAR ALARM** equipment, send SAE for free list or a cheque/PO for £11.50 for our special offer of a full sized signwritten bell cover to: Centurion, Dept EE, 265 Wakefield Road, Huddersfield, W. Yorkshire. Access & Barclaycard. Telephone orders on 0484 35527.

**ENAMELLED COPPER WIRE.** 10 swg to 45 swg. S.A.E. for quotation by return, cheapest prices. 102 Parrswood Road, Manchester 20.

**LEARN ELECTRONICS** at home. Experiment kit covers audio, radio, digital, optoelectronics, timers. Instruction book with full circuits for forty projects, component layouts, and theory section. Sixty parts supplied, including transistors, LEDs, earphone, loudspeaker, ferrite-rod, reed-switches etc. No soldering, components can be re-used many times. Uses two 3-volt batteries (not supplied). Send cheque/PO for £25 (includes UK P&P and VAT) to VYTRON (EE-04), 5 Mariners Drive, Portishead, Bristol BS20 8ET.

**PARAPHYSICS JOURNAL** (Russian translations): psychotronic generators, Kirlianography, gravity lasers, telekinesis. Details: SAE 4 x 9in, Paralab, Downton, Wilts.

**SPARE PARTS FOR ALL DIGITAL WATCHES.** Batteries 65p; pins; display; back lights etc. Plus reports, publications charts, send SAE for full list. PROFORDS, Copners Drive, Holmer Green, Bucks HP15 6SG.

## DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries —you fit them. Begin now. Send £9 for complete kit and get into a fast growing business. Prompt despatch.

**BOLSTER INSTRUMENT CO. (EE36)**  
11 Percy Avenue, Ashford, Middx., TW15 2PB

**CORDLESS TELEPHONES**, make your own inexpensive units. Send £3.00 for simple easy to follow plans to J. F. ASHLEY, Birley Grange, Cottage Farm, Baslow Road, Cuthorpe, Derbyshire.

## THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4. 01 531 1568

### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.30	1.90	1.00	0.80
35 to 39	3.52	2.10	1.15	0.85
40 to 43	4.87	2.65	2.05	1.46
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

### SILVER PLATED COPPER WIRE

14 to 30	8.63	3.86	2.28	1.50
14 to 30	3.97	2.41	1.39	0.94

### TINNED COPPER WIRE

10 x 10 mtr reels 3 amp PVC cable mixed colours 5.00 Prices include P & P vat. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

## INDEX TO ADVERTISERS

Absonglen .. . . .	278	Global Specialist .. . . .	271	Radio Component Specialists .. . . .	288
Alcon .. . . .	280	Greenweld .. . . .	220	Radionic .. . . .	222
ARA Electronics .. . . .	284	Home Radio .. . . .	280	Radio TV Components .. . . .	285
Benningcross .. . . .	283	Intertext (ICS) .. . . .	220	Rapid Electronics .. . . .	221
Bi-Pak .. . . .	225	Litesold .. . . .	280	Science of Cambridge .. . . .	276-277
BK Electronics .. . . .	Cover III	Magenta Electronics .. . . .	222-223	Selray Book .. . . .	224
B.N.R.E.S. .. . . .	275	Maplin Electronics Supplies Ltd. .. . . .	Cover iv	Silica Shop .. . . .	Cover ii
Bull, J. .. . . .	279	Namel Electronics .. . . .	284	Tempus .. . . .	281
Chordgate .. . . .	288	NME .. . . .	224	Titan Transformers .. . . .	280
Cricklewood Electronics .. . . .	282	Phonosonic .. . . .	218	T.K. Electronics .. . . .	218
Dziubas, M. .. . . .	220	Powell, T. .. . . .	278	Vero Electronics .. . . .	283
E.D.A. .. . . .	226	Watford Electronics .. . . .	219	West London Direct Supplies .. . . .	288
Electronize Design .. . . .	284	Wilmslow Audio .. . . .	218		
Electrovalue.. . . .	278				
Enfield Electronics .. . . .	224				

# MIGHTY NINETY PACKS

**SUPER VALUE PACKS ALL AT 90p each  
BUY SIX PACKS AND GET A SEVENTH  
FREE**

Please add 15p per pack postage  
Please allow 7 days delivery.

MN1. 200 1 & 1-watt Resistors.	MN37. 10 assd audio connectors. Din phono etc.
MN3. 100 1 & 2-watt Resistors.	MN38. 1 PCB with triac control IC data Inc.
MN4. 50 Wirewound Resistors.	MN39. 1 oscillator PCB loads of components (no data).
MN5. 100 metal oxide Resistors. 1%, 2% and 5%.	MN40. 50 Polystyrene capacitors.
MN6. 12 assd potentiometers.	MN41. 12 BC54C (plastic BC109C) transistors.
MN7. 25 assd skeleton preset Resistors.	MN42. 10 BC107 Transistors.
MN8. 50 assd Electrolytic Capacitors.	MN43. 10 BC108 Transistors.
MN9. 100 assd Ceramic Capacitors Pile, disc, tub and monolithic etc.	MN44. 10 Screwfix S.P.C.O. min. slide switches.
MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.	MN45. 35 assd diodes Zener, rect., signal, switch-in.
MN11. 20 assd Silver Mica Capacitors.	MN46. 15 assd Zener diodes.
MN12. 8 Tantalum Bead Capacitors (optional values).	MN47. 3 x 68 mfd 16v tantalum bead capacitors.
MN13. 20 assd Transistors. BC, 2N Series + Power etc.	MN48. 200 items 4BA assd-length screws, nuts & washers.
MN14. 40 IN4148 Diodes.	MN49. 200 items 6BA assd-length screws nuts & washers.
MN15. 20 min. wire-ended Neons.	MN50. 3 pieces of veroboard useful sizes, min total 35 sq inch.
MN17. 2 12-volt Relays. Ex nearly new equip.	MN51. 10 x 0 2" red LED.
MN18. 3 Encapsulated Reed Relays 9-12v coil, d-pole and i-pole.	MN52. 10 x 0 125" red LED.
MN19. 2 24-volt Relays. Ex nearly new equip.	MN53. 20 x 0 1 mid 25 ceramic disc caps.
MN20. 1 240-110 to 12-volt. 100ma Transformer.	MN55. 10 watt audio amp board with circuit.
MN21. 1 240-110 to 24-volt 100ma Transformer.	MN56. 10 14 pin low profile IC skit DIL.
MN22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green.	MN57. 10 16 pin low profile IC skit DIL.
MN23. 300 assd screws, nuts, washers, self-tappers etc.	MN58. 2 x CA723 Voltage Regulator.
MN24. 100 assd small springs.	MN59. 1 x LM380 2 watt audio amp IC + 555 timer IC.
MN25. 50 assd pop rivets.	MN60. 10 assd TTL IC's.
MN26. 50 assd insulated crimp.	MN61. 3 x TIP 32 Transistor.
MN27. 200 items, grommets, soakers, cable markers, plastic screws, sleeving, tie wraps etc.	MN62. 3 x TIP 31 Transistor.
MN28. 20 assd fuses. 1/2" 20mm etc.	MN63. 50 mixed polyester caps C280, Siemens etc.
MN29. 75mts equipment, wire, assd colours and sizes.	MN64. 5 Press to make min switches.
MN30. 3 x 2m length, 3 core, mains cable.	MN65. 3 BF245 FETs.
MN31. 12 assd trimmer capacitors, compression film, Air-spaced etc.	MN66. Bank of 11 push switches 4 interlocked, 4 latch, 3 momentary.
MN32. 15 30pF Beehive trimmers.	MN68. 200 assd veropins, turret tags, PCB pins etc.
MN33. 20 coil formers, ceramic, plastic, reed relay etc.	MN69. 4 min push to break switch.
MN34. 25 min glass reed switch.	MN70. PCB with 3 x 250V AC 4 amp push SW with attractive chrome plastic knobs 1 x BD241, 1 x BC300, 2 x BC237, 1 x BC204, 4 x IN4002, 2 x CMOS 4025, 200mm fuse holder + 22 resistors, capacitors, diodes etc.
MN35. 10 assd switches, toggle, slide, micro etc.	MN71. IZN414 RADIO IC.

# CHORDGATE LIMITED

75 FARINGDON ROAD  
SWINDON, WILTS. Tel. (0793) 33877  
Retail shop at above address

## MAINS INTERCOM



NO BATTERIES NO WIRES ONLY £29.95

PER PAIR  
+ VAT £4.50  
+ P & P £1.95

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1/2-mile on the same mains phase. On/off switch. Volume control, with 'buzzer' call and light indicator. Useful as inter-office intercom between office and warehouse, in surgery and in homes. Also available F.M. mode!

## NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£18.95  
+ VAT £2.85  
+ P & P £1.65

Latest transistorised Telephone Amplifier, with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control. Conversation recording, model at £20.95 + VAT £3.15. P&P £1.65.

## DOOR ENTRY SYSTEM

No house / business / surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged, and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock); mains power unit, cable (4 pairs) 50ft and wiring diagram. Price £29.95 + VAT £9.00 + P&P £2.58. Kit with two phones £69.95 + VAT £10.50 + P&P £2.81.

**PLEASE ALLOW 8-12 DAYS FOR DELIVERY**  
10-day price refund guarantee on all items  
Access and Barclaycard welcome.

**WEST LONDON DIRECT SUPPLIES EE 4**  
169 KENSINGTON HIGH STREET.  
LONDON, W8 Tel: 01-937 5548

PLEASE  
MENTION

EVERYDAY  
ELECTRONICS

WHEN REPLYING  
TO  
ADVERTISEMENTS

## BAKER 50 WATT AMPLIFIER

£69

Post S2



Superior quality ideal for Hi-Fi/PA systems. Double and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm.

AC 240V (120V available). Blue wording on black cabinet.

**BAKER 150 Watt AMPLIFIER 4 Inputs £89**

DRILL SPEED CONTROLLER LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. £3 DELUXE MODEL Ready Built. 800 watts. £5

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high, medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £3.95

## SOUND TO LIGHT CONTROL KIT MK II

Complete kit of parts, printed circuit. Main transformer. 3 channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi. £18. 200W Watt Recessed White Light Bulbs. Cabinet extra £4.00. Post 95p. 200 Watt Recessed White Light Bulbs. Cabinet extra £4.00. Post 95p. Edison Screw 75p each or 6 for £4 or 12 for £7.50.

**MAINS TRANSFORMERS Primary 240V A.C. POST 250-0-250V 70mA. 6-6V 2A. £4.00**  
**250-0-250V 80mA. 6-3V 3.5A. 6-9V 1A. £5.00**  
**350-0-350V 250mA. 6-3V 6Amp C.T. £12.00**  
**300-0-300V 120mA. 2-6V 2A C.T. 5V 2A. £13.00**  
**220V 45mA. 6-3V 2A. £2.50**

## GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available

2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V ... £8.00 £2

1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11.50 £2

3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50 £2

5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £16.00 £2

5.5-10-16V 1/2 ... £2.50 80p 12-0-12V 2a ... £2.50 £1

6V 1/2 ... £2.00 £1 15-0-15V 2a ... £3.75 £1

6-6.5V 1/2 ... £3.50 £1 20V 1a ... £3.00 £1

9V 250mA ... £1.50 80p 20V 2a ... £3.50 £1

9V 3a ... £3.50 £1 20-20V 1a ... £3.50 £1

9-9.5V 50mA ... £1.50 80p 20-40-60V 1a ... £4.00 £2

10-10V 2a ... £3.00 £1 25-0-25V 2a ... £4.50 £1

10-20-40V 2a ... £3.50 £1 28V 1a Twice ... £5.00 £2

12V 100mA ... £1.50 80p 30V 1a ... £3.50 £1

12V 750mA ... £2.00 80p 30V 5a and ... £2.50 £1

12V 3a ... £3.50 £1 17-0-17V 2a ... £5.00 £2

12V 2a ... £3.50 £1 35V 2a ... £4.00 £1

**TOROIDAL 30-0-30V 4 Amp +20-0-20V 4 Amp £10.00**

**CHARGE TRANSFORMERS-RECTIFIERS**

6-12V 3a ... £4.00 £2 6-12V 2a ... £1.00 80p

6-12V 2a ... £6.50 £2 6-12V 4a ... £8.00 80p

## R.C.S. LOUDSPEAKER BARGAINS

3 ohm, 6 x 4in. 5in. 7 x 4in. 6.5-50, 8 x 5in. 32-00. 6in. 33-00. 8in. 33-50. 10in. 34-00. 12in. 36-00. 8ohm, 2in. 32-30. 3in. 5 x 3in. 5in. 33-50. 8in. 33-50. 16ohm, 6 x 4in. 5in. 32-50. 8in. 32-50. 10 x 6in. 34-00. 25ohm, 3in. 34in. 30in. 32-50. Many others in stock.

## R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA POST 75p £3.95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240a. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.

## PP BATTERY ELIMINATOR. BRITISH MADE £4.50

Main power pack 9 volt 400 ma Post 75p stabilised, with overload cutout. Plastic case size 3 x 3 x 2.5. Suitable Radio/Cassettes.

DELUXE SWITCHED Model 3-6-7-9V 400 ma £7.50.

## THF "INSTANT" BULK TAPE ERASER

Suitable for cassettes and all sizes of tape reels.

A.C. mains 200/240V. £9.50 Post 85p Leaflet S.A.E.

## HEAD DEMAGNETISER PROBE £5.00

A.C. ELECTRIC MOTORS POST 75p.

2 Pole, 240V, 0.2 Amp. Spindle-1.43 x 0-212in. 2 Pole, 240V, 0.15 Amp. Double spindle-1.75 x 0-16in. Each 1.2 Pole, 120V, -5 Amp. Spindle-0.75-0.2in. Two in series - 240V, 50p each. Brush Motor. From a Food Mixer 240V. -3 Amp High Speed and Powerful Spindle-0.5-0.25in. 2.5in. B.R. Motor £4. Garrard Motor £5.

## ALUMINIUM CHASSIS 18 s.w.g. Underlined, 4 sides, riveted corners: 6 x 4 x 2in. £1.45; 8 x 6 x 2in. £1.80; 10 x 7 x 2in. £2.30; 12 x 9 x 2in. £3.00; 16 x 6 x 2in. £2.90; 12 x 3 x 2in. £1.80; 12 x 8 x 2in. £2.60; 16 x 10 x 2in. £3.20.

## ALU ANGLE BRACKET 6 x 1 x 1 in. 25p.

## ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.50; 14 x 9in. £1.45; 6 x 4in. 45p; 12 x 8in. £1.10; 10 x 7in. 95p; 8 x 6in. 72p; 12 x 6in. 72p; 16 x 10in. £1.65; 16 x 6in. £1.10; ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.

6 x 2 x 2in. £1.00; 3 x 2 x 1in. 80p; 6 x 4 x 2in. £1.60; 8 x 6 x 2in. £2.50; 12 x 3 x 2in. £2.75; 6 x 4 x 3in. £1.80; 10 x 7 x 3in. £2.20.

## HIGH VOLTAGE ELECTROLYTIC 32-32/320V £5.00

8/800V ... £1.20 50/500V ... £1.20 32-32/320V £1.20

32/360V ... £1.50 220/450V ... 95p 32-32/32/320V £1.20

32/500V ... £1.80 8/16/450V ... 75p 16-32-32/32/320V £1.20

## DE LUXE BSR HI-FI AUTOCHANGER

Stereo Ceramic Cartridge

Play 12in., 10in. or 7in. records Auto or Manual. A high quality unit 240V AC.

Size 13 1/2 x 11 1/2in.

Above motor board 3in. Below motor board 2in.

BSR Single Player P204 cueing device, ADC. QLM 30/3 Magnetic cartridge.

Garrard Single Player 730 BP metal turntable, cueing device, Snake arm, Magnetic cartridge. £27.50 post £2

BSR P170 Single Player. Slim arm, Ceramic cartridge, Cueing device, Auto stop. £20 post £2

B.B.R. P232. Belt drive, ceramic cartridge, snake arm, cueing device. £24 post £2

B.B.R. Single Player. 12V D.C. motor, belt drive, magnetic cartridge. £20. post £2

## Radio Component Specialists

337, WHITEHORSE ROAD, CROYDON, SURREY, U.K. TEL: 01-684 1665

Post 65p Minimum. Callers Welcome. Closed Wed. Same day despatch. Access-Barclay-Visa. Lists 3p.




APPROVED  
thandar  
STOCKIST

# B.K. ELECTRONICS
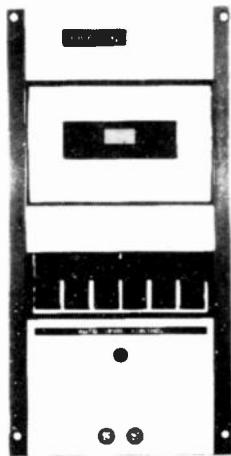
## A SOUND CHOICE

APPROVED  
thandar  
STOCKIST

★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS  
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



### STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter Auto stop Six piano type keys record, rewind fast forward, play, stop and eject Automatic record level control Main inputs plus secondary inputs for stereo microphones **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K **Output level:** 400mV to both left and right hand channels **Output Impedance:** 10K **Signal to noise ratio:** 45dB **Wow and flutter:** 0.1% **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5½in x 11½in. Clearance required under top panel 2½in. Supplied complete with circuit diagram and connecting diagram Attractive black and silver finish

**Price £26.70 + £2.50 postage and packing**  
Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.

**NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").** These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15 units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price -


**15"** 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz Frequency Response to 2.5KHz Sensitivity 97dB Price £32 each. f2 50 Packing and Carriage each

**12"** 100 watt R.M.S. Impedance 8 ohm, 50 oz. magnet, 2" aluminium voice coil. Resonant Frequency 25Hz Frequency Response to 4KHz Sensitivity 95dB Price £23.70 each. f2 50 Packing and Carriage each

**8"** 50 watt R.M.S. Impedance 8 ohm, 20 oz magnet 1" aluminium voice coil. Resonant Frequency 40Hz Frequency Response to 6KHz Sensitivity 92dB Also available with black cone and black protective grill Price £8.90 each f1 25 Packing and Carriage each
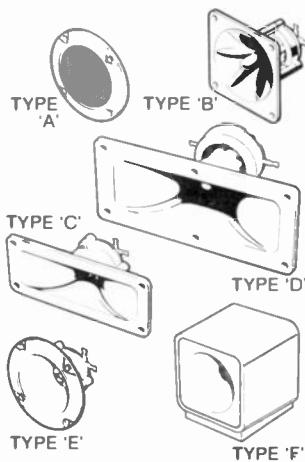
### PIEZOELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



**TYPE 'A'** (KSN1038A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £3.45 each.

**TYPE 'B'** (KSN1005A) 3½" super horn. For general purpose speakers, disco and P.A. systems, etc. Price £4.35 each.

**TYPE 'C'** (KSN6016A) 2" - 5" wide dispersion horn. For Hi-Fi systems and quality discs, etc. Price £5.95 each.

**TYPE 'D'** (KSN1025A) 2" - 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2,000 c/s). Suitable for Hi-Fi systems and quality discs. Price £6.95 each.

**TYPE 'E'** (KSN1038A) 3" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems, etc. Price £4.35 each.

**TYPE 'F'** (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each.

U.K. post free (or SAE for Piezo leaflets).



### 1 K-WATT SLIDE DIMMER

- ★ Controls loads up to 1KW.
- ★ Compact Size 4½" x 1½" x 2½".
- ★ Easy snap in fixing through panel/cabinet cut out.
- ★ Insulated plastic case.
- ★ Full wave control using 8 amp triac.
- ★ Conforms to BS800.
- ★ Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's/theatres, etc.

**Price £11.70 each + 50p P&P. (Any quantity.)**

### GENERAL PURPOSE 4½" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems, etc.

- ★ Rolled fabric surround
- ★ Twin cone
- ★ 8 ohm impedance
- ★ 15 watt R.M.S.
- ★ 1" voice coil
- ★ 13 oz. magnet
- ★ Frequency range 50/15,000Hz.

**Price £6.90 each + 75p P&P.**



### B.S.R. P232 TURNTABLE

P232 Turntable ★ 'S' shaped tone arm  
★ Belt driven ★ Aluminium platter  
★ Cueing lever ★ 240 volt AC operation (50Hz)  
★ Cut-out template supplied  
★ Used as standard by Hi-Fi and Disco manufacturers  
★ Fitted with either a magnetic or ceramic cartridge, please state cartridge required



**Price £22.50 + £2.50 P & P.**

### OMP POWER AMPLIFIER MODULES



100 WATTS R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. Vu meter available as an optional extra.

**SPECIFICATION:**  
Max. output power 100 watts R.M.S. (OMP 100)


Loads: (Open and short circuit proof) 4-16 ohms  
Frequency Response: 20Hz-25KHz ± 3dB  
Sensitivity: for 100 watts 500mV at 10K

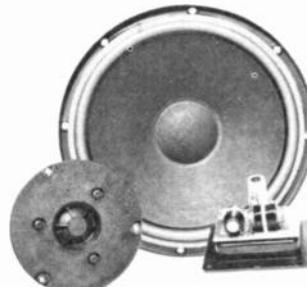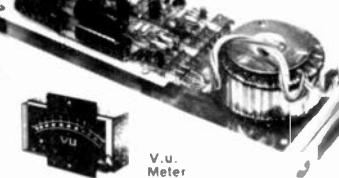T.H.D. 0.01%  
Size: 360 x 115 x 80mm  
Prices: OMP 100 £29.95 P & P £2.00  
V.U. Meter £6.50



**MULLARD 40 WATT R.M.S. 8 ohm SPEAKER SYSTEM.** Designed by Mullards specialist team in Belgium. Comprising of a Mullard 8" woofer with foam surround, a Mullard 3" dome tweeter and a cleverly designed B.K. Electronics crossover combining spring loaded loudspeaker terminals and recessed mounting panel. Supplied complete with installation and cabinet details.

**Price £13.90 + £1.50 P & P per kit.**

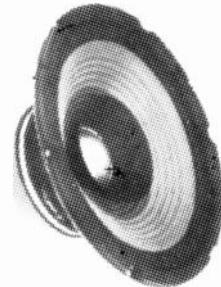

**12" 80 watt R.M.S. loudspeaker**  
A superb general purpose twin cone loudspeaker. 50 oz magnet 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome

**Price £17.95 ea + £2.50 P & P.**

# B.K. ELECTRONICS

DEPT E.E.

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.




# EXPRESS from MAPLIN


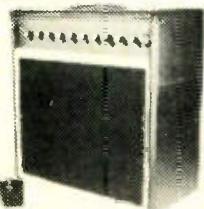
## COMBO-AMPLIFIER

Easy to build portable 120W MOSFET amp for all stage musicians. Built-in flanger, five step equaliser, two inputs for guitars, keyboards or microphones, low-noise pre amp.

Full details in our book. Price 60p.  
Order As XA01B.



## STOP-WATCH

Multi-mode 8 digit stopwatch accurate to hundredths of a second. Easy to build - complete kits available.  
Full details in our projects book.  
Price 60p.  
Order As XA02C.



## MILES PER GALLON METER

Digital display shows you how economical your driving is as you go along.  
Complete kits available.  
Full details in our projects book.  
Price 60p.  
Order As XA02C.



## DIGITAL MULTI-TRAIN CONTROLLER

Control up to 14 trains individually on the same track with any four simultaneously! Low cost kits available.  
Full details in our projects book. Price 60p.  
Order As XA02C.

Photo by W.A. Sharman.


## HOME SECURITY SYSTEM



Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability.  
Full details in our projects book.  
Price 60p.  
Order As XA02C.
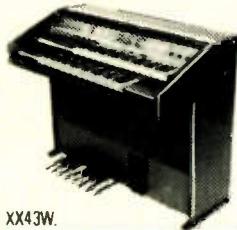
## MATINÉE ORGAN

Easy-to-build, superb specification.  
Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50.  
Order As XH55K.  
Complete kits available:  
Electronics - £299.95,  
Cabinet - £99.50 (carriage extra).  
Demo cassette price £1.99. Order As XX43W.



\*Don't miss out - get a copy of our catalogue now!  
Over 140,000 copies sold already!

\*On sale now in all branches of WHSMITH price £1.

\*320 big pages packed with data and pictures of over 5,500 items.



### Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded.  
If you live outside the U.K. send £1.68 or 12 International Reply Coupons. EE4/82

Name \_\_\_\_\_

Address \_\_\_\_\_

**MAPLIN**  
ELECTRONIC  
SUPPLIES LTD.

All mail to:

P.O. Box 3, Rayleigh, Essex SS6 8LR  
Tel: Sales (0702) 552911 General (0702) 554155

Shops at:

159 King St., Hammersmith, London W6. Tel: 01-748 0926  
284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000  
Note: Shops closed Mondays