

Easy to build projects for everyone

Everyday

SEPT. 82

70p

ELECTRONICS

SOUND SPLITTER


FOR MUSICAL INSTRUMENTS



SCHOOLS
Electronic Design Award
COMPETITION
Full Report inside

MONTHLY PLANNER
CB BATTERY
CHARGER
SCREEN WASHER DELAY

ELECTRONIC IGNITION KIT

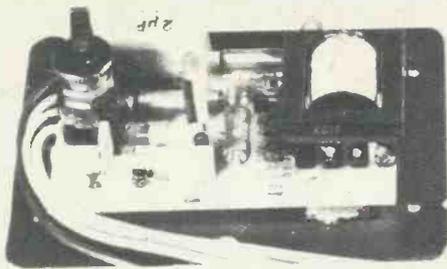

Buy NOW!
7% PRICE INCREASE
EFFECTIVE 1st OCT

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

PEAK PERFORMANCE — higher output voltage under all conditions.

IMPROVED ECONOMY — no loss of ignition performance between services.

FIRES FOULED SPARK PLUGS no other system can better the capacitive discharge system's ability to fire fouled plugs.

ACCURATE TIMING — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

SMOOTH PERFORMANCE — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

BETTER STARTING — full spark power even with low battery.

CORRECT SPARK POLARITY unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

L.E.D. STATIC TIMING LIGHT for accurate setting of the engine's most important adjustment.

LOW RADIO INTERFERENCE fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

DESIGNED IN RELIABILITY an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN
ELECTRONICS TODAY INTERNATIONAL JUNE '81 ISSUE
and EVERYDAY ELECTRONICS DECEMBER '81 ISSUE

FITS ALL NEGATIVE EARTH VEHICLES,
6 or 12 volt, with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS
Some older current impulse types (Smiths pre '74) require an adaptor —
PRICE £2.95

STANDARD CAR KIT £14.85
ASSEMBLED AND TESTED £24.95

PLUS £1

TWIN OUTPUT KIT £22.94
For MOTOR CYCLES and CARS with twin ignition systems
ASSEMBLED AND TESTED £34.70

U.K. P.&P.

Prices include V.A.T.

ELECTRONIZE DESIGN Dept. C

Goods normally despatched within 7 days

Magnus Road, Wilnecote,
Tamworth. B77 5BY
Phone 0827-281000



BARCLAYCARD

VISA

DIMENSIONS:
Length 12.5 cm
Width 8.9 cm
Height 4.3 cm
Lead length 100.0 cm

TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µS at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DISCHARGE system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

SUPER POWER DISCHARGE CIRCUIT A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

HIGH EFFICIENCY INVERTER A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

PRECISION SPARK TIMING CIRCUIT This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

TYPICAL SPECIFICATION


	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY	36 mJ	10 mJ
(STORED ENERGY)	135 mJ	65 mJ
SPARK DURATION	500 µS	160 µS
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	26 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µS	30 µS

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.


Everyday ELECTRONICS

VOL. 11 NO. 9 SEPTEMBER 1982

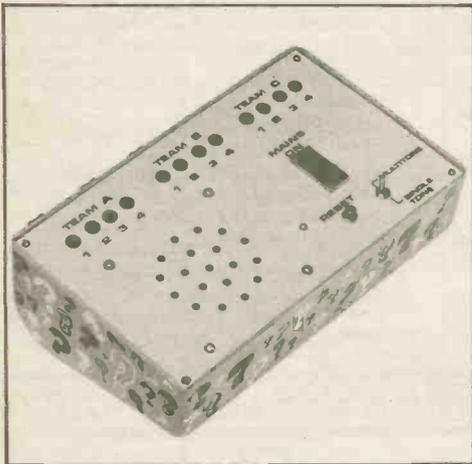PROJECTS . . . THEORY . . . NEWS . . .
COMMENT . . . POPULAR FEATURES . . .



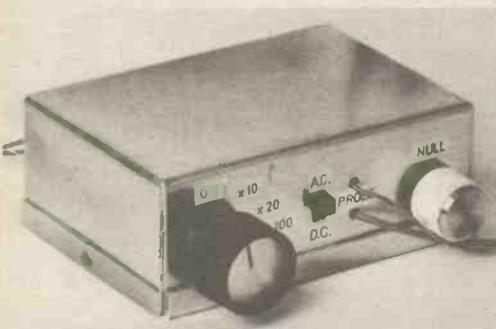SCHOOLS Electronic Design Award COMPETITION



A full report appears on page 590.

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

PROJECTS

- SOUND SPLITTER** by J. D. Rogers 560
A multi-effects unit for the musician
- CB BATTERY CHARGER** by A. Flind 568
Constant current charger for NiCad cells
- SCREEN WASHER DELAY** by G. L. Stoneman 576
Single operation extended wash time
- MONTHLY PLANNER** by A. P. Donleavy 581
Electronic calendar with event memory
- TEMPERATURE INTERFACE FOR THE TRS80** 599
by O. N. Bishop
Construction and software
- CONTINUITY TESTER** by J. Moulder 604
Audible circuit checker

SERIES

- TEACH-IN 82** by O. N. Bishop 571
Part 12: Computing circuits
- A.C. MAINS** by A. Kenyon 596
Part 3: Phase relationships; Power factor

FEATURES

- EDITORIAL** 559
The Young Generation; New Season Is A'Coming
- JACK PLUG AND FAMILY** by Doug Baker 566
Cartoon
- SHOP TALK** by Dave Barrington 567
Product news and component buying
- COUNTER INTELLIGENCE** by Paul Young 570
A retailer comments
- EVERYDAY NEWS** 577, 590
What's happening in the world of electronics
- PLEASE TAKE NOTE** 577
Circuit Exchange—Invader Landing Game
- FOR YOUR ENTERTAINMENT** by Barry Fox 578
Resistance to Space, Junk Mail, Car Statics
- RADIO WORLD** by Pat Hawker G3VA 580
A Better Picture, The Sting
- CONSUMER ELECTRONICS SHOW** by Barry Fox 588
Report from America
- READERS LETTERS** 589
Your news and views
- SEDAC** 592
The Twelve winning designs
- SQUARE ONE** 607
Beginner's Page: Ohm's law

Our October issue will be published on Friday, September 17. See page 587 for details.

Readers Services ● Editorial and Advertisement Departments 559

BI-PAK

BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a BI-Pak Catalogue. Have one by you all the time—it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p&p.

8 Bit MICROPROCESSOR

National INS8080AN 40 Pin DIL N Channel Silicon GATE MOS TECHNOLOGY As used in Nationals N8080 Micro Computer Family

Instruction Cycle Time 2 uS

Supplied with functional Block Diagram

BRAND NEW —

NOT seconds or reclaims

100% perfect ORDER NO. SX8080

Normal Sell price £4.50 each

Our BI-PAK Special Price

SO HURRY — LIMITED STOCKS

only £2.00

40 Pin IC Socket to fit SX8080
ORDER NO. 1609

Offer price **30p**

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification:

● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz—3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%

BI-PAK'S give away price

£2.25 each.

You could not Build one for this price.

MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch, LED indicators at each of the five charging points.

Charges: — Power: —
PP3 (9V) 220-240V AC
U12 (1.5V penlite) Dims: —
U11 (1.5V "C") 210 x 100 x 50mm
U2 (1.5V "D") **£6.95**

POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug. Input: — 240V AC 50HZ Output: —3, 4.5, 6, 7.5, 9 & 12V DC Rating: —300 ma MW88

TRIACS — PLASTIC

4 AMP — 400v — T0202 — TAG 136G.
1 OFF 10 OFF 50 OFF 100 OFF
40p £3.75 £17.50 £30.00
8 AMP 400v — T0220 — TAG 425
60p £5.75 £27.50 £50.00

2N3055 The best known Power Transistors in the World — 2N3055 NPN 115w.
Our BI-PAK Special Offer Price:
10 off 50 off 100 off
£3.50 £16.00 £30.00

BD312 COMPLIMENTARY PNP POWER TRANSISTORS: TO 2N3055
Equivalent MJ2955 — BD312 — T03
SPECIAL PRICE £0.70 each
10 off £6.50

5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes: — 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm **£1.75**

5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. **£1.75**

5T41 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers: — H 0 and H 1 Hex key wrenches: — 1.5, 2 and 2.5mm **£1.75**

5T51 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes: — 4, 4.5, 5, 5.5 and 6mm. **£1.75**

BUY ALL FOUR SETS: 5T21-5T51 and get

HEX KEY SET FREE

HEX KEY SET ON RING.

Sizes: 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm.

Made of hardened steel.

HX/1. **£1.25**

TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera.

Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductor devices to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation

Price —
— Beat the Budget
— Down with Depression

JUST £6.50.

O/no SX85

Send your orders to Dept EE 9
BI-PAK PO BOX 6 WARE HERTS
SHOP AT 3 BALDOCK ST.
WARE HERTS



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.

Remember you must add VAT at 15% to your order.
Total. Postage add 75p per Total order

Bradley Marshall Ltd

OF EDGWARE ROAD

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS

Tel: 723-4242

PROBABLY THE LARGEST STOCK OF ICs & TRANSISTORS IN THE SOUTH TRY US FIRST

LARGE RANGE OF ACCESSORIES

Plugs
Sockets
Audio Connectors
Veroboard
IC Sockets
Soldering equipment
Screw drivers (BAHCO)
Sifam Knobs etc.

LARGE RANGE OF ICs

Transistors
Capacitors
Diodes
Triacs
Thyristors
Opto
Resistors
Potentiometers
Fuses
Bridges
Please send S.A.E. for list.

SPECIAL OFFER

STEINAL
MULTICHECK
£7.50
+ VAT

Normal price £10.26

BUY WITH ACCESS BARCLAYCARD A/EXPRESS DINERS

Just phone we do the rest

MAIL ORDER FASTER SERVICE PHONE 723-4242

16, 24, 40 WAY RIBBON CABLE £1.10; £1.40; £2.20 metre

Header plugs 14 way, 16 way, 24 way, 40 way

BAHCO TOOLS

SIDE CUTTERS
2132 £7.10
2112 £9.40

END CUTTERS
2211 £10.43

PLIERS

2411 £6.75
2415 £6.78

ICE MULTIMETERS

Microtest 80 £16.60
Supertest 680 R £32.00
Supertest 680E £24.50

EXPERIMENTER BREADBOARD'S

EXP 325 EXP 600
EXP 350 EXP 650
EXP 300 EXP 4B

LOGIC PROBES

LP1 £31.00
LP2 £18.00

EXPERIMENTER KITS

PB6 £9.20
PB100 £11.80

PLEASE REMEMBER To ADD 15% VAT

BRADLEY MARSHALL LTD FOR

Crimson Elektrik

PROFESSIONAL AMPLIFIER MODULES

PRICE LIST —
ELECTRONIC MODULES & ASSEMBLIES — APRIL 1981

CODE	DESCRIPTION	Less VAT	VAT	INC VAT	WT (Kg)
		£	£	£	
CE 608	Power Amplifier Module	18.26	2.74	21.00	0.16
CE 1004	Power Amplifier Module	21.30	3.20	24.50	0.20
CE 1008	Power Amplifier Module	23.90	3.60	27.50	0.21
CE 1704	Power Amplifier Module	30.43	4.57	35.00	0.22
CE 1708	Power Amplifier Module	30.43	4.57	35.00	0.22
CE 3004	Power Amplifier Module	42.60	6.40	49.00	0.40
BD 1	Bridge Driver Module	7.13	1.07	8.20	0.06
TR 80	Toroidal Transformer 80VA	18.00	2.70	20.70	2.00
TR 150	Toroidal Transformer 150VA	20.07	3.01	23.08	2.35
TR 250	Toroidal Transformer 250VA	25.43	3.81	29.24	3.35
TR 250Q	Toroidal Transformer (low noise)	33.20	4.98	38.18	2.80
B 6	Bridge Rectifier (6 amp)	0.99	0.15	1.14	0.02
B12	Bridge Rectifier (12 amp)	1.80	0.27	2.07	0.03
C4700/40	Reservoir Capacitor and Clip	1.91	0.29	2.20	0.09
C4700/63	REservoir Capacitor and Clip	2.40	0.36	2.76	0.11
C4300/63	Reservoir Capacitor and Clip	2.60	0.39	2.99	0.11
CPS 80	Power Supply	22.82	3.42	26.24	2.10
CPS 80D	Dual Power Supply	27.63	4.14	31.77	2.25
CPS 150	Power Supply	25.86	3.88	29.74	2.50
CPS 150D	Dual Power Supply	31.65	4.75	36.40	2.60
CPS 250	Power Supply	32.03	4.80	36.83	3.50
CPS 250D	Dual Power Supply	39.43	5.91	45.34	3.65
TS 70	Thermal Switch 70°C	1.92	0.29	2.21	0.02
HS 50	50mm Heatsink	1.60	0.24	1.84	0.15
HS 100	100mm Heatsink	2.60	0.39	2.99	0.30
HS 150	150mm Heatsink	3.65	0.55	4.20	0.45
FM 1	Fan Mounted on 2 x HS 100	32.13	4.82	36.95	1.20
FM 2	Fan Mounted on 2 x HS 150	36.10	5.42	41.52	1.50
CPR 1X	Pre-Amplifier Module	31.30	4.70	36.00	0.15
MC 2	Moving Coil Pre-Pre-Amplifier Module	20.00	3.00	23.00	0.07
REG 1	Regulated Power Supply	8.09	1.21	9.30	0.07
TR 6	6VA Mains Transformer	2.87	0.43	3.30	0.21
XO 2	2 Way Crossover Module	17.39	2.61	20.00	0.07
XO 3	3 Way Crossover Module	26.09	3.91	30.00	0.07
MU 1	Muting Circuit for XO 2 or XO 3	8.35	1.25	9.60	0.04
CK 1010	Complete Pre-Amplifier Kit	78.26	11.74	90.00	2.50
CK 1040	Complete 40 Watt Power Amplifier Kit	103.48	15.52	119.00	7.30
CK 1100	Complete 100 Watt Power Amplifier Kit	129.56	19.44	149.00	7.30
MC 2K	Add On Moving Coil Kit	21.74	3.26	25.00	0.12
PSK	Pre-Amplifier Power Supply Kit	17.39	2.61	20.00	0.75

SOLE DISTRIBUTION BRADLEY MARSHALL LTD OF EDGWARE RD
325 EDGWARE RD. LONDON W21 BN
TEL: 01-723 4242


Make up your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS and HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project—you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- INSTRUMENT PRE AMP** Aug. 82. £6-57
- TWO TONE DOORBELL ALARM** Aug 82. £8-25
- CB ROGER BLEEPER** Aug 82. £7-92
- BRAKE LIGHT RELAY** July 82. £4-49
- 2-WAY INTERCOM** July 82. £3-85
- ELEC/TRONIC PITCH PIPE** July 82. £2-59
- REFLEX TESTER** July 82. £6-81
- SEAT BELT REMINDER** June 82. £3-49
- EGG TIMER** June 82. £4-63
- TWO TONE TRAIN HORN WITH REMOTE TRIGGER OPTION** May 82. £10-53
- CAR LED VOLTMETER** less case, May 82. £2-74
- LIGHTNING CHESS BUZZER**, May 82. £5-80
- 2k RAM PACK** Apr 82 less case. £12-89
- V.C.O. SOUND EFFECTS UNIT** Apr 82. £10-81
- CAMERA OR FLASH GUN TRIGGER** Mar 82. £11-60 less tripod bushes
- POCKET TIMER** Mar 82. £3-47
- GUITAR TUNER** Mar 82. £14-65
- CAR OVERHEATING ALARM**, Feb. 82. £8-99
- SIMPLE STABILISED POWER SUPPLY**, Jan. 82. £22-39
- MINI EGG TIMER**, Jan. 82. £3-69
- SIREN MODULE**, Jan. 82. less speaker. £5-21
- MODEL TRAIN CHUFFER**, Jan. 82. £7-73
- SQUARE SIX**, Dec. 81. £4-40
- GUITAR ADAPTOR**, Dec. 81. £3-52
- REACTION METER**, Dec. 81. £16-41
- ELECTRONIC IGNITION**, Nov. 81. £24-33
- SIMPLE INFRA RED REMOTE CONTROL**, Nov. 81. £15-99
- PRESSURE MAT TRIGGER ALARM**, Nov. 81. £5-86 less mats
- EXPERIMENTER CRYSTAL SET**, Nov. 81. Less aerial. £5-60
- Headphones**, £2-98 extra
- CAPACITANCE METER**, Oct. 81. £21-98
- SUSTAIN UNIT**, Oct. 81. £11-93
- 'POPULAR DESIGNS'**, Oct. 81.
- TAPE NOISE LIMITER**, £4-28
- HEADS AND TAILS GAME**, £2-36
- CONTINUITY TESTER**, £3-70
- PHOTO FLASH SLAVE**, £3-24
- FUZZ BOX**, £8-82
- OPTO ALARM**, £6-34
- SOIL MOISTURE UNIT**, £5-43
- ICE ALARM**, £7-38
- 0-12V POWER SUPPLY**, Sept. 81. £16-84
- CMOS CAR SECURITY ALARM**, Sept. 81. £8-49
- CMOS DIE**, Sept. 81. £7-47
- LED SANDGLASS**, Aug. 81. £7-98
- CMOS METRONOME**, Aug. 81. £7-70
- COMBINATION LOCK**, July 81. Less case. £18-30
- BURGLAR ALARM SYSTEM**, June 81 less ball, loop & Mics. £38-30
- TAPE AUTO START**, June 81. £11-96
- LIGHTS REMINDER AND IGNITION LOCATOR** E.E. May 81. £5-29
- SOIL MOISTURE INDICATOR** E.E. May 81. £3-83
- GUITAR HEADPHONE AMPLIFIER** E.E. May 81. £3-96
- PHONE BELL REPEATER / BABY ALARM** E.E. May 81. £5-29
- INTERCOM**, April 81. £20-76
- SIMPLE TRANSISTOR & DIODE TESTERS**, Mar. 81. Ohm meter version £1-89. Led version £2-56
- MINI SIREN**, Mar. 81. £7-52
- LED DICE**, Mar. 81. £7-89
- LED FLASHER**, Mar. 81. £4-01
- MODULATED TONE DOORBELL**, 'Mar. 81. £8-21
- BENCH POWER SUPPLY**, Mar. 81. £49-98
- THREE CHANNEL STEREO MIXER**, Feb. 81. £17-47
- SIGNAL TRACER**, Feb. 81. £7-64 less probe.
- NI-Cd BATTERY CHARGER**, Feb. 81. £12-72
- ULTRASONIC INTRUDER DETECTOR**, Jan. 81 less case. £49-98
- 2 NOTE DOOR CHIME**, Dec. 80. £9-65
- LIVE WIRE GAME**, Dec. 80. £10-94
- GUITAR PRACTICE AMPLIFIER**, Nov. 80. £11-99 less case. Standard case £3-88. High quality case £8-33
- SOUND TO LIGHT**, Nov. 80. 3 channel. £19-95
- TRANSISTOR TESTER**, Nov. 80. £10-87 inc. test leads.
- AUDIO EFFECTS UNIT FOR WEIRD SOUNDS**, Oct. 80. £12-26
- BICYCLE ALARM**, Oct. 80. £9-88 less mounting brackets.
- IRON HEAT CONTROL**, Oct. 80. £5-48
- TTL LOGIC PROBE**, Sept. 80. £4-85
- ZENER DIODE TESTER**, June 80. £8-23
- 4 STATION RADIO**, May 80. £15-33 less case.
- LIGHTS WARNING SYSTEM**, May 80. £4-38
- BATTERY VOLTAGE MONITOR**, May 80. £4-83
- CABLE & PIPE LOCATOR**, Mar. 80. £3-85 less coil former.
- KITCHEN TIMER**, Mar. 80. £13-70
- STEREO HEADPHONE AMPLIFIER**, Mar. 80. £16-97
- MICRO MUSIC BOX**, Feb. 80. £15-20
- Grey Case** £3-99 extra.
- SIMPLE SHORT WAVE RECEIVER**, Feb. 80. £24-17. Headphones £2-98
- SLIDE/TAPE SYNCHRONISER**, Feb. 80. £11-50
- MORSE PRACTICE OSCILLATOR**, Feb. 80. £4-32
- SPRING LINE REVERB. UNIT**, Jan. 80. £24-17
- UNIBOARD BURGLAR ALARM**, Dec. 79. £5-64
- BABY ALARM**, Nov. 79. £8-98
- CHASER LIGHTS**, Sept. 79. £21-97
- SIMPLE TRANSISTOR TESTER**, Sept. 79. £6-88
- DARKROOM TIMER**, July 79. £2-71
- ELECTRONIC CANARY**, June 79. £5-48
- MICROCHIME DOORBELL**, Feb. 79. £14-82
- THYRISTOR TESTER**, Feb. 79. £3-54
- FUSE CHECKER**, Oct. 78. £2-16
- SOUND TO LIGHT**, Sept. 78. £7-87
- CAR BATTERY STATE INDICATOR**, Sept. 78. Less case. £1-96
- R.F. SIGNAL GENERATOR**, Sept. 78. £24-98
- IN SITU TRANSISTOR TESTER**, June 78. £6-33
- WEIRD SOUND EFFECTS GENERATOR**, Mar. 78. £5-28
- AUDIO VISUAL METRONOME**, Jan. 78. £5-63
- ELECTRONIC TOUCH SWITCH**, Jan. 78. £2-56 less case.
- RAPID DIODE CHECK**, Jan. 78. £2-57
- PHONE/DOORBELL REPEATER**, July 77. £8-98
- ELECTRONIC DICE**, Mar. 77. £5-31

SOLDERING/TOOLS

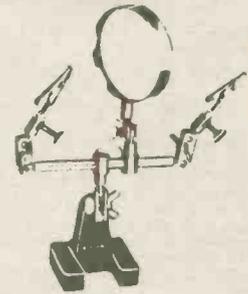- ANTEX X5 SOLDERING IRON 25W** £5-48
- SOLDERING IRON STAND** .. £2-40
- SPARE BITS**, Small, standard, large, 65p each. For X5 + X25
- SOLDER**, Handy size 99p
- SOLDER CARTON** £1-84
- DESOLDER BRAID** 69p
- HEAT SINK T.WEEZERS** £29p
- DESOLDER PUMP** £6-48
- HOW TO SOLDER LEAFLET** 12p
- LOW COST CUTTERS** £1-69
- LOW COST LONG NOSE PLIERS** £1-68
- WIRE STRIPPERS & CUTTERS** £2-69



HELPING HANDS JIG £6-30

Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (25 x 1 magnifier attached), used and recommended by our staff.

- VERO SPOT FACE CUTTER** £1-49
- PIN INSERTION TOOL** £1-98
- VEROPINS (pk of 100) 0-1"** 52p
- MULTIMETER TYPE 1 (1,000 opv)** £6-68
- MULTIMETER TYPE 2 (20,000 opv) with transistor tester**, Very good £14-76
- CROCODILE CLIP TEST LEAD SET**, 10 leads with 20 clips 99p
- RESISTOR COLOUR CODE CALCULATOR** 21p

- CONNECTING WIRE PACK TYPE ED. 11 colours** 49p
- ILLUMINATED MAGNIFIERS**
Small 2" dia. (5x mag.) £1-14
Large 3" dia. (4x mag.) £2-40
- CAST IRON VICE** £2-98
- SCREWDRIVER SET** £1-98
- POCKET TOOL SET** £3-98
- DENTISTS INSPECTION MIRROR** £2-85
- JEWELLERS EYEGLASS** £1-50
- PLASTIC TWEZERS** 69p
- PAIR OF PROBES WITH LEADS (cc)** 77p

TEACH IN 82

All top quality components as specified by Everyday Electronics. Our kit comes complete with FREE COMPONENT IDENTIFICATION SHEET. Follow this educational series and learn about electronics—Start Today.

LIST 1 and LIST 2 together £27-98. LIST 3 £5-98.

★ ★ ★ SPECIAL OFFER ★ ★ ★
LISTS 1, 2 and 3 all bought together £33-48.

WOODEN CASE KIT also available £11-98—wood, formica, glue, screws etc. Cut to size.
12 part series, reprints available of previously published parts, 45p each.

LISTS 1, 2, AND 3 ALL AVAILABLE NOW. ALSO WOODEN CASE KIT.

BOOKS

- SEMICONDUCTOR DATA BOOK** Newnes £5-90
- ELECTRONIC PROJECTS FOR HOME SECURITY** £3-35
- ELECT. PROJECTS IN PHOTOGRAPHY** £3-35
- 110 ELECT. ALARM PROJECTS** £5-35
- MODEL RAILWAY PROJECTS** £1-95
- BASIC ELECTRONICS**, Theory and practice £7-98
- BEGINNERS GUIDE TO BUILDING ELECT. PROJECTS** £1-50

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board.

Adventures with Microelectronics £2-55

Component pack £29-64 less battery.

ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.

Adventures with Electronics £2-40. **Component pack** £17-98 less battery.

ADVENTURES WITH DIGITAL ELECTONICS

New book by Tom Duncan in the popular 'Adventures' series. This book of entertaining and instructive projects is designed for hobbyists and students. It provides a stepping stone to the microprocessor.

The first part deals with the properties of some basic ICs used in digital electronics.

The second part gives details of how to build eight devices—shooting gallery, 2-way traffic lights, electronic adder, computer space invaders game, etc.

For each project there is an explanation of 'how it works' and also suggestions for 'things to try'.

No soldering—all circuits built on 2 Bimboard 1 breadboards.

Adventures with Digital Electronics book £3-25. **Component pack** £42-50, ref. EEDC. All the components needed including 2 breadboards and hexadecimal keyboard. Available less breadboards £29-98, ref. EEDF. Both less battery.

MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST
Price list included with orders or send one (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order.

MORE E.E. KITS PLUS H.E. and E.T.I. PROJECT KITS IN THE PRICE LIST.

MAGENTA gives you **FAST DELIVERY OF QUALITY COMPONENTS & KITS**. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—**HAVE YOU TRIED US?**

MAGENTA ELECTRONICS LTD.

EB43, 135 HUNTER ST. BURTON-ON-TRENT, STAFFS., DE14 2ST. 0283 65435. MON.-FRI. 9-5. MAIL ORDER ONLY. ADD 45p P. & P. TO ALL ORDERS. PRICES INC. VAT



Normal despatch by return of post. **OFFICIAL ORDERS WELCOME.** OVERSEAS. Payment must be in sterling, IRISH REPUBLIC and BFPO: UK PRICES. EUROPE: UK PRICES plus 10%. ELSEWHERE: Write for quote.

ENFIELD ELECTRONICS

WHEN ORDERING, PLEASE ALLOW 12 DAYS FOR DELIVERY.

NOISE FILTER SYSTEM

A sophisticated combination of filters designed to eliminate interfering noises from all vehicular sources including ignition spark, alternator/generator, other accessories, metal to metal contact etc.

Contents:- Generator noise filter, alternator noise filter, Dual line noise filter and ignition noise filter.

Price £8.50
Order No. NFS-1000

This 3½ inch super horn (Flush Flange) piezo ceramic tweeter converts electrical energy into acoustic energy at an efficiency in excess of 50%, a level not possible with any other type of loudspeaker. Economy is added to high efficiency by the elimination of crossover networks, because the unit rejects low frequency power. It has a high impedance of over 1,000 ohms at 1 kHz and 20 ohms at 40 kHz and it presents no added load to the amplifier.

A Super Special Offer of £4.65
Order No. LOS2



For up to the minute prices please ring: 01-366-1873. Please add 15% VAT £1.00 p & p per item orders.



Altai Multimeter & Transistor Tester
DC volts 0-1v-5v-2.5v-10v-50v-250v-1000v ±3%
AC volts 0-10v-50v-250v-1000v ±3%
DC current 0-50uA-2.5mA-25mA-0.25A ±3%

Resistance:
Minimum 0-2-2-200-200k ohms } ±3%
Midscale 20-200-20k-200k ohms }
Maximum 2k-20k-2m-20m ohms }
As a transistor tester
Leakage current 0-150uA at X1k range } ±5%
0-15mA at X10 range }
0-150mA at X1 range }
Price £14.95
Order No. YN 360TR

A superb stereo headphone

Specifications:
1) sensitivity 110dB at 1,000Hz with 1mw
2) Frequency response: 20-19,000Hz
3) UNIT impedance 8 ohms
4) matching impedance 4-16 ohms
5) Maximum Input 0.5 watts per channel
6) Individual slide volume control (stereo/mono switch)
7) 10 foot coiled cord with stereo phone plug
8) Leathery-soft ear pads and head cushion
price £5.95.
Order No. LE-76VS



Universal NI-CAD, battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.

Charges:- PP3 (9V), U12 (1.5V penlite), U11 (1.5V "C"), U2 (1.5V "D"), Power:- 220-240V AC, Dims:- 210 x 100 x 50mm.
Super Special Offer at only £7.50.
Order No. MW 398



IDEX

stereo headphone
Sensitivity 98dB at 1kHz with 1mw.
Frequency response 20-25,000 Hz. Impedance 35 ohms.
Maximum input 0.4 watts. 7ft cord with 3.5 stereo phone plug.

Price £7.50
Order No. MHD-3

AS YOU HAVE SEEN FROM OUR PREVIOUS ADVERTISEMENTS, WE STOCK A VAST RANGE OF PRODUCTS—GIVE US A RING FOR YOUR NEEDS—WE STOCK EVERYTHING FOR THE ELECTRONICS ENTHUSIAST AT VERY COMPETITIVE PRICES.



208 Baker Street, Enfield, Middlesex.
01-366 1873.



METERS: 110 x 82 x 35mm
30µA, 50µA, 100µA. £5.90.
Post 50p.

METERS: 45 x 50 x 34mm
50µA, 100µA, 1mA, 5mA, 10mA,
25v, 1A, 2A, 5A, 25V.
£2.90. Post 30p.

METERS: 60 x 47 x 33mm
50µA, 100µA, 1mA, 5mA, 10mA,
100mA, 1A, 2A, 25v, 50v,
50-0-50µA, 100-0-100µA. £4.76.
VU meters. £5.32.
Post on above meters 30p.

Silicone grease 50g £1.32 Post 14p.

NI-CAD BATTERY CHARGER

Led indicators charge-test switch.
For PP3, HP7, HP11 & HP2 size batteries.
Price £5.85 Post 94p.

MULTI-METER

7N 360TR
20,000 ohm/volt
DC Volts: 0-1,
0-5, 2-5, 10-150—
250-1,000v.
AC Volts: 10-50,
250-1,000

RESISTANCE RANGES
X1, X10, X1K,
X10K
£14.10
P.&P. 87p

TRANSFORMERS

240v Primary
3-0-3v 100mA 82p
6-0-6v 100mA 87p
6-0-6v 250mA £1.22
12-0-12v 50mA 92p
12-0-12v 100mA £1.15

Post on above transformers 48p.

9-0-9v 1A £1.80
12-0-12v 1A £2.40
15-0-15c 1A £2.60
6-3v 1½A £1.80
6-0-6v 1½A £2.10

Post on above transformers 87p.

All above prices include V.A.T. Send 80p for new 1982 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

All goods despatched within 3 days from receipt of the order.

M. DZIUBAS

158 Bradshawgate, Bolton
Lancs. BL2 1BA




Constructor Series Speakers

IT'S SO EASY

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit. No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of.

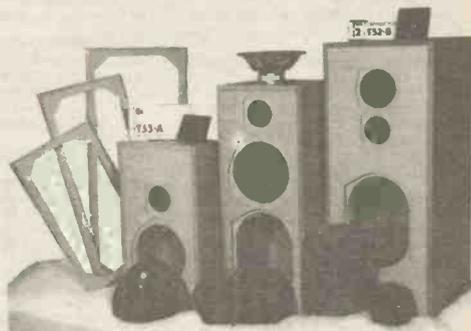Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc. The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl. Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.



Prices: CS1 (As 101) £110 pr. inc. VAT, plus carr./ins. £ 5.50
CS1A (simplified LS3/5A) £103 pr. inc. VAT, plus carr./ins. £ 5.50
CS3 (as 103.2) £129 pr. inc. VAT, plus carr./ins. £10.00
CS5 (as Carlton II) £192 pr. inc. VAT, plus carr./ins. £15.00
CS7 (as Cantata) £250 pr. inc. VAT, plus carr./ins. £18.00



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

1982 Catalogue — £1.50 post free

Lightning service on telephoned credit card orders!

Rapid Electronics

Tel: 0206 36412
Hill Farm Industrial Estate
Boxted
Colchester Essex CO4 5RD



CONNECTORS

DIN	Plug Skt	Jack	Plug Skt
2 pin	9p 9p	2.5mm	10p 10p
3 pin	12p 10p	3.5mm	9p 9p
5 pin	13p 11p	Standard	16p 20p
Phono	10p 12p	Stereo	24p 25p
1mm	12p 13p	4mm	18p 17p

UHF (CB) Connectors
PL259 Plug 40p Reducer 14p
SO239 square chassis sckt 38p
SO239S round chassis socket 40p

IEC 3 pin 250V/6A
Plug chassis mounting 38p
Socket free hanging 60p
Socket with 2m lead 120p

SWITCHES

Miniature toggle
SPST 55p, SPDT 60p, DPDT 65p.
Miniature toggle
SPDT 80p, SPDT centre off 90p.
Standard toggle SPST 35p, DPDT 48p.
Miniature DPDT slide switch 12p.
Push to make 12p. Push to break 22p.
Rotary type adjustable stop
1P12W 2P6W 3P4W 4P3W all 55p each
DIL switches
4 SPST 80p, 6 SPST 80p, 8 SPST 100p.

CAPACITORS

Polyester. Radial leads. 250V, C280 type.
0.1, 0.015, 0.022, 0.033, 6p; 0.047, 0.068, 0.1, 7p; 0.15, 0.22, 9p; 0.33, 0.47, 13p; 0.68, 20p; 1µ, 23p.
Electrolytic. Radial or axial leads.
0.47/63V, 1/63V, 2.2/63V, 4.7/63V, 10/25V, 7p; 22/25V, 47/25V, 8p; 100/25V 9p; 220/25V, 14p; 470/25V, 22p; 1000/25V, 30p; 2200/25V, 50p.
Tag end Power Supply Electrolytics.
2200/40V 110p; 4700/40V 160p; 2200/63V 140p; 4700/63V 230p.

Polyester. Miniature Siemens PCB.
1n, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 7p; 22n, 33n, 47n, 68n, 8p; 100n, 9p; 150n, 11p; 220n, 13p; 330n, 20p; 470n, 26p; 880n, 29p; 1µ, 35p; 2µ2, 50p.
Tantalum bead.
0.1, 0.22, 0.33, 0.47, 1.0 @ 35V, 12p; 2.2, 4.7, 10 @ 25V, 20p; 15/16V, 30p; 22/16V, 27p; 33/16V, 45p; 47/16V, 27p; 47/16V, 70p; 68/16V, 40p; 100/10V, 90p.
Ceramic disc. 22p-0.01µ 50V, 3p each.
Multilayer miniature ceramic plate.
1-8P to 100P 5p each.
Polystyrene. 5% tolerance.
10p-1000p 6p, 1500-4700p 8p, 6800-0.012µ 10p.
Trimmers. Mullard 808 Series.
2-100P 2F, 2-220P 30p, 5-5.65P 35p.

POTENTIOMETERS

Rotary. Carbon track Log or Lin 1K-2M2.
Single 3p. Stereo 85p. Single switched 80p.
Slide 60mm travel single Log or Lin 5K-500K.
63p each.
Preset. Submin. hor. 100 ohms-1M, 7p each.
Cermat precision multiturn, 0.75W 3/4in.
100 ohms to 100K, 88p each.

TRANSFORMERS

Miniature mains.
606V, 909V, 12012V all @ 100mA 100p each.
PCB mounting. Miniature.
3VA 0-6, 0-6 @ 0.25A; 0.9-0.9 @ 0.15A; 0-12, 0-12 @ 0.12A, 200p each.
6VA 0-6, 0-6 @ 0.5A; 0.9-0.9 @ 0.3A; 0-12, 0-12 @ 0.25A, 270p each.
High quality. Split bobbin construction.
6VA 0-6, 0-6 @ 0.5A, 0.9-0.9 @ 0.3A, 0-12, 0-12, 0-12V @ 0.3A 220p each.
12VA 0-6, 0-6 @ 1A, 0-9, 0-9 @ 0.8A, 0-12, 0-12 @ 0.5A, 0-15, 0-15 @ 0.4A, 295p each (plus 40p carriage).
25VA 0-6, 0-6 @ 1.5A, 0-9, 0-9 @ 1.2A, 0-12, 0-12 @ 1A, 0-15, 0-15 @ 0.8A 330p each (plus 60p carriage).
50VA 0-12, 0-12 @ 2A, 0-15, 0-15 @ 1.5A 440p each (plus 25p carriage).

PCB MATERIALS

Aifa transfer sheets—please state type (e.g. DIL pads etc.) 45p
Dalo each resist pen 100p
Fibre glass board 3-75" x 8" 80p
Ferric Chloride 250ml bottle 100p

CABLES

20 metre pack single core connecting cable ten different colours 65p
Speaker cable 10p/m
Standard screened 16p/m
Twin screened 24p/m
2-5A 3 core mains 23p/m
10 way rainbow ribbon 85p/m
20 way rainbow ribbon 120p/m

HARDWARE

PP3 battery clips 8p
Red or Black crocodile clips 8p
Black pointer control knob 15p
UL Ultrasonic transducers 35p
6V Electronic buzzer 60p
12V Electronic buzzer 65p
PB2720 Piezo transducer 75p
64mm 84 ohm speaker 70p
64mm 8 ohm speaker 70p
20mm panel fuseholder 25p

Simply phone
0206 36412
with your order



COMPONENT KITS

An Ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices.
Ceramic Capacitor Kit. Contains 10 of each value from 22p to 0.01µ (135 caps.) 370p.
Polyester Capacitor Kit. Contains 5 of each value from 0.01 to 1µf (65 caps.) 575p each.
Preset Kit. Contains 5 of each value from 100 ohms to 1M (total 65 presets) 425p each.

Nut and Bolt Kit. Total 300 items 180p.

25 6BA 1/4 bolts 25 4BA 1/4 bolts
25 6BA 1/2 bolts 25 6BA 3/4 bolts
50 6BA nuts 50 6BA washers
50 6BA washers 50 6BA washers

VERO WIRING PEN

Pen + spool 310p
Spare spool 75p
Combs 6p

TRIACS

Antex CS 17W Soldering iron 450p
2-3 and 4-7mm bits to suit 65p
CS 17W Element 210p
Antex XS 25W Soldering iron 480p
3-3 and 4-7mm bits to suit 65p
Solder pump Desoldering tool 480p
Spare nozzle for above 70p
10 metres 22 swg solder 100p
Soldering iron stand for above 190p

RESISTORS

1/2W 5% Carbon film E12 series 4-7Ω-10M 1p each.
1/2W 5% Carbon film E12 series 4-7Ω to 4M7, 2p each.
1/2W 1% Metal film. E24 series 10Ω-1M, 6p each.

PANEL METERS

Size 60 x 46 x 35mm
0-50µA 0-500mA
0-100µA 0-1A
0-1mA 0-50V AC
0-10mA VU
0-50mA 0-300V AC
0-100mA 0-25V
495p each 0-30V DC

BRIDGE RECTIFIERS

1A 50V 22 6A 100V 80
1A 400V35 6A 400V 95
2A 200V40 VM18 DIL
2A 400V45 0-9A200V 50

RAPID BOXES

Aluminium (Plastic)
3 x 2 x 1in 70p With lid + screws
4 x 3 x 1 1/2in 85p 3 x 2 x 1in 55p
4 x 3 x 2in 100p 4 1/2 x 3 x 1 1/2in 88p
6 x 4 x 2in 120p 7 x 4 x 2in 160p
6 x 4 x 3in 150p

OFFER YOU THE BEST DEAL

ORDERING INFO
All prices exclude VAT. Please add to total order. Please add 50p carriage to all orders under £15 in value. Send cheque/PO or Access/Visa number with your order. Please note new address. Callers most welcome—we are just 10 minutes from the centre of Colchester. Telephone orders welcome with Access and Visa. Official orders welcome from colleges and schools etc. Export orders no VAT but please add carriage. All components brand new + full spec.

REGULATORS

78L05 30 79L05 65
78L12 30 79L12 65
78L15 30 79L15 65
78L05 40 79L05 45
78L12 40 79L12 45
78L15 40 79L15 45

DIODES

BY127 12 *1N4001 3
0A47 10 1N4002 5
0A90 9 1N4006 7
0A90 7 1N4007 7
0A200 8 1N5401 15
0A202 8 1N5404 16
1N914 4 1N5406 17
*1N4148 2 400mV zen. 6

FREE RESISTORS!

Yes that's right! Its giveaway month at Rapid!
On all orders over £15 received we give you 100 1/2W 5% resistors absolutely free of charge.
Free pack contains 10 each of 10 different popular values. Offer expires 30th September 1982. Please mention this magazine.

LINEAR

★555CMOS80	ICL7611	95	LM377	150	LM13600	120	NE570	400	TL071	30	
556 CMOS 150	ICL7622	180	LM380	65	MC1310	150	NE571	400	TL072	50	
709	ICL8038	320	LM382	120	MC1496	68	RC4136	68	TL074	95	
*741	ICL8211A	200	LM384	130	LM1922	400	RC4558	60	TL081	25	
748	35	ICM7224	785	LM386	65	ML924	185	SL480	170	TL082	45
9400CJ	350	ICM7555	80	LM387	120	ML925	210	SN7618	150	TL170	55
AY-3-1270	840	LF351	45	LM393	100	LM926	140	SN76477	250	ULA2240	120
AY-3-8910	600	LF353	85	LM399	25	LM927	140	SN76629	250	ULN2003	85
AY-3-8912	625	LF356	90	LM725	350	LM928	140	TBA1205	70	ULN2004	30
CA3046	60	LM10	360	LM733	75	LM929	140	TBA800	80	XR2006	90
CA3080	65	LM301A	25	LM741	14	MM5387A	465	TBA810	96	ZN414	100
CA3090A	Q375	LM18	120	LM747	75	NE529	225	TBA820	80	ZN423	135
CA3130E	90	LM324	40	LM748	40	NE531	250	TBA850	290	ZN444	35
*CA3140E	45	LM334Z	100	LM790	200	NI 544	250	TDA1008	320	ZN425E	350
CA3161E	100	LM335Z	125	*LM3909	70	*NE555	16	TD1022	525	ZN426E	330
CA3189	290	LM339	50	LM3911	120	NE555	45	TD1024	125	ZN427E	650
*CA3240E	11M	LM348	65	LM3914	200	NE566	150	TL061	40	ZN428E	480
ICL7106	790	LM358	50	LM3915	225	NE567	100	TL062	60	ZN459	285
								TL064	96	ZN1034E	200

TRANSISTORS

AC125	35	BC157	10	BC548	10	BF800	25	TP129A	40	*ZTX107	8	2N3053	23
AC126	25	BC158	10	BC549	10	BF801	25	TP129B	55	*ZTX108	8	2N3054	55
AC127	25	BC159	8	BC550	10	BF802	25	TP129C	60	*ZTX109	12	2N3055	50
*AC128	20	BC160	45	BC551	10	BF803	25	TP130A	45	*ZTX300	14	2N3442	120
BC140	22	BC168C	10	BC552	10	BF804	25	TP130B	50	*ZTX301	16	2N3422	6
AC187	22	BC169C	10	BC553	10	BF805	25	TP130C	60	*ZTX302	15	2N3703	9
AC188	22	BC170	10	BC554	10	BF806	25	TP131A	55	*ZTX303	10	2N3705	9
AD142	120	BC171	8	BC555	10	BF807	25	TP131B	45	*ZTX304	17	2N3706	9
AD149	80	BC172	2	BC556	10	BF808	25	TP132A	45	*ZTX305	15	2N3707	10
AD181	40	BC177	18	BC557	10	BF809	25	TP132B	45	*ZTX502	15	2N3708	10
AD182	25	BC178	18	BC558	10	BF810	25	TP132C	45	*ZTX503	18	2N3709	10
AF126	40	BC179	18	BC559	10	BF811	25	TP133A	60	*ZTX504	25	2N3712	190
AF126	50	BC182	10	BC560	10	BF812	25	TP133B	60	*ZTX505	25	2N3773	210
AF139	40	*BC182L	8	BC561	10	BF813	25	TP134A	60	*ZTX506	25	*2N3819	48
AF186	70	BC183	10	BC562	10	BF814	25	TP134B	60	*ZTX507	20	2N3823	60
AF239	75	BC183L	10	BC563	10	BF815	25	TP135A	60	*ZTX508	20	2N3826	60
BC107B	12	BC184L	7	BC564	10	BF816	25	TP135B	60	*ZTX509	20	2N3827	60
*BC108	9	BC212	10	BC565	10	BF817	25	TP136A	60	*ZTX510	20	2N3828	60
BC108C	12	BC213	10	BC566	10	BF818	25	TP136B	60	*ZTX511	20	2N3829	60
*BC109	9	BC213L	10	BC567	10	BF819	25	TP137A	60	*ZTX512	20	2N3830	60
BC109C	12	BC214	10	BC568	10	BF820	25	TP137B	60	*ZTX513	20	2N3831	60
BC140	22	*BC214L	7	BC569	10	BF821	25	TP138A	60	*ZTX514	20	2N3832	60
BC115	22	BC237	10	BC570	10	BF822	25	TP138B	60	*ZTX515	20	2N3833	60
BC117	22	BC238	14	BC571	10	BF823	25	TP139A	60	*ZTX516	20	2N3834	60
BC119	35	BC308	15	BC572	10	BF824	25	TP139B	60	*ZTX517	20	2N3835	60
BC137	40	BC327	14	BC573	10	BF825	25	TP140A	60	*ZTX518	20	2N3836	60
BC139	40	BC328	14	BC574	10	BF826	25	TP140B	60	*ZTX519	20	2N3837	60
BC140	40	BC337	14	BC575	10	BF827	25	TP141A	60	*ZTX520	20	2N3838	60
BC141	30	BC338	14	BC576	10	BF828	25	TP141B	60	*ZTX521	20	2N3839	60
BC142	25	BC477	30	BC577	10	BF829	25	TP142A	60	*ZTX522	20	2N3840	60
BC143	25	BC478	30	BC578	10	BF830	25	TP142B	60	*ZTX523	20	2N3841	60
BC147	8	BC479	30	BC579	10	BF831	25	TP143A	60	*ZTX524	20	2N3842	60
BC148	8	BC547	40	BC580	10	BF832	25	TP143B	60	*ZTX525	20	2N3843	60
BC149	9												

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/ P.O. OR BANKER'S DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 50p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. (ACCESS orders by telephone welcome).

VAT Export orders no V.A.T. Applicable to U.K. Customers only. Unless stated otherwise all prices are exclusive of V.A.T. Please add 15% to total cost including P & P.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am-6.00 pm. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in nF)
40V: 1nF, 1.5n, 2n, 3n, 4.7n, 6.8n 10p; 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 16p; 100n, 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 66p; 2µF 82p; 4µF 85p.
100V: 10n, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n 38p; 1µF 42p; 1µ5 45p; 2µF 48p; 4µF 58p. 1000V: 1nF 17p; 10nF 30p; 15nF 40p; 22n 36p; 33n 42p; 47n, 100n 55p.

POLYESTER RADIAL LEAD CAPACITORS (250V)
10nF, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 17p; 680n 19p; 1µF 23p; 1µ5 40p; 2µF 46p.

ELECTROLYTIC CAPACITORS: (Values in µF) 500V: 10µF 52p; 47 78p; 63V: 0.47, 1.0 1-5, 2.2, 3.3, 4.7, 8p; 10 10p; 15, 22 12p; 33 15p; 47 12p; 68 20p; 100 19p; 220 26p; 1000 70p; 2200 98p; 5µF: 68 20p; 100 17p; 220 24p; 40V: 8, 15p; 22 9p; 33 10p; 330 32p; 1000 48p; 2200 90p; 25V: 1.5, 4.7, 10, 22, 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 1500 42p; 2200 50p; 3300 76p; 4700 92p; 15V: 2.5, 4.0 8p; 47 68, 100 9p; 125 12p; 220 13p; 330 16p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 4700 79p.
TAG END CAPACITORS: 64V: 2200 13p; 3300 19p; 4700 24.5p. 50V: 2200 11p; 3300 15.4p. 40V: 4700 16p. 25V: 2200 9p; 3300 9p; 4000, 4700 98p; 10,000 32.5p.

TANTALUM Bead CAPACITORS: 35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 22p, 16V 2; 2, 4, 3.3 16p; 4.7, 6.8, 10 18p; 15 35p; 22 30p; 33, 47 40p; 100 55p; 10V: 1.5, 2.2 25p; 3.3, 4.7 35p; 100 55p.

MYLAR FILM CAPACITORS: 100V: 1nF, 2n, 4n, 4.7n, 10n 6p; 15nF, 22n, 30n, 40n, 47n 7p; 56n, 100n, 200n 9p. 470n/50V 12p.

MINIATURE TYPE TRIMMERS: 4-6pF, 2-10pF 22p; 2-25pF, 5-65pF 30p; 10-85pF 35p.

COMPRESSION TRIMMERS: 3-40pF, 10-30pF 20p; 20-250mF 28p; 100-580pF 35p; 400-1250pF 48p.

POLYSTYRENE CAPACITORS: 100pF to 1nF 8p; 1-5nF to 12nF 10p.

SILVER MICA: 2pF, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180 15p; 200, 220, 250, 270, 300, 330, 360, 390, 470, 600, 800, 820 21p; 1000, 1200, 1800, 2000 30p; 3300, 4700 60p.

CERAMIC CAPACITORS: 50V 0.5pF to 10nF 4p; 22n to 100n 7p.

EURO BREADBOARD £5-20.

VOLTAGE REGULATORS*
1A TO3 +ve
5V 7805 145p 7905 220p
12V 7812 145p 7912 220p
18V 7815 145p 7915 220p
18V 7818 145p

1A TO220 Plastic Casing
5V 7805 40p 7905 45p
12V 7812 40p 7912 45p
18V 7815 40p 7915 45p
18V 7818 40p 7918 45p
24V 7824 40p 7924 45p

100mA TO92 Plastic Casing
5V 78L05 30p 79L05 60p
5V 78L02 30p
8V 78L02 30p
12V 78L12 30p 79L12 60p
18V 78L15 30p 79L15 60p

723 38 LM317T 125 78H05+5V/5A 550
CA3085 95 LM323K 50
LM3000H 170 TAA550 50 78HG 5A +5V
LM305H 148 TBA625B 75 to +25V 599
LM309K 135 TBA625B 75 79HG 5A -2-25
LM317K 320 TDA1412 150 to -24V 685p

Z81 16K RAM pack.
16K RAM Pack, Fully built & tested. Plugs straight on to your Z81. Only £16-99

We stock a wide selection of Computer ICs, Printers, Floppy Disc Drives, BBC Micro upgrade Kits, Micro peripherals, Books etc. at very competitive prices.

DENCO COILS RDT2 145p
*DP VALVE TYPE RFC 5 140p
Range 1 to 5 Bl., RFC7(19mH) 160p
Rd., Y. Wht.122p IFT 13; 14; 15; 6-7 B.Y.R. 110p 18; 17; 120p
1-8 Green 150p IFT 18/1-6 135p
T 1 to 5 Bl., Y.I., IFT 19/465 152p
Rd., Wht. 150p TOC 125p
B9A Valve Holder MW/5FR 122p
60p MW/LF 5FR 154p

VEROBOARDS -1'
clad plain
2 1/2 x 3 1/2 80p 65p
2 1/2 x 5 91p
2 1/2 x 3 1/2 91p
2 1/2 x 5 105p 87p
2 1/2 x 1 1/2 360p 32p
2 1/2 x 1 1/2 470p
Pkt. of 100 pins 50p
Spot Face Cutter 135p
Pin Insertion Tool 178p

COPPER clad boards
Fiberglass
6 x 6" 90p
6 x 12" 150p
S.R.B.P.
9.5 x 8" 85p
BY184
VM18 DIL 55

We stock a wide selection of Electronic Books and Magazines

7400 14	74141 55	LS93 23	CMOS	4512 42	LM386 90
7401 11	74142 175	LS95 40	4000 10	4514 115	LM387 120
7402 11	74143 210	LS96 95	4001 10	4515 115	LM389 95
7403 12	74144 210	LS107 40	4002 12	4516 65	LM1458 35
7404 13	74145 50	LS109 23	4006 50	4518 40	LM2917 193
7405 15	74146 70	LS112 40	4007 14	4519 30	LM3900 50
7406 20	74150 50	LS114 22	4008 32	4520 70	LM3901 85
7407 20	74151 40	LS122 36	4009 24		LM3911 125
7408 14	74153 40	LS123 36	4010 24		LM3914 180
7409 14	74154 55	LS124 90	4012 16		LM3915 200
7410 14	74155 40	LS125 24	4013 20		LM3916 220
7411 14	74156 40	LS126 25	4014 46		LM3960 110
7412 18	74157 30	LS132 40	4015 40		MC1304P 260p
7413 18	74159 80	LS133 30	4016 20		MC1488 95
7414 20	74160 60	LS136 24	4017 32		MC1495 95
7415 20	74161 48	LS138 28	4018 45		MC1498 95
7416 20	74162 48	LS139 28	4019 25		MC1499 95
7417 20	74163 48	LS140 28	4020 42		MC1499 95
7418 20	74164 48	LS141 28	4021 40		MC1498 70
7419 20	74165 48	LS153 40	4022 40		MC1498 70
7420 20	74166 48	LS155 30	4023 13		MC1502 90
7421 20	74167 150	LS156 36	4024 32		MC1502 90
7422 20	74170 125	LS157 26	4025 13		MC1502 90
7423 22	74171 75	LS158 30	4026 80		MC1502 90
7424 22	74172 75	LS160 35	4027 20		MC1502 90
7425 22	74173 60	LS161 35	4028 45		MC1502 90
7426 22	74174 54	LS162 35	4029 45		MC1502 90
7427 22	74175 50	LS163 35	4030 15		MC1502 90
7428 22	74176 45	LS164 35	4031 125		MC1502 90
7429 22	74177 45	LS165 60	4032 80		MC1502 90
7430 22	74178 80	LS166 52	4033 125		MC1502 90
7431 22	74179 80	LS167 52	4034 140		MC1502 90
7432 22	74180 40	LS170 70	4035 45		MC1502 90
7433 22	74181 115	LS171 50	4036 275		MC1502 90
7434 22	74182 60	LS174 50	4037 110		MC1502 90
7435 22	74183 95	LS175 40	4038 110		MC1502 90
7436 22	74184 95	LS181 95	4039 290		MC1502 90
7437 22	74185 250	LS183 180	4040 40		MC1502 90
7438 22	74186 80	LS180 36	4041 40		MC1502 90
7439 22	74187 46	LS191 36	4042 40		MC1502 90
7440 22	74188 46	LS192 36	4043 40		MC1502 90
7441 22	74189 46	LS193 36	4044 40		MC1502 90
7442 22	74190 46	LS194 33	4045 45		MC1502 90
7443 22	74191 46	LS195 33	4046 45		MC1502 90
7444 22	74192 46	LS196 33	4047 40		MC1502 90
7445 22	74193 46	LS197 33	4048 40		MC1502 90
7446 22	74194 46	LS198 33	4049 25		MC1502 90
7447 22	74195 46	LS199 33	4050 25		MC1502 90
7448 22	74196 46	LS200 275	4051 45		MC1502 90
7449 22	74197 46	LS201 275	4052 45		MC1502 90
7450 22	74198 46	LS202 36	4053 50		MC1502 90
7451 16	74199 46	LS203 37	4054 50		MC1502 90
7452 16	74200 46	LS204 55	4055 85		MC1502 90
7453 16	74201 46	LS205 13	4056 85		MC1502 90
7454 16	74202 46	LS206 13	4057 85		MC1502 90
7455 16	74203 46	LS207 13	4058 85		MC1502 90
7456 16	74204 46	LS208 13	4059 85		MC1502 90
7457 16	74205 46	LS209 13	4060 85		MC1502 90
7458 16	74206 46	LS210 13	4061 85		MC1502 90
7459 16	74207 46	LS211 13	4062 85		MC1502 90
7460 16	74208 46	LS212 13	4063 85		MC1502 90
7461 16	74209 46	LS213 13	4064 85		MC1502 90
7462 16	74210 46	LS214 13	4065 85		MC1502 90
7463 16	74211 46	LS215 13	4066 85		MC1502 90
7464 16	74212 46	LS216 13	4067 85		MC1502 90
7465 16	74213 46	LS217 13	4068 85		MC1502 90
7466 16	74214 46	LS218 13	4069 85		MC1502 90
7467 16	74215 46	LS219 13	4070 85		MC1502 90
7468 16	74216 46	LS220 13	4071 13		MC1502 90
7469 16	74217 46	LS221 13	4072 13		MC1502 90
7470 16	74218 46	LS222 13	4073 13		MC1502 90
7471 16	74219 46	LS223 13	4074 13		MC1502 90
7472 16	74220 46	LS224 13	4075 13		MC1502 90
7473 16	74221 46	LS225 13	4076 13		MC1502 90
7474 16	74222 46	LS226 13	4077 13		MC1502 90
7475 16	74223 46	LS227 13	4078 13		MC1502 90
7476 16	74224 46	LS228 13	4079 13		MC1502 90
7477 16	74225 46	LS229 13	4080 13		MC1502 90
7478 16	74226 46	LS230 13	4081 13		MC1502 90
7479 16	74227 46	LS231 13	4082 13		MC1502 90
7480 16	74228 46	LS232 13	4083 13		MC1502 90
7481 16	74229 46	LS233 13	4084 13		MC1502 90
7482 16	74230 46	LS234 13	4085 13		MC1502 90
7483 16	74231 46	LS235 13	4086 13		MC1502 90
7484 16	74232 46	LS236 13	4087 13		MC1502 90
7485 16	74233 46	LS237 13	4088 13		MC1502 90
7486 16	74234 46	LS238 13	4089 13		MC1502 90
7487 16	74235 46	LS239 13	4090 13		MC1502 90
7488 16	74236 46	LS240 13	4091 13		MC1502 90
7489 16	74237 46	LS241 13	4092 13		MC1502 90
7490 16	74238 46	LS242 13	4093 13		MC1502 90
7491 16	74239 46	LS243 13	4094 13		MC1502 90
7492 16	74240 46	LS244 13	4095 13		MC1502 90
7493 16	74241 46	LS245 13	4096 13		MC1502 90
7494 16	74242 46	LS246 13	4097 13		MC1502 90
7495 16	74243 46	LS247 13	4098 13		MC1502 90
7496 16	74244 46	LS248 13	4099 13		MC1502 90
7497 16	74245 46	LS249 13	4100 13		MC1502 90
7498 16	74246 46	LS250 13	4101 13		MC1502 90
7499 16	74247 46	LS251 13	4102 13		MC1502 90
7500 16	74248 46	LS252 13	4103 13		MC1502 90

TEACH-IN 81 all parts available.

POTENTIOMETERS (ROTARY)
Carbon Track. 0-25V Log & 0-5V Linear
600Ω, 1K & 2K (Lin. only) Single 30p
5K-2 MΩ single gang 30p
5

Everyday ELECTRONICS

VOL. 11 NO. 9 SEPTEMBER 1982

Editor

F. E. BENNETT

Assistant Editor

B. W. TERRELL B.Sc.

Production and News Editor

D. G. BARRINGTON

Projects Editor

G. P. HODGSON

Art Editor

R. F. PALMER

Assistant Art Editor

P. A. LOATES

Technical Illustrator

D. J. GOODING Tech. (CEI)

Secretary

JACQUELINE DOIDGE

Editorial Offices

KINGS REACH TOWER

STAMFORD STREET

LONDON SE1 9LS

Phone: 01-261 6873

Advertisement Manager

R. SMITH

Phone: 01-261 6671

Representative

R. WILLET

Phone: 01-261 6865

Classified Supervisor

B. BLAKE

Phone: 01-261 5897

Make-Up and Copy Department

Phone: 01-261 6615

Advertisement Offices

KINGS REACH TOWER

STAMFORD STREET

LONDON SE1 9LS

THE YOUNG GENERATION

Electronics casts its spell at an early age and younger members of our society are readily attracted to this technology. Whilst at school many children become actively involved in experimenting and building projects to meet actual needs or perhaps just to satisfy inquisitive minds.

If given but a modicum of encouragement by members of teaching staff, this youthful enthusiasm is likely to be self-sustained throughout the final and formative years at school. Even more fortunate are those children who have a teacher with a similar interest in electronics. With such a mentor to guide and advise them in these (usually extra-curricular) activities, young minds will develop their appetite for electronics in the best and most logical manner.

Schools, themselves, can gain materially from the practical work of their electronically inclined pupils, a fact most clearly demonstrated by the Schools Electronic Design Award Competition (SEDAC), sponsored by Mullard Ltd and this magazine. The culmination of this competition was the presentation of prizes by the Parliamentary Under-Secretary of State, Department of Education and Science. The Minister praised the endeavours and inventiveness of the young entrants and the excellence of their working models: he was particularly pleased by the practical aspect of the competition and welcomed this encouragement of interest in electronics and computers amongst the young. The Minister voiced one regret: that was concerning the absence of girls amongst the finalists. We agree with him that this cannot be because of lack of interest in electronics among schoolgirls—our own evidence points to the contrary. So come on girls, don't let the fellows get away with it at next year's SEDAC.

The success of our first national schools competition has been well noted. We are delighted to announce that Mullard Ltd have agreed to join us in sponsorship of a second Schools Competition, to be launched this autumn. Full details will appear in next months EVERYDAY ELECTRONICS.

NEW SEASON IS A'COMING

October is always a notable month on account of the renewed activity amongst constructors after a summer lull. It is also the optimum time for newcomers to make a start in this stimulating and useful leisure pursuit.

Next month we will give a pair of transistors with every copy and inside will be suitable designs for their use. For those hovering on the edge there's encouragement to take the plunge in the first of a six-part series, *Introducing Electronics*.

Finally, to something over which we have little control. Economic facts of life make it necessary for the price of EVERYDAY ELECTRONICS to be increased to 80p as from next month. But it will be well worth every penny.



Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price 80p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.


Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.

Subscriptions

Annual subscription for delivery direct to any address in the UK: £11.00. Overseas: £12.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, Kings Reach Tower, Stamford Street, London SE1 9LS.

SOUND SPLITTER

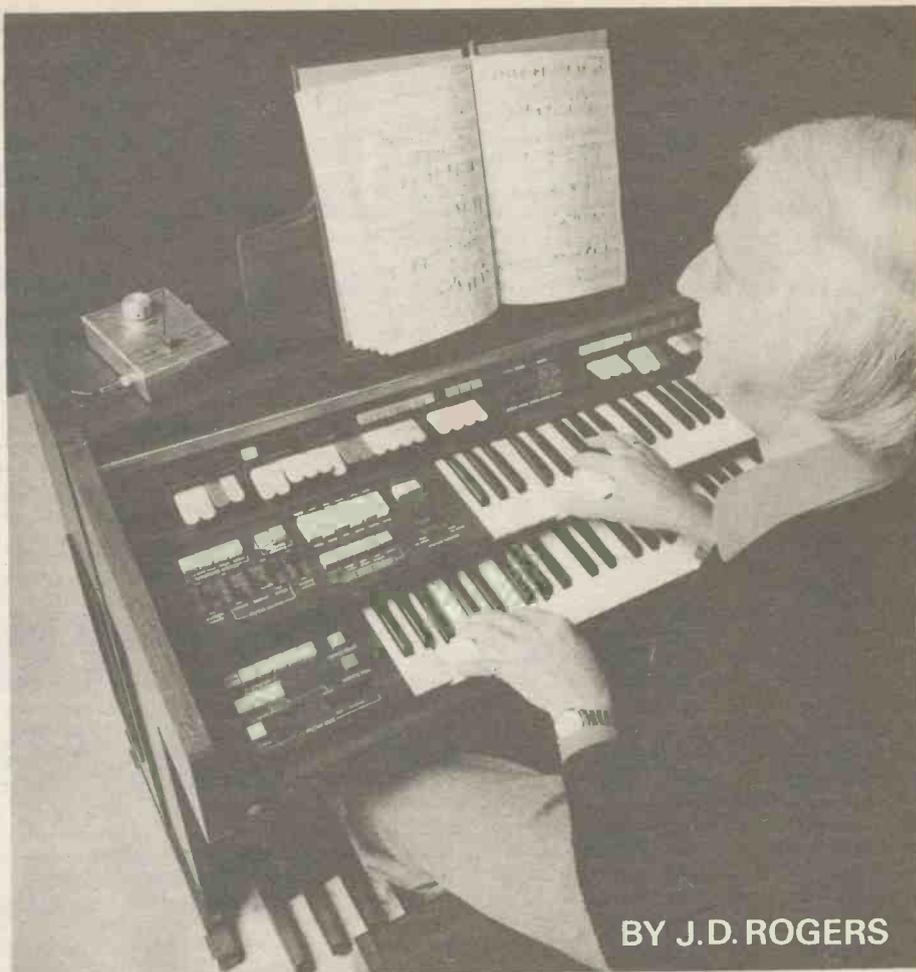

BY J. D. ROGERS

CIRCUITS to give a stereo simulation from a mono input have been published before but these are normally for hi fi use and are not suitable for the musician. It might also be said that a "stereo" splitter would be of little value to the average musician with only one amplifier. In this unit however, the stereo splitter circuitry is modified so as to be useful with even a small, single input amplifier.

The unit combines an improved pseudo-stereo effect with two other useful functions, described later, to give a device which has a wide range of applications.

The unit is simple to use and easy to construct, no test equipment is needed and no setting up or adjustments are required. The circuit contains only two i.c.s, both common types, there are no unusual components and it uses a standard size Veroboard and ready made case.

To describe the unit itself and describe its applications it is best to consider both of these together, and this is done later, under a separate heading for each of the three modes of operation. These modes are

selected by a small toggle switch on the side of the unit and are: SWITCHER MODE, FREQUENCY SPLIT MODE and CROSSMIX MODE. Regardless of which of these modes is set, selecting NORMAL on the footswitch will always give a "straight" signal at the main output.

All effect/normal signal routing is performed by electronic (f.e.t.) switches, as this is superior to normal switching and does away with the need to use a d.p.d.t. footswitch. A wider choice of footswitch is made available since a s.p.s.t. or indeed any type of footswitch can be used, and yet always give smooth and reliable switching. This is because the footswitch itself only has to carry a d.c. command voltage while the actual audio signal switching takes place on the circuit board.

CIRCUIT OPERATION

The circuit diagram for the Sound Splitter is shown in Fig. 1.

Although the circuit uses six op-amps, these are contained in just two packages, IC1 and IC2 one dual and one quad. IC1a acts as a input buffer and a preamplifier. At its input is a network which adds a treble pre-emphasis.

When footswitch S1 is set to NORMAL (contacts open) a negative voltage is fed to the gates of the two f.e.t.s. (TR1, TR2) and this switches them both off. IC1b therefore has only R11 in its negative feedback loop and so it acts simply as a unity gain inverting amplifier stage.

Its signal passes via R17 to the output (TR2 has no effect as it is off) where C9 and R19 form a treble cut (de-emphasis) filter to cancel out the effect of the pre-emphasis that was added at the input. This restores a virtually flat response overall and the net result is noise (hiss) reduction, since any noise arising from any source within the unit is reduced by being attenuated at the last possible point, the output. The circuitry is low noise anyway, but this gives a further improvement.

EFFECT SWITCHING

Now consider the same parts of the circuit when EFFECT is selected. Now S1 is closed so the voltage sent to the f.e.t. gates is positive, which switches them both on. IC1c and d form two bandpass filters and so will only pass certain sections of the audio spectrum, in this case centred at

Front cover: courtesy Bert Kempster, Riverside Organ Studios Ltd, Crawley.

approximately 300Hz and 3kHz. These bands are now added (via TR1, now on) to IC1b where, being in antiphase to the main signal (via R10), they cancel out parts of the response. The output of IC1b therefore becomes notched.

C7 is also brought into circuit when TR1 comes on, increasing the negative feedback around IC1b so reducing the gain, but only at high frequencies. The result is that frequency response above 7kHz is removed. Fig. 3a shows the final response.

COMPENSATION

Since three bands have now been removed from the response, a noticeable drop in overall sound level would be heard upon switching between NORMAL and EFFECT, so TR2 has been included to compensate for this by bringing R16 into circuit whenever EFFECT is selected. This gives a general level boost and also reduces the treble de-emphasis at the output, so even though response around 3kHz and above 7kHz has been removed, the overall "brightness" is preserved. The final result is a unique change of timbre without any volume loss.

The other, more important, reason for including TR2 is to ensure that when NORMAL is selected the main output is isolated from the other channel crossmix network (C10, C11, R26).

So much for the main signal path, now consider the secondary channel, which consists of IC2a and b and associated components. Normally the signal from the preamp (via R20) plus an identical but inverted signal from IC1b (via R21) are fed to IC2b and these cancel to give zero output.

When EFFECT is selected however, parts of the main signal are removed, as described earlier, and where this takes place the two inputs to IC2b can no longer cancel out and so there is now an output at these frequencies, that is around 300Hz, 3kHz and above 7kHz. See Fig. 2b.

This can be summarised as "whatever is removed from the main channel appears in the secondary channel".

The secondary path continues to IC2a, which, with VR1 forms a centre zero volume and phase control. When VR1 is at zero resistance IC2a is an inverting amp; when VR1 is at full resistance IC2a is a non-inverting


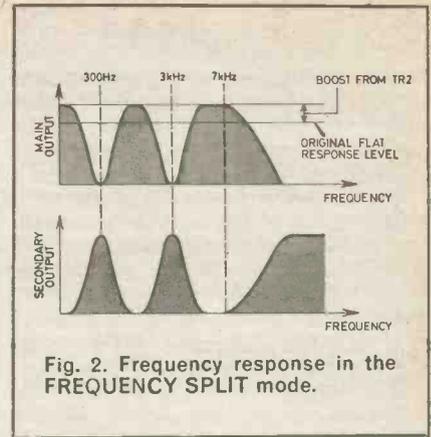


Fig. 2. Frequency response in the FREQUENCY SPLIT mode.

amp; when VR1 is at 10kΩ resistance then there is no output at all since IC2a is equally inverting and non-inverting.

Finally, the signal is fed via C10, C11, R26, R27 to the secondary output jack SK3. R26, C10, C11 only have effect when CROSSMIX mode is selected. C11 is included so as not to lose, in crossmixing mode, the feature whereby a second amp does not have to handle low frequencies. It forms a highpass filter with R26 whenever

Fig. 1. The complete circuit diagram of the Sound Splitter.

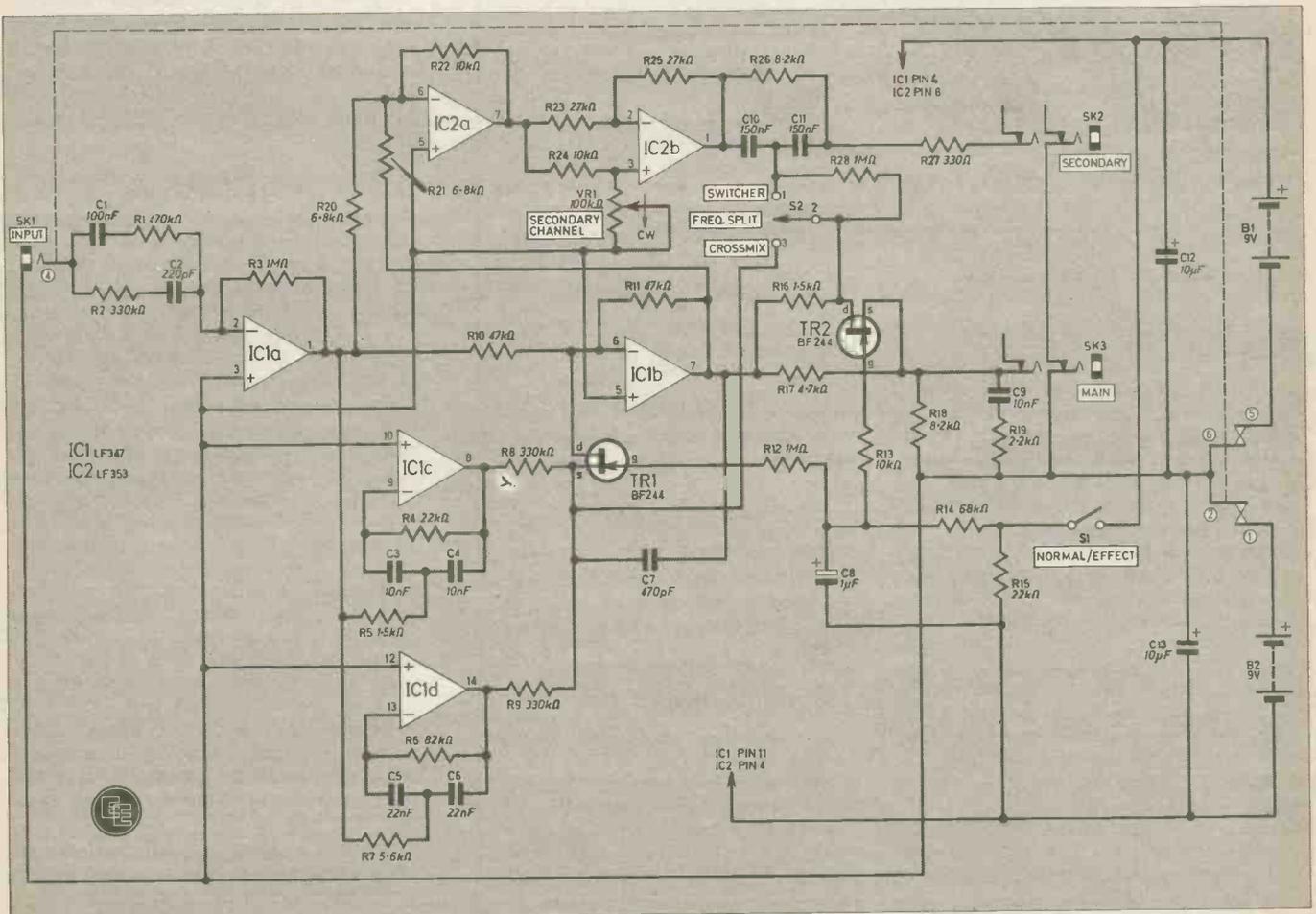

CROSSMIX mode is selected thus preventing bass signals from the main output getting into the secondary output. R27 is included to isolate the output of the op-amp from cable capacitance which could otherwise cause instability.

R28 is placed across S2 to prevent switch clicks by equalising any small d.c. offsets that could otherwise accumulate, but it is of sufficiently large value as to have negligible effect on the actual audio signals.

SWITCHER MODE

In SWITCHER mode pressing the footswitch routes the signal alternately to the two outputs (MAIN and SECONDARY). SWITCHER mode allows better use to be made of any amp with two or more inputs or channels, that is most amps. Each channel can be set up for a different sound and then selected remotely and instantly by the footswitch. It also allows any

other effects unit (or combinations of effects units), placed in either the main or the secondary path(s) to be switched, see Fig. 3b and c.

So as to allow improvement of other effects units, the level of the secondary output has been made variable, by means of VR1. Designers of effects circuits can only have an average input level in mind, so it is likely that any real instrument output is either too low (so you don't get the best signal-to-noise ratio from the effect) or too high (so it overloads). This control allows the "drive level" to any effect unit to be boosted (up to $\times 3$) or reduced compared to the instruments original level. To find the best level, turn the control until maximum output is obtained without distortion occurring.

If you do not have two inputs on your amp, then the simple and inexpensive "Two-way Remixer" box (described later) can be used instead.

This accepts any two inputs and combines them into one output.

SPLIT MODE

When set to NORMAL, there is a "straight" signal from the MAIN output, but upon pressing the footswitch certain bands of frequencies are removed from it, thus altering the response.

To keep the overall volume constant a general boost is automatically applied, enough to make up for the removed bands. So, just by using the MAIN output on its own, this mode provides a footswitchable tonal change effect, from normal to a lighter, coloured, sound not possible using normal tone controls. See Fig. 3a.

The missing bands of frequencies are not lost, but are transferred to the previously "dead" SECONDARY output. All of the audio frequency spectrum is therefore still passed but is split into two complementary outputs, whatever is absent from one will be present in the other, see Fig. 2.

Having generated these two outputs, what to do with them is up to the user, but some tried suggestions are:

(1) To a simple passive remixer (see Fig. 7). This then allows you pan between two entirely opposite tonal responses. The relative volumes of these can be balanced by using VR1 to preset the level of the secondary output.

(2) To two channels of the same amp. Each channel now handles different parts of the signal, so tone controls and any built-in effects (such as reverb or tremolo) can be applied to some frequencies and not to others, with some unusual results. The footswitch can be used to return to normal single channel operation of the amp at any time.


(3) To two separate amps (or to two sides of a P.A. system). This produces a pseudo-stereo effect which gives a spatial enhancement or "spread" of the sound.

Two useful features are that (i) it is possible to use a much smaller amp/speaker for the secondary channel since its output signal consists only of certain bands of the audio spectrum, the lowest of which is centred around 300Hz, so there is no deep bass present which would require a more substantial amp/speaker to handle it. And (ii) the second amp can be positioned any distance away and its volume conveniently "remote controlled" by VR1 on this unit. See Fig. 3f.


(4) One output via effects unit(s), the other straight. Then as in (1), (2) or (3) above.

(5) Both outputs via effects unit(s). Then as (1), (2) or (3) above.

Fig. 3. A few applications of the Sound Splitter from the simple to the more complex. Set the footswitch to EFFECT for the stated effect in each case.

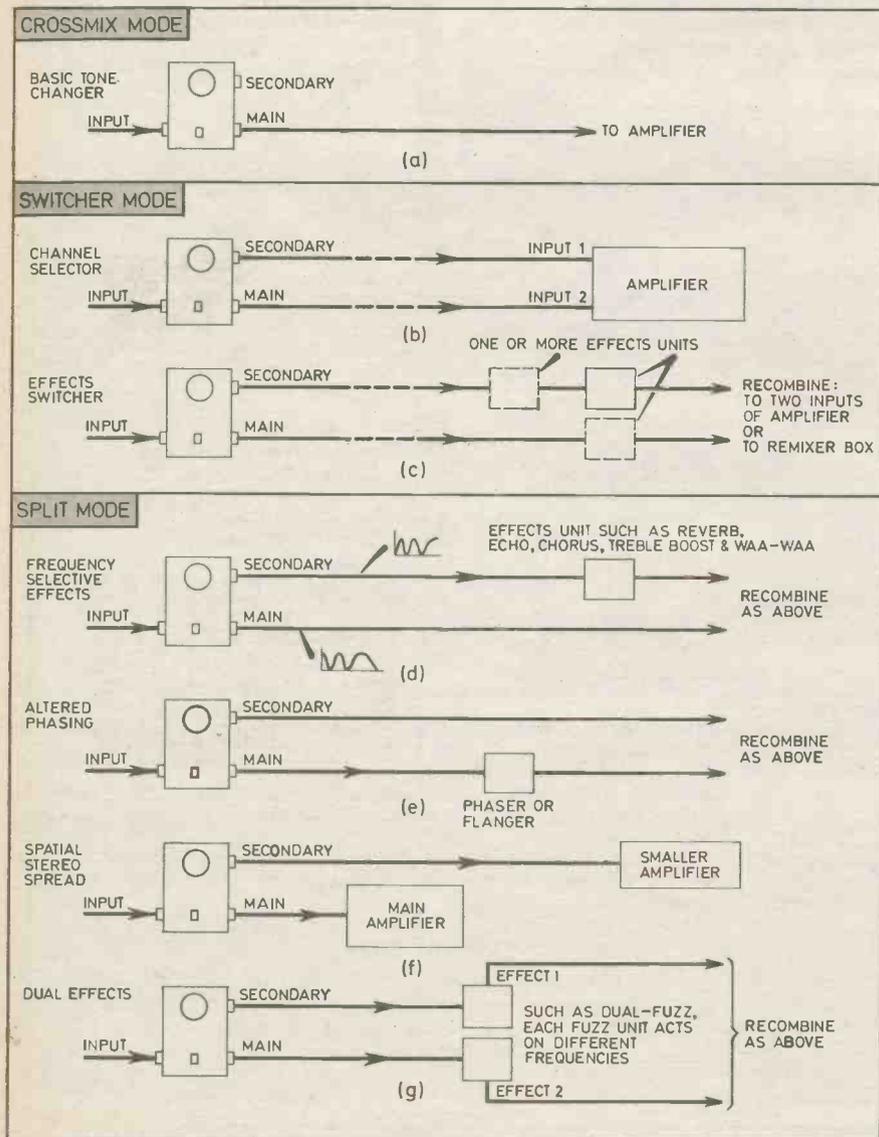

CONSTRUCTION starts here

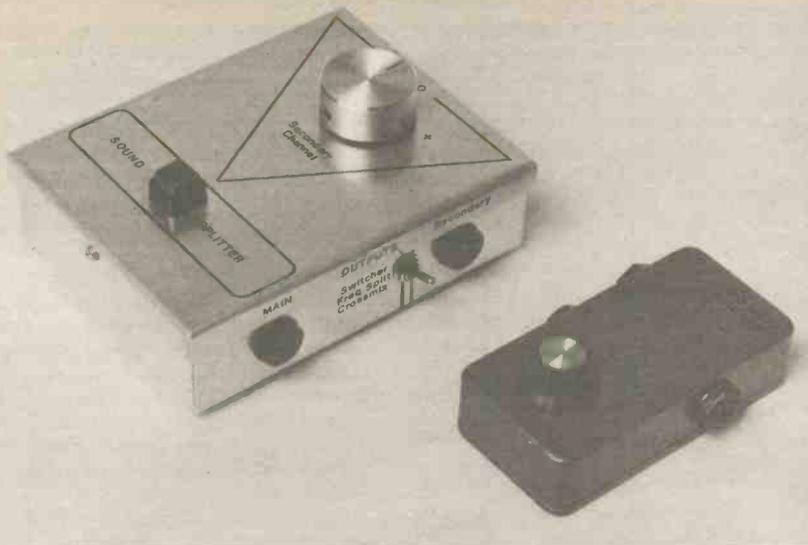

Prototype Sound Splitter and Two-Way Remixer,

COMPONENT ASSEMBLY

Construction is straightforward, but is most convenient if carried out in a certain order. If you follow the stage-by-stage instructions given here, and tick off each part as you proceed it will ensure that everything gets done with the least possible effort and that nothing is forgotten.

The majority of the components are mounted on a piece of 0.1 inch

With the latter two methods, novel variations on existing effects are possible by feeding the effect with certain frequencies only and allowing the others to bypass it or even to go via another effects unit. Here then are hundreds of possibilities to be explored, just a few examples are given in Figs. 3d, e and g.

All of the effects using the frequency split mode have been found to sound better or worse depending on the relative phases of the final signals appearing at the speaker(s). There is no way of predicting whether a signal via any particular route will end up being inverted as this depends on many stages in the circuits within the amp(s) and any effects unit(s) used, as well as on which way the speakers are wired.

To take all possible situations into account, the Sound Splitter SECONDARY output has been given the facility whereby it can be of either phase relative to the other output. It is controlled by VR1, which has a centre zero arrangement. Volume increases towards either side of centre but the phase of the output is different depending on whether it is in the +ve or the -ve half of its rotation, as marked on the panel.

CROSSMIX MODE

In the CROSSMIX mode there is normally "straight" signal from the main output and upon pressing the footswitch the frequency splitting as described above occurs, but in this mode the two channels are internally cross-mixed in such a way as to produce new tonal colours.

These are available from either one of the outputs and can be varied by using VR1 to alter the percentage of the mix coming from the secondary channel. In this mode then, VR1 effectively becomes an unusual tone control.

COMPONENTS

Resistors

R1	470kΩ	R15	22kΩ
R2	380kΩ	R16	1.5kΩ
R3	1MΩ	R17	4.7kΩ
R4	22kΩ	R18	8.2kΩ
R5	1.5kΩ	R19	2.2kΩ
R6	82kΩ	R20	6.8kΩ
R7	5.6kΩ	R21	6.8kΩ
R8	330kΩ	R22	10kΩ
R9	330kΩ	R23	27kΩ
R10	47kΩ	R24	10kΩ
R11	47kΩ	R25	27kΩ
R12	1MΩ	R26	8.2kΩ
R13	10kΩ	R27	330Ω
R14	68kΩ	R28	1MΩ

All ½ watt carbon film ±5%

Capacitors

C1	100nF polyester type C280	C8	1μF 25V elect.
C2	220pF polystyrene	C9	10nF polyester type C280
C3	10nF polyester type C280	C10	150nF polyester type C280
C4	10nF polyester type C280	C11	150nF polyester type C280
C5	22nF polyester type C280	C12	10μF 10V tantalum
C6	22nF polyester type C280	C13	10μF 10V tantalum
C7	470pF polystyrene		

Semiconductors

TR1, 2	BF244 n-channel f.e.t. (2-off)
IC1	LF347 quad j.f.e.t. op-amp
IC2	LF353 dual j.f.e.t. op-amp

Miscellaneous

VR1	100kΩ carbon log. potentiometer
S1	s.p.s.t. footswitch
S2	s.p.d.t. centre-off miniature toggle
SK1	stereo jack socket with d.p.d.t. switched contacts (Tandy 274-277)
SK2, SK3	standard jack socket with break contacts (2 off)
B1, B2	PP3 9V battery (2 off)

Stripboard: 0.1 inch matrix size 24 strips × 37 holes; aluminium case with lid size 125 × 100 × 40mm; control knob with index marker; PP3 battery clips (2 pairs); Veromounts.

Two-Way Remixer

R1, R2	150kΩ ½W carbon (2-off)
VR1	47kΩ carbon linear potentiometer
SK1, 3	standard jack socket (2-off)
SK2	standard jack socket with break contacts
Case: 100	× 50 × 25mm enamel finish aluminium diecast box (Maplin DCM5002).

See
**Shop
Talk**

page 567

COMPONENTS
approximate
cost **£12**
Remixer **£3.50**

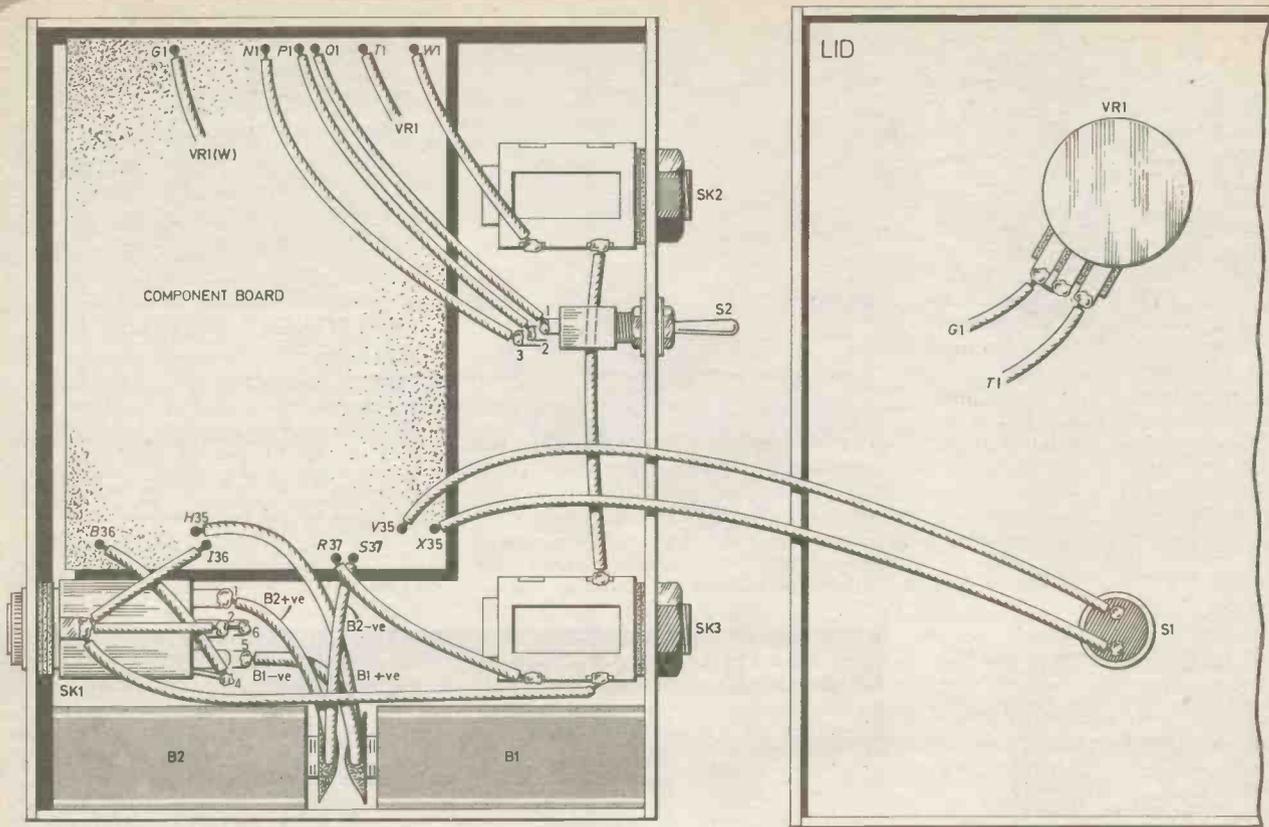


Fig. 5. Complete interwiring details.

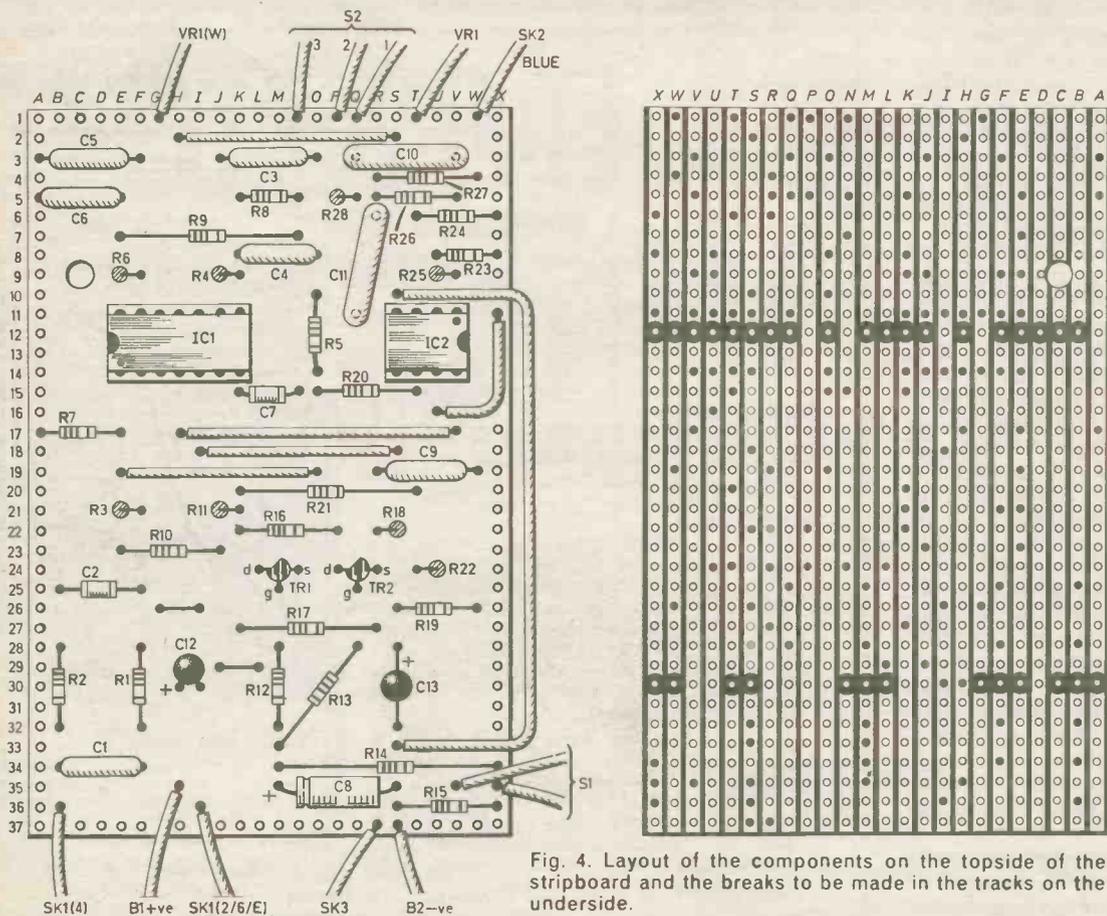


Fig. 4. Layout of the components on the topside of the stripboard and the breaks to be made in the tracks on the underside.

Veroboard size 24 strips \times 37 holes as shown in Fig. 4. Cut the board to size and then make all the necessary breaks in the copper tracks using a spot face cutter or a small drill bit (about 3mm diameter). Drill the board fixing hole where shown in Fig. 4. The other three corners of the board should be supported by pieces of plastic foam stuck to the bottom of the case. In fact, separated Veromounts are ideal for this, just stick squares of either type of the velcro material where the three other corners of the board will rest.

By having just one bolt point and three resilient mounts the board is well anchored and is insulated from the metal case but is not held too rigidly, so accidental knocks to the case are less likely to be transmitted through and damage the board.

CIRCUIT BOARD

Begin board construction by soldering in all of the flat-lying resistors, then the 220pF and 470pF capacitors.

Solder in the six larger of the links. Use insulated wire for these so as to prevent any shorts should the links flex and touch other components.

Solder in the two smaller links, using bare wire.

Insert and solder in the two i.c. sockets, then the eight vertically mounted resistors and finally the rest of the capacitors. Next solder sufficient lengths of insulated stranded wire to the board to reach the appropriate case mounted components.

Position and solder in place the two transistors and then insert the i.c.s into their sockets, carefully checking their orientation.

CASE DETAILS

Drill out holes in the case, for the footswitch, the potentiometer, the toggle switch and the three jack sockets, following the dimensions given in Fig. 6 (unless of course a different case is used). A small hole is also required in the bottom of the case to put a small bolt through to hold the circuit board in place. The two jack sockets at the lower end have been placed so as to act as battery retainers. A strip of plastic foam across the bottom can be added to keep the batteries firmly in place.

Clean the case before proceeding to letter it. Letraset or similar rub-down transfers will give a professional finish. Either the panel design shown on the prototype can be followed or the constructor can make up a design to suit himself.

Fix the lettering for protection with a clear varnish. Letraset 101 aerosol is most convenient and gives a tough enough finish. When the varnish has

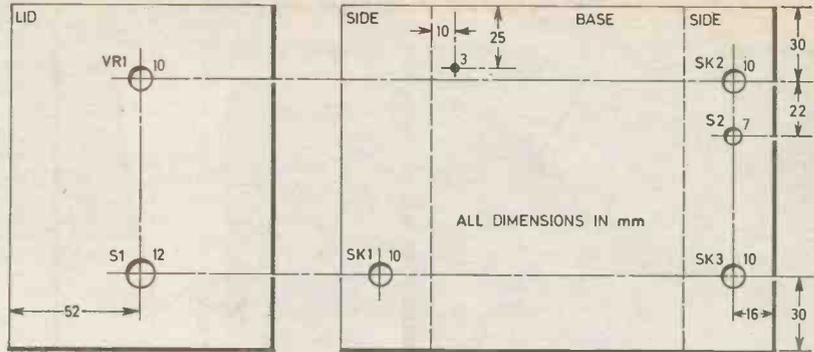


Fig. 6. Case drilling details.

dried, mount the sockets, potentiometer and two switches. Put four stick-on rubber feet on the case underside. See Fig. 5.

Interwire just the case mounted components, as shown, using the usual multi-strand hook-up wire, neatly routing all leads around the bottom of the case out of the way. Next interwire the circuit board to the case mounted components, keeping the wiring neat as before. After checking all connections, bolt the board into the case.

REMIXER BOX

Apart from its intended use with the Sound Splitter, the remixer box is a generally useful unit to have around, and being purely passive it needs no batteries.

The circuit for the Two-Way Remixer is shown in Fig. 7. The two

input signals to A and B are "mixed" across VR2, the amount of each appearing at the output depending on the resistance between VR2 wiper and the input socket. With the wiper in its mid-position, the output contains equal amounts of signals at A and B.

The two 150k Ω resistors R1 and R2 ensure that there is always a d.c. reference path for any connection to the box, these resistors are placed prior to the potentiometer VR2 where they do not cause unnecessary reduction of the signals.

Construction is very simple, any metal box can be used as long as it is big enough to contain three plastic jack sockets and a potentiometer, see Fig. 8.

A Maplin type DCM5002 diecast box was used for the prototype. The jack sockets had to have their con-


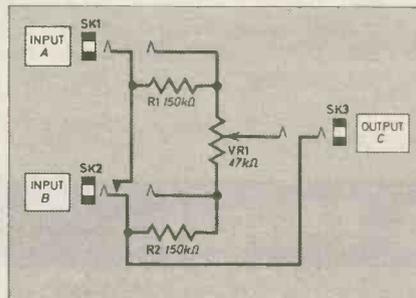


Fig. 7. Circuit diagram for the Two-Way Remixer.

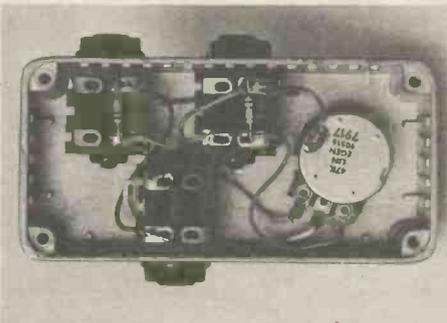

Interior view of the completed prototype Remixer.


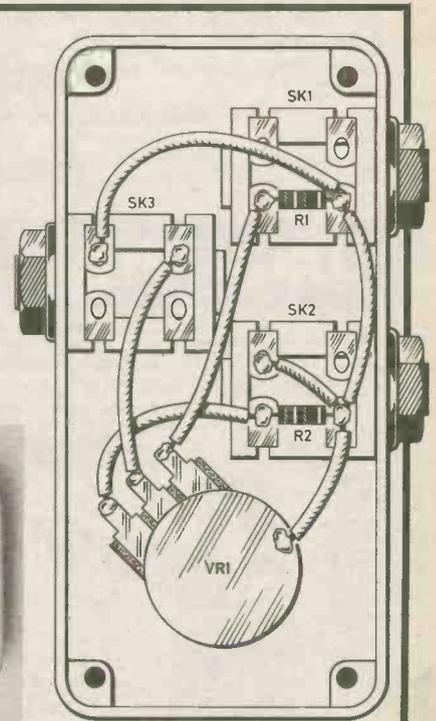
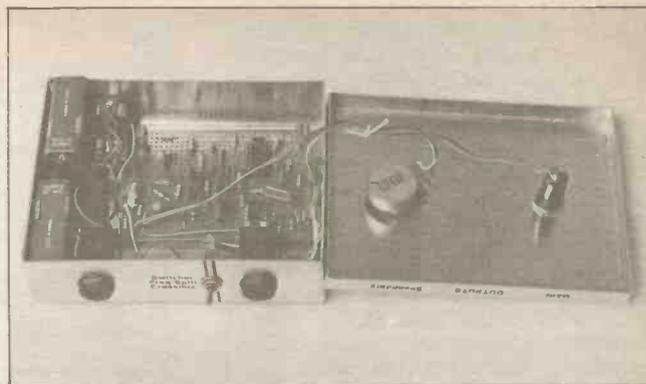


Fig. 8. Layout and wiring of the Remixer components in the diecast aluminium box.

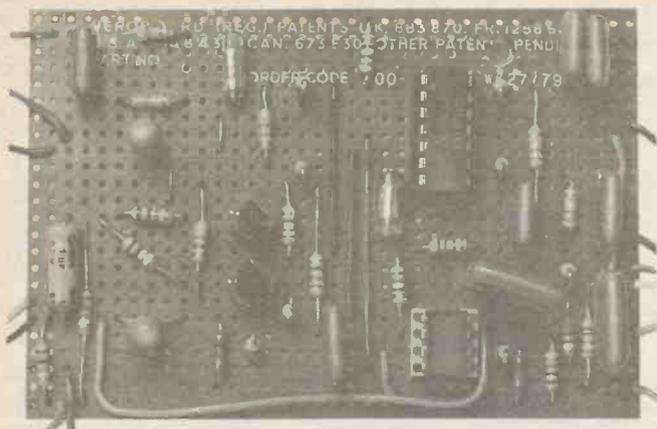

The completed Sound Splitter unit with lid removed showing batteries in position.

Left. Close-up view of the Sound Splitter component board.

tacts folded down flat to fit into this particular box and a few strips of insulation tape were stuck on the inside of the case lid to prevent the contacts shorting to the metal case.

The earth contacts of the three sockets are wired together and, since they are all plastic types, the metal case must be earthed via the potentiometer, by soldering an "earth lead" to the back of its case.

When there is no jack inserted in B then the unit is still usable simply as a volume control for the A input, because the B input is automatically earthed by the normally closed contact on the socket itself.

EARTHING CONSIDERATIONS

Problems can occur whenever two separate signal paths are in use from a common source, because of the formation of earth loops, which invariably give rise to unacceptable mains hum.

However, these situations are auto-

matically prevented in the Splitter by means of a break contact on the main output jack SK2 which, when a plug is inserted, disconnects the earth to the secondary output jack. So, whenever both outputs are in use, only the lead from the main output will be directly earthed (the other lead will still be earthed, but from the "other end" via the amp.).

If only the secondary output is being used, then its earth will remain connected, thus all situations are catered for.

CONCLUSION

The unit will accept an input from any instrument or other audio source, and the input jack switches on the batteries when a plug is inserted. Battery drain is low (about 10mA) so two PP3 batteries should last a long time.

The Sound Splitter is an effects unit in its own right, and of course can be used as such, however, its


real versatility lies in the many interesting ways in which it can be used in conjunction with any other effects unit and the Two-Way Remixer. Used in this way it can help in the musicians constant search for different sounds by squeezing a few more variations out of existing types of effects.


As mentioned earlier there are so many combinations possible, simple and complex, that it is pointless to try and list them here, it is really up to the user to discover uses to suit his own equipment, taste and style of playing.

Finally, for anyone who wishes to experiment with further effects, a useful control to add is a 47kΩ log. potentiometer connected between the "capacitor ends" of R5 and R7. This allows the peaks of both the band pass filters in the unit to be swept to different frequencies, eventually forming into a single peak when the potentiometer is at zero ohms. ✧

JACK PLUG & FAMILY...

BY DOUG BAKER

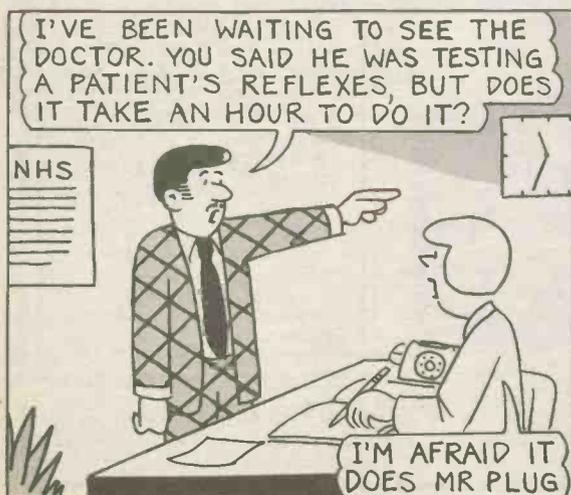

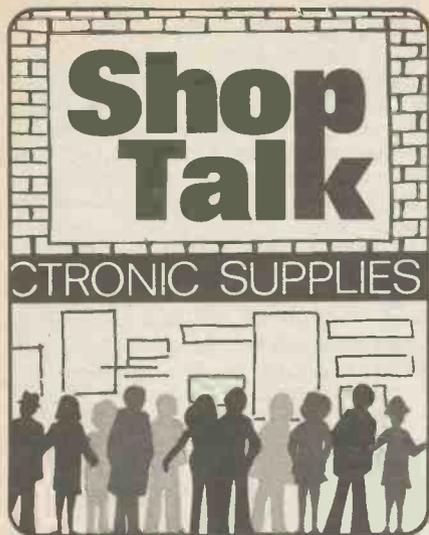

By Dave Barrington

Mastering PCBs

Making printed circuit boards is a highly skilled profession and an art. So any news of a product that makes it easier for the non-professional to produce boards of a high quality is most welcome.

One such system is the new CM100 Circuit Maker kit from Electrolube. Due to space considerations, it is not possible to evaluate the kit from a "hands-on" viewpoint but the problems of making p.c.b.s will be the subject that we will return to at a later date.

The kit provides all the necessary hardware and chemicals to produce positive photographic film masters from published layout diagrams and a final definitive circuit board.

The kit can be broken down into two groups or packs consisting of equipment and chemicals for making the film positive masters and one for making the final printed circuit board. Amongst the film processing equipment is a photoflood bulb used for activating the sensitised film when placed over the published master diagram.

We like the idea of a special "jig" which can be used as an exposure frame for the photographic part of the process, as well as a component assembly frame. A foam-backed plate, which forms part of the frame, is ideal for holding components in place whilst any excess leads protruding on the underside of the board can be trimmed prior to soldering. It is also claimed that the foam backing is heat-resistant which allows the components to be held firmly during the soldering operation.

It is obvious that a great deal of thought and attention to detail has gone into making the CM100 kit as extensive as possible. As well as containing six double-sided copper-clad fibreglass circuit boards (no single-sided!), plus such items as rubber gloves, retouching pen, photographic dishes, thermometer, etchant and drills, there are workbench charts and an instruction manual.

Selling for about £70, first impressions would seem to indicate that the kit is rather an expensive outlay, but when weighed against the cost of purchasing finished boards it appears to be a reasonable investment.

For more details of prices and local

stockists of the CM100 Circuit Maker contact Electrolube Ltd., at Dept EE, Blakes Road, Wargrave, Berks, RG108AW.

Catalogues Received

A new 21-page components catalogue has just been received from Rapid Electronics. The Autumn '82 Catalogue includes a wider range of Linear devices, plus data sheets, an extended range of capacitors and p.c.b. mounting transformers.

Copies of the Rapid Components Catalogue can be obtained by sending 45p to Rapid Electronics, Hill Farm Industrial Estate, Boxted, Colchester, Essex, CO4 5RD. The catalogue will be sent free to customers who place orders for goods totalling over £10.

A Shortform catalogue just published by Keyswitch Varley contains abbreviated data on their range of relays, solenoids, controllers, timers and switches.

New products described in the 12-page catalogue include a range of 1-, 2-, 3- and 4-pole reed relays, 30A power relays and a solid state relay. Recent additions are a range of DIP slide switches and a double wound solenoid with integral solid state switch.

Copies of the Shortform catalogue are available from Keyswitch Varley Ltd., Dept EE, Tom Cribb Road, Thamesmead, London SE28 0BH.



The CM100 Circuit Maker from Electrolube

Booklet

A 20-page pocket guide entitled "The 100 Most Asked Questions and Answers" has just been released by the Ferguson Video Advisory Service to show the capability of the Videostar range.

Aimed at both the customer and trade staff, the booklet covers all aspects of their video equipment and accessory range, plus a section devoted to cross compatibility with other makes. It also contains some general information on lighting, sound recording and connecting leads.

Copies of the booklet are available free from Thorn EMI Ferguson Ltd., Dept EE, Cambridge House, Great Cambridge Road, Enfield, Middlesex, EN1 1UL. A stamped addressed envelope would be appreciated.

Public Address Amplifier

We have been informed that all semi-conductors used in the P.A. amplifier (May/Aug) can be supplied by Hart Electronic Kits, Pennyland Mill, Oswestry, Shropshire.

CONSTRUCTIONAL PROJECTS

Monthly Planner

A source of supply for the 1-bit clock timer, IC1, which forms the heart of the

Monthly Planner project has proved the most difficult item to locate.

The E 050-16 clock chip is not normally available in the UK but the author, Mr Donleavy has made special arrangements with the Swiss manufacturers to supply them to E.E. readers.

The E 050-16 costs £6.50 and the crystal 90p from A. P. Donleavy, 13 Wasdale Road, Liverpool 9. Add 20p postage and packing for all orders.

The clock chip is available separately, but the crystal can only be supplied together with the E 050-16 device. However, other crystals can be used in the circuit.

The rest of the semiconductor devices should be available from Ambit, Enfield, Electrovalue, Magenta and Watford Electronics.

The miniature keyboard push switches are now generally available and is left to individual choice on the type of switch used here.

Continuity Tester

Practically any of the low-voltage piezoelectric transducers, available from most of our advertisers, should be suitable for the Continuity Tester. The device used in our model was the PB2720 (with case) obtainable from Ambit.

The size of plastics case is not critical and any type may be used.

Screen Washer Delay

The relay used in the Screen Washer Delay is a low-profile encapsulated type with a 1000 ohm coil. This is a RS encapsulated reed relay and is coded Blue, stock number 348-986. Any RS component supplier will be able to obtain this item.

Note that the casing of capacitor C1 must be completely isolated from any metal when installed in a vehicle. This can be accomplished by wrapping in insulating tape or rolled in a strip of polythene sheet.

Temperature Interface for TRS-80

A couple of special i.c.s are required for the TRS-80 Interface project. The LM334Z, adjustable current source used as a remote temperature sensor, is available from Maplin Electronic Supplies; order No. WQ32K. The TL507C, single slope analogue to digital converter, may be obtained from most Tandy shops; stock No. 276-1789.

The printed circuit board has been designed to accommodate a specific RS transformer, stock No. 207-829. This transformer is available through any RS component dealer. Other suitably rated transformers may be fitted to the case and wired to the appropriate p.c.b. locations.

The double-sided (20 + 20 way) wire-wrap edge connector may prove difficult to locate and may need to be cut from a larger version. One such item is the 2 x 22-way strip from Watford Electronics which will allow alignment guides to be fitted.

Sound Splitter


There should be no component buying problems for the Sound Splitter or the add-on mixer unit.

A suitable jack socket for SK1 is the "stereo phone jack" from Tandy stores, stock number 274-277.

On its own, a useful application for the Two-Way Remixer box is to couple two instruments to a single input amplifier.

CB BATTERY CHARGER

BY A. FLIND

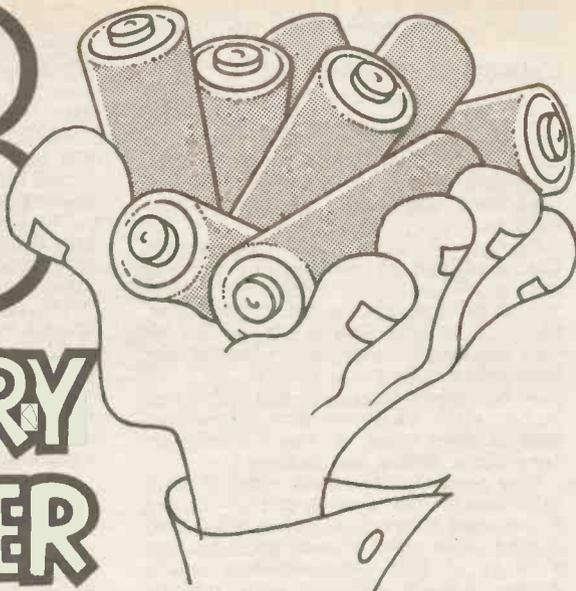

SINCE the long-awaited advent of legal CB radio, several types of 40-Channel hand-held portable rigs have become available and are growing increasingly popular. Most of these use HP7 type batteries, but with a current drain of 0.5A or more when transmitting, the cost of ordinary dry batteries quickly leads most users to invest in a set of rechargeable ni-cads.

The problem of supplying a suitable charger for these arises. Commercial chargers often cost as much as the batteries themselves and few incorporate any kind of automatic "full-charge" sensing feature. The

charger described here is the author's answer to this problem, at around half the cost of most units.

It provides fully automatic, trouble-free performance and is simple to construct. It was designed to charge the complement of ten AA sized (HP7) ni-cads in the Harvard 410T rig, however, the Dixons' Harrier WT2 40-channel handheld appears to be identical to the Harvard, and the Tandy Realistic 1001 also uses the same battery complement. Possibly other portables such as the DNT and Alba are similarly powered, so this charger design may prove useful to many readers.

RECHARGEABLE NI-CADS

A few facts about the ni-cad cells themselves may be of interest before continuing. Most readers will probably be aware that these are available as direct replacements for the common sizes of 1.5V dry cell, and that they can be recharged up to 1,000 times.

In general they should be charged by a constant current, the value of which is normally quoted as being about a tenth of the cell's capacity in ampere-hours (Ah). The AA size has a capacity of 0.5 Ah so the charge rate should be around 50mA. It is also stated that they cannot be damaged by long term continuous overcharging at this rate, however, it cannot be seen to do them much good either.


Since the cell voltage rises quite steeply when the fully charged condition is reached, it is a fairly simple matter to detect this and reduce the charge rate accordingly. An advantage of this type of charger is that the battery can be connected at any time for "topping-up", regardless of its initial state of charge.

It is unwise to let batteries of ni-cad cells become completely exhausted as one cell will inevitably run down before the others, which then "reverse-charge" the flat cell and cause permanent damage to it. So topping-up whenever the equipment is not in use will greatly reduce the risk of this occurring.

CIRCUIT DESCRIPTION

Fig. 1 shows the complete circuit of the CB Battery Charger. Transformer T1, bridge rectifier D1 to D4

Fig. 1. Circuit diagram of the CB Battery Charger.

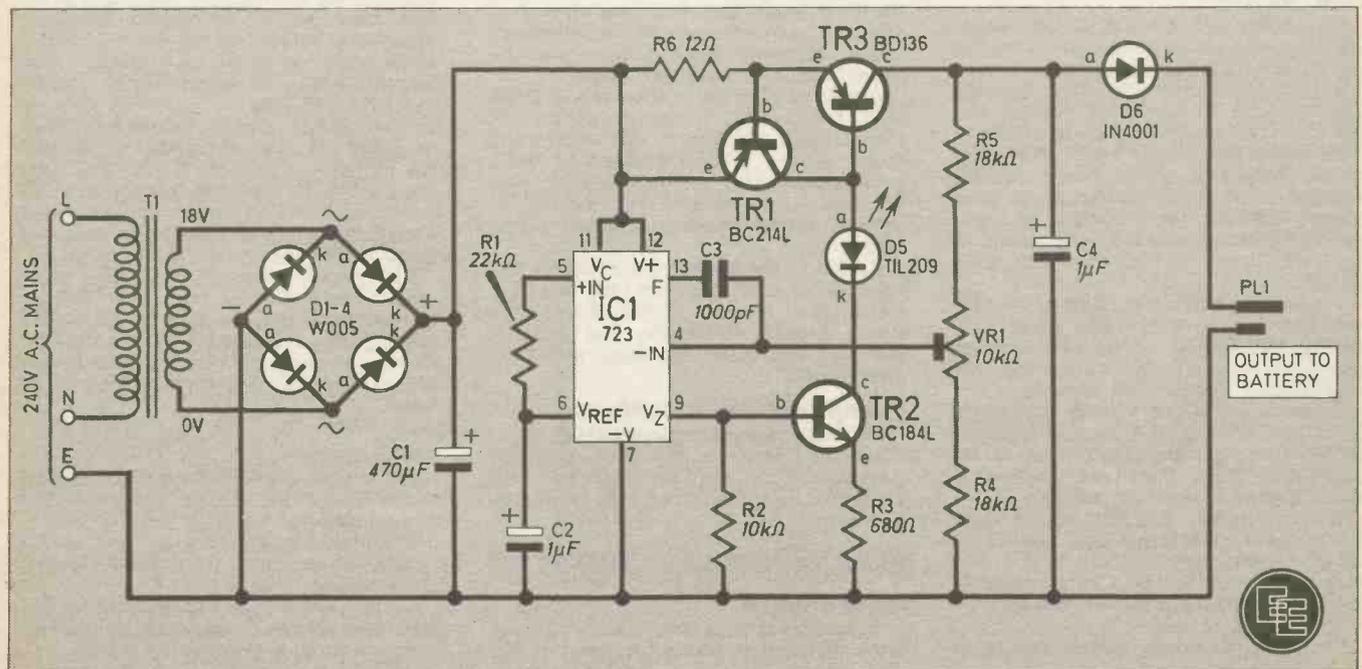

and capacitor C1 provide a smoothed d.c. supply of about 20V. The circuit has to charge the battery on a fixed current until a pre-set full-charge voltage is reached and then maintain this voltage by reducing the current.

The LM723 regulator i.c. was chosen for the circuit as it contains a stable reference voltage source and an amplifier for comparing this reference with the battery voltage. The reference voltage of about 7V appears at pin 6 and any noise present is decoupled by C2 before it is connected to the non-inverting amplifier input on pin 5. The inverting amplifier input, pin 4, is connected to the potential divider R4, R5 and VR1 placed across the circuit's output.

The chip also has provision for current limiting, but the operation of this is not really sharp enough for the present purpose so a constant current generator circuit based on TR1 and TR3 has been incorporated.

The action of this configuration is quite simple. A silicon transistor begins to conduct when its base-to-emitter voltage exceeds about 0.6V. The bias current supplied by TR2 to TR3 causes TR3 to conduct until the voltage across R6 reaches 0.6V, at which point TR1 starts to conduct away surplus bias current to progressively limit the conduction of TR3. Thus the current through TR3 can be calculated from Ohm's law as being $0.6V/R6$, and it will remain virtually constant regardless of load and voltage conditions.

So provided the voltage fed back from the output potential divider is lower than the reference voltage, the output of IC1 will be fully positive, causing TR2 to supply about 10mA of bias to the constant current generator. This bias passes through the l.e.d. D2 which indicates that charging is in progress.

Once the feedback voltage reaches the reference value however, the drive to TR2, and hence the bias is rapidly reduced, so the output current drops to a value just sufficient to maintain the output voltage at the desired level and the l.e.d. virtually extinguishes, indicating that charging is complete.



CIRCUIT BOARD

Construction, using the simple p.c.b. shown in Fig. 2 is quite straightforward. This diagram also shows the layout of all components. It's a sensible precaution to mount the transformer T1, D1-D4 and C1 first, and then to carefully apply power and check that the voltage across C1 is around 20 to 25V d.c. Remember that

COMPONENTS

Resistors

- R1 22k Ω
 - R2 10k Ω
 - R3 680 Ω
 - R4, 5 18k Ω (2 off)
 - R6 12 Ω
- All $\frac{1}{4}$ W carbon $\pm 5\%$

See
**Shop
Talk**

page 567

Capacitors

- C1 470 μ F 63V elect.
- C2 1 μ F 35V tantalum
- C3 1000pF ceramic
- C4 1 μ F 63V elect.

Semiconductors

- D1-4 W005 50V, 1A rectifier
- D5 T1L209 miniature red l.e.d.
- D6 1N4001 silicon
- TR1 BC214L silicon *pnp*
- TR2 BC184L silicon *nnp*
- TR3 BD136 silicon *pnp*
- IC1 LM723 adjustable voltage regulator

Miscellaneous

- T1 Miniature mains transformer, 9V-0-9V secondary
 - VR1 10k Ω miniature horizontal preset
 - PL1 Plug to suit host CB equipment (the prototype uses a 2.5mm jack plug)
- Single sided glass fibre p.c.b., 116 x 36mm; plastic case, 120 x 65 x 40mm (type BIM 2004); mains lead; twin cored lead; 7/0.2mm wire; l.e.d. mounting clip; mount-hardware for T1 (4 BA).

Approx. cost **£13.00**
Guidance only

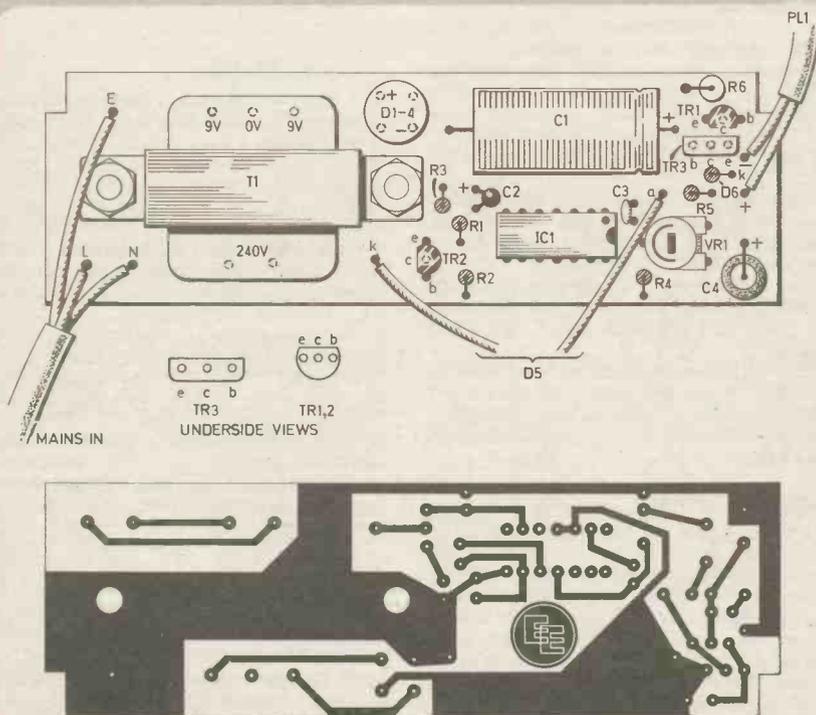


Fig. 2. Actual size p.c.b. artwork and component layout. T1 mounting holes may require slight adjustment to suit individual transformers. The photograph shows the authors hand-held CB rig being charged by the prototype unit.

some parts of the p.c.b. will be live at 240V mains whilst testing, so take adequate precautions when doing this.

The transformer is an inexpensive 9-0-9V miniature type, the centre-tap of which is unused so that it provides an 18V output. It is fastened to the board with a couple of 4BA screws.

After assembling the rest of the circuit, check with an ammeter that the output of the unit into a resistance of 100 ohms is around 50 to 60mA. Setting the output voltage requires a little more care.

The voltage of a ni-cad cell when approaching the fully charged condition is about 1.45V, so the unit should be set to supply this value multiplied by the number of cells in the battery. The author's CB rig is the Harvard model 410T, which contains ten cells but also incorporates an internal silicon diode in series with the batteries in its charging circuit, so an extra 0.6V has to be added to compensate for

this, bringing the total to $14.5V + 0.6V = 15.2V$.

A check of the circuit diagram of your rig will show whether it contains a similar internal diode. Note that the voltage setting must be made with the charger supplying some current, so a resistance of 1k Ω should be placed across the output before carefully adjusting VR1 for the correct output voltage.

The finished board is designed to slip into the moulded mounting slots provided in the specified case, and on the author's prototype, the cable strain relief clamps are simply a few turns of insulating tape around the input and output leads. A small hole is drilled for the l.e.d. which is then secured by means of a mounting clip.

FAST CHARGER

Experimenters might like to note that this circuit can be adapted quite simply for other output voltages and currents. A further interesting ap-

plication would lie in the construction of a "fast" charger. The ten-hour charge rate usually quoted for ni-cads is the maximum at which they will withstand indefinite overcharging; if provision is made to reduce the supply current when the charge is complete they can be charged in far shorter times, down in fact to as little as fifteen minutes.

A charge rate of 1A, completing the charge in 30 minutes is apparently quite feasible for the AA size. Note that if they are overcharged at these higher currents gas will form and they will vent, thereby losing electrolyte. The "button" types of cell have no provision for pressure venting and under similar conditions may explode, so don't try it with these!

However, with an up-rated transformer and some heatsinking for TR3 this design could be modified into an efficient high speed charging system. □



Out and About

Recently it occurred to me that it might be of interest to look in on component and equipment suppliers, giving a short history and other points concerning their businesses.

There can be few if any of our readers who are not acquainted with the firm of J. Bull. I have no doubt, that many readers have in the past called at his shop in Croydon to purchase goods. Unfortunately, a large increase in rent forced him to move to Haywards Heath and store the greater part of his stock on his farm a few miles away. It was with expectation and excitement that I drove down to his home near Brighton to learn his story, which is an interesting one.

Jesse Bull served with the Fleet Air Arm during World War II and started up his business in 1946 with his gratuity. The bulk of his business was and still is Mail Order, and originally he specialised mainly in "Kits". His first Kit was a television set made mainly from ex-RAF radar parts and used a 5-inch green tube. It proved to be very popular because commercially made sets were in short supply.

The advent of the transistor gave a real boost to the sales and the company sold over 50,000 transistor radio kits. Older readers may remember, "The Good Companion" "The Pocket Four" and the "Solderless Three".

The importation of cheap Japanese sets gradually put paid to this market. Although

Jesse still sells the more popular Kits, the emphasis has shifted more to bargain lines which are regularly displayed in his adverts. In addition he issues a monthly bargain list. I was particularly taken with his offer of 10 kilo (22 lb) of components for £14.50 including postage and packing, this seemed to be an offer that cannot be refused.

When we had finished our discussion, Jesse took me around the sheds that house his stock. Each shed is 100 yards long and about 15 yards wide, and is packed with every conceivable piece of electronic equipment you can imagine. You name it, I am sure Jesse Bull must have it.

After we had examined two of the sheds, he smiled at me and said, "Do you want to see any more?" I had to reply honestly, "As interesting as they are, I will take the rest as read!"

Computer Doctor

Turning again to computers, in this country we don't seem to use them as frequently in diagnostic medicine as they do in Russia. Over there, due to the shortage of Doctors, 85 per cent of whom are women, the computer is often substituted for the G.P. and hard as it is to believe they claim a better success rate than the real G.P.s.

While I was trying to evaluate how this would work out in practice, my resident Imp, who can never be entirely suppres-

sed, paints the picture for me. "Can't you imagine it?" he says, "This poor chap goes into the surgery with an ingrowing toenail, sits down at the computer and presses all the relevant buttons.

"Unfortunately unknown to him, this machine is malfunctioning due to a couple of dry joints on one of the circuits and having put him out cold with a smart tap on his 'noggin' with a Black Jack, proceeds to operate. When the poor man regains consciousness he finds either he has had a vasectomy or is minus an ear!"

While reluctantly agreeing with my Imp, I have an answer, which is this, that even real flesh and blood doctors make similar mistakes, usually by getting their patients mixed up!

Ship's Doctor

I must confess this method of treating patients, is rather like the method used in small ships. On a ship of less than 5,000 tons, a Doctor need not be carried. This chore being carried out by the Captain or Mate.

To assist them they have a Board of Trade Medicine Chest, which contains all the medicants likely to be required on the voyage. These are numbered and there is a book of instructions.

If, for example, a sick sailor complains of headaches, the book would instruct the Locum to give him one tablet number 6. On returning to port, the skipper would report to the port Medical Officer, who would question him about any sickness on the voyage.


I must conclude with the story of the skipper reporting to the Medical Officer, which goes as follows: M.O. "Well Captain, did you have a good voyage?" Captain. "Splendid, thank you." M.O. "Any medical problems?" Captain, "Not really, I did have one of the crew who had stomach pains and I had run out of pill number 12."

M.O. "Oh! What did you do?" Captain, "Oh! it was quite simple really, I gave him one number 7 and one number 5!"

I am confident that computerised medicine will do better than that.

EE TEACH-IN 82

PART 12 BY O.N. BISHOP

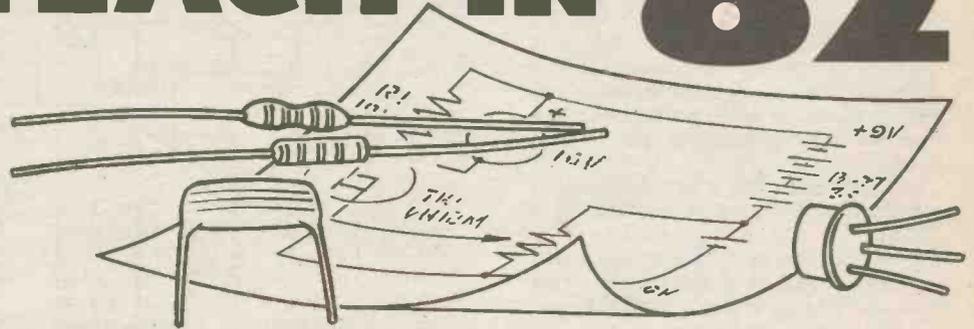

BASIC ELECTRONIC THEORY WITH EXPERIMENTS COMPUTING CIRCUITS

IN THIS final instalment of the series we bring our study of electronics up to date. We see how some of the simple circuits we have already studied can be put together to make more elaborate systems capable of performing calculations and logic.

The term "computer" is taken to refer to the digital computer nowadays, since most of the computers we use are of this type. Analogue computers operate in a different way and, although they have been replaced by the digital computer as a calculating or logical tool, they still have important applications.

They are usually based on the operational amplifier (see Part 7, EE April 1982). Indeed it was the need for high-performance amplifiers for use in analogue computers which gave rise to the 741 and other op-amps which are still so widely used today. Before we see how op-amps are used for calculating, we must study one more amplifying circuit.

INVERTING AMPLIFIER

The circuit configuration in Fig. 12.1 is different from the other op-amp circuits we have studied in that the input voltage is fed to the inverting input (-) of the amp-

lifier. Consequently, an increase of V_{IN} produces a decrease of V_{OUT} , and the other way about.

Since the output signal is fed back through R_{24} to the negative input, this amplifier has negative feedback. The amplifier is stable only when both of its inputs are at the same voltage. Since the non-inverting input is at 0V, the amplifier can be stable only when the inverting input too is at 0V.

We can think of R_{23} and R_{24} as a potential divider (Fig. 12.2). For any given value of V_{IN} , the amplifier adjusts V_{OUT} until the voltage at the inverting input (-) is exactly 0V. In effect, if V_{IN} is a positive voltage, a current flows from the input of VR_1 , through R_{23} , R_{24} , and into the output of IC_1 . If this current is I , and knowing that the p.d.s. are as shown in Fig. 12.2, we can calculate that:

$$I = \frac{V_{IN}}{R_{23}} = \frac{-V_{OUT}}{R_{24}}$$

The negative sign is needed because V_{IN} and V_{OUT} have opposite signs. Rearranging this equation we get:

$$\text{Amplification} = \frac{V_{OUT}}{V_{IN}} = \frac{-R_{24}}{R_{23}}$$

With the values given in Fig. 12.1, the amplification is $\times(-10)$. Note that the amplification depends only on the ratio between R_{23} and R_{24} . It does not depend upon the gain of the op-amp circuit, or variations in the manufacture of the op-amp, or the temperature in which it is operating.

If we use two high-precision resistors with high temperature stability, amplification is precisely determined and is stable. This is essential if we are to use the circuit for computing.

Note that the calculation above does not include any current flowing into or out of the inputs of the op-amps. A small current (about 100nA for the 741) flows to the base of each of the input transistors. These currents should be equal, otherwise an offset p.d. will appear between the inputs, causing errors in operation.

In Fig. 12.3, R_{26} is roughly equal to R_{23} , R_{24} and R_{25} in parallel. These are effectively in parallel since one end of each is at 0V under stable conditions. Since the current through R_{26} is only 100nA, the p.d. across it is only 0.0034V. We can consider the input voltage to be almost 0V, and the description above still holds good.

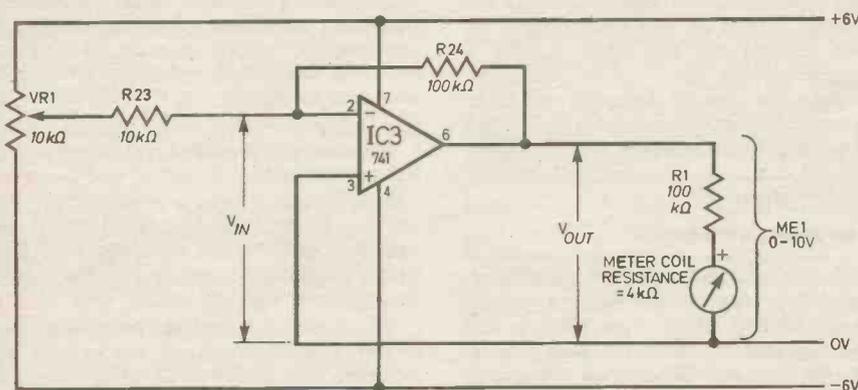


Fig. 12.1. Using an op-amp as an inverting amplifier. Offset null compensation is not essential and is omitted. You could connect up this circuit on *Minilab* and test its action. For positive input voltages from VR_1 , reverse the connections to the meter.

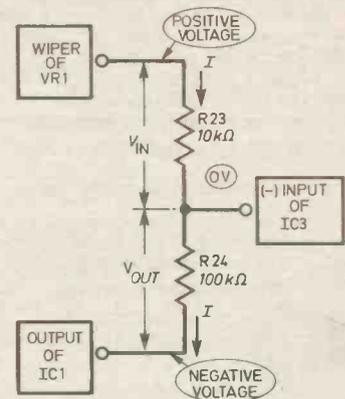


Fig. 12.2. The resistors of the inverting amplifier re-drawn as a potential divider. The current flowing to the (-) input can be ignored as it is very small.

EXPERIMENT 12.1

Op-amp adder

The circuit in Fig. 12.3 is recognisable as an inverting amplifier, but it has two inputs, via R23 and R25. Since R23, R24 and R25 all have the same value, the gain of the amplifier is 1. We will be using only positive inputs, so outputs will be negative and the meter connections are reversed accordingly.

R27/R28 and R29/R30 are potential dividers used for providing known input voltage:

$$V_A = (12 \times 270 / (150 + 270) - 6)V = 1.7V$$

$$V_B = (12 \times 270 / (180 + 270) - 6)V = 1.2V$$

The exact voltages at A and B depend upon the actual values of the resistors; use the meter to check that they are near to the expected values. Then reconnect the meter to the output of the op-amp.

Connect flying lead X to point A. With a gain of 1 the output should be $-V_{IN}$, so the meter should read 1.7V. Connect X to B; the meter should read 1.2V. Input Y is identical to input X, so you should obtain the same pair of results by using lead Y instead and connecting it to A and B in turn.

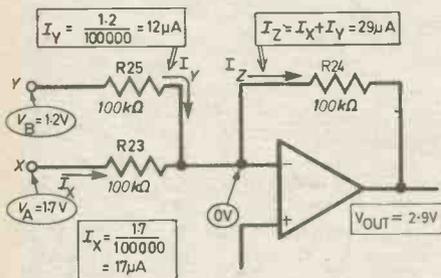


Fig. 12.5. Potentials and currents in the adder when inputs are 1.2V and 1.7V.

Now connect lead X to A and lead Y to B. Does the meter read 2.9V? The op-amp acts to bring its inverting input to 0V. The currents which are flowing through R24 and R25 (Fig. 12.5) combine and flow through R26. Thus the output voltage must be $-100000 \times 29 \times 10^{-6} = -2.9V$, which appears on the meter as 2.9V. The currents are added, so the output voltage is the sum of the two input voltages.

Answers to Part II

- 11.1. Its voltage is easily transformed.
- 11.2. So that current is relatively small and little power is lost from heating the cables.
- 11.3. 0V.
- 11.4. +339V.
- 11.5. 114V.
- 11.6. 6.25mA.
- 11.7. 1.11A, r.m.s.
- 11.8. 8.4V.
- 11.9. 10.6V.
- 11.10. It increases in amplitude.

EXPERIMENT 12.1

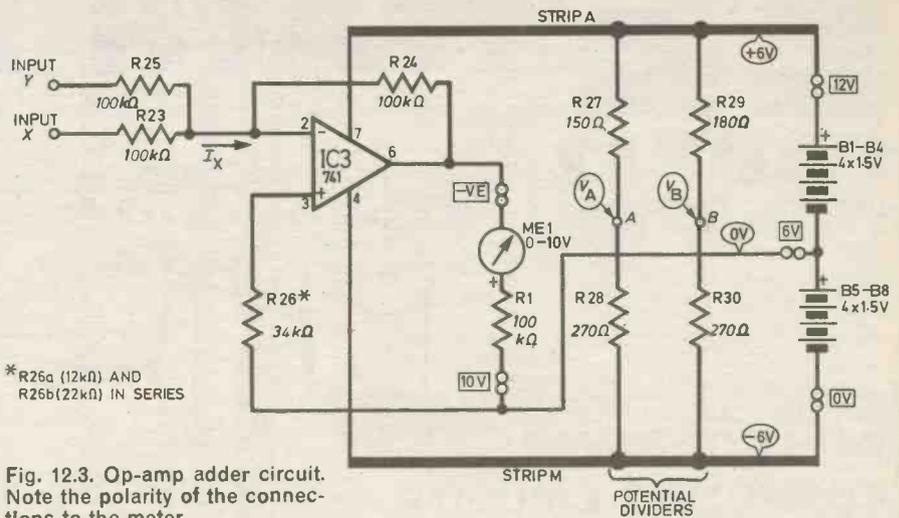


Fig. 12.3. Op-amp adder circuit. Note the polarity of the connections to the meter.

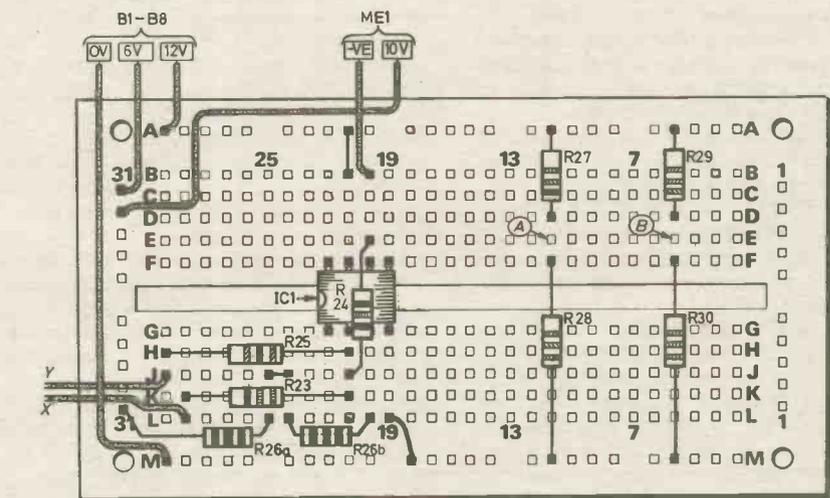


Fig. 12.4. The layout of the components on the Verobloc for the circuit in Fig. 12.3.

Make the connections needed to find the sum of 1.2 and 1.2, and read the result. Now find the sum of 1.7 and 1.7. You could experiment with other resistors in the potential divider to get different sets of input voltages and add them. If R29 is changed to 330Ω, V_{IN} is $-0.6V$. Now you can find the sum of 1.7 and -0.6 , in other words, subtract 0.6 from 1.7. Read the meter to find the answer to $(1.7 - 0.6)$.

EXPERIMENT 12.2

An op-amp differentiator

The mathematical operation of differentiation is a way of calculating a *rate of change*. In Part 9 (EE June 1982) it was explained that the current flowing into or out of a capacitor depends on the *rate of change of voltage*. In this circuit (Fig. 12.6) we change the voltage on one side of a capacitor. The current flowing out of the other side goes to an op-amp.

The layout for this Experiment is shown in Fig. 12.7. To begin with, the capacitor is charged to +6V. Now press and hold S1 to discharge C9 through R23. Note the maximum value reached by the needle of the meter. It kicks up, showing that voltage is falling, but quickly returns to 0V as the capacitor discharges and the rate of fall of V_{IN} decreases to zero (see Fig. 9.5).

Release S1: the meter kicks down, as the voltage increases.

Now replace R23 by a wire link, so that C9 may be discharged more rapidly. Press and hold S1. The rate of change of V_{IN} is much greater now, and the needle moves much further up the scale.

This is only a simple demonstration, but it shows how an op-amp can be used to calculate *rate of change of voltage*. Such a circuit could be used in real-time computing, for example, when we want to measure a rate of change of a quantity such as velocity, to calculate acceleration.

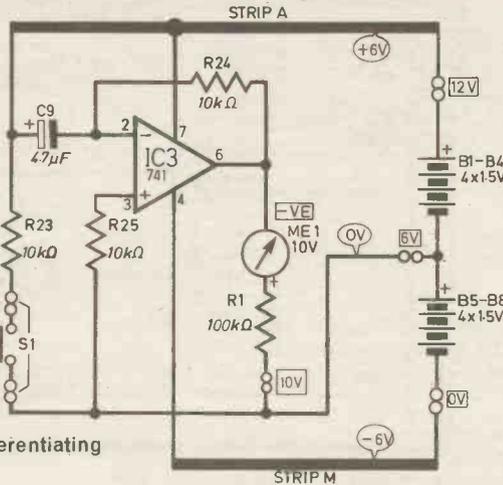


Fig. 12.6. Op-amp differentiating circuit.

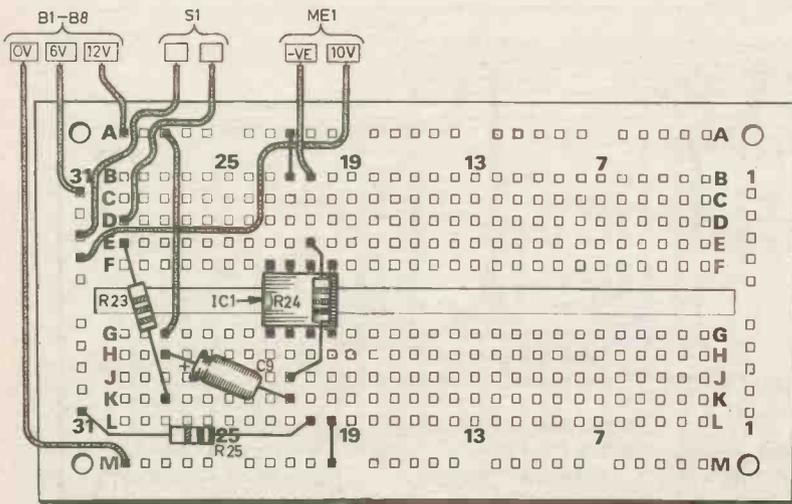


Fig. 12.7. The layout of the components on the Verobloc for the circuit in Fig. 12.6.

QUESTION TIME

- 12.1. Which of the quantities in this list is *not* an analogue quantity: velocity of a car, engine temperature, the number of wheels on the car, the amount of fuel in the tank.
- 12.2. If R24 in Fig. 12.1 is replaced by a 1.2MΩ resistor, what will be the gain of the circuit?
- 12.3. If the circuit of Fig. 12.1 has $V_{IN} = -20mV$, what is its output?
- 12.4. If a circuit is set up as in Fig. 12.2, but with three inputs, and the input voltages are 1.2V, 0.4V and -1.1V, what is the output voltage?
- 12.5. If in Fig. 12.6, C9 was connected to +3V instead of +6V, and S1 was NOT pressed, what would be the reading on the meter?

Suppose that the counter has 8 flip-flops in series (Part 4, EE January 1982), then the greatest binary number the counter can register is 1111 1111, or 255 in decimal. The velocity may range smoothly from 0 to 100 metres per second, but the count can take only 256 distinct values in the range 0000 0000 to 1111 1111. We can have a count of 134, or one of 135, but we can not have anything in between. Instead of having a *single* meter to indicate the quantity, we need several lamps or other devices, one to indicate the state of each digit.

The great advantage of representing values in digital form is that it is so much easier to deal with them at high speed with relatively simple and reliable circuits. We have already seen in Part 4, how the two kinds of binary digit are represented by 0V and +5V respectively, and how gates can be built which will perform logical operations. Now we will see how these gates can be used for performing calculations.

ANALOGUE AND DIGITAL

It is implied in the previous sentence that we can represent velocity by a voltage. Both are analogue quantities in that they can vary smoothly over a given range and be represented by the position of a pointer on a scale.

The velocity of a vehicle over the range 0 to 100 metres per second can be represented in an electronic speedometer by voltages in the range 0V to +5V (Fig. 12.8a). Then a voltage of 3.524V, represents a velocity of 70.48 metres per second. For each possible value in the range of velocities there is a corresponding voltage. As the velocity changes and hence the voltage changes, an op-amp differentiator could compute acceleration in metres per second per second.

We can also represent velocity as a binary digital number, as in Fig. 12.8b. The voltage is fed to a voltage-controlled oscillator, and the number of pulses per second is counted.

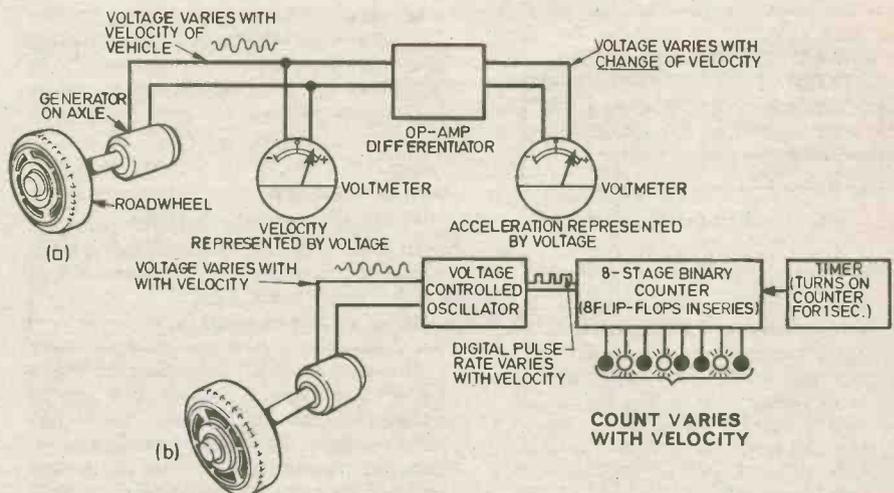


Fig. 12.8. Analogue and digital quantities. (a) a wholly analogue system using an analogue computer (b) analogue input converted to digital form. The digital output can be fed to a digital computer to calculate other quantities (for example, acceleration).

EXPERIMENT 12.3

A Half-Adder

The circuit in Fig. 12.9 (Verobloc layout in Fig. 12.10) includes a logic gate which we have not used before, an EXCLUSIVE-OR gate. The arrangement of the four gates within the 4070 i.c. is just the same as that of the 4011 (see Fig. 4.10), but their action is different. The EXCLUSIVE-OR gate has two inputs. Its output is high when either one input or the other input, (but not both), inputs is high. Table 12.1 is its truth table, and Table 12.2 reminds us of the truth table for NAND gates.

The half-adder circuit has two inputs, which are normally held low by R23 and R24. When the buttons are pressed, the corresponding inputs are made high. The state of the outputs is shown by the l.e.d.s; a "0" is represented by the l.e.d. being off, a "1" by it being on.

Try the combinations of inputs listed in Table 12.3, by pressing the corresponding buttons and note the state of the outputs. Use the truth tables to work out how the circuit operates.

We think of this circuit as having two inputs, representing two numbers which are to be added together. Each number has only 1 digit, so the numbers to be added can be either 0 or 1. If you press neither button, this is equivalent to adding $0 + 0$. Their sum is indicated by the state of D3 (column ZS in the table). You will have found that $0 + 0 = 0$, $0 + 1 = 1$, and $1 + 0 = 1$.

When we sum 1 and 1 in binary arithmetic, the result is 10 (= 2 in decimal). In

Table 12.1: EXCLUSIVE-OR.

Inputs		Output
A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

Table 12.2: NAND.

Inputs		Output
A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

Table 3: Results of testing Half-Adder.

Inputs		Outputs	
A(S1)	B(S2)	ZC(D2)	ZS(D3)
0	0		
0	1		
1	0		
1	1		

EXPERIMENT 12.3

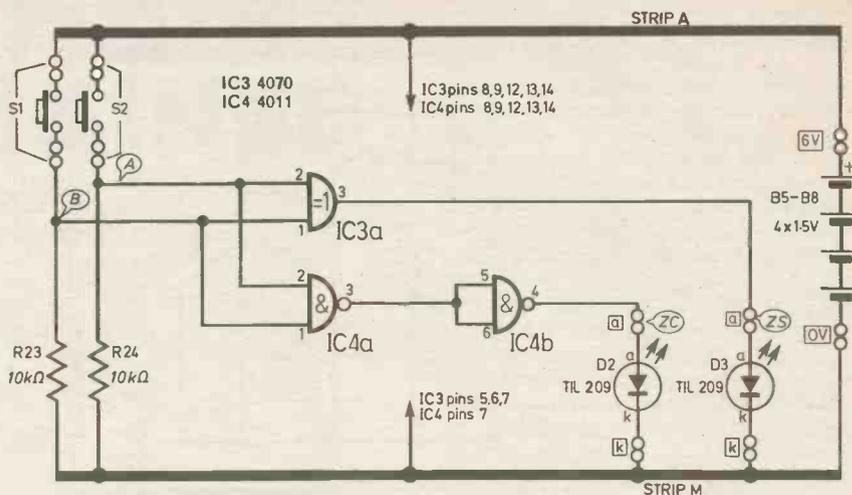


Fig. 12.9. Circuit of a half-adder.

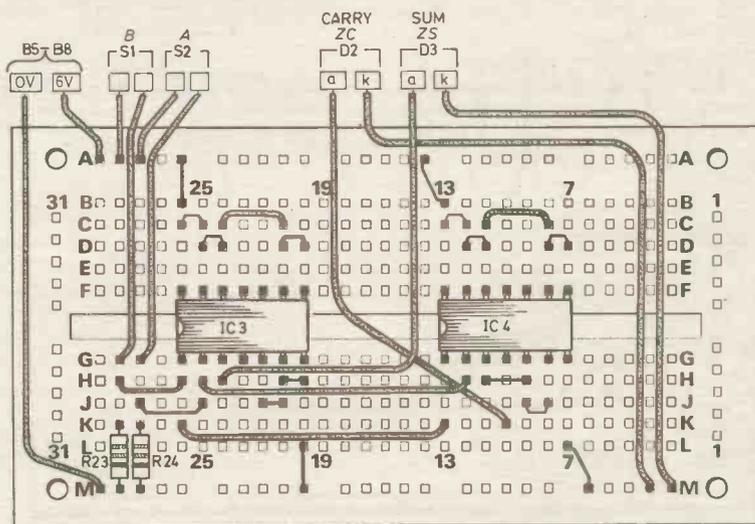


Fig. 12.10. The layout of the components on the Verobloc for the circuit in Fig. 12.9. Unused inputs are connected to 0V or +6V so that the i.c.s operate correctly.

effect we say "1 plus 1 gives 0, carry 1". The 1 is carried over into the next column on the left, and we write down the answer, 10. In this circuit the carry digit is represented by D2 (column ZC).

FULL ADDER

The half-adder can perform only the most basic of summing operations. It sums two 1-digit numbers and produces a 1-digit answer, with a carry digit.

When we add numbers on paper we sum one column at a time and take the carry digit over to be added in the next column to the left. Similarly, we could have several half-adders, each dealing with the corresponding digits from two multi-digit numbers, and passing the carry digit to the next half-adder to the left. This gives a full-adder, which can consist of enough half-adders to allow it to sum two numbers of any given number of digits.

EXPERIMENT 12.4

Full Adder

Fig. 12.11 shows a 2-digit full adder. It can add a number A^1A (where A is the least significant digit), to a number B^1B , giving the sum as a 2-digit number Z^1Z , with a third carry digit, ZC .

It is clear from Fig. 12.11 that this circuit consists of two half-adders. Digits A and B go to the first half-adder (IC3a, IC4a and IC4b), and digits A^1 and B^1 go to the second (IC3b, IC4c and IC4d). The carry digit from the first half-adder is added to the sum digit of the second half-adder by the EXCLUSIVE-OR gate (IC3c), just as we add in the carry digit in ordinary arithmetic.

The suggested Verobloc layout for Expt. 12.4 is shown in Fig. 12.12.

The A^1 and B^1 digits are given the value "1" by pushing the flying leads A^1 and B^1 into sockets A20 and A22.

EXPERIMENT 12.4

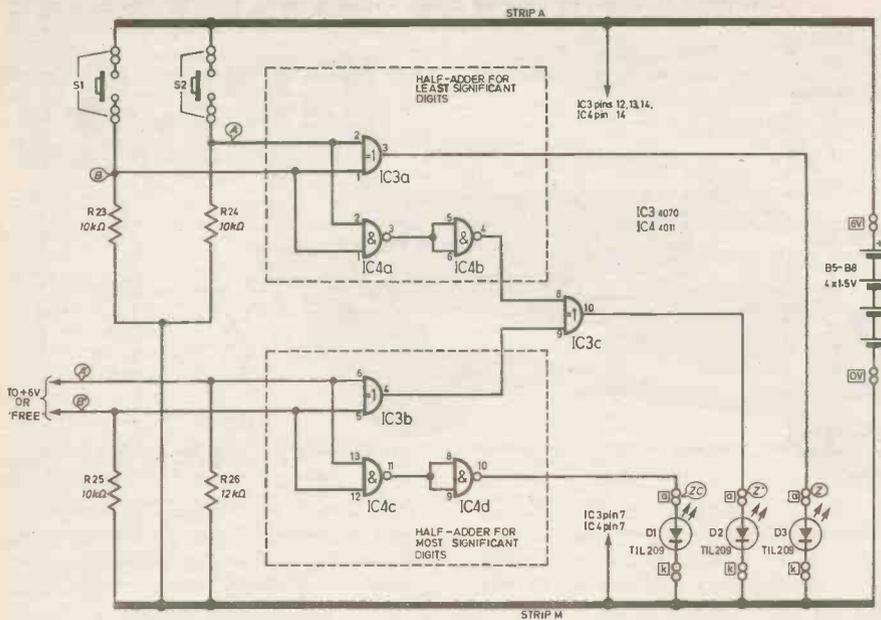


Fig. 12.11. Logic diagram of a 2-digit full adder.

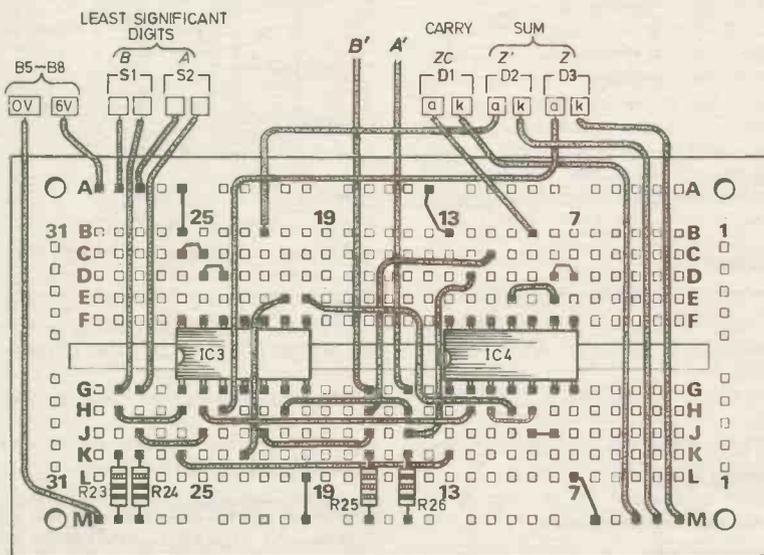


Fig. 12.12. The layout of the components on the Verobloc for the circuit of Fig. 12.11.

As an example of how to use the circuit, try the addition, $1 + 3$. A^1A is 01, B^1B is 11 (the binary equivalent of decimal 3). A^1 is to be 0 so lead A^1 can be left loose; B^1 is to be 1, so push lead B^1 into socket A22. Then press S1 and S2 to make both A and B represent 1. You should find that D3 and D2 do not light, but D1 does. This indicates the sum 100 (equivalent to decimal 4).

Answers to Part 12

- 12.1. Number of wheels.
- 12.2. 120 times.
- 12.3. $+2 \cdot 4V$.
- 12.4. $(1 \cdot 2 + 0 \cdot 4 - 1 \cdot 1)V = 0 \cdot 5V$.
- 12.5. C9 is charged to +3V so V_{IN} is not changing. Its rate of change is zero, so V_{OUT} is zero.

Try adding other pairs of numbers, such as $1 + 2$, $2 + 2$, $2 + 3$, and $3 + 3$.

The readout can be made much clearer by using the *Minilab* DISPLAY MODULE. Remove the connections to D1, D2 and D3. Now make these connections to the DISPLAY MODULE:

- Digit Z—from J24 to display a
- Digit Z¹—from B22 to display b
- Digit ZC—from B9 to display c

Connect display d and L inputs to the 0V rail (strip M of the Verobloc). Switch on the module (S8), and you can now read the answers directly in decimal; the DISPLAY MODULE does the binary-to decimal decoding for you. Run through all the sixteen different sums that the adder can do, from $0 + 0$ to $3 + 3$, and check that it gives the right answers.

OTHER CALCULATIONS

Readers who are proficient in binary arithmetic will know that binary subtraction can be performed by a routine which essentially consists of addition. We can multiply two numbers together by a series of additions.

For example, to find 3×5 , we add three fives together. First we add $5 + 5 = 10$, then we add a third 5 to that sum to get 15. All we need is a full adder, and a way of counting how many times the addition has been performed. This is just what happens in a microprocessor when it has been programmed to multiply.

Division can be done by repeated subtraction. To divide 15 by 5 we subtract 5 from 15, leaving 10. We continue subtracting 5 from the remainder until the result is zero. Zero is reached on the third subtraction, so $(15 \div 5) = 3$. This is how logic circuits are able to perform the four basic operations of arithmetic.

MICROPROCESSOR

To perform other mathematical operations we simply have to arrange for a sequence of such operations to be performed. A microprocessor, the heart of the microcomputer, can be programmed to perform such sequences and thus can be made to carry out all kinds of mathematical operation.

The circuits which are used in a computer are basically very simple ones, concerned with elementary logical operations such as NAND and NOR, and the simple addition of two binary digits. The reason that computers seem to have almost human powers is that they can be programmed to perform a sequence of tens of thousands of such simple operations in a single second without making mistakes.

It is hoped that readers who have followed this series will have gained some insight into the inner workings of many of the electrical appliances such as thermostats, radio sets, and amplifiers, which are so common in our homes today. It is also hoped that this final part of the series will have helped take some of the mystery out of the mighty microcomputer. □



SCREEN WASHER DELAY

BY G. L. STONEMAN

WITH all the rain, sleet and snow that seems to deluge our cars every year, windscreens tend to become soiled very quickly, leading to a reduction in the driver's visibility. To overcome this problem, the driver must regularly operate the windscreen washers. This results in the driver removing his hand from the steering wheel and interrupting concentration on the road ahead.

This article describes the construction of a simple but effective device that operates the electric screen washers for a period up to about 10 seconds or so after a single press of a switch, thereby ensuring that one hand does not have to leave the steering wheel for more than a second or two allowing the driver to concentrate more on driving.

The circuit is designed for operation in cars with a negative earth but details are also provided for modifications to allow it to be fitted and used on positive earth vehicles.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Screen Washer Delay is shown

in Fig. 1. It can be seen that only a few components are required.

When the washer switch is pressed, C1 is immediately charged up to 12V and the relay contacts close. When S1 is released, C1 slowly discharges through the coil of RLA. During this time, the relay contacts RLA1 stay closed and supply power to the windscreen washer motor, resulting in a stream of water to the screen.

As C1 discharges through the relay coil, the current through the relay decreases and eventually a point is reached where this current is insufficient to operate the relay. The contacts then open resulting in the pump motor turning off. VR1 is used to set the operating time of the pump motor.

COMPONENTS

The relay used on the prototype was a low-profile p.c.b. encapsulated reed type with a 1,000 ohm 9-12V coil. This is colour coded blue. If a different type of relay is used, one that has two pairs of contacts, combined wash and wipe with one-shot operation could be achieved.

Capacitor C1 should be one with axial leads (one from each end) rated 16V or more. The can should be completely insulated before mounting using p.v.c. tape or tubing.




CIRCUIT BOARD

Construction is straightforward with the components being mounted on a piece of 0.1 inch pitch stripboard measuring 13 strips by 24 holes.

Begin by drilling the two 6BA clearance holes in the board for mounting purposes. Use the 4-way terminal block as a template for this using the two outermost holes. The board is to be secured using the terminal block fixings through the case.

Fig. 1. The complete circuit diagram of the Screen Washer Delay

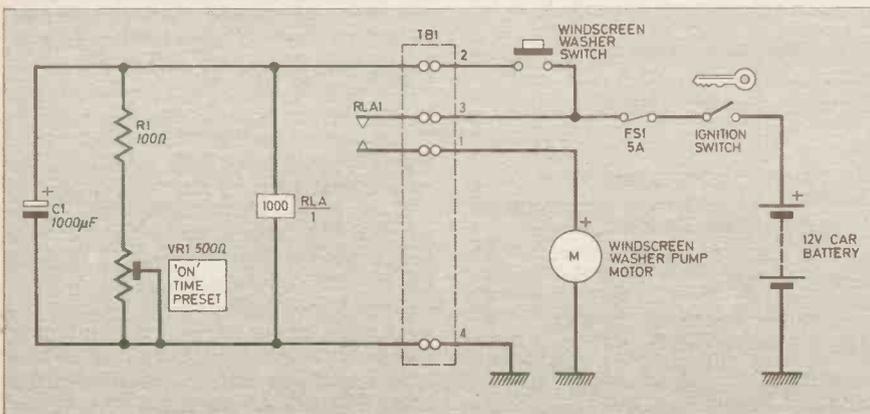

COMPONENTS

- R1 100Ω ½ W carbon ±5%
- C1 1,000μF 16V elect. axial leads
- VR1 470 ohm miniature horizontal preset
- RLA encapsulated reed type relay, 1,000 ohm coil, 9 to 12V operating voltage
- FS1 5A with in-line fuseholder

Stripboard: 0.1 inch matrix, 13 strips × 24 holes; 5A screw terminal block, 4-way; 6BA fixings: 25mm long screw, nuts (2 off), 5mm long spacer; plastics case, Vero 202-21025K; rubber grommet; 5A auto connecting wire.

Approx. cost £3.20
Guidance only

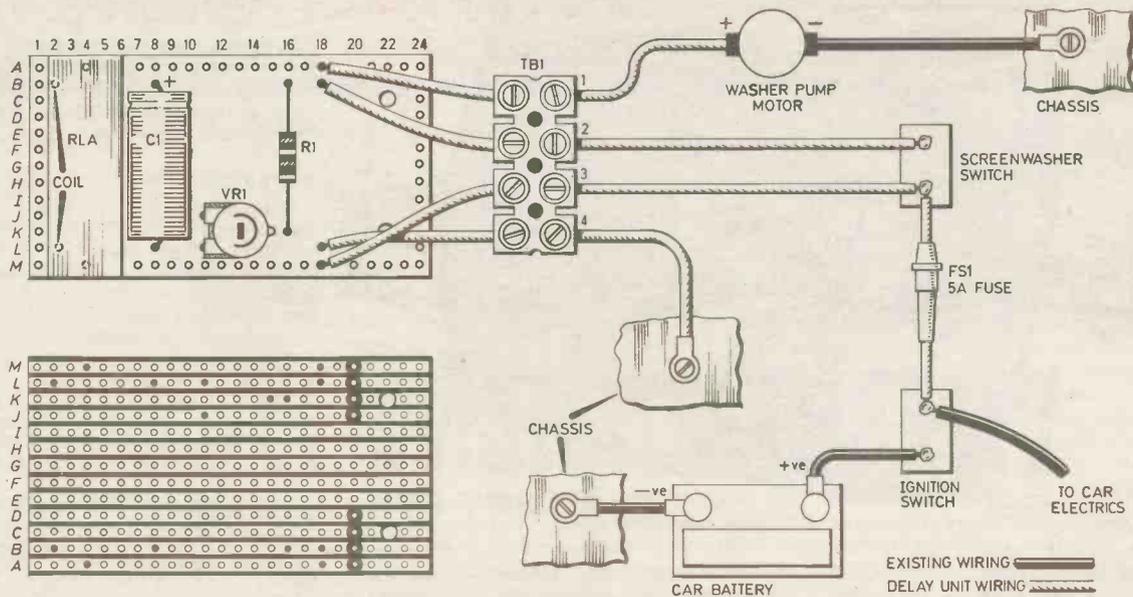


Fig. 2. Layout of the components on the stripboard, breaks to be made on the underside and wiring details to the existing car electrics.

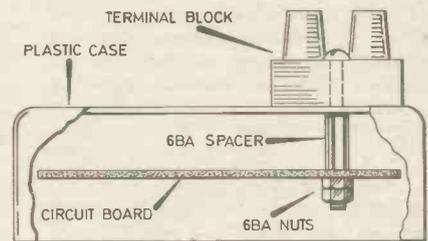


Fig. 3. A suggested method of mounting the component board in the case.

Also use the terminal block as a template for drilling the holes in the case.

Make the necessary breaks in the copper tracks using a spot-face cutter or small drill bit. These are necessary to isolate the fixings from the components soldered to the tracks.

Position and solder the components and flying leads to the board according to the layout in Fig. 2. A suitable case for this project is the General Purpose Plastic Box from Vero, size 72x50x25mm. Drill a hole of size suitable for a grommet to be fitted to carry the wires from the board to the terminal block fitted to the case top.

Fit the board and terminal block to the case and wire the flying leads to TB1. Fig. 3 shows the suggested way of mounting the board using a

lock-nut arrangement. This is necessary as the unit will be subjected to vibration in the car.

INSTALLATION

Wiring to the existing car electrics is also shown in Fig. 2. Do not use single-core wiring for this. Use 5A wire intended for use on a car, readily available from car spares shops. Fig. 2 shows wiring for a negative earth system. For positive

earth cars, simply reverse the capacitor, C1, and the connections to the pump motor. In either case make sure that a 5A fuse is fitted, connected to the "live when on" terminal on the ignition switch, (or a suitable terminal in the fuse box).

The unit should be mounted in a dry place away from exhaust fumes and extreme temperatures. It could be fitted to a suitable position inside the car, on the parcel shelf perhaps using self adhesive foam pads. ☐

NEWS

GIRL GRANTS

Only two per cent of engineering technicians in British industry are female. To encourage more girls into technician employment the Engineering Industry Training Board is offering 250 grants to firms willing to recruit girls over and above their normal planned technician intake.

Each grant is worth £6,000 and the scheme starts in September 1982.

Fibrevision

Eighteen lucky families in Milton Keynes are having a free trial of British Telecom's Fibrevision, the "wired city" of the future. Through optical cable they get five TV channels, pay-TV, Prestel and FM radio selected by hand-held infra-red control.

Sir Michael Edwardes, of British Leyland fame, is to be a part-time director of Project Mercury, private industries answer to British Telecom.

Intelpost, the Royal Mail's high-speed public facsimile transmission service, is now extended to cover the whole of Holland.

SPEAKING BOOK

Following on from TT's educational "Speak and Spell" for children, the company has developed a logical follow-on in the form of a talking book. The text has a bar-code which is scanned manually with a lightpen by the child to produce the spoken sound.

It will be available in the USA by Christmas and in the UK next year.

PLEASE TAKE NOTE

**CIRCUIT EXCHANGE—
INVADER LANDING GAME**
(August 1982)

The circuit diagram incorrectly shows the cathodes (k) of the i.e.d.s D3 to D12 connected to the positive supply rail (B1+). This link must be removed, leaving these i.e.d.s connected to the negative supply via the 470 ohm resistor, R8 (as shown).



Resistance to Space

Everything electronic and mechanical goes wrong in the end. And it isn't just domestic equipment that fails. This is why satellites, which are beyond the reach of a repair engineer, must be made to the highest possible standard of reliability. But *Meteosat-1*, the European weather satellite which was launched in November 1977, failed almost exactly two years later. The power supply just shut down. So a replacement, *Meteosat-2* had to be built and launched in June 1981. So what went wrong with *Meteosat-1*?

The answer is to be found in the April 1982 issue of the journal of the Institution of Electronic and Radio Engineers, albeit in very obscure wording. After the failure a team of aerospace experts met at the European Space Agency Research Centre in Darmstadt, West Germany, and built a breadboard replica of the circuit that had failed in space. With this circuit they then tried to simulate the fault.

To quote the IERE journal "It appeared that a digital circuit, which was designed to be triggered only in the case of over-current, was able to oscillate depending on the value of a resistor. Technological studies showed in fact that a degradation mode specific to this resistor caused its resistance value to be equal to this critical value".

When you translate this technical "gob-bledegook" into plain words, it means that a single resistor in the power supply changed value as it aged. This tripped a safety circuit breaker like a fuse, in the satellite power supply.

Thankfully *Meteosat-2* has different resistors. It also has relays which can bypass the protection devices if they go haywire.

So far *Meteosat-2* has been working without problems. But when you get down to the nitty gritty, the stark truth is that a meteorological satellite which costs tens of millions of pounds to put into orbit failed because a single resistor developed a fault.

Domestic Facsimiles

There's a lot of talk these days about document transmission systems, for use

in homes and small offices. Already of course large offices have facsimile equipment which can transmit pictures over the telephone line.

This is possible, despite the small bandwidth of a phone line, because the transmitting machine scans the source picture slowly, to produce a slow or low frequency stream of information. This is sent down the phone line to control a receiver which prints out a copy picture at equally slow rate, for instance onto heat sensitive paper.

There are obvious advantages in having a facsimile machine in the home, hooked up to a telephone. Where it's impossible to describe something by spoken word, you can send pictures or graphs down the line. Where there are strings of facts and numbers to be communicated, it's safer to send them as a written page.

Domestic facsimile reception could eventually replace the postman. Transmission and delivery take only as long as the machines take to scan a page. You don't even have to be at home to receive the transmission. If a message comes in while you are out, it's there waiting for you on your return, like a spoken message on an answering machine.

Japanese Line

Needless to say the Japanese are already excited about domestic facsimile systems. The Japanese Post Office, Nippon Telegraph and Telephone (NTT) is hard selling Minifax. Even by the end of last year NTT had installed nearly 4,000 Minifax units in Japanese homes, for a connection fee of around £12 and a monthly rental of £8.

The NTT sales campaign was based on the idea of using Minifax instead of telephone answering machines. But now the practical problems have started to emerge.

Junk Mail

The Minifax receiver cannot distinguish between messages which the subscriber wants to receive, and those which are unwelcome. So obscene callers can send lewd pictures and text down the phone line to unsuspecting victims.

Perhaps even worse, advertising firms can deluge subscribers with unwanted material. This isn't just inconvenient to the recipient, it is also very expensive. The subscriber has to pay for all the paper used by his Minifax machine to receive whatever comes down the line.

At the moment junk mail sent through the post doesn't cost the recipient anything. You can even get your own back on anyone who sends you too much junk mail, by simply returning it to sender without a postage stamp. The originator of the junk mail then has to pay twice the normal postage and very soon strikes your name off their mailing list. But the owner of a Minifax has no choice but to pay for all junk mail.

Car Statics

A tip on static. Modern cars have nylon or similar man-made fibre upholstery. This wears well but can generate very high voltages of static electricity when rubbed, for instance when the driver or passenger slides across a seat. Then when you get out of the car and put a key in the door to lock it, you get a very unpleasant jolt as a spark jumps across.

Car owners try all kinds of cures. Often you'll see a length of chain or conductive fibre trailing from the rear bumper. This is intended to keep the car at earth potential. But static is an unpredictable beast and you'll often still get just the same belt from an earthed car.

The reason is that your body picks up the high voltage charge as you get out of the car and separate yourself from the nylon upholstery. This leaves two oppositely

charged objects, the car and your body or your highly charged body and an earthed car. Either way you'll get a shock when you touch the car again—unless the weather is damp so that the charge leaks away naturally, very quickly.

The trick

The trick for dry weather, which took me an infuriatingly long time to learn, is to get out of the car in a special way. As you lift off the car seat you make sure you are holding the car metal work with a wide firm grip. So as you leave the car seat any static equalises or discharges through the wide contact area of your hand.

Usually you won't feel a thing. And you won't get a shock when you touch the car door with a key because there's no longer any charge to jump across.

ELECTRONIC HOBBIES FAIR


Alexandra Pavilion November 18 – 21 1982

Launched in response to demand for a major national show of the highest quality, EVERYDAY ELECTRONICS, PRACTICAL ELECTRONICS and PRACTICAL WIRELESS are presenting the biggest and best event ever to be staged for the electronic hobbies enthusiast.

If your company is involved in the manufacture of electronic components, equipment, ancillary systems for

electronic projects, home computers, amateur radio, citizens band, video games, musical instruments – you should be there!

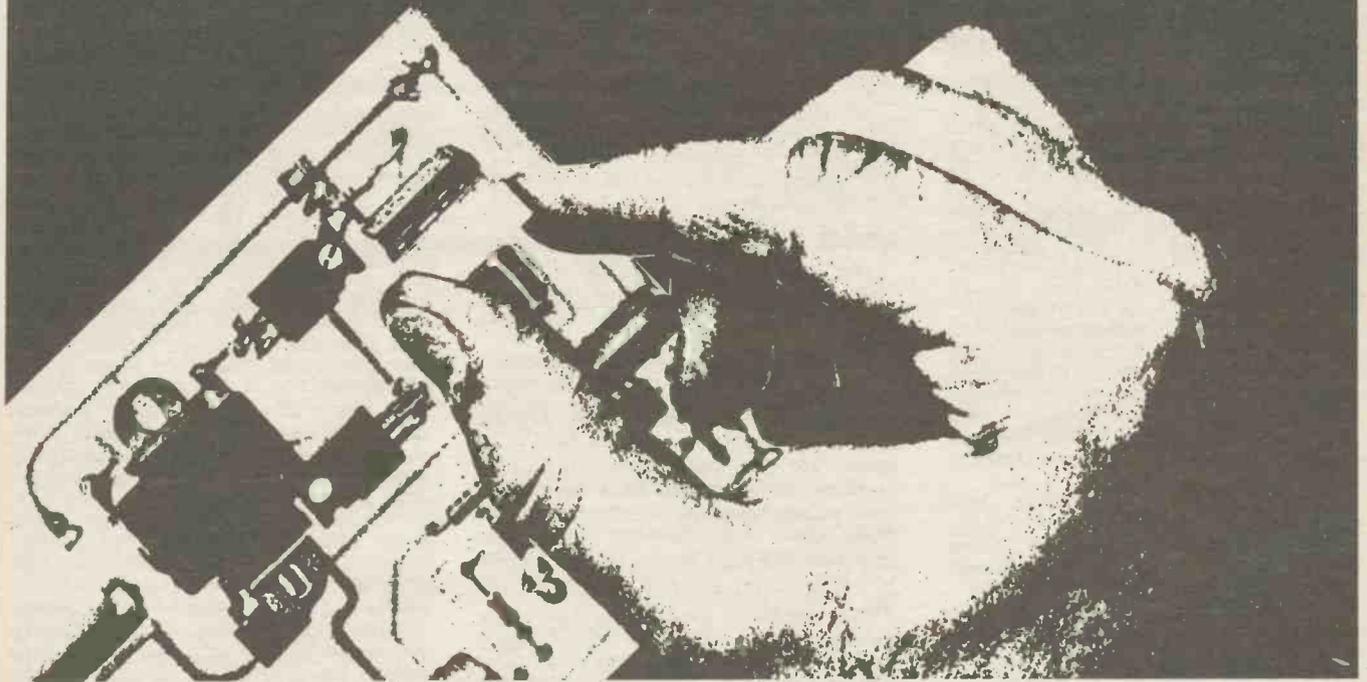For further information about exhibiting contact: The Exhibition Manager, Electronic Hobbies Fair, IPC Exhibitions Ltd., Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ. Tel: 01-643 8040. Extn. 4873.



Please send me details about exhibiting at the



Name _____
Position In Company _____
Company _____
Address _____
Tel _____

Send to: The Exhibition Manager, Electronic Hobbies Fair, IPC Exhibitions Ltd., Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ.

RADIO WORLD

By Pat Hawker, G3VA

A Better Picture?

NEW and developing technology makes interesting reading and journalists not unnaturally tend to play up the importance of each and every advance. On the other hand, a considerable number of last year's "exciting new breakthroughs" gradually sink unsung out of sight. "In five years time everybody will be..." is an attractive cliché since the writer is usually well aware that in five years time nobody, except possibly himself, will remember that over-confident forecast and hold it against him.

The number of financially successful inventors (or nowadays the more usual research and development teams) is relatively small: "Pioneerin' don't pay" was a classic belief of Andrew Carnegie. But the consumer electronics industry keeps on hoping: video discs, digital audio, large-screen projection television, direct-broadcast satellites, the electronically wired city, high definition television and of course home computers are all seen as growth areas.

However, the industry does display some worries about all-digital audio that has to compete with high-quality analogue audio, a branch of the industry that is currently feeling the effects of the long industrial recession. Similarly with video discs that have arrived on the scene rather later than expected and without the record as well as playback facility of the video cassette recorders which have proved one of the few really popular new products of recent years.

Surprisingly VCRs have been in greater demand in Europe than in either the USA or Japan.

Cinema Quality

What about high-definition television (HDTV)? Japanese, American and Irish broadcasting organisations (NHK, CBS and RTE) recently co-operated in demonstrating the remarkable NHK 1125-line system with wide-screen (1.85:1 aspect ratio) and separation of the chrominance and luminance components.

All who saw the demonstration agree that the system provides a superb picture, virtually the equivalent of good cinema film. You can sit very close to the screen without being worried by the line structure. Several forms of display device, including a widescreen picture tube and high-resolution projection systems, have been successfully developed.

But there are problems. The 27MHz of basic video bandwidth cannot be accommodated in our broadcast bands, not even the European 12GHz satellite band although CBS wants to try using two adjacent DBS channels in the United States, when that country begins direct-broadcast satellite services.

To obtain real benefit it needs a large screen. We still seem some way off from a high-resolution, large-screen display system within reach of many viewers.

HDTV does offer the possibility of all-video cinema presentations or for the dubbing of electronic video on to film. The idea of using 1000 line television to make cinema films is an old one.

In 1951-52 a British company, High Definition Films, had a black-and-white 1000-plus line system and showed that with such a system the very high cost of film making could be reduced. But I do not think they ever overcame the problem that film-makers, particularly the production teams, much prefer the techniques used in film (short sequences, single camera, post-production editing) to those of the large multi-camera electronic studio. Paradoxically, electronic production can today closely resemble that of film—though this then tends to put the cost of video up because of the high cost of machine-time for intensive editing.

The old question "how good is good enough?" may well be asked, and certainly I suspect it will be some time before many viewers in their own homes will be watching pictures of the quality shown in Killarney. Though all credit to the Japanese engineers who began work on the system in 1970 and have since made remarkable progress.

Solar Storms

The month of June witnessed some severe solar flares and other disturbances that had the effect of upsetting h.f. propagation conditions. These included

The Sting

Did they fall or were they pushed? That seems to be the question that can be resolved only in the American courts.

I refer to the astonishing "Japscam" operation in which major Japanese electronics firms admit they parted with \$648,000 for secret information that they thought would allow them to market computers plug-compatible to those of the giant IBM firm. The money was paid to a Silicon Valley consultancy firm Glenmar. But Glenmar happened to be a "front" for an FBI operation "Pengem" (Penetrating the Grey Electronics Market).

The Japanese firms claim they had no knowledge that the secret data was "stolen". Indeed, since it was material fed by IBM to the FBI for this operation it was arguably not "unlawfully" obtained by Glenmar—and indeed this type of sting operation does appear to have more than an element of "agent provocateur" about it.

The Americans are clearly worried about the continued flow of information and high-technology to East Europe, and competitive "know how"

at least one almost total "blackout" during which it is possible to spin the dials of a powerful shortwave receiver and yet hear no signals except those within ground-wave distances.

It is a strange experience to find usually crowded frequencies devoid of all activity. Total blackouts occur only during daylight and often seem most severe between about 5 and 10MHz.

More complaints

The Home Office report on the investigation by British Telecom engineers of complaints about interference to television and radio reception for 1981 shows very substantial increases both in complaints received (70,452, up 96.85 per cent) and completed investigations (60,571 up 47.42 per cent). Much (but not all) of the increase is due to interference from the 27MHz amplitude-modulated CB rigs before the issue of licences for 27MHz f.m.

It is also clear that much of this interference was *not* due to spurious or harmonic radiation from the CB transmitters but reflects the vulnerability of so much domestic electronic equipment to strong local signals, in other words poor "electromagnetic compatibility" (emc). Domestic equipment is much less affected by f.m. signals but the report does further dent the original Home Office case for advocating 934MHz for CB on the grounds that lower frequencies would cause interference due to harmonics.

The investigators found 14,359 cases where complaints were due to CB rigs, considerably more than the usual worst offender—the thermostats in central heating systems etc. which accounted in 1981 for 8,318 complaints. A large proportion of the CB interference was found to be due to direct breakthrough into the audio stages of solidstate domestic equipment and a lot could be prevented if manufacturers added some bypass capacitors and ferrite-bead chokes.

also to Japan. FBI have recently been briefing American electronics firms about techniques of industrial espionage that are far more sophisticated than the usual stories of bugging the boardroom.

In the UK, one gains the impression that inter-firm competition does include a certain amount of trickery. For example there appear to be firms that advertise non-existent jobs and then pump applicants about what their present firms are up to. But in-depth acquisition of design data is probably a good deal less common—partly I suspect because so many British firms and engineers are firmly convinced that if an idea is "not invented here" (NIH) it *must* be worthless!

Perhaps the most surprising feature of the incident is the lavish amount that the Japanese firms admit paying. By any standard, £350,000 is a fantastic sum to pay for information received, whether acquired legally or illegally, and shows the scale on which the computer industry now operates.



MONTHLY PLANNER

BY A. P. DONLEAVY

THIS project describes the construction of a calendar, which displays the date and a particular event which is to occur on that day, for example, a visit to the dentist or perhaps a birthday. There are nine possible events, one of which can be selected for a particular day.

The design uses two simple 64-bit RAM memories to store the events for the month. These memories are easily programmed using d.i.l. switches and the information for any particular day can be changed at any time.

SYSTEM OPERATION

Fig. 1 gives a block diagram of the system illustrating the various functions. The crystal controlled clock produces one negative going pulse every 24 hours. This is fed to a decimal counter which displays the date information and also to a binary counter.

The outputs from the binary counter are connected to the address inputs of the memory. Each binary number from the counter represents a day of the month. The information in the memory store for that day is then displayed in the EVENT DISPLAY.

Thus there are then two counters which operate in parallel, the decimal counter for the date and the binary counter for the memory address. The binary counter resets itself and the decimal counter on the 32nd pulse.

CIRCUIT DESCRIPTION

The circuit is shown in Fig. 2. IC1 an E050-16, provides the clock pulses. A brief description of the function of this i.c. may be of interest. It is made by MEM, part of a Swiss watch making concern, and is primarily intended for industrial timekeeping uses. The chip uses 32,768Hz crystal and an internal dividing circuit to provide negative going pulses at intervals of seconds, minutes, hours and days at pins 12, 11, 10 and 7 respectively.

The crystal XTAL1 acts as the time base for IC1. For correct functioning there should be a 1.5V difference between pins 16 and 1 of IC1 and this is provided by D1 and R1, using the forward volt drop of the l.e.d.

The daily output pulses from pin 7, IC1, are fed via R2 to input pins

9 of IC3 and 2 of IC4a. IC2 and 3 are both CMOS 40110 counter/latch and drivers for a seven segment display.

These two i.c.s count the daily pulses and display the date. When the count of IC2 goes from 9 to 0, a pulse appears at the CARRY output, pin 10, which is connected to the CLOCK UP input of IC3. The CLOCK DOWN facility of these i.c.s is not used, nor the LATCH and TOGGLE facilities. Hence, pins 7, 6 and 4 are tied to earth.

The two MAN3740 displays are common cathode types with their cathodes connected to the collector of TR1 for a reason which will be explained later.

BINARY COUNTERS

IC4, is a 4520 CMOS dual four-bit binary counter. The two counters are connected together to form an eight-bit binary counter and this is done by connecting the Q4 output (most significant bit) of one counter, pin 6, to the ENABLE input of the other counter. The ENABLE and CLOCK inputs of this i.c. can be reversed causing it to increment on a different polarity pulse transition.

Since one count is required for each day of the month, a maximum of 31 counts are required, so that the counter is arranged to reset itself at a count of 32. This represents a binary output of 00100000, the 1 being on pin 12. The RESET inputs of IC4 are 7, 15, and for the decimal counters, IC2, IC3 it is pin 5.

IC7 and IC6 are two CMOS 64-bit random access memories (RAM) with a 16 x 4 arrangement. That is 16 locations with a 4-bit word. The two memories together provide 32 locations, of which a maximum of 31 will be used for the days of the month.

The information stored in a location is essentially a number from 0 to 9 written in b.c.d. (binary coded decimal). The outputs from the memories are from pins 5, 7, 9, 11, and are fed to the inputs of IC8, a CMOS b.c.d. to decimal decoder, the 74C42. Thus the four-bit word written in the selected memory location is displayed directly as a

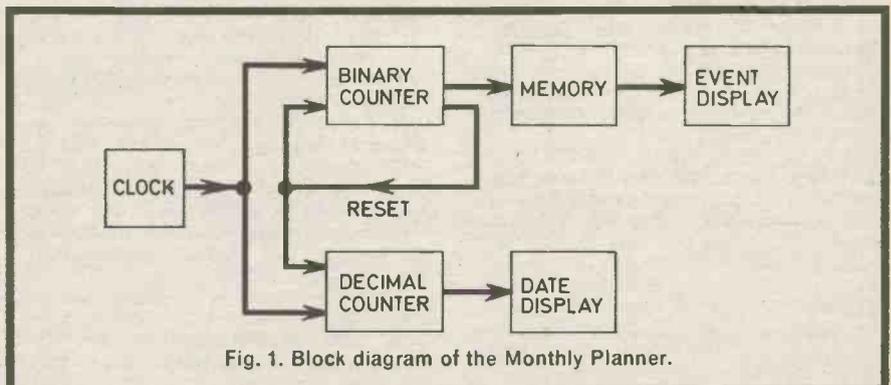


Fig. 1. Block diagram of the Monthly Planner.


number 0 to 9 by the l.e.d.'s connected to the outputs of IC8. The outputs of IC8 are normally high, and go low when selected.

As previously stated, each memory has 16 locations numbered from !0000 to 1111. So for example, on the third day of the month the binary

counter will be at 0010 since the first location is at zero (0000) and not at 1 (0001). The corresponding ADDRESS (location) inputs (pins 13, 14, 15 and 1) of the two memories are connected to each other, as are the DATA inputs (pins 4, 6, 10 and 12) and outputs (5, 7, 9 and 11).

Memory enable, ME, inputs are arranged so that if IC6, for example, is at logic 1, then IC7 is at logic zero and vice versa. This is achieved with the arrangement of the four NAND gates of IC5. When the ME pin is at 1, the outputs of the i.c. have a high impedance; and give out no informa-

Fig. 2. Monthly Planner circuit diagram. Note that SX need not be an actual switch as this is only required to ground pin 5 of IC1 at midnight


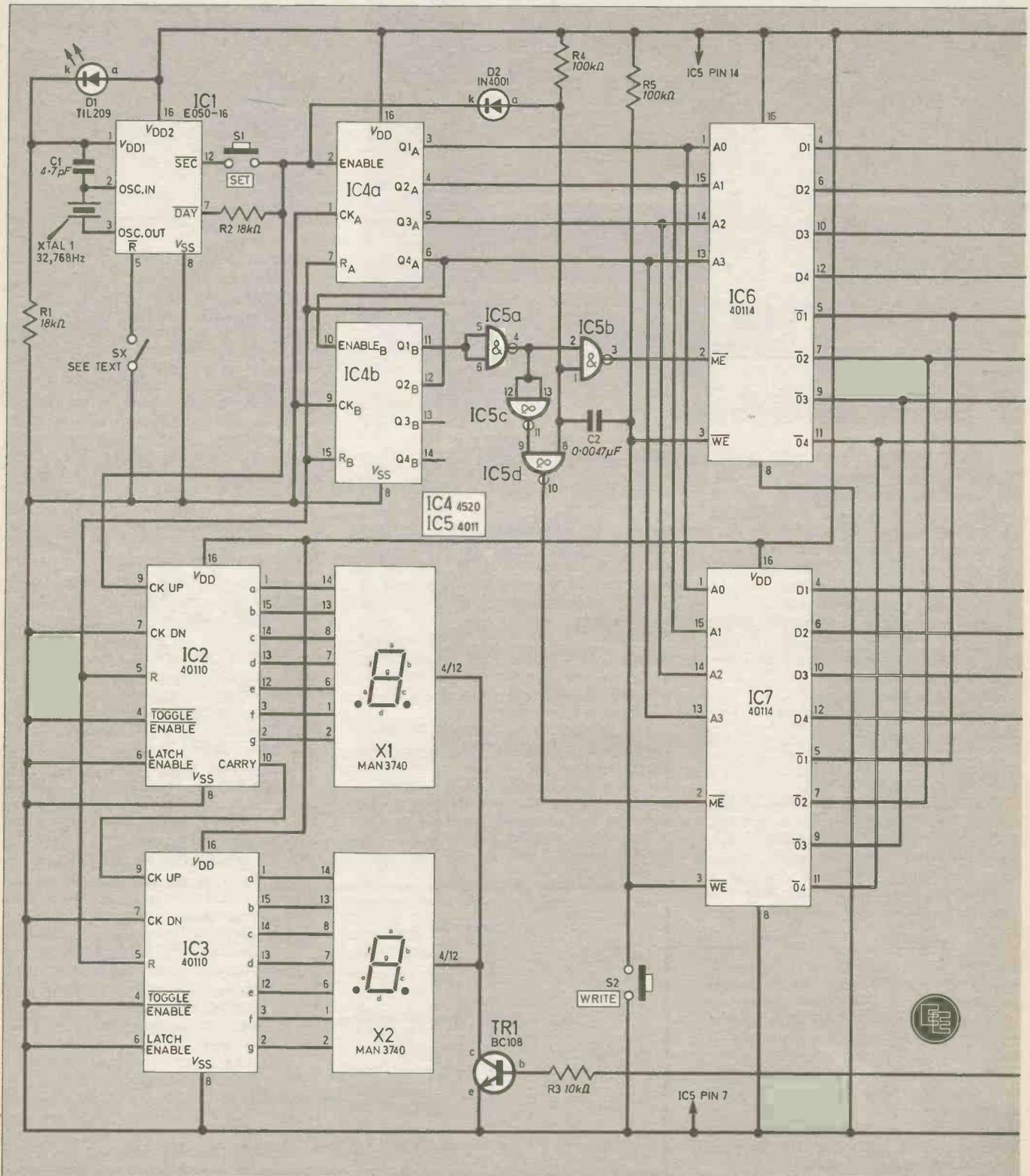


tion (having tri-state or three-state outputs). Also the inputs will not accept new information. Hence the i.c. is ineffective in the circuit.

Between the counts of 0 and 15, pin 11 of IC4 is at 0, so IC6 WE is at 0 and IC7 ME is at 1. Thus IC6 is the active memory. Between the counts

on the first day of the month. S3 to S6 input data to the memory.

Fig. 3. Power supply circuit. Note that some 9V adaptors drop below 9V under load so an extra diode in series with D13 may be necessary to prevent B1 discharging.

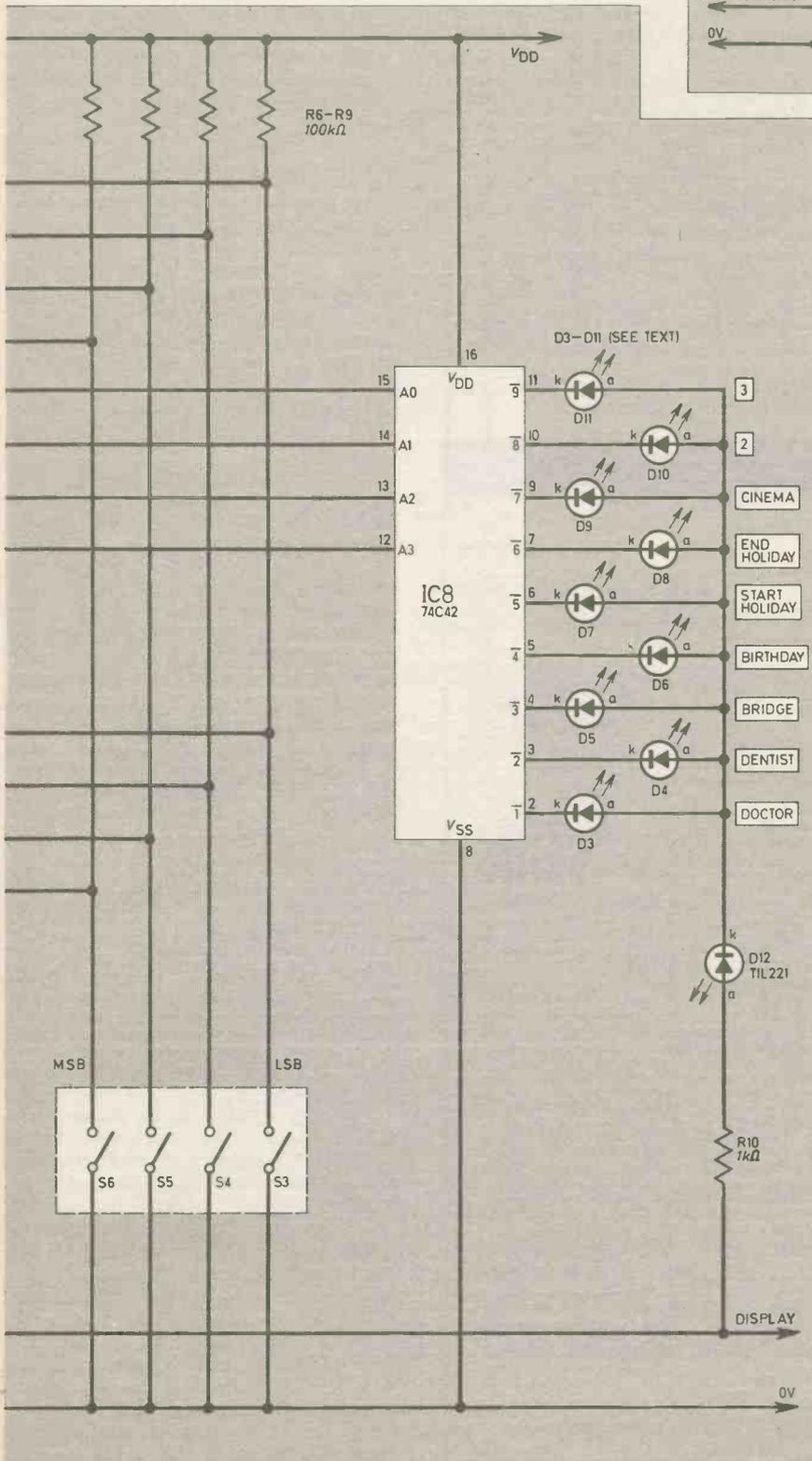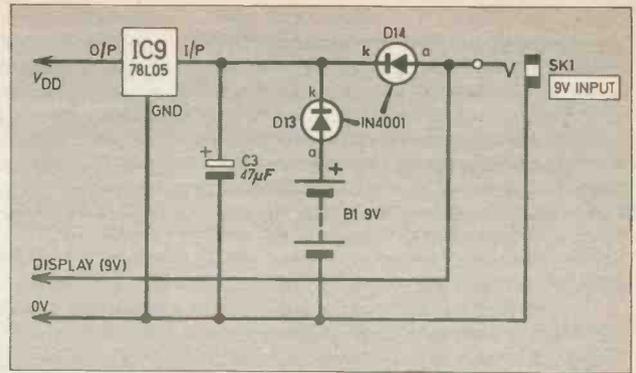

of 16 and 31, pin 11 of IC4 is at 1, thus IC6 WE is at 1 and the IC7 ME is at 0. IC7 is now the active memory.

To read information from the memory, the write enable WE input must be at 1. A READ cycle is accomplished by causing a 1 to 0 transition of the ME pin while the WE remains high. This happens as follows. The output of IC1 is a negative pulse of about 32µs. The falling edge of this pulse increments the binary counter (IC4), thus establishing the address. This pulse is also applied to pins 8 and 1 of IC5 via D2, causing the ME pin of whichever memory i.c. is active to go high.

The rising edge of the time pulse will then cause the ME of the active chip to go low again, thus fulfilling the requirements for the information in the memory to be transferred to the outputs. This sequence of events happens automatically as the timing pulses arrive from IC1, since the WE (pin 3) are held high by R5, as S2 is normally open.

MEMORY INPUT

To write information into the chip the WE input must be low, and the ME input must see a 1 to 0 transition. To do this, when S1 is pressed the counters will increment one count every second until the required date is reached. On pressing S2, the WE input goes low, and the ME input also sees a 1 to 0 transition from the negative pulse transmitted via C2 and R5. D2 is included to stop this WRITE pulse from being transmitted to the inputs of IC3 and IC4 and incrementing the counters.

On receiving this 1 to 0 transition, the data at the inputs of the i.c. is written into the memory at the selected location. The DATA inputs are pins 4, 6, 10 and 12, and in this design represent the range from the LSB (least significant bit) to the MSB (most significant bit) in that order. Pins 4, 6, 10 and 12 are tied to VDD by R9 R8 R7 and R6 respectively.

By switching in any of S3 to S6, the information can be set. For example, if S3 and S4 are closed, the information presented to the DATA

inputs is 0011 (3). However, the information at the outputs is the complement of the inputs. So if 0011 is set at the input, the outputs would give 1100.

This difficulty is easily overcome merely by relabelling the switch positions 1 instead of 0, and 0 instead of 1. Having set the switches to the desired information, pressing S2 will write the information into the memory.

POWER SUPPLY

Almost all the current in the circuit is consumed by the displays and the i.e.d.s. The unit is therefore intended to be powered by a 9v calculator adaptor, which allows a permanent display of the date and event. However IC1 is only specified to a maximum of 5.5V. So a 5V regulator, IC9, is used to provide the V_{DD} voltage.

However, should for any reason the power supply be cut off, then all the stored information will be lost. To avoid this, a back up battery is used. The circuit in Fig. 3 shows the

arrangement. When the power is coming from the adaptor and is cut, the base current supply to TR1, and also the supply to D3 to D12, is cut. Hence, the displays are disconnected, but the back up battery supplies current to the i.c.s and the information is retained.

The current supply in this case is about 2mA so a PP3 battery can supply enough current for many hours. Diodes D13 and D14 stop one supply feeding current into another.

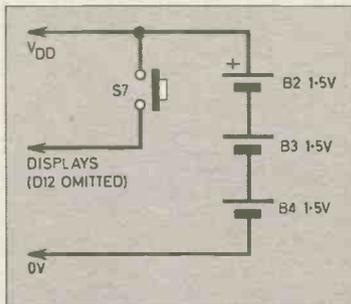


Fig. 4. Optional battery only power supply. The display is enabled with S7.

If the 9V adaptor voltage drops below 9V on load, a 1N4001 diode must be added in series with D13, effectively reducing the voltage at which the back-up battery is brought in.

Therefore, the output of the adaptor must be measured, on load, to determine if this diode is required.

For flexibility in positioning, the supply circuit shown in Fig. 4 can be used. Using 3 1.5V cells, the display will only light when the additional switch, S7, is pressed. With the low consumption the battery life should be over a year.

COMPONENTS

D1 may be any red i.e.d. but a 3mm is advised for size consideration. Use good quality i.e.d.s for D8 to D11 since the current drive from the output of IC8 is not high. Any colour or size may be chosen, the prototype used a 3mm with a mixture of colours. D12 should be a green i.e.d. since the circuit is employing the forward voltage drop to prevent the diodes from passing current into the outputs, which are off.

The seven segment displays may be any one of the following: TIL313, DL304, HP5082 as they are pin for pin equivalents of the MAN3740.

The two 40114 memories given in the components list are pin for pin equivalents for 74C89 i.c.s. It would be possible to use a 74LS42 (TTL) for IC8, but the overall current would increase by about 8mA which would slightly reduce the back-up battery life in the situation where the mains adaptor is frequently disconnected.

Switches S1 and S2 are push-to-make circuit board mounted types, designed for making up keyboards.

CIRCUIT BOARD

All components except for D3 to D11 are mounted on a piece of 0.1 inch matrix stripboard, 62 holes x 39 strips. Fig. 5 shows the layout. This diagram also shows the breaks made in the copper tracks.

Use of i.c. sockets is recommended since the removal of i.c.s is often necessary when debugging circuits.

There are many wiring connections to be made, and many breaks to be made in the tracks, so some constructional errors may occur, so take care.

The 8-pin d.i.l. switch is mounted on the copper side of the board, using small pieces of wire soldered to the tracks and soldered to the d.i.l. tags on the other side of the board. Discarded leads are useful for this.

Solder the capacitors, transistors, and diodes as close to the board as possible so that they do not stand proud of the mounted ICs. Use veropins for making the connections from the board to i.e.d.s D3 to D11.

COMPONENTS

Resistors

- | | | | |
|-------|----------------------|------|-----------------------|
| R1, 2 | 18k Ω (2 off) | R4-9 | 100k Ω (6 off) |
| R3 | 10k Ω | R10 | 1k Ω |
- All $\frac{1}{4}$ W carbon $\pm 5\%$

Capacitors

- | | |
|----|--------------------------------------|
| C1 | 4.7pF sub-miniature ceramic plate |
| C2 | 0.0047 μ F polyester, axial lead |
| C3 | 47 μ F 16V tantalum bead |

Semiconductors

- | | |
|------------|-----------------------------------------------------------------------------------------|
| D1 | Miniature (3mm) red i.e.d. |
| D2, 13, 14 | 1N4001 silicon rectifier (3 off) |
| D3-11 | Miniature (3mm) i.e.d. colours to suit (9 off) |
| D12 | TIL221 0.2in green i.e.d. |
| TR1 | BC108 silicon npn |
| IC1 | E050-16 1-bit clock timer |
| IC2, 3 | 40110B CMOS decade up/down counter/driver (2 off) |
| IC4 | 4520B CMOS dual binary up/down counter |
| IC5 | 4011B CMOS quad 2-input NAND gate |
| IC6, 7 | 40114B (74C89) 64-bit random access memory (2 off) |
| IC8 | 74C42 CMOS b.c.d. to decimal decoder |
| IC9 | 78L05 5V, 100mA regulator |
| XTAL1 | 32,768Hz miniature tubular quartz crystal |
| X1, 2 | MAN3740 (TIL313, DL304 or HP5082) 0.3in high, 7-segment, common cathode display (2 off) |

Miscellaneous

- | | |
|-------|---------------------------------------------------------------|
| S1, 2 | Push-to-make miniature keyboard switch (2 off) |
| S3-6 | 4-s.p.s.t. 8-pin d.i.l. switch |
| S7* | Push-to-make miniature push button |
| SK1 | P.C.B. mounting power socket to suit plug on 9V mains adaptor |
| B1 | 9V PP3 battery |
| B2-4* | 1.5V size AA batteries (3 off) |

0.1in stripboard, 62 holes by 39 strips; single sided copper clad Paxolin or s.r.b.p. sheet, 175 x 125mm (front piece); wooden picture frame, internal dimensions 175 x 125mm; red plastic display filter, 65 x 35mm; 9V mains adaptor; PP3 battery clip; 3mm i.e.d. mounting clip (9 off); 16 pin d.i.l. holder (7 off); 14 pin d.i.l. holder (3 off); 1/0.6mm sleeved wire for board links; 7/0.2mm wire for interconnections; 6BA or M2.5 spacers, 13mm long (4 off); 6BA or M2.5 screws, 6mm long (8 off); 6BA or M2.5 nuts (3 off); 6BA or M2.5 nylon screw, 6mm long.

* Components marked thus are only required for battery only operation.

COMPONENTS
approximate
cost **£34.00**
excluding 9V P.S.U.

See
**Shop
Talk**
page 567

MONTHLY PLANNER

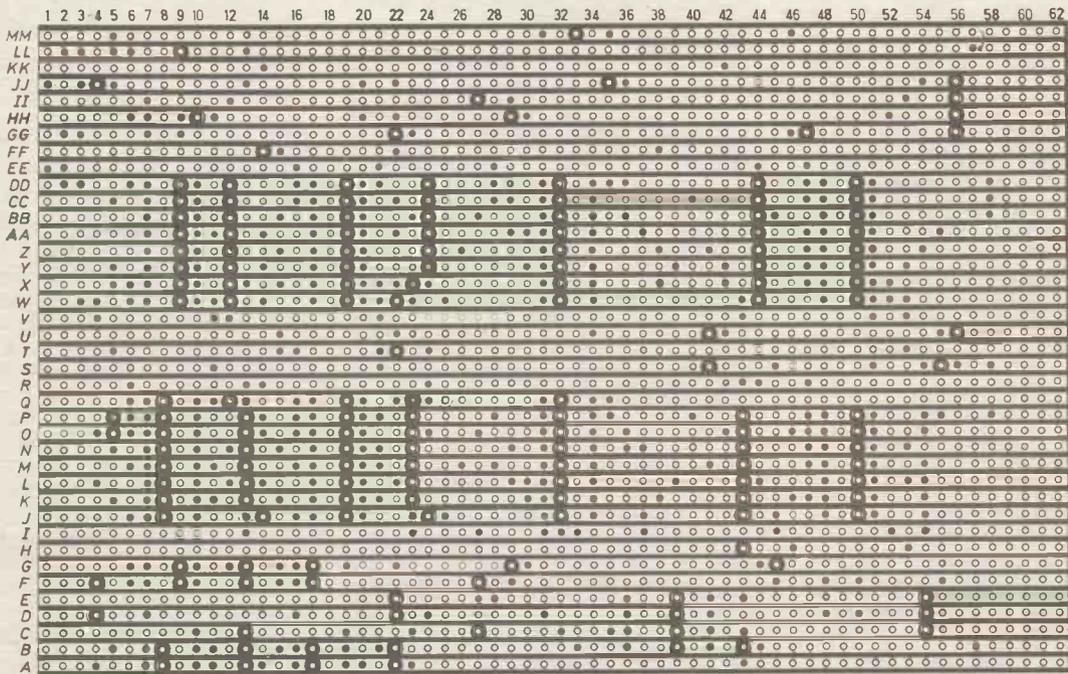
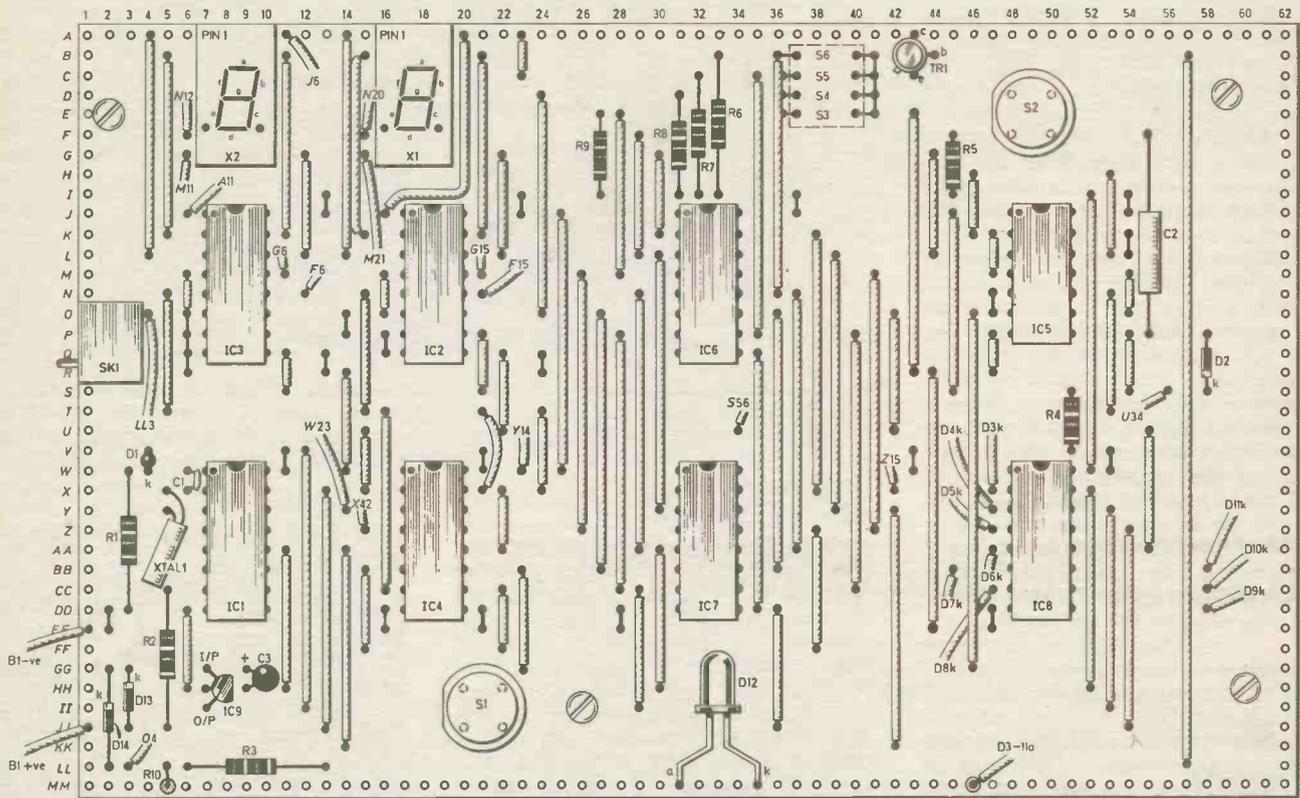


Fig. 5. Stripboard component layout. Note that the 8-pin d.i.l. switch (S3 to S6) is mounted on the copper track side of the board. The underside view shows the positions of the track breaks but omits the d.i.l. switch for clarity.

FRAME

Owing to the nature of the project, the unit should ideally be housed in something more attractive than the usual plastic box. To this end, the prototype was housed in a commercially available photograph frame of internal dimensions 125 x 175mm, the glass is replaced by a piece of p.c.b. of the same size. Use metal polish to polish the copper to a bright finish. Copper board with a paxolin base, besides being much cheaper, is also better than glass fibre for this purpose, since the woven texture of glass fibre tends to come through the copper.

Drill the holes for the diodes D3 to D11, the holes for S1 and S2, and cut out a rectangle 43 x 25mm for the display window. Repolish the board if necessary. Also drill the pillar support holes using the p.c.b. as a template and finally spray a clear varnish on the board to stop the copper from tarnishing. The use of copper board as a frontpiece can be made to look very effective.

On the prototype model, two white panels of self-adhesive p.v.c. sheet were stuck in the position shown in the accompanying photographs. On this, the functions of each event l.e.d. can be written in felt pen (although we used Letraset on the model) and wiped off should the event change.

Another possibility, if the picture frame system is used, is to use a card over the frontpiece with suitable cutouts for the displays and l.e.d.s, and to replace this every month with a fresh set of events written in.


The strip board is held to the frontpiece using four 0.5in long 6BA spacers. The switches S1 and S2 should just protrude through the holes drilled in the frontpiece. Use a red plastic filter to cover the window for the display. The l.e.d.s are held in place on the frontpiece using bezel clips.

The back up battery can be tied to the stripboard using wire threaded through the holes.

SETTING UP

No calibration is required since the timing depends on the crystal frequency and any minor trimming of this crystal would be beyond the means of most constructors.

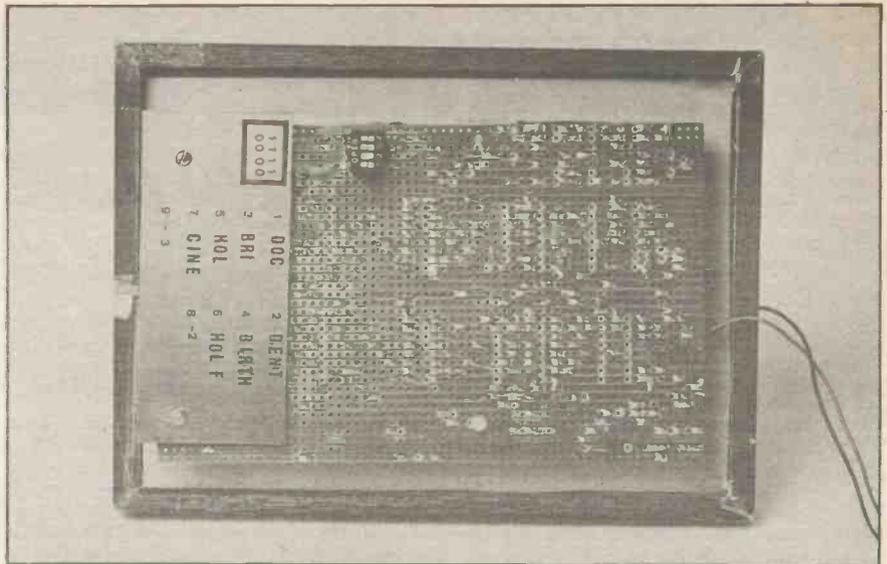So assuming the unit is debugged and working, the first thing to be done is to synchronise the binary and decimal counters. Do this by pressing S1 (SET) and waiting until the date display resets to 1. This may take a long time depending on the random number in the binary counter when first switched on. A quicker way is to momentarily short pin 5 of IC2 or IC3 to V_{DD} . The display will zero.



Rear view of the framed Monthly Planner showing the position of d.i.l. switches S3 to S6. An additional board was fixed to the rear of the prototype unit to show the codes for each event (given here as a decimal number). Note the use of the nylon screw in hole //26.

Note the date, when automatically reset by the binary counter, will reset itself to 01 and not 00, for the following reason. The binary counter increments on the leading edge of the pulse so on the 32nd pulse both counters are reset by the leading edge, a process which takes less than 1 μ s, and 32 μ s later the trailing edge of the timing pulse increments the date (decimal) counter. The difference in count will always be the same and therefore is of no consequence for the working of the unit.

Table 1. Event input codes. Note switch open = 0 and switch closed = 1.

EVENT	BINARY CODE			
	S6	S5	S4	S3
No event	0	0	0	0
Doctor (D3)	0	0	0	1
Dentist (D4)	0	0	1	0
Bridge (D5)	0	0	1	1
Birthday (D6)	0	1	0	0
Start holiday (D7)	0	1	0	1
End holiday (D8)	0	1	1	0
Cinema (D9)	0	1	1	1
Aux. 2 (D10)	1	0	0	0
Aux. 3 (D11)	1	0	0	1

The unit can now be programmed. When the programming switches S3 to S6 are open then the information at the programming inputs are 1111, and 0000 when all these switches are closed. However, because the information of the output is the complement of that of the input, it will be necessary to label the open position as an "0" and closed position as "1" S3, S4, S5 and S6 represent the LSB to the MSB respectively.

To aid the setting up procedure, a small plate was screwed to the back of the stripboard and labelled with the event codes and the "1" and "0" positions of switches S3 to S6.

EVENT INPUT

To write the events for each day of the month into the memory, the procedure is as follows:

Suppose that, for example, the bridge club meet on the first day of the month, then ensure that the date reads 01 and set up the code for BRIDGE on switches S3 to S6. From Table 1, that code is 0011 (switches S3 and S4 closed and S5 and S6 open) and when set, press S2 (WRITE) and the information is put into the memory.

Proceed to day 02 by pressing S1 (SET) and enter the code for the event planned for this day. If nothing is planned, the memory must be told by writing in the NO EVENT code, 0000 (all switches open) and pressing S2 (WRITE).

Continue through all the days in the month, inserting the relevant event code for each with S3 to S6.

Remember that NO EVENT must be entered on all days on which nothing is scheduled. It is not necessary to use all nine event codes and events can be duplicated on different days should, for example, the dentist need be visited twice in the same month.

To make the timer send out its daily pulse at midnight to change the date, it will be necessary to stay up once until midnight and momentarily short pin 5 of IC1 to 0V ("sx" on fig. 2). This resets all the internal counters. This operation will need to be performed again if the power from both the supplies it cut.

The information written into the memory can be read non destructively any amount of times merely by pressing S1 until the required date is reached. Finally, when the monthly information has been written, the correct date is set with S1. □

**Everyday
ELECTRONICS**

Free TRANSISTORS

For use with the **OCT. issue**
General Purpose Pre-amplifier
and Sine Wave Generator

OCT 1982

ISSUE ON SALE
FRIDAY, SEPT 17

For Beginners—New 6 Part Series

INTRODUCING **ELECTRONICS**

An easy treatment of the basic theory from d.c. circuits through to analogue and digital systems. Illustrated with simple experiments using standard components connected up with 2-amp terminal blocks. The solderless technique employed makes this the ideal series for newcomers.

SEDAC

Prize Winning Project

COMPUTER EXPANSION SYSTEM

A motherboard for the ZX81 Computer containing 4K bytes of static RAM. Plugs into the back of the ZX81 to provide unique address decoding signals for a further eleven 1K blocks, and these with buffered address and control lines and data bus are available at three parallel single-sided sockets for user defined expansion. Equipped with RESET and assisted +5V supply.

PLUS

**OPTICAL TACHOMETER
CAR LIGHTS ALERT
SIMPLE SHORT WAVE RADIO**



Consumer Electronics Show

IN America, interest in hi fi and audio is still declining; the video cassette market is stabilising; video-discs are not selling as well as expected and the video games market is booming so fast it could soon produce a glut of outmoded games cartridges on the market and commercial casualties among firms selling them. These are the clear signs which emerge from the 1982 Summer Consumer Electronics Show, held in Chicago, in June.

CES is now acknowledged as the largest, and most important, exhibition of its kind in the world. It is also the most influential. Around 70,000 wholesalers, retailers and journalists from all round the world congregate for four days to look at new products from over a thousand companies. What they see, think, order for their shops and write about in print can have a decisive effect on what the public buys over the next year.

HI-FI AND COMPUTERS

In America, as in Europe, the audio and hi fi trade is suffering badly both from the recession and widespread interest in video. The large manufacturers hope that things will pick

up again when the Compact digital audio disc is launched. But lack of interest amongst American record companies has put back the digital disc launch until at least this time next year, or six months after the launch scheduled for Europe and Japan.

Home computer sales are clearly on the rise and it was good to see Britain's own Sinclair system attracting much attention on the Timex stand. It sells in the USA for just under one hundred dollars.

VIDEO MARKET

The video cassette market in America has now stabilised, with a split of around two-to-one between VHS and Beta formats. Plans to launch the European V2000 format have now been shelved.

JVC has now shown a miniature VHS portable recorder, called VHS-C. This is smaller and lighter than any other portable recorder using half inch tape, because it uses a scaled down version of the standard VHS cassette. The tape can be replayed either in the portable, or in a standard domestic VHS recorder using a dummy VHS cassette in which the mini cassette is temporarily housed.

Stereo VHS recorders, with Dolby B noise reduction, are now available, along with pre-recorded stereo VHS software. So far there has not been a stereo Beta machine on sale in the USA, although they are available in Japan. Sound quality is always a problem with stereo on a domestic video format, because the slow running tape has only a narrow audio track, and splitting it in half for stereo degrades the already poor signal-to-noise ratio.

Sony has now developed a system for encoding stereo sound inside the video waveform. Although the company refuses to explain how this is done, it seems that the waveform coding is in addition to a conventional linear track in mono or stereo. This preserves compatibility with existing Beta machines and tapes.

LASERS AND DISCS

Laservision players and videodiscs have been on sale in the USA since December 1978 and the cheaper RCA Selectavision disc system has been sold since March 1981. Both formats were on show at Chicago, with much puff and publicity. But the retail sales of both formats have been disappointing. This has caused JVC and

Thorn-EMI to pull the plug on VHD, the third videodisc system which was scheduled for launch around the world this summer. No firm date for a VHD launch has been set.

The US trade breathed an audible sigh of relief at the delay on VHD because shop keepers already have difficulty in explaining to customers the difference between the two incompatible disc formats. They do not welcome the added confusion of a third, and again, incompatible format.

VIDEO GAMES

The video games market is booming, largely because several companies are now making games cartridges for consoles sold by other companies. It is, for instance, now possible to buy a games cartridge

for an Atari video game from nearly a dozen different software companies.

Even Mattel, makers of the rival Intellivision system, now offer Atari cartridges. But to confuse the issue even further Atari has now announced the launch of another games console which is incompatible with the Atari units and cartridges already on the market.

As most of the games available are either banal, boring or pander to our baser violent instincts, the video games explosion is not altogether welcome. Also, because of competition, ever-more complex games appear every day. So some manufacturers may soon go out of business and suffer the same fate as the video graphic blips which their game players must strive to eliminate.

TELEVISION

The USA has not yet agreed on a standard for the transmission of stereo sound with TV. Three different multiplex systems have been proposed, none the same as that being recommended as the European standard. There is also no agreement on a.m. stereo, with six competitive systems trying to win support on the open marketplace. There is no agreement yet on direct broadcasting by satellite. But many video buffs now own three metre wide dishes which enable them to tap into the satellite links between cable stations. In this way they can watch pay TV programmes free of charge—at least until the stations start electronic scrambling. □



LETTERS

Everyone needs a Woolies

Dear Mr. Fox,

I am writing to you to defend the vicious attack you made on Woolworth's employees in your article *For Your Entertainment* on MFP (Music for Pleasure) records in the July Issue of *EVERYDAY ELECTRONICS*.

First of all I don't understand what you mean by "shops like Woolworths". Firstly you should have written "shops like Woolworth", and secondly there is no other shop like Woolworth. The reason for this is that Woolworth is a general store stocking a lot of different items, and not specialising in any fields whatsoever.

When you say "shops like Woolworths" I suppose you mean shops such as Boots and Tesco whose names are mentioned at the end of many adverts with Woolworth in the "and other leading stores" category. Well these stores specialise in toiletries and food respectively. Other "general stores" are usually very big, for example, Bentalls, Chiesmans, like their prices! So you see there is no other shop like Woolworth. Anyway I digress.

As for the "assistants often know next to nothing about what's available", firstly it's very difficult to keep track of what

albums are sold as the stock is very large, and there is usually more than one helper in the record department, so that one rarely knows what has and has not been sold, and thus what is and what is not in stock. After all the assistants are only human and not computers as most customers would want them to be.

Secondly, with regard to actual MFP records, do you know how difficult it is to stock them? Obviously not if what you write is anything to go by. I can tell you that Woolworth only sells them as a service and not as a profit making item. This must be true for all the stores that sell MFP records. This therefore is bound to get the albums neglected and put to the back "out of the way". Also the suppliers of these albums don't go out of their way to help the retailers. All they do is give the retailer an MFP turnstile rack and a batch of records to fill it up with and that's it.

Only when one particular album has sold an obvious greater amount than the others can a retailer order a set of that particular record. That is a very rare occurrence and more often than not what happens is that when the stocks in the MFP rack have become low, the suppliers are informed and another batch of assorted records is sent up. You'd be very lucky to get one of the more popular albums!

So you see it's very difficult for a retailer to keep track of what's in the rack. This explains both the knowing "next to nothing" and why other specialist shops do not stock MFP records: they're just too much bother!

I have worked on and off for Woolworth for two and a half years now, and am fed up with people "slanging them off" at every opportunity. It is a good general store with the items sold being of good quality. Any item which is not will automatically be exchanged since the after-sales service is on the whole very efficient. Most important is the fact that the prices are kept as low as possible.

I hope you publish this letter so that the readers of your article will be able to hear both sides of the story. It's rotten to take the poor service of the suppliers of MFP records out on Woolworth, it's not Woolworth's fault!

Martin Gosling,
Chessington,
Surrey.

I am quite happy for the editor to publish your letter in its entirety.

I am sorry you think I made a vicious attack on Woolworth. I can only say I have watched what I regard to be the decline of British Woolworth with disappointment.

Two stores near my home in North London have recently closed and I can't say I am surprised. Prices were high compared to other shops. The range of goods was very poor.

In America the story is very different. Frankly I would not be surprised if Woolworth finally go out of business in Britain, although I would be sorry because we need a general store of this type.

I note your comments on MFP with interest.

Barry Fox.

Everyday News

TOP MARKS FOR SCHOOLS

Minister applauds budding engineers at SEDAC prizegiving ceremony

THE first Schools Electronic Design Award Competition (SEDAC), sponsored jointly by Mullard Ltd, and EVERYDAY ELECTRONICS, reached a splendid and exciting climax on June 29 when the final judging and presentation of prizes took place in Mullard House, London.

The finalists—12 in all—came from schools all over the country. From Durham, Middlesex, Dorset, Surrey, Leicester, West Midlands, Lancashire, Cornwall and Yorkshire. It said something for the determination of the contestants that, in spite of a crippling rail strike, there was a 100 per cent turn out.


Opening the prizegiving ceremony, Ivor Cohen, managing director of Mullard Ltd., stressed the importance of technology to the future of the country and praised the enthusiasm and hard work that schools had obviously put into their projects.

Pat Barnes, managing director of the Youth & Practical Group, IPC Magazines Ltd., endorsing Mr. Cohen's remarks, said: "If SEDAC has helped concentrate attention on the importance of encouraging an interest in technology among our youngsters—all of whom are growing up in an age of increasing technological development—the efforts of all those concerned with organising the competition have been amply rewarded."

The prizewinners, who received their awards from William Shelton, MP, Parliamentary Under-Secretary of State, Department of Education & Science, were as follows:

- 1st: Peel Sixth Form College, Bury, Lancs. £150
The SEDAC Trophy and components to the value of £100.
- 2nd: Burscough Priory High School, Burscough, Lancs. £100 and components to the value of £100.
- 3rd: Mellow Lane Comprehensive School, Hayes, Middlesex. £50 and components to the value of £100.

The runners-up were Belmont Comprehensive School, Durham; Queen Elizabeth's School, Wimborne, Dorset; St. Peter's & Merrow Grange Comprehensive School, Guildford, Surrey; Lutterworth Grammar School, Leics; High Park School, Stourbridge, W. Midlands; Richard Lander School, Truro, Cornwall; Aireborough Grammar School, Leeds, Yorks; Tettenhall College, Wolverhampton, W. Midlands; and Hollins High School, Accrington, Lancs. All received components to the value of £50.

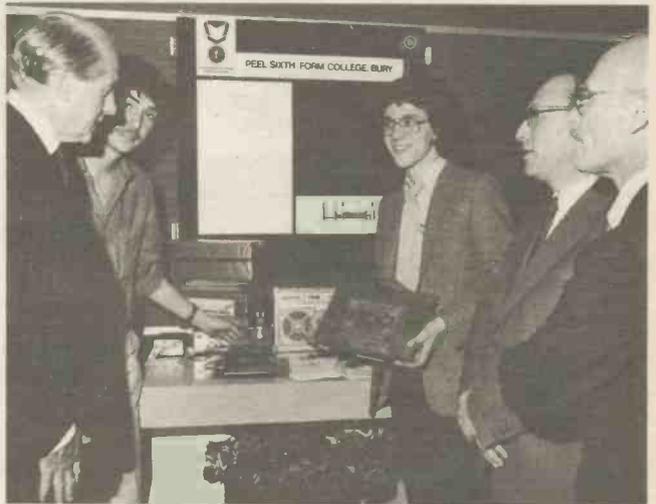

The proud winners of the 1982 SEDAC Trophy, Anthony Hudson and Martin Lysejko of Peel Sixth Form College show off the trophy to the Minister William Shelton, MP, Ivor Cohen of Mullard and Pat Barnes of IPC Magazines Ltd.

The top prizewinners' project was a ZX81 Microcomputer Expansion System, Burscough Priory High School's entry was an Oscilloscope Companion. And a Velocity Measurer won third prize for Mellow Lane Comprehensive.

In his address the Minister congratulated all concerned and said he was impressed especially by the practical aspect of the competition—for in addition to preparing a written paper the contestants had to produce a working model for final assessment. Mr Shelton emphasised the government concern that involvement in technical subjects such as electronics be fully encouraged amongst our school children. Registering some surprise that there were no girls amongst the finalists, Mr. Shelton hoped the fair sex would demonstrate their interest in technology by coming forth in strength in next year's competition.

Winding up the ceremony, Mr Barnes made the announcement that the competition would be run again in 1983.





SEDAC TROPHY

A specially designed trophy was awarded to the winner of the Schools Electronic Design Award Competition.

As a fitting symbol of contemporary electronics this trophy is in the form of a high grade glass fibre printed circuit board. The copper tracks are gold plated.

The p.c.b. is mounted on a polished wooden base and this carries a small brass plate engraved with the name of the school and title of the winning project.

JUDGING PANEL

Scrutiny of Papers (Stage 1) and evaluation of working models (Stage 2) was performed by a panel of four judges representing the two sponsoring parties. The panel members were:

Gerald Crowther	Head of Application Laboratory, Mullard Limited.
John Warren	Technical Manager, Consumer Electronics Division, Mullard Ltd.
Fred Bennett	Editor, EVERYDAY ELECTRONICS.
Brian Terrell	Assistant Editor, EVERYDAY ELECTRONICS.


The judges' task was difficult and exacting. After long and careful deliberation—with the objects of the Competition always in mind—the declared results were agreed unanimously.

The judges wish to record their admiration for the generally high standard throughout, both in the presentation of written work and in the practical realisation of the designs. All students participating deserve the highest commendation. Those who, in several instances, worked entirely alone merit additional praise. All did honour to their schools, a fact that will surely be recognised by these establishments. Their efforts provide a model for members of other schools to emulate in future contests.

(far left) Simon Rainey of Burscough High describes the merits of his Oscilloscope Companion project to the Minister. This won Simon second prize in the competition.

(centre) Balijinder Dhanda, Michael Finnemore and Michael Stallery, from Mellow Lane Comprehensive, look anxiously as judges inspect their Velocity Measurer. This project was eventually placed third.

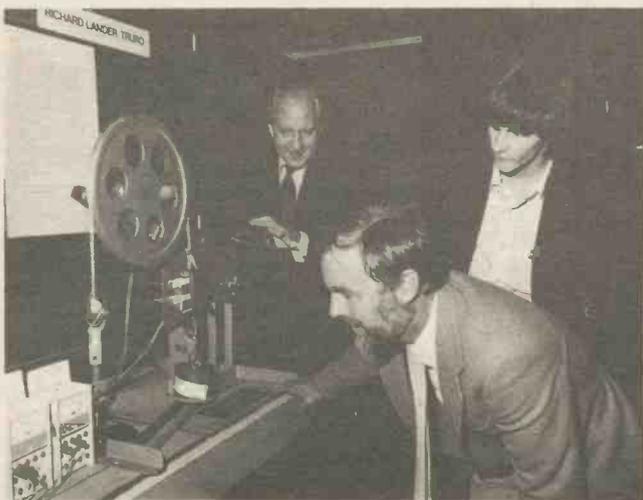(below) Putting the Minister to the test on his Digital Readout Ergometer is Mark Vaughan of Richard Lander School.



A VISITOR'S VIEW

On June 29, the 12 finalists for the 1982 Schools Electronic Design Award Competition all gathered together at Mullard House in London to meet the judges and the press to demonstrate and discuss the end result of the past few months labours. As the final decision as to who was the overall winner of SEDAC 82 was not to be made until the judging panel had seen all the finalists involved and chatted to the pupils, the atmosphere was one of tense excitement.

And indeed it was a close run event, for the quality of the entries was very high.

It is interesting to note that out of the 12 finalists, no fewer than five had utilised computers in their entries (four of these the ubiquitous Sinclair ZX81!) thus illustrating the mating of these two branches of technology—electronics and computing.

But perhaps the most important factor to emerge was the sheer usefulness of all the entries; all had been designed with a specific application in mind. Ranging from the Bee Hive Temperature Meter from Aireborough Grammar School which evolved from a liaison between the school's bee-keeping club and electronics club, to the sophisticated ZX81 Microcomputer Expansion System from Peel Sixthform College.

This was the eventual winner and consists of an ingenious system to extend the application of the ZX81 to enable it to be used as a teaching aid. By means of a motherboard plugged into the back of the Sinclair unit, additional daughterboards are incorporated into the system, each with a specific function or task. The example on show at the judging ceremony analysed the classic physics experiment of determining the acceleration due to gravity and displayed the result graphically on the screen.

This project was developed by two sixthformers, in what proved to be a most successful team of one hardware man and one software man.

The second prize, a solo

effort from Burscough High School, went to the Oscilloscope Companion. This equipment will also perform a very valuable function within the school, for it is, as its name suggests, a unit to expand the facilities available on a simple single beam oscilloscope.

The third prize winner also has its application rooted in the school's physics laboratory, for Mellow Lane Comprehensive School's Velocity Measurer supersedes the old "ticker tape timer" in performing velocity measurements even on objects as diverse as parachutes and rolling footballs!

However, it was not necessary to be at "the state of the art" to be considered as a winner. Provided that the idea was good and the execution of that idea practical, the entries did not have to be too sophisticated circuit-wise. This was illustrated by some of the runners up and in particular St Peters and Merrow Grange Comprehensive School with their Logic Demonstrator, a console type unit to teach the principles of Boolean algebra.

Although the complete list of all the other runners up is too long to describe in detail, another one does deserve a mention as it proved quite popular with those attending the prize-giving, and that is The Electronic Pressure Gauge from The Hollins County High School.

This project measures lung pressure and displays the result on a graph of pressure vs. time and also calculates and records maximum level attained. Quite entertaining when invited to blow into a piece of plastic pipe and have the results appear before your eyes!

The overall impression was one of competence and confidence amongst the pupils in an event thoroughly enjoyed by all those who took part. Which brings us back to the purpose of SEDAC; if these are the electronics engineers of tomorrow then the future certainly looks good. Congratulations to students and staff alike.

SCHOOLS Electronic Design Award COMPETITION

THE TWELVE WINNING DESIGNS

Bee Hive Temperature Meter


Aireborough Grammar

Mr. B. Thorp (teacher), Andrew Smith (12),
Jonathan Green (12), David Allewell (13),
Andrew Green (13)

THE beekeeping club at the school wanted to follow movement of the bee cluster in a hive during the winter months, and analyse the movement with respect to external factors and conditions. It was decided to use a temperature sensor to determine the cluster position from the body heat of the bees. The information was gathered from ten sensors at known positions in the hive.

A digital voltmeter was used in the project in a novel way to allow the display reading to be interpreted directly as degrees Celsius.

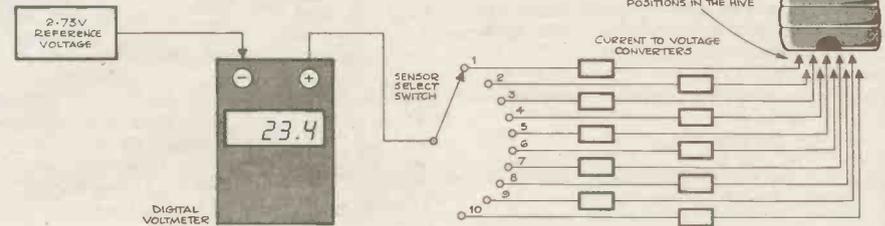Ten precision temperature sensors are used to monitor the temperature at the top of each frame in the hive. These sensors operate in a similar manner to a Zener diode, and have a breakdown



voltage directly proportional to the absolute temperature ($^{\circ}\text{K}$). The output voltage obeys a linear relationship with temperature and is equal to $10\text{mV}/^{\circ}\text{K}$. On board calibration circuitry provides an accuracy of 1°K .

The sensor voltage feeds one input of the digital voltmeter. The other input is maintained as 2.73V by means of a precision voltage reference i.c. Thus the reading on the display is in degrees Celsius ($0^{\circ}\text{C} = 273^{\circ}\text{K}$).


Computer Control Interface

Belmont Comprehensive

Mr. S. Duncan (teacher), David Morton (14),
David Williamson (14)

A COMPUTER interface unit allows a computer access to the "real world". This project has been designed to provide such access for the very popular ZX81 Personal Computer. It plugs into the ZX81 bus and is constructed to show how software may be used to control external devices, in this case two filament lamps. The lamps may be replaced by other electronic devices such as relays, thyristors, motors, electric valves to control complex circuitry and machinery.

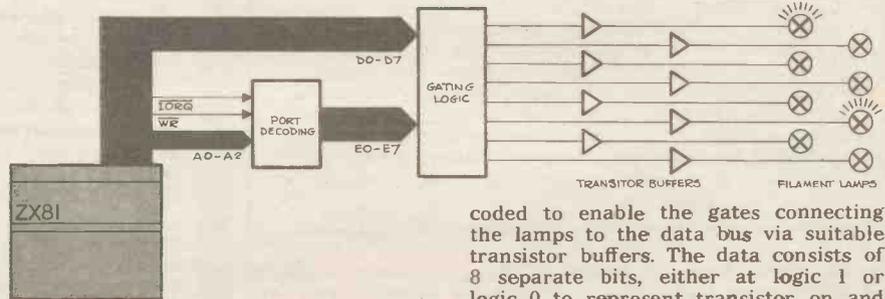The control information reaches the various external devices along the computer data bus (8-bits wide) and is routed to the appropriate device by decoding the information appearing on the address lines at this time.



The existing software commands the computer to repeatedly send data to a particular port number, 0C. The port number appears on the lower half of the address bus at this time and is de-

coded to enable the gates connecting the lamps to the data bus via suitable transistor buffers. The data consists of 8 separate bits, either at logic 1 or logic 0 to represent transistor on and off states respectively. The data is modified for each successive "out" command so the transistors are constantly being turned on and off which results in the lamps flashing on and off.

Oscilloscope Companion


Burscough Priory High

Mr. M. Earnshaw (teacher), Simon Rainey (16)

THIS inexpensive unit will convert a single beam 'scope with ext. sync. input to a dual beam version, expand the Y-amp volts/cm in both directions, allow current measurements to be taken from the screen display, display peak levels for easy reading from screen and has a time base delay. A precision rectifier/buffer is incorporated to allow a voltmeter to be connected for more accurate measurements of voltage and current.

The unit plugs directly into the oscilloscope Y-amp input set to $1\text{V}/\text{cm}$ and signals to be investigated fed to left and/or right channel inputs on the unit. By means of a number of switches, the input signals may be routed through to any of the Companion's function blocks.

Input impedance is in the order of

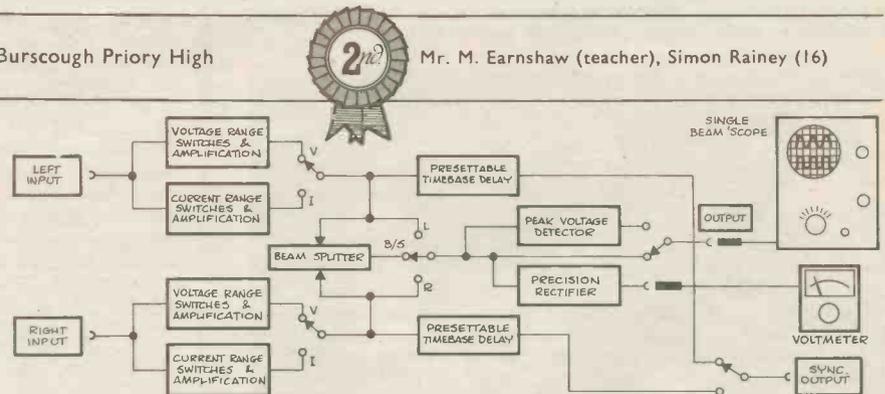

10,000 megohms which makes special measurements possible such as those associated with bio-activity and pH values. Input voltages from 1mV to 50V in 15 ranges may be measured.

The Beam Splitter facility permits two waveforms to be displayed simul-


taneously, one above the other readily allowing frequency and phase shift comparisons to be made. Either waveform may be used for synchronisation.

The Peak Voltage Detector detects the highest positive input voltage and remembers it for about 10 seconds.

This project was devised to overcome the inaccuracies associated with the ticker tape method of determining the velocity and equations of motion of a moving object using a ZX81 computer for data processing.

Velocity measurement experiments conducted in the school laboratory usually employ a "standard" three-wheel trolley and this has been retained in this project with no external connections. Ultrasonic soundwaves are used to transmit the data obtained on the moving trolley to an u/s receiver on the mains unit. This data is fed to the ZX81, processed and returned to the main unit display circuitry after completion of the experimental "run".

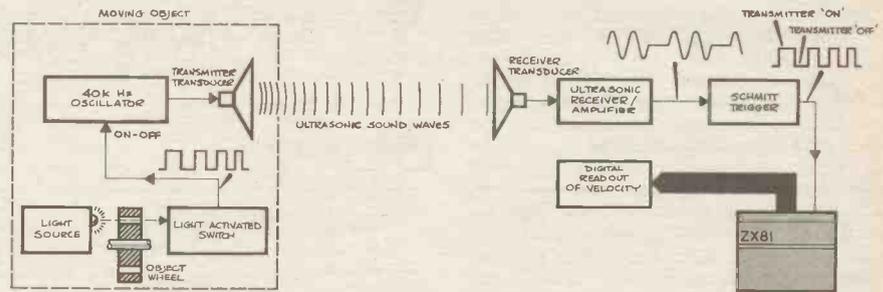One of the trolley wheels is drilled with two small holes diametrically opposite. These act as windows to open or close an optical link, an l.e.d. light



source on one side of the wheel and a light activated switch on the other. As the trolley moves, the light activated switch operates and turns the ultrasonic oscillator on. The on-to-off rate of the ultrasonic transmitter is therefore proportional to the velocity of the trolley. The transmitter on and off periods are

converted to logic 1's and 0's respectively. The software instructs the ZX81 to periodically read in this data to compute and store the trolley velocity. At the end of the "run" after a set number of readings, the ZX81 outputs the calculated velocity to the display and TV screen in chronological order.

Electronic Pressure Gauge


Hollins County High

Mr. J. S. Hagan (teacher), Darryl Grimshaw (16),
Michael Howarth (16)

This project was designed and developed for use in the school science laboratories where lung pressure was required to be measured. It replaces the previous difficult to control water manometer method. It also has other applications in the laboratory where pressure measurements are to be taken, and with suitable software could be employed as a fluid flowmeter with results displayed on a TV screen.

A ZX81 Microcomputer is interfaced to the Gauge hardware which reads in data processed by the on-board circuitry to plot a graph of pressure vs time, and calculate and display the maximum pressure level attained.

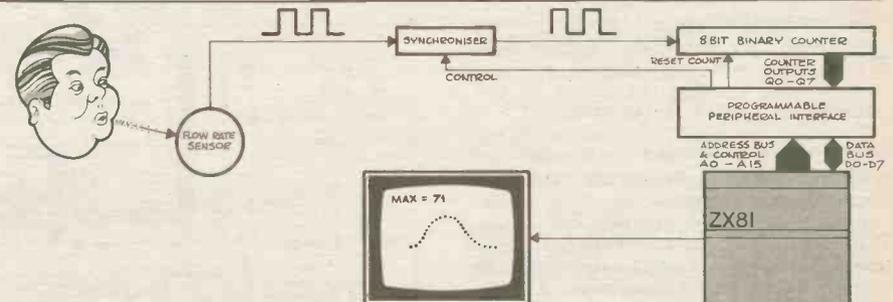The pressure produced by a person blowing down the plastic tube feeding the flowmeter sensor causes a paddle in the sensor to rotate at a speed pro-



portional to the applied pressure. Internal Hall effect switches in the sensor produce a train of pulses at its output. The pulse rate is thus proportional to the applied pressure.

These pulses are fed to a synchroniser circuit and then reach an eight-bit

counter. The software previously loaded into the ZX81 from cassette tape periodically reads the data in the counters, and then causes them to be reset for the next count sample while using the read information to plot the graph and compute maximum value.


Digital Results Storage System

Lutterworth Grammar

Mr. H. Rigby (teacher), Richard Moulds (18)

This system has been designed to automatically collect and store the results obtained from experiments, into a solid state memory device. After the experiment, the memory may be repeatedly scanned and the retrieved data processed to make it suitable for inputting to an oscilloscope or X-Y plotter, to obtain a quick graphical representation of the results. It is suited to those experiments where the results are in the form of a varying frequency (a train of pulses) or can be converted to this form.

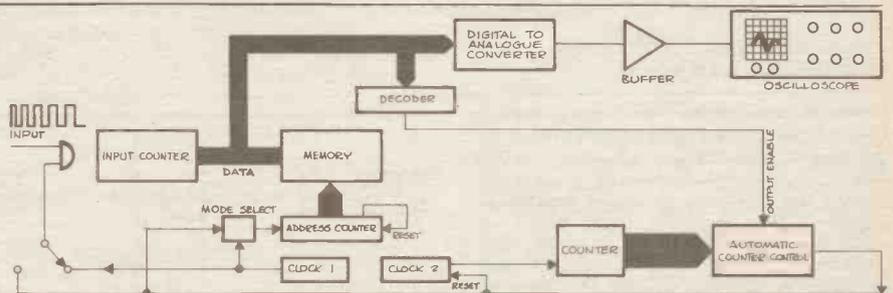The system can therefore condense the results of long duration experiments—possibly taking days to complete and display them over any time period (a few seconds for example) which is determined by the memory scanning rate. Also, very short duration experiments, say in the order of a few hundredths of a second, may be expanded by suitable setting of the memory scan rate control.



The system works by counting pulses over a preset period or over a period automatically determined by the time taken to fill the data input counter. The counting can take place continuously or at a predetermined count rate.

Basic operation is as follows: pulses arriving from the experimental output being monitored are gated to a counter. The counter outputs form the data to be written to memory. Internal address coding selects memory location and a

control signal is generated to write the data into the location. The address is caused to advance by one, ready for the next data word. In this way the memory is filled with the experimental result in digital form.

To output this data to a 'scope, internal circuitry repeatedly scans all relevant memory locations in sequence. The information is fed to an 8-bit D to A converter and its output scaled before reaching the 'scope for display.

Velocity Mesurer




Mellow Lane Comprehensive

Mr. S. Webster (teacher), Michael Stollery (14)
Michael Finnemore (15), Baljinder Dhanda (15)

THE Velocity Mesurer can be used in the laboratory with greater ease and accuracy than with conventional methods of taking velocity measurements, such as with the electro-mechanical ticker timer. It is capable of measuring small changes in velocity at selectable sampling rates, and to store this data in a semiconductor memory. After the experiment, the data may be read out in single steps to allow a velocity-time graph for any moving object to be plotted.

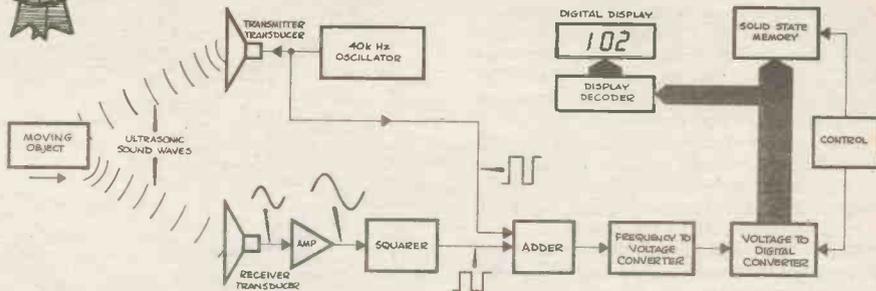The project uses ultrasonics for determining velocity of the object based on the Doppler effect. The unit emits a constant frequency 40kHz sound wave. This reaches the object and is reflected back to an ultrasonic transducer mounted on the unit. The moving object causes the reflected sound waves to apparently increase in frequency in proportion to its velocity.



The circuitry computes the difference in transmitted and reflected frequencies to calculate the speed of the object.

Sixteen spot velocity measurements are made during the motion of the object on release of the START switch, 5 per second, 10 per second or 50 per second depending on the setting of the Speed Selector Control Switch.

Outputs exist on the unit (1) to allow connection to a proprietary memory bank to store the results of many experiments which is able to feed a chart reader to automatically produce velocity-time graphs; (2) for connection to an oscilloscope to display velocity directly.

ZX81 Expansion System

Peel Sixth Form College



Mr. H. Meredith (teacher), Martin Lysejko (18),
Anthony Hudson (18)


PLUGGING this expansion system into the back of a ZX81 computer immediately adds another 4K bytes to the existing 1K bytes of RAM on board.

The system has its own regulator which helps share the load with the ZX81 resident regulator, and three 37 pin expansion sockets.

Signal lines A0 to A9, RD, WR and \emptyset from the ZX81 bus are buffered. High order address decoding generates 16 enable lines, with the lower 5 lines enabling RAM and the upper 11 lines reaching the expansion sockets.

RAM consists of $8 \times 2,114$ static RAMS (each 4 bits \times 1,024) configured to realise 8 bits \times 4,096. It is kept low in the memory map to ensure continuous RAM for Basic.

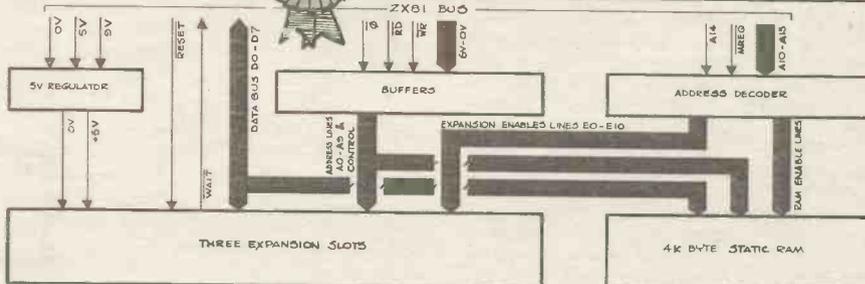The expansion socket bus reaches the 3 sockets wired in parallel and consists of the following: 0V, +5V, A0-A9 (buffered), D0-D7, \emptyset WR, RD, RESET, WAIT and 11 enable lines labelled E0-



E10. The latter are active low and enable blocks of 1,024 memory locations. These can be used to enable RAM, EPROM, I/O and any other device which is capable of supporting a bus.

The particular value of this piece of equipment (Motherboard) is its ability to allow inexpensive ZX81 computers to be used for acquiring data from in-progress experiments and display the processed results on a t.v. screen. Addi-

tional hardware (daughter boards plugged into the sockets) and software are needed to accomplish this.

Some ideas in mind for daughter boards and software are: measurement and graphical display of radioactive decay; a spectrum analyser; an I/O board for digital control applications; a serial I/O port for communication to RS232 devices such as printers/terminals.

Coulomb Meter


Queen Elizabeth

Mr. C. E. Saunders (teacher), G. Rafferty (17),
M. Shillabeer (16), S. Melhuish (15)

IN the school science laboratory, experiments are often carried out which require the calculation of the electric charge which has flowed in the circuit during the experiment. If the current is constant, this is easily done using an ammeter and a timepiece. In some electrolysis experiments the current can change considerably during the process. This makes continuous monitoring necessary with regular adjustments to maintain constant current.

A more accurate, reliable and easier to use system was sought and resulted in the design and development of the Coulomb Meter.

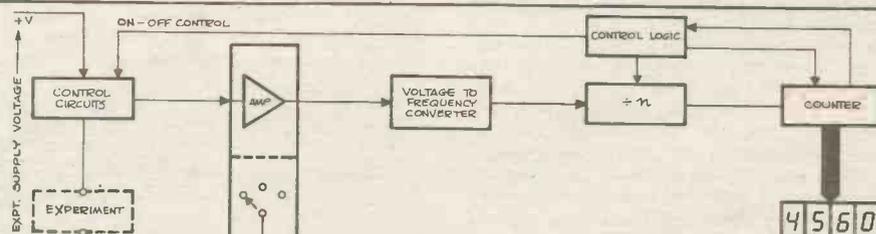The meter is able to read up to 1,000 coulombs and has a sensitivity from 1μ C/sec to 10^{-4} C/sec in five switched ranges. The large l.e.d. display which indicates charge flow is capable of being set in a count-up or count-down mode



to/from a preset value. When the preset value is reached, the unit switches off power to the experimental apparatus.

Experimental current flow passes through the range select/amplifier circuitry to produce a potential difference which is applied to the control inputs of a voltage-to-frequency stage (v.c.o.).

The output frequency is thus proportional to the current flowing.

The high frequency oscillator output reaches divider circuitry to produce a 10Hz display counter input for 1A experimental current to 0.1C.


Presettable inputs to the counter are set by means of b.c.d. thumbwheel switches. When the set value is reached, a control signal is produced that switches off experimental current flow.

An ergometer is a piece of machinery designed to allow the work input for a particular task to be determined. The machine to be used with this project consists of a wheel attached to a set of pedals by means of a chain. A piece of rope is hung over the wheel rim held taut by mass at one end. As the wheel is turned via the pedals, a force due to friction is transferred to the rope to lift the mass.

This force multiplied by the revs/sec of the wheel enables the applied work to be determined.

It was originally intended that the work done would be displayed on a 7-segment read-out. However, difficulties were encountered in the realisation of this and the circuitry modified to produce two analogue signal read-outs on scaled meters.

The force due to friction was deter-

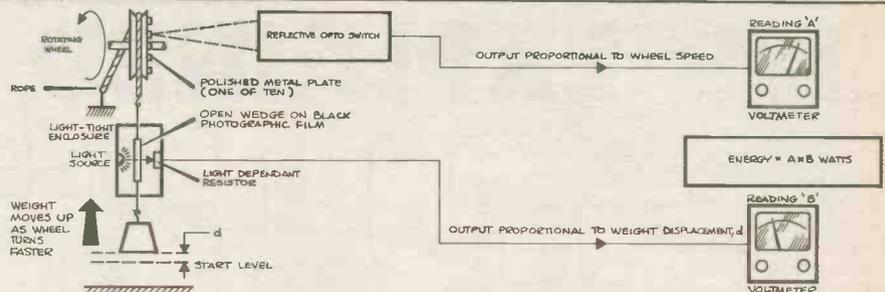

mined using an optical method. An l.e.d. was situated on one side of a photographically produced and calibrated clear wedge on black film. On the other side of the film was a light dependent resistor. The assembly was mounted in a light-tight box. The film was attached to the rope. As the rope was made to lift the mass, the film

moved to allow more light from the l.e.d. to reach the l.d.r. and provide a reading proportional to the force.


The rotational speed of the wheel was measured using a reflective optical switch. An analogue signal was produced from this to appear on a second voltmeter. Multiplying the two readings gives the applied work.

Logic Demonstrator

The Logic Demonstrator is intended for the student and others wishing to gain hands-on experience in investigating the functions of various logic gates and to assist one in understanding the basic concepts of Boolean algebra. It will also provide a useful "breadboard" for checking out project designs using NAND, AND, NOR, OR, EXNOR, EXOR and NOT gates. Logic circuits may be quickly "assembled" using only linked-plugs (wire with a plug at each end) before committing the design to permanent form.

A useful feature is the logical expression, circuit symbols and truth table displays for the six basic gates.

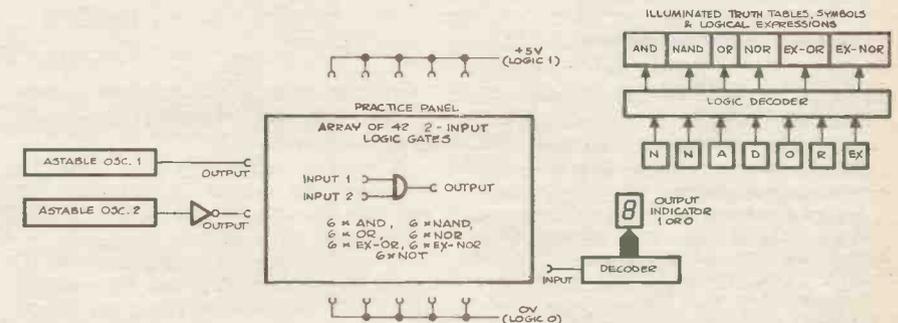An array of 42 logic gates (six of each of the seven types mentioned above) is available to the user. Each input and output is accessible to the



user via sockets on the top panel. A set of jumper leads allow these to be easily interconnected as required. Two pulse generator outputs are provided in the design at similar sockets for feeding clock driven logic circuits, as are


banks of logic 1's (+5V) and logic 0's (0V). The generators may be switched to be in phase or in antiphase. Outputs are monitored on a seven-segment display arranged to read 1 for logic high and 0 for logic low.

Analogue to Digital Converter

This project illustrates how a micro-computer may, with suitable interface techniques, access, process and display analogue data from measurement transducers obtained during the course of experiments. Many existing laboratory experiments and equipment for measuring physical parameters provide an analogue output such as electronic thermometers, pH meters, sound level meters, radiation detectors and so on.

This piece of equipment will process analogue signals and convert them into digital data (8-bits wide) which can be recognised and used by the micro-computer. Although designed for use through the PET User Port, it could be easily adapted for use with other computers with suitable software.

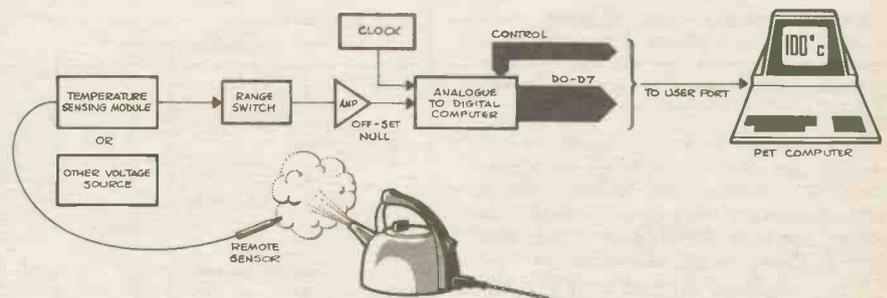
Most of the electronics is contained in a single integrated circuit package known as an analogue-to-digital converter. An analogue signal (within a specific voltage range) is inputted to the converter i.e. analogue input and is



clocked into the chip to provide a digital representation of the input voltage level in the form of an 8-bit word (eight binary bits). The number of samples taken is dependent on the clock rate which has been selected to give a conversion rate of 28,000/sec. The 8-bit wide information reaches the microcomputer data bus when enabled by a command from the software.

On board scaling circuitry is included in the design to allow input voltage signals of up to 10V peak to be processed. Two input modules were provided for demonstration: (1) a direct input module with 100 ohm switchable shunt. This simulates a load provided by a 1mA, 100 ohm meter and (2) a temperature module for displaying the temperature of the remote probe.

A.C. MAINS EXPLAINED

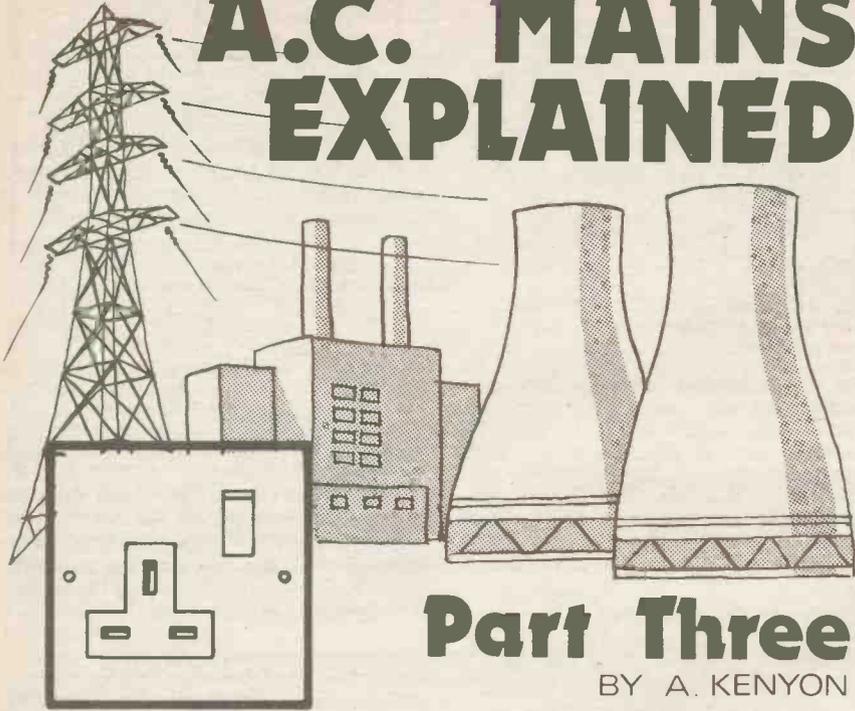

Part Three

BY A. KENYON

IN ORDER to explain the differences between true power and apparent power in the examples discussed last month, it is necessary to examine the relationship between the alternating current waveform and the alternating voltage waveform in a reactive circuit.

PHASE SHIFT

In a purely resistive a.c. system, the current through a resistor rises and falls together with the voltage across it and as such, is said to be in phase with it.

However, in a capacitive a.c. system, the current through a capacitor "leads" the voltage across it by a quarter of a cycle. That is, when the voltage waveform is at zero, the current waveform is at its peak, so it is said to have a phase difference of a quarter of a cycle (or 90 degrees, as one complete cycle is equal to 360 degrees).

In the third case, the inductive a.c. system, the current through an inductor "lags" behind the voltage across it by a quarter of a cycle. Again, the phase shift is 90 degrees but this time in the opposite direction.

The waveform diagrams in Fig. 3.1 illustrate these three cases and also show the conventional method of representing the phase relationship by means of a phasor diagram. The phasor diagram shows both the voltage and current as vector quantities (a line with both magnitude and direction), which are imagined to revolve anticlockwise about a fixed point, 0.

By convention, the current phasor is taken as the reference phase and is drawn horizontally.

A useful mnemonic to help remember the phase relationship in reactive circuits is the word *CIVIL*, to be read as follows:

In a capacitor (C), the current (I) leads the voltage (V), but the voltage (V) leads the current (I) in an inductor (L).

POWER IN A.C. CIRCUITS

If a 24 ohm resistor is connected across the 240V, 50Hz supply, the current through it would be 10A. Now, as the voltage and current are in phase in a purely resistive system, the power consumed by the resistor is equal to $V \times I$, that is, $240V \times 10A = 2,400W$. It follows that if the circuit was left on for one hour, the electricity meter would register 2.4 units used (as one unit equals one kilowatt-hour).

If the 76mH inductor is connected in parallel with this resistor, the current through each branch of the circuit would be measured as 10A (remember that the inductor also has an impedance of 24 ohms at 50Hz) but the current drawn from the supply would be 14.14A. This is shown in Fig. 3.2.

Furthermore, if the circuit was again left on for one hour, the electricity meter would still only register 2.4 units, indicating that 2,400W (the true power) was being used. The apparent power is $14.14A \times 240V = 3,394W$.

The phasor diagram in Fig. 3.2 shows why the current flowing from the supply is 14.14A. Note that I_R is in phase with V_S (the supply voltage) whereas I_L is lagging by 90 degrees, so that the resultant current (I_Z) is the vector sum of these two, that is 14.14A.

This resultant current can also be calculated by the application of Pythagoras' theorem, which states that for a right angled triangle, the square of the hypotenuse equals the

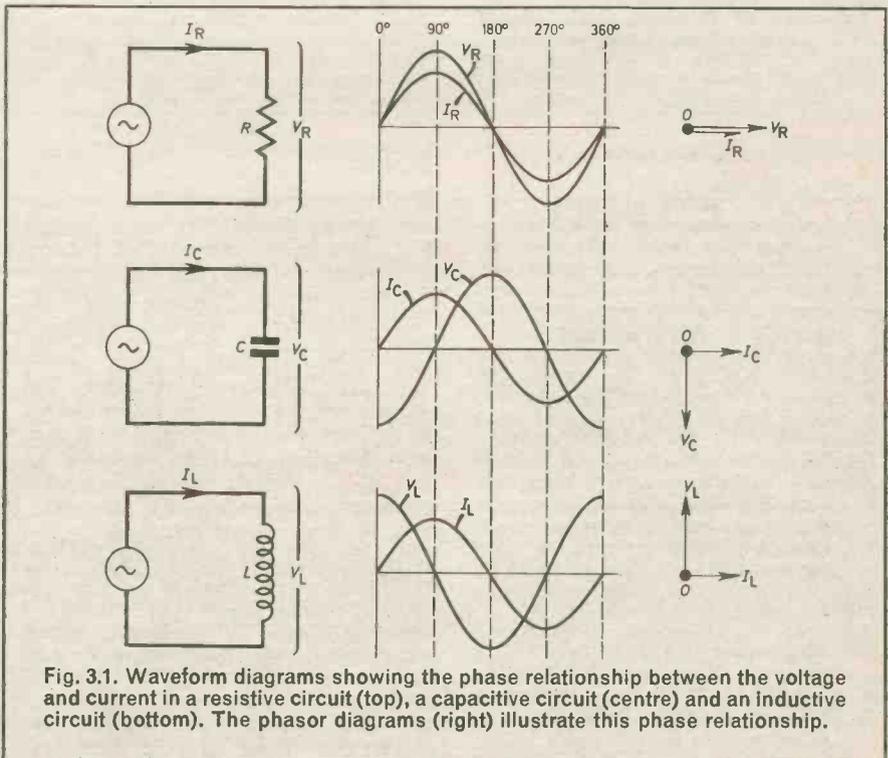


Fig. 3.1. Waveform diagrams showing the phase relationship between the voltage and current in a resistive circuit (top), a capacitive circuit (centre) and an inductive circuit (bottom). The phasor diagrams (right) illustrate this phase relationship.

sum of the squares of the other two sides. So the resultant current, $(I_2) = \sqrt{I_R^2 + I_L^2} = \sqrt{200} = 14.14A$.

POWER FACTOR

So far, it has been established that the product of the supply voltage and the measured current is the apparent power (equal to 3,394W) and that registered on the electricity meter is the true power (equal to 2,400W). The ratio of true power to apparent power is known as the power factor.

So for the circuit shown in Fig. 3.2, the power factor is $2,400/3,394 = 0.707$ (note that the power factor cannot exceed one).

From the phasor diagram in Fig. 3.2, it can be seen that the angle ϕ (greek symbol phi) is the angle at which the resultant current lags behind the applied voltage, and in this case it is 45 degrees. The cosine (abbreviated to cos) of this angle is equal to the ratio of the in phase current to the resultant current which equals $10/14.14 = 0.707$.

This shows that the cosine of the phase angle (cos ϕ) equals the power factor.

The lagging (out of phase) current component in a reactive system does no work and therefore does not register on the electricity meter. For this reason it is known as the wattless component of the current. It is the in phase current which actually does the work in registering the true power.

Therefore, in order to calculate the in phase current, multiply the resultant current (I_2) by the power factor (cos ϕ), remembering that, in a prac-

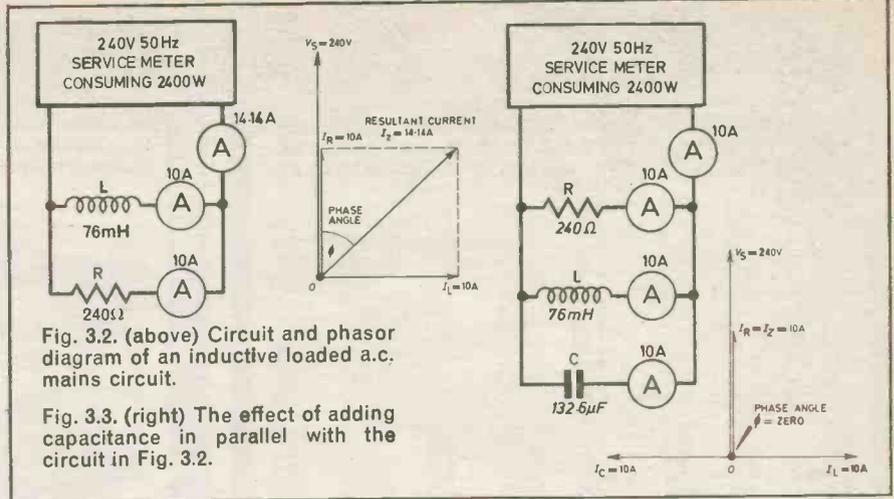


Fig. 3.2. (above) Circuit and phasor diagram of an inductive loaded a.c. mains circuit.

Fig. 3.3. (right) The effect of adding capacitance in parallel with the circuit in Fig. 3.2.

tical circuit, the resultant current is the easiest to measure with an ammeter. In our example, $I_R = I_2 \times \cos \phi = 14.14A \times \cos 45^\circ = 14.14 \times 0.707 = 10A$.

Similarly, the true power is the product of the apparent power and the power factor = $240V \times 14.14A \times 0.707 = 2,400W$. This is the figure originally registered on the kWh service meter.

POWER FACTOR CORRECTION

Industrial electrical equipment and transformers contain coils and windings and will therefore have inductance properties and lagging, out of phase current components. This type of equipment will also carry wattless current, sometimes called reactive volt-amperes.

Take for example, a 500kVA transformer supplying a works having many electric motors to drive production machinery, the total power factor of which adds up to 0.76. This transformer on full load at unity power factor could supply 500kW, but because the power factor is 0.76, the true power on full load is only $500 \times 0.76 = 380kW$.

If the power factor could be improved to say, 0.92 at 380kW, the transformer loading would be reduced to only 413kVA, which would leave an additional 87kVA to supply an extra load.

In order to improve the power factor, it is necessary to reduce the phase angle, (φ), the net result of this being that cos φ (the power factor) will increase. This is achieved by adding a capacitor in parallel with the inductive load. Fig. 3.3 shows this done to the original example.

As the 132.6μF capacitor has an impedance of 24 ohms at 50Hz, the current through it (I_C) will also be 10A. However, the current drawn from the supply is reduced to 10A from the 14.14A in the example shown in Fig. 3.2.

So the capacitive current has cancelled the effect of the inductive

current and this can be illustrated by removing the resistive element from the circuit. The supply current will drop to zero but the current through both the reactive branches remains at 10A each.

PARALLEL RESONANCE

This effect is known as parallel resonance and occurs when the inductive reactance equals the capacitive reactance. The impedance of a parallel resonant circuit is infinity at its resonant frequency. The formula for calculating the frequency at which a parallel LC circuit resonates (the same formula, incidentally, as used in radio transmission and reception) is:

$$\text{frequency } (f) = \frac{1}{2\pi \sqrt{LC}}$$

where L = inductance in henries
C = capacitance in farads
 $\pi = 3.142$ (pi)

The phasor diagram shown in Fig. 3.3 gives the phase relationship between the respective current components in the circuit. Note that I_C leads the supply voltage (V_S) by 90 degrees and is therefore acting in the opposite direction to I_L meaning the resultant current will be equal in magnitude and direction to I_R.

So the true power and the apparent power are equal in this case giving a power factor of one. This is verified by observing that the resultant current is neither leading nor lagging, therefore angle φ = zero and cos φ = 1.

The power factor can therefore be improved by adding capacitance in parallel with the inductive load. In reality it is not practical to increase the power factor to more than 0.92 since when the equipment is switched off (assuming a unity power factor), the high voltages induced upon the change from parallel to series resonance could damage the windings of the electrical equipment.

To be continued

QUESTION TIME

- The information plate on a piece of electrical equipment reads as follows: 240V—1 ph—15A—cos φ=0.8. How many units will the equipment use per hour?
- What are the in phase and wattless components of the equipment in 3.1?

PART 2 ANSWERS

- (a) $X_C = \frac{1}{2\pi \times 3.142 \times 2,000 \times 0.00004} = 80\Omega$
(b) $X_C = \frac{1}{2\pi \times 3.142 \times 50 \times 0.00004} = 80\Omega$
therefore current, $I = V/X_C = 240V/80\Omega = 3A$
- An inductive reactance is causing the current to flow giving rise to apparent power. However, as no true power is being consumed, the disc on the electricity meter would be stationary.

ambit[®] INTERNATIONAL

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST.

CMOS-TTL :

4001	0.11	4518	1.25	74LS10	0.12	74LS138	0.30
4007	0.13	4516	0.60	74LS11	0.12	74LS139	0.30
4009UB	0.25	4518	0.35	74LS12	0.12	74LS145	1.20
4010	0.30	4520	0.60	74LS13	0.20	74LS151	0.30
4011	0.11	4521	1.30	74LS14	0.30	74LS153	0.27
4012	0.14	4522	0.89	74LS20	0.12	74LS154	0.99
4013	0.25	4528	0.80	74LS21	0.12	74LS155	0.35
4016	0.22	4527	0.80	74LS22	0.12	74LS156	0.37
4017	0.40	4528	0.65	74LS26	0.14	74LS157	0.30
4019	0.38	4529	0.70	74LS27	0.12	74LS158	0.30
4020	0.55	4531	0.85	74LS28	0.15	74LS160	0.37
4021	0.58	4532	1.80	74LS30	0.12	74LS161	0.70
4022	0.55	4534	4.00	74LS32	0.12	74LS162	0.37
4023	0.15	4536	2.50	74LS33	0.15	74LS163	0.37
4024	0.33	4538	0.85	74LS38	0.14	74LS164	0.40
4025	0.15	4539	0.80	74LS40	0.13	74LS165	0.60
4027	0.26	4543	0.80	74LS42	0.30	74LS175	0.40
4030	0.35	4549	3.50	74LS47	0.35	74LS189	0.85
4043	0.60	4553	2.70	74LS48	0.45	74LS170	0.90
4044	0.60	4554	1.20	74LS49	0.55	74LS173	0.60
4046	0.60	4555	0.35	74LS51	0.13	74LS174	0.40
4049UB	0.24	4556	1.80	74LS54	0.25	74LS181	1.05
4050	0.24	4557	2.30	74LS55	0.14	74LS181	1.05
4051	0.55	4558	0.80	74LS73	0.21	74LS190	0.60
4060	0.75	4559	3.50	74LS74	0.16	74LS191	0.60
4066	0.30	4560	2.50	74LS75	0.22	74LS192	0.45
4068	0.46	4561	1.80	74LS76	0.20	74LS193	0.42
4069UB	0.14	4562	2.50	74LS78	0.19	74LS194	0.35
4070	0.16	4566	1.20	74LS83	0.40	74LS195	0.35
4071	0.16	4568	1.45	74LS85	0.60	74LS196	0.55
4072	0.16	4569	1.70	74LS86	0.14	74LS221	0.60
4073	0.16	4571	1.80	74LS90	0.20	74LS240	0.80
4075	0.16	4572UB	0.22	74LS92	0.31	74LS241	0.80
4076	0.55	4580	3.25	74LS93	0.31	74LS242	0.70
4077	0.18	4581	1.40	74LS95	0.40	74LS243	0.70
4078	0.18	4582	0.70	74LS96	1.20	74LS244	0.60
4081	0.46	4583	0.60	74LS107	0.25	74LS245	0.80
4093	0.30	4584	0.27	74LS109	0.20	74LS257	0.40
4175	0.80	4585	0.45	74LS112	0.20	74LS258	0.37
4502	0.60	40174	1.05	74LS113	0.20	74LS260	0.50
4503	0.50	40195	1.08	74LS114	0.19	74LS266	0.22
4506	0.16	74LS00	0.10	74LS122	0.35	74LS273	0.70
4507	0.37	74LS01	0.10	74LS124	1.80	74LS279	0.38
4508	1.50	74LS02	0.11	74LS123	0.35	74LS365	0.32
4510	0.55	74LS03	0.11	74LS125	0.24	74LS366	0.34
4511	0.46	74LS04	0.12	74LS126	0.24	74LS367	0.32
4512	0.55	74LS05	0.13	74LS132	0.42	74LS368	0.35
4514	1.25	74LS08	0.12	74LS133	0.24	74LS373	0.70

Memory Micros Linears:

LM10CN	3.88	SL1611	1.60	KB4433	1.52	U265	3.16
L149	1.86	SL1612	1.60	KB4413	1.95	U266	2.43
U237B	1.28	SL1613	2.06	KB4436	2.53	LC7137	7.50
U247B	1.28	SL1620	2.17	KB4437	1.75	ICM7216B	19.50
U257B	1.28	SL1621	2.17	KB4445	1.29	ICM7216C	19.95
U267B	1.28	SL1623	2.44	KB4446	2.75	ICM7217A	9.50
LM324	0.45	SL1625	2.17	NE5044	2.26	SPB647	6.00
LM339N	1.60	SL1630	1.62	MCS229	9.60	95H90	7.80
LF347	1.60	SL1640	1.89	SL6270	2.03	HD10551	2.45
LM348	0.90	SL1641	1.89	SL6310	2.03	HA12009	6.00
LF351	0.49	TDA2002	1.25	SL6440	3.38	HD44015	4.45
LF353	0.78	ULN2242	3.05	SL6500	3.75	HD44752	8.00
LM380N	1.00	ULN2283	1.00	SAS6610	1.48	MC14515P	6.00
ZN419CE	1.98	CA3089	1.84	SL6640	2.75	Z80A	3.75
ZNA427E/B	3.20	CA3130E	0.90	SL6690	2.20	Z80A P10	3.50
NE544	1.80	CA3130T	0.90	SL6700	2.35	Z80A CTC	4.00
NE555N	0.20	CA3140E	0.46	SAS6710	1.48	Z80A DMA	9.95
SL560C	1.98	CA3189E	2.20	LS7225	3.65	Z80A DART	7.50
NE564	4.29	CA3240E	1.27	ICM7555	0.94	Z80A S10/1	11.00
NE567	1.30	MC3357	2.85	ICL8038CC	4.50	Z80A S10/2	11.00
uA741CN	0.20	ULN3859	2.95	TK10170	1.87	Z80A S10/9	9.95
TBA820M	0.78	LM3900	0.60	TK10321	2.75	Z8001	65.00
ZNA1034	2.10	LM3909N	0.58	HA11223	2.15	8255	2.58
LM1035	4.50	LM3914N	2.80	HA11225	1.48	6800P	2.90
TDA1062	1.95	KB4412	1.95	HA12002	1.22	6809	8.75
TDA1083	1.95	KB4417	1.80	HA12402	1.95	6802	3.50
TDA1090	3.05	KB4420B	1.09	HA12411	1.20	68A00P	4.25
HA1197	1.00	KB4423	2.30	HA12412	1.55	68B00P	4.65
MC1350	1.20	KB4424	1.65	LF13741	0.33	2114-L2	1.49
HA1370	1.90	KB4430	2.30	MKS0075	3.85	4116-2	1.59
HA1388	2.75	KB4431	1.95	MM53200	3.90	2732	4.00
SL1610	1.60	KB4432	1.95	U264	2.27	2716	3.00

AND THERE'S PLENTY MORE IN THE CATALOGUE 70p inc.

Coils, Filters: Toko, Murata, NTK, Cathodeon.

SFE6.0MA	0.80	CDA10.7MA	0.70	10M15D	14.50
SFE10.7	0.80	SFE27MA	0.94	LFB4	1.95
SFE10.7MA	0.45	SAF10.7MC-Z	3.75	LFB6/CFU455H	1.95
CFSB10.7	0.50	MF45510A212118.55		LF88	1.95
SFE10.7MJ	0.50	MFL45501L	11.95	LFB10	1.95
SFA10.7MF	0.75	10M15A	1.99	LFB12/CFU455F	1.95
SFE10.7ML	0.70	21M15A	3.45	LFH6S/	
SFE10.7MX	0.95	45M15A	5.95	CFW455HT	2.45
CFSH10.7M1	0.50	10M22D	17.20	LFH8S	2.45
CFSH10.7M2	0.50	10M8D	15.50	LFH12S/	
CFSH10.7M3	0.50			CFW455FT	2.45

TOKO FIXED VALUE CHOKES (E12 Values)

7BA - 1 to 1000uH	16p	10RB - 1 to 120mH	33p
8RB - 1 to 33mH	19p	10RB - .15 to 1.5H	43p

RETAIL SHOP OPENING HOURS
Monday to Thursday 8.30-6.30
Friday 8.30-8.30 Saturday 9.00-5.30
(Access + Barclaycard orders accepted)

NOW IN STOCK
MF10 - National's new Dual Switched Capacitor Filter.
Price £5.05


ALL PRICES SHOWN EXCLUDE VAT. P&P 50p per order.

AMBIT INTERNATIONAL DEPT.EE
200 North Service Road, Brentwood, Essex
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

ambit[®] INTERNATIONAL


THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST.

BAND 2 TUNERHEADS (Varicap Tuning)

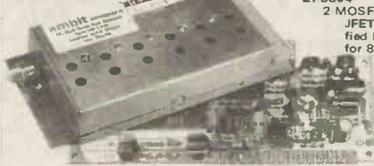

EF5804
2 MOSFET of stages MOSFET mixer, JFET IF preamp, with internally amplified PIN diode AGC. Tuning voltage for 88-108MHz f.z. 8V. Buffered LO output. AGC input 145 x 70 x 24mm.
Stock No. 1-24 25+
40-05804 Kit 24.95 19.95

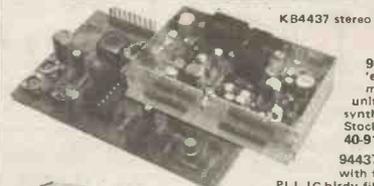7255 The latest complete FM tunerhead from RF input to stereo output. MOSFET RF stages, HA11225 IF and AGC.
7255 special offer price: £30.00 plus VAT



KB4437 stereo decoder. 7255 special offer price: £30.00 plus VAT

911225A The 911225A is the 7230 'edit' and shrunk into a screened metal case, 37 x 56 x 24mm. The unit is ideally suited to use with synthesised tuner systems.
Stock No. 1-24 25+
40-91225 Built 20.82 16.25

944378 'Hyperfl' series decoder module with the TOKO KB4437 pilot cancel PLL IC bldy filter and the KB4438 muting stereo audio preamp with 26/38kHz pilot tone filtering.
Stock No. 1-24 25+
40-04378 Built 19.95 18.05



DFCM500 Wide range digital frequency/capacitance meter. Frequency ranges: 0-1MHz, 1-50MHz and 80-500MHz. 8 digit LED display, mains or Ni-Cad battery operation.
Stock No. 1-24 25+
40-01500 Kit 95.95 86.50

AUTOBRIDGE
An Automatic power tracking VSWR and self-ranging power meter. Complete Kit: All PCBs, board mounted components, meters, case (furnished), transformer etc.
Stock No: 40-40400 £52.86 + £1.50 P&P



FET DIP OSCILLATOR
An essential piece of test equipment for the RF constructor. GDO or WM function covering 1.6-215MHz in five ranges. Audio and meter indication. Kit includes: fibre glass PCB, all components, all hardware, punch, painted and screen printed case, wire etc. for coils and printed scale.
Stock No: 1-24 25+
40-16215 Kit 17.90 16.20



10MHz SSB GENERATOR
PCB. All components, eight-pole crystal filter.
Stock No. Price
40-10700 £29.65



R&W PROJECT AND DATABRIEF PCBs
High quality glass fibre printed circuit boards for projects and Databriefs published in Radio & Electronics World.
27MHz Deviation Meter £1.98
PA105 £3.39
TV Pattern Generator £5.70
MC145181 £2.57
2m Pre-amp £0.97
KB4417 (Undrilled) £0.60
0-30V PSU £3.92
2m PA Mk II £5.14
ULN3859 (Undrilled) £0.84
SSB Exciter £3.37
HA12017 £2.16
Up Converter £4.75



2m PRE-AMP
Very compact low-noise MOSFET 2m pre-amp. Gain 22dB. Noise figure; less than 1.5dB, I/p and o/p impedance; 50 ohm size; 34 x 9 x 15mm. From April '82 R&W.
Stock No. 1-24 25+
40-14400 Kit 2.55 2.30



70cm PRE-AMP
Compact low-noise pre-amp. Gain at 433MHz: 13dB. I/P and O/P Impedance 50ohms. Size 50 x 10 x 17mm. From March '82 R&W.
Stock No. 1-24 25+
40-07000 Kit 3.90 3.60



2m POWER AMP
20 watt 144MHz linear power amplifier. 10dB gain, 2W input - 20W output. Automatic switched relay. Bypasses power amp in receiver mode. Developed from original class C version in Dec 81 R&W. High power output relay. Pre-drilled heatsink, optional RX pre-amp. Kit only.
Stock No. 1-24 25+
40-14421 Less Preamp 28.50 25.65
40-14422 With Preamp 30.40 27.36

AND THERE'S PLENTY MORE IN THE CATALOGUE 70p inc.

RETAIL SHOP OPENING HOURS
Monday to Thursday 8.30-6.30
Friday 8.30-8.30 Saturday 9.00-5.30
(Access + Barclaycard orders accepted)


NOW IN STOCK
MF10 - National's new Dual Switched Capacitor Filter.
Price £5.05

ALL PRICES SHOWN EXCLUDE VAT. P&P 50p per order.

AMBIT INTERNATIONAL DEPT.EE
200 North Service Road, Brentwood, Essex
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

TEMPERATURE INTERFACE FOR THE TANDY TRS-80

BY O.N. BISHOP

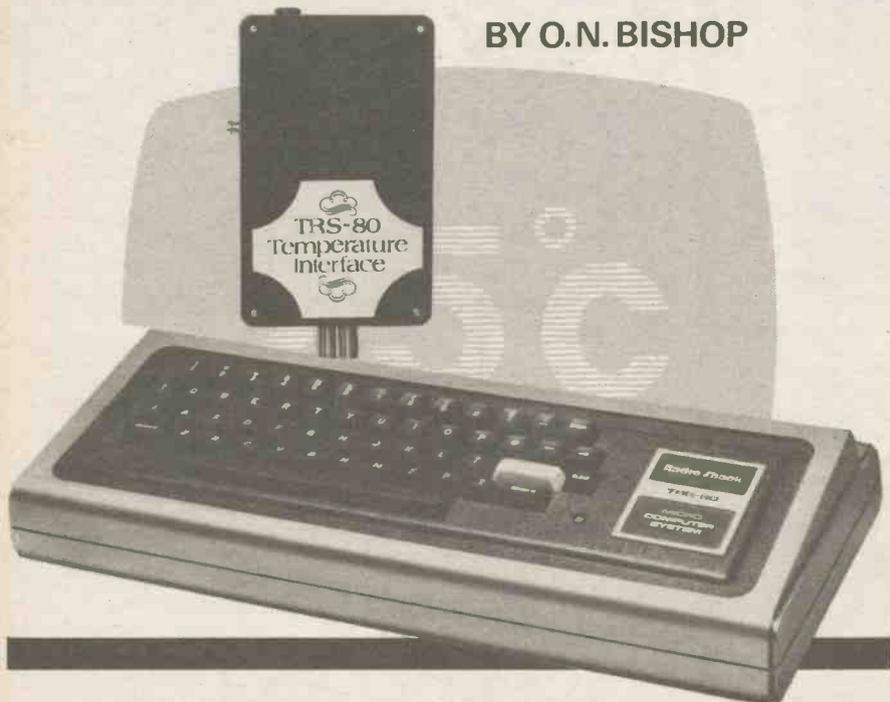

LAST month dealt with the circuit for this Interface describing in detail how it works. In this second and final part, details are given for the assembly and testing, together with the necessary software to run the system.

PRINTED CIRCUIT BOARD

The components are to be assembled on a single-sided p.c.b. The full size pattern to be etched is shown in Fig. 5.

The layout of the components on the board, and wiring to case mounted components are shown in Fig. 6. First of all drill the four fixing holes in each corner. The specified plastic snap-fixing stand-off pillars used in the prototype require a hole diameter in the board of 3.2mm. The hole size to fit these to the case needs to be 5mm diameter. Use the p.c.b. as a template when drilling the case and then enlarge case holes to 5mm.

Begin assembly by soldering in all the link wires, 22 s.w.g. tinned copper wire was used on the prototype. Next fit and solder the i.c. sockets and resistors and voltage regulator followed by the capacitors and bridge rectifier.

Do not fit T1 or insert the i.c.s. yet.

The reason for the suggested order of assembly will become apparent as

you proceed.

Attach sufficient lengths of stranded insulated wire to reach the case mounted components, including a suitable length of 3-core mains cable.

20-way ribbon cable fitted with an edge connector attached is required to connect to the TRS-80. Separate one end of the 30cm long ribbon cable into 20 separate wires, each about 4cm long. Strip about 5mm from each end and tin. Solder these ends into the board in a regular order, see photographs. T1 may now be soldered in place.

If you contemplate expanding the interface sometime, it may be a good idea to carry out the preliminary wiring for this now. The remaining seven decoded address lines, Q1 to Q7 from IC9, data lines D1 to D7, RD, WR, +5V and 0V may be picked up from the underside of the p.c.b. and connected to an 18-pin d.i.l. socket for example mounted on the case. This allows connection to other interfaces using similar circuitry to IC3a/IC4a in the main unit.


Prepare the case to suit the case mounted components, D1, S1, SK1 and a 13mm diameter hole for mains cable bush and fit these, with exception of the bush, in place.


With the plastic stand-off pillars in position in the case, the board can then be aligned with these pillars and firmly pushed onto them to hold the board secure. Feed the mains cable through its entry hole in the case (do not fit the strain relief bush yet). Wire the board to the case mounted components, with sleeving fitted over D1 leads and S1 tags.

EDGE CONNECTOR

The connections to the computer are by way of a 20-way ribbon cable

Fig. 5. P.C.B. pattern viewed from the copper track side.

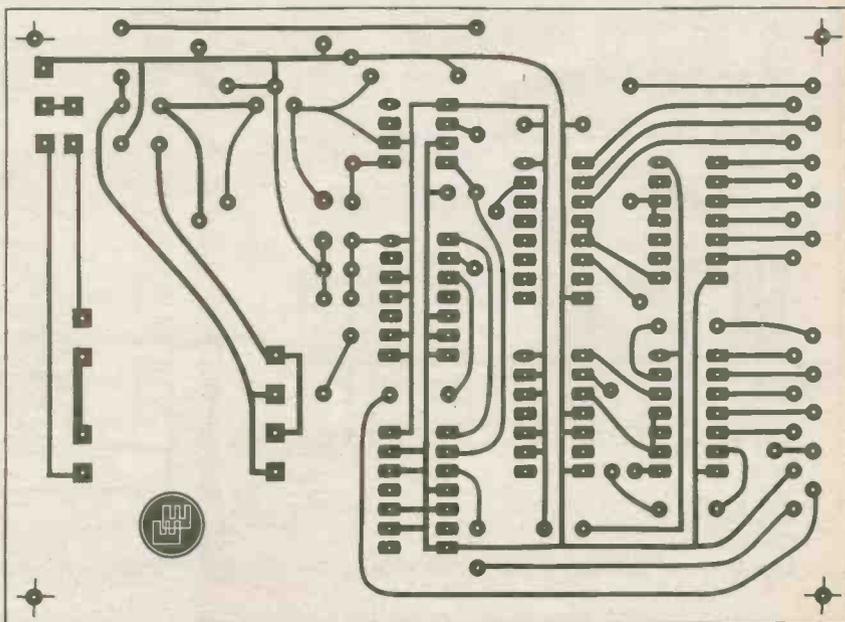

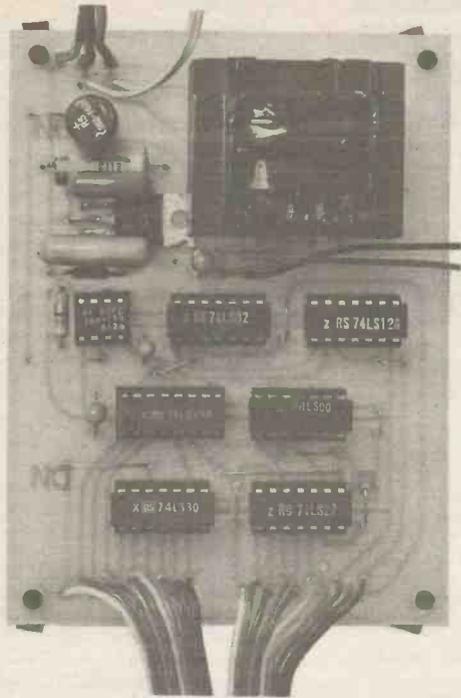

Above and below. Shows the assembled prototype p.c.b. fitted with the snap-fixing stand-off pillars.

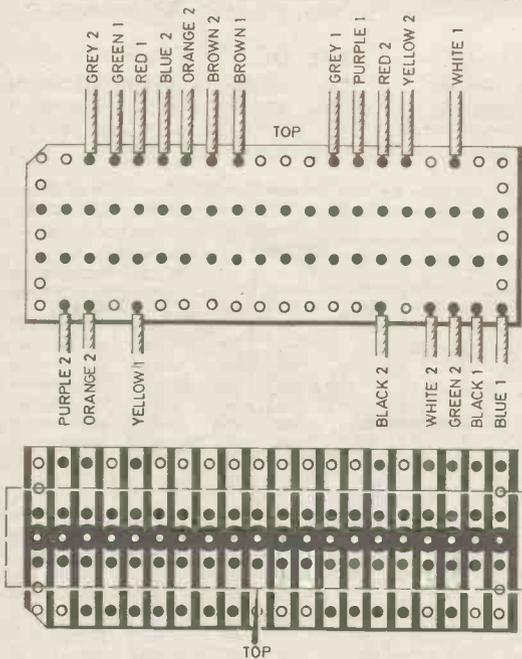
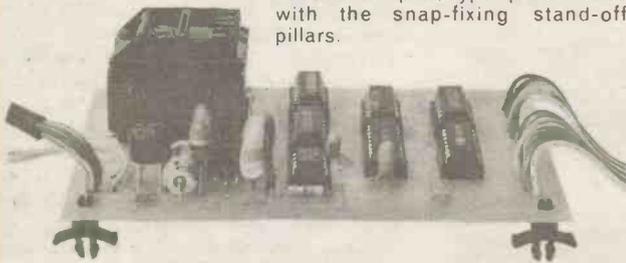


Fig. 8. Wiring and connection details to the strip-board holding the 22 + 22 way edge connector. The labelling of the wires assumes that two 10-way ribbon cables have been used, called 1 and 2.

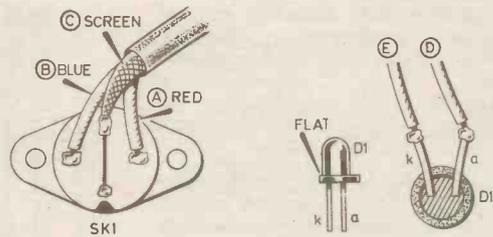
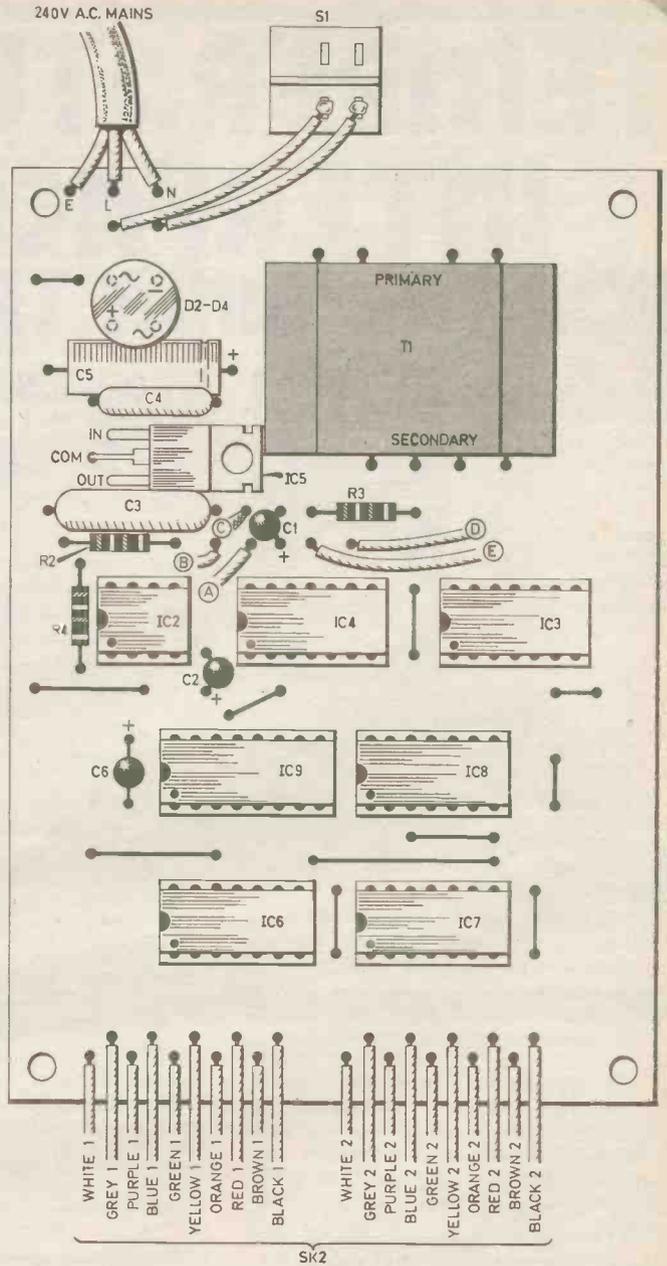


Fig. 6. Layout of the components on the p.c.b. top side with complete interwiring information.

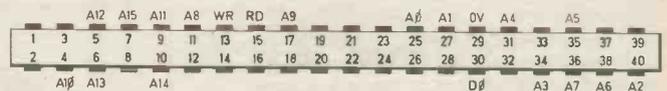


Fig. 7. The TRS-80 expansion outlet viewed from the rear. Only the relevant tracks have been labelled.

(or two 10-way ribbons). The cable is already connected at the p.c.b. end and now requires a 20 + 20 way edge connector to be fitted to the other. Fig. 7 shows the arrangement of the signals viewed from the rear of the TRS-80 Level I and Level II. The top set of "fingers" are labelled as odd numbers, 1 to 39, with 1 at top left. The lower finger set is labelled using the even numbers between 2 and 40, 2 being immediately below 1. The circuit diagram has been labelled accordingly.

The TRS-80 needs a 20 + 20 way socket but this is not easy to obtain. You can use a more readily available 22 + 22 type and not use the positions at either end. The end pins should be removed and small pieces of s.r.b.p. slotted in their place. These will act as position guides since the TRS-80 does not have a polarising slot. This arrangement was adopted on the prototype. Mark the top of the socket with a label or paint to avoid the risk of plugging it on the TRS-80 board upside down. (If you are using a different computer, you will need to obtain a diagram of the edge connector, plug or socket and make connections accordingly.)


The colours shown in Figs. 6 and 8 are those found on most kinds of ribbon cable. If you keep to this system of colours, it will help to reduce wiring errors. For convenience in wiring up, the edge connector and ribbon cable are joined on a short length of stripboard. The socket is mounted on the copper track side and the wires brought in from the plain side to the appropriate track. This can be seen in Fig. 8 and the photographs. Take special care that the connections are made to the correct locations. The wires ends should be stripped and tinned before soldering to the stripboard. Check out each connection thoroughly after you have finished soldering the wires in place, using a magnifying glass to discover any solder bridges that may have occurred.

It is worth while to use a multimeter to test for short circuits between each line and adjacent lines, and eliminate these before going any further.

The WR line is not used in this project, but since there is one spare wire in the cable and WR could be used for any user designed interface projects, it might as well be wired in now.

THERMOMETER PROBE

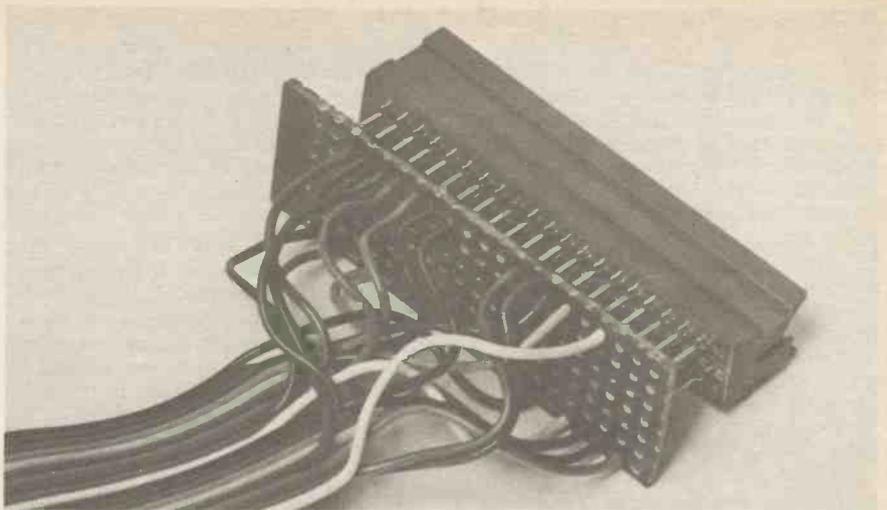The construction of the probe is shown in Fig. 9. A twin screened cable terminated in a 3-pin DIN plug connect the probe to the rest of the circuit via SK1. The cable can be several metres or even tens of metres long. In the prototype, the lead was about 1 metre long. There was evidence that unshielded lead



The stripboard/edge connector fully wired. The two outermost connector positions should be fitted with inserts to act as alignment guides.

picked up electromagnetic interference which, by causing short voltage spikes across R3, resulted in spurious triggering of the converter, IC2. It was found that this could be reduced by wiring C6 to the output of IC2. For this reason it is strongly recommended that shielded cable is used for the probe. However, do not run the lead close to sources of electromagnetic interference. The magnetic field from the coil of the tube of a video monitor can give rise to serious interference. For the same reason, keep the leads and the probe well away from TV sets, loudspeakers, and electric bells or buzzers.


Slip a short length of sleeving over one wire before soldering it to the V+ wire of the i.c. An overlap joint is sufficient. It is advisable to use a heat shunt while soldering. Slide the sleeving over the joint. Next twist the wires of a 270Ω resistor to the R and V- wires of the i.c. Make sure

that the resistor wires are not short-circuiting the wires of the i.c. Solder the resistor in place. Although a 0.25W resistor can be used, a smaller (0.125W) resistor is to be preferred. Now slip a short length of sleeving on to the lead. Solder the wire to the V- lead, and slide the sleeving over the joint. Finally, slide a piece of wide-bore sleeving or 5mm plastic tube over the whole assembly except for the body of the i.c. Note that the screen is not connected at the sensor end of the cable.

Strip the free end of the cable and separate and trim the three conductors. Make sure that these do not touch each other when soldered to PL1 as shown in Fig. 9. Sleeving may be required over the connections.

TESTING

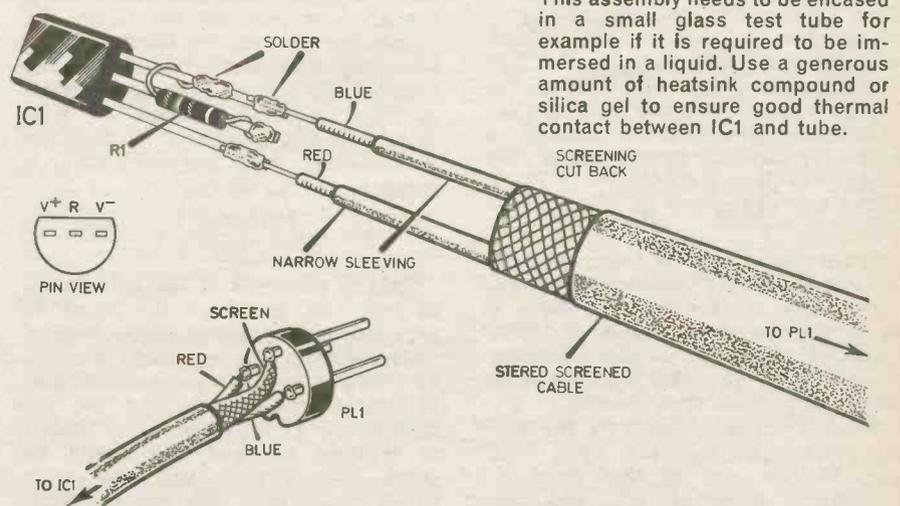Before plugging the i.c.s. into their sockets, the power supply section should be checked. First check for



This assembly needs to be encased in a small glass test tube for example if it is required to be immersed in a liquid. Use a generous amount of heatsink compound or silica gel to ensure good thermal contact between IC1 and tube.

Fig. 9 Construction of the sensor assembly. The sleeving should be pushed over the soldered connections on IC1. It is important that the screening is not connected or in contact with the leads of IC1.

continuity between all the 0V line connections.

With one lead from an ohmmeter connected to the mains earth lead, work through the board using the circuit diagram to check that all the connections to the 0V rail are made. Check the +5V likewise with one ohmmeter lead connected to the +ve end of R4.

If these checks prove satisfactory, the unit may be plugged into the mains and switched on. A spot check across the power supply rails using a voltmeter set to 10V or more should give a reading of 5V. If so, switch off and insert the i.c.s.

The decoding may now be tested by connecting the appropriate inputs of IC7 and IC9 to the 0V line. This is easier done at the edge connector using short lengths of wire temporarily soldered to the appropriate wire-wrap pins.

Unconnected inputs of TTL i.c.s. act as if they were high, so this in effect provides the address 60,000. The output A from pin 15 of IC9 should be low. If you make any one or more of the inputs to IC6 low, or disconnect any one or more of the inputs to IC3 or IC5, A should go high. Switch off.

Plug the edge-connector on to the computer board, taking care that the contacts on the connector are exactly aligned with the contacts on the board. Switch on the computer. If you fail to obtain the usual display (MEMORY SIZE?, on TRS-80) switch off. It is likely that one or more of the cable connections is wrong, or that there is still a short circuit between lines. If all is in order, switch on the power to the interface. Again, if the display changes, switch off both the interface and the computer and check for wiring errors.

The simplest test is to read the state of the output of IC2, using the PEEK command, as in Program A. With TRS-80, high memory addresses are differently coded, so that, instead of PEEK (60000), we use PEEK (-5536). The result of PEEKING depends on the computer. With the TRS-80, an open data line is read as high (1), so when the output of IC2 is high, all lines are high (1111 1111) giving the equivalent of 255 in decimal.

When the output is low, the data lines hold 1111 1110, which is equivalent to 254. As the program runs, a rapid succession of 255's or 254's should scroll up the screen, changing from 255 to 254 and back to 255, about once every 2.5 seconds.

Other computers, such as the ZX-81, return "0" for each open data line. The display will thus show alternating series of 0's and 1's, changing from 0 to 1 and back to 0 about once every 2.5 seconds.

Should the program produce

nothing but 255 or 0, switch off and check the circuit for wiring errors. It may be that you have two address-lines crossed, giving an address outside the range of the decoder. Another possible fault is a dry joint on one or more of the lines of the ribbon cable.

CALIBRATING

The simplest way of using the thermometer is to use a BASIC program such as Program B. This reads the output from IC2 over and over again, waiting for it to go low (line 40). As soon as it goes low it begins to count how many times it reads a low output (line 50). It continues to do this until it goes high again. The number N is proportional to the time spent in the low condition. All that is then needed is to multiply N by a constant factor to convert it to a temperature expressed in degrees.

It was found in trials that when the probe was immersed in water containing melting ice (0 degrees C), the count N was 111. The count increased to 119 when the probe was allowed to warm up to room temperature (20 degrees C). This is as expected, since the count is proportional to absolute temperature and 20 degrees C is 293 K degrees.

The effect of an increase of temperature of 20 degrees is an increase of only 8 counts. There can be only eight different readings between 0 and 20 degrees C, giving a resolution of less than 2 degrees. This may be sufficient precision for triggering alarm systems, but is not good enough when temperature is to be precisely known. To obtain maximum counts the program has been written so as to run as fast as possible.

Variables A to Y are defined as integers and it uses variables instead of constants (line 20). Even so, resolution needs to be improved.

The simplest way to do this is that adopted in the program. The reading operation is repeated six times, the first being ignored, for it might have been begun during a low pulse. The total of the five remaining counts is M (line 70). Tests showed this total to be 555 at 0 degrees C, so that the temperature, X, in degrees Celsius is given by:

$$X = \left(\frac{273 \times M}{555} \right) - 273$$

This is the basis of the calculation in line 100, in which the result is rounded to the nearest whole degree.

To calibrate the Interface, a means of taking a spot temperature reading of the sensor is required. In the absence of a thermometer, a beaker of melting ice and salt could be used. This is at a temperature of 273°K (0°C). With this and any other liquid bath method, the sensor must be isolated from the liquid, see Fig. 9. Run program B.

The total count will be displayed with the calculated temperature. Allow the sensor temperature to stabilise. This will be evident from the display. Mentally note the constant total count and run program B from line 200. After typing in new value for Z, run the program to read the sensor temperature in degrees C. Line 95 may be deleted if not required.

HIGHER RESOLUTION

To achieve even higher resolution we need read the output of IC2 many more times during each low pulse. This can readily be done by using the machine-code routine of Program C. The program waits until output goes low, then reads and counts until it goes high again. This routine is extremely fast, giving a count in the region of 44000 at 0 degrees C. The program is written in Z80 machine code and can be accessed by the USR(0) command in the TRS-80. Program D shows how this may be done. A count of 44000 at 0 degrees C increases to 47223 at 20 degrees C, an increase of 161 counts per degree. Thus it is possible to resolve temperatures to the nearest 0.01 degrees. At this speed it becomes possible to detect occasional spikes on the output, which give rise to very low counts. Such counts are excluded by line 80 of program D.

A complication arises because the value returned from the routine is treated as a "signed number". Being greater than 32767 (0111 1111 1111), its most significant digit is '1', and it is taken to be a negative number. The remaining 15 digits are evaluated as if it were positive, and a negative sign is placed in front of the result. To obtain its true value as a 16-digit number, we subtract it from 65536 (line 90). The calculation of temperature, rounded to the nearest hundredth of a degree, is done on the same line. The equation on which this is based is:

$$\text{Temp.} = \frac{273 \times X}{44000} - 273 \\ = (0.06245 \times -273) \text{ degrees K}$$

Derive and insert the calibration factor as described in the previous section. The routine from line 200 calculates Z.

With this established, other temperatures are obtained by the calculation in the program. It is important to allow the sensor several minutes to come to a steady temperature before attempting to calibrate it. The output of the i.c. is upset by sudden changes of temperature, presumably because some parts of the i.c. acquire the new temperature before other parts and the balance of the circuit is disturbed. □

TEMPERATURE INTERFACE SOFTWARE

Program A: Testing

```
10 PRINT PEEK (-5536)
20 GOTO 10
```

Program B: Reading Temperature

```
1 CLS
5 Z = 1
10 DEFINT A - Y
20 X = -5536: Y = 255
30 FOR K = 1 TO 6
40 IF PEEK (X) = Y THEN 40
50 IF PEEK (X) < > Y THEN N = N + 1: GOTO 50
60 IF K = 1 THEN 80
70 M = M + N
80 N = 0
90 NEXT K
95 PRINT M; " ";
100 PRINT "TEMPERATURE = "; INT (Z*M - 272.5)
110 M = 0
120 GOTO 30
200 CLS
210 PRINT "TO CALCULATE CALIBRATION FACTOR, Z"
220 PRINT "TEMP. IN DEGREES K = ";
230 INPUT A
240 PRINT "COUNT = ";
250 INPUT B
260 PRINT "Z = "; A/B
270 PRINT "ENTER THIS VALUE FOR Z IN LINE 5"
```

Program C

```
00100 ; PROGRAM TO READ THERMOMETER
7D00 00110 ORG 7D00H
7D00 00120 LD HL, 00H ; CLEAR HL REGISTER
7D03 210000 00130 WAIT LD A, (0EA60H) ; READ OUTPUT
7D06 FEFF 00140 CP 0FFH ; IS OUTPUT HIGH?
7D08 CA037D 00150 JP Z, WAIT ; STILL HIGH, SO WAIT
7D0B 3A60EA 00160 COUNT LD A, (0EA60H) ; READ OUTPUT
7D0E FEFE 00170 CP 0FEH ; IS OUTPUT LOW?
7D10 C29A0A 00180 JP NZ, 0A9AH ; HIGH AGAIN, RETURN TO BASIC
7D13 23 00190 INC HL ; COUNTING NO. OF LOW READS
7D14 C30B7D 00200 JP COUNT ; FOR NEXT READ
0000 00210 END
00000 TOTAL ERRORS
Count 7D0B
Wait 7D03
```

Program D: Reading Temperatures to 0.01 degrees


```
1 CLS
5 Z = 1
10 DATA 33, 0, 0, 58, 96, 234, 254, 255, 202, 3, 125, 58, 96, 234, 254, 254, 194, 154, 10, 35, 195, 11, 125: ' Program in decimal
20 FOR J = 0 to 22: ' Putting program into memory
30 READ D
40 POKE 32000 + J, D
50 NEXT J
60 POKE 16526, 0: POKE 16527, 125: ' Starting address of program
70 X = USR(0): ' Go to program
80 IF X < 50 AND X > 0 THEN 70: ' Reject small counts
85 PRINT (65536 + X); " ";
90 PRINT "TEMPERATURE = "; INT (Z*(65536 + X) - 27299.5)/100
100 GOTO 70: ' To take next reading

200 CLS
210 PRINT "TO CALCULATE CALIBRATION FACTOR, Z"
220 PRINT "TEMP. IN DEGREES K = ";
230 INPUT A
240 PRINT "COUNT = ";
250 INPUT B
260 PRINT "Z = "; (100*A)/B
270 PRINT "ENTER THIS VALUE FOR Z IN LINE 5"
```

MODIFICATIONS


There is an error on the circuit diagram, Fig. 2 published last month. The "short" across R2 should of course not be there.

It was found necessary to use screened cable to connect the sensor to the unit in order to minimize the effect of e/m noise pick-up giving rise to false triggering of IC2 and thus "odd" calculations. Consequently, PL1 and SK1 have been re-specified as 3-pin DIN plug and socket respectively. Twin screened cable should be added to the Component List. The circuit diagram front end should be modified as shown below. The likelihood of false triggering may be further reduced with C2 2.2µF.

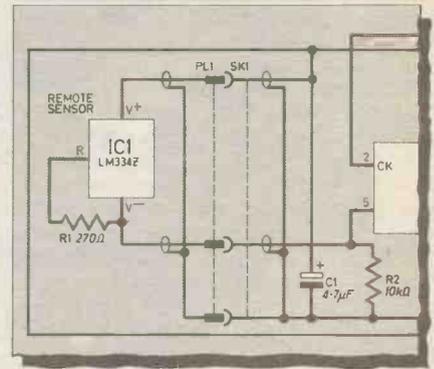

CONTINUITY TESTER

By J. Moulder

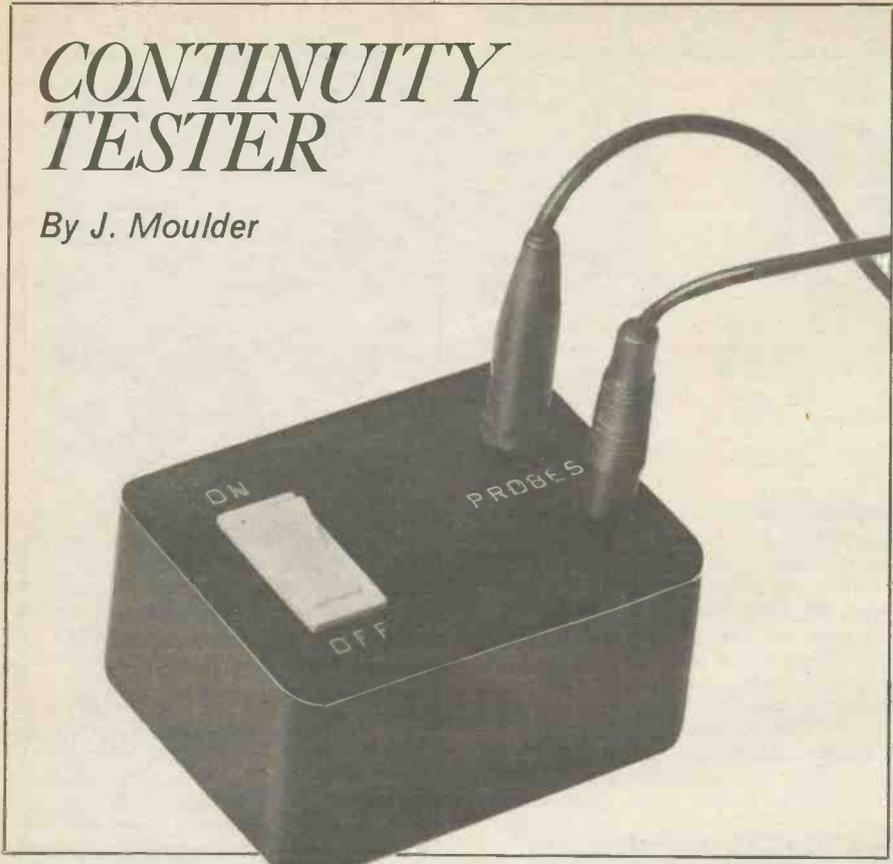

A CONTINUITY tester is a valuable piece of equipment used to determine whether a component or circuit has a broken connection. That is, it tests for the continuity of current flowing.

It can also be used to check fuses, bulbs, wires and certain semiconductors, including diodes and transistors.

DESIGN CONSIDERATIONS

This circuit has been designed to overcome difficulties often associated with basic continuity testers. These are:

1. Difficulty in establishing if continuity has been made.
2. High probe current damaging semiconductor junctions.
3. Inability to pre-determine the maximum resistance that the tester "sees" as continuity.
4. Variation in the tone produced by the tester according to the resistance being checked.
5. High stand-by current.

The first problem was simply overcome by giving the Continuity Tester an audio output, not a visual indication, thus allowing the user to concentrate on the component under test, and with a probe current of less

than 1mA, the second problem was also removed.

Provision of a potentiometer in the tester input circuit permits the user to programme the resistance at which the unit registers continuity and by incorporating an oscillator with a tone frequency independent of test resistance, difficulties 3 and 4 were erased.

The stand-by current was reduced to an almost negligible level by using ultra-low power CMOS circuitry thus overcoming the last problem.

CIRCUIT DESCRIPTION

The tester employs a CMOS 4011 i.c., consisting of four NAND gates, three of which form an oscillator, the remaining gate acts as an inverter to enable the oscillator. See Fig 1.

IC1b, c and d form the "ring of three" oscillator, the frequency of which can be calculated with the formula:

$$\text{frequency (f)} = \frac{1}{R2 \times C1} \text{ Hz}$$

where R2=resistance in ohms
C1=capacitance in farads

With the components used in this circuit, the frequency will be approximately 1kHz.

The last NAND gate, IC1a, is made into an inverter by wiring its two inputs together. Its output is connected to the oscillator which will only oscillate when the output of IC1a is high (logic 1). This will only occur when a low resistance path is connected between SK1 and SK2, thus forming a potential divider along with R1 and VR1.


TRANSDUCER

The oscillator drives WD1, a piezo ceramic transducer. This type of device consists of a piece of ceramic material deposited on a circular brass "resonator" and it produces a very high output when energised. This makes it more efficient for this application than a traditional speaker, particularly considering its low power consumption and diminutive size.

CIRCUIT BOARD

Fig. 2 shows the construction of the circuit board on 0.1 inch strip-board, 12 strips by 19 holes. It is best to start with the i.c. holder for IC1 and then solder in the wire links (9 in all), VR1, the resistors and the capacitor.

Fig. 1. The complete circuit diagram for the Continuity Tester.

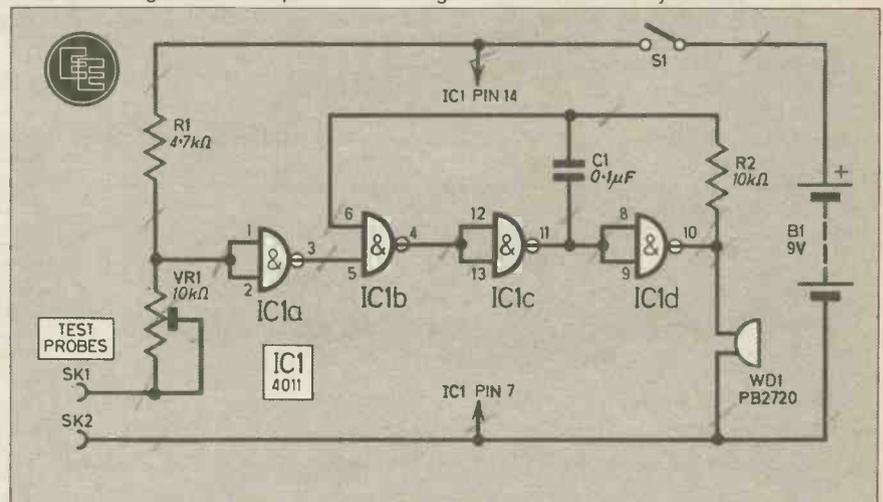

Next, the flying leads of 7/0.2mm equipment wire should be added, and these should be about 100mm long. Finally solder the leads from the piezo ceramic transducer into position, taking great care as these tend to be a little fragile, and to complete this stage of construction, add the battery clip (remember that the red lead goes to switch S1).

THE CASE

The tester is now ready to go into its case, and the prototype was fitted into a plastic box, 75x55x35mm. The red and black banana sockets and the rocker switch are mounted on the outside of this case as shown.

The piezo ceramic transducer (WD1) is glued onto the inside of the case with a contact adhesive (such as "Evostick") and the battery B1 is taped to the inside of the lid. When all the flying leads have been soldered in place, the unit can be completed by slotting the board into the space between the battery and the plastic body of the rocker switch.

SETTING UP

To set up the Continuity Tester, a small screwdriver and 1.5 kilohm resistor are required.

With the unit open so as to give access to VR1, switch on and connect the 1.5 kilohm resistor between the two probes. A 1kHz tone may be heard but don't worry if it is not at this stage.

Adjust VR1 until the tone just ceases and if the unit was not initially making the tone, VR1 must be rotated until it does and then adjusted to the point where it ceases. It is important that this adjustment is exact so that the tester is sensitive to this resistance.

The value 1.5 kilohm was chosen as the maximum resistance at which the Continuity Tester "sees" as continuity for the prototype as it is a practical value. However, the constructor may wish to substitute a different value here.

The unit is now ready to test components and circuits, and Fig. 3 and 4 show how it can be used to check diodes and transistors

COMPONENTS

Resistors

R1 4.7kΩ R2 10kΩ
All 1/4W carbon ±5%

Capacitors

C1 0.1μF polycarbonate

Semiconductors

IC1 4011B CMOS quad 2-input NAND gate

Miscellaneous

RV1 10kΩ miniature horizontal preset

S1 on/off rocker switch

B1 9V PP3 battery

SK1 4mm banana socket, red

SK2 4mm banana socket, black

WD1 PB2720 piezo ceramic transducer

Stripboard, 0.1 inch matrix, 12 strips by 19 holes; plastic case 75 x 55 x 35mm; 14 pin d.i.l. holder; battery clip; 7/0.2mm equipment wire; probes (2 off, one red, one black) on 4mm banana plugs.

Approx. cost £6.20
Guidance only

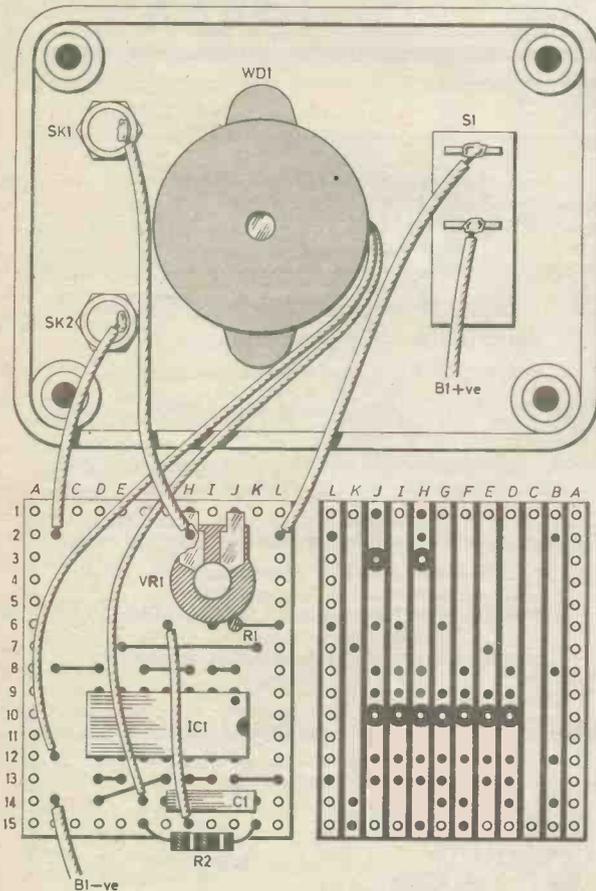


Fig. 2. Stripboard layout and inter-wiring diagram.

SEMICONDUCTOR TESTING

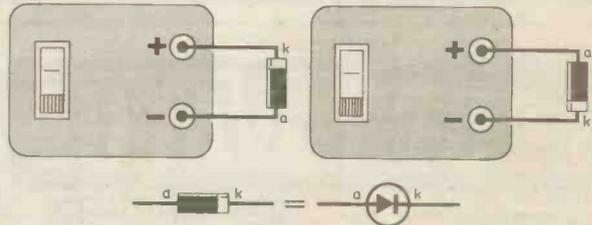


Fig. 3. Method of testing a diode with the Continuity Tester unit. If the cathode (k) is first connected to the positive (red) terminal as shown, the diode should not conduct. By reversing the diode across the terminals as shown in the right hand diagram, the tone should sound, indicating conduction. If the tone sounds for both tests or does not sound at all, then the diode is defective.

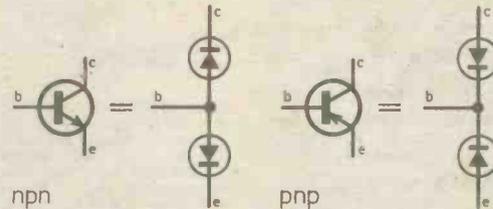


Fig. 4. When testing a transistor with the Continuity Tester, the device must be thought of in terms of the equivalent circuits shown. For example, an npn transistor is equivalent to two diodes, connected in series by their anodes (a), the base (b) being at this junction. Then by testing each "diode" in turn using the procedure given in Fig. 3, that is the base-collector junction and then the base-emitter junction, thus checking the function of the transistor. The pnp transistor is tested in a similar manner, remembering that the diodes in the equivalent circuit are reversed.

LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts. i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder and hook-up wire. Self assembly simulated wood cabinet — only £4.50 + £1.50 p+p.

Featured in April issue of P.E. Reprint 50p. Free with kit.

ELECTRONICS ONLY!

Ideal for updating your existing cassette. Includes pcb diagram, all semiconductors, IC's, Capacitors, resistors. +£1.40p&p

£18-95

£32-95

+ £2.75 p&p.



P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP
- TAPE COUNTER
- SWITCHABLE E.Q.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

STEREO AMPLIFIER KIT


- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard stereo preamplifier module. • Attractive black vinyl finish cabinet, 9" x 8 1/2" x 3 3/4" (approx).
- 10+10 stereo converts to a 20 watt disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs — tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features slider controls, push button switches, fascia, knobs and contrasting case. Instructions 50p — supplied free with kit.

£16-50 + £2.90 p&p.

SPECIFICATIONS: Suitable for 4 to 8 ohm speakers. Frequency response: 40Hz - 20KHz. Input sensitivity: P.U. 150mV, Aux. 200mV, Mic. 1.5mV. Tone controls: Bass ±12dB @ 60Hz, Treble ±12dB @ 10KHz. Distortion: 0.1% typ. @ 8W. Mains supply: 220-250v 50Hz.

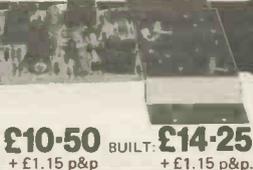8" SPEAKER KIT— Two 8" twin cone domestic speakers. £4.75 a stereo pair plus £1.70 p&p.



KIT: **£10-50** + £1.15 p&p
BUILT: **£14-25** + £1.15 p&p

125W HIGH POWER AMP MODULE

SPECIFICATIONS. Max output power: 125w rms. Operating voltage (D.C.): 50-50 max. Loads: 4 - 16 ohms. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100 watts: 400mV @ 47K. Typical T.H.D. @ 50 watts: 4 ohms: 1%. Dimensions: 205 x 90 and 190 x 36 mm.



P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System.

FEATURES: VHF, MW, LW bands, interstation muting and AFC on VHF. Tuning meter. Two back printed pcb's. Ready made chassis and scale. Aerial: AM — ferrite rod, FM — 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" app. Complete with diagram and instructions. Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 3/4". **£3.50** Plus **£1.50** p&p. Reprint 50p — FREE with kit.



£17-95 + £2.50 p&p.

SPECIAL OFFER! TUNER KIT PLUS:

- Matching I.C. 10 watt per channel Power amp kit.
- Mullard LP1183 built pre-amp, suitable for ceramic pickup and aux. inputs.
- Matching power supply kit with transformer.
- Matching set of 4 slider controls for bass, treble + vols. **£21.95** + **£3.80** p&p.

All mail to: 21A HIGH STREET, ACTON, W3 6NG. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/6/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. Send S.A.E. for full list of products. Telephone or mail orders by ACCESS are welcomed.

ALL CALLERS TO: 323 Edgware Rd, London W2. Tel: 01-723 8432. 9.30 - 5.30, closed all day Thurs. ALL PRICES INCLUDE VAT AT 15%.



ELECTROVALUE

A SPECIAL SUMMER PROMOTION

FREE VOUCHERS TO SAVE YOU UP TO

£2-10



Send for EV Catalogue 82 before Aug. 31 (50 pages A4 — 70p post paid) and we give you **THREE 70p. REFUND VOUCHERS FREE!** Each is valid at any time for spending singly on any one C.W.O. order minimum list value £10 to quickly represent a useful saving for you. Send 70p now for your catalogue and 3 vouchers by return.

+ USUAL DISCOUNTS + FREE POSTAGE

DISCOUNTS

5% on orders over £23 (inc V.A.T.)
10% on orders over £57.50 (inc V.A.T.) on most catalogue items, but not on payments by credit cards.

POSTAGE

Not charged on U.K. C.W.O. orders over £5.75 inc V.A.T. If less, add 40p handling charge.

ELECTROVALUE LTD. 2nd St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB.
Telephone Egham (STD 0784; London 87) 33603; Telex 264475.
Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA.
Telephone 061 432 4945.

- ★ SEMI-CONDUCTORS/ICs/OPTOs
 - ★ COMPUTERS/SOFTWARE
 - ★ CAPACITORS/RESISTANCES
 - ★ CONNECTORS/SWITCHES/KNOBS
 - ★ POTS/FERRITES
 - ★ BOOKS/BOXES/TOOLS
- and more and more and more



Bigger and Better for 1982
the colourful Wilmslow Audio brochure
— the definitive loudspeaker catalogue!

Everything for the speaker constructor — kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★
two listening lounges
(Customer operated demonstration facilities)
- ★ Ample parking ★

Send **£1.50** for catalogue
(cheque, M.O. or stamps — or phone with your credit card number)

- ★ Access — Visa — American Express accepted ★
- also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

Lightning service on telephoned credit card orders!



SQUARE ONE FOR BEGINNERS

SO WHAT is this mysterious form of energy called electricity?

It's not mysterious at all, and the voltage and current of an electricity supply can be explained quite simply if we use the example of water flowing in a pipe, for instance in a basic central heating system.

In our central heating system, three points must be remembered. Firstly, if water is to flow in the pipes, they must be connected into a complete loop or "circuit". Secondly, the water must be pumped around the system to maintain the flow, and lastly, the same water must be moving round all the time; no water is added or removed.

VOLTAGE AND CURRENT

The voltage in an electric circuit can be thought of as the pressure at which the water is pumped around the system and the current is the amount of water actually flowing through it.

Note that if you were to cut the water pipe and block off the two exposed ends (in effect, break the circuit), no water could flow. Similarly, in an electric circuit, if the circuit is broken, no current would flow.

However, in the water system, the pump could still be operating at the same pressure even though no water is actually moving. Again, in our electric circuit, the voltage can still be present even if the current flow is interrupted.

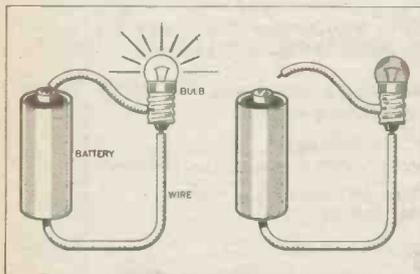


Fig. 1. Demonstration of current flow.

This is illustrated in a simple circuit consisting of a battery (a voltage source), a small light bulb (to indicate the flow of a current) and two wires to make the "circuit".

When these components are connected as shown in Fig. 1a, a current flows and lights the bulb. It is the battery that provides the voltage (or pressure) for this current to flow.

If one wire is now removed from the battery as shown in Fig. 1b, no current can flow and the bulb goes "out". However, the voltage is still present on the battery.

UNITS OF ELECTRICITY

The voltage (V) is measured in volts (V). As a voltage is a "pressure" or force, it is also referred to as an electro-motive force (e.m.f.).

To give an idea of various voltages, the cylindrical torch light battery (say an SP11) produces 1.5V, the PP3 transistor radio type battery can supply 9V and the mains voltage is 240V.

These high voltages are potentially very dangerous and must be treated with great care.

The current (I) flowing in a circuit is measured in amperes (A). The abbreviation for amperes is not *amps* as this could cause confusion with the abbreviation for an amplifier.

Again to give some idea of practical current values, a torch bulb may require as little as one twentieth of an ampere (0.05A), whereas a two bar electric fire uses as much as 12A!

RESISTANCE

Having established the basic concepts of voltage and current, we can look at another property affecting the electric circuit; that of resistance (R). Resistance in a circuit literally "resists" the flow of current through the circuit and if we return to the central heating system comparison, resistance can be thought of as the bore (the inside diameter) of the pipes.

So a small bore pipe restricts the flow of water, meaning it has a high resistance, and a large bore pipe permits a lot of water to flow as it has a low resistance. Similarly in the electric circuit, a high resistance limits the current flow and a low resistance allows more current to flow.

The unit of resistance is the ohm (given the greek symbol omega, Ω) and a resistor is a component that has a definite known value of resistance. It is the most widely-used type of component and is commonly available in resistance values ranging from one ohm to ten million ohms.

OHM'S LAW

The most important fundamental law governing all electric and electronic circuit theory is Ohm's law. This concerns the relationship between voltage, current and resistance in a circuit and states that the current flowing through a circuit is proportional to the voltage applied to that circuit and inversely proportional to the resistance in that circuit.

What this means in real terms is that voltage, current and resistance are governed by the formula:

$$\text{voltage}(V) = \text{current}(I) \times \text{resistance}(R)$$

It also follows that:

$$I = V \div R \text{ and } R = V \div I$$

These three formulae derived from Ohm's law allow us to calculate an unknown quantity in a circuit if we know the other two quantities. For example, if a 10 ohm resistor is connected across a 12V car battery, the current through it can be calculated from $I = V/R$. Therefore $I = 12/10 = 1.2A$.

A simple way to remember this relationship between V, I and R is to draw a triangle as shown in Fig. 2.

Then by covering the unknown quantity with a finger, the relationship between the other two quantities will be exposed in the triangle.

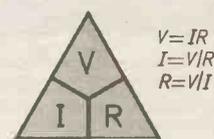


Fig. 2. Ohm's law triangle.

POWER

The power (P) developed in a circuit is the product of the voltage and the current and is measured in watts (W). So in our previous example, the power developed in the 10 ohm resistor is equal to $12V \times 1.2A = 14.4W$.

A similar triangle can be constructed to remember the relationship between P, V and I and this is shown in Fig. 3.

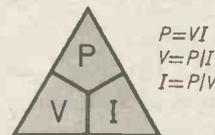


Fig. 3. Power equation triangle.

MULTIPLES AND SUB-MULTIPLES

When dealing with voltages, currents, wattages and resistances, sometimes the values are very large or very small numbers and to make these numbers a little easier to understand they are expressed as multiples and sub-multiples.

The following are the most commonly used:

- micro (μ) = one millionth of ($\times 0.000001$ or $\times 10^{-6}$)
- milli (m) = one thousandth of ($\times 0.001$ or 10^{-3})
- kilo (k) = one thousand times ($\times 1,000$ or $\times 10^3$)
- mega (M) = one million times ($\times 1,000,000$ or $\times 10^6$)

For example:

- one microvolt ($1\mu V$) = $0.000001V$
- four milliamperes (4mA) = $0.004A$
- six kilowatts (6kW) = $6,000W$
- two megohms ($2M\Omega$) = $2,000,000\Omega$

MASTER ELECTRONICS NOW! The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

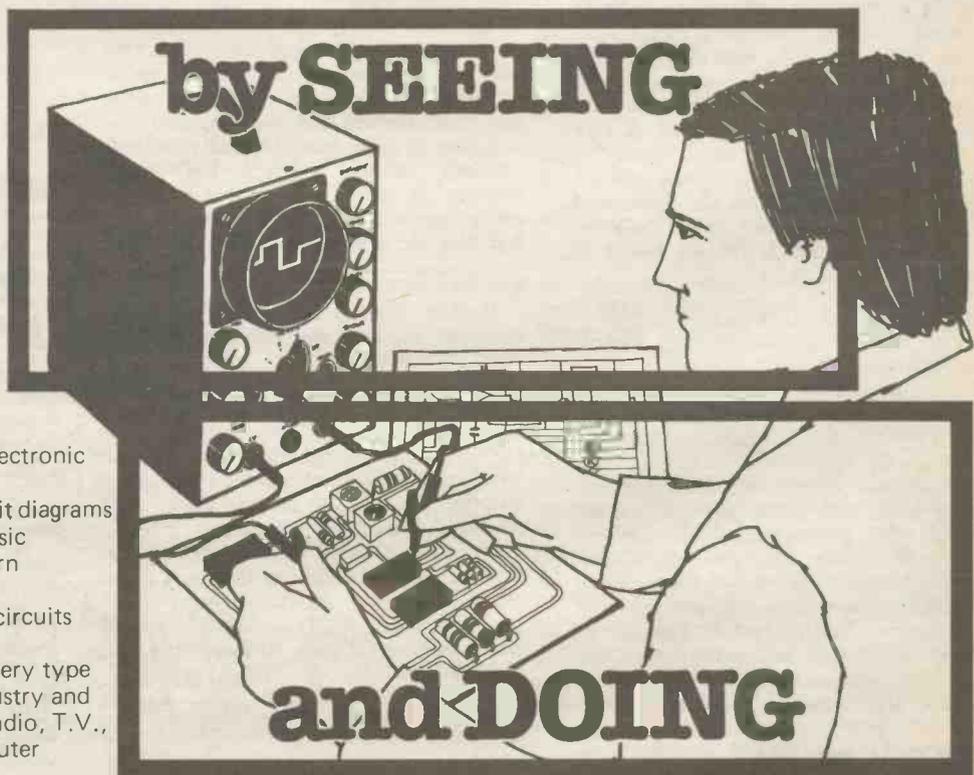

New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!

COLOUR BROCHURE



Please send your brochure without any obligation to

I am interested in:

NAME _____

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

ADDRESS _____

OTHER SUBJECTS _____

POST NOW TO:

BLOCK CAPS PLEASE

EE/9/820

British National Radio & Electronics School Reading, Berks. RG1 1BR.

Multicore makes soldering easy fast & reliable

Ersin Multicore

Ersin Multicore, solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required. Comes in handy dispensers and tool box reels in two different alloys 40/60 tin/lead for general purpose electrical soldering and 60/40 tin/lead ideal for small components and fine wire soldering.



Size PC115 60/40 tin/lead
£1.38 Handy pack 0.028mm dia



Size 3 40/60 tin/lead
£4.37 Per reel 1.6mm dia



Size 10 60/40 tin/lead
£4.37 Per reel 0.71mm dia



Size 19A 60/40 tin/lead
£1.15 Handy pack 1.22mm dia

Multicore Savbit

Multicore Savbit, solder increases the life of your soldering bit by 10 times, for better soldering efficiency and economy. Comes in two handy dispensers and tool box reels.



Size 5 Savbit
£1.15 Per pack 1.2mm dia



Size 12 Savbit
£4.37 Per reel 1.2mm dia



Size SV130 Savbit
£1.73 Per pack 0.048mm dia

Multicore Alu-Sol

Multicore Alu-Sol, solder contains 4 cores of flux, suitable for most metals especially aluminium. Comes in handy dispensers on tool box reels.

Size AL150 Alu-Sol
£2.07 Per pack 0.048mm dia



Size 4 Alu-Sol
£7.82 Per reel 1.6mm dia



Multicore Solder Wick

Multicore Solder Wick, absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds.

Size AB10 Solder Wick
£1.43 Per pack



Multicore Tip Kleen

Multicore Tip Kleen, soldering iron tip wiping pad. Replaces wet sponges.



Size 2 Tip Kleen
£0.92 Per pack

Bib Wire strippers and cutters

Wire strippers and cutters, with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.



Size 9 Wire Strippers
£2.69 Per pair

All prices inclusive of VAT. Available from most electrical and DIYs stores. If you have difficulty in obtaining any of these products send direct with 50p for postage and packing. For free colour brochure send S.A.E.

Bib Audio/Video Products Limited
(Solder Division), Kelsey House,
Wood Lane End, Hemel Hempstead,
Hertfordshire, HP2 4RQ.
Telephone: (0442) 61291
Telex: 826437



"...the quality of the colour display is excellent". Popular Computing Weekly.

"The graphics facilities are great fun". Personal Computer World.

"...the Spectrum is way ahead of its competitors". Your Computer.

"The world's best personal computer for under £500."

Chris Sinclair

Sinclair ZX Spectrum 16K RAM £125, 48K RAM £175.

This is the astonishing new ZX Spectrum – a powerful professional's computer in everything but price!

There are two versions – 16K or a really powerful 48K. Both have a full 8 colours, sound generation, a full-size moving-key keyboard and high-resolution graphics. Plus established Sinclair features such as 'one-touch' keyword entry, syntax check and report codes!

Key features of the Sinclair ZX Spectrum

Full colour – 8 colours plus flashing and brightness-intensity control.

Sound – BEEP command with variable pitch and duration.

Massive RAM – 16K or 48K.

Full-size moving-key keyboard – all keys at normal typewriter pitch, with repeat facility on each key.

High resolution – 256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.

ASCII character set – with upper- and lower-case characters.

High speed LOAD & SAVE – 16K in 100 seconds via cassette, with VERIFY and MERGE for programs and separate data files.

The ZX Printer – available now

The printer offers ZX Spectrum owners the full ASCII character set – including lower-case characters and high-resolution graphics.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

ZX Microdrive – coming soon

Each Microdrive will hold up to 100K bytes on a single interchangeable microfloppy – with a transfer rate of 16K bytes per second. And you'll be able to connect up to 8 ZX Microdrives to your ZX Spectrum – they're available later this year, for around £50.

How to order your ZX Spectrum

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST – use the coupon below. You can pay by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

sinclair ZX Spectrum

Sinclair Research Ltd,
Stanhope Road, Camberley, Surrey,
GU15 3PS. Tel: Camberley (0276) 685311.

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX Spectrum – 16K RAM version	100	125.00	
	Sinclair ZX Spectrum – 48K RAM version	101	175.00	
	Sinclair ZX Printer	27	59.95	
	Printer paper (pack of 5 rolls)	16	11.95	
	Postage and packing: orders under £100	28	2.95	
	orders over £100	29	4.95	
			TOTAL £	

Please tick if you require a VAT receipt

*I enclose a cheque/postal order payable to Sinclair Research Ltd for £ _____

*Please charge to my Access/Barclaycard/Trustcard account no. _____ Please print.

 *Please delete/complete as applicable.

Mr/Mrs/Miss _____


Address _____

FREEPOST – no stamp needed. Prices apply to UK only. Export prices on application. EVE 809

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

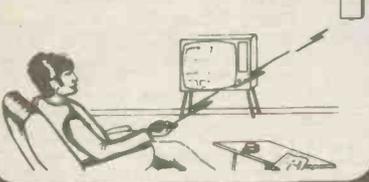- TDR300K Remote Control Dimmer **£14.30**
- MK6 Transmitter for above **£4.20**
- TD300K Touchdimmer **£7.00**
- TDE/K Extension kit for 2-way switching for TD300K **£2.00**
- LD300K Rotary Controlled Dimmer **£3.50**



DISCO LIGHTING KITS

DL 1000K
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control.



DLZ1000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum.

Optional opto input DLA1
Allowing audio ("beat")
—light response. **Only £8.00 60p**

TEACH-IN '82

- EE Minilab **£13.50**
 - Parts 1-6 **£7.50**
 - Parts 7-12 **£4.90**
- Special price for all kits purchased together **£23.50**
woodwork not included
The above kits include all the components specified in the Teach-In '82 projects parts 1 — 12 plus sockets for ICs specified.

LCD 3 1/2 DIGIT MULTIMETER
16 ranges including DC and AC voltage, DC current and resistance+NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x88x31mm. Requires PP3 9v battery. **ONLY £31.00**

REMOTE CONTROL

Published remote control systems tend to be quite complex requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using Infra-red, our KITS range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs or three analogue outputs for controlling, e.g., TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, triacs, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices. We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself—SEND US 35p and a stamped addressed envelope for your copy TODAY!



DISPLAYS

- COX87A 0.5" dual, c.a. Red **£1.80**
- DL340M 0.1" 4-Digit c.c. **£4.50**
- FND 500 0.5" c.c. **85p**
- FND 507 0.5" c.a. **85p**



- MP463 4-digit 0.5" multiplexed c.c.
- LED Clock Display **£2.20**

Liquid Crystal Display, 3 1/2 digit, 0.5" digits, d.I.I. package **£8.00**

- KL901 9-digit, 7-seg. 0.1" c.c. LED calculator display with red filter **55p**

TRANSISTORS

- BC108 **8p**
- BC109 **15p**
- BC182 **8p**
- BC182L **8p**
- BC212 **9p**
- BC212 **9p**
- BC327 **12p**
- BC337 **13p**
- BFY50 **20p**
- TIP31A **40p**
- 2N3055 **45p**
- 2N3442 **115w 140v**
- 2N3819 N ch fet **20p**

VAMOS POWER FETS

- VN10KM 0.5A/60V **52p**
- VN66AF 2A/60V **88p**

24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



- CT1000K Basic Kit **£14.90**
- CT1000K with white box (56/131 x 71mm) (Ready Built) **£17.40 £22.50**

DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7106 chip (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.



Price **£15.50**

3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK102. **£5.00**

FREE SHORT FORM CATALOGUE — send SAE (6" x 9"). We also stock Vero, Books, Resistors, Capacitors, Semi-Conductors etc.


FAST SERVICE · TOP QUALITY · LOW LOW PRICES

ALL PRICES EXCLUDE VAT

No circuit is complete without a call to —

TK ELECTRONICS
11 Boston Road
London W7 3SJ

EE

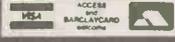


TEL: 01-567 8910 ORDERS
01-579 9794 ENQUIRIES
01-579 2842 TECHNICAL AFTER 3PM

Add 55p postage & packing +15% VAT to total. Overseas Customers: Add £1.75 (Europe), £4.50 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability. 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)

OPEN




Guess who builds this great

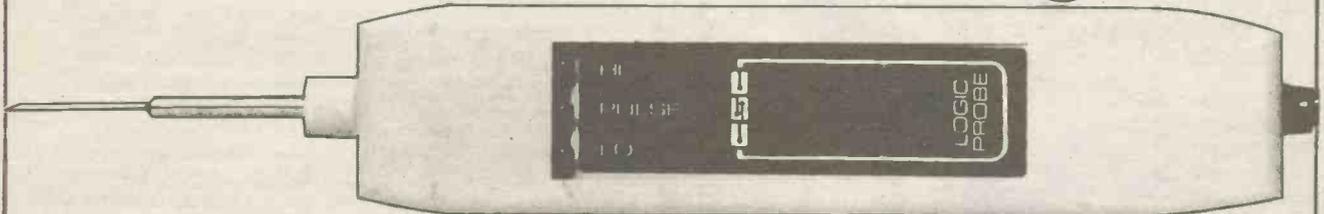

Logic Probe...YOU! for only £12.50


With this easy-to-build Logic Probe Kit from GSC and just a few hours of easy assembly — thanks to our very descriptive step-by-step manual — you have a full performance logic probe.

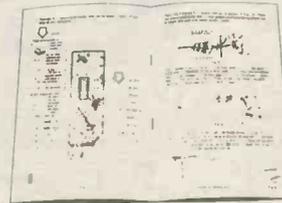With it, the logic level in a digital circuit is indicated by light from the Hi or Lo LED; pulses as narrow as 300 nanoseconds are stretched into blinks of the Pulse LED, triggered from either leading edge. You'll be able to probe deeper into logic with the LPK-1, one of the better tools from GSC.



Complete, easy-to-follow instructions help make this a one-night project.

GLOBAL SPECIALTIES CORPORATION

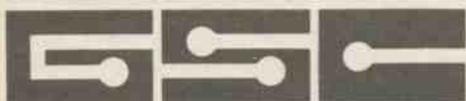

G.S.C. (UK) Limited, Dept. 42
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ.
Telephone: Saffron Walden (0799) 21682
Telex: 817477.

GLOBAL SPECIALTIES CORPORATION. DEPT 42
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name _____

Address _____

Inc P&P and 15% VAT
LPK-1 £15.52

I enclose cheque/
PO for £ _____

FREE Catalogue
tick box

Phone your order with Access, Barclaycard
or American Express Card No. _____

Expiry date _____

Beginners' luck

30% OFF
10 selected kits
for first-time
builders




Shortwave
Listener's
Receiver

With Heathkit, you're all set for a great deal. And not just big savings.

Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need is there.

Digital Clock

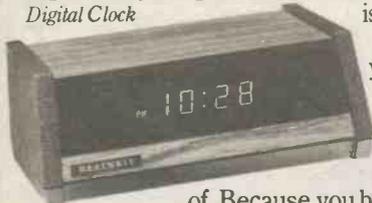

Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud


of. Because you built it yourself.

There are 10 great kits to start you off. An interesting choice of a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

All at 30% off to first-timers. Send for your catalogue right now for a start.



Windspeed and Direction
Indicator

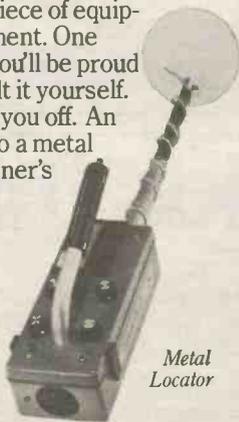

Metal
Locator

To Heath Electronics
(UK) Limited, Dept (EE 9),
Bristol Road, Gloucester GL2 6EE.

EE 9

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name _____

Address _____



HEATH **You build on our experience**
HEATHKIT

C.B. EXTRA! FABULOUS FRONTS

FRONT-END ADD-ON DIY KITS FOR GREATER FUN FROM YOUR RIG

These are suitable for CB or standard audio use depending on socket type chosen (you will need two sockets—see below).

COMPRESSOR. Really helps avoid blasting your mods and adjacent channels! Preset it for the maximum that your rig will like and your signal strength won't top it. SET-133-LS £12-37

FUNNY TALKER MK2. Modified ring modulator for fascinating metallic and modulated quality to your voice. Includes new high-gain pre-amp, voltage stabiliser, and output level control. SET-99MK2-LS £19-06

Add-on kit for MK1 users to convert to the MK2 (box not required). SET-99ADN £3-39

MULTIPLIER. Are you using several front-end add-ons? This unit splits the microphone signal in up to 8 directions for feeding various extras, and also contains a six-input mixer for recombining the add-on signals onto one line. An extra two kits read for each to-from direction. SET-132-LS £11-60

MUSICAL CALL SIGN. Programme your own individual 8-note call sign. Push button operated for use when you want. SET-121-LS £14-23

ROGER TWO-GONG. Two-tone gong-like sound automatically activated at the end of transmission. SET-126-LS £12-31

SIGNAL COMPARATOR. Uses special three-colour LEDs to give a visual indication of speech level. Also compares microphone level with levels from other units such as Roger Bleeps, etc. Helps avoid overmodulation and cross-channel break-through. SET-129-LS £16-70

SIMPLE REVERB. Enhances the spacious quality of your transmission, and at full control can produce that 'Monster-from-the-Deep' effect. With control over balance, echo and duration. The response from listeners is astonishing! SET-122-LS £20-39

SINGLE ROGER. Gives a single bleep of a preset duration and pitch when the microphone switch is released at the end of transmission. SET-127-LS £10-87

SPEECH PROCESSOR. Dramatically improves the intelligibility of speech signals. We are making many sales on this directly because people have heard it on the air! SET-110-LS £11-77

VOICE FILTER. For limiting the frequency band-width that reaches the rig from the microphone, helping to reduce background noise. Six selectable ranges plus by-pass. SET-131-LS £12-75

VOICE OPERATED SWITCH. Avoid the danger and inconvenience of hand-held mobile transmission and let your voice do the switching for you! SET-123-LS £13-80

CB POWER SUPPLY. From the mid-range of 13-8 volts, can be set anywhere between about 10v and 15v at approx. 300mA. Ideal for driving all these various CB add-ons! (Mic skts not reqd). SET-130-LS £13-85

CONNECTORS AVAILABLE

4-pin chas skt	SKT-SC4	46p
4-pin line skt	SKT-LS4	POA
4-pin chas plug	PLG-SP4	46p
4-pin line plug	PLG-LP4	62p
5-pin DIN 180° skt	SKT-KS	16p
5-pin DIN 180° plug	PLG-KP	34p
Std jack skt mono	SKT-US	20p
Std jack plug mono	PLG-UP	18p

If connectors ordered with kits no P&P charge, else add 60p to total.

Sets include electronic components, PCB, instructions, box. Prices incl. UK P&P, 15% VAT, E.&O.E. Subject to stock. Terms C.V.O. mail order or collection by appointment. Access & Barclay accepted. Send S.A.E. (3 x 4 or bigger) for further details. Despatch usually 7 days on most items. Other kits in prep. Exports welcome, send £1 for Export list.

PHONOSONICS

DEPT EE29, 22 HIGH STREET, SIDCUP,
KENT DA14 6EH. 01-302-6184 MON-FRI
FOUNDED 1972. A DECADE OF DESIGN AND DELIVERY!

(DUE TO POPULAR DEMAND) EXTENDED OFFER!

As an introduction to CRICKLEWOOD ELECTRONICS LTD., (Marshall's Old Shop), 40 Cricklewood Broadway, London NW2 3ET tel: 01 452 0161 Whilst stocks last and only if accompanied by this Ad.

DESOLDERING TOOL



Now every one can afford one of these superb, anodised aluminium high pressure hand desoldering tools at nearly half our normal price. Normal Price £6-50 + VAT with this ad £3-85 + VAT. Spare Teflon screw-in noses 75p + VAT.

JAPANESE TRANSISTORS May not be as hard to replace as you think. Phone our equivalent service on 01 452 0161 (everyday except Wednesdays) or write. We have thousands of Transistors, ICs, LEDs in stock, as well as every conceivable type of component—Why not make CRICKLEWOOD ELECTRONICS your personal ELECTRONICS HOBBY CENTRE? We have the goods!

Now you need no longer grope in the dark. For a miniature price you can catch those volts move! See those resistors jump to life!

THE MIGHTY MINI MULTI-TESTER 2,000 ohms per volt. DC & AC Voltage ranges: 10v, 50v, 250v, 1000v. DC current ranges 100mA. Resistance ohms x 10, ohms x 100db from -10db to +22db. Mirror arc scale, overload protected, complete with battery, test leads & instructions. Usual price £8-65 + VAT; with this Ad: £4-95 + VAT.



ORDER FORM

Name _____
Address _____

Desoldering tools @ £3-85 = £.....
Spare Teflon noses @ .75 = £.....
Mighty Mini Testers @ £4-95 = £.....
Postage, packing and Insurance @ 60p per one device 25p for each additional device £.....

Sub total £.....
Add 15% VAT £.....
£.....

I enclose cheque no/P.O. no. _____
Alternatively please credit my VISA/ACCESS no. _____

Signature _____
This offer applies to UK only. Please allow 7-10 days delivery. Overseas customers please do not add VAT but allow enough to cover postage.
TRADE ENQUIRIES WELCOME.

CRICKLEWOOD ELECTRONICS LTD.
40 Cricklewood Broadway, London NW2 3ET tel 01 452 0161

CLASSIFIED

The prepaid rate for classified advertisements is 31 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.24 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury

notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

Receivers and Components

P.C. BOARD S.S. 12in×12in 3 for £2.00, glass fibre P.C board S.S. or D.S. 12in×12in £1.00 each. Add 60p P&P any quantity. **COOPER**, 16 Lodge Road, Hockley, Birmingham B18 5PN.

POWER SUPPLIES, chassis mounted (unboxed). Output fully variable between 5 Volts and 27 Volts. Maximum current 1 Amp between 11 and 15 Volts. £8 post paid. **RUSSELL**, 33 Longridge Avenue, Stalybridge, Cheshire.

BUILD YOURSELF a Valve Radio or Amplifier! We can supply most parts and data. Lists 65p or SAE enquiries. New Valves! ECH81/80½ p, EF80/67p, EF85/69p, EF86/83p, ECC83/86p, EL34/£2.18½ p, EL84/80½ p, EZ80/75p. P&P/75p. Holders (B7G/PCB, 23p), Transformers, Capacitors, Resistors, etc. Callers welcome. Letchworth Electronic Components, Spirella Building, Bridge Road, Letchworth, Herts SG6 4ET. Tel: (04626) 70354.

SCOOP PURCHASE! TELEPHONES

Black GPO type for extension use. As new only £4.75 each. Carriage £1.75. 2 for £12 including carriage. **HAVE YOU SEEN THE GREEN CAT?** 1000s of new components, radio, electronic, audio at unbelievably low prices. Send 40p and receive list and FREE RECORD SPEED INDICATOR. Try a JUMBO PACK. Contains transistors, caps, resistors, pots, switches and radio and electronic devices. Over £50 for £11. Carriage £2.50. **MYERS ELECTRONICS**. Dept E.E., 12/14 Harper Street, Leeds LS2 7EA. Tel: 452045. Open 9 to 5. Mon to Sat. Callers welcome.

MANUFACTURERS SURPLUS new components, ICs, transistors, diodes, capacitors, resistors, etc. 100 assorted £1.25 post free. **U.H.A. Ltd**, 62 Wellington Road South, Stockport, Cheshire.

P.C. BOARD D.S. 7in×7in 30p; 9in×9in 40p; 9in×13in 50p; S.S. 15in×7in 40p; 18in×6in 50p. P&P 10p per £1.00. **TULETT**, Kempes Corner House, Boughton Aluph, Ashford, Kent.

Receivers and Components

TURN YOUR SURPLUS capacitors, transistors etc., into cash. Contact **Coles Harding & Co.**, 103 South Brink, Wisbech, Cambs. 0945-584188. Immediate settlement.

AERIAL BOOSTERS trebles incoming signal, price £7.00. SAE leaflets. **VELCO ELECTRONICS**, Ramsbottom, Lancashire BL0 9AG.

CHEAP COMPONENTS SUPPLIED, telephone **J. G. Electronics** day or evening Medway 250271 for prices and details.

For Sale

NEW BACK ISSUES OF "EVERYDAY ELECTRONICS". Available 85p each Post Free, cheque or uncrossed PO returned if not in stock. **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

Veteran & Vintage

"SOUNDS VINTAGE"

The only magazine for all vintage sound enthusiasts, packed with articles by top writers, covering gramophones, phonographs, 78s, wireless, news, history, reviews, etc. Bi-monthly. Annual subscription £8.75 (airmail extra). Send 75p for sample copy. 212 Lower High St., Watford, Herts.

Educational

COURSES—RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination and obtain your licence, with an RRC Home Study Course. For details of this and other courses (GCE, professional examinations, etc) write or phone—**THE RAPID RESULTS COLLEGE, DEPT JR2**, Tuition House, London SW19 4DS. Tel: 01-947 7272 (9 am-5 pm) or use our 24 hour Recordacall Service: 01-946.1102 quoting Dept JR2.

Equipment Wire

MULTI-COLOUR WIRE-PACKS

28 Different Colours/Bi-colours

DEF 61-12 (part 6) Type 2

Black · Blue · Brown · Green · Grey · Orange
Pink · Red · Violet · White · Yellow · Green/Red
Green/Yellow · Grey/Blue · Grey/Black
Orange/Red · Orange/Black · Pink/Black
Purple/Red · Red/Black · Red/Blue · Red/Brown
Red/Green · White/Black · White/Red
Yellow/Green · Yellow/Red · Yellow/Black

5 metres of each
7/0.2 set £6.55 16/0.2 set £9.95

Start Technology
a division of Space Applications Ltd

Def. EE
The Mallings
Sawbridgeworth
Hertfordshire
CM21 9LY
0278 724970

no extras
for VAT p&p
inclusive prices

Courses

SOUND ENGINEERS

If you're following a career in Sound Engineering or interested in learning all aspects of recording studios you should attend one of our weekend studio courses. Topics covered include:

- The basics of studio construction, wiring and materials used.
- Types of microphone uses, techniques, and limitations.
- Use of 2" 16 track machine, lining up, remotes, etc.
- Use of 24 Channel Desk and all controls.
- Effect equipment, ADT, reverb, Echo, etc.
- Ancillary equipment.
- Mixing and Editing.

There are a maximum number of 8 students on each course and every one is tutored to their own level of knowledge with regard to their needs and interest. The cost is £98 for the weekend including hotel accommodation overnight. **Details: please phone 01-580 4720 or 01-636 5308 during office hours.**

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for..... insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)

NAME

ADDRESS

EVERYDAY ELECTRONICS

Classified Advertisements Dept., Room 2612, King's Reach Tower, Stamford Street, London SE1 9LS Telephone 91-261 5942

Rate:
31p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53826. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

9/82

Service Sheets

BELL'S TELEVISION SERVICE for service sheets on Radio, TV etc. £1.25 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to **BTS, 190 King's Rd. Harrogate, N. Yorkshire.** Tel: 0423 55885.

Full size Service Sheets by return £2 each plus L. S.A.E. except C.T.V./Music Centres from £3. Repair data with circuits named T.V.s or early VHS/Phillips Video Recorders £8-50. L. S.A.E. for free 50p magazine/quotations/etc.

T.I.S. (E.E.), 76 Churches, Larkhall, 0698-883334. Lanarks ML9 1HE.

Books and Publications

SEVEN PRECISE PRACTICAL REFERENCE BOOKS, advance your Electronics Knowledge, £2-00 each plus £1-50 P&P. Microprocessors, Memory, Transistor Logic, Linear, Fets, C/Mos, Interface Circuits. E. R. Books, West Haven, Marlton TQ3 1SJ. Offer open three months only.

Miscellaneous

FIBRE OPTIC GLASS LIGHT GUIDE. 0.064" distal diameter, £1-50 metre 0.031", £1-00 metre. Minimum order £3-00. Nyewood Equipment, 91 Tilmore Gardens, Petersfield, Hampshire.

BEGINNERS KIT covers RADIO, DIGITAL, OSCILLATORS, TIMERS. Instructions and parts for fifteen projects (except 3 volt battery), £9-50. **VYTRON (EE-27)**, 5 Mariners Drive, Portishead, Bristol BS20 8ET.

FREE MULTIMETER (Brand new)! When you order over £25 worth of our second-hand Test Gear. For details large SAE to: **S.H.E., 5 St Joseph's Park, Ballycruttle, Downpatrick.**

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4. 01 531 1568

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 34	3-30	1-90	1-00	0-80
35 to 39	3-52	2-10	1-15	0-85
40 to 43	4-37	2-65	2-05	1-46
44 to 47	8-37	5-32	3-19	2-50
48 to 49	15-96	9-58	6-38	3-69

SILVER PLATED COPPER WIRE

14 to 30	6-63	3-86	2-28	1-50
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3-97	2-41	1-39	0-94
----------	------	------	------	------

10 x 10 mtr reels 3 amp PVC cable mixed colours 3-80
Prices include P & P vat. Orders under £2 add 20p.
SAE for list of copper and resistance wire. Dealer enquiries welcome.

TELETEXT (Oracle/Ceefax) add-on adaptors for your existing television. Only £149.95 inclusive. Also Prestel. Fantastic colour graphics for microcomputers. Avon Office Services (EE), **FREPOST**, Bristol BS10 6BR (0272) 502008 anytime.

ELECTRONIC GAMES. Build your own microchip games from our detailed circuits. SAE for details. **GHT Ltd**, PO Box DR95, Dover, Kent CT16 1UL.

DIGITAL WATCH REPLACEMENT PARTS. Batteries, displays, backlights, etc. Also reports publications charts. SAE for full list. **PROFORDS**, Copners Drive, Holmer Green, Bucks HP15 6SGA.

LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Send cheque or P.O. to:
Roden Products, Dep EE
High March, Daventry,
Northants, NN11 4QE.

£4.70



MIGHTY NINETY PACKS


**SUPER VALUE PACKS ALL AT 90p each
BUY SIX PACKS AND GET A SEVENTH FREE**

Please add 20p per pack postage
Please allow 7 days delivery.

- | | |
|-----------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| MN2. 200 Ω & $\frac{1}{2}$ -watt Resistors. | MN36. 10 sub-min SP. C/O slide switch. |
| MN3. 100 1 & 2-watt Resistors. | MN37. 10 asstd audio connectors. Din phono etc. |
| MN4. 50 Wirewound Resistors. | MN40. 50 Polystyrene capacitors. |
| MN5. 100 metal oxide Resistors. 1%, 2% and 5%. | MN45. 35 asstd diodes Zener, rect, signal, switching. |
| MN8. 12 asstd potentiometers. | MN46. 15 asstd Zener diodes. |
| MN7. 25 asstd skeleton pre-set Resistors. | MN48. 200 items 4BA asstd length screws, nuts & washers. |
| MN8. 50 asstd Electrolytic Capacitors. | MN49. 200 items 6BA asstd length screws nuts & washers. |
| MN9. 100 asstd Ceramic Capacitors Pile, disc. tub and monolithic etc. | MN50. 3 pieces of veroboard useful sizes, min total 35 sq inch. |
| MN10. 100 mixed capacitors: Polyester, Polystyrene Metallised, Radial and Axial types. | MN51. 10 x 0.2" red LED. |
| MN11. 20 asstd Silver Mica Capacitors. | MN52. 10 x 0.125" red LED. |
| MN12. 8 Tantalum Bead Capacitors (useful values). | MN53. 20 x 0.1 mfd 25v ceramic disc caps. |
| MN13. 20 asstd Transistors. BC, 2N Series + Power etc. | MN54. 20 x 0.01 mfd 25v ceramic disc caps. |
| MN14. 40 IN4148 Diodes. | MN55. 10 watt audio amp board with circuit. |
| MN16. 20 min, wire-ended Neons. | MN56. 10 14 pin low profile IC skt DIL. |
| MN17. 2 12-volt Relays. Ex nearly new equip. | MN57. 10 16 pin low profile IC skt DIL. |
| MN19. 15 P.C.B. mounting M.E.S. lampholders. | MN60. 10 asstd TTL IC's. |
| MN20. 1 240-110 to 12-volt. 100ma Transformer. | MN63. 50 mixed polyester caps C280, Siemens etc. |
| MN21. 1 240-110 to 24-volt 100ma Transformer. | MN64. 5 Press to make min switches. |
| MN22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green. | MN68. 200 asstd veropins. turret taps, PCB pins etc. |
| MN23. 300 asstd screws, nuts, washers, self-tappers etc. | MN70. PCB with push SW with attractive chrome plastic knobs 1 x BD241, 1 x BC300, 2 x BC237, 1 x BC204, 4 x 1N4002, 2 x CMOS 4025, 200mm fuse holder + 22 resistors, capacitors, diodes etc. |
| MN25. 80 Assoc. rubber grommets. | MN71. IZN414 RADIO IC. |
| MN29. 75mts equipment wire, asstd colours and sizes. | |
| MN30. 3 x 2m length, 3 core, mains cable. | |
| MN32. 15 30pF Beehive trimmers. | |
| MN34. 25 min glass reed switch. | |
| MN35. 10 asstd switches: toggle, slide, micro etc. | |

BAKER 50 WATT AMPLIFIER

£69 Post £2

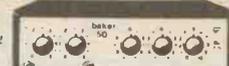

Superior quality ideal for Hi-Fi systems. Discos and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available).

BAKER 150 Watt Amplifier 4 Inputs £89
Mono Slave 150V £75. post £2 Stereo Slave £125. post £2
DRILL SPEED CONTROLLER LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. £3
DELUXE MODEL Ready Built. 800 watts. £5

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high, medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2-95

SOUND TO LIGHT CONTROL KIT MK II

Complete kit of parts, printed circuit. Mains transformer, 3 channels. Up to 1,000 watts each. Will operate from 200MV to 100 watt signal source. Suitable for home Hi-Fi £15 and all Disco Amplifiers. Cabinet extra £4-50. Post 95p
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4 or 12 for £7-50.

MAINS TRANSFORMERS Primary 240V A.C. POST
250-0-250V 70mA. 6.5V. 2A £4-50 £2
250-0-250V 80mA. 6.3V 3.5A. 6.3V 1A £5-00 £2
350-0-350V 250mA. 6.3V 6Amp C.T. £12-00 £2
220V 25mA. 6V 1A £2. 220V 45mA. 6V 2A £3-00 £1
250V 60mA 6.3V 2A £3-50 £1

General purpose (tapped outputs available)
2 amp 4, 6, 8, 10, 12, 15, 18, 25 and 50V. £6-00 £2
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9-00 £2
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £10-50 £2
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12-50 £2
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £16-00 £2
6-8-10-16V 1a £2-50 80p 12-0-12V 2a £3-50 £1
8V 1a £2-00 £1 15-0-15V 2a £3-75 £1
6-0-6V 1a £3-50 £1 20V 1a £3-00 £1
9V 250ma £1-50 80p 20V 3a £3-50 £1
9V 3a £3-50 £1 20-0-20V 1a £3-50 £1
9-0-9V 50ma £1-50 80p 20-40-60V 1a £4-00 £2
10-0-10V 2a £3-00 £1 25-0-25V 2a £4-00 £2
10-30-10V 2a £3-50 £1 28V 1a Twice £5-00 £2
12V 100ma £2-00 £1 30V 1/4a £3-50 £1
12V 750ma £2-00 80p 30V 5a £5-00 £2
12V 3a £3-50 £1 34-0-34V 6a £12-00 £2
12V 2a £3-00 £1 35V 2a £4-00 £1
TOROIDAL 30-0-30V 4 Amp +20-0-20V 4 Amp £10-00 £2

CHARGER TRANSFORMERS RECTIFIERS
6-12V 2a £4-00 £2 6-12V 4a £2-00 80p
6-12V 4a £2-50 £2 6-12V 4a £2-00 80p

R.C.S. LOUSPEAKER BARGAINS
3 ohm. 6 x 4in. 5in. 7 x 4in. £2-50. 8 x 6in. £3-00.
6in. £2-00. 8in. £3-60. 10in. £4-50. 8 ohm. 21in. £2-00.
3in. 5 x 3in. 5in. £2-50. 8in. £4-50. 10in. £5-00. 12in. £6-00.
16 ohm. 3in. 6 x 4in. 6in. £2-50. 8in. £3-50. 10 x 6in. £4-00.
25ohm. 3in. 3.5 ohm. 3in. £2-50. Many others in stock.
Speakers Covering Material Samples 51p. stamps.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 75p £3.95
All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.

PF BATTERY ELIMINATOR. BRITISH MADE £4.50
Mains Transformer Rectifier 9 volt 400ma. Post 75p
stabilised, with overload cutout. Plastic case size 6 x 5 1/2 x 2 1/2.
Suitable Radio/Cassettes. Fully isolated and Smoothed.
DELUXE Switched Model 6-7-1-9V 400ma. £7-50. post £1

THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes and all sizes of tape reel.
A.C. mains 200/240V. **£9.50**
Ideal all Computer, Tapes, Discs, Cassettes.
HEAD DEMAGNETISER PROBE £5-00.

A.C. ELECTRIC MOTORS POST 75p.
2 Pole, 240V, 0.2 Amp. Spindle—
1.43 x 0.212in. £1.75. 2 Pole,
240V, 0.15 Amp Double spindle—
1.75 x 0.16in. Each £1.2 Pole.
120V, 0.5 Amp Spindle—0.75 x
0.2in. Two in series—240V, 50p.
each. Brush Motor. From a Foot
Mixer 240V, 3 Amp High Speed
and Powerful Spindle—0.5 x
0.25in. £2.95. Good Selection.
B.S.R. Motors £4. Garrard Motors £5.

ALUMINIUM CHASSIS 18 s.w.g. Undrilled. 4 sides, riveted corners: 6 x 4 x 2 1/4in. £1.45; 8 x 6 x 2 1/4in. £1.80; 10 x 7 x 2 1/4in. £2.30; 14 x 9 x 2 1/4in. £3.00; 16 x 6 x 2 1/4in. £2.90; 12 x 3 x 2 1/4in. £1.80; 12 x 8 x 2 1/4in. £2.60; 16 x 10 x 2 1/4in. £3.20.

ALI ANGLE BRACKET 6 x 4 x 1/2 in. 25p.
ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.50; 14 x 9in. £1.45; 6 x 4in. 45p; 12 x 8in. £1.10; 10 x 7in. 85p; 8 x 6in. 75p. 14 x 3in. 72p; 12 x 3in. 72p; 18 x 10in. £1.85; 16 x 6in. £1.10; ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK. 4 x 2 1/2 x 2in. £1.00; 3 x 2 x 1in. 80p; 6 x 4 x 2in. £1.60; 8 x 6 x 3in. £2.50; 12 x 5 x 3in. £2.75; 6 x 4 x 3in. £1.80; 10 x 7 x 3in. £3.

HIGH VOLTAGE ELECTROLYTICS 32 + 32/350V 50p
8/450V 45p 50/450V 95p 32 + 32/500V £1.80
32/350V 45p 220/450V 85p 32 + 32 + 32/352V 75p
32/500V 75p 8 + 16/450V 75p 16 + 32 + 32/500V £2

DE LUXE BSR HI-FI AUTOCHANGER

Stereo Ceramic Cartridge
Plays 12in., 10in., or 7in.
records Auto or Manual. A high
quality unit 240V A.C. Post
Size 13 1/2 x 11 1/2in.
Above motor board 3 1/2in.
Below motor board 2 1/2in. **£20**
Post on All Decks £2.

BSR Single Player P204 cueing device, Ceramic £15 post £2
or with ADC. QLM 30/3 Magnetic cartridge. £20 post £2

Jarrard Single Player SP25, MK4, metal turntable, cueing device. Balanced arm Bias Compensator. £30 post £2

BSR P170 Single Player. 8 1/2in arm. 240V. A.C. Ceramic cartridge. Cueing device. Auto stop. £20 post £2

B.S.R. P232. Belt drive, magnetic cartridge, snake arm, cueing device. 12 volt D.C. £24 post £2

B.S.R. Single Player. 9 volt D.C. motor, rim drive, ceramic cartridge. £18 post £2

Radio Component Specialists
337, WHITEHORSE ROAD, CROYDON,
SURREY, U.K. TEL: 01-684 1665
Post 65p Minimum. Callers Welcome. Closed Wed.
Same day despatch. Access-Barclay-Visa. Lists 31p.

CHORDGATE LIMITED

RETAILER SHOPS AT
**75 FARRINGTON ROAD
SWINDON, WILTS.**
Tel. (0793) 33877
**21 DEPTFORD BROADWAY
LONDON SE8**

INDEX TO ADVERTISERS

Ambit	598
Bib-Audio	609
Bi-Pak	554
B.K. Electronics	Cov. III
B.N.R.E.S.	608
Bradley Marshall	554
Chordgate	615
Cricklewood Electronics	612
Dziubas, M... .. .	556
Electronic Hobbies Fair	579
Electronize Design	Cov. II
Electrovalue	606
Enfield Electronics	556
Global Specialties	611
Greenweld	616
Heath-kit	612
Intertext-ICS	613
Lightning Components	616
Literacy	616
Litesold	613
Magenta Electronic Supplies Ltd.	555
Maplin Electronics	Cov. IV
Phonosonics	612
R & T.V. Components	606
Radio Component Specialists	615
Rapid Electronics	557
Sinclair Research	610
Titan Transformers	613
T.K. Electronics	611
Watford Electronics	558
Wilmslow Audio	556, 606

SUMMERTIME SALE!!


DEDUCT 20% OFF ALL ORDERS OVER £10

from this advert (except 5mm red LED SCOOP)
All prices include VAT at 15%—just add 50p post

1982/3 CATALOGUE

- Bigger! Better! Buy one!!**
Only 75p inc. post—Look what you get!!
- Vouchers worth 50p
 - 1st class reply paid envelope
 - Wholesale list for bulk buyers
 - Bargain List with hundreds of surplus lines
 - Huge range of components
 - Low, low prices
- Sent free to schools, colleges etc.

LIE DETECTOR

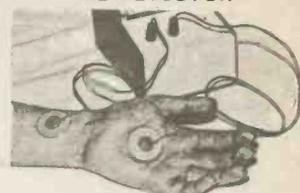

This beautifully made precision instrument is not a toy or gimmick, it was originally on an Open University course to measure changes in emotional balance by detecting small changes in skin resistance. Full details of how to use it are provided, together with a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 x 4½V batteries. Overall size 155 x 100 x 100mm. The 100-0-100uA 4" panel meter is worth more than we're asking for the whole unit!! £7-95

COMPONENTS

- 2200uF 100V cans 77 x 35mm 75p each; 10 for £5-50
- MK 4027 shift register 8 for £8
- 2708 EPROM £1-50
- MIR50 infra red 5mm LED 30p
- DM160 tuning indicator 50p
- AY-5-4007D 24DIL chip counter/ 4 decade up/down 7 seg o/p 0-6MHz. —12, —5V supply £1
- FND501 + 1 0-5in red display comm. cathode 25p
- MAN6710 Dual digit Red 0-56in 7 seg display. Supplied with pin-out and data £1
- Murata ceramic filter 5-5MHz 40p
- 10M ½W resistors 5% carbon film. Pack of 200 for £1

COMPONENT PACKS

- K503 150 wirewound resistors, 1W-12W. Wide range of values, £2
- K518 200 disc ceramic caps. Big variety of values and voltages £1

DISC CERAMICS

- 0-22uF 12V 9mm dia. Ideal for decoupling 100 for £2-75; 1000 £20
- 0-5uF 12V 15mm dia. 100 £1-50; 1000 £12

SWITCH BARGAIN

- Push-on, push-off "table lamp" type, rated 2A 250V ac. 10p each, 15 for £1, 100 for £5

741 OP-AMP—12 for £1

- A recent purchase of Raytheon IC's included a large quantity of 14 DIL 741 op-amps, so take advantage while stock lasts 12 741's £1

'STARBIRD'

Gives realistic engine sounds and flashing laser blasts—accelerating engine noise when module is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt. clip (needs PP3). PCB size 130 x 60mm. Only £2-95

1000 RESISTORS £2-50

We've just purchased another 5 million preformed resistors, and can make a similar offer to that made two years ago, at the same price!! K523—1000 mixed ½ and ¾W 5% carbon film resistors, preformed for PCB mntg. Enormous range of preferred values 100 for £2-50; 5000 £10; 20k £36

5mm red LED SCOOP G1 type

- 25 £1-95
- 100 £5-00
- 250 £13-50
- 1K £39-50
- 5K £185-00

GREENWELD

443D Millbrook Road, Southampton, SO1 0HX

LIGHTNING

DO YOU NEED :- Electronic components, Tools, Test Equipment, Cases, Cabinets and Hardware etc. IN A HURRY? THEN YOU NEED:-

LIGHTNING Electronic Components.

WHY?

Because LIGHTNING Strikes out where others fail:-

- Express Despatch
- All Low Prices
- In Depth Stock
- All New Guaranteed Goods from Leading Manufacturers

With all that going for us, going to you can you really afford to be without a copy of our brand new exciting CATALOGUE?

Many Prices Reduced — Many More Stock Lines

Send for YOUR Copy Now, ONLY 70p Post Paid

LIGHTNING ELECTRONIC COMPONENTS

84 Birchmoor Road, Birchmoor, Tamworth, Staffs. B78 1AB. (NOTE New Address)




National Literacy Week
6-12 September 1982



Literacy

...don't take it as read

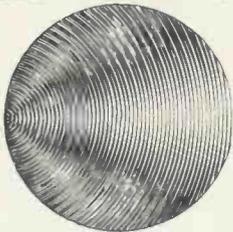For further information contact:
Adult Literacy & Basic Skills Unit, Kingsbourne House,
229/231 High Holborn, London WC1V 7DA.
Telephone: 01-405 4017




APPROVED
thandar
STOCKIST

B.K. ELECTRONICS

A SOUND CHOICE

APPROVED
thandar
STOCKIST

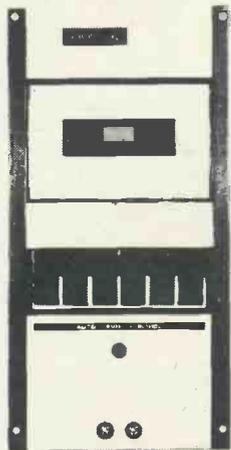★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



6 piano type keys

STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.

NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price: -


15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz. magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

8" 50 watt R.M.S. Impedance 8 ohm, 20 oz magnet, 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz, Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. **Price: White cone £8.90 each. Black cone/grill £9.50 each.** P. & P. £1.25.

PIEZO ELECTRIC TWEETERS - MOTOROLA

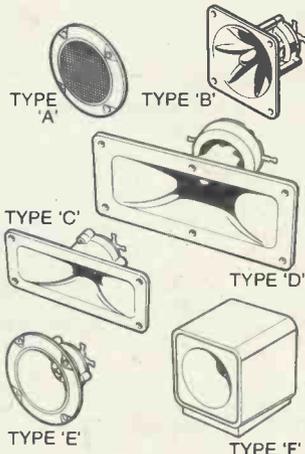Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN1036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. **Price £3.45 each.**

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems, etc. **Price £4.35 each.**

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For Hi-Fi systems and quality discos, etc. **Price £5.45 each.**

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2,000 c/s). Suitable for Hi-Fi systems and quality discos. **Price £6.90 each.**

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems, etc. **Price £4.35 each.**

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. **Price £10.75 each.**

U.K. post free (or SAE for Piezo leaflets).



1 K-WATT SLIDE DIMMER

- ★ Controls loads up to 1KW.
 - ★ Compact Size 4 1/2" x 1 1/2" x 2 1/4".
 - ★ Easy snap in fixing through panel/cabinet cut out.
 - ★ Insulated plastic case.
 - ★ Full wave control using 8 amp triac.
 - ★ Conforms to BS800.
 - ★ Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's/theatres, etc.
- Price £11.70 each + 50p P&P. (Any quantity.)**



1000 MONO DISCO MIXER

completely built and tested employing modern I.C. circuitry. Can be mounted vertical or horizontal into cabinet, console, etc. Two turntable inputs (ceramic) plus aux. (tape) and mic. inputs. Headphone monitor socket. Compatible with OMP100 Power Amp. (500mV O/P). Controls: Microphone talk over switch with separate volume, treble and bass. Three main fader (level) controls with master volume, treble and bass. Monitor selector switch with monitor level control. Mains On/Off switch. Smart black finish. Size: 535 x 110 x 60mm. Power requirements: 240V A.C. **Price: £39.99 + £2.25 P & P.**



B.S.R. P232 TURNTABLE

- P232 Turntable ★ 'S' shaped tone arm
- ★ Belt driven ★ Aluminium platter
 - ★ Cueing lever ★ 240 volt AC operation (50Hz)
 - ★ Cut-out template supplied
 - ★ Used as standard by Hi-Fi and Disco manufacturers
 - ★ Fitted with either a magnetic or ceramic cartridge, please state cartridge required
- Price £22.50 + £2.50 P & P.**



POWER AMPLIFIER MODULES


100 WATTS R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. Vu meter available as an optional extra.

SPECIFICATION: Max. output power 100 watts R.M.S. (OMP 100)

Loads: (Open and short circuit proof) 4-16 ohms
Frequency Response: 20Hz-25KHz ±3dB
Sensitivity: for 100 watts 500mV at 10K

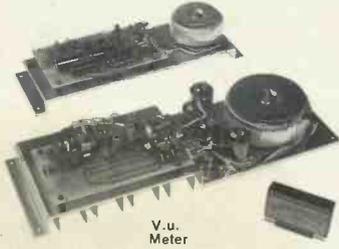T.H.D. 00.1%
Size: 360 x 115 x 80mm
Prices: OMP 100 £29.99 P & P £2.00
V.u. Meter £6.50




V.u. Meter

A PURPOSELY DESIGNED 40 WATT R.M.S. 8 OHM SPEAKER SYSTEM RECENTLY DEVELOPED BY MULLARD'S SPECIALIST TEAM IN BELGIUM. Kit comprises a Mullard 8" Woofer with foam surround and aluminium voice coil. Mullard 3" high power dome tweeter. B.K.E. built and tested crossover, based on Mullard circuit combining low loss components, glass fibre board and recessed loudspeaker terminals. Recommended cabinet size 240 x 216 x 445mm. A superb sound at a relatively low cost.

Price £14.90 + £1.50 p & p per kit.

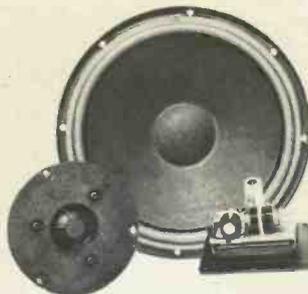New 5" 30 watt mini version of above now available. Recommended cabinet size 180 x 155 x 295mm **Price £13.90 + £1.00 p & p per kit.**



12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz. magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. **Attractive blue cone with aluminium centre dome.**

Price £17.99 ea + £2.50 P & P.



B.K. ELECTRONICS

DEPT. E.E.

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.




Make it with MAPLIN

KEYBOARD KIT WITH ELECTRONICS FOR ZX81

- * A full size, full travel 43-key keyboard that's simple to add to your ZX81 (no soldering in ZX81).
- * Complete with the electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections making entry far easier.
- * Powered from ZX81's own standard power supply - with special adaptor supplied.
- * Two-colour print for key caps.
- * Amazing low price.

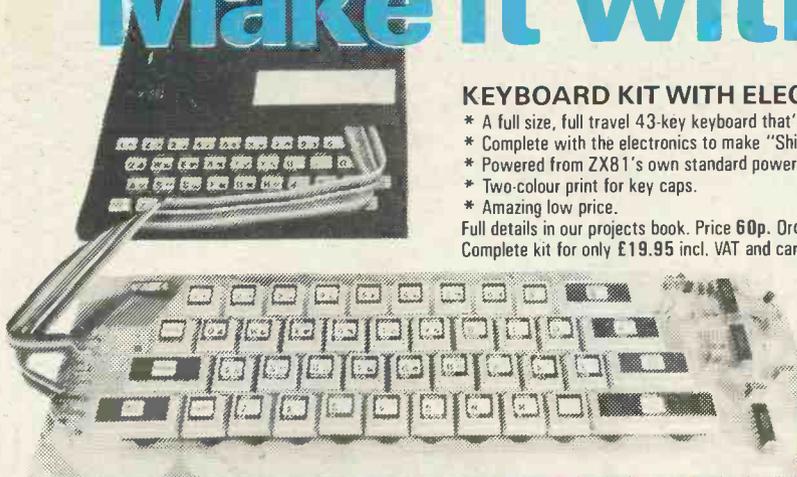Full details in our projects book. Price 60p. Order As XA03D.
Complete kit for only £19.95 incl. VAT and carriage. Order As LW72P.



25W STEREO MOSFET AMPLIFIER

A superb new amplifier at a remarkably low price.



- * Over 26W per channel into 8Ω at 1kHz both channels driven.
- * Frequency response 20Hz to 40kHz ± 1dB.
- * Low distortion, low noise and high reliability power MOSFET output stage.
- * Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
- * Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in our projects book. Price 60p. Order As XA03D
Complete kit for only £49.95 incl. VAT and carriage. Order As LW71N

MATINÉE ORGAN

Easy-to-build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50. Order As XH55K.
Complete kits available:
Electronics - £299.95,
Cabinet - £99.50 (carriage extra).
Demo cassette price £1.99. Order As XX43W.



HOME SECURITY SYSTEM

Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability. Full details in our projects book. Price 60p. Order As XA02C.



MAPLIN'S FANTASTIC PROJECTS

Full details in our project books only 60p each.

In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier · Universal Timer with 18 program times and 4 outputs · Temperature Gauge · Six Vero Projects

In Book 2 (XA02C) Home Security System · Train Controller for 14 trains on one circuit · Stopwatch with multiple modes · Miles-per-Gallon Meter

In Book 3 (XA03D) ZX81 Keyboard with electronics · Stereo 25W MOSFET Amplifier · Doppler Radar Intruder Detector · Remote Control for Train Controller

In Book 4 (XA04E)* Telephone Exchange expandable up to 32 extensions · Ultrasonic Intruder Detector · Frequency Counter 10Hz to 650MHz · Remote Control for 25W Stereo Amplifier

*Projects for book 4 were in an advanced state at the time of writing, but contents may change prior to publication (due 14th Aug 1982).

MORE GREAT KITS FROM MAPLIN

Matinée Organ (see box above)

Spectrum Synthesiser. Full details in book XH56L. Price £1.00

3800 Synthesiser } Full details in book XF11M. Price £2.00

5600S Synthesiser }

150W Power Amp Kit LW32K. Price £17.95*

75W MOSFET Power Amp Kit LW51F. Price £11.49*

50W Power Amp Kit LW35Q. Price £14.95*

15W Power Amp Kit YQ43W. Price £6.45*

8W Power Amp Kit LW36P. Price £4.45*

*Construction details with kit. (Power supply not included - details with kit).

MAPLIN

ELECTRONIC SUPPLIES LTD.

All mail to:

P.O. Box 3, Rayleigh, Essex SS6 8LR

Tel: Sales (0702) 552911 General (0702) 554155

Shops at:

159 King St., Hammersmith, London W6. Tel: 01-748 0926

284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000

Lynton Square, Perry Barr, Birmingham. Tel: (021) 356 7292

Note: Shops closed Mondays

Maplin launches MAPCARD

A new way of buying from Maplin!

Now Maplin have their own credit card. You could have one too!

APPLY NOW!

Write to our Rayleigh address for details or pick up a leaflet in our shops.



NEW SHOP IN BIRMINGHAM

Visit our brand new shop in Birmingham for our complete range of electronic components and computers.

Come and see us at Lynton Square, Perry Barr, Birmingham (just off the junction of the Outer Ring Road A4040 and Birchfield Road A34). Tel: 021-356-7292. Excellent free parking.

Opening Tuesday 24th August, 1982



Don't miss out - get a copy of our catalogue now! Over 140,000 copies sold already!

On sale now in all branches of WHSMITH price £1.

320 big pages packed with data and pictures of over 5,500 items.



Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&tp). If I am not completely satisfied I may return the catalogue to you and have my money refunded.

If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____

Address _____

Delivery within 14 days

EE682