


Easy to build projects for everyone

# Everyday ELECTRONICS

OCT. 82  
80p

## FREE TRANSISTORS

FOR USE WITH  
OUR CIRCUITS

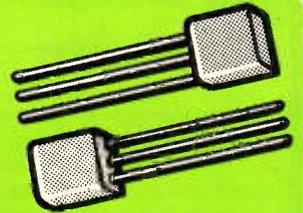


## SEDAC Prize Winning Project COMPUTER EXPANSION SYSTEM
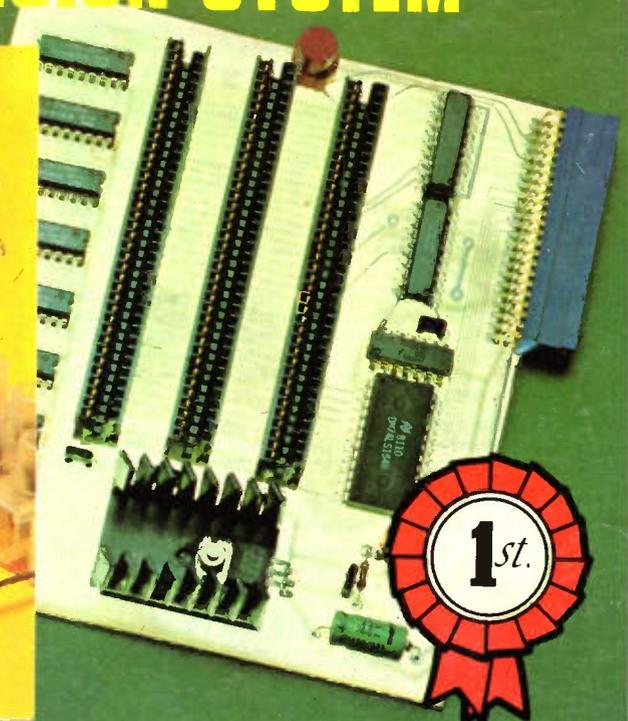
### INTRODUCING ELECTRONICS

*Six Part Series*




*An easy way to learn  
-with Simple Experiments*



### SIMPLE S.W. RADIO CAR LIGHTS ALERT OPTICAL TACHOMETER

# ELECTRONIC IGNITION KIT

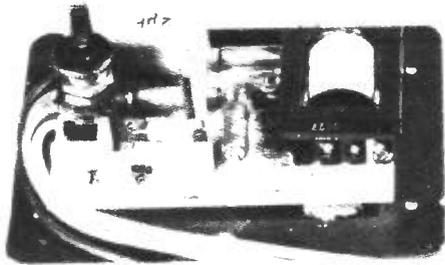

**TOTAL ENERGY DISCHARGE** electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** — higher output voltage under all conditions.

**IMPROVED ECONOMY** — no loss of ignition performance between services.

**FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

## PLUS

**SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** — full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

## IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

## AS REVIEWED IN

**ELECTRONICS TODAY INTERNATIONAL JUNE '81 ISSUE**  
and **EVERYDAY ELECTRONICS DECEMBER '81 ISSUE**

**FITS ALL NEGATIVE EARTH VEHICLES,**

**6 or 12 volt, with or without ballast**

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS**

Some older current impulse types (Smiths pre '74) require an adaptor —  
PRICE £2.95

**STANDARD CAR KIT £14.85**  
**ASSEMBLED AND TESTED £24.95**

PLUS £1

**TWIN OUTPUT KIT £22.94**

U.K. P.&P.

For MOTOR CYCLES and CARS with twin ignition systems  
**ASSEMBLED AND TESTED £34.70**

Prices include V.A.T.

## ELECTRONIZE DESIGN Dept. C

Goods normally despatched within 7 days

Magnus Road, Wilnecote,  
Tamworth. B77 5BY  
Phone 0827-281000

BARCLAYCARD

VISA

**DIMENSIONS:**  
Length 12.5 cm  
Width 8.9 cm  
Height 4.3 cm  
Lead length 100.0 cm

## TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µs at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DISCHARGE system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

**SUPER POWER DISCHARGE CIRCUIT** A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

**HIGH EFFICIENCY INVERTER** A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

**PRECISION SPARK TIMING CIRCUIT** This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

## TYPICAL SPECIFICATION


	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY (STORED ENERGY)	36 mJ	10 mJ
	135 mJ	65 mJ
SPARK DURATION	500 µs	160 µs
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	26 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µs	30 µs

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.
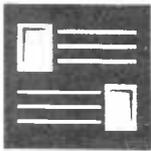
# Everyday ELECTRONICS

VOL. 11 NO. 10 OCTOBER 1982

PROJECTS . . . THEORY . . . NEWS . . .  
COMMENT . . . POPULAR FEATURES . . .



## YOUR FREE TRANSISTORS

See pages 628 and 632



## START NOW

Our policy is to make electronics an easy to follow and enjoyable hobby. First steps can be difficult, and so in presenting a new six-part series **Introducing Electronics**, we have deliberately eliminated the business of soldering. Just a screwdriver and wire cutters are required to start off on practical work, because all connections between components are made by means of screw-terminal blocks. And with the longer evenings coming, what could be a better time to start studying electronics than now?

## SCHOOLS Electronic Design Award COMPETITION

### CALLING ALL SCHOOLS

The second Schools Electronic Design Award Competition (SEDAC) is announced in this issue. Please turn to page 647 for full details.

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

## PROJECTS

- SINE WAVE GENERATOR** by R. A. Penfold 628  
Covers 15Hz—1.5MHz in 5 ranges
- GENERAL PURPOSE PRE-AMPLIFIER** by R. A. Penfold 632  
Wide band, low noise unit
- ZX81 EXPANSION SYSTEM** by M. Lysejko and A. Hudson 636  
More memory plus communication slots
- OPTICAL TACHOMETER** by P. Leah 648  
Digital measurement of revolutions per minute
- LIGHTS ON ALERT** by T. R. de Vaux-Balbirnie 662  
Looks after your car battery
- SIMPLE SW RADIO** by A. Sproxton 665  
Two-transistor t.r.f. circuit

## SERIES

- INTRODUCING ELECTRONICS** by G. Hylton 642  
Part 1: From Electrons to Electronics
- A.C. MAINS EXPLAINED** by A. Kenyon 668  
Part 4: The final part; Three phase power; A.C. motors

## FEATURES

- EDITORIAL** 627  
Wide Choice; Come To The Fair
- FREE TRANSISTORS** 631  
Parameters of this month's two free transistors
- SHOP TALK** by Dave Barrington 635  
Product news and component buying
- JACK PLUG AND FAMILY** by Doug Baker 635  
Cartoon
- FOR YOUR ENTERTAINMENT** by Barry Fox 646  
On the Line, Testing Time, Protected Network
- SCHOOLS COMPETITION** 647  
Details of SEDAC 1983
- COUNTER INTELLIGENCE** by Paul Young 655  
A retailer comments
- RADIO WORLD** by Pat Hawker G3VA 656  
Made in Britain?, TV Across Frontiers
- EVERYDAY NEWS** 658  
What's happening in the world of electronics
- PRESTEL** by C. Stringer G3RSK 660  
Your Phone-in Teletext
- BOOKS IN BRIEF** 670  
A selection of technical books recently received
- CIRCUIT EXCHANGE** 673  
A forum for readers' ideas
- SQUARE ONE** 674  
Beginners page: Circuit symbols and abbreviations

Our November issue will be published on Friday, October 15. See page 641 for details.

Readers Services ● Editorial and Advertisement Departments 627

# ambit<sup>®</sup> INTERNATIONAL

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST.

CMOS-TTL :							
4001	0.11	4515	1.25	74LS10	0.12	74LS138	0.30
4007	0.13	4516	0.60	74LS11	0.12	74LS139	0.30
4009B	0.25	4518	0.35	74LS12	0.12	74LS149	1.20
4010	0.30	4520	0.60	74LS13	0.20	74LS151	0.30
4011	0.11	4521	1.30	74LS14	0.30	74LS153	0.27
4012	0.14	4522	0.89	74LS20	0.12	74LS154	0.99
4013	0.25	4526	0.60	74LS21	0.12	74LS155	0.35
4016	0.22	4527	0.80	74LS22	0.12	74LS156	0.37
4017	0.40	4528	0.65	74LS26	0.14	74LS157	0.30
4019	0.38	4529	0.70	74LS27	0.12	74LS158	0.30
4020	0.55	4531	0.65	74LS28	0.15	74LS160	0.37
4021	0.55	4532	0.80	74LS30	0.12	74LS161	0.37
4022	0.55	4534	4.00	74LS32	0.12	74LS162	0.37
4023	0.15	4536	2.55	74LS33	0.15	74LS163	0.37
4024	0.33	4538	0.85	74LS38	0.14	74LS164	0.40
4025	0.15	4539	0.80	74LS40	0.13	74LS165	0.60
4027	0.28	4543	0.80	74LS42	0.30	74LS168	0.70
4030	0.35	4549	3.50	74LS45	0.35	74LS169	0.85
4043	0.37	4553	2.50	74LS48	0.45	74LS170	0.90
4044	0.60	4554	1.20	74LS49	0.55	74LS173	0.60
4046	0.60	4555	0.35	74LS51	0.13	74LS174	0.40
4049B	0.24	4556	0.40	74LS54	0.14	74LS175	0.40
4050	0.24	4557	2.30	74LS55	0.14	74LS181	1.05
4051	0.15	4558	0.80	74LS73	0.21	74LS190	0.60
4060	0.75	4559	3.50	74LS74	0.16	74LS191	0.60
4066	0.30	4560	2.50	74LS75	0.22	74LS192	0.45
4068	0.16	4561	1.00	74LS76	0.20	74LS193	0.42
4069B	0.14	4562	2.50	74LS78	0.19	74LS194	0.35
4070	0.18	4566	1.20	74LS83	0.40	74LS195	0.35
4071	0.16	4568	1.45	74LS85	0.60	74LS196	0.55
4072	0.18	4569	1.70	74LS86	0.14	74LS221	0.50
4073	0.16	4581	0.18	74LS90	0.28	74LS240	0.80
4075	0.16	4572UB	0.22	74LS92	0.31	74LS241	0.70
4076	0.55	4580	3.25	74LS93	0.21	74LS242	0.70
4077	0.18	4581	1.40	74LS95	0.40	74LS243	0.70
4078	0.18	4582	0.70	74LS96	1.20	74LS244	0.60
4081	0.12	4583	0.80	74LS107	0.25	74LS245	0.80
4093	0.40	4584	0.30	74LS109	0.20	74LS257	0.40
4175	0.80	4585	0.45	74LS112	0.20	74LS258	0.37
4502	0.60	40174	1.05	74LS113	0.20	74LS260	0.50
4503	0.50	40195	1.08	74LS114	0.19	74LS266	0.22
4506	0.70	74LS00	0.10	74LS122	0.35	74LS273	0.70
4507	0.37	74LS01	1.10	74LS124	1.80	74LS279	0.35
4508	1.50	74LS02	0.11	74LS123	0.35	74LS365	0.32
4510	0.55	74LS03	0.11	74LS125	0.24	74LS366	0.34
4511	0.45	74LS04	0.12	74LS126	0.24	74LS367	0.32
4512	0.55	74LS05	0.13	74LS132	0.42	74LS368	0.35
4514	1.25	74LS08	0.12	74LS133	0.24	74LS373	0.70

### Memory Micros Linears:

LM10CN	3.88	SL1611	1.60	K84433	1.52	U265	3.16
L149	1.86	SL1612	1.60	K84413	1.95	U266	2.43
U237B	1.28	SL1613	2.06	K84436	2.53	LC7137	7.50
U247B	1.28	SL1620	2.17	K84437	1.75	ICM72168	19.50
U257B	1.28	SL1621	2.17	K84445	1.29	ICM7216C	19.95
U267B	1.28	SL1623	2.44	K84446	2.75	ICM7217A	9.50
LM324	0.45	SL1625	1.62	NE5044	2.26	SP8647	6.00
LM339N	0.45	SL1630	1.44	MCS5229	9.60	95H90	7.80
LF347	1.60	SL1640	1.89	SL6270	2.03	HD10551	2.45
LM348	0.90	SL1641	1.89	SL6310	2.03	HA12009	6.00
LF351	0.49	TDA2002	1.25	SL6440	3.38	HD44015	4.45
LF353	0.76	ULN2242	3.05	SL6900	3.75	HD44752	8.00
LM380N	1.00	ULN2283	1.00	SA5610	1.48	MC145151P	6.00
ZN419CE	1.98	CA3089	1.84	SL6840	2.75	Z80A	3.75
ZN427E/8	6.28	CA3130E	0.80	SL6690	3.20	Z80A P10	3.50
NE544	1.80	CA3130T	0.90	SL6700	2.35	Z80A CTC	4.00
NE555N	0.20	CA3140E	0.46	SAS6710	1.48	Z80A DMC	9.95
SL560C	1.98	CA3189E	2.20	LS7225	3.65	Z80A DART	7.50
NE564	4.29	CA3240E	1.27	ICM7555	0.94	Z80A S10/1	11.00
NE567	1.30	MC3357	2.85	ICL8038CC	4.50	Z80A S10/2	11.00
uA741CN	0.20	LN3859	0.95	TK10170	1.87	Z80A S10/9	9.95
TBA820M	0.78	LM3909	0.68	TK10321	2.75	Z8001	65.00
ZNA1034	2.10	LM3914N	2.80	HA11223	2.15	8255	2.58
LM1035	4.50	LM3914N	2.80	HA11225	1.45	6800P	2.90
TDA1062	1.95	K84412	1.95	HA12002	1.22	6809	8.75
TDA1083	1.95	K84417	1.80	HA12402	1.95	6802	3.50
TDA1090	3.05	K844208	1.09	HA12411	1.20	68A00P	4.25
HA1197	1.00	K84423	2.30	HA12412	1.55	68B00P	4.65
MC1350	1.20	K84424	1.65	LF13741	0.33	2114-L2	1.49
HA1370	1.90	K84430	2.30	MK50375	3.85	4116-2	1.59
HA1388	2.75	K84431	1.95	MM53200	3.90	2732	4.00
SL1610	1.60	K84432	1.95	U264	2.27	2716	3.00

AND THERE'S PLENTY MORE IN THE CATALOGUE 70p inc.

### Coils, Filters: Toko, Murata, NTK, Cathodeon.

SFE6.0MA	0.80	CDA10.7MA	0.70	10M15D	14.50
CFSE10.7	0.80	SFE27MA	0.94	LFB4	1.95
SFE10.7MA	0.45	SAF10.7MC-Z	3.75	LFB6/CFU455H	1.95
CFSB10.7	0.50	MF45510AZ1218.55	15.55	LFB8	1.95
SFE10.7MJ	0.50	MFL45501L	11.95	LFB10	1.95
SFA10.7MF	0.75	10M15A	1.99	LFB12/CFU455F	1.95
SFE10.7ML	0.70	21M15A	3.45	LFH6S/	2.45
SFE10.7MX	0.95	45M15A	5.95	CFW455HT	2.45
CFSH10.7M1	0.50	10M22D	17.20	LFH8S	2.45
CFSH10.7M2	0.50	10M8D	15.50	LFH12S/	2.45
CFSH10.7M3	0.50			CFW455FT	2.45

### TOKO FIXED VALUE CHOKES (E12 Values)

7BA - 1 to 1000uH	16p	10RB - 1 to 120mH	33p
8RB - 1 to 33mH	19p	10RB - .15 to 1.5H	43p

### RETAIL SHOP OPENING HOURS

Monday to Thursday 8.30-6.30  
Friday 8.30-8.30 Saturday 9.00-5.30  
(Access + Barclaycard orders accepted)

NOW IN STOCK  
MF10 - National's new Dual  
Switched - Capacitor Filter:  
Price £5.05

ALL PRICES SHOWN EXCLUDE VAT. P&P 50p per order.

AMBIT INTERNATIONAL DEPT.EE

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

# DIGITAL MULTIMETERS

## FROM ONLY £39

(plus VAT, p&p)



Get your hands on a low-cost, high-performance digital multimeter.

Choose from these three models:

EDM-101, at £39 (+VAT, p&p), has 5 functions and 19 ranges, plus diode test (200mV to 1000Vdc; 200 and 600Vac; 200µA to 2Adc; 200 Ω to 20M Ω).

T100 (illustrated), at £49 (+VAT, p&p), incorporates 7 functions and 29 ranges including diode test and a direct 10A input. (200mV to 1000Vdc or 750Vac; 200µA to 10Aac or dc; 200 Ω to 20M Ω).

T110, at £59 (+VAT, p&p), has an additional buzzer for fast continuity testing.

Send your order in today!

### VAKO DISPLAY SYSTEMS LTD

Pass Street, Werneth, Oldham, Lancs OL9 6HZ

Tel: 061-652 5111 Telex: 668250

Please send me:

..... EDM-101 multimeters at £46.60 (incl.VAT, p&p) .....

..... T100 multimeters at £58.10 (incl.VAT, p&p) .....

..... T110 multimeters at £69.50 (incl.VAT, p&p) .....

Cheque/P.O. enclosed payable to  
Vako Display Systems Ltd. for: £

Name: .....

Address .....

Please allow 14 days for delivery.

TRADE COUNTER CALLERS WELCOME.



# ELECTRONICS IS A FINE HOBBY

## VELLEMAN-KIT



In less than a year we have become well-known for our varied and interesting range of electronic kits and our efficient service.

Graded by difficulty, the kits are of high quality, well packaged and have applications covering a wide field.

The range includes kits using microprocessors, infra-red systems, power supplies, dimmers, motor control units, amplifiers, sound and light units, digital counters, timers, VU's and many, many more.

New kits are:

- K2580 — electronic powerswitch dimmer.....£9.34
- K2581 — stereo volume and tone control.....£11.27
- K2582 — stereo audio input selector.....£11.27

**Stockists:**

S. & R. Brewster Ltd, Union Street, Plymouth, Devon.  
 Priest Electronics Systems, Lindley, Huddersfield.  
 Baxol Tele Exports Ltd, Post Rathdrum, Co. Wicklow, Rep. of Ireland.

The Velleman 'top ten' are:

- K1682 — Microprocessor timer .....£48.37
  - K1771 — FM Oscillator .....£5.45
  - K1798 — Stereo VU using LED's .....£16.91
  - K1823 — 1 amp Power supply .....£6.99
  - K2544 — Complex sound generator .....£8.28
  - K2569 — Three tone chime.....£6.56
  - K2575 — Microprocessor doorbell.....£15.53
  - K2577 — Motor speed control .....£7.57
  - K2578 — Eprom programmer.....£207.00
  - K2579 — Start stop timer .....£6.21
- (prices include VAT)

SEND FOR FREE ILLUSTRATED CATALOGUE OF COMPLETE RANGE

Enquiries from Retailers invited

**VELLEMAN (U.K.) LIMITED**

P.O. Box 30, St. Leonards-on-Sea, East Sussex,  
 TN37 7NL, England. Telephone: 0424 753246.



**Bigger and Better for 1982**  
 the colourful Wilmslow Audio brochure  
 — the definitive loudspeaker catalogue!

Everything for the speaker constructor — kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★  
 two listening lounges  
 (Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue  
 (cheque, M.O. or stamps — or phone with your credit card number)

- ★ Access — Visa — American Express accepted ★  
 also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!

Please allow 7 days for delivery



## TECHNICAL TRAINING IN ELECTRONICS, TELEVISION AND AUDIO

IN YOUR OWN HOME — AT YOUR PACE

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

### City & Guilds Certificates

Radio Amateurs  
 Basic Electronic Engineering (Joint C&G/ICS)

### Certificate Courses

TV and Audio Servicing  
 Radio & Amplifier Construction  
 Electronic Engineering\* and Maintenance  
 Computer Engineering\* and Programming  
 Microprocessor Engineering\*  
 TV, Radio and Audio Engineering  
 Electrical Engineering,\* Installation  
 and Contracting \*Quality for IET Associate Membership



Approved by CACC



Member of ABCC

### POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_



Post to: Dept 2682  
 ICS School of Electronics  
 160 Stewarts Road,  
 London SW8 4UJ



01-622 9911  
 (All Hours)

# The Rapid Electronics

Tel: 0206 36412  
Hill Farm Industrial Estate  
Boxted  
Colchester Essex CO4 5RD



TRANSISTORS		BC548	10 BF840	23 TIP29A	40 *ZTX107	8 2N3053	23
AC125	35 BC157	10 BC550	10 BF820	25 TIP29B	55 *ZTX108	8 2N3054	55
AC126	25 BC158	10 BC558	10 BF825	25 TIP29C	60 ZTX109	12 2N3055	50
AC127	25 BC159	10 BCV71	10 BF830	25 TIP30A	45 ZTX100	14 2N3442	120
*AC128	20 BC180	45 BCV72	10 BF835	25 TIP30B	50 ZTX301	16 *2N3702	8
AC176	25 BC188	10 BD115	10 BF840	25 TIP30C	60 ZTX302	15 2N3703	8
AC177	25 BC189	10 BD131	10 BF845	25 TIP31	55 ZTX304	17 *2N3704	8
AC187	25 BC190	10 BD135	10 BF850	25 TIP32A	45 ZTX500	20 2N3705	9
AC188	22 BC170	10 BD140	10 BF855	25 TIP32B	45 ZTX501	15 2N3706	10
AD142	120 BC171	10 BD133	10 BF860	25 TIP32C	60 ZTX502	15 2N3707	10
AD149	80 BC172	10 BD135	10 BF865	25 TIP33A	50 ZTX503	15 2N3708	10
AD161	40 BC177	10 BD136	10 BF870	25 TIP33C	75 ZTX504	18 2N3709	10
AD162	40 BC178	10 BD137	10 BF875	25 TIP34	85 ZTX505	25 2N3772	190
AF124	60 BC179	10 BD138	10 BF880	25 TIP34A	60 ZTX506	20 2N3773	210
AF126	50 BC182	10 BD139	10 BF885	25 TIP35	160 ZTX507	20 2N3820	40
AF139	40 *BC182L	10 BD140	10 BF890	25 TIP35A	160 ZTX508	20 2N3821	40
AF186	70 BC183	10 BD204	10 BF895	25 TIP36A	170 ZTX509	20 2N3822	65
AF239	75 BC183L	10 BD206	10 BF900	25 TIP36C	195 ZTX510	35 2N3866	90
BC167	10 BC184	10 BD206	10 BF905	25 TIP41A	60 ZTX511	20 2N3906	10
BC107B	12 *BC184L	10 BD222	10 BF910	25 TIP42A	60 ZTX512	22 2N3903	10
BC108B	12 BC212L	10 BF182	10 BF915	25 TIP42B	90 ZTX513	20 2N3904	10
BC108C	12 BC213	10 BF184	10 BF920	25 TIP42C	90 ZTX514	20 2N3905	10
*BC109	9 BC213L	10 BF185	10 BF925	25 TIP43	90 ZTX515	20 2N3906	10
BC109C	12 BC214	10 BF186	10 BF930	25 TIP43A	90 ZTX516	20 2N3907	10
BC114	22 *BC214L	10 BF195	10 BF935	25 TIP43B	90 ZTX517	20 2N3908	10
BC115	22 BC237	10 BF196	10 BF940	25 TIP43C	90 ZTX518	20 2N3909	10
BC117	22 BC238	10 BF197	10 BF945	25 TIP43D	90 ZTX519	20 2N3910	10
BC119	35 BC308	15 BF198	10 BF950	25 TIP43E	90 ZTX520	20 2N3911	10
BC137	40 BC327	14 BF199	10 BF955	25 TIP43F	90 ZTX521	20 2N3912	10
BC139	40 BC328	14 BF200	10 BF960	25 TIP43G	90 ZTX522	20 2N3913	10
BC140	30 BC337	14 *BF244B	22 MPSA12	30 TIS90	30 2N2905	22 2N5485	36
BC141	30 BC338	14 BF245	30 MPSA55	30 TIS91	30 2N2906	22 2N5777	45
BC142	25 BC477	30 *BF256B	45 MPSA56	30 *VN10KM	2N2906	25 2N5027	30
BC143	25 BC478	30 *BF257	32 MPSU05	45 2N2906A	25 40360	40	
BC147	8 BC479	26 *BF258	22 MPSU06	45 2N2907	25 40361	40	
BC148	8 BC517	40 *BF259	45 MPSU50	45 *VN2907A	40 40362	50	
BC149	9 BC547	7 BF337	40 MPSU56	45 VNE64F	95 2N2926	9 40408	70

LINEAR		ICL7611	95 LM377	150 LM13600	120 NE570	400 TL071	30
*555 CMOS	80 IC17621	180 *LM380	65 LM380	120 MC1310	150 NE571	400 TL072	50
555 CMOS	150 IC18022	180 LM381	120 MC1496	60 *RC4136	68 TL074	95	
709	25 ICL8038	320 LM392	120 MC3340	135 *RC4558	60 *TL081	25	
*74J1	14 ICL8211A	200 LM394	120 ML922	40 SL480	170 *TL082	45	
9400C	35 ICL8221	350 LM398	120 ML924	195 SL481	90 *TL083	95	
AY-3-1270	840 LF351	45 LM393	100 ML926	140 SN76477	250 *UA2240	120	
AY-3-8910	600 LF353	85 LM709	25 ML927	140 SP8629	250 ULN2003	85	
AY-3-8912	825 LF356	90 LM725	350 ML928	140 TBA120S	70 ULN2004	85	
CA3046	60 LM10	350 LM733	75 ML929	140 TBA800	80 *XR2206	300	
CA3089	215 LM311	75 LM741	14 LM857A	96 ZN414	100		
CA3090A	Q375 LM318	120 LM1458	40 NE531	250 TBA820	80 ZN423	135	
CA3130E	90 LM324	40 LM2917	200 NE544	250 TDA1008	320 ZN424	135	
*CA3140E	45 LM334Z	100 LM3900	50 *NE555	16 TDA1022	325 ZN426	330	
CA3151E	100 LM3909	125 *LM3909	70 *NE556	45 TDA1024	125 ZN427E	850	
CA3189	290 LM339	50 LM3911	120 NE565	120 TL061	60 ZN428	40	
*CA3240E	110 LM348	85 LM3914	200 NE566	150 TL062	60 ZN459	285	
ICL7106	790 LM358	50 LM3915	220 NE567	100 TL064	96 ZN1034E	200	

CMOS		*4017	38 4036	275 4055	95 4082	16 4502	60 4529	150 4532	80 4533	20 4534	485 4535	110 4536	110 4537	140 4538	140 4539	140 4799	140 4800
------	--	-------	---------	----------	---------	---------	---------	----------	---------	---------	----------	----------	----------	----------	----------

LS TTL		LS21	12 LS76	18 LS125	26 LS161	37 LS221	70 LS365	30
*LS00	11 LS26	14 LS83	40 LS132	42 LS163	37 LS241	69 LS366 <td>30</td>	30	
LS01	11 LS27	12 LS85	52 LS136	26 LS164	43 LS242	75 LS368 <td>35</td>	35	
LS02	11 LS30	12 LS86	18 *LS138	32 LS165	75 LS243	75 *LS373	65	
LS03	12 LS32	13 *LS90	28 *LS139	32 LS166	75 *LS244	80 LS374	65	
LS04	12 LS33	13 *LS92	32 *LS141	32 LS167	75 *LS245	70 LS375	65	
LS05	12 LS34	13 *LS93	28 *LS142	32 LS168	75 *LS246	70 LS376	65	
LS08	12 LS38	13 *LS95	40 *LS148	32 LS174	45 LS251	35 LS378	60	
LS09	12 *LS42	32 LS96	95 LS151	38 LS175	45 LS252	35 LS390	55	
LS10	12 *LS47	32 LS107	40 LS153	40 LS190	45 LS258	35 LS393	55	
LS11	12 LS28	22 LS108	21 LS154	90 LS191	45 LS259	75 LS399	175	
*LS12	14 LS51	14 LS112	14 LS155	25 LS192	45 LS262	75 LS399	175	
*LS13	22 LS55	14 LS113	23 LS156	36 LS193	45 LS273	68 LS670	88	
LS14	38 LS73	18 LS114	22 *LS157	30 LS195	38 LS279	35		
LS15	12 *LS74	18 LS122	38 LS158	30 LS196	50 LS283	40		
LS20	12 LS75	22 LS123	38 LS160	37 LS197	60 LS353	88		

CRYSTALS		290	6-0M	200
100KHz	370	6-144M	180	
1MHz	300	7-0M	250	
1-008M	370	8-0M	170	
1-8432	300	10-0M	180	
2-0M	270	12-0M	280	
2-4576M	220	16-0M	240	
3-276M	240	18-0M	240	
3-579M	120	18-432	220	
4-0M	150	38-667	320	
4-184M	150	16-0M	220	
4-3M	125	116M	300	
5-0M	240			

## NEW CATALOGUE

Our latest catalogue has just been released containing over 2000 stock lines all at extremely competitive prices backed by Rapids return of post service. Stocks include Denco coils, tools, Verocases, data sheets etc. etc. Send 45p for your copy now (sent free of charge with all orders over £10).

### TRANSFORMERS

Miniature mains. 50V, 90V, 120V all @ 100mA 100p each. PCB mounting. Miniature. 3VA 0-6, 0-6 @ 0.25A; 0-9, 0-9 @ 0.15A; 0-12, 0-12 @ 0.12A, 20A; 0-25A, 0-9, 0-9 @ 0.15A; 0-12, 0-12 @ 0.6, 0-6 @ 0.5A; 0-9, 0-9 @ 0.3A; 0-12, 0-12 @ 0.25A, 270p each. High quality. Split bobbin construction. 6VA 0-6, 0-6 @ 0.5A, 0-9, 0-9 @ 0.4A, 0-12, 0-12 @ 0.3A, 220p each. 12VA 0-6, 0-6 @ 1A, 0-9, 0-9 @ 0.8A, 0-12, 0-12 @ 0.5A, 0-15, 0-15 @ 0.4A. 225p each (plus 40p carriage). 25VA 0-6, 0-6 @ 1.5A, 0-9, 0-9 @ 1.2A, 0-12,



# Probably the fastest microcomputer in the universe

## the **JUPITER ACE** only £89.95.



### Key Features

- Revolutionary microcomputer language FORTH.
- Full-size moving-key keyboard.
- User-defined high-resolution graphics.
- Programmable sound generator.
- Floating point arithmetic.
- Fast cassette interface.
- Upper and lower case ascii character set.
- 24 x 32 character flicker-free display.

### The Jupiter Ace uses FORTH

The Ace is set apart from all other personal computers on the market by its use of a revolutionary language called 'FORTH'. Some computer languages are easy for humans to understand, others are easy for computers; FORTH is most unusual in being both. Its underlying principles are so simple that it takes even a newcomer to computers only a few minutes to learn how to do calculations on the Ace, yet the very same principles are powerful enough to allow you to invent your own extensions to the language itself.

At the same time, the memory-saving coded form used to store your programs inside the Ace allows it to obey them very fast — typically in less than a tenth of the time it would take to do the same thing using a different language. Amongst other things, this makes the Ace ideal for games.

FORTH's unique combination of speed, versatility and ease of programming has already made it a prime choice for professional applications as diverse as pub games and radio telescopes, and gained it an enthusiastic national user group. Now the Jupiter Ace can bring this addictive language into your own home.

### Designed by Jupiter Cantab

Leading computer Designers Richard Altwasser and Steven Vickers have a reputation for pushing technology forwards. After playing the major role in creating the ZX Spectrum they formed Jupiter Cantab to develop their latest brainchild the Jupiter Ace. Jupiter Cantab, 22, Foxhollow, Bar Hill, Cambridge, CB3 8EP

### All inclusive Price

For £89.95 you receive your Jupiter Ace, a mains adaptor, all the leads needed to connect to most cassette recorders and T.V.s (colour or black and white), a software catalogue and a manual.

The manual is a complete introduction to the world of personal computing and a course in FORTH programming on the Ace.

Even if you are a complete newcomer to computers, the manual will guide you step by step from first principles to confident programming.

The price includes postage packing and V.A.T.

### Technical Specification

#### Hardware

**Processor/Memory**  
Z80A running at 3.25 MHz.  
8K bytes ROM 3K bytes RAM.

#### Input

40 moving-key keyboard with auto-repeat on every key.

#### Output

Memory-mapped 32 x 24 character display with high resolution user graphics. Output to drive normal UHF TV set on channel 36.

#### Sound

Provided by internal loudspeaker.

#### Cassette

Load Save & Verify at 1500 baud, separate data storage.

#### Software, FORTH

##### Data Structures

Integer, Floating point and String data may be held as constants, variables or arrays with multiple dimensions and mixed data types.

##### Control Structures

IF-THEN-ELSE, DO-LOOP, BEGIN-WHILE-REPEAT, BEGIN-UNTIL, all may be mixed and nested to any depth.

##### Operators

Mathematical +, -, X, ÷,  
Logical AND, OR, NOT,  
XOR.  
Comparison <, >, =.

##### Program Editing

FORTH words may be listed, edited and redefined. Comments are preserved when words are compiled.

### Order Form

The **Jupiter Ace** is available only by mail order. Please allow up to 28 days for delivery.

Send cheque or postal order with the form to:—  
JUPITER CANTAB, 22 FOXHOLLOW, BAR HILL, CAMBRIDGE CB3 8EP

Please send me:—

JUPITER ACE MICROCOMPUTER(S) @ £89.95.

Name. Mr/Mrs/Miss

Address

EE

F



# ENFIELD ELECTRONICS

WHEN ORDERING, PLEASE ALLOW 12 DAYS FOR DELIVERY.



## NOISE FILTER SYSTEM

A sophisticated combination of filters designed to eliminate interfering noises from all vehicular sources including ignition spark, alternator/generator, other accessories, metal to metal contact etc.

Contents:- Generator noise filter, alternator noise filter, Dual line noise filter and ignition noise filter.

Price £8.50  
Order No. NFS-1000

This 3 1/2 inch super horn (Flush Flange) piezo ceramic tweeter converts electrical energy into acoustic energy at an efficiency in excess of 50%, a level not possible with any other type of loudspeaker. Economy is added to high efficiency by the elimination of crossover networks, because the unit rejects low frequency power. It has a high impedance of over 1,000 ohms at 1 kHz and 20 ohms at 40 kHz and it presents no added load to the amplifier.

A Super Special Offer of £4.65  
Order No. LO52



For up to the minute prices please ring: 01-366-1873. Please add 15% VAT & £1.00 p & p per item ordered.



## Altai Multitester & Transistor Tester

DC volts 0-1v-5v-2.5v-10v-50v-250v-1000v ±3%  
AC volts 0-10v-50v-250v-1000v ±3%  
DC current 0-50uA-2.5mA-25mA-0.25A ±3%

Resistance:  
Minimum 0-2.2-200-200k ohms } ±3%  
Midscale 20-200-20k-200k ohms }  
Maximum 2k-20k-2m-20m ohms }

As a transistor tester  
Leakage current 0-150uA at X1k range } ±5%  
0-15mA at X10 range }  
0-150mA at X1 range }

Price £14.95  
Order No. YN 360TR

## A superb stereo headphone

- Specifications:
- 1) sensitivity 110DB at 1,000Hz with 1mw
  - 2) Frequency response: 20-19,000Hz
  - 3) UNIT impedance 8 ohms
  - 4) matching impedance 4-16 ohms
  - 5) Maximum input 0.5 watts per channel
  - 6) Individual slide volume control (stereo/mono switch)
  - 7) 10 foot coiled cord with stereo phone plug
  - 8) Leathery-soft ear pads and head cushion

price £5.95.  
Order No. LE-76VS



Universal NI-CAD, battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.

Charges:- PP3 (9V), U12 (1.5V penlite), U11 (1.5V "C"), U2 (1.5V "D"). Power:- 220-240V AC. Dims:- 210 x 100 x 50mm. Knock down price only while stocks last. only £6.00

Order No. MW 398

## IDEX

stereo headphone  
Sensitivity 98dB at 1kHz with 1mw.  
Frequency response 20-25,000 Hz. Impedance 35 ohms. Maximum input 0.4 watts. 7ft cord with 3.5 stereo phone plug.

Price £7.50  
Order No. MHD-3



AS YOU HAVE SEEN FROM OUR PREVIOUS ADVERTISEMENTS, WE STOCK A VAST RANGE OF PRODUCTS—GIVE US A RING FOR YOUR NEEDS—WE STOCK EVERYTHING FOR THE ELECTRONICS ENTHUSIAST AT VERY COMPETITIVE PRICES.



208 Baker Street, Enfield, Middlesex.  
01-366 1873.



# EUROPA ELECTRONICS

Mail Order to: 160 High Road, Willesden Green, London NW10.

Tel: 01-459-2480

Retail Shop: North Parade Electronics, Mollison Way, Edgware, Middlesex.

Post & Packing: Add 50p to all orders under £5.  
VAT: All UK orders add 15% to total cost including p. & p.  
All devices are new, full spec and guaranteed.

## ELECTROLYTIC CAPACITORS (Axial & Radial) Values in uf.

63V: 1, 2, 2.3, 3, 4, 7, 6, 8, 10 6p; 15, 22, 33 8p;  
25V: 47, 100 8p; 220, 330 12p;  
16V: 470 14p; 1000 20p;  
10V: 1000 15p; 2200 25p.

## POLYESTER CAPACITORS (Radial Lead) 250V. Values in nf.

2n2, 3n3, 4n7, 6n8, 10n, 15n, 22n, 33n, 47n 8p; 68n, 100n 8p; 150n, 220n, 330n 10p;  
470n 15p; 680n 20p; 1000n 25p.

## POLYESTER CAPACITORS (Radial Lead) 100V Values in nf.

1n, 1n5, 2n2, 3n3, 4n7, 6n8, 10n 8p; 15n, 22n, 33n, 47n 8p.

## CERAMIC CAPACITORS 50V (Radial Lead).

22pf-47,000pf E12 Values 4p each.

## POTENTIOMETERS: Carbon track, 0.25W log & linear values.

5K-2M single gang 30p  
5K-2M single gang D/P switch 78p  
5K-2M dual gang stereo 88p

## PRESET POTENTIOMETERS Horizontal & Vertical.

0-1W 100R-1 Meg 7p  
0-25W 100R-1 Meg 10p

## RESISTORS 5% Carbon Film. E24 values.

0-25W 1R-5M 1p  
0-5W 1R-5M 1.5p

## SWITCHES

Slide 1A 14p  
DPDT 15p  
DPDT c/off 15p

## Sub-miniature Toggle

SPST on/off 54p  
SP c/over 60p  
DPDT 75p  
DPDT c/off 88p

## Push Button

Push to Make 15p  
Push to Break 25p

## VOLTAGE REGULATORS (PLASTIC)

5V 1A 7805 45p 7905 45p  
12V 1A 7812 40p 7912 45p  
15V 1A 7815 40p 7915 45p  
18V 1A 7818 40p 7918 45p  
24V 1A 7824 40p 7924 45p

## OPTO ELECTRONICS

2N5777 45p ORP60 120p  
OCPT71 180p ORP61 120p  
ORP12 120p TIL78 55p

## LEDS

3mm 5mm includ. clip  
Red 11p 12p  
Green 14p 14p  
Yellow 14p 14p

## 7 Segment Displays

TIL321 115p DL704 99p  
TIL322 115p DL707 99p

## DIODES

0A47 8p  
0A90 9p  
0A91 9p  
0A200 9p  
0A202 9p  
1N914 4p  
1N916 4p  
1N4148 4p  
1N4001 5p  
1N4004 6p  
1N4007 7p

## BRIDGE RECTIFIERS

1A 50V 19p  
1A 100V 20p  
1A 400V 25p  
2A 100V 30p  
2A 400V 45p

## ZENER DIODES

2-7-33V  
400mW 9p

## DIL SOCKETS

Low Profile  
8 pin 8p 20 pin 22p  
14 pin 10p 24 pin 25p  
16 pin 10p 40 pin 30p

## VEROBOARDS 0-1in

2 1/2 x 3 1/2" 3p clad plain 52p  
2 1/2 x 5" 83p  
3 1/2 x 3 1/2" 83p  
3 1/2 x 5" 79p  
3 1/2 x 1 1/2" 325p 211p  
4 1/2 x 1 1/2" 425p  
Pkt of 100 pins 50p  
Spot face cutter 118p  
Pin insertion tool 162p

## TRANSISTORS

AD161 42p  
AD162 42p  
BC107 10p  
BC108B 12p  
BC109 10p  
BC109C 12p  
BC177 16p  
BC178 16p  
BC179 20p  
BC182L 10p  
BC183L 10p  
BC184L 10p  
BC212L 10p  
BC213L 10p  
BC214L 10p  
BC547 12p  
BC548 12p  
BC549C 14p  
BC556 15p  
BC557 15p  
BC558 15p  
BC559 15p  
BFY51 23p  
BFY52 23p  
TIP29A 32p  
TIP30A 35p  
TIP31A 38p  
TIP32A 38p  
TIP33A 65p  
TIP34A 74p  
TIP41A 50p  
TIP42A 55p  
TSA43 32p  
2N2846 45p  
2N2904 28p  
2N2905 26p  
2N2906 26p  
2N2907 26p  
2N3053 28p  
2N3055 48p  
2N3702 10p  
2N3703 10p  
2N3704 10p  
2N3705 10p  
2N3706 10p  
2N3707 10p  
2N3708 10p  
2N3709 10p  
2N3819 22p  
2N3903 15p  
2N3904 15p  
2N3905 15p  
2N3906 15p  
2N5457 30p  
2N5458 30p  
2N5459 30p

## 4000 CMOS

4000 10p  
4001 10p  
4002 12p  
4010 24p  
4011 10p  
4012 16p  
4013 20p  
4015 40p  
4017 32p  
4018 45p  
4019 25p  
4023 13p  
4024 32p  
4030 15p  
4047 40p  
4068 14p  
4069 13p  
4070 13p  
4071 13p  
4072 13p  
4073 15p  
4075 13p  
4077 13p  
4078 15p  
4081 13p  
4082 13p  
4093 20p  
4095 95p  
4096 70p  
4501 28p  
4506 35p  
4507 35p  
4510 46p  
4512 42p  
4518 40p  
4520 70p

## LINEAR IC's

741 14p  
743 38p  
CA3140 40p  
LM301A 24p  
LM380 75p  
LM381N 145p  
LM382 125p  
NE555 16p  
NE556 45p  
NE565 120p  
NE567 155p  
NE568 155p  
TBA800 80p  
TBA810 95p  
TBA820 80p  
ZNA223 135p  
ZNA25E 350p

## TTL STANDARD

74 Series Series  
7400 11p 11p  
7401 11p 11p  
7402 11p 11p  
7403 12p 12p  
7404 12p 12p  
7408 14p 12p  
7409 15p 12p  
7410 14p 13p  
7411 20p 15p  
7412 20p 25p  
7413 20p 25p  
7414 20p 30p  
7420 16p 13p  
7427 22p 12p  
7428 25p 14p  
7430 15p 12p  
7447 35p 35p  
7448 40p 45p  
7450 16p 15p  
7474 20p 16p  
7475 25p 20p  
7476 30p 20p  
7485 60p 48p  
7490 25p 28p  
7491 35p 60p  
7492 25p 32p  
7493 25p 23p  
7494 35p  
7495 35p  
7598 40p 90p  
74107 22p 45p  
74121 27p  
74122 40p 36p  
74123 40p 38p  
74160 60p 40p  
74161 48p 40p  
74162 48p 40p  
74163 48p 40p  
74164 48p 45p  
74165 48p 60p  
74166 48p 52p  
74190 50p 36p  
74191 50p 36p  
74192 50p 36p  
74193 50p 36p  
74194 45p 36p  
74195 46p 36p  
74356 48p 60p  
74365 40p 32p  
74366 40p 32p  
74367 40p 32p  
74368 50p 50p  
74390 48p 46p  
74393 99p 42p  
74490 120p 200p

# Beginners' luck

**30% OFF**  
10 selected kits  
for first-time  
builders



Shortwave  
Listener's  
Receiver

With Heathkit, you're all set for a great deal. And not just big savings. Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need is there.



Digital Clock

Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud

of. Because you built it yourself. There are 10 great kits to start you off. An interesting choice of kits from a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

All at 30% off to first-timers. Send for your catalogue right now for a start.



Windspeed and Direction  
Indicator



Metal  
Locator

To Heath Electronics  
(UK) Limited, Dept ( EE 10 ),  
Bristol Road, Gloucester GL2 6EE

To start me off, please send me  
a copy of the new Heathkit catalogue.  
I enclose 28p in stamps. EE 10

Name \_\_\_\_\_  
Address \_\_\_\_\_



**HEATHKIT**  
You build on our experience

## Bradley Marshall Ltd OF EDGWARE ROAD

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS  
Tel: 723-4242

<b>PROBABLY THE LARGEST STOCK OF ICs &amp; TRANSISTORS IN THE SOUTH TRY US FIRST</b>	<b>SPECIAL OFFER</b> STEINAL MULTICHECK £7.50 + VAT Normal price £10.26	<b>BAHCO TOOLS SIDE CUTTERS</b> 2132 £7.10 2112 £9.40 <b>END CUTTERS</b> 2211 £10.43 <b>PLIERS</b> 2411 £6.75 2415 £6.78
	<b>LARGE RANGE OF ACCESSORIES</b> Plugs Sockets Audio Connectors Veroboards IC Sockets Soldering equipment Screw drivers (BAHCO) Sifam Knobs etc.	<b>BUY WITH ACCESS BARCLAYCARD A/EXPRESS DINERS</b> Just phone we do the rest
<b>LARGE RANGE OF ICs</b> Transistors Capacitors Diodes Triacs Thyristors Opto Resistors Potentiometers Fuses Bridges Please send S.A.E. for list.	<b>MAIL ORDER FASTER SERVICE PHONE 723-4242</b>	<b>EXPERIMENTER BREADBOARD'S</b> EXP 325 EXP 600 EXP 350 EXP 650 EXP 300 EXP 4B
	16, 24, 40 WAY RIBBON CABLE £1.10; £1.40; £2.20 metre Header plugs 14 way, 16 way, 24 way, 40 way	<b>LOGIC PROBES</b> LP1 £31.00 LP2 £18.00
<b>PLEASE REMEMBER To ADD 15% VAT</b>		

### BRADLEY MARSHALL LTD FOR

## Crimson Elektrik PROFESSIONAL AMPLIFIER MODULES

PRICE LIST —  
ELECTRONIC MODULES & ASSEMBLIES

CODE	DESCRIPTION	Less	VAT	INC	WT
		VAT	£	VAT	(Kg)
CE 608	Power Amplifier Module	18.26	2.74	21.00	0.16
CE 1004	Power Amplifier Module	21.30	3.20	24.50	0.20
CE 1008	Power Amplifier Module	23.90	3.60	27.50	0.21
CE 1704	Power Amplifier Module	30.43	4.57	35.00	0.22
CE 1708	Power Amplifier Module	30.43	4.57	35.00	0.22
CE 3004	Power Amplifier Module	42.60	6.40	49.00	0.40
BD 1	Bridge Driver Module	7.13	1.07	8.20	0.06
TR 80	Toroidal Transformer 80VA	18.00	2.70	20.70	2.00
TR 150	Toroidal Transformer 150VA	20.07	3.01	23.08	2.35
TR 250	Toroidal Transformer 250VA	25.43	3.81	29.24	3.35
TR 250Q	Toroidal Transformer (low noise)	33.20	4.98	38.18	2.80
B 6	Bridge Rectifier (6 amp)	0.99	0.15	1.14	0.02
B12	Bridge Rectifier (12 amp)	1.80	0.27	2.07	0.03
C4700/40	Reservoir Capacitor and Clip	1.91	0.29	2.20	0.09
C4700/63	Reservoir Capacitor and Clip	2.40	0.36	2.76	0.11
C4300/63	Reservoir Capacitor and Clip	2.60	0.39	2.99	0.11
CPS 80	Power Supply	22.82	3.42	26.24	2.10
CPS 80D	Dual Power Supply	27.63	4.14	31.77	2.25
CPS 150	Power Supply	25.86	3.88	29.74	2.50
CPS 150D	Dual Power Supply	31.65	4.75	36.40	2.60
CPS 250	Power Supply	32.03	4.80	36.83	3.50
CPS 250D	Dual Power Supply	39.43	5.91	45.34	3.65
TS 70	Thermal Switch 70°C	1.92	0.29	2.21	0.02
HS 50	50mm Heatsink	1.60	0.24	1.84	0.15
HS 100	100mm Heatsink	2.60	0.39	2.99	0.30
HS 150	150mm Heatsink	3.65	0.55	4.20	0.45
FM 1	Fan Mounted on 2 x HS 100	32.13	4.82	36.95	1.20
FM 2	Fan Mounted on 2 x HS 150	36.10	5.42	41.52	1.50
CPR 1X	Pre-Amplifier Module	31.30	4.70	36.00	0.15
MC 2	Moving Coil Pre-Pre-Amplifier Module	20.00	3.00	23.00	0.07
REG 1	Regulated Power Supply	8.09	1.21	9.30	0.07
TR 6	6VA Mains Transformer	2.87	0.43	3.30	0.21
XO 2	2 Way Crossover Module	17.39	2.61	20.00	0.07
XO 3	3 Way Crossover Module	26.09	3.91	30.00	0.07
MU 1	Muting Circuit for XO 2 or XO 3	8.35	1.25	9.60	0.04
CK 1010	Complete Pre-Amplifier Kit	78.26	11.74	90.00	2.50
CK 1040	Complete 40 Watt Power Amplifier Kit	103.48	15.52	119.00	7.30
CK 1100	Complete 100 Watt Power Amplifier Kit	129.56	19.44	149.00	7.30
MC 2K	Add On Moving Coil Kit	21.74	3.26	25.00	0.12
PSK	Pre-Amplifier Power Supply Kit	17.39	2.61	20.00	0.75

SOLE DISTRIBUTION BRADLEY MARSHALL LTD OF EDGWARE RD  
325 EDGWARE RD, LONDON W21 BN  
TEL: 01-723 4242



# Everyday ELECTRONICS

VOL. 11 NO. 10 OCTOBER 1982

**Editor**  
F. E. BENNETT

**Assistant Editor**  
B. W. TERRELL B.Sc.

**Production and News Editor**  
D. G. BARRINGTON

**Projects Editor**  
G. P. HODGSON

**Art Editor**  
R. F. PALMER

**Assistant Art Editor**  
P. A. LOATES

**Technical Illustrator**  
D. J. GOODING Tech. (CEI)

**Secretary**  
JACQUELINE DOIDGE

**Editorial Offices**  
KINGS REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS  
Phone: 01-261 6873

**Advertisement Manager**  
R. SMITH  
Phone: 01-261 6671

**Representative**  
R. WILLETT  
Phone: 01-261 6865

**Classified Supervisor**  
B. BLAKE  
Phone: 01-261 5897

**Make-Up and Copy Department**  
Phone: 01-261 6615

**Advertisement Offices**  
KINGS REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS

## WIDE CHOICE

**E**LECTRONICS appeals to all sorts of people, and it follows that constructors interests and needs vary, as does depth of knowledge and practical experience. Yet electronics offers something to all, for the possible applications are vast, and the level of technology employed can range from simple one- or two-transistor circuits, to involved systems based on microchips.

For examples it is necessary only to turn the following pages. The *General Purpose Pre-Amplifier* and the *Sine Wave Generator* come into the first category; what is more, the two transistors required in either design will be found mounted on the front cover of this month's issue. Higher technology is represented by the *Computer Expansion System*, winner of the Schools Electronics Design Award Competition; and the *Optical Tachometer*, which breaks new ground as an instrument for use with rotating mechanisms.

A useful car gadget and a simple short wave radio complete this month's complement of projects and underline the wide scope of home constructed electronics.

## COME TO THE FAIR

Have a day out with the family at the first Electronics Hobby Fair. Alexandra Pavilion in north London is the venue for this new style exhibition sponsored by EVERYDAY ELECTRONICS and our associate journals *Practical Electronics* and *Practical Wireless*. The dates to remember are November 18-21.

Names long familiar to readers of our advertisements pages will materialise there as exhibitors; visitors will have the opportunity to browse around their stands, purchase their wares or just chat up the proprietors of businesses that year in and year out satisfy the needs of constructors and experimenters. The staff of EE, PE and PW will be in attendance and look forward to meeting their readers.

Other major attractions are laid on. The new Alexandra Pavilion—already dubbed “a palace of light”—will be an appropriate setting for this most enlightening of shows with its happy gathering of electronics enthusiasts, their families and friends, together with traders, professional organisations—in fact all who share some interest, be it great or small, in this exciting, ever expanding field of technology. Further details appear on page 657. Be seeing you.



## Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

## Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

## Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

## Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.

## Subscriptions

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £13.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, Kings Reach Tower, Stamford Street, London SE1 9LS.



BY R. A. PENFOLD

# SINE WAVE GENERATOR

\*A GOOD USE FOR YOUR FREE TRANSISTORS

THIS simple but extremely useful piece of test equipment gives a sinewave output of reasonable purity over an approximate frequency span of 15Hz to 1.5 MHz. It is ideal for applications such as frequency response and voltage gain measurement of audio circuits, and it can also be used in the alignment and testing of medium and longwave radios as the higher frequency ranges of the unit extend well into the radio frequency spectrum.

The five frequency ranges of the Sinewave Generator are nominally as follows:

- Range 1 15Hz to 150Hz
- Range 2 150Hz to 1.5kHz
- Range 3 1.5kHz to 15kHz
- Range 4 15kHz to 150kHz
- Range 5 150kHz to 1.5MHz

The maximum output amplitude is approximately 1 volt r.m.s., and this can be continuously varied down to zero by means of two attenuator controls. The output level is accurately stabilised and there is no significant variation in the output level over the frequency range of the unit. This is really a simple form measurement since it is not necessary repeatedly to check that the output level of the unit is still correct when making measurements at various frequencies.

## THE WIEN NETWORK

In common with most good quality sinewave generators, this one is based on a Wien network, and Fig. 1 shows

the arrangement used in this type of circuit. This is really as simple form of C-R bandpass filter which gives losses that are at a minimum at a frequency which can be calculated using the following formula:

$$f = \frac{1}{2RC}$$

This assumes that R1 and R2 are of equal value, and that C1 and C2 are also of the same value (which is invariably the case for practical designs). At this frequency of peak response there is zero phase shift through the network.

In order to use a Wien network in an oscillator it is merely necessary to use the network to provide positive feedback over an amplifier; but the

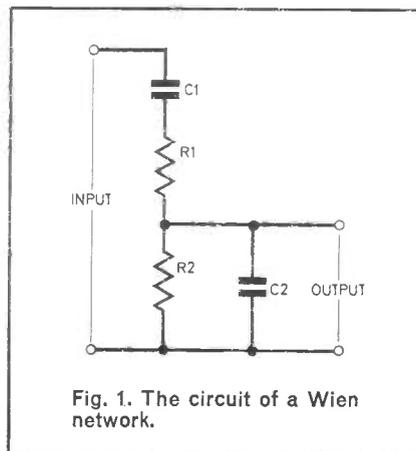


Fig. 1. The circuit of a Wien network.

losses through the network must be counteracted by the gain of the amplifier to a high degree of accuracy if a good quality sinewave output is to be obtained.

## NEED FOR AUTOMATIC GAIN CONTROL

Too much gain results in the circuit oscillating too strongly and the output becoming clipped and badly distorted. This results in strong harmonics (multiples of the fundamental frequency) on the output signal, which would give inaccurate results when using the generator for frequency response measurements.

Inadequate gain results in a failure of the circuit to oscillate.

In practice it is necessary to have some form of automatic gain control circuit which maintains the gain of the amplifier at just the right level, and compensates for factors such as changes in supply voltage and variations in loading of the output when necessary.

## CIRCUIT DIAGRAM

The circuit diagram of the sinewave generator is shown in Fig. 2, and the amplifier used in the unit is a simple two-transistor complementary type. This gives a reasonably high input impedance so that there is negligible loading on the Wien network, and a fairly low output impedance so that the output level is not affected significantly with normal loading of the output. The input is to the base of TR1 and the output is taken from the collector of TR2 via d.c. blocking capacitor C14.

## SWITCHED CAPACITORS

The Wien network has two sets of five switched capacitors (C3 to C7 and C9 to C13), and these give the unit its five ranges. C3 has been given a value of only 82pF rather than the expected value of 100pF due to the input capacitance of the amplifier which effectively boosts the value of C3 to approximately the required capacitance of 100pF. This input capacitance is not high enough to have any significant effect on the other four ranges.

The two resistances in the Wien network are formed by R3 plus VR1a in series, and R7 plus VR1b in series. VR1 enables the oscillator to be tuned over the ranges quoted earlier. R1, R2, and C2 are used to bias the amplifier through part of the Wien network.

## THERMISTOR STABILISING

Thermistor RTH1 is used to stabilise the gain of the amplifier at the correct level, and the R53 (or RA53) type thermistor used here is a special device which is contained in a vacuum in a glass encapsulation. This largely isolates it from the ambient

temperature, and it instead responds to the current flowing through the component and the consequent heat produced.

At switch-on RTH1 will be at a relatively low temperature and will therefore have a fairly high resistance. RTH1 is connected so that it provides negative feedback from the output of the amplifier to the emitter of TR1, and with a high resistance through RTH1 there is little feedback and the amplifier has a high voltage gain. This results in strong oscillation.

The strong output signal results in a large current flow through RTH1, causing it to heat up and its resistance to fall. The gain of the circuit thus falls and gentle oscillation is produced.

### RISE OR FALL IN OUTPUT


If the output signal level should fall for some reason, the current flow through RTH1 will decline and its temperature will reduce. This gives a rise in resistance, more voltage gain through the amplifier, and stronger oscillation which increases the output signal back to virtually its original level.

An increase in output has the opposite effect with RTH1 passing a stronger current so that its resistance decreases, the voltage gain of the amplifier is reduced, and the output signal is returned to almost its original level.

This method of stabilisation is very simple and only uses a single component, but it is very efficient and the output signal level is well stabilised.
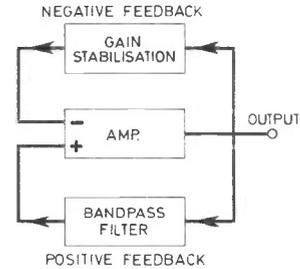
## HOW IT WORKS

The circuit is based on an amplifier which is made to oscillate by the application of frequency selective positive feedback, and the circuit oscillates at the frequency at which the most feedback is provided. This frequency can be varied over wide limits and the output frequency can be varied from sub-audio to high frequencies well into the radio frequency spectrum.



In order to obtain a reasonably pure sinewave output, or an output signal which contains just one frequency in other words, it is necessary to have the voltage gain of the amplifier at precisely the right level. This is achieved using a circuit that automatically sets the gain of the amplifier at the right level by applying a controlled amount of negative feedback over the amplifier.

### OUTPUT ATTENUATOR

VR2 is a volume control type output attenuator which enables the output signal level to be set at any desired level between zero and the maximum output level of about 1 volt r.m.s.


Adjusting the output level using VR2 can be rather awkward when very low signal levels are required, and an additional (final) attenuator which consists of R10 and R11 can be switched into circuit to reduce the output by about 40dB (by a factor of 100). VR2 then gives an output signal which can be varied from zero to about 10mV r.m.s, and output

levels of under a millivolt can then be accurately and easily set.



Power is obtained from an ordinary PP3 size 9 volt battery, and the current drain of around 10mA gives a reasonable battery life.

**COMPONENTS**  
 approximate  
 cost **£15.00**

Fig. 2. Circuit diagram of the Sine Wave Generator.

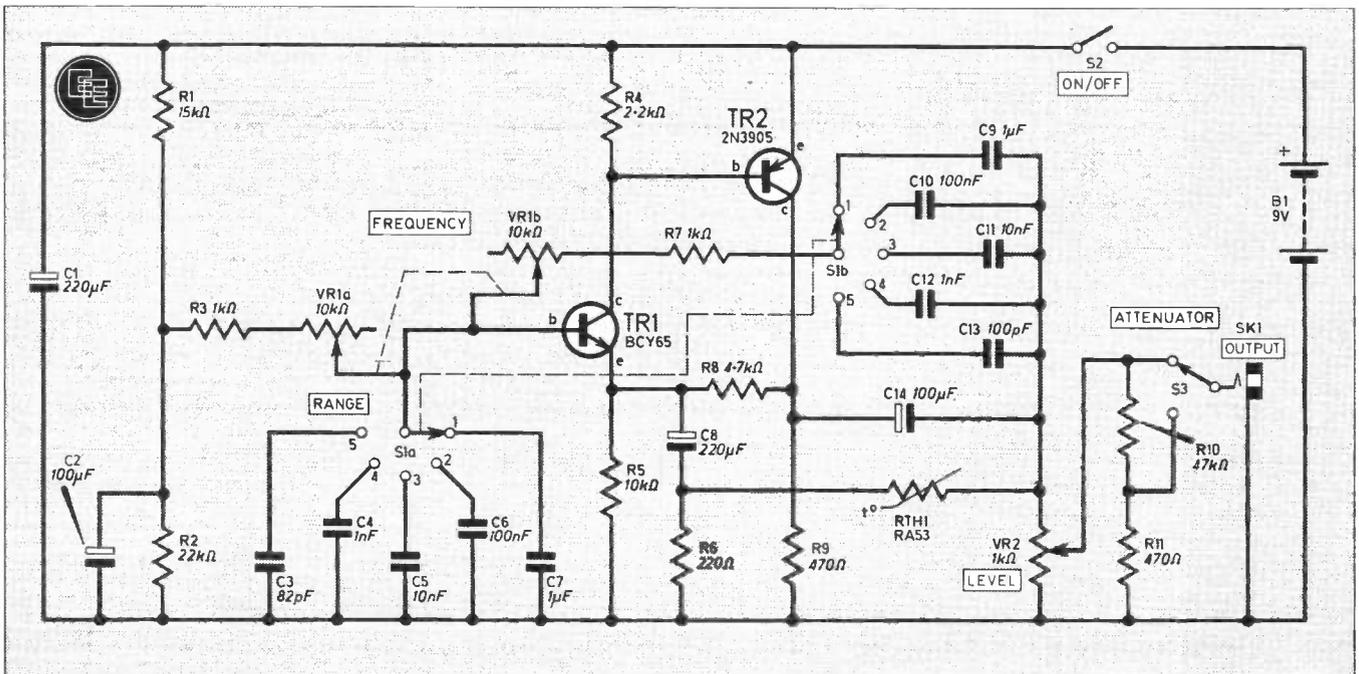

# SINE WAVE GENERATOR

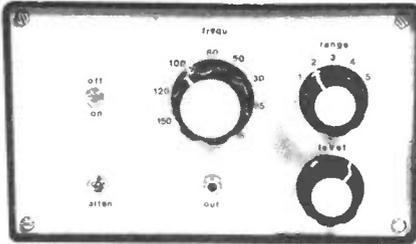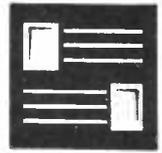

## COMPONENTS

### Resistors

R1	15k $\Omega$
R2	22k $\Omega$
R3, 7	1k $\Omega$ (2 off)
R4	2.2k $\Omega$
R5	10k $\Omega$
R6	220 $\Omega$
R8	4.7k $\Omega$
R9	470 $\Omega$
R10	47k $\Omega$
R11	470 $\Omega$
All $\frac{1}{4}$ W 5% carbon	

See  
**Shop  
Talk**

page 635

### Potentiometers

VR1	10k $\Omega$ logarithmic dual-gang carbon
VR2	1k $\Omega$ linear carbon

### Capacitors

C1, 8	220 $\mu$ F 10V elect (2 off)
C2, 14	100 $\mu$ F 10V elect (2 off)
C3	82pF polystyrene
C4, 12	1nF polycarbonate (2 off)
C5, 11	10nF polycarbonate (2 off)
C6, 10	100nF polycarbonate (2 off)
C7, 9	1 $\mu$ F polycarbonate (2 off)
C13	100pF polystyrene

### Semiconductors

TR1	BCY65EP npn silicon
TR2	2N3905 pnp silicon

### Switches

S1	6-way 2-pole rotary with adjustable end stop
S2	s.p.s.t. miniature toggle
S3	s.p.d.t. miniature toggle

### Miscellaneous

B1	9 volt PP3 size
RTH1	thermistor, n.t.c. (RS type RA53 or R53)
SK1	3.5mm jack
Sloping front case (Maplin type M1005); 0.1 inch matrix strip-board 36 holes by 14 strips; battery connector; control knobs; Veropins; connecting wire; 6BA fixings; solder.	



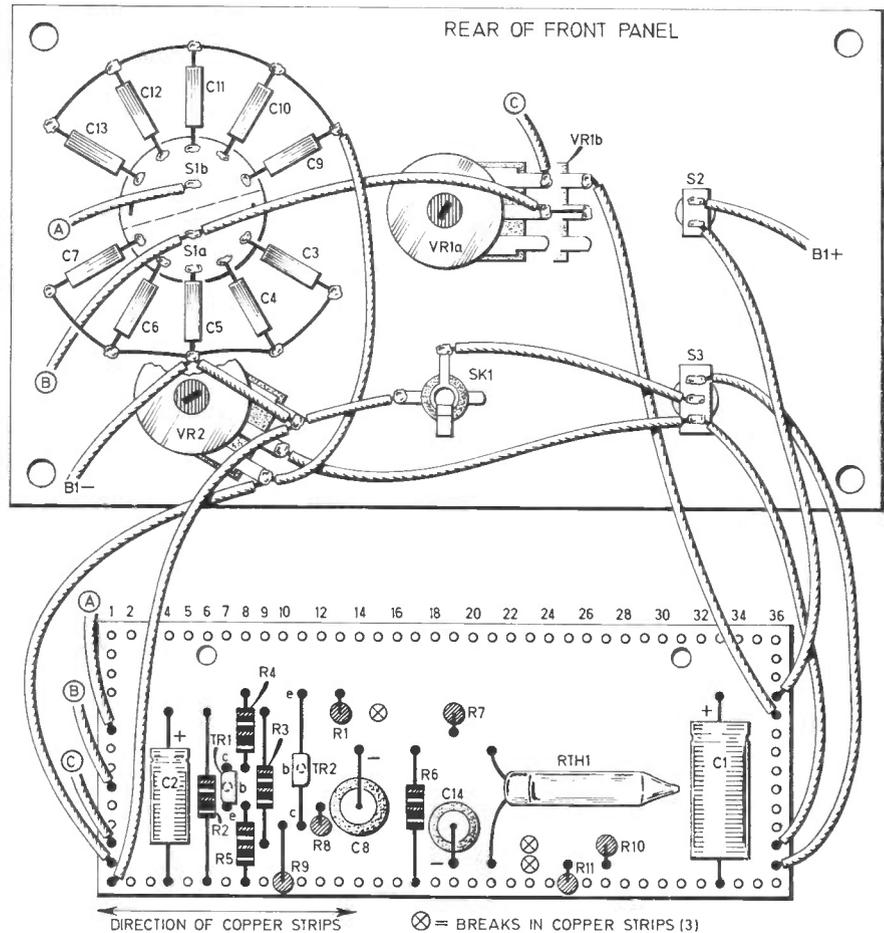


Fig. 3. The completed assembly, showing the front panel components and their interconnections to the circuit board. Note the breaks required in the copper strips as indicated on the top view of the circuit board.

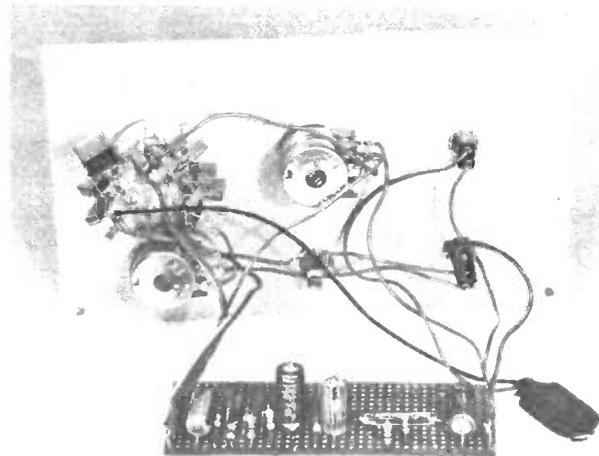The circuit board and (right) the complete assembly.



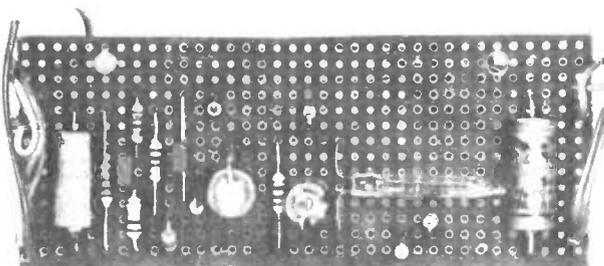

## CONSTRUCTION

A sloping front case measuring about 161×96×61mm is used for this project, although any case of about this size should be perfectly acceptable. The front panel layout used for the prototype can be seen from the photographs, and the unit will be easy to wire up and use if this general arrangement is copied.

The component panel is a 0.1 inch matrix stripboard having 36 holes 14 copper strips, and details of this are provided in Fig. 3. Construction of the board follows the normal pattern with a board of the specified size first being cut out using a hacksaw, the breaks in the copper strips and the two mountings then being made, after which the components are soldered into place and Veropins are fitted at points where connections to the off-board components will be made. The completed board is mounted on the base panel of the case, to the rear of the unit and on the left hand side.

This still leaves a substantial amount of wiring, to the off-board components, all of which is illustrated in Fig. 3.

## OFF-BOARD COMPONENTS

C3 to C7 and C9 to C13 are mounted direct on S1, and these need to be physically small components if they are to fit comfortably into the available space. They also need to have a tolerance of 5 per cent or less, and

this leaves little choice to polycarbonate capacitors for the higher value capacitors.

These kind of capacitors are really intended for printed circuit mounting, but they will fit readily onto the tags of S1 provided you do not bend the leadout wires (which could easily result in them becoming detached).

The other wiring is quite straight forward and is completed using multi-strand p.v.c. insulated connecting wire.

## CALIBRATION

To be of most use the unit should have a scale calibrated in terms of output frequency marked around the control knob of VR1. In order to give reasonably linear scaling VR1 is a logarithmic potentiometer used in reverse (i.e., clockwise adjustment of VR1 gives a reduction in output frequency).

The easiest way of calibrating the unit is to use a frequency meter of some kind to aid the location of the various calibration points. Note that it is only necessary to calibrate the unit on one range since switching from one range to the next increases the output frequency by a factor of ten.

Thus, for example, the point on the scale that corresponds to 100Hz on range 1 obviously corresponds to 1kHz on range 2, 10kHz on range 3, 100kHz on range 4, and 1MHz on range 5.

If access to a frequency meter is not possible an alternative method is to use another (ready calibrated) signal generator to provide tones of known frequency, with the outputs of the two signal generators being monitored using crystal earphones, high impedance headphones, or amplifiers and loudspeakers so that the generators can be tuned by ear to the same frequency.

Another method is to use an oscilloscope to measure the output frequency, and although this is not likely to be quite as accurate as using a frequency meter or accurately calibrated signal generator to calibrate the unit.

## MUSICAL INSTRUMENTS AND AURAL TUNING

If no suitable test equipment for calibration purposes is available another method is to use a musical instrument to provide tones of known frequency. The output of the signal generator must be monitored using a crystal earpiece, headphones, or amplifier and loudspeaker, so that it can be tuned by ear to the same frequency as the reference note from the musical instrument.

The 'A' above middle C is at a frequency of 440Hz and this frequency doubles for each octave increase in pitch, and halves for each octave decrease in pitch. The 'B' below middle C is at approximately 250Hz (actually 246.94Hz), the 'G' below middle C at about 200Hz (196Hz to be exact), and the F below middle C is at approximately 175Hz (174.61 is the precise figure). Again, octaves above and below these notes can be used to provide further calibration points on the scale.

## SETTLING DOWN PERIOD


One final point to note is that the thermistor gain stabilisation circuit does not respond very rapidly to changes in loading, adjustments to the frequency controls, and so on.

After such changes, it therefore usually takes a second or two for the unit to settle down and give a good quality output of the correct amplitude, and the resultant momentary losses of output signal or signal purity are normal for this type of equipment and are not indicative of a fault.


## \* FREE TRANSISTORS \*
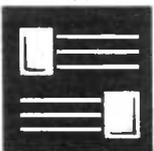
### PARAMETERS AND OUTLINES

The 2N3905 and BCY65EP may be used to replace the transistor types listed in the table, but not all of these devices may be used as replacements for the 2N3905 and BCY65EP. You are advised to check with the relevant data sheet for circuits operating at high voltages.




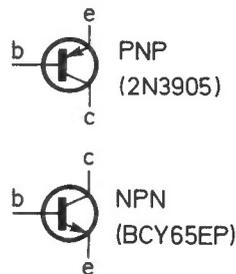E-LINE PACKAGE WITH TO-92 LEAD CONFIGURATION.



CIRCUIT SYMBOLS

Parameter	2N3905	BCY65EP
Application	General purpose	Low noise amplifier
Construction	PNP Silicon	NPN Silicon
Case	E-Line (TO-92)	E-Line (TO-92)
$V_{CB}$	-40V	60V
$V_{CE}$	-40V	60V
$V_{EB}$	-5V	7V
$I_C$	-200mA	100mA
$P_{TOT}$	500mW @ 25°C amb 1.2W @ 25°C case	400mW @ 25°C amb 1W @ 45°C case
$h_{FE}$	50 to 150 $I_C = -10mA$ $V_{CE} = -1V$	180 to 310 (250 typ.) $I_C = 2mA$ $V_{CE} = 5V$
$h_{fe}$ @ 1kHz	50 to 200 $I_C = -1mA$ $V_{CE} = -10V$	175 to 350 (260 typ.) $I_C = 2mA$ $V_{CE} = 5V$
$f_T$ (min)	200MHz	125MHz
Suitable replacements for:	BC159, BC212, BC214, BC388, BC478, BC479, BC558, BFX85, 2N3702, 2N3906.	BC107, BC108, BC109, BC147, BC148, BC149, BFX95, ZTX107, ZTX108, ZTX109, 2N2926, 2N3702.

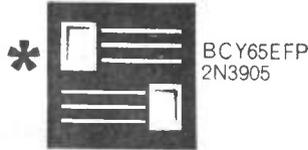

# GENERAL PURPOSE PRE-AMPLIFIER

BY R.A. PENFOLD

\* A SIMPLE PROJECT FOR YOUR FREE TRANSISTORS

ALTHOUGH there are a great many electrical and electronic standards there is no standard output level for items of audio equipment and musical instruments. Likewise there is no standard sensitivity for audio amplifiers of various types. This can lead to problems of incompatibility, however, with so many different types of signal source commonly available a single output level and input sensitivity for all types of audio frequency equipment is probably not practical.

Where an item of gear has an excessive output level for the equipment with which it is to be used there may well be no problem if the two units are coupled direct to one another, and a simple attenuator is all that is required if overloading should become evident. A more common problem is that of having a low level signal from (say) a microphone which is inadequate to drive the input of an amplifier.

In such cases the cure is to use a suitable preamplifier, and in most cases the versatile preamplifier described in this article should be capable of giving proper matching between the two items of equipment concerned.

## SWITCHED GAIN LEVELS

The circuit provides three switched levels of voltage gain and these are approximately 26dB (20 times), 40dB

(100 times), and 56dB (500 times). The input impedance of the unit is about 10 kilohms and the output impedance is reasonably low.

When used at the low gain setting the preamplifier is suitable for applications such as matching a low out-

put electric guitar to an insensitive power amplifier, and in the higher gain settings it is able to boost low level signals such as those from a microphone to a high enough level to drive power amplifiers and musical effects units.

The signal to noise ratio of the unit is very good with an output noise level (input short circuited) of only about 400 microvolts on the highest gain setting, and less than this on the other gain settings. In most applications this will result in an unweighted signal-to-noise ratio of 60dB or better.

## THE CIRCUIT


Fig. 1 shows the circuit diagram of the preamplifier, and a two-stage direct-coupled configuration is used.

The base of TR1 is biased to about half the supply potential by R1 and R2, and this gives a potential of a little under 4 volts at the emitter of TR1 due to the voltage drop of about 0.6 volts or so from the base to the emitter.

The collector and emitter currents of TR1 are virtually identical, and the voltage across R3 is therefore a little more than half that developed across R4 since it is a little more than half the value of R4. This results in TR1 being biased to give a collector potential of about 7 volts, and permits an unclipped voltage swing of approximately 4 volts peak-to-peak at the output of this stage. This is more than adequate for the input stage of a preamplifier.

TR1 is a low noise device and is operated at a collector current of only about 200µA in order to give the circuit a good signal-to-noise ratio.

Fig. 1. The circuit diagram of the General Purpose Pre-Amplifier.

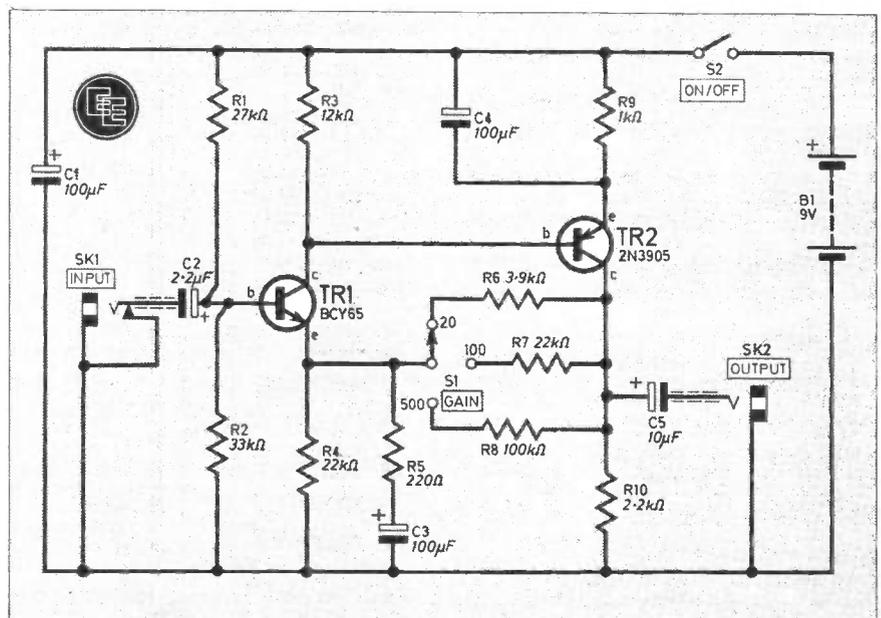

## SECOND STAGE

TR2 is used in a similar configuration to TR1, but this is a *npn* type instead of an *npn* device, and it is biased from the output of TR1.


Due to the voltage drop from the base of TR2 to its emitter there is about 1.5 volts across R9, and thus about 3.3 volts across R10. This gives a maximum unclipped output voltage swing of approximately 6.6 volts which should be perfectly adequate, and is obviously approaching the maximum that can be attained using a 9 volt battery supply.

TR2 is run at a higher current than TR1 (about 1.5mA) in order to help give the circuit a fairly low output impedance.

R4 and R9 introduce a great deal of negative feedback and give the circuit a voltage gain of only about unity. This aids accurate biasing of the circuit, but it is necessary to decouple some of this feedback at audio frequencies in order to give the circuit a useful level of voltage gain at these frequencies. R5 and C3 remove most of the audio frequency feedback from TR1, and C4 eliminates the audio feedback over TR2.

This gives the circuit a high voltage gain of typically over 60dB (1,000 times), and this is too high for the majority of applications. The voltage gain of the circuit is reduced to the required level by using a resistor to couple negative feedback from the


## HOW IT WORKS

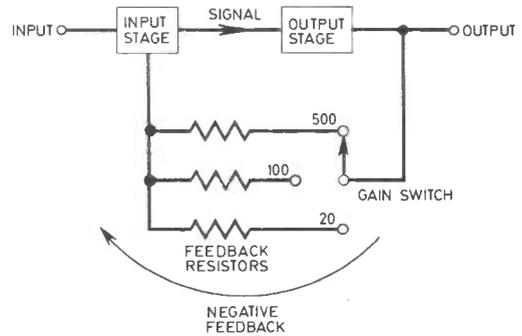

The circuit has two stages of amplification; a low noise input stage and an output stage that enables the unit to provide sufficient output voltage and current to drive most amplifiers, mixers, etc.

Both stages give a fairly high level of voltage gain, and the total gain of the amplifier is more than a thousand. This is higher than would normally be required, and the gain is reduced to the required level by coupling some of the output signal back to the input stage so that it has a cancelling effect on the input signal.

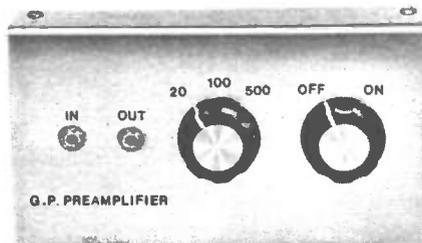This is known as "negative feedback" and in addition to reducing the voltage gain of the circuit it also has the beneficial effects of reducing noise and distortion to a similar degree. There are three switched levels of feedback so that three levels of voltage gain are available from the preamplifier.



collector of TR2 to the emitter of TR1

### VOLTAGE GAIN CONTROL

The voltage gain of the circuit is approximately equal to the value of this feedback resistor divided by R5, plus one. Three feedback resistors are used with the required resistor being selected using S1. This gives the circuit its three levels of voltage gain, and the values of R6 to R8 have been chosen to give the approximate voltage gains specified earlier.

A break contact on input socket SK1 is used to short circuit the input of the amplifier when no input is connected to the unit. This minimises any noise at the output of the unit and eliminates the slight risk of instability when no signal source is connected to the unit.

The current consumption of the circuit is less than 2mA and a PP3 size 9 volt battery is an adequate power source for the preamplifier.



### METAL CASE

In order to minimise problems with stray pick-up it is recommended that a metal case is used for this project, and an inexpensive aluminium type measuring 133×70×39mm is ideal. The two controls and two sockets are mounted on the front panel, and apart from the battery and the three feedback resistors the components are all fitted on a 0.1 inch matrix stripboard having 24 holes by 14 strips.

### CIRCUIT BOARD

Details of the component panel and all the other wiring are shown in Fig. 2. A stripboard of the specified size is not available and it is necessary to cut the board down to size using a hacksaw. There are just two breaks in the copper strips and a single link wire. Fit Veropins to the board at the points where connections to off-board components such as S1 and S2 will be made.

## COMPONENTS

### Components

R1	27kΩ
R2	33kΩ
R3	12kΩ
R4, 7	22kΩ (2 off)
R5	220Ω
R6	3.9kΩ
R8	100kΩ
R9	1kΩ
R10	2.2kΩ
All 1/4W 5% carbon	

See  
**Shop  
Talk**

page 635

### Capacitors

C1,3,4	100μF 10V elect (3 off)
C2	2.2μF 63V elect.
C5	10μF 25V elect.



### Semiconductors

TR1	BCY65EP <i>npn</i> silicon
TR2	2N3905 <i>npn</i> silicon

### Miscellaneous


SK1,2	3.5mm jacks (2 off)
S1	3 way 4 pole rotary switch
S2	rotary on/off type switch
B1	9 volt PP3 type
Metal case; control knobs; battery connector; 0.1 inch stripboard 14 strips by 24 holes; 6BA fixings; wire; etc.	

Approx. cost  
Guidance only **£4.00**

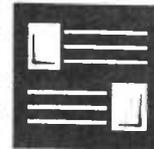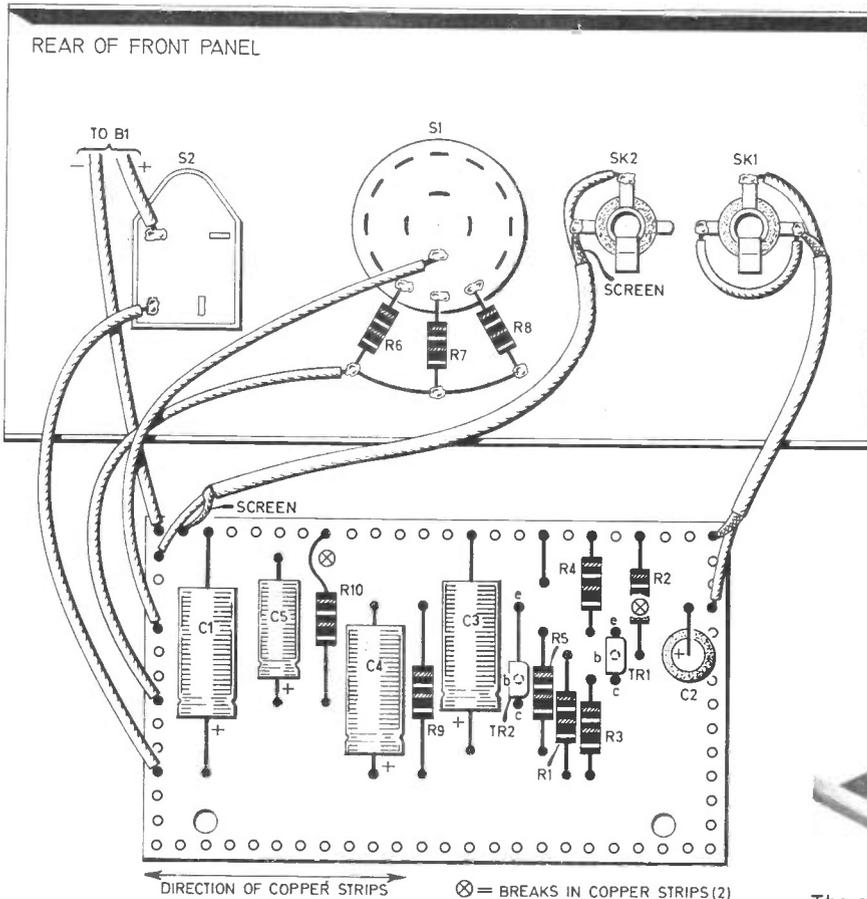



## GENERAL PURPOSE PRE-AMPLIFIER

Fig. 2. Circuit board component layout and interwiring to the front panel components.

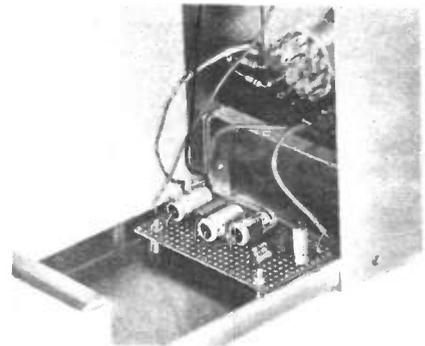

The circuit board mounted in position on spacers.

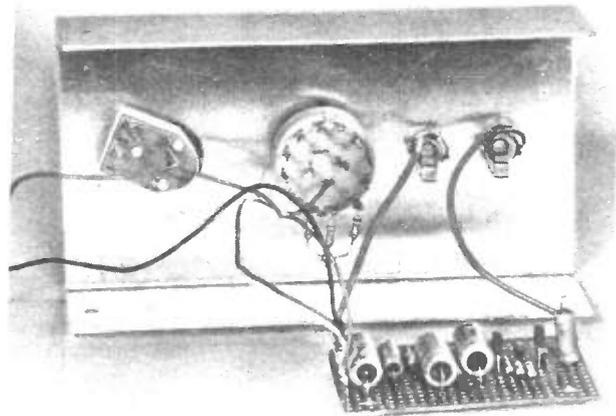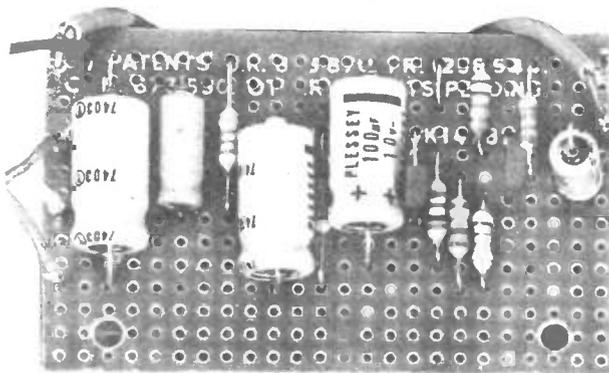Layout of components on the circuit board and (right) wiring to the front panel.



Once the board has been finished and thoroughly checked it can be mounted on the rear panel of the case using 6BA fixings. Use 6.35mm spacers over the mounting screws to ensure that the soldered joints on the underside of the board are kept well clear of the metal case.

### CRITICAL POINTS


Next the three feedback resistors are fitted onto S1 and the other wiring is added to complete the unit.

It is advisable to use screened leads for the connections from the component panel to SK1 and SK2 since the input and output of the amplifier are in-phase, and any stray feedback between the two is likely to result in instability.

For the same reason the component layout of the preamplifier is quite critical and it is not advisable to alter this in any way unless you are sure of what you are doing.
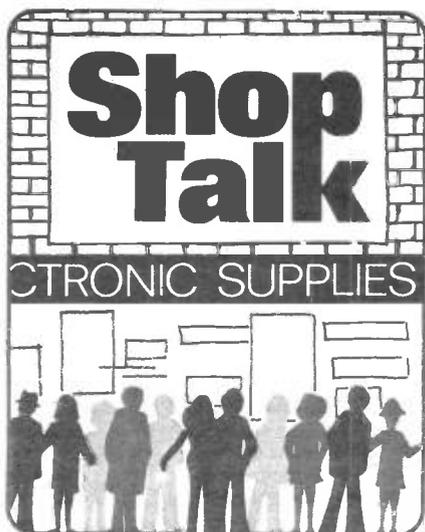
### USING THE PREAMPLIFIER

In use the preamplifier should be used on the lowest gain setting that gives satisfactory results as this minimises the risk of overloading and also gives the lowest levels of noise and distortion. The unit is not really suitable for use with high impedance signal sources such as crystal microphones, but as these are not in common use these days this is not really a major drawback. □




By Dave Barrington
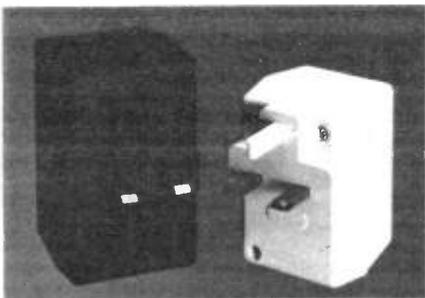
### Case For Power

We have, over the past few months, published designs which have included separate circuits for a.c. mains to low voltage d.c. supplies. Even this month's article for a *Optical Tachometer* contains one such circuit.

West Hyde Developments are now marketing a range of cases specifically designed to house power supplies for low voltage equipment such as calculators, radios and games.



The case, available in two sizes, will accommodate the components of a power supply, including the transformer. It features a plastics earth pin and brass live and neutral pins to allow the unit to be plugged directly into a 13A mains socket. Safety, it is claimed, is assured with the inclusion of a special internal moulding which, as well as retaining the earth pin, separates the mains input from the low voltage output circuitry and transformer.

Stockists and prices can be obtained from West Hyde Developments Ltd., Dep EE, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET.

### On The Move

We have just been informed that components supplier T. Powell has just moved premises to a more central London location.

They are now trading from 311 Edgware Road, London, W2.

## CONSTRUCTIONAL PROJECTS

### General Purpose Preamplifier

All components for the *General Purpose Preamplifier* should be readily available from most component suppliers. This project has been specially designed around the transistors given Free with this issue.

The on/off switch S2 used in the prototype was a mains rotary type and is listed by Rapid Electronics. This switch could be a common on/off toggle type.

### Sinewave Generator

The *Sinewave Generator* is another project that has been specially designed around the transistors given Free with this issue.

The 6-way 2-pole rotary switch, with adjustable end-stop, is available from Watford Electronics. The sloping-front case called up in the components list is a Maplin M1005 type, although any plastics case with a metal front panel of similar dimensions can be used.

The thermistor used in this project is the RA53 from RS Components. Any *bona-fide* RS components supplier will be able to obtain this item and should be ordered as stock number 151-114.

This device is also stocked and listed as a R53 thermistor by some suppliers.

### Simple Shortwave Radio

Except for the coils used in the *Simple Shortwave Radio* the rest of the components for this project should not cause any undue purchasing problems.

The coil used in the receiver is an old Wearite type which is no longer produced. However, we understand that T. Powell is producing a complete kit of parts, including coil, for this project.

### Optical Tachometer

We do not expect any component buying problems for the *Optical Tachometer* project.

The most expensive item in this project is the sloping-front case. Once again, any case with similar or larger dimensions may be used.

### ZX81 Expansion System

Several of the components listed in the *ZX81 Expansion System* are "specials" and are not "off-the-shelf" items.

The 37-way single-sided edge connectors will have to be cut from a larger version. This and the double sided 23-way wirewrap edge connector are available from Watford Electronics.

The designers used a 23 + 23 wirewrap connector, for pin lead length, and bent the pins to the required right-angle. Readers should enquire before purchase that it is possible to bend the pins, it has been found that on some types they may snap off.

The monolithic ceramic capacitors used for the decoupling capacitors are Siemens types. These are stocked by Electrovalue and have 5mm lead spacing. When ordering quote Ceramic B37449 and value.


Similar capacitors are held by Maplin, Bradley Marshalls and Cricklewood Electronics.

The miniature p.c.b. pushbutton switch is a RS type (No. 334-892) and available from any recognised RS Components supplier.

The double-sided printed circuit board is only available from Bytor Computers, Bright Street Works, Bright Street, Bury, Lancs BL96AQ, and cost £9-85, including postage and packing.

## JACK PLUG & FAMILY...

BY DOUG BAKER

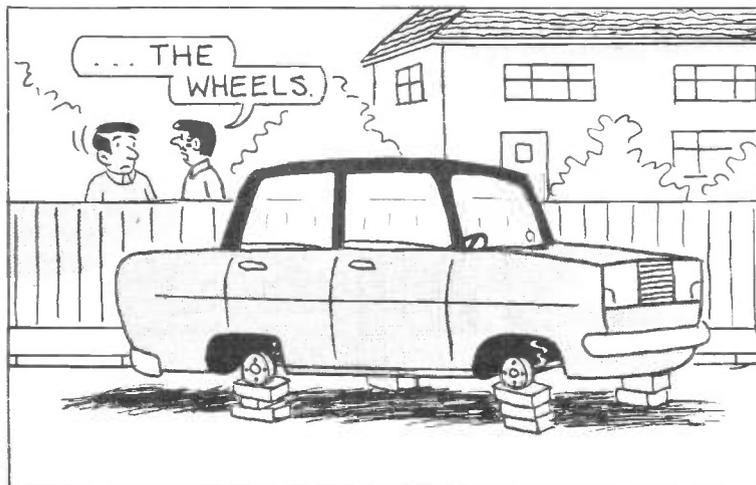

# EXPANSION SYSTEM FOR THE ZX81



BY  
M. LYSEJKO  
A. HUDSON

WHEN the ZX81 Microcomputer was unveiled in early 1981, Sinclair Research, the designers of the computer, surprisingly announced that they would not be providing any add-on hardware for the ZX81 apart from a printer and a ram pack. They were leaving this to other firms to supply.

Since then a large number of small businesses have sprung up to supply a varied and useful range of accessories, memory packs, interfaces and so on, to readily convert the memory intensive machine for monitoring and control applications in the home and laboratory.

This project falls into this category and is believed to be unique in its overall capabilities: it provides an

additional 4 kbytes of static RAM, and decoding to allow up to 11 more 1k blocks for memory, I/O or any device capable of supporting a bus. The decoding, address data and control busses are made available at three parallel expansion slots.

The ZX81 is a domestic computer which even novices are expected to find easy to use. This project has been designed to be compatible with this concept, but at the same time it has almost limitless capabilities for the more advanced user.

The Expansion System mates with the ZX81 to form a larger memory (5k total) monitoring and control capable system simply by easing its edge connector onto the ZX81 expansion slot.

The advantages of a larger memory system are manifold, such as allowing longer programs to be entered, larger data handling facilities, and a semi-memory mapped display, which will prove very useful for games programmers. You will also discover that LISTING and PRINTING are carried out much faster.

## EXPANSION SLOTS

The expansion slots referred to above are three 37-pin single sided 0.1 inch pitch card edge connectors with a polarising key fitted at position 35. This aligns the socket contacts with the finger set (tracks) on the daughterboards to be plugged in. The use of single-sided sockets allows prototype circuitry constructed on 0.1 inch Veroboard to be plugged in and tested before committing to a p.c.b.

Using these slots, electronic devices can be readily interfaced with the ZX81. For example, an RS232 printer interface, extra memory, joysticks, sound generator, digital and analogue I/O devices. Some of these "daughterboards" are in an advanced state of development: RS232, Sound Generator, 5 kbytes memory. Full details of these may be obtained from the suppliers of the p.c.b.—see Shop Talk.

Table 1. Expansion bus details

Pin No.	Function	Pin No.	Function	Pin No.	Function
1	RESET	13	RD	25	E1
2	WAIT	14	WR	26	E2
3	A4	15	D5	27	E3
4	A5	16	D6	28	E4
5	A6	17	D2	29	E5
6	A7	18	D4	30	E10
7	A8	19	D3	31	E9
8	A9	20	D1	32	E8
9	A3	21	D0	33	E7
10	A2	22	D7	34	E6
11	A1	23	Ø	35	KEY
12	A0	24	E0	36	+5V
				37	0V

8k RAM	0000-1FFF	
Vacant 8k block	2000-3FFF	
Internal 1k RAM	4000-43FF	
1st additional 1k RAM	4400-47FF	
2nd additional 1k RAM	4800-4BFF	
3rd additional 1k RAM	4C00-4FFF	
4th additional 1k RAM	5000-53FF	
RAM ↓	E0	5400-57FF
	E1	5800-5BFF
	E2	5C00-5FFF
	E3	6000-63FF
	E4	6400-67FF
	E5	6800-6BFF
	E6	6C00-6FFF
	E7	7000-73FF
	E8	7400-77FF
	E9	7800-7BFF
I/O ↑	E10	7C00-7FFF

Fig. 1. Memory map with Expansion System plugged in.

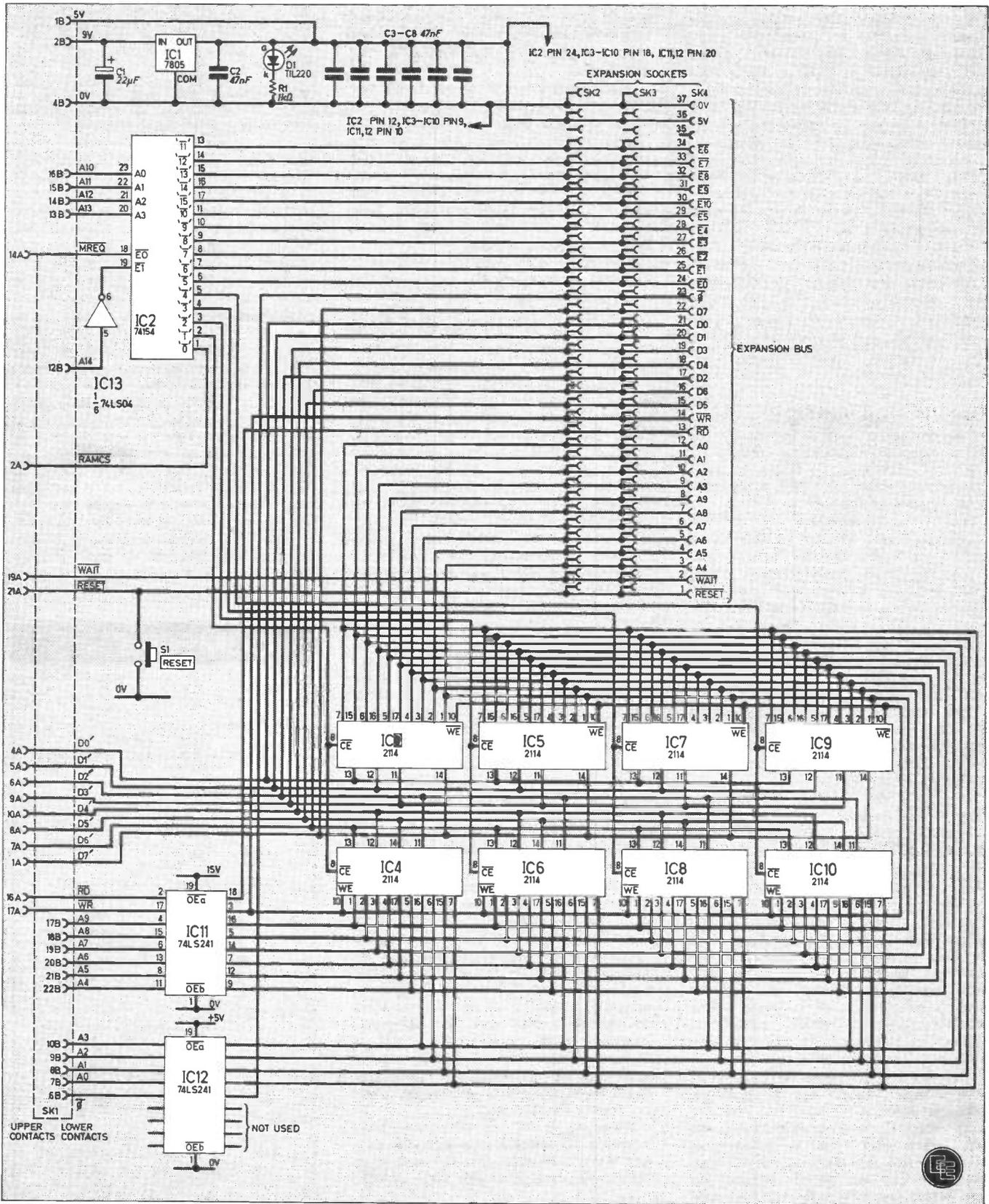


Fig. 2. The complete circuit diagram for the Expansion System for the ZX81.



## EXPANSION BUS

The address lines A0 to A9,  $\overline{RD}$ ,  $\overline{WR}$  and  $\overline{OE}$  signals reach the expansion slots via buffers. The upper address lines A10 to A14 are decoded to yield 16 enable lines. The lower five are used for resident RAM with the remainder going to the expansion slots for user defined applications. The RAM is kept low in the memory map to ensure continuous RAM for BASIC.

All enable lines are active low, and enable blocks of 1024 memory locations. They can be used for RAM, ROM, EPROM and any other device capable of supporting a bus.  $\overline{WAIT}$ ,  $\overline{RESET}$ , 0V and +5V complete the lines to the expansion slots to give the expansion bus shown in Table 1. The bars over the functions indicate they are active low.

The memory map with the Expansion System plugged into ZX81 is shown in Fig. 1.

## CIRCUIT DESCRIPTION

The complete circuit diagram for the Expansion System is shown in Fig. 2. It contains 12 digital i.c.s, a voltage regulator i.c. and a handful of discrete components.

IC1 is a monolithic 5V voltage regulator. Input voltage to this i.c. is picked up from the 9V rail in the ZX81. This is the input voltage to the ZX81 from its power supply unit and will be in the range 7 to 11V. The resulting 5V output from IC1 is coupled to the ZX81 internal supply so that the total system load is shared by IC1 and the regulator already in the ZX81.

The function of the regulator is to supply a steady 5V at up to 1A. If the input is 9V, then IC1 must dissipate 4 watts when supplying 1A, hence the inclusion of the heatsink.

L.e.d. D1 is included to indicate that power is being supplied to the extension board. Decoupling capacitors C3 to C8 are distributed around the board to eliminate high frequency oscillations on the power supply lines.

IC2 is a 4-to-16 line decoder. This has two "enable" controls. When either or both are at logic 1, all outputs are at logic 1 regardless of the states of the four inputs (A0 to A3). The latter represents a four-bit binary number (16 states). This number specifies which output is turned on (at logic 0) with the remaining 15 outputs off (logic 1).

The logic 0 will only be present if both enable inputs are at logic 0. Address line A14, via an inverter IC13, controls one enable input, so only when the c.p.u. is addressing memory with A14 high (greater than 16k) will any one of the outputs go low. When memory is being addressed  $\overline{MREQ}$  which controls the other enable input is at logic 0.

The outputs corresponding to the

five lowest binary inputs (memory locations 4,000 to 53FF) act as chip enables ( $\overline{CE}$ ) for each of the five 1k blocks of resident RAM. The remainder reach the expansion slots to allow up to a further 11 1k blocks to be accessed.

Address lines A0 to A9 from the ZX81 are buffered by permanently enabled tri-state buffers IC11 and IC12. These buffered lines are used for addressing the on-board 4k of static RAM and reach the expansion slots.  $\overline{OE}$ ,  $\overline{RD}$ , and  $\overline{WR}$  lines are also buffered and run to the expansion slots. Buffered  $\overline{WR}$  as explained later is used also for writing to RAM.

The data bus, which allows communication between the c.p.u. and the on-board RAM and any peripherals connected to the expansion slots is not buffered as this will be carried out on the individual daughterboards which plug into the expansion slots.

To effect a reset on the ZX81 the power supply input jack plug must be removed for a brief instant. To overcome this unsatisfactory arrangement, a RESET button has been built-in on the Expansion System. On pressing S1, the system is initialised. All memory is cleared and the ZX81 re-evaluates its system variable, Ramtop, which tells the ZX81 how much memory is available. If a software "bug" occurs which and the keyboard does not react, RESET may be used.

The RAM i.c.s chosen here are the readily available and inexpensive 2114 types. These are configured as 1024×4 bit locations. Two of these are needed to realise a 1024×8 bit arrangement (1k bytes) and four of these pairs, IC3/4, IC5/6, IC7/8, IC9/10 provide the 4k of additional RAM. Normally when using 2114 RAM, the high order nibble (D4-D7) is held in one i.c. with the low order nibble (D0-D3) in the other half of the pair. However, in this project, the data lines are shared differently.

The 2114 has ten address lines, A0 to A9, to uniquely select any one of its 1024 locations. Data input and output share the same pins. To select the chip, its  $\overline{CE}$  pin must be placed at logic 0. If the  $\overline{WE}$  pin is high with  $\overline{CE}$  low, internal circuitry places the addressed data on the data bus (read mode). If now  $\overline{WE}$  is made low, internal circuitry puts the information on the data bus into the addressed location (write mode). When  $\overline{CE}$  is high, the data pins are put in a third state known as the high impedance state, and effectively disconnects the i.c. from the data bus.

Thus A0 to A9 selects a particular location,  $\overline{CE}$  selects a specific i.c. pair and data is written into or read from the i.c. depending on the state of  $\overline{WE}$ .

## PRINTED CIRCUIT BOARD

All the components are mounted on a single printed circuit board. The

board is a very special type which has not to date appeared in EE. It is a double-sided board with plated through holes. This means that there is a copper track pattern on each side of the board. The two patterns are accurately aligned and joined together at the appropriate places by a copper lining on the surface of each hole which connects the copper pads on each side of the hole. This requires a complex and special technique and equipment not available to the home constructor. For this reason no p.c.b. master patterns have been given, but a supplier for this p.c.b. is given in Shop Talk.

The layout of the components on the topside of the board is shown in Fig. 3. As the board is plated through, only the component leads on the board underside need to be soldered.

Carefully position and solder all the i.c.s paying attention to their orientation. There is a notch at pin 1 body end. Next fit the resistor and capa-

## COMPONENTS

### Resistor

R1 1k $\Omega$   $\frac{1}{4}$ W carbon  $\pm 5\%$

### Capacitors

C1 22 $\mu$ F 16V elect.  
C2-C9 47nF monolithic ceramic (8 off)

### Semiconductors

D1 TIL220 red l.e.d.  
IC1 7805 5V 1A voltage regulator i.c. (To-220 case)  
IC2 74154 TTL 4-to-16 line decoder  
IC3-10 2114LC-1 static RAM, 1024 × 4 bit (8 off)  
IC11, 12 74LS241 TTL low power Schottky octal buffer, tri-state (2 off)  
IC13 74LS04 TTL low power Schottky hex inverting buffer

### Miscellaneous

S1 miniature p.c.b. switch  
SK1 23+23 way 0.1 inch pitch edge connector with wire-wrap pins  
SK2-SK3 37-way 0.1 inch pitch edge connector (3 off)  
Printed circuit board: double-sided plated through holes size 145 × 130mm; heatsink 10.5°C/W type TV2; 6BA nut, bolt and washer; self adhesive feet 5.6mm high (2 off)

Guidance only **£36** including p.c.b.  
Approx. cost

citors followed by the l.e.d. Note that the l.e.d. has a flat on its body alongside the cathode (k) lead. The three sockets SK2-SK4 should have a polarising key fitted at position 35. A piece of stripboard may be used for this, glued in place. Solder the sockets in place.

SK1 needs to have angled pins. This type may be difficult to locate and is more expensive than the

straight pin versions. However, types with miniwrap wire-wrapping pins may easily be bent to the required shape by bending the two rows through 90 degrees. A piece of 0.1 inch stripboard may be used for this purpose, using the holes closest to one end.

This socket should also be fitted with a polarising key at position 3. The pins and track wipers may need to

be removed to fit this. A small piece of stripboard can be used as the "key" and glued in place.

You should check with the supplier of the straight pin socket to find out that the leads may be bent without causing the pin to fracture. With one particular socket tried (manufacturer unknown) the pins snapped off when they were bent.

Next bend the leads on IC1 so that when positioned on the board the fixing hole in its tab aligns with the hole in the p.c.b. Apply some heat-sink compound to the underside of IC1 so as to make good thermal contact with the heatsink. Position the heatsink on the board and bolt IC1 to the board through the heatsink using a 10mm long bolt, nut and shakeproof washer. Solder IC1 to the board. Finally position and solder S1 to complete the construction.

Thoroughly inspect the board construction, checking for component


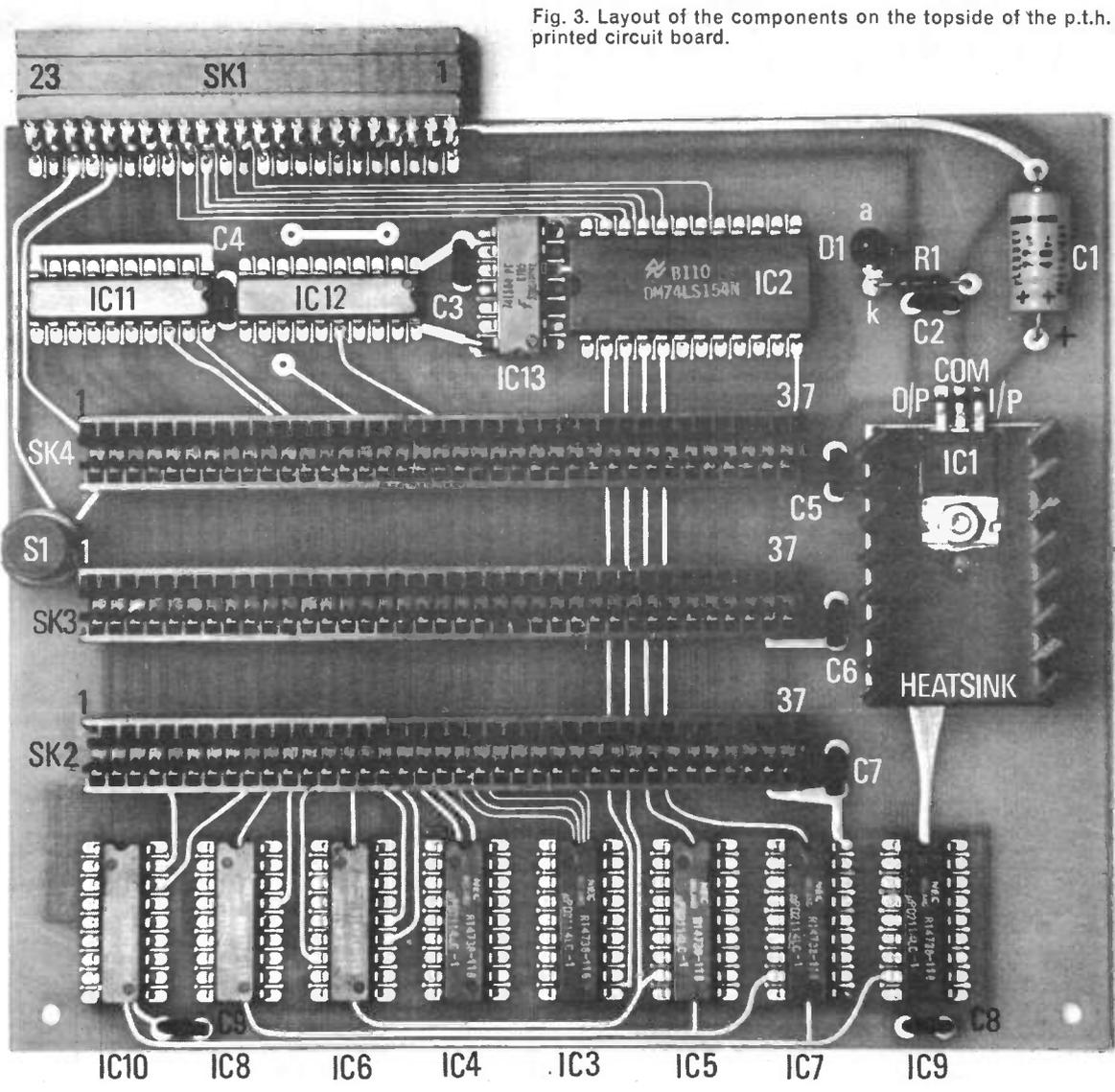



Fig. 3. Layout of the components on the topside of the p.t.h. printed circuit board.

Table 2. IC2 decoding check table

Pin No.	13B	14B	15B	16B	IC2 pin no.	reading OV, remainder 5V
Function	A13	A12	A11	A10		
0	0	0	0	0	1	—
0	0	0	0	1	2	—
0	0	0	1	0	3	—
0	0	0	1	1	4	—
0	0	1	0	0	5	—
0	0	1	0	1	6	24
0	0	1	1	0	7	25
0	0	1	1	1	8	26
1	0	0	0	0	9	27
1	0	0	0	1	10	28
1	0	0	1	0	11	29
1	0	0	1	1	12	30
1	0	1	1	1	13	34
1	1	0	0	0	14	33
1	1	0	0	1	15	32
1	1	1	0	0	16	31
1	1	1	0	1	17	30

Expansion slot no.		
Conditions		
12B	14A	Output
A14	MREQ	State
0	0	All high
0	1	All high
1	0	As Tbl.
1	1	All high

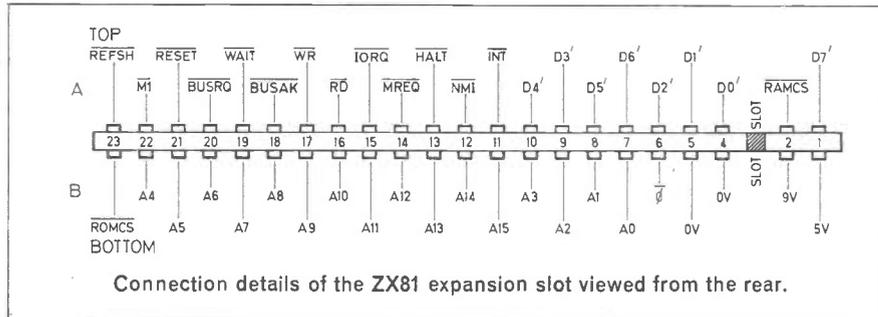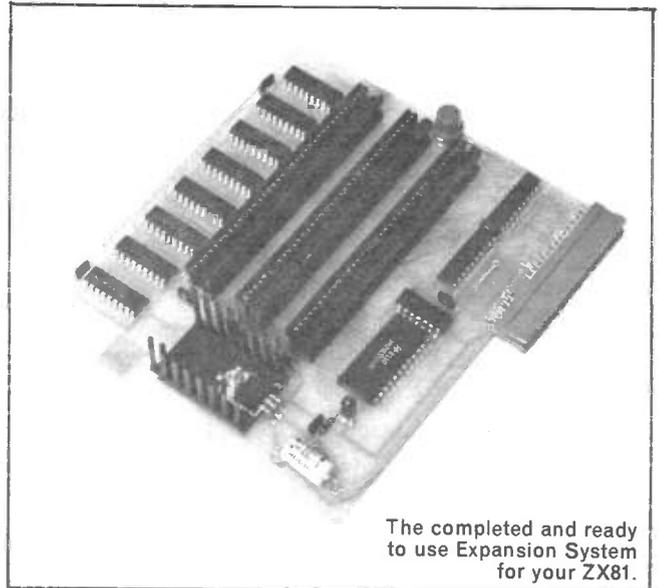

position, orientation and that all component leads have been soldered. Make sure that there are no solder bridges between the tracks and pads.

Fit the specified rubber feet. These will hold the board at the correct height to align with the ZX81 expansion slot. The unit may then be plugged into the ZX81 and tested.

### TESTING

The Expansion System must always be inserted before the ZX81 power supply is connected, and removed after the supply has been disconnected.

On connecting the power supply, the l.e.d. D1 should illuminate. A Ramtop test should yield 21504 which will indicate that a large part of the construction is functioning satisfactorily, since RAM read and write will have been carried out. Press RESET to initialise and test the reset switch.

Disconnect the ZX81 power supply and remove the board. To check the

remainder of the circuitry you will need a 9V supply. A PP9 battery will be suitable. Connect this across C1. This can be done easily by fitting a battery connector with miniature crocodile clips.

Connect the negative probe of a voltmeter set to read 10V d.c. to the -ve side of C1. Place the +ve probe on the output pin of IC1. You should read 5V. Touch the +ve probe onto each of the V<sub>CC</sub> pins of all the i.c.s on board. You should read 5V in all cases. Check also that the 5V is available at expansion slot position 36. Also connect the probe to expansion slot positions 24 to 34 to read 5V in all positions. Pins 1 to 5 on IC2 should also give a reading of 5V.

To check the decoding of IC2 you will need to make up some means of connecting a voltage level to some of the pins on SK1, namely 1B, 4B, 12B, 13B, 14B, 15B and 16B, and 14A. A piece of 0.1 inch pitch stripboard, 5 strips wide by about 10 holes long



with flying leads attached to one end can be used for 12B to 16B. For pin 14A on SK1, a miniature crocodile clip or hook probe fitted with a flying lead can be fitted to the pin at its point of entry into the body of SK1.

A 4-strip wide piece of stripboard, same length as before, fitted with flying leads at strip positions 1 and 4 (position 3 slotted) will provide the logic level source for the inputs to IC2. A solderless breadboard will be found most useful for connecting the inputs as required, otherwise the lead ends will have to be twisted together. The 5V lead from 1B will be used for logic 1, the 0V from 4B for logic 0. Use Table 2 to check the operation of IC2.

If the above tests have all been satisfactorily completed, the Expansion System is ready for use, to give one immediate additional 4k bytes of memory and the necessary signals to communicate with daughterboards of your design. □

A prototype Sound Generator daughterboard also fitted with a capacitance-discharge monitoring circuit board.

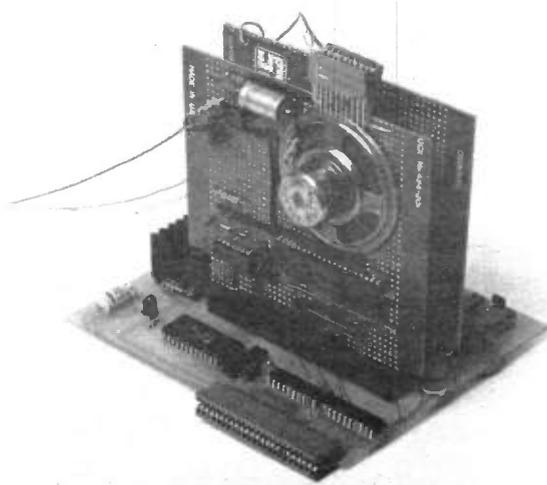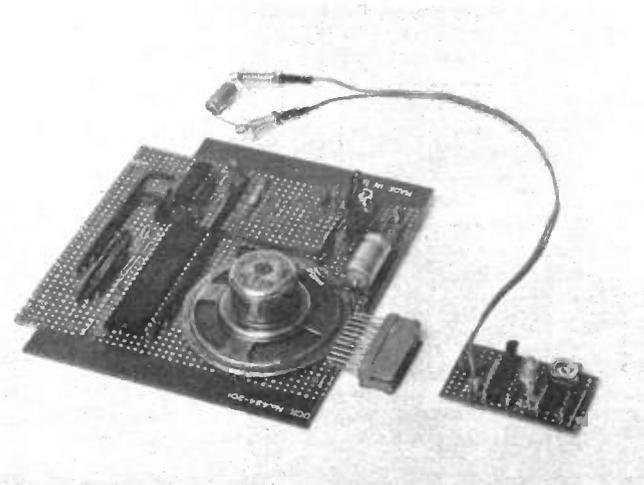The Expansion System fitted with two prototype daughterboards, both build on 0.1 inch pitch stripboard.



## WHAT IS **it** ALL ABOUT?

### THE ELECTRONICS OF INFORMATION TECHNOLOGY

Baffled by this "new" technology? This important series of articles sets out to explain the various electronic techniques involved and how they will fit together, in combinations of varying size and complexity, to meet the demands of commerce, industry, public services and ordinary individuals for rapid access to information and data of all kinds, as well as computing facilities, in the years immediately ahead.

Specially written for the electronics experimenter, technician or engineer, this series provides a new view of electronics. It should not be missed by anyone wishing to understand the techniques that are helping to mould the future.

## THE NOVEMBER ISSUE ALSO FEATURES

### DIGITAL METRONOME

Provides direct readout of pulses per minute, updated automatically to register changes in tempo as selected by user. Mains operated. Easy to calibrate. Always accurate. An essential instrument for the professional music teacher, this Digital Metronome will also be a most valuable aid for musicians of all classes. Also fitted with switchable audible/visual output.

### OSCILLOSCOPE COMPANION SEDAC PRIZE WINNING PROJECT

This unit will convert a single beam c.r.o. with external sync. input to a dual beam version and provides additional features permitting accurate measurement of voltage and current.


### COMBINATION LOCK

Self-contained, battery operated. Selection of correct 5-digit number actuates relay which can be used to operate electro mechanical lock or other mechanism. The number sequence is entered by means of a single rotary dial. The combination may be easily altered.

### ZX TAPE CONTROLLER

Designed for use in conjunction with the ZX81 or Spectrum micro-computer and a standard cassette recorder. Allows "load" and "save" operations to be carried out without need to unplug cassette leads. Contains microphone and loudspeaker; also a tape erase facility.
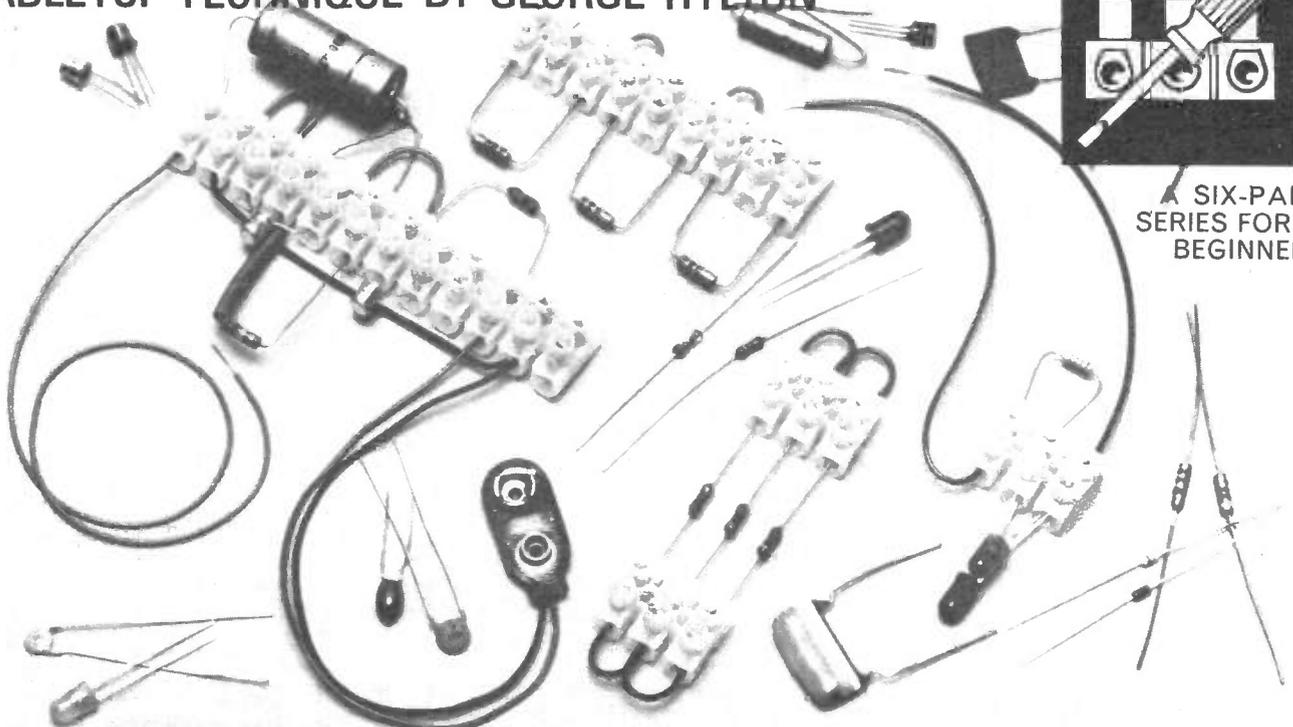
## A NEW SERIES FEATURING A TEARLESS TABLETOP TECHNIQUE BY GEORGE HYLTON



A SIX-PART  
SERIES FOR THE  
BEGINNER

# INTRODUCING ELECTRONICS

## Part I FROM ELECTRONS TO ELECTRONICS

IN 1899, J. J. Thompson made experiments with a cathode-ray tube which may be said to mark the beginning of electronics. He showed that the mysterious "cathode rays" which travelled through the tube under the influence of an electric field were in reality little bits of matter, each with a definite mass and a definite electric charge. They were named "electrons". In giving them that name, a more precise and scientific meaning was given to a word which had been around for a very long time.

"Elektron" was the ancient Greek word for amber. Amber is a fossilised natural resin. Like the synthetic resins of today amber is a good insulator. Rubbed with dry cloth or fur it acquires an electric charge which attracts bits of dust and fluff. The Greeks knew this, but didn't follow it up,

When, in later ages, learned men discovered that other substances, such as wax and glass, have similar properties, they needed a word which meant amber-like to describe these properties. Being scholars, they used the Greek word to coin their new

term: the new word, meaning amber-like, was "electric".

So in calling the particles of the cathode rays electrons, scientists were really harking back to the very beginnings of electrical science. Long before the discovery of the electron as a carrier of electric charge and therefore a vehicle for electric currents there were other pioneers, such as the American, Benjamin Franklin, who searched for some explanation of electrical phenomena. For many years they managed to explain the observed effects of "electricity" by assuming that matter was permeated by an invisible, weightless "electric fluid". If an object had more than the normal amount of electric fluid in it, it was said to be "charged" with electricity.

### TWO KINDS OF ELECTRICITY

So far, so good. But it soon became apparent that there were two kinds of electricity, positive and negative. Were there two kinds of fluid? Not necessarily, since a deficiency of fluid could give one sort of charge (say negative) and an excess of fluid the

other sort (positive). Quaint though the idea may seem, it had a lot going for it.

With our modern knowledge of matter whose every molecule contains electrons which can be made to hop from atom to atom under the influence of electric forces, the fluid idea can be seen as a pretty good guess. The only really unfortunate thing about it was that the early investigators guessed wrong about polarity. They assumed that the fluid flowed from positive to negative. When it was realised that electric currents were movements of negative charges carried by electrons, flowing from negative to positive, the "wrong" way, it was too late to do anything about it.

Fortunately things have got a little easier with the invention of transistors. Transistor physicists got into the habit of regarding the "gap" left in an atom by the departure of an electron as a real thing, a "positive hole".

A hole behaves in much the same way as a positive charge. Under the influence of the battery voltage it

moves round a circuit from positive to negative, the "right" way. So by forgetting about the real electrons and thinking only of holes we can reconcile the conflict between electron flow and conventional current flow.

## ELECTRIC CELL

Luckily there were no such problems in the 1820s, when an obscure German scientist, Georg Simon Ohm, set about the task of obtaining a better understanding of current flow. For his experiments he used a relatively new invention, the electric cell.

The cell had been developed by the Italian, Volta, following a chance discovery by his fellow-countryman, Galvani, in quite a different area—biology. Galvani noticed that under certain conditions the legs of a newly-killed frog twitched as if given an electric shock. Investigation showed what the essential conditions were: wet frogs' legs had to be in contact with two different metals.

Looked at with modern knowledge, the explanation is that the two metals form the electrodes (electric gateways) of an electric cell. The moisture forms the electrolyte (like the acid in a car battery). The resulting current, though feeble, is enough to trigger the nerves into activity and hence the muscles they control. The discovery led to the development of the "electrochemical cell", in which current is generated as a result of chemical changes.

In Ohm's day it wasn't certain that the kind of electricity produced by a "voltaic cell" was the same as the "frictional electricity" produced by rubbing an insulator. For this reason Ohm avoided the term and called his circuit a "galvanic chain".

The electric-fluid idea suggested comparisons with the flow of water. If, as it seemed, the electric fluid could flow freely through metal wires then surely these could be likened to water-pipes? The cell which provided the driving force must then be the equivalent of the elevated tank or reservoir which provides the head of water (the pressure), to drive water through the pipe when we turn on the tap.

## RESISTANCE

Friction impedes the flow, so a thin or long pipe lets through less water than a thick or short one, with the same pressure. Does this apply to electric conductors? Ohm was able to show that it does. Thin wires allow less current flow than thick ones, for the same electric pressure (voltage). Long wires allow less than short ones.

It also turned out that different metals (iron, copper, silver, and so on) allow different currents to flow, even when they are the same length and thickness.

In a word, different conductors offer different degrees of *resistance* to the flow of current. The idea of resistance as something definite and measurable was Ohm's real contribution to electrical science. The idea had far-reaching implications, which is why even today it is in universal use in electronics.

The existence of resistance meant that the strengths of currents could be controlled and adjusted. Ohm's law (current increases in proportion to the driving voltage or "electromotive force" and decreases in proportion to the resistance in a circuit) paved the way to electrical engineering.

## EXPERIMENTAL WORK

There were no ammeters in Ohm's day to indicate the strengths of currents. Like him, we'll do some practical work using only a very crude current indicator.

For the purpose of this series of articles we shall dispense with solder and join up our circuits with the aid of screw terminals. These can be bought in the form of electricians terminal blocks, made of plastic, and usually containing twelve double terminals. (They can be divided into smaller blocks by cutting them with a sharp knife.)

It is essential to use the smallest size of terminal block, known as a 2-amp block. Larger ones (5-amp and upwards) will not accept some of the



Fig. 1.1. A suitable battery holder fitted with 4 × 1.5V (type AA) cells. Also shows battery clip with flying leads.

components we shall be using. You'll also need some ordinary electronic hookup wire and various components which will be specified as we go along.

## POWER SUPPLY

For the power source we shall use a six-volt battery. The most convenient form is a plastic holder into which fit four small 1.5V dry cells of the HP7 type or equivalent. These are connected in series by the holder to yield 6V. Get a holder with a press stud connector as used in transistor portable radios and get a connector to fit, with flying leads. See Fig 1.1.

## CURRENT INDICATOR


We shall use a lamp to indicate that current is flowing. Ordinary filament lamps need too much current so we'll make up a special indicator lamp using two l.e.d.s (light emitting diodes) one red, the other green. An l.e.d. lights up when current flows through it in a particular direction—in at its anode (entry gate) and out at its cathode (exit gate). The cathode leadout is usually marked by a small 'flat' next to it on the l.e.d. plastic case.


Unlike a resistance, an l.e.d. does not pass a current which rises smoothly as the applied voltage rises. Instead, it allows no current at all to flow at very low voltages, then, once

Shows the components used in this month's practical work. The screwdriver has a wire cutter/stripper in the handle and is the only tool required. No wire shown.


## Components

Quantity	Description
4	2-amp 12-way screw terminal blocks (some for later use)
1	Battery holder to hold 4 × HP7 (type AA) batteries, with integral battery connector
4	HP7 (type AA) 1.5V batteries
3 metres	P.v.c. covered light duty stranded wire; selection of colours to make up 3 metres
1	Battery clip with flying leads to suit battery holder
1	220 ohm ¼W carbon ±5% tolerance resistor
3	1 kilohm ¼W carbon ±5% tolerance resistors
1	TIL220 red light emitting diode
1	TIL221 green light emitting diode

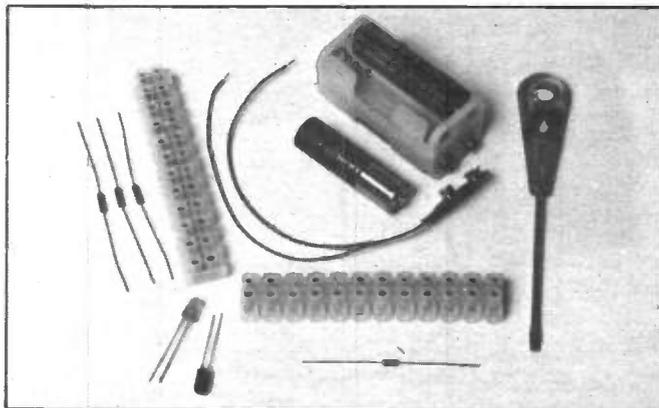


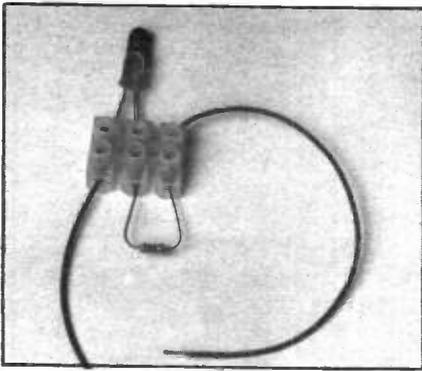


The assembled Current Indicator Lamp.

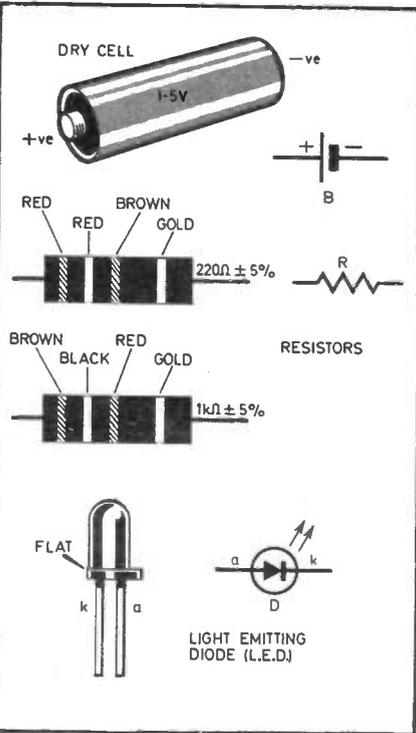

Shows the physical representation of the components and their circuit symbols used this month. The resistors have their value printed on the body in the form of a Colour Code. The decoding for the two different values is provided for those unfamiliar with this system.

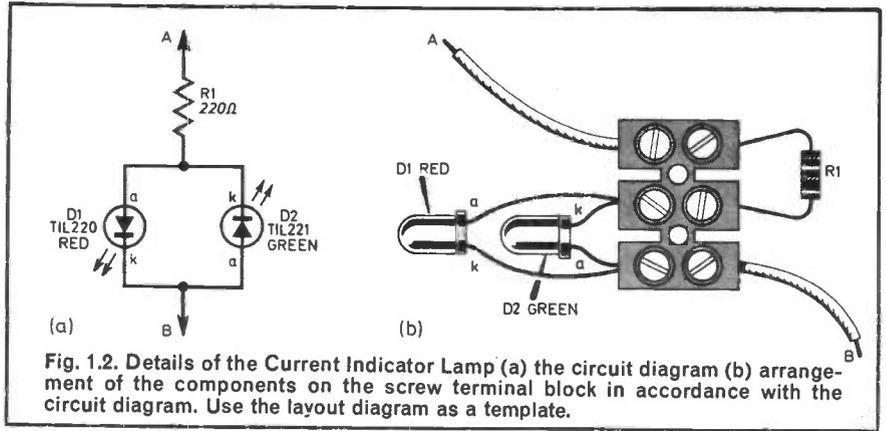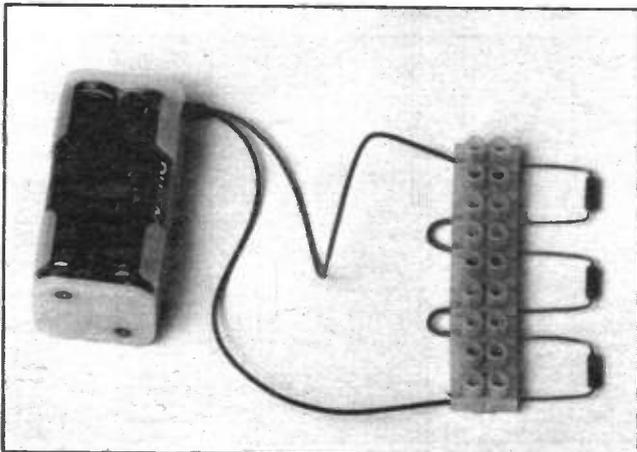The circuit of Fig. 1.3 fully assembled on the block from which the Indicator block was cut.



a certain voltage is reached, the current flow builds up very rapidly, a small additional increase in voltage then producing a large increase in current.

This "non-ohmic" behaviour makes it only too easy to destroy an l.e.d. by applying too much voltage. In practical l.e.d. circuits the designer always ensures that the current is limited to a safe amount. The easiest way is to connect a resistance so that the current must flow through this to get to the l.e.d., see Fig. 1.2a. If the resistance is large enough the current is not able to exceed the safe value. (This varies according to the type of l.e.d. but most will take 20 milliamps safely.)

For our Current Indicator Lamp we use two l.e.d.s, connected in parallel but "back to back". The red l.e.d. lights when current flows from A to B and the green l.e.d. when current flows from B to A. Fig. 1.2b indicates how the connections can be made using three terminals of a block. It will be convenient to cut off a strip

of three connections so that the indicator forms a separate unit which can be moved around as required.

Check the Indicator by connecting A and B to your 6V battery. The brightness of the l.e.d. is as great as it can be in our experiments. You will see that they are not very bright and don't show up well in sunlight or a brightly lit room.

### CURRENT IN A CIRCUIT

In Fig. 1.3a the three resistances are in series. That is, the current flows through one resistance after another on its round trip from positive battery terminal to negative.

Does the current get weaker as it goes through the resistances? This can be checked by inserting the indicator into the circuit at points A, B, C and D. If the current grows weaker the l.e.d. will glow less brightly at the further points. Connecting up the resistors as in Fig. 1.3b creates suitable links which can be removed to insert the Indicator.


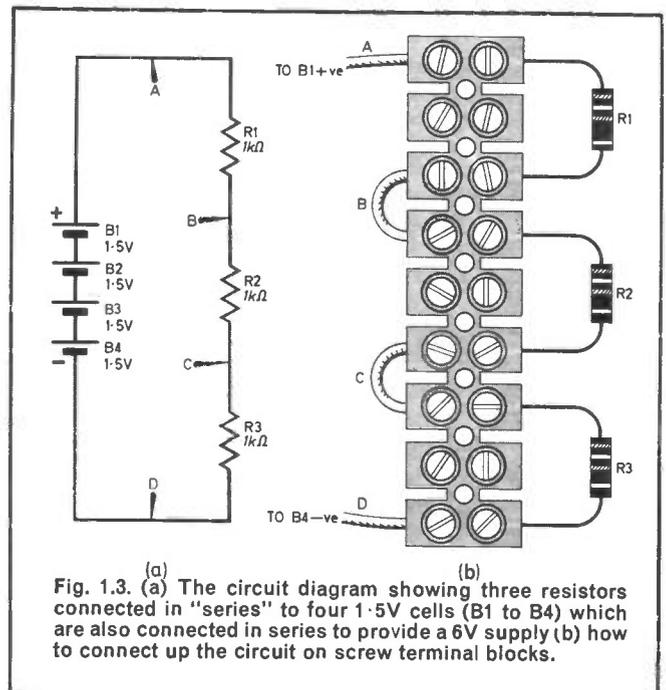


Fig. 1.3. (a) The circuit diagram showing three resistors connected in "series" to four 1.5V cells (B1 to B4) which are also connected in series to provide a 6V supply (b) how to connect up the circuit on screw terminal blocks.

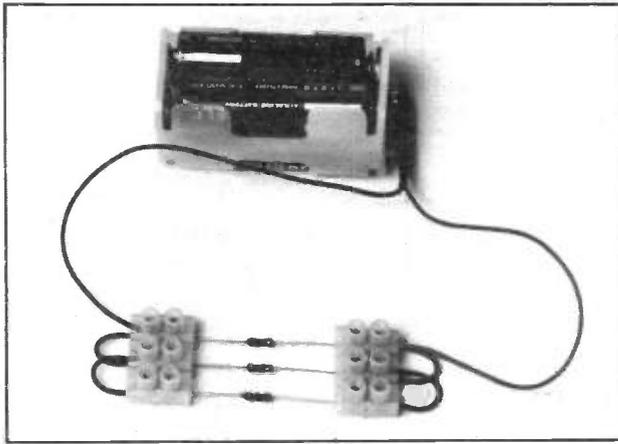

The circuit of Fig. 1.4 fully assembled. The two blocks need not be cut as shown. The remaining 9-way and one 12-way block may be used instead.

You should find that the current is the same at all points. The l.e.d. lights only dimly because the resistances in a series circuit add up. In this case they add to  $3k\Omega$  (3 kilohms=3,000 ohms). If you short out one resistor the l.e.d. will be brighter, and two shorted makes it brighter still.

In a series circuit, the battery voltage is shared out among the various resistances in proportion to their size (that is their ohms values, not their physical dimensions). With three equal resistances, our 6 volts (6V) is shared equally. If you could measure the voltage across each individual resistor it would be 2V.

If two of our resistors were replaced by a single one of value equal to 2 kilohms the current would remain the same but the voltage drop across the  $2k\Omega$  would be 4V. The voltage drop across the total  $3k\Omega$  in the circuit must be 6V, because this is what we apply to the circuit from our battery.

Note that the ratio of voltage to resistance is the same whether we consider individual  $1k\Omega$  resistances or combine them into larger resistances:  $2V/1k\Omega = 4V/2k\Omega = 6V/3k\Omega$ . In every case the ratio is 2. But two what? In fact, two milliamperes. The ratio of voltage to resistance is the current. If you divide volts by kilohms (thousands of ohms,  $k\Omega$ ) the answer comes out in thousandths of amperes, milliamperes.

Don't worry if these units are unfamiliar, or if you're not much of a hand at maths. It needn't stop you having fun with electronics.

## RESISTORS IN PARALLEL

If you now rearrange your three  $1k\Omega$  resistances, connecting them in parallel (Fig. 1.4) the full battery voltage is applied to each. Each resistance passes a current of  $6V/1k\Omega = 6mA$  so a lamp placed in circuit at points B, C, or D will glow more brightly than in the series circuit.

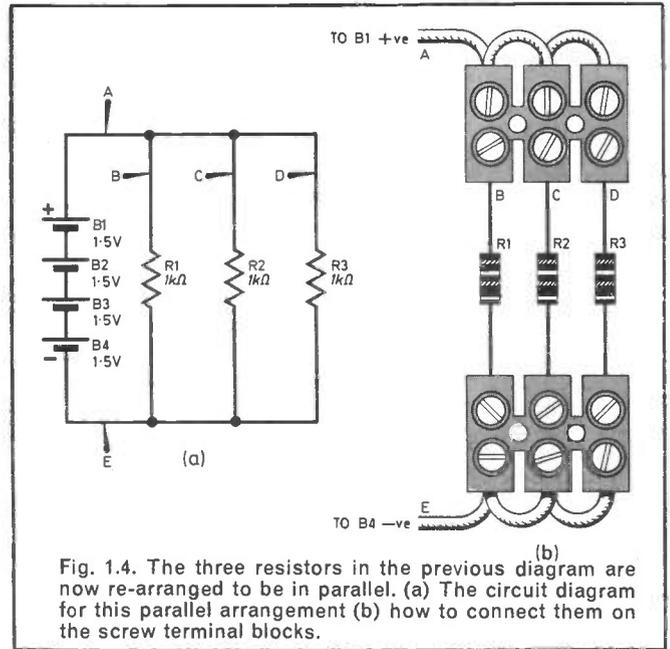


Fig. 1.4. The three resistors in the previous diagram are now re-arranged to be in parallel. (a) The circuit diagram for this parallel arrangement (b) how to connect them on the screw terminal blocks.


At point A, the total current of 18mA passes and a lamp here glows more brightly still. This shows that when resistances are in parallel the combination allows more current to pass than each individual resistance would.

Common sense tells us that in our case, with three equal resistances, and three lots of current, the combination is equivalent to one resistance of one-third the value of the individual ones. In this case the equivalent resistance

is  $1k\Omega/3 = 333$  ohms. If there had been only two  $1\Omega$  resistances in parallel the equivalent would have been  $1k\Omega/2 = 500$  ohms.



By looking at the circuit you can see that if an extra, very high resistance were connected in parallel it would allow only a small additional current to flow. In parallel circuits, it is the lowest resistances which have the greatest effect.

To be continued

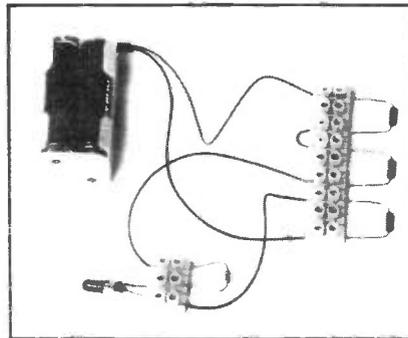


Placing the Indicator in series with the circuit of Fig. 1.3 at point C.

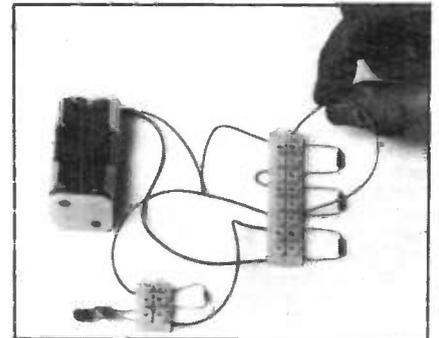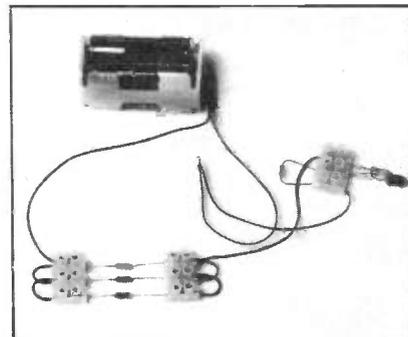
Inserting the Indicator at point A in the circuit of Fig. 1.4.



Shorting out the two upper resistors will cause the Indicator brightness to increase.

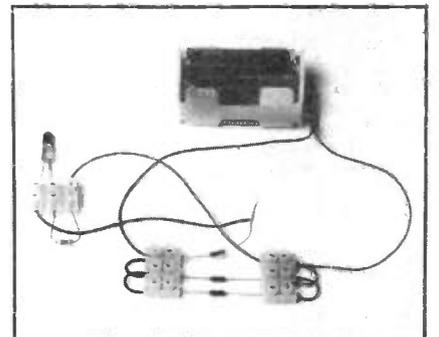Inserting the Indicator at point B in the circuit of Fig. 1.4.



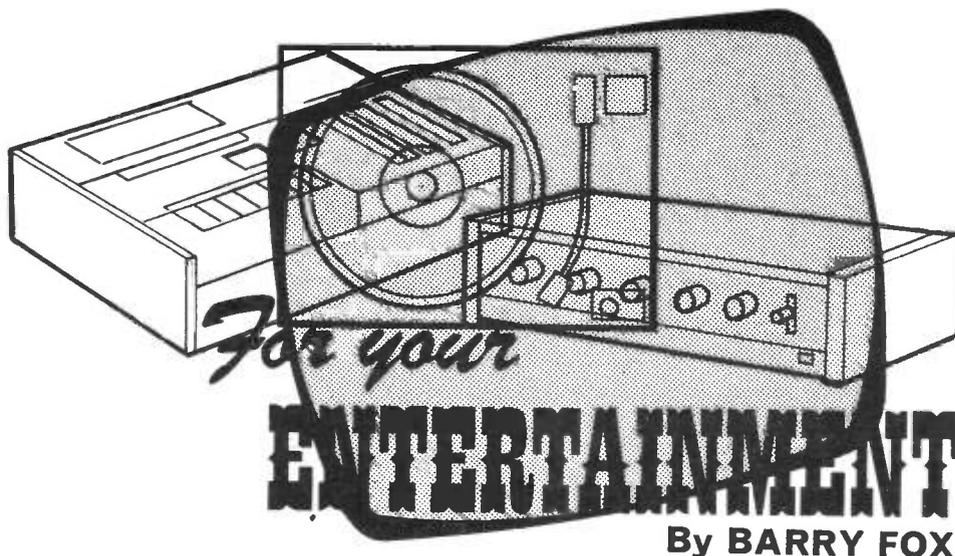

## On The Line

I make no apology for returning to the subject of telephones. Liberalisation, or *supposed* liberalisation, of the British telephone service is in the news again. But it's also in a mess. And there has been some interesting feedback from the trade on my previous pieces.

The Government has now brought in new laws which will make it illegal to advertise a telephone, or any gadget for connection to the telephone lines, without marking it as officially approved, or non-approved.

The new laws will also make it illegal to sell a phone that isn't marked in this way. Note well, however, the subtle but important fact that the new laws don't make it illegal to sell non-approved telephones or to use them.

The idea is to give the public a clear choice between buying authorised and illicit equipment. If subscribers buy an authorised phone then they can legitimately have it installed by British Telecom (née the Post Office) and use it without fear of retribution. If they buy unauthorised equipment, they will have to connect it themselves and risk falling foul of British Telecom.

The Department of Industry, which has brought in the new laws, says it is backing British Telecom to the hilt over BT's rights to demand that any telephone subscriber disconnects unauthorised equipment. If subscribers refuse to disconnect unauthorised equipment, BT can disconnect their telephone lines at the exchange.

## Red or Green

Unfortunately it's not half as straightforward as at first appears. There has already been confusion over when and how the new laws come into force. The restriction on advertising (Telecommunications Order 490 of 1982) came into force on July 1 1982. But the restriction on marking (Order No. 491) is in two parts.

It is now illegal for shops to display equipment without also displaying a notice which says whether it is authorised or not. But only after November 1 1982 must the equipment itself be clearly marked with a "green for go" approved

label, or a "red for no-go" label for prohibited equipment.

If you think this sounds confusing you are in good company. Even the Department of Industry got it wrong in a statement to the press which told editors that equipment must carry the go and no-go labels from June 1 1982. As a result some newspapers got it wrong too.

Why, you may well ask, is it taking so long for approved telephones to get into the shops. The British Telecommunications Act, which came into force on October 1 1981, ended British Telecom's monopoly. And it gave the British public a chance to buy their own telephones outright (over and above the first which always has to be rented from British Telecom).

But, even by the end of March 1982, when those marking orders were laid before Parliament, there still wasn't a single authorised phone for sale in the shops. There was however a wide range of unauthorised phones. And anyone who connected these was at the risk of being harassed by British Telecom.

Even the Chairman of the Football Association in Lancaster Gate wasn't immune. "It has been brought to my notice that you have connected a telephone that is not approved", BT told the FA. I look forward to receiving your confirmation in writing that this telephone has been permanently disconnected."

## Testing Time

The snag is that the Department of Industry opened the legal door to authorised telephones before organising an authorisation system. In July 1981, when the Telecommunications Act received Royal Assent, the DOI asked the British Electrotechnical Approvals Board (BEAB) to arrange a test programme.

BEAB needed standards for testing. These had to be drawn up by the British Standards Institution (BSI) which in July 1981 set up five separate committees to examine the problems. One committee alone had representatives from over twenty official bodies as diverse as British Gas, The Dept. of Industry, British Telecom, The Independent Broadcasting Authority, The Oil Industry and the Post Office Engineering Union.

To try and get things moving, at the end of 1981, the Department of Industry asked British Telecom to do some interim testing. BT has charged £2,000 a phone to do some stop-gap tests and by the time this article appears in print there should be a few BT-approved phones on sale in the shops.

If you are an *afficionado* of exotic phones, don't get too excited. The phones approved by British Telecom in the Spring of 1982 were from GEC, STC, Plessey and Thorn-Ericsson. Approval was automatic and no charge was made because these companies were already supplying telephones to British Telecom. So what initially goes on sale to rival British Telecom will in fact be nothing more than telephones that are already available from British Telecom!

Some foreign firms have refused to submit their phones for this interim testing, because they fear a rough ride from British Telecom. Out of ninety-five phones that were submitted in another batch for paid testing, only nine were passed on by the Department of Industry to British Telecom. These came from six companies (Conversation Pieces, Astral Telecom, Ace Telecom, Store-a-call, GEC and STC) and some are foreign.

Tests on these phones should have been completed by now, so if any pass muster they might soon be in the shops. Telephones approved by the BBT should be in the shops by October, exactly one year after the new law came into force. Then liberalisation will begin to mean something.

## Protected Network

The British telephone network must, of course, be protected against unauthorised connections which can either create dangers, by putting mains onto the line, or degrade the service. But over the last year I've been appalled by the muddle, and misinformation surrounding liberalisation of our telephones.

There is little doubt that firms in the business of selling telephone equipment are being hamstrung by red tape. At a conference called to discuss recent "privatisation" developments, John Wakeham, the Minister responsible, got so confused when answering my questions that two of his colleagues had to seek me out afterwards to give clear, corrected facts.

When Sir George Jefferson, Chairman of British Telecom, guested on the Jimmy Young radio show to answer listeners' questions on telephones he told one lady: "It is illegal to connect a purchased telephone in place of a British Telecom one."


But it isn't illegal or punishable by law. It contravenes the telephone regulations and is punishable by BT who can disconnect your phone lines.

Interestingly the new laws, on marking and advertising, mean that it is perfectly legal and legitimate to advertise and sell non-approved telephones as long as they are clearly marked as such. Purchasers can then perfectly legitimately connect them to a private system, for instance a business intercom.

As one journalist put it to John Wakeham recently. "So it's all right to sell dangerous sub-standard equipment provided it only fouls up a private network and only electrocutes engineers who aren't working for British Telecom?"

# 1983 SCHOOLS Electronic Design Award COMPETITION

over  
**£2,000**  
in Prizes

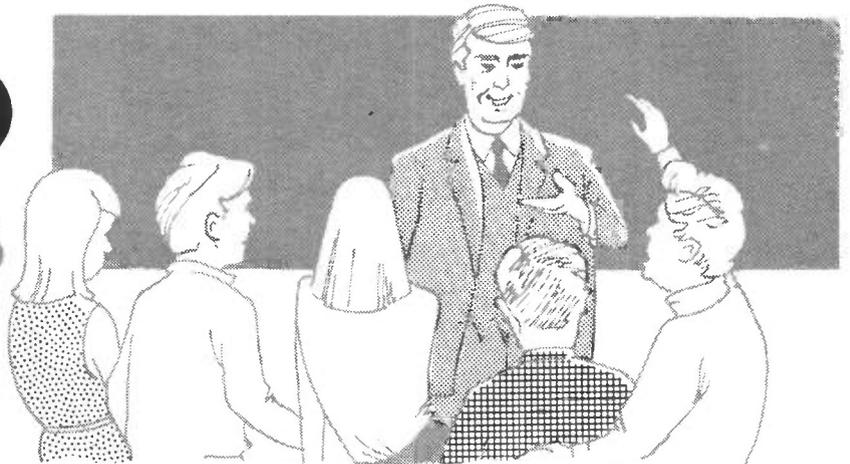

Mullard Ltd—the largest electronic components company in the UK—and EVERYDAY ELECTRONICS join forces to present this rewarding challenge to Secondary Schools...

## DESIGN A PIECE OF ELECTRONIC EQUIPMENT HAVING A DIRECT PRACTICAL APPLICATION IN A SCHOOL'S SCIENCE LABORATORY

This competition is open to any United Kingdom Secondary School, State or Independent. Pupils of either sex in the age group 11-18 are eligible to participate in a team representing their school.

The competition will be conducted in two stages.

### STAGE 1

Submission of Papers describing the proposed project with full circuit details.

Papers will be judged for novelty, ingenuity and viability. Particular attention will be given to originality and good circuit design technique.

Schools whose designs are adjudged to be the most promising will be asked to produce a working model.

### STAGE 2

Models will be examined and prize winners selected on the basis of mechanical design, neatness of wiring and general assembly, plus operational performance.

*All models will be exhibited at Mullard House, London, where the official presentation of prizes will be made at the end of June 1983. Representatives of finalists will be invited to stay overnight in London as guests of the SEDAC sponsors.*

**FIRST PRIZE** The SEDAC Trophy  
and £300\*

**SECOND PRIZE** £200\*

**THIRD PRIZE** £100\*

\* Plus a selection of components valued at £200

**NINE RUNNERS UP** a selection of components  
valued at £100

*In addition, all twelve finalists will receive a certificate and one year's subscription to EVERYDAY ELECTRONICS.*

Science teachers of Secondary Schools are invited to apply for a Registration Form which contains full details of this competition.

Write to: Schools Competition, Room 2130, Kings Reach Tower, Stamford Street, London SE1 9LS.

**Secondary School Pupils**—make sure your school accepts this challenge and enters this contest. So bring this announcement to the attention of your science teacher or the head of your school.


Closing date for Registration : November 15 1982

Closing date for submission of Papers : January 31 1983



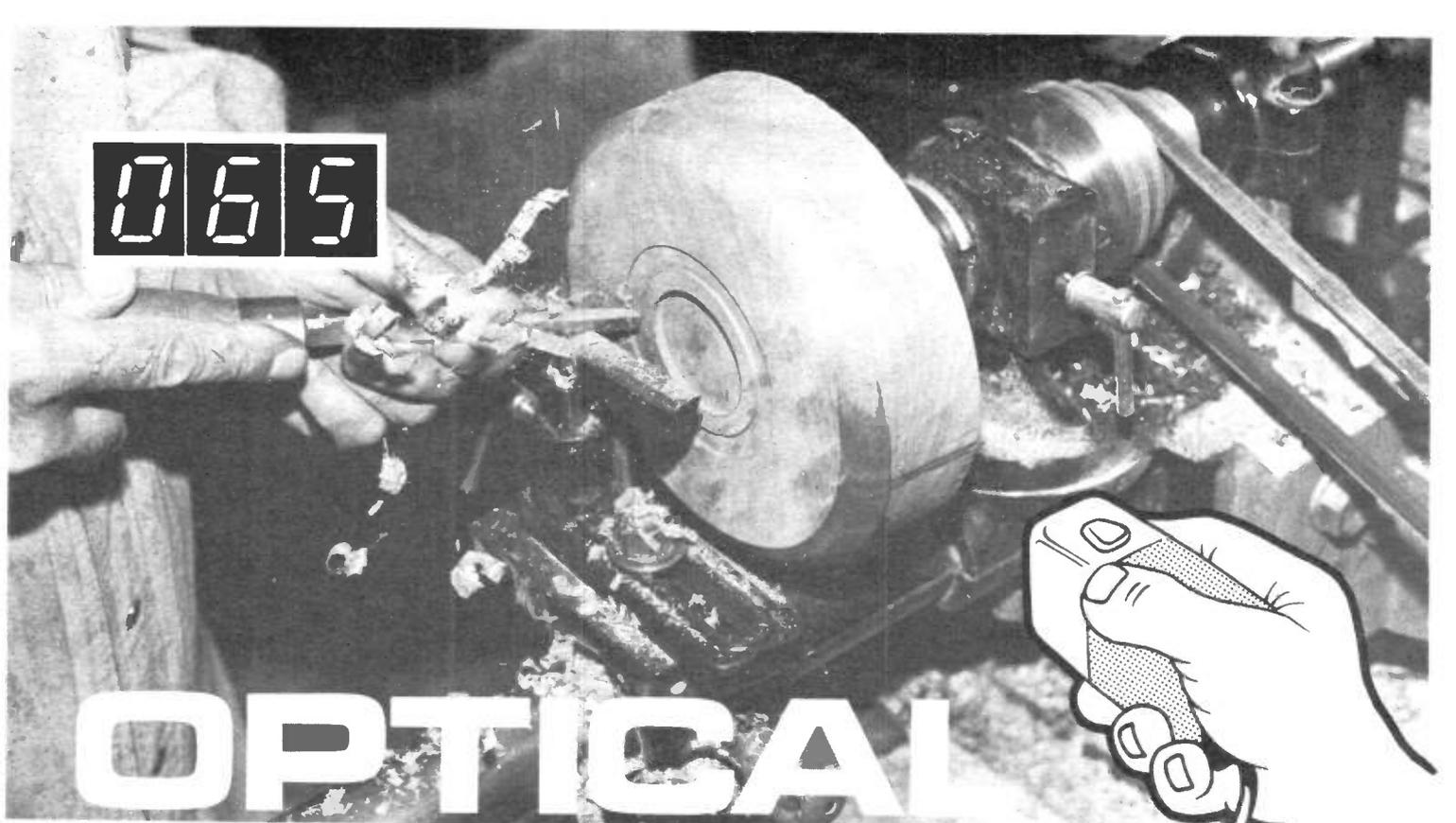**SCHOOLS ELECTRONIC DESIGN AWARD COMPETITION (SEDAC)  
SPONSORED BY MULLARD LTD AND EVERYDAY ELECTRONICS**





065

# OPTICAL TACHOMETER

by P.H. Leah

**O**PTICAL Tachometers have the advantage of measuring the number of revolutions per minute (r.p.m.) of any rotating object, such as a wheel, disc or shaft, without having to make actual physical contact with it.

By placing a reflective mark (a piece of white tape or a chalk mark, for example) on the rotating surface and holding the Tachometer detector in close proximity, an accurate reading of the number of times the mark passes the detector is obtained. The detector generates a pulse for every revolution of the object.

In the Optical Tachometer described here, the time between successive pulses from the detector is measured and digitally converted to read revolutions per minute on a numerical display. The display holds the measurement for approximately three seconds and is then reset before the measurement is retaken.

Two ranges are included, 400 to 5,000 r.p.m. and 4,000 to 25,000 r.p.m. each with an accuracy of 5 per cent.

## PRINCIPLE OF OPERATION

With reference to the block diagram given in Fig. 1, the photodiode detector "detects" a difference in reflected light intensity from the rotating disc, each time the mark passes it. A lamp in the detector provides a local light source. The photodiode output is amplified to produce a pulse for each revolution.

Conventional frequency measurement techniques of counting incoming pulses over a known time period cannot be used for determining the relatively slow time periods of mechanical rotations. The measurement of a wheel rotating at 3,000 r.p.m. would take at least 10 seconds to obtain an accurate reading. Lower speeds of rotation would take even longer.

So consequently a novel but simple measurement and conversion technique is employed in this Tachometer.


The main unit measures the time interval between three successive out-pulses from the detector (that is, two

revolutions). So, assuming the detector is picking up pulses from a wheel rotating at 1,200 r.p.m., for example, this time interval will be 100 milliseconds (1,200 r.p.m. = 20 revs/sec, therefore on revolution takes 50 milliseconds).

A counter (A) is enabled for this period, whilst being clocked by a 833Hz clock. Hence 83 clock pulses will be counted and stored in binary form. This count of 83 presets another counter (B), and exactly 10,000 clock pulses are passed to this pre-settable counter.

The output pulses from the second counter (B), equal to  $10,000/83=120$ ,

Fig. 1. Block diagram of the Optical Tachometer.

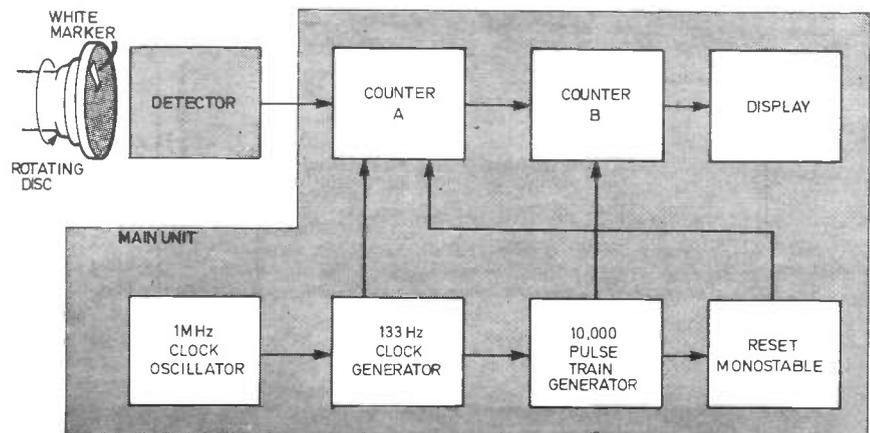

are then counted by a three digit binary coded decimal counter and displayed on a digital readout. As only three digits are used for the display, a multiplication factor of 10 must be applied to the display to give the correct reading of 1,200 r.p.m.

A basic clock frequency of 8.33kHz is used for the higher range measurements (4,000 to 25,000 r.p.m.) therefore a multiplication factor of 100 must be applied to the display reading.

### DETECTOR CIRCUIT

The detector circuit, shown in Fig. 2, comprises of two operational amplifiers in series. IC12, a CA3240 dual op-amp was selected for the detector for its relatively low noise and high impedance f.e.t. input.

IC12a is connected as a simple amplifier to amplify the variation in reverse leakage current through the photodiode, D1. The greater the intensity of light falling on the diode, the greater the reverse current through it will be. R13 provides additional bias current in order to ensure the output voltage of IC12a remains within the active region of the amplifier, even under extreme conditions of illumination. R17 is the feedback resistor for IC12a.

Under artificial light conditions, the output of IC12a at pin 1 will be about 2V and will change to approximately 1V by placing a cover over D1.

The output of the first op-amp is connected via R18 and R19 to the inputs of IC12b. This op-amp is wired with positive feedback by connecting the output at pin 7 to the positive input, pin 5, via R20. This feedback ensures that the amplifier output switches between the supply rails,  $V_{DD}$  and  $V_{SS}$ . It also means that the output switches between these two states at a very small difference in the input voltage, and will remain in that state.

As R18 and R19 are equal values, the current flowing into pins 5 and 6

Complete Optical Tachometer Unit



## COMPONENTS

### Resistors

R1	4.7k $\Omega$	R13	1.5M $\Omega$
R2	3.3k $\Omega$	R14,15	2.2k $\Omega$ (2 off)
R3	100k $\Omega$	R16,17,20	1M $\Omega$ (3 off)
R4-10	680 $\mu\Omega$ (7 off)	R18,19	20k $\Omega$ (2 off)
R11	100k $\Omega$	R21	390 $\Omega$
R12	1k $\Omega$	R22	150 $\Omega$

All  $\frac{1}{4}$ W carbon film  $\pm 5\%$

### Capacitors

C1	68pF polystyrene
C2	10 $\mu\text{F}$ , 10V elect.
C3	1,500pF ceramic
C4,5	47 $\mu\text{F}$ , 6.3V tantalum (2 off)
C6	1,000pF ceramic
C7,8,9	0.01 $\mu\text{F}$ ceramic (3 off)
C10	1,000 $\mu\text{F}$ 25V elect.


### Semiconductors

D1	Photodiode IPL 33 (equivalent to RS 305 462)
D2,3	1N4002 silicon rectifier (2 off)
TR1,2,3	2N3702 silicon <i>npn</i> (3 off)
TR4	BC109 silicon <i>npn</i>
IC1	4001B CMOS quad 2-input NOR gate
IC2,3	4520B CMOS dual 4-bit binary counter (2 off)
IC4	40103B CMOS 8-stage presettable down counter
IC5	4553B CMOS 3-digit b.c.d. counter
IC6	4511B CMOS b.c.d. to 7-segment driver/decoder
IC7,10	4011B CMOS quad 2-input NAND gate (2 off)
IC8,9,11	4518B CMOS dual b.c.d. counter (3 off)
IC12	CA3240 dual f.e.t. op-amp
IC13	7805 5V, 1A regulator
X1-3	DL704 0.3in. high 7-segment, common cathode display (3 off)

### Miscellaneous

S1	s.p.d.t. miniature toggle
S2	s.p.s.t. miniature toggle
VR1	1k $\Omega$ miniature horizontal preset
T1	miniature mains transformer, 9.0-9V, 0.5A secondary
LP1	12V, 0.5W filament lamp

Single sided p.c.b. 128 x 128mm and 75 x 28mm (2 pieces); 0.1in. matrix stripboard, 26 strips by 20 holes; console type case, 220 x 174 x 100mm (Vero type no. 202-21032D); pocket torch; 16 pin d.i.l. holder (9 off); 14 pin d.i.l. holder (3 off); 8 pin d.i.l. holder; lamp holder (2 off); red display filter 25 x 65mm; twin screened cable; mains cable; 7/0.2mm equipment wire; M2.5 or 6BA screw, 25mm long (4 off); M2.5 or 6BA nut (8 off); M2.5 or 6BA nylon nut (4 off); transformer mounting hardware.

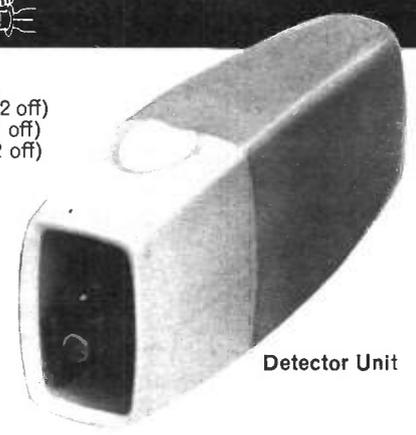

Detector Unit


See  
**Shop  
Talk**  
page 635

**COMPONENTS**  
approximate  
cost **£29.80**  
excluding case

of IC12b will be identical. However, an additional current will flow into pin 5 via the feedback resistor, R20. Hence, if the output is at  $V_{DD}$ , pin 5 will be positive with respect to pin 6.

A sudden change in light intensity falling on D1 will cause a rapid drop in voltage at pin 1, the output of IC12a. This fall in voltage will simultaneously appear at pin 5 of IC12b

Fig. 2. Circuit diagram of the detector unit. Photodiode D1 is an IPL 33.

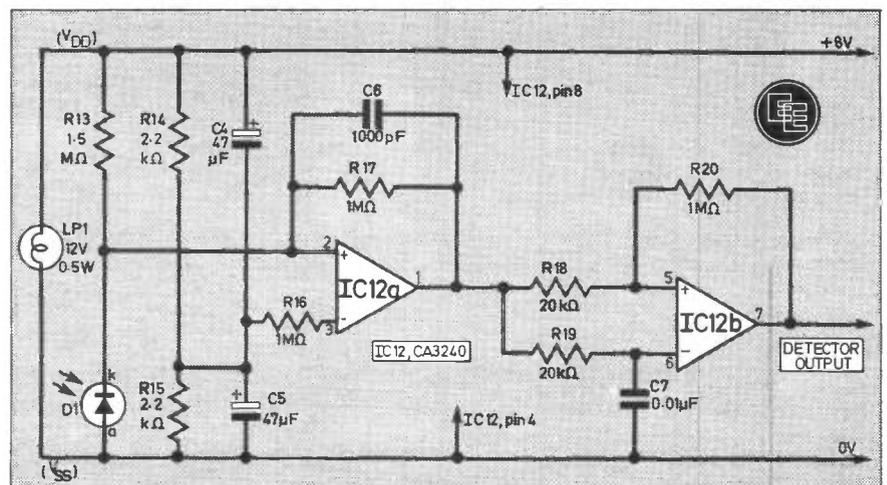

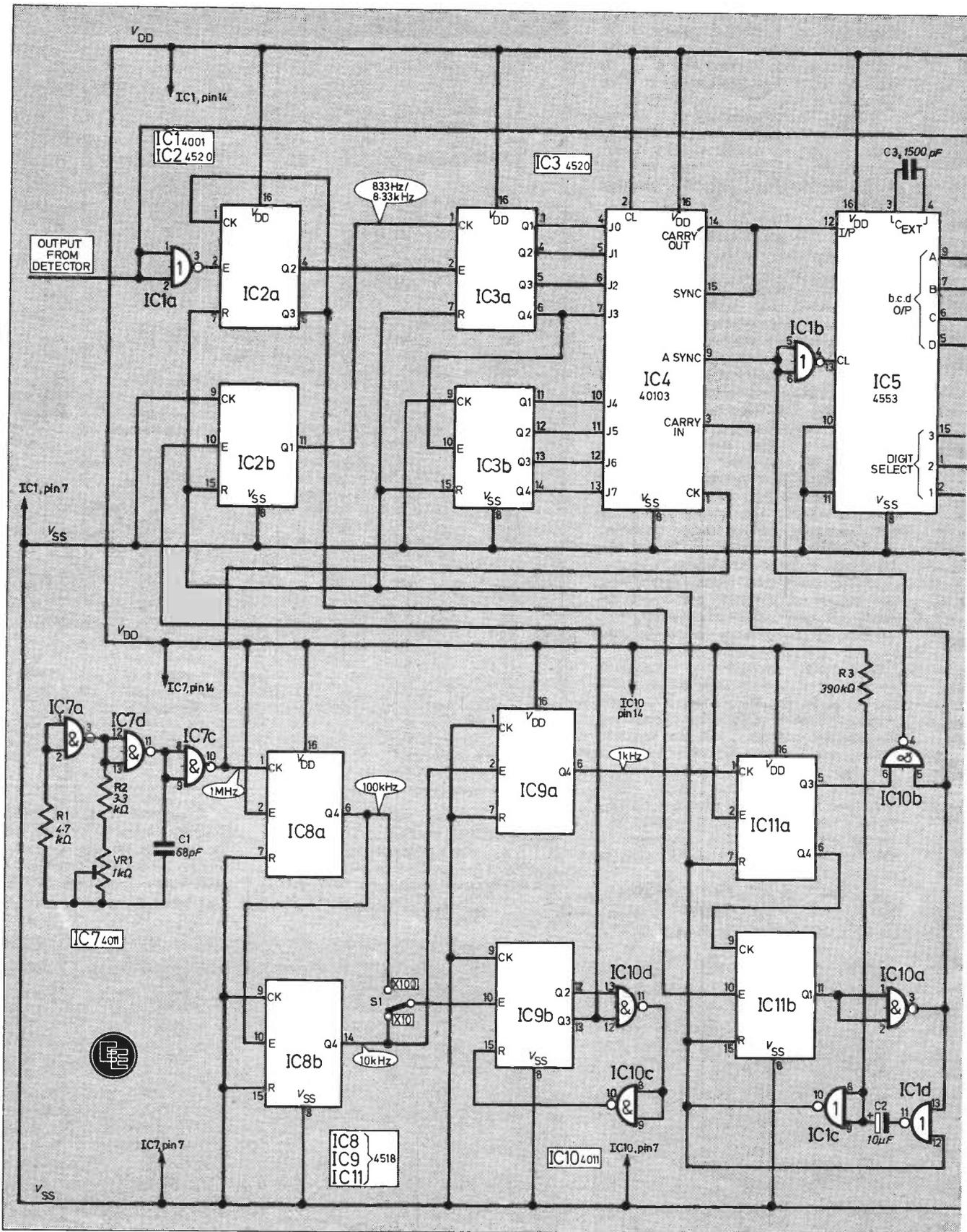


Fig. 3. Circuit diagram of the Optical Tachometer main unit. Frequencies quoted are for use when setting-up and fault-finding.



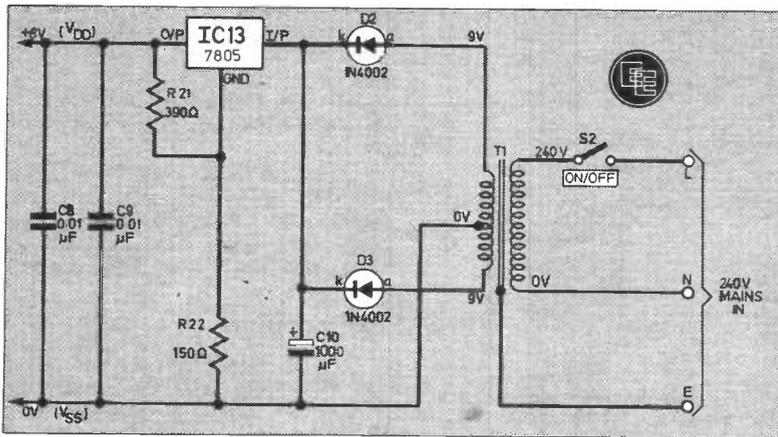


Fig. 4. Circuit diagram of the power supply section. C8 and C9 are decoupling capacitors and are placed on the main unit p.c.b. close to the i.c.s.

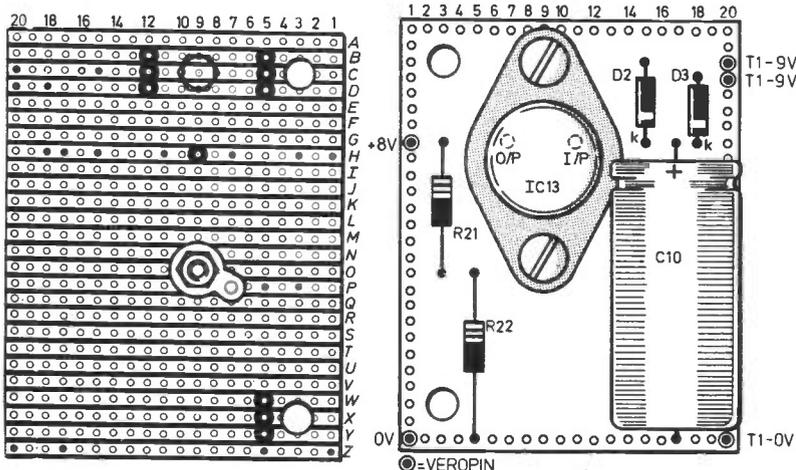


Fig. 5. Power supply stripboard layout. Note that the solder tag on the underside must be soldered to track P. The regulator, IC13, used by the author is the larger TO3 device (shown here), however, the smaller 7805 (TO220) type can be used with suitable track modifications.

to power the Optical Tachometer from a 9V battery. However the author utilised a regulated mains power supply, the circuit of which is shown in Fig. 4.

The full wave rectified output from the 9-0-9V centre tapped transformer T1 is about 12V. This is smoothed by reservoir capacitor C10 before it is connected to the regulator IC13. This regulator, although a 5V type, has the output effectively boosted to 8V with R21 and R22 without loss of regulation.

C8 and C9 are supply decoupling capacitors to suppress any noise on the supply rail. These are particularly important for counting circuits.



## PRINTED CIRCUIT BOARDS

With the exception of the power supply, the prototype was laid out on two printed circuit boards. The component layout and track pattern artwork of the detector circuit p.c.b. is shown in Fig. 7 and the component layout and track pattern artwork of the counter p.c.b. is shown in Figs. 6 and 8. Both printed circuit boards are shown full size and all holes are 1mm, except for the board mounting holes which are 3mm.

Particular care should be taken in placing the CMOS devices on the counter p.c.b. as the orientation of the i.c.s vary. This was necessary to aid the track layout. Also, a number of wired links are necessary on this circuit board as cross-overs could not be avoided. The use of low profile i.c. sockets is recommended, or Soldercon pins, so that i.c.s. may be removed without damage to the board.

Regarding the detector circuit board, both the photodiode, D1, and the 12V bulb, LP1, were mounted in bulb holders which were glued with epoxy resin (such as Araldite) to the p.c.b. It is essential that the diode is mounted slightly forward of the 12V bulb so that direct light does not impinge directly on the diode. Also, the diode should just extend beyond the detector printed circuit board.

## MECHANICAL ASSEMBLY

The detector printed circuit board was designed to push fit into a pocket size torch, once the bulb, reflector and switch mechanism had been removed. It is held in place using a padding of foam rubber at the bottom of the

Counter IC11b is enabled only after the fifth pulse from the detector is counted by IC2a, and the output at pin 11 of IC11b is a 50Hz signal having an equal mark to space ratio. Hence a logic 1 (high) appears for exactly 10ms, the time it takes for 10,000 pulses from the 1MHz oscillator to be counted. Thus the 10ms pulse enables IC4 whilst the 1MHz oscillator clocks IC4.

The resulting pulse train from pins 14 and 15 of IC4 is clocked into IC5, a CMOS three digit b.c.d. counter, to be counted and displayed.

The falling edge of the 10ms enable pulse activates the reset monostable comprising of NOR gates IC1c and IC1d. The resulting reset pulse of approximately three seconds duration, resets IC2, IC3 and IC11, thus inhibiting further counting during those three seconds.

After the rest period, a further measurement will commence.

## DISPLAY

IC5 provides a binary coded decimal, three digit multiplexed display. The b.c.d. outputs are connected to IC6, a CMOS b.c.d. to seven segment driver/decoder which drives the displays X1 to X3 via current limiting resistors R4 to R10.

The digit driver transistors TR1 to TR3 operate directly from the multiplexed digit select outputs of IC5 to switch on the displays as appropriate (at a rate faster than the eye can detect).

The decimal points of all the digits are commoned to provide an indication that a pulse is being received from the detector. They are driven by TR4. If the decimal points fail to illuminate it shows that no pulses are reaching the main circuit.

## POWER SUPPLY

As the unit only requires about 180mA at 8V d.c. it would be possible

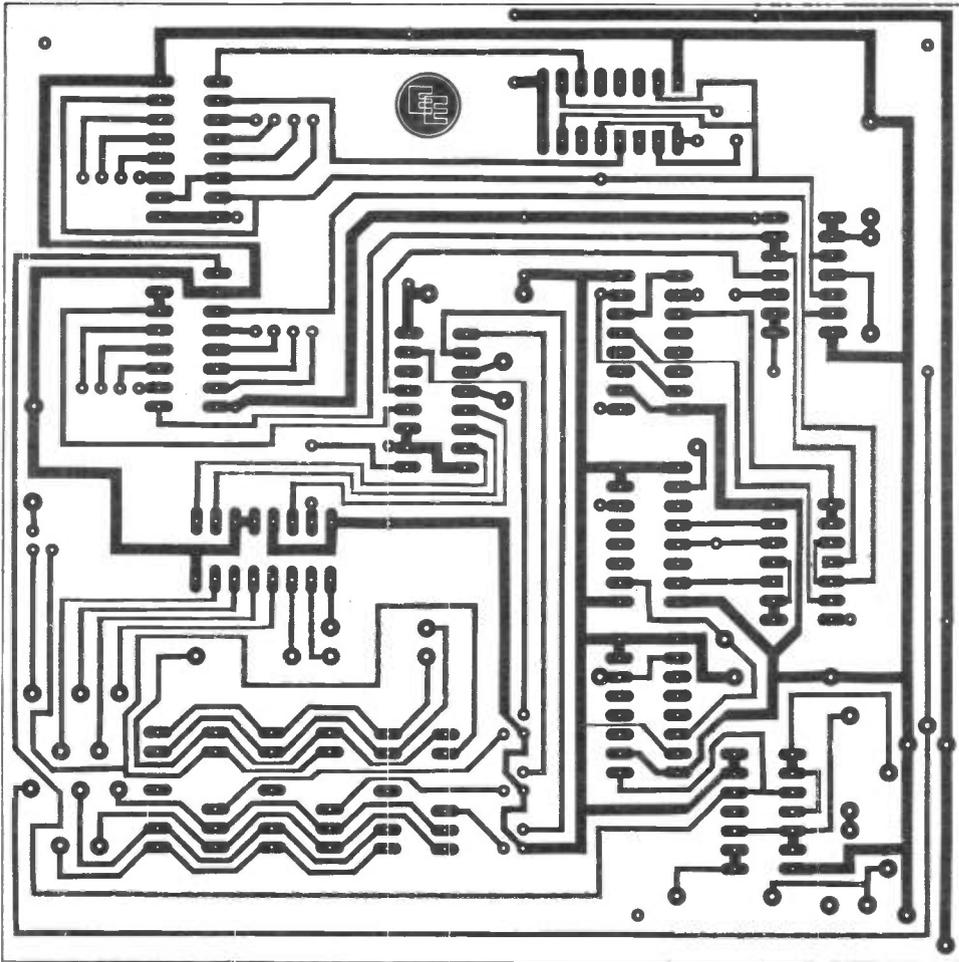


Fig. 6. Full size p.c.b. track pattern for the main unit.

torch such that the photodiode touches the clear plastic cover of the torch. Therefore light from the bulb will not reflect off the clear plastic onto the photodiode. The flexible screened cable carrying the power supply and detector output, enters the torch through a hole in the base of the torch.



The power supply and counter p.c.b. were mounted in a Vero console type Instrument Case. As the display circuit is mounted on the main p.c.b., the complete board is attached to the lid of the Instrument Case using the three mounting holes drilled in the p.c.b.

A rectangular hole 35×13mm needs to be cut into the case lid for the display, and should be backed by a red display filter glued to the lid, to emphasise the digits. Three holes for the range switch, the on-off switch and the detector cable must also be drilled.

The power supply was mounted on 0.1mm matrix stripboard as shown in Fig. 5, which was attached to the base of the Instrument Case using the threaded holes already provided in the case. If mains power is chosen, a further hole must be drilled in the Instrument Case for the Mains Cable.
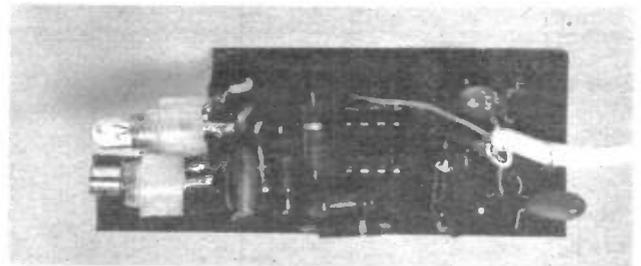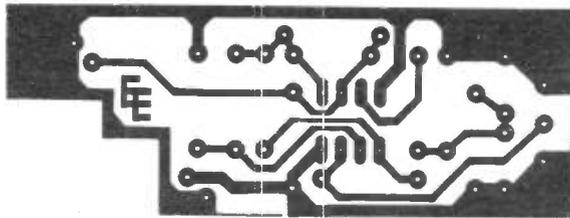
#### TESTING AND SET-UP

Testing and setting up the Instrument is greatly simplified if an oscilloscope is available, but can be accomplished using a voltmeter. Only the 1MHz oscillator needs to be accurately set up by adjusting VR1. This can either be achieved by monitoring IC7c pin 10 and adjusting VR1 until a 1MHz reading is obtained, or by pointing the detector directly at, and in close proximity to, a mains operated lamp.



Detector p.c.b. (above) and power supply wiring (below)


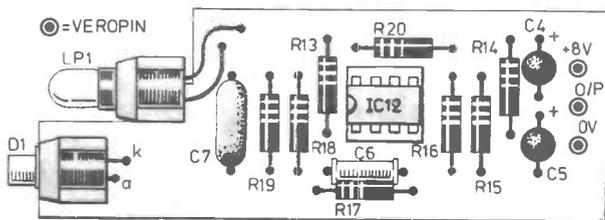


Fig. 7. Full size p.c.b. track pattern and component layout for the detector unit. Note that both LP1 and D1 use lampholders glued to the board.

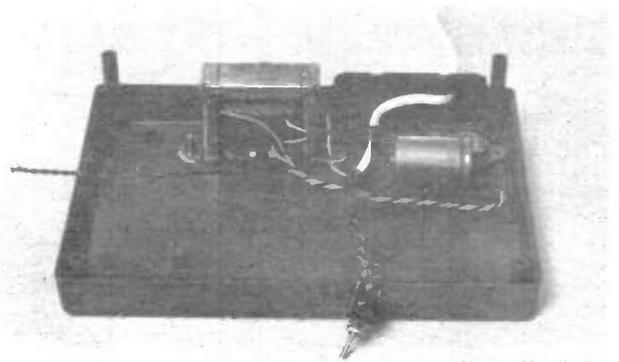

A normal tungsten filament lamp will suffice, and with the Instrument set on its high range, VR1 should be adjusted until a reading of 6,000 r.p.m. (that is a display of 60) is observed.

It should be noted that a 50Hz mains supply provides 3,000 cycles per second. During each cycle, two peaks of intensity are obtained, one of the negative going half and one on the positive going half of each cycle. Hence a reading of 6,000 r.p.m. is detected rather than 3,000 r.p.m.


Having set up the Instrument, it can be tested at relatively low speeds switching it to the lower range and moving a white card about 12mm in front of the detector. Do not point the detector directly at an artificial light during this test. The three decimal points on the LED display should be illuminated during the period that the card is directly over the detector, and should not be illuminated when the card is moved away.

If the card is rapidly moved across the detector at a regular rate, a reading of around 50 (that is, 500 r.p.m.) should be displayed by the Instrument. Although this test does not utilise all aspects of the Instrument, it proves that the logic and the detector is functioning correctly.
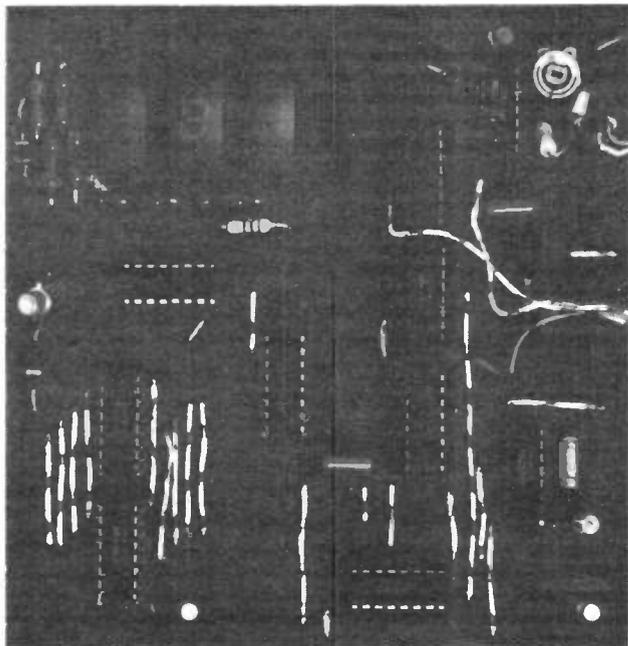
## FAULT FINDING

There is unfortunately no easy method of fault finding if the Instrument fails to operate correctly, and it is a case of laboriously plodding through the circuitry. Here an oscilloscope is essential.

Check for the obvious things first, such as ensuring that the supply voltage has not fallen below 8V. Then



Main unit p.c.b. from the prototype Optical Tachometer. Note the use of sleeved wires for the on-board links to prevent short circuits. The power wires (top right) are connected to the power supply board and the three wires to S1 go straight to the range switch on the front panel.

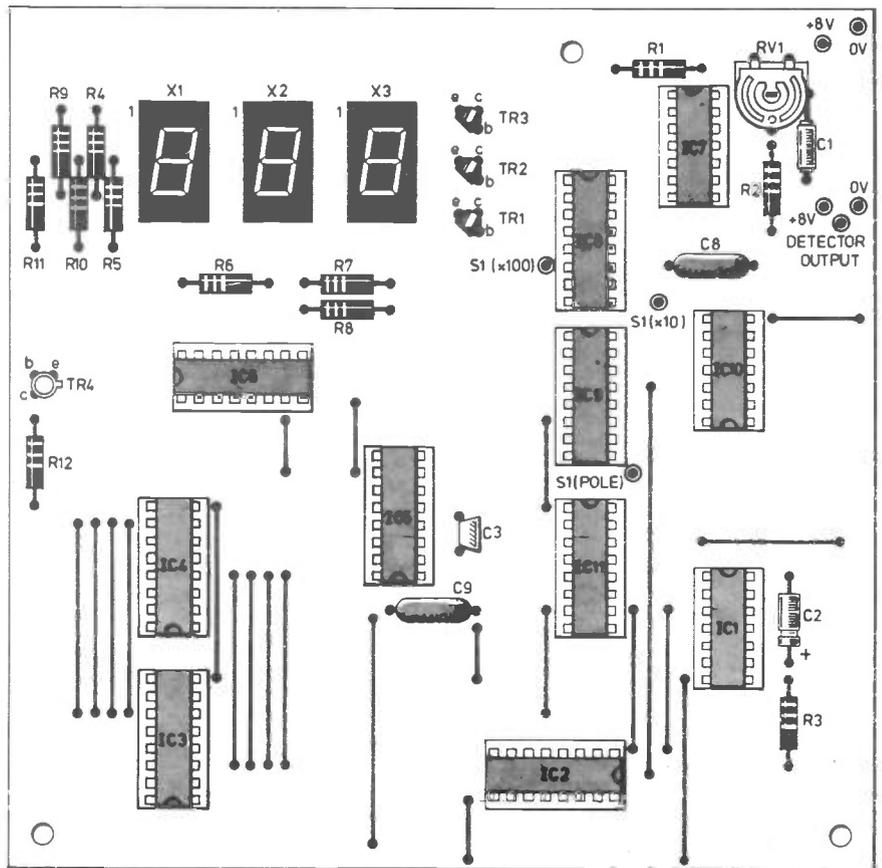


Fig. 8. Component layout for the Optical Tachometer main unit. Connection to the detector is made via a twin-cored screened cable, the screen forming the 0V line.

check that the 1MHz oscillator is operating correctly and that 100Hz is available at IC11 pin 6 while 833Hz is available at pin 11 IC2.

Next identify whether the detector is operating correctly by monitoring the output voltage at IC12 pin 7. This should switch between the Supply Rails as the difference in reflected light is detected.

If all is correct so far, then the conversion or display circuits must be at fault. However, if all digits are displaying something, even if it is all zeros it indicates the display circuit is operating correctly and therefore the control circuitry may be faulty.

When fault finding in CMOS circuits the low logic level should be at 0V while the high level logic state should be 8V. However, any voltage below 3.5V will appear as a low logic state while any voltage in excess of 4.5V will appear as the high voltage state to the input of a CMOS device.

## ACCURACY

As a digital method of calculating the rotations speed is employed, a quantisation error is introduced. This error is greatest at the high end of the ranges where it is approximately five per cent, whereas the error at the lower end of the scale is only one per cent. Further, the quantisation levels become more apparent at the higher end of the ranges.

For instance, when measuring a rotational speed of approximately 4,000 r.p.m. on the low range, readings of either 384, 400 or 416 will be displayed. There will be no intermediate readings. However, on the higher range, readings of either 40, 41, or 42 will be obtained.

## PRACTICAL CONSIDERATIONS

As explained previously, the detector picks up differences in light intensity which impinge directly on the photodiode. It is also very sensitive. False readings will result when using the instrument if an external light source, such as an electric light, shines directly on the photodiode. Also false readings will result if the rotating object produces more than

one change in reflected light intensity during each revolution.

Most metal objects will reflect light continuously but at fluctuating levels during each revolution, which makes a regular output pulse from the detector difficult to obtain.

Under such circumstances, it may be necessary to place a matt surfaced sticking tape or masking tape over the complete circumference of the metal shaft, and make a small mark. A contrasting colour to that of the sticking tape should be used. Hence a relatively even reflection will be obtained during most of each revolution, but a different reflection will be obtained when the marked surface is directly under the detector head.

Where possible the rotating object should be revolved slowly at first to

ensure that the detector is operating correctly. The decimal points on the display should all illuminate and switch off during each revolution.

If the speed of rotation of the revolving object is outside the range of the instrument, spurious readings will be displayed, particularly at the low end of the scales.

Finally, as a point of interest, the following speeds of rotation were measured from a few common household items, when used at constant speeds: hand drill 500r.p.m.; electric power drill 2,700 r.p.m.; electric toy racing car 7,000r.p.m.

Note that the speed of an electric power drill quoted by the manufacturer is the minimum speed when on load. Off load the drill will run faster. □

# COUNTER INTELLIGENCE

By PAUL YOUNG

## Component Guide for Neophytes

Although we know that new readers join us all the year round, it is reasonable to assume that a greater influx of neophytes occurs during the Autumn and Winter. On that assumption I usually write a few words of a didactic nature on the subject of obtaining supplies.

Before commencing any design make sure that all the parts required are freely available. Any items that are special are dealt with under the *Shop Talk* banner.

This still leaves the run of the mill components, such as, resistors, capacitors, and potentiometers. You may be lucky enough to have a good supplier near at hand. If you have you are a lucky person. Most of us are obliged to resort to Mail Order suppliers. Luckily there are plenty to choose from, as will be seen from the advertisements.

The next point I must emphasise, is that the field of electronics is now so vast that most retailers can only deal with a small segment of it. Therefore to get all your requirements you will have to deal with at least two or three.

My advice is this: first of all obtain three or four catalogues and study them carefully. Next, make a few notes on the prices and availability of parts. To avoid disappointment, plan well ahead, in other words, start collecting all the bits you need for your second project before you have finished the first.

Always help your supplier to help you, for example, if he encloses an order form make sure you use it. Write your name and address clearly, and if like me you have an illegible scrawl, either type it, or print it in block capitals.

Never put queries on the bottom of your order form, because it will probably delay the delivery of your goods. We always try and be helpful in replying to queries, but we do expect them to relate to the goods we stock. Today postage is an expensive item so always make sure you enclose a stamped addressed envelope.

One tip that most readers quickly discover for themselves, is the advantage of hanging on to the bits and pieces you

don't use and to build up that ubiquitous Junk Box. One friend of mine used to beg an old un-wanted television chassis off the local repair man and then proceed to strip off all the useful pieces. It cost him nothing except his time, it gave him plenty of practice in de-soldering and he could set himself up for the season in potentiometers, resistors, capacitors and some transistors and I.C.s.

## Electrohyper

The other day I was walking round what is called a "Hypermarket" which is an outsize Supermarket when it struck me that they sold everything, well nearly everything. The only omission, and I have no doubt that you have already guessed what it is, Electronic Components, but who knows, one day that gap may be filled—just think what that would mean, while Mum buys the groceries, Dad can sneak off to buy his goodies.

The nearest thing I have seen to this, is a self service component store in Paris called Radio Prem. Even here, items that were very small and very expensive, had to be purchased at the counter, for obvious reasons.

## Friendly CB

I am still stumbling on articles on CB Radio in the most unlikely places. The latest is in a publication called, *The*

*Home and Freezer Digest* (July 1982). I must say it was most interesting, being mainly a series of letters from readers saying how CB had changed their lives.

There are now a large number of CB Clubs and one of their exercises is called a *Fox Hunt*, where one member with a mobile rig drives on ahead and the rest try and track him down by his broadcasts. It sounds to me like a lot of fun!

I would like to include a short quote from one of the letters which seems to me significant. "I do not know whether CB attracts good people, or whether becoming a 'Breaker' makes you into a very helpful person.

"Last night in a gale, two breaker friends in a particularly isolated spot came on channel; some tiles had blown off their roof—I know for a fact that a couple of other breakers are round there now fixing it for them." This seems to be a recurring theme in the use of CB and it is a nice thought in a naughty world.

## Hypnotic Young

I must relate to you how Paul Young was brought down a peg or two. The other night I was speaking to a colleague on the phone when out of the blue he suddenly said "You write that page in EVERYDAY ELECTRONICS don't you?" "Well yes I do, do you like it?" "Yes I do, I always read it going home in the train, it sends me to sleep." Collapse of P.Y.



## EDITORIAL VACANCY

Excellent career opportunity for electronics enthusiast. EVERYDAY ELECTRONICS invites applications from persons between 20 and 30 years of age, having sound technical knowledge and some practical experience in building electronic circuits. Also essential is a good standard in English and ability to write clearly on technical matters. (Appropriate journalistic training will be given to successful candidate.)

Write with brief details of education, professional career and non-vocational experience of electronics. Address application to The Editor, Everyday Electronics, IPC Magazines Ltd, Kings Reach Tower, Stamford Street, London SE1 9LS.

# RADIO WORLD

By Pat Hawker, G3VA

## Made in Britain?

The British government seems convinced that "new technology"—in particular electronics and "information technology"—holds the key to the restoration of the economy and to offsetting the effects of the decline of the traditional industries. Much though one would wish to endorse such sentiments there is relatively little evidence that our electronics industry is in any shape to take the lead. Indeed, it often seems that one of the industries most in need of a revival is consumer electronics.

For about a decade only a tiny minority of domestic and portable radio sets on sale in the UK have actually been designed and built here with British made components. Even though many sets are still marketed with British brand names local production is negligible.

But it is sad when long-established firms find themselves in difficulties. The Rank Organisation has announced that its high-quality loudspeaker "Wharfedale" factory at Bradford is to close.

A firm that under G. A. Briggs did so much to create a public demand for higher quality audio. Gilbert Briggs not only wrote a series of entertaining, widely read and pioneering books on high-fidelity but also took over the Festival Hall in London for a number of memorable lecture demonstrations.

Then again the family business of A. J. Balcombe has gone into voluntary liquidation. It was founded as long ago as 1917 by Alfred Balcombe (hence the brand name "Alba"). As a manufacturer of radio receivers it was never a large firm but it has managed to outlast larger rivals.

## Who remembers?

It is now many years since Mr. E. K. Cole ran "Ekco" the firm that showed that a plastics cabinet could be made attractive by good design. Similarly Mr. Frank Murphy created the almost legendary series of Murphy radios in the 1930s remembered for their exceptionally well-designed wooden cabinets.

Even earlier Mr. Leslie McMichael, a founder member of the Wireless Society of London, was making broadcast receivers. Now McMichael, as a subsidiary of GEC, is back in the broadcast business—but at the capital equipment end making, for example, highly complex television digital standards converters.

Even 25 years ago there were still very many British firms in the radio and television business. Who now remembers the original R.G.D. de luxe models or such names as Etronic, Beethoven, Pilot, Romac, Masteradio, Defiant, Sobell, Ambassador and consumer models by English Electric, Cossor, Philco, Ever Ready . . . Many, many others came and went or were amalgamated into larger concerns or pulled out of the consumer side of electronics.

## The Rising Sun

It must be admitted that the radio and television industry has always been highly competitive and not all the British products were anything special. Over the past two decades much business has been lost to the Far East not on account of "cheap labour" but because of more inspired marketing and manufacturing policies with emphasis on reliability, good production engineering and the building up of an overall brand image rather than concentrating on individual models.

With notable exceptions the bulk of British firms did not go out of their way to win the respect of their customers and, unfortunately, it was often those producing the best sets that were most cavalier in their attitudes. Nor, of course, were they helped in the post-war period by the ever changing "stop-go" credit restrictions.

Others were let down by the component firms who somehow never seemed to acquire the mass-production expertise of the Americans, let alone the Japanese. Quality-assurance and zero-defect production were often talked about—not always implemented.

Before we can hope to gain a "world lead" in new technologies we need to make sure that we can produce basic electronic equipment well. In this respect one must pay tribute to the Thorn group whose "TX" colour television chassis is well thought of not only by André Previn! On the other hand the attempts to marry

British and Japanese techniques at Rank-Toshiba and GEC-Hitachi have not proved notably successful.

## Repairs for the blind

More and more the standard transistor radio set is regarded virtually as a "disposable" item of "throw-away electronics". The High Street radio trade often shows little interest in undertaking repairs and these can often prove uneconomical both to the dealer and the owner.

Often what goes wrong is simple to put right, the cost is the time it takes to trace the fault. This makes it possible for those with plenty of spare time and the necessary skills to undertake a most valuable service on behalf of a group of people particularly dependent on radio—the blind.

For example, a former colleague, a highly professional IBA television transmitter engineer now retired, tells me that he has been keeping busy and happy by repairing radio sets on behalf of his local Association for the Blind, work that appears to be of little or no interest to local dealers. He has so far restored to good working order some 350 sets, sometimes using parts "cannibalised" from those that are beyond repair.

He finds that something like 10 per cent of the sets that pass through his hands can be restored to working order after simply resoldering connections on the printed circuit boards.

## TV Across Frontiers

The problems that have still to be faced before there is genuine international television are highlighted by the efforts of the Dutch Minister of Culture to stop the distribution on the many Dutch cable systems of the pictures received from the Russian *Gorizont* satellite, on the grounds that the USSR has not granted permission to the Dutch cable companies to receive these programmes.

The companies have also been told they must ensure that their systems do not carry the programmes of the 100 or so "cable TV pirates". These firms have developed ways of inserting their programmes into the cable networks after the closedown of normal programmes, often showing tapes of X films and old movies from VCR machines and financed by advertisements from local shopkeepers.

For many years international committees have been earnestly discussing questions relating to "cultural or economic imperialism", the effects of "exposure to outside ideas and lifestyles", the concept of "prior consent" and "participation", the protection of copyright and "intellectual property

rights' and so on—but almost invariably they have been unable to come to any firm decisions.

In the UK it is not possible for a cable operator to distribute any programme channel without the permission of the Home Office. It is still all a very tangled web.

## Walkabout TV

The success of walkabout audio is encouraging a revival of interest in the Dick Tracy concept of wristwatch TV. The Japanese firm of Seiko, well known for their digital watches, are planning to make a watch that also includes a 1.2in diagonal liquid-crystal video display.

The watch will have a thin flexible connection to a pocket unit which not only includes all the TV circuits but also a stereo VHF/FM radio and headphone socket. It is claimed the television display will be sufficiently clear as to permit the reading of graphics material and to see ball games.

In Japan the 525-line version will sell for under £200. So it will soon be walkabout TV.



# ELECTRONIC HOBBIES FAIR

Alexandra Pavilion London November 18 – 21 1982

**The biggest and best event ever to be staged for the electronic hobbies enthusiast!**

Walk into a whole world of electronic equipment. – Everything from resistors, IC's to home computers, transmitting and receiving units, citizens band radio and peripheral equipment, video games, musical instruments, radio control models. . . In fact whatever your particular electronic hobby you'll find this show will be the most interesting and informative way to discover all the latest developments in your particular field.

Other attractions will include radio and TV transmission, electric vehicles, radio controlled models, and demonstrations by local and national organisations.

This is the age of the train – British Rail are offering a cheap rate rail fare from all major

stations in the country direct to Alexandra Palace – a bus will be waiting on your arrival to take you to the show. Ticket price also includes admission to the exhibition – so let the train take the strain to the Electronic Hobbies Fair.

Ticket prices at the door are £2 for adults, £1 for children but party rates are available for 20 people or more. To find out more, contact the Exhibition Manager, Electronic Hobbies Fair, IPC Exhibitions, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 400. Tel: 01-643 8040.

Electronic Hobbies Fair is sponsored by Practical Electronics, Everyday Electronics and Practical Wireless and is organised by IPC Exhibitions Ltd.

#### OPENING TIMES

Thursday 18 Nov. – 10.00-18.00

Friday 19 Nov. – 10.00-18.00

Saturday 20 Nov. – 10.00-18.00

Sunday 21 Nov. – 10.00-17.00



## 50p OFF

admission if you produce this coupon at the door of Electronic Hobbies Fair. Valid one per person only any day.

EE1

# Everyday News



## A STAR IS BORN

*A new computer language from a new firm*

HAVING been deeply involved in the development work for the now famous Sinclair ZX81 and Spectrum home computers, Richard Altwasser and Steven Vickers have joined the ranks of the new wave of entrepreneurs and formed a new British company called Jupiter Cantab to exploit their ideas in the computing field.

Their first offering to the home computer market is the Jupiter Ace. It features full-size moving keyboard, user-defined high resolution graphics and sound.

The Ace is set apart from other personal computers in that it uses a new high-speed programming language called FORTH. The claim for FORTH is that it is as equally easy for humans to understand as computers.

Richard and Stephen discovered FORTH at the same time and immediately recognised it as the ideal language for microcomputers.


They claim that FORTH is both fast and compact because it is compiled, yet its compiled code is accessible to the user in the simplest way imaginable. You give each compiled routine a name, a FORTH "word", and to run it you just type in the word.

By stringing old words together you can define new words. This process lies at the root of FORTH's power and enables the user, starting from the standard words

provided in the firmware, to define an infinite variety of your own words.

The machine is available only by mail order for an all-inclusive price of £89.95 from Jupiter Cantab Ltd., Dept EE, 22 Foxhollow, Bar Hill, Cambridge CB3 8EP. For your money you receive the Ace home computer, mains adaptor, leads to connect to most cassette recorders and black and white or colour TV's, a software catalogue and an instruction manual.

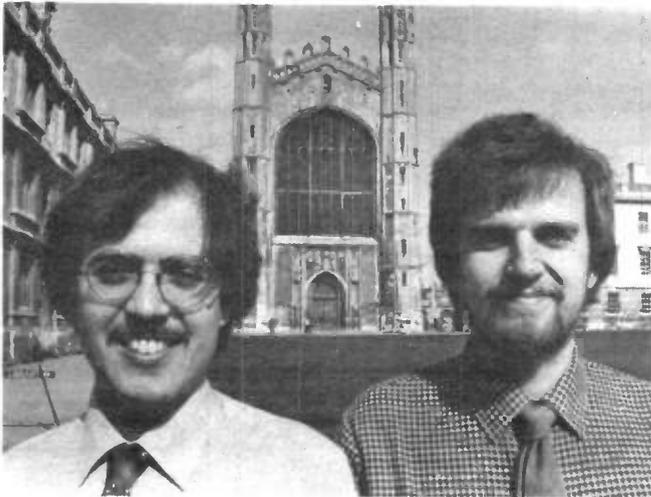We understand that a colour board to plug into the back of the machine is currently under final development.



### Message from Busby

*Is British Telecom unhappy at the Government's intention at selling its 51 per cent holding and establishing a public limited company? This seems evident from some of the comments released by BT.*

"This is, of course, a matter for Government and Parliament. The Board has not been consulted about this decision, but the Secretary of State has now promised the fullest consultation with the Board on the development and implementation of his proposals.

"Until detailed proposals have been made known, and there has been an opportunity to consider them, the Board cannot express any general view on the proposals. . . . The proposals clearly raise issues beyond the establishment of British Telecom as a public limited company and will have far reaching consequences for the whole of telecommunication in the UK.

"The Board is concerned that a regulatory regime should not unfairly fetter British Telecom or frustrate the commercial enterprise that BT has already shown in response to competition.

"The Board can say at this stage, however, that given the right conditions it would welcome freedom from what the Secretary of State has described as the web of Government control and interference."

### Soft Centre

Britain's strength in software engineering was confirmed with the opening of a £7 million facility at Pine-wood, Wokingham, by Hewlett-Packard.

It will be the company's world-wide development

centre for office systems and Britain was chosen, said David Packard at the opening, because the country has the reputation for producing some of the world's finest software engineers.

### Communications Crisis

*"A massive effort to thwart any meaningful action," on the liberalisation of telecommunications, is the conclusion of a document, "The Report of the Communications Crisis Committee."*

The document is a joint effort by a number of associations and companies in the communications industry who have invested money as a result of the Government's pledge of liberalisation in telecommunications.

In conclusion the report goes on to say: "Unless action is effectively taken immediately, the UK future in Information Technology and Telecommunications will be ruined and the very business and enterprise we need, will be killed off.—Action Now!"



## ANALYSIS

### INTELLIGENCE

The word "intelligence" signifies sagacity and understanding. It also means information gathered openly or, in a more sinister sense, secretly. Both definitions have come into neat conjunction through allegations that two famous Japanese companies have unlawfully conspired to discover trade secrets of IBM, which doubtless include progress on fifth generation computers embodying artificial intelligence—the thinking computer.

Thinking systems are not exactly new. In the pre-electronic age the centrifugal governor provided constant speed control of a steam engine under varying load by mechanical linkage feedback to the steam inlet valve. Fifty years ago the simple electrical thermostat in a closed loop system was maintaining temperature at a constant pre-set level. Both were primitive examples of built-in "intelligence".

What is new is the extra versatility afforded by cheap computing power. The *Temperature Interface For The TRS-80* described in the Aug-Sept '82 issues of EE is an example of how a basically simple sensing device can have its utility enhanced by a computer.

Just as the image of robots conjures up frightening visions of mechanical supremacy over man, so the idea of artificial intelligence implies an intellectual superiority equally disturbing. Computer programs have been developed which can challenge even Grand Masters at chess but the programs were developed by humans. So do we need to worry?

That we do worry is indicated by the introduction of "friendly" systems, the terminal which greets you with a "good morning" and is polite when pointing out you have made an input error. Another indication is that enhancement of today's docile obedient systems into possibly active thinking ones for specialised tasks, i.e. the addition of artificial intelligence, is now coming to be described as "expert systems", a less disturbing phrase. Such subtle changes are supposed to make us feel more comfortable in the presence of powerful machines.

Expert systems will be both powerful and friendly and will seem to have intelligence. They will do a lot more, faster, better, more conveniently and economically than at present. But, broken down into small subsystems, each will be found to be simple in principle and function and only cleverly interfaced (and by humans!) to make an "intelligent" whole. They will be a valuable aid in assisting human thought and action but need never dominate mankind.

Brian G. Peck

### Courses ...

Two short courses on ergonomics and computer systems, one for commercial organisations and one for the process industries, are being organised by HUSAT, at Loughborough University of Technology.

"Human Aspects of Computer Systems, designed for commercial organisations, will run from 19 to 24 September 1982 and "Human Aspects of Computer Systems in Process Control, will run from 17 to 22 October 1982.

Further details can be obtained from Rachel Shattock, HUSAT, Dept of Human Sciences University of Technology, The Elms, Elms Grove, Loughborough, Leics, LE11 1RG.

An evening course designed to prepare students for the Radio Amateur Examination in May/June 1983 is to be run by the Newcastle upon Tyne at the Gosforth Secondary School, Gosforth, commencing in September.

Held on Tuesdays of each week from 7pm to 9pm. Enquiries should be addressed to The Principal, Gosforth Adult Association, Gosforth Secondary School, Gosforth, Newcastle upon Tyne. Tel. N-U-T 668439.

**Prism Microproducts of Islington, London, is shortly to begin selling the Sinclair ZX81, as a wholesaler, through High Street computer stores.**

**Sinclair Research have also announced that the ZX81 is to be available from Boots and Greens as well as the usual W. H. Smiths outlets.**

The Southern Centre of the Royal Television Society, in conjunction with Southampton Technical College, are presenting a course of nine evening lectures during the autumn. The course is designed for the benefit of those interested in the engineering in television studios. Each session will be devoted to the theory and operation of a particular equipment or system.

The course commences on 19 October and applications should be made to: Mr C. Terry, Educational Television Unit, Southampton Technical College, St Mary Street, Southampton SO9 4WX.

**Sinclair ZX81 breaks the £50 barrier for Personal Computers with the announcement that it is now reduced from £69.95 to £49.95 including VAT.**

**Arthur C. Clarke, the science fiction writer and scientific research worker, has won the Marconi International Fellowship Award for 1982.**

### OPPOSITION

*The Post Office Engineering Union is opposing the connection of the private Mercury telephone system, now under construction, to the national networks.*

### School Computing

More than 2,500 primary schools are being assisted by a £9 million government grant to buy microcomputers. This is a new scheme following on that for secondary schools in which it is estimated that all 6,000 now have at least one microcomputer.

### TELEPORT

**A planned satellite communications centre, dubbed Teleport, on Staten Island, New York, will have 17 earth stations with access to 22 domestic satellites.**

**It will be linked to the World Trade Centre complex and other local business communities by fibre optic cable.**

### Reading Aid for the Disabled

An electronic reading aid incorporating the latest in fibre optics has been developed by engineers at Wormald International, a New Zealand company specialising in aids for the disabled.

The aid, called Viewscan, is portable and can be used by the partially sighted at work, school or in the home. It is designed to produce a magnified image of reading material when such material is scanned by a hand-held camera.

A miniature bulb illuminates the page via a high resolution fibre optic ribbon in the camera. The image is transmitted to a photo diode array and the signal from this is fed directly to two microprocessors in the display unit. A buffer memory then reassembles the information into moving lines of print.

The orange display screen, selected for maximum visibility, is a flat neon matrix panel and can be switched easily from a positive to a negative image. Magnification is achieved electronically and there are eight settings from X4 to X64.



# PRESTEL

YOUR PHONE-IN  
TELETEXT

by Cyril Stringer  
G3RSK



**T**HERE are several visual data retrieval services available to the public in this country; the BBC provide CEEFAX whilst ITV provided ORACLE. Claimed to be the most advanced system in the world at the moment is PRESTEL. It was developed at the British Telecom Research Establishment at Martlesham in 1975 during experiments to produce the video phone.

Unlike CEEFAX and ORACLE, both of which provide a one-way information service only, PRESTEL utilises the national telephone line network to provide a two-way data communication service. It is also capable of storing vast amounts of information at regional computer centres with the ability to obtain additional or specialised data from other regional or national centres, if called upon to do so.

## PRESTEL CAPABILITIES

The present PRESTEL system is restricted to that of an Information Provider, but there are several additional fields of service which may be provided to cater for future trends and markets. The five main fields are:

**Information**—The provision of topical/reference information, classified ads and shopping aids. Topical information can be sub-divided to cover such items as news, sports results, weather forecasts and timetables.

Each subject can be further sub-divided; news can be local, national, international, business or financial. This kind of service also forms the basis of CEEFAX and ORACLE.

**Message Communication**—Information is stored and then forwarded by the computer to the called subscriber. Such transmissions are preceded by an audio tone announcement.

This aspect of the service bears a similarity to telex, the main difference being the ability to receive, store and release messages at random, thus easing telex congestion. It will play an important future role in the lives of deaf people who are unable to take advantage of the conventional telephone.

**Education**—PRESTEL can be deployed in three areas of education: As a conventional information service; courses and facilities available, entry qualification requirements.

A learning device to relieve the pressure on teachers and lecturers.

A method of self testing pupils and students. Their work is prepared, marked, and graded—all by computer.

**Calculation Service**—Since there are many cheap but sophisticated calculators on the market, the aim of the calculation service would be a compromise between such machines and the more complex programmable types often beyond the reach of the public.

The effectiveness of such a service lies in the fact that no specialised computer language is required.

**Personal Information**—In the case of personal information, use is made of the two-way communication facility where the user can *insert* data into the computer to be recalled collectively by action groups, committees, industries, or individuals with a commodity to sell or an idea to discuss, but where secrecy of information would not be a prime factor.

With such a vast amount of stored information it is essential that it can be recalled easily whilst being both accurate and constantly updated. This is achieved by a nationwide network of 26 GEC 4082 computers into which data is fed and stored from Government Departments, companies, and special information providers.

There are at least 150 contributors of data information, these include: Currys, Cosmos Air Travel, Data Stream International, The Economist, English Tourist Board, Greater London Council, National Computing Centre and Open University.

## HOW THE SYSTEM WORKS

The standard arrangement of the PRESTEL system is shown in Fig. 1.

The "*Residential Terminal*" consists of a remote keypad connected through an adapted domestic television set to a

standard telephone line which passes through the local Telephone Exchange and Access Unit, into the Viewdata Computer Centre. The telephone handset is only used for the initial call to the local computer centre, all other instructions are carried out by the keypad.

Instead of a keypad, the "*Business Terminal*" uses a full keyboard incorporated in the user's television equipment to facilitate full message transmission over the telephone line network.

The "*Information Provider Editing Terminal*" uses a full message and editing keyboard. This allows the information provider to amend and upgrade data being fed into the computer.

Also fed into the computer centre with the user terminals are Data Information Bases; these provide the source of all stored information, and are separated into two categories: The Public Base, provides business and residential information; and The Private Base, provides company information. Any user has full access to both sources.

A 12-button keypad is the minimum requirement for access to the computer with code designations 0 to 9, ★ (star) and # (square) normally laid out in the internationally agreed format for telephone keypads. Additional command buttons can be provided to meet specific requirements.

The domestic television receiver must also comply with British Telecom standards and incorporate a Barrier Isolation Unit which prevents high voltages inherent in television equipment from being presented to the telephone line, without inhibiting the transmission and reception of speech and data.

The Access Unit provides interface—a common connection—between the user terminal, telephone network, and computer.

At the Viewdata Computer Centre, which can be regional or national, information is released to the user at the rate of 1200 Bits/sec (120 characters per second) so that one page of information is presented within three or four seconds.

By comparison, the user-to-computer signalling rate is only 75 Bits/sec which is more than sufficient to cater for manual keypad commands.

Since it is not possible to send "logic" down a telephone line, the data is converted into two audio frequency tones which represent mark and space levels. At 1200 Bits/sec the mark tone is 1.3kHz and the space tone is 2.1kHz. At 75 Bits/sec the mark tone is 390Hz and the space tone 450Hz.

The tones are generated by oscillators in the transmit-end Modems (modulator/demodulator) and demodulated by an f.m. detector in the receive-end Modem where they are converted into digital information and subsequently into alphagraphics, the now familiar computer screen type characters which can be displayed in seven different colours.

## USING PRESTEL

To make use of PRESTEL, the customer picks up his telephone and dials the local computer centre.

When connection is established the computer returns a 1.3kHz tone which switches the television receiver to the "Data Mode" and advises the computer by a return signal that it is ready to accept data. The telephone receiver is now left at the side of the cradle for the duration of the data transmission.

User identity is then requested by the computer; a 16-digit code number which can be entered by the keypad or

returned automatically. On receipt of the code number the computer releases the first page of data. This is usually Page 0, the Master Index Page.

Page 0 offers headed options numbered 0 to 9. The user keys in the required option number relating to business, home or general interest. A further 10 options are presented and the caller continues to choose options until the desired page of data is obtained. This system is known as the Tree Type Selection Method and is shown in Fig. 2.

Before any page of data is released charges for the page are displayed, thus giving the user the opportunity to continue with a programme or cancel.

Five simple keyboard commands have been devised to make operation of the system as simple as possible:

1. ★0 # Return to the top of the tree.
2. ★# Recall the previous page.
3. ★00 Recall the current page.
4. ★N # Jump to a known page number eg. ★357#, thus bypassing the tree selection system.
5. ★★ Correct a miskeying error.

## CHARGES

Charges for the service comprise of three components: the normal telephone charge for a local call to the computer centre; a time based charge for use of the computer/data base; and finally the information provider charge per selected page. The latter can range from one to 50 pence.

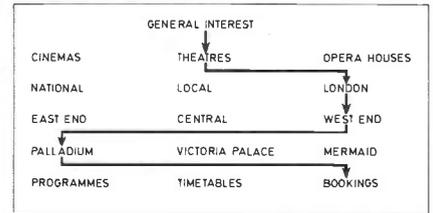


Fig. 2. Tree selection method

In addition, British Telecom charge a quarterly rental for the provision of a PRESTEL jack.

## FUTURE POTENTIAL

Today there are over 10,000 PRESTEL customers but present costs restrict its widespread use outside the business sector. The service should, however, be within the reach of most people before 1990.

There are many technical problems to overcome, mostly concerned with matching internationally linked systems. Alphagraphics and foreign language characters must be standardised and modems compatible, but when this is achieved millions of pages of reference will be available worldwide.

There can be no doubt that PRESTEL has proved the enormous potential of the British telecommunications industry—a potential which can only reveal more exciting developments as we race towards the 21st century. □


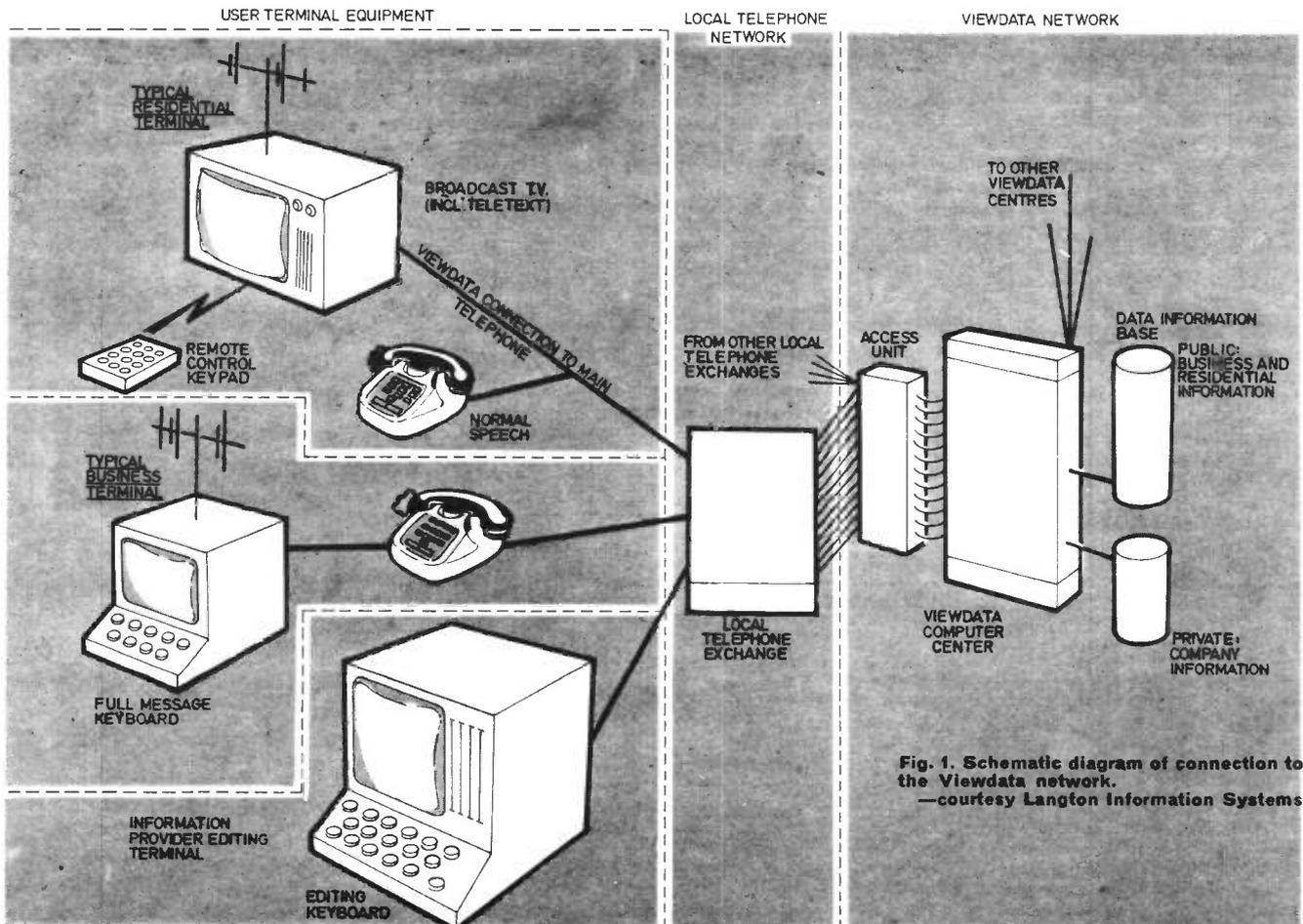


Fig. 1. Schematic diagram of connection to the Viewdata network.  
—courtesy Langton Information Systems

# CAR LIGHTS ALERT

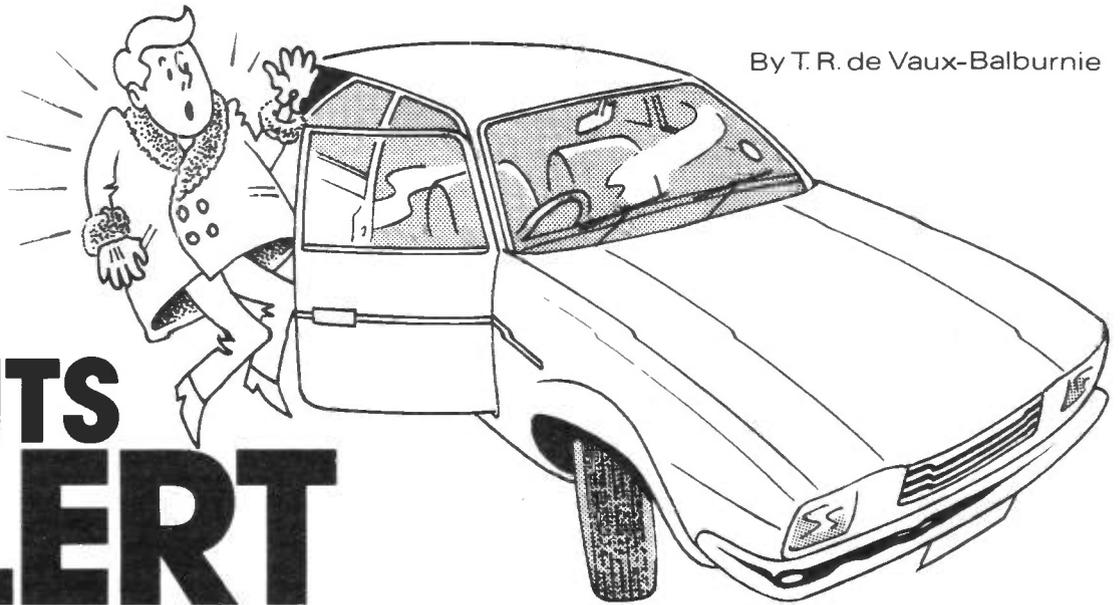

EVERY driver must have regretted leaving the car lights switched on unintentionally and returning to find the battery "flat". Although several circuits have been published to guard against such a mishap, this one has the advantages of simplicity and low cost.

With this system, a warning will sound if the lights remain switched on after a car front door is opened. Should the driver wish to leave the lights switched on for any reason, then the warning will be simply ignored since the sound will stop when he closes the door behind him.

This project is only suitable for negative-earth cars having a courtesy light operated by switches in the door pillars. Most cars in use today fall into this category. Should the courtesy light tend to flicker in operation, or fail to work at all, the switches should be checked and any faulty ones replaced before building commences.

## CIRCUIT DESCRIPTION

The existing relevant car electrics, consisting of the courtesy light and door switches, is shown in Fig. 1 with the electronics to be installed.

The new part contains only two active components. These are a 555 timer i.e. IC1 and a transistor TR1. These, together with a few additional components, form a slow-running oscillator and the control to start and stop it. With the specified values of components the rate of oscillation is about 2 per second that is 2Hz. This is obtained at the output (pin 3) of IC1. The output is connected to a solid state buzzer whose tone is therefore pulsed about twice per second. This leads to a very distinctive sound which easily carries above other noises in the car.

The rate of bleeping will depend on component tolerances and on per-

sonal taste so a control, VR1, is included. This may be adjusted to give the desired effect.

A connection from the courtesy light switch is taken to the base of the transistor, TR1, via a current-limiting resistor, R4. With the doors closed, therefore, the base of TR1 will be connected to the positive terminal of the car battery via the courtesy light bulb. This holds TR1 "on" so pin 4 of IC1 will be approximately earth potential. This effectively inhibits its action. When a door is opened, the base of TR1 is "earthed" through the door pillar switch. TR1 switches off and pin 4 of IC1 rises to near full battery positive potential. The i.c. is enabled and oscillation commences.


## CIRCUIT BOARD

The circuit is built on a piece of 0.1 inch matrix stripboard 14 strips by 21 holes in size as can be seen in Fig. 2. Although the 8-pin d.i.l. socket should be soldered in position along with the other components, the i.c. should not be inserted until later. Particular care must be taken when soldering TR1 in position.

There are several inter-strip links to make and some of the copper tracks on the underside need to be cut. VR1 should be left set at about mid-position.

The red (positive) flying lead of the buzzer may be soldered to the circuit panel. This component will not work if connected the wrong way

Fig. 1. Circuit diagram for the Car Lights Alert. Only suitable for negative earth vehicles.

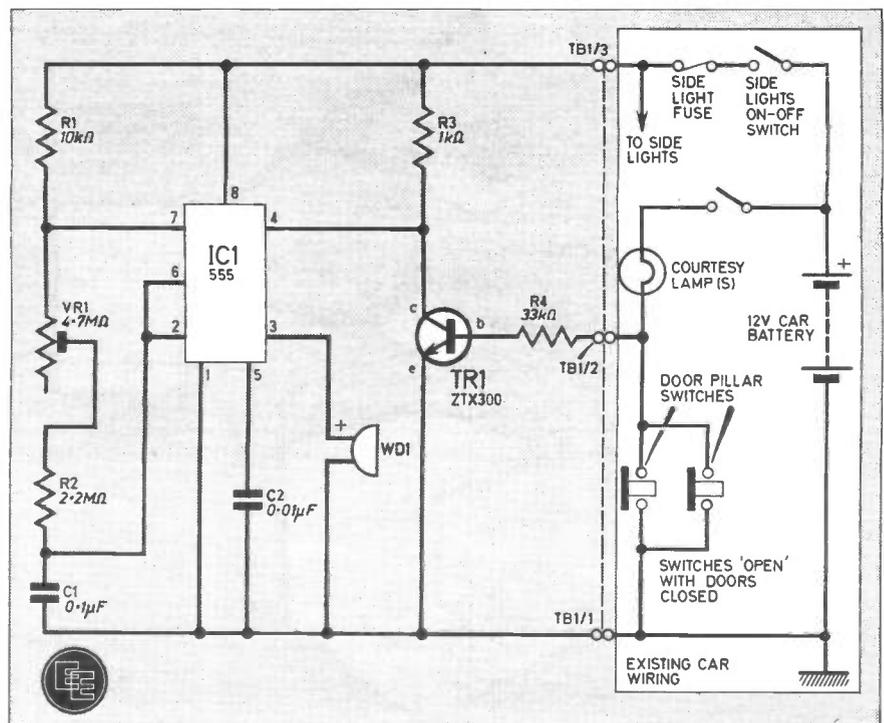

# CAR LIGHTS ALERT

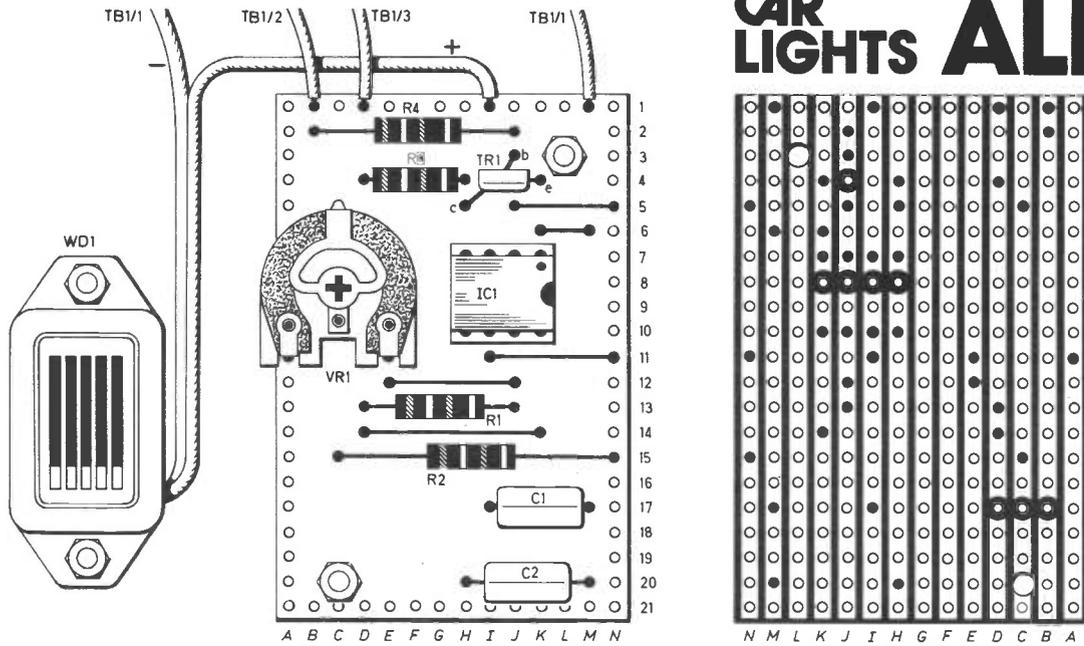


Fig. 2. Layout of components on the topside of the stripboard and details of breaks to be made in the copper tracks on the underside.


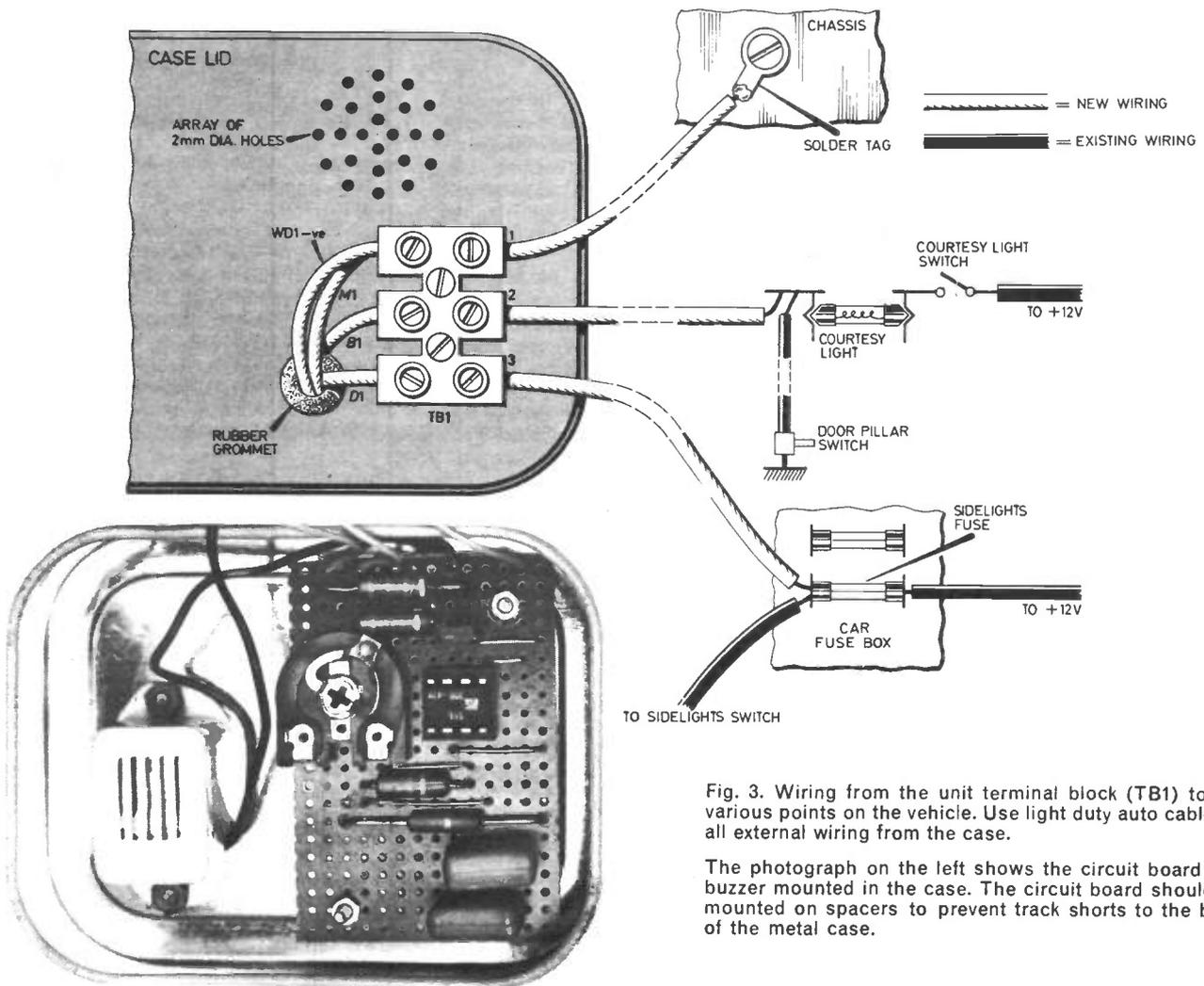


Fig. 3. Wiring from the unit terminal block (TB1) to the various points on the vehicle. Use light duty auto cable for all external wiring from the case.

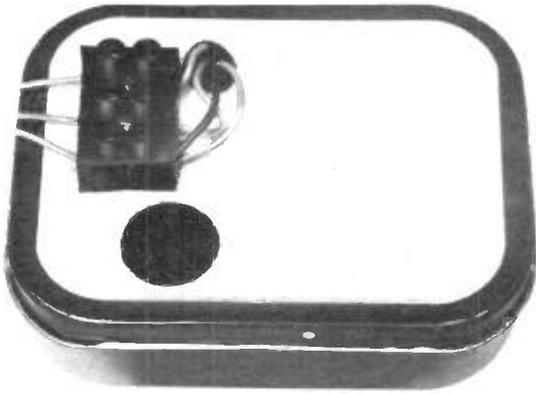The photograph on the left shows the circuit board and buzzer mounted in the case. The circuit board should be mounted on spacers to prevent track shorts to the base of the metal case.



The completed unit with a 3-way terminal strip fixed to the lid of the case.

round. A final check should be made to ensure that no connections have been missed and that no copper strips have been accidentally bridged with solder or swarf from the "cut" locations.

### TESTING

The circuit may be tested using a 9 volt battery but, of course, the sound will not be as loud as when it is connected to the 12 volt car system. Referring to Fig. 2 make connections to strip *B* (Courtesy Light), strip *D* (Lighting Fuse) and strip *M* (Negative) on the circuit panel. Connect the black flying lead of the buzzer to the latter. Insert the i.c. making sure that it is the right way round (see the small dot on the body).

Lay the circuit panel on an insulating surface to ensure that the copper strips are isolated from one another. Now connect the lead from strip *D* to the positive terminal of the battery and the lead from strip *M* to the negative terminal. If all is well, the buzzer will start bleeping. Gentle adjustment of VR1 will alter its rate.

If the connection from strip *B* is touched onto the negative terminal of the battery the buzzer should continue to sound but when it is touched on the positive terminal it should stop.

### BUILDING INTO THE CASE

A small plastic case is best for the project since there will be no problems with insulation. On the other hand, constructors may have metal boxes available such as tobacco or throat lozenge tins. The prototype was built into one of the latter. The circuit board was attached using 8BA nuts and bolts in the positions indicated. Short pieces of plastic wall plug (about 4mm long) or other spacers should be placed on the shanks of the bolts to hold the copper strips and connections well clear if a metal box is used.

In the prototype the buzzer was mounted inside the case. A corresponding hole was made in the lid to allow the sound through and a scrap of black material was stuck on the

inside to prevent debris entering the box. Where less room is available, the buzzer may be mounted on top.

A three-way terminal block is mounted on the lid to accept the wires from strips *B*, *D* and *M*, together with the negative connection of the buzzer (see Fig. 3). The wires must pass through a rubber grommet.

### INSTALLING IN THE CAR

Some cars have a fuse, or fuses, to protect the lights—others do not. If the car in question is so fitted then locate one by checking that one or more sidelights go off when it is removed. A fuse protecting the rear number plate light would do just as well since this works in conjunction with the sidelights.

A fuse protecting the headlights will not do since the main and dipped beam filaments will be protected by individual fuses and the project would not work if the lights were left switched on in the opposite sense. In any case, it is usually desirable for the alarm to sound if sidelights only are left switched on.

To make a connection to the fuse, first make sure that the "lamp side" is selected so that the new circuit is protected as well. To confirm this, use a 12 volt bulb with one terminal earthed to a metal part of the car. Remove the fuse, switch on the sidelights and touch the other test lamp lead to each terminal of the fuse holder in turn. In one position the lamp will stay off. This is the correct terminal of the fuse to use. Switch off the lights and then make a proper connection using a spade connector. If all the available outlets have been used already, obtain a "piggy-back" connector from a motor accessory shop.

If the car does not have fuses for the lighting circuits then make a connection to any sidelight between the lighting switch and the lamp. Generally there will be a "bullet" type connector which may be used for this. The wiring diagram in the car handbook will help.

Do not run the wire straight back to the unit but include a line fuse (of the type used for car radios). This should be fitted with a low value fuse rated at about 3A.

Next, make a connection to the courtesy light circuit between the lamp and door pillar switch. Again, a bunch of bullet connectors may be found and the one responsible for the courtesy light determined by disconnecting them one at a time. Often it is easier to remove a switch from the door pillar and make a direct connection there.

## COMPONENTS

### Resistors

- R1 10k $\Omega$
- R2 2.2M $\Omega$
- R3 1k $\Omega$
- R4 33k $\Omega$
- All  $\frac{1}{4}$ W carbon  $\pm 5\%$

See  
**Shop  
Talk**  
page 635

### Capacitors

- C1 0.1 $\mu$ F plastic or ceramic
- C2 0.01 $\mu$ F plastic or ceramic

### Semiconductors

- TR1 ZTX300 *n*p*n* silicon
- IC1 555 timer i.c.

### Miscellaneous

- VR1 4.7M $\Omega$  miniature horizontal carbon preset
- WD1 12V solid state buzzer
- TB1 5A 3-way screw terminal strip

Stripboard: 0.1 inch matrix size 14 strips  $\times$  21 holes; rubber grommet; auto connectors; light duty auto cable; tinned copper wire; 2BA solder tag and self-tapping screw to suit; case, plastic (preferred) or metal size approx. 100  $\times$  75  $\times$  25mm; 8BA fixings: 10mm long screws (4 off); nuts (4 off); washers (4 off); 4mm spacers (2 off).

Guidance only **£3.30**  
Approx. cost excluding case

Run the two wires to the terminal block on the unit. These wires should be of proper light duty auto-type. Do not use single solid core wire as this will fail in service. If the wires must pass through metal then a rubber grommet should be used.

Finally make the earth connection to the unit. Perhaps there is an existing point nearby. If not, drill a small hole in a metal part and make the connection using a solder tag secured with a self-tapping screw.

### FINAL CHECK

Before hiding the project under the dashboard, give it a final test. Switch the lights on and open either front door. The buzzer should bleep. Check with the engine running also.

Note that the buzzer will begin to sound immediately if the courtesy light bulb fails. It will also operate if the side-lights are on and the courtesy light is switched on manually. If this proves to be a nuisance then an on-off switch may be included in the run of wire to the lighting fuse to inhibit the circuit on these occasions.

If the lights are left on intentionally, then the buzzer will stop sounding when the car door is closed but, of course, it will sound when the user returns to the car and opens the door.

This simple project will help you to keep a charged battery and prevent frayed nerves.  $\nabla$



BY A. SPROXTON

**T**HE interest in the simple short wave receiver never abates and here is a neat and effective receiver using two transistors. There is no great difficulty in constructing it, but the parts need careful positioning if it is to fit together, so keep closely to the measurements and other details as given in the diagrams.

The receiver tunes approximately 10.8MHz to 30MHz and is capable of long distance reception when used with a reasonably effective aerial. This could be 20ft to 30ft of wire out-of-doors, high and clear of buildings if possible. An earth is not essential but is beneficial.

### CIRCUIT DESCRIPTION

The circuit diagram for the Simple Short Wave Radio is shown in Fig.1.

Signals picked up by the aerial are fed via preset trimmer C1 to the aerial coil L1. This is tuned by variable capacitor C3 to the desired frequency, and this signal is then applied to the gate of the field effect transistor TR1. Demodulation of the signal takes place in TR1 and the resultant audio signal is passed on to the second transistor TR2 which acts as an audio amplifier. The signal at the collector of TR2 is at a sufficient level to operate a set of headphones;

these are connected via jack socket SK2

VR2 is a preset gain control which controls the level of input applied to the base of TR2.

A low value variable capacitor C4 connected in parallel with C3 provides a fine tuning control.

In the drain circuit of TR1 is a second coil L2. This is wound on the same former as L1 and is thus inductively coupled to L1. Some of the radio frequency (r.f.) signal amplified by TR1 is fed back inductively into L1, so reinforcing the original signal and increasing the sensitivity of this stage. The amount of r.f. signal fed back is determined by the setting of the potentiometer VR1 which is usually referred to as the reaction control. The effectiveness of this type of receiver circuit depends very largely on the careful use of this reaction control.

The receiver is powered from a 9V layer dry battery. The battery is automatically connected whenever the headphones plug is inserted into jack socket SK2 (the switch S1 is an integral part of SK2).



### CIRCUIT BOARD

Start with the circuit board. This is a piece of perforated s.r.b.p. board and can be either 0.1 or 0.15in matrix but the overall size must not exceed 2<sup>5</sup>/<sub>8</sub>in x 1<sup>3</sup>/<sub>4</sub>in.

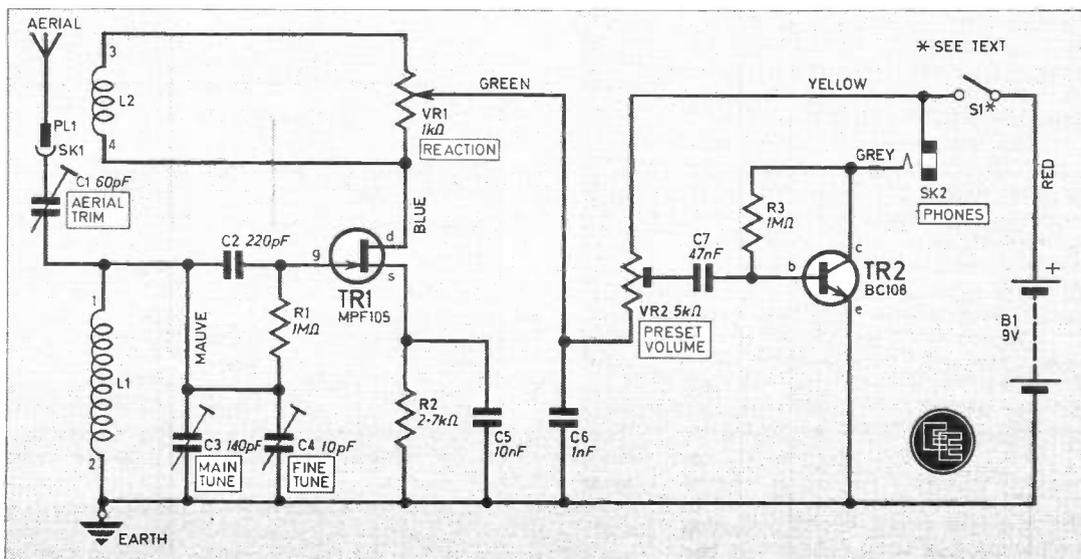


Fig. 1. Circuit diagram of the Simple Short Wave Radio. The first transistor TR1 is the detector, and TR2 is the audio amplifier. Positive feedback (or reaction) is applied to the aerial input via L2.

# COMPONENTS

## Resistors

- R1 1M $\Omega$
- R2 2.7k $\Omega$
- R3 1M $\Omega$
- All  $\frac{1}{4}$ W carbon  $\pm 10\%$

See  
**Shop  
Talk**

page 635

## Potentiometers

- VR1 1k $\Omega$ , linear
- VR2 5k $\Omega$  horizontal skeleton

## Capacitors

- C1 60pF (max) preset trimmer
- C2 220pF silver mica or polyester
- C3 140pF variable (Jackson 87/073)
- C4 10pF variable (Jackson C804)
- C5 0.01 $\mu$ F polyester
- C6 0.001 $\mu$ F polyester
- C7 0.047 $\mu$ F polyester

## Semiconductors

- TR1 MPF105 f.e.t.
- TR2 BC108 npn transistor

## Miscellaneous

- B1 9V PP3 battery
- L1, L2 Aerial and reaction coils (Wearite PA3)
- S1 part of SK2
- SK1 Aerial socket (2mm)
- SK2 jack socket 3.5mm with switch

Pair of PP3 battery connectors. Perforated s.r.b.p. board (0.1 or 0.15in matrix)  $2\frac{3}{8} \times 1\frac{1}{2}$ in maximum. Six double-ended solder pins. Bracket (R8). Plastics case  $5\frac{1}{2} \times 2\frac{1}{8} \times 1\frac{1}{2}$ in. Three knobs; two 6BA  $\times \frac{1}{2}$ in round head screws. One 6BA  $\times \frac{1}{2}$ in round head screw. Four 6BA nuts; two 6BA solder tags. One 4BA  $\times \frac{1}{2}$ in round head screw. Two 4BA nuts; two 4BA washers; one 8BA nut. Four lengths of coloured flexible wire (1 foot).

Approx. cost  
Guidance only **£12.50**

# SIMPLE SHORT WAVE RADIO

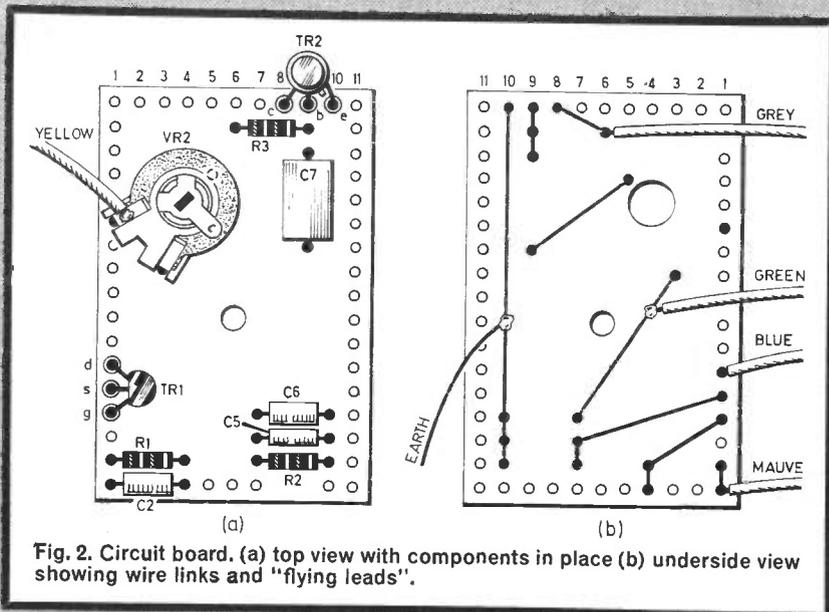


Fig. 2. Circuit board. (a) top view with components in place (b) underside view showing wire links and "flying leads".

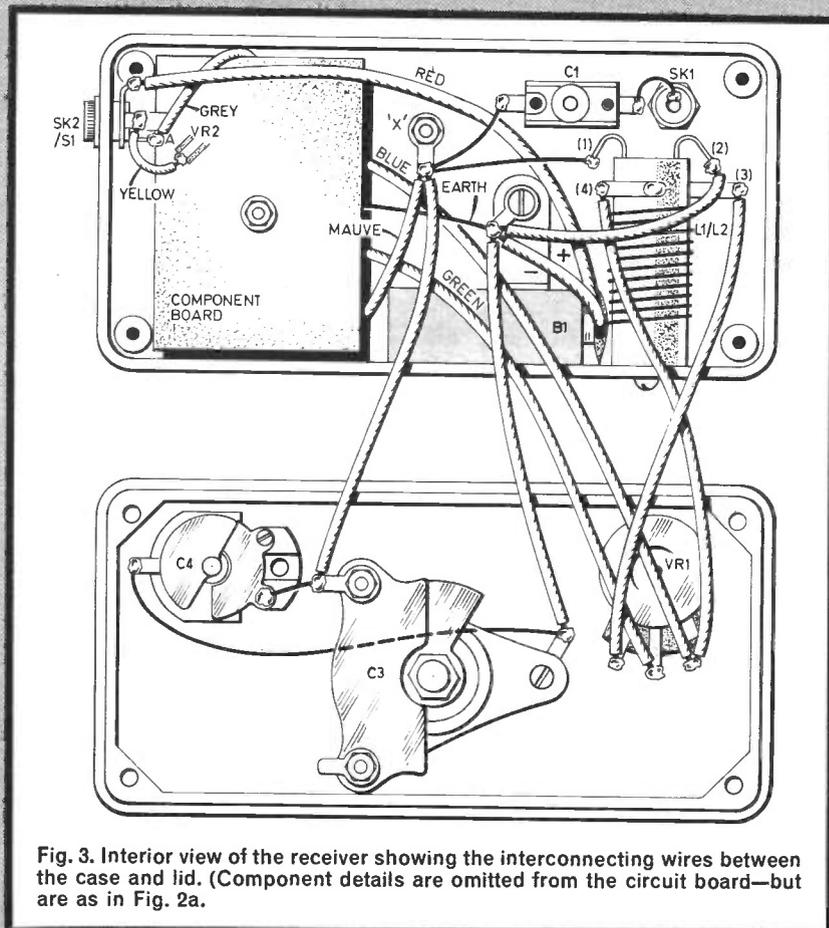


Fig. 3. Interior view of the receiver showing the interconnecting wires between the case and lid. (Component details are omitted from the circuit board—but are as in Fig. 2a.)

When you have cut the board to size, study Fig. 2. Position VR2 approximately as shown and drill a  $\frac{1}{4}$ in hole where the centre point is. Remove VR2 and place the board in the case as shown in Fig. 3. Mark where the hole at the centre of VR2 is on the case, and drill a  $\frac{1}{4}$ in hole in the case at this point. (VR2 controls the volume but as it will be at maximum most of the time, it can be adjusted by a small screwdriver externally, this is why the holes are required).

Replace VR2 on the board and fit all the components as shown in Fig. 2a. Insert the six double-ended pins (three for each transistor) in the positions shown. Wire up on the underside of the board as shown in Fig. 2b.

You should have six wires coming from the board including the earth wire. A glance at Fig. 3 will give you an idea how long they will need to be.

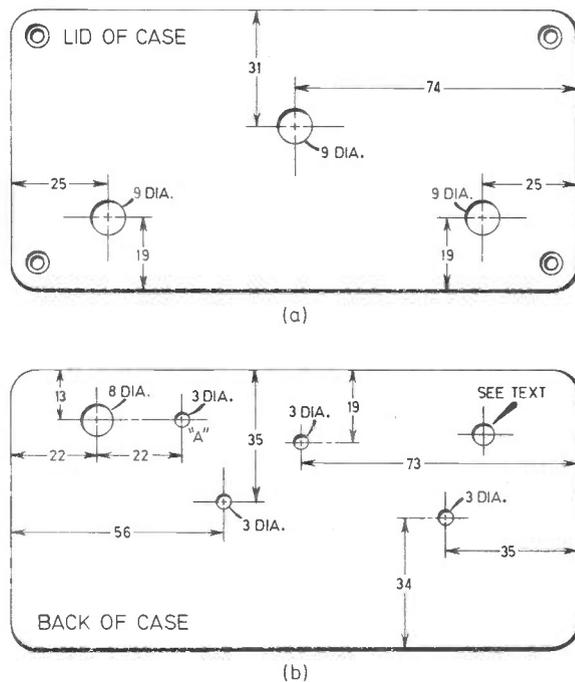
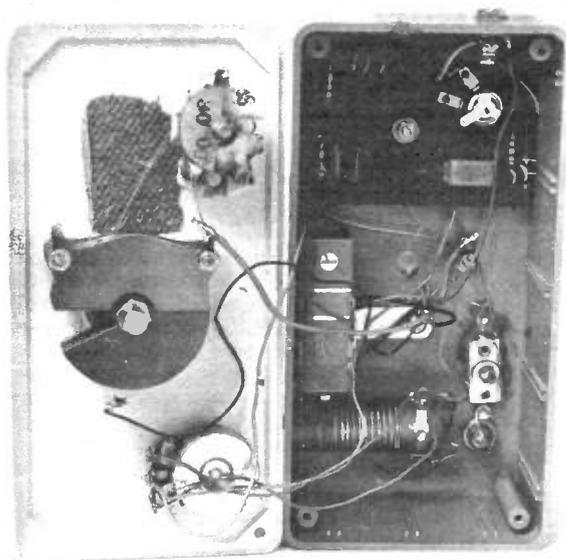


Fig. 4. (Above, right) Case drilling details (a) lid of case (b) back of case.

Photo (Above) The completed Simple Short Wave Radio with case lid "opened" (Right) general exterior view of the Radio.

It might help you to use a different colour for each wire, as shown in the illustrations. (These colours are also marked on the circuit diagram to assist identification.)

## PREPARING THE CASE

Place the board in the case and drill a small hole near the centre, through the board and the case. Fix it to the case with a 6BA  $\times \frac{1}{4}$  in nut and bolt.

Drill the holes in the back of the case as shown in Fig. 4b but concerning the screw used to fix the bracket, it might be safer to place the PP3 battery in the case, put the bracket against it and then mark the hole (the purpose of the bracket is to keep the PP3 in position). This hole should be big enough for a 4BA  $\times \frac{1}{2}$  in screw and this is fitted with an extra nut and washer at the back allowing it to double as an earthing point.

## HINTS AND TIPS

Most of the holes required can be made with a small hand drill. With care the bigger holes can be made with a soldering iron. Enlarge the hole gradually cutting away the surplus with a sharp knife, finish off with a round file.

Position the coil as shown, but near the back of the case. Mark the position for the coil fixing screw on the side of the case. Drill hole and secure coil with 6BA screw. Solder lengths of wire on the four coil tags; two of these can be fairly short but the other two have to reach to VR1 on the front panel.

## AERIAL TRIMMER


As you will wish to adjust the aerial trimmer C1 externally this component requires a simple modification. Remove the adjusting screw and insert from the other end. Screw it up tight and on the end put on an 8BA nut and turn until the end of the screw is just showing. SOLDER NUT ON TO SCREW. Bend the tags out straight until they are in line with the body.

Now place C1 in the case so that the screw head is in the centre of hole marked "A" Fig. 4b. Fix C1 to the case with Araldite, putting a small quantity at either end and being careful it doesn't touch any moving parts.

The 6BA screw nut and solder tag at point "X" (Fig. 3a) is only there as a convenient place for the four connections shown.

A 3.5mm jack socket SK2 is fixed in the side of the case (the position is not very critical). This jack socket functions both for connecting the headphones and as an on/off switch. (The jack socket may need a slight adjustment, if the extra contact is a "break contact" instead of "make contact". Take a small pair of pliers and gently bend out the bottom contact until the spring flies clear, then bend it in again and adjust, until it only touches with the jack plug in position).

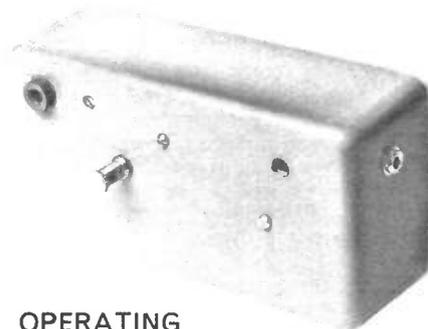Drill the holes in the lid of the case with three  $\frac{3}{8}$  in holes to take C3, C4 and VR1 according to Fig. 4a. It should be possible to complete the wiring by reference to Fig. 2 and Fig. 3.



## OPERATING

Connect up the PP3 battery. Turn VR2 to the position for maximum volume. Connect the aerial and earth and insert the jack plug of the headphones. Turn VR1 clockwise until a slight "plop" is heard. If you hear nothing, try turning VR1 fully anticlockwise. If you get the noise in this position, just reverse the two outer connections on VR1.


If you hear nothing either way, try putting the lead from the TR1 on the other end of VR1.

Turn VR1 until the plopping sound is just heard, and then try tuning with the main tuning capacitor C3. At some point you should get a series of whistles. Carry on tuning using the bandspread capacitor C4 and at the same time gradually reducing the amount of reaction by turning VR1 anticlockwise, you should then hear a station. Take a small screwdriver and adjust C1 for the best results.

Quite exceptional results can be obtained with this receiver, but they are dependent on the critical use of VR1 and careful tuning.

Don't forget to unplug your headphones after you have finished otherwise you will quickly run down your battery!!

# A.C. MAINS EXPLAINED

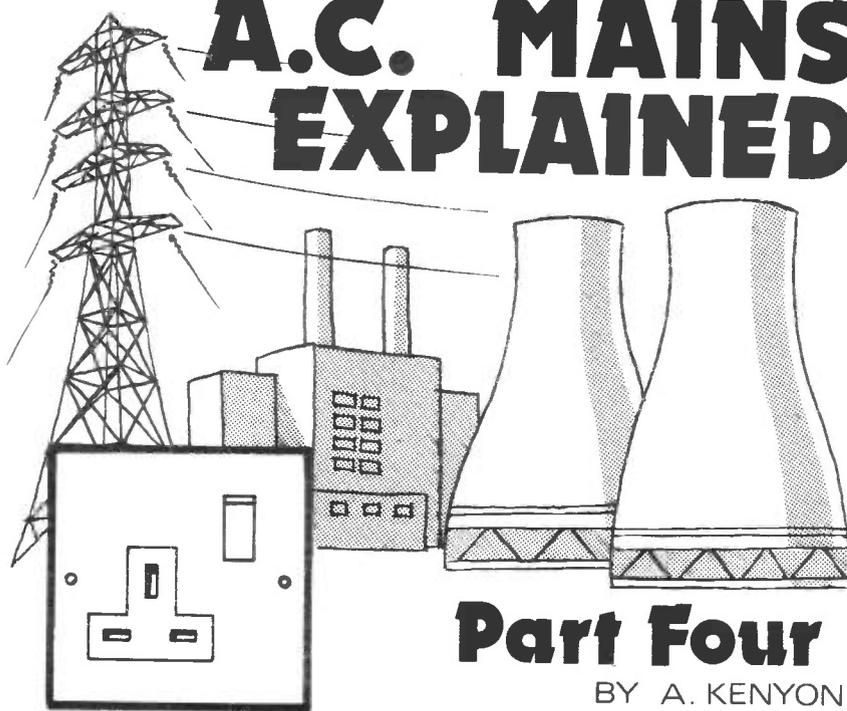

## Part Four

BY A. KENYON

IT HAS been shown that the power in a single phase circuit is equal to the voltage  $\times$  current  $\times$  power factor. However, except for ring mains and lighting circuits, most industrial equipment, such as motors and heating batteries, is supplied from a three phase supply having no neutral.

This type of equipment, termed **balanced three phase loads**, can be connected in one of two ways, known as **star** and **delta** formation.

### POWER IN THREE PHASE

To consider power in a three phase system, the heater battery will be examined, as these have purely resistive elements and therefore a power factor of one, thus keeping the calculations simple.

Fig. 4.1. Three-phase 15kW balanced load heater battery connected in star formation.


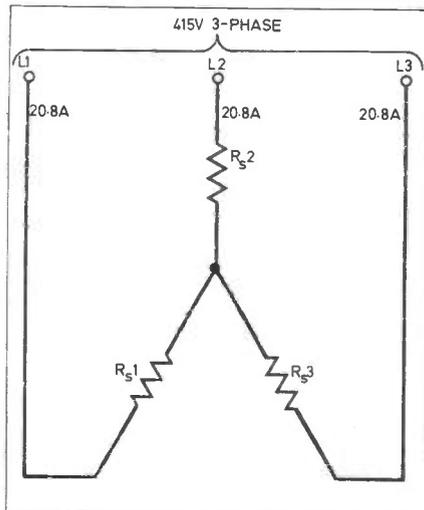


Fig. 4.1 shows a 15kW balanced load heater battery connected in star formation across a 415V, three phase supply and Fig. 4.2 shows the 15kW balanced load heater battery connected across the same supply but in delta formation. Note that neither system has a neutral wire and the reason for this is that in any four wire balanced load system (independent of power factor), no current flows in the neutral conductor therefore the fourth (neutral) wire serves no useful purpose.

In the case of the star formation, the star point is at the same potential as the neutral, so all calculations can be made with the assumption that the star point is virtually the neutral.

So, a balanced three phase load, in

Fig. 4.2. Three-phase 15kW balanced load heater battery connected in delta.

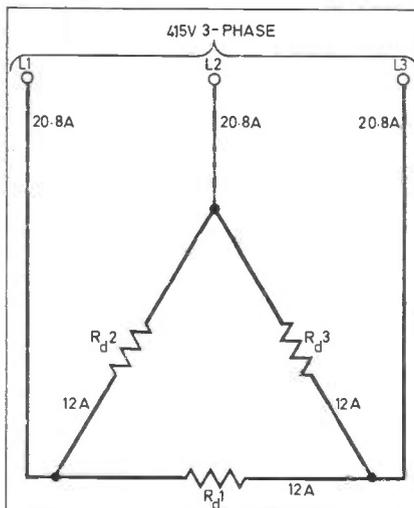

star or delta formation, requires only three wires from the three power lines, L1, L2 and L3.

Since the load is balanced, the three line currents supplying either the star or the delta system will be equal. Similarly, when the star and delta balanced loads both have the same power rating, the line currents will be the same for each.

### STAR CONNECTION

For the 15kW balanced load, each phase is rated at 5kW. Therefore line current =  $5,000W \div 240V = 20.8A$  for each phase. The total input to the system is then  $3 \times 240V \times 20.8A = 15,000VA$  but since the power factor = 1 (purely resistive system), the input power is also equal to 15,000W.

In part one of this series it was stated that the line voltage =  $\sqrt{3} \times$  the phase to neutral voltage (star point in this case) =  $1.73 \times 240V = 415V$ .

So **power = 1.73  $\times$  line voltage  $\times$  line current  $\times$  power factor =  $1.73 \times 415V \times 20.8A \times 1 = 15kW$ .**

### DELTA CONNECTION

As the load is also the 15kW balanced load, the line current will still be 20.8A, but in this case each heater element is connected across 415V (2 phases) so the current in each branch is  $5,000W \div 415V = 12A$ . This is equal to the line current  $\div \sqrt{3} = 20.8A \div 1.73 = 12A$ .

Input to the system therefore =  $3 \times 415V \times 20.8A / 1.73 = 15,000VA$  but again power factor = 1, so power = 15kW.

Once again, **power = 1.73  $\times$  line voltage  $\times$  line current  $\times$  power factor.** This is true of any balanced load, three-phase system.

### A.C. MOTORS

Although a.c. motors vary in shape and size, the most common types can be divided into two classes. **Universal** commutator motors as used on single phase portable appliances such as domestic vacuum cleaners and hedge cutters and on industrial drills, grinders and polishers, or **Induction** motors, either single or three phase, used to drive commercial and industrial machinery.

Whatever the type of motor, whether a.c. or d.c., the principle of producing a rotating drive is the same, namely, that if an electrical conductor carrying a current is placed in a magnetic field, it is acted upon by a force which pushes it in one direction or the other depending upon the direction of flow of the current, or the direction of the magnetic field. If either the current ceases to flow, or there is no magnetic field, the force acting on the conductor disappears. See Fig. 4.3.

Fig. 4.4 shows the two conductors wound in a loop (or turn) around an

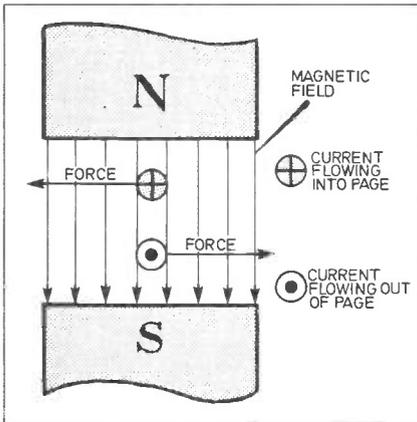


Fig. 4.3. The effect of placing a current carrying conductor in a magnetic field.

iron cylinder (imagine the rear ends away from you joined together). The top conductor moves to the left and the bottom one moves to the right until they reach a horizontal position where they remain at rest pulling away from each other, or if the current is reversed, pushing towards each other.

If, however, a number of loops are wound on the cylinder, spaced at regular intervals as shown in Fig. 4.5, and the current through each loop is reversed when it reaches the horizontal position, the cylinder will keep rotating. The component which changes the direction of flow of the current in the conductors at the horizontal position is called a **Commutator**.

Universal motors either a.c. or d.c., have the field coils (which create the magnetic field) connected in **series** with the commutator supplying the **armature** (the iron cylinder having the loops or turns of wire wound onto it). This ensures that the magnetic field and current in the armature conductors are always present at the same time. See Fig. 4.6.

### A.C. INDUCTION MOTORS

For simplicity of explanation, the principles of the working of a 2 pole, 3-phase induction motor will be considered. The term **Stator** refers to the stationary part of the motor which is

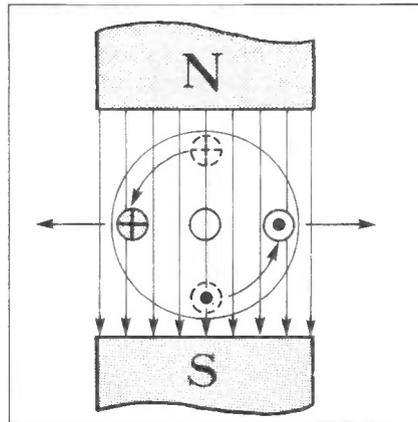
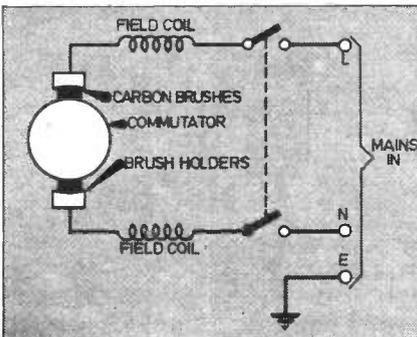


Fig. 4.4. The effect of winding the conductors onto a cylindrical former.

bolted to a solid concrete bed or screwed down to the bench. The term **rotor** refers to the inner part of the motor to which is attached the driving shaft and is inductively turned as explained. See Fig. 4.7 for construction of induction motor.

In Part One of this series, it was shown how a three phase supply is generated by three conductors separated by 120 degrees rotating in a magnetic field. A little imagination will show that the same result can be achieved by keeping the conductors stationary and rotating the magnetic field at 3,000 r.p.m. (As a matter of fact, this is how modern alternators operate.)

If the three voltages from the alternator are connected to three coils on a motor stator, each coil being displaced 120 degrees from the other, the coils will produce in the stator, a rotating magnetic field which rotates at the same speed as that in the alternator which is producing the voltage. This principle is known to electronics engineers in the form of the magstrip transmitter and receiver, (that is, if the transmitter continues to rotate, the receiver follows it and rotates at the same speed).

Conductor A will move to the left

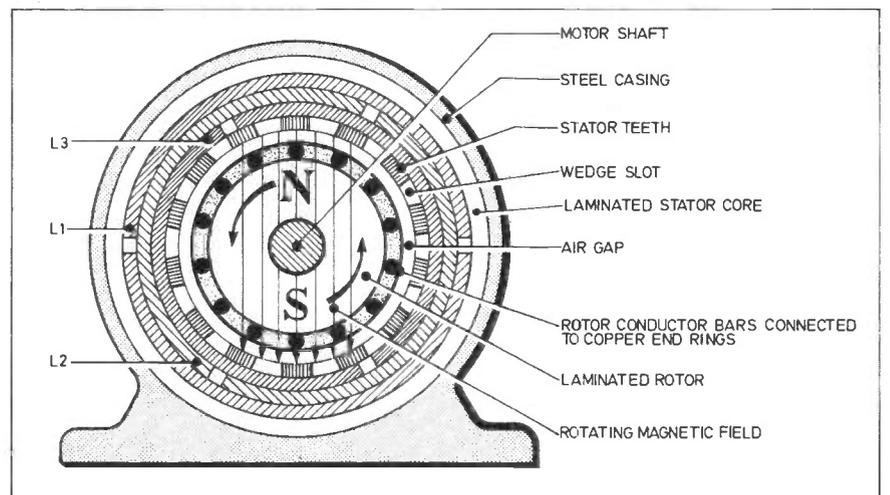


Fig. 4.7. Section through a 2-pole, 3-phase squirrel cage induction motor. Note that as all three phases (L1, L2 and L3) are balanced, no neutral conductor is required.

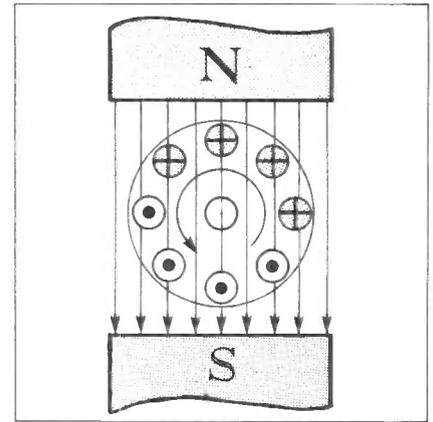


Fig. 4.5. The effect of adding turns and reversing the current every half revolution.

### HOW DOES THE ROTOR TURN?

To see how the rotor turns, consider Fig. 4.8. Imagine the motor bolted to a bench with the three phase supply to the stator switched off. The rotor will be stationary as will the shaft and the two particular rotor conducting bars A and B. Now the supply is switched on. Immediately a stator magnetic field is produced which is rotating at 3,000 r.p.m. and when a magnetic field cuts across a conductor, a voltage is produced in the conductor. Also, if the direction of motion of the magnetic field is reversed, the polarity of the induced voltage is reversed.

The rotating magnetic field is cutting conductor A from right to left and conductor B from left to right therefore if A is positive at the front end, B is negative at the front end, but since the two conductors are connected to copper end rings, a current will flow away from us in A and towards us in B. Here, therefore are the conditions required for rotation, namely, current flowing in a conductor when under the influence of a magnetic field.

Conductor A will move to the left

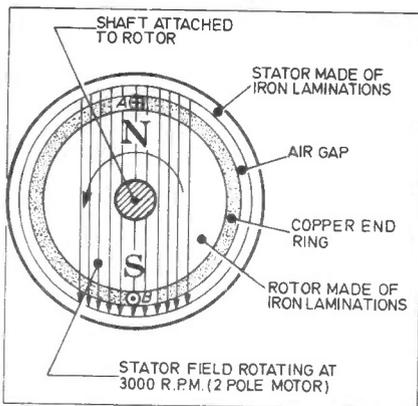


Fig. 4.8. Section through the motor in Fig. 4.7 to illustrate how the rotor turns.

and conductor *B* to the right. However, because the field itself is now rotating, the conductors will follow the field, gradually slipping behind it until the field has left *A* and *B*, but because other conductors are spaced around the rotor, they will take over the force of rotation and the whole rotor will continue to be motivated. The rotor can never reach the speed of the rotating field (known as **synchronous speed**) otherwise the field would not cut the rotor conductors to produce the current necessary to ensure rotation.

In practice, the rotor speed is usually about 95 per cent of the speed of rotation of the stator field, hence a two pole motor runs approximately 95 per cent  $\times 3,000 = 2,850$  r.p.m. the difference in speed being called the **slip** of the rotor.

It will be seen that on start up, the rate of the field cutting the conductors is maximum, gradually decreasing until full speed is attained. Hence the starting current is much higher than the running current, usually about four times greater.

### STARTING OF INDUCTION MOTORS

Small induction motors up to about 10 horsepower are usually started **direct on Line** (D.O.L.) where a starting current of up to 70 amperes is the maximum that the supply authority will permit. Machines started D.O.L. are capable of starting at full load.

Motors over 10 h.p. are usually started **star/delta** which means that their separate three phase coils are first connected in star formation and then switched to delta. This simply means that the motor is started at one third of its rated horsepower which reduces the starting current accordingly. Subsequently the horsepower at starting is reduced to one

### PART 3 ANSWERS

$$3.1 \text{ True power} = V \times I \times \cos \phi$$

$$= 240 \times 15 \times 0.8 = 2,880\text{W}$$

therefore 2.88 units consumed per hour.

$$3.2 \text{ In-phase current} = I \times \cos \phi$$

$$= 15 \times 0.8 = 12\text{A.}$$

$$\text{Wattless current} = \sqrt{15^2 - 12^2}$$

$$= \sqrt{225 - 144} = \sqrt{81} = 9\text{A.}$$

third, so the load on the motor has also to be reduced when starting, returning to full load when in the delta position.

Unfortunately a time interval occurs when the motor is disconnected from the mains supply while the changeover from star to delta takes place which again increases the starting current due to the fall back in speed.

A method of starting three phase induction motors which is becoming more popular is known as **part wind**. The stators of these machines are wound with two parallel windings which are connected one after the other. Although such machines still require 50 per cent off-loading at start, the fact that there is no time break as the windings are paralleled ensures a smooth acceleration to full speed. □

## BOOKS in BRIEF

**Servicing Home Video Cassette Recorders** by Martin Hobbs. (Haydon—distributed by John Wiley and Sons Ltd) Limp £9.85. Deals with the circuitry and mechanical features of typical recorders with Beta and VHS formats and designed to handle NTSC standard signals. An American publication aimed at the US market. A store of practical information for those involved in maintaining these machines.

**Essential Electronics an A to Z guide** by George Loveday. (Pitman) Limp £5.95. A comprehensive reference *cum* text book, subjects appear in alphabetical order. Good for rapid access to vital facts. Thorough treatment with worked out examples.

**How to Identify Unmarked ICs** by K. H. Recorr (Bernard Babani Ltd.) Limp £0.65. Not a book but chart giving step-by-step instructions for identifying logic i.c.s. of unknown origin using a simple multimeter. Useful only for TTL and the earlier RTL and DTL logic families.

**Multi-Circuit Board Projects** by R. A. Penfold (Bernard Babani) Limp £1.95. 21 simple projects that can all be constructed on the same printed circuit board. For further simplicity (and economy) all circuits use components from the same basic list of just over 20 items, meaning the constructor can re-use them to make all the projects.

**Popular Electronic Circuits Book 2** by R. A. Penfold (Bernard Babani Ltd) Limp £2.25. Another collection of over 70 designs from this well-known author covering the usual range of audio, radio, test-gear, home and car circuits. No constructional details given, just the circuit and a brief description but nothing too difficult for those with some experience.

**International Diode Equivalents Guide** by Adrian Michaels (Bernard Babani Ltd) Limp £2.25. As one would expect from an equivalents book, this one lists American, European and in some cases, Japanese equivalents of semiconductor diodes. Covers other diode derived devices, including thyristors, Zeners, i.e.d.s etc, but does not include any electrical or operating parameters for the semiconductors listed. Of more use to service technician and designer than the hobbyist.




**The 6809 Companion** by M. James (Bernard Babani Ltd) Limp £1.95. Written for the "average assembly language programmer" so if you don't fall into this category then this book may be a little difficult to follow. The 6809 is a sophisticated 8-bit microprocessor from the Motorola 6800 family and Mr James' companion is largely a software manual dedicated exclusively to it. Not for the beginner.

**Introduction to 6800/6802 Microprocessor Systems** by R. J. Simpson and T. J. Terrell (Newnes-Butterworth) Limp £6.95. The 6800 and 6802 constitute Motorola's early contribution to the microprocessor revolution, both being powerful 8-bit devices and this book is intended for students, technicians and engineers who wish to acquire an understanding of this processor family. It is a comprehensive introduction covering digital concepts, system hardware, programming and finally, hands-on investigation using a dedicated evaluation system. The text is really written as a course tutor for those with access to such an evaluation system, but could still benefit those without.


**26 Basic Programs For Your Micro** by Derrick Daines (Newnes-Butterworth) Limp £4.95. A batch of new games programs, only two of which have been published before, written for the personal computer and requiring a maximum of 15K of memory. They are all written in an easy sub-set of Basic so the reader should have little difficulty in translating them to suit any micro, for example into Sinclair Basic. Each game has a descriptive introduction, a program listing and a sample run plus a few notes to bring points of interest to the attention of the reader.

**IC Projects For Beginners** by F. G. Rayer (Bernard Babani Ltd) limp £1.95. Usual format for a book of this type, with circuit diagrams, stripboard layouts and wiring diagrams for a number of relatively simple projects all using inexpensive and easily obtainable integrated circuits. Subjects include radio, audio, power supplies, timers and oscillators and brief descriptions of the i.c.s. used are also given.

**The Art Of Programming The 1K ZX81** by M. James and S. M. Gee (Bernard Babani Ltd) limp £1.95. Having read the manual supplied with the Sinclair to acquire a grounding in Basic, this book makes a good next step for the programmer who wants to make the most of the 1K on-board memory. A descriptive text that uses programs to illustrate features including chapters on randomness, graphics, peeking and poking and finally some useful hints on memory saving. Some interesting games also featured.

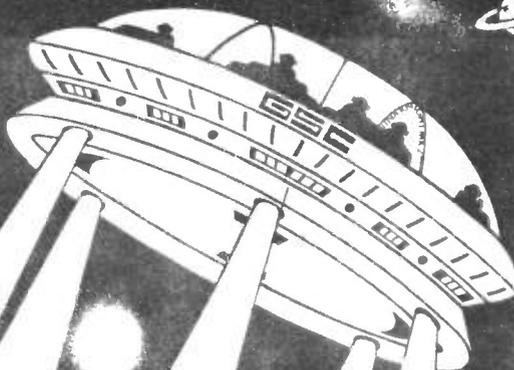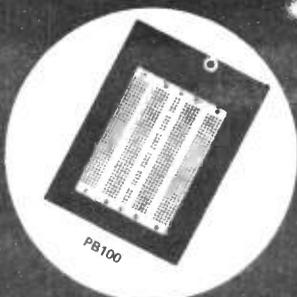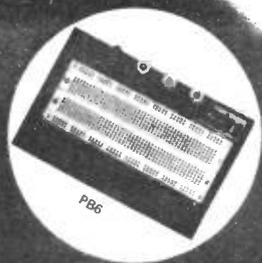

# NEW & FREE FROM GSC

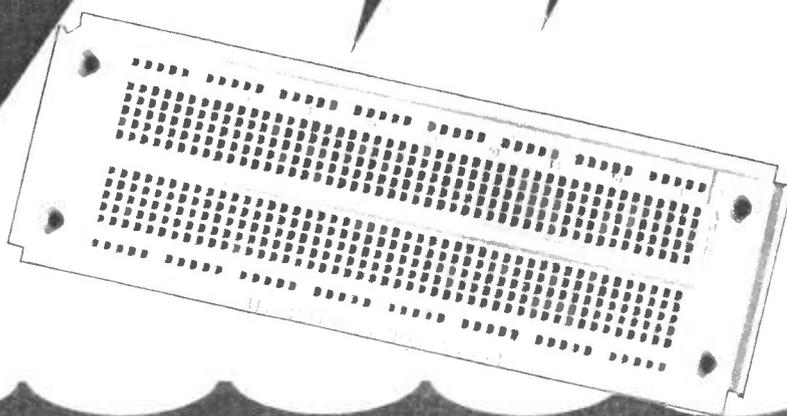

## NEW AND FREE FROM GSC.

**NEW** an exciting range of projects to build on the EXP300 breadboards.

**NOW** anybody can build electronic projects using "Electronics-by-numbers", its as "Easy as A, B, C with G.S.C!"

**FREE** project

### MUSICAL DOORBELL OF THE 3RD KIND

You've seen the film, now haunt your visitors with the tune!

Each time the doorbell is pushed the eerie tune plays out, then switches off to conserve battery power.

**HOW DO YOU MAKE IT.**

Our **FREE** project gives you clear "step-by-step" instructions. For example "take Resistor No.1 and plug it into hole numbers B45 and B47".

"Take IC No.1 and plug it into hole numbers E35 to E42 and F35 to F42, (pin 1 on the IC goes into F35)"

"Take... Well! why not "clip-the-coupon" and get your **FREE** step-by-step instruction sheet and your **FREE** 12 projects with each EXP300 bought and your **FREE** catalogue and.....

## EXPERIMENTOR BREADBOARDS

The largest range of breadboards from GSC. Each hole is identified by a letter/number system. EACH NICKEL SILVER CONTACT CARRIES A LIFE-TIME GUARANTEE.

All modular construction means that any Experimentor breadboard can be "snap-locked" together to build breadboards of any size.



**EXP325**  
The 'one-chip' breadboard Takes 8, 14, 16 and up to 22 pin IC's Has 130 contact points including 2 bus bars.



**EXP350**  
The 'beginners breadboard' For limited period you can have **FREE** 12 'Electronics by Numbers' PROJECTS



The most 'widely-bought' breadboard Don't miss out on our 'NEW AND FREE' projects They can be built on the EXP300

**EXP600**  
The Hobbyist microprocessor board  
**EXP650**  
The 'one-chip microprocessor' board  
**EXP4B**  
'Snaps on' four extra bus bars  
**PB6**  
The ultimate breadboard kit  
**PB100**  
The most kit for the least money

## NEW AND FREE FROM G.S.C.

### 24 HOUR SERVICE.

Tel (0799) 21682 with your Access, American Express, Barclaycard number and your order will be put in the post immediately.

Goods despatched within 48 hours.

**TO ORDER JUST CLIP THE COUPON.**

Experimenter Breadboards	Unit Price Inc. P & P + 15% VAT	Quantity Required
Exp 325	£2 76	
Exp 350	£4 65	
Exp 300	£8 05	
Exp 600	£8 74	
Exp 650	£5 17	
Exp 4B	£3 62	
PB 6	£12 36	
PB 100	£15 52	

NAME .....

ADDRESS .....

I enclose cheque/PO for £ .....

Debit my credit card No. ....

Expiry date .....

Please send free catalogue Tick  Dept 4P


GLOBAL SPECIALTIES CORPORATION



GSC Unit 1, Shire Hill Ind. Estate  
Saffron Walden, Essex. CB11 3AQ  
Telephone (0799) 21682, Telex 817477.  
Dept. 4P
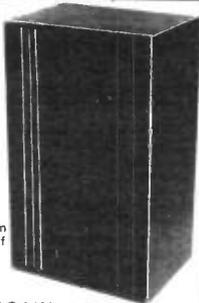
## SUPER HI-FI SPEAKER CABINETS

Made for an expensive Hi-Fi outfit - will suit any decor. Resonance free. Cut-outs for 6 1/2" woofer and 2 1/2" tweeter. The front material is Dacron. The completed unit is most pleasing. Supplied in pairs, price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.00 the pair.



## GOODMANS SPEAKERS

6 1/2" 8 ohm 25 watt £4.50. 2 1/2" 8 ohm tweeter. £2.50. No extra for postage if ordered with cabinets. Xover £1.50.

## UNIVAC KEYBOARD BARGAIN

50 keys together with 5 miniature toggle switches all mounted on a p.c.b. together with 12 i.c.'s many transistors and other parts.

£13.50 + £2.00 post. This is far less than the value of the switches alone. Diagram of this keyboard is available separately for £1.



## VENNER TIME SWITCH

Mains operated with 20 amp switch, on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic case £1.75 or metal case £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

## THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 - 100°C. There is also a thermostatic pad which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 - however, you can have the parcel for £2.50.

## TREMENDOUS OFFER!

Your Chance of a lifetime

We have to clear a big store. 100 tons of stock must go. 10 kilo parcel of unused items. Minimum 1,000 items includes panel meters, timers, thermal trips, relays, switches, motors, drills, taps and dies, tools, thermostats, coils, condensers, resistors, etc. etc. Individually these must cost in excess of £100.

YOURS FOR ONLY £11.50 plus £3.00 post.

## EXTRACTOR FAN

Mains operated - ex-computer

5" Woods extractor £5.75, Post £1.25.

5" Plannair extractor £6.50, Post £1.25

4" x 4" Muffin 115v. £4.50, Post 75p.

4" x 4" Muffin 230v. £5.75, Post 75p.




## 8 POWERFUL BATTERY MOTORS

For models, maccanos, drills, remote control planes, boats, etc. £2.95.
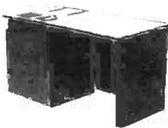
## INSTRUMENT BOX WITH KEY

Very strongly made (ply-wood sides with hard board top and bottom). This is black grained effect, vinyl covered, very pleasing appearance. Internal dimensions 12 1/2" long, 4 1/4" wide, 6" deep. Ideal for carrying your multi range meter and small tools and for keeping them in a safe place. £2.30. Post paid if ordered with other goods, otherwise £1.00.




## COMPUTER DESK

Size approx 4' x 2' x 26" high. These were made for hard work, the top being formica covered. Suitable for housing instruments or for use as office desks. Beautifully made, these cost over £100 each, our price only £11.50 each, however, you must arrange to collect.

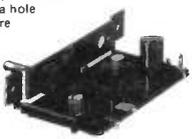
## MINI MONO AMP

on p.c.b., size 4" x 2" approx. Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amplifier. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



# TERRIFIC VALUE KITS!

## 3 CHANNEL SOUND TO LIGHT KIT

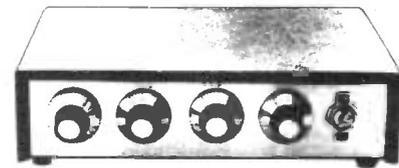

Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

## TANGENTIAL BLOW HEATER

2.5 Kw quiet, efficient instant heating from 230/240 volt mains. Kit consists of blower as illustrated, 2.5 Kw element, control switch and data all for £4.95, post £1.50.



## CAR STARTER AND CHARGER KIT

In an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises 250 watt mains transformer, 40 amp bridge rectifier, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £12.50 + £3.00 post.

## 6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in Radio Constructor. Complete kit includes case materials, six transistors and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy if you have an amplifier to connect it to or a pair of high resistance headphones. Price £11.95.

## MEDIUM & 2 SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginners model. Price £2.30. Crystal earpiece 65p. High resistance headphones (gives best results) £3.75 kit includes chassis and front, but not case.

## TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox - all electronic parts and circuit. £2.30. (Not licencable in the U.K.)

## RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 comp. kit. (Not licencable in the U.K.)

## FM RECEIVER

Made up and working, complete with scale and pointer needs only headphones, ideal for use with our surveillance transmitter or radio mike. £5.85. or kit of parts £3.95.

## 3 - 30v VARIABLE VOLTAGE POWER SUPPLY UNIT

With 1 amp DC output, for use on the bench, students, inventors, service engineers, etc. Automatic short circuit and overload protection. In case with a volt meter on the front panel. Complete kit £13.80

## INTERRUPTED BEAM

This kit enables you to make a switch that will trigger when a steady beam of infra red or ordinary light is broken. Main components - relay, photo transistor, resistors and caps, etc. Circuit diagram but no case. Price £2.30

## IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - complete mains operated kit, case included £11.95 plus £2.00 post.

## RADIO STETHOSCOPE

Easy to fault find start at the aerial and work towards the speaker - when signal stops you have found the fault. Complete kit £4.95.

## MUGGER DETERRENT

A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

## MORSE TRAINER

Complete kit for only £2.99.

## DRILL SPEED CONTROLLER

Complete kit for £3.95.

## INVISIBLE AND SILENT SENTINEL

Ultra sonic beam when broken could warn you of visitor - two complete kits - US transmitter & VS receiver - relay to operate light or bell £9.50.

## BURGLAR ALARM

Complete kit includes 6" external alarm bell, mains power unit, control box with keyswitch, 10 window/door switches, 100 yards of wire. With instructions £29.50.



# J. BULL (Electrical) Ltd.

(Dept. EE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £10 add 50p service charge. Monthly account orders accepted from schools and public companies. Access & Barclaycard orders phone Haywards Heath (0444) 454563. Bulk orders: Write for quote. Delivery by return.
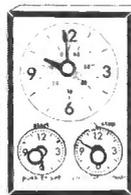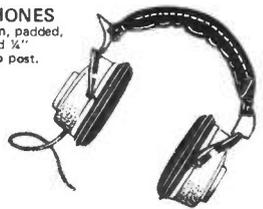
## STEREO HEADPHONES

Very good quality, 8 ohm, padded, terminating with standard 1/4" jack plug. £2.99 plus 60p post.



## TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs FOR ONLY £2.50.

## ROPE LIGHT

4 sets of coloured lamps in translucent plastic tube arranged to give the appearance of a running or travelling light. With variable speed control box, ideal for disco or shop window display. Complete, made up, ready to plug into mains. £36.00 + £2 post.

## ZX81 OWNERS

Make yourself a full size keyboard! Key switches complete with plain caps, 6 for £1.15. Easily divisible.



## DELAY SWITCH


Mains operated - delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps - second contact opens a few minutes after the 1st. £1.95.

## ROTARY WAFER SWITCHES

5 amp silver plated contacts. 1/4" shaft. 1" dia. wafer. Single wafer types, 29p each, as follows:  
 1 pole 12 way      2 pole 6 way      3 pole 4 way  
 4 pole 3 way      6 pole 2 way      4 pole 3 way  
 Two wafer type, 59p each, as follows:  
 2 pole 12 way      4 pole 5 way      4 pole 6 way  
 6 pole 2 way      8 pole 3 way      12 pole 2 way  
 3 wafer types 99p each,      6 pole 5 way      6 pole 6 way  
 9 pole 4 way      12p 3 way      18p 2 way
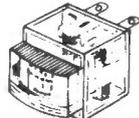
## LEVEL METER

Size approximately 3/4" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200uA, 60p



## WATERPROOF HEATING WIRE

60 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses - around water pipes, under grow boxes in gloves and socks.

## MOTORS FOR ROBOTICS

If its a toy robot you are making then one of our eight battery motors (see centre column) may do. If its a bigger one, however, then see below. If still not big enough then enquire - we have larger motors but these are usually mains driven.

## 12v MOTOR BY SMITHS

Made for use in cars, these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. These have a good length of 1/2" spindle - price £3.45. Ditto, but double ended £4.25.



Ditto, but permanent magnet & various spindle sizes £3.75.

## EXTRA POWERFUL 12v MOTOR

Made to work battery lawn mower, this probably develops up to 1/4 h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. £6.90 + £1.50 post. (This is easily reversible with our reversible switch - Price £1.15).

## GO KART MOTOR

12 - 24 Volt operated easily very speed and reverse - terrific power. Price £9.50.



These are powerful mains operated induction motors with gear box attached. The final shaft is a 1/2" rod with square hole, so you have alternative coupling methods - final speed is approx. 5 revs/min, price £5.50. - Similar motors with final speeds of 80, 100, 160 & 200r.p.m. same price.

## REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Framco Company this is a very robust motor, size approximately 7 1/2" long, 3 1/2" dia. 3/8" shaft, Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

- 1 Framco motor with gear box
- 1 manual reversing and on/off switch
- 1 push to start switch
- 1 x 100w auto transformer
- 2 limit stop switches
- 1 circuit diag. of connections.

£19.50 plus postage £2.50.


**FREE** OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

# CIRCUIT EXCHANGE

This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised.

Payment is made for all circuits published in this feature.

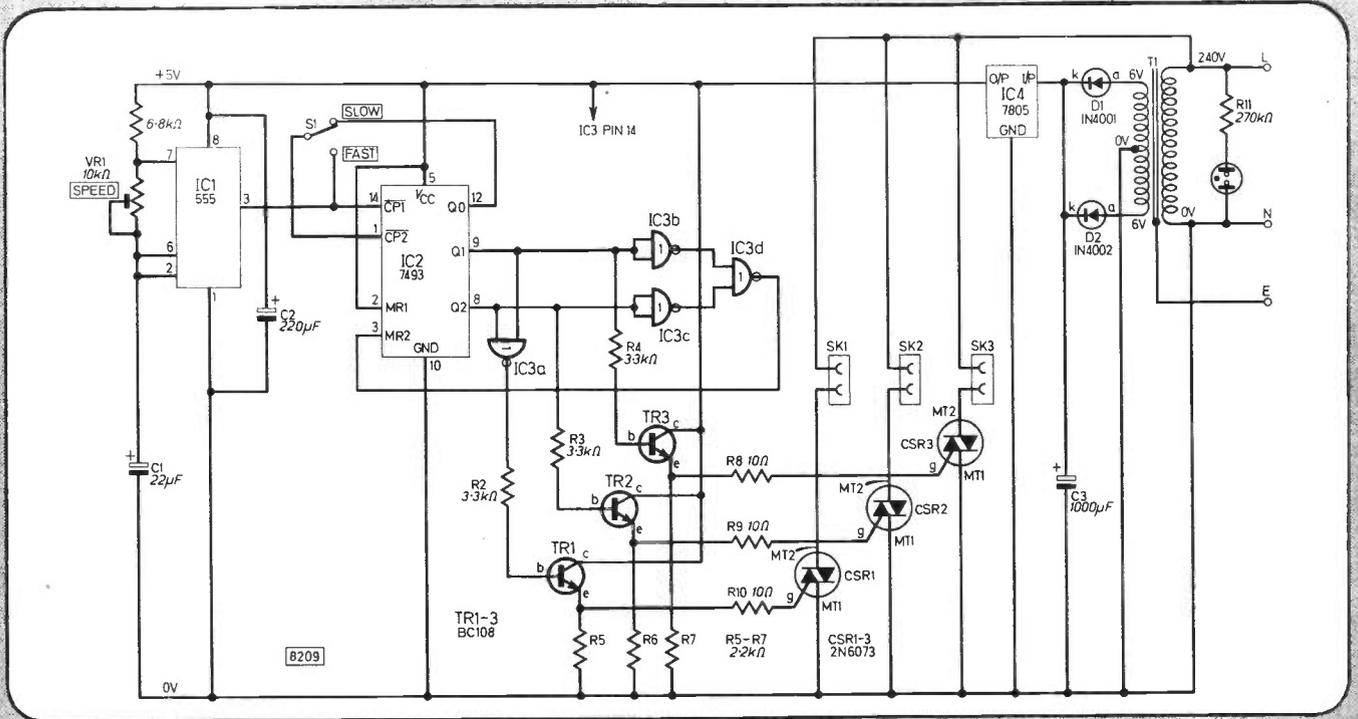Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.



## CHASER LIGHT

The power supply section of this circuit is conventional with full-wave rectification of the output from a 6-0-6V transformer. This is regulated by IC4, a 7805, to give a 5V supply. Note that the neutral is connected to the 0V line and the earth is not.

The 555 i.c. IC1, forms the driver oscillator for the circuit and VR1 controls the frequency.

When a 555 timer i.c. switches, it can put a "glitch" on the power line which would interfere with the operation of the TTL flip-flop i.c.s, so C2 is included to cure this problem and should be mounted as close as possible to IC1 pin 8.

sible to IC1 pin 8.

The output from IC1 is connected to pin 14, IC2, the clock input of a TTL 7493 4-bit binary ripple counter. The other clock input at pin 1 is switchable between the output of IC1 and the first output (pin 12) of the ripple counter, giving FAST and SLOW ranges.


The counter works as follows: Initially both the outputs used (pins 8 and 9) are low, therefore the output of IC3a is high. After the first pulse, pin 9 will be high and pin 8 will be low. The next pulse causes pin 9 to go back to low and pin 8 goes high. The third pulse results in both outputs going high and this is

detected by a composite AND gate, IC3b, c and d. This resets the counter output back to zero (two lows).

Thus IC3a output, IC2 pin 9 and IC2 pin 8 go high in succession, and these outputs are taken to transistors TR1, 2 and 3, which serve as TTL to triac interfaces. The triacs CSR1, 2 and 3 are therefore triggered in sympathy with the outputs.

The triacs specified can handle up to 700W per channel. However, if full sized bulbs and holders prove to be a little too costly, three sets of Christmas-tree lights could be used.

C. G. Bulman,  
Droitwich,  
Worcs.

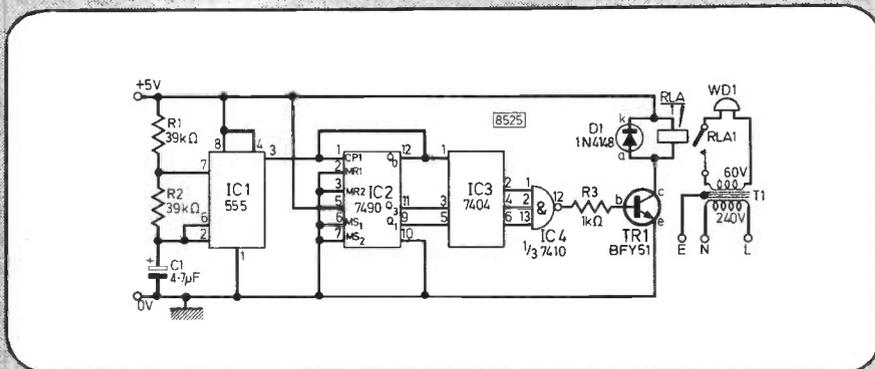

## PHONE BELL REPEATER

The circuit shown left was used in our school play to provide an automatic ringing sound on an old unused standard telephone.

The 555 timer, IC1, provides a square wave of approximately 0.6 seconds frequency which is counted by the IC2, a decade counter. Two pulses are selected by the gates to switch a relay, via the transistor TR1, and sound a bell.


P. K. Yeoman,  
Haywards Heath,  
Sussex.

# SQUARE One FOR BEGINNERS


FOR newcomers, some of the mystic of electronics is undoubtedly created by symbols used in circuit diagrams as well as the enigmatic "shorthand" used in text.

Here are the circuit symbols for the more commonly used electronic components.

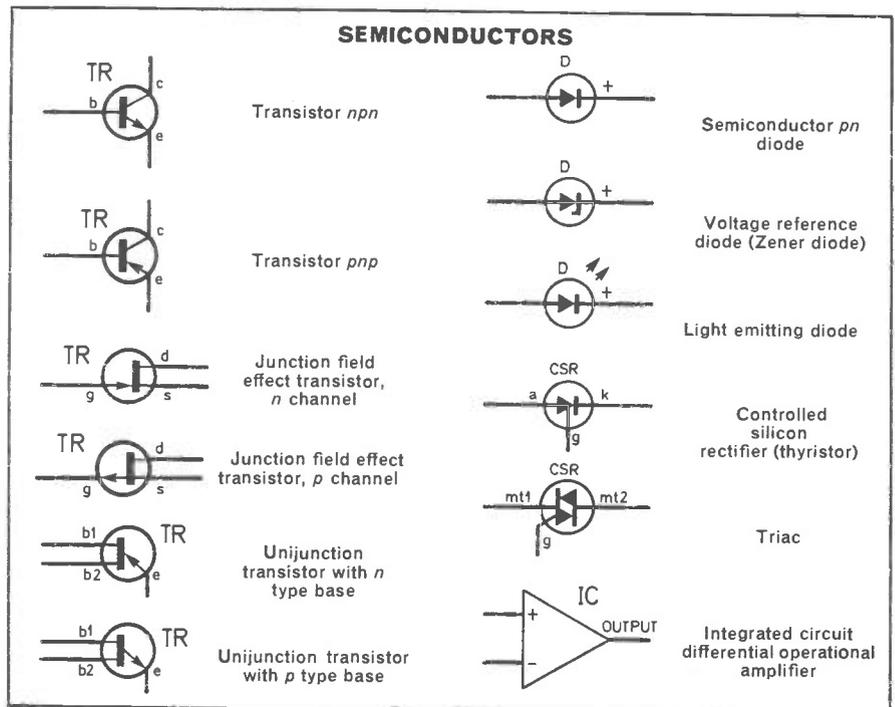
Abbreviations in common use are listed together with their plain language meaning.



### RESISTORS AND POTENTIOMETERS

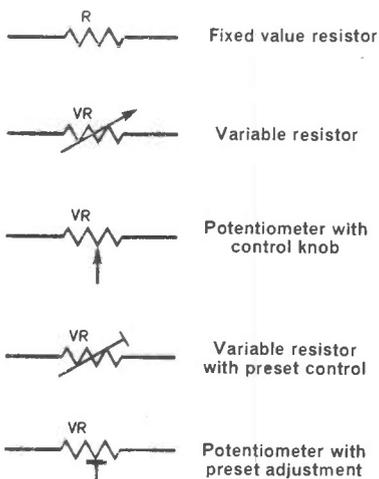

### CAPACITORS

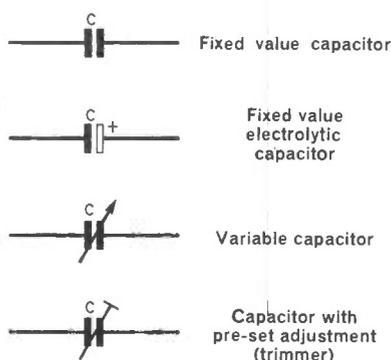

### ABBREVIATIONS IN COMMON USE

<b>A</b>	ampere (amp)	lin.	linear
a.c.	alternating current	l.t.	low tension
a.f.	audio frequency	log.	logarithmic
a.f.c.	automatic frequency control	l.w.	long wave
a.g.c.	automatic gain control	<b>M</b>	mega ( $\times 1,000,000$ )
a.m.	amplitude modulation	m	metre (measurement of length)
<b>BA</b>	British Association (nut and bolt sizes)	m	milli ( $\div 1,000$ )
b.f.o.	beat frequency oscillator	mm	millimetre
bit	binary digit	<b>MOS</b>	metal oxide silicon
<b>C</b>	coulomb	m.w.	medium wave
c	centi ( $\div 100$ )	n	nano ( $\div 1,000,000,000$ )
cm	centimetre	npn	transistor structure
<b>CMOS</b>	complimentary metal oxide silicon	pnp	transistor structure
c.r.o.	cathode-ray oscilloscope	op-amp	operational amplifier
c.r.t.	cathode-ray tube	p	pico ( $\div 1,000,000,000,000$ )
c.w.	continuous wave	p.d.	potential difference
d	deci ( $\div 10$ )	p.i.v.	peak inverse voltage
dB	decibel	p-p	peak-to-peak
d.c.	direct current	p.t.f.e.	polytetrafluoroethylene
d.i.l.	dual-in-line	p.v.c.	polyvinyl chloride
<b>DIN</b>	Deutsche Industrie Nummer	r.f.	radio frequency
d.p.d.t.	double-pole double-throw	r.m.s.	root-mean-square
elect.	electrolytic	s.p.c.o.	single-pole changeover
e.h.t.	extra high tension	s.p.s.t.	single-pole single-throw
e.m.f.	electromotive force	s.r.b.p.	synthetic resin bonded paper
e.m.u.	electromagnetic unit	s.s.b.	single sideband
e.s.u.	electrostatic unit	s.h.f.	super high frequency
eV	electron volt	s.w.g.	standard wire gauge
<b>F</b>	farad	<b>T</b>	tera ( $\times 1,000,000,000,000$ )
f.e.t.	field effect transistor	t.r.f.	tuned radio frequency
f.s.d.	full scale deflection	<b>TTL</b>	transistor transistor logic
f.m.	frequency modulation	u.h.f.	ultra high frequency
<b>G</b>	giga ( $\times 1,000,000,000$ )	u.j.t.	unijunction transistor
g	gram	<b>V</b>	volt
<b>H</b>	henry	v.c.o.	voltage controlled oscillator
Hz	hertz (cycles per second)	v.h.f.	very high frequency
h.f.	high frequency	v.l.f.	very low frequency
h.t.	high tension	<b>W</b>	watt
i.c.	integrated circuit	w.w.	wire wound
i.f.	intermediate frequency	<b>X</b>	reactance
k	kilo ( $\times 1,000$ )	<b>Z</b>	impedance
l.e.d.	light emitting diode	%	per cent
l.d.r.	light dependent resistor	<b>S</b>	micro ( $\div 1,000,000$ )
l.f.	low frequency	$\Omega$	ohm

# BI-PAK BARGAINS



**5T21 SCREWDRIVER SET**  
6 precision screwdrivers in hinged plastic case. Sizes — 0.8 1.4 2.2 4. 2.9 and 3.8mm **£1.75**

**5T31 NUT DRIVER SET**  
5 precision nut drivers in hinged plastic case. With turning rod. Sizes — 3.3 5.4 4.5 and 5mm **£1.75**

**5T41 TOOL SET**  
5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers — H 0 and H 1 Hex key wrenches — 1.5 2.0 and 2.5mm **£1.75**

**5T51 WRENCH SET**  
5 precision wrenches in hinged plastic case. Sizes — 4 4.5 5 5.5 and 6mm **£1.75**

BUY ALL FOUR SETS 5T21-5T51 and get  
HEX KEY SET **FREE**  
HEX KEY SET ON RING  
Sizes: 1.5 2.2 2.5 3 4 5 5.5 and 6mm.  
Made of hardened steel  
HX/1 **£1.25**



## "IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty.*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.  
\*Quantities approximate. count by weight.

**25** pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240° In-line 3-6 Pin, Speakers, Phono, Jack Stereo and Mono etc. Valued at well over £3 normal Order No. SX25

Our Price: **1.50** per pak. Guaranteed to save you money.  
SX26 3 Pks of 6 pin 240° DIN Plugs and Chassis Sockets 50p  
SX27A 60 Assorted Polystyrene Bead Capacitors Type 9500 Series PPD £1.00  
SX28A 50 Assorted Silver Mica Caps. 5.6pF-150pF £1.00  
SX29A 50 Assorted Silver Mica Caps. 180pF-4700pF £1.00  
SX30A 50 High Voltage Disc Ceramics 750v min up to 8KV Assorted useful values £1.00  
SX31A 50 Wirewound 9 watt (avg) Resistors Assorted values 10hm-12K £1.00

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty.*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pf 5.6pf	£1
SX19	100	Mixed Ceramics 60pf 0.5mf	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-10000µl	£1
SX24	20	Tantalum Beads, mixed	£1

\*Quantities approximate. count by weight

## BARGAINS

SX91	20 x Large 2" RED LED	£1
SX42	20 small 125 RED LED's	£1
SX43	10 Rectangular Green LED's 2	£1
SX46	30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded. New	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fit size 29 x 20mm	50p
SX49	20 Assorted Slider Knobs. Black/Chrome, etc.	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

## BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m  
LCD 10 MEGOHM INPUT IMPEDANCE  
\*3 1/2 digit \*16 ranges plus hFE test facility for PNP and NPN transistors \*Auto zero, auto polarity \*Single-handed pushbutton operation \*Over range indication \*12 5mm (1/2-inch) large LCD readout \*Diode check \*Fused circuit protection \*Test leads, battery and instructions included  
Max indication 1999 or — 1999  
Polarity indication Negative only  
Positive readings appear without + sign  
10 Megohms  
Zero adjust Automatic  
Sampling time 250 milliseconds  
Temperature range — 5°C to 50°C  
Power Supply 1 x PP3 or equivalent 9V battery  
Consumption 20mW  
Size 155 x 88 x 31mm

RANGES  
DC Voltage 0-200mV  
0-2-20-200-1000V Acc. 0.8%  
AC Voltage 0-200-1000V  
Acc. 1.2% OC Current 0.200uA  
0-2-20-200mA 0-10 A Acc. 1.2%  
Resistance 0-2-20-200K ohms  
0-2 Megohms Acc. 1%

BI-PAK VERY LOWEST POSSIBLE PRICE **£35.00** each




## MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to max of 1 1/2". Approx size 80 x 120 x 66mm  
Bi-Pak's Mini Vice at a Mini Price only


**£2.50**

ORDER NO. SX82

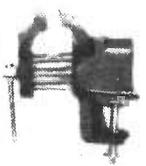
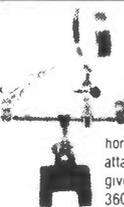
## The Third and Fourth Hand...

... you always need but have never got 'until now'  
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2 diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier.  
Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**  
Without magnifier ORDER NO. T400 **£4.75**



SX52 6 Black Heatsink will fit TO-3 and TO-220 Ready drilled. Half price value **£1**

SX53 1 Power finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design, pre drilled.  
TO-3 Size 45mm square 20mm high 40p  
TO-66 size 35mm x 30mm x 12mm 35p  
SX54 1 Heat Efficiency Power Finned Heatsink 90mm x 80mm x 35mm High. Drilled to take up to 4 x TO-3 devices **£1.50** each

## SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq. Ins.	Price
FB1	4	9 x 2 1/2"	100	£1.50
FB2	3	11 x 3"	100	£1.50
FB3	4	13 x 3"	156	£2.00

## DOUBLE SIDED FIBREGLASS BOARD


FB4	2	14 x 4"	110	£2.00
-----	---	---------	-----	-------

## SILICON POWER TRANSISTORS — T03

NPN like 2N3055 — but not full spec  
100 watts 50V min.  
10 for **£1.50** — Very Good Value  
100s of uses — no duds  
Order No. SX90
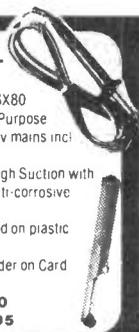
## BI-PAK SOLDER-DESOLDER KIT

Kit comprises ORDER NO. SX80  
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit  
1 Quality Desoldering pump High Suction with automatic ejection Knurled anti-corrosive casing and teflon nozzle  
1.5 metres of De-soldering braid on plastic dispenser  
2 yds (1.83m) Resin Cored Solder on Card  
1 Heat Shunt tool Tweezer Type  
Total Retail Value over **£12.00**  
OUR SPECIAL KIT PRICE **£8.95**



## BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises  
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit  
1 Sheet PCB Transfers 210mm x 150mm  
1 Etch Resist Pen  
1 1/2 lb pack FERRIC CHLORIDE crystals  
3 sheets copper clad board  
2 sheets Fibreglass copper clad board  
Full instructions for making your own PCB boards  
Retail Value over **£15.00**  
OUR BI-PAK SPECIAL KIT PRICE **£9.75**  
ORDER NO. SX81



**PROGRAMMABLE UNI-JUNCTION TRANSISTOR**  
PJT case T0106 plastic MEU22 Similar to 2N6027/6028 PNP Silicon  
Price: 1.9 10 49 50-99 100+ Normal Retail  
Each: 20p 18p 15p 13p Price **£0.35** each

SX33A 6 small (mm) (SDST/SPDT Toggle Switches 240V 5amp **£1.00**  
SX35A 6 small (mm) Rocker Switches 240V 5amp **£1.00**  
SX32A 12 Assorted Jack & Phono plugs, sockets and adaptors, 2.5m, 3.5mm and standard sizes **£1.00**  
SX71 50 BC108 "Fallouts" Manufacturers out of spec on volts or gain You test! **£1.00**  
SX72 A mixed bundle of Copper clad Board Fibre glass and paper. Single and double sided. A fantastic bargain **£1.00**

## 5 watt (RMS) Audio Amp

High quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module

Specification  
\* Max Power Supply 30v \* Power Output 5 watts RMS \* Load Impedance 8-16 ohms \* Frequency response 50Hz to 25KHz—3db \* Sensitivity 70mv for full output \* Input Impedance 50k ohms \* Size 85 x 64 x 30mm \* Total Harmonic distortion less than 5%  
BI-PAK'S give away price

**£2.25**

You could not Build one for this price.



## TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's oplo's, all of which are current everyday usable devices in all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues as well

over £25.00 Our Fight Against Inflation Price —  
— Beat the Budget  
— Down with Depression **JUST £6.50.**




SX38 100 Silicon NPN Transistors—all perfect Coded mixed types with data and eqvt sheet. No rejects. Real value. **£3.00**

SX39 100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt. sheet. No rejects. Fantastic value. **£3.00**

**2N3055** The best known Power Transistors in the World — 2N3055 NPN 115w.  
Our BI-PAK Special Offer Price:  
10 off 50 off 100 off  
**£3.50 £16.00 £30.00**

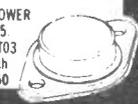**BD312** COMPLIMENTARY PNP POWER TRANSISTORS: TO 2N3055 Equivalent MJ2955 — BD312 — T03 SPECIAL PRICE **£0.70** each 10 off **£6.50**



## MORE BARGAINS!

SX51	60 metres PVC covered Hook-up wire single and stranded. Mixed colours	£1
SX58	25 Assorted TTL Gates 7400 Series. 7401-7460	£1
SX59	10 Assorted Flip Flops and MSI TTL	£1
SX60	20 Assorted Slider Potentiometers	£1
SX62	40 Assorted Pre Sets Hor/Vert etc.	£1
SX79	10 Reed Switches — glass type 3 Micro Switches — with lever	£1

# BI-PAK

Send your orders to Dept EE10 BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDOCK ST WARE HERTS  
TERMS: CASH WITH ORDER SAME DAY DESPATCH. ACCEPTS BARCLAYCARD ALSO ACCEPTED TEL (0920) 3182 GIRO 388 7006 ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 75p per Total order.

# Sinclair ZX Spectrum

**16K or 48K RAM...  
full-size moving-  
key keyboard...  
colour and sound...  
high-resolution  
graphics...**

**From only  
£125!**



First, there was the world-beating Sinclair ZX80. The first personal computer for under £100.

Then, the ZX81. With up to 16K RAM available, and the ZX Printer. Giving more power and more flexibility. Together, they've sold over 500,000 so far, to make Sinclair world leaders in personal computing. And the ZX81 remains the ideal low-cost introduction to computing.

Now there's the ZX Spectrum! With up to 48K of RAM. A full-size moving-key keyboard. Vivid colour and sound. High-resolution graphics. And a low price that's unrivalled.

## **Professional power— personal computer price!**

The ZX Spectrum incorporates all the proven features of the ZX81. But its new 16K BASICROM dramatically increases your computing power.

You have access to a range of 8 colours for foreground, background and border, together with a sound generator and high-resolution graphics.

You have the facility to support separate data files.

You have a choice of storage capacities (governed by the amount of RAM). 16K of RAM (which you can upgrade later to 48K of RAM) or a massive 48K of RAM.

Yet the price of the Spectrum 16K is an amazing £125! Even the popular 48K version costs only £175!

You may decide to begin with the 16K version. If so, you can still return it later for an upgrade. The cost? Around £60.

## **Ready to use today, easy to expand tomorrow**

Your ZX Spectrum comes with a mains adaptor and all the necessary leads to connect to most cassette recorders and TVs (colour or black and white).

Employing Sinclair BASIC (now used in over 500,000 computers worldwide) the ZX Spectrum comes complete with two manuals which together represent a detailed course in BASIC programming. Whether you're a beginner or a competent programmer, you'll find them both of immense help. Depending on your computer experience, you'll quickly be moving into the colourful world of ZX Spectrum professional-level computing.


There's no need to stop there. The ZX Printer—available now—is fully compatible with the ZX Spectrum. And later this year there will be Microdrives for massive amounts of extra on-line storage, plus an RS232/network interface board.



## **Key features of the Sinclair ZX Spectrum**

- Full colour—8 colours each for foreground, background and border, plus flashing and brightness-intensity control.
- Sound—BEEP command with variable pitch and duration.
- Massive RAM—16K or 48K.
- Full-size moving-key keyboard— all keys at normal typewriter pitch, with repeat facility on each key.
- High-resolution—256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.
- ASCII character set—with upper- and lower-case characters.
- Teletext-compatible—user software can generate 40 characters per line or other settings.
- High speed LOAD & SAVE—16K in 100 seconds via cassette, with VERIFY & MERGE for programs and separate data files.
- Sinclair 16K extended BASIC—incorporating unique 'one-touch' keyword entry, syntax check, and report codes.

# um

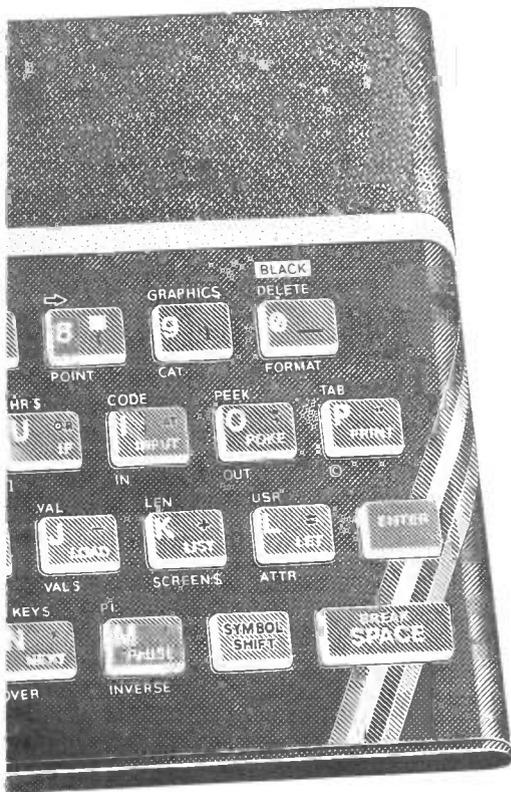


## The ZX Printer – available now

Designed exclusively for use with the Sinclair ZX range of computers, the printer offers ZX Spectrum owners the full ASCII character set – including lower-case characters and high-resolution graphics.

A special feature is COPY which prints out exactly what is on the whole TV screen without the need for further instructions. Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

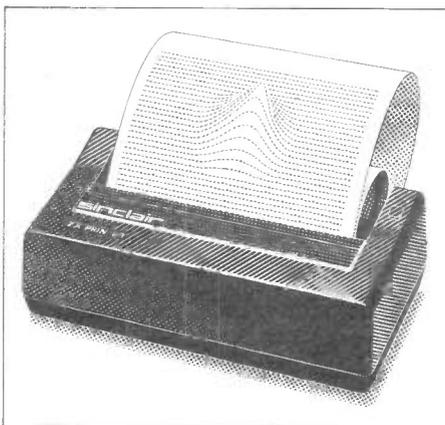The ZX Printer connects to the rear of your ZX Spectrum. A roll of paper (65ft long and 4in wide) is supplied, along with full instructions. Further supplies of paper are available in packs of five rolls.



## The ZX Microdrive – coming soon


The new Microdrives, designed especially for the ZX Spectrum, are set to change the face of personal computing.

Each Microdrive is capable of holding up to 100K bytes using a single interchangeable microfloppy.

The transfer rate is 16K bytes per second, with average access time of 3.5 seconds. And you'll be able to connect up to 8 ZX Microdrives to your ZX Spectrum.

All the BASIC commands required for the Microdrives are included on the Spectrum.

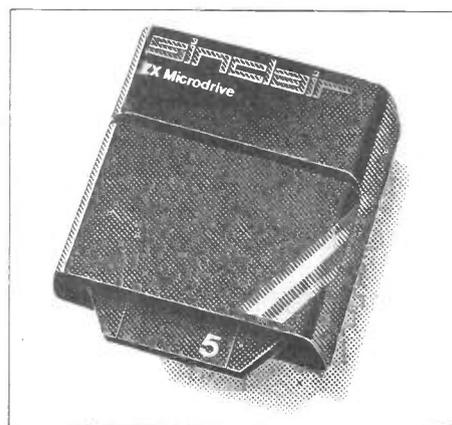A remarkable breakthrough at a remarkable price. The Microdrives are available later this year, for around £50.



## RS232/network interface board

This interface, available later this year, will enable you to connect your ZX Spectrum to a whole host of printers, terminals and other computers.

The potential is enormous. And the astonishingly low price of only £20 is possible only because the operating systems are already designed into the ROM.

# ZX Spectrum

Available only  
by mail order  
and only from

# sinclair

Sinclair Research Ltd,  
Stanhope Road, Camberley,  
Surrey, GU15 3PS.  
Tel: Camberley (0276) 685311.

## How to order your ZX Spectrum

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST – use the no-stamp needed coupon below. You can pay by cheque, postal order, Access,

Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR.

Order

Qty	Item	Code	Item Price £	Total £
	Sinclair ZX Spectrum – 16K RAM version	100	125.00	
	Sinclair ZX Spectrum – 48K RAM version	101	175.00	
	Sinclair ZX Printer	27	59.95	
	Printer paper (pack of 5 rolls)	16	11.95	
	Postage and packing: orders under £100	28	2.95	
	orders over £100	29	4.95	
			Total £	

Please tick if you require a VAT receipt

\*I enclose a cheque/postal order payable to Sinclair Research Ltd for £ \_\_\_\_\_

\*Please charge to my Access/Barclaycard/Trustcard account no. \_\_\_\_\_

\*Please delete/complete as applicable

Signature \_\_\_\_\_

PLEASE PRINT


Name: Mr/Mrs/Miss \_\_\_\_\_

Address \_\_\_\_\_

EVE 810

**FREEPOST – no stamp needed. Prices apply to UK only. Export prices on application.**
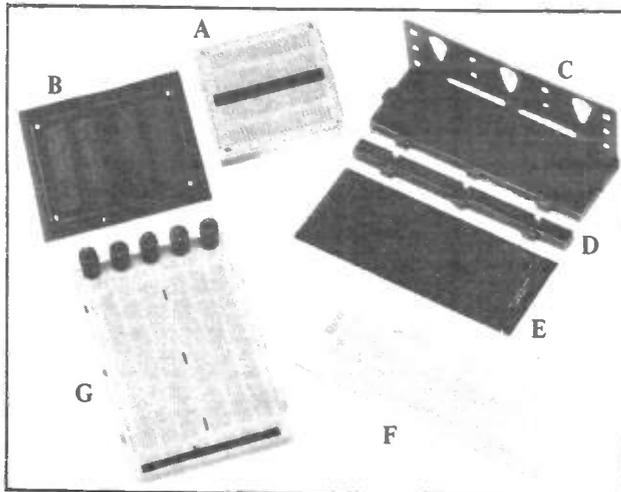
# THE BIGGEST NAME IN BRITISH BREADBOARDS



All BOSS Breadboards directly accept .3", .4", .5" & .6" pitch DIL IC's and have numbered and lettered rows and columns allowing exact location indexing.

- A. **EuroBreadBoard**. 500 contacts, ideal for schools and training establishments.
- B. **EuroSolderBoard**. Exact printed circuit board copy of 'A' enabling progression to permanent and rugged assembly.
- C. **BIMBOARD 1**. 550 contacts plus component support bracket. **BIMBOARD's 2, 3 and 4** also available providing 1100, 1650 and 2200 contacts respectively.
- D. **BIMBUSTRIP**. 2 additional power lines, slot onto any 'C', 'G' or **BIMBOARD DESIGNER**.
- E. **PC BIMBOARD**. Exact printed circuit board copy of 'C' plus 'D' enabling permanent pcb circuits to be generated.
- F. **Layout Pad**. Exact paper copy of 'E' for planning or recording layouts.
- G. **MPUroBreadBoards**. 1422 contacts including power bus strips on all sides. Specifically for MPU circuits it is standard 160 x 100mm Eurocard size.

Adventures with Microelectronics. A beginners book based on **BIMBOARD 1**. Covers simple circuits, built step by step and includes component lists and sources.

Note: All **BIMBOARD's 1, 2, 3 and 4**, **BIMBUSTRIP** and **MPUroBreadBoards** slot onto each other thereby providing larger circuit development working areas.

**JUST RELEASED  
BIMBOARD DESIGNERS.**  
Incorporate 2 **BIMBOARDs** (4 to special order) plus integral fixed 5V and adjustable  $\pm 5V$  to  $\pm 15V$  power supplies.

# BOSS

**INDUSTRIAL MOULDINGS LIMITED**

James Carter Rd, Mildenhall, Suffolk, IP28 7DE  
Tel: Mildenhall (0638) 716101 Telex 818758


TWO FABULOUS OFFERS FROM

# ALCON

**TESTER 20**  
20k $\Omega$ /V a.c. & d.c.  
**THE  
PROFESSIONAL  
SOLUTION  
TO GENERAL  
MEASUREMENT  
PROBLEMS**

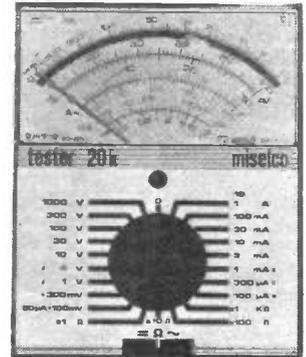**ONLY £29.75**

inc. VAT, P&P, complete with carrying case, leads and instructions.



The best instrument for the workshop, school, toolbox, TV shop and anywhere accurate information is needed quickly and simply.

**Accuracy:** d.c. ranges and  $\Omega$  2%, a.c. 3% (of f.s.d.)  
**40 ranges:** d.c. V 100mV, 1.0V, 3.0V, 10V, 30V, 100V, 300V, 1000V.  
d.c. I 50 $\mu$ A, 100 $\mu$ A, 300 $\mu$ A, 1.0mA, 3mA, 10mA, 30mA, 100mA, 1A, 10A. a.c. V 10V, 30V, 100V, 300V, 1000V.  
a.c. I 3mA, 10mA, 30mA, 100mA, 1.0A, 10A.  
 $\Omega$  0-5.0k $\Omega$ , 0-50k $\Omega$ , 0-500k $\Omega$ , 5M $\Omega$ , 50M $\Omega$ .  
dB from -10 to +61 in 5 ranges.

**Dimensions:** 105 x 130 x 40mm.

and the **INCREDIBLE**



**MINI 20**

**28 ranges**  
20k $\Omega$ /V d.c. & 4k $\Omega$ /V a.c.  
(With protective fuse)

**THE IDEAL  
INSTRUMENT  
FOR THE  
CONSTRUCTOR**

**ONLY £21.60**

(complete with carrying case, leads and instructions)  
Goods normally by return of post.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10.00.

The 28 ranges cover all likely requirements. Operation is straightforward, just turn the selection switch to the required range.

**Accuracy:** 2% d.c. and resistance, 3% a.c.  
**28 ranges:** d.c. V 100mV, 3V, 10V, 30V, 100V, 300V, 600V. d.c. I 50 $\mu$ A, 600 $\mu$ A, 6mA, 60mA, 600mA. a.c. V 15V, 50V, 150V, 500V, 1500V.  
a.c. I 30mA, 300mA, 3.0A. Ohms 0-2k $\Omega$ , 0-2M $\Omega$ .  
dB from -10 to +62 in 6 ranges.

**Dimensions:** 105 x 130 x 40mm.

For details of these and the many other instruments in the Alcon range, including multimeters, components measuring, automotive and electronic instruments please write or telephone:

**ALCON** Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

# ELECTRONIC HOBBIES FAIR


Alexandra Pavilion November 18 – 21 1982

Launched in response to demand for a major national show of the highest quality, EVERYDAY ELECTRONICS, PRACTICAL ELECTRONICS and PRACTICAL WIRELESS are presenting the biggest and best event ever to be staged for the electronic hobbies enthusiast.

If your company is involved in the manufacture of electronic components, equipment, ancillary systems for

electronic projects, home computers, amateur radio, citizens band, video games, musical instruments – you should be there!

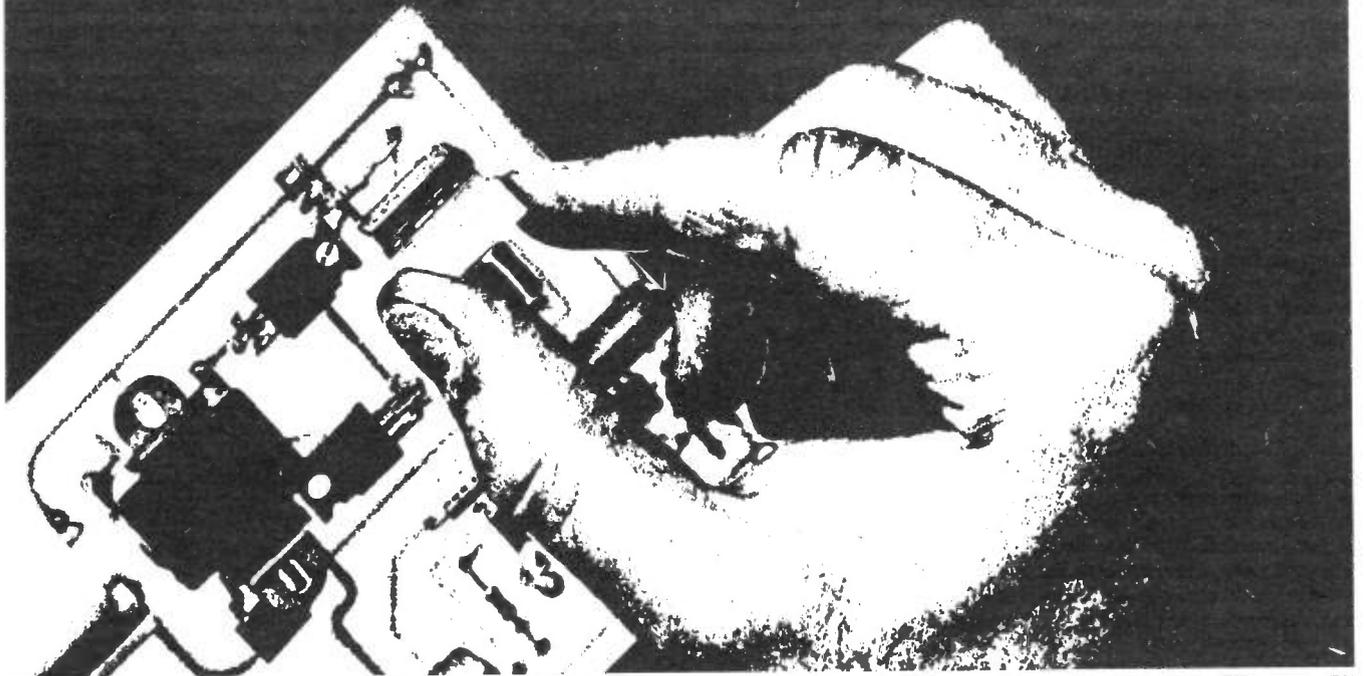For further information about exhibiting contact: The Exhibition Manager, Electronic Hobbies Fair, IPC Exhibitions Ltd., Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ. Tel: 01-643 8040. Extn. 4873.



Please send me details about exhibiting at the



Name \_\_\_\_\_

Position in Company \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

Tel \_\_\_\_\_

Send to: The Exhibition Manager, Electronic Hobbies Fair, IPC Exhibitions Ltd., Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ.

## METERS

Large range of types in stock, also probes, leads, accessories etc.

**PANEL MOUNTING** in 50, 100, 500µA, 1, 5, 10, 50, 100, 500mA; 1A either model.



### MULTIMETERS

NH56A



New — 20KΩV AC/DC/RES/ΩdB in 23 ranges; 130 x 88 x 37mm  
£11.20N

20KΩV AC/DC/RES/ΩdB/transistor Test; in 21 ranges; 145 x 96 x 45mm  
£16.45N

LCO 3 digit (1999) Push button 26 ranges; 170 x 80 x 38mm  
£32.00N

50 x 45mm  
£2.68

### SOLDERING IRONS

Also large stocks of bits, desoldering devices, accessories etc.

ANTEX C-240V £4.60N; X-25-240V £5.30N; CSBP £5.45N; XSBP £5.55N; S14 Stand £1.70N.  
DRYX 50 watt watt, controlled £13.75N; Stand £4.00N.  
SOLDER 500gms/18 SWG £7.60; Rosolter braid 1.5m 54p.

DISCOUNTS ON ALL ITEMS EXCEPT PRICES MARKED N

### SWITCHES — Wavechange

Type CK — 1P/12 way; 2P/6 way; 3P/4 way; 4P/3 way; 4Way; Min. Toggles — S7101 SPOT 57p; S7201 OPOT 80p; S7301 3POT £1.84; S7401 4POT £2.75; S7211 1P3W £1.40; Centre off S7103 SPOT 71p; S7203 DPOT 98p. Push Button min 8531 make/8533 break 62p; 8225 OPOT £1.34.  
DUAL IN LINE, ERG colour coded 0.3" x 0.1" format. On/OH single throw 2P SOS2 54p; 4P SOS4 95p; 6P SOS6 £1.38; 8P SOS8 £1.87; 10P SOSO £2.10.  
Low cost D-FL 4P ONS04 85p; 8P ONS08 £1.00.

### KEYBOARD

For use with 2XB1 £31.30N; Keyboard Case £13.68N.

### NICAD CHARGERS

For PP3-NC75G £4.95N; For AAC or O-NC1230 £8.20N.

### BOXES

High quality Black ABS plastic or diecast plain or stove grey

L	W	D	ABS	PLAIN	STOVE GREY
50	50	25	5001P	90p	5001 123p
100	60	25	2002	96p	5002P 156p
113	63	31	2003	109p	5003P 143p
121	66	40	2004	115p	5004P 182p
152	82	50	2005	134p	5005P 218p
192	113	61	2006	235p	5006P 314p



### VERO RANGE Plastic Boxes

L	W	D	Price
72	47	25	21024 50p
120	50	35	21390 78p
180	110	55	21391 145p

### G RANGE Professional Instrument Cases

134	90	44	21089	£7.28N
224	140	64	21090	£11.02N
302	170	84	21091	£14.98N

# ELECTROVALUE

FOR SERVICE YOU CAN TRUST

### VEROBOX CASES

ABS, Lt. grey top, dk. grey bottom + 2 ali panels

L	D	H	TYPE	PRICE
205	140	40	21034	£4.52
205	140	75	21035	£6.02
205	140	110	21036	£8.54
180	120	39	21037	£4.11
180	120	65	21038	£4.40
180	120	90	21039	£4.88
155	85	39	21040	£3.31
155	85	60	21041	£3.61
155	85	80	21042	£4.30
125	65	30	21047	£2.35
125	65	39	21048	£2.89
125	65	50	21049	£3.37

CATALOGUE 82 70p POST FREE INC. 70p REFUND VOUCHER

### CAPACITORS

#### POLYSTYRENE, SIEMENS

5% Tolerance 160V  
5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF 15p; 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 1n, 1n2, 1n5, 1n8, 2n2, 2n7, 3n3, 3n9, 4n7 12p; 5n6, 6n8, 8n2, 10n 13p.

CERAMIC Very small 1.8, 2.2, 2.7 etc. up to 1n 5p each. 1n5, 2n2, 3n3, 4n7, 6n8 5p; 10n, 22n, 8p; 33n, 47n 7p; 100n 8p.

POLYESTER, SIEMENS LAYER TYPE 7.5mm lead spacing 100V  
1n, 1n5, 2n2, 3n3 5p; 4n7, 6n8, 8n2, 10n, 12n, 15n, 18n, 22n, 27n, 33n, 39n, 47n 7p; 56n, 68n 8p; 82n, 100n 9p; 120n, 150n 11p; 180n, 220n 12p; 270n, 330n, 390n, 470n 15p; 560n, 680n 24p, 10mm spacing 1µF 25p, 15mm spacing 2µF 35p, 22.5mm spacing 1µF 400V 54p; 3.3µF 100V 88p, in-depth stocks.

### ELECTROLYTICS

NON-polar (for LS X-overs) 50V peak 2µF 20p; 4µF 28p; 6, 8, 10, 16µF 32p; 25µF 37p; 40, 60µF 59p; 100µF 89p.

POLARISED SIEMENS or MULLARD FOR QUALITY (µF/V) 1/63, 2/283, 4/763, 6/8/40, 10/25, 22/10 ea. 10p; 10/40, 22/25, 47/10 11p; 47/25 12p; 100/10 13p; 100/25, 100/40 15p; 220/10, 220/16 16p; 220/25 18p; 220/40 20p; 470/10, 470/16, 470/25, 1000/10 19p; 470/40, 1000/16 27p; 1000/25 35p; 1000/40, 2200/16 44p; 1000/63 78p; 2200/40, 4700/16 73p.

Pluggable SIEMENS single ended  
1/63, 2/283, 4/763 10p; 10/63, 22/63 12p; 22/40, 47/16 10p; 47/40 12p; 47/63 15p; 100/16, 100/25 12p; 100/40 15p; 100/63 20p; 220/10, 220/16, 220/25 13p; 470/6, 3, 15p; 470/10 18p; 470/16 18p; 470/25 22p; 470/40 26p; 1000/10 24p; 1000/16 23p.

Large Caps — SIEMENS  
2200/63 £1.77; 4700/40 £1.78; 4700/63 £2.88; 4700/100 £5.54; 10000/16 £1.93; 10000/25 £2.78; 22000/16 £3.20; 22000/25 £4.73.

TANTALUM  
0.1/35, 0.22/35, 0.47/35, 1/35, 2.2/16, ea. 13p; 2.2/35, 4.7/16, 10/6, 3 18p; 4.7/35, 10/16, 22/6, 3, 10/25 18p; 22/16, 22/25, 33/10, 47/6, 3, 100/3 30p.

LOW LEAKAGE Ali, single ended  
0.1/50, 0.22/50, 0.47/50, 4.7/35 10p; 1/50, 2.2/50, 4.7/50, ea. 12p; 10/16, 22/6, 10p; 10/35, 22/10, 22/16, 22/35, 47/6, 47/10 12p; 47/16, 100/6 12p.

NORMAL DESPATCHES WITHIN 24 HOURS

## RESISTORS

½, ¼, ⅓ watt — all 2p each, 10 of one value 15p.  
2% Mullard metal film 5.1 ohms — 300K 5p each, 10 of one value 40p.  
5% wire wound 3W or 7W, most £12 values 1.2 ohms to 8K2 9p ea. 10 for 70pN.

● ALL MERCHANDISE BRAND NEW & GUARANTEED TO SPEC. ●

### POTENTIOMETERS

Carbon rotary (P20) 100 ohms-4M 7in, 220 ohms-2M2 log, ea. 32p, w. switch 90p.  
Dual gang (JP20) 4K7-1M2 lin or log 95p, w. switch £1.50.

### SLIDERS

58mm, low cost 10K-1M log only 29p. Std. 58mm mono 4K7-1M lin or log 79p, stereo matched £1.29. Graduated bezels ea. 34p.

### PRESET

Min. 10mm dia. Horiz. or vert. 100 ohms-1M 13p.

Preset Cermet rectangular type 89P, 100Ω-1M, ea. £1.08.

Preset Cermet 10mm dia. Horiz. or vert. 100Ω-1M 29p.

Plassey MPWT moulded carbon 47 ohms-2M2 ea. 59p.

### CMOS SUPER SAVERS!

4000	14	4015	55	4027	32	4059	18
4001	13	4016	25	4028	50	4070	22
4002	14	4017	42	4029	67	4071	18
4006	59	4018	55	4030	50	4072	18
4007	14	4019	38	4041	60	4081	18
4008	50	4020	53	4042	52	4082	18
4009	35	4021	50	4043	56	4093	38
4010	35	4022	18	4044	55	4510	50
4011	14	4023	18	4046	75	4511	55
4012	15	4024	44	4049	25	4516	53
4013	28	4025	18	4050	28	4518	45
4014	60	4026	104	4060	90	4520	88

ACCESS & VISA accepted via mail order or telephone. Giro A/c no. 38/671/4002

V.A.T. additional at 15% on total value of all U.K. orders.

FREE POSTAGE and packing on U.K. C.W.O. orders value £5.75 (inc. VAT) and upwards Under £5.75 add 40p (inc. VAT).

DISCOUNTS on orders over £23.00 — 5%  
on orders over £57.50 — 10%

Discounts do not apply to 'Net' items (shown by N after the price) or to orders paid for by credit card

### MAIL ORDERS TO HEAD OFFICE & SHOP —

ELECTROVALUE LTD, 26D St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0NB.

Telephone Egham (STD 0784; London 87) 33603; Telex 264475.

Northern Branch (Personal shoppers only) 880 Burnage Lane, Burnage, Manchester M19 1NA. Telephone 061 432 4945.

Computing Shop: 700 Burnage Lane, Manchester. Tel: 061 431 4888.

Shop hours (all addresses) Mon-Fri 9am-5.30pm, Sat 9am-1.0pm.

# Hear what you're missing

Tired of reading the same old names, the same old reviews and the same old recommendations? Well we've put together an audio spectacular... controversial, informative and fun... and so it should be!

In the October issue

\* Countdown to Compact Disc — No. 1 of a NEW SERIES

\* Reviewed — Bang & Olufsen Beocord 9000 cassette deck and Sony PCM audio processor... digital recording for amateurs.

PLUS!

Tales of woe from our Audioclinic, and some big surprises from America's biggest electronics extravaganza

PRACTICAL October issue OUT NOW



## TITAN TRANSFORMERS AND COMPONENTS

CENTRAL HALL CHAMBERS, GRIMSBY DN32 7EG

Mail Order only — Prices include 15% VAT

Inverters—high quality frequency stable 12 volts DC. 240 AC/50Hz/100, 250 and 300 watt. 24 volts DC/240 AC/50Hz/500 watt.

Voltage Stabilisers—Coarse or fine regulation. High speed Null switching 170/260V/50Hz. 100VA to 5KVA plus other sizes.

Adaptors—Switchable 6·7·5-9V 300MA unregulated. 6·7·5-9V 250 MA regulated.

Battery chargers—2 volts & 6 volts, power supplies and a full range of transformers.

Send S.A.E. for details of product you are interested in.

## WHY USE STRIPBOARD?

Make your own PCB. It's easy:  
"GET YOU STARTED" KIT  
12V Mini Drill (takes ½A).  
1mm Bit.  
25 sq. ins. Copper Clad.  
PCB Etchant for ½ ltr.  
Tweezers and Dish.  
Fine Etch Resist Pen.  
Instructions. Only £6.00.  
"SUPER" KIT As above with:  
3 Pens, Fine-Med.-Thick.  
75 sq. ins. Copper Clad.  
3 Sheet Transfers—Etch Resist.  
Only £8.50.

SIMPLE PCB DRILL  
12V Motor with chuck attached with 3 collets 0·8 to 2·0mm. £4.50.  
PCB ETCHANT  
Double strength to make ½ ltr. solution. 90p.  
ETCH RESIST PENS  
Set of 3, Fine-Med.-Thick. £1.80.  
COPPER CLAD BOARD  
6" x 6" x 1mm on Pax. 25p sheet.  
Prices are inclusive but add 60p P & P to each order.  
Cheques & P.O.'s payable to POPS Components.

## POPS COMPONENTS

38 Lower Addiscombe Rd, Croydon CR0 6AA

# AUDIO ELECTRONICS

## TEST EQUIPMENT SPECIALISTS

RETAIL-EXPORT-MAIL ORDER ALL MODELS ON DISPLAY

CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK

ALL PRICES INCLUDE VAT

### DIGITAL MULTIMETERS All models complete with leads and batteries



Hand Held Models 3 1/2 digit LCD (UK C/P 65p)	2010A LED 31 range 10A AC/DC basic 0.1% (Sabtronics)	£81.50
KD25C 13 Range 0.2A DC with carry case	TM353 LCD 27 range 2A AC/DC basic 0.15% (Sinclair)	£86.25
KD30C 26 range 1A AC/DC 200 Meg ohm with carry case	2015A LCD 31 range 10A AC/DC basic 0.1% (Sabtronics)	£89.50
28 range 10A AC/DC version of above	TM351 LCD 29 range 10A AC/DC basic 0.1% (Sinclair)	£113.85
2033A 26 range push button 2 amp AC/DC	2001 LCD 28 range plus 5 range capacitance meter 10A AC/DC Basic 0.1% (Pantec)	£108.00
188m/6011A 15 range + Hfe tester push button 10A DC	TM451 4 1/2 digit 0-03% basic. All facilities Sinclair	£171.00
188m 30 range plus Hfe tester. Rotary switch 10A AC/DC	1503A 4 1/2 digit LCD 30 ranges 10A AC/DC 4 MHz counter. 4 kHz oso 0.05% basic (Thurby)	£171.00
2037A 28 range 0.1% 2A AC/DC + 2 temp. ranges push button	1503HA As above but 25A and 0.03% AC Adaptors (2U10A & 20:5A only)	£189.75
129 25 range 0.8% basic 10A AC/DC rotary switches (Keithley)	Cases TM351/353 £6.84; 2001 £7.50; 1503 £20.45	£5.69
130 As model 129 but 0.5% basic	Touch and hold probe THP 20	£14.95
Bench Models 3 1/2 digit LCD unless stated (UK C/P 90p)		

### FREQUENCY COUNTERS (All models battery operated) (UK C/P £1)

PFM200A Pocket 8 digit LED 200 MHz 10 mV (Thandar)	8000B 9 digit LED 3 range 1000 MHz Bench (Sabtronics)	£178.00
Max 50 50 MHz 6 digit LED Pocket (GSC)	TF040 8 digit LCD 40 MHz (600 MHz with TP600) (Thandar)	£126.50
Max 550 6 digit LED Pocket (GSC)	TF200 8 digit LCD 2 range 200 MHz (600 MHz with TP600) (Thandar)	£166.75
8110A 8 digit LED 2 range 100 MHz Bench (Sabtronics)	TP600 600 MHz prescaler (Thandar)	£43.13
8610A 8 digit LED 3 range 600 MHz Bench (Sabtronics)	TP400 1 MHz prescaler	£74.75
Max 100 5Hz-100MHz 8 digit bench LED (GSC)	OPTIONS	
8610B 9 digit LED 3 range 600 MHz Bench (Sabtronics)	TF series carry case	£6.84
	AC adaptors	£5.69
	'8' series AC adaptors	£5.69
	All model probe kits	£7.95

### HAVE A BANANA! Low cost reliable meters (All supplied with batts/leads) (UK C/P 55p)

BANANA 15 range pocket 20K/Volt plus cont. buzzer	AT1020 18 range Deluxe 2KV & Hfe Tester	£17.50
MH55 10 range pocket 2K/Volt	TMK500 23 range plus 12A DC plus cont. buzzer 30K/Volt	£21.50
ST5 11 range pocket 4K/Volt	188m 36 range large scale 10A AC/DC 50K/Volt	£28.50
NH56R 22 range pocket 20K/Volt	AT210 21 range 12A AC/DC 100K/V	£29.50
YN360TR 19 range plus Hfe test 20K/Volt	360TR 23 range large scale 10A AC/DC Hfe test 50 meg ohm 1KV AC/DC 100 K/Volt	£34.95
KRT5001 16 range 10 amp DC range double 50K/Volt	Choose from UK's largest range	
ST303TR 21 range plus Hfe Test 20K/Volt		

### OSCILLOSCOPES Full specifications - state model - send S.A.E.

(UK C/P Single trace £3.00; SC110 £1.00; Dual Trace £4.00; Sargan £3.00)		SARGAN UK made dual trace scopes
SC110A New Model 10 MHz battery portable (Thandar)		DT10 10 MHz
HM307 10 MHz with built in component tester (Hameg)		DT15 15 MHz
3030 15 MHz with built in component tester (Crotech)		DT20 20 MHz
HM203 Dual Trace 20 MHz (Hameg)	OPTIONAL PROBES (All models)	
3131 Dual Trace 15 MHz plus component tester (Crotech)	X1 £7.95; X10 £9.45; X1-X10 £10.50	
CS1582A Dual Trace 10 MHz (Trio)		
CS1586A Dual Trace 20 MHz (special price saving £43.00) (Trio)		

### GENERATORS All mains operated (UK C/P £1.00)

AUDIO 4 band Sine/SQ output		TE220 Max. distortion 1% 20Hz/200KHz	£69.95
LAB27 Max. distortion 0.5% - 1% (Leader) 10Hz-1MHz		LAB27 Max. distortion 0.5% - 1% (Leader) 10Hz-1MHz	£80.25
AB202A Max. distortion 0.5% (Trio) 20Hz-200KHz		AB202A Max. distortion 0.5% (Trio) 20Hz-200KHz	£78.20
RF (All with Int./Ext. Mod. Var. O-P)		TE200 100 KHz - 100 MHz 6 band (300 MHz harm)	£56.95
LSG17 100KHz-150MHz (450MHz Harm) Leader		LSG17 100KHz-150MHz (450MHz Harm) Leader	£71.30
88402 100 KHz - 30 MHz 6 band (Trio)		88402 100 KHz - 30 MHz 6 band (Trio)	£88.00
FUNCTION All sine/sq/triangle/TTL etc.		5020A 1 Hz - 200 KHz (Sabtronics)	£90.00
T8100 1 Hz - 100 KHz (Thandar)		T8100 1 Hz - 100 KHz (Thandar)	£86.95
T8102 0.2 Hz - 2 MHz (Thandar)		T8102 0.2 Hz - 2 MHz (Thandar)	£168.75
PULSE Various O-Ps and functions - VERY FAST		T8105 5 Hz - 5 MHz (Thandar)	£97.75
T8105 5 Hz - 5 MHz (Thandar)		4001 Ultra-variable 0.5Hz-5MHz (GSC)	£113.85

### JUST A SELECTION OF OUR LARGE IN-STOCK RANGE

ORDER BY POST (OR PHONE) OR CALL IN ALL PRICES INCLUDE VAT

Cubegate Limited

# AUDIO ELECTRONICS

301 Edgware Rd. London W2 1BN  
Tel: 01-724 3564

Also at Henrys Radio 404 Edgware Rd. W2

FREE Catalogue send large 20p SAE

# ambit INTERNATIONAL

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST.



BAND 2 TUNERHEADS (Varicap Tuning) EF5804  
2 MOSFET of stages MOSFET mixer, JFET IF preamp, with internally amplified PIN diode AGC. Tuning voltage for BB-108MHz is 2.5V. Buffered LO output AGC input 145 x 70 x 24mm.  
Stock No. 1-24 25+  
40-05804 Blt 24.95 19.65



7255 The latest complete FM tunerhead from RF input to stereo output. MOSFET RF stages, HA11225 IF and PLL IC birdy filter and the TOKO K84437 pilot carrier stereo audio preamp with 26/38kHz muting stereo filter.  
Stock No. 1-24 25+  
40-04378 Built 19.95 18.05



911225A The 911225A is the 7230 'edited' and shrunk into a screened metal case, 97 x 56 x 24mm. The unit is ideally suited to use with synthesised tuner systems.  
Stock No. 1-24 25+  
40-91225 Built 20.82 16.25




944378 'Hydarfi' series decoder module with the TOKO K84437 pilot carrier stereo audio preamp with 26/38kHz muting stereo filter.  
Stock No. 1-24 25+  
40-04378 Built 19.95 18.05



DFCM500 Wide range digital frequency/capacitance meter. Frequency ranges; 0-1MHz, 1-50MHz and 80-500MHz. 8 digit LED display, mains or Ni-Cad battery operation.  
Stock No. 1-24 25+  
40-01500 Kit 95.95 86.50



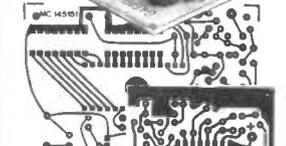AUTBRIDGE  
An Automatic power tracking VSWR and self-ranging power meter. Complete Kit: All PCBs, board mounted components, meters, case (undrilled), transformer etc.  
Stock No: 40-40400 £52.86 + £1.50 P&P



FET DIP OSCILLATOR  
An essential piece of test equipment for the RF constructor. GDO or WM function covering 1.6-215MHz in five ranges. Audio and meter indication. Kit includes, fibre glass PCB, all components, all hardware, punch, painted and screen printed case, wire etc. for coils and printed scale.  
Stock No. 1-24 25+  
40-16215 Kit 17.90 16.20



10MHz SSB GENERATOR  
PCB. All components, eight-pole crystal filter.  
Stock No. Price  
40-10700 £29.65



R&W PROJECT AND DATABRIEF PCBs  
High quality glass fibre printed circuit boards for projects and Databriefs published in Radio & Electronics World.  
27MHz Deviation Meter PA105 £1.98  
TV Pattern Generator MC145151 £2.57  
2m Pre-amp K84417 (Undrilled) £0.60  
0.30V PSU 2m PA Mk II £5.14  
ULN3859 (Undrilled) £0.64  
SSB Exciter HA12017 £2.16  
Up Converter £4.75



2m PRE-AMP  
Very compact low-noise MOSFET 2m pre-amp. Gain 22dB. Noise figure, less than 1.5dB. I/P and O/P impedance; 50 ohm size; 34 x 9 x 15mm. From April '82 R&W.  
Stock No. 1-24 25+  
40-14400 Kit 2.55 2.30

70cm PRE-AMP  
Compact low-noise pre-amp. Gain at 433MHz; 13dB. I/P and O/P impedance 50 ohms. Size 50 x 10 x 17mm. From March '82 R&W.  
Stock No. 1-24 25+  
40-07000 Kit 3.90 3.60

2m POWER AMP  
20 watt 144MHz linear power amplifier. 10dB gain, 2W input - 20W output. Automatic switched relay. By-passes power amp in receiver mode. Developed from original class C version in Dec 81 R&W. High power output relay. Pre-drilled heatsink, optional RX pre-amp. Kit only.  
Stock No. 1-24 25+  
40-14421 Less Preamp 28.50 25.65  
40-14422 With Preamp 30.40 27.36

### AND THERE'S PLENTY MORE IN THE CATALOGUE 70p inc.

RETAIL SHOP OPENING HOURS  
Monday to Thursday 8.30-6.30  
Friday 8.30-8.30 Saturday 9.00-5.30  
(Access + Barclaycard orders accepted)

NOW IN STOCK  
MF10 - National's new Dual Switched-Capacitor Filter.  
Price £5.05

PRICES SHOWN EXCLUDE VAT. P&P 50p per order. Normal delivery 48 hours

AMBIT INTERNATIONAL DEPT. EE  
200 North Service Road, Brentwood, Essex  
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

# THE FUTURE IS HERE..



This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory. You learn the practical way in easy steps mastering all the essentials of your hobby — to start or further a career in electronics — as a self-employed servicing engineer. All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time for advice or help during your work. A certificate is given at the end of every course.

**New Job? New Career? New Hobby? Get into ELECTRONICS Now!**

**Training People For Tomorrow**


British National Radio  
& Electronics School

**POST  
NOW**

**SPECIALISTS IN ELECTRONICS TRAINING FOR OVER 40 YEARS**

# CONQUER THE CHIP
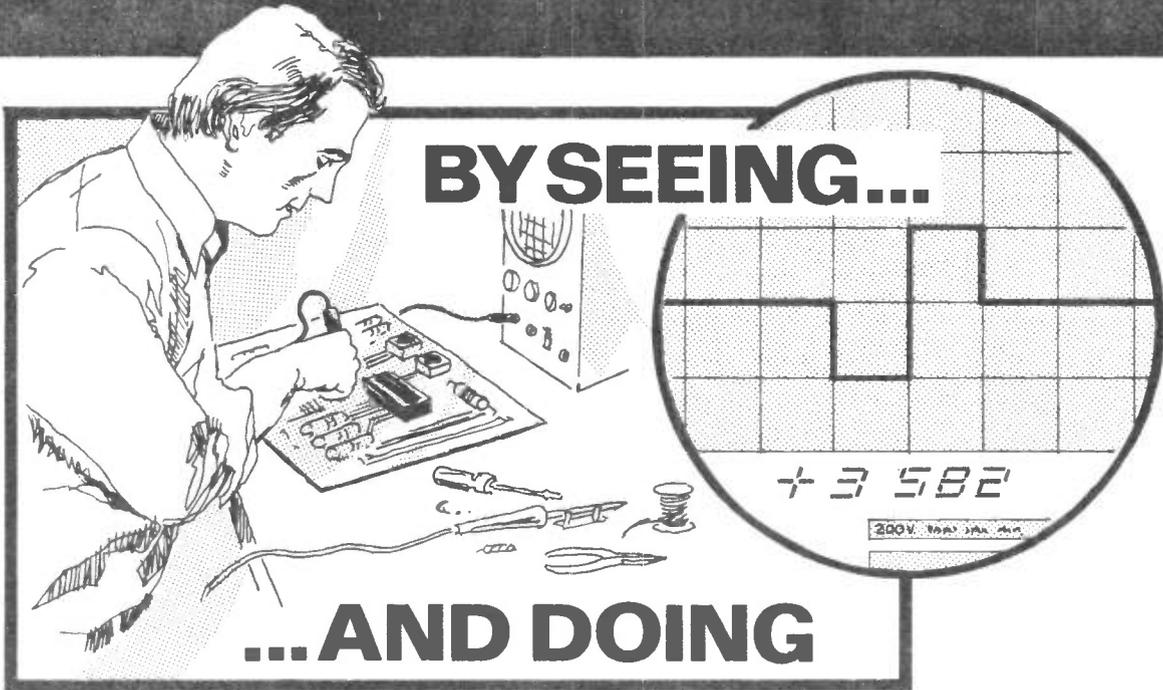
## The PRACTICAL way to master electronics in your own home



- Build a modern oscilloscope.
- Recognise and handle current electronic components.
- Read, draw and understand circuit diagrams.
- Carry out 40 experiments on basic electronic circuits used in modern equipment.
- Build and use digital electronic circuits and current solid state 'chips'.
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

### FREE!

COLOUR BROCHURE



POST NOW TO:—

Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I am interested in:—

- COURSE IN ELECTRONICS as described above
- MICROPROCESSORS AND COMPUTER TECHNOLOGY
- RADIO AMATEUR LICENCE
- OTHER SUBJECTS — List below

BLOCK CAPS PLEASE




EE/10/820

British National Radio & Electronics School Reading, Berks. RG1 1BR.

### HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TDR300K Remote Control Dimmer	£14.30
MK6 Transmitter for above	£ 4.20
TD300K Touchdimmer	£ 7.00
TDE-K Extension kit for 2-way switching for TD300K	£ 2.00
LD300K Rotary Controlled Dimmer	£ 3.50

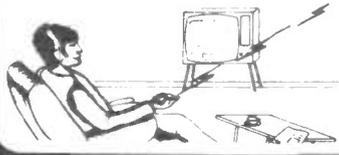

### DISCO LIGHTING KITS

**DL 1000K**  
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **Only £14.60**



**DL2100K**  
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1 Allowing audio ("beat")—light response. **60p**

**NEW DL3000K**  
This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust—simply connect to mains supply & lamps. **Only £11.95** (1Kw/Channel)

### TEACH-IN '82

EE Minilab ..... £13.50  
Parts 1-6 ..... £7.50  
Parts 7-12 ..... £4.90  
Special price for all kits purchased together ..... £23.50  
woodwork not included  
The above kits include all the components specified in the Teach-In '82 projects parts 1—12 plus sockets for ICs specified.

### REMOTE CONTROL

Published remote control systems tend to be quite complex, requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infra-red, our KITS range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs or three analogue outputs for controlling, e.g., TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, triacs, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices. We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself! SEND US 30p and a stamped addressed envelope for your copy TODAY!



**LCD 3 1/2 DIGIT MULTIMETER**  
16 ranges including DC and AC voltage, DC current and resistance+MPN & PNP transistor gain and diode check, input impedance 10M. Size 155x88x31mm. Requires PP3 9v battery. **ONLY £31.00**

### TRANSISTORS

BC108 ... 8p	BFY50 ... 20p
BC109 ... 15p	TIP31A ... 40p
BC182 ... 8p	TIP32A ... 40p
BC182L ... 8p	2N3055 ... 45p
BC212 ... 8p	2N3442
BC212 ... 9p	115w 140v
BC327 ... 12p	..... 90p
BC337 ... 13p	2N3819 N ch fet ..... 20p

**VMOS POWER FETS**  
VN10KM 0.5A/60v ..... 52p  
VN66AF 2A/60v ..... 88p

### 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at preset times once per day. Kit contains: AY-5 1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



CT1000K Basic Kit ..... £14.90  
CT1000K with white box (56 131 x 71mm) (Ready Built) ..... £22.50

### 3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK102. **£5.00**

### DISPLAYS

CQX87A 0.5" dual, c.a. Red £1.80  
DL340M 0.1" 4-Digit c.c. £4.50  
FND 500 0.5" c.c. 85p  
FND 507 0.5" c.a. 85p  
MP463 4-digit 0.5" multiplexed c.c. LED Clock Display ..... £2.20



Liquid Crystal Display, 3 1/2 digit, 0.5" digits, d.i.l. package ..... £6.00  
KL901 9-digit, 7-seg, 0.1" c.c. LED calculator display with red filter ..... 55p

**FREE SHORT FORM CATALOGUE**—send SAE (6" x 9"). We also stock Vero, Books, Resistors, Capacitors, Semi-Conductors etc.

Add 55p postage & packing +15% VAT to total Overseas Customers.  
Add £1 75 (Europe), £4.50 (elsewhere) for p&p. Send S A E for further STOCK DETAILS. Goods by return subject to availability. 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)

### DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multi-meter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.



**Price £15.50**

**FAST SERVICE · TOP QUALITY · LOW LOW PRICES** ALL PRICES EXCLUDE VAT  
No circuit is complete without a call to

**TK ELECTRONICS**  
11 Boston Road London W7 3SJ

TEL: 01-567 8910 ORDERS  
01-579 9794 ENQUIRIES  
01-579 2842 TECHNICAL AFTER 3PM

## HOME CONSTRUCTOR TURNTABLE KITS

### INPUT DESIGN LTD

THE LEADING MANUFACTURERS OF TURNTABLES IN KIT FORM

NORMAL RETAIL PRICE £49.50

**SPECIAL INTRODUCTORY OFFER TO READERS OF EE**  
**£44** inc VAT (P & P £1.95)

This kit includes AC Synchronous motor (as used on £350 decks), Pulley, Belt, Drive Hub, Spindle, Bearing, Glass Platter, Felt Mat, Switch, Electronics, Cable and full instructions together with blueprint for plinth assembly. Any other parts (ie Lid) available as optional extras.

**5 YEAR GUARANTEE—MONEY BACK IF NOT SATISFIED**

• KITDECK 2 Still £115 •

Pay by Barclaycard, Access or CWO. Export: Write for Pro-forma.

**INPUT DESIGN LTD**  
Palace Street, Biggleswade, Beds. SG15 5DP.  
Telephone: Biggleswade (0767) 316655 Telex: S26671



**METERS: 110 x 82 x 35mm**  
30µA, 50µA, 100µA. £5-90. Post 50p.

**METERS: 45 x 50 x 34mm**  
50µA, 100µA, 1mA, 5mA, 10mA, 25v, 1A, 2A, 5A 25V. £2-90. Post 30p.

**METERS: 60 x 47 x 33mm**  
50µA, 100µA, 1mA, 5mA, 10mA, 100mA, 1A, 2A, 25v, 50v, 50-0-50µA, 100-0-100µA. £4-76. VU meters. £5-32. Post on above meters 30p.

Silicone grease 50g £1-32 Post 14p.

**NI-CAD BATTERY CHARGER**  
Led indicators charge-test switch. For PP3, HP7, HP11 & HP2 size batteries. Price £5-85 Post 94p.

### MULTI-METER

7N 360TR  
20,000 ohm/volt  
DC Volts: 0-1, 0-5, 2-5, 10-150—250-1,000v.  
AC Volts: 10-50, 250-1,000



**RESISTANCE RANGES**  
X1, X10, X1K, X10K  
£14-10  
P.&P. 87p

### TRANSFORMERS

<b>240v Primary</b>		
3-0-3v	100mA	82p
6-0-6v	100mA	87p
6-0-6v	250mA	£1-22
12-0-12v	50mA	92p
12-0-12v	100mA	£1-15
Post on above transformers 48p.		
9-0-9v	1A	£1-80
12-0-12v	1A	£2-40
15-0-15c	1A	£2-60
6-3v	1 1/2A	£1-80
6-0-6v	1 1/2A	£2-10
Post on above transformers 87p.		

All above prices include V.A.T. Send 80p for new 1982 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

All goods despatched within 3 days from receipt of the order.

**M. DZIUBAS**  
158 Bradshawgate, Bolton  
Lancs. BL2 1BA

# E.E. PROJECT KITS

I.C.s  
TRANSISTORS  
CAPACITORS

TOOLS  
RESISTORS  
HARDWARE

CASES  
KITS

# MAGENTA

Make up your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS and HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project—you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- INSTRUMENT PRE AMP** Aug. 82. £7-02
- TWO TONE DOORBELL ALARM** Aug 82, less case and bell transformer. £8-82
- CB ROGER BLEEPER** Aug 82 £8-47
- BRAKE LIGHT RELAY** July 82. £4-70
- 2-WAY INTERCOM** July 82. £4-11
- ELECTRONIC PITCH PIPE** July 82 £4-91
- REFLEX TESTER** July 82. £7-07
- SEAT BELT REMINDER** June 82. £3-73
- EGG TIMER** June 82. £4-95
- TWO TONE TRAIN HORN WITH REMOTE TRIGGER OPTION** May 82. £11-26
- CAR LED VOLTMETER** less case, May 82. £2-89
- LIGHTNING CHESS BUZZER** May 82. £8-28
- 2k RAM PACK** Apr 82 less case £13-78
- V.C.O. SOUND EFFECTS UNIT** Apr 82 £11-56
- CAMERA OR FLASH GUN TRIGGER** Mar 82. £12-41 less tripod bushes.
- POCKET TIMER** Mar 82. £3-71
- GUITAR TUNER** Mar 82. £15-83
- CAR OVERHEATING ALARM** Feb. 82. £9-61
- SIMPLE STABILISED POWER SUPPLY** Jan. 82. £24-58
- MINI EGG TIMER** Jan. 82. £3-94
- SIREN MODULE** Jan. 82, less speaker, £5-57
- MODEL TRAIN CHUFFER** Jan. 82. £8-27
- SQUARE SIX** Dec. 81. £4-70
- GUITAR ADAPTOR** Dec. 81. £3-76
- REACTION METER** Dec. 81. £17-55
- ELECTRONIC IGNITION** Nov. 81. £25-88
- SIMPLE INFRA RED REMOTE CONTROL** Nov. 81. £18-98
- PRESSURE MAT TRIGGER ALARM** Nov. 81. £8-27 less mats.
- EXPERIMENTAL CRYSTAL SET** Nov. 81, Less aerial. £5-99
- Headphones** £2-98 extra.
- CAPACITANCE METER** Oct. 81. £23-51
- SUSTAIN UNIT** Oct. 81. £12-76
- 'POPULAR DESIGNS', Oct. 81.**
- 'TAPE NOISE LIMITER'** £4-37
- HEADS AND TAILS GAME** £2-52
- CONTINUITY TESTER** £3-95
- PHOTO FLASH SLAVE** £3-46
- FUZZ BOX** £7-29
- OPTO ALARM** £6-78
- SOIL MOISTURE UNIT** £5-81
- ICE ALARM** £7-39
- 8-12V POWER SUPPLY** Sept. 81. £17-98
- CMOS CAR SECURITY ALARM** Sept. 81. £9-08
- CMOS DIE** Sept. 81. £7-99
- LED SANDGLASS** Aug. 81. £8-53
- CMOS METRONOME** Aug. 81. £8-23
- COMBINATION LOCK** July 81. Less case. £19-58
- BURGLAR ALARM SYSTEM** June 81 less bell, loop & Mic's. £40-98
- TAPE AUTO START** June 81. £12-78
- LIGHTS REMINDER AND IGNITION LOCATOR** E.E. May 81. £5-66
- SOIL MOISTURE INDICATOR** E.E. May 81. £4-09
- GUITAR HEADPHONE AMPLIFIER** E.E. May 81. £4-23
- PHONE BELL REPEATER / BABY ALARM** E.E. May 81. £5-66
- INTERCOM** April 81. £22-23
- SIMPLE TRANSISTOR & DIODE TESTERS** Mar. 81. Ohm meter version £2-92, Led version £2-73
- MINI SIREN** Mar. 81. £8-04
- LED DICE** Mar. 81. £8-44
- LED FLASHER** Mar. 81. £4-29
- MODULATED TONE DOORBELL** Mar. 81. £8-64
- BENCH POWER SUPPLY** Mar. 81. £53-47
- THREE CHANNEL STEREO MIXER** Feb. 81. £18-69
- SIGNAL TRACER** Feb. 81. £8-17 less probe.
- NI-Cd BATTERY CHARGER** Feb. 81. £13-91
- ULTRASONIC INTRUDER DETECTOR** Jan. 81 less case. £53-47
- 2 NOTE DOOR CHIME** Dec. 80. £10-32
- LIVE WIRE GAME** Dec. 80. £11-78
- GUITAR PRACTICE AMPLIFIER** Nov. 80. £12-82 less case. Standard case £3-84. High quality case £8-33.
- SOUND TO LIGHT** Nov. 80. 3 channel. £21-34
- TRANSISTOR TESTER** Nov. 80. £11-63 inc. test leads.
- AUDIO EFFECTS UNIT FOR WEIRD SOUNDS** Oct. 80. £13-11
- BICYCLE ALARM** Oct. 80. £10-35 less mounting brackets.
- IRON HEAT CONTROL** Oct. 80. £5-86
- TTL LOGIC PROBE** Sept. 80. £5-18
- ZENER DIODE TESTER** June 80. £8-66
- 4 STATION RADIO** May 80. £16-29 less case.
- LIGHTS WARNING SYSTEM** May 80. £4-68
- BATTERY VOLTAGE MONITOR** May 80. £5-16
- CABLE & PIPE LOCATOR** Mar. 80. £4-11 less coil former.
- KITCHEN TIMER** Mar. 80. £14-65
- STEREO HEADPHONE AMPLIFIER** Mar. 80. £18-15
- MICRO MUSIC BOX** Feb. 80. £16-26
- Grey Case £3-99 extra.**
- SIMPLE SHORT WAVE RECEIVER** Feb. 80. £25-88, Headphones £2-95
- SLIDETAPE SYNCHRONISER** Feb. 80. £12-30
- MORSE PRACTICE OSCILLATOR** Feb. 80. £4-62
- SPRING LINE REVERS. UNIT** Jan. 80. £25-86
- UNIBOARD BURGLAR ALARM** Dec. 79. £8-03
- BABY ALARM** Nov. 79. £9-60
- CHASER LIGHTS** Sept. 79. £23-40
- SIMPLE TRANSISTOR TESTER** Sept. 79. £7-30
- DARKROOM TIMER** July 79. £2-89
- ELECTRONIC CANARY** June 79. £5-86
- MICROCHIME DOORBELL** Feb. 79. £15-83
- THYRISTOR TESTER** Feb. 79. £3-78
- FUSE CHECKER** Oct. 78. £2-31
- SOUND TO LIGHT** Sept. 78. £8-42
- CAR BATTERY STATE INDICATOR** Sept. 78, Less case. £2-09
- R.F. SIGNAL GENERATOR** Sept. 78. £28-72
- IN SITU TRANSISTOR TESTER** June 78. £6-77
- WEIRD SOUND EFFECTS GENERATOR** Mar. 78. £5-39
- AUDIO VISUAL METRONOME** Jan. 78. £5-98
- ELECTRONIC TOUCH SWITCH** Jan. 78. £2-73 less case.
- RAPID DIODE CHECK** Jan. 78. £2-74
- PHONE/DOORBELL REPEATER** July 77. £7-46
- ELECTRONIC DICE** Mar. 77. £5-88

## SOLDERING/TOOLS

- ANTEX X5 SOLDERING IRON** 25W ..... £5-48
- SOLDERING IRON STAND** .. £1-98
- SPARE BITS**. Small, standard, large, 65p each. For X5 + X25
- SOLDER**. Handy size ..... 99p
- SOLDER CARTON** ..... £1-84
- DESOLDER BRAID** ..... 69p
- HEAT SINK TWEEZERS** .... 29p
- DESOLDER PUMP** ..... £6-48
- HOW TO SOLDER LEAFLET** 12p
- LOW COST CUTTERS** ..... £1-69
- LOW COST LONG NOSE PLIERS** ..... £1-68
- WIRE STRIPPERS & CUTTERS** ..... £2-69



MULTIMETER TYPE 2. (YN360TR) 20K o.p.v. with transistor tester. £14-75

### HELPING HANDS JIG £6-30

Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (25 x 1 magnifier attached), used and recommended by our staff.

- VERO SPOT FACE CUTTER** ..... £1-48
- PIN INSERTION TOOL** ..... £1-98
- VEROPINS (pk of 100) 0-1"** ..... 52p
- MULTIMETER TYPE 1 (1,000 opv)** £5-48
- SET, 10 leads with 20 clips** ..... 99p
- RESISTOR COLOUR CODE CALCULATOR** ..... 21p
- CONNECTING WIRE PALETTE** ED. 11 colours ..... 49p

- ILLUMINATED MAGNIFIERS**
- Small 2" dia. (5x mag.) ..... £1-14
- Large 3" dia. (4x mag.) ..... £2-40
- CAST IRON VICE** ..... £2-98
- SOLDERDRIVER SET** ..... £1-98
- POCKET TOOL SET** ..... £3-98
- DENTISTS INSPECTION MIRROR** ..... £2-85
- JEWELLERS EYEGLASS** ..... £1-50
- PLASTIC TWEEZERS** ..... 69p
- PAIR OF PROBES WITH LEADS (cc)** ..... 77p

## TEACH IN 82

All top quality components as specified by Everyday Electronics. Our kit comes complete with FREE COMPONENT IDENTIFICATION SHEET. Follow this educational series and learn about electronics—Start Today.

LIST 1 and LIST 2 together £27-98. LIST 3 £3-98.

★ ★ ★ SPECIAL OFFER ★ ★ ★  
LISTS 1, 2 and 3 all bought together £33-48.

WOODEN CASE KIT also available £11-98—wood, formica, glue, screws etc. Cut to size.

12 part series, reprints available of previously published parts. 45p each.  
**LISTS 1, 2, AND 3 ALL AVAILABLE NOW.**  
**ALSO WOODEN CASE KIT.**

## BOOKS

- SEMICONDUCTOR DATA BOOK** Newnes ..... £5-90
- ELECTRONIC PROJECTS FOR HOME SECURITY** ..... £3-35
- ELECT. PROJECTS IN PHOTOGRAPHY** ..... £3-35
- 110 ELECT. ALARM PROJECTS** ..... £5-35
- MODEL RAILWAY PROJECTS** ..... £1-95
- BASIC ELECTRONICS**. Theory and practice ..... £7-98
- BEGINNERS GUIDE TO BUILDING ELECT. PROJECTS** ..... £1-50

## ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board.

Adventures with Microelectronics £2-55

Component pack £29-64 less battery.

## ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.

Adventures with Electronics £2-40. Component pack £18-98 less battery.

## ADVENTURES WITH DIGITAL ELECTRONICS

New book by Tom Duncan in the popular 'Adventures' series. This book of entertaining and instructive projects is designed for hobbyists and students. It provides a stepping stone to the microprocessor.

The first part deals with the properties of some basic ICs used in digital electronics.

The second part gives details of how to build eight devices—shooting gallery, 2-way traffic lights, electronic adder, computer space invaders game, etc.

For each project there is an explanation of 'how it works' and also suggestions for 'things to try'.

No soldering—all circuits built on 2 Bimboard 1 breadboards.

Adventures with Digital Electronics book £3-25. Component pack £42-50, ref. EEDC. All the components needed including 2 breadboards and hexadecimal keyboard. Available less breadboards £29-98, ref. EEDF. Both less battery.

### MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST  
Price list included with orders or send sase (9 x 4)  
CONTAINS LISTS MORE KITS, PCBs & COMPONENTS

### 1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order.

MORE E.E. KITS PLUS H.E. and E.T.I. PROJECT KITS IN THE PRICE LIST.


MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?
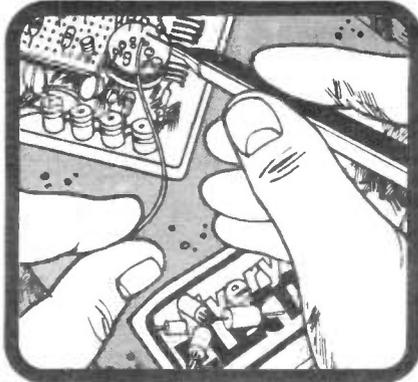
## MAGENTA ELECTRONICS LTD.

ED44, 135 HUNTER ST. BURTON-ON-TRENT, STAFFS., DE14 2ST. 0283 65435. MON.-FRI. 9-5. MAIL ORDER ONLY. ADD 45p P. & P. TO ALL ORDERS. PRICES INC. VAT



Normal despatch by return of post.  
OFFICIAL ORDERS WELCOME.  
OVERSEAS. Payment must be in sterling, IRISH REPUBLIC and BFPO: UK PRICES.  
EUROPE: UK PRICES plus 10%.  
ELSEWHERE: Write for quote.



# CLASSIFIED

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.24 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury

notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

## Receivers and Components

**TURN YOUR SURPLUS** capacitors, transistors etc., into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. 0945-584188. Immediate settlement.

**AERIAL BOOSTERS** trebles incoming signal, price £7.00. SAE leaflets. **VELCO ELECTRONICS**, Ramsbottom, Lancashire BL0 9AG.

**P.C. BOARD S.S.** 12in x 12in 3 for £2.00, glass fibre P.C board S.S. or D.S. 12in x 12in £1.00 each. Add 60p P&P any quantity. **COOPER**, 16 Lodge Road, Hockley, Birmingham B18 5PN.

**300 SMALL COMPONENTS**, transistors, diodes. £1.70 71bs assorted components £4.25 10lbs £5.75. Forty assorted 74 series ICs on panel £1.70. 500 capacitors £3.20. List 20p refundable. Post 60p. Optional insurance 20p. **J. W. B. RADIO**, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

### RIDICULOUS RESISTOR SALE

½ watt carbon film resistors. 5% tol. High quality resistors made under exacting conditions by automatic machines. E12 range 1R0 to 10M0. Lot A. 1000. (25 per value). £8. Lot B. 500 (25 per value) £4.25. Lot C. 100 (25 per value) 90p. Orders over £5 post free. Otherwise postage 15p in £1.  
1000 PCB type **RESISTORS**. £2.50. Bulk purchase enables to offer 1000 mixed preformed. 5% tol. carbon film resistors for PCB mounting. Huge range of preferred values. £2.50 per 1000. 4000 for £8. Postage 15p in £1.  
**AC ADAPTORS**. Ideal for powering small transistor radios and calculators. Input 240V 50Hz. Output 6V 100 m.a. Fitted with calculator plug. Very compact. Should be £3. Our price £1.75. p.p. 25p. 2 for £3.25 post free. 9V 150 m.a. version. £2.50 each. p.p. 25p. 2 for £4.50 post free. **HAVE YOU SEEN THE GREEN CAT?** 1000s of new components, electronic, radio, audio, TV, computers at unbelievably low prices. Send 50p and receive list and **FREE RECORD SPEED INDICATOR**.

### MYERS ELECTRONICS

Dept E.E. 12/14 Harper Street, Leeds LS2 7EA. Tel. 452045.  
New retail premises at above address. Callers welcome 9 to 5. Mon. to Sat.

### Equipment Wire

#### MULTI-COLOUR WIRE-PACKS

28 Different Colours/Bi-colours

DEF 61-12 (part 6) Type 2

Black · Blue · Brown · Green · Grey · Orange

Pink · Red · Violet · White · Yellow · Green/Red

Green/Yellow · Grey/Blue · Grey/Black

Orange/Red · Orange/Black · Pink/Black

Purple/Red · Red/Black · Red/Blue · Red/Brown

Red/Green · White/Black · White/Red

Yellow/Green · Yellow/Red · Yellow/Black

5 metres of each  
7/0.2 set **£6.55** 16/0.2 set **£9.95**

**Start Technology**  
a division of Space Applications Ltd

Ret. EE  
The Millings  
Sawbridgeworth  
Hertfordshire  
CM21 9LY  
0273 724370

no extras  
for VAT p&p  
inclusive prices

**POWER SUPPLIES**, chassis mounted (unboxed). Output fully variable between 5 Volts and 27 Volts. Maximum current 1 Amp between 11 and 15 Volts. £8 post paid. **RUSSELL**, 33 Longridge Avenue, Stalybridge, Cheshire.

## Veteran & Vintage

### "SOUNDS VINTAGE"

The only magazine for all vintage sound enthusiasts, packed with articles by top writers, covering gramophones, phonographs, 78s, wireless, news, history, reviews, etc.  
Bi-monthly. Annual subscription **£8.75** (airmail extra). Send 75p for sample copy.  
**212 Lower High St., Watford, Herts.**

## Educational

**COURSES—RADIO AMATEURS EXAMINATION.** City and Guilds. Pass this important examination and obtain your licence, with an RRC Home Study Course. For details of this and other courses (GCE, professional examinations, etc) write or phone—**THE RAPID RESULTS COLLEGE**, DEPT. JR2, Tuition House, London SW19 4DS. Tel: 01-947 7272 (9 am-5 pm) or use our 24 hour Recordcall Service: 01-946 1102 quoting Dept JR2.

### Courses

**CONQUER THE CHIP**—master modern electronics the practical way by seeing and doing in your own home. Write for your free colour brochure now to **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**, Dept C3, Reading, Berks RG1 1BR.

## Service Sheets

**BELL'S TELEVISION SERVICE** for service sheets on Radio, TV etc. £1.25 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to **BTS**, 190 King's Rd. Harrogate, N Yorkshire. Tel: 0423 55885.

Full size Service Sheets by return **£2** each plus L. S.A.E. except C.T.V./Music Centres from **£3**. Repair data with circuits named T.V.s or early VHS/Phillips Video Recorders **£8-50**. L. S.A.E. for free 50p magazine/quota-tions/etc.

**T.I.S. (E.E.)**, 76 Churches, Larkhall, 0698-883334. Lanarks ML9 1HE.

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for.....

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)


NAME .....

ADDRESS .....

### EVERYDAY ELECTRONICS

Classified Advertisements Dept., Room 2612, King's Reach Tower, Stamford Street, London SE1 9LS Telephone 01-261 5942

Rate: 31p per word, minimum 12 words. Box No. 60p extra.

## Miscellaneous

**PEN WATCH**—Slim stainless steel pen, combining quartz 5 function watch, easy battery change, uses 'Parker' refill, guaranteed. ONLY £3.99. TAIT'S MAIL ORDER, 31 Lime Grove, Addlestone, Surrey.

**FIBRE OPTIC GLASS LIGHT GUIDE.** 0.064" distal diameter, £1.50 metre 0.031", £1.00 metre. Minimum order £3.00. Nyewood Equipment, 91 Tilmore Gardens, Petersfield, Hampshire.

**SEND SAE (15½p)** for our catalogue for details of ADS 6809 single board computer IEEE S-100 standard, S-100 promblaster cluge card, synthetalker etc. Also competitive prices for linear, CMOS, TTL and other kits. MICRO TIMES, 19 Mill Street, Bideford, North Devon EX39 2JR.

**LEARNING MICROCHIPS?** How to build and understand your own working microchip circuits. Electronic games, Burglar alarms, Information sheets. SAE for details. All mail to: G.H.T. LTD, PO Box DR95, Dover, Kent CT16 1UL.

## THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4, 01 531 1568

### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.30	1.90	1.00	0.80
35 to 39	3.52	2.10	1.15	0.85
40 to 43	4.87	2.65	2.05	1.46
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

### SILVER PLATED COPPER WIRE

14 to 30	6.63	3.86	2.28	1.50
31 to 34	7.97	4.41	2.61	1.75
35 to 39	9.31	5.06	3.04	2.00
40 to 43	10.65	5.71	3.47	2.25
44 to 47	11.99	6.36	3.90	2.50
48 to 49	13.33	7.01	4.33	2.75

### TINNED COPPER WIRE

14 to 30	3.97	2.41	1.39	0.94
31 to 34	4.76	2.89	1.61	1.11
35 to 39	5.55	3.37	1.83	1.28
40 to 43	6.34	3.85	2.05	1.45
44 to 47	7.13	4.33	2.27	1.62
48 to 49	7.92	4.81	2.49	1.79

10 x 100 mtr reels 3 amp PVC cable mixed colours 5.00

Prices include P & P vat. Orders under £2 add 20p.

SAE for list of copper and resistance wire. Dealer enquiries welcome.

**ELECTRONIC GAMES.** Build your own microchip games from our detailed circuits. SAE for details. GHT Ltd, PO Box DR95, Dover, Kent CT16 1UL.

**TELETEXT (Oracle/Ceefax)** add-on adaptors for your existing television. Only £149.95 inclusive. Also Prestel. Fantastic colour graphics for microcomputers. Avon Office Services (EE), FREEPOST, Bristol BS10 6BR (0272) 502008 anytime.

## LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec.

This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Sand cheque or P.O. to:  
Roden Products, Dep EE  
High March, Daventry  
Northants, NN11 4QE

**£4.70**

including p & p

**BEGINNERS KIT** covers RADIO, DIGITAL, OSCILLATORS, TIMERS. Instructions and parts for fifteen projects (except 3 volt battery), £9.50. VYTRON (EE-27), 5 Mariners Drive, Portishead, Bristol BS20 8ET.

**SOUND LIGHT.** 750W output, housed plastic box, £13.75; burglar alarm with buzzer, mains operation, £19.50. S. DOLBEAR, 38 Avondale Crescent, Grangetown, Cardiff.

**DIGITAL WATCH REPLACEMENT PARTS.** Batteries, displays, backlights, etc. Also reports publications charts. SAE for full list. PROFORDS, Copners Drive, Holmer Green, Bucks HP15 6SGA.

**FREE MULTIMETER** (Brand new)! When you order over £25 worth of our second-hand Test Gear. For details large SAE to: S.H.E., 5 St Joseph's Park, Ballycruttle, Downpatrick.

# MIGHTY NINETY PACKS

**SUPER VALUE PACKS ALL AT 90p each  
BUY SIX PACKS AND GET A SEVENTH FREE**

Please add 20p per pack postage

Please allow 7 days delivery.

- MM2. 200 ¼ & ½-watt Resistors.
- MM3. 100 1 & 2-watt Resistors.
- MM4. 50 Wirewound Resistors.
- MM5. 100 metal oxide Resistors. 1%, 2% and 5%.
- MM6. 12 asstd potentiometers.
- MM7. 25 asstd skeleton preset Resistors.
- MM8. 50 asstd Electrolytic Capacitors.
- MM9. 100 asstd Ceramic Capacitors P1te, disc. tub and monolithic etc.
- MM10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.
- MM11. 20 asstd Silver Mica Capacitors.
- MM12. 8 Tantulum Bead Capacitors (useful values).
- MM13. 20 asstd Transistors. BC, 2N Series + Power etc.
- MM14. 40 IN4148 Diodes.
- MM15. 20 min. wire-ended Neons.
- MM17. 2 12-volt Relays. Ex nearly new equip.
- MM18. 15 P.C.B. mounting M.E.S. lampholders.
- MM20. 1 240-110 to 12-volt. 100ma Transformer.
- MM21. 1 240-110 to 24-volt 100ma Transformer.
- MM22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green.
- MM23. 300 asstd screws, nuts, washers, self-tappers etc.
- MM25. 80 Assoc. rubber grommets.
- MM29. 75mts equipment, wire, asstd colours and sizes.
- MM30. 3 x 2m length, 3 core, mains cable.
- MM32. 15 30pF Beehive trimmers.
- MM34. 25 min glass reed switch.
- MM35. 10 asstd switches, toggle, slide, micro etc.
- MM36. 10 sub-min SP. C/O slide switch.
- MM37. 10 asstd audio connectors. Din phono etc.
- MM40. 50 Polystyrene capacitors.
- MM45. 35 asstd diodes Zener, rect, signal, switching.
- MM46. 15 asstd Zener diodes.
- MM48. 200 items 4BA asstd length screws, nuts & washers.
- MM49. 200 items 6BA asstd length screws nuts & washers.
- MM50. 3 pieces of veroboard useful sizes, min total 35 sq inch.
- MM51. 10 x 0.2" red LED.
- MM52. 10 x 0.125" red LED.
- MM53. 20 x 0.1 mfd 25v ceramic disc caps.
- MM54. 20 x 0.01 mfd 25v ceramic disc caps.
- MM55. 10 watt audio amp board with circuit.
- MM56. 10 14 pin low profile IC skt DIL.
- MM57. 10 16 pin low profile IC skt DIL.
- MM60. 10 asstd TTL IC's.
- MM63. 50 mixed polyester caps C280, Selmens etc.
- MM64. 5 Press to make min switches.
- MM69. 200 asstd veropins, turret tags, PCB pins etc.
- MM69. 4 min push to break switch.
- MM70. PCB with push SW with attractive chrome plastic knobs 1 x BD241, 1 x BC300, 2 x BC237, 1 x BC204, 4 x 1N4002, 2 x CMOS 4025, 200mm fuse holder + 22 resistors, capacitors, diodes etc.
- MM71. IZNA14 RADIO IC.

# CHORDGATE LIMITED

RETAILER SHOPS AT  
**75 FARRINGTON ROAD  
SWINDON, WILTS.**  
Tel. (0793) 33877  
**21 DEPTFORD BROADWAY  
LONDON SE8**

## BAKER 50 WATT AMPLIFIER

£69 Post 22



Superior quality ideal for Halls/PA systems, Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available).

## BAKER 150 Watt AMPLIFIER 4 Inputs £89

Mono Slave 150W £75. post £2 Stereo Slave £125. post £2  
**DRILL SPEED CONTROLLER LIGHT DIMMER KIT.** Easy to build kit. Controls up to 480 watts AC mains. £3  
**DELUXE MODEL Ready Built.** 800 watts. £5

**STEREO PRE-AMP KIT.** All parts to build this pre-amp. 3 inputs for high, medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2.95

## SOUND TO LIGHT CONTROL KIT MK II

Complete kit of parts, printed circuit. Mains transformer. 3 channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi £15 and all Disco Amplifiers. Cabinet extra £4.50. Post 95p  
**OR COMPLETE READY BUILT CABINET £27**  
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4 or 12 for £7.50.

## MAINS TRANSFORMERS Primary 240V A.C. POST

250-0-250V 80mA. 6.3V 3.5A. 6.3V 1A ..... £5.00 £2  
350-0-350V 250mA. 6.3V 6Amp C.T. .... £12.00 £2  
220V 25ma. 0V 1A £2. 220V 40ma. 6V 2A ..... £3.00 £1

250V 60ma 6.3V 2A ..... £3.50 £1

General purpose tapped outputs voltages available.

2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V. .... £8.00 £2

1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 45, 60 ..... £8.00 £2

2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 45, 60 ..... £10.50 £2

3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 45, 60 ..... £12.50 £2

5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 45, 60 ..... £18.00 £2

6.3-10-16V 1a ..... £2.50 80p 12-0-12V 2a ..... £3.50 £1

6V 1a ..... £2.00 £1 15-0-15V 2a ..... £2.75 £1

6-0-6V 1½a ..... £3.50 £1 20V 1a ..... £3.00 £1

9V 250ma ..... £1.50 80p 20V 3a ..... £3.50 £1

9V 3a ..... £3.50 £1 20-0-20V 1a ..... £3.50 £1

9-0-9V 50ma ..... £1.50 80p 20-40-60V 1a ..... £4.00 £2

10-0-10V 2a ..... £3.00 £1 25-0-25V 2a ..... £4.50 £2

10-30-40V 2a ..... £3.50 £1 15-0-15V Twice ..... £5.00 £2

12V 100ma ..... £1.50 80p 30V 1½a ..... £2.50 £1

12V 750ma ..... £2.00 80p 30V 5a ..... £5.00 £2

12V 3a ..... £3.50 £1 34-0-34V 6a ..... £12.00 £2

12V 2a ..... £3.00 £1 35V 2a ..... £4.00 £1

TOROIDAL 30-0-30V 4 Amp + 20-0-20V 1 Amp £10.00 £2

## CHARGER TRANSFORMERS 2 ELECTIFIERS

6-12V 3a ..... £4.00 £2 6-12V 2a ..... £1.00 80p

6-12V 4a ..... £8.50 £2 6-12V 4a ..... £2.00 80p

## R.C.S. LOUSPEAKER BARGAINS

3 ohm. 6 x 4in, 5in, 7 x 4in. £2.50. 8 x 5in. £3.00.

6in. £3.00. 8in. £3.50. 10in. £4.00. 8 ohm. 2½in. £2.00.

3in., 5 x 3in, 5in. £2.50. 8in. £4.50. 10in. £5.00. 12in. £6.00.

16 ohm. 3½in. 6 x 4in. 5in. £2.50. 8in. £3.50. 10 x 6in. £4.00.

25ohm. 3in. 35 ohm. 3in. £2.50. Many others in stock.

Speaker Covering Material Samples 31p. stamps.

## R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 75p £3.95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.

## PP BATTERY ELIMINATOR. BRITISH MADE £4.50

Mains Transformer Rectifier 9 volt 400ma. Post 75p

stabilised, with overload cutout. Plastic case size 5 x 5½ x 2½.

Suitable Radio/Cassettes. Fully Isolated and Smoothed.

DELUXE Switched Model 8-6-7½-9V 400ma. £7.50. post £1

## THE "INSTANT" BULK TAP ERASER

Suitable for cassettes and all sizes of tape reels.

A.C. mains 200/240V. £9.50 Post

Ideal all Computer, 95p

Tapes, Discs, Cassettes.

## HEAD DEMAGNETISER PROBE £5.00.

A.C. ELECTRIC MOTORS POST 75p.

2 Pole, 240V, 0.2 Amp. Spindle—

1.43 x 0.212in. £1.75. 2 Pole,

240V, 0.15 Amp Double spindle—

1.75 x 0.16in. Each £1.2

120V, .5 Amp Spindle—0.75 x

0.2in. Two in series — 240V. 50p

each. Brush Motor. From a Food

Mixer 240V, .3 Amp High Speed

and Powerful Spindle—0.5 x

0.25in. £2.95 Good Selection.

B.S.R. Motors £4. Garrard Motors £5.

## ALUMINIUM CHASSIS 18 s.w.g. Undrilled, 4 sides, riveted corners: 6 x 4 x 2½in. £1.45; 8 x 6 x 2½in. £1.80; 10 x 7 x 2½in. £2.30; 14 x 9 x 2½in. £3.00; 16 x 6 x 2½in. £2.90; 12 x 3 x 2½in. £1.80; 12 x 8 x 2½in. £2.60; 16 x 10 x 2½in. £3.20.

ALI ANGLE BRACKET 6 x ¼ x ½in. 25p.

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.50; 14 x 9in. £1.45; 6 x 4in. 43p; 12 x 8in. £1.10; 10 x 7in. 96p; 8 x 6in. 72p.

14 x 3in. 72p; 12 x 5in. 72p; 16 x 10in. £1.68; 16 x 6in. £1.10.

ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.

4 x 2½in. £1.00; 3 x 2½in. 80p; 6 x 4½in. £1.60; 8 x 6 x

3in. £2.50; 12 x 5 x 3in. £2.75; 6 x 4 x 3in. £1.80; 10 x 7 x 3in. £3.

HIGH VOLTAGE ELECTROLYTICS 32+32/350V ..... 50p

8/450V ..... 45p 60/450V ..... 95p 32+32/800V ..... £1.80

32/350V ..... 45p 220/450V ..... 95p 32+32+32/352V 75p

32/500V ..... 75p 8+16/450V ..... 75p 16+32+32/500V £2

## BSR HI-FI AUTOCHANGER £18

Stereo Ceramic Cartridge

Plays 12in., 10in., or 7in.

records Auto or Manual.

Quality unit 240V AC

Size 13½ x 11½in.

Post on Deck £2

BSR Single Player P204 cueing device, Ceramic £15 post £2 or with ADC. QLM 30/3 Magnetic cartridge. £20 post £2

BSR P184 QUALITY DECK. BELT DRIVE

VARIABLE SPEEDS, 12in Turntable with

Strobe Markings, Balanced Arm, Magnetic

Cartridge £47 post £3

BSE P170 Single Player. Slim arm. 240V. AC.

Ceramic cartridge. Cueing device. Auto stop.

£20 post £2

B.S.R. P232. Belt drive, magnetic cartridge,

snake arm, cueing device. 12 volt D.C.

£24 post £2

B.S.R. Single Player. 9 volt D.C. motor, rim

drive, ceramic cartridge. £18 post £2

## Radio Component Specialists

337, WHITEHORSE ROAD, CROYDON, SURREY, U.K. TEL: 01-684 1665

Post 65p Minimum. Callers Welcome. Closed Wed. Same day despatch. Access-Barclay-Visa. Lists 31p.

# LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer.

You only supply solder and hook-up wire.

Self assembly simulated wood cabinet - only £4.50 + £1.50 p&p.

Featured in April issue of P.E. Reprint 50p. Free with kit.

## ELECTRONICS ONLY!

Ideal for updating your existing cassette. Includes pcb diagram, all semiconductors, IC's, Capacitors, resistors. +£1.40p&p

**£18-95**

**£32-95**

+ £2.75 p&p.




# P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP
- TAPE COUNTER
- SWITCHABLE E.Q.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES
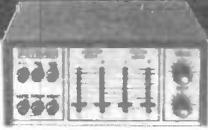
## STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard stereo preamplifier module.
- Attractive birch vinyl finish cabinet, 9" x 8 1/4" x 3 3/4" (approx).
- 10+10 stereo converts to a 20 watt disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features slider controls, push button switches, fascia, knobs and contrasting case. Instructions 50p - supplied free with kit.



**£16-50** + £2.90 p&p.

**SPECIFICATIONS:** Suitable for 4 to 8 ohm speakers. Frequency response: 40Hz - 20KHz. Input sensitivity: P.U. 150mV, Aux 200mV, Mic. 1.5mV. Tone controls: Bass +12dB @ 60Hz, Treble +12dB @ 10KHz. Distortion 0.1% typ. @ 8W. Mains supply: 220-250V 50Hz.

**8" SPEAKER KIT -** Two 8" twin cone dome tic speakers. £4.75 a stereo pair plus £1.70 p&p.

## P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July 81 issue).

For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. **FEATURES:** VHF, MW, LW bands, interstation muting and AFC on VHF. Tuning meter. Two back printed pcb's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" app. Complete with diagram and instructions. Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 3/4". £3.50 Plus £1.50 p&p. Reprint 50p - FREE with kit.



**£17-95** + £2.50 p&p.

**SPECIAL OFFER! TUNER KIT PLUS:**  
 + Matching I.C. 10 watt per channel Power amp kit.  
 + Mullard LP1183 built pre-amp, suitable for ceramic pickup and aux. inputs.  
 + Matching power supply kit with transformer.  
 + Matching set of 4 slider controls for bass, treble + vols. £21.95 + £3.80 p&p.

## 125W HIGH POWER AMP MODULE

**SPECIFICATIONS.** Max output power: 125w rms. Operating voltage (DC): 50-80max. Loads: 4 - 16 ohms. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100 watts: 400mV @ 47K. Typical T.H.D. @ 50 watts: 4 ohms: 1%. Dimensions: 205 x 90 and 190 x 36 mm.



**KIT: £10-50** + £1.15 p&p  
**BUILT: £14-25** + £1.15 p&p


All mail to: 21A HIGH STREET, ACTON, W3 6NG. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/6/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. Send S.A.E. for full list of products. Telephone or mail orders by ACCESS are welcomed.

ALL CALLERS TO: 323 Edgware Rd, London W2. Tel: 01-723 8432, 9.30 - 5.30, closed all day Thurs. ALL PRICES INCLUDE VAT AT 15%.



# INDEX TO ADVERTISERS

Alcon .. .. .	678	Input Design .. .. .	684
Ambit .. .. .	618, 681	Intertest-ICS .. .. .	620
Audio Electronics .. .. .	681	Jupitar Cantab .. .. .	623
Bi-Pak .. .. .	675	Lightning Components .. .. .	622
B.K. Electronics .. .. .	Cov. III	Magenta Electronic Supplies Ltd. .. .. .	685
B.N.R.E.S. .. .. .	682, 683	Maplin Electronics .. .. .	Cov. IV
Boss Industrial .. .. .	678	Phonosonics .. .. .	622
Bradley Marshall .. .. .	625	Pops Components .. .. .	680
Bull, J. .. .. .	672	R. & T.V. Components .. .. .	688
Chordgate .. .. .	687	Radio Component Specialist .. .. .	687
Cricklewood Electronics .. .. .	619, 622	Rapid Electronics .. .. .	621
Dziubas, M. .. .. .	684	Sinclair Research .. .. .	676, 677
Electronic Hobbie Fair .. .. .	679	Titan Transformers .. .. .	680
Electronize Design .. .. .	Cov. II	T.K. Electronics .. .. .	684
Electrovalue .. .. .	680	Vako Display Systems .. .. .	618
Enfield Electronics .. .. .	624	Veleman UK .. .. .	620
Europa Electronics .. .. .	624	Watford Electronics .. .. .	626
Global Specialties Corporation .. .. .	671	Wilmslow Audio .. .. .	620
Greenweld .. .. .	622		
Heath-kit .. .. .	625		

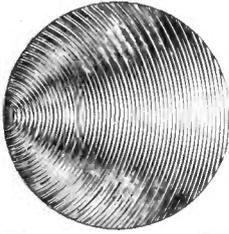

APPROVED  
**thandar**  
STOCKIST

# B.K. ELECTRONICS

## A SOUND CHOICE

APPROVED  
**thandar**  
STOCKIST


★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS  
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY

### STEREO CASSETTE TAPE DECK MODULE.

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K **Signal to noise ratio:** 45dB **Wow and flutter:** 0.1% **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

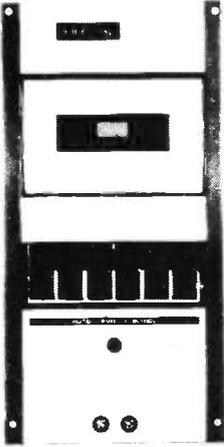**Price £26.70 + £2.50 postage and packing.** Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.



6 piano type keys

**NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").** These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price: -


**15" 100 watt R.M.S.** Impedance 8ohm 59 oz magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.

**12" 100 watt R.M.S.** Impedance 8 ohm, 50 oz magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

**8" 50 watt R.M.S.** Impedance 8 ohm, 20 oz magnet, 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz, Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. **Price: White cone £8.90 each, Black cone/grill £9.50 each, P. & P. £1.25.**
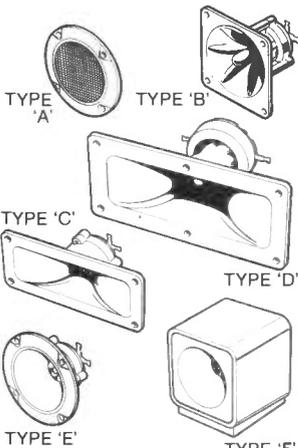
### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



**TYPE 'A'** (KSN1036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. **Price £3.45 each.**

**TYPE 'B'** (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems, etc. **Price £4.35 each.**

**TYPE 'C'** (KSN6016A) 2" x 5" wide dispersion horn. For Hi-Fi systems and quality discos, etc. **Price £5.45 each.**

**TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2,000 c/s). Suitable for Hi-Fi systems and quality discos. **Price £6.90 each.**

**TYPE 'E'** (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems, etc. **Price £4.35 each.**

**TYPE 'F'** (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. **Price £10.75 each.**

U.K. post free (or SAE for Piezo leaflets).



### 1 K-WATT SLIDE DIMMER

- ★ Controls loads up to 1KW.
- ★ Compact Size 4 1/2" x 1 1/2" x 2 1/2".
- ★ Easy snap in fixing through panel/cabinet cut out.
- ★ Insulated plastic case.
- ★ Full wave control using 8 amp triac.
- ★ Conforms to BS800.
- ★ Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's/theatres, etc.

**Price £11.70 each + 50p P&P. (Any quantity.)**



**1000 MONO DISCO MIXER**—completely built and tested employing modern I.C. circuitry. Can be mounted vertical or horizontal into cabinet, console, etc.

Two turntable inputs (ceramic) plus aux. (tape) and mic. inputs. Headphone monitor socket. Compatible with OMP100 Power Amp. (500mV O/P). Controls: Microphone talk over switch with separate volume, treble and bass. Three main fader (level) controls with master volume, treble and bass. Monitor selector switch with monitor level control. Mains On/Off switch. Smart black finish. Size: 535 x 110 x 60mm. Power requirements: 240V A.C.

**Price: £39.99 + £2.25 P & P.**



### B.S.R. P232 TURNTABLE

- P232 Turntable ★ 'S' shaped tone arm
- ★ Belt driven ★ Aluminium platter
- ★ Cueing lever ★ 240 volt AC operation (50Hz)
- ★ Cut-out template supplied
- ★ Used as standard by Hi-Fi and Disco manufacturers
- ★ Fitted with either a magnetic or ceramic cartridge, please state cartridge required

**Price £22.50 + £2.50 P & P.**



### POWER AMPLIFIER MODULES


100 WATTS R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. Vu meter available as an optional extra.

**SPECIFICATION:**  
Max. output power 100 watts R.M.S. (OMP 100)

Loads: (Open and short circuit proof) 4-16 ohms  
Frequency Response: 20Hz-25KHz ± 3dB  
Sensitivity: for 100 watts 500mV at 10K

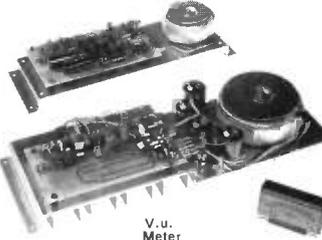T.H.D. 00.1%  
Size: 360 x 115 x 80mm  
Prices: OMP 100 £29.99 P & P £2.00  
V.u. Meter £6.50




V.u. Meter

### MULLARD SPEAKER KITS

A PURPOSELY DESIGNED 40 WATT R.M.S. 8OHM SPEAKER SYSTEM RECENTLY DEVELOPED BY MULLARD'S SPECIALIST TEAM IN BELGIUM. Kit comprises a Mullard 8" Woofer with foam surround and aluminium voice coil, Mullard 3" high power dome tweeter. B.K.E. built and tested crossover, based on Mullard circuit combining low loss components, glass fibre board and recessed loudspeaker terminals. Recommended cabinet size 240 x 216 x 445 mm.

A superb sound at a relatively low cost. Complete with instructions. **Price £14.50 + £1.50 p & p per kit.**

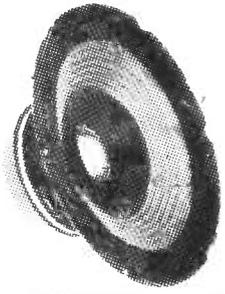New 5" 30 watt mini version of above now available. Recommended cabinet size 180 x 155 x 295 mm. **Price £13.90 + £1.00 p & p per kit.**



### 12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker 50 oz magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. **Attractive blue cone with aluminium centre dome.**

**Price £17.99 ea + £2.50 P & P.**

# B.K. ELECTRONICS

DEPT E.E.

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY


★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



# Make it with MAPLIN
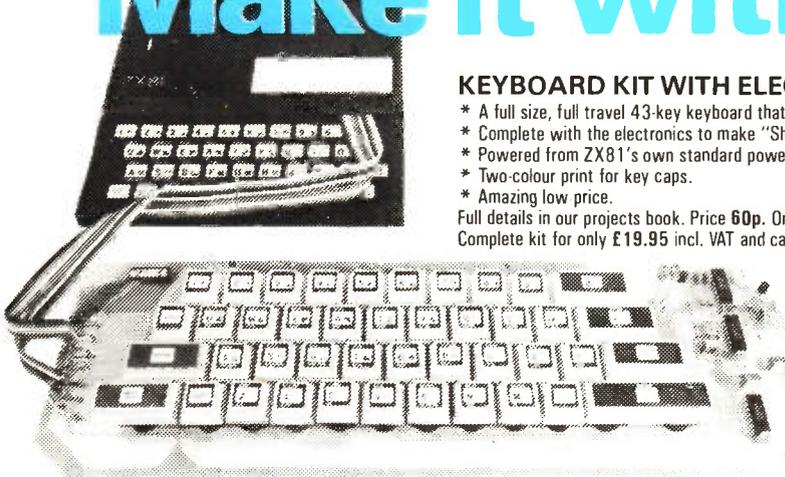
## KEYBOARD KIT WITH ELECTRONICS FOR ZX81

- \* A full size, full travel 43-key keyboard that's simple to add to your ZX81 (no soldering in ZX81).
  - \* Complete with the electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections making entry far easier.
  - \* Powered from ZX81's own standard power supply - with special adaptor supplied.
  - \* Two-colour print for key caps.
  - \* Amazing low price.
- Full details in our projects book. Price 60p. Order As XA03D.  
Complete kit for only £19.95 incl. VAT and carriage. Order As LW72P.



## 25W STEREO MOSFET AMPLIFIER

A superb new amplifier at a remarkably low price.



- \* Over 26W per channel into 8Ω at 1kHz both channels driven.
- \* Frequency response 20Hz to 40kHz ±1dB.
- \* Low distortion, low noise and high reliability power MOSFET output stage.
- \* Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
- \* Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in our projects book. Price 60p. Order As XA03D  
Complete kit for only £49.95 incl. VAT and carriage. Order As LW71N

## MATINÉE ORGAN

Easy-to-build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50. Order As XH55K.

Complete kits available:  
Electronics - £299.95,  
Cabinet - £99.50 (carriage extra).  
Demo cassette price £1.99. Order As XX43W.



## HOME SECURITY SYSTEM

Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability. Full details in our projects book. Price 60p. Order As XA02C.



## MAPLIN'S FANTASTIC PROJECTS

Full details in our project books only 60p each.

In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier · Universal Timer with 18 program times and 4 outputs · Temperature Gauge · Six Vero Projects

In Book 2 (XA02C) Home Security System · Train Controller for 14 trains on one circuit · Stopwatch with multiple modes · Miles-per-Gallon Meter

In Book 3 (XA03D) ZX81 Keyboard with electronics · Stereo 25W MOSFET Amplifier · Doppler Radar Intruder Detector · Remote Control for Train Controller

In Book 4 (XA04E)\* Telephone Exchange expandable up to 32 extensions · Ultrasonic Intruder Detector · Frequency Counter 100Hz to 500MHz Remote Control for 25W Stereo Amplifier

\*Projects for book 4 were in an advanced state at the time of writing, but contents may change prior to publication (due 14th Aug 1982).

## MORE GREAT KITS FROM MAPLIN

Matinée Organ (see box above)

Spectrum Synthesiser. Full details in book XH56L. Price £1.00

3800 Synthesiser } Full details in book XF11M. Price £2.00

5600S Synthesiser }

150W Power Amp Kit LW32K. Price £17.95\*

75W MOSFET Power Amp Kit LW51F. Price £11.49\*

50W Power Amp Kit LW35Q. Price £14.95\*

15W Power Amp Kit YQ43W. Price £6.45\*

8W Power Amp Kit LW36P. Price £4.45\*

\*Construction details with kit. (Power supply not included - details with kit).

## Maplin launches MAPCARD

A new way of buying from Maplin!

Now Maplin have their own credit card. You could have one too!

**APPLY NOW!**

Write to our Rayleigh address for details or pick up a leaflet in our shops.



## NEW SHOP IN BIRMINGHAM

Visit our brand new shop in Birmingham for our complete range of electronic components and computers.


Come and see us at Lynton Square, Perry Barr, Birmingham (just off the junction of the Outer Ring Road A4040 and Birchfield Road A34). Tel: 021-356-7292. Excellent free parking.

Opening Tuesday 24th August, 1982

Don't miss out - get a copy of our catalogue now! Over 140,000 copies sold already!

On sale now in all branches of WHSMITH price £1

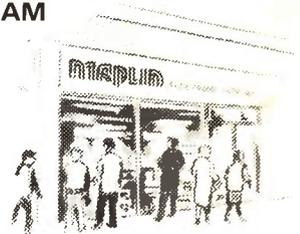320 big pages packed with data and pictures of over 5,500 items



## Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded.  
If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name \_\_\_\_\_

Address \_\_\_\_\_

Delivery within 14 days

EE/10/82

# MAPLIN

ELECTRONIC SUPPLIES LTD.

All mail to:

P.O. Box 3, Rayleigh, Essex SS6 8LR

Tel: Sales (0702) 552911 General (0702) 554155

Shops at:

159 King St., Hammersmith, London W6. Tel: 01-748 0926

284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000

Lynton Square, Perry Barr, Birmingham. Tel: (021) 356 7292

Note: Shops closed Mondays