

FLANK  
Easy to build projects for everyone


**Everyday**

MARCH 83  
80p

# ELECTRONICS

# FREE

## WIRE BENDING GAUGE

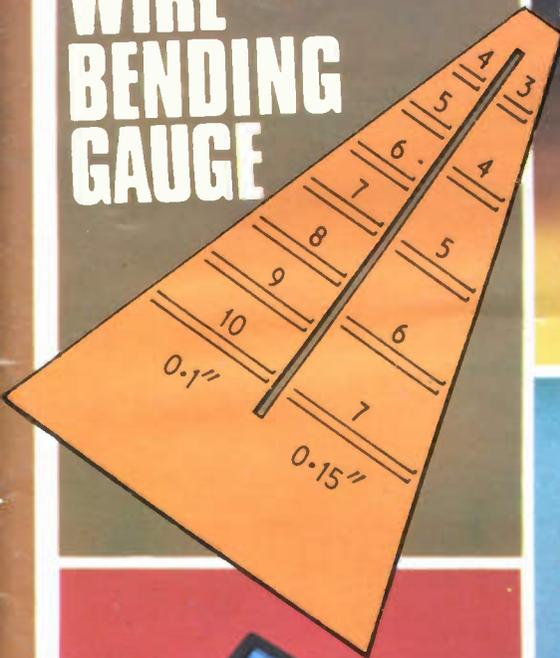

### TEST GEAR 83

### DUAL POWER SUPPLY



**FIRST of NEW SERIES**


### EXPANDED KEYBOARD for the ZX81



### MULTI-STATION INTERCOM



## Car Thermometer

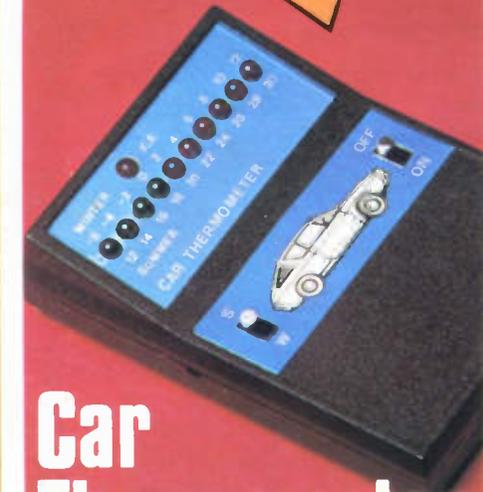

electronize

# AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

## ELECTRONIC IGNITION



### IS YOUR CAR AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines max. (even with 8 cylinders).
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best. Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.

★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the 'near misfires' whilst an electronic filter smooths out the effects of contact bounce etc.

Most **NEW CARS** already have **ELECTRONIC IGNITION**. Update **YOUR CAR** with the most powerful system on the market - 3½ times more spark power than inductive systems - 3½ times the spark energy of ordinary capacitive systems, 3 times the spark duration.

Total Energy Discharge also features: **EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, LED STATIC TIMING LIGHT, LOW RADIO INTERFERENCE, CORRECT SPARK POLARITY** and **DESIGNED IN RELIABILITY**.

★ **IN KIT FORM** it provides a top performance system at less than half the price of competing ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

**FITS ALL NEGATIVE EARTH VEHICLES**

6 or 12 volt, with or without ballast.

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS:** (Older current impulse types need an adaptor).


**STANDARD CAR KIT £15.90**  
**Assembled and Tested £26.70**

PLUS  
P. & P.  
£1 (U.K.)

**TWIN OUTPUT KIT £24.55**  
For Motor Cycles and Cars with twin ignition systems  
**Assembled and Tested £36.45**

Prices  
include  
VAT
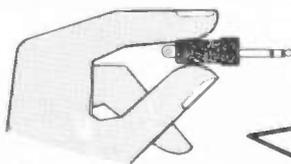
## PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



- ★ **2000 COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
- ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
- ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
- ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
- ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.



Don't Wait Until  
Its too Late ~  
Fit one **NOW!**

★ **DISABLES IGNITION SYSTEM** when alarm is armed.

★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.

**FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES.**  
**SUPPLIED COMPLETE WITH ALL NECESSARY LEADS AND CONNECTORS PLUS TWO KEY PLUGS**

**CAR ALARM KIT £24.95**

PLUS  
P. & P.  
£1 (U.K.)

**ASSEMBLED AND TESTED £ 37.95**

Prices  
include  
VAT



Access and Visa  
Welcome. Write or  
Phone Quoting Number



## ELECTRONIZE DESIGN

Dept. C · Magnus Rd · Wilnecote  
Tamworth · B77 5BY  
tel: 0827 281000
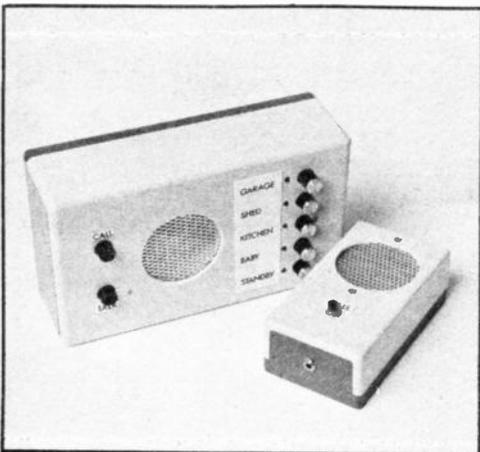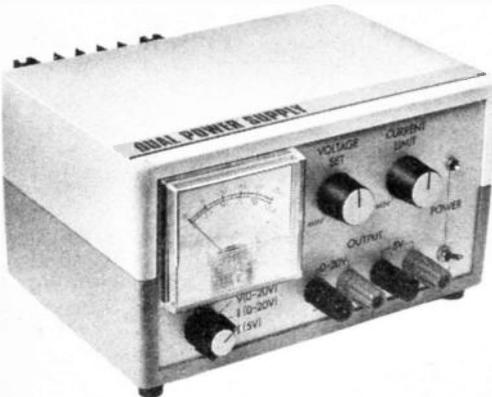
# Everyday ELECTRONICS

VOL. 12 NO. 3 MARCH 1983

PROJECTS... THEORY... NEWS...  
COMMENT... POPULAR FEATURES...



© IPC Magazines Limited 1983. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

## PROJECTS

- MULTI-STATION INTERCOM** by T. Rule 138  
Keep in touch around the home
- CAR THERMOMETER** by M. Plant 150  
Monitor the outside air temperature
- BUZZ OFF!** by T. R. de Vaux-Balbirnie 154  
A game for a steady hand
- TEST GEAR 83—DUAL POWER SUPPLY** by J. R. W. Barnes 159  
Variable output: 0 to 20V. Fixed output: 5V 1A for powering TTL
- EXPANDED ADD-ON KEYBOARD FOR THE ZX81** by J. M. Stejskal 170  
For speedier program entry
- EPROM PROGRAMMER FOR THE ACORN ATOM** by D. C. Grindrod 178  
Part 2: Construction and software

## SERIES

- INTRODUCING ELECTRONICS** by George Hylton 146  
Part 6: Digital Electronics
- THE ELECTRONICS OF INFORMATION TECHNOLOGY** by T. Ivall 166  
Part 5: Information Units

## FEATURES

- EDITORIAL** 137  
Test Gear 83; A Gift For Constructors
- SHOPTALK** by Dave Barrington 145  
Product news and component buying
- WIRE BENDING GAUGE** 156  
How to use your free gift
- FOR YOUR ENTERTAINMENT** by Barry Fox 158  
Why Markets Are Lost; Buying a Home Computer
- COUNTER INTELLIGENCE** by Paul Young 165  
A retailer comments
- CIRCUIT EXCHANGE** 173  
A forum for readers' ideas
- ACORN ATOM USER'S REPORT** by T. J. Johnson 174  
Putting a home computer through its paces
- EVERYDAY NEWS** 176  
What's happening in the world of electronics
- RADIO WORLD** by Pat Hawker G3VA 182  
The Electronics Epoch; Crystal-Ball Gazing

## FREE WITH THIS ISSUE

EE WIRE BENDING GAUGE (cover mounted)

Our April 1983 issue will be published on Friday, March 18. See page 157 for details.

Readers Services • Editorial and Advertisement Departments

137



ONLY  
**£4.95**

### "BIG TRAK" MOTORIZED GEARBOX

These units are as used in the "Big Trak" computerized vehicle, and offer the experimenter in robotics the opportunity to purchase the electro-mechanical parts required in building remote controlled vehicles. The unit comprises:

- (a) 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle;
- (b) A gearbox contained within the black ABS housing reducing the final drive speed to approx. 50rpm.

Data is supplied with the unit showing various options on driving the motors, as well as a direction controller circuit, enabling the unit to turn right, left or go straight ahead.

### SIMON GAME

... is back again. Another supply of ready built PCB's for this flashing light/pulsating tone computerised game is now with us. Supplied tested and working with speaker & instructions. **£4.95.**

### REED RELAYS


Manufacturers rejects - DIL and other PCB mounting types. SP, DP and 4P - make, break & c/o contacts. Not tested, may be only partially working or o/c etc, so very low price - pack of 10 assorted **£1;** 25 **£2.00;** 100 **£7.00**

### IN4148 - BEST PRICE EVER

Supplied in packs of 100, by Toshiba **£2** per pack; 3 packs **£5.50;** 10 packs **£15;** 25 packs **£32;** 100 packs **£115.**
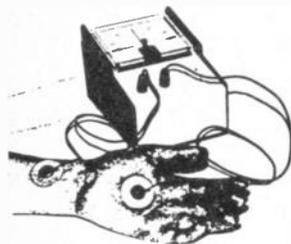
### FERRIC CHLORIDE

New supplies just arrived - 250mg bags of granules, easily dissolved in 500ml of water. Only **£1.15.** Also abrasive polishing block **95p.**



### LIE DETECTOR

Not a toy, this precision instrument was originally part of an "Open University" course, used to measure a change in emotional balance, or as a lie detector. Full details of how to use it are given, and a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 4V batts. Overall size 155x100x100mm. Only **£9.95** - worth that for the case and meter alone!!

### AA NI-CADS - 10 for £9.95

Brand new nickel cadmium batteries by GE, standard 1.2V @ 450mA/H. Professional quality with solder tabs both ends. Special price, **£1.40 ea;** 10 for **£9.95;** Box of 80 **£65.** Ni-cad Charger: Charges up to 4 AA, C or D cells + PP3. Only **£7.95.**



NOW  
REDUCED  
TO **£3.95**

### ELECTRO-DIAL

Electrical combination lock - for maximum security - pick proof. 1 million combinations!! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid. Overall dia. 65mm x 60mm deep. Only **£3.95.**

### STABILIZED PSU PANEL

A199 A versatile stabilized power supply with both voltage (0-30V) and current (20mA-2A) fully variable. Many uses inc. bench PSU, Ni-cad charger, gen. purpose testing. Panel ready built, tested and calibrated. **£7.75.** Suitable transformer and pots. **£6.00.** Full data supplied.

### BRAND NEW VEROBLOC KIT!!!

Just published by Babani, Mr. R. A. Penfold's new book, "30 SOLDERLESS BREADBOARD PROJECTS" - this book features 30 different projects for assembly on a Verobloc, and the kit contains all parts necessary to make:

- Audio Amplifiers
- Light & Dark Activated Switches & Alarms
- Timers
- Metronome
- Oscillators & Tone Generators
- Warbling Door Buzzer
- Two-tone Train Horn
- Touch Switch
- Reaction Game
- Sound Activated Switch
- Radio Receivers
- Fuzz Unit ... + lots more!!

The introduction shows all the different components and explains how to use the breadboard. The Verobloc layout is shown for every project together with the circuit diagram and an explanation of how it works. Ideal for beginners in electronics, but also suitable for more advanced students.

The complete kit is contained in an attractive plastic case, which can be divided up into 15 compartments in which your components may be stored.

Complete Kit, including book, Verobloc & all parts **£24.95;** Book only **£2.25;** Kit without Verobloc **£20.45.**

TWO FABULOUS OFFERS FROM

# ALCON

**SUPER 20**  
20k $\Omega$ /V a.c. & d.c.

**A SUPER  
PROTECTED  
UNIVERSAL  
MULTIMETER**

Undestructible, with automatic protection on all ranges but 10A.

**ONLY £33.50**

inc. VAT, P&P, complete with carrying case, leads and instructions.



This special offers is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £20.00.

**Accuracy:** d.c. ranges and  $\Omega$  2% a.c. 3% (of f.s.d.)  
**39 ranges:** d.c. V 100mV, 1-0V, 3-0V, 10V, 30V, 100V, 300V, 1000V.  
d.c. I 50 $\mu$ A, 100 $\mu$ A, 300 $\mu$ A, 1.0 $\mu$ A, 3mA, 10mA, 30mA, 100mA, 1A, 10A  
a.c. V 10V, 30V, 100V, 300V, 1000V.  
a.c. I 3mA, 10mA, 30mA, 100mA, 1.0A, 10A.  
 $\Omega$  0-5.0k $\Omega$ , 0-50k $\Omega$ , 0-500k $\Omega$ , 5M $\Omega$ , 50M $\Omega$ .  
dB from -10 to +61 in 5 ranges.

**Dimensions:** 105 x 130 x 40mm.


### TESTER 50 39 ranges

50k $\Omega$  V a.c. and d.c.  
With protective diodes and quick-acting 1-25A fuse.

**THE  
PROFESSIONAL  
SOLUTION  
TO GENERAL  
MEASUREMENT  
PROBLEMS**

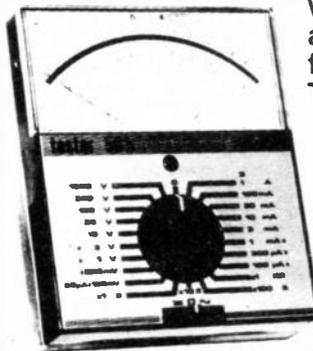**ONLY £36.30**

incl. VAT, P&P, complete with carrying case, leads and instructions. Goods normally by return of post.



The best instrument for the workshop, school, toolbox, TV shop and anywhere accurate measurement is needed quickly and simply.

**Accuracy:** d.c. ranges and  $\Omega$  2% a.c. 3% (off.s.d.)  
**39 ranges:** d.c. V 150mV, 1V, 3V, 10V, 30V, 100V, 300V, 1000V;  
d.c. I 20 $\mu$ A, 100 $\mu$ A, 300 $\mu$ A, 1-0mA, 3mA, 10mA, 30mA, 100mA, 1A, 3A.  
a.c. V 10V, 30V, 100V, 300V, 1000V;  
a.c. I 3mA, 10mA, 30mA, 100mA, 1A, 3A.  
Ohms 5k $\Omega$ , 50k $\Omega$ , 500k $\Omega$ , 5M $\Omega$ , 50M $\Omega$ .  
dB from -10 to +61 in 5 ranges.

**Dimensions:** 105 x 130 x 40mm.

For details of these and the many other instruments in the Alcon range, including multimeters, components measuring, automotive and electronic instruments, please write or telephone:

## ALCON Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

# GREENWELD

443D MILLBROOK ROAD, SOUTHAMPTON SO1 0HX  
All prices include VAT - just add 50p post. Tel. (0703) 772501



**MINI-MULTI TESTER** Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC volts 10, 50, 250, 1000, AC volts 10, 50, 250, 1000, DC amps 0 - 100 mA.




Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

FREE Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

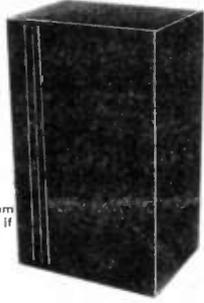**SUPER HI-FI SPEAKER CABINETS**

Made from an expensive Hi-Fi outfit - will suit any decor. Resonance free. Cut-outs for 6 1/2" woofer and 2 1/2" tweeter. The front material is Mason. The completed unit is most pleasing. Supplied in pairs, price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.00 the pair.



**GOODMANS SPEAKERS** 6 1/2" 8 ohm 25 watt £4.50. 2 1/2" 8 ohm tweeter. £2.50. No extra for postage if ordered with cabinets. Kover £1.50. **OTTO** but for 8" speaker and 4" tweeter. £7.50 + £3.50.



**VENNER TIME SWITCH**

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic base £1.75 or metal case £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

**THERMOSTAT ASSORTMENT**

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses, appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 - 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 - however, you can have the parcel for £2.50.

**50 THINGS YOU CAN MAKE**

Things you can make include Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will still have hundreds of parts for future projects. Our 10Kg parcel contains not less than 1,000 items - panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and data on the 50 projects.

**YOURS FOR ONLY £11.50 plus £3.00 post.**

**EXTRACTOR FANS**

Mains operated - ex-computer. Woods extractor 4" x 4" Muffin 115v. 5" - £5.75, Post £1.25. £4.50. Post 75p. 6" - £6.95, Post £1.25. 4" x 4" Muffin 230v. 5" Plannair extractor £5.75. Post 75p. £6.50. Post £1.25.



**ROTARY WAFER SWITCHES**

5 amp silver plated contacts. 3/8" shaft, 1" dia. wafer. Single wafer types, 29p each, as follows: 1 pole 12 way, 2 pole 6 way, 3 pole 4 way, 4 pole 3 way, 6 pole 2 way, 4 pole 4 way. Two wafer type, 59p each, as follows: 2 pole 12 way, 4 pole 5 way, 4 pole 6 way, 6 pole 2 way, 8 pole 3 way, 12 pole 2 way. 3 wafer types 99p each, 9 pole 4 way, 6 pole 5 way, 6 pole 6 way, 12p 3 way, 18p 2 way.

**EXTRA POWERFUL 12v MOTOR**

Made to work battery lawnmower, this probably develops up to 1/2 h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. £6.90 + £1.50 post. (This is easily reversible with our reversing switch - Price £1.15).

**MINI MONO AMP**

on p.c.b., size 4" x 2" approx. Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amplifier. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.




**POPULAR PROVEN PROJECTS**

**MULTI-CHANNEL or ROBOT CONTROLLER**

This is two kits. The 8 channel transmitter kit and the 8 channel receiver kit. Each kit comes with diagrams and notes, but no circuit boards, the component layout being left to you. The data shows how to drive, reverse and steer two or more motors. With spare channels to perform other functions. Price £9.50 for both kits.

**3 CHANNEL SOUND TO LIGHT KIT**

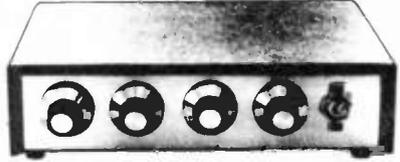

Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting leads. Special price is £14.95 in kit form or £25.00 assembled and tested. Case & metal Chassis No. Fully punched and prepared.

**WHY BE COLD - Build a tangential blower heater.**

**TANGENTIAL BLOW HEATER**

2.5 Kw quiet, efficient instant heating from 230/240 volt mains. Kit consists of blower as illustrated, 2.5 Kw element, control switch and data all for £4.95, post £1.50.



**CAR STARTER AND CHARGER KIT**

In an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250 watt mains transformer, 40 amp bridge rectifier, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £12.50 + £3.00 post.

**TRANSMITTER SURVEILLANCE**

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox - all electronic parts and circuit. £2.30 (not licencable in the U.K.).

**RADIO MIKE**

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 complete kit. (not licencable in the U.K.).

**FM RECEIVER**

Made up and working, complete with scale and pointer needs only headphones, ideal for use with our surveillance transmitter or radio mike. £5.85, or kit of parts £3.95.

**3 - 30v VARIABLE VOLTAGE POWER UNIT**

With 1 amp DC output, for use on the bench, students, inventors, service engineers, etc. Automatic short circuit and overload protection. In case with a volt meter on the front panel. Complete kit £13.80.

**INTERRUPTED BEAM**

This kit enables you to make a switch that will trigger when a steady beam of infra red or ordinary light is broken. Main components - relay, photo transistor, resistors and capacitors, etc. Circuit diagram but no case. Price £2.30.

**IONISER KIT**

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - complete mains operated kit, case included. £11.95 plus £2.00 post.

**RADIO STETHOSCOPE**

Easy to fault find - start at the aerial and work towards the speaker - when signal stops you have found the fault. Complete kit £4.95.

**INVISIBLE AND SILENT SENTINEL**

Ultra-sonic beam when broken could warn you of visitor - two kits - transmitter & receiver. To operate light or bell. £9.50.

**BURGLAR ALARM**

Complete kit includes 6" extrenal alarm bell, mains power unit, control box with keyswitch, 10 window/door switches, 100 yards of wire. With instructions. £29.50.

**12v MOTOR BY SMITHS**

Made for use in cars, these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3 1/2" dia. These have a good length of 1/2" spindle - price £3.45. Ditto, but double ended £4.25. Ditto, but permanent magnet. £3.75.



**WATERPROOF HEATING WIRE**

60 ohms per yard, this is a heating element wound on a fibre glass cord and then covered with p.v.c. Dozens of uses - around water pipes, under grow boxes in gloves and socks. 23p a metre.

**J. BULL (Electrical) Ltd.**

(Dept. EE) 34 36 AMERICA LANE, HAYWARDS Heath, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £10 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclay orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: write for quote. Delivery by return. Shop open 9.00 - 5.30, mon to Fri, not Saturday.

**SCHOOLS-LABS-STORES-WORKSHOPS-FACTORIES-**

Your chance to re-stock at less than cost prices!!!

**LIGHTING & POWER CABLES**

Copper clad. PVC sheathed. Made by Volex to BSS	
1.5mm single	per 100 metres £2.00
1.5mm flat twin	per 100 metres £3.50
1.5mm flat 3 core & E	per 100 metres £5.50
4mm single	per 100 metres £3.00
6mm flat 3 core	per 100 metres £27.50
16mm flat twin & E	per 100 metres £47.50
Telephone and multiway cables. Reliance as used by GPO.	
15 core	per 200 metres £60.00
10 core	per 200 metres £40.00

**THERMOSTATS & HEAT SWITCHES**

Thermostat: 3 level contact type	.30
10 amp appliance type thermostat. Spindle adjust	.40
Contact type with changeover, 10 amp switches, 0 - 100°C	.56
Wall mounting, metal case, c/o contacts low voltage	£2.30

**TIMERS & CLOCKS WITCHES**

Time and Set Switches. Smiths. Glass fronted 25 amp, 230v	£2.30
24 Hour time switch. 100 amp Smiths and clockwork reserve. Ex-Electricity Company	£5.50
Cooker clock switch. Smiths 12 hour	£1.00
Clockwork operated switches:	
15 amp, 230v. On time up to 10 minutes	£1.37
120 minutes	£1.37
30 minutes	£1.37
360 minutes	£1.37
OMRON mini-timer, ref. STP NH	£3.50

**BEEPERS - SIRENS - BELLS - BUZZERS**

Siren/Hooter - Delta 6 or 12v DC or 24v AC	.37
Open type buzzer, ex GPO, 10 - 20V	.30
Undermode bell, 4v - 9v	.85
Fire alarm bell, 12" gong, heavy cast iron construction	£12.00

**COUNTERS**

6 digit counter. Mains operated. Not resettable	.60
Ditto, but even numbers only	.50
6 digit counter. 48v DC, 115v AC. Resettable	£1.00

**SWITCHES - ROCKER, TOGGLE, ETC.**

Rocker switches: white push into hole 1" x 7/16". All rated 10 amp, AC 250 volt. on/off	.12
changeover centre off	.15
on/off with neon	.20
push to make spring return	.20
push to break spring return	.20
Larger two circuit one on one with mounting plate	.20
13 amp rocker switch. Car Fastener (DoT)	.15
Pistol Grip Switch: with lock-on as in electric drills	.30
Interlocking switch: blow heater, 3 rockers, 10 amp	.20
Micro switches: V3 types, 10 amp c/o contacts	.20
mains button operated: 15 amp c/o contacts	.25
10 amp on/off	.15
15 amp on/off	.20
Lever operated add	.10
Lever with roller operation add	.15
Miniature types: Burgess V4TG c/o	.58
Two mounted with roller operator	.65
Glass reed switches: 60 watt 10p. 40 watt 5p.	
flat multi stackable 60 watt	.50
Operating coils for reed switch multi voltage 3, 6, 9, or 12	.50
Ceramic magnets Mullard	.10
Mini Magnet	.15

**MISCELLANEOUS ITEMS**

Neon Mains indicators. Standard	.15
Extra small	.25
Bench isolation mains in 230/240v output. 250 Watts	£4.50
Mains input. Porcelain removable fuse	.20
Light operated switch 12 volt. Encapsulated	£1.25
Insulating board, srpb etc. Approx 10 tons. Sheet size 4' x 4' or larger. Various thicknesses, price per lb.	.50
Ditto, Tufnol, price per lb.	£2.00
Aerosol can ICI Fluon lubricant	.35
Varicap P.B. TV tuner	.50
Battery holder takes 6 U2 batteries, snap connector	.25
Car Battery clips, as for charger, + and - . per pair	.10

**MAINS TRANSFORMERS**

6 volt 1 amp	.50	35 volt 2 amp	£2.00
6.3 volt 2 amp	£1.00	38 volt 2 1/2 amp	£2.50
12 volt 1/2 amp	.75	26 volt 10 amp	£4.00
12 volt 4 amp	£2.00	50 volt 2 amp	£2.00
12 volt 1 amp	£1.00	12 - 0 - 12, 2 amp	£2.50
8.5 - 0 - 8.5 1 amp	£1.00	12 - 0 - 12, 1 amp	£2.00
18 volt 1 amp	£1.50	100W auto 115v c/p	£2.00
25 volt 1 1/2 amp	£1.50		

**MOTORS - MAINS & BATTERY**

3 - 6 volt battery motor, very small	.15
3 - 12 volt battery motor, very low current	.20
Mains motor with gear box	5 rev minute £2.25
	80 rev per minute £3.00
	110 rev minute £2.00
	200 rev minute £1.50
Mains motor, double ended fan motor	£1.20
Ditto single ended fan motor	£1.00
Fan blade for above	.50
Mains motor, double ended, very powerful 1 1/2" stack	£1.50
Mains instrument motors	1 rev 24 hours £1.50
	1 rev 1 hour £1.50
with gear box:	
	4 rev minute £1.50
	2 rev minute £1.50
	1 rev minute £1.50
Motor clockwork, set up to 1 hour	.38
Motor, clockwork set up to 1 hour with ringer	.75
Mains motor 1/2 h.p. 1425 revs, ex-computer	£2.25
Vent opening motor with end stop switches	£12.50
12 volt motors, Smiths, single ended 1/2" spindle	£1.50
12 volt motors, Smiths, double ended 1/2" spindle	£2.00
12 volt motors, P magnet type, single ended	£1.75
1 1/2 h.p. motor 3450 rpm 100 volt. 50Hz. New	£5.00

**SPECIAL TERMS.** For items in this column. Offer no less than 10 of any item. Then add VAT at 15%, and 20% for carriage in the case of transformers and electric motors. All other items in this column are free post & packing.



# BI-PAK BARGAINS



**5T21 SCREWDRIVER SET**  
6 precision screwdrivers in hinged plastic case. Sizes — 0 8 1 4 2 2 4 2 9 and 3 8mm **£1.75**

**5T31 NUT DRIVER SET**  
5 precision nut drivers in hinged plastic case. With turning rod. Sizes — 3 3 5 4 4 5 and 5mm **£1.75**

**5T41 TOOL SET**  
5 precision instruments in hinged plastic case. Crosspoint (Philips) screwdrivers — M 0 and M 1 Hex key wrenches — 1 5 2 and 2 5mm **£1.75**

**5T51 WRENCH SET**  
5 precision wrenches in hinged plastic case. Sizes — 4 3 5 5 5 5 and 6mm **£1.75**

**BUY ALL FOUR SETS** 5T21 5T51 and get **HEX KEY SET FREE**  
HEX KEY SET ON RING  
Sizes 1 5 2 7 5 3 4 5 5 and 6mm  
Made of hardened steel  
HX 1 **£1.25**



## "IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed All Type Resistors	£1
SX11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm 2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.  
\*Quantities approximate, count by weight

## "GUARANTEED TO SAVE YOU MONEY"

SX27A	60 Assorted Polystyrene Bead Capacitors. Type 9500 Series PPD	£1.00
SX28A	50 Assorted Silver Mica Caps 56pF-150pF	£1.00
SX29A	50 Assorted Silver Mica Caps 180pF-4700pF	£1.00
SX30A	50 High Voltage Disc Ceramics 750V min up to 8KV. Assorted useful values	£1.00
SX31A	50 Wirewound 9 watt (arg) Resistors. Assorted values 1 ohm-12K	£1.00

**AUTO SCREWDRIVER/DRILL**  
Automatic spiral ratchet. Complete with 2 screwdriver blades, 5 & 65mm, 1 screwdriver cross point No. 1 & three drills — 2, 2.8 and 3.65mm — A MUST FOR ALL HOBBY-BUILDERS & CONSTRUCTORS. Order No. ASD/1 **£3.50** each

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 10pF 56pF	£1
SX19	100	Mixed Ceramics 68pF 0.5mF	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics all sorts	£1
SX23	50	Quality Electrolytics	£1

\*Quantities approximate, count by weight

## BARGAINS

SX91	20 x Large 2" RED LED	£1
SX42	20 small 125 Red LEDs	£1
SX43	10 Rectangular Green LEDs 2	£1
SX46	30 Assorted Zener Diodes 250mV-2 watt mixed voltages. all coded New	£1
SX47	4 Black Instrument Knobs—angled with pointer 1/4" Standard screw. Fit size 29 x 20mm	50p
SX49	20 Assorted Slider Knobs Black/Chrome etc	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

## BRAND NEW LCD DISPLAY MULTIMETER.

RE 188m  
LCD 10 MEGOHM INPUT IMPEDANCE  
3 1/2 digit \* 16 ranges plus hFE test facility for PNP and NPN transistors \* Auto zero auto polarity \* Single handed pushbutton operation \* Over range indication \* 12 5mm (1/2 inch) large LCD readout \* Diode check \* Fast circuit protection \* Test leads battery and instructions included

Max indication 1999 or — 1999  
Polarity indication Negative only  
Positive readings appear without + sign


input impedance 10 Megohms  
Zero adjust Automatic  
Sampling time 250 microseconds  
Temperature range — 5°C to 50°C  
Power Supply 1 x PP3 or equivalent 9V battery

Consumption 20mW  
Size 155 x 88 x 31mm

RANGES  
DC Voltage 0 200mV  
0 2 20 200 1000V Acc. 0 8%

AC Voltage 0 200 1000V  
Acc. 1 2% DC Current 0 200uA  
0 2 20 200mA 0 10 A Acc. 1 2%

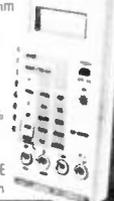Resistance 0 2 20 200K ohms  
0 2 Megohms Acc. 1%  
BI PAK VERY LOWEST POSSIBLE PRICE  
**£35.00** each



## SIREN ALARM MODULE

American Police type screamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. 5 watt, 12v max.

**£3.85**  
Order No. BP124.




## The Third and Fourth Hand...



... you always need but have never got until now  
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**  
Without magnifier ORDER NO. T400 **£4.75**
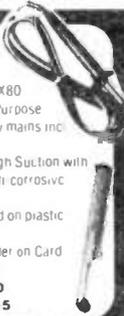
## BI-PAK SOLDER-DESOLDER KIT

Kit comprises ORDER NO. SX80  
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16 (4.7mm) bit  
1 Quality Desoldering pump. High Suction with automatic ejection. knurled anti corrosive casing and teflon nozzle  
1 5 metres of the soldering braid on plastic dispenser  
2 vds (1 83mm) Resin Cored Solder on Card  
1 Heat Shunt tool tweezers Type  
Total Retail Value over **£12.00**  
OUR SPECIAL KIT PRICE **£8.95**



## BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises  
1 Expo Mini Drill 10 000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit  
1 Sheet PCB Transfers 210mm x 150mm  
1 Etch Resist Pen  
1 1/2 lb pack FERRIC CHLORIDE crystals  
3 sheets copper clad board  
2 sheets Fibreglass copper clad board  
Full instructions for making your own PCB boards  
Retail Value over **£15.00**  
OUR BI PAK SPECIAL KIT PRICE **£9.75**  
ORDER NO. SX81



**PROGRAMMABLE UNIJUNCTION TRANSISTOR**  
PUT case 10106 plastic MEU22 Similar to 2N6027/6028 PNP Silicon  
Price 1-9 10-49 50-99 100+ Normal Retail  
Each 20p 18p 15p 13p Price £0.35 each

SX33A	6 small (min) (SDST/SPDT Toggle Switches 240v 5amp	£1.00
SX35A	6 small (min) Rocker Switches 240v 5amp	£1.00
SX32A	* 2 Assorted Jack & Phono plugs, sockets and adaptors, 2.5m, 3 1/2mm and standard sizes	£1.00
SX71	50 "C108" Fallouts' Manufacture, 5 out of spec on volts or gain You test!	£1.00
SX72	A mixed bundle of Copper clad Board Fibreglass and paper Single and double sided. A fantastic bargain	£1.00

## REGULATED VARIABLE Stabilised POWER SUPPLY

Variable from 2.30 volts and 0.2 Amps. Kit includes —  
1 VPS30 Module, 1 — 25 volt 2 amp transformer, 1 — 0 50v 2" Panel Meter, 1 — 0 2 amp 2" Panel Meter, 1 — 470 ohm wirewound potentiometer, 1 — 4K7 ohm wirewound potentiometer, Wiring Diagram included. Order No. VPS30 KIT **£7.00**

## MINIATURE FM TRANSMITTER


Freq: 95-106MHz. Range: 1/2 mile  
Size: 45 x 20mm. Add: 9v batt. **ONLY £5.50**  
Not licenced in U.K.  
Ideal for: 007-MIS-FBI-CIA-KGB etc.



## TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year! A host of Electronic components including potentiometers — rotary and slider presets — horizontal and vertical Resistors of mixed values 22ohms to 2M2 — 1 8 to 2 Watt! A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire nuts, bolts, grommets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's oplo's, all of which are current everyday usable devices in a fantastic Parcel. No rubbish! all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation — Beat the Budget — Down with Depression

**JUST £6.50.**

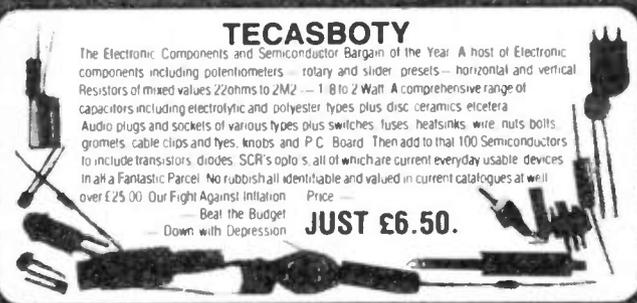

SX38 100 Silicon NPN Transistors — all perfect Coded mixed types with data and eqvt sheet. No rejects Real value **£3.00**

SX39 100 Silicon PNP Transistors — all perfect Coded mixed types with data and eqvt sheet. No rejects. Fantastic value **£3.00**

**2N3055** The best known Power Transistors in the World — 2N3055 NPN 115W  
Our BI-PAK Special Offer Price:  
10 off **50 off 100 off**  
£3.50 **£16.00 £30.00**

**BD312** COMPLIMENTARY PNP POWER TRANSISTORS TO 2N3055  
Equivalent M12955 — BD312 — 103  
SPECIAL PRICE £0.70 each  
10 off **£6.50**



## MORE BARGAINS!

SX51	60 metres PVC covered Hook-up wire single and stranded. Mixed colours	£1
SX58	25 Assorted TTL Gates 7400 Series 7401-7460	£1
SX59	10 Assorted Flip Flops and MSI TTL	£1
SX60	20 Assorted Slider Potentiometers	£1
SX62	40 Assorted Pre-Sets Hor/Vert etc	£1
SX79	10 Reed Switches — glass type 3 Micro Switched — with lever	£1

# BI-PAK

Send your orders to Dept. EEB BI-PAK P.O. BOX 6 WARE WERTS, SHOP AT 3 BALDOCK ST. WARE WERTS.  
TERMS: CASH WITH ORDER SAME DAY DESPATCH. ACCESS BARCLAYCARD ALSO ACCEPTED. TEL (0520) 3182 GYRO 388 7006  
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.

Remember you must add VAT at 15% to your order. Total Postage add 75p per total order.

# BI-PAK BARGAINS

## TRIACS — PLASTIC

4 AMP — 400v — TO202 — TAG 136G	100 OFF	50 OFF
1 OFF	£3.75	£30.00
40p	£3.75	£17.50
3 AMP 400v — TO220 — TAG 425		
60p	£5.75	£27.50
		£50.00

## SLIDER POTENTIOMETERS

ALL AT 50p PER PAK

SX63 5 x 470 ohms Lin	SX67 5 x 47k Lin
SX64 5 x 1k Lin	SX68 5 x 47k Log
SX65 5 x 22k Lin	SX69 5 x 100 Lin
SX66 5 x 22k Log	SX70 5 x 1 meg Lin

SX40 250 Silicon Diodes—Switching like IN4148 DO-35 All good—uncoated Worth double our price 45v 75mA	£1.25
SX41 250 Silicon Diodes—General Purpose like OA200/202 BAX13-16 Uncoated 30-100v 200mA DO-7	£1.25

SX44 10 5A SCR's TO64 3 x 50v 3 x 100v 2 x 200v 2 x 400v Super value less than 1/2 price	£1
SX45 10 5A SCR's TO66 2 x 50v 2 x 100v 4 x 200v 2 x 400v All coded Brand new a giveaway!	£1

## MINIATURE TOOLS FOR HOBBYISTS

**Miniature round nose side cutters** — insulated handles 4 1/2 inch length. Order No Y043.

**Miniature long nose pliers** — insulated handles 5 1/2 inch length. Order No Y044.

**Miniature bend nose pliers** — insulated handles 5 1/2 inch length. Order No Y045.

**Miniature end nippers** — insulated handles 4 1/2 inch length. Order No Y046.

**Miniature snipe nose pliers** with side cutter and serrated jaws — insulated handles 5 inch length. Order No Y042.

**All with insulated handles**

**FLEXEY DRIVER**

A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch. Order No FS-1 Flat blade 4mm FS-2 Cross point no 1 **£1.75 each.**

**GRIP DRIVER**

Binch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No SD-1 Flat blade 4mm SD-2 Cross point no 0 **85p each.**

**INEXPENSIVE TOOLS OF IMMENSE VALUE**

Combined with stripper, cutter, crimper incl 25 asset terminals for crimping. Order No WS2. Our low price **£1.20 each.**

ALL AT **1.25** each

## BA, NUT DRIVER SET

Set of 5 BA spanner shafts plus universal handle in roll-up wallet. Sizes OBA 2-4-6-8BA. Order no: T192 **£2.75 set**

## NEON SCREWDRIVER

7 1/2 inch blade order no NS1 **£0.85p each**  
5 1/2 inch blade order no NS2 **£0.50p each**

## Guarantee

Satisfaction or your money back has always been BI-PAK'S GUARANTEE and it still is. All these Sale items are in stock in quantity and we will despatch the same day as your order is received.

## EXPERIMENTOR BOXES — ALUMINIUM — PLASTIC ALUMINIUM BOXES

Made with Bright Aluminium folded construction with deep lid and screws

SIZE	L	W	H	Order No	Price
5 1/4	2 1/4	1 1/2	1 1/2	159	<b>83p</b>
4	2 1/4	1 1/2	1 1/2	161	<b>83p</b>
4	2 1/2	2	1 1/2	163	<b>83p</b>
3	2	1	1 1/2	164	<b>87p</b>
8	6	3	1 1/2	166	<b>£1.06</b>
6	4	2	1 1/2	167	<b>£1.12</b>

## Plastic Boxes

Coloured Black Close fitting Flanged Lid, fixing screws into brass bushes

SIZE	L	W	H	Order No	Price
4	2	1	1 1/2	141	<b>£1.00</b>
4 1/2	2 1/2	1 1/2	1 1/2	143	<b>£1.30</b>
6	3 1/2	2	1 1/2	144	<b>£1.60</b>

Plastic as above but with aluminium top panel **£1.40**

Plastic sloping front

SIZE	L	W	H	Order No	Price
5 1/4	4	2 1/4	1 1/2	146	<b>£1.40</b>
5 1/4	4	2 1/4	2	148	<b>£2.14</b>

All measurements for boxes are shown in inches. L = Length W = Width H = Height

## IC SOCKETS

The lowest price ever.

The more you buy the cheaper they come!

Pin	10 off	50 off	100 off
8 pin	85p	£3.50	£6.00
14 pin	90p	£3.75	£6.50
16 pin	95p	£4.00	£7.00

## VOLTAGE REGULATORS

### TO220

	Positive +	Negative -
7805	50p	7905 - 55p
7812	50p	7912 - 55p
7815	50p	7915 - 55p
7824	50p	7924 - 55p

## BI-PAK'S OPTO 83 SPECIAL

A selection of Large & Small size LED's in Red, Green, Yellow and Clear, plus shaped devices of different types. 7 Segment displays, photo transistors, emitters and detectors. Types like MEL11, FPT100 etc. Plus Cadmium Cell ORP71 and germ. photo transistor OCP71. TOTAL OF 25 pieces.

O/N/O SX574	Valued	Normal Retail	£12.00
		Our Price	<b>£5.00</b>

## SEMICONDUCTORS FROM AROUND THE WORLD

**100** A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices

Guaranteed Value over £10 at Normal Retail Price

£4.00

Data etc. in every pak Order No: SX56

## MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch LED indicators at each of the five charging points

Charges	Power
PP3 (9v)	220 240V AC
U12 (1.5V penlite)	Dim's -
U11 (1.5V C)	210 x 100 x 50mm
U2 (1.5V 0)	<b>£6.95</b>

## POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi-plug. Input - 240V AC 50Hz Output 3 4 5 6 7 5 9 & 12V DC Rating - 300ma MW8B

## 1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncod. J — you select for VLTS. ALL perfect devices — NO odds Min 50v 50 for £1.00 — worth double ORDER NO: SX76

Silicon General Purpose NPN Transistors TO-18 Case Lock In leads — coded CV7644 Similar to BC147 — BC107 — 789 ALL NEW! VCE 70v IC500mA Hfe 75-250 50 off 100 off 500 off 1000 off	Order as CV7644
PRICE	<b>£2.00 £3.80 £17.50 £30.00</b>

Silicon General Purpose PNP Transistors TO-5 Case Lock In leads coded CV9507 similar 2N2905A to BF130 VC 60 IC 600mA Min Hfe 50 ALL NEW! 50 off 100 off 500 off 1000 off	Order as CV9507
PRICE	<b>£2.50 £4.00 £19.00 £35.00</b>

## Silicon NPN'L' Type Transistors

TO-92 Plastic centre collector Like BC182L — 183L — 184L VCE0 45 VCE0 30 IC200mA Hfe 100-400

ALL perfect devices — uncod. ORDER AS SX183L

50 off	100 off	500 off	1000 off
<b>£1.50</b>	<b>£2.50</b>	<b>£10.00</b>	<b>£17.00</b>

## PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line VCE0 40 VCE0 35 IC 300mA Hfe 50-400

Brand New — Uncod. — Perfect Devices

50 off	100 off	500 off	1000 off
<b>£2.00</b>	<b>£3.50</b>	<b>£15.00</b>	<b>£25.00</b>

Order as ZTXPNP

## DIGITAL VOLT METER MODULE

3 x 7 segment displays Basic Circuit 0-2V± instructions provided to extend voltage & current ranges. Operating voltage 9/12v. Typ. Power Consumption 50mA O/N/O: SX99 Once only price **£9.95**

## ELECTRONIC SIREN 12v DC

Red plastic case with adjustable timing. Warning. Emission high pitched wailing note of varying pitch. 100 cycles per minute. (Dims. 90mm [ou] 50mm [dep]) Power: 17 v DC


Our Price: **£5.50**

## SILICON BRIDGE RECTIFIERS

Comprising 4 x 1 1/2 amp rectifiers mounted on PCB. VRM — 150 vits IFM — 1.5 Amps Size: 1 inch square

10 off	£1.00
50 off	£4.50
100 off	£7.50

Order No. As: 4RI BRect.

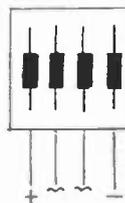

## MULTITESTERS

1,000 opv Including test leads & Battery AC volts - 0-15-150-500-1,000 DC volts - 0-15-150-500-1,000 DC currents - 0-1ma-150ma Resistance - 0-25 k ohms 100 K ohms Dims - 90 x 61 x 30mm

O/N/O: 1322. OUR PRICE **£6.50 ONLY**

## HOME TWEETER

Dome Tweeter for systems up to 50w. Impedance 8 ohms. Frequency Response 2000-20000Hz. Dims 98mm dia x 31mm deep.

OUR PRICE **£2.95**. O/N/O: DMT200

30,000 opv Including test leads and case AC volts - 0-25-10-25-100-250-500-1,000 DC volts - 0-0-25-1-2-5-10-25-100-250-1,000 DC current - 0-50ua 0-5ma-50ma 0-12amps Resistance - 0-6k ohms-70k ohms-6meg ohms-60meg ohms Decibels - 20db to plus 56db Short test - Internal buzzer Dims - 160 x 110 x 50mm

O/N/O: 1315. OUR PRICE **ONLY £24.75**

## SPECIAL OFFER OF STEREO AUDIO MODULES

Fully built and tested in our factory. A COMPLETE SET TO GIVE YOU 70 WATTS TOTAL 35 WATTS (rms) PER CHANNEL 55w POWER SUPPLY

Kit comprises:

- 2 x AL80 Power Amplifiers
- 1 x SPM120/55 Power Supply
- 1 x PA200 Stereo Pre-Amplifier
- 1 x Transformer 55w
- 1 x Front Panel - Black with White lettering
- 4 x Black Knobs with White Pointers
- 2 x Coupling Capacitors & 1 Reservoir Capacitor. Full hook-up chart

NORMAL RETAIL PRICE **£52**. COMPLETE **SAVING £14**

Our SPECIAL OFFER Price For 1 MONTH ONLY

Order by phone NOW with your Credit Card. Ring: Sue on 0920 3442/3182 for immediate despatch (Order as: SX70 watt AUDIO KIT)

**£38 COMPLETE**

# BI-PAK

Send your orders to Dept. EE3 BI-PAK PO BOX 6 WARE HERTS. SHOP AT 3 BALDLOCK ST. WARE HERTS. TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS. BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRD 388 7006. ADD 15% VAT and 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us in Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total: Postage add 50p per Total order.

# T.V. SOUND TUNER BUILT AND TESTED



**£22.95** + £2.00 p&p.

E.T.I. kit version of above without chassis, case and hardware. £12.95 plus £1.50 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 1/4" x 8 1/2" x 3 3/4".

## PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT




**£32.95** + £2.75 p&p.

• NOISE REDUCTION SYSTEM • AUTO STOP • TAPE COUNTER • SWITCHABLE E.O. • INDEPENDENT LEVEL CONTROLS • TWIN V.U. METER • WOW & FLUTTER 0.1% • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES. Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts. i.e. semiconductors, resistors capacitors, hardware top cover, printed scale and mains transformer. You only supply solder and hook-up wire. Featured in April issue P.E. Reprint 50p. Free with kit. **Self assembly simulated wood cabinet** - £4.50 + £1.50 p&p.

**SPECIAL OFFER!**  
£31.00 plus £2.75 p&p  
Complete with case.

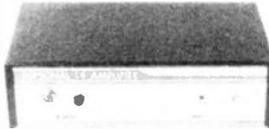
## PERSONAL LS AMP KIT

Amplifier for your personal stereo cassette player as featured in January issue of Everyday Electronics. Turn your personal stereo into a mains powered home unit.



Parts: Stereo power amp PCB with all components, £3.50 + 75p p&p. Power supply unit, £1.95 + £1.50 p&p. Pair of 4 1/2" elliptical speakers, £1.50 the pair, + £1.00 p&p. Input & output sockets & plugs, £1.50. Recommended case (for the power supply and amp only), £2.95 + 80p p&p. P&P inclusive price of £1.75 for two or more articles.

## P.E. STEREO TUNER KIT

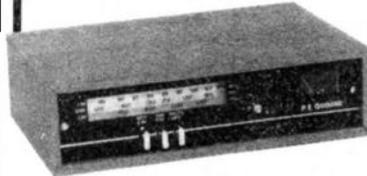

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July '81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System. **FEATURES:** VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

**£17.95**  
Plus £2.50 p&p.

Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 3/4". **£3.50** Plus £1.50 p&p.


## 125W HIGH POWER AMP MODULES

**KIT** £10.50 + £1.15 p&p  
**BUILT** £14.25 + £1.15 p&p

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is performed and ready to use.

Supplied with all parts, circuit diagrams and instructions.

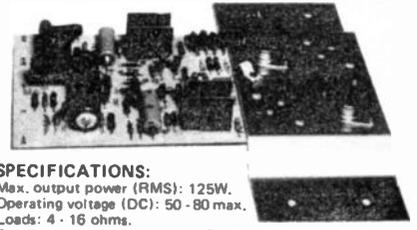**ACCESSORIES:** Suitable mains power supply kit with transformer: £8.50 plus £2.00 p&p. Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



### SPECIFICATIONS:

Max. output power (RMS): 125W.  
Operating voltage (DC): 50 - 80 max.  
Loads: 4 - 16 ohms.  
Frequency response measured @ 100 watts: 25Hz - 20KHz.  
Sensitivity for 100 watts: 400mV @ 47k.  
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.  
Dimensions: 205 x 90 and 190 x 36 mm.

## BSR RECORD DECK


Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx. **£12.95** + £1.75 p&p.



**SPECIAL OFFER!** Replacement stereo cassette tape heads - £1.80 ea. Mono £1.50 ea. Erase 70p ea. Add 50p p&p to order.

## Special Offer! AUDAX 45 WATT TWO WAY SPEAKERS

**£36.95** a pair  
Plus £7.00 p&p

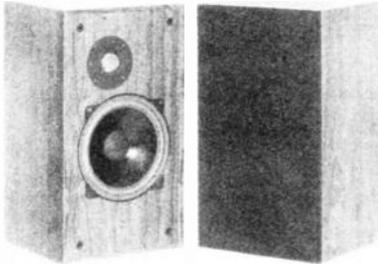

Originally made to sell for over £70. Unit comprises 8" bass/mid range and 4" soft dome tweeter and a 6 element crossover. Mirror image. Finished in rosewood. Size: 470mm high x 264mm wide x 225mm deep. Empty cabinets available separately if required. **£9.95** pair + £4.75 p&p.

## SPEAKER KIT


**2 WAY 10 WATT**  
8" bass/mid range and 3 1/2" tweeter. Complete with screws, wire, crossover components and cabinet. All wood pre-cut - no cutting required. Finish - chipboard covered wood simulate, size 14 1/2" x 8 1/2" x 4". **PAIR for ONLY**  
**£12.50** plus £1.75 p&p.


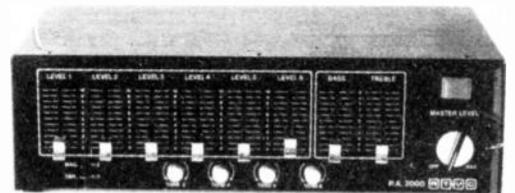
## MONO MIXER AMP

Ideal for Church halls & Club houses. **£45.00** + £2.00 p&p.

**50 WATT** Six individually mixed inputs for two pick ups (Car. or mag.), two moving coil microphones and two auxiliary for tape tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux. inputs. Size: 13 1/2" x 6 1/2" x 3 1/2" app. Power output 50 watts R.M.S. (cont.) in use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.



Matching AKG Microphone to suit (with speech and music filter). Complete with lead. **ONLY** £9.95 plus 75p p&p.

Telephone or mail orders by ACCESS welcome.

All mail to:  
**21A HIGH STREET, ACTON W3 6NG.**  
Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/10/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch. RTVC Limited reserve the right to up-

date their products without notice. All enquiries send S.A.E.

All callers to: **323 EDGWARE ROAD, LONDON W2.** Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 6. Prices include VAT.



# Everyday ELECTRONICS

VOL. 12 NO. 3 MARCH 1983

## Editor

F. E. BENNETT

## Assistant Editor

B. W. TERRELL B.Sc.

## Production and News Editor

D. G. BARRINGTON

## Projects Editor

G. P. HODGSON

## Art Editor

R. F. PALMER

## Assistant Art Editor

P. A. LOATES

## Technical Illustrator

D. J. GOODING Tech. (CEI)

## Secretary

JACQUELINE DOIDGE

## Editorial Offices

KING'S REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS  
Phone: 01-261 6873

## Advertisement Manager

R. SMITH  
Phone: 01-261 6671

## Representative

R. WILLET  
Phone: 01-261 6865

## Classified Supervisor

B. BLAKE  
Phone: 01-261 5897

## Make-Up and Copy Department

Phone: 01-261 6615

## Advertisement Offices

KING'S REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS

## TEST GEAR 83

It was as far back as 1974 that we published a comprehensive set of test instruments under the title *EE Test Gear Five*. This series proved to be very popular and instruments built to these designs will have been giving good service in workshops and dens up and down the country over the last nine years or so. Equipment of this kind generally has a long life. The devoted constructor or experimenter treats his equipment with respect and it is not likely to suffer misuse in the hands of others.

Electronic technology has of course been developing over these nine years and some different needs have arisen in regard to test equipment used in pursuance of our hobby. Such needs have been recognised and covered by individual items of equipment presented in our pages from time to time. Now the time seems right to present a new set of instruments. There is another reason also, that is to satisfy the needs of a new generation of readers. Over a period most hobbyists will acquire or build individual items of test gear, but acquisition on this casual basis is not the most ideal arrangement. Far better to have a set of co-ordinated units planned to give comprehensive facilities.

With the introduction of *Test Gear 83* constructors now have the opportunity to build a set of matching instruments designed to meet practically all requirements of the average hobbyist in the light of the present state of the art. The first instrument is covered in this issue and the remaining instruments will be published one per month in the following issues of *EE*.

The completed instruments will add distinction to the hobbyist's workshop and provide lasting evidence of their builder's skill. But far more important, this collection of test gear will be of incalculable value in the years ahead. *Test Gear 83* will prove a sound investment of time and money.

## A GIFT FOR CONSTRUCTORS

Despite its simple appearance, the tool attached to our front cover will be an important accessory for the constructor's work bench. Anyone who assembles circuits will quickly discover how useful this wire bending gauge is in forming resistor and capacitor leads to suit horizontal or vertical mounting of these components and with a spacing to suit a selected number of holes on an 0.1 inch matrix board.



## Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

## Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in *EVERYDAY ELECTRONICS*, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

## Back Issues


Certain back issues of *EVERYDAY ELECTRONICS* are available worldwide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

## Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.
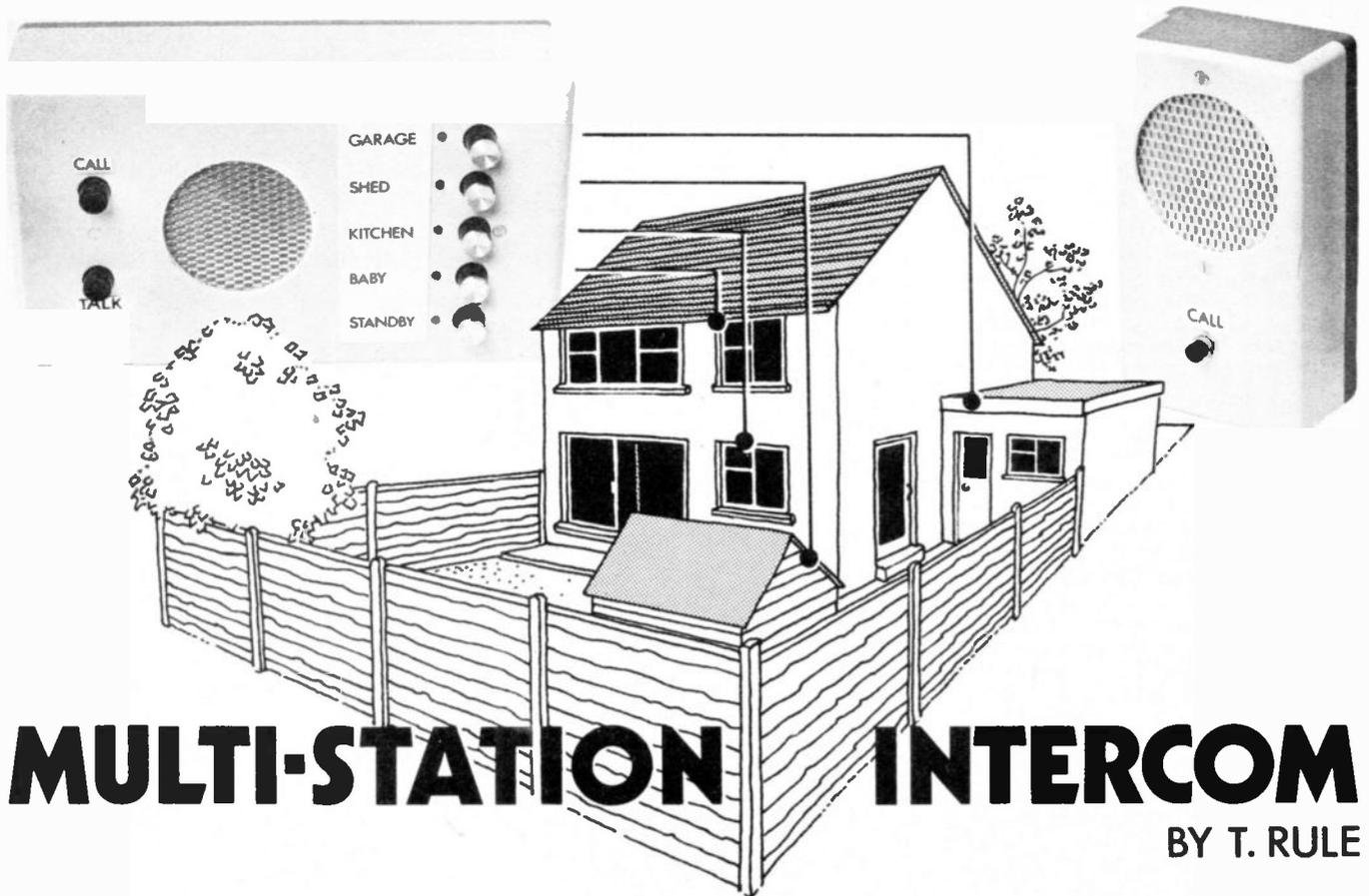
## Subscriptions

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £13.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.



THE unit to be described can be built to connect to any number of slave units via a two-wire interconnecting lead. Designed to provide private intercommunication between the master unit and any slave, it can also be used as a baby alarm or a general security system, and provides a means of listening into the slave units. For example, if a slave unit is mounted outside somewhere in the grounds of the property, it is possible to listen in on that unit for any intruders who may be nearby.

The basic unit described here has been built to supply four slave units and operate from a PP3 battery, and be used

for simple intercom purposes. If it is intended for use as a baby alarm or security system a simple mains power supply should be used instead of the battery, but with a suitable switch to change over in the event of mains supply failure. A circuit for this is suggested.

### DESCRIPTION OF SYSTEM

The unit is simple to construct and all parts are available from a number of advertisers. Fig. 1 shows a block diagram of the basic circuit. One speaker (LS2) is connected to the amplifier input via the PRESS TO TALK switch S1, and the other

speaker LS1 is connected to the amplifier output. Pressing the switch to change over the two speakers enables communication from one to the other, depending on which one is used as the microphone at any time. The PRESS TO TALK switch is mounted on the master unit. In the standby position the slave speaker is used as a microphone and can be listened into by the master unit.

With an intercom system it is important to be able to "call" a selected slave or conversely for a slave to be able to "call" the master unit. This is made possible here by connecting some of the output back to the input via a phase-shift

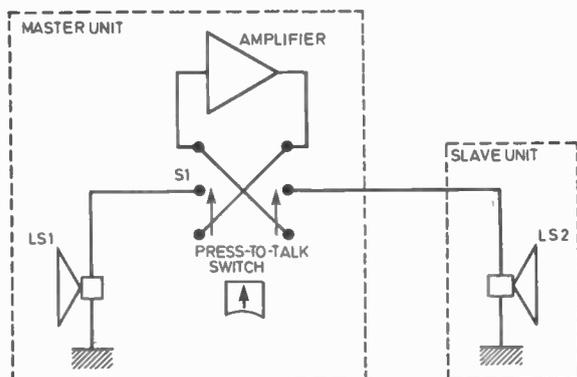


Fig. 1. Block schematic of the basic intercom circuit.

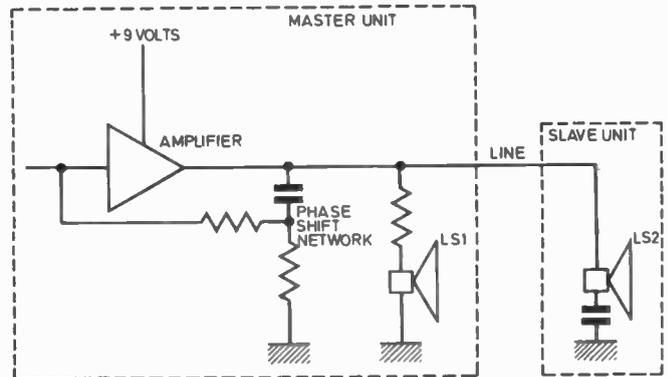


Fig. 2. Basic circuit when the master "calls".



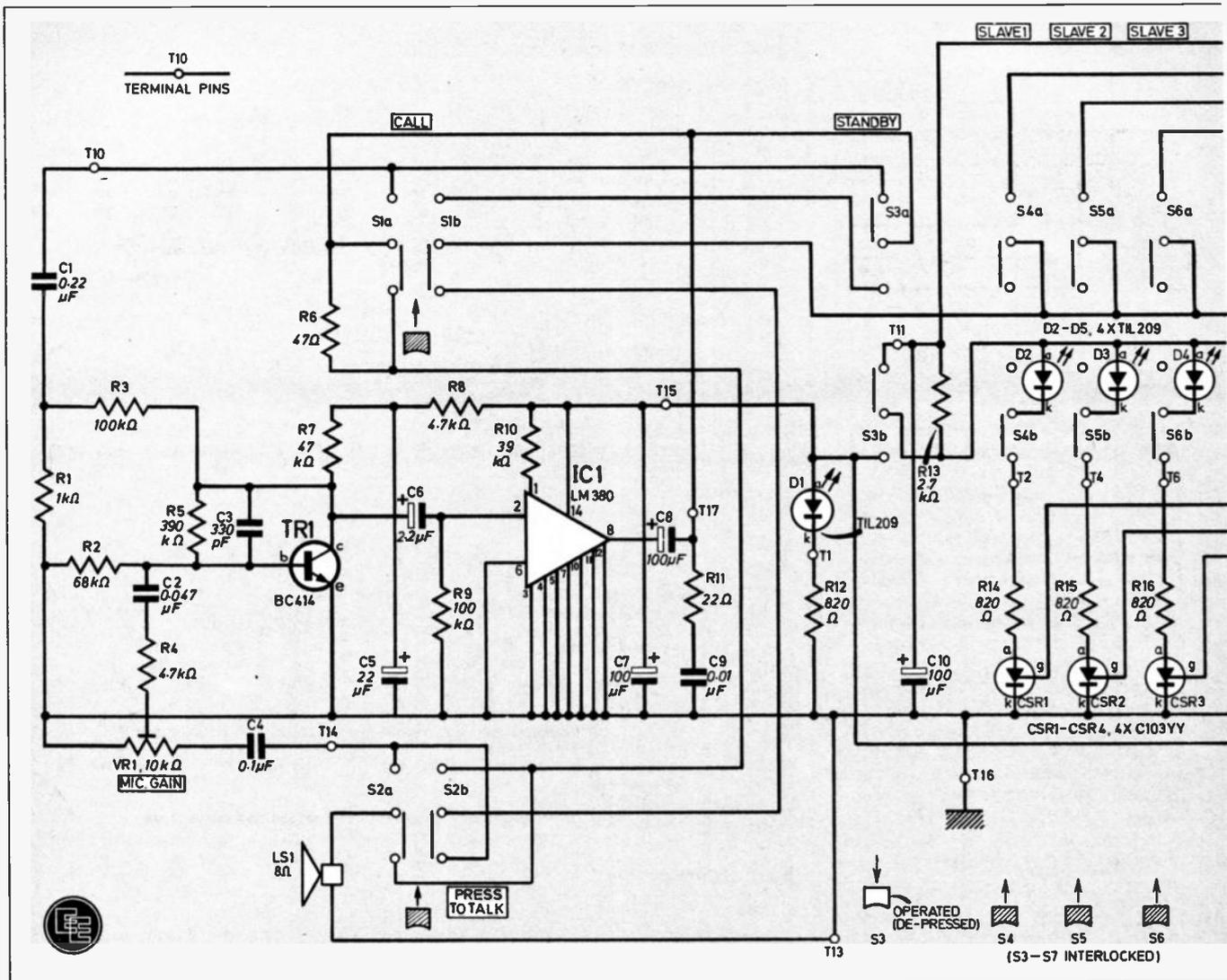


Fig. 4. Complete circuit diagram for the Multi-Station Intercom. All switches are shown in the standby position. The circuit for the slave unit is shown in the panel on the far right.

Switches S3 to S7 are interlocked push-button types and only one can be depressed at a time. Depressing a button automatically releases any other that may have been depressed.

The basic amplifier uses the LM380 integrated circuit IC1 but as this has a fixed gain an extra transistor stage TR1 has been added to improve the sensitivity.

If a slave is selected (assuming Slave 1) the speaker unit on that line will act as a microphone and is connected via S4a, S1b, and S2b to the input of TR1. The output of IC1 connects to the master speaker via S1a and S2a.

When S2 is pressed to change over the connections the two speaker systems are reversed and the master speaker becomes the microphone and the slave the speaker.

### CALLING A SLAVE

A slave is selected by pressing S4, S5, S6 or S7. The slave is then called by

pressing switch S1. The power supply is then connected via S3b (now in the lower position) and some of the output of IC1 is connected to its input via C7, S1a, C1, R1, R2, C5, causing the amplifier to oscillate. At the same time the slave speaker is connected to the output of IC1 via S1b and S3a (now in its lower position). The master speaker is also connected to the output but via a limiting resistor R3 to reduce the volume of the calling tone.

Releasing S1 reverts the circuit back to its normal mode and two-way communication can take place. The PRESS TO TALK switch S2 MUST be pressed each time the master speaks in order that its speaker becomes the microphone and the slave the loudspeaker.

### SLAVE TO MASTER

With all switches in the standby position, if a slave calls the positive supply is connected to the amplifier IC1 via the

slave speaker voice coil, and D9 (assuming Slave 1 is calling). The supply is also connected to the gate of CSR1 via R18 turning it "on" and so lighting up D2.

As some of the output from IC1 is connected to its input via S3a in the "standby" position the circuit will oscillate and put a tone onto the master unit speaker. This tone will also be heard at the slave due to its speaker being in series with the supply to IC1.

The master unit then selects the line calling and the circuit again reverts back as shown in Fig. 1.

Selecting the calling line also disconnects the supply to the thyristor CSR1 via S4b and switches off the l.e.d. indicator D2. An l.e.d. indicator D1 is also connected to the IC1 supply and indicates when the unit is "on". To check that the whole system is "off" with no calls waiting it is only necessary to check that all the l.e.d.s are extinguished.

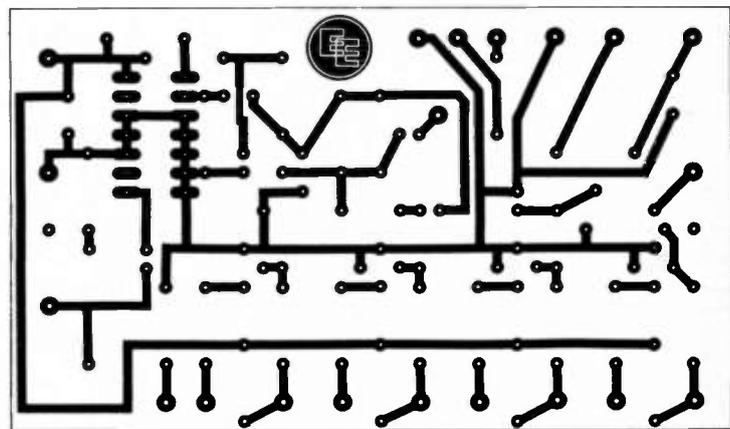
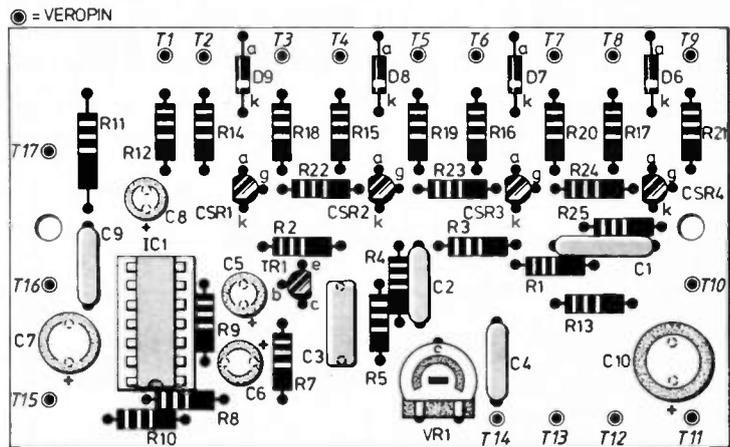
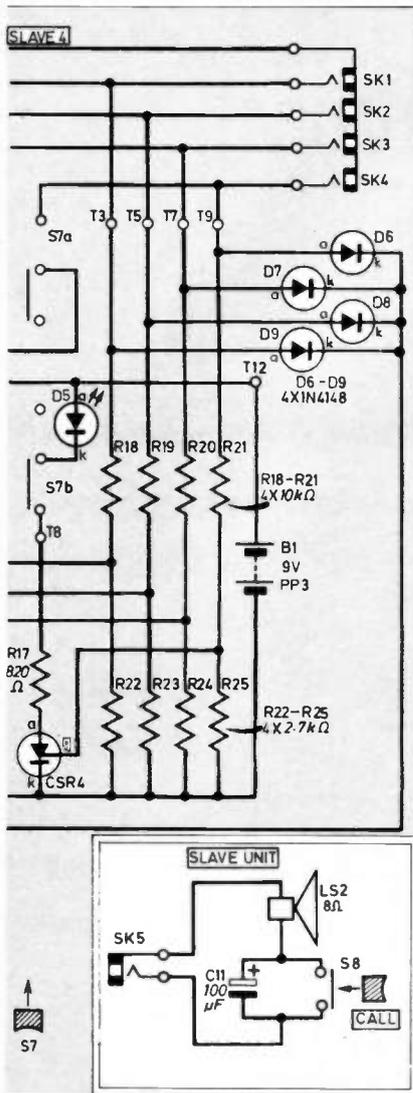


Fig. 5. Component layout on the topside of the circuit board and full size printed circuit board master.

## SENSITIVITY CONTROL

A preset potentiometer VR1 is provided so that the sensitivity can be adjusted to a suitable level, however this control will normally be used in its maximum position if monitoring of a slave is desired.

The actual audio frequency of the calling tone will be dependent on a number of things, for example, the type of speakers used, state of the battery voltage, etc. The frequency can be modified by changing the values of C1 and/or R1. In any event the tone produced when called by a slave will be lower in pitch than when the master unit calls and C1 and/or R1 may need adjusting for the most suitable sound.

Note that R13 is shorted out when in the "standby" position. This enables the full supply voltage to be applied to IC1 (for calling) via the line and slave unit. When the line is selected this resistor

maintains voltage on the line to operate the thyristors should another line call, but allows an "audio earth" via C10 for the slave speaker/microphone. If the audio earth was via the supply line, instability would result.

## CONSTRUCTION

One printed circuit board is used and this carries the bulk of the components. The full-size pattern appears in Fig. 5. Be careful to maintain the correct polarity of all electrolytics and diodes and also check the position of pin 1 of the LM380 before soldering it into place or plugging into a socket.

## WIRING

There is a considerable amount of hard wiring on this project and, although the actual layout is not critical, care should



be taken regarding connections to the various switches. It is suggested that suitable coloured leads be wired to the switches first and then the p.c.b. placed into position and its terminal pins connected up. Leave the leads long enough so that the board can be lifted clear for any servicing that may be required at a later date. The full interwiring is shown in Fig. 6.

## SUB-PANEL

All components are mounted on a sub-panel as shown in Fig. 7. Mark out the aluminium accurately but only pilot drill in the first instance with a 1mm drill. By doing this the sub-panel can be used as a marking template for the front panel of the case, thus ensuring exact register of the two sets of holes.

Note that certain holes are NOT required in the front panel, these are holes lettered "A" and "E".

# MULTI-STATION INTERCOM

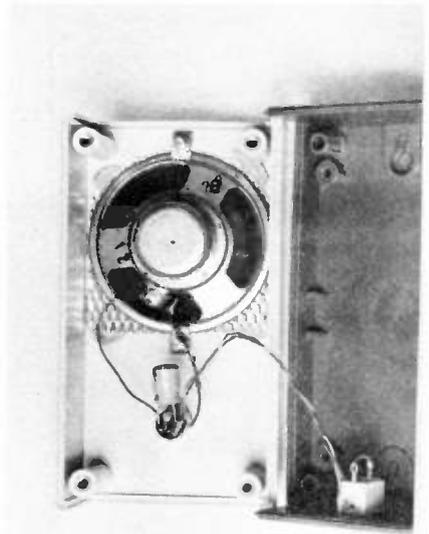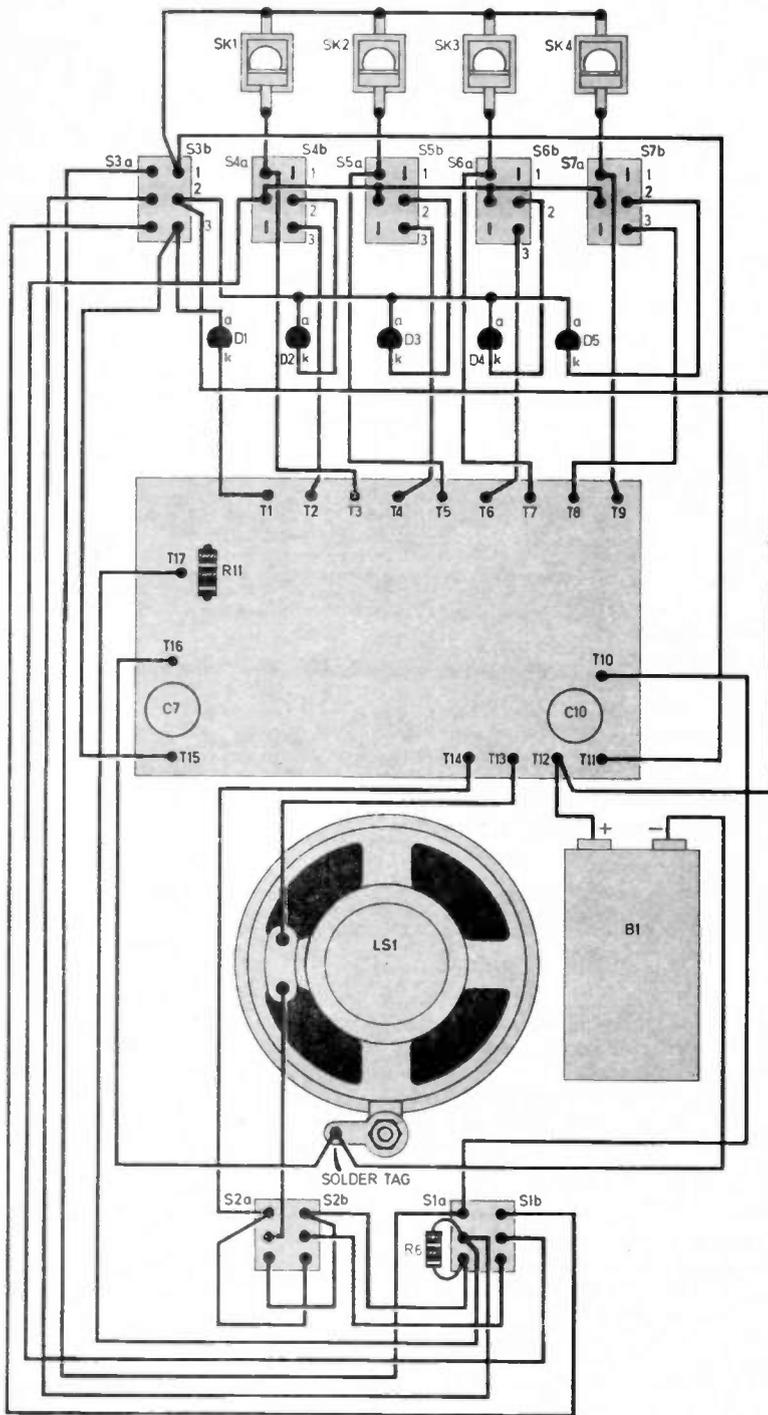

Wiring and component layout inside the completed slave unit.

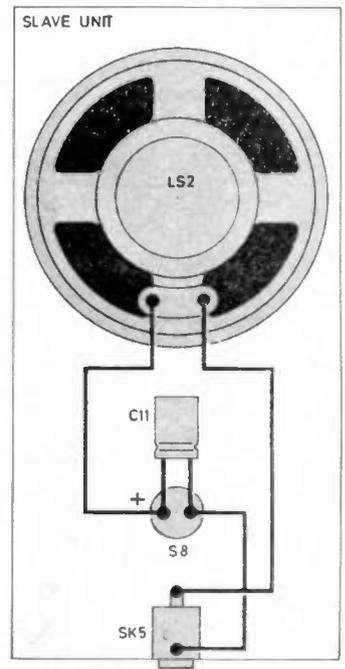
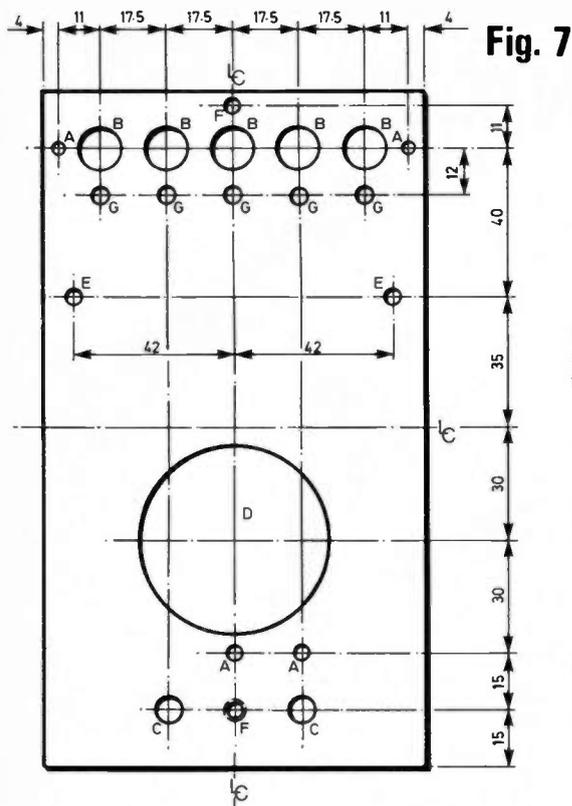


Fig. 6. Interwiring details for the master control and one slave unit. The case mounted components have been laid "flat" for clarity of wiring.

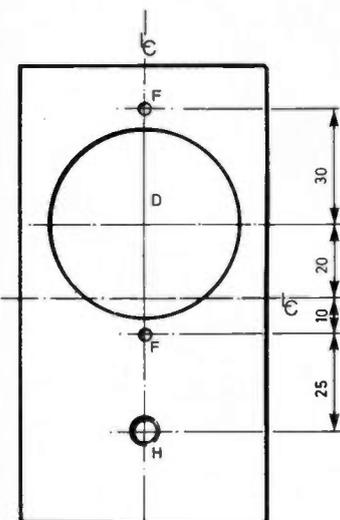


**Fig. 7**

Fig. 7. Measurement and drilling details for the sub-panel.

HOLE mm	A	B	C	D	E	F	G
SUB PANEL	3	11	6.5	50	4	3	SEE TEXT 1
FRONT OF CASE	-	11	11	50	-	3 SUNK	TO SUITED SEE TEXT


NOTES: DRILL ALL HOLES 1mm DIA & USE AS FRONT PANEL TEMPLATE BEFORE MAKING FULL SIZE HOLES 'G' TO FRONT PANEL ONLY



**Fig. 10**

HOLE DATA  
 1 'D' HOLE 50mm DIA  
 2 'F' HOLES 3mm DIA  
 1 'H' HOLE 7mm DIA


1 JACK (SK5) HOLE 6.2mm DIA (IN CENTRE OF END PANEL)

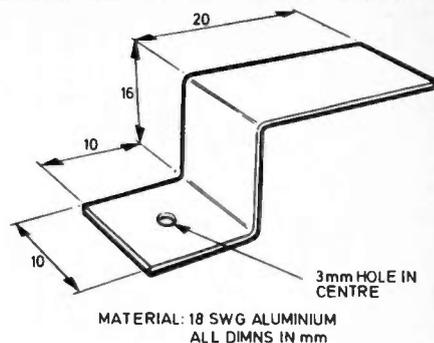

**Fig. 8**

MATERIAL: 18 SWG ALUMINIUM  
 ALL DIMS IN mm

Fig. 8. Details of the battery bracket.

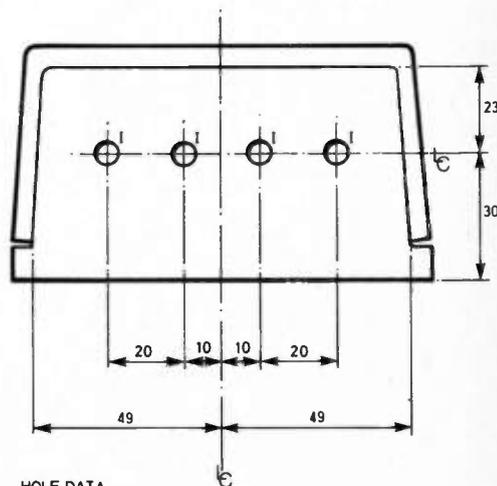


**Fig. 9**

Fig. 9. Drilling details for the end panel of the master unit case.

Fig. 10. Slave panel drilling details. A 6.2mm hole should be made in the centre of the end panel for the slave jack socket.

HOLE DATA  
 4 'I' HOLES 6.2mm DIA

Fig. 11. Suggested sub-assembly for the five indicator l.e.d.s.

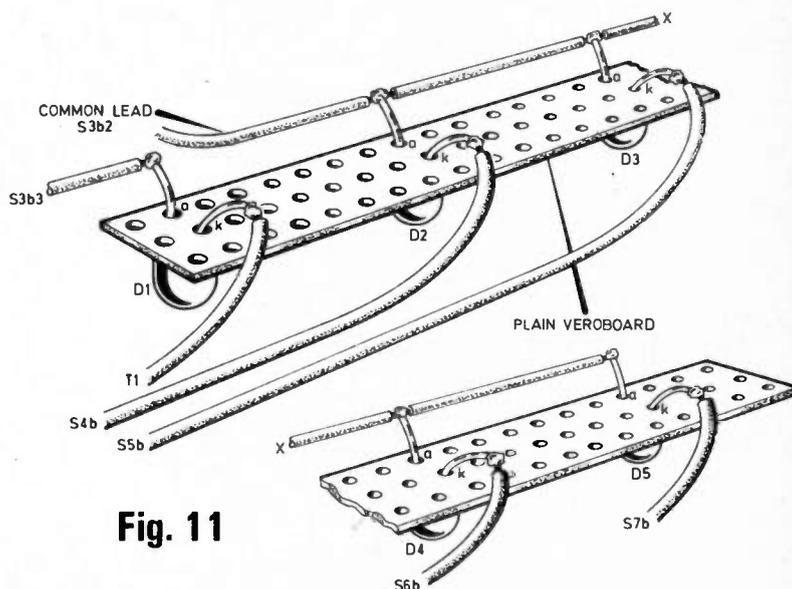

**Fig. 11**

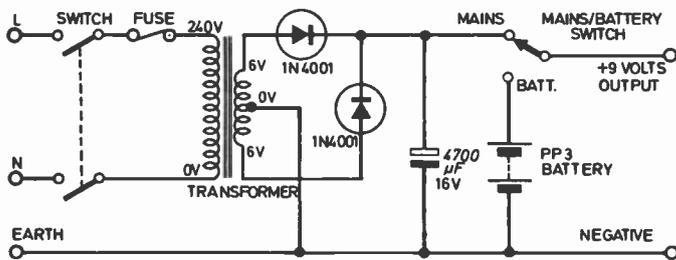


Fig. 12. Suggested circuit diagram for a mains/battery power supply.

Four plastic feet are fitted to the inside of the case to maintain the correct distance between the sub-panel and case. Two 6BA screws with nuts for spacers are also used to hold the sub-panel in position.

A small metal bracket holds the PP3 battery in place and this is made as shown in Fig. 8. This bracket is not required if a mains power supply is used.

### CASE DRILLING

Fig. 9 shows the holes required in the end of the case for the miniature jack sockets and Fig. 10 shows the drilling required for the slave units. When cutting the 50mm hole in the cases a "Q" Max cutter can be used but warm the case to about 20°C before cutting (warm the cutter as well); this will enable the plastics case to be cut cleanly without splitting. If cutting is attempted with the plastic very cold it will split.

### LED ASSEMBLY

The I.e.d.s are held in place by first mounting onto a strip of plain perforated board, Fig. 11, and a strip of foam mounted along its back. This sub-assembly is then sandwiched between the case and sub-panel. Using a 0.1in. board the I.e.d.s will be spaced every seven holes, that is, six holes between each I.e.d. In any event the I.e.d.s should be a firm fit into the holes in the case, but the use of this extra

Completed prototype of the master unit. The plain perforated board has been replaced by a printed circuit board.

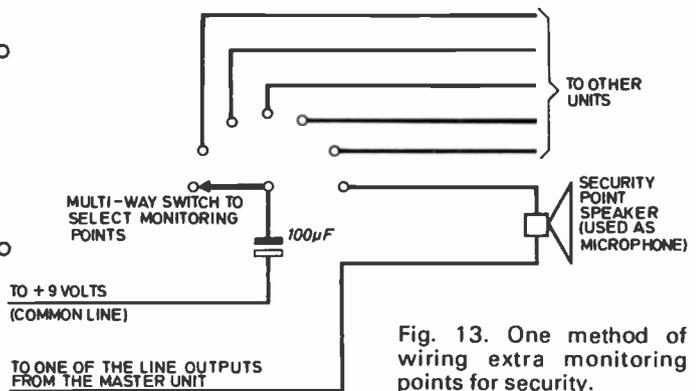
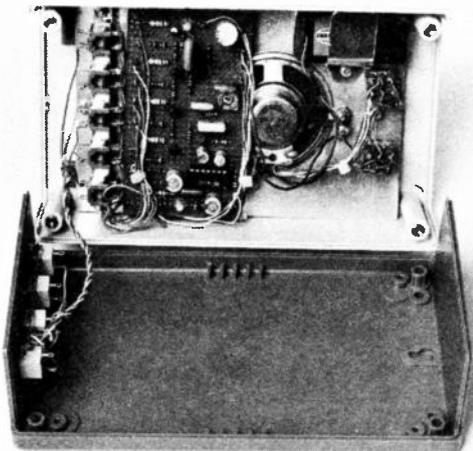


Fig. 13. One method of wiring extra monitoring points for security.

mounting strip makes for easy handling during wiring and assembly, or when servicing, as the five I.e.d.s can be handled as a single assembly.

The loudspeaker apertures are covered with a suitable fret before final assembly and this may be either a metal or cloth type. Metal is preferred as it will provide greater protection for the speaker units. The fret is held in place by the use of white Bostik (the writer uses Bostik 4 multi-tile adhesive).

The cases specified have special mouldings in the backs which can be knocked out to provide holes for fixing the units to a wall. Depending on the labelling, the units can be mounted either way round.

### MOUNTING THE SUB-PANEL

When mounting the five-way push-button unit onto the sub-panel, space it away from the panel approximately 7mm, by using 6BA screws with nuts as spacers. This ensures the actual buttons will be at the same height as the "call" and "PT" buttons. To ensure smooth operation of the buttons it is important that all burrs are removed from the holes in both the sub-panel and case.

### INSTALLATION

No problems should be encountered here as the "lines" are low impedance and only passing a very low current, a few milliamps. Standard type bell wire may be used for indoor wiring but if cable runs are made outdoors bell wire will be unsuitable as it is not weather-proof. For outdoor cable runs p.v.c. covered cable should be used. On NO account must any direct connection be made between these "lines" and the mains or telephone

wires, they may however be laid alongside such cables if this is unavoidable. In this event some mains borne interference may be heard on the intercom system. Each end of a "line" should be terminated with a 3.5mm miniature jack plug which is then plugged into the slave unit.

### OPERATION

Select the line required, sounds should be heard from the slave unit (assuming that someone is there). Press the CALL button, a tone should be heard at both ends of the line. When the slave answers, press the PRESS TO TALK button before speaking and release it to listen.

When on standby, a "slave" may be called by pressing the CALL button. Again a tone should be heard at both ends. Select the line that is calling and press the PRESS TO TALK button to answer, release to listen again.

As each slave calls, the appropriate I.e.d. should indicate which line has called. If a conversation is in progress and another slave calls, the I.e.d. will indicate that a call is waiting, and this can be answered by selecting that line and either dealing with the call or asking them to wait until you can call back. If a conversation is already in progress, no tone will be heard if additional lines call in.

### MAINS POWER SUPPLY

If several slave units are being used, it would be wise to operate the system from the mains. A suggested circuit for this is shown in Fig. 12. An extra jack socket should be fitted to the master unit and the battery connections taken to this with a suitable lead then going to the power supply.

### USE AS A SECURITY UNIT

By using the circuit shown in Fig. 13 any number of extra "microphones" can be selected so that it is possible to listen in to a number of positions. It is not possible for these to call the master, although the master can call them if required and engage in normal two-way communication. This facility could also be useful where, for example, a number of children's rooms need to be monitored. Other uses will no doubt come to mind. □



By Dave Barrington

### Screened Plastic Boxes

The complete BIM2000 range of plastic multi-purpose cases from Boss are now available internally coated with 0.05mm thick, black EMI/RFI conductive shielding.

Having all the normal electrical screening protection facilities associated with steel or diecast aluminium enclosures, it is claimed that these ABS boxes also have the added advantage of light weight and easy drilling.

Available initially in black only, the deep profile lids are firmly secured to the base by screws running into brass hank bushes which not only ensure a good electrical connection for total screening but also provide protection against the ingress of moisture.

The cases are moulded in seven sizes ranging from 100 x 50 x 25mm to 190 x 110 x 90mm. For further details of the complete range contact: Boss Industrial Mouldings Ltd., Dept EE, James Carter Road, Mildenhall Suffolk IP28 7DE.

### Catalogue

A new shortform hobbyist catalogue featuring a wide range of products for the electronics enthusiast has just been issued by the Retail Division of BICC-Vero.

Products covered in the 6-page colour catalogue include circuit boards, solderless breadboards, boxes, tools and a wide range of accessories.

Copies of the "The Hobby Herald" catalogue are available Free from BICC-Vero Packaging, Dept EE, Retail Department, Industrial Estate, Chandlers Ford, Eastleigh, Hants SO5 3ZR. A large stamped addressed envelope would be appreciated.

### Coloured Knobs

A new range of control knobs, with coloured caps and "skirts", are now being stocked by Ambit International.

These knobs are from the well-known Ritel of Switzerland range and at present consist of matt black bodies with a selection of different coloured caps, pointers, skirts and dials. They also feature push-fit brass collet fixing.

Another ten finishes are available to special order. For more details of the complete range contact: Ambit International.

## CONSTRUCTIONAL PROJECTS

### Car Thermometer

The most expensive item in the *Car Thermometer* is the temperature sensing device and could cause purchasing problems.

The case of this device is stamped with the type number 590kH and as far as we have been able to establish is only stocked by RS Components (order code 308-809). This is an expensive item.

We would point out that RS Components will only supply to *bona fide* traders and readers will have to order through their local component supplier. If any readers are able to "throw" any further light on a source of supply, or equivalent, for the temperature sensor we will be pleased to hear from them.

This project has been specially designed to fit into a small hand-held case with sloping display panel. This case is available from Lascar Electronics Ltd., Dept EE, Module House, Whiteparish, Salisbury. It is also available from Verospeed, Dept EE, Boyatt Wood, Eastleigh, Hants SO5 4ZY, and is listed as a hand-held case for digital panel meter (stock no. 89-25463J).

### Dual Power Supply

The mains transformer used in the prototype *Dual Power Supply* was custom-made by Samson's (Electronics) Ltd., Dept EE, 9 Chapel Street, London NW1. A similar mains transformer with 24V 1.5A and 9V 1.5A secondaries could be used but, because of physical size, may require altering the layout within the case.

The heatsink and meter were purchased from Ambit International and the Sifram front panel knobs are stocked by Electrovalue and Marshall's.

It is quite in order to use 0.47Ω 3W wire-wound resistors for R1 and R8.

### Multi-Station Intercom

The two-tone moulded plastics cases called for in the *Multi-Station Intercom* are Verobox types and should be available from most component suppliers. Stockists include Bi-Pak, Maplin, Magenta, Electrovalue, and Verospeed.

The sockets SK1 to SK5 are 3.5mm miniature types with normal closed contacts. All the interlocking switches (S3 to S7), mounting plate and knobs are available from Maplin.

The thyristors (CSR1 to CSR4), type C103YY, appear to be only available from RS Components.

### Expanded Add-On Keyboard for the ZX81


It is quite possible that many of the add-on keyboards now on the market could benefit from the *Expanded Add-On Keyboard for the ZX81* project, however, these have not been investigated by us. The keyboard used in the prototype was obtained from Redditch Electronics (Dept. EE), 21 Ferney Hill Avenue, Redditch, Worcs B97 4RU.

The additional keyboard switches and switch "tops" are available from Redditch or Maplin. The Verostrip is available from Vero Electronics.

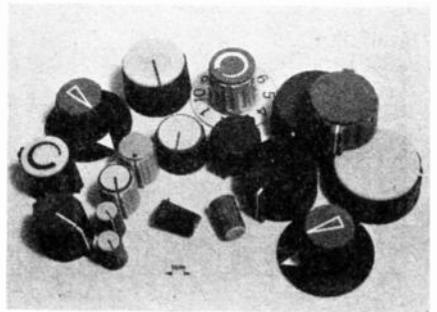
### Buzz Off

The 12V audible warning device used in the prototype of the *Buzz Off!* model was obtained from RS Components, stock number 248-808. However, most of the solid-state buzzers on the market are rated from 6V to 20V operation and could be used.

These devices appear to be about half the price of the RS item. Stockists of these buzzers include Electrovalue, Maplin, Magenta, TK Electronics and Ambit.




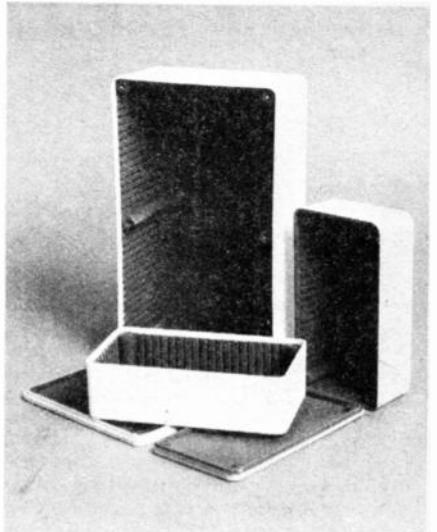Selection of control knobs from Ambit International.



New range of "screened" plastic cases from Boss Industrial Mouldings Ltd.

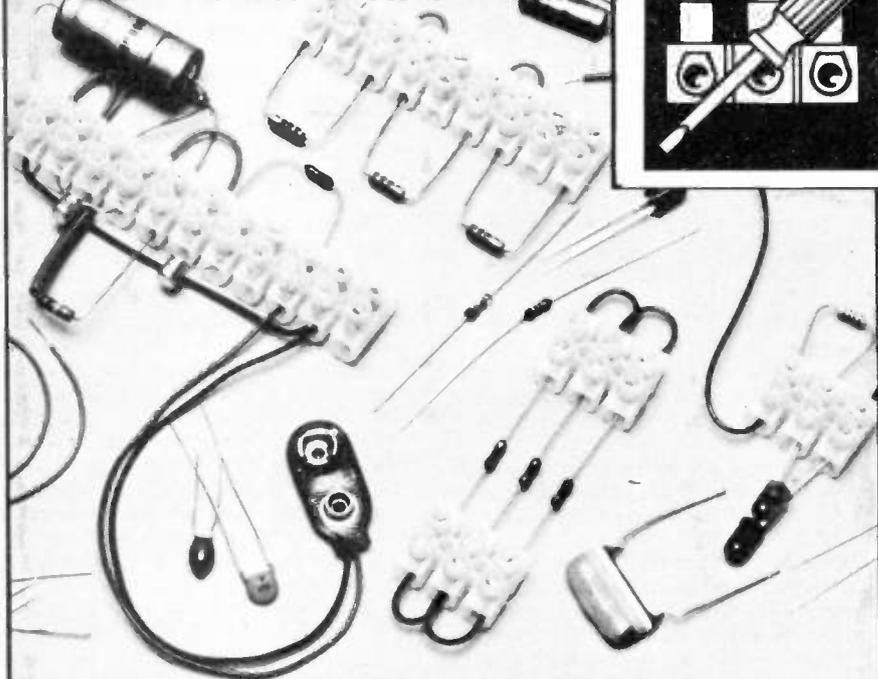A NEW SERIES FEATURING A TEARLESS  
TABLETOP TECHNIQUE BY GEORGE HYLTON



## INTRODUCING ELECTRONICS Part 6 DIGITAL ELECTRONICS

IN THIS, the last of the present series, we'll take a quick look at digital electronics. Since this topic includes practically the whole of computing and much of modern communications, it will have to be a rather superficial look. However, interested readers can obtain more detailed knowledge, in a painless way, by following *The Electronics of Information Technology* now running in this magazine.

### DIGITS: WE ALL KNOW THEM

There's nothing strange about digits. We have five on each hand. Most of us learn to count on them, thereby gaining our first practice in digital computing! We are also familiar with the idea of sending messages in Morse Code, an early form of digital communication.

### BACON AND BINARY

It all started long before the electrical age. When the Spanish Armada appeared in the Channel, warning beacons were lit on hilltops to send the message across the country. A beacon is either lit or not. This *on-or-off* feature is characteristic of digital communications.

Of course, you can light one beacon

for an early warning, two for a more urgent one and three for imminent danger—but the on-off nature of the individual fire remains.

This is in distinction from *analogue* signals, where the intensity of the signal is varied in step with the information to be conveyed, as in a.m. radio where the strength of the transmitter is made to change in step with the sounds at the studio microphone.

The trouble with analogue signals is that they are very susceptible to interference. Imagine how difficult it would have been to signal with beacons by varying their brightness in an *analogue* way. Even if it could have been accomplished at the transmitting end, how difficult it would have been for a watcher many miles away to read the variations, perhaps through mist or haze, even though he had no doubt that a beacon was lit.

### SIMPLER WITH DIGITS

The "all-or-nothing" nature of digital signals makes the problem so much simpler.

Morse Code is only partly digital. The lengths of the digits vary (dots or dashes) and this is an analogue feature. True digital codes, with all the elements or

"bits" the same length, are used in machine telegraph systems like teletype, but in fact the basic five-bit code of early teleprinters and teletypes pre-dates the electrical age by several centuries. It was invented by Shakespeare's contemporary, Francis Bacon, for use as a diplomatic code.

Bacon showed how a code message could be hidden in a plain language message. The example he gives shows how the sentence:

STAY TILL I COME TO YOU

can be made to conceal the very different one:

FLY!

The trick is to modify the letters of the plain message in some unobtrusive way; for example, to write some a tiny bit above the line and others a tiny bit below. Each letter can then have one of two positions, high or low. The intended reader then groups the letters of the plain message into lots of five and rewrites them as "highs" (H) or "lows" (L). So STAY TILL I COME TO YOU may become, say, HLLH LHHLL LLLHH LLL.

The LLL at the end are spares, because the first three groups are all that are needed. The decoder looks up his code book and finds that HLLH means "F", LHHLL = "L", and LLLHH = "Y". Message read, he packs his bags and leaves!

### DIGITAL ELECTRONIC CODES

Bacon's code is a true binary code, with the essential "all-or-nothing" character of the individual elements. In transistor terms, we may agree to say that there is a "high" (H) when a transistor collector goes positive and a "low" (L) when it falls to zero.

These two states, which in practice correspond to, say, transistor off, and passing no current, and transistor hard on, passing so much current that all the supply voltage is dropped across a collector load resistance, can also be designated "1" and "0". So HLLH could be written 11001. This looks like a number and can indeed be treated as one. Thus, doing subtraction, we could say that  $11110 - 01110 = 10000$ .

We have now arrived at a strange state of affairs where 0's and 1's can signify either letters or numbers, and having turned letters into numbers we can then add or subtract them! In fact, anything that can be turned into an electrical signal can be "digitised" and the digits manipulated.

If you watch TV, then practically every day you see some of the tricks which can be performed by digitising the TV picture then manipulating the digits as numbers. The picture can be made to expand, contract, change shape, split into several identical pictures, even fold over like the page of a book or wrap itself round a cylinder. All done by digits.

## PULSE CODE MODULATION

In the communications field, an important development is the now widespread use of digitised speech. Many years ago, long before the transistor, a British engineer worked out the basic principles. Last month we noted how in an a.m. radio receiver the detector in effect produces a string of samples of the original programme. So long as there are enough samples, the gaps can be filled in and the original programme waveforms recreated.

In *Pulse Code Modulation* the speech is sampled at a high rate (at least 8000 times a second). This gives a sequence of samples whose size depends on the intensity of the speech at the instant of sampling (Fig. 6.1). Instead of transmitting these as variable-amplitude analogue signals, each sample is digitised, that is turned into a string of 0's and 1's. This is transmitted (with the usual advantages of a binary system) and turned back into analogue signals at the receiver.

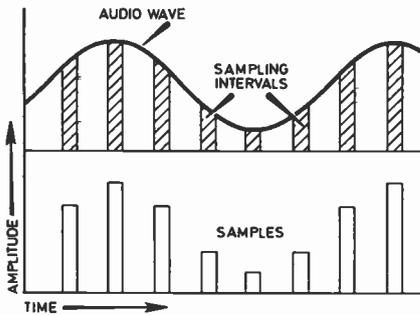


Fig. 6.1. Sampling an audio signal.

If the sampling time is short (say one microsecond), then the gap in time which comes before the next sample is due can be filled with samples of other speech waveforms. In this way a number of different conversations can be interleaved

in time. At the receiving end, accurate timing circuits sort them out again.

In this way, many speech channels can be interleaved in time, transmitted over the same cable, and sorted out again. In the new telephone exchanges, all the speakers' voices will travel along the same "highway". To connect two speakers together, timing "gates" will be opened just long enough to let through the samples of their voices, then closed to exclude everybody else's.

## NOT, OR, AND, NAND, NOR

The basic digital circuits are rather boring. They are either the equivalent of switches which open to let signals pass (Fig. 6.2) or "inverters" which turn 1's into 0's, and vice-versa.

A single *n*pn transistor with a collector load resistance can act as an inverter. A large positive input to its base causes the collector voltage to fall from a positive value (= "1", say) to zero (= "0", say).

In computer jargon, a "1" at the input becomes a "not 1" at the output. An inverter is often called a NOT circuit.

Fig. 6.2a is an OR gate because signals are passed on if switch A or B or C is closed. Fig. 6.2c is an AND gate because no signal is passed on unless A and B and C are closed.

The common transistor equivalents such as (b) and (d) also invert, so they are NOT OR (= NOR) gates and NOT AND (= NAND) gates. In this example they are 3-input gates but other numbers of inputs can be catered for.

Gates in integrated circuits are more complicated but their function is the same. Combinations of these simple circuits are all that is needed to form the hardware of computers, capable, when programmed, of adding and subtracting binary numbers. Multiplication and division can be performed by repeated addition or subtraction.

It may be inexpressibly tedious for a human being to work out  $7 \times 3$  as  $3 + 3 + 3 + 3 + 3 + 3 + 3 = 21$ , but a computer never complains. Of course, there is no such thing as 3 in binary codes. But combinations of 1's and 0's can be made to stand for any number. Thus 3 becomes 11 in binary. It looks complicated, but that's merely because of unfamiliarity.

## FLIP-FLOPS AND THINGS

Let's look at some slightly less boring binary circuits. In Fig. 6.3, provided the resistances are correct, TR1 is turned hard on when S1 is in position 1, and off in position 2. The l.e.d. lights or not, accordingly.


In real life binary circuits, the transistors are controlled mostly by voltages or currents from other circuits rather than by switches. The next circuit (Fig. 6.4) illustrates the point.

Here, each transistor is controlled by the collector voltage of the other. If TR1 is on, its collector voltage is low so there is no voltage to drive current through R2 to turn on TR2. This in turn means that TR2 collector voltage is high, which is just what is needed to turn on TR1.

Unless you do something about it, the circuit will stay in this state for ever. What you do is move the bit of wire which serves as S1 from its central, neutral position to position 1. This shorts out TR1 base current, turning TR1 off. Its collector voltage goes high and this turns TR2 on. The circuit has "changed state". It stays that way when S1 is returned to neutral (2). This is memory, of a sort. The circuit remembers what state it has been put into.

To reverse the state, move S1 to 3. And so on. You can also reverse the state by touching your switch wire on to the collector of whichever transistor is NOT conducting. In these ways the circuit can be made to "flip" out of one state and "flip" into the other, as often as you like.

Fig. 6.2. Theoretical diagram representing the various basic gates used in logic circuits. (a) shows an OR; (b) NOR; (c) AND, and (d) NAND gate.

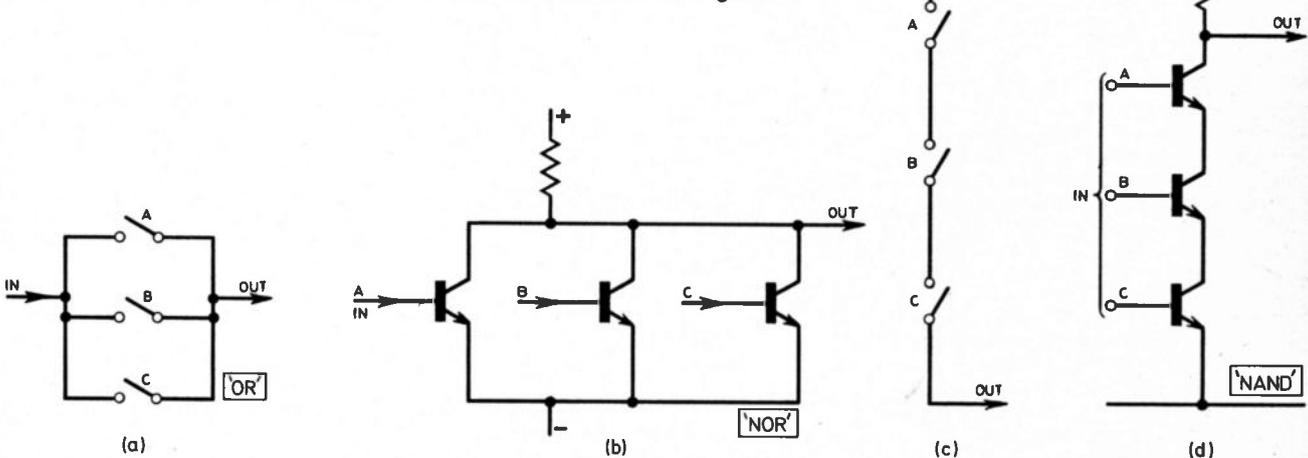


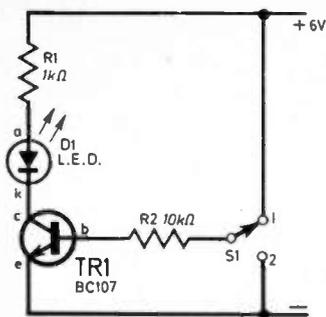
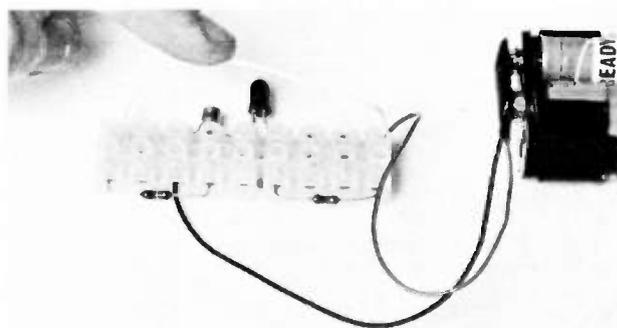
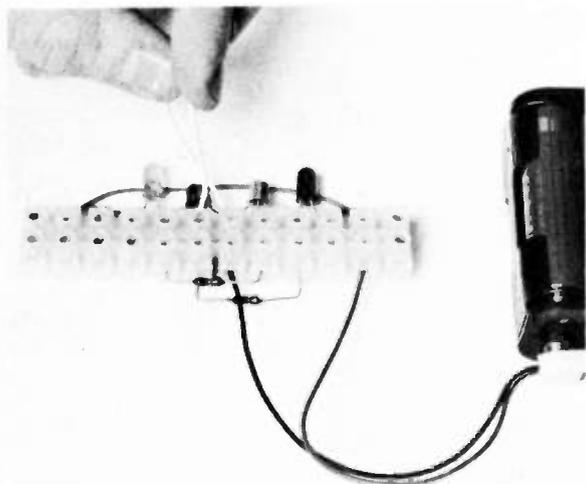


Fig. 6.3. Simple "flip-flop" circuit and demonstration model wiring (right). Photo on the right shows TR1 being switched on by the "wire" switch S1.

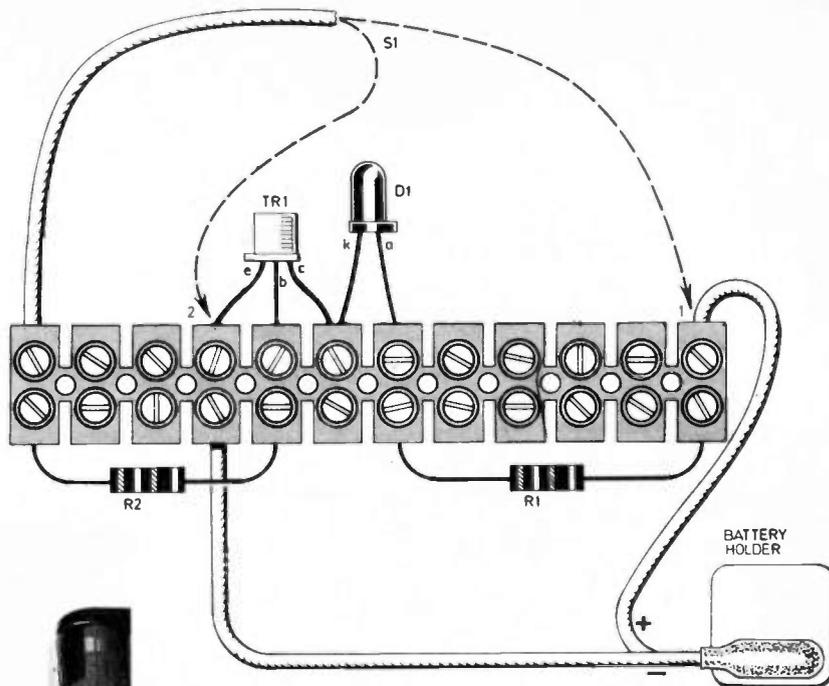

Shorting out TR1 base to switch on TR2, see Fig. 6.4.


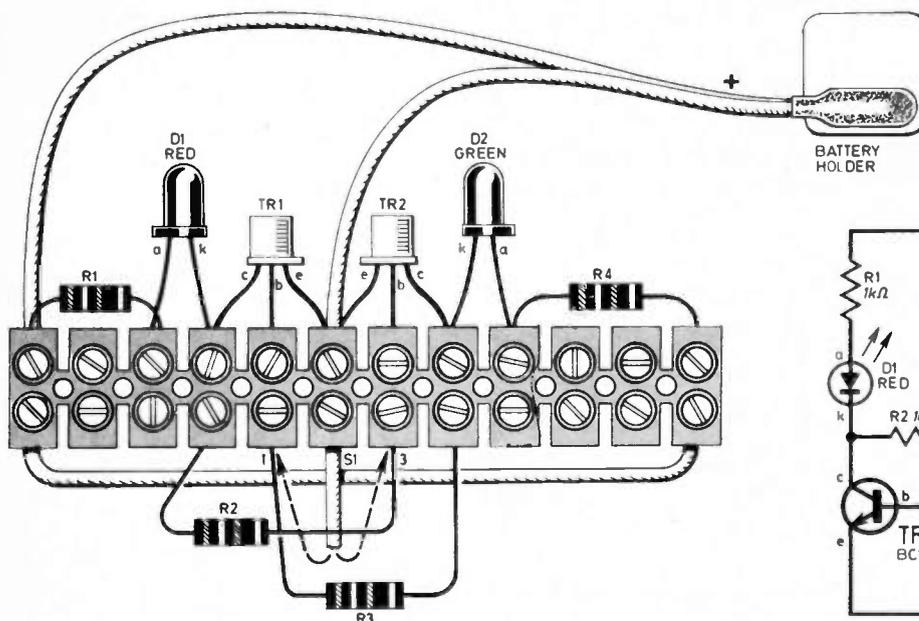


Fig. 6.4. Circuit diagram and demonstration model using another transistor to control the flip-flop circuit of Fig. 6.3.

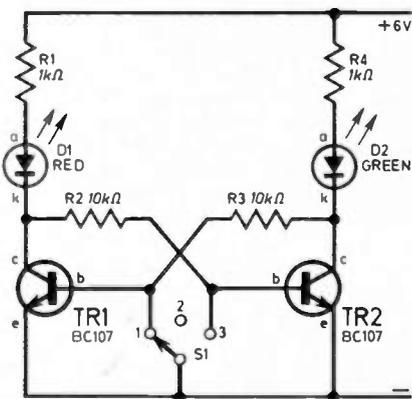


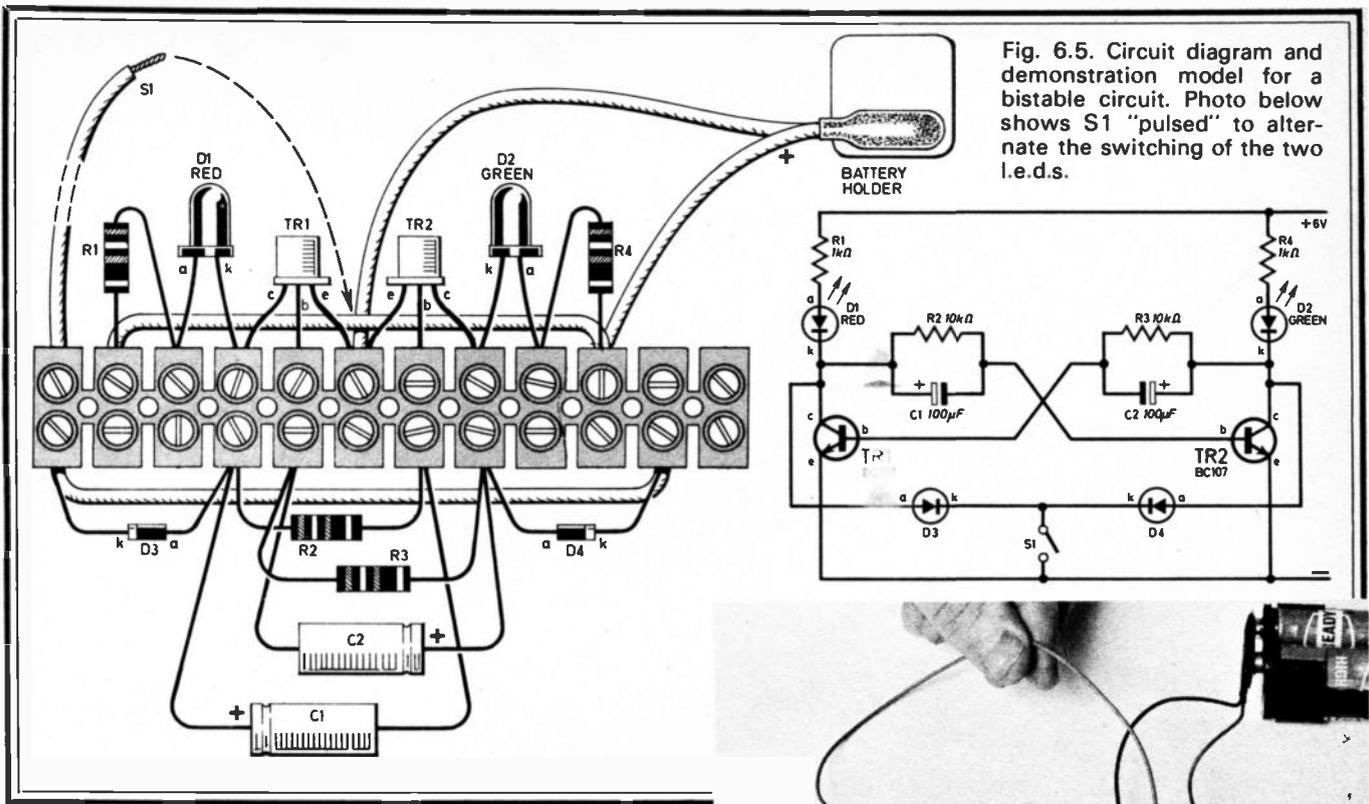


Fig. 6.5. Circuit diagram and demonstration model for a bistable circuit. Photo below shows S1 "pulsed" to alternate the switching of the two l.e.d.s.

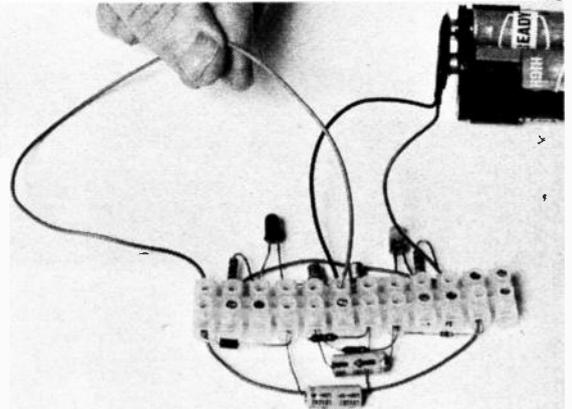

## BISTABLES

Circuits like this, which can be put into either of two states and stay there are called *bi-stable* circuits, or just *bistables* for short. There is obviously something very binary about them, and they become of use for computing when modified so that they change state every time an input pulse is applied, even though it is applied simultaneously to both transistors.

You can do the trick by adding two capacitors and two diodes (Fig. 6.5). A diode allows current to pass only in the direction of its "arrowhead" triangle. With S1 open, whichever way current tries to flow it is blocked by one diode. But when S1 is closed, current can flow through both diodes, to the negative line. In effect, this connects the collectors to negative and turns off both transistors.

But with S1 open, one collector is "high". Its associated capacitor charges.

It takes time to discharge a capacitor, as you know. If S1 is given just a quick flip, some charge remains, and it is always of the correct polarity to reverse the state of the circuit. So, by repeatedly flipping S1 the state can be changed again and again. In a real-life circuit S1's job might be performed by another transistor, turned on by pulses to its base. These pulses could be derived from one of the collectors of another bistable.

Note that any *one* transistor, say TR2, changes state every alternate time S1 is closed. If output pulses are taken from TR2, there are only half as many output pulses as operations of S1. If S1 is replaced by a pulse-driven transistor, the bistable divides the number of input

pulses by two. Two bistables, one driven from the other, divide by 4. Three divide by 8... and so on. Chains of bistables like this form *counters*.

Such is the art of i.c. manufacture that a chain of 14 bistable or "flip-flops", each in fact containing several transistors, can be bought for about 50 pence. The i.c. also contains a circuit which resets the whole thing to zero when required. A four-stage counter, which is capable of counting up to 16, is often arranged to reset every time it reaches 10. This makes it into a *decade counter*.

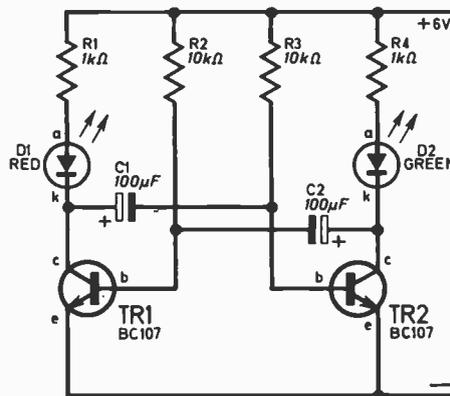


Fig. 6.6. Circuit diagram for an "astable" oscillator which can be built from components from Fig. 6.5.

Bistables can also be connected in such a way that they act as stores or registers which remember a string of digits. The string can be moved along the chain, to emerge eventually at the other end. This is a *shift register*, or moving store. Bistables can also be used as static stores or memories. Most pocket calculators nowadays have such memories. Computers have very large ones capable of storing thousands of digits.

## WINKER

If you want to experiment with computer i.c.s you will be well advised to buy one of the many excellent multi-socket "breadboards" now available for the purpose. I.C.s and components can be plugged in at will and linked up with pushed-in wires. For about £8 you can get a breadboard big enough for nearly all the projects you'll want to try out.

I hope you have enjoyed this series. If so, keep reading, because there are plans for some follow-up articles using the terminal-block solderless technique.

As a final experiment you might like to convert your bistable into an *astable*, that is an oscillator (Fig. 6.6). I'll leave you to work out the changes in connections from the earlier circuit! □

# Car Thermometer



BY M. PLANT

TODAY'S driver could well profit from a knowledge of the air temperature around the car, especially if used to provide a warning of possible ice formation on the road surface.

So, what kind of thermometer would be suitable for use in a car to meet this need and yet also have sufficient range to measure anticipated maximum summer temperatures?

## ANALOGUE OR DIGITAL?

To keep the thermometer small and rugged, a digital circuit design using i.e.d. or l.c.d. displays is called for, since a moving coil meter for an analogue display would make a bulkier and less durable thermometer. Digital design also makes the inclusion of an alarm function easier.

However, 7-segment displays are expensive, and one solution is to use discrete i.e.d.s in a bargraph display of the type used for VU meters. Such a display of, say, ten i.e.d.s in a horizontal format functions as an analogue display but they light in discrete steps.

## BARGRAPH

The 3914 i.c. is purpose-designed to drive a ten i.e.d. bargraph to give an analogue display of the voltage it senses. It is housed in an 18-pin package and the i.e.d.s are normally mounted in-line to give a bar or moving dot display. Its principal advantages compared with a con-

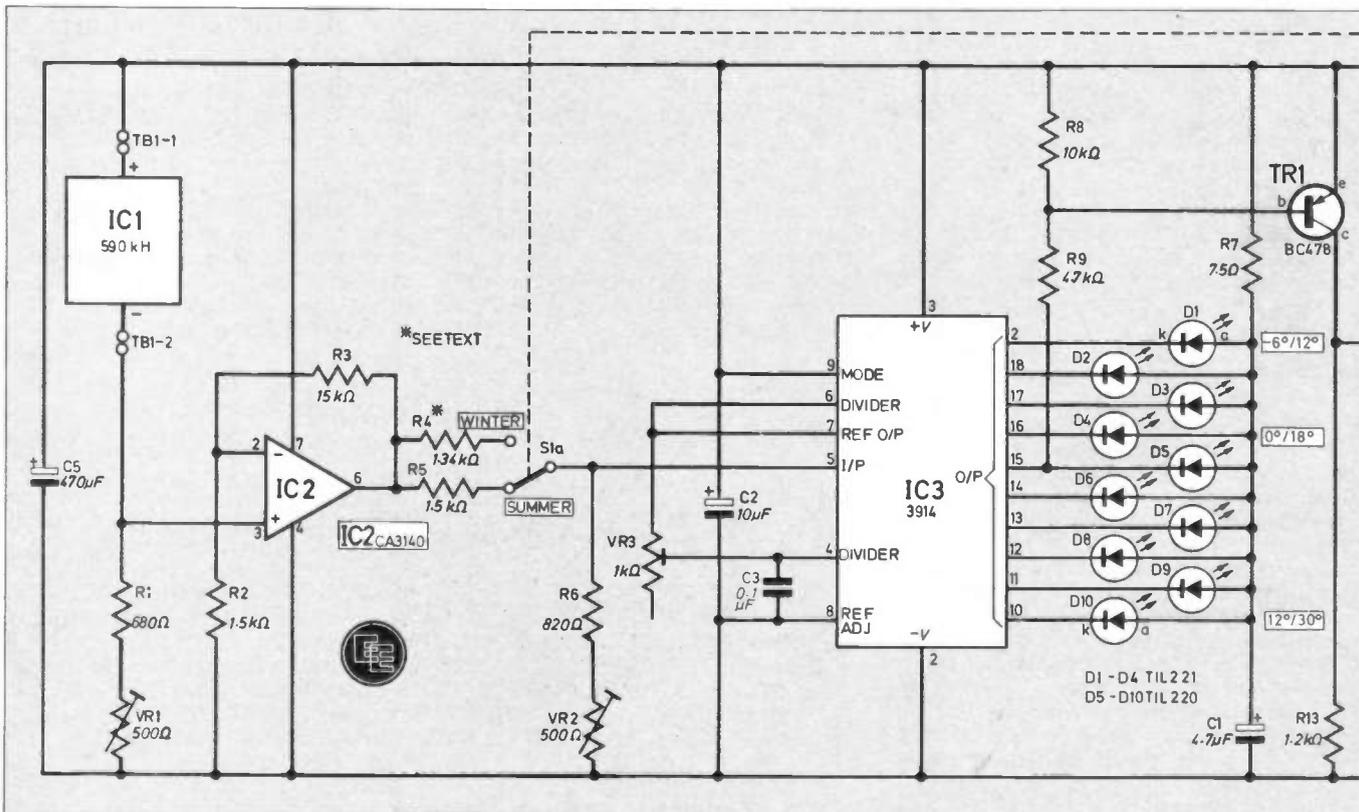


Fig. 1. Complete circuit diagram of the Car Thermometer. Note that the temperature sensor, IC1, is connected to the terminal



# Car Thermometer

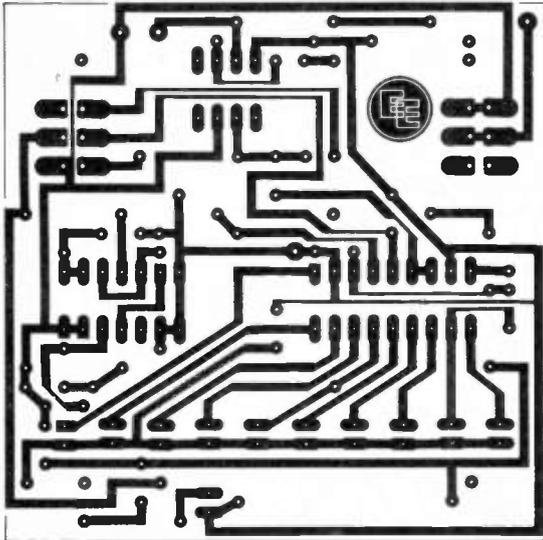


Fig. 2. Full size p.c.b. artwork and component layout. All the l.e.d.s are soldered into the board at the same height of approximately 20mm (to the top of the lens).


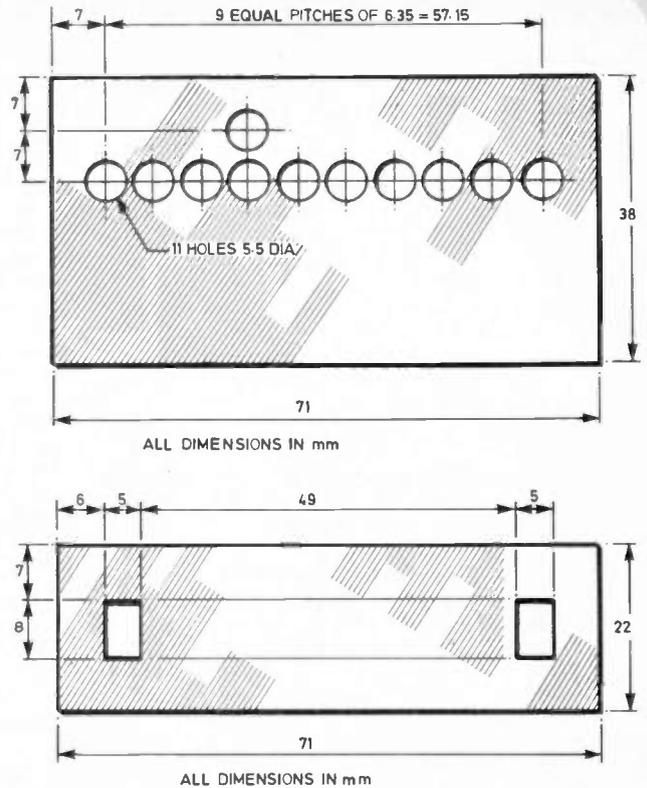


Fig. 3. Drilling details for the display panel and switch label. Both are specifically designed for the Lascar hand-held case.

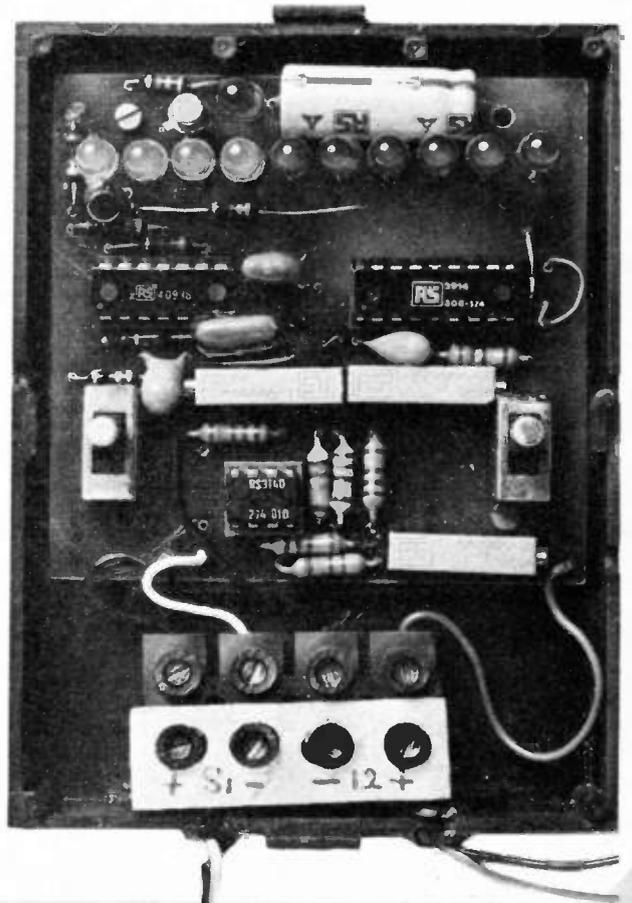

# CONSTRUCTION starts here

## CIRCUIT BOARD

The p.c.b. layout shown in Fig. 2 makes circuit assembly of the thermometer straightforward. This board is designed to fit inside the lower half of the hand-held case. The l.e.d.s are soldered direct to the p.c.b., the height being chosen so that they just pass through holes drilled into the display plate when the unit is assembled.

The ice warning l.e.d. is mounted by the side of the 0°C l.e.d. The first four l.e.d.s which indicate below freezing on the WINTER scale are green and the rest red.

All the components except the temperature sensor are mounted on the p.c.b. There are a few problems which might arise in using the 3914 and these were anticipated in the component layout. One problem is that the l.e.d. currents sum at the 0V terminal (pin 2) of this i.c. and any resistance between pin 2 and the battery terminal will cause voltage drops which can make the 3914 oscillate.

Oscillation in the 3914 is usually manifested by a slow turning on and off of the display. Thus the battery negative lead is taken direct to pin 2 and C4 decouples the power supply close to the 3914. Similarly, C1 between the l.e.d. anode common and pin 2 has a decoupling role and reduces the possibility of oscillation due to any resistance between pin 3 and anode common.

Resistor R4 has a calculated value of 1.34 kilohms, and is made up from two resistors connected in series, nominal values of 510 ohms and 820 ohms. The precise value of this resistor is determined by the value of the internal reference voltage of the 3914 and corresponds to the internal reference voltage of 1.26V. The resistors were selected using a digital ohmmeter.

Constructors are advised to select a value close to 1.34 kilohms assuming

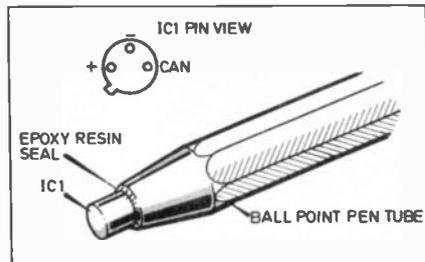


Fig. 4. Method of mounting the temperature sensor, IC1, in a plastic ball point pen tube.

their 3914 has the same internal reference voltage. Should, in subsequent use after calibration, the scale be inaccurate, a change to one of the two resistors making up R4 can be made.

The four external connections to the unit (to power supply and sensor) are made via a four-way terminal block, TB1. It is important to check that correct polarities are observed to the sensor. A pair of leads two or three metres long, if necessary, can be used to connect the sensor to the terminal block and care should be taken to ensure that the soldered joints close to the sensor are insulated from each other, and from any exposure to external water.

The sensor should be glued with epoxy resin into the end of a plastic ball point pen tube for protection as shown in Fig 4. Note that pin 3 (case) of IC1 is not used and should be cut off close to the case.

## CALIBRATION

This exercise necessitates the adjustment of VR1, VR2 and VR3 with a possible change to the value of R4 or R5. However, the procedure is quite straightforward and you only need some glasses of water at 12°C and 30°C, measured using an accurate thermometer, and some melting ice in another glass.

Connect the unit to a 9V, PP7 battery or to a 12V d.c. power supply and put the sensor in the water at 12°C, using the thermometer to keep the water well stirred. Switch on the unit and select the SUMMER range. Use a digital voltmeter (if available) to measure the voltage at pin 6 of IC2 and adjust VR1 until a reading of 285mV is obtained. This reading corresponds to an absolute temperature of 285K (12°C). Move the sensor to water at 30°C and you should find that the voltmeter now reads 303mV. VR1 should not now be touched again.

Note that the sensor, amplifier and digital voltmeter constitute a digital thermometer whose scale is linear and reads in degrees absolute (Kelvin).

Adjust VR2 until all the l.e.d.s are on making sure that D10 just comes on. Put the sensor in water at 12°C again, and adjust VR3 so that D1 just comes on. Move the sensor back to water at 30°C and once again check that D10 is just on. No further adjustment to VR2 and VR3 should be necessary. They have set the scale of the thermometer to a 18°C span.

Switch S1 to WINTER and put the sensor in melting ice at 0°C. The first four (green) l.e.d.s should be on, and the ice alarm D11 should begin to flash on and off. Remove the sensor from the melting ice and allow it to warm up. As it does so D5 will light and the alarm will go off.

Place the sensor in the water at 12°C and the last l.e.d. in the scale will just come on. If it does not, a change to one of the resistors R4 or R5 is necessary. Select another resistor to correct the error using the fact that reducing the value of R4 (or R5) causes the scale to over-read and increasing the value causes the scale to under-read.

## COMPONENTS

### Resistors

R1	680Ω ±2%
R2,5	1.5kΩ ±2% (2 off)
R3	15kΩ ±2%
R4	1.34kΩ (see text)
R6	820Ω ±2%
R7	7.5Ω
R8,10	10kΩ (2 off)
R9	4.7kΩ
R11	470Ω
R12	100kΩ
R13	1.2kΩ

All ±2% resistors are metal oxide, all other types are ±5% carbon

See  
**Shop  
Talk**  
page 145

### Capacitors

C1	4.7μF 25V tantalum bead
C2,4	10μF 25V tantalum bead (2 off)
C3	0.1μF polyester
C5	470μF 25V elect.

### Semiconductors

D1-4	T1L221 0.2in. green l.e.d. (4 off)
D5-11	T1L220 0.2in. red l.e.d. (7 off)
TR1,2	BC478 silicon <i>npn</i> (2 off)
IC1	590kH temperature sensor TO-5 package
IC2	CA3140 CMOS op-amp
IC3	3914 linear bargraph display driver
IC4	4093 CMOS quad 2-input NAND Schmitt trigger

### Miscellaneous

S1,2	d.p.d.t. sub-miniature slide switch with chrome tang (2 off)
VR1,2	500Ω multiturn preset (2 off)
VR3	1kΩ multiturn preset
TB1	4-way terminal block

Hand-held instrument case; single sided p.c.b. 70 x 70mm; 18-pin d.i.l. holder; 14-pin d.i.l. holder; 8-pin d.i.l. holder; 7/0.2mm wire; used ball point pen tube; epoxy resin adhesive.

Approx. cost

Guidance only


**£16**

## INSTALLATION

The thermometer is now ready to use in the car. Connect the unit to the car battery via the ignition switch, carefully observing to polarity, and mount the unit in a position not illuminated by direct sunlight otherwise the scale will be difficult to read.

The sensor should be located away from engine or exhaust heat but able to sense the ambient air temperature without being directly exposed to the airstream; or to rain and road spray. A good position for the sensor is behind the front bumper guard but fit the sensor inside a short length of tube open at one end and mounted with its open end pointing earthwards. □

## IMPROVED VERSION OF AN OLD GAME

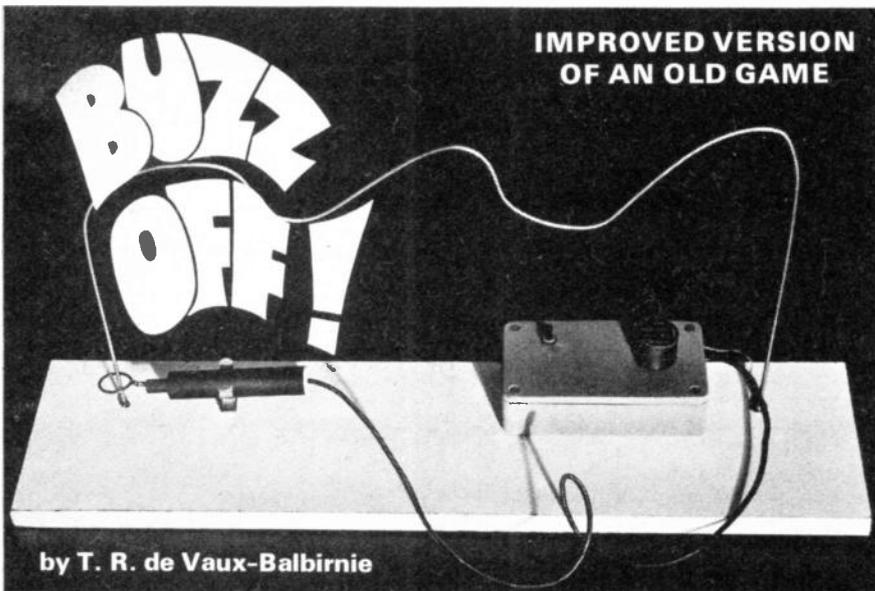

by T. R. de Vaux-Balbirnie

At village fêtes up and down the country you will see this time-honoured game. No-one seems to know what it is really called but the idea is simple enough. If you can guide the hand-held loop around a bent wire obstacle course without touching it, you win. If you touch the wire with the loop a bell rings and you lose!

### ORIGINAL SYSTEM

The circuit normally used is extremely simple—just a battery and bell connected in series, Fig. 1. The bent wire and hand-held loop form a “switch” so that the circuit is completed when the two touch.

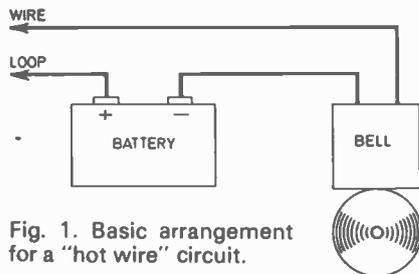


Fig. 1. Basic arrangement for a “hot wire” circuit.

Although satisfactory, this system suffers from two defects. Firstly, if the player touches the wire *momentarily* then the bell might fail to ring due to its rather slow response time. Secondly, since the current required to operate the bell flows through the wire and loop, poor contact between the two will prevent the circuit from working. It is therefore necessary to keep the wire and loop very clean to avoid erratic operation.

### RAPID RESPONSE

The author examined the basic circuit and improved it while still preserving the traditional form of the game.

The first improvement was to ensure that the device would sound for a definite time even after *momentary* contact between wire and loop. This avoids disputes

as to whether the player actually touched the wire or not. The second improvement makes sure that the circuit works reliably even where very poor contact exists.

In the prototype, the bell was replaced by an audible warning device. This consumes less current than a bell, is cheaper, more reliable and gives a louder sound. Experiments with the prototype were unsuccessful when an ordinary bell or buzzer was used.

### CIRCUIT DESCRIPTION

The circuit diagram for the Buzz Off! is shown in Fig. 2.

The main part of the circuit consists of the ever popular 555 timer i.c. This is connected as a monostable—that means it remains off until triggered whereupon it switches on for a predetermined time then reverts to its original state. The *trigger* referred to is provided by contact between the wire and hand-held loop.

The time during which the circuit is on depends on the values of R1 and C1. Using the component values suggested this time will be about half a second and

this was thought appropriate. For a longer time, R1 could be increased and for a shorter time reduced.

The output of the i.c. is obtained at pin 3 and is connected to the base of TR1 which does the actual job of operating the audible warning device. VR1 matches the output from the i.c. to the transistor.

For the prototype, three type 1289 4.5V batteries were connected in series, Fig. 3, and these gave excellent results. The suggested audio-warning device does not perform well on less than a 12-volt supply although a 9V battery will do for testing. The current requirement is about 10mA on standby and 100mA whilst actually sounding.

## COMPONENTS

### Resistors

R1 5.6M $\Omega$   
R2 47k $\Omega$   
R3 220 $\Omega$   
All  $\frac{1}{2}$ W carbon  $\pm 5\%$

See  
**Shop  
Talk**  
page 145

### Capacitors

C1 0.01 $\mu$ F polyester  
C2 0.1 $\mu$ F polyester

### Semiconductors


TR1 BFY51 *n*p*n* silicon  
IC1 NE555 timer

### Miscellaneous

VR1 1k $\Omega$  miniature horizontal preset  
S1 s.p.s.t. miniature toggle  
WD1 12V buzzer (see text)  
B1 13 $\frac{1}{2}$ V (see text)  
0.1 inch matrix stripboard 9 strips by 22 holes; plastics case 115 x 95 x 37mm (ABS box MB3); 8-pin d.i.l. i.c. socket; chipboard: 460 x 110 x 15mm; 100mm tinned copper wire 16 s.w.g.; 800mm flexible wire; connecting wire; wire coat hanger.

Approx. cost  
Guidance only **£7**

Fig. 2. Complete circuit diagram for the Buzz Off!

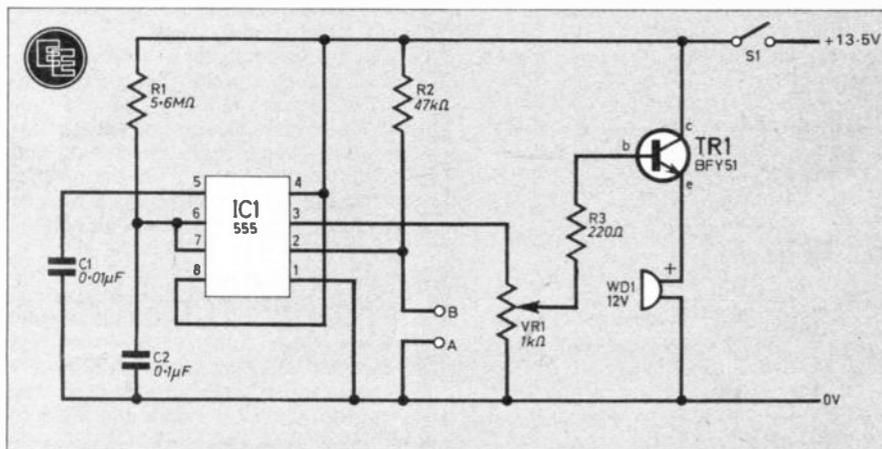

# CONSTRUCTION starts here

## CIRCUIT BOARD

The circuit is built on a small piece of 0.1 inch matrix stripboard 9 strips by 22 holes in size. Use an 8-pin i.c. socket and do not insert the i.c. until all assembly work is completed. Cut the copper tracks in the places indicated on the underside diagram, Fig. 4, especially not forgetting the row between the pins of the i.c. socket.

Although any small plastics box may be used to house the project, the suggested one has convenient slots for easy mounting of the circuit panel.

## POWER SUPPLY

The audio-warning device may be placed inside the box with only the top part protruding through a hole cut in the lid. If this is made a tight fit then no further support will be needed. Holes need to be drilled in the case for S1, external battery leads, and for connections to the loop and wire. If the box is large enough, the batteries may be placed inside, but a better plan is to use external batteries especially where heavy use is anticipated.

## WARNING DEVICE

The alternative audible warning device will operate from a 9-volt supply. It may be mounted on top of the case using small nuts and bolts. Although much smaller it is also quieter in operation so, for loudest results, the recommended audio-warning device should be used. Whichever device is chosen, it is essential to observe the polarity. The recommended audio-warning device has spade type connectors marked "+" and "-". The alternative has flying leads—red for positive and black for negative. Soldered connections may be made to spade connectors so long as they are made quickly. On the other hand, the proper connectors are cheap and may be obtained from a motor accessory shop.

The switch S1 is mounted in the hole in the lid and wired into the positive battery lead. Some connections need to be made to the copper strip side of the circuit panel. These should be made with great care to avoid short circuits.

## LOOP HANDLE

The hand-held loop consists of a piece of thick (16 s.w.g.) copper wire bent around a wooded dowel and twisted tightly around it using pliers or a vice. The diameter of the loop is left to the constructor since it is this which determines the difficulty of the game.

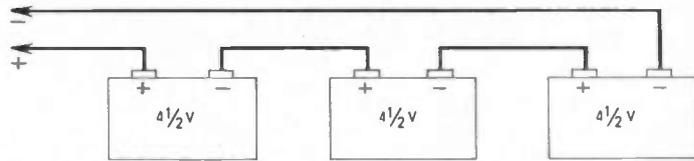


Fig. 3. Connecting three batteries in series to power the Buzz Off! circuit.

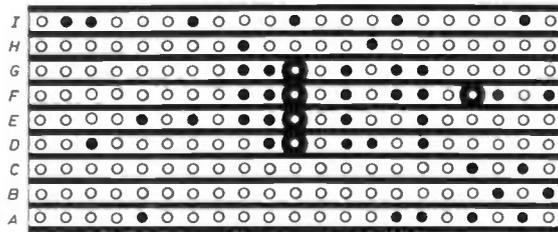
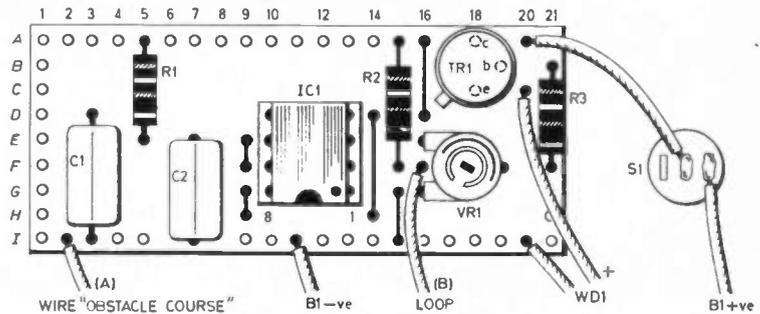


Fig. 4 (Above). Component layout, interwiring details and underside of the stripboard showing breaks (5 off) in the copper strips. Note that there should be 22 holes not 21 as shown.


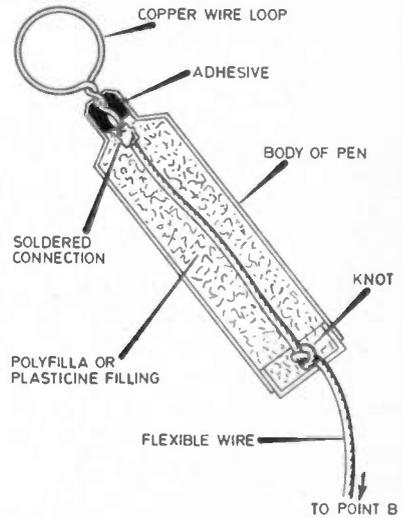


Fig. 5 (Right). Suggested method of construction for the hand-held loop.

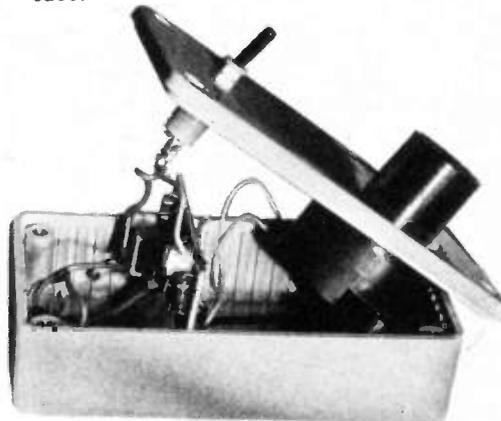Completed prototype of the Buzz Off! The siren protrudes through a cut-out in the case lid. The circuit board slides into slots in the side of the case.



The handle consists of an old felt tip pen. After dismantling this and washing it out, the copper loop has a length of flexible wire soldered to it and adhesive used to secure the parts together, see Fig. 5. The wire is knotted and passed through a hole drilled in the base of the pen body. This knot will protect the soldered connection from the rough service which the loop is likely to receive.

The best wire to use is the "extra flexible" variety. This resists bending very well. If it is not available, ordinary stranded wire will give reasonable service. When the project has been finally tested, the body of the pen may be filled with Plasticine to give a pleasant feel to the handle. The free end of the wire is taken to point B on the circuit panel and soldered into position.

## COAT HANGER

The wire *obstacle course* is made from

an old wire coat hanger mounted on a chipboard base. The baseboard used for the prototype was made from 15mm thick chipboard about 460mm long by 110mm wide. After untwisting the coat hanger and bending the wire into a suitable shape, the hand-held loop is threaded onto it.

The ends of the wire are then secured through holes in the baseboard. If BA taps and dies are available, the ends of the wire may be threaded and secured using two nuts and washers at each end. A solder tag may be used at one end to make the connection to point A. The wire may also be secured in the holes by using epoxy resin adhesive. A soldered or tightly twisted connection may then be used for connection to point A.

If sharp ends of wire protrude through the baseboard, rubber feet may be used to keep it clear of the table. Finally, a spring clip on the baseboard may be used

to keep the hand-held loop tidy while the game is not being used.

## CIRCUIT TEST

Testing may be carried out using a 9V battery. Set VR1 to approximately mid-travel, keep the loop clear of the wire and switch on. The audio-warning device may give a single "bleep" which may be ignored. Now touch the loop against the wire for an instant. There should be a short bleep. Some adjustment to VR1 may be needed for best results. If the circuit tends to trigger falsely—to bleep even when the loop and wire have not touched—then R2 may need to be altered in value.

If the length of the bleep is too short, R1 may be increased in value and vice-versa.


This game is certainly good for fund-raising. You are sure to be in demand when word gets around! □

## HOW TO USE YOUR
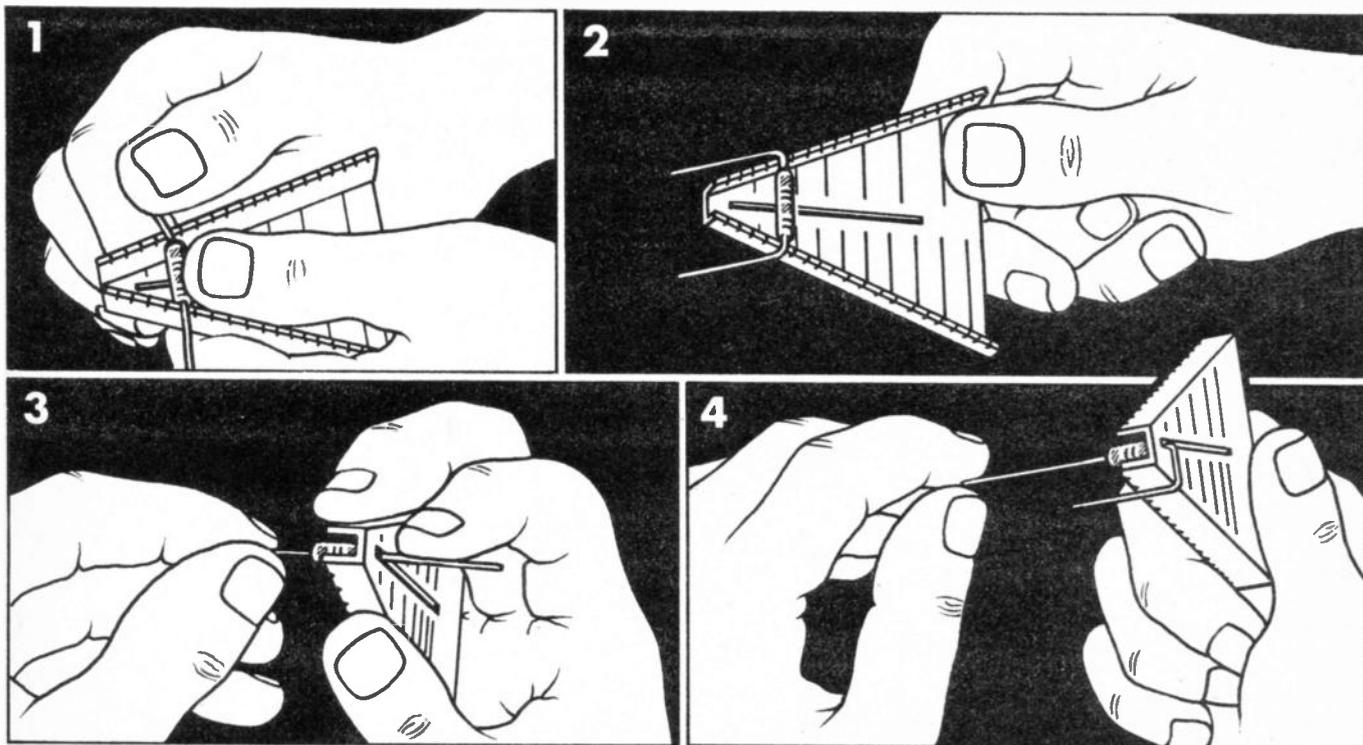
# WIRE BENDING GAUGE

The Wire Bending Gauge given free with this issue is intended to be used for bending the leads on small components such as resistors and axial lead capacitors. It provides a quick, accurate and safe means of bending the leads to span an exact number of holes on perforated circuit boards. There are guides for both horizontal and vertically mounted components on 0.1 and 0.15 inch pitch boards. The numbers represent the number of holes to be spanned, including mounting holes.

**Horizontal mounting.** (1) Place the component in the notches to span the requisite number of holes for the appropriate pitch. Hold component body and bend one lead at a time to make the leads parallel; (2) ready for insertion. **Vertical mounting.** (3) Place component in slot and bend protruding lead through 90 degrees. Slide component along slot to required span guide lines and bend once again through 90 degrees over gauge edge as shown in (4). Move component to tip of gauge to remove.



# APRIL ISSUE

**GO TO WORK  
ON THESE  
GRADE 1  
PROJECTS**


**EGG  
TIMER**


**CAR RADIO  
LS BOOSTER**

**ZX  
SPECTRUM  
AMPLIFIER**

**FUNCTION  
GENERATOR**

**FLANGER  
SOUND  
EFFECT**

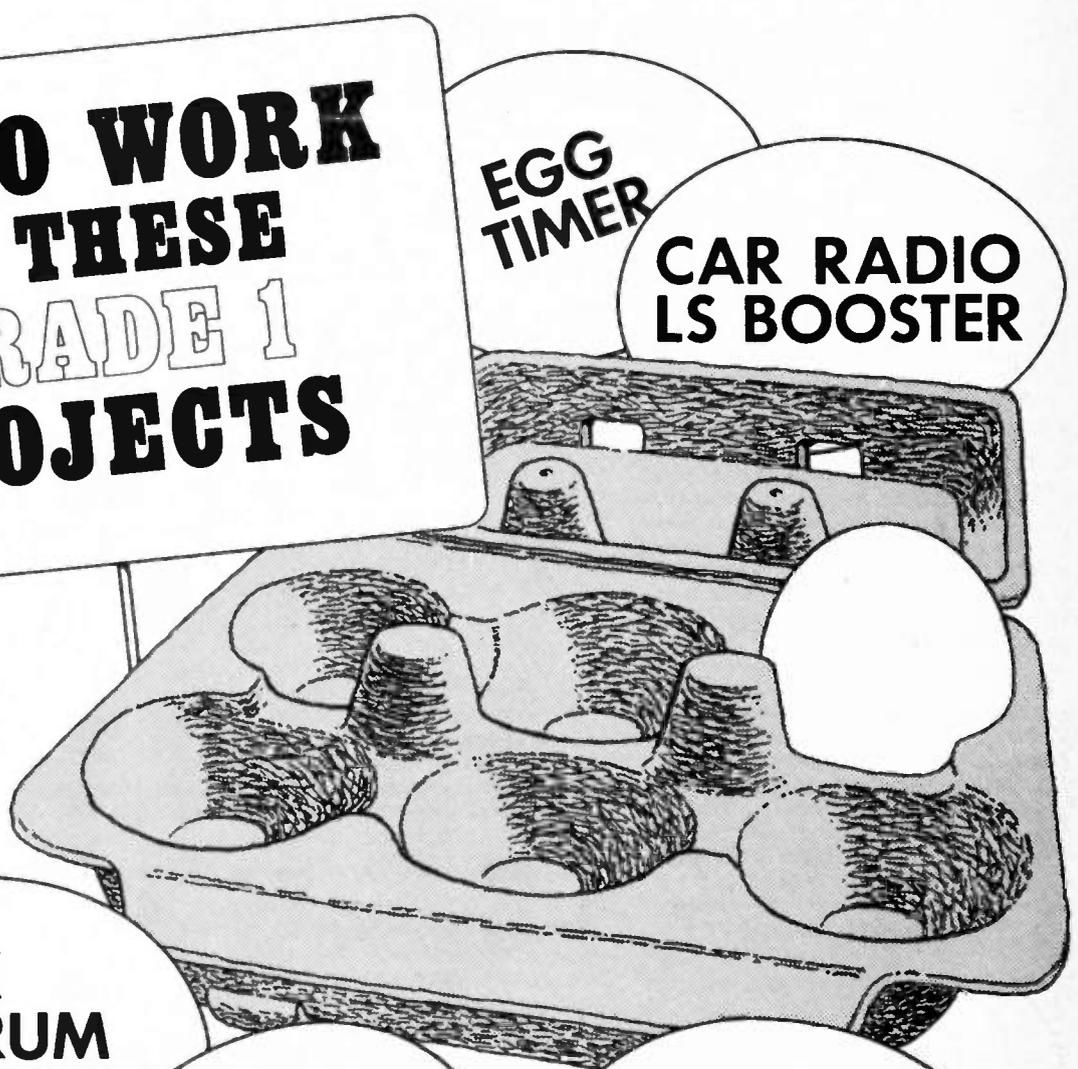

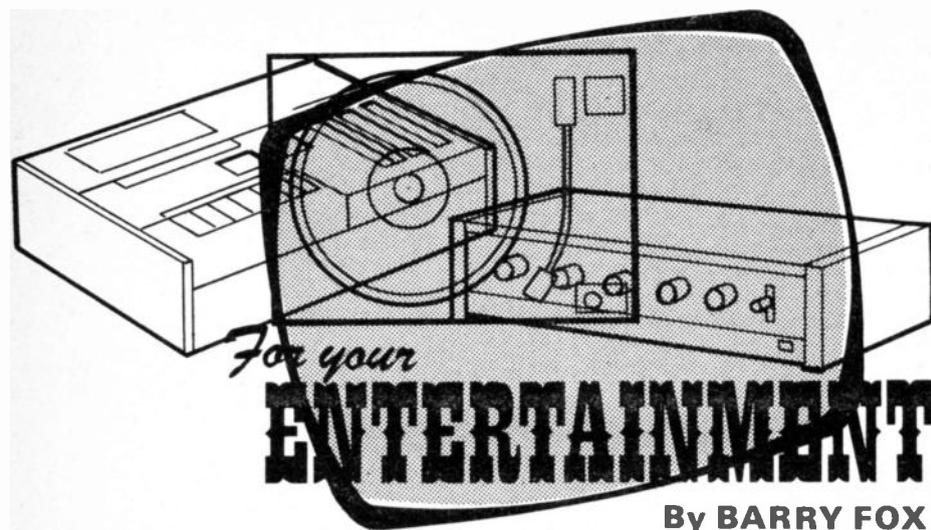

## Why Markets Are Lost

Over the last 15 years I've watched the British consumer electronics industry be decimated by Far Eastern competition. But I'm sorry to say that many firms, now out of business, have reaped no more than they deserved. They didn't plan ahead, they didn't keep in touch with what their customers wanted and they didn't keep up to date with technology, production efficiency and quality control. So they went out of business when better, cheaper and more reliable products from Japan started to flood in. Now exactly the same thing is beginning to happen to the motor industry.

Recently, partly out of national loyalty, I bought British when I needed a new car. I chose an MG Metro because I admired some of its elegant design features. Like, for instance, the way the driver's switch panel has a blanked off socket into which the owner can push-fit Leyland switches to add optional extras, such as front fog lamps. As the switch pushes home it mates with contacts on the edge of a printed circuit board which is connected to the main wiring loom. As the Leyland circuit diagram for the car shows, it is then only necessary to connect a relay and fog lights at the free end of the wire, near the front radiator.

## The Missing Wire

Thinking to myself, at last we're learning from the Japanese, I bought and fitted the necessary switch, relay and fog lights. But then I found that, although the switch mated with the p.c.b., the fog lamp wire shown on the circuit diagram wasn't anywhere to be seen. The dealer who had sold me the car was puzzled and suggested I contact the service division of British Leyland. Two months later I had still not solved the problem but I'd learned an awful lot about the problems Leyland must face in the future. What I found out could also, incidentally, be very useful for anyone else who has recently bought a Metro car, and for dealers who are selling them.

The Supercover guarantee department of British Leyland referred my query to the

BL Customer Service Department. Unfortunately they couldn't read a circuit diagram, and told me that the wire was missing because it was shown in the circuit diagram only as a dotted line, meaning that it was optional. In fact, it's clearly shown in Leyland's own circuit as a hard wire. I persisted and my query was then passed to another customer relations person at British Leyland. He ducked the issue altogether. "Your best course of action will be to consult your local dealer". So I wrote back again explaining that it was only because the dealer was puzzled that I had written to British Leyland for advice in the first place.

## Do It Yourself

I heard nothing, so phoned British Leyland Customer Relations to try and sort things out once and for all. At first they tried to tell me that the wire was there but I couldn't see it. Then they finally owned up.

## Buying A Home Computer

The national press carried a report of boom sales in home computers in the last Christmas shopping rush. This is doubtless because home computers are now cheaper than a computer controlled home TV game.

Despite all the fancy talk about home computers making domestic life and business more efficient, there's no doubt that most people who buy them end up using them mainly to play games. A friend in America recently told me that although many businessmen now feel obliged to buy and install a computer system in their office, to look "on the ball", most of them only use their impressive installations to play exotic TV games.

I also heard recently of problems some users are having with their home computer disc drives. It's easy to forget that although the microprocessor inside a computer is a wonder of modern technology, and can in

The wire which makes it easy for Metro owners to fit their own fog lights has been omitted from the wiring loom to save money. Dealers hadn't been told and the circuit diagram hadn't been changed. "It is necessary to supply and fit the necessary wiring yourself," wrote Leyland, enclosing a scrappy Xeroxed sheet showing where the missing wire should be fitted to the p.c.b.

My mind boggling, I asked the British Leyland Press Office how much money the company was saving by omitting one metre of low current wire at the production stage, and leaving the customer to rebuild it into the car after purchase. The press officer came back to me (or more accurately waited until I got impatient and phoned her), to tell me that she had been assured by BL's electrical engineers and product planners that the wire wasn't missing after all!

After yet more phone calls and letters I finally got something approaching the full story. The wire in question was in all the original Metro range, but is now being omitted. With curious logic it's been omitted first from the most expensive cars, the MG Metro and the Van den Plas. No-one could say for sure who had made the decision.

## Incomprehensible

So, if you want to fit fog lamps to a new Metro car by using the standard switches that interface with the p.c.b., then don't doubt your sanity if you can't find the wire that is shown on the circuit diagram.

Meanwhile, British Leyland is getting £990 million of public money over two years. That's nearly £10 million a week. This money is intended to help the company fight off Japanese competition. When I was in Japan recently, at a trade seminar, I told the story of the missing Metro wire. The Japanese press and businessmen present looked at me as if I was mad. The idea of treating a customer that way is totally alien to Japanese industry. And that's why they are winning the trade war.

theory last forever, the same is certainly not true of disc drives.

These are complicated mechanical beasts, that will eventually go wrong or wear out. In some cases they may only last a few months, and if the drive is built into the main computer housing, then you'll have to return the whole system for repair. The cost of the strip down and replacement of a drive can be well over £100.

Don't rely on the guarantee to help you. Often you'll find it offers only three month's free parts and labour. You may be able to contest this under the British consumer laws, but you could well end up with a fight on your hands.

So, before buying a computer ask yourself three questions. Do I really want one; how easy will it be to repair or replace a disc drive; and am I getting a good guarantee.


# TEST GEAR 83 DUAL POWER SUPPLY

UNIT ONE

BY J. R. W. BARNES
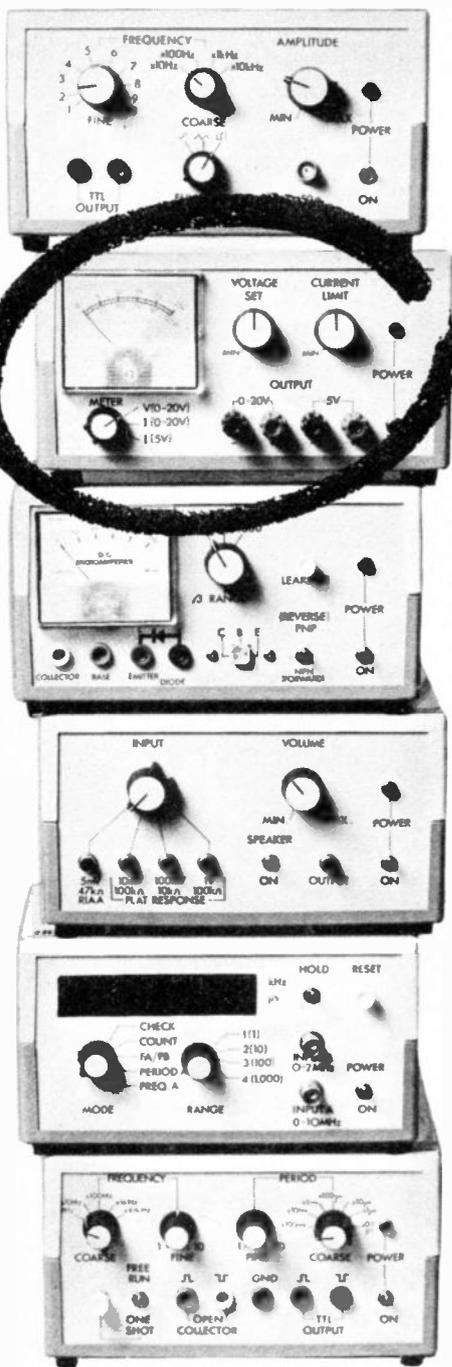
## THE TEST GEAR 83 SERIES CONSISTS OF:

- DUAL POWER SUPPLY ● FUNCTION GENERATOR ● TRANSISTOR TESTER  
 PULSE GENERATOR ● LABORATORY AMPLIFIER ● FREQUENCY METER



IN 1974 EVERYDAY ELECTRONICS published a series of articles, *E.E. Test Gear Five* specially designed for the constructor.

Since 1974 there have been many major advances in the world of electronics and we now introduce a new series of six instruments, under the title *Test Gear 83*.

### TEST GEAR 83

This new generation of test equipment reflects the upward trend in technology. Of the original five, two have been kept, the Power Supply and the Transistor Tester, both being new and considerably updated designs. The A.F. Oscillator has been abandoned in favour of a Function Generator, and the R.F. Generator has gone completely. In addition, there is a Laboratory Amplifier, a Pulse Generator and Digital Frequency Meter.

The reasons for building your own test equipment, however, remain the same. Electronics is a craft, and with widely available integrated circuits, sometimes likened to building blocks, most of the old terrors of electronics have disappeared. The average man (or woman) in the street can be as happily engaged in building and experimenting, as the technically trained expert. It is the nature of electronics that allows useful and satisfying involvement at all levels.

Throughout the design of the Test Gear 83 projects, emphasis has been placed on two main areas; firstly, the price/performance ratio while at the same time designing units that will provide a sufficiently high specification, so they will be of use for many years. The other area of concern is on ease of construction.

All the units will be built on printed

circuit boards, whilst this adds to the construction time it has been the authors experience that constructional errors are less likely to occur, and the project works first time.

### DUAL POWER SUPPLY

A power supply is a key component in any electronic system. Although batteries may be used to supply the finished project they are not flexible enough for development work. Also, with batteries becoming increasingly more expensive the idea of running projects from the mains becomes attractive. This unit has been designed to supply the essential requirements of a home constructor's workshop at a reasonable cost. It provides two stable, well regulated outputs, with low ripple.

The main output provides 0 to 20V and has constant current overload protection which can be set in the range 0 to 1.2A.

The second output provides a fixed 5V output and is primarily intended for experimenting with TTL logic. The maximum current available is fixed at 1A.

A meter is provided for measuring the output voltage, current on the main output and the current drawn from the 5V output. Both supplies are short-circuit protected.


### CIRCUIT DESCRIPTION

The circuit diagram of the unit is shown in Fig. 1. The circuit can be split into sections, the main output and the secondary output. The secondary output will be considered first.

The circuit is very conventional in the fact that all the work is done by the three terminal regulator integrated circuit, IC1.

### SPECIFICATION

Variable output		Fixed output	
Range:	0 to 20V d.c.	Output:	5V d.c.
Max. current:	1.2A	Max. current:	1A
Ripple:	10mV peak-to-peak (supplying 15V at 1A)	Ripple:	8mV (supplying 1A)
Load regulation:	0.08% (measured at 20V between 0 and 1A)	Load regulation:	1.5% (between 0 and 1A)
Line regulation:	0.0065% (input voltage varied between 230V and 250V)	Meter:	General 3 ranges V(0-20V), I(0-20V), I(5V)
		Terminals:	4mm banana sockets

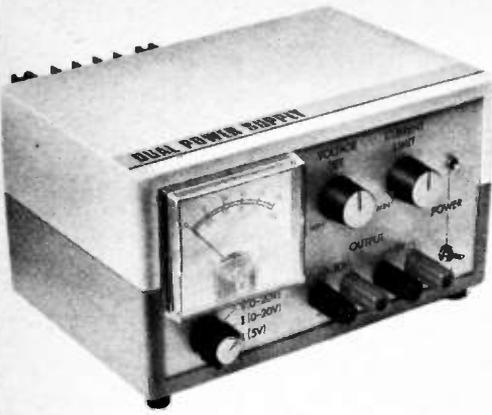

The a.c. input is provided by the transformer and is rectified and smoothed by the bridge rectifier D1-D4, and capacitor C1, respectively. The low value resistor R1 is used to sense the output current for the meter.

With an output current of 1A, half a volt is developed across R1. R2 is chosen to make the meter 0-625V full scale. The

capacitors C2 and C10 are to prevent high frequency oscillations.

The main output is more complex, rather than use another monolithic regulator i.e. the higher stability of a LM723 was sought. The reason for this is because in a simple series regulated supply, a large amount of power is dissipated in the output transistor causing it to run hot. In a monolithic regulator this raises the temperature of the voltage reference and causes it to drift.

### EXTERNAL AMPLIFIER

In a design using a discrete output transistor, the transistor and the reference are in thermal isolation. A very stable reference is provided by IC2. Readers familiar with the LM723 regulator will know of its inability to regulate at low output voltages, that is less than two volts. This limitation arises from the error amplifier, so in this design an external amplifier, so in this design an external amplifier is used, a CA3140, IC3.


This amplifier will work with its input close to 0V. The voltage reference from pin 6, IC2 is fed via the voltage control potentiometer VR1 to the non-inverting input of IC3. A portion of the output voltage is feedback to the inverting input via the potential divider R10, R11. This feedback loop keeps the output voltage constant. The output of IC3 is used to drive the series pass Darlington pair made of transistors TR2 and TR3.

### CURRENT LIMITING

The error amplifier in IC2 and its associated output transistor are used to limit the supply to IC3 to a maximum of 27V. The output current is sensed by resistor R8, when the current flowing through this is 1.2A, 0.625V is developed across it. If this were directly connected to pins 2 and 3 of IC2 this would result in the supply to the op-amp being reduced thus keeping the output current constant.

The current limit circuit is biased by

Fig. 1. Complete circuit diagram for Unit One, the Dual Power Supply. The main output provides 0 to 20V with constant current overload protection within range 0 to 1.2A. The second output provides a fixed 5V 1A supply specifically for experimenting with TTL logic.

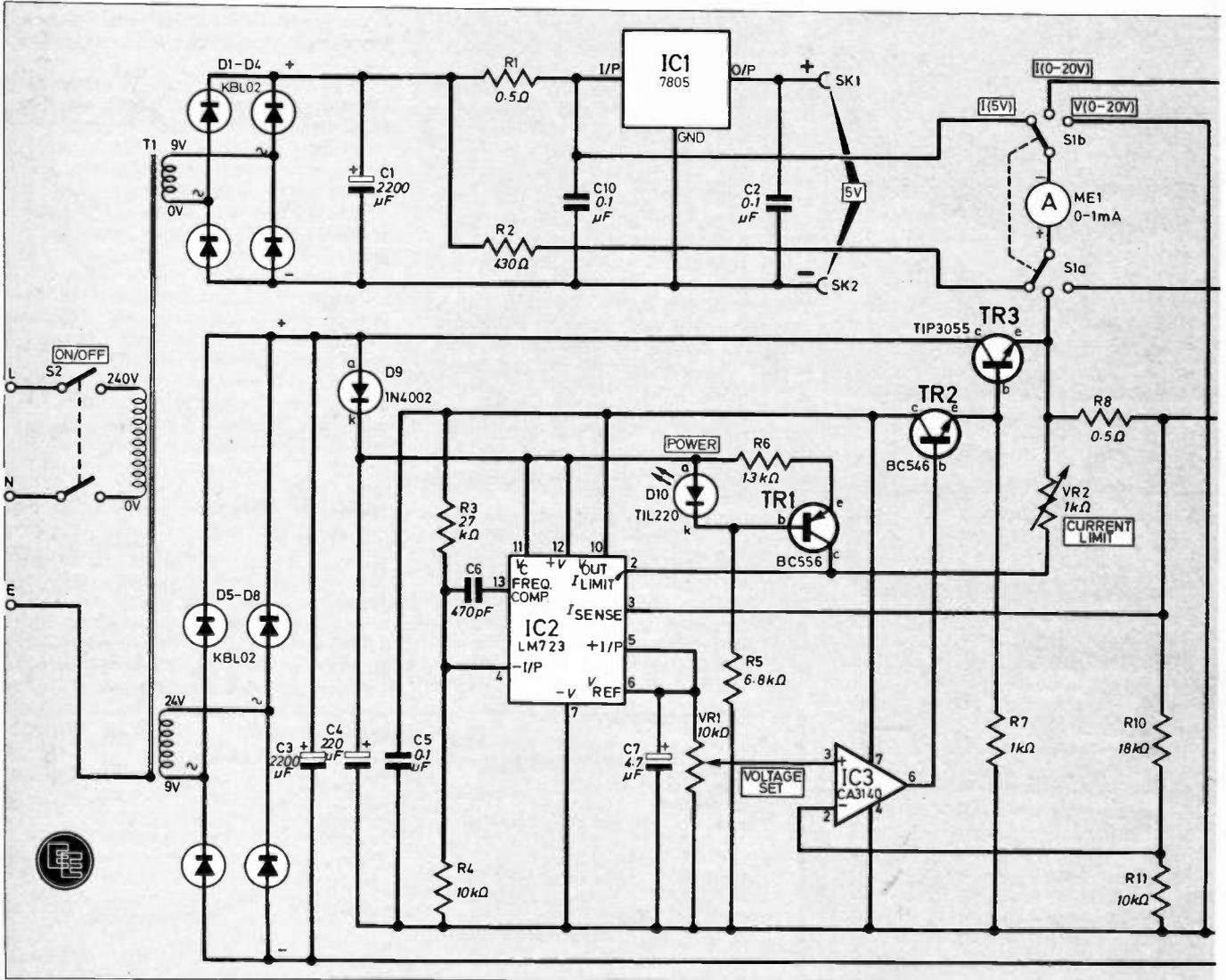

driving a constant current of 0.75mA from the current source TR1 and its associated components, through VR2. The voltage across VR2 is added to that across the sense resistor, increasing the current limits sensitivity.

The sense resistor is also used by the metering circuit to display output current.


The d.c. is provided by the 24V secondary from T1, bridge rectifier D5-D8 and capacitor C3.

# CONSTRUCTION

starts here
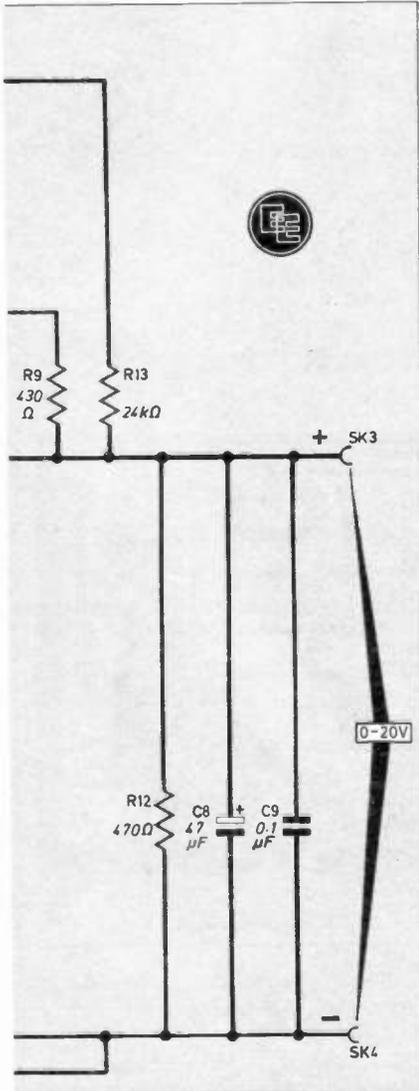
## CIRCUIT BOARDS

The prototype was housed in a Vero case type 202-21036C. This case will be used throughout the *Test Gear 83* series



## COMPONENTS

### Resistors

R1,8	0.5Ω (2 off) 3W wire-wound	R6	1.3kΩ
R2,9	430Ω (2 off)	R7	1kΩ
R3	27kΩ	R10	18kΩ
R4,11	10kΩ (2 off)	R12	470Ω 3W wire-wound
R5	6.8kΩ	R13	24kΩ

All 1/4W carbon ±5% unless otherwise stated

### Capacitors

C1	2200μF 25V elect.
C2,5,10	0.1μF 160V Siemens (3 off)
C3	2200μF 40V elect.
C4	220μF 40V elect.
C6	470pF disc ceramic
C7	4.7μF 10V tantalum bead
C8	47μF 25V elect.
C9	0.1μF ceramic

### Semiconductors

D1-4	KBLO2 200V, 4A bridge rectifier
D5-8	KBLO2 200V, 4A bridge rectifier
D9	1N4002
D10	TIL220 red l.e.d.
TR1	BC556 <i>npn</i> silicon
TR2	BC546 <i>npn</i> silicon
TR3	TIP3055 <i>npn</i> silicon plastic power
IC1	7805 5V, 1A regulator
IC2	LM723 adjustable voltage regulator
IC3	CA3140 MOSFET op-amp

### Miscellaneous

T1	mains transformer with 24V, 1.5A and 9V, 1.5V secondaries
ME1	1mA f.s.d. panel meter with 120Ω coil (type ML52)
S1	2-pole, 6-way midget rotary with adjustable stop
S2	d.p.d.t. miniature mains toggle
VR1	10kΩ control potentiometer
VR2	1kΩ control potentiometer
SK1,3	insulated terminal post red
SK2,4	insulated terminal post black

Vero case type 202-21036C; single-sided p.c.b. size 120 x 85mm and 85 x 75mm; heatsink size 89 x 75 x 51mm rated at 1.5°C/W; control knob (3 off); l.e.d. holder; Veropins; 7/0.2mm wire; 14/0.2mm wire; mains cable; grommet; P-clip; 14-pin d.i.l. holder; 8-pin d.i.l. holder; mounting hardware (M2.5 or 6BA).

See  
**Shop  
Talk**

page 145

**COMPONENTS**  
approximate  
cost **£35**

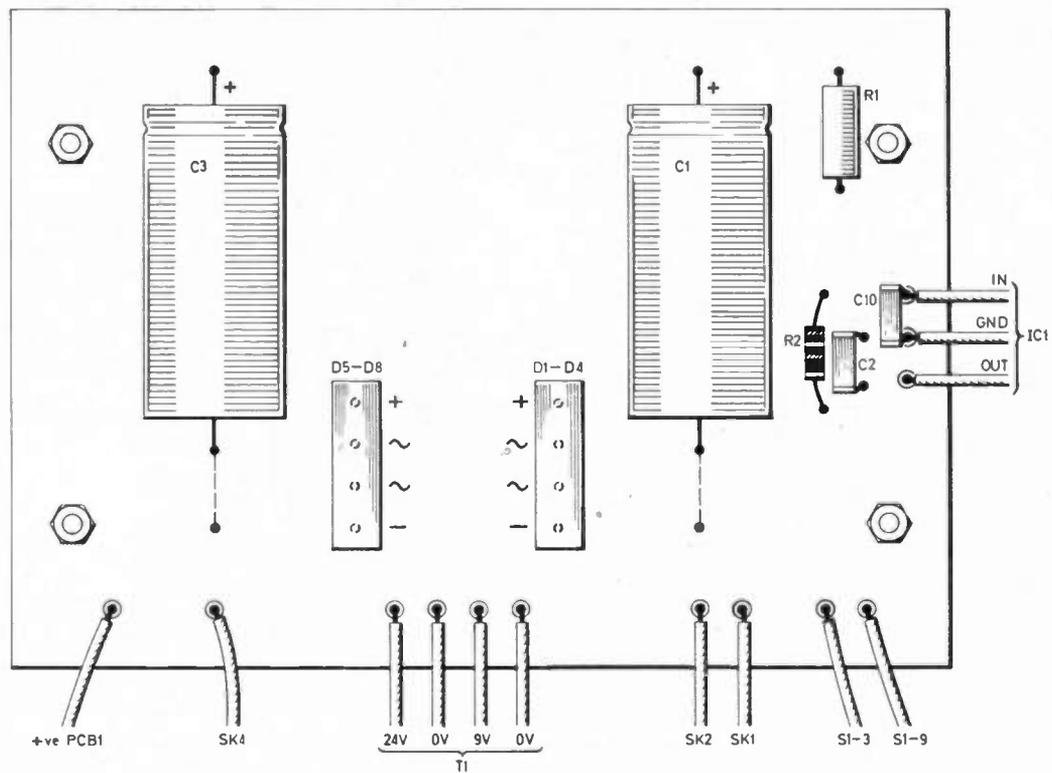


Fig. 2. Component layout and full size printed circuit board master (opposite page) for the 0-20V variable supply.

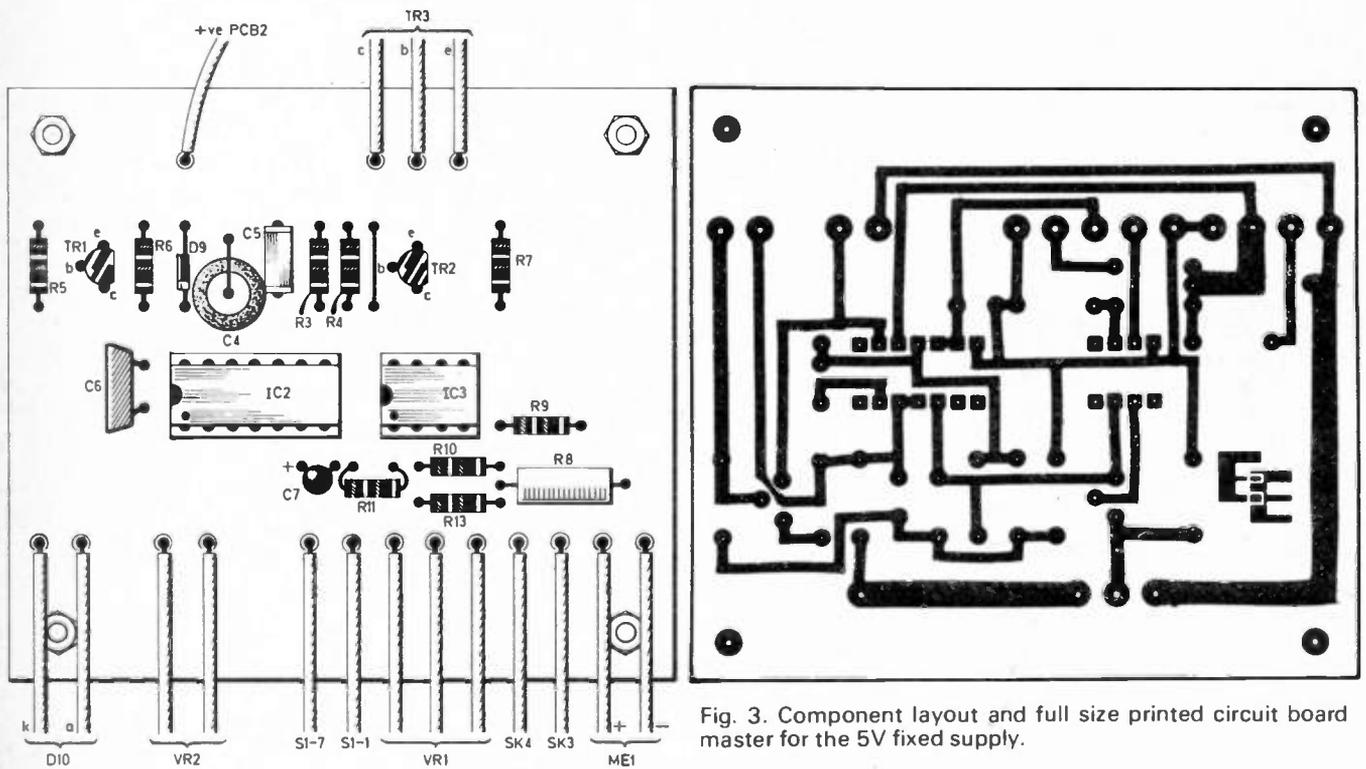


Fig. 3. Component layout and full size printed circuit board master for the 5V fixed supply.

and should be available through the normal Vero distributors.

Begin construction with the circuit boards. If you are making the boards yourself pay special attention to their external dimensions. The prototype boards were laid out with etch resistant dry transfers. The p.c.b. artworks and component layout diagrams are shown in Fig. 2 and Fig. 3.

Solder the components to the board in the normal manner beginning with the passive components and the wire link, working through to the transistors and the diode. It will be found helpful if Veropins are inserted in the board where the flying leads leave it. Note that additional holes have been provided to allow for different sizes of capacitors, particularly C1 and C3 the smoothing capacitors.

## CASE

Once the circuit boards are complete, the case can be prepared. Remove the four screws at the corners of the base, allowing the two halves to be separated. Remove the front and rear panels. To assist in marking out and to protect the panels from scratches it is advisable to fasten a piece of graph paper with double-sided tape. Mark the centre of the holes according to the dimensions given in Fig. 4 and then lightly centre-punch them. Without removing the protective paper, drill the holes. For the large holes it is better to drill a small hole (about 3mm) first and then drill the hole to the right size.

The large circular hole for the meter can be made two ways: either drill a series of small holes round the circumference and punch out the middle, then finish with a file; or use an Abra file in a hacksaw frame.

## REAR PANEL

The rear panel holds the heatsink. The heatsink used on the prototype is available from Ambit International, Part 21-08030.

A 30mm diameter hole was cut to be the centre of the heatsink in the rear panel to allow the transistor TR3 to be mounted, see Fig. 5. Note that no insulating kit is used on this transistor so the rear panel and the heatsink are connected to the collector of the transistor and should not be earthed. The 5V regulator is mounted with a mica washer and an insulating bush. To aid heat transfer, a thin smear of heatsink compound should be applied to both sides of the washer and the power transistor.

Solder three wires to the leads of TR3, before mounting the rear p.c.b. on stand-offs over the transistor. The rear panel assembly can now be replaced in the lower half of the case.

Screw all the front panel components in place having first cut to size the spindles on the potentiometers and the switch. At this stage it is best to attach wires to the panel mounting components, paying

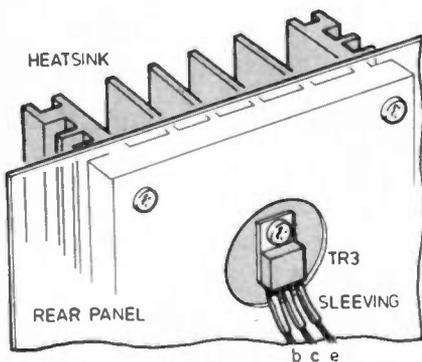
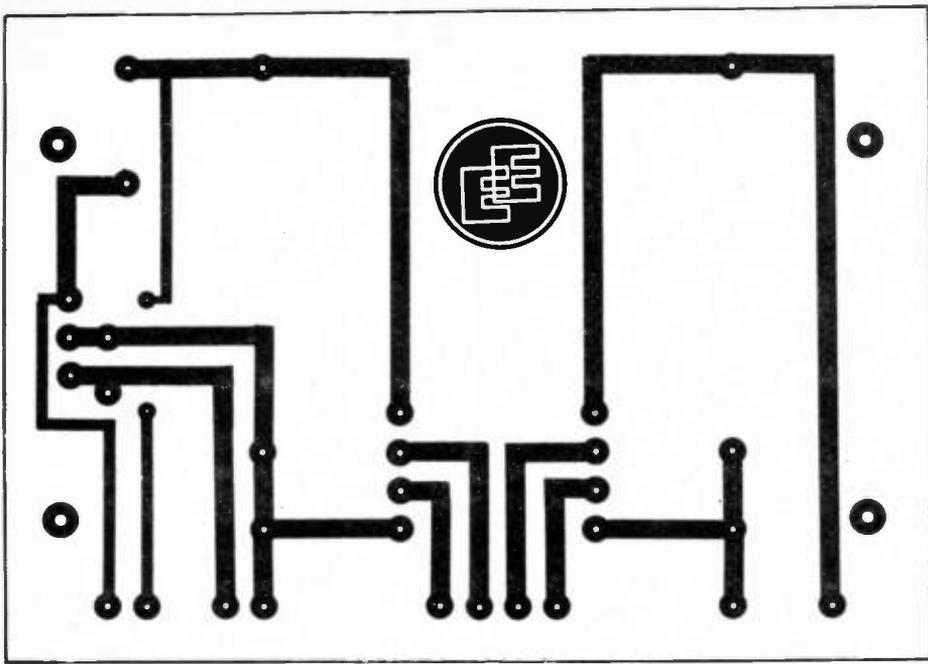


Fig. 5 (Left). Mounting details for transistor TR3. Note that no insulating kit is used on this transistor so the rear panel and the heatsink are connected to the collector and should not be "earthed".

Fig. 4 (Below). Drilling details for the front aluminium panel.



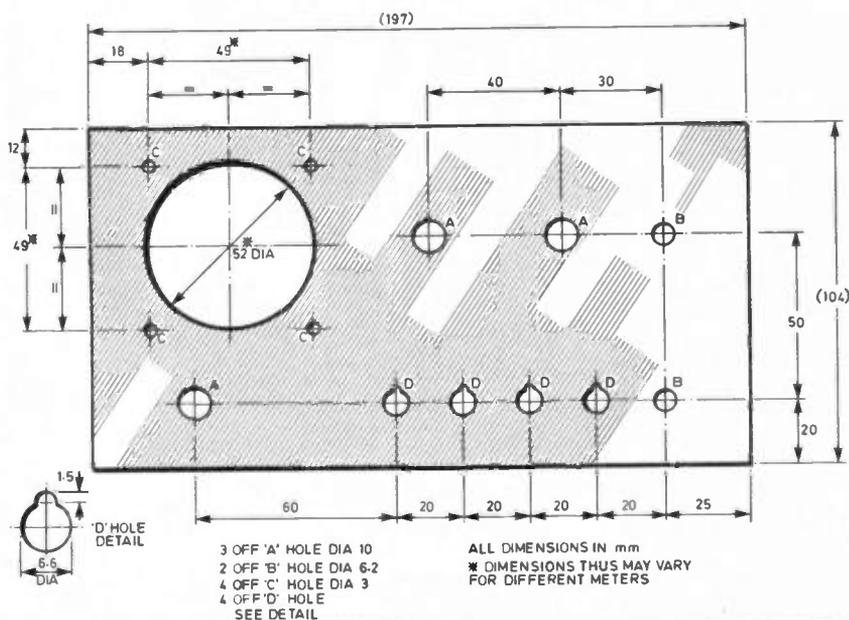


Fig. 6. Interwiring details for the front, base and rear panels.

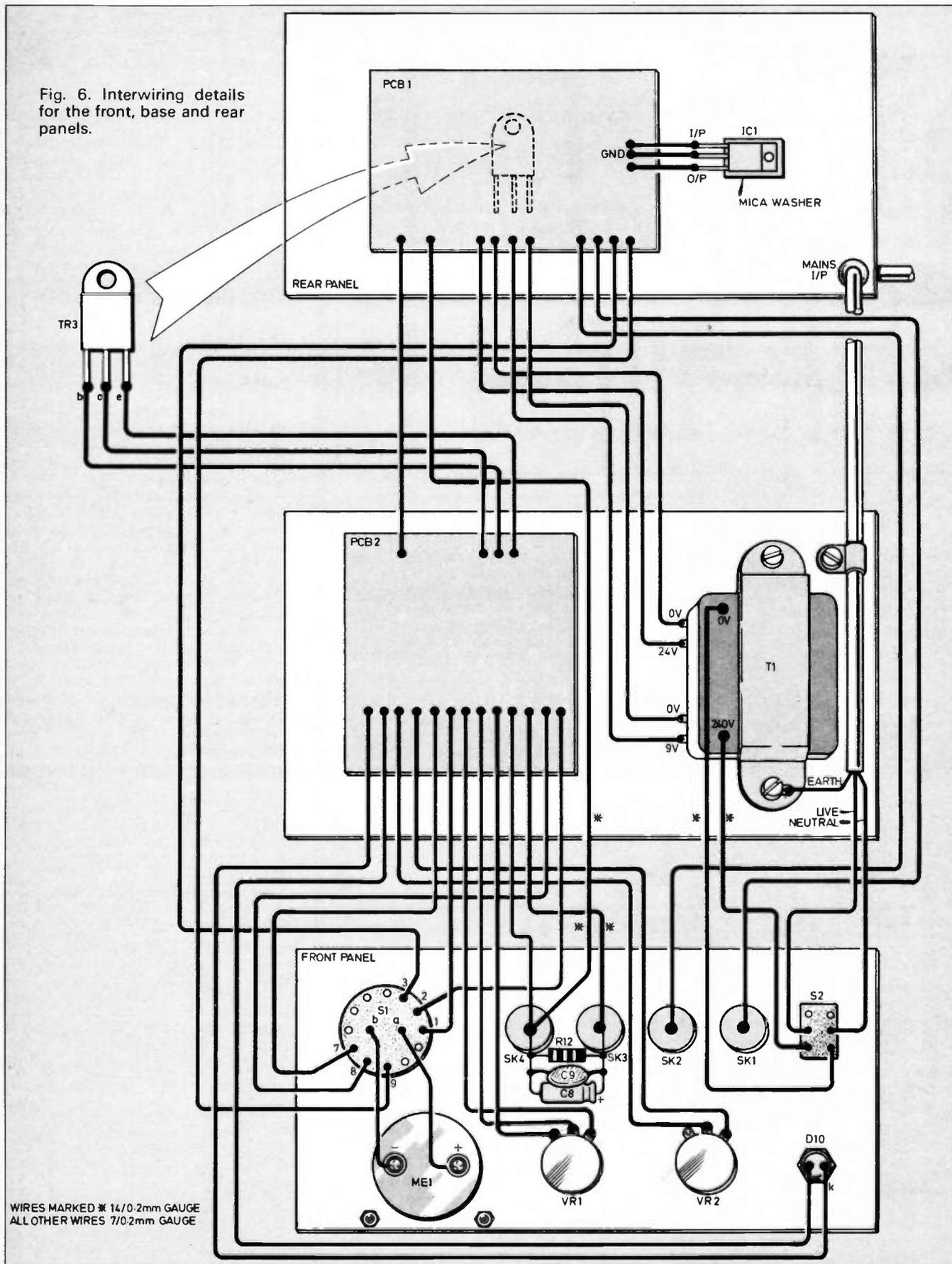

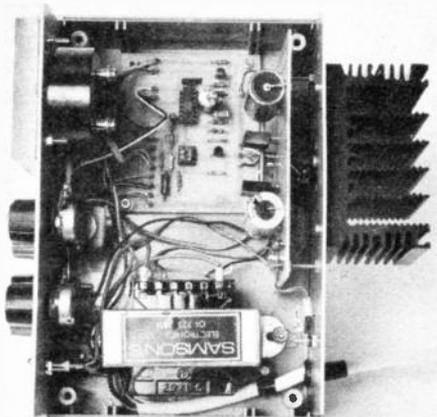WIRES MARKED \* 14/0.2mm GAUGE  
ALL OTHER WIRES 7/0.2mm GAUGE





Front panel layout and lettering.

(Left). Positioning of mains transformer, and circuit boards within the case. The boards are held "proud" by their mounting nuts and bolts.

(Bottom left). Circuit board and TR3 on the rear panel.

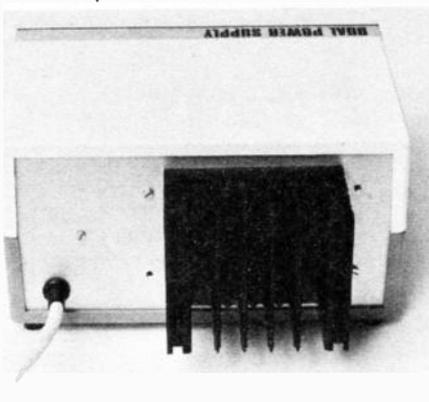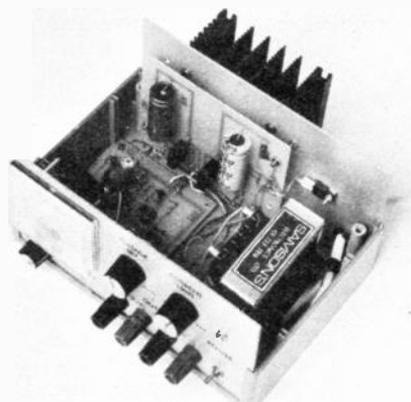The heatsink mounted on the exterior of the rear panel.



attention to the two thick wires, see Fig. 6. These wires must be thick or poor regulation will result. Once this has been done the panel can be slid into its mounting slots and the other ends of the wires be soldered.

## IN USE

The power supply can be used to replace the power supply of a circuit under test. Turn the METER switch to voltage V (0-20V) and with no load connected and the current control turned up set the required voltage. Switch to the current setting I (0-20V) and turn the current control to zero. The load can now be connected and the CURRENT LIMIT control can now be increased. When the current stops rising the power supply is then operating in the constant voltage mode.

Should the load try and draw more current than the threshold, the supply will limit the current by reducing the voltage, that is, go into the constant current mode. The supply may be used in the constant current mode for recharging Ni-Cad batteries, take care though, not to exceed the manufacturers rated current.

When the supply is delivering a small output, a large voltage is developed across the series transistor and it will dissipate a lot of power. To avoid overheating the supply should not be operated in this condition for excessive lengths of time. The prototype was short circuited for a quarter of an hour with no ill-effects, although this is not recommended! □

# COUNTER INTELLIGENCE

By PAUL YOUNG

## Computer Holiday

Earlier this year I found myself, probably like the rest of you, bombarded with alluring holiday literature. There was no escaping it, the newspapers, the radio, the television, all combined to part you from your money in exchange for a fortnight's sunshine.

Unable to withstand the pressure I went to see my bank manager and tried to lull him into a sense of false security with talks of luxury cruises. "Yes, Young, I agree with you in principal, but I think I would be a lot happier if you went for a row round the Serpentine, it would be more in keeping with your present financial status."

Encouraged by his friendly remarks I had another look at the brochures and the following caught my eye. It was a picture of a young man and a young woman sunbathing, and the caption below said, "Don't just lie there, do something". It was an advertisement for a holiday on the shores of the Mediterranean, and thrown in at no extra cost was a course on computer programming. The idea being that when you were bored stiff with doing nothing you

could learn something useful. Alas, the nearest I shall get to it is lying under my Solarium with my minicomputer, and trying to persuade my friends I have been away on one of these specials.

## Paranormal

I think most readers will know I have a slight interest in the paranormal. I don't dabble in it but when a story comes along that has a slight electronic flavour about it, I unhesitatingly pass it on to my readers. Such an opportunity occurred recently and I seized it with both hands.

A short time ago I watched a programme on television. It concerned an old Inn situated in Wales. It had been there since before the Norman Conquest. Many people who had lived there testified that it was haunted, voices and footsteps, and even an organ had been heard playing.

An electronics expert became interested and examined the building, particularly the stone it was made of. It was a coarse local stone, but it had thin streaks running through it which he decided were metal or silicon.

Would it be possible, he thought, for these stones to act as a tape-recorder, and would it be possible to drive out the sound by applying a high voltage to the wall? With the permission of the Inn keeper, he and a friend drove long nails into the wall and arranged a time switch to apply a high voltage at 2.30am. A tape-recorder was left running to record the results.

At this point in the programme the commentator said, "I will now play you the tape". For the next few seconds there was silence and then a babel of strange voices and an organ playing weird music. It was really eerie and quite uncanny to listen to.

I thought I would try this experiment myself. I was just about to drive a six-inch nail into the wall when my better half said, "I shouldn't do that if I were you". I expostulated that I was interested in science and wanted to hear these strange voices and language. My spouse came back, "If you knock that nail in you will hear some unusual language without any voltage being applied."

Oh well, perhaps she is right; anyway, one shouldn't dabble in this kind of thing—there may be something in it.



WE encounter information as a measurable quantity most straightforwardly in storage systems. Their storage capacities are specified in units called **bits** (short for binary digits, to be explained below). A small random access memory, for example, might have a capacity of 1,024 bits. A magnetic disc store might have a capacity of 10 megabytes (where 1 byte is a group of 8 bits).

Another type of hardware for which a measure of information is used is data transmission equipment. Here, of course, we are concerned with a *rate* of flow of information from one terminal to another and this rate is measured in **bits per second**. British Telecom's Prestel service, for example, sends information over telephone circuits at 1,200 bits/second in one direction and at 75 bits/second in the other direction. A much faster system used by British Telecom, for data and other information, works at 2,048 kilobits/second.

### UNIT OF INFORMATION

The need for a universally accepted unit of information is as important as the need for universally accepted units of length, mass, time, electric current and the many others derived from them.

Without agreement on these units throughout the world—even though conversions between different systems of units may sometimes be necessary—not only science and engineering but the practical affairs of everyday life would come to a messy halt.

In a telecommunications system, for example, to make sure that a physical channel like a coaxial cable will actually convey information at the rate you wish to supply it from a given type of terminal, you must be able to measure the transmission capacity of the channel and the generating capacity of the terminal in the same units.

### ORIGIN OF BINARY CODE

But why have we chosen the bit, or binary digit, as the unit for measuring information?

Just as the foot as a unit of length originally came from the adult human foot, so there is an historical background to the newer unit as well. The whole history of signalling, whether by light, sound, mechanical movement or electricity, shows that methods using **two opposing states** have been both practical and effective. They are simple and unambiguous.

We have used light/darkness in lamps and heliographs, sound/silence in sirens and foghorns, left/right positions of galvanometer needles in telegraph instruments, hole/no-hole in punched paper tape and on/off in various electrical systems.

Samuel Morse devised his now famous code with its two symbols, long and short, to make use of the two positions of the armature, and the resulting black/white inked pattern, in his electromagnetic telegraph. In turn, the code was utilised in later signalling systems. In modern communications and electronics, of course, there are various techniques for providing the two states—for example, two different voltage levels of two different frequencies.

So the development over the years of a useful technology for sending information in terms of two states has been a strong incentive for us to consider information as being reducible to this simple binary form. But apart from the practical considerations there is also a good theoretical basis for the binary digit as a unit of information.

### SELECTION OF SIGNS

The communication of information is fundamentally a selection of signs from a fixed and agreed set of signs. This is so whether we are concerned with selecting sounds from a vocabulary, letters from an alphabet or words from a dictionary.

When we write in English we successively select letters from a set limited to 26. In another language the total number in the set might well be different. One might invent a written language with an alphabet of only 12 characters, or 7, or 4—or only two, say ■ and ▲. It would be

Optical fibre cable (left) that will replace the old style metal conductor and metal sheathed coaxial cable (right) in modern telecommunications networks are shown for comparison in this British Telecom picture. Optical fibres have a much greater transmission capacity than traditional coaxial cables. Pulse rates in excess of 140 million per second have been achieved over distances of 100km without intermediate amplification.



perfectly feasible to provide enough combinations of ■s and ▲s to signify all the meanings we wanted (though most of the words would have large numbers of these signs).

Two signs are, of course, the smallest possible "alphabet". Below that no choice is available. Thus a selection from two possible signs—a binary choice—is the elemental choice. In the numeration of binary arithmetic the two signs are conventionally written as 1 and 0, but the actual characters used are quite unimportant.

So, if the **binary choice** is the basic element of selection it is also the basic element of information, on the principle of selecting from a set discussed above. When we make a choice of one sign in a binary system of notation we are automatically implying "one out of two". For historical reasons the two written numerals of binary arithmetic have become well established, so it is now conventional to describe the choice as being one out of two *digits*. Hence the binary digit, or **bit**.

A store designed to hold binary information is a group of two-state elements (electronic devices or magnetic cells), one for each binary digit. The capacity of the store is simply the number of two-state elements available to hold the digits. But what about information that is not already in binary digital form, such as sound or vision signals?

## SUCCESSIVE BINARY CHOICES

By making a succession of binary choices we can make selections from much larger sets than just two signs—as large as we want, in fact. Fig. 5.1 shows how a selection can be made of one sign (the letter F) from an eight-character

alphabet by a series of three binary choices. Therefore the number of bits of information contained in the knowledge that one letter has been selected from an alphabet of eight\* is 3. If this whole selection were made in, say, a tenth of a second the information rate would be 30 bits per second.

Now let us see how this principle can be applied to information in electrical signals. First, in place of the eight letters write a set of eight voltages on a scale. Then add a horizontal time scale to allow a signal to be represented as a voltage/time graph. The result is Fig. 5.2.

We can now select by a series of binary choices any one voltage from a group of eight voltages, and the information contained in the knowledge that this particular voltage has been selected is 3 bits. This signal is not actually drawn as a continuous voltage/time graph but is defined approximately by an invisible line passing through the points marked at the different voltage levels.

If we doubled the number of voltages in the set to 16 the signal would be defined more accurately by more points, as shown in Fig. 5.3, but because more binary choices would be required to allow this, the information content of any one point on the graph would become 4 bits.

In theory, to define any signal perfectly would require an infinite number of voltage level points, infinitely close together (see Part 1 on "Representing information electrically"). In practice, it does not have to be all that great; for example, a good quality television signal calls for a minimum of eight binary choices (8 bits) which means selections from a set of 256 voltage levels.

\*The generalised formula is: number of bits =  $\log_2 N$ , where  $N$  is the number of signs in the set.

## INFORMATION RATE

The information *rate* of the signal in Fig. 5.2 is determined by the time intervals between the voltage points defining the graph. This varies between 60 milliseconds (giving 16.6 bits/second) and 360 milliseconds (giving 2.8 bits/second).


In practice we have to allow for the highest information rate necessary for the class of signal we are dealing with. A television signal, for example, calls for a maximum information rate of about 11 million bits/second, while a telephone voice signal requires a maximum rate of about 8,000 bits/second.

## INFORMATION CHANNELS

A channel is a means of transmitting an individual, recognisable signal or train of information—say a voice signal or telex message—from one place to another. Usually this transmission is in one direction only, but sometimes the term "channel" implies bi-directional transmission. The physical means of transmission ranges from a simple pair of wires, as used for the domestic telephone line, to coaxial cables, radio links, waveguides and optical fibres.

By using carriers (Part 3) or time-sharing methods (Part 4) we can accommodate a whole group of channels within a single transmission system such as a coaxial cable, without the individual trains of information interfering with each other. This is **multi-channel transmission**.

What mainly matters in information technology is the capacity of a channel to convey information—the maximum flow rate in bits per second that it will handle. This depends on a number of physical quantities in the transmission system. One is the electrical power in the **signal**; another is the electrical power in the **noise** (unwanted random fluctuations) introduced by the transmission system itself.

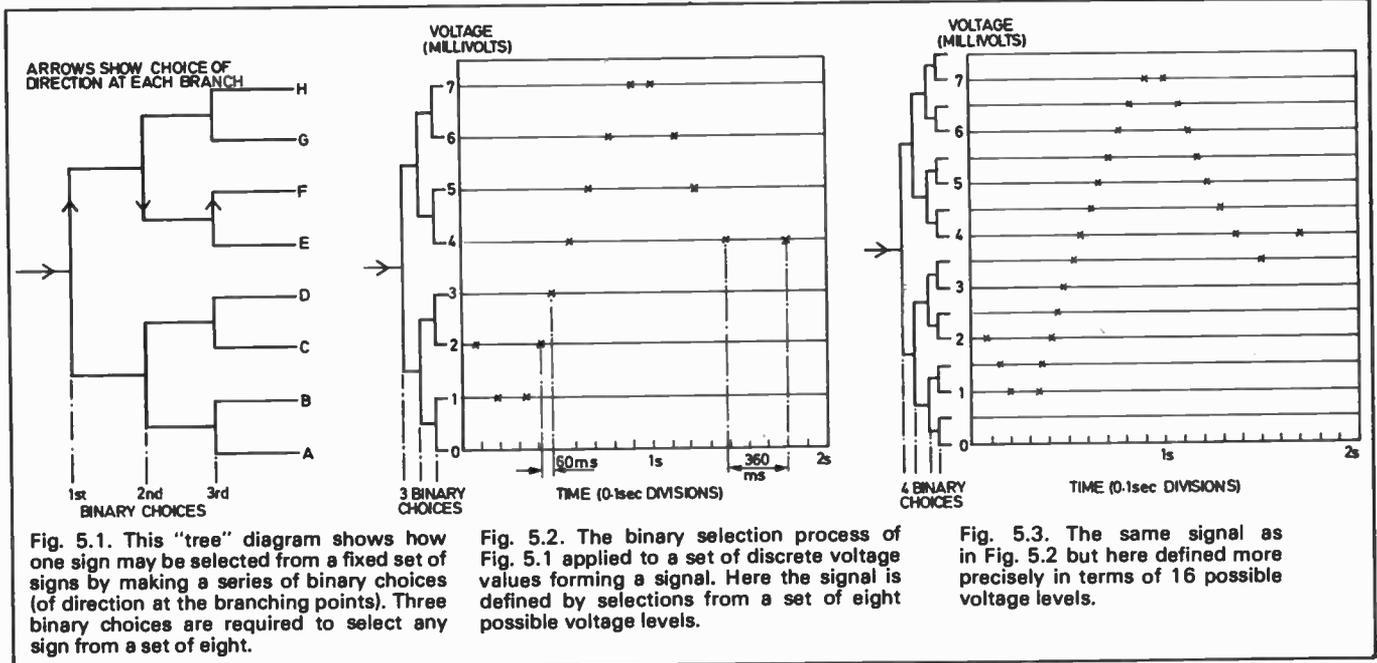

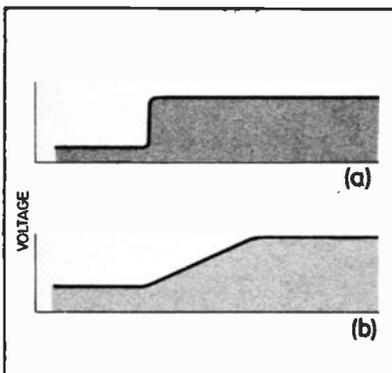


Fig. 5.4. Parts of two signals, illustrating different rates of change of voltage with time.

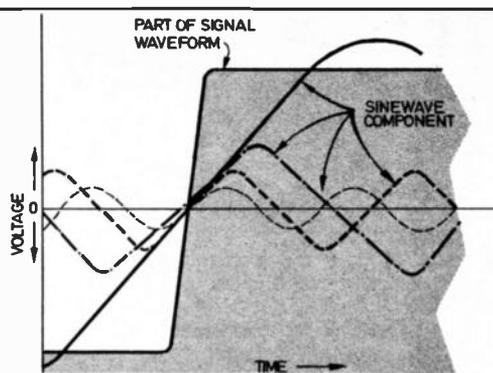


Fig. 5.5. How a signal waveform may be analysed into a set of sine-wave components (Fourier analysis). Not all of the components that make up this signal waveform are shown here.

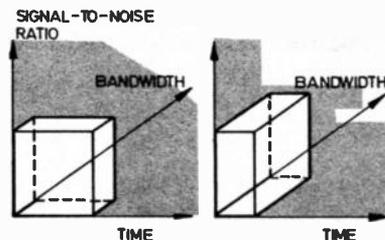


Fig. 5.6. Three-dimensional analogy in which the box is a quantity of information (bits). In transmitting a given quantity of information (the volume of the box), the time taken, bandwidth and signal-to-noise ratio may be exchanged with each other. These two examples illustrate an exchange of time and bandwidth (signal-to-noise ratio remaining constant).

## SIGNAL-TO-NOISE RATIO

The presence of noise sets a limit to the number of distinct levels in a signal waveform that can be detected, (Fig. 5.2 and Fig. 5.3). Sufficient power in the signal will make the effect of this noise insignificant, but there are practical limits to the amount of power that can be transmitted. The relationship of these two (average) powers—the signal-to-noise ratio—is therefore important in determining the accuracy of the information received at the end of the channel.

Another factor determining the accuracy of signal transmission is the ability of the channel to convey the variations of the electrical quantity (Part 1) that represent information—more specifically, the *rate of change* of these variations. For example, Fig. 5.4 shows parts of two signal waveforms, each of which is a transition between two steady voltages. In (a) the rate of change of voltage with time is higher than the corresponding rate of change in (b).

In a channel using, say, a wire cable as a transmission medium, the resistance and reactance of the wire together limit the rate of change of an electrical quantity that can be sent along it. Consequently, if the signal waveform at the input of the channel contains higher rates of change than the medium can transmit, the waveform received at the end will be distorted and hence the information will contain errors.

For example, the transition at (a) in Fig. 5.4 could be considered as part of a signal fed to the input of a channel. If the channel were incapable of transmitting this rate of change the signal as received at the end of the channel would be something like (b).

## BANDWIDTH

The ability of a channel to convey such rates of change is determined by its **bandwidth**, measured in hertz (Hz). This term may require some explanation. Any signal waveform can be analysed into a number of sine-wave components of

different magnitudes, frequencies and phases.\* This is illustrated in Fig. 5.5 which shows some, but by no means all, of the sine-wave components which, when added together, constitute the signal waveform shown.

Each component has a maximum rate of change. A channel will convey a limited range of these sine-wave components, and the bandwidth of the channel is the extent of the continuous range, in Hz, over which the channel transmits a specified proportion of the original signal power. The bandwidth of a typical telephone voice channel, for example, is about 4,000Hz.

The channel's bandwidth therefore indicates the rates of change that can be transmitted and, as a result, the number of independent levels of a waveform that can be conveyed by it in a given time. It is therefore a factor in determining the maximum information rate in bits/second.

## THREE QUANTITIES

So signal power, noise power and bandwidth together determine the highest rate at which a channel can convey information. The exact relationship of the three quantities to this maximum rate is given by an expression\* which enables the channel to be matched to a given source of information, or vice-versa.

In some IT systems it is possible to adjust the rate at which information is generated at the source—to alter the length of time available to convey a given number of bits. This enables us to alter

\* Mathematically inclined readers will know this as **Fourier analysis**. The sine-wave components are expressible mathematically as the terms of a Fourier series (named after the French mathematician and physicist J. P. J. Fourier).

\* Derived by C. E. Shannon.  $C = W \log_2(1 + S/N)$ , where  $C$  = maximum capacity of channel in bits/second,  $W$  = bandwidth in hertz,  $S$  = mean signal power in watts, and  $N$  = mean noise power in watts.

the bandwidth and/or signal-to-noise ratio required. A graphical analogy of this inter-dependence is given by the "box" diagrams in Fig. 5.6.

The volume of the box, the triple product of time, bandwidth and signal-to-noise ratio, is proportional to a given number of bits of information. Obviously it is possible, as shown by the two examples, to change the time available, the bandwidth and the signal-to-noise ratio (actually it is  $\log_2$ ), in various ways that will maintain constant the volume representing the quantity of information.

A good example of this, known to some experimenters, is slow-scan television. If you increase the length of time available to send a given quantity of information in a picture, you can transmit the picture in a channel of smaller bandwidth than would otherwise be possible.

To be continued

**PRACTICAL ELECTRONICS**  
MARCH 1983

**FREE SCRATCH PAD**

**PROJECTS**

- Ice/Lights Alarm
- Car Accessory Power Supply
- 4½ Digit Frequency Meter
- Case Alarm

**FEATURES**

- Circuit Layout Simplified using the free Scratch Pad
- Into The Real World—Interfacing micros
- Microfile: 1802 data

**PLUS**

Extra Ingenuity Unlimited

**ON SALE NOW**

# ELECTROVALUE

- 24 HOUR NORMAL DESPATCH TIME
- ESTABLISHED 1965
- ALL GOODS GUARANTEED BRAND NEW AND TO SPECIFICATION
- APPOINTED SIEMENS DISTRIBUTORS

### CAPACITORS

Polystyrene, Siemens  
5% Tolerance 160V  
5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF 15p;  
47, 56, 68, 82, 100, 120, 150, 180, 220,  
270, 330, 390, 470, 560, 680, 820pF, 1n,  
1n2, 1n5, 1n8, 2n2, 2n7, 3n3, 3n9, 4n7,  
10p; 5n6, 6n8, 8n2, 10n, 13p  
Ceramic, Vario, small 1.8, 2.2, 2.7 etc. up to  
1n5 each, 1n5, 2n2, 3n3, 4n7, 6n8, 5p;  
10n, 22n, 6p, 33n, 47p, 100n, 8p  
Polyester, Siemens Layer Type 7.5mm  
lead spacing 10025  
1n, 1n5, 2n2, 3n3, 6p, 4n7, 6n8, 8n2, 10n  
12n, 15n, 18n, 22n, 33n, 47n, 7p, 56n, 68n,  
7p, 82n, 100n, 9p, 120n, 150n, 15p, 180n,  
220n, 12p, 270n, 330n, 390n, 390n, 470n,  
15p, 150n, 680n, 24n, 10mm spacing, 1uF  
5p, 15mm spacing, 2.2 5p, 22 5p, 22mm  
spacing, 1uF 400V 50p, 3.3uF 100V 69n; in  
depth stocks

## I.C.s - DIGITAL & ANALOGUE

DIGITAL			
74LS161	36	7413	18
74LS163	36	7414	20
74LS164	30	7420	15
74LS165	50	7430	14
74LS166	60	7440	10
74LS173	45	7443	32
74LS174	45	7443	32
74LS175	40	7444	60
74LS191	36	7447	36
74LS193	40	7448	40
74LS195	39	7450	14
74LS196	48	7451	14
74LS197	60	7453	14
74LS201	14	7454	14
74LS221	48	7454	14
74LS240	55	7460	14
74LS241	55	7470	24
74LS242	55	7472	24
74LS244	55	7474	26
74LS245	55	7474	26
74LS251	70	7475	25
74LS252	70	7475	25
74LS253	70	7480	35
74LS257	30	7482	65
74LS259	55	7487	65
74LS266	20	7483	38
74LS273	55	7483	38
74LS279	30	7486	18
74LS299	150	7489	159
74LS367	30	7490	30
74LS368	28	7491	35
74LS373	60	7492	25
74LS374	55	7493	25
74LS378	60	7494	35
74LS393	45	7495	35
74100	11	74100	45
74101	11	74107	20
74102	11	74121	24
74103	12	74123	34
74104	12	74123	34
74105	15	74126	33
74106	20	74141	51
74107	20	74151	40
74108	20	74154	60
74109	24	74155	39
74110	14	74156	40

CMOS			
4001	10	4001	10
4002	10	4002	10
4006	14	4006	14
4007	14	4007	14
4008	14	4008	14
4009	14	4009	14
4010	24	4010	24
4011	11	4011	11
4012	16	4012	16
4013	20	4013	20
4014	25	4014	25
4015	25	4015	25
4016	35	4016	35
4017	65	4017	65
4018	65	4018	65
4019	25	4019	25
4020	60	4020	60
4021	18	4021	18
4022	39	4022	39
4023	14	4023	14
4024	35	4024	35
4025	13	4025	13
4026	25	4026	25
4027	20	4027	20
4028	35	4028	35
4029	34	4029	34
4030	15	4030	15
4041	45	4041	45
4042	20	4042	20
4043	24	4043	24
4044	34	4044	34
4046	46	4046	46
4049	23	4049	23
4050	33	4050	33
4060	40	4060	40
4069	13	4069	13
4070	39	4070	39
4071	13	4071	13

## BOXES

High quality Black ABS plastic or die-cast plain or stove grey

L	W	D	ABS	Plain	Stove Gr
100	60	25	2002	5001P	5001
113	83	31	2003	5002P	5002
121	66	40	2004	5004P	5004
152	82	50	2005	5005P	5005
192	113	61	2006	5006P	5006

## VEROBOX CASES

to give a completely professional finish to a much valued project.  
ABS, light grey top, dark grey bottom + 2 anodised panels

L	W	D	TYPE	PRICE
205	140	40	21034	£4.52
205	140	75	21035	£5.02
205	140	110	21036	£6.54
180	120	65	21037	£3.13
180	120	65	21038	£4.40
180	120	90	21039	£4.69
155	85	39	21040	£3.31
155	85	39	21041	£3.31
155	85	80	21042	£3.31
125	65	30	21047	£2.48
125	65	39	21048	£3.15
125	65	50	21049	£3.56

## SEMICONDUCTORS

1N914	03	2N3819	22	AA118	14
1N914B	10	2N3820	40	AA119	13
1N916	52N	3B23	60	AC126	25
1N4007	06	2N3904	15	AC127	25
1N4148	03	3N3906	15	AC128	25
1N5402	14	2N4036	46	AC151R	55
2N4058	18	2N4058-62	09	AC153K	20
2N6957	23	2N4124	25	AC176	25
2N930	20	2N4284	30	AC177	156
2N1132	23	2N4286	18	AC178	120
2N1302	110	2N4289	23	AC179	99
2N1303	58	2N4291	24	AC179	99
2N1304	62	2N4292	21	AC179	170
2N1305	62	2N4293	62	AC179	170
2N1306	90	2N4294	32	AD136	50
2N1307	87	2N4295	110	AD142	80
2N1308	147	2N4296	108	AD149	240
2N1309	99	2N4547	32	AD161	35
2N1599	100	2N4548	32	AD162	35
2N1613	25	2N4549	38	AF114	37
2N1711	25	2N4550	38	AF115	37
2N1893	32	2N6057	376	AF116	37
2N2184	31	6F40	152	AF117	110
2N2193A	25	16F40	106	AF124	37
2N2222A	25	40F40	226	AF126	37
2N2359A	21	4036PDIS	1	AF200	240
2N2484	25	40362	85	AF220	37
2N2646	46	40406	71	AF239	114
2N2904	28	40408	86	AF279	30
2N2904A	25	40412	106	AF127	204
2N2905A	26	40430	100	AFY16	327N
2N3053	23	40594	123	AFY180	317N
2N3054	56	40595	123	AFY186155N	317N
2N3055	46	40636	147	AFY42	461N
2N3405	64	40639	146	AU106	240
2N3663	15	A930	16	AU111	(use)
7402-11	08	AA113	13	AU116	(use)
2N3771	10	AA116	9	AU120	96
2N3794	21	AA117	13	BD140	25N

## METERS

Large range of types in stock, also probes.  
Inlets, accessories  
PANEL METER in 50, 100, 500A, 1, 5, 10, 50, 100, 500mA, 1A, other models

**MULTIMETERS**

NH56A NEW 20kV V A.C./D.C. RES/DC in 23 ranges. 130 x 88 x 37mm. £11.20N

YMK60TR 20kV V A.C./D.C. dB Trans. in 21 ranges. 100 x 95 x 45mm. £16.45N

BC214	09	BFR39-11	23	E120	76
BC214L	09	BFR79-21	23	E206	154
BC238C	09	BFT65	119	E833	20
BC239C	09	BFT66	192	MJ2955	90
BC258S	09	BFX29	24	MJ3430	56
BC278	16	BFX84	24	MJ29355	95
BC300	32	BFX85	24	MJ3055	70
BC301	24	BFX87	28	MPF102	40
BC303	30	BFX88	26	MP5653	40
BC305	21	BFX91	30	MP5654	40
BC328	11	BFY51	24	MPSA12	38
BC337	14	BFY52	24	MPSA63	38
BC338	11	BFY90	143	NAS2065	81
BC413	09	BR34	70	OA47	32
BC414	09	BR64	110	OA90	10
BC477	24	BRY39	46	OA91	10
BC546	10	BSX20	22	OA95	DIS
BC547	09	BSX26	22	OA202	14
BC548	09	BSX63	769N	OC28	75
BC549	09	BT106	147	OC29	75
BC550	10	BT108	136	OC35	75
BC556	10	BT105	170	OC38	90
BC557	09	BU124	65	OC84	25
BC558	09	BU208	180	PM7A2	373
BC559	09	BUX26	360N	PN70	10
BC560	10	BUX28	546	PN72	05
BC579	38	BUX81	744	O4006LT	104
BC680	43	BUX85	249	O4010LT	115
BC681	157	BV210A	478	O4205H	460
BC682	10	BU215	12.27	O7200	189
BC683	10	BU220	523	O7200D	104
BC684	18	BU223	781	TAG3-400	100
BC685	32	BU224	12.50	TAG209-400	85
BC686	46N	BU232	625	TAG209-600	130
BC687	48	BU233	844	TI0C6D	48
BC688	25	BU241A	637	TI0C6M	55
BC689	27	BU242A	637	TI0C6G	60
BC690	27	BU245	12.76	TI0C6D	64
BC691	30	BU248	18.94	TI0C6D	64
BC692	30	BU250A	763	TI0C26D	51
BC693	42N	BU254A	21.43	TI0C26E	106
BC694	42N	BU259	21.43	TI0C26G	106
BC695	35	BU283	11.29	TI0C31A	36
BC696	35	BU283A	11.96	TI0C32A	36
BC697	35	BU284A	12.75	TI0C32B	36
BC698	25	BU287	25	TI0C32C	36
BC699	25	BU288	25	TI0C32D	36
BC700	25	BU289	25	TI0C32E	36
BC701	25	BU290	25	TI0C32F	36
BC702	25	BU291	25	TI0C32G	36
BC703	25	BU292	25	TI0C32H	36
BC704	25	BU293	25	TI0C32I	36
BC705	25	BU294	25	TI0C32J	36
BC706	25	BU295	25	TI0C32K	36
BC707	25	BU296	25	TI0C32L	36
BC708	25	BU297	25	TI0C32M	36
BC709	25	BU298	25	TI0C32N	36
BC710	25	BU299	25	TI0C32O	36
BC711	25	BU300	25	TI0C32P	36
BC712	25	BU301	25	TI0C32Q	36
BC713	25	BU302	25	TI0C32R	36
BC714	25	BU303	25	TI0C32S	36
BC715	25	BU304	25	TI0C32T	36
BC716	25	BU305	25	TI0C32U	36
BC717	25	BU306	25	TI0C32V	36
BC718	25	BU307	25	TI0C32W	36
BC719	25	BU308	25	TI0C32X	36
BC720	25	BU309	25	TI0C32Y	36
BC721	25	BU310	25	TI0C32Z	36
BC722	25	BU311	25	TI0C33A	36
BC723	25	BU312	25	TI0C33B	36
BC724	25	BU313	25	TI0C33C	36
BC725	25	BU314	25	TI0C33D	36
BC726	25	BU315	25	TI0C33E	36
BC727	25	BU316	25	TI0C33F	3

# EXPANDED ADD-ON KEYBOARD *for the* ZX81



BY J. M. STEJSKAL

**T**HIS project describes the circuitry and its construction for extending the ZX81 add-on keyboard to provide a number of single stroke entry functions. These functions would normally be entered using SHIFT with another key. For example, to enter TO, SHIFT is held down while 4 is pressed.

The add-on keyboard seen here is that available from Redditch Electronics. We expect that the additions described here will be suitable for use with keyboards from other suppliers. We have not tried these, however.

Since the ZX81 user is no longer obliged to hold down the SHIFT key for much of the time, the typing becomes more comfortable and speedier with these additions.

## ZX81 KEYBOARD

The relevant section of the ZX81 keyboard circuit is shown in Fig. 1. The 40 key-switch positions are arranged on a 5 x 8 grid. There is no contact between column and row until the key at their intersection is pressed. When doing this

the information on the column line is transferred to the appropriate row line(s).

The ZX81 keyboard routine uses the upper half of the CPU address bus to repeatedly shift a logic 0 along address lines A8 to A15. This strobing happens very rapidly. The information appearing on the KBD bus (0 to 4) when a key is pressed tells the system which key has been pressed. If no key has been pressed, all logic 1's are on the bus resulting from the 10kΩ pull-up resistors to +5V.

If, say, the "1" key is pressed, then when A11 next goes low, KBD0 will also go low with the remainder of this bus staying high. This information is read into ICA by a scanning routine and the pressed key determined.

How the low gets on the KBD line happens in the following way. When the address line goes low, and the key makes contact, a series circuit across the +5V and logic 0 is made with one of the 10kΩ resistors and the diode. It is the junction of these two components which is read on the KBD line. Since the forward drop across a diode such as those in the ZX81 is about 0.7V, it is below the logic 1 threshold and is thus read as a 0 as required.

## CIRCUIT DESCRIPTION

The complete circuit diagram for the Expanded Add-On Keyboard for ZX81 is shown in Fig. 2. There are three different circuit configurations according to the position of the switch on the keyboard matrix, see Fig. 1. The add-on keyboard is in parallel with this using KBD0 to KBD4 and A8 to A15.

Fig. 2 (opposite). The complete circuit diagram for the extra keys to be fitted to the proprietary add-on keyboard.


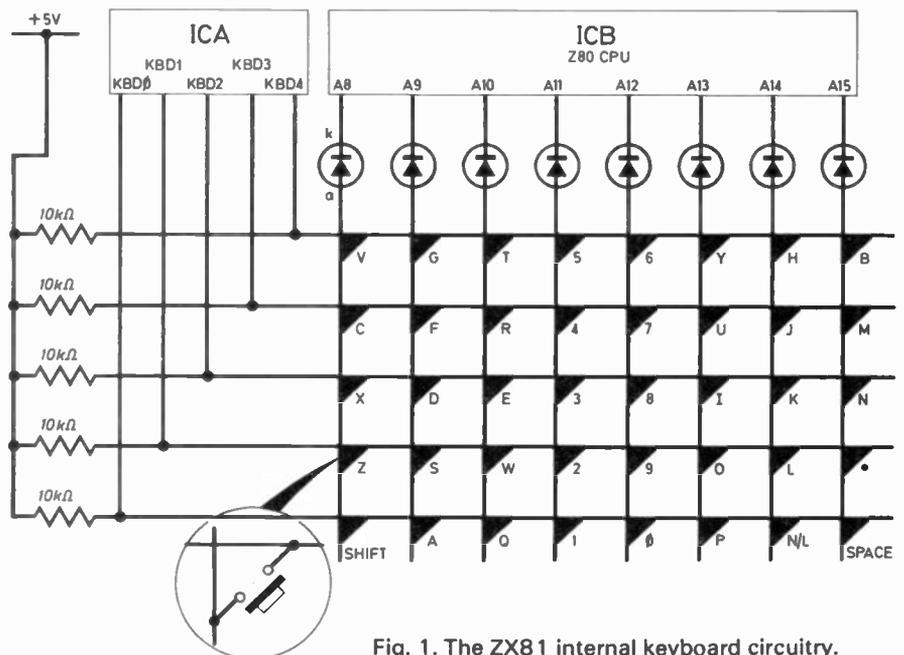


Fig. 1. The ZX81 internal keyboard circuitry.

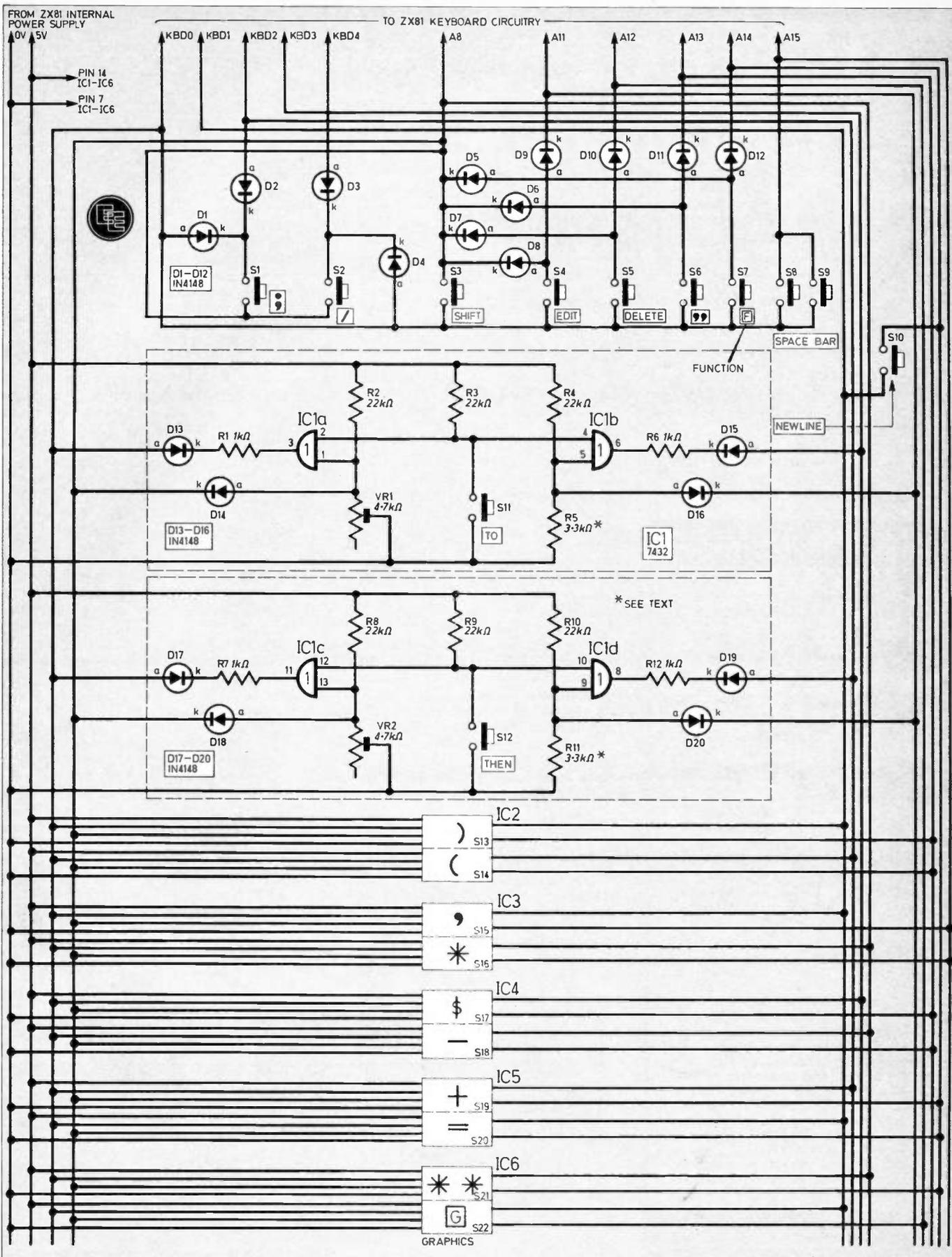

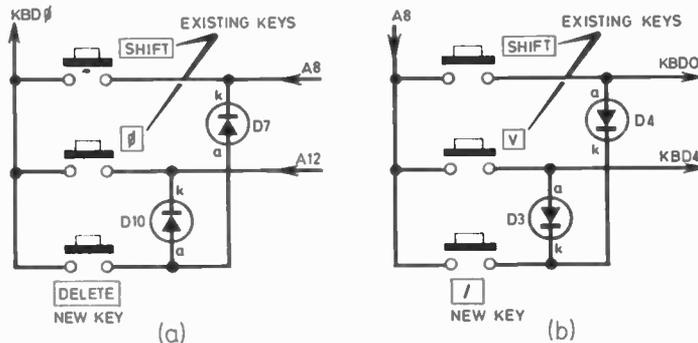


Fig. 3. Two of the three different switch-circuits used in the design, re-drawn for clarity.

The operation of two of these three different circuit arrangements is best explained by means of the re-drawn sections in Fig. 3.

The circuit in Fig. 3a is for use with any, or all, characters on line KBD0 which connects them to the SHIFT key, but where their address lines are different.

The characters that can be used with this circuit are: A,Q,I,O,P,NEWLINE, SPACE. The following are used here: I(EDIT), Ø(RUBOUT), P("), NEWLINE(FUNCTION). As an example, Fig. 3a shows the circuit for the DELETE key. Both switches, SHIFT and Ø, work independently as before, the two diodes D7 and D10 preventing any interconnections between the two. When the common key DELETE (RUBOUT) is pressed, then the logic levels on A8 and A12 are successively passed to KBD0, thus producing the same effect as a "SHIFTed I", that is, DELETE.

As already mentioned, only the frequently used characters have been selected here: EDIT, DELETE, ", FUNCTION ( ). Although there is no special arrangement for any delay, the SHIFT always comes on first, without fail, making the circuit reliable and cheap.

The other circuit, in Fig. 3b, is suitable for keys: Z(:), X(;), C(?) and V(/). Two of these have been selected here: X(;), and V(/). The example shown is for the division sign "/".

The circuit in Fig. 3(b) is similar to that in (a) but this time it is the address line which is common to two keyboard lines: A8 is commoned with SHIFT and V to realise /. If when / is pressed, a logic low is placed on A8 it will be transferred to both KBD0 and KBD4 which is the required condition for SHIFTed V.

Three of the extra key-switches are connected in parallel with existing keys, moving them to more convenient positions. Like all other extra keys, they can still be used in their original position. They are: SHIFT on the right-hand side of the keyboard, SPACE on a long space-bar and NEWLINE at the bottom left-hand corner. The space-bar shown here is from an old ASCII keyboard and is fitted with a key-switch at each end.

Although the remaining 28 key-switches do not have a common line with SHIFT key, all or any may be connected for single shifted-key operation by using a pair of logic gates for each function. Twelve keys were selected to appear on the prototype keyboard, any of which may be substituted by those of the constructor's choice. The twelve are: 4(TO), 3(THEN), Ø( ), I( ), (.), B(\*), U( ), J(-), K(+), L(=), H(\*\*) 9 (GRAPHICS) G.

Two separate sections to produce TO and THEN are shown in detail in Fig 2. Each is made up from two OR gates and are seen to be identical.

The components in the other circuits are identical, the only difference being that the b and d gates in each pair of gates might be connected to a different KBD-line and/or A-line. One gate in every pair operates the SHIFT. VR1 and R5 arrange the delay required for SHIFT to operate first.

With S11 not pressed, a logic high (1) reaches one input of each of the two OR gates IC1a and IC1b causing each output to be at logic 1. The other input to each gate is held at logic 0 by the potential divide effect of R2/VR1 and R4/R5. When S11 is pressed the outputs of IC1a and IC1b drop to logic 0.

Now each keyboard line is strapped to +5V by its own resistor (in the ZX81). The ZX81 internal circuitry looks for a logic 0 appearing on one of the lines at the appropriate time when being strobed by A8 to A15 outputs. When the output of IC1 goes low, a low is read in on KBD0. This, together with the low logic reaching A8 from pin 1, simulates SHIFT being pressed. IC1b goes low also at the same time, with a logic 0 being placed on KBD3 and A11. The values of VR1 and R5 are chosen so that SHIFT acts before 3, giving SHIFTed 3. This is TO, the required result. (To be continued)

## COMPONENTS

### Resistors

R1,R6,R7, R12 1kΩ (6 off each)  
 R2,R3,R4, } 22kΩ (6 off each)  
 R8,R9,R10 }  
 R5,R11 3.3kΩ (6 off each)  
 All ¼W or ½W carbon ±5%

### Potentiometers

VR1,VR2 4.7kΩ sub-miniature vertical skeleton presets (6 off each)


### Semiconductors

D1-D12 1N4148, 1N914 or similar switching diodes (12 off)  
 D13-D20 1N4148 or similar (12 off each)  
 IC1-IC6 7432 TTL Quad 2-input OR gates (6 off)

### Miscellaneous

S1-S22 p.c.b. mounting momentary action push-to-make keyboard switch (22 off)  
 Verostrip: 64 strips, 36 strips (2 off); fibre glass board (un-coppered, for board D) size 207 x 30mm; top caps for above switches: single (18 off), double (2 off), treble (1 off, or separate space bar, see text); 14-pin d.i.l. i.c. sockets (6 off); lightweight stranded p.v.c. covered wire—selection of colours; metal for brackets and fixing hardware as required.

Approx. cost Guidance only **£17.50**

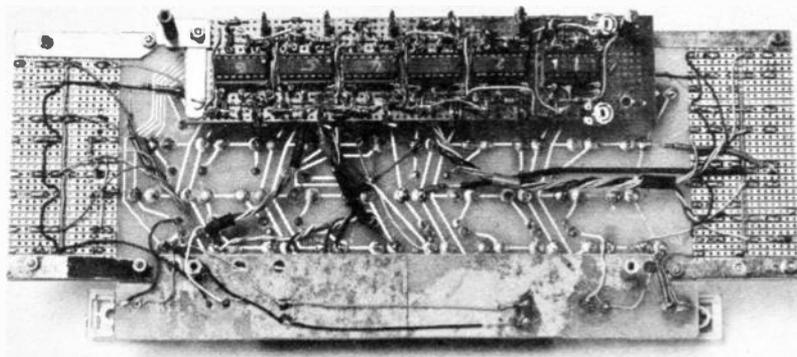

# CIRCUIT EXCHANGE

This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised.


Payment is made for all circuits published in this feature.

Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.
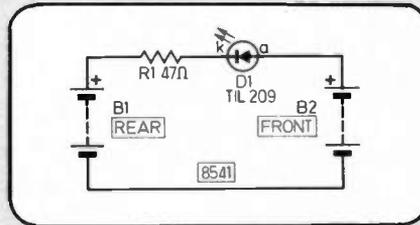
## REAR-LIGHT FAILURE INDICATOR

THE question of whether or not the rear light is working is a constant worry for cyclists riding at night.

This simple circuit lights an l.e.d. if the rear-light battery is flat. The circuit uses the front-light battery as the power source for the l.e.d., and the l.e.d. is mounted on the steering column of the cycle. If the rear-light battery is flat there is a potential difference across the l.e.d. and it will



glow, informing the cyclist of the urgent need to change the battery.


Andrew Marshall,  
Old Basford,  
Nottingham.

## QUICK POLARITY TESTER

IN THE prototype of the Quick Polarity Tester the connections to the battery were for negative earth vehicles, as shown in the circuit diagram, but for positive earth vehicles the connections to the battery *must* be reversed.

To test this, connect up the battery terminals to the car cigarette lighter (+ to pin, - to chassis). It was found best to use "Christmas Tree" bulbs as these were small, although other bulbs could be used.

Alexis Landa,  
Ilfracombe,  
Devon.

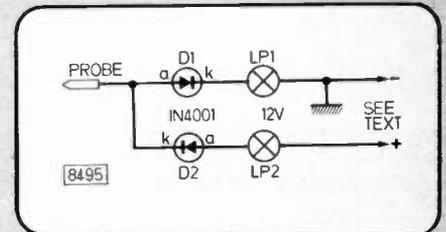

## SPEED CHESS AND DRAUGHTS TIMER

Stimulated by the Lightning Chess Buzzer featured in an earlier issue of *EE*, I have designed another timer based on the 4017 CMOS chip.


A NAND gate oscillator formed by IC1a and IC1b feeds the clock of the decade counter IC2. This causes the line of l.e.d.s D1 to D10 to light in sequence unless the reset switch S1 is operated.

If a player fails to complete his move within the time set by potentiometer VR1

then the yellow l.e.d. D10 will light and an alarm will sound. This alarm is triggered by the oscillator IC1c/IC1d and indicates a time fault.

As shown, the maximum time is adjustable up to 15 seconds, by increasing the value of C2 the time maximum may be increased in proportion.


Andrew Knight,  
Langley,  
Southampton.

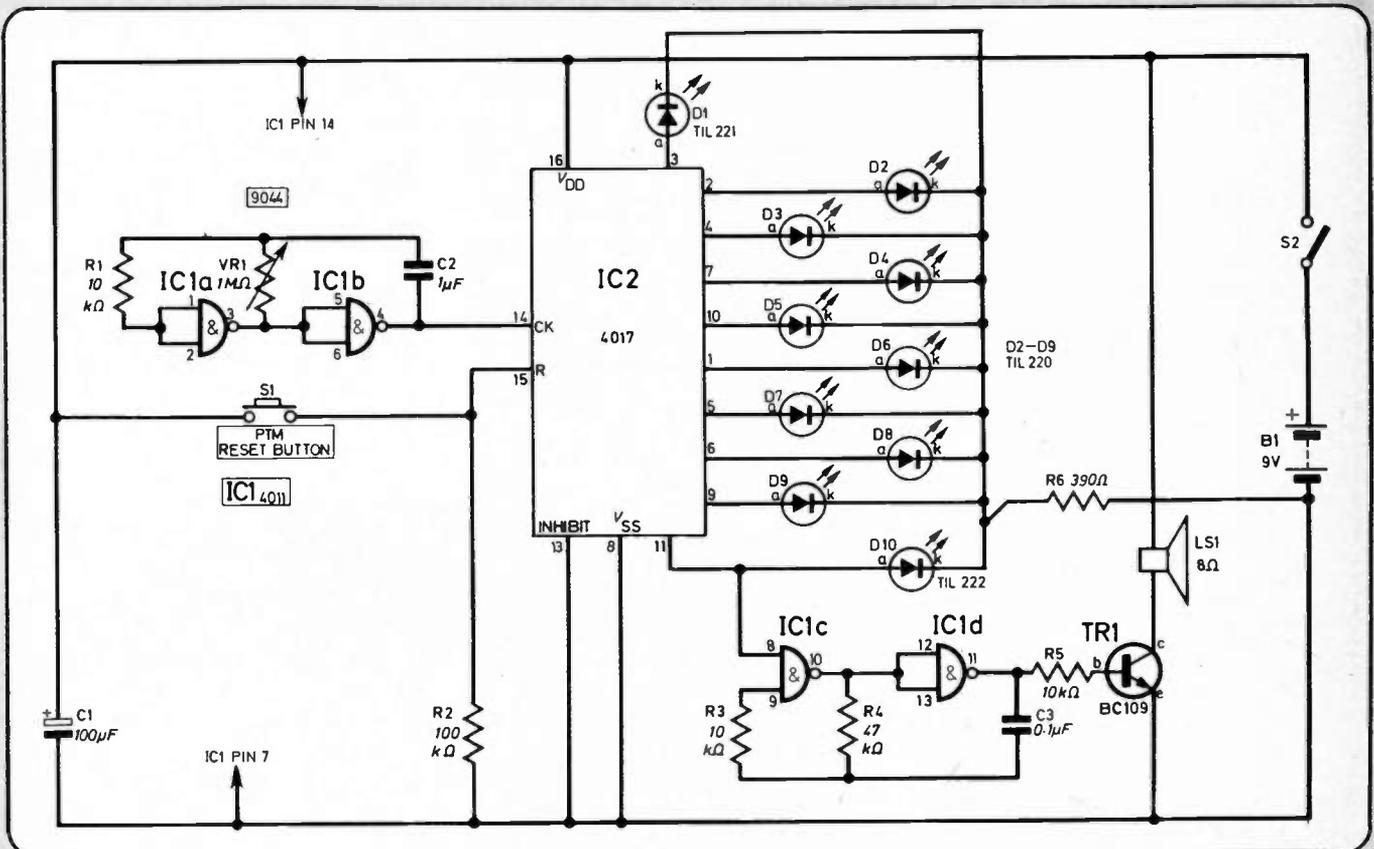

# ACORN ATOM

## A USER'S REPORT

BY T. J. JOHNSON

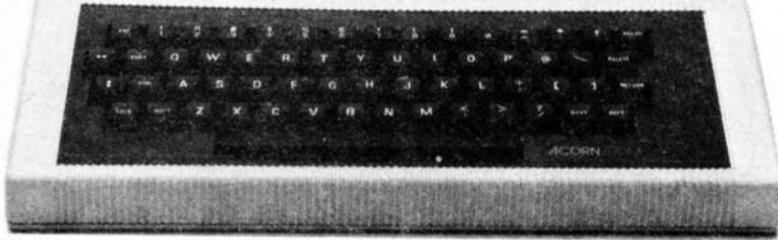

**T**HERE are two basic versions of the Acorn Atom home computer and both are available as kits or ready made. The first, commonly referred to as the "minimum" system, has 8K of ROM and 2K of RAM. The second, often called the "expanded" system, has 12K of ROM and 12K of RAM. The one point to note is that the expanded system has the optional floating point ROM fitted—a most valuable addition.

I purchased the minimum system in kit form for really only one reason, and that was to save money. I found that there was nothing particularly instructive about constructing the kit, so unless you have very shallow pockets it is better to purchase the assembled and tested version.

### THE KIT

The Atom kit comes complete with concise and very compact assembly instructions, and was obviously written with the more experienced constructor in mind. Although the kit is remarkably easy to construct, it is definitely not recommended for beginners who lack experience in soldering.

I experienced no great difficulties in assembling the kit, and found that the Atom was complete and ready for use in a little over three hours. The one frustrating moment came when fitting the keyboard.

The construction of the keyboard is such that you have to insert the fine gold-plated contact wires (over 100!) into the large diameter p.c.b. holes. This may sound easy but it can prove frustrating, especially when you think you have the keyboard fitted and are just about to solder the wires to the p.c.b., then you discover that a single contact wire has become trapped under the keyboard, with the result that you have to remove it and start all over again. This is the one major criticism I have with the kit.

A short lead also needs to be made which connects the Atom cassette interface socket with your recorder. The manual shows the required connections for the Atom end. For the recorder end

you should either refer to its manual and/or solve the connections by trial and error.

When trying out the Atom for the first time, be sure to check each key, and every key, in turn. I found when power was first applied that, whichever key I pressed the figure "8" appeared on the VDU. After much fault-tracing it turned out to be the "8" key at fault with a permanent short across it. The fault was cleared, of course, but it does illustrate the point earlier about the difficulty of fitting the keyboard.

### EXPANSION

The expandability of the Atom is perhaps one of its major assets. The minimum system can be expanded in a variety of ways. For example: by adding extra RAM—here 10K may be fitted on the board with a further 64K as an additional "card"; a colour encoder card and extra ROM in the form of two further i.c.s. All these additions may be mounted inside the case of the Atom.

The usual printer and floppy discs may also be connected to the Atom by way of the various expansion sockets on the rear. These expansion sockets also carry the Address, Data and Control lines of the CPU as well as various control signals which may be used for further expansion, for example, extra RAM and ROM.

*[The Atom is also equipped with latched ports. These have been employed in the design of an Eprom Programmer, see page 178].*

### CASSETTE FILING

The cassette operating system of the Atom is exceptionally good, despite its very slow transfer rate of 300 bits per second, when compared with other machines. I use a Ferguson model 3240 recorder of some 10 years vintage and well-worn heads, and apart from the initial troubles when first setting the system up, have experienced no difficulties in saving or loading programs on tape.

The cassette operating system is very tolerant of input/output levels from the

recorder and thus probably makes it one of the better systems available.

### THE LANGUAGE

The language used on the Acorn Atom is of course Basic—with a few variations on the "standard" Basic.

It would be impracticable in a short report such as this to list all the variations, and in the long run it would be of no practical use, unless you intend to translate one form of Basic program to another. If you have some sort of electronics background or a logical mind you should have no trouble in getting to grips with the language. I will confess that before I bought the Atom I had no previous knowledge of Basic apart from the many programs I had seen in magazines. Providing you have had a similar experience it will not be difficult to progress through the Basic manual supplied with the unit.

Possibly one area of programming which is difficult to understand is Assembler Programming using mnemonics. The Atom manual gives an introduction to assembler programming, but from my point of view is very lacking in detailed explanations of the various instructions.

### GRAPHICS

Most home computers have some form of graphics capabilities, either black and white and/or colour. The Atom has both, providing the colour encoder card is used. In its lowest graphics mode the resolution is  $64 \times 48$  pixels and in the highest mode is  $256 \times 192$  pixels (slightly lower when colour is used).

I found the graphics quite difficult to grasp at first, particularly the fifteen PLOT commands, and also when incorporating these instructions in a games program. The graphics are, however, very good and should not prove difficult after a certain amount of practice.

It is worthwhile to point out that the VDU is memory mapped, that is, each of the 512 points on the screen may be POKED with any desired character, thus providing an additional graphics mode.

### CONCLUSIONS

Obviously, since this is the first and only home computer I am likely to buy, I am slightly biased in favour of the Atom.



Since owning the Atom for some 12 months, I have had the opportunity to try several other machines, both "home" types and "commercial" types of computer. In nearly every case, I prefer the Atom for its simplicity and ease of use.

I believe the computing power of the Atom is somewhat under-estimated and consider the Atom a most worthwhile investment. It is very simple to use, its language is easy to learn, and it is very easily expandable. For a relatively small outlay I have a very powerful computing machine that I do not consider will be obsolete in ten years' time. □

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.
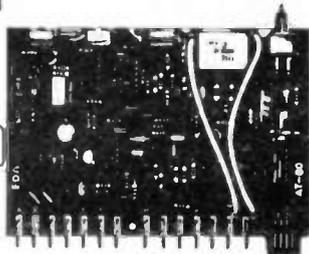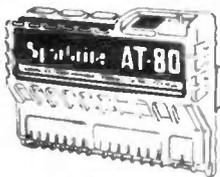
# Sparkrite

BRANDEADING ELECTRONICS  
NOW AVAILABLE IN KIT FORM



## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble


## VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories 2,000 miles 180 gallons 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!



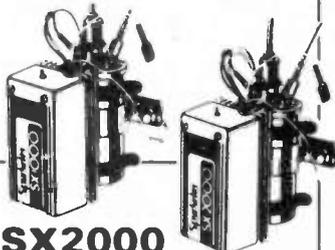
## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



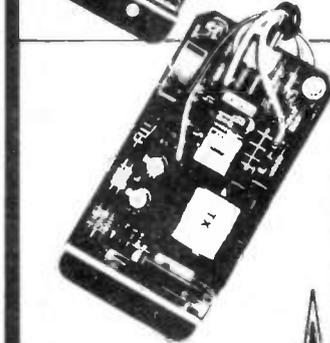
## TX1002 Electronic Ignition

- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble.


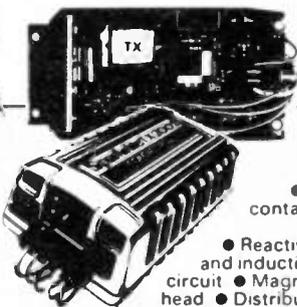
## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




## TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge
- Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents

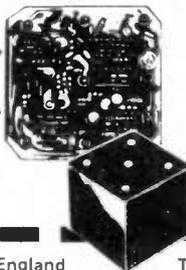**SPECIAL OFFER**  
"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street, Walsall, West Midlands, WS1 3DE England

Tel: (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

NAME \_\_\_\_\_ EE  
ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR  
£ \_\_\_\_\_ KIT REF \_\_\_\_\_  
CHEQUE NO \_\_\_\_\_

PHONE YOUR ORDER WITH  
SEND ONLY SAE IF BROCHURE IS REQUIRED



BRANDEADING BRITISH ELECTRONICS  
CUT OUT THE COUPON NOW!

PRICES INC. VAT POSTAGE & PACKING

# Everyday News

## PERSONAL PAYPHONE

**M**ANY small businesses would like to provide their customers or staff with a payphone service, but the current wall-mounted model may not suit their particular situation. Now, British Telecom have introduced a push-button payphone only nine inches square and seven inches high and weighing less than 7lb that also doubles as a private phone.

Called the Payphone 100, it can be left permanently coin-operated or, at the turn of a key, switched from a payphone to an ordinary phone and back again. When used as a payphone it accepts 2p, 5p, 10p and 50p coins and will refund unused coins at the end of a call.

The table-top payphone is particularly useful for small businesses who want to provide their customers or visitors with the use of a phone but who do not want to give away free calls. Typical users will be hairdressers, pubs, clubs, wine bars, garages, surgeries and shops. Another possibility could be for the person who has a "friendly neighbour".

Designed for use with the new socket system, it is ideal for those businesses who have only one telephone line. A single payphone allows this line to be used for both private and customer use.

When operating in the payphone mode, local trunk and international calls can be made but calls to or via the operator, except for 999 emergency calls, are not possible. When switched to "private" use all services are available.

The annual Leeds Electronics Show will take place from 5 to 7 July in the Departments of Electrical and Electronic Engineering, University of Leeds.

### Training for the Micro

An advanced microprocessor training course, that can be used for "distance learning", has been developed at the IBA's Harman Engineering Training College, Seaton, Devon. The initial requirement was to provide theoretical and practical training for field engineers maintaining the microprocessor-based transmission equipment used in the new Regional Operations Centres and Channel 4 transmitting installations, including control and telemetry systems.

The programme is broken down into three stages: Microprocessor basics using a modified version of the M6800 D2 kit. Digital diagnostics for broadcast systems, including signature analysis. High-level language programming, using the Apple II microcomputer.

Renters of the Payphone 100 will be billed for calls at the normal rate but people using the phone will have to insert coins at the higher coinbox rate. The renter retains the extra cash.

The user is warned of "credit expiry" by a flashing l.e.d. and a warning tone. A cash-box full sensor helps to prevent jammed coin slots.



### Inventer's Workshop

In a bid to attract local inventors with new ideas into the field of microelectronics, the Microelectronics Applications Research Institute (MARI), Newcastle upon Tyne, has set up a Microelectronics Innovation Workshop.

The innovation centre supports the use of the workshop and individuals are closely supervised by MARI staff. It is claimed that this facility is unique in that individuals receive assistance at the early stages of the invention which, at present, no other organisation provides. People can experiment and test their ideas without having to set up their own expensive production facilities, and at the same time attract customers or backers.

### Japanese Buy British

Logic analysers made by British instrumentation specialists, Thandar Electronics, are being exported to Japan.

The initial order, worth £100,000, is claimed to represent a classic "reverse technology coup" for the St Ives, Huntingdon-based company which exports over 50 per cent of its output.



### SHIP-SHAPE

A contract to provide a combined radar and electro-optic weapons control system, to be installed in one of the Royal New Zealand Navy's Leander Class Frigates, has been awarded to RCA Missile and Surface Radar.

This contract is part of plans to modernise and improve the Royal New Zealand Navy ships capabilities.

In addition to weapons control, the radar can be used for navigation, surveillance, aircraft control, drone control, and in search and rescue missions.

### CLUB SPOT

The ACC National Prestel Committee, acting in its role as the national body representing the computer hobbyist, has linked up with Micronet 800 to create Club Spot 800, a new service to involve ordinary computer enthusiasts in Prestel editing.

Club Spot 800 will contain news and ideas about micros and micro clubs, plus programs, sales and wants, and general views.

To introduce the new service a conference is being held on February 26, starting at 2pm, at the Institute of Grocery Distribution, Grange Lane, Lechmore Heath, Watford. Registration is free in advance or £5 for those turning up on the day (subject to space being available).

For more details contact: R. Steele, ACC National Prestel Committee Secretary, St John's College, Oxford OX1 3JP.

● The Pontefract & District Amateur Radio Society is holding its annual "Component Fair" on Sunday, March 13, at the Carleton Grange Community Centre, Carleton, Pontefract. Time: 11am to 4.30pm (10.30am for the disabled).

For more information contact: Mr P. N. Butterfield, G4AAQ, Pontefract & District ARS, 43 Lynwood Crescent, Pontefract WF8 3QT.



## —ANALYSIS—

### BELTS AND BRACES

When the first experimental communications satellites, *Telstar* and *Relay*, flew into orbit in 1962 many experts forecasted that the days of submarine cable in international traffic were numbered. When, three years later, *Early Bird* was launched into geostationary orbit 23,000 miles out in space earlier fears seemed confirmed. The submarine cable was doomed.

What a pity, we thought, so soon after the big technological breakthrough in 1956, the year when repeater technology had improved to the point when it was possible to use telephony by cable across the Atlantic Ocean, 90 years after the laying of the first successful transatlantic telegraph cable.

And yet here we are in 1983, two decades after *Telstar*, with more submarine cables than ever and new ones being laid on the ocean beds every year. What the experts didn't see was that a mature technology was still capable of "stretch". Or that new, however exciting at first sight, is not necessarily better or even cheaper.

Two main developments saved the submarine cable from extinction. One was the development of solid-state wide-band repeaters which enabled many more simultaneous telephone conversations. Thus, in a single decade, cost per telephone channel fell by a factor of 20. The other was the phenomenal growth of world telecommunications traffic now shared by both cable and satellite.

A political factor, not to be ignored, is that communications satellites are vulnerable to destruction by killer satellites which, for all we know, may already be deployed ready for action. Safety lies in both belts and braces to keep our communications trousers up, with terrestrial h.f. radio as an emergency piece of string in our pocket should belts and braces be shot away.

While cable has not only miraculously survived but actually flourished it is to have a change of character. Next year a UK-Netherlands cable will be completed at a cost of £85 million. It will carry 4200 simultaneous telephone conversations to bring the southern North Sea network to a total capacity of some 14,000 circuits. It will be the most up-to-date in the world.

But it is also expected to be the last of its type to find a land-fall in the UK, using analogue speech over wires. All subsequent submarine cables, say British Telecom, are being planned to use digital speech transmitted through optical fibre. This doesn't mean a threat to satellites. Both systems are needed and can live happily side-by-side, belted and braced in mutual support.

Brian G. Peck

### INFORMATION DEGREE

British Telecom is to help two Universities produce information technology experts who will run the advanced telecommunications systems of tomorrow.

In partnership with the Universities of Aston and York, British Telecom will develop new degree courses for training 60 students to become electronic engineers with skills in telecommunications and computing.

British Telecom will pay the Universities £100,000 a year for new equipment and additional teaching staff. This support will be guaranteed for five years.

Most of the places on the courses will go to school-leavers with good "A" level grades, but some may be given to suitably qualified technicians already in Telecom's employment. The new courses will begin in 1984.

### Lord of the Spectrum

*The Hobbit*, a full-colour adventure simulation based on J. R. R. Tolkien's fantasy land, is amongst new software for the ZX Spectrum and ZX81 personal computers announced by Sinclair Research.

The player assumes the role of Bilbo and undertakes a series of adventures in which he will meet and interact with all the novel's other leading characters.

Depending on his decisions each game will develop differently.

Compiled by Melbourne House to use the full potential of the 48K Spectrum, features include original artist-designed graphics and a built-in 500 word "inglish" vocabulary to instruct the computer. The package, price £14.95, comes complete with a copy of the novel.

### JUST THE TICKET

Government approval of British Rail's plans to invest £21 million in new ticket issuing machines will soon bring BR's ticket offices into the micro age. Up to £17 million of the investment is for a new all-purpose ticket issuing system and the remaining £4 million is for PORTIS, a portable version of the main system for use by guards on pay trains.

Subject to satisfactory evaluation of the prototypes, the new machines should come into operation in mid-1984 and be fully established by the middle of 1986.

### ORIC GOES INTO PRODUCTION

A new computer named Oric I has just gone into mass production. Over 250,000 of these machines are expected to be sold in its first year. Its market will be that at present enjoyed by the ZX Spectrum and will be the first competitor to a Sinclair computer.

Based on our impressions of a pre-production model we received, the company responsible for the Oric, **Oric Products International Ltd.** have a machine to be proud of in both appearance and performance.

The computer is equipped with a unique type of keyboard with space bar forming one of the 57 positive action keys on a qwerty arrangement, extensive colour, music and sound effects capabilities.

There is an r.g.b. output as well as u.h.f. The cassette tape in/out runs at 2400 Baud (!!!). There is access to the bus at the rear of the computer and an output suitable for driving a Centronics-type interface. Available with 16K and 48K RAM. A **Technical Review of Oric I** will appear shortly in EE.



# — EPROM — PROGRAMMER FOR THE ACORN ATOM



## PART TWO

BY D. C. GRINDROD

**T**HE second and final part of this project deals with the construction, software and testing.

### CIRCUIT BOARDS

Two circuit boards are used in the construction of the Eprom Programmer, one to hold the power supply components and the other for the EPROM socket and d.i.l. connection sockets for connecting to the Atom.

Begin with the power supply board, this is shown in Fig. 3. The layout of the components on the topside is shown together with the breaks to be made on the underside. The prototype used a p.c.b. mounting type transformer. If this is not available, a chassis mounting type may be used, suitably positioned on the case with its leads connected to T1 fixing location as shown.

Make the required breaks in the copper strips and then solder the components in place as shown in Fig. 3. The leads on the i.c.s need to be formed to fit the board.

A small piece of adhesive paper stuck to the board should be used to identify the pins on PL6. If the voltages become transposed, then the EPROM would become permanently damaged.

When you are satisfied that all components are correctly wired up the power supply board may be tested. Temporarily

connect a mains cable and plug across the primary of T1. Set VR2 to its midway position.

Fix a length of 4-way ribbon cable to SK5. Label the positions of the individual sockets in SK5: 0V, 5V, 25V and B as appropriate. Plug into PL6 on the board and with a voltmeter, check that the +5V supply is present. It may vary a little from +5V but should never exceed 5.25V else the EPROM will become damaged.

The 25V supply at this time should read between 15 and 30 volts. Adjust VR2 until the reading is 25 volts, exactly. Next adjust VR1 until the voltage at B is about 22 volts with respect to the 0V rail. It may be trimmed in later.

Since the 7805 regulator incurs a 20V drop it will get hot. If the Eprom Programmer is expected to be in use for prolonged periods at a time the use of a heatsink is recommended or use a reduced secondary tapping such as 9V.


The topboard connects ports A, B and C to the EPROM socket and control switches.

Dual-in-line sockets were used for ports A and B due to their cheapness and reliability. A standard 5-way 270° DIN socket was used for port C. There is no reason why a different connector system could not be used.

The topboard is shown in Fig. 4. It has been drawn as in the prototype but a square piece of stripboard could be used.

In the prototype the SK5 was a 24-pin Zero Insertion Force (z.i.f.) socket. As its name implies it exerts no force on the pins of the EPROM being programmed or read. It drops into holes in the socket and moving the lever to a horizontal position causes the socket contacts to grip the EPROM pins. Move the lever to a vertical position to release the grip and allow the EPROM to be removed.

The z.i.f. socket was plugged into a low profile 24-pin socket soldered to the board, but it may be soldered to the board direct if desired.

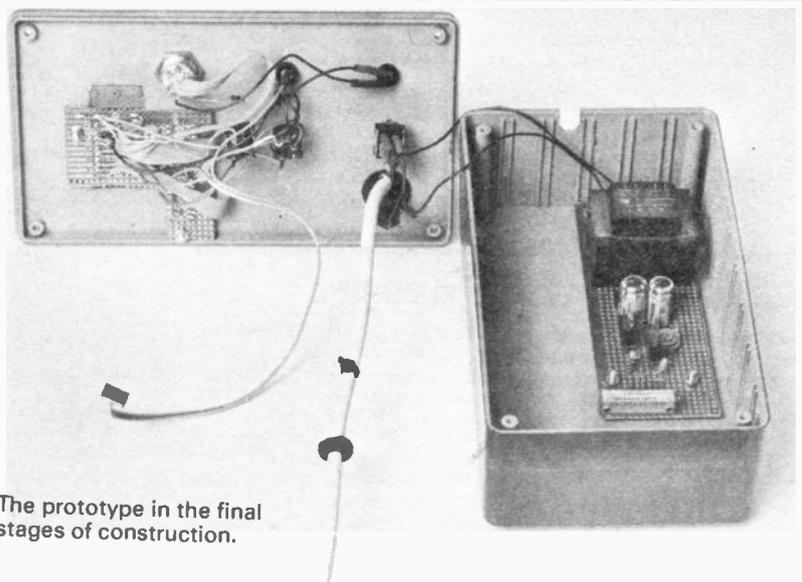

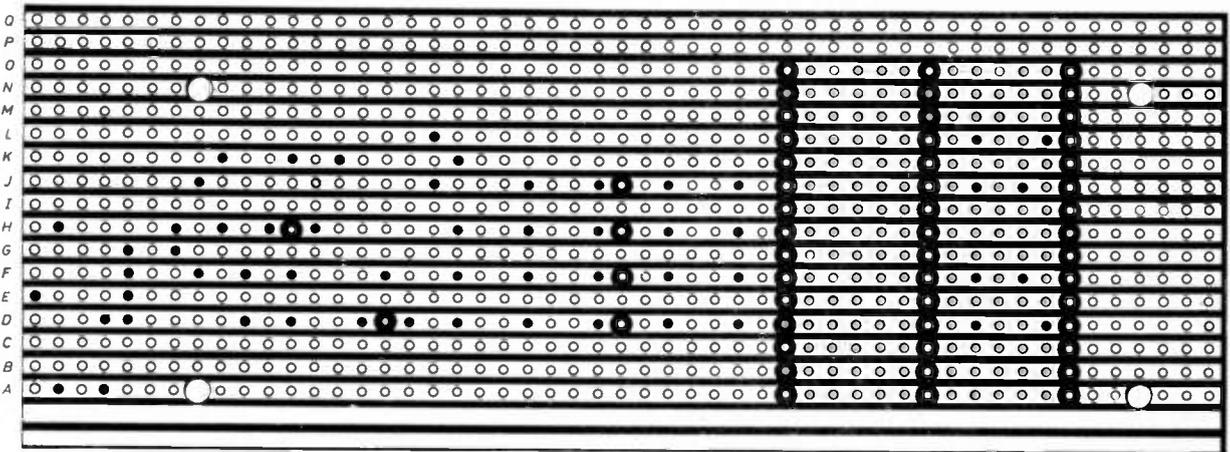
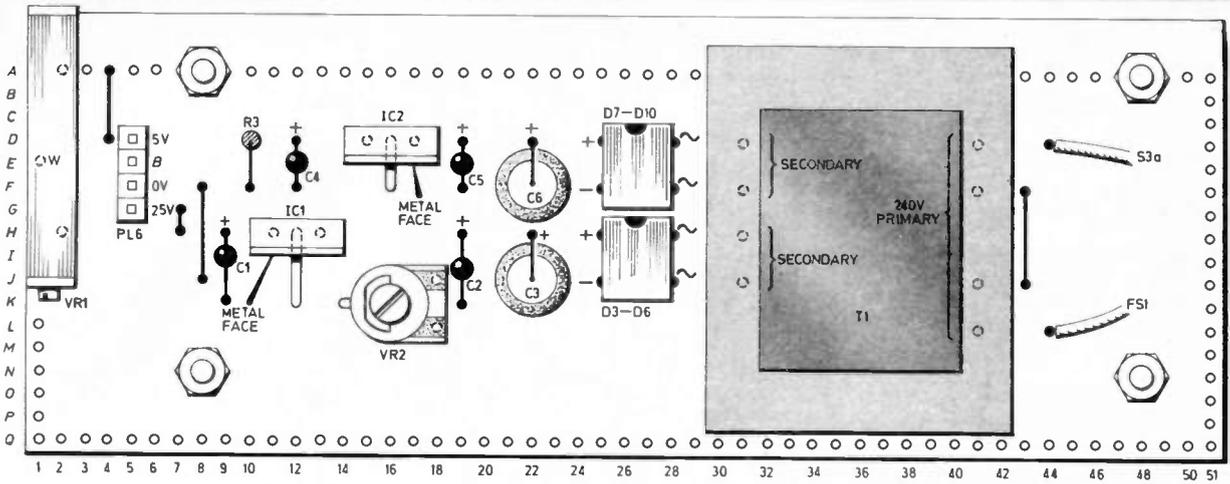


Fig. 3. The layout of the components for the power supply section of the Eprom Programmer and the breaks to be made on the copper side of the board, with drilling details.



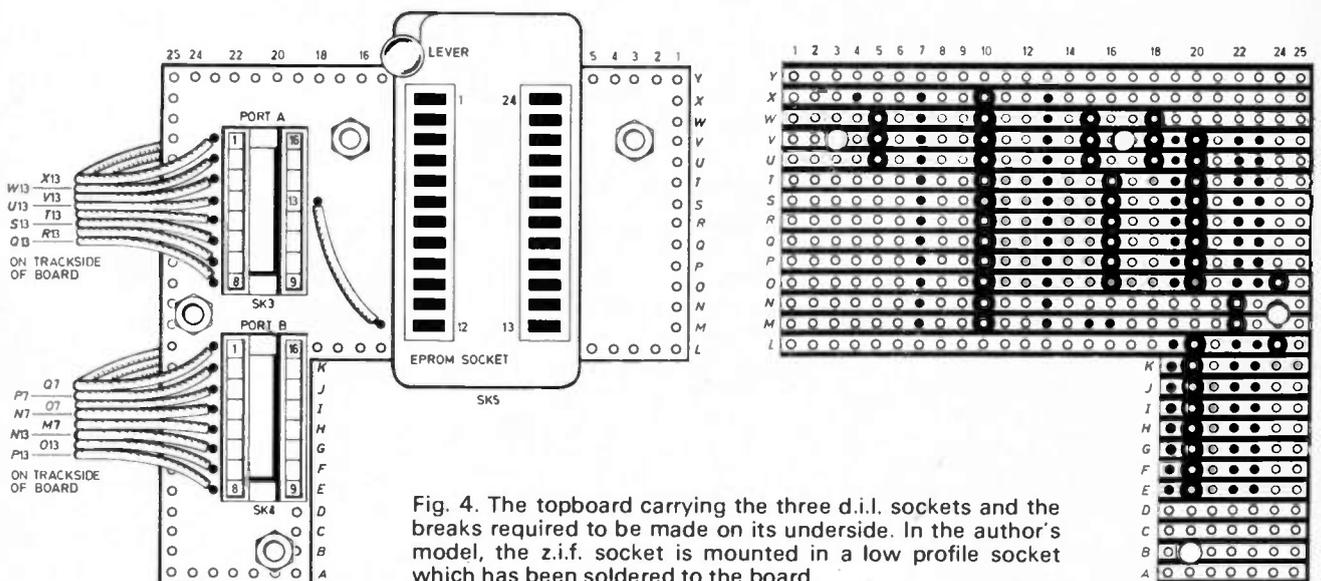


Fig. 4. The topboard carrying the three d.i.l. sockets and the breaks required to be made on its underside. In the author's model, the z.i.f. socket is mounted in a low profile socket which has been soldered to the board.

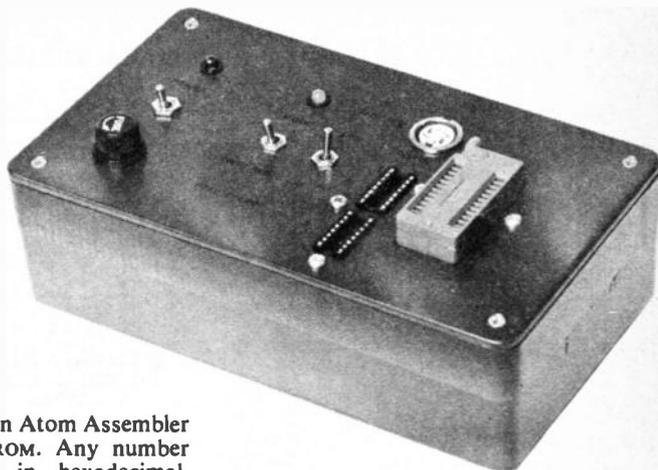

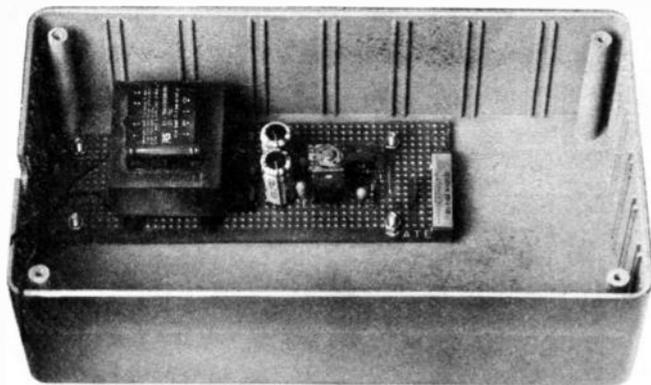

match with the socket on the Programmer. Full pinning details are provided in Fig. 2 to allow these leads to be constructed.

## SETTING UP

The power supply board will not at this stage be mounted in the case. After all interconnections have been made check that there are no solder bridges between adjacent tracks on the upper circuit board.

Next check for continuity between the EPROM socket SK5 and the input sockets, SK2, SK3 and SK4. Check the routes for each position of S1. Check also for continuity of the supply lines from SK6 to the SK5 positions pin 12, 21 and 24, for all combinations of S1 and S2. Remember that A11 floats for 2K EPROMs and that CB2 is on pin 18 for 2K types and pin 20 for 4K types.

Plug SK6 into PL6, plug the unit into the mains and switch on. The power on i.e.d. D2 should light up. The bi-coloured i.e.d. should be lit either red or green according to the setting of S2. Operate S2 and adjust VR1 until both green and red are of equal brightness. Check that the +5V rail is still within limits as VR1 does lift its level by 0.1V or so. If all is well, switch off at the mains and secure in the case.

Switch on again and check the power supply pins on SK5. You should read 5V (5.25V max.) between pins 24 and 12, and 25V between pins 21 and 12 for S2 in PROG mode and 5V when in the READ mode.

A final check should be made using an ohmmeter between adjacent pins on SK5. Shorted tracks on the data or address busses could cause the 6522 (VIA) or 8255 to source too much current and possibly become damaged.

It is good practice to leave the MODE switch in the READ position until the program wants it changed. This prevents any accidental programming by erroneous port values before they are initialised.

## SOFTWARE

The software for the Eprom Programmer is in two parts: Program A, the control program in Basic for programming the EPROM; and Program B, a machine

code program written in Atom Assembler form to read the EPROM. Any number prefixed by "£" is in hexadecimal. Characters in lower-case represent inverse video characters.

## TESTING

Connect the Eprom Programmer to the Atom and switch on the latter. The computer should function normally. Turn on the Programmer.

First of all load the byte £AA into RAM at say £8200, then enter the Basic control program, Program A. Set mode switch to PROG and run the program without an EPROM in place. When asked for EPROM start and end address, type in 00F. After "PROGRAMMING COMPLETE" message is received, measure address bus and data bus voltage levels at SK5. The voltage level from D0 to D7 should alternatively read 0V and 5V or very near these values. A0 to A3 should read 5V and the remaining address lines, 0V. If not, find out why not before proceeding.

With the Programmer turned off, insert an EPROM. Set S2 to READ S1 to appropriate size and then switch on.

Load a small program into RAM at say £8200 then enter Program A. Now run the program and follow the instructions. On completion, remember to set mode switch to READ. Enter Program B and run it to get the program assembled.

As mentioned earlier the variables are passed to the machine code routine via the integer variables A, B and C.

A = EPROM start address

B = RAM start address

C = EPROM end address

If we want to load the EPROM contents into RAM at say £8200 then we type:

A=0;B£8200;C=end address of eprom\*; LINK £2890

followed by return. This address is given by the Basic control program.

The cursor will reappear almost instantly. (The execution times are 45µs (2K) 165µs (4K).) To check this set TOP (?18=£82) and type E.; RUN. If all is well then save the machine code on tape thus:

\*SAVE "EPROM READ" 2890 28DF

(Left). Early stage of assembly. Power supply board in position in base of case. (Above). The completed unit.

A2	CO	A0	00	A9	FF	8E	0C
88	8C	02	88	8D	03	88	AE
3D	03	AC	3E	03	8E	02	B0
84	81	86	83	AE	22	03	AC
23	03	A9	00	85	80	8E	01
B8	AD	00	88	91	80	AD	3F
03	C5	83	D0	05	EC	24	03
FO	14	E8	C8	E0	00	D0	05
EE	02	B0	E6	83	C0	00	D0
DD	E6	81	18	90	D8	60	

Hex dump of the program.

Table 2: Allocation of ports

PORT	ADDRESS	USE
PORT A	£8800	ADDRESS LINES A0 TO A7
PORT B	£B801	DATA BUS TO/ FROM EPROM
PORT C	£B002	ADDRESS LINES A8 TO A11

## CONCLUSION

This article has outlined the essentials of programming EPROMs and reading their contents. If more serious applications are required the machine code routine could be modified to be called by the burning program, and compare memory and EPROM for verification by changing the STA instruction in line 100 to a CMP instruction and writing an error routine for mismatch of contents.

Erasure of the EPROM is achieved by exposure to ultraviolet light of wavelength 2537°A with minimum integrated dose of 15W/sec/cm<sup>-2</sup>.

The author found an 8W Sylvania germicidal lamp at 2cm a suitable eraser. Erasure takes about 15 minutes. In the erased state each EPROM location contains 255. □

# RADIO WORLD

By Pat Hawker, G3VA

## The Electronics Epoch

The development of radio and electronics over the past 100 years has had a profound effect on everyday life, though I am not sure that I go along with those who say that information technology will prove to be the coming of the second industrial revolution.

Despite the impact of electronics on our whole way of life—for better or for worse—the subject has not been very well served by the historians. There are few books that treat the subject analytically and dispassionately and too many that are concerned with claiming credit for particular persons and countries.

Baird did not “invent” television. Marconi, although he himself invented very little, still has the best claim to have developed radio communication despite the, in some ways, valid claims on behalf of Popov, Loomis, Tesla, Hughes, Jackson and others.

Watson-Watt certainly developed radar in the UK, but there were others working on similar lines in other countries, and it can be argued that the greatest British contribution was the 1940 development at the University of Birmingham by H. A. H. Boot and J. T. Randall of the cavity magnetron as a high-power generator of centimetric waves.

However, even this device owed something to the arrival in England, in May 1940, of the French scientist Maurice Ponte who brought across the Channel his resonating segment magnetrons which the British team recognised as having saved them six months of work.

## International Help

The need for international co-operation on the writing of scientific and technical history has been brought home to me by receiving a much-appreciated copy of the magnificently-produced book “The Electronic Epoch”. This has been written by the talented Elizabeth Antebi, a writer and producer with French broadcasting, supported by an impressive international team of scientific advisers. The UK is represented by Dr William Gosling, formerly Professor at Bath University and now research director of Plessey.

This large, heavily-illustrated book, printed in Japan, with the English-language version published by the Van Nostrand Reinhold Company, must be the first time that a serious attempt has been made to produce an international synthesis of the whole electronic epoch in both words and pictures. Subjects covered include communications, television, consumer elec-

tronics, medical electronics, radar and radio navigation.

Elizabeth Antebi has gone to enormous trouble to collect a vast number of historical photographs and to ensure that the text comes at least as close to historical truth as is possible in an industry where “not invented here” is still too often a reason for condemning new technology.

## Electronic Umpiring

This year has seen the first live television transmission of a Test Match direct from Australia though once again the midnight start emphasised the unsolvable problem of large time differences. But the recent Test series also underlined the problem presented by instant slow-motion replay on television where the audience can see all-too-clearly that umpires sometimes make mistakes.

Clearly the ability of television to undermine confidence in umpiring decisions is something that needs to be considered

## Crystal-Ball Gazing

If at times historians get things wrong so do those who attempt to predict the future of developing technology. I have been amused to discover from various compilations (including R. L. Weber’s “A random walk in science”, published by The Institute of Physics) some predictions that the experts concerned must have come to wish they had never made:

“There is no plea which will justify the use of high-tension and alternating currents, either in a scientific or a commercial sense . . . I can see no justification for the introduction of a system which has no element of permanency and every element of danger to life and property”—Thomas Edison, 1889, in advocating d.c. mains.

“As far as sinking a ship with a bomb is concerned, you just can’t do it”—US Rear-Admiral Clark Woodward (1939) on bombing from aircraft.

“Wireless is totally unsuited for war; the enemy could either hear all conversations, or could jam transmissions so nothing can be heard”—an earlier American rear-admiral in 1903.

“That is the biggest fool thing we have ever done. The bomb will never go off, and I speak

seriously. In tennis one has seen the growing tendency to question the judgement of linesmen, although this has not been entirely solved by introducing a degree of electronic instrumentation. Yet for horse-racing few would dispute the value of the camera for close finishes—and the value of the special television recordings when objections are raised.

## Action Replay

There would seem little logical reason why in cricket, the umpire in cases of doubt should not ask a clubhouse “referee” to advise him on the basis of an action replay, using perhaps a pocket radio. To prevent too many hold-ups to the game some rules would have to be worked out on how often, or just when, this facility could be used, otherwise we might have more attempts to intimidate umpires by players! But it seems absurd if the television audience can see so clearly that decisions made in good faith by the umpires are wrong.

as an expert on explosives”—yet another US admiral: William Leahy to President Truman, 1945, on the atomic bomb.

When in 1913, Lee de Forest, who first put a grid into a diode valve, was charged with fraudulently using the US mail to persuade the public to invest in his company, the District Attorney claimed: “De Forest has said . . . it would be possible to transmit the human voice across the Atlantic before many years. Based on these absurd and deliberately misleading statements, the misguided public has been persuaded to buy stock”. It was only two years later, 1915, that the first radio transmission of speech across the Atlantic was accomplished!

On the other hand, it is easy to be a little over-confident. The French engineer Edouard Belin, in January 1926, said: “I am certain that before the end of 1926 an orator speaking into the microphone will have both his voice and his image transmitted simultaneously all over the globe”. He was roughly 40 years out—the first genuine world programme by satellite on television was in 1965.

The Chinese have a proverb that the fish are the last to discover water; and Nicholas Butler once said: “An expert is one who knows more and more about less and less”.

For a detailed booklet on remote control — send us 30p and S.A.E. (6" x 9") today.

### HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

**TDR300K Remote Control £14.30**

MK6 Dimmer Transmitter for above **£ 4.20**

**TD300K Touchdimmer £ 7.00**

**TDE/K Extension kit for 2-way switching for TD300K £ 2.00**

**LD300K Rotary Controlled Dimmer £ 3.50**



### DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.



Price **£15.50**

### 3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK102 **£5.00**

### XK113 MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. **£5.00**

### COMPONENT PACKS

- PACK 1 650 Resistors 47 ohm to 10 Mohm — 10 per value **£4.00**
- PACK 2 40 x 16V Electrolytic Capacitors 10µF to 1000µF — 5 per value **£3.25**
- PACK 3 60 Polyester Capacitors 0.01 to 1µF/250V — 5 per value **£5.55**
- PACK 4 45 Sub-miniature Presets 100 ohm to 1 Mohm — 5 per value **£2.90**
- PACK 5 30 Low Profile IC Sockets 8, 14 and 16 — pin — 10 of each **£2.40**
- PACK 6 25 Red LEDs (5mm dia.) **£1.25**

### MINI KITS

**MK1 TEMPERATURE CONTROLLER/THERMOSTAT**  
Uses LM3911 IC to sense temperature (80°C max.) and triac to switch heater. 1KW **£4.80**

**MK2 Solid State Relay**  
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. **£2.80**

**MK3 BAR/DOT DISPLAY**  
Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.50**

**MK4 PROPORTIONAL TEMPERATURE CONTROLLER**  
Based on the SL444t zero voltage switch, this kit may be wired to form a "burst fire" power controller, enabling the temperature of an enclosure to be maintained to within 0.5°C. Max. load 3KW **£5.55**

**MK5 MAINS TIMER**  
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 mins. to 35 hrs. Longer or shorter periods may be realised by minor component changes. Max. load 1KW. **£4.50**

### LCD 3 1/2 DIGIT MULTIMETER

16 ranges including DC voltage (200 mv-1000 v) and AC voltage, DC current (200 mA-10 A) and resistance (0-2 M) — NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x80x31 mm. Requires PP3 9v battery. Test leads included **ONLY £29.00**

### ELECTRONIC LOCK KIT XK101

This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40uA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £10.50**

Electric lock mechanisms for use with latch locks and above kit **£13.50**

### DISCO LIGHTING KITS

**DL1000K**  
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£14.60**

**DL2100K**  
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1  
Allowing audio ("beat") —light response. **60p**

**DL3000K**  
This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust — simply connect to mains supply & lamps. (1Kw/Channel) **Only £11.95**

Have you got our **FREE ORANGE CATALOGUE** yet? NO?! Send S.A.E. 6" x 9" TODAY!!

It's packed with details of all our KITS plus large range of SEMICONDUCTORS, including CMOS, LS TTL, linear, microprocessors and memories, full range of LEDs, capacitors, resistors, hardware, relays, switches etc.

We also stock VERO and Antex products as well as books from Texas Instruments, Babani and Elektor.

**ALL AT VERY COMPETITIVE PRICES.**

**ORDERING IS EVEN EASIER — JUST RING THE NUMBER YOU CAN'T FORGET FOR PRICES YOU CAN'T RESIST.**

**5-6-7 8-9-10**

and give us your Access or Barclaycard No. or write enclosing cheque or postal order. Official orders accepted from schools, etc.

**Answering service evngs & weekends**

**ALL PRICES EXCLUDE VAT**

**EE**

Add 55p postage & packing +15% VAT to total Overseas Customers;  
Add £2.50 (Europe), £6.00 (elsewhere) for p&p  
Send S.A.E. for further STOCK DETAILS.  
Goods by return subject to availability.  
9am to 5pm (Mon to Fri)  
10am to 4pm (Sat)

**FAST SERVICE · TOP QUALITY · LOW LOW PRICES**

No circuit is complete without a call to —




**TK ELECTRONICS**

11 Boston Road  
London W7 3SJ



TEL: 01-567 8910 ORDERS  
01-579 9784 ENQUIRIES  
01-579 2842 TECHNICAL AFTER 3PM

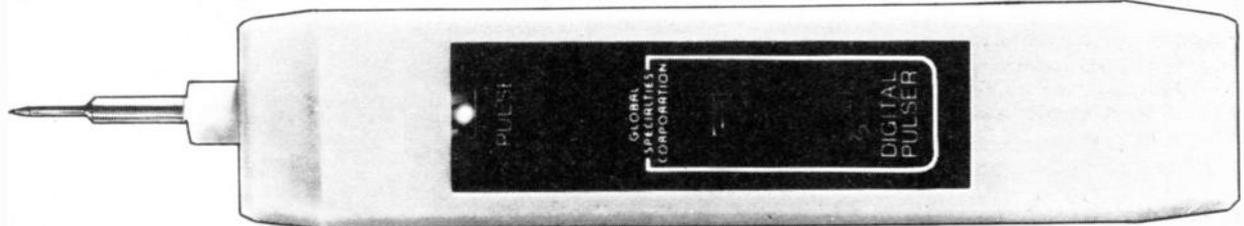
**Do you know anybody who can build a Digital Pulser for only £18.00? \***



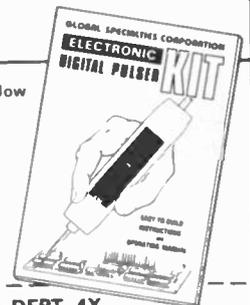**The answer is yes — its YOU!**

With GSC's new DPK-1 kit, you can build a sophisticated portable test instrument for stimulus/response testing. It automatically delivers just the right signal for whichever logic family you're using — and it's equally suited to single pulses or pulse trains at a frequency of 100 per second. The fully featured DPK-1 kit includes all components, leads, circuit board and case — and is supplied complete with detailed assembly instructions and an operating manual. Get rid of your digital hang-ups; send off for a DPK-1 straight away.

Easy to follow Instruction Manual with every Kit



**GLOBAL SPECIALTIES CORPORATION**



**G.S.C. (UK) LIMITED**  
UNIT 1, SHIRE HILL INDUSTRIAL ESTATE  
SAFFRON WALDEN, ESSEX CB11 3AQ  
Telephone: Saffron Walden (0799) 21682  
Telex: 817477

**GLOBAL SPECIALTIES CORPORATION (UK) LIMITED, DEPT. 4X**  
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

<b>DIGITAL PULSER KIT DPK-1</b>	<b>*£22.42</b> (inc. P & P & 15% VAT)	Quantity Reqd.	For FREE catalogue tick box <input type="checkbox"/>
---------------------------------	--	----------------	--

Name \_\_\_\_\_ Address \_\_\_\_\_

I enclose PO/Cheque for £ \_\_\_\_\_ or debit my

Barclaycard/Access/American Express. No. \_\_\_\_\_ exp date \_\_\_\_\_

# Sinclair ZX Spectrum

**16K or 48K RAM...  
full-size moving-  
key keyboard...  
colour and sound...  
high-resolution  
graphics...**

**From only  
£125!**

First, there was the world-beating Sinclair ZX80. The first personal computer for under £100.

Then, the ZX81. With up to 16K RAM available, and the ZX Printer. Giving more power and more flexibility. Together, they've sold over 500,000 so far, to make Sinclair world leaders in personal computing. And the ZX81 remains the ideal low-cost introduction to computing.

Now there's the ZX Spectrum! With up to 48K of RAM. A full-size moving-key keyboard. Vivid colour and sound. High-resolution graphics. And a low price that's unrivalled.

## **Professional power— personal computer price!**

The ZX Spectrum incorporates all the proven features of the ZX81. But its new 16K BASIC ROM dramatically increases your computing power.


You have access to a range of 8 colours for foreground, background and border, together with a sound generator and high-resolution graphics.

You have the facility to support separate data files.

You have a choice of storage capacities (governed by the amount of RAM). 16K of RAM (which you can uprate later to 48K of RAM) or a massive 48K of RAM.

Yet the price of the Spectrum 16K is an amazing £125! Even the popular 48K version costs only £175!

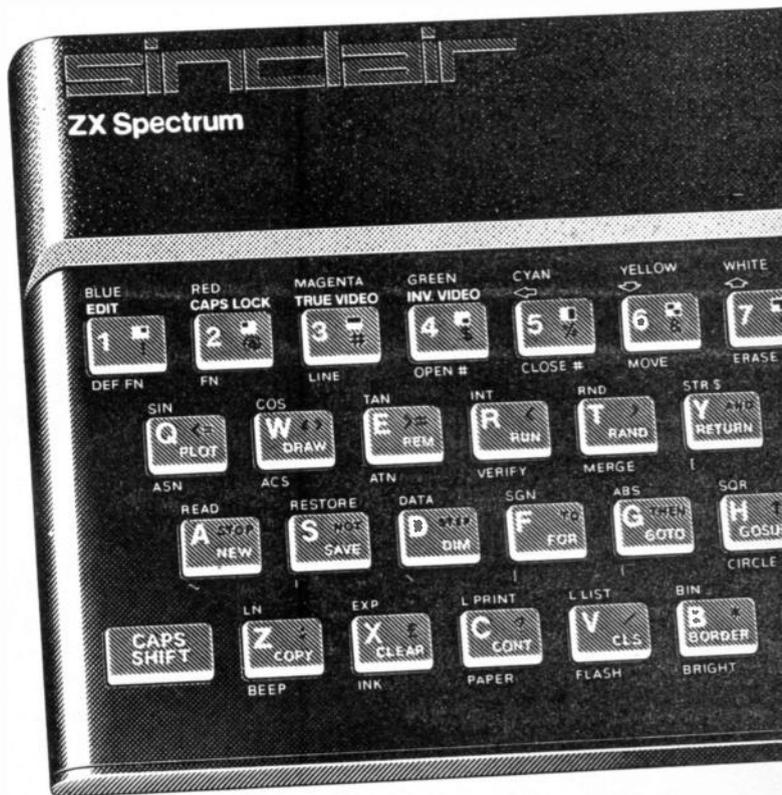You may decide to begin with the 16K version. If so, you can still return it later for an upgrade. The cost? Around £60.



## **Ready to use today, easy to expand tomorrow**

Your ZX Spectrum comes with a mains adaptor and all the necessary leads to connect to most cassette recorders and TVs (colour or black and white).

Employing Sinclair BASIC (now used in over 500,000 computers worldwide) the ZX Spectrum comes complete with two manuals which together represent a detailed course in BASIC programming. Whether you're a beginner or a competent programmer, you'll find them both of immense help. Depending on your computer experience, you'll quickly be moving into the colourful world of ZX Spectrum professional-level computing.

There's no need to stop there. The ZX Printer—available now—is fully compatible with the ZX Spectrum. And later this year there will be Microdrives for massive amounts of extra on-line storage, plus an RS232/network interface board.



## **Key features of the Sinclair ZX Spectrum**

- Full colour—8 colours each for foreground, background and border, plus flashing and brightness-intensity control.
- Sound—BEEP command with variable pitch and duration.
- Massive RAM—16K or 48K.
- Full-size moving-key keyboard—all keys at normal typewriter pitch, with repeat facility on each key.
- High-resolution—256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.
- ASCII character set—with upper- and lower-case characters.
- Teletext-compatible—user software can generate 40 characters per line or other settings.
- High speed LOAD & SAVE—16K in 100 seconds via cassette, with VERIFY & MERGE for programs and separate data files.
- Sinclair 16K extended BASIC—incorporating unique 'one-touch' keyword entry, syntax check, and report codes.

# um



## The ZX Printer - available now

Designed exclusively for use with the Sinclair ZX range of computers, the printer offers ZX Spectrum owners the full ASCII character set - including lower-case characters and high-resolution graphics.

A special feature is COPY which prints out exactly what is on the whole TV screen without the need for further instructions. Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your ZX Spectrum. A roll of paper (65ft long and 4in wide) is supplied, along with full instructions. Further supplies of paper are available in packs of five rolls.



## The ZX Microdrive - coming soon

The new Microdrives, designed especially for the ZX Spectrum, are set to change the face of personal computing by providing mass on-line storage.

Each Microdrive can hold up to 100K bytes using a single interchangeable storage medium.

The transfer rate is 16K bytes per second, with an average access time of 3.5 seconds. And you'll be able to connect up to 8 Microdrives to your Spectrum via the ZX Expansion Module.

A remarkable breakthrough at a remarkable price. The Microdrives will be available in the early part of 1983 for around £50.



## ZX Spectrum software on cassettes - available now

The Spectrum software library is growing every day. Subjects include games, education, and business/household management. Flight Simulation... Chess... Planetoids... History... Inventions... VU-CALC... VU-3D... Club Record Controller... there is something for everyone. And they all make full use of the Spectrum's colour, sound, and graphics capabilities. You'll receive a detailed catalogue with your Spectrum.

## ZX Expansion Module

This module incorporates the three functions of Microdrive controller, local area network, and RS232 interface. Connect it to your Spectrum and you can control up to eight Microdrives, communicate with other computers, and drive a wide range of printers.

The potential is enormous, and the module will be available in the early part of 1983 for around £30.

# sinclair

Sinclair Research Ltd, Stanhope Road, Camberley, Surrey GU15 3PS. Tel: Camberley (0276) 685311.

## How to order your ZX Spectrum

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST - use the no-stamp needed coupon below. You can pay by cheque, postal order, Access,

Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR.

Order

Qty	Item	Code	Item Price £	Total £
	Sinclair ZX Spectrum - 16K RAM version	100	125.00	
	Sinclair ZX Spectrum - 48K RAM version	101	175.00	
	Sinclair ZX Printer	27	59.95	
	Printer paper (pack of 5 rolls)	16	11.95	
	Postage and packing: orders under £100	28	2.95	
	orders over £100	29	4.95	
				Total £

Please tick if you require a VAT receipt

\*I enclose a cheque/postal order payable to Sinclair Research Ltd for £

\*Please charge to my Access/Barclaycard/Trustcard account no.

\*Please delete/complete as applicable

Signature

PLEASE PRINT

Name: Mr/Mrs/Miss

Address

EVE 903

FREEPOST - no stamp needed. Prices apply to UK only. Export prices on application.

CALL IN AND SEE FOR YOURSELF

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

## DIGITAL MULTIMETERS (UK C/P Free)



**HAND HELD**  
 K025C\*13 range 0.2A DC 2 meg ohm £24.95  
 K030C\*26 range 1A AC/DC 20 meg ohm £34.95  
 K055C\*28 range 10A AC/DC 20 meg ohm £39.95  
 6010+ 22 range 10A AC/DC 20 meg ohm £34.40  
 7030+ As 6010 but 0.1% basic £41.30  
 188M 18 range 10A DC 2 meg plus Hfe tester £39.95  
 189M 30 range 10A AC/DC 20 meg plus Hfe tester £69.95

**HAND HELD AUTO RANGE**  
 DMZ350\*21 range 10A AC/DC 20 meg ohm (Miniature) £49.95  
 M030 16 range 0.2A AC/DC 2 meg ohm £41.95  
 M030/B As above plus cont. buzzer £44.50  
 M031 22 range 10A AC/DC 2 meg ohms plus cont. buzzer £58.95



**BENCH MODELS (3 1/2 digit unless stated)**  
 TM353\*27 range LCD 2A AC/DC £86.25  
 TM355\*29 range LED 10A AC/DC £86.25  
 TM351+ 29 range LCD 10A AC/DC £113.85  
 2001 28 range LCD 10A AC/DC plus 5 range Cap. Meter with case £104.00  
 TM451 4 1/2 digit LCD every facility (0.02%) £171.00  
 1503a 4 1/2 digit LCD every facility (0.05%) £171.00  
 1503Ha 0.03% basic version of above £189.00  
 \*Optional carry case £2.95 with free carry case  
 \*Optional carry case £6.84

EDUCATIONAL DISCOUNTS AVAILABLE FOR ALL STOCKS - PLEASE ENQUIRE

## FREQUENCY COUNTERS



**PFM200A** 200 MHz hand held pocket 8 digit LED £67.50  
 B110A 8 digit LED bench 2 ranges 100 MHz £77.00  
 B510B 9 digit LED bench 2 ranges 800 MHz £113.85  
 B000B 8 digit LED 3 ranges 1 GHz £178.00  
 TF040\* 8 digit LCD 40 MHz £128.50  
 TF200\* 8 digit LCD 200 MHz £166.75  
 \* Optional carry case £6.84  
 Prescalers - Extended range of most counters  
 TP600 600 MHz £43.00  
 TP1000 1 GHz £74.00

## SIGNAL GENERATORS



**FUNCTION:** All sine/square/triangle/TTL etc  
 TG100 1 Hz - 100 KHz £90.00  
 TG102 0.2 Hz - 2 MHz £166.75  
**PULSE**  
 TG105 Various facilities: 5 Hz - 5 MHz £97.75  
**AUDIO:** Multiband Sine/Square  
 LAG27 10 Hz to 1 MHz £86.00  
 AG202A 20 Hz to 200 KHz £78.00  
**RF**  
 SG402 100 KHz to 30 MHz £59.95  
 LSG17 100 KHz to 150 MHz £71.00

AUDIO • RF • FUNCTION • PULSE

## ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100m with carry case £63.00

## MULTIMETERS

(UK C/P 65p)  
 Y7206 20k/V 19 range pocket meter £7.95  
**SPECIAL PRICE**  
 CT081 50k/V 21 ranges. Range doubler 10A DC. SPECIAL PRICE £15.95  
 ETC5000/5001 21 ranges. 50k/V. Range doubler. 10A DC. £16.50  
 TMX500 23 ranges 30k/V. 12A DC plus cont. buzzer. £23.95  
 NH56R 20k/V. 22 range pocket £10.95  
 EU102 14 range 2k/V pocket £5.95  
 830A 26 range 30k/V. 10A AC/DC overload protection, etc. £23.95  
 360TR 23 range 100k/V. Large scale 10A AC/DC plus Hfe £36.95  
 AT1020 18 range 20k/V. Deluxe plus Hfe tester £17.50  
 ST303TR 21 range 20k/V plus Hfe tester £16.95

## VARIABLE POWER SUPPLIES

PP241 0/12/24V. 0/1A £35.00  
 PP243 3 amp version £59.95 (UK C/P £1.00)

## DIGITAL THERMOMETER

TM301 LCD -50°C to +75°C with thermocouple £68.43

## AC CLAMP METER

ST300 0/300A: 0/600 VAC. 0/1 Kohm 9 ranges. With carry case (UK C/P 65p) £28.50

## LOGIC PROBES

LP10 10 MHz £28.50  
 LPD076 50 MHz £56.90

## OSCILLOSCOPES



Full specification any model on request. SAE by post.  
**'HM' Series NAMEG: 'SC' THANDAR: 'CS' Series TRIO: '3' Series CRDTECH**  
**SINGLE TRACE**  
 3030 15 MHz 5mv. 95mm tube plus component tester C/P £3.00 £172.50  
 SC110A\* Miniature 10 MHz battery portable. Post free £171.00  
 HM103 15 MHz 2mv. 6 x 7 display plus component tester C/P £3.00 £177.00  
 \* Optional carry case £6.84 AC adaptor £6.69  
 Nicads £12.50  
**DUAL TRACE (UK C/P £4.00)**  
 HM203/4 Dual 20 MHz plus component tester £276.00  
 CS1566A Dual 20 MHz. All facilities £299.00  
 HM204 Dual 20 MHz plus component tester. Sweep delay. £419.75  
**OPTIONAL PROBE KITS**  
 X1 £7.95 X10 £9.45  
 X1 - X10 £10.50 X100 £16.95

STOCKISTS FOR TRIO: NAMEG: CRDTECH: SAFFAN SCOPES. MOST MODELS IN STOCK.

## HIGH VOLTAGE METER

Direct reading 0/40 KV. 20K/Volt. (UK C/P 65p) £18.40

## DIGITAL CAPACITANCE

Q1 1 to 2000 mfd LCD 8 ranges. 0M6013 £57.95 (Carry case £2.95)


## TRANSISTOR TESTER

Direct reading PNP/NPN, etc. TC1 (UK C/P 65p) £21.95

FREE CATALOGUES SEND LARGE SAE (UK 20p)


Order by Post with CHEQUES/ACCESS VISA or via our telephone your orders. All orders despatched within 5 days unless advised.

## PLASTIC CASES

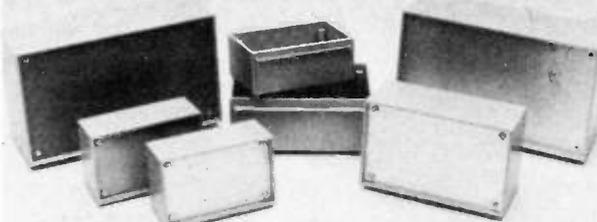

beige cases offer choice of front panels; grey plastic (P), silver plastic (M) and aluminium (A). PCB slots and 10° tilt vertically or desk style.

TYPE	EXTERNAL DIMENSIONS	PRICE EACH		
		P	M	A
10	85 x 60 x 40	0.99	1.16	1.22
20	110 x 75 x 50	1.20	1.49	1.72
30	155 x 95 x 60	2.10	2.51	2.74

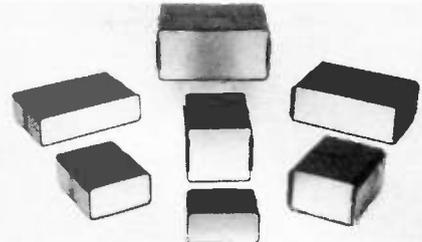


BLACK CASES WITH BLACK AND SILVER END PANELS. PCB BOSSES. TOP SCREWS TO BOTTOM.

TYPE	EXT DIMS	EACH	TYPE	EXT DIMS	EACH
110	115 x 74 x 64	2.47	220	220 x 140 x 64	4.81
115	115 x 140 x 64	2.85	221	220 x 140 x 84	6.53
116	115 x 140 x 84	4.52	222	220 x 140 x 114	7.68
117	115 x 140 x 114	5.38			

Mail Order only. All prices include VAT and P&P. Send large SAE for Catalogue of boxes, knobs, power supplies (from 5A to 150A), controllers and more.

DEPT. EE3, 2 THE WILLOWS, HERSTMONCEUX, East Sussex, BN27 4LE. Tel. 0323 832571.
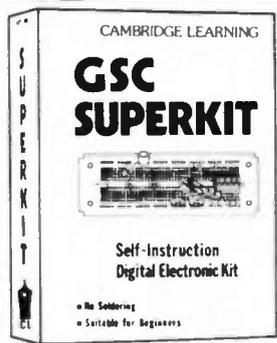
# A PRACTICAL DIGITAL ELECTRONIC KIT FOR LESS THAN £20



SUITABLE FOR BEGINNERS  
 NO SOLDERING!

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains: seven LS TTL integrated circuits, breadboard, LEDs, and all the DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19.90p inc VAT and p&p. This course is for true beginners - the only extra you need is a 4 1/2V battery.

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.

This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Cheque with order to:- Cambridge Learning Limited, Unit 34 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs. PE17 4BR, England. or tel 0480 67446 with credit card details

# Cambridge Learning

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project—you will need to order the instruction reprint at an extra 45p each. Reprints available separately 45p each + p. & p. 45p.

- DOUBLE DICE Jan. 83. £10-82
- ELECTRONIC V/I METER Dec. 82. £11-38
- ZX TAPE CONTROL Nov. 82. £6-48
- PHOTO FINISH Nov. 82. £5-98
- SINE WAVE GEN Oct. 82. £16-65
- G. P. PRE-AMP Oct. 82. £5-64
- LIGHTS ON ALERT Oct. 82. £4-25
- CONTINUITY CHECKER Sept. 82. £4-97
- SOUND SPLITTER Sept. 82. £13-77
- SOUND REMINDER Sept. 82. £3-70
- SCREEN WASH DELAY Sept. 82. £4-48
- INSTRUMENT PRE AMP Aug. 82. £7-02
- TWO TONE DOORBELL ALARM Aug. 82, less case and bell transformer. £8-82
- CB RINGER BLEEPER Aug. 82. £8-47
- BRAKE LIGHT RELAY July 82. £3-30
- 2-WAY INTERCOM July 82. £4-11
- ELECTRONIC PITCH PIPE July 82. £4-91
- REFLEX TESTER July 82. £7-67
- SEAT BELT REMINDER June 82. £3-73
- EGG TIMER June 82. £6-95
- TWO TONE TRAIN HORN WITH REMOTE TRIGGER OPTION May 82. £11-26
- CAR LED VOLTMETER less case, May 82. £2-89
- LIGHTNING CHESSE BUZZER. May 82. £2-89
- V.C.O. SOUND EFFECTS UNIT Apr. 82. £11-56
- CAMERA OR FLASH GUN TRIGGER Mar. 82. £12-41 less tripod bushes.
- POCKET TIMER Mar. 82. £3-71
- GUITAR TUNER Mar. 82. £15-63
- CAR OVERHEATING ALARM. Feb. 82. £9-61
- SIMPLE STABILISED POWER SUPPLY. Jan. 82. £24-58
- MINI EGG TIMER. Jan. 82. £3-94
- SIREN MODULE. Jan. 82. less speaker. £5-57
- MODEL TRAIN CHUFFER. Jan. 82. £8-27
- SQUARE SIX. Dec. 81. £4-70
- GUITAR ADAPTOR. Dec. 81. £3-76
- REACTION METER. Dec. 81. £17-55
- ELECTRONIC IGNITION. Nov. 81. £25-98
- SIMPLE INFRA RED REMOTE CONTROL. Nov. 81. £16-98
- PRESSURE MAT TRIGGER ALARM. Nov. 81. £8-27
- EXPERIMENTER CRYSTAL SET. Nov. 81. Less aerial. £5-99
- Headphones. £2-98 extra.
- CAPACITANCE METER. Oct. 81. £23-51
- SUSTAIN UNIT. Oct. 81. £12-76
- 'POPULAR DESIGNS'. Oct. 81. £4-95
- TAPE NOISE LIMITOR. £4-57
- HEADS AND TAILS GAME. £2-52
- CONTINUITY TESTER. £3-95
- PHOTO FLASH SLAVE. £3-46
- FIZZ BOX. £7-29
- OPTO ALARM. £5-78
- SOIL MOISTURE UNIT. £5-61
- ICE ALARM. £7-89
- 0-12V POWER SUPPLY. Sept. 81. £17-98
- CMOS CAR SECURITY ALARM. Sept. 81. £3-08
- CMOS DIE. Sept. 81. £7-99
- LED SANDGLASS. Aug. 81. £8-53
- CMOS METRONOME. Aug. 81. £8-23
- COMBINATION LOCK. July 81. Less case. £19-58
- BURGLAR ALARM SYSTEM. June 81 less bell, loop & Mic's. £40-99
- TAPE AUTO START. June 81. £12-70
- LIGHTS REMINDER AND IGNITION LOCATOR E.E. May 81. £5-66
- SOIL MOISTURE INDICATOR E.E. May 81. £4-09
- GUITAR HEADPHONE AMPLIFIER E.E. May 81. £4-23
- PHONE BELL REPEATER / BABY ALARM E.E. May 81. £5-66
- INTERCOM. April 81. £22-23
- SIMPLE TRANSISTOR & DIODE

- TESTERS. Mar. 81. Ohm meter version £2-02. Led version £2-73
- MINI SIREN. Mar. 81. £8-04
- LED DICE. Mar. 81. £8-44
- LED FLASHER. Mar. 81. £4-29
- MODULATED TONE DOORBELL. Mar. 81. £8-64
- BENCH POWER SUPPLY. Mar. 81. £53-47
- THREE CHANNEL STEREO MIXER. Feb. 81. £18-69
- SIGNAL TRACER. Feb. 81. £8-17 less probe
- NI-Cd BATTERY CHARGER. Feb. 81. £13-61
- ULTRASONIC INTRUDER DETECTOR. Jan. 81 less case. £53-47
- 2 NOTE OOR CHIME. Dec. 80. £18-32
- LIVE WIRE GAME. Dec. 80. £11-78
- GUITAR PRACTICE A MPLIFIER. Nov. 80. £12-82 less case. Standard case £3-88. High quality case £4-33
- SOUND TO LIGHT. Nov. 80. 3 channel. £21-34
- TRANSISTOR TESTER. Nov. 80. £11-63 inc. test leads.
- AUDIO EFFECTS UNIT FOR WEIRD SOUNDS. Oct. 80. £13-11
- BICYCLE ALARM. Oct. 80. £18-35 less mounting brackets.
- IRON HEAT CONTROL. Oct. 80. £5-06
- TTL LOGIC PROBE. Sept. 80. £5-18
- ZENER DIODE TESTER. June 80. £8-06
- 4 STATION RADIO. May 80. £18-29 less case.
- LIGHTS WARNING SYSTEM. May 80. £4-68
- BATTERY VOLTAGE MONITOR. May 80. £5-18
- CABLE & PIPE LOCATOR. Mar. 80. £4-11 less coil former.
- KITCHEN TIMER. Mar. 80. £14-65
- STEREO HEADPHONE AMPLIFIER. Mar. 80. £18-15
- MICRO MUSIC BOX. Feb. 80. £16-26
- Grey Case £3-99 extra.
- SIMPLE SHORT WAVE RECEIVER. Feb. 80. £25-06
- Headphones £2-06
- SLIDE/TAPE SYNCHRONISER. Feb. 80. £12-30
- MORSE PRACTICE OSCILLATOR. Feb. 80. £4-62
- SPRING LINE REVERB. UNIT. Jan. 80. £25-86
- UNIBOARD BURGLAR ALARM. Dec. 79. £8-93
- BABY ALARM. Nov. 79. £9-60
- CHASER LIGHTS. Sept. 79. £23-40
- SIMPLE TRANSISTOR TESTER. Sept. 79. £7-30
- DARKROOM TIMER. July 79. £2-89
- ELECTRONIC CANARY. June 79. £5-80
- MICROCHIME DOORBELL. Feb. 79. £15-85
- THYRISTOR TESTER. Feb. 79. £3-78
- FUSE CHECKER. Oct. 78. £2-31
- SOUND TO LIGHT. Sept. 78. £8-42
- CAR BATTERY STATE INDICATOR. Sept. 78. Less case. £2-09
- R.F. SIGNAL GENERATOR. Sept. 78. £26-72
- IN SITU TRANSISTOR TESTER. June 78. £6-77
- WEIRD SOUND EFFECTS GENERATOR. Mar. 78. £5-58
- AUDIO VISUAL METRONOME. Jan. 78. £5-96
- ELECTRONIC TOUCH SWITCH. Jan. 78. £2-73 less case.
- RAPID DIODE CHECK. Jan. 78. £2-74
- PHONE/DOORBELL REPEATER. July 77. £7-46
- ELECTRONIC DICE. Mar. 77. £5-68

## SOLDERING/TOOLS

- ANTEX X5 SOLDERING IRON 25W ..... £5-48
- SOLDERING IRON STAND ..... £1-98
- SPARE BITS. Small, standard, large, 65p each. For X5 + X25
- SOLDER. Handy size ..... 99p
- SOLDER CARTON ..... £1-84
- DESOLDER BRAID ..... 69p
- HEAT SINK TWEEZERS ..... 29p
- DESOLDER PUMP ..... £6-48
- HOW TO SOLDER LEAFLET ..... 12p
- LOW COST CUTTERS ..... £1-69
- LOW COST LONG NOSE PLIERS ..... £1-68
- WIRE STRIPPERS & CUTTERS ..... £2-69



MULTIMETER TYPE 2 (YN360TR) 20K o.p.v. with transistor tester. £14-75

### HELPING HANDS JIG £6-30

Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5 x magnifier attached), used and recommended by our staff.

- VERO SPOT FACE CUTTER ..... £1-49
- PIN INSERTION TOOL ..... £1-06
- VERO PINS (pk of 100) 0.1" ..... 52p
- MULTIMETER TYPE 1 (1,000 opv) £1-18
- SET, 10 leads with 20 clips ..... 99p
- RESISTOR COLOUR CODE CALCULATOR ..... 21p
- CONNECTING WIRE PACK TYPE ED. 11 colours ..... 49p

### ILLUMINATED MAGNIFIERS

- Small 2" dia. (5x mag.) ..... £1-14
- Large 3" dia. (4x mag.) ..... £2-40
- CAST IRON VICE ..... £2-06
- SCREWDRIVER SET ..... £1-08
- POCKET TOOL SET ..... £3-98
- DENTISTS INSPECTION MIRROR ..... £2-85
- JEWELLERS EYEGLASS ..... £1-50
- PLASTIC TWEEZERS ..... 69p
- PAIR OF PROBES WITH LEADS (cc) ..... 77p

## TEACH IN 82

All top quality components as specified by Everyday Electronics. Our kit comes complete with FREE COMPONENT IDENTIFICATION SHEET. Follow this educational series and learn about electronics—Start Today.

LIST 1 and LIST 2 together £27-98. LIST 3 £5-98.

★ ★ SPECIAL OFFER ★ ★ ★  
LISTS 1, 2 and 3 all bought together £33-48.

WOODEN CASE KIT also available £11-98—wood, formica, glue, screws etc. Cut to size.

12 part series, reprints available of previously published parts. 45p each.

LISTS 1, 2, AND 3 ALL AVAILABLE NOW.  
ALSO WOODEN CASE KIT.

## BOOKS

- SEMICONDUCTOR DATA BOOK Newnes ..... £5-98
- ELECTRONIC PROJECTS FOR HOME SECURITY ..... £3-35
- ELECT. PROJECTS IN PHOTOGRAPHY ..... £3-35
- 110 ELECT. ALARM PROJECTS ..... £3-35
- MODEL RAILWAY PROJECTS ..... £1-95
- BASIC ELECTRONICS. Theory and practice ..... £7-98
- BEGINNERS GUIDE TO BUILDING ELECT. PROJECTS ..... £1-50

## ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bim-board 1 bread board.

Adventures with Microelectronics £2-55

Component pack £29-64 less battery.

## ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.

Adventures with Electronics £2-40. Component pack £18-98 less battery.

## ADVENTURES WITH DIGITAL ELECTONICS

New book by Tom Duncan in the popular 'Adventures' series. This book of entertaining and instructive projects is designed for hobbyists and students. It provides a stepping stone to the microprocessor.

The first part deals with the properties of some basic ICs used in digital electronics.

The second part gives details of how to build eight devices—shooting gallery, 2-way traffic lights, electronic adder, computer space invaders game, etc.

For each project there is an explanation of 'how it works' and also suggestions for 'things to try'.

No soldering—all circuits built on 2 Bimboard 1 breadboards.

Adventures with Digital Electronics book £3-25. Component pack £42-50, ref. EEDC. All the components needed including 2 breadboards and hexadecimal keyboard. Available less breadboards £29-98, ref. EEDF. Both less battery.

**MORE KITS AND COMPONENTS IN OUR LISTS**

FREE PRICE LIST  
Price list included with orders or send see (9 x 4)  
CONTAINS LOTS MORE KITS, PCBs COMPONENTS

### 1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery.

Send 80p in stamps or add 80p to order.

MORE E.E. KITS PLUS H.E. and E.T.I. PROJECT KITS IN THE PRICE LIST.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

**MAGENTA ELECTRONICS LTD.**  
EH48, 135 HUNTER ST. BURTON-ON-TRENT, STAFFS., DE14 2ST. 0283 85435. MON.-FRI. 9-5. MAIL ORDER ONLY.  
ADD 45p P. & P. TO ALL ORDERS. PRICES INC. VAT



Normal despatch by return of post.  
OFFICIAL ORDERS WELCOME.  
OVERSEAS. Payment must be in sterling.  
IRISH REPUBLIC and BFPO: UK PRICES.  
EUROPE: UK PRICES plus 10%.  
ELSEWHERE: Write for quote.

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



New Job? New Career? New Hobby? Get into **Electronics Now!**

**FREE!**  
COLOUR BROCHURE



Please send your brochure without any obligation to

I am interested in:

NAME \_\_\_\_\_

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_

POST NOW TO:

BLOCK CAPS PLEASE

EE/3/820

**British National Radio & Electronics School** Reading, Berks. RG1 1BR.



## Receivers & Components

### NEW SURPLUS RELEASE

**EX GOVT LEAD ACID ACCUMULATORS.** Brand new 10V 5ah famous manufacture. Easily tapped in 2v stages. Size only 7" x 5" x 2". Ideal for emergency lighting and power supplies. Burglar alarms etc. Must have cost Govt. over £20 each. Our price £5.50 each, carriage £2.50. 2 for £10 carriage £3.50 4 for £18 carriage £5. 8 for £32 carriage £10. All despatched unfilled. Robust wooden tray with carrying handles. Holds 8 accumulators £5.

**CORDLESS INDUCTIVE LOOP HEADPHONES.** Self powered. Input via loop or external min BNC socket. Contains transistorised high gain amplifier. Operates from internal batteries. Noise excluding muffs. Switch on when placed on head. Special offer white stocks last £6 p.p. £2. 2 pairs for £12 post free.

**LIGHTWEIGHT HEADSETS** (Govt. release). Brand new 600 ohms impedance. A bargain at £3.50 p.p. £1. 2 pairs for £7 post free.

**RIDICULOUS RESISTOR SALE.** Brand new 1/2 watt carbon film resistors. 5% tol. High quality resistors made to exacting specifications by automatic machines. E12 Range 1R0 to 10M in lots of 1000 (25 per value). Only £8 per 1000. Lots of 5000 for £35. 1 R0 to 10M. 1000 PCB type resistors £2.50. Bulk purchase enables us to offer 1000 mixed pre-formed carbon film resistors. 5% tol. for PCB mounting. Huge range of preferred values. £2.50 per 1000. 4000 for £8. Postage 15p in £1.  
**GENUINE AFV TANK HEADSETS AND MIKE** £3.50 per pair. p.p. £1. 2 pairs £7 post free. All headphones fitted with Ex-ministry plug. Standard jack plugs available 25p each. 2 for 40p. Headphone extension sockets available at 25p each. 2 for 40p. Impedance of first two items 600 ohms All headphones in good condition.

### SCOOP PURCHASE

**PYE POCKET PHONE RECEIVERS** Type PF1 normal free 450mHz. Supplied in used condition less battery. £4.50 each. Carriage £1. 2 pairs £9.00 post free. 4 pairs £16.00 post free.

**THE GOVT. SURPLUS WIRELESS EQUIPMENT HANDBOOK.** Gives detailed information and circuit diagrams for British and American Government Surplus Receivers Transmitters and Test Equipment etc. Also suggested modification details and improvements for surplus equipment. Incorporated is a Surplus/Commercial cross referenced valve and transistors guide. The standard reference work in this field. Only £7.50 p.p. £1.50. No VAT on books.

**New release of MODERN DYNAMIC MOVING COIL MICRO-PHONES.** 200 ohms impedance. Switch incorporated. Most with lead and DIN plug. Used but nice condition. 3 designs of case housing. Price one mike our choice £2 plus 50p p.p. Bargain offer all 3 mikes £4.50 p.p. £1

**GENUINE EX-GOVT COLLAPSIBLE AERIALS.** A fully adjustable highly efficient whip aerial in 5 sections. Length 1 1/2 metres. Closed 300 m/m. Copper plated sections. As used on Ex Govt Manpacks. Brand new in makers boxes £2.50 each. p.p. 75p 2 for £5 post free.

**HAVE YOU SEEN THE GREEN CAT.** 1000x of new components, radio, electronic, audio at unbelievably low prices. Send 50p and receive catalogue and FREE RECORD SPEED INDICATOR.

**MINI JUMBO PACK** (£20 worth) for £5 p.p. £1.50. PLEASE ADD 15% VAT to all orders including carriage and p.p.

**Myers Electronic Devices**

Dept EE1, 12/14 Harper Street, Leeds LS2 7EA. Leeds 452045. New retail premises at above address (opposite Corals). Callers welcome 9 to 5 Mon to Sat. Sunday 10 to 1 by appointment. **GOVT. SURPLUS ITEMS ALWAYS IN STOCK.**

# Everyday ELECTRONICS

Reach effectively and economically to-days enthusiasts anxious to know of your products and services through our semi-display and classified pages. Semi-display spaces may be booked at £7.24 per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 31 pence per word (minimum 12 words), box number 60p extra. All cheques, postal orders,

## Receivers & Components

**ELECTRONIC COMPONENTS MERSEYSIDE.** Myca Electronics, 2 Victoria Place, Seacombe Ferry, Wallasey, L44 6NR. Mail order. Send 50p for price list refundable off first order. 051-638 8647.

**AERIAL BOOSTERS** trebles incoming signal, price £7.00. SAE leaflets. **VELCO ELECTRONICS,** Ramsbottom, Lancashire BL0 9AG

## BUMPER BOX OF BITS

WOW!!! We've got so many components in stock, we can't possibly list them all!! - So buy a box, in it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's etc, coils, pots . . . and so on. All modern parts - guaranteed at least 1000 items, minimum weight 10lbs. ONLY £8.50 inc.

**ELECTRONICS WORLD**  
1d Dews Road, Salisbury, Wilts, SP2 7SN  
(Prop: Westbrough Ltd)

**VERO BOARD 0.1 PITCH,** 95 x 292mm £3.50 each, 112 x 177mm £2.95 each. Prices inclusive of VAT, p&p 30p. Send cheque or PO with order to: Coxon Electronics, 47 Steepturpike, Matlock, Derbyshire, DE4 3DP.

**TURN YOUR SURPLUS** capacitors, transistors etc., into cash. Contact Coles Harding & Co., 103 South Brink Wisbech, Cambs. 0945-584188. Immediate settlement.

## Service Sheets

**BELL'S TELEVISION SERVICE** for service sheets on Radio, TV etc. £1.25 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Rd., Harrogate, N. Yorkshire. Tel: 0423 55885.

**ANY PUBLISHED, FULL-SIZE SERVICE SHEET** by return £2 + LSAE. CTV/music centres £3. Repair data with all circuits, layouts, etc. your named TV or Video £8.50. Free 50p mag. All orders, queries - T.I.S. (E.E.), 76 Churches, Larkhall, Lanarkshire.

## Miscellaneous

### LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Send cheque or P.O. to: Roden Products, Dep EE High March, Daventry, Northants, NN11 4QE

**£4.70** including p & p

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for .....  
Insertions. I enclose Cheque/P.O. for £ .....  
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)


NAME .....

ADDRESS .....

### EVERYDAY ELECTRONICS

Classified Advertisement Dept., Room 2812, King's Reach Tower, Stamford Street, London SE1 9LS Telephone 01-281 5942

Rate: 31p per word, minimum 12 words. Box No. 60p extra.

# AT YOUR SERVICE

etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

## Miscellaneous Cont.

### THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4, 01 531 1568

#### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.30	1.90	1.00	0.80
35 to 39	3.52	2.10	1.15	0.85
40 to 43	4.87	2.65	2.05	1.46
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

#### SILVER PLATED COPPER WIRE

14 to 30	7.09	4.20	2.43	1.72
----------	------	------	------	------

#### TINNED COPPER WIRE

14 to 30	3.97	2.41	1.39	0.94
----------	------	------	------	------

#### FLUXCORE SOLDER

	5.75	3.16	1.73	0.96
--	------	------	------	------

Prices include P & P vat. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

DIGITAL WATCH REPLACEMENT PARTS. Batteries, displays, backlights, etc. Also reports, publications, charts. SAE for full list. PROFORDS, Copners Drive, Holmer Green, Bucks HP15 6SA.

## FREE CATALOGUE OF BURGLAR ALARM EQUIPMENT

TOP QUALITY D.I.Y. SYSTEMS AND PARTS AT TRADE PRICES

SEND S.A.E. OR PHONE:  
C-TEC SECURITY, Dept. EE,  
60, MARKET ST, WIGAN  
(0942) 42444

INGERSOLL PERSONAL STEREO FM/AM receiver features - individual volume controls, stereo beacon, fingertip tuning, feather-weight headphones, requires PP3 battery £12.95 p&p 80p. RADIO WATCH - normal size quartz L.C.D. watch combining AM radio complete with featherweight headphones, only £11.95 p&p 45p. TAIT'S MAIL ORDER, 31 Lime Grove, Addlestone, Surrey.

### SILVER OXIDE BATTERIES

Save pounds on silver oxide and alkaline button cells. Fully guaranteed. e.g.: LR44 for Pentax ME Super camera only 42p each post free.

For FREE EQUIVALENTS CHART and price list send s.a.e. to:

H. M. WHEELER & CO.,  
(Unit 1), 15 Hawthorn Crescent,  
Bewdley, Worcs. DY12 2JE.

## Courses

CONQUER THE CHIP—master modern electronics the practical way by seeing and doing in your own home. Write for your free colour brochure now to BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept C3, Reading, Berks RG1 1BR.


# HOW DARE THEY!

If you see an advertisement in the press, in print, on posters or a cinema commercial which makes you angry, write to us at the address below. (TV and radio commercials are dealt with by the I.B.A.)

The Advertising Standards Authority. ✓  
If an advertisement is wrong, we're here to put it right.  
ASA Ltd, Brook House, Torrington Place, London WC1E 7HN

## INDEX TO ADVERTISERS

Alcon .....	130
Ambit .....	189
Audio Electronics .....	186
Bi-Pak .....	134, 135
B.K. Electronics .....	Cover III
B.N.R. & E.S. ....	188
Bull J. ....	132
C-Tec Security .....	191
Cambridge Learning .....	186
Cricklewood Electronics .....	131
Dziubas M. ....	192
Electrains .....	186
Electronics World .....	190
Electronize Design .....	Cover II
Electrovalue .....	169
Enfield Electronics .....	191
G.S.C. ....	183
Greenwell Electronics .....	130
H. M. Wheeler .....	191
I.C.S. ....	192
Magenta Electronics .....	187
Maplin Electronics .....	Cover IV
Myers Electronics Devices .....	190
Pops Components .....	189
R & TVC .....	136
Rapid Electronics .....	133
Roden Products .....	190
Scientific Wire Co. ....	191
Sinclair Products .....	184, 185
Sparkrite .....	175
Titan Transformers .....	191
T.K. Electronics .....	183
Wilmslow Audio .....	189

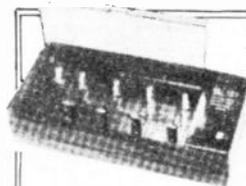

Universal Ni-CAD, battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.

Charges:- PP3 (9V), U12 (1.5V penlite), U11 (1.5V "C"), U2 (1.5V "D"). Power:- 220-240V AC. Dims:- 210 x 100 x 50mm. Knock down price only while stocks last.

Only £8.00  
Order No. MW 398

#### Multimeter & Transistor Tester

DC volts 0-1v-5v-2.5v-10v-50v-250v-1000v ±3%

AC volts 0-10v-50v-250v-1000v ±3%

DC current 0-50uA-2.5mA-25mA-0.25A ±3%

Resistance:

Minimum 0-2-2-200-200k ohms

Midscale 20-200-20k-200k ohms

Maximum 2k-20k-2m-20m ohms

As a transistor tester

Leakage current 0-150uA at Z1k range

0-15mA at X10 range

0-150mA at X1 range

PLEASE ADD 15% VAT & £1 P&P

Only  
£11.95  
Order No.  
HT 320

±5%  
Please allow  
10 days delivery



ENFIELD  
ELECTRONICS

208 BAKER ST., ENFIELD,  
MIDD. Tel: 01-366 1873



## TITAN TRANSFORMERS

DUNCOMBE STREET, GRIMSBY,  
SOUTH HUMBERSIDE DN32 7EG.

### INVERTERS

12/24 volt DC input from car battery to 240 volt AC output at 100, 250, 500 and 1000 VA.

Plus, powerlift, autocharger, powersaver, powermonitor, autochangeover and battery isolator as optional extras.

### TRANSFORMERS

12/24 volt }  
30/60 volt } Range

Autotransformers, safety isolating equipment P.C.B's etc.

### BATTERY CHARGERS - 2 volt.


### ADAPTORS

6 volt to 7.5 volt to 9 volt switchable. 300MA regulated  
6 volt to 7.5 volt to 9 volt switchable. 250MA unregulated

Send SAE for prices and info. by return.

Mail Order Prompt Service

# Make the connection with Access

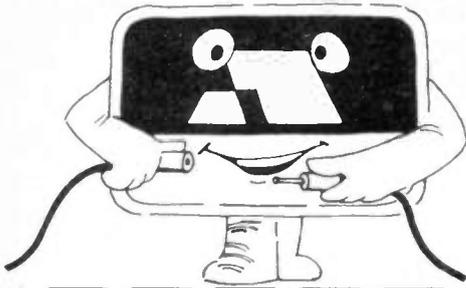

and receive a regular postal delivery of Everyday Electronics. It's easy, it's straightforward and it's quick. Just use the subscription order form to get your Access card account charged with the price of a subscription or order your subscription through Access on the phone: (01) 886 6433. If you pay by cheque or postal order, use the subscription order form in the usual way.

## SUBSCRIPTION ORDER FORM

I wish to become a subscriber to **Everyday Electronics** for one year and enclose cheque/postal order value ..... no ..... made payable to IPC Magazines Ltd.

Complete this portion if you are using your Access card account. I authorise you to debit my Access card account with the above amount.

My Access no is

Name: \_\_\_\_\_

Address: \_\_\_\_\_

Signature: \_\_\_\_\_

## Subscription Rates:

UK, Isle of Man, Channel Islands and Irish Republic £11

Overseas £12

Unless you are phoning your order, complete and post this order form to:

**Everyday Electronics**,  
2613 King's Reach Tower,  
Stamford Street,  
London SE1 9LS.



**METERS: 110 x 82 x 35mm**  
30µA, 50µA, 100µA. £5.90.  
Post 50p.

**METERS: 45 x 50 x 34mm**  
50µA, 100µA, 1mA, 5mA, 10mA,  
25v, 1A, 2A, 5A 25V.  
£2.90. Post 30p.

**METERS: 60 x 47 x 33mm**  
50µA, 100µA, 1mA, 5mA, 10mA,  
100mA, 1A, 2A, 25v, 50v,  
50-0-50µA, 100-0-100µA. £4.78.  
VU meters. £5.32.  
Post on above meters 30p.

**Silicone grease 50g £1.32 Post 14p.**

**NI-CAD BATTERY CHARGER**  
Led indicators charge-test switch.  
For PP3, HP7, HP11 & HP2 size batteries.  
Price £5.85 Post 94p.

### MULTI-METER

7 N 360 TR  
20,000 ohm/volt  
DC Volts: 0-1,  
0-5, 2-5, 10-150-  
250-1,000v.  
AC Volts: 10-50,  
250-1,000

**RESISTANCE RANGES**  
X1, X10, X1K,  
X10K  
£14.10  
P.&P. 87p



### TRANSFORMERS

240v Primary  
3-0-3v 100mA 82p  
6-0-6v 100mA 87p  
6-0-6v 250mA £1.22  
12-0-12v 50mA 92p  
12-0-12v 100mA £1.15  
Post on above transformers 48p.

9-0-9v 1A £1.80  
12-0-12v 1A £2.40  
15-0-15c 1A £2.60  
6-3v 1½A £1.80  
6-0-6v 1½A £2.10  
Post on above transformers 87p.

All above prices include V.A.T. Send 80p for new 1982 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

All goods despatched within 3 days from receipt of the order.

# M. DZIUBAS

158 Bradshawgate, Bolton  
Lancs. BL2 1BA

## FREE CAREER BOOKLET

### Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today—at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

**ELECTRONICS ENGINEERING**

**TV & AUDIO SERVICING**

**ELECTRICAL ENGINEERING**

**RUNNING YOUR OWN BUSINESS**

Name .....

Address .....

**ICS**  
Division of National Education Corporation

ICS  
Dept E629  
160 Stewarts Road,  
London SW8 4UJ



01-622 9911  
(all hours)



APPROVED  
**thandar**  
STOCKIST

# B.K. ELECTRONICS

## A SOUND CHOICE

APPROVED  
**thandar**  
STOCKIST

★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS  
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY

### STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V. **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2 in x 11 1/2 in. Clearance required under top panel 2 1/2 in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price **£26.70** + **£2.50** postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) **£3.50**.



6 piano type keys

### LOUDSPEAKERS

15" 100 watt R.M.S. (HI-FI, P.A., BASS GUITAR). Die cast chassis, 2" aluminium voice coil, white cone with aluminium centre dome. 8 ohm imp., Res. Freq. 20Hz., Freq. Resp. to 2.5KHz., Sens. 97dB. (As photograph). Price: **£32.00** + **£3.00** carriage.

12" 100 watt R.M.S. (HI-FI). Die cast chassis, 2" aluminium voice coil. Black cone. 8 ohm imp. Res. Freq. 20Hz., Freq. Resp. to 4.5KHz. Sens. 95dB. (As photograph). Price: **£23.50** + **£3.00** carriage.

8" 50 watt R.M.S. (HI-FI, P.A.). 1 1/2" aluminium voice coil. White cone. 8 ohm imp. Res. Freq. 40Hz., Freq. Resp. to 6KHz. Sens. 92dB. Also available with black cone fitted with black metal protective grille. (As photograph). Price: White Cone **£8.90**, Black Cone/Grille **£9.50** P & P **£1.25**.

12" 85 watt R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO). 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: **£22.00** + **£3.00** carriage.

12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO). 2" aluminium voice coil. Twin cone. 8 ohm imp. Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price: **£22.00** + **£3.00** carriage.

15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp. Res. Freq. 40Hz., Freq. Resp. to 4KHz.. Price: **£47.00** + **£4.00** carriage.

### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speakers systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

**TYPE 'A'** (KSN1036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price **£3.45** each.

**TYPE 'B'** (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems, etc. Price **£4.35** each.


**TYPE 'C'** (KSN6016A) 2" x 5" wide dispersion horn. For Hi-Fi systems and quality discos, etc. Price **£5.45** each.

**TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2,000 c/s). Suitable for Hi-Fi systems and quality discos. Price **£6.90** each.

**TYPE 'E'** (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems, etc. Price **£4.35** each.

**TYPE 'F'** (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price **£10.75** each.

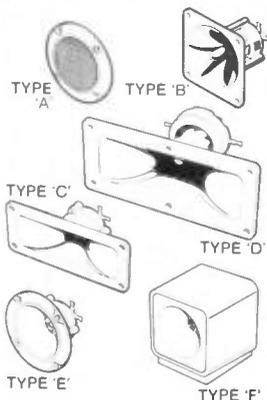U.K. post free (or SAE for Piezo leaflets).



### 1 K-WATT SLIDE DIMMER

- ★ Controls loads up to 1KW.
- ★ Compact Size 4 1/2" x 1 1/2" x 2 1/2".
- ★ Easy snap in fixing through panel/cabinet cut out.
- ★ Insulated plastic case.
- ★ Full wave control using 8 amp triac.
- ★ Conforms to BS800.
- ★ Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's/theatres, etc. Price **£11.70** each + 50p P&P. (Any quantity.)



### HOBBY KITS. PROVEN DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH INSTRUCTIONS.

**FM MICROTRANSMITTER (BUG).** 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt). Price: **£6.58**.

**DIGITAL THERMOMETER.** -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70mm (9 volt). Price: **£22.94**.

**3 WATT FM TRANSMITTER.** 3 watt. 85/115MHz varicap controlled. Professional performance. Range up to 3 miles. 35 x 84 x 12mm (12 volt). Price: **£10.64**.

**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER.** 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates a relay with 2amp/240V contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt) Price: **£14.38**. Transmitter 80 x 50 x 15mm (9/12 volt) Price: **£9.15**. P & P ALL KITS + 50p. S.A.E. for complete list.

### B.S.R. P232 TURNTABLE

- ★ P232 Turntable ★ 'S' shaped tone arm
- ★ Belt driven ★ Aluminium platter
- ★ Cueing lever ★ 240 volt AC operation (50Hz)
- ★ Cut-out template supplied
- ★ Used as standard by Hi-Fi and Disco manufacturers
- ★ Fitted with either a magnetic or ceramic cartridge, please state cartridge required. Price: **£22.50** + **£2.50** P & P.



### POWER AMPLIFIER MODULES

**100 WATT R.M.S. AND 300 WATT R.M.S. MODULES**

Power Amplifier Modules with integral toroidal transformer power supply, and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. An LED Vu meter is available as an optional extra.

### SPECIFICATION

- Max Output Power:
  - 110 watts R.M.S. (OMP 100)
  - 310 watts R.M.S. (OMP 300)
- Loads: Open and short circuit proof. 4-16 ohms
- Frequency Response: 20Hz-25KHz ±3dB.
- Sensitivity for Max. Output:
  - 500mV at 10K (OMP 100) 1V at 10K (OMP 300)
  - T.H.D.: Less than 0.1%.
- Supply: 240V 50Hz
- Sizes: OMP 100 360 x 115 x 72mm
- OMP 300 460 x 153 x 66mm
- Prices: OMP 100 **£31.50** each + **£2.00** P&P
- OMP 300 **£89.00** each + **£3.00** P&P
- Vu Meter **£6.50** each + 50p P&P

Purposefully designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter.


B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system—recommended cabinet size 240 x 216 x 445mm. Price: **£14.90** each + **£2.00** P&P.

5" 30 W system—recommended cabinet size 160 x 175 x 295mm. Price: **£13.90** each + **£1.50** P&P.


Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self-adhesive vinyl etc.

8" system cabinet kit. **£8.00** each + **£2.50** P&P.

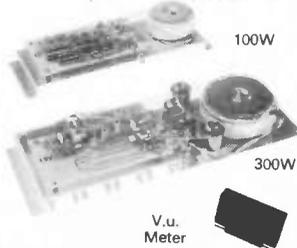
5" system cabinet kit. **£7.00** each + **£2.00** P&P.



### MULLARD SPEAKER KITS

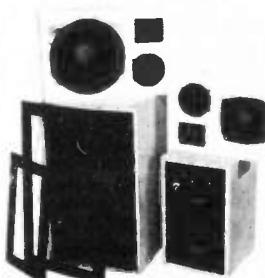

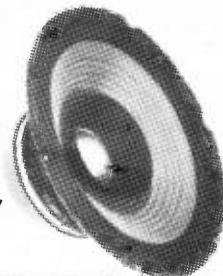**12" 80 watt R.M.S. loudspeaker**  
A superb general purpose twin cone loud-speaker. 50 oz. magnet. 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8 ohm. **Attractive blue cone with aluminium centre dome.** Price: **£17.99** each + **£3.00** P & P.



# B.K. ELECTRONICS

DEPT E.E.

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



# SPEECH SYNTHESISER FOR ZX81 and VIC20

## THE MAPLIN TALK-BACK

Now your computer can talk!

- ★ Allophone (extended phoneme) system gives unlimited vocabulary.
- ★ Can be used with unexpanded VIC20 or ZX81 — does not require large areas of memory.
- ★ In VIC20 version, speech output is direct to TV speaker with no additional amplification needed.
- ★ Allows speech to be easily included in programs.

Complete kit only £24.95.

Order As LK00A (VIC20 Talk-Back).  
LK01B (ZX81 Talk-Back).

Full construction details in Maplin Projects Book 6.  
Price 70p. Order As XA06G (Maplin Mag Vol. 2 No. 6).



### KEYBOARD WITH ELECTRONICS FOR ZX81



- ★ Full size, full travel keyboard that's simple to add to your ZX81 (no soldering in ZX81).
  - ★ Complete with electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections.
  - ★ Powered (with adaptor supplied) from ZX81's own standard power supply.
- Full details in Project Book 3 (XA03D) Price 60p.  
Complete kit (excl. case) £19.95. Order As LW72P.  
Case £4.95. Order As XG17T.  
Ready built-in case £29.95. Order As XG22Y.

### OTHER KITS FOR ZX81

- 3-Channel Sounds Generator (Details in Book 5). Order As LW96E. Price £10.95.
- ZX81 Sound On Your TV Set (Details in Book 6). Order As LK02C. Price £19.95.
- ZX81 I/O Port gives two bi-directional 8-bit ports (Details in Book 4). Order As LW76H. Price £9.25.
- ZX81 Extensible board will accept 16K RAM and 3 other plug-in modules.
- PCB: Order As GB08J. Price £2.32.
- Edge Connectors (4 needed): Order As RK35Q. Price £2.39.

### HOME SECURITY SYSTEM

Six independent channels — 2 or 4 wire operation. External horn. High degree of protection and long term reliability. Full details in Projects Book 2. (XA02C) Price 60p



### MATINEE ORGAN

Easy-to-build, superb specification. Comparable with organs selling for up to £1000. Full construction details in our book (XH55K). Price £2.50. Complete kits available. Electronics (XY91Y) £299.95\*. Cabinet (XY93B) £99.50\*. Demo cassette (XX43W) £1.99.



\*Carriage extra


### 25W STEREO MOSFET AMPLIFIER



- ★ Over 26W/channel into 8Ω at 1kHz both channels driven
- ★ Frequency response 20Hz to 40kHz ±1dB.
- ★ Low distortion, low noise and high reliability power MOSFET output stage.
- ★ Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
- ★ Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet. Full details in Projects Book 3. Price 60p (XA03D). Complete kit only £49.95 incl. VAT and carriage (LW71N).
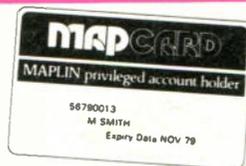
### BUY IT WITH MAPCARD

Send now for an application form — then buy it with MAPCARD. MAPCARD gives you real spending power — up to 24 times your monthly payments, instantly.



All prices include VAT & carriage. Please add 50p handling charge to orders under £5 total value.

### MAPLIN'S FANTASTIC PROJECTS

Full details in our project books. Issues 1 to 5: 60p each. Issue 6: 70p.

- In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • Six Vero Projects.
- In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.
- In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W MOSFET Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.
- In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to 600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.
- In Book 5 (XA05F) Modem to European standard • 100W 240V AC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Sounder.
- In Book 6 (XA06G)\* Speech Synthesiser for ZX81 & VIC20 • Module to Bridge two of our MOSFET Amps to make a 350W Amp • ZX81 Sound on your TV • ZX81 Interface for Modem • Scratch Filter • Doorbell for Deaf • Simple FM Tuner\* • Damp Meter\*.

\*Projects for Book 6 were in an advanced state at the time of writing, but contents may change prior to publication (due 11th February 1983).

### MAPLIN'S NEW 1983 CATALOGUE

Over 390 pages packed with data and pictures and all completely revised and including over 1000 new items. On sale in all branches of WHSMITH Price £1.25.



### Post this coupon now!

Please send me a copy of your 1983 catalogue. I enclose £1.50 (inc p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.90 or 10 International Reply Coupons. Despatched by return of post.

Name \_\_\_\_\_

Address \_\_\_\_\_

EE

# MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD.

P.O. Box 3, Rayleigh, Essex SS6 8LR

Telephone: Sales (0702) 552911 General (0702) 554155

Shops at:

Note: Shops closed Mondays

159 King St., Hammersmith, London W6. Telephone: 01-748 0926

284 London Rd., Westcliff-on-Sea, Essex. Telephone: (0702) 554000

Lynton Square, Perry Barr, Birmingham. Telephone: (021) 356 7292