

EVERYDAY

461

ELECTRONICS and computer **PROJECTS**

DECEMBER 1983

90p

XMAS IDEAS

MAGIC CANDLE

**CHILDRENS
DISCO LIGHTS**

NOVEL EGG TIMER

ENVIRONMENTAL DATA RECORDER



Australia \$1.60 New Zealand \$1.60 Malaysia \$4.95 JR £1.38 (inc V.A.T.)

electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS YOUR CAR

AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
 - ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
 - ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
 - ★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smoothes out the effects of contact bounce etc.
 - ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
 - ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3 1/2 times the power of inductive systems, 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:
Performance at only 6 volts (max. supply 16 volts)
 SPARK POWER — 140W, SPARK ENERGY — 36mJ
 SPARK DURATION — 500µs, STORED ENERGY — 100mJ
 LOADED OUTPUT VOLTAGE
 50pF load — 38kV, 50pF + 800k — 26kV
- We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ **All ELECTRONIZE electronic ignitions feature:**
EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
 - ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2uF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most NEW CARS already have electronic ignition. Update YOUR CAR

ELECTRONIZE ELECTRONIC CAR ALARM



HOW SAFE IS YOUR CAR ?

More and more cars are stolen each week and even a steering lock seems little help. But a car thief will avoid a car that will cause him trouble and attract attention. If your car has a good alarm system - well there are plenty of other cars to choose from.

LOOK AT THE PROTECTION AN ELECTRONIZE ALARM CAN GIVE :

- ★ **MINIATURE KEY PLUG** A miniature jack plug attaches to your key ring and is coded to your particular alarm.
- ★ **205 INDIVIDUAL COMBINATIONS** The key plug contains two 1% tolerance resistors, both must be the correct value and together give 205 different combinations.
- ★ **ATTRACTS MAXIMUM ATTENTION** This alarm system not only intermittently sounds the horn, but also flashes the headlight and prevents the engine being started.
- ★ **60 SECOND ARM PERIOD** Once triggered the alarm will sound for 60 seconds, unless cancelled by the key plug, before resetting ready to be triggered again.
- ★ **30 SECOND EXIT DELAY** The system is armed by pressing a small button on a dashboard mounted control panel. This starts a 30 second delay period during which the owner can open and close doors without triggering the alarm.
- ★ **10 SECOND ENTRY DELAY** When a door is opened a 10 second delay operates to allow the owner to disarm the system with the coded key plug. Latching circuits are used and once triggered the alarm can only be cancelled by the key plug.
- ★ **LED FUNCTION INDICATOR** An LED is included in the dashboard unit and indicates the systems operating state. The LED lights continuously to show the system is armed and in the exit delay condition. A flashing LED indicates that the alarm has been triggered and is in the entry delay condition.
- ★ **ACCESSORY LOOP - BONNET/BOOT SWITCH - IGNITION TRIGGER** These operate three separate circuits and will trigger the alarm immediately, regardless of entry and exit delays.
- ★ **SAFETY INTERLOCK** The system cannot be armed by accident when the engine is running and the car is in motion.
- ★ **LOW SUPPLY CURRENT** CMOS IC's and low power operational amplifiers achieve a normal operating current of only 2.5 mA.
- ★ **IN KIT FORM** It provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, random selection resistors to set the code and full set of components etc. In fact everything down to the last washer plus easy to follow instructions.

fill in the coupon and send to:

Please send more information

ELECTRONIZE DESIGN Dept C · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- Assembled ready to fit £26.70 £19.95
 D.I.Y. parts kit £15.90 £14.95

TWIN OUTPUT for cars and motor cycles with dual ignition

- Twin, Assembled ready to fit £36.45 £29.95
 Twin, D.I.Y. parts kit £24.55 £22.95

INDUCTIVE DISCHARGE (12 volt only)

- Assembled ready to fit £15.55 £12.75

Goods normally despatched within 7 days.
 Prices Include VAT £1-00 PP(UK) per Unit.

CAR ALARM (12 volt negative earth)

- Assembled ready to fit (All wires and connectors incl.) £27.95 £33.70
 D.I.Y. parts kit £24.95 £22.40

I enclose cheque/postal order OR debit my Access/Visa card

VISA ACCESS

Name _____


Address _____

Code _____

EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 12 NO. 12 DECEMBER 1983

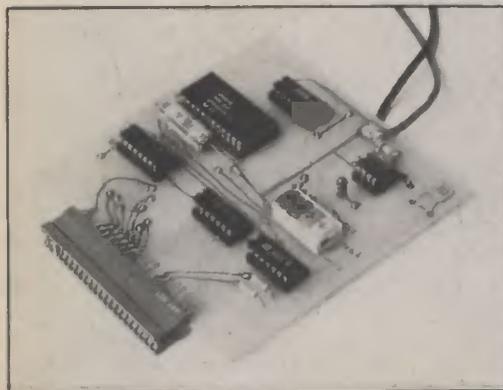PROJECTS ... THEORY ... NEWS ...
COMMENT ... POPULAR FEATURES ...



© IPC Magazines Limited 1983. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our January 1984 issue will be published on Friday, December 16. See page 825 for details.

Everyday Electronics, December 1983

PROJECTS

- TRS-80 TWIN CASSETTE INTERFACE** by S. Rainey 790
Two cassette deck operation without Expansion Interface
- CHILDREN'S DISCO LIGHTS** by T. R. de Vaux-Balbirnie 796
Light display for a children's party
- MAGIC CANDLE** by T. R. de Vaux-Balbirnie 798
Blow it out and it relights itself!
- ENVIRONMENTAL DATA RECORDER**
By M. Lawrie & L. Wilkinson 807
Field data storage for Spectrum users
- 4-CHANNEL HIGH SPEED ADC**
by J. Adams & G. M. Feather 816
- NOVEL EGG-TIMER** by I. Hickman 826
Time your eggs to perfection
- CONTINUITY TESTER** by R. A. Penfold 830
Useful test instrument for electronic circuits
- TOUCH OPERATED DIE** by C. J. Bowes 834
With a choice of either dot or numeric display

SERIES

- TEACH-IN 84** by G. Hylton 802
Part 3: Potentiometers and Transistors
- MICROCOMPUTER INTERFACING TECHNIQUES**
by J. Adams & G. M. Feather 814
Part 6: Analogue Data Multiplexing and 4-Channel High Speed ADC

FEATURES

- EDITORIAL** Quite simple; Another Schools Winner 789
- BOOK REVIEWS** A selection of recent releases 795, 828
- CIRCUIT EXCHANGE** 800, 839, 840
A forum for readers' ideas
- PLEASE TAKE NOTE** 800
Multimod, Speech Synthesiser for the BBC Micro
- SHOPTALK** by Dave Barrington 801
Product news, component buying and EE PCB Service
- COUNTER INTELLIGENCE** by Paul Young 812
A retailer comments
- SEDAC 1984** Schools electronic design award competition 813
- EVERYDAY NEWS** 822
What's happening in the world of electronics
- FOR YOUR ENTERTAINMENT** by Barry Fox 824
Confusing Law; Citizen's Band TV; Flat-Screen TV; Hot Memory
- RADIO WORLD** by Pat Hawker G3VA 829
Where have all the viewers gone; Still spinning; Pen Radios
- NEW PRODUCTS** 841
Facts and photos of instruments, equipments and tools
- INDEX VOLUME 12** 842

Readers' Services • Editorial and Advertisement Departments 789

781

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE — OF ELECTRONICS!
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



CACC

British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!
COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

BLOCK CAPS PLEASE
EE/12/841

I am interested in:

- COURSE IN ELECTRONICS
as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS
please state below.

OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)



British National Radio & Electronics School Reading, Berks. RG1 1BR

CRICKLEWOOD ELECTRONICS LTD

40 Cricklewood Broadway London NW2 3ET Tel 01-5220161 01-450 0995 Tlx 914977

Here's a selection from our vast stocks. Full price list free on request. Orders by phone on credit card or by mail order. Callers welcome. All products first grade franchised source. All in stock (items dispatched same day). Official orders welcome from Govt. Dealers, schools etc. Please add 60p p&p + 15% VAT. Overseas orders no VAT but allow £2.00 min. p&p. Quantity discounts negotiable.

Stocking parts other stores cannot reach!

RESISTORS 2.2 100 11p 2.2 350 30p 3.3 25 10p CARBON FILM 5% H1STAR LOW NOISE 47 16 8p 101 to 10MΩ 1W E24 5p 1W E24 11p 1W E24 21p 1W E12 6p 2W E12 12p METAL FILM ULTRA STABLE 0.4W EXTRA LOW NOISE 100 to 1MΩ 2% E24 5p 1% E24 6p 1% E24 6p LOW OHMIC GLAZE W/W 0.22 to 0.22 2p E24 11p WIREWOUND ON CERAMIC E12 SERIES 2 to 3 WATT 0.22 to 330Ω 28p 4 to 7 WATT 0.47 to 330Ω 33p 10 to 11 WATT 10 to 330Ω 37p POTS & PRESETS ROTARY POTS LOW NOISE 100 to 100K 4K7 to 2MΩ LM 4K7 to 2MΩ LM LOG As above with DP wipers switch 90p As above stereo (no switch) 1.00 PRE SETS PINK (DUST PROOF) E3 100 to 10MΩ Mini Vertical 15p Standard Vert 18p Standard Horz 18p CERMET 20 TURN PRECISION PRE SETS % E3 Series 500 to 500K 89p CAPS CERAMIC 150V DISC (PLATE) E12 MICRO MINI typically 50p 1nf to 10nf 7p POLYCARB 50V 100 to 100K SIEMENS 75mm MINI BLOC E12 250V 1nf to 50nf 7p 8nf to 47nf 8p 56nf to 150nf 10p 100V 12.0 12.0 20p 180nf to 270nf 14p 330nf to 390nf 14p 470nf to 560nf 20p 680nf 30p 1µF (10mm) 35p POLYESTER 250V RADIAL (C200) 10nf 15nf 22nf 33nf 47nf 68nf 100nf 150nf 220nf 330nf 470nf 13p 680nf 18p 1µF 22p 1.5, 2.2 35p FEEDTHROUGH 1N1 500V 7p 1N1 500V 7p HIGH VOLTAGE Capacitors please enquire many types in stock TANT BEADS 1 35V 14p 2 25V 14p 3 35V 14p 4 75V 14p 5 35V 14p 10 35V 14p 22 35V 14p 33 35V 18p 47 35V 18p 7 15V 18p 47 35V 20p 8 25V 21p 6 8 35V 21p 10 16V 18p 10 15V 27p 10 15V 22p 15 16V 30p 15 25V 32p 2 16V 30p 33 10V 30p 47 3V 14p 47 6V 34p 47 16V 39p 100 13V 32p 100 10V 55p ELECTROLYTICS Mantly Matsuda 1 (Panasonic) 6p Siemens AXIALS (Wires each) ent 47 63 8p 47 100 9p 47 350 30p 1 63 8p 1 100 9p 1 500 40p 2 2 75 8p 2 2 63 8p Single sided 100 to 160 1.55 100 to 220 1.90 200 to 220 2.15 233 to 220 3.99 Double sided 100 to 160 1.65 100 to 220 2.15 200 to 114 2.21 233 to 220 4.55 Developer for above 100 not used Solder (Hydri) deli 500ml 2.50 2N2905 28p 2N2905A 29p 2N2906 25p 2N2906A 26p 2N2907 25p 2N2907A 26p 2N2920 8.50 2N2920B 25p 2N2924 15p 2N2925 15p 2N2926 10p 2N3053 27p 2N3054 16p 2N3055 60p 2N3055H 120p 2N3250 36p 2N3251 36p 2N3439 98p 2N3440 80p 2N3441 1.25 2N3442 1.25 2N3445 4.80 2N3446 6.09 2N3447 6.72 2N3448 1.80 2N3468 1.00 2N3512 1.06 2N3525 2.65 2N3526 5.6p 2N3638A 70p 2N3702 10p 2N3703 10p 2N3710 14p 2N3716 14p 2N3705 10p 2N3706 10p 2N3707 10p 2N3708 10p 2N3709 10p 2N3710 10p 2N3711 10p 2N3712 10p 2N3713 1.38 2N3714 2.38 2N3715 3.31 2N3716 3.60 2N3717 3.99 2N3718 4.38 2N3719 4.77 2N3720 5.16 2N3721 5.55 2N3722 5.94 2N3723 6.33 2N3724 6.72 2N3725 7.11 2N3726 7.50 2N3727 7.89 2N3728 8.28 2N3729 8.67 2N3730 9.06 2N3731 9.45 2N3732 9.84 2N3733 10.23 2N3734 10.62 2N3735 11.01 2N3736 11.40 2N3737 11.79 2N3738 12.18 2N3739 12.57 2N3740 12.96 2N3741 13.35 2N3742 13.74 2N3743 14.13 2N3744 14.52 2N3745 14.91 2N3746 15.30 2N3747 15.69 2N3748 16.08 2N3749 16.47 2N3750 16.86 2N3751 17.25 2N3752 17.64 2N3753 18.03 2N3754 18.42 2N3755 18.81 2N3756 19.20 2N3757 19.59 2N3758 19.98 2N3759 20.37 2N3760 20.76 2N3761 21.15 2N3762 21.54 2N3763 21.93 2N3764 22.32 2N3765 22.71 2N3766 23.10 2N3767 23.49 2N3768 23.88 2N3769 24.27 2N3770 24.66 2N3771 25.05 2N3772 25.44 2N3773 25.83 2N3774 26.22 2N3775 26.61 2N3776 27.00 2N3777 27.39 2N3778 27.78 2N3779 28.17 2N3780 28.56 2N3781 28.95 2N3782 29.34 2N3783 29.73 2N3784 30.12 2N3785 30.51 2N3786 30.90 2N3787 31.29 2N3788 31.68 2N3789 32.07 2N3790 32.46 2N3791 32.85 2N3792 33.24 2N3793 33.63 2N3794 34.02 2N3795 34.41 2N3796 34.80 2N3797 35.19 2N3798 35.58 2N3799 35.97 2N3800 36.36 2N3801 36.75 2N3802 37.14 2N3803 37.53 2N3804 37.92 2N3805 38.31 2N3806 38.70 2N3807 39.09 2N3808 39.48 2N3809 39.87 2N3810 40.26 2N3811 40.65 2N3812 41.04 2N3813 41.43 2N3814 41.82 2N3815 42.21 2N3816 42.60 2N3817 42.99 2N3818 43.38 2N3819 43.77 2N3820 44.16 2N3821 44.55 2N3822 44.94 2N3823 45.33 2N3824 45.72 2N3825 46.11 2N3826 46.50 2N3827 46.89 2N3828 47.28 2N3829 47.67 2N3830 48.06 2N3831 48.45 2N3832 48.84 2N3833 49.23 2N3834 49.62 2N3835 50.01 2N3836 50.40 2N3837 50.79 2N3838 51.18 2N3839 51.57 2N3840 51.96 2N3841 52.35 2N3842 52.74 2N3843 53.13 2N3844 53.52 2N3845 53.91 2N3846 54.30 2N3847 54.69 2N3848 55.08 2N3849 55.47 2N3850 55.86 2N3851 56.25 2N3852 56.64 2N3853 57.03 2N3854 57.42 2N3855 57.81 2N3856 58.20 2N3857 58.59 2N3858 58.98 2N3859 59.37 2N3860 59.76 2N3861 60.15 2N3862 60.54 2N3863 60.93 2N3864 61.32 2N3865 61.71 2N3866 62.10 2N3867 62.49 2N3868 62.88 2N3869 63.27 2N3870 63.66 2N3871 64.05 2N3872 64.44 2N3873 64.83 2N3874 65.22 2N3875 65.61 2N3876 66.00 2N3877 66.39 2N3878 66.78 2N3879 67.17 2N3880 67.56 2N3881 67.95 2N3882 68.34 2N3883 68.73 2N3884 69.12 2N3885 69.51 2N3886 69.90 2N3887 70.29 2N3888 70.68 2N3889 71.07 2N3890 71.46 2N3891 71.85 2N3892 72.24 2N3893 72.63 2N3894 73.02 2N3895 73.41 2N3896 73.80 2N3897 74.19 2N3898 74.58 2N3899 74.97 2N3900 75.36 2N3901 75.75 2N3902 76.14 2N3903 76.53 2N3904 76.92 2N3905 77.31 2N3906 77.70 2N3907 78.09 2N3908 78.48 2N3909 78.87 2N3910 79.26 2N3911 79.65 2N3912 80.04 2N3913 80.43 2N3914 80.82 2N3915 81.21 2N3916 81.60 2N3917 81.99 2N3918 82.38 2N3919 82.77 2N3920 83.16 2N3921 83.55 2N3922 83.94 2N3923 84.33 2N3924 84.72 2N3925 85.11 2N3926 85.50 2N3927 85.89 2N3928 86.28 2N3929 86.67 2N3930 87.06 2N3931 87.45 2N3932 87.84 2N3933 88.23 2N3934 88.62 2N3935 89.01 2N3936 89.40 2N3937 89.79 2N3938 90.18 2N3939 90.57 2N3940 90.96 2N3941 91.35 2N3942 91.74 2N3943 92.13 2N3944 92.52 2N3945 92.91 2N3946 93.30 2N3947 93.69 2N3948 94.08 2N3949 94.47 2N3950 94.86 2N3951 95.25 2N3952 95.64 2N3953 96.03 2N3954 96.42 2N3955 96.81 2N3956 97.20 2N3957 97.59 2N3958 97.98 2N3959 98.37 2N3960 98.76 2N3961 99.15 2N3962 99.54 2N3963 99.93 2N3964 100.32 2N3965 100.71 2N3966 101.10 2N3967 101.49 2N3968 101.88 2N3969 102.27 2N3970 102.66 2N3971 103.05 2N3972 103.44 2N3973 103.83 2N3974 104.22 2N3975 104.61 2N3976 105.00 2N3977 105.39 2N3978 105.78 2N3979 106.17 2N3980 106.56 2N3981 106.95 2N3982 107.34 2N3983 107.73 2N3984 108.12 2N3985 108.51 2N3986 108.90 2N3987 109.29 2N3988 109.68 2N3989 110.07 2N3990 110.46 2N3991 110.85 2N3992 111.24 2N3993 111.63 2N3994 112.02 2N3995 112.41 2N3996 112.80 2N3997 113.19 2N3998 113.58 2N3999 113.97 2N4000 114.36 2N4001 114.75 2N4002 115.14 2N4003 115.53 2N4004 115.92 2N4005 116.31 2N4006 116.70 2N4007 117.09 2N4008 117.48 2N4009 117.87 2N4010 118.26 2N4011 118.65 2N4012 119.04 2N4013 119.43 2N4014 119.82 2N4015 120.21 2N4016 120.60 2N4017 120.99 2N4018 121.38 2N4019 121.77 2N4020 122.16 2N4021 122.55 2N4022 122.94 2N4023 123.33 2N4024 123.72 2N4025 124.11 2N4026 124.50 2N4027 124.89 2N4028 125.28 2N4029 125.67 2N4030 126.06 2N4031 126.45 2N4032 126.84 2N4033 127.23 2N4034 127.62 2N4035 128.01 2N4036 128.40 2N4037 128.79 2N4038 129.18 2N4039 129.57 2N4040 129.96 2N4041 130.35 2N4042 130.74 2N4043 131.13 2N4044 131.52 2N4045 131.91 2N4046 132.30 2N4047 132.69 2N4048 133.08 2N4049 133.47 2N4050 133.86 2N4051 134.25 2N4052 134.64 2N4053 135.03 2N4054 135.42 2N4055 135.81 2N4056 136.20 2N4057 136.59 2N4058 136.98 2N4059 137.37 2N4060 137.76 2N4061 138.15 2N4062 138.54 2N4063 138.93 2N4064 139.32 2N4065 139.71 2N4066 140.10 2N4067 140.49 2N4068 140.88 2N4069 141.27 2N4070 141.66 2N4071 142.05 2N4072 142.44 2N4073 142.83 2N4074 143.22 2N4075 143.61 2N4076 144.00 2N4077 144.39 2N4078 144.78 2N4079 145.17 2N4080 145.56 2N4081 145.95 2N4082 146.34 2N4083 146.73 2N4084 147.12 2N4085 147.51 2N4086 147.90 2N4087 148.29 2N4088 148.68 2N4089 149.07 2N4090 149.46 2N4091 149.85 2N4092 150.24 2N4093 150.63 2N4094 151.02 2N4095 151.41 2N4096 151.80 2N4097 152.19 2N4098 152.58 2N4099 152.97 2N4100 153.36 2N4101 153.75 2N4102 154.14 2N4103 154.53 2N4104 154.92 2N4105 155.31 2N4106 155.70 2N4107 156.09 2N4108 156.48 2N4109 156.87 2N4110 157.26 2N4111 157.65 2N4112 158.04 2N4113 158.43 2N4114 158.82 2N4115 159.21 2N4116 159.60 2N4117 160.00 2N4118 160.39 2N4119 160.78 2N4120 161.17 2N4121 161.56 2N4122 161.95 2N4123 162.34 2N4124 162.73 2N4125 163.12 2N4126 163.51 2N4127 163.90 2N4128 164.29 2N4129 164.68 2N4130 165.07 2N4131 165.46 2N4132 165.85 2N4133 166.24 2N4134 166.63 2N4135 167.02 2N4136 167.41 2N4137 167.80 2N4138 168.19 2N4139 168.58 2N4140 168.97 2N4141 169.36 2N4142 169.75 2N4143 170.14 2N4144 170.53 2N4145 170.92 2N4146 171.31 2N4147 171.70 2N4148 172.09 2N4149 172.48 2N4150 172.87 2N4151 173.26 2N4152 173.65 2N4153 174.04 2N4154 174.43 2N4155 174.82 2N4156 175.21 2N4157 175.60 2N4158 175.99 2N4159 176.38 2N4160 176.77 2N4161 177.16 2N4162 177.55 2N4163 177.94 2N4164 178.33 2N4165 178.72 2N4166 179.11 2N4167 179.50 2N4168 179.89 2N4169 180.28 2N4170 180.67 2N4171 181.06 2N4172 181.45 2N4173 181.84 2N4174 182.23 2N4175 182.62 2N4176 183.01 2N4177 183.40 2N4178 183.79 2N4179 184.18 2N4180 184.57 2N4181 184.96 2N4182 185.35 2N4183 185.74 2N4184 186.13 2N4185 186.52 2N4186 186.91 2N4187 187.30 2N4188 187.69 2N4189 188.08 2N4190 188.47 2N4191 188.86 2N4192 189.25 2N4193 189.64 2N4194 190.03 2N4195 190.42 2N4196 190.81 2N4197 191.20 2N4198 191.59 2N4199 191.98 2N4200 192.37 2N4201 192.76 2N4202 193.15 2N4203 193.54 2N4204 193.93 2N4205 194.32 2N4206 194.71 2N4207 195.10 2N4208 195.49 2N4209 195.88 2N4210 196.27 2N4211 196.66 2N4212 197.05 2N4213 197.44 2N4214 197.83 2N4215 198.22 2N4216 198.61 2N4217 199.00 2N4218 199.39 2N4219 199.78 2N4220 200.17 2N4221 200.56 2N4222 200.95 2N4223 201.34 2N4224 201.73 2N4225 202.12 2N4226 202.51 2N4227 202.90 2N4228 203.29 2N4229 203.68 2N4230 204.07 2N4231 204.46 2N4232 204.85 2N4233 205.24 2N4234 205.63 2N4235 206.02 2N4236 206.41 2N4237 206.80 2N4238 207.19 2N4239 207.58 2N4240 207.97 2N4241 208.36 2N4242 208.75 2N4243 209.14 2N4244 209.53 2N4245 209.92 2N4246 210.31 2N4247 210.70 2N4248 211.09 2N4249 211.48 2N4250 211.87 2N4251 212.26 2N4252 212.65 2N4253 213.04 2N4254 213.43

FREE GREEN CATALOGUE
SEND SAE TODAY

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting

- TDR300K Remote Control Dimmer £14.30
- MK6 Transmitter for above £4.20
- TD300K Touchdimmer £7.00
- TS300K Touchswitch £7.00
- TDE/K Extension kit for 2-way switching for TD300K £2.50



DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3/2 digit liquid crystal display. This kit will form the basis of a digital multi-meter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week



Price £15.50

CHRISTMAS PRESENTS GALORE

3-NOTE DOOR CHIME
Based on the SAB0500 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS! Order as XK102. **£5.00**

LIGHT DIMMER KIT
Contains all components, including front panel and knob, to make a dimmer for lights up to 300W. **£3.50**

LCD 3 1/2 DIGIT MULTIMETER
16 ranges including DC voltage (200 mv-1000V) and AC voltage, DC current (200 mA-10 A) and resistance (0-2 M) + NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x88x31 mm. Requires PP3 9v battery. Test leads included. **ONLY £29.00**

MW RADIO KIT
Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2 cms. Requires PP3 9V battery. **IDEAL FOR BEGINNERS. £5.00**

BEGINNERS STARTER PACKS

Containing selection of electronic components including transistors, LEDs, diodes, capacitors, ICs etc. together with a descriptive booklet with 10 easy-to-build projects plus a solderless circuit board enabling the components to be re-used. Requires 9V battery. Discreet component pack (no ICs) £5.00 Integrated circuit pack £6.00

STOCKING FILLERS All full spec. branded devices.

- PACK (1) 650 Resistors 47 ohm to 10Mohm — 10 per value £4.00
- PACK (2) 40 x 16V Electrolytic Capacitors 10µF to 1000µF — 5 per value £3.25
- PACK (3) 60 Polyester Capacitors 0.01 to 1µF/250V — 5 per value £5.55
- PACK (4) 45 Sub-miniature Presets 100 ohm to 1 Mohm — 5 per value £2.90
- PACK (5) 30 Low Profile IC Sockets 8, 14, and 16 pin — 10 of each £2.40
- PACK (6) 25 Red LEDs (5mm dia.) £1.25

TEACH-IN 84
Complete kit of top quality components as specified by EE including EBBO starter packs. **£15.80**

ELECTRONIC LOCK KIT XK101
This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40mA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £10.50**

Electric lock mechanisms for use with latch locks and above kit **£13.50**

DISCO LIGHTING KITS

DL1000K
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£14.60**

DL2100K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1
Allowing audio ("beat")
—light response. **60p**

DL3000K
This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust—simply connect to mains supply & lamps. **Only £11.95**

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to



ELECTRONICS
11-13 Boston Road
London W7 3SJ

Add 65p postage & packing + 15% VAT to total
Overseas Customers:
Add £2.50 (Europe), £6.00 (elsewhere) for p&p
Send S.A.E. for further STOCK DETAILS.
Goods by return subject to availability.

OPEN 9am to 5pm (Mon to Fri)
10am to 4pm (Sat)

ALL PRICES EXCLUDE VAT



EE

TEL: 01-567 8910 ORDERS
01-579 9794 ENQUIRIES
01-579 2842 TECHNICAL AFTER 3PM

G.P.E. SELF-FEED SOLDERING IRON Patented
A new concept in miniature soldering iron design



This new development in Soldering Irons combines light weight (80g.) with unique one-handed operation. Solder is housed in the transparent handle and applied directly to the joint by turning the serrated wheel (located in the handle) with the index finger, allowing a clean, bright joint to be made every time. To renew the solder, the spring clip at the end of the handle is released, the cap is removed and a refill is inserted.

ORDERING INFORMATION. (MAIL ORDER ONLY)
Soldering Iron 240v, 18w. Fitted with 2.3mm Dia. Bit. Complete with 4 metres of solder. Price £14.95.
Solder refills (Pack of 4) Price £2.44.
Spare Bits. Tip. Dia. 2.3mm, 3mm or 4.7mm.
Price £1.36 each.

All prices include VAT and P & P. S.A.E. for details.

Manufactured and supplied by:

GARDNER PRECISION ENGINEERING
North Road, Woking, Surrey GU21 5DS.
Tel. Woking 20722

TWO GREAT HOBBIES ... IN ONE GREAT KIT!



The K5000 Metal Detector Kit combines the challenge of DIY electronics assembly with the reward and excitement of discovering Britain's buried past.

As a Metal Detector—the K5000 boasts the proven pedigree of C-Scope, Europe's leading detector manufacturer. As a Kit—simplified assembly techniques require little technical knowledge, and no complex electronic test equipment. All stages of assembly are covered in a finely-detailed 36 page manual.

Detector Features Analytical Discrimination & Ground Exclusion
Ask at your local Hobby/Electronics shop or use the coupon and send with your remittance to:-
C-Scope International Ltd., PO Box 36, Ashford, Kent TN23 2LN
Please allow 14 days for delivery.

Please send me K5000 Kits @ £119.99(+£3.00 p+p) each.

<input type="checkbox"/> Please debit my Barclaycard/Access	<input type="text"/>
<input type="checkbox"/> I enclose Cheque/PO	£
Name	
Address	

EE

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite

SELF ASSEMBLY ELECTRONIC KITS

PRICES REDUCED
ON SUPER SAVE
D.I.Y. KITS



SX 1000 Electronic Ignition

- Inductive Discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Patented clip-to-coil fitting ● Easy to assemble, easy to fit ● Contact breaker triggered - includes bounce suppression circuit.


SUPER SAVE



SX 2000 Electronic Ignition

- Reactive Discharge ● Combines inductive & capacitive energy storage ● Gives highest possible spark energy ● Patented clip-to-coil fitting ● Easy assembly sequence ● Contact breaker triggered - includes bounce suppression circuit.

SUPER SAVE

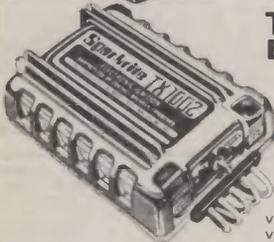

TX 1002 Electronic Ignition

- Inductive discharge ● Extended dwell circuit stores greater energy in coil ● Three position changeover switch ● Contactless or contact breaker triggered ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● Easy to build ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.



TX2002 Electronic Ignition

- Two separate systems in one unit! ● Reactive Discharge OR Inductive Discharge, with three position changeover switch ● Gives highest possible spark energy ● Clip-to-coil or remote mounting ● Rugged die-cast case ● Contactless or contact breaker triggered ● Contactless adaptors included for majority of 4 & 6 cylinder vehicles ● For details of vehicles fitted by contactless trigger, ring Technical Service Dept on (0922) 611338-9.

AT-40 Electronic Car Alarm


- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed using concealed switch ● 30 second delay-to-arm, 7 second entry delay ● Can alternatively be wired to exterior key switch ● Flashes headlights & sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Low consumption C-MOS circuitry.



NEW

AT-80 Electronic Car Security System

- Guards doors, boot, bonnet from unauthorised entry ● Armed/disarmed from outside vehicle by magnetic key fob passed across sensor pad adhered to inside of windscreen ● Individually programmable code ● 30 second delay-to-arm ● Flashes headlights and sounds horn intermittently for 60 seconds when activated ● Security loop protects accessories ● Function lights to assist setting-up ● Low consumption C-MOS circuitry.

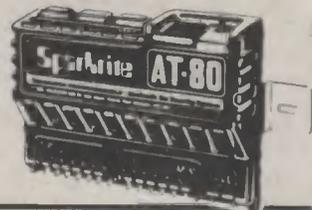

SUPER SAVE

ULTRASONIC Intruder Detector

- Supplementary to AT-40 & AT-80 ● Will work in conjunction with any door switch input or voltage sensing alarm ● Detects attempted break-in and movement within passenger compartment & triggers alarm ● Includes high efficiency ultrasonic transducers ● Crystal controlled for low drift ● Ingenious sensitivity control allows freedom from false alarms ● Low current consumption



NEW

VOYAGER Car Drive Computer

- 12 functions centred on Fuel, Speed, Distance and Time ● Single chip microprocessor ● Large high brightness fluorescent display with auto-dimming feature ● High accuracy distance & fuel transducers included ● Displays MPG, L/100km and miles/litre at the flick of a switch ● Visual & audible warnings of excess speed, ice, lights-left-on ● Independent LOG & TRIP functions ● Low consumption crystal controlled circuitry.



SPECIAL OFFER
"FREE" MAGIDICE KIT WITH
ALL ORDERS OVER £40.00



MAGIDICE Electronic Dice

- Triggered by waving hand over dice ● Completely random selection ● Bleeps & flashes during 4 sec tumble ● Throw displayed for 10 seconds then flashes to conserve battery ● Low consumption C-MOS circuitry.

82 BATH ST., WALSALL WS1 3DE.

SUPER SAVE

SPARKRITE (A Division of Stadium Ltd.) 82 Bath Street, Walsall, WS1 3DE England Tel: (0922) 614791

Allow 28 days for delivery

KIT	OLD PRICE	NEW PRICE
SX 1000	£12.95	£11.95
SX 2000	£18.95	£18.95
TX 1002	£22.95	£22.95
TX 2002	£32.95	£32.95
AT-40	—	£9.95
AT-80	£32.95	£24.95
ULTRASONIC	—	£17.95
VOYAGER	£64.95	£64.95
MAGIDICE	£9.95	£6.95

NEW!
NEW!

NAME _____
ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF. _____

CHEQUE No. _____

PRICES INC. VAT, POSTAGE & PACKING.

PHONE YOUR ORDER WITH



EE/12/83

BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

BI-PAK BARGAINS

TRIACS - PLASTIC

4 AMP - 400v - TQ22 - TAG 136G	
1 OFF	10 OFF
40p	£3.75
8 AMP - 400v - TQ220 - TAG 425	
60p	£5.75
	100 OFF
	£30.00
	£50.00

MINIATURE FM TRANSMITTER

Freq: 95-106MHz. Range: 1/2 mile
Size: 45 x 20mm. Add: 9v batt.
Not licenced in U.K. **ONLY £5.50**
Ideal for: 007-M15-FBI-CIA-KGB etc.

PROGRAMMABLE UNIUNION TRANSISTOR

PUT case TO106 plastic MEU22 Similar to 2N6027/
6028 PNP Silicon
Price: 1-9 10-49 50-99 100+
Each 20p 18p 15p 13p
Normal Retail Price £0.35 each.

VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/2 Watt Pre-Formed	£1.00
VP3	200	1/2 Watt Min Carbon Resistors Mixed	£1.00
VP4	150	1/2 Watt Resistors 100 ohm - 1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc 1pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc. 68pf - 015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	L280 Type Caps Metal Foil Mixed	£1.00
VP11	100	Electrolytics - All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 56pf - 150pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	50	High Voltage Disc. Ceramic 750v - 8Kv Mixed	£1.00

VALUE PACKS

Pak No.	Qty	Description	Price
VP16	50	Wirewound Res. 9W (avg) Ass. 1 ohm - 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Rocker Switches 5 Amp 240v	£1.00
VP21	20	Pcs 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00

VALUE PACKS

Pak No.	Qty	Description	Price
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots 40 mm 22K 5 x Log 5 x Lin	£1.00
VP25	10	Slider Pots 40 mm 47K 5 x Log 5 x Lin	£1.00
VP26	20	Small .125" Red LED'S	£1.00
VP27	20	Large 2" Red LED'S	£1.00

TRANSISTOR CLEARANCE

All Sorts Transistors, A mixed Bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack Includes Instructions For Making Simple Transistor Tester. Super Value. Order No VP60 **£1.00**

SEMICONDUCTORS FROM AROUND THE WORLD

100 A collection of Transistors, Diodes, Rectifiers & Bridges SCR's, Triacs, I.C.'s & Opto's all of which are current every-day useable devices.

Guaranteed Value Over £10 Normal Retail Price.

Data etc in every pack. Order No. VP56
Our Price **£4.00**

BI-PAK'S OPTO SPECIAL

A selection of large and small sized LED's in various shapes, colours, together with 7 Segment Displays both anode & cathode plus photo transistors emitters and detectors. Cadmium Cell ORP12 and Germ. photo transistor OCP71 included. In all a total of 25 Opto pieces valued over £12 Normal Price

Order No. VP57
Our Super Value
Price Just **£5.00**

VALUE PACKS

Pak No.	Qty	Description	Price
VP28	10	Rectangular 2" Green LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vts. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vts. Coded	£1.00
VP31	10	5 Amp SCR's TO-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR's TO-66 Up To 400v Uncoded	£1.00
VP33	200	Sil. Diodes Switching Like IN4148 DO-35	£1.00
VP34	200	Sil. Diodes Gen. Purpose Like DA200/BAX13/16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP36	8	Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vts. Coded	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1/2" Std	£1.00
VP42	10	Black Heatsinks To Fit TO-3, TO-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x TO-3 2 x TO-66 Size	£1.00
VP44	1	Large Power Heatsink 90 x 80 x 35 mm Drilled For Up To 4 TO-3 Devices	£1.00
VP45	50	BC107/8 Type NPN Transistors Good Gen. Purpose Uncoded	£1.00
VP46	50	BC177/8 Type PNP Transistors Good Gen. Purpose Uncoded	£1.00
VP47	10	Silicon Power Trans. Similar 2N3055 Uncoded	£1.50

TEACHIN 84

Complete kit of component parts.
Price **£21.50**

BI-PAK SOLDER - DESOLDER KIT

Kit comprises: ORDER NO. VP80
1 High Quality 25 watt General Purpose Light Weight Soldering Iron 240v mains incl 3/16" (4.7mm) bit
1 Quality Desoldering Pump High Suction with automatic suction knurled anti-corrosive casing and Teflon nozzle
1.5 metres of De-Soldering braid on plastic dispenser
2 yds (1.83m) Resin Cored Solder on Card
1 Heat Shunt tool tweezer Type
Total Retail Value over **£12.00**
OUR SPECIAL KIT PRICE **£9.95**

DIGITAL VOLT METER MODULE

3 x 7 segment displays Basic Circuit. 0-2v instructions provided to extend voltage & current ranges Operating voltage 9/12v. Typ. Power Consumption 50mA
O/No. VP99 Once only price **£9.95**

SINGLE SIDED FIBREGLASS BOARD

Order No	Pieces	Size	Sq. Ins	Price
FB1	4	9 x 23"	100	£1.50
FB2	3	11 x 3"	100	£1.50
FB3	4	13 x 3"	156	£2.00

DOUBLE SIDED FIBREGLASS BOARD


Order No	Pieces	Size	Sq. Ins	Price
FB4	2	14 x 4"	110	£2.00

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 3 x Twist Bits
1 Sheet PCB Transfers 210mm x 150mm
1 Etch Resist Pan
1 1/2 pack FERRIC CHLORIDE crystals
3 sheets copper clad board
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards
Retail Value over **£15.00**
OUR BI-PAK SPECIAL KIT PRICE **£9.95**
ORDER NO. VP81

SILICON BRIDGE RECTIFIERS

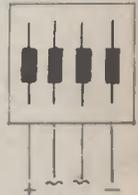Comprising 4 x 1 1/2 Amp rectifiers mounted on PCB. VRM - 150 vits IFM - 1.5 Amps



Size: 1 inch square
10 off £1.00
50 off £4.50
100 off £7.50

ORDER NO: 4R1 B
Rect.

HYBRID LED COLOUR DISPLAYS

Red, Green, Yellow - .3/.5/.6 inch Mixed types and colours NUMERIC & OVER-FLOW Common Anode/Cathode. GaAsP/GaP. Brand New, Full Data incl.

10 pieces (our mix) **£4.00**
Normal Retail Value Over **£10.00**
Order No. VP58

IC BARGAINS

VP40	30	Assorted 74 Series TTL I.C.'s Gates, Flip-Flops & M.S.I.'s + Data Book. All New. Normal Retail Value Over £5.00.	£2.50
VP41	30	Assorted CMOS I.C.'s CD4000 Series Pack Includes 00/09/12/14/18/21/23/25/28/30/35/44/68 AY/AE Types Plus Data Sheet Value Over £8.00. Normal retail.	£2.50

YOU MAY ORDER any ONE TYPE of the above CMOS at £2.00 per 25 pieces. ORDER AS VP41 + type number required.

RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size. 2 cross point size 4 & 6. 1 Ratchet handle. 5-in-1 Kit **£1.45** each. O/No 329B

INTRUSION ALARM

The DOOR BIRD DB 2000 alerts you before your door is opened. Just hang on the inside door knob - alarm is activated as soon as the outside door knob is touched.



ONLY **£3.95**

OUR GREAT NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

Send your orders to Dept. EE12 BI-PAK PO BOX 6, WARE, HERTS. SHOP AT 3 BALDOCK ST., WARE, HERTS.
TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182, GIRD 388 7006.
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 75p per Total order.

BI-PAK

T.V. SOUND TUNER BUILT AND TESTED



£24.95 + £2.00 p&p.
E.T.I. kit version of above without chassis, case and hardware. £12.95 plus £1.50 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 3/4" x 8 1/2" x 3 3/4".

PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT



£32.95 + £2.75 p&p.

• NOISE REDUCTION SYSTEM • AUTO STOP • TAPE COUNTER • SWITCHABLE E.O. • INDEPENDENT LEVEL CONTROLS • TWIN V.U. METER • WOW & FLUTTER 0.1% • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts. I.e. semiconductors, resistors capacitors, hardware top cover, printed scale and mains transformer. You only supply solder and hook-up wire. Featured in April issue P.E. Reprint 50p. Free with kit. Self assembly simulated wood sleeve — £4.50 + £1.50 p&p.

SPECIAL OFFER!
£31.00 plus £2.75 p&p
Complete with case.

STEREO CARTRIDGES



PHILIPS
Magnetic cartridge with diamond stylus. Model No. GP-397 III. Output: 2mV. Separation 22dB. Stylus 0.6mm diameter. **£3.95 each** plus 60p P&P.

GARRARD
Sonotone Garrard Ceramic cartridge. 75mV. With turnover Sapphire stylus. **£2.95 plus 60p p&p.**



SPEAKER KIT 2 WAY 10 WATT


8" bass/mid range and 3 1/4" tweeter. Complete with screws, wire, crossover components and cabinet. Cabinet comes in flat pre-mitred D.I.Y. form. Finish - chipboard covered wood simulate. size 14 1/2" x 8 1/2" x 4". **PAIR for ONLY £12.50 plus £1.75 p&p.**



MONO MIXER AMP

Ideal for Church halls & Clubhouses. **£45.00** + £2.00 p&p.

50 WATT Six Individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux. inputs. Size: 13 1/2" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

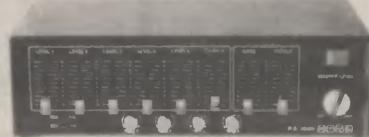

Matching AKG Microphone to suit (with speech and music filter). Complete with lead. **ONLY £9.95 plus 75p p&p.**

VHF STEREO TUNER KIT



• **SPECIAL OFFER!** •
£13.95 Plus £2.50 p&p.

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July '81 Issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System. **FEATURES:** VHF, MW, LW Bands, Interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to strict P.E. specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

HI-FI TWEETER BARGAIN

GOODMANS TWEETERS
8 ohm soft dome radiator tweeter or (3 3/4" sq.) for use in up to 40W systems; with 2 element crossover. **£3.95 each** (p&p £1) or **£6.95 pair** (p&p £1.50)



AUDAX 8" SPEAKER

HIGH QUALITY 40 WATTS RMS BASS/MIDRANGE

Ideal for either Hi-Fi or Disco use this speaker features an aluminium voice coil a heavy 70 mm diameter magnet. Frequency res: 20Hz to 7kHz. Impedance: 8 ohms.



£5.95
+£2.20 p&p

125W HIGH POWER AMP MODULES

KIT £10.50 + £1.15 p&p
BUILT £14.25 + £1.15 p&p

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and Instructions.

ACCESSORY: Stereo/mono mains power supply kit with transformer. **£10.50 plus £2.00 p&p.**



SPECIFICATIONS:

Max. output power (RMS): 125W.
Operating voltage (DC): 50 - 80 max.
Loads: 4 - 16 ohms.
Frequency response measured @ 100 watts: 25Hz - 20KHz.
Sensitivity for 100 watts: 400mV @ 47K.
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.
Dimensions: 205 x 90 and 190 x 36 mm.

STEREO CASSETTE DECK

Stereo cassette tape deck transport with electronics. Manufacturer's surplus - brand new and operational - sold without warranty.

£11.95
plus £2.50 p&p.

Just requires mains transformer and input/output sockets and a volume control to complete.

Supplied with full connection details.



All mail to:
21A HIGH STREET, ACTON W3 6NG.
Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/9/83 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to up-

date their products without notice. All enquiries send S.A.E.

ALL CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432.
(5 minutes walk from Edgware Road Tube Station)
Now open 6 days a week 9 - 6. Prices include VAT.

Telephone or mail orders by ACCESS welcome.





ENFIELD ELECTRONICS

208 Baker Street, Enfield,
Middlesex. EN1 3JY Tel: 01-366 1873



TRANSISTORS

AC125	30p	BC183C	-12p
AC126	30p	BC183L	12p
AC127	30p	BC183BL	12p
AC128	30p	BC184	12p
AC132	30p	BC184B	12p
AC141	30p	BC194L	12p
AC142	30p	BC186	30p
AC176	30p	BC187	30p
AC187	30p	BC212A	14p
AC188	30p	BC212L	12p
AD149	80p	BC213	12p
AD161	45p	BC213B	12p
AD162	45p	BC213L	12p
BC107	12p	BC214	12p
BC107A	14p	BC214B	14p
BC107B	14p	BC214L	14p
BC108	12p	BF194	14p
BC108A	14p	BF196	14p
BC108B	14p	BF198	14p
BC108C	14p	BF199	14p
BC109	14p	BF200	35p
BC109B	14p	BF224B	35p
BC109C	14p	BF244B	35p
BC140	35p	BF256	35p
BC141	35p	BF257	35p
BC142	35p	BF258	35p
BC143	35p	BF259	35p
BC147	12p	BF584	40p
BC148	12p	BF595	30p
BC157	12p	BF939	20p
BC158	12p	BF979	30p
BC159	12p	BF980	30p
BC160	12p	BF981	30p
BC161	12p	BF982	30p
BC167	15p	BF985	30p
BC168	12p	BF987	30p
BC169	12p	BF988	30p
BC170	20p	BF990	28p
BC171	13p	BF991	22p
BC172A	13p	BF992	22p
BC173	13p	BF993	22p
BC177	20p	BR939	40p
BC178	20p	BSK20	30p
BC179	20p	BSK29	35p
BC181	20p	BU105	20p
BC182	12p	BU205	20p
BC182B	14p	BU208A	22p
BC182L	12p	MJE295	90p
BC183	12p	MJE340	50p
BC183B	12p	MJE371	90p

MJE2955	110p	ZTX303	20p	2N1304	80p
MJE3055T	80p	ZTX304	20p	2N1305	80p
MPSA06	25p	ZTX330	35p	2N1307	70p
MPSA56	30p	ZTX500	18p	2N1308	80p
MPSU05	85p	ZTX501	18p	2N1613	36p
MPSU56	60p	ZTX502	18p	2N2222A	30p
OC22	150p	ZTX503	18p	2N2369A	28p
OC23	150p	ZTX504	30p	2N2646	68p
OC26	100p	ZTX531	30p	2N2904A/5A	30p
OC28	200p	ZTX550	30p	2N2906A	60p
OC36	220p	ZTX596	35p	2N2907A	60p
OC41	75p	2N698	45p	2N2926G	12p
OC42	75p	2N699	45p	2N2926R	12p
OC43	75p	2N706A	26p	2N2926Y	12p
OC76	60p	2N708	30p	2N3053	30p
OC81	60p	BC237	18p	2N3054	75p
OC82	60p	BC238B	18p	2N3055E	60p
OC84	50p	BC307	18p	2N3442	150p
OC85	50p	BC308	14p	2N3615	200p
OC86	50p	BC327	16p	2N3702	12p
OC87	50p	BC337	16p	2N3704	12p
OC88	50p	BC338	16p	2N3705	12p
OC89	50p	BC441	36p	2N3706	12p
OC90	50p	BC461	36p	2N3707	12p
OC91	50p	BC477	36p	2N3708	12p
OC92	50p	BC478	36p	2N3710	12p
OC93	50p	BC479	36p	2N3711	12p
OC94	50p	BC487	36p	2N3712	12p
OC95	50p	BC488	36p	2N3713	12p
OC96	50p	BC489	36p	2N3714	12p
OC200	50p	BC593	36p	2N3818	12p

TTL

7400	18p	7417	28p	7447	75p	7486	35p	74119	70p	74160	65p	74190	58p
7401	18p	7420	20p	7448	50p	7489	140p	74121	35p	74161	55p	74191	55p
7402	18p	7421	28p	7450	21p	7490	37p	74122	41p	74162	46p	74192	55p
7403	18p	7422	28p	7451	20p	7491	45p	74123	41p	74163	46p	74193	55p
7404	18p	7423	28p	7452	20p	7492	40p	74124	70p	74164	46p	74194	52p
7405	18p	7424	28p	7453	21p	7493	41p	74125	65p	74165	60p	74195	52p
7406	32p	7425	30p	7454	21p	7494	41p	74126	50p	74166	60p	74196	55p
7407	32p	7426	30p	7455	21p	7495	41p	74127	50p	74167	60p	74197	55p
7408	32p	7427	30p	7456	21p	7496	41p	74128	50p	74168	60p	74198	55p
7409	32p	7428	30p	7457	21p	7497	41p	74129	50p	74169	60p	74199	55p
7410	18p	7429	25p	7458	21p	7498	41p	74130	50p	74170	60p	74200	55p
7411	26p	7430	25p	7459	21p	7499	41p	74131	50p	74171	60p	74201	55p
7412	26p	7431	25p	7460	21p	7500	41p	74132	50p	74172	60p	74202	55p
7413	26p	7432	25p	7461	21p	7501	41p	74133	50p	74173	60p	74203	55p
7414	26p	7433	25p	7462	21p	7502	41p	74134	50p	74174	60p	74204	55p
7415	26p	7434	25p	7463	21p	7503	41p	74135	50p	74175	60p	74205	55p
7416	26p	7435	25p	7464	21p	7504	41p	74136	50p	74176	60p	74206	55p
7417	26p	7436	25p	7465	21p	7505	41p	74137	50p	74177	60p	74207	55p
7418	26												

EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 12 NO. 12 DECEMBER 1983

Editor

F. E. BENNETT

Assistant Editor

B. W. TERRELL B.Sc.

Production and News Editor

D. G. BARRINGTON

Projects Editor

G. P. HODGSON

Technical Sub-Editor

R. A. HOOPER

Art Editor

R. F. PALMER

Assistant Art Editor

P. A. LOATES

Technical Illustrator

D. J. GOODING Tech. (CEI)

Secretary

JACQUELINE DOIDGE

Editorial Offices

KING'S REACH TOWER
STAMFORD STREET
LONDON SE1 9LS
Phone: 01-261 6873

Advertisement Manager

R. SMITH
Phone: 01-261 6671

Representative

R. WILLET
Phone: 01-261 6865

Classified Supervisor

B. BLAKE
Phone: 01-261 5897

Make-Up and Copy Department

Phone: 01-261 6615

Advertisement Offices

KING'S REACH TOWER
STAMFORD STREET
LONDON SE1 9LS

QUITE SIMPLE

SMALL is beautiful. This adage has relevance to our hobby. Experienced constructors will agree that satisfaction derived from one's efforts is not directly proportional to the component count nor to the overall complexity of the design. A simple circuit using few, if indeed any, i.c.s can provide much enjoyment during its construction and this enjoyment is compounded when the completed project is seen to give pleasure (however simple and innocent) to others.


Computer projects apart, our complement of designs in this final issue for the year is unashamedly biased towards the simple and novel—in particular to projects having a part to play over the Christmas period. In this age of video and computer games, and other kinds of sophisticated electronic toys, it may be questioned whether interest can be aroused in so modest a device as a *Magic Candle*; or whether children will be attracted and excited by a flashing light display emitting merely a watt or two of illumination. But surely it will be a sad state of affairs if over-exposure to high-technology-based consumer products jades our ability to be enthralled and amused by unpretentious objects. And this applies most especially in the case of young children.

At this time, Christmas presents are uppermost in our minds and suggestions are always welcome. Well here's one. Egg-timers are not exactly a rarity, but this month's design is novel in that it generates a reasonable imitation of a clucking chicken. Perhaps a useful and amusing gift to make for ma or the wife?

ANOTHER SCHOOLS WINNER

The *Environmental Data Recorder* featured in this issue won for its schoolgirl and schoolboy designers the third prize in this year's Schools Electronic Design Award Competition. It provides yet another fine example of the enterprise and technical ability that exists amongst scholars in our secondary schools. Though conceived and designed with science department studies in mind, the *Environmental Data Recorder* is likely to find many uses amongst personal computer owners.

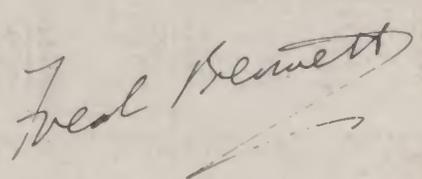It is hoped that the appearance of this article will also act as a reminder—and a stimulant—to scholars throughout the UK who have produced an interesting piece of electronic equipment to enter this year's SEDAC. Schools please note that Registration should be made by November 30, 1983.



Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in *EVERYDAY ELECTRONICS*, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Back Issues

Certain back issues of *EVERYDAY ELECTRONICS* are available worldwide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.


Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.

Subscriptions

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £13.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

TRS-80 TWIN CASSETTE INTERFACE

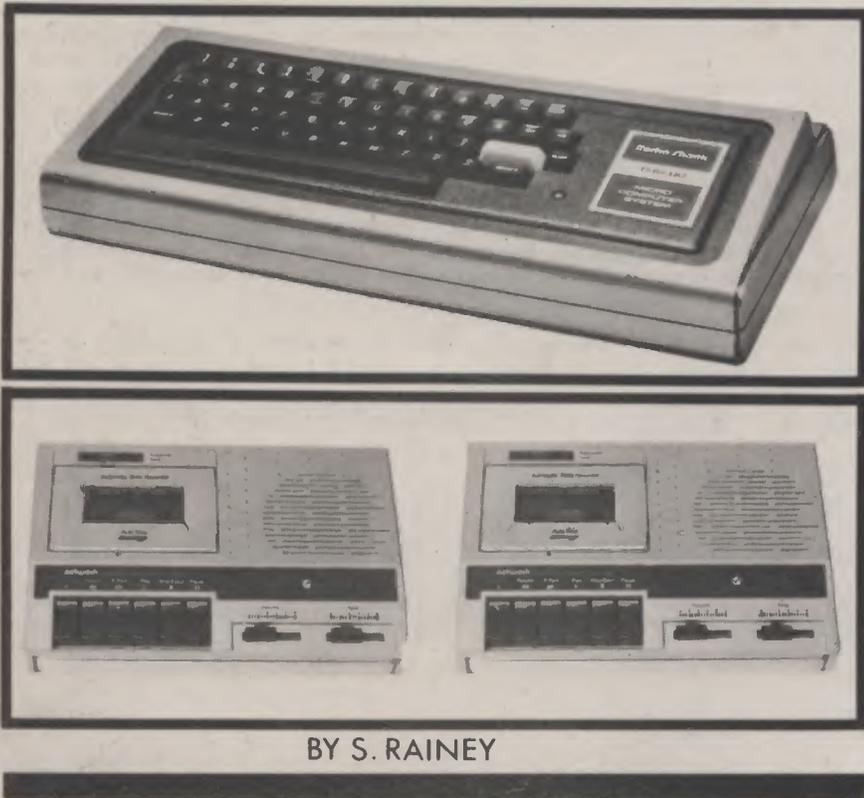

OWNERS of the TRS-80 Model I Level II Microcomputer will know that this computer has the capability of driving two cassette decks. However, with just the basic system, only one may be used, since only one I/O port is provided. On adding the expensive and now discontinued Expansion Interface, two cassette I/O ports are provided. This project provides two cassette ports for the basic system without the need for the Expansion Interface.

CIRCUIT DESCRIPTION

Before the operation of the circuit can be understood it is necessary to understand its purpose. Those familiar with Level II Basic will know that any tape I/O command may have the suffix #-1, or #-2, placed after it. A #-1 denotes that the next cassette I/O must go to cassette deck No. 1, while a #-2 denotes that the I/O must go to cassette deck No. 2.

If the Basic interpreter detects a #-1, then a 00 is written to memory location

37E4H, whereas if a #-2, is detected then FFH is written to this location. In both cases the actual I/O goes through port FFH, the cassette port on the rear of the Model I Console. All that has to be done then is to look at memory location

37E4H and use its state to select either cassette deck.

The circuit consists of four basic sections (see Fig. 1). There is an address decoder which monitors the address bus and when the value 37E4H is present it enables the data latch. The data latch monitors data line 0 and, when enabled, reads and stores the state of this data line.

The output of the data latch, which is an echo of its input, is presented to the relay driver and relays. The relays are used to switch the I/O port between the two cassette decks. Finally, there is a small power supply to power the whole circuit.


ADDRESS DECODER

The address decoder consists of IC1, IC2, IC3a, IC3b, and IC4. To understand its working we must consider the binary equivalent of 37E4H, which is what actually appears on the 16 address lines, see Fig. 2. As can be seen, when this location appears on the address bus, A2, 5, 6, 7, 8, 9, 10, 12 and 13 all go high, that is, they have a potential of 5V. A0, 1, 3, 4, 11, 14 and 15 all go low; they have a potential of 0V. IC1 and IC2 are the major components of the decoder and are 8-input NAND gates. When all eight inputs are high then the output goes low. A2, 5, 6, 7, 8, 9, 10 and 12 are connected to the eight inputs of IC1. See Fig. 3.

As can be seen from Fig. 2, all these address lines go high when 37E4H is addressed and so the output of IC1 will go low. A0 goes low when 37E4H is addressed and this low, along with the low from the output of IC1, is applied to the inputs of the 2-input NOR gate, IC3a. The output of this NOR gate will therefore go high and is applied to one of the inputs of the other 8-input NAND gate, IC2. A1, 3, 4, 11, 14 and 15 all go low when 37E4H is addressed and these are each inverted by one of the six inverters making up IC4. The six highs from the outputs of IC4 are applied to six of the inputs of IC2. Finally, A13, which goes high when 37E4H is addressed, is applied to the last input of IC2. Since all eight inputs of IC2 are now high, the output will go low.

We have now uniquely decoded the memory address 37E4H which appears

Fig. 1. Block diagram of the TRS-80 Twin Cassette Interface.

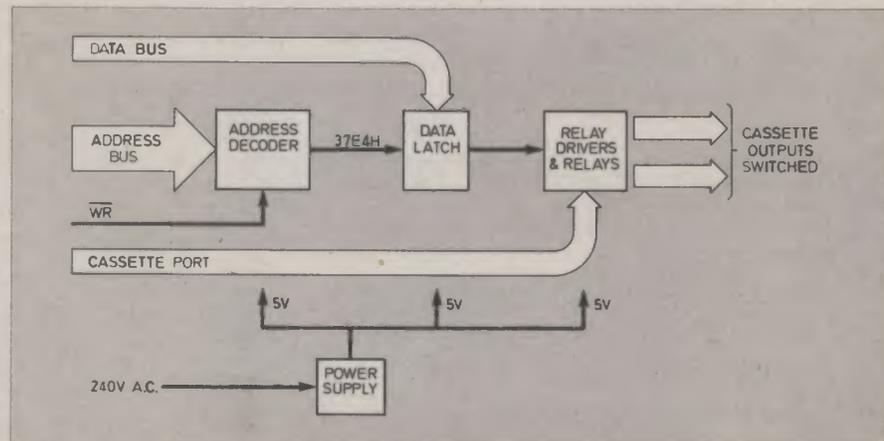

as a low on the output of IC2. It is now necessary to decide whether or not the computer wants to write to or read from this memory location. If this was not done, the data latch may become active at the wrong time and hence remember the wrong data.

The computer tells us when it wants to write to a memory location by sending a low on its WR output. The "bar" means that this output is true when it is low and hence is normally high.

The WR signal is connected to one of the inputs of IC3b, a 2-input NOR gate. The output of IC2 (the output of the address decoder) is connected to the other input of IC3b. Since both inputs of IC3b will be low when the computer wants to write to 37E4H, the output will go high. This output is used to control the data latch, IC5.

DATA LATCH

The data latch consists of a D-type flip-flop which forms half of IC5. For

ADDRESS LINE	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0	
STATE	0	0	1	1	0	1	1	1	1	1	0	0	1	0	0		= 37E4H
	0 = 0V 1 = 5V																

Fig. 2. Binary state of the TRS-80 address bus at 37E4H.

those unfamiliar with the operation of the D-type flip-flop, a brief description is given.

This type of flip-flop has two inputs and two outputs. One input is the D, or data, input and the other is the CLK, or clock input. The two outputs are Q and \bar{Q} .

If the CLK input is kept low then the outputs remain in a constant state no matter what signal is present at the D input.


However, when the CLK input is taken high, the outputs begin to echo the signal at the D input. Q takes the same state as the D input while \bar{Q} takes the opposite state. When the CLK input goes low then whatever state is present on the D input

will be latched into the flip-flop and remembered until another high CLK step.

The outputs will be kept in their respective states, whatever they were when the CLK input went low.

The D input of the flip-flop IC5 is connected to the first data line of the computer, D0. Normally this is changing state many thousand times a second as data is moved about the computer. However, since 37E4H is not being written to, the CLK input of the flip-flop will be low and so the signal at the D input will have no effect.

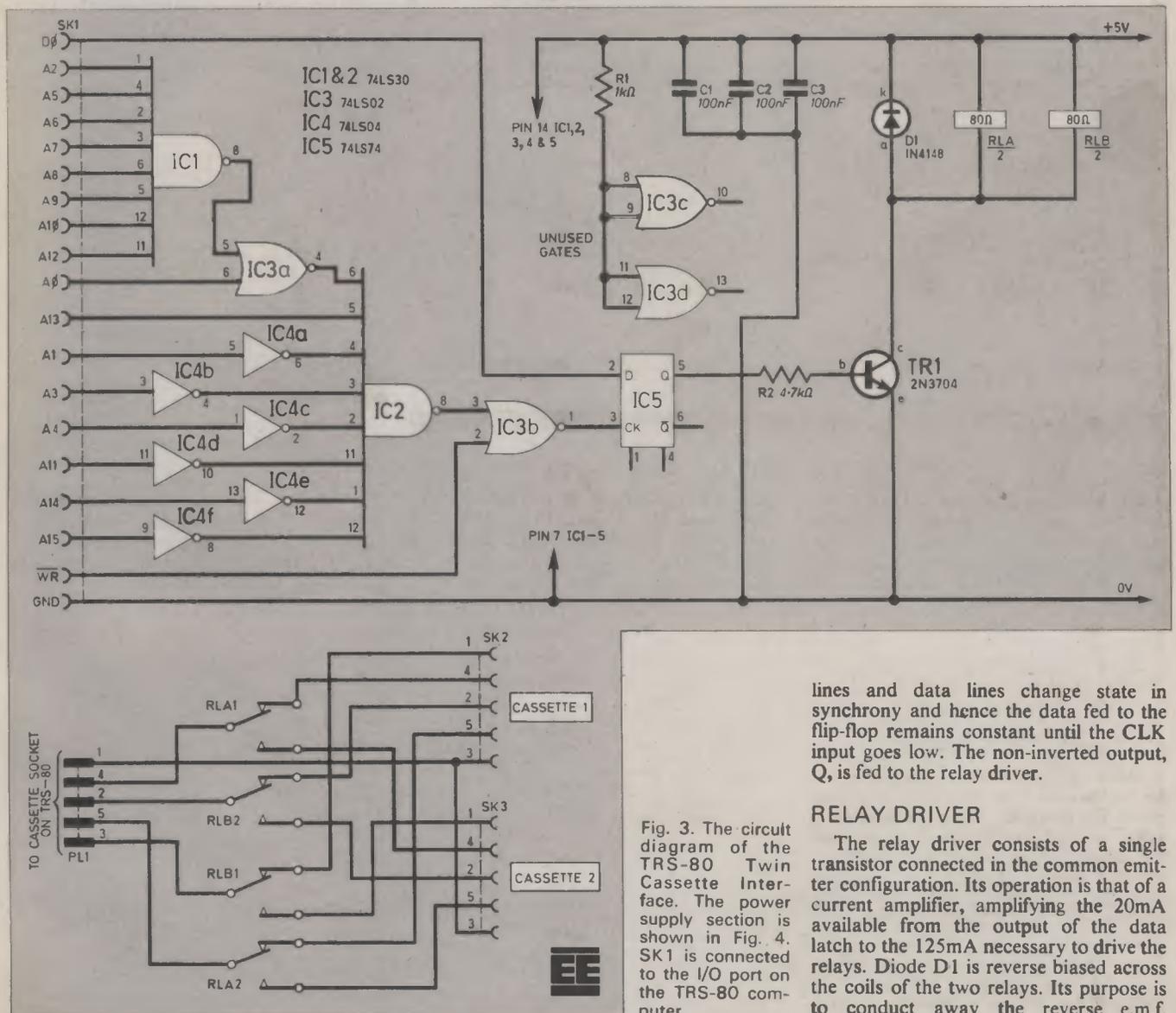
When 37E4H is written to, the CLK input goes high and the state of D0 is latched into the flip-flop. The timing of the computer is such that the address



lines and data lines change state in synchrony and hence the data fed to the flip-flop remains constant until the CLK input goes low. The non-inverted output, Q, is fed to the relay driver.

RELAY DRIVER

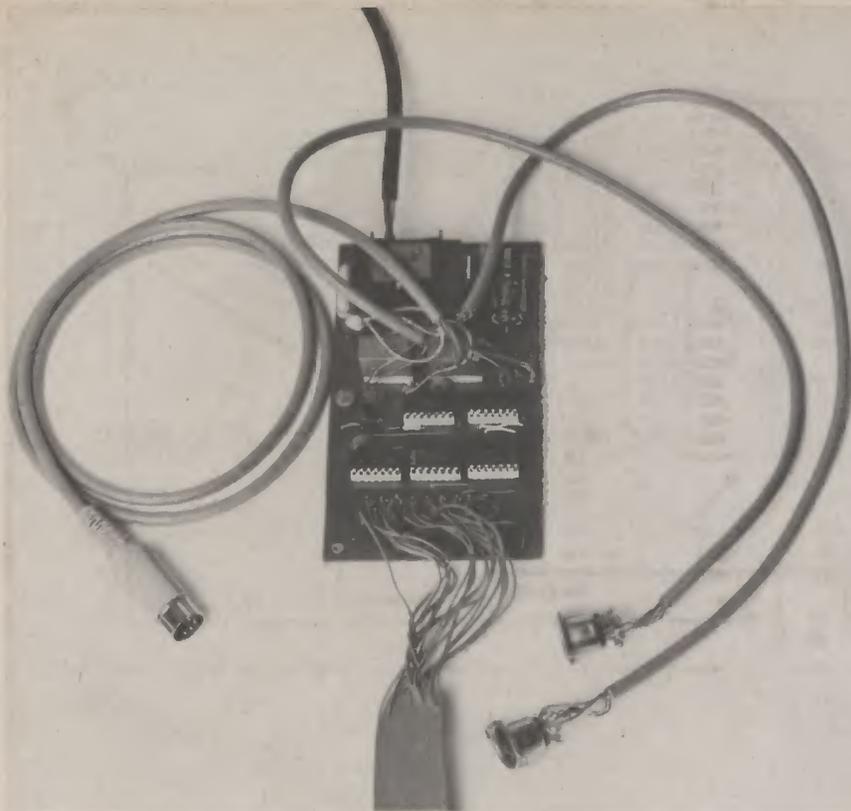The relay driver consists of a single transistor connected in the common emitter configuration. Its operation is that of a current amplifier, amplifying the 20mA available from the output of the data latch to the 125mA necessary to drive the relays. Diode D1 is reverse biased across the coils of the two relays. Its purpose is to conduct away the reverse e.m.f.



produced by the relays as they turn off, and hence protect the transistor.

The contacts of the two relays form four single-pole changeover switches. These are used to switch four of the five data routes from one cassette deck to the other. The only route not switched is the common motor switch connection. Note that it is necessary to switch the earth line as well as the signal paths since otherwise bad hum loops or even cassette malfunctions can occur.

As has already been described, a 00 is written to 37E4H when cassette 1 is to be used and FFH is written to this location when cassette 2 is to be used. Thus the output of the data latch will be low for cassette 1 and high for cassette 2. The relays will be off for cassette 1 and on for cassette 2.

The relay contacts are wired up so as to connect cassette 1 to the cassette port when the relays are off and to connect cassette 2 to the port when the relays are on.

POWER SUPPLY

The power supply is based on the widely known 78 series of voltage regulators. The output of T1 is 6V a.c. and this is rectified by D3-D6, a bridge rectifier. Smoothing of the supply is achieved using C6, a 1000 μ F electrolytic capacitor. The 8.5V d.c. across C6 is applied to the input of IC6, a 5V, 500mA positive voltage regulator. The output of IC6 is +5V d.c. C4 is placed across the output of the regulator to reduce any high frequencies on the supply line. R3 and

D2, an l.e.d., form an indicator to tell when the interface is on. See Fig. 4.

Finally, C1, C2 and C3 are placed around the circuit to further decouple the supply for the TTL i.c.s. IC3c and IC3d have their inputs connected to +5V via R1, a 1k Ω resistor. This is done since floating inputs are damaging to TTL i.c.s.

PRINTED CIRCUIT BOARD

It is recommended that the circuit be built on a printed circuit board since the many interconnections become difficult on stripboard. Once the p.c.b. has been made up, preferably using glass-fibre board, it should be scrutinised for bridges between the tracks.

The actual-size master printed circuit board pattern used for the prototype is shown in Fig. 5. This is available from the *EE PCB Service*, Order code 8312-03. The layout of the components on the topside of this board is also shown in Fig. 5.


Using a fine tipped soldering iron and thin solder, construction can begin. Start by soldering in all the wire links followed by the Veropins, if these are to be used. Next, solder in the i.c. sockets. The relays are best mounted in low profile i.c. sockets, since otherwise removal will be difficult should they become faulty.

Mount the resistors and capacitors next, ensuring C6 is fitted the right way round. Now fit the transformer and finally solder in the transistor and voltage regulator. Ensure these latter components are fitted correctly.

After fitting the diode, the i.c.s may be inserted, checking their orientation is correct. Now fit the relays. The main board is now finished.

Some method of connecting the main board to the expansion socket on the Console is necessary, and a good method, especially if another peripheral is connected, is to make the header shown in Fig. 6. A double-sided p.c.b. is soldered to a 40-way edge connector and also forms an edge connector for another peripheral. Taps are taken from the appropriate lines using Veropins. Although not the neatest way of making connection, it is certainly effective.

Fig. 4. The power supply circuit diagram. Note that the mains earth is not required.

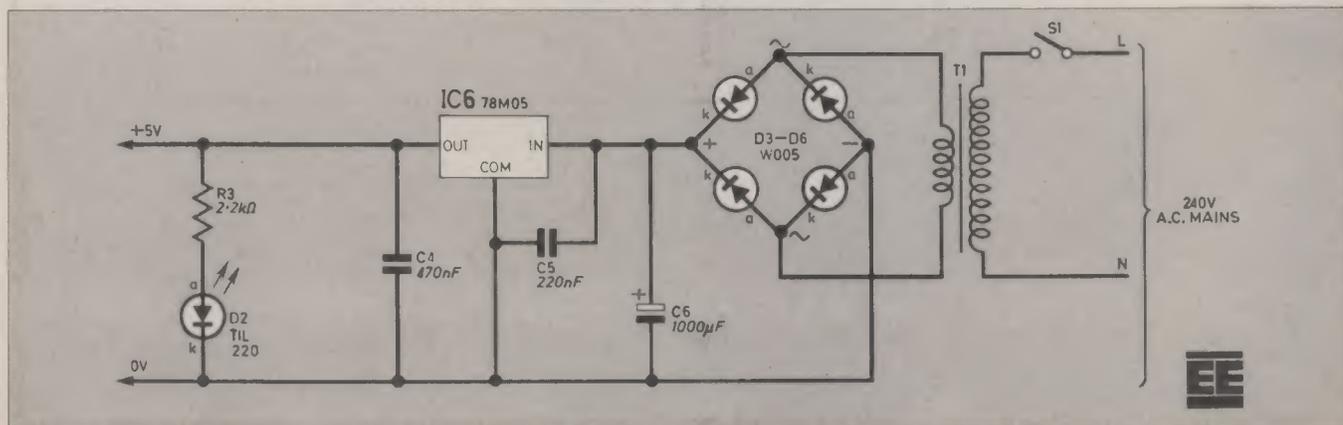

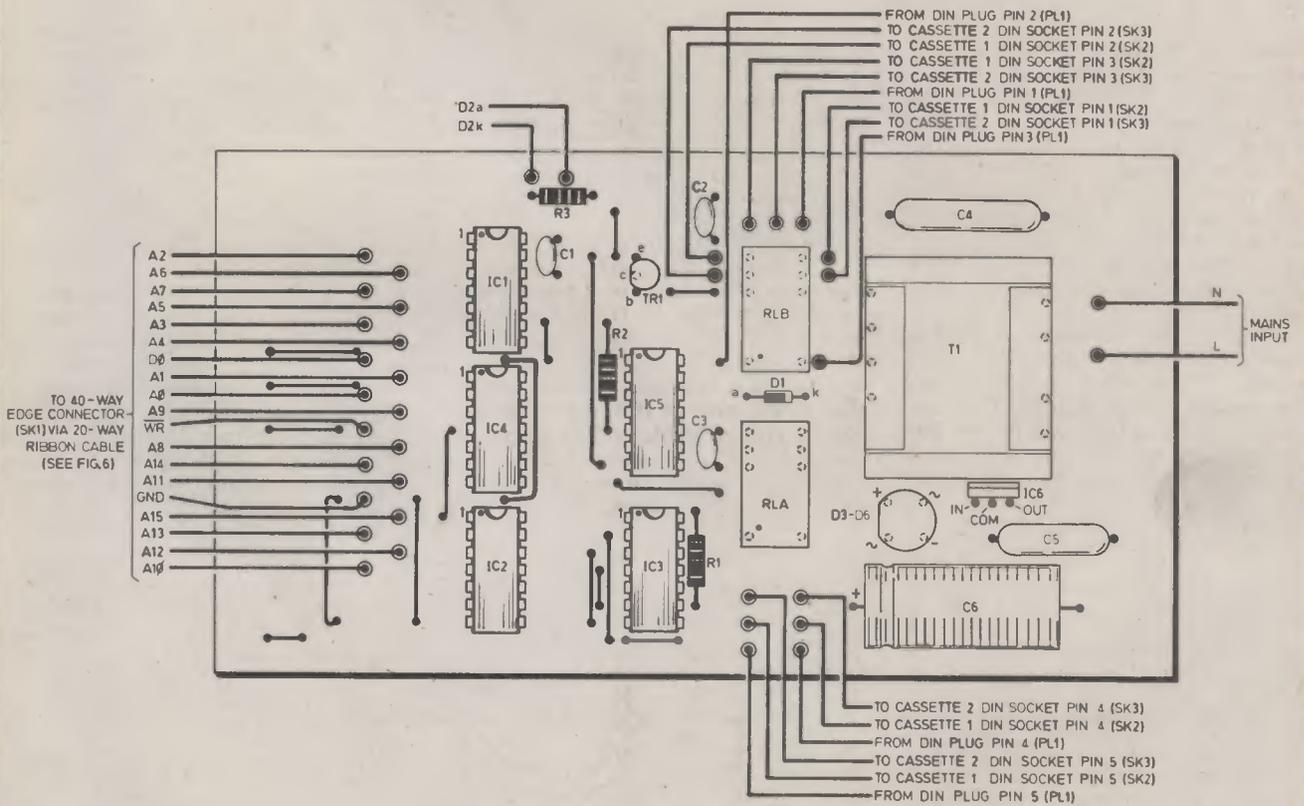
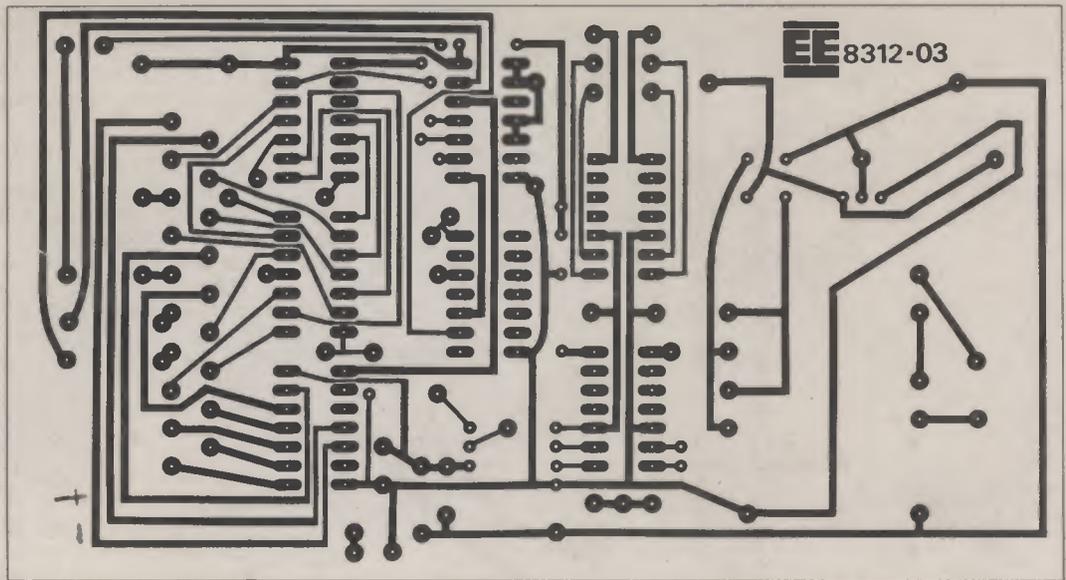


Fig. 5. The full-size p.c.b. track artwork and component layout diagram. This board is available from the *EE PCB Service*, Order code 8312-03. All wires (including the ribbon cable) must be terminated with a Veropin. Note that the mains input cable will require a clamp to act as strain relief at the point of entry on the case.

COMPONENTS

Resistors

- R1 1k Ω
- R2 4.7k Ω
- R3 2.2k Ω
- All $\frac{1}{4}$ W carbon $\pm 5\%$

See
**Shop
Talk**

page 801

Capacitors

- C1,2,3 100nF miniature ceramic
- C4 470nF polyester type C280
- C5 220nF polyester type C280
- C6 1000 μ F 16V elect.

Semiconductors

- D1 1N4148 silicon diode
- D2 TIL220 red l.e.d.
- D3-D6 W005 1A 50V bridge rectifier
- TR1 2N3704 silicon *n*p*n*
- IC1,2 74LS30 TTL low power Schottky 8-input NAND gate (2 off)
- IC3 74LS02 TTL low power Schottky quad 2-input NOR gate
- IC4 74LS04 TTL low power Schottky hex inverter
- IC5 74LS74 TTL low power Schottky dual D-type flip-flop
- IC6 78M05 +5V monolithic voltage regulator

Miscellaneous

- SK1 20 + 20 way double-sided card edge connector
- SK2,3 5-pin DIN 180° socket
- PL1,2 5-pin DIN 180° plug (2 off)
- PL3,4 3.5mm jack plug (2 off)
- PL5 2.5mm jack plug
- S1 s.p.s.t. mains on-off toggle
- T1 mains/0-6V, 0-6V 1.5VA per secondary winding, type Clairtronic 9300
- RLA, RLB Ultra miniature d.i.l. relay, 6V, coil resistance 80 ohms double-pole change-over contacts (Maplin BK48C) (2 off)

Printed circuit boards: single-sided size 135 x 75mm; *EE PCB Service*, Order code 8312-03; double-sided size 53 x 37mm, *EE PCB Service*, Order code 8312-09; single-sided Veropins (72 off); 20-way ribbon cable (1 metre); d.i.l. i.c. sockets, 14-pin (7 off); mains cable (2 metres); 4-core individual screen screened cable (2 metres); 3mm fixing hardware; plastics case, size 160 x 100 x 75mm approximately; tinned copper wire for board links.

Approx. cost
Guidance only

£22
excluding case

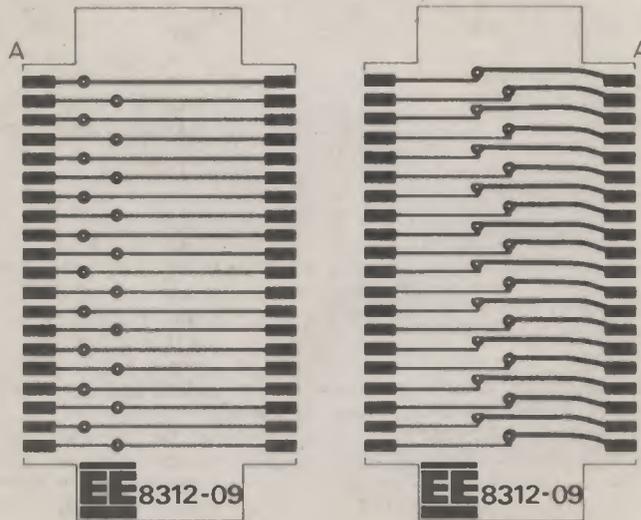
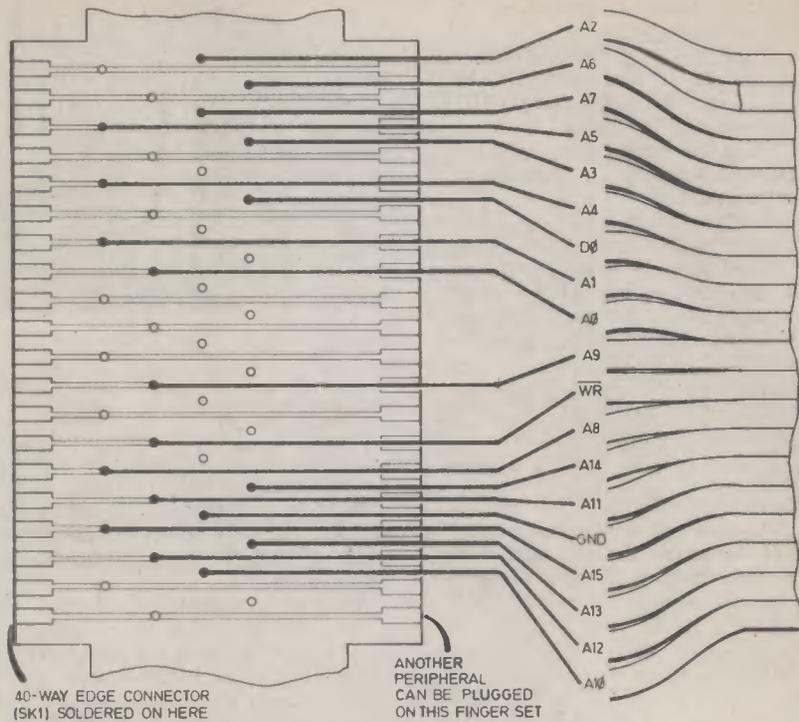


Fig. 6. Full-size track artwork of the double-sided header p.c.b. This board carries the 40-way edge connector (SK1) and also permits additional peripherals to be plugged into the TRS-80 I/O port. Top view shows the ribbon cable wiring.

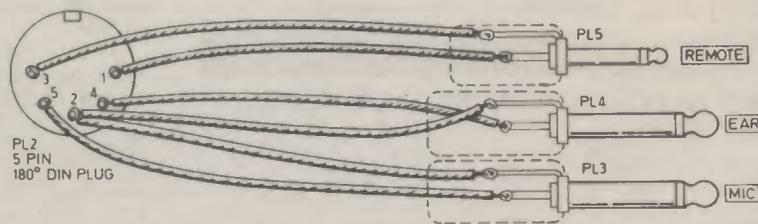


Fig. 7. Wiring of the cassette lead to connect the interface to the cassette player. If the 4-core screen cable is used, the screens must *not* be used for the REMOTE (PL5) connections.

CABLES

A length of 20-way ribbon cable is used to link the header to the main p.c.b., as shown in Figs. 5 and 6.

A length of four-core screened cable is used to connect the cassette port to the p.c.b. A 5-pin 180° DIN plug (PL1) should be soldered on the end of this as shown. Using the same cable, two 5-pin 180° DIN sockets (SK2 and SK3) are wired to the board.


The whole project may be fitted into a small plastic box. A metal box is not recommended since it would have to be earthed and the bodies of the DIN sockets are connected to computer ground. A slot may be cut in the end of the box to take the ribbon cable. Remember to pass the cable through this slot before soldering to the main p.c.b. The two output sockets, on/off switch and power indicator can be mounted as desired.

You should already have one cassette lead but another one is required for connection to the second cassette deck. This may be made up from a length of the 4-core screened cable. A 5-pin 180° DIN plug (PL2) is soldered to one end as shown. The other end is stripped back about 100mm and mini-jack plugs are soldered to the ends. Two of the ends have 3.5mm jack plugs (PL3 and PL4) while the third has a 2.5mm plug (PL5). A mark such as a piece of insulation tape wrapped around the plug should be made on the plug which goes to the ear socket of the cassette deck. The connections for this lead are shown in Fig. 7.

If the recommended four-core individual screen cable is used, then none of the screens should be used in the cassette motor control circuit (REMOTE). Instead, two of the insulated cores should be used.

TESTING

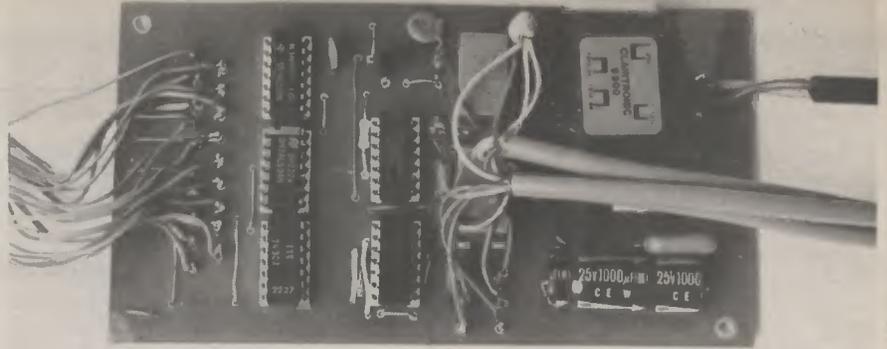First, connect the header to the expansion port of the keyboard Console. Ensure the header is the right way round. With the interface turned off and disconnected from the mains, switch on the computer. If all is well, the familiar MEMORY SIZE? will appear. Press



The complete prototype printed circuit board assembly.

<ENTER>. If the READY prompt appears, then all is well with the wiring. If anything unusual happens, check the connections at both ends of the ribbon cable and also check for solder bridges between tracks of both the main and header printed circuit boards.

With the computer turned off, switch on the interface. The two relays should click on. If not, check the main board for broken tracks or solder bridges. If the power light does not come on then, check out the power supply first. If the l.e.d. glows very bright, then it is probably the voltage regulator at fault. Should the relays click on, then switch on the TRS-80. All should be well, but if not it will either be IC1, IC2 or IC3 at fault.

To the MEMORY SIZE? prompt press <ENTER>. Once in Basic enter POKE 14308,0

The relays should switch off. If so, enter

POKE 14308,255

The relays should switch on. If all is well, continue at the next paragraph. If not, it could be any one of the i.c.s at fault. Check the connections to each one in turn and ensure that no links are missing. Note that there is a link underneath one of the i.c. sockets and this may have been missed out.

Next, connect the interface to the cassette port and connect two cassette

decks to the interface. Place a tape with a program on it into cassette 1 and set it to play.

Type in
CLOAD#-1

The cassette should turn on and the program should load. If not, check the wiring to the relays and the lead to the cassette port. If all this fails it is probably a fault with one of the relays.

If all is well, then insert a tape with a program on it into cassette 2.

Type in
CLOAD#-2


The cassette should turn on and the program load. If not, check out the wiring as for the first cassette. Now test the saving by loading a program and entering either

CSAVE#-1, "A" or CSAVE#-2, "A" as appropriate.

IN USE

In use, the interface may be left turned off if only one cassette is required. However, it should not be turned on while the computer is on else the computer will probably crash. All the usual cassette I/O commands may be used, but now with the suffix #-1, or #-2. For CSAVE or CLOAD there is no need to add the suffix if the first cassette is to be used. □

BOOK REVIEWS

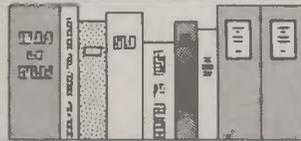

BASIC ELECTRICAL INSTALLATIONS 3rd EDITION

Author M. Neidle
Price £3.95 Limp edition
Size 254 x 229mm. 77 pages
Publisher Macmillan Press
ISBN 0 333 34681 5

FOR students following electrical installation courses this book should provide some very useful reference material. All the

material contained within has been thoroughly revised in line with new installation developments and techniques.

The book contains 13 chapters starting with basic electrical theory and finishing up with an introduction to the electrical installation industry. A welcome addition to this type of book is a chapter dealing with Care and Safety which gives advice on handling materials and equipment, tool care, safety at work, electric shock treatment, and fire protection.

The text and worked examples are approached in a clear and orderly manner and each new topic has plenty of diagrams to support the text.

R.A.H.

Books in Brief

Electronic Science Projects by O. Bishop (Bernard Babani). Limp £2.25. A different type of electronics book in that all the projects have a strong scientific bias. There are 12 projects starting with A Simple Infra-red Laser and finally a more complex electronic project called Measuring the Earth's Electric Field.



CHILDRENS DISCO LIGHTS

BY T.R. de Vaux - Balbirnie

HAVE SOME PARTY FUN WITH THE CHILDREN'S LIGHT DISPLAY

WHEN the author's eight-year-old wanted some flashing lights for a Christmas party, some careful thought was needed. Mains-operated equipment was banned. A similar ban would also be placed on direct connections to the audio equipment.

When the problem was discussed, it appeared that any small coloured lights would be suitable just as long as they flashed in time to the music.

A circuit was devised which involves no connections to the record-player, operates from a battery and is cheap to construct. A "string" of small coloured bulbs, Christmas tree lamps for example, flash when the music plays. The sound from the audio equipment is picked up by a microphone built into the case of the project. This is interesting since the lights not only respond to music but also to other sounds in the room. Naturally, this system has limitations and is hardly suitable for serious use.

CIRCUIT DESCRIPTION

The circuit diagram for the Children's Disco Lights is shown in Fig. 1. The microphone, in reality a miniature

loudspeaker, LS1 picks up the sound of the music. This gives a weak electrical signal at its terminals which is amplified by TR1 and associated components.

This amplified signal is applied through C2 to the non-inverting input (pin 3) of the operational amplifier IC1. This input also receives a steady 4.5V, approximately, due to the potential divider formed by R3 and R4. VR1, a miniature preset potentiometer, supplies a steady voltage to the inverting input of IC1 (pin 2). Before use VR1 will be adjusted so that the steady voltage at the inverting input is just above that at the non-inverting input. Under these conditions the op-amp will be off with no output at pin 6.

When the music plays there will be a small voltage superimposed on the steady one existing at pin 3. Thus, the voltage here will exceed that at pin 2 and the op-amp will switch on and off in time with the music. The light-emitting diode, D1, in the output circuit of the op-amp will then flash in sympathy. The l.e.d. is necessary to help in adjusting VR1 at the testing stage.

The output pulses need to be lengthened and smoothed to some extent to make them more suitable for operating

filament lamps. This is achieved by D2 and C3. The pulses are then passed onto the Darlington lamp driver stage TR2 and TR3. This operates the bulbs in the collector circuit. VR2 is used to match the output of the op-amp to the lamp driver stage.

No input sensitivity control is included. To adjust the response of the circuit to the loudness of the music, the case is simply moved to the best distance from the record-player loudspeaker.


COMPONENT BOARD

The component board is a piece of 0.1in matrix stripboard having 14 strips by 29 holes and can be seen in Fig. 2. Note that all the 13 breaks in the copper track should be made in the board before any of the components are soldered in place. A holder should be used for IC1 so that damage does not occur to the i.c.

CASE

The plastics case used for the prototype measures 147 x 76 x 45mm although any case of similar size should be suitable. Prepare the case by making a

Fig. 1. The complete circuit diagram for the Children's Disco Lights.

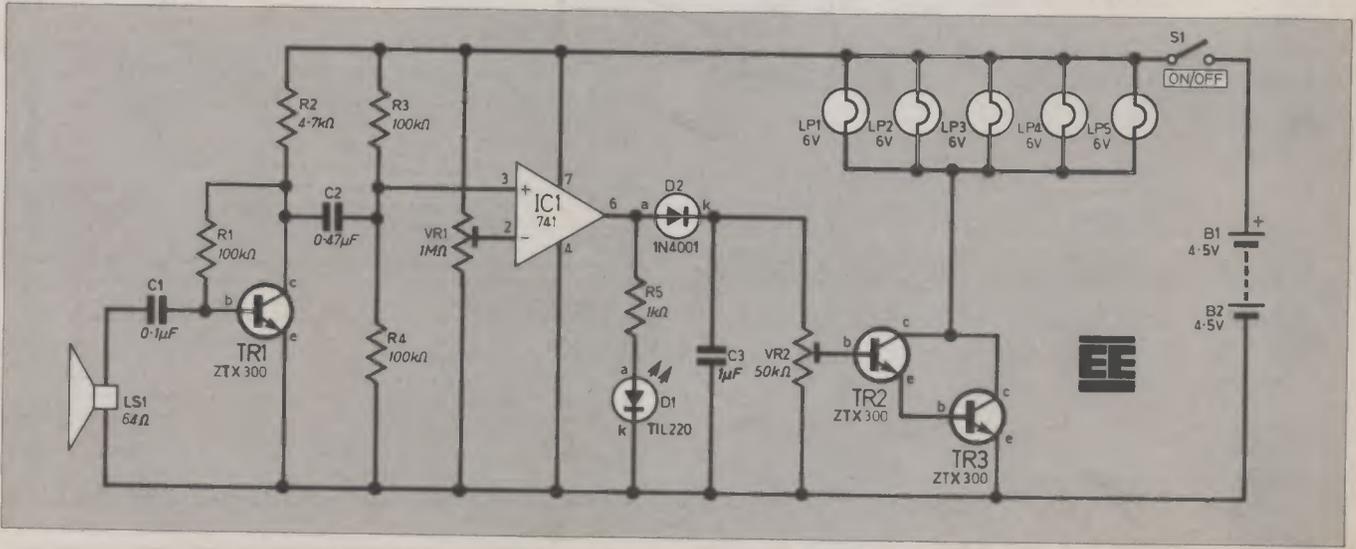

matrix of holes for the loudspeaker, for S1 and for the battery and lamp leads. The loudspeaker is fixed in place using a quick setting epoxy resin.

LAMPS

The lamp driver can handle current up to 500mA, so up to eight 6V, 0.06A lamps may be used in parallel. Alternatively, Christmas tree lights may be used as in the prototype. These must be of the 6V-type normally used in 240V, 40 lamp sets. Direct solder joints may be made to the lamps which are then connected in parallel as shown in Fig. 2.

Note: up to six Christmas tree lamps may be used but only five are shown connected on the prototype.

ADJUSTING AND TESTING

Do not place the circuit panel in the runners of the case yet. Adjust VR1 and VR2 to approximately mid-track position. Connect up the battery and switch on. Adjust VR1 until the balance point is reached where D1 is off.

Adjust VR2 so that the filament lamps glow dimly, this usually gives best results. Snap the fingers near the loudspeaker and if all is well, the i.e.d. and filament lamps will flash. The adjustment of VR1 is critical. If the slider is adjusted too far clockwise the circuit will lack sensitivity or fail to work at all.

COMPONENTS

Resistors

R1,3,4 100k Ω (3 off)
R2 4.7k Ω
R5 1k Ω
All $\frac{1}{4}$ W carbon $\pm 5\%$

Capacitors

C1 0.1 μ F polycarbonate
C2 0.47 μ F polycarbonate
C3 1 μ F polycarbonate

Semiconductors


D1 TIL220 0.2in red i.e.d.
D2 1N4001 rectifier
TR1,2,3 ZTX300 silicon npn (3 off)
IC1 741 op-amp

Miscellaneous

S1 s.p.s.t. miniature toggle switch
VR1 1M Ω lin. miniature carbon preset
VR2 50k Ω lin. miniature cermet preset
LS1 miniature, 60-80 Ω , 60mm dia. approx.
LP1-5 6V, 0.06A filament lamps
B1,2 See text
Stripboard: 0.1in matrix size 14 strips x 29 holes, plastic case, 147 x 76 x 45mm (ABS box 2005); 7-pin d.i.l. i.c. holder.

Approx. cost
Guidance only

£9.00

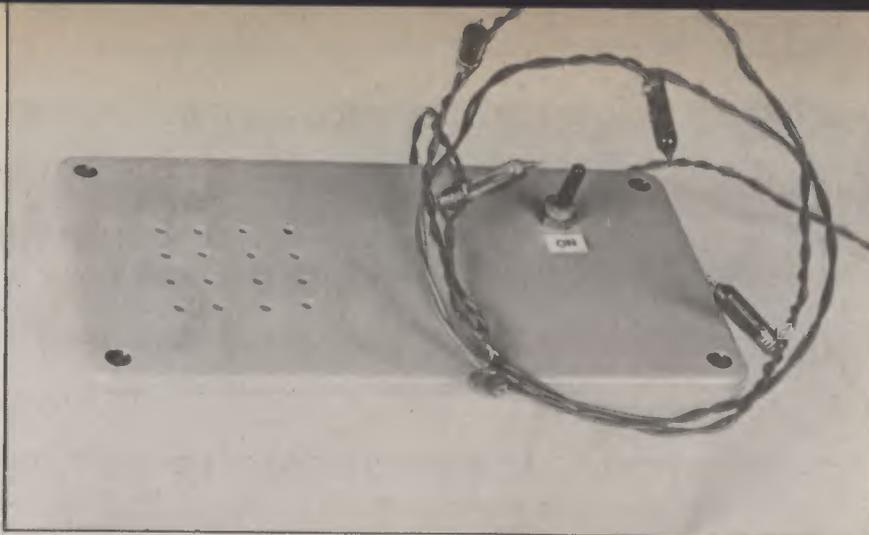

If adjusted too far anti-clockwise, the lamps will be on continuously. VR2 may need final adjustment to obtain the most satisfactory setting. Note that the adjustment of VR2 depends on the number and type of lamps in the chain. When music is played, the lamps should flash in sympathy.

results are obtained by using a larger external battery. Excellent service is given from two 4.5V type 1289 batteries connected in series. Alkaline batteries or Nickel-Cadmium rechargeable batteries would also be a wise choice.

PRESENTATION

This is left to the imagination of the user. The lamps may simply be strung up. Alternatively, they may be pushed through the eyes, nose and mouth of a large mask. Another possibility is portable use with the lamps placed around a hat and the battery in a pocket. □

POWER SUPPLY

Depending on the number of lamps and periods of use, a small battery (a PP3 for example) will probably give poor service. It may seem tempting to house the battery inside the case but much better

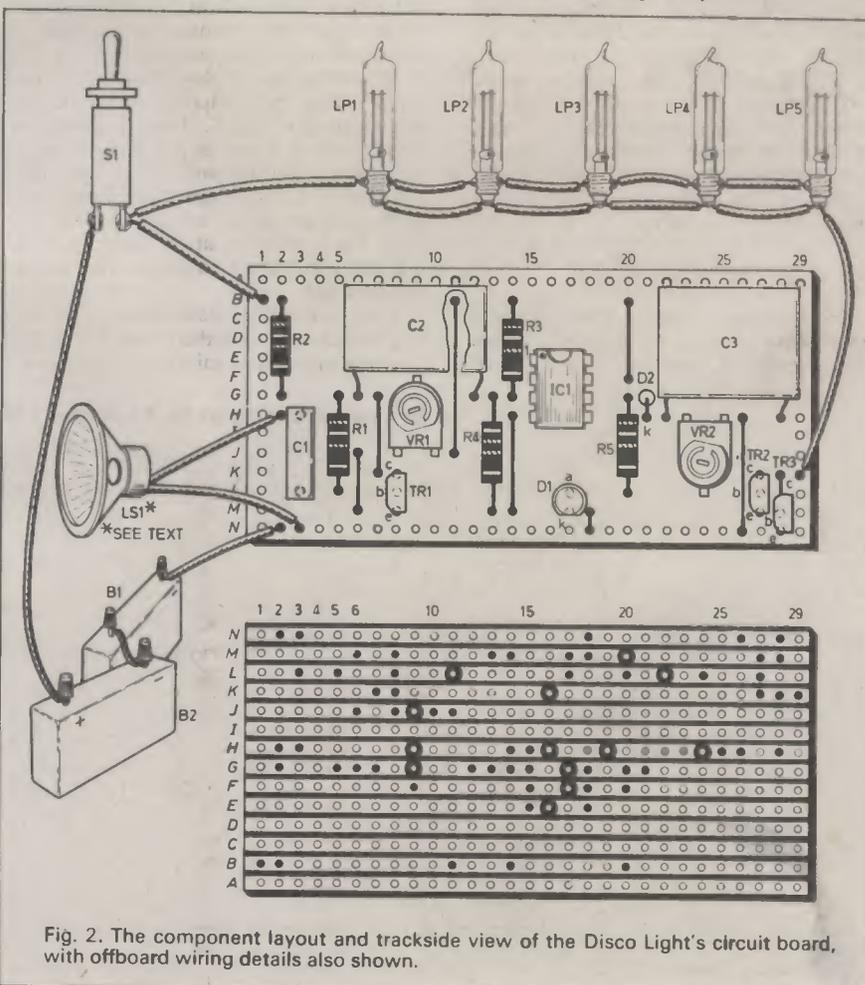


Fig. 2. The component layout and trackside view of the Disco Light's circuit board, with offboard wiring details also shown.



MAGIC CANDLE

BY T.R. de Vaux-Balbirnie

A FILAMENT LAMP "CANDLE" THAT CAN BE BLOWN OUT BUT MAGICALLY RELIGHTS

THE Magic Candle was originally intended as a Christmas novelty but it could be used as part of a conjuring routine, as a game or simply as a conversation piece at a party.

It appears as a large candle having a filament lamp instead of a flame. After switching on, the lamp may be "blown out" and after several seconds, relights itself. This gives children great delight.

CIRCUIT OPERATION

The action of this project depends on the two thermistors, RTH1 and RTH2 (see circuit diagram, Fig. 1). These components have fixed resistors, R1 and R2, respectively, "strapped" to them with thin wire "piggy-back" fashion. Since R1 and R2 are connected in parallel across the supply battery, they will become warm soon after switching on as their power rating is slightly exceeded.

This in turn will warm the thermistors. Some heat will be developed by the thermistors themselves as they are connected in series across the battery but this will be much less than that developed by the fixed resistors. Thermistors are temperature dependent resistors and RTH1 and RTH2 are negative coefficient types which reduce resistance on heating.

RTH1 and RTH2 form a potential divider and a voltage is developed at pin 3

of IC1. The value of this voltage will depend on the relative temperatures of RTH1 and RTH2. Thus, if the temperature of RTH1 becomes less than that of RTH2 the voltage will fall and vice-versa.

OPERATIONAL AMPLIFIER

The Operational Amplifier, IC1, compares the voltages at its two inputs. The voltage at pin 3 is applied to the non-inverting input (marked +) while a voltage obtained according to the setting of VR1 is applied to the inverting input (marked -). If the voltage at the non-inverting input exceeds that at the inverting input then the op-amp switches on. Otherwise it will be off. It is working as a comparator.

When on, the op-amp operates TR1 hence the filament lamp in its collector circuit. In its "normal" state, both thermistors will be warmed equally and so attain the same temperature. The voltage at pin 3 will then be approximately on half of the battery voltage, about 4.5V. One reason why this value cannot be predicted accurately is because thermistors, even of the same type, are not truly identical in performance. VR2 is adjusted so that the voltage applied to the inverting input (pin 2) is just less than that at pin 3. The lamp will then be on.


To "blow out the candle," breath is directed at RTH1. This component will be slightly cooled while the temperature of RTH2 remains unchanged. The action of the potential divider will now be upset resulting in a fall in voltage at pin 3. This is now less than that at the inverting input so TR1 and the lamp will switch off.

After a few seconds, RTH1 will regain its former temperature, its resistance will fall and the lamp switch on again.

IMMUNITY

The reason for providing two thermistors instead of just one and a fixed resistor, is to give some measure of temperature stability. If the project were moved to a room at a different temperature then both thermistors would be equally affected. In theory, the voltage at pin 3 would not change. How well this is realised in practice depends on the particular thermistors being used.

Fig. 1. Circuit diagram of the Magic Candle.

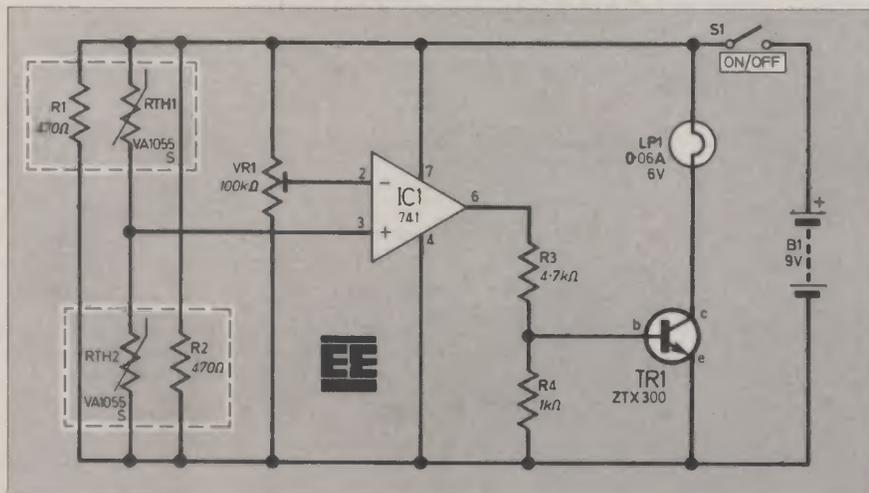

COMPONENTS

Resistors

R1,2	470Ω $\frac{1}{4}$ W (2 off)
R3	4.7kΩ $\frac{1}{4}$ W
R4	1kΩ $\frac{1}{4}$ W

Semiconductors

RTH1,2	VA1055S miniature rod thermistor (2 off)
TR1	ZTX300 npn silicon
IC1	741 op-amp

Miscellaneous

VR1	100kΩ miniature horizontal preset
B1	PP6 9V battery
LP1	6V, 60mA m.e.s. bulb
S1	miniature toggle switch
0.1in matrix stripboard, 11 strips by 19 holes; cardboard tube (for candle body); battery clip; 8-pin d.i.l. holder; fine copper wire (see text).	

Approx. cost
Guidance only

£3.80

CARDBOARD TUBE

Before constructing the circuit panel, a cardboard tube (a kitchen roll tube for example) should be chosen large enough to accommodate the circuit panel and the battery. The current requirement is about 100mA which is too high for a standard PP3 battery. If the reader intends using such a small battery, then the alkaline version (Duracell type) is strongly advised since this will give far better service.

A PP6 battery may be used but this will require a tube of greater diameter than a standard kitchen roll. It is also possible to house the battery in an ornamental base. A large battery is better where heavy use is contemplated.

SENSORS

The next job is to prepare the pairs of components RTH1/R1 and RTH2/R2. These are bound together using about four turns of fine copper wire (thin fuse wire will do)—see Fig. 2.

Construct the circuit panel using a piece of 0.1in matrix stripboard, 11 strips by 19 holes as shown in Fig. 3. Although the i.c. socket should be soldered in position along with the other components, the op-amp itself should not be inserted in it until the end. Make the five breaks in the copper strips; four between the i.c. socket pins and one between the terminals of VR1 and insert the five inter-strip links.

Check all wiring and make certain that no "bridges" exist between adjacent copper tracks. Connect the lamp on two short (20mm) leads to strips B and K and two longer leads for the battery connections to strips B and I.

CHECKING

The circuit may be checked before fitting it into the candle body. Connect

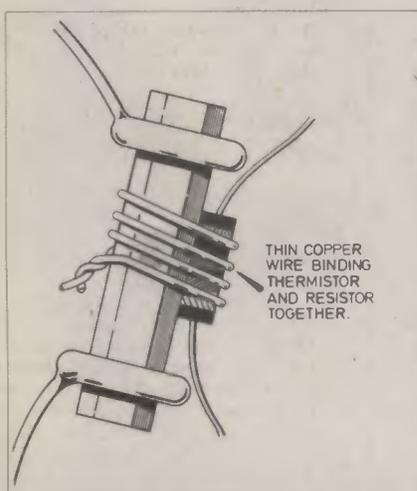
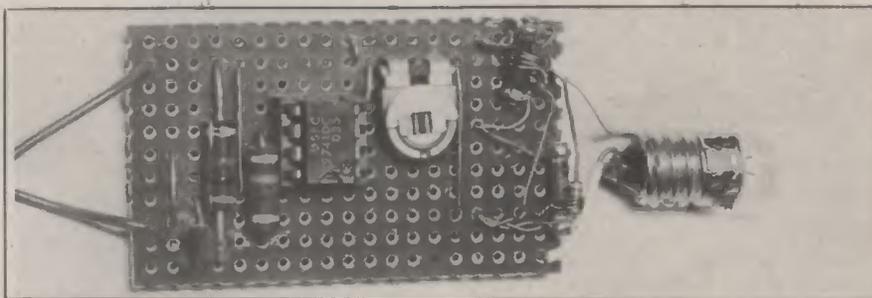


Fig. 2. The method of fixing R1 to RTH1 (and R2 to RTH2) using fuse wire. Note these resistors *must* be $\frac{1}{8}$ W components.

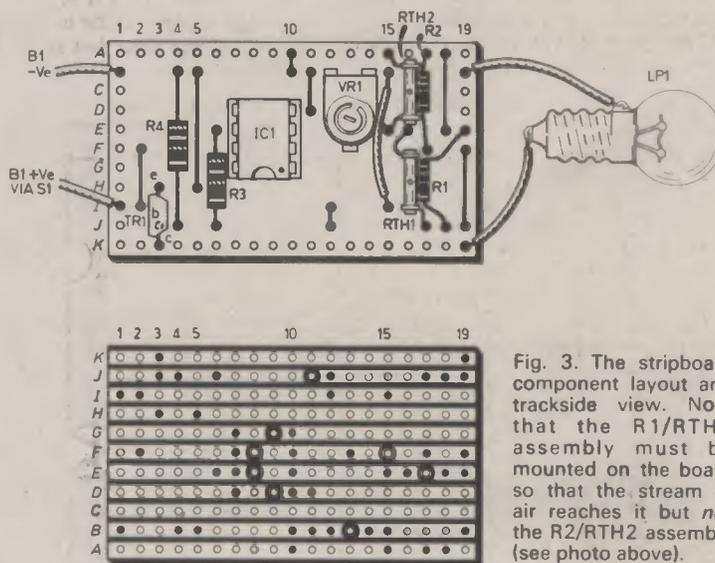


Fig. 3. The stripboard component layout and trackside view. Note that the R1/RTH1 assembly must be mounted on the board so that the stream of air reaches it but *not* the R2/RTH2 assembly (see photo above).



the battery and wait one minute for the thermistors to reach their operating temperature. Whether the lamp lights or not is unimportant at the moment. Adjust VR1 *very carefully* to the point where it can be switched on or off by small movements of the slider. Leave VR1 adjusted so that the lamp is *just* on. Using a drinking straw, blow at RTH1 but not at RTH2. The lamp should go off and after a short while come on again. Repeat and adjust VR1 for best operation.

If all is well, the "candle" body may be prepared. Here, any artistic talents the reader might have may be freely exercised. The hole in the top of the candle is made rather large on purpose (about 12mm). The real reason for this is to allow breath to reach RTH1. It will be noted that the arrangement of the circuit panel when in position is such that RTH1 will be in "direct line of fire" of breath while RTH2 is shielded.

FINAL TESTING

When finally testing the assembled project, the shielding effect of the tube may necessitate further adjustment to VR1 for best operation. It may be found

necessary to make a small hole in the side of the tube to allow for adjustment of VR1. The circuit panel may be held in position using a small piece of plastic foam. The leads of RTH1 and RTH2 may be gently bent as necessary to give the correct effect.

A miniature toggle switch may be used as an on-off switch or the battery simply disconnected when the project is not in use.

Readers are advised to switch off when the project is not actually in use since the battery will soon run down otherwise.

If a base is not used it may be necessary to place a piece of "Plasticine" or similar material low down in the tube to aid stability.

VARIATIONS

A variation of the Magic Candle is to blow it on as well as off! For this, RTH2 must be accessible for breath as well as RTH1. If RTH1 is blown at then the lamp will go off. If breath is now directed at RTH2 instead, the lamp will instantly re-light! By knowing this trick, readers may make a good "magic" routine. □


CIRCUIT EXCHANGE

FOUR-DIGIT COMBINATION LOCK

THIS circuit is a 4-digit combination lock with the added feature of resetting itself if the user makes an incorrect entry, which makes it virtually "unpickable" along with the 11,880 permutations of the combination!

It uses four 7400 quad 2-input NAND gates (TTL) that go to make up four bistables and inverters. The keyboard used is a 12-key type with 12 contacts and 1 common contact. The inputs to the bistables are connected to the contacts on the keyboard corresponding to the digits used in the combination. All the unused contacts are connected to the reset inputs.

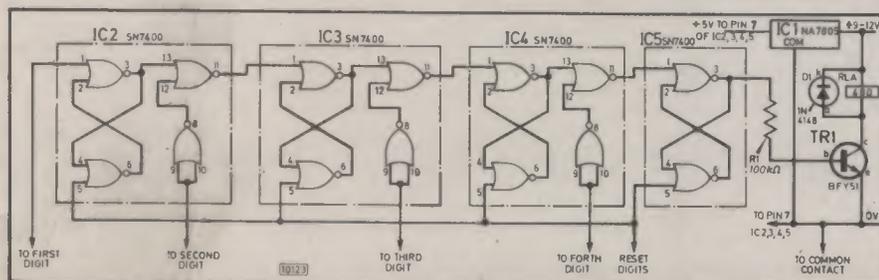The final bistable, after the correct combination has been entered, drives TR1 which operates the relay. The gates are powered by the voltage regulator (5V) which runs off of the supply voltage of 9 to 12V.




TEMPERATURE SENSOR

THE unit is very simple. It uses the fact that a germanium transistor has a varying resistance according to the temperature. It can be used as a boiling liquid alarm or for finding the temperature of a bath by putting the sensor in the water and turning the knob until the l.e.d. lights up, then reading out the temperature.

As the circuit diagram shows, the transistor collector and emitter are connected between the positive supply line and the wiper at VR1. This acts as a potential divider. The output is fed to a Darlington pair which works the alarm.

The unit reads from about 30 degrees

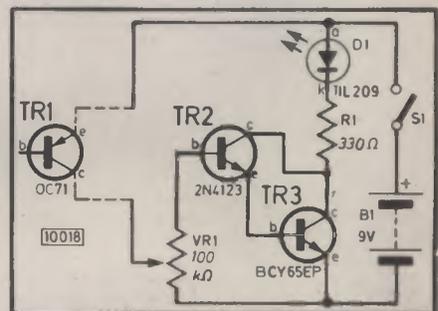

C to 100 degrees C but this depends on the potentiometer.

David Corder,
Kirky Stephen, Cumbria.

PLEASE TAKE NOTE

Speech Synthesiser for the BBC Micro (November 1983)

The circuit diagram Fig. 2 (page 699) shows two pins on IC1 labelled "27". The pin connecting to R9/C5 should be labelled "24".

The user port pin numbering on pins 8, 10, 12 and 13 of the circuit diagram are incorrect and should be re-numbered 6, 8, 10, 12, respectively.

The printed circuit board is correct.

Multimod (November 1983)

Circuit diagram (Fig. 1, page 705) shows the bottom half of S1 drawn incorrectly; the pole should be connected to 0V not to B2 +ve as shown. Wiring diagram (Fig. 4, page 707) is correct.

SHOP TALK



BY DAVE BARRINGTON

CONSTRUCTIONAL PROJECTS

TRS-80 Twin Cassette Interface

The p.c.b. mains transformer used in the *TRS-80 Twin Cassette Interface* is available from Rapid Electronics. This should be ordered as: PCB min. mains transformer, 3VA 0-6, 0-6 at 0.25A. Price £2.87 inclusive. Other transformers may be used but this may necessitate altering the p.c.b. copper strip layout.

The miniature d.i.l. 6V 80-ohm coil relays, with double-pole changeover contacts, are available from Maplin Electronic Supplies: Order code, BK48C Ultra Mln, Relay 6V (DPDT).

For those readers who do not wish to make up their own cassette lead, one may be purchased from any Tandy store; ask for a Model I CPU to audio cassette lead, Code 26-1207 (£2).

Novel Egg Timer

The 14-bit binary counter (4060B) and the CMOS dual 4-input AND gate (4082B) integrated circuits used in the *Novel Egg Timer* are available from Enfield Electronics,

Teach-In 84

Readers wishing to purchase kits for the new *Teach-In 84* series may obtain them from the following advertisers. Prices appear in their relevant advertisement in this issue.

We understand that advertisers have had difficulty in obtaining the EBBO boards which has meant a delay in sending out kits. This problem has now been resolved and the back-log of orders completed.

SUPPLIERS OF KITS FOR TEACH-IN 84

Please refer to advertisement on page stated.

Greenweld Electronics (page 846)
43 Millbrook Road,
Southampton, SO1 0HX.

Magenta Electronics (page 848)
135 Hunter Street,
Burton-on-Trent, Staffs
DE14 2ST.

TK Electronics (page 784)
11 Boston Road,
London, W7 3SJ.

Rapid, Benningcross, Cricklewood and Magenta Electronics.

We have not been able to locate a "readily" available source for a 40-ohm loudspeaker. However, one of the 64-ohm, 64mm diameter range of miniature loudspeakers stocked by most of our advertisers will work in this circuit.

The final choice of housing is left to the individual, but a plastics or "soft" toy from

one of the large multiple stores or toy shops would make a novel finish to this project. Also, the completed board and speaker could be housed in one of those "egg baskets" in the shape of a chicken that are very popular.

Environmental Data Recorder

The MK5168 single channel 8-bit analogue-to-digital converter i.c. used in the *Environmental Data Recorder* may be obtained from Lock Distribution Ltd., P.O. Box L064, Neville Street, Oldham, Lancs OL9 6PY. The inclusive cost is £10.76.

Microcomputer Interfacing Techniques

The only device likely to cause any purchasing problems in this month's *Microcomputer Interfacing Techniques* is the ZN448 8-bit A-to-D Converter used in the *Digital Board*. This device is available from Magenta Electronics, Dept EE, 135 Hunter Street, Burton-on-Trent, DE14 2ST. Price £10.85 plus 50p postage.

We do not expect any component purchasing problems for the "Christmas Ideas" and the remaining constructional projects in this issue.

EE PRINTED CIRCUIT BOARD SERVICE

Printed circuit boards for certain EE constructional projects are now available from the EE PCB Service, see list below. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Remittances should be sent to: EE PCB Service, Everyday Electronics Editorial Offices, King's Reach Tower, Stamford Street, London SE1 9LS.

Cheques should be crossed and made payable to IPC Magazines Ltd.

We regret that the ordering codes for the August projects have been incorrectly quoted in the Sept-Oct issues. Correct codes are given below.


Please note that when ordering it is important to give project title as well as order code.

Readers are advised to check with prices appearing in current issue before ordering.

PROJECT TITLE	Order Code	Cost
Eprom Programmer, TRS-80 (June 83)	8306-01	£9.31
Eprom Programmer, Genie (June 83)	8306-02	£9.31
Eprom Programmer, TRS-80 & Genie (June 83)	8306-03	£1.98
User Port Input/Output <i>M.I.T. Part 1</i> (July 83)	8307-01	£4.82
User Port Control <i>M.I.T. Part 1</i> (July 83)	8307-02	£5.17
Storage Scope Interface, BBC Micro (Aug 83)	8308-01	£3.20
Car Intruder Alarm (Aug 83)	8308-02	£5.15
High Power Interface <i>M.I.T. Part 2</i> (Aug 83)	8308-03	£5.08
Pedestrian Crossing Simulation <i>M.I.T. Part 2</i> (Aug 83)	8308-04	£3.56
Electronic Die (Aug 83)	8308-05	£4.56
High Speed A-to-D Converter <i>M.I.T. Part 3</i> (Sept 83)	8309-01	£4.53
Signal Conditioning Amplifier <i>M.I.T. Part 3</i> (Sept 83)	8309-02	£4.48
Stylus Organ (Sept 83)	8309-03	£6.84
Distress Beacon (Sept 83)	*8309-04	£5.36
Distress Beacon Pocket Version (Sept 83)	8309-05	£3.98
D-to-A Converter <i>M.I.T. Part 4</i> (Oct 83)	8310-01	£5.77
High Power DAC Driver <i>M.I.T. Part 4</i> (Oct 83)	8310-02	£5.13
Electronic Pendulum (Oct 83)	8310-03	£5.43
TTL/Power Interface for Stepper Motor <i>M.I.T. Part 5</i> (Nov 83)	8311-01	£5.46
Stepper Motor Manual Controller <i>M.I.T. Part 5</i> (Nov 83)	8311-02	£5.70
Digital Gauss Meter (Nov 83)	8311-03	£4.45
Speech Synthesiser for BBC Micro (Nov 83)	8311-04	£3.93
Car On/Off Touch Switch (Nov 83)	8311-05	£3.11
4-Channel High Speed ADC (Analogue) <i>M.I.T. Part 6</i> (Dec 83)	8312-01	£5.72
4-Channel High Speed ADC (Digital) <i>M.I.T. Part 6</i> (Dec 83)	8312-02	£5.29
TRS-80 Twin Cassette Interface (Dec 83)	8312-03/09	£7.43
Environmental Data Recorder (Dec 83)	8312-04	£7.24
Touch Operated Die (Dot matrix) (Dec 83)	8312-05/06	£4.34
Touch Operated Die (7-segment) (Dec 83)	8312-05/07	£4.34
Continuity Tester (Dec 83)	8312-08	£3.41

*Set of four boards.

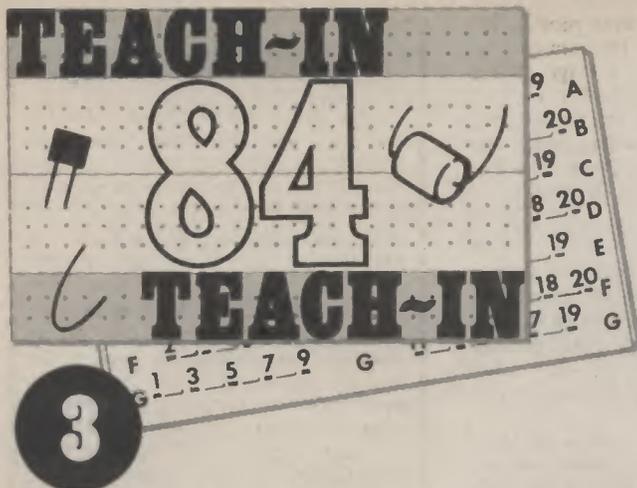M.I.T.— Microcomputer Interfacing Techniques, 12-Part Series.



A TWELVE-PART HOME STUDY COURSE IN THE PRINCIPLES AND PRACTICE OF ELECTRONIC CIRCUITS. ESSENTIALLY PRACTICAL, EACH PART INCLUDES EXPERIMENTS TO DEMONSTRATE AND PROVE THE THEORY.

USE OF A PROPRIETARY BREADBOARD ELIMINATES NEED FOR SOLDERING AND MAKES ASSEMBLY OF CIRCUITS SIMPLE.

THE IDEAL INTRODUCTION TO THE SUBJECT FOR NEWCOMERS. ALSO A USEFUL REFRESHER COURSE FOR OTHERS.

POTENTIOMETERS & TRANSISTORS

BY GEORGE HYLTON

THIS MONTH we'll start making an acquaintance with the transistor. Not before time, you may say. However, all that work you've done on resistance, voltage and current will now begin to pay off. You need just one more bit before we can really get started.

VOLTAGE DIVIDERS

Two resistances, R1 and R2, are connected in series (Fig. 3.1) across a battery. Each of these resistances "feels" the same current, and in its struggle to resist this current flow it consumes a portion of the voltage.

How big a portion? You will know from previous experiments that it depends on the relative sizes (ohmic values) of the resistances. If R1 and R2 are equal then each "drops" half of the voltage. Don't take my word for it. Try it.

Use 1kΩ resistors to keep the meter loading effect small, and remember that your resistors have a tolerance, so the voltage across R1 may not be *exactly* the same as across R2. (With 5 per cent tolerance resistors the worst that can happen is that one resistance is 5 per cent high and the other 5 per cent low. The difference in voltages can't be more than 10 per cent.)

If R1 is twice R2 then it drops twice as much voltage as the latter. If we divide our 9V into three equal parts, R1 drops

two parts (two-thirds) and R2 one part (one-third), or in actual voltages, 6V and 3V, respectively. If we regard 9V as the input and 3V as the output of the circuit then the action of the circuit is to divide the input voltage by 3.

The circuit is a *voltage divider* (also called a *potential divider*). It is used a lot, because it often happens that we need to apply less than the full voltage to some part of a complex circuit.

We'll be doing it in earnest later in this article. First, however, I'd like to make the point that you can use this type of circuit to divide a voltage by any number, not just three.

What fixes the number? It's the relative sizes of the resistances. If for example R1 is eight times R2, then R1 must absorb eight times the voltage. Thus if R2 drops 1V, R1 must drop 8V. For an input of 9V, 1V comes out. The division is by 9.

Suppose we need a ten-fold reduction in voltage. If we imagine the output to be 1V, the input must be 10V. The "unwanted" 9V must be lost in R1. So for a ten-fold reduction in voltage R1 must be, not ten times R2, but nine times R2. It works like this for any required reduction. If the circuit is to divide the input voltage by 100, then R1 must be 99 times R2.

In articles on electronics you'll come across the expression: "voltage attenuation factor". Attenuation means reduction, and a factor is a number. So "voltage attenuation factor" is the number by which the voltage is divided. In our type of voltage divider R1 is greater than R2 and the number of times greater is one less than the voltage attenuation factor.

VOLUME CONTROLS

Resistances behave in the same way towards a.c. and d.c. So voltage dividers of our type can be used to reduce or attenuate a.c. signals as well as d.c. voltages. Often an adjustable form of attenuator is needed. The volume control is the most familiar type. It adjusts the voltage which goes into the audio part of a receiver, or into an audio amplifier.

To make the attenuation adjustable, a resistive track (a-b in Fig. 3.2) is provided with a sliding contact c. By moving this contact to different parts of the track, different amounts of attenuation can be obtained.

With the sliding contact at a, the full input voltage is passed onto the output. With c down at b, there is no output: the attenuation is infinite. So in theory a volume control can attenuate by any factor from 1 to infinity. In practice, it can't manage that very well, but 1-100 or even 1-1,000 is practicable.

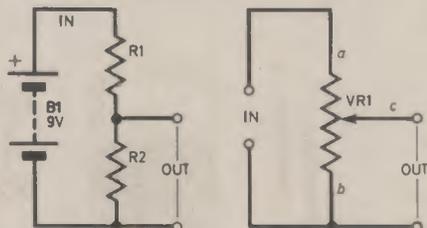


Fig. 3.1. Resistors R1 and R2 form a voltage divider across the 9V battery.

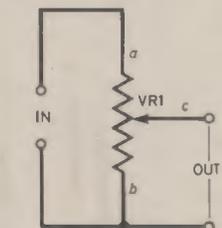


Fig. 3.2. A volume control or "potentiometer" has a resistance track a-b and a sliding contact c.

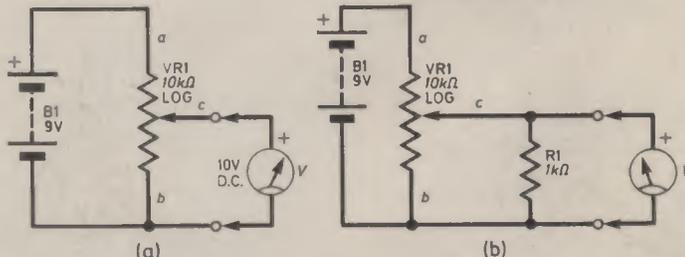


Fig. 3.3(a). How a potentiometer can "tap off" any portion of an input voltage. (Experiment 3.1); (b) Connecting R1 as a relatively low resistance "load" has a marked effect on the output voltage. (Experiment 3.2).

EXPERIMENT 3.1

PREPARING YOUR POT

Get an ordinary rotary type of volume control of the type known as a "10k Ω log. law potentiometer." Connect a length of insulated wire to each of its three tags. If you start with lengths of about 300mm (12in) they will end up about right.

To make connections without soldering, first make sure the tags are clean and bright. Then strip off about 40mm (1½in) of insulation from one end of each of these leads. Wrap this bared wire firmly round and round a tag, squeezing it from time to time with pliers to give it extra grip. When all the bared wire is wrapped, continue with a few turns of the insulated part: this helps to hold the bared wire in place. Do this for each lead.

If possible, use wire of a different colour for each lead. If not, mark the free ends of the leads in some way. You will need to strip off a few millimetres of insulation later, so don't put your markers right at the end. When all three tags are connected, twist the wires together. Finally strip off about 6mm (¼in) of insulation from the free ends, for plugging into your breadboard.

Your finished volume control should look like the one in the photograph. When the spindle is turned fully clockwise the internal sliding contact touches terminal *a*. In the fully anti-clockwise position it touches *b*.

If you connect an ohmmeter to terminals *b* and *c*, the resistance indicated increases as the spindle turns clockwise.

For *a* and *c*, anti-clockwise motion increases the resistance. (Remember to reset your meter to a voltage range immediately after making this test.)

Connect your volume control to your 9V battery (Fig. 3.3a) and measure the output voltage as shown. Note that this can be set to anything from 0V to 9V.

LOADING ERROR

When a resistance is connected across the output of a voltage divider the output voltage falls. This is because extra current flows through R1 (Fig. 3.1) or the corresponding resistance in Fig. 3.3a, which is the upper part of the track; that is, from *a* to *c*.

The amount of extra current depends on the size of the "load"; in other words, the resistance connected across the output. If this is very large, little extra current flows through R1 and the output voltage is not much reduced. But a low-resistance load pulls down the voltage seriously.

EXPERIMENT 3.2

To illustrate this, connect a 1k Ω resistor to your 10k Ω potentiometer (Fig. 3.3b). Note that if the resistor is unplugged when the slider is set at an intermediate position the voltage indicated jumps up. This loading effect is worst at the point where, in the absence of a load, the meter reads half the battery voltage.

The loading effect can be reduced by making the divider resistances small compared with the load resistance. This

CURRENT FLOW

One point which causes difficulty may as well be dealt with here. Currents are flows of electric charges. An electric charge can be positive or negative. If positive, the charge travels in the same direction as the current. If negative, it travels in the opposite direction. It so happens that most real-life currents are flows of negative charges, carried by electrons. So an electron, being negative, goes in the opposite direction to the current. To deal with this anomaly, the current, which is universally regarded as flowing from positive to negative, is sometimes called conventional current.

Only physicists and transistor designers need worry about whether currents are carried by positive or negative charges. As engineers we can forget about the nature of the charge carriers and design purely in terms of conventional flow of current from positive to negative. The arrow-like parts of the standard symbols for transistors and diodes always point in the direction of conventional current flow. All the circuits in this *Teach In* are described in terms of conventional current flow from positive to negative.

means wasting current in R1 and R2 (or your "potentiometer") but this is often tolerable.

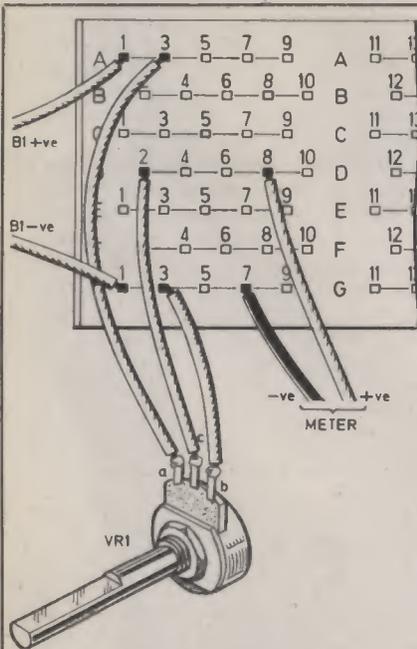


Fig. 3.4. The circuit of Fig. 3.3(a) assembled on the EBBO Block.


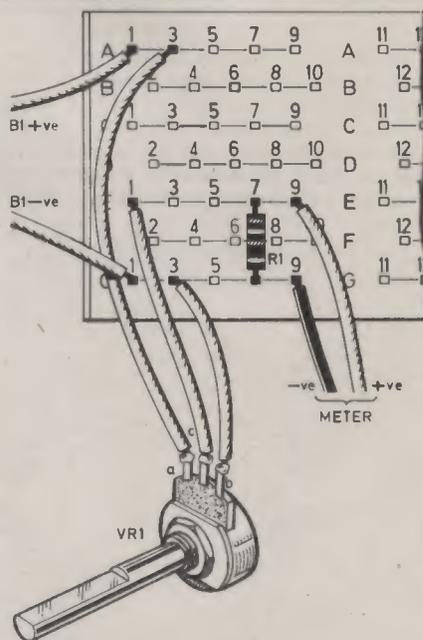


Fig. 3.5. The circuit of Fig. 3.3(b) assembled on the EBBO Block.

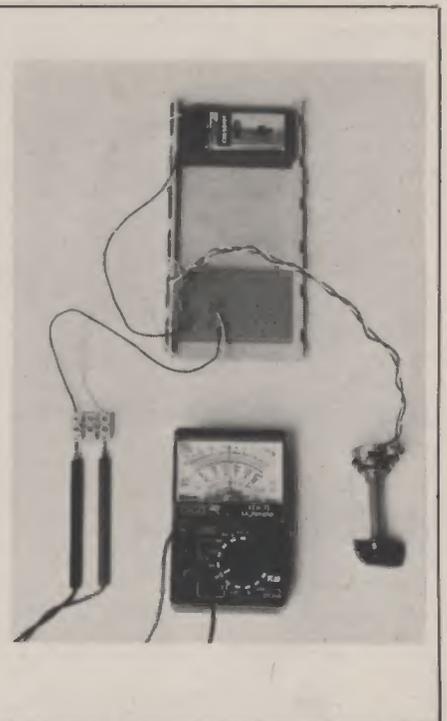

EXPERIMENT 3.3

TURNING ON A TRANSISTOR

Our next experiment will be to find out how much voltage is needed to "turn on" a transistor; that is, to make it pass current.

Referring to Fig. 3.6, a transistor has three terminals or "electrodes": they are, base (*b*), collector (*c*) and emitter (*e*). The main current path through a transistor lies between collector and emitter. The little arrow on the emitter (*e*) shows the permitted direction of current flow. (Transistors are one-way devices; current can flow only in permitted directions.)

To permit current to flow via the collector-emitter (*c-e*) path the transistor must be turned on by driving a small current through the base-emitter path. Our 10kΩ potentiometer allows us to adjust this current by applying any part of the battery voltage to the resistor R1. The meter (on its 2.5V range if you are using the KEW75) measures the resulting voltage between base (*b*) and emitter (*e*). We'll call this voltage V_{BE} for short.

With the kind of transistor we are using at the moment (an *npn* transistor) the normal direction of current flow is *into* the base and *into* the collector and *out of* the emitter. Collector and base are then positive with respect to the emitter.

CURRENT INDICATOR

To show that collector current is flowing, connect a l.e.d. and limiting resistor as shown (Fig. 3.6), making all connections within one half of your EBBO discrete component module.

My test results were:

D1 just glowing $V_{BE} = 0.65V$
D1 bright $V_{BE} = 0.75V$

To pinpoint the "bright" setting of VR1, I first turned it fully up then gently back to find the point where the l.e.d. just began to dim. Transistors vary. Your voltages may be somewhat different.

The collector current with the l.e.d. bright is actually about 7mA. Assuming the "dim" current to be 1mA, we can look at our results like this:

$V_{BE} = 0.65V$ makes 1mA flow into the collector
 $V_{BE} = 0.75V$ makes 7mA flow into the collector

From this you can see that (for my BC107B) a change in V_{BE} of 0.1V produced a change in collector current (I_C) of 6mA.

This ability of a change in V_{BE} to produce a corresponding change in collector current (I_C) is an important transistor characteristic. It has a name: *mutual conductance* or *transconductance*, and a symbol, gm:

$$g_m = (\text{Change in } I_C) / (\text{Change in } V_{BE})$$

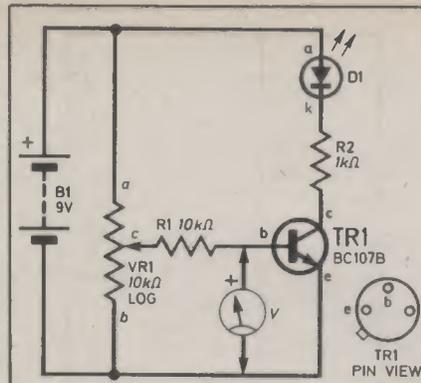


Fig. 3.6. How much base voltage is needed to turn on a transistor? (Experiment 3.3).

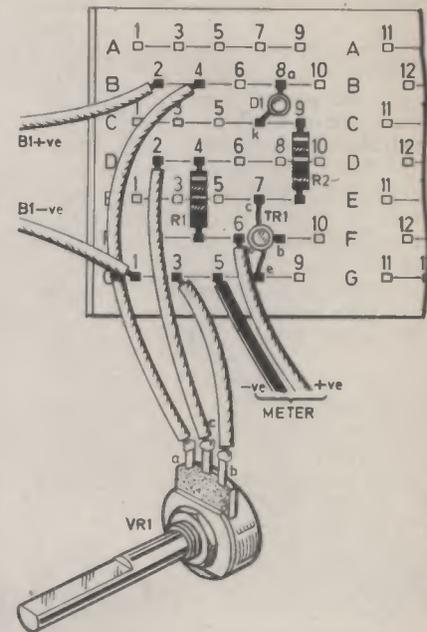
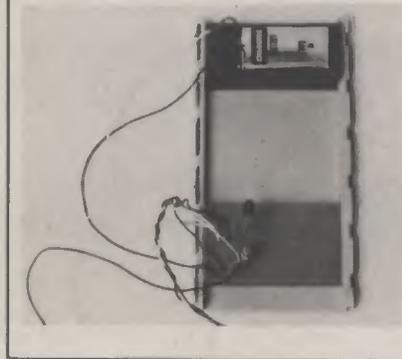


Fig. 3.7. The circuit of Fig. 3.6 assembled on the EBBO Block.


For small values of I_C , this is expressed in mA (of I_C) and volts (of V_{BE}). Then, gm comes out in milliamps per volt (mA/V). However, mA/V also has a name: 1mA/V = 1 milli-siemens (1mS).

My figures indicate a mutual conductance of about 60mS.

VOLTAGE AMPLIFICATION

As the collector current increases, more voltage is dropped by the l.e.d. and R2. With the l.e.d. just glowing, the total drop across it and R2 is about 3V. When the l.e.d. is bright, the drop is nearly 9V. So a change of 6V in the collector part of the circuit has been produced by a change of 0.1V at the base.

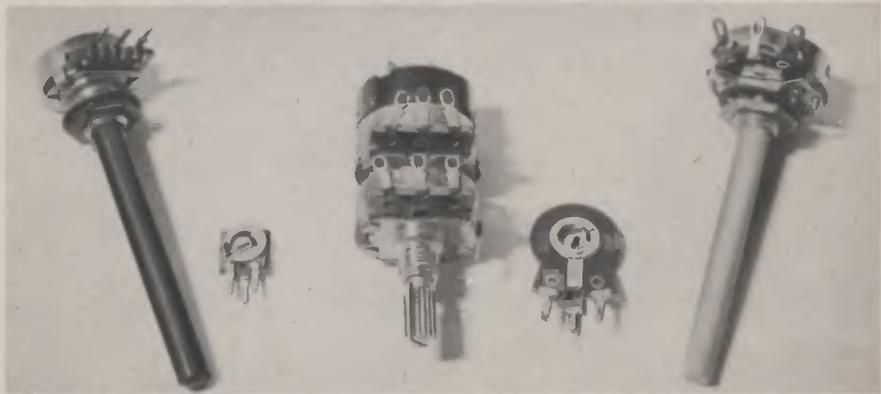POTENTIOMETERS (left and right) normal panel mounting volume controls; (centre) twin-ganged type with mains switch at rear. The two smaller components are preset potentiometers for direct mounting on circuit boards, screwdriver adjustment.



If the change in V_{BE} (0.1V) is an input signal, and the change in collector voltage an output signal, then the transistor has amplified the input sixty-fold. In engineer's talk, the *voltage gain* is 60.

CURRENT AMPLIFICATION

A transistor amplifies current, too. The input is the current which flows into the base (and out at the emitter along with the main current from the collector). The output current is the collector current. It is true that for an *npn* transistor this "output" flows *into* the transistor. But we'll see in a later article how it can be taken elsewhere.

To investigate current amplification, it is necessary to know the base current, I_b . The most direct way of finding I_b is to connect a current meter in the base circuit (Fig. 3.8a). In practice, this is neither practical nor safe. Meters when switched to "current" ranges are easily overloaded by accidental momentary connection across the power supply. In this particular circuit there is a design error which almost guarantees it will happen!

If VR1 slider is moved up to the top of the track (a), which is the same thing as battery +, current can flow freely from battery + through the meter, through the base and emitter and back to battery -. The transistor base-emitter "junction" offers little resistance, and the resulting large current wrecks both transistor and meter.

Some meters are protected internally against overload but it is always better to play safe and measure voltages rather than currents.

On a voltage range the meter always has a fairly high resistance. (For a KEW7S, whose sensitivity is $2k\Omega/V$ d.c., the resistance is $2k\Omega$ times the voltage range to which the meter is set. On the 10V d.c. range it is $2k\Omega \times 10 = 20k\Omega$.)

EXPERIMENT 3.4

In any case, the base current is likely to be too small to measure on a cheap meter. We'll avoid the problem by using the circuit Fig. 3.5b. This makes use of the fact that if we know the voltage across a resistance we can find the current flowing through it.

Here, the base current sets up a voltage across R_1 , $100k\Omega$. Every volt applied to $100k\Omega$ produces a current of 10 microamps ($10\mu A$), that is, ten-millionths of an amp or a hundredth of a milliamp.

The voltmeter doesn't measure the voltage across R_1 , but merely the voltage at one end. Fortunately, we can estimate

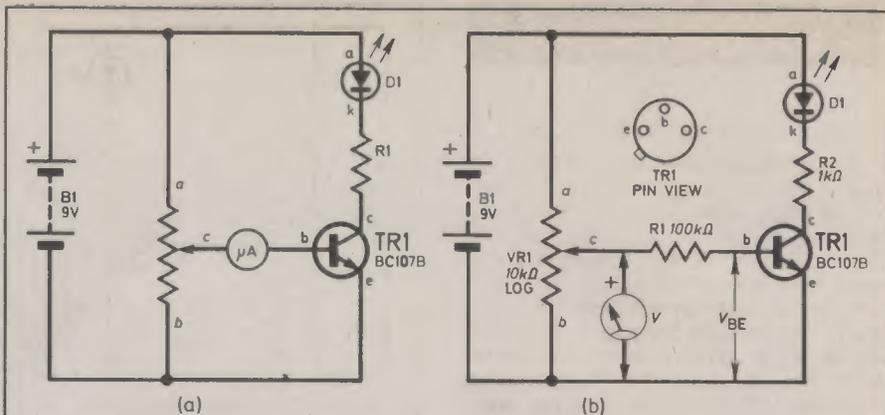


Fig. 3.8. How base current governs collector current; (a) A not very good way of finding out; (b) This way is safer, but the base current must be estimated. (Experiment 3.4).

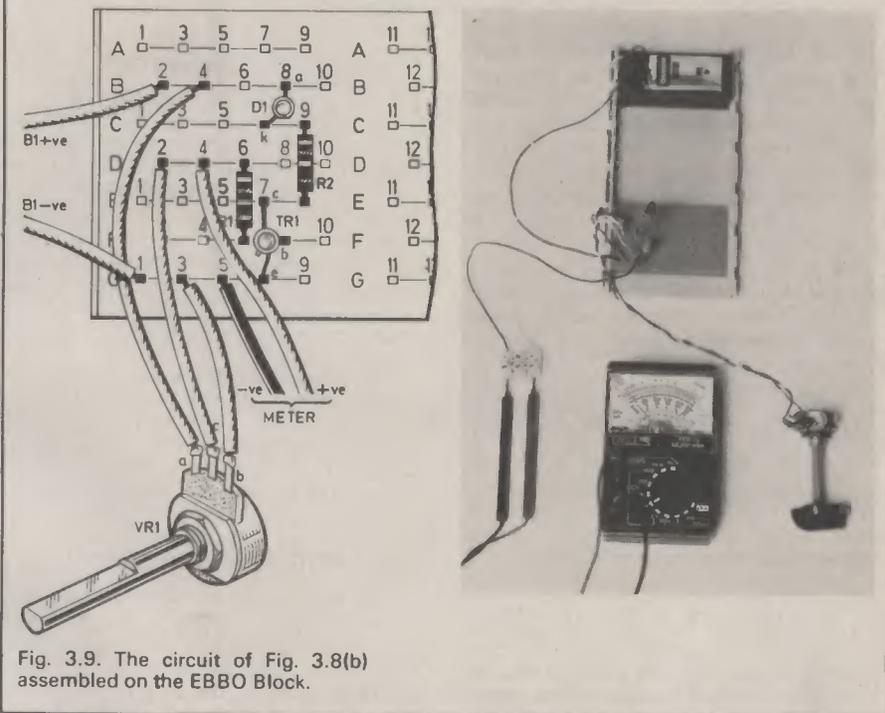


Fig. 3.9. The circuit of Fig. 3.8(b) assembled on the EBBO Block.

TRANSISTORS. High gain, small signal, metal can types as used in this series.



the voltage at the other end. It is V_{BE} , which is never very far from 0.7V. (The most extreme values of V_{BE} you are likely to come across in silicon transistors are 0.4V and 1V; that is, $0.7V \pm 0.3V$). Let's call it 0.7V.

My voltmeter readings were:

D1 dim 1V
D1 bright 4V

Knocking off 0.7V for V_{BE} , the voltages across R_1 must have been about 0.3V and 3.3V. The corresponding base currents are $3\mu A$ and $33\mu A$.

In the "l.e.d. dim" case, if I_C was 1mA ($1,000\mu A$) the current amplification was $1,000/3 = 333$. In the "l.e.d. bright" case, if I_C was 6mA ($6,000\mu A$) my BC107B had a current gain (I_C/I_b) of 180.

You may suspect that the current gain of a transistor varies with its collector current. It does. But our results are based

CHECK YOUR PROGRESS

Questions on *Teach-In 84 Part 3*
Answers next month

- Q3.1 In the circuit of Fig. 3.8b, why can't the meter be connected across R1 to measure the voltage directly?
- Q3.2 A transistor has a current amplification factor (h_{FE}) of 100. If its base current is $10\mu\text{A}$ what is its:
(a) collector current;
(b) emitter current.
- Q3.3 The burglar alarm circuit of Fig. 3.11 makes use of the fact that the resistance of the light-dependent resistor PCC1 falls considerably when a beam of infra-red light strikes it. If the alarm bell is to sound when an intruder's body interrupts the beam how must the circuit work?

- Q3.4 The collector current of a transistor is to be used to light a l.e.d. If $V_{CC} = 6\text{V}$ and the current must not exceed 20mA what minimum value of current-limiting resistance is required? (The l.e.d drops 2V at 20mA .)

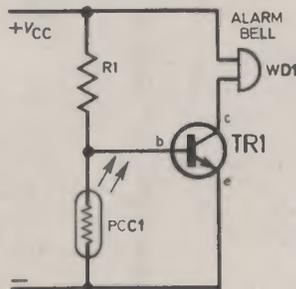


Fig. 3.11. See Q3.3.

ANSWERS TO PART 2

- Q2.1 (a) 2mA ; (b) 9.9V ; (c) $18\text{k}\Omega$.
- Q2.2 (a) $9\text{k}\Omega$; (b) $3\text{k}\Omega$ (the lowest two resistors are short circuited); (c) $1\text{k}\Omega$ (current can flow from X to Y via any one of the resistors so they are all in parallel).
- Q2.3 3mA . There is 4V across the parallel resistors so the $2\text{k}\Omega$ passes 2mA and the $4\text{k}\Omega$ passes 1mA .
- Q2.4 4V . The meter acts as a resistance of $10\text{k}\Omega$. In parallel with R2 this makes $5\text{k}\Omega$. The total resistance is then $R1 (10\text{k}\Omega) + 5\text{k}\Omega = 15\text{k}\Omega$. 12V applied to $15\text{k}\Omega$ drives 0.8mA , which produces 4V in flowing through the $5\text{k}\Omega$. So 4V appears across the meter and this is what it indicates.

on estimates and are very rough. The real value of the current gain for a BC107B is likely to be 200-500.

BIASING

Transistors are often used to amplify small voltages and currents (small signals). For example, the output from a record-player magnetic pickup may be only a thousandth of a volt (= 1 millivolt, 1mV ; $1,000\text{mV} = 1\text{V}$). Such a small voltage can't turn on a transistor, which, as we've seen, needs about 0.7V (= 700mV).

To make the amplification of small signals possible, the transistor is turned on, permanently, by a steady d.c. voltage or current from the power supply. The signal is added to this, so that the transistor is turned on a bit more.

In this way, a small signal can produce an increase in collector current even though, on its own, it couldn't make any collector current flow. The output signal is the increase in collector current, which can be separated from the steady current caused by the turning-on voltage or current.

This trick of turning on a transistor like this is called *biasing*. Purely by way of illustration, Fig. 3.10 illustrates how a gramophone amplifier might be set up. The voltage divider, R1, R2 sets up enough base-emitter voltage to produce a suitable collector current. This flows through a loudspeaker. Any variations in this steady current at audio frequency produces sound.

To insert these variations the magnetic pickup is connected in the base lead. Any

voltage developed in the pickup coil then adds to or subtracts from the 700mV bias. So as the pickup generates its few millivolts of audio signal (which is a.c., not d.c.) the collector current rises and falls in sympathy. These a.c. variations superimposed on the steady d.c. produce sound in the speaker.

That, at any rate, is the theory. In practice, it won't work, because a single transistor doesn't amplify enough. Also, this circuit is badly affected by variations in the supply voltage (V_{CC}) and temperature, which changes the required V_{BE} of the transistor.

Next time we'll look at more practical circuits and at a useful way of separating the output signal from the steady collector current.

● If you are buying as you go along you'll need a crystal earphone and at least two 100nF ($0.1\mu\text{F}$) capacitors, 30V (minimum) working, non-polarised. Disc types with long leads are most convenient. Also a $1,000\mu\text{F}$ electrolytic capacitor, 16V (minimum).

Next

month: Transistors and Capacitance

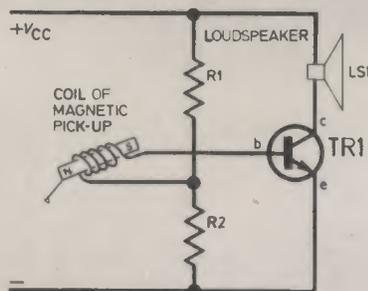


Fig. 3.10. An illustrative, but impractical, audio amplifier circuit.



Is Your Youngster's Future Worth 90p per Month?

Electronics and computer-based industries offer many job opportunities to the technically trained. Your son or daughter's career prospects could be enhanced if they have a knowledge of electronics.

Our twelve-part series *Teach-In 84* has been planned with this object in view. An ideal home-study course with practical experiments, easily performed without soldering.

Make sure of your copy of *EVERYDAY ELECTRONICS* by placing a firm order with your Newsagent NOW!

Everyday Electronics, December 1983

TELL A
FRIEND!


BIOLOGICAL AND ENVIRONMENTAL SCIENCE STUDIES OFTEN REQUIRE CONSTANTLY CHANGING INFORMATION TO BE MONITORED OVER A PERIOD OF TIME. THE ENVIRONMENTAL DATA RECORDER USES EXTERNAL SENSORS TO MEASURE THESE PARAMETERS AND STORE THE RESULTS DIGITALLY IN A RANDOM ACCESS MEMORY, HAVING FIRST CONVERTED THE ANALOGUE INPUT WITH AN 8-BIT ANALOGUE-TO-DIGITAL CONVERTER. THE RESULTS CAN BE READ FROM THE MEMORY BACK IN THE LABORATORY USING THE SINCLAIR ZX SPECTRUM COMPUTER.



TOTALLY PORTABLE AND USING RECHARGEABLE BATTERIES, THIS UNIT IS IDEAL FOR FIELD WORK.

ENVIRONMENTAL DATA RECORDER

BY M. LAWRIE & L. WILKINSON

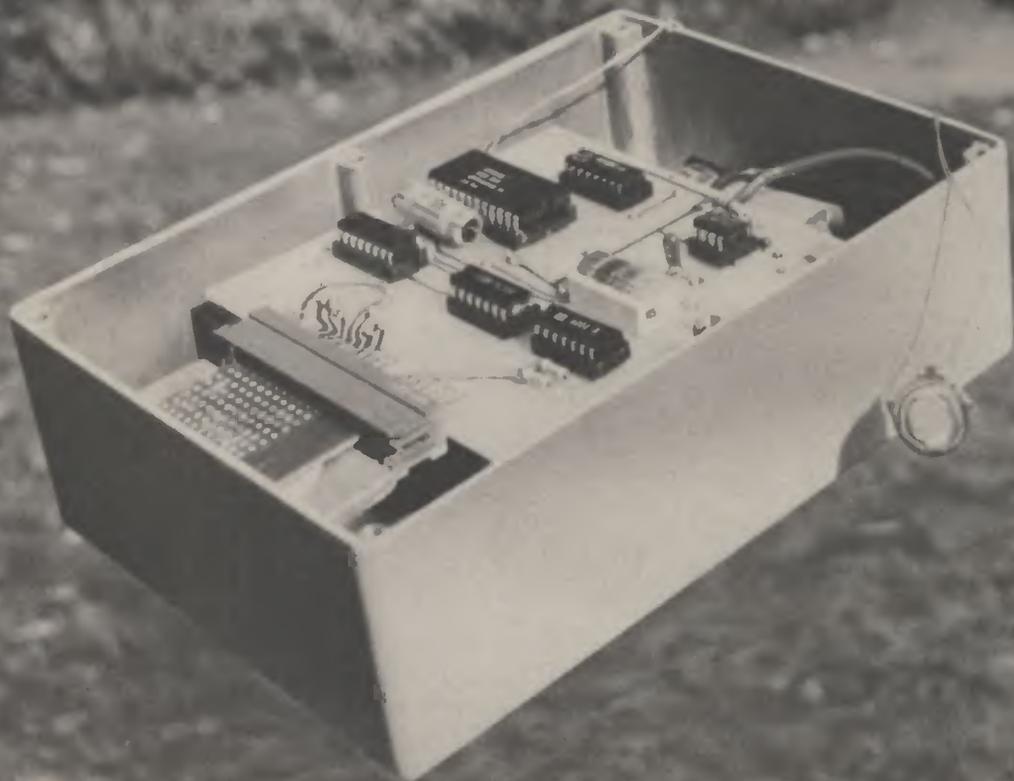

WHEN measuring changes in biological and environmental science experiments, the quantities being measured often change very slowly. For this reason it may take days, or even weeks, to take readings of, say, pH changes in water over a length of time. If the experiments are being carried out-of-doors, then the problems of setting up the experiment and collecting the readings are far greater.

DESIGN CONSIDERATIONS

The unit described here is designed to be waterproof and weatherproof which can be left on site using its own power supply. It can be fitted with many different sensors, for example, oxygen probes, pH probes, light dependent resistors (for light) and thermistors (for heat) and with these it can measure oxygen level changes, pH level changes, light level changes and temperature changes.

The Environmental Data Recorder can take readings ranging from over 500 per second to over once per hour. The data is stored digitally in a 2K byte memory that can be read at a later date by plugging it into the expansion slot of the Sinclair ZX Spectrum. A short program is used to put the data or a graph of the results onto the screen. It is helpful to have a Sinclair ZX Printer to get a hard copy of the graph or data.

When designing the circuit, several points had to be considered because it (a) is to be portable so it must be a physically small unit, (b) should have a low power consumption, (c) must be able to be plugged into the back of the Spectrum without losing any data or crashing the computer, and (d) must be able to be used over a long period, continuously for a month if necessary.

CIRCUIT DETAILS

The unit works in one of two modes, first WRITE then READ. Switches S1 to S3 select the mode. The RESET switch (S4) resets the address counter to zero in either mode. Fig. 1 shows a block diagram of the unit in WRITE mode. Brief operating descriptions follow. The full circuit diagram is shown in Fig. 2.

The MV5516 CMOS static RAM (IC5) was used because its low power consumption when not selected (\overline{CE}_1 and \overline{CE}_2 both at logic 1) uses only about $1\mu A$.

The MK5168 analogue-to-digital converter (IC3) was selected for its simplicity of operation. In the basic unit described here, the reference voltage (pin 4) is +5V but may be changed for other applications. To measure changes in light intensities, an ORP12 light dependent resistor (l.d.r.) was connected across the analogue input and +5V. If absolute values of intensity are needed, calibration against a standard must be carried out.

If other level changes are to be recorded, the output voltage of the sensor should be in the range of 0 to +5V, so a buffer or attenuator may be needed.

Provision for easy change of WRITE pulse times (the time between each successive sample) has not been made. The time may be changed by altering the values of R3, R4 and C1. The timing period is approximately $0.7 \times R3 \times C3$ (R4 must be small compared with R3). With $R3 = 3.3M\Omega$, the period is approximately 2.3 seconds times capacitance of C1 in microfarads. With a $1500\mu F$ capacitor, a reading will be recorded approximately once per hour. For all periods greater than 0.7 seconds, R4 should be $1k\Omega$. For periods shorter than this, R4 should be increased.

Equations for calculating the component values for a 555 timer as an astable multivibrator are given below.

Output high for

$$0.685 \times (R3 + R4) \times C1 \text{ seconds}$$

Output low for

$$0.685 \times R4 \times C1 \text{ seconds}$$


Period of one cycle

$$= 0.685 \times (R3 + 2R4) \times C1 \text{ seconds.}$$

WRITE MODE

Data is entered into the random access memory (RAM) on the falling edge of the clock oscillator (IC4) output. On this edge, the 12-bit counter is advanced one address and the memory (IC5) and A/D converter (IC3) are also selected.

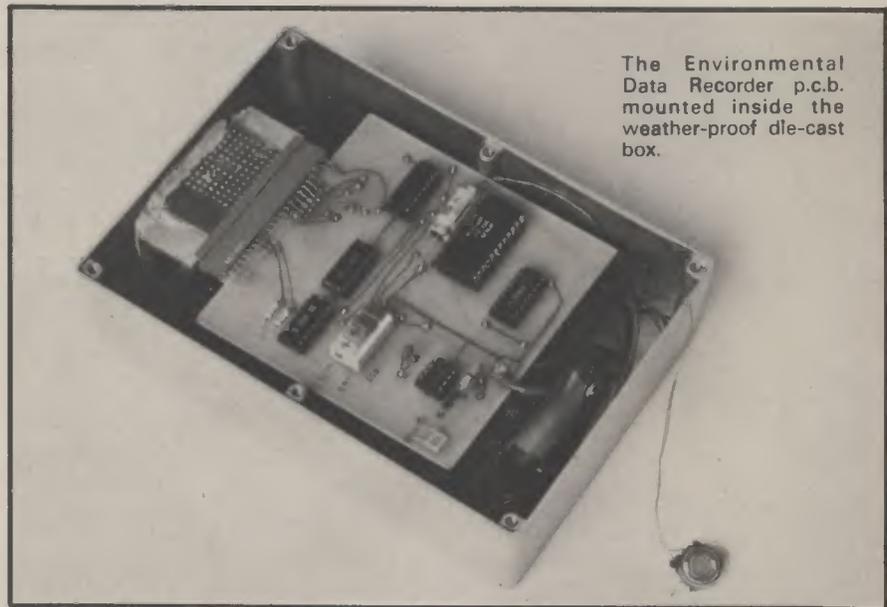The BUSY line (pin 3, IC3) goes low when conversion is complete. This level,



The Environmental Data Recorder p.c.b. mounted inside the weather-proof die-cast box.

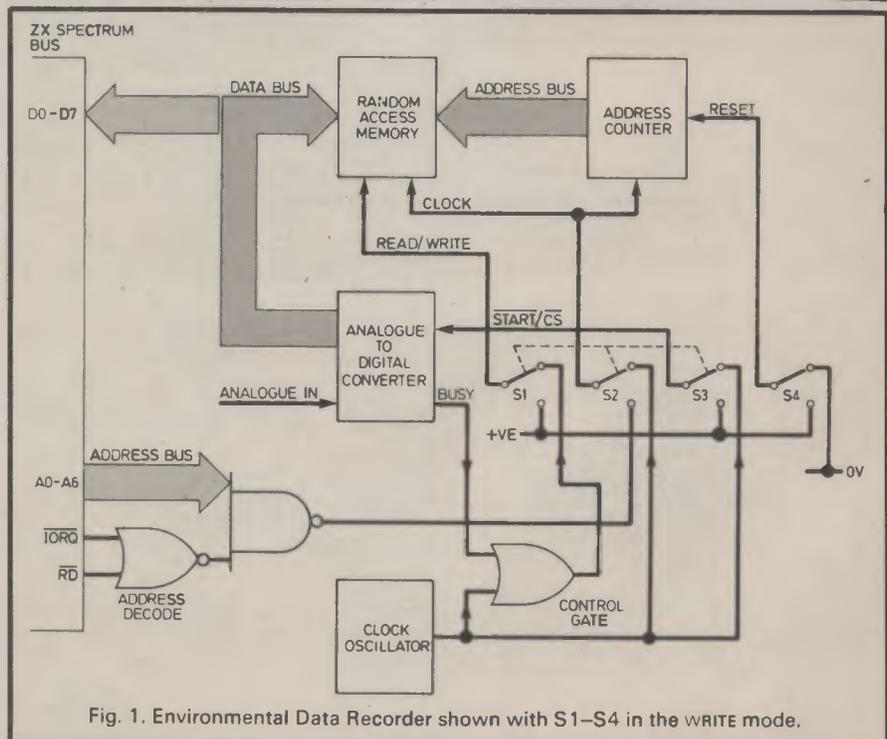


Fig. 1. Environmental Data Recorder shown with S1-S4 in the WRITE mode.

and the clock are fed to an OR gate (in the circuit, two NOR gates, IC2b and IC2c) and the output of this selects READ if high and WRITE if low.

The process repeats itself on the next falling edge from the clock oscillator. In this way, the analogue value on pin 4 of IC3 is converted to an 8-bit digital representation and written into the memory with every sample pulse.

READ MODE

When switches S1-S3 are taken to the READ position (opposite to that shown in Figs. 1 and 2), the A/D converter is turned off as the CS input (pin 5) is taken to +5V. With the unit plugged into the back of the Spectrum, IC1, an 8-input NAND gate, is switched on (as it takes its

power from the computer *not* the battery pack).

The program selects ports 255 or 127 (via the command IN255 or 127) and so pulses the 12-bit address counter adding one to the memory address. Data is read from the memory after each address has been incremented.

CIRCUIT BOARD

The circuit is constructed on a double-sided p.c.b., 100 x 100mm, the track pattern and component layout of which is shown in Fig. 3. This board is available from the *EE PCB Service*, Order code 8312-04 or can be made using the usual methods, although special care must be taken as it is double-sided, to ensure alignment of the two artworks.


The 26 shorting pins (the links between the top and bottom tracks) must first be inserted. Note that these must be soldered on both sides. Next, the resistors and capacitors are inserted and some of the leads require soldering on both sides.




The d.i.l. i.c. holders are then soldered in place but the i.c.s are not plugged-in until later. Note that IC3 and IC5 face the opposite direction to all the other i.c.s. Finally, the d.i.l. switch (S1-S4) and the 23-way edge connector are fitted.

EDGE CONNECTOR

The 23-way double-sided edge connector has the polarising key fitted at position three and this is mounted to the left side when viewed from the top with the connector pointing down (as in Fig. 3).

Fig. 2. Complete circuit diagram of the Environmental Data Recorder in WRITE mode. To set to READ mode, S1-S3 are switched to opposite position. PCC1 is connected to the analogue input to measure light intensity.

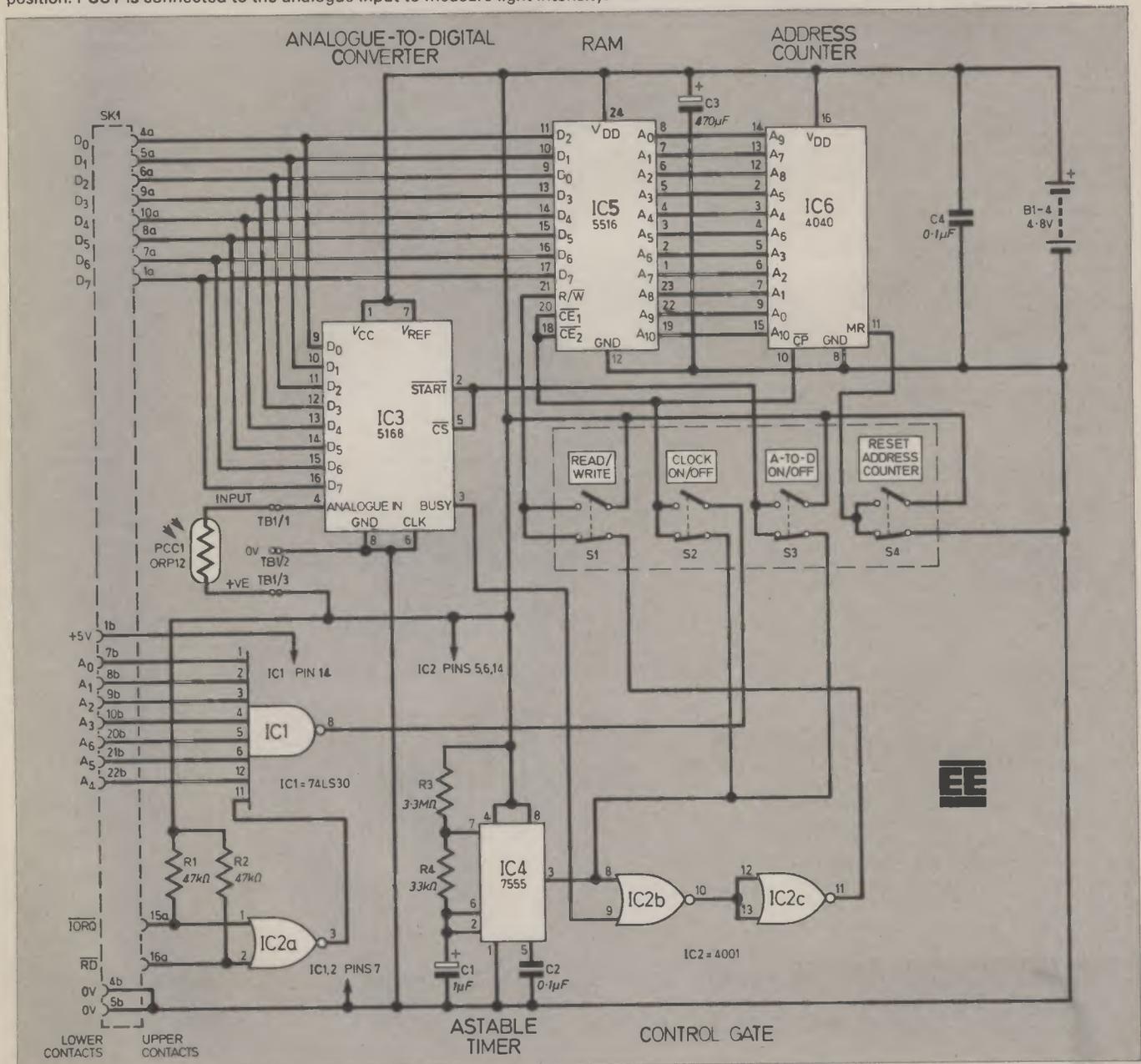

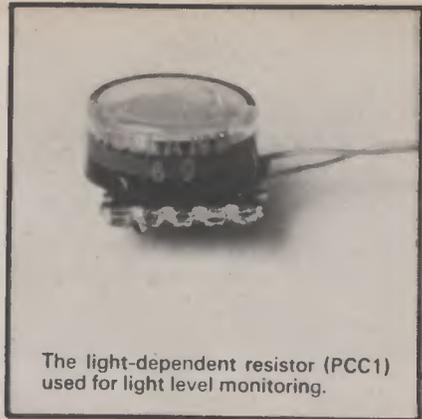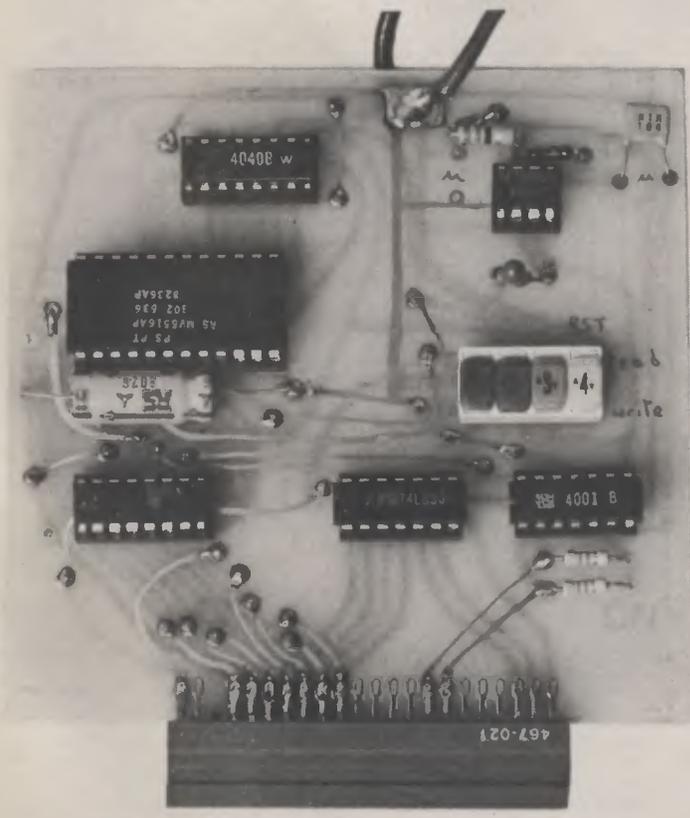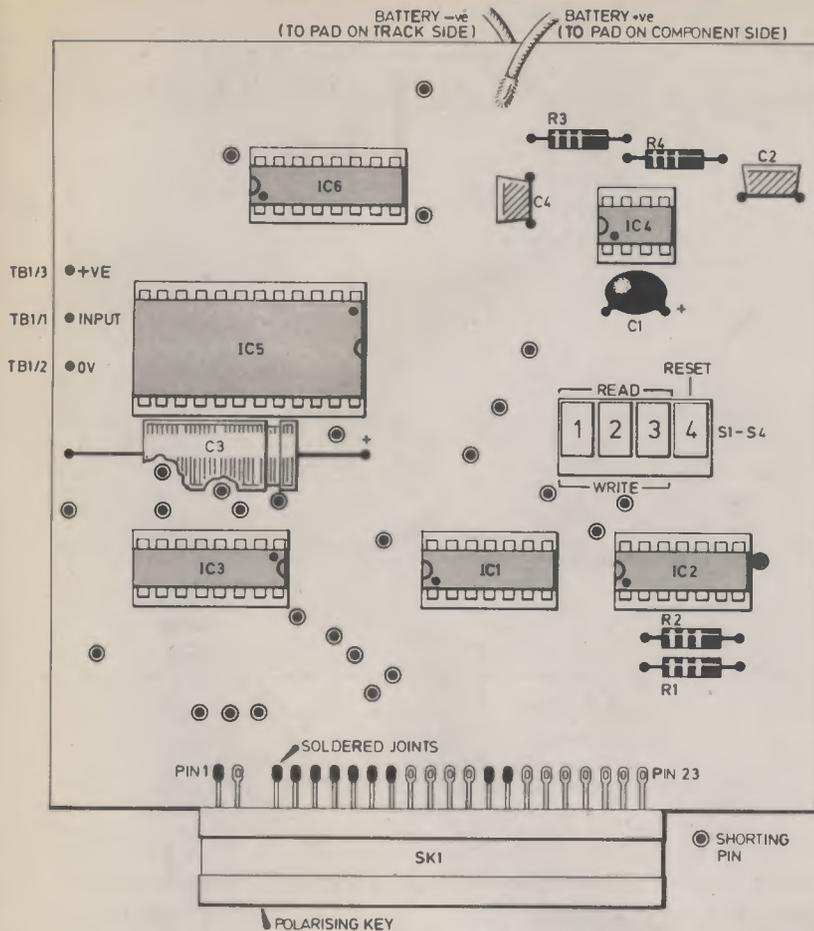

The light-dependent resistor (PCC1) used for light level monitoring.

The last connections are the wires to the battery pack and to the sensor (on the prototype, a light dependent resistor, PCC1).

The battery wires should be long enough to allow the board to be withdrawn from the case to be plugged onto the Spectrum computer. Ensure that there is no short circuit on these leads as the low internal resistance of the cells compared with their high output can produce a lot of heat quickly!

When assembly is complete, the i.c.s can be inserted into their holders, observing the correct orientation shown in Fig. 3.

CASE

The Environmental Data Recorder p.c.b. is mounted into a watertight case when out in the field, which also houses the battery pack. This is a holder for four C size (HP11) ni-cad rechargeable batteries and it is held in place with double-sided adhesive tabs.

The prototype was housed in a die-cast box, 170 x 120 x 50mm with a specially fabricated bracket at one end to hold the edge connector of the board. (See photographs.) This bracket must use an insulating material (plain matrix board for example) to slot into the connector to prevent short circuits.

INSTRUCTIONS

To use the Data Recorder, the following set of instructions must be followed. First set up the correct sample period with the selected values of R3, R4 and C1 on the astable timer (IC4), the calculations for which are given in the circuit description.

1. Set switches S1, 2 and 3 to the down position (WRITE) and S4 to the up (RESET).
2. Place the ni-cad batteries in the holder (observing the correct polarity) to switch the unit on.
3. When ready, set S4 to the down position to begin recording.
4. Place the board onto its holder in the case and seal the lid.
5. When the readings are complete, set all the switches to the up position (S1-S3 to READ and S4 to RESET):


SOFTWARE

```
10 REM Environmental Data
   Recorder
20 REM (c) Everyday Electronics
30 REM December 1983
40 FOR n=175 TO 0 STEP -1
50 PLOT IN 255,n
60 IF n=0 THEN GO TO 80
70 NEXT n
80 PAUSE 10
90 COPY
100 CLS
110 GO TO 40
```

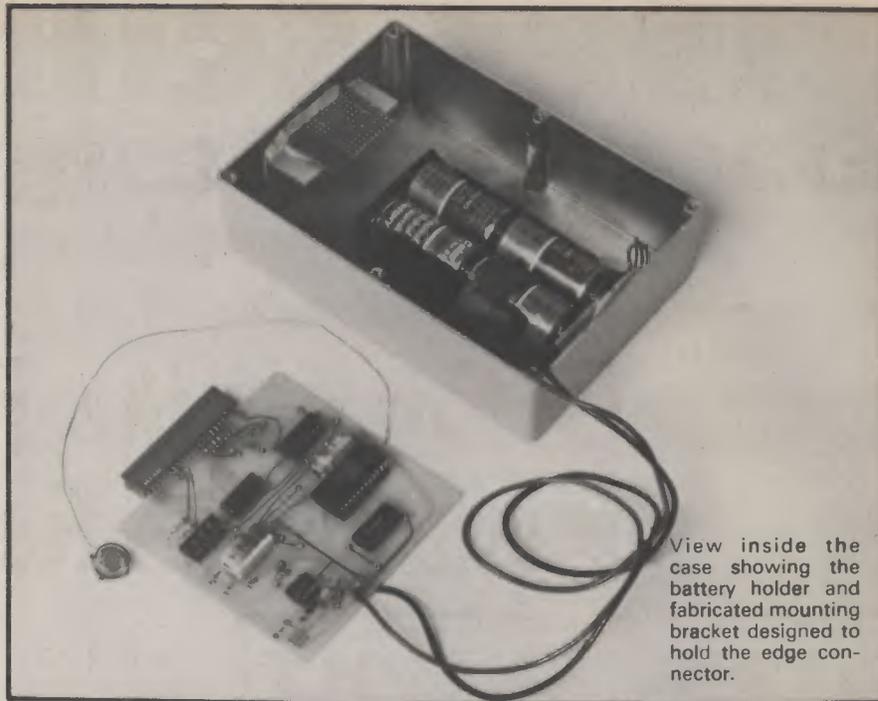6. Remove the module from the case (but do not disconnect batteries) and plug onto the Spectrum edge connector—with or without the ZX Printer.
7. Connect the Spectrum power supply.
8. Enter the program (listed separately) and set S4 to the down position. RUN the program.
9. When complete, remove Spectrum power supply.
10. Remove batteries from holder (to switch Data Recorder off).

CONCLUSION

Like many electronics systems, further developments can be carried out. The Environmental Data Recorder described



View inside the case showing the battery holder and fabricated mounting bracket designed to hold the edge connector.

here uses less than 2mA compared with over 8mA in the original prototype unit presented for SEDAC. The timing circuit has been completely redesigned and the selection logic simplified.

Further developments could include multi-channel A/D conversion; using

switches to select the timing period and increasing the memory. A selectable voltage gain unit buffering the analogue input would be a useful feature. The prototype has been used extensively for light level comparison and no problems have been found. □

COUNTER INTELLIGENCE

BY PAUL YOUNG

Boost For CB

The other day I was idly wondering why the good people advocating a Citizen's police watch to assist the police and prevent burglaries, did not suggest that they use Citizen's Band Radio, when I spotted an intriguing piece in a national newspaper. It appears that young girls are using CB radio to lure men to their doom. My male colleagues would no doubt phrase this differently.

No, Paul Young is not leading a headlong rush to the nearest CB emporium. When you reach my mature and serene age and I sincerely hope you will, you will appreciate the wisdom of the great Groucho. When, in his eighties, he was asked if he still chased the girls, he replied: "Yes, but only downhill".

I mention all this, particularly for the benefit of my lady readers (if I have any). If your husband hints that you might like to buy him a CB radio for Christmas, I would suggest you should reply: "Of course darling, so long as I can have an extension speaker to listen in to you."

Finally, the CB jargon for a meeting of two CB enthusiasts is: "Eyeball to Eyeball". I wonder what the word spinners will dream up for this type of assignment? I

could think of a few, but I fear in a respectable family magazine like ours, they would not be printable.

All At Sea

I don't often get angry, my blood pressure prevents it but I must confess to getting hot under the collar, when I read of the plight of the transatlantic yachtsman Tom McClean.

He was crossing the atlantic in a yacht just about eleven foot in length. His only communication was through British radio amateurs. Along comes two officials from the licensing department and forbids the two "Hams" to communicate with him because he has no licence.

How I would love to have the power to act like Gilbert's Mikado and make the punishment fit the crime. I would place the two bureaucrats in an eleven foot yacht in mid-atlantic, not without a paddle but without any communication.

Time Out

Hardly a week goes by without some funny story concerning digital watches. The latest concerns a small boy riding home on his bicycle wearing his sister's watch.

Suddenly the strap broke, and in order

not to lose it, he put it in his mouth. Then to add to his misery, he hit a bump which caused him to swallow it.

He went along to his G.P. who was certainly a bit behind the times, and obviously not a reader of EE. "That's all right son, I will follow its progress with my stethoscope."

The final outcome was a happy one, his grandfather gave him a Silver Hunter with a tick that would have done credit to Big Ben, and, to phrase it delicately, in due course time passed.

Atomic Cars

Seeing a headline a short time ago: "New 'A' Car Craze Sweeps Britain", I immediately jumped to the wrong conclusion. "Aha!" I said, "atomic driven cars, the obvious answer", only to find they were talking about number plates. Rather a let down I'm afraid, though I am certain the day will come when we shall be driving them.

Consider for example, the Polaris submarine. The fuel container is about the size of a dustbin but the atomic contents, not only propel the vessel, it also provides all the power for heating, cooking, lighting and all ancillary equipment and even turns the sea-water into oxygen for breathing. Unbelievably, it only needs replacing every seven years. Translate that into car terms and think what it could do!

Alas, they may not arrive in my life time, but by way of compensation I see the Wizard of Electronics, I mean of course Sir Clive Sinclair, hopes to have his Electric Car coming off the production line by the end of 1984. So, if you see me running up the road singing: "I'm Off to See the Wizard", you will know the reason why.

1984 SCHOOLS Electronic Design Award COMPETITION

*Build for the Future
and Reap the Rewards*



THE TWELVE FINALISTS WILL SHARE OVER £3000 AND PARTICIPATE IN AN ALL-EXPENSES-PAID TWO-DAY VISIT TO LONDON DURING JULY 1984

For the third year running Mullard Ltd.—the largest electronic components company in the UK—and Everyday Electronics join forces to present a rewarding challenge to Secondary Schools within the United Kingdom.

As distinct from the two previous contests, this year the conditions have been somewhat broadened so that entries can relate to *electronic equipment having practical use anywhere within the school, or at any external event in which the school participates.*

FIRST PRIZE The Sedac Trophy and £300

SECOND PRIZE £200

THIRD PRIZE £100

NINE RUNNERS-UP. A selection of components valued at £100.

Plus a selection of components valued at £200

In addition, all twelve finalists will receive a certificate and one year's subscription to EVERYDAY ELECTRONICS—and will enjoy an all-expenses-paid two-day visit to London during July 1984.

Science teachers of Secondary Schools are invited to apply for a Registration Form which contains full details of this competition.

Write to: SEDAC Schools Competition, Room 2130, King's Reach Tower, Stamford Street, London SE1 9LS.

Secondary School Pupils—make sure your school accepts this challenge and enters this contest. So bring this announcement to the attention of your science teacher or the head of your school.

Closing date for Registration:

30 November 1983

Closing date for submission of Papers:

31 January 1984



SCHOOLS ELECTRONIC DESIGN AWARD COMPETITION (SEDAC)
SPONSORED BY MULLARD LTD AND EVERYDAY ELECTRONICS



MICROCOMPUTER INTERFACING TECHNIQUES

INCLUDING MANY USEFUL CONSTRUCTIONAL PROJECTS

PART SIX: ANALOGUE DATA MULTIPLEXING AND 4-CHANNEL ADC

BY J. ADAMS B.Sc., M.Sc. & G.M. FEATHER B.Sc.

In Part 4 of this series, the techniques of analogue-to-digital conversion were discussed and a practical single channel system, using the successive approximation type of converter, was described.

In this part, the associated techniques of analogue data multiplexing and signal conditioning will be dealt with together with the construction of a high speed four channel data acquisition system.

The first part of a series dealing with transducers for use with this (and other) systems will be published in later issues of EE.

SIGNAL CONDITIONING

The output voltage ranges of transducers to be used with ADCs will not usually be compatible with the analogue input voltage range of the converter.

As an example, a bridge network used for developing an analogue voltage which represents the deflection of a strain gauge might produce only a few millivolts, which is far too small to apply directly to the input of the ADC.

Some form of amplification is then usually necessary and circuits based upon operational amplifiers are generally employed. The simple theory of operational amplifiers with applied negative feedback is well known, but it is helpful to deal briefly with it here.

In Fig. 6.1a, the operational amplifier is used in the inverting mode, that is, the input and output signals are out of phase with each other and the voltage gain, G , of the arrangement is dependent only on the values of input resistor R_{IN} and feed-

back resistor R_F . The voltage gain may be obtained from the simple formula

$$G = R_F/R_{IN}$$

Note that the feedback signal is applied to the invert (-) input of the device, so giving negative feedback.

Fig. 6.1b shows a non-inverting amplifier configuration and, in this case, the voltage gain G may be calculated using the formula

$$G = 1 + (R_F/R_1)$$

The input impedance of this arrangement is very high indeed—a desirable feature if it is to be used to amplify analogue voltages from transducers which may themselves possess relatively high source impedances.

In the practical four-channel system described, each analogue input is applied to its own signal conditioning amplifier, the non-inverting configuration being used. The analogue signal range of each channel is 0–100mV full scale and the full scale input range of the ZN448 ADC used is 2.5V. The amplifiers are thus required to give a voltage gain of $(2.5/0.1) = \times 25$.

Using the voltage gain formula, we see that:

$$25 = 1 + (R_F/R_1)$$

and, choosing a value of 10k Ω for R_1 , then R_F should have a value of 240k Ω . The accuracy of the system is partly dependent upon the amplifier gains, and close tolerance resistors should be used for these components. (The channel gain is easily changed by using another value for R_F , but voltage gains of more than

$\times 100$ should not be attempted with a single operational amplifier.)

LOW-PASS FILTERING

Many transducers develop very low level signals and problems can arise with spurious signals originating from, for example, voltages induced into the system by 50Hz mains fields. Careful circuit layout and screening is helpful, but with data acquisition systems in which the signals are sampled and measured very rapidly, serious errors can arise if false signals are present.

Since most analogue quantities encountered will change fairly slowly, the corresponding electrical signals developed by the transducers will be of very low frequency and some signal conditioning circuits entail the use of low-pass filters which allow only the low frequency signal voltages to be passed onto the output, higher frequency spurious signals being heavily attenuated.

The response of a typical low-pass filter is shown in Fig. 6.2. A later article dealing with the development of a single conditioning amplifier for very low level biological signals will include a more detailed description of a typical low-pass filter.

BBC Microcomputer users will be aware that the model B already possesses a 4-channel analogue input facility. The ADC employed is a 12-bit device but its conversion time is rather slow. Transducers intended for application with the system described in this article can be employed with the BBC machine if the analogue section of the circuit is con-

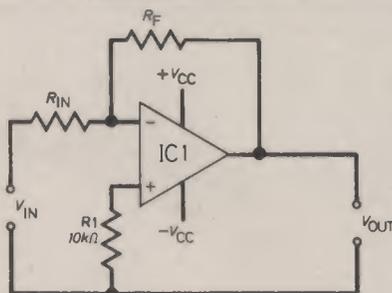


Fig. 6.1a. The operational amplifier shown is being used in the inverting mode.

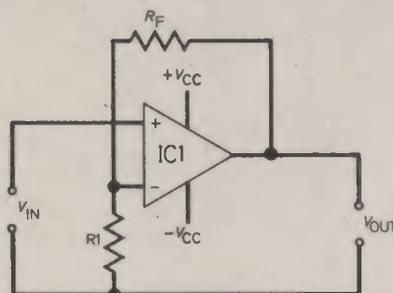


Fig. 6.1b. The configuration for a non-inverting amplifier.


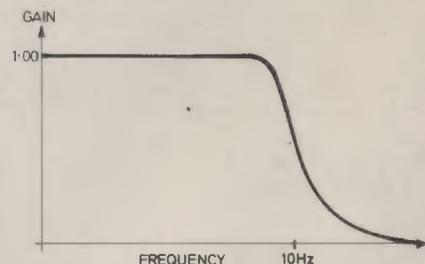


Fig. 6.2. The response for a typical low-pass filter.

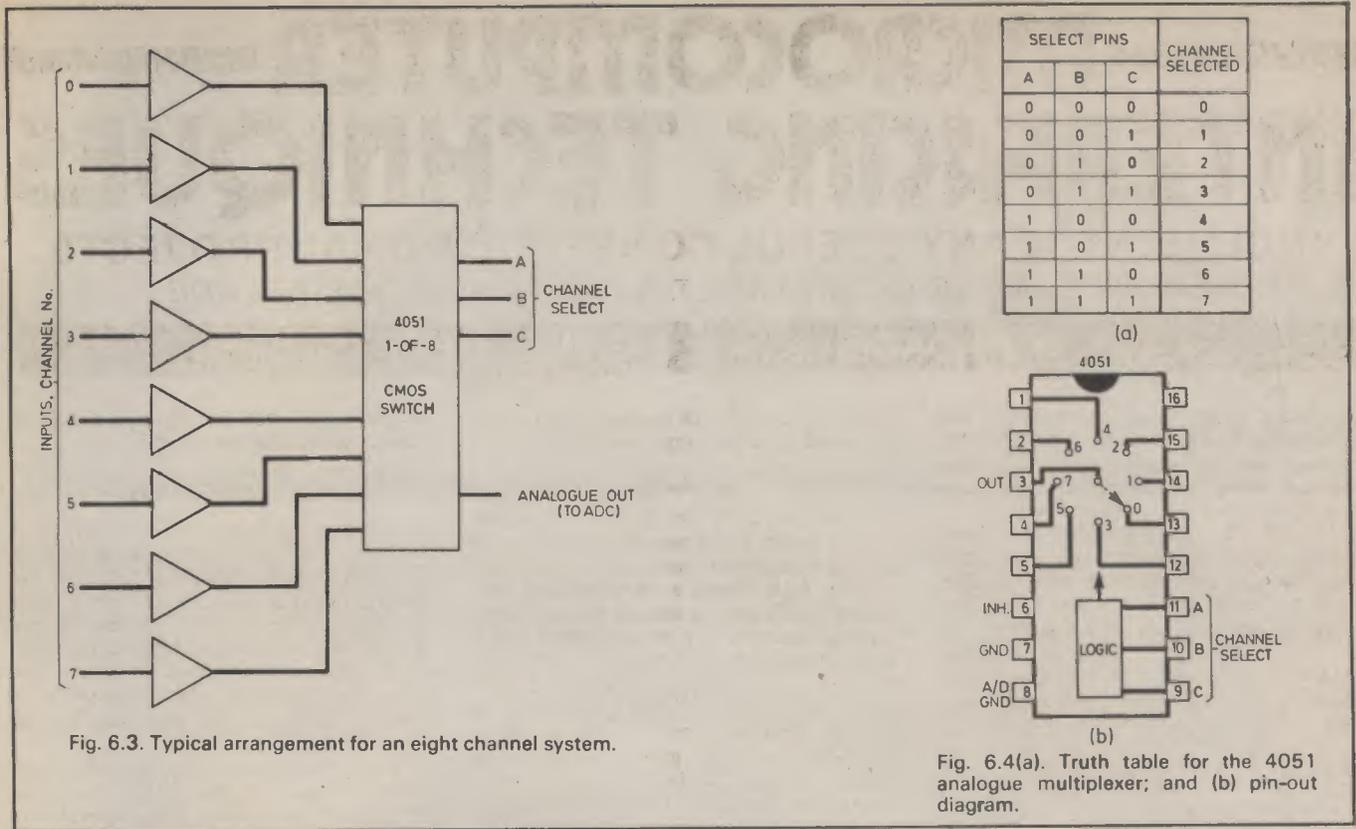

structed and the amplifier gains are altered to an appropriate value. Details of this are given at the end of the article.

ANALOGUE MULTIPLEXING

ADCs offering multiple analogue input channels are available, for example, National Semiconductors ADC0816/ADC0817 Single Chip Data Acquisition System allows 16 analogue inputs), but Ferranti's ZN448 is a single channel device only.

In order to accommodate several channels of analogue data, some form of multiplexing technique is necessary, in which the individual channels are connected one at a time to the input of the ADC. Integrated circuit switches which can perform this function are available in both CMOS and TTL; the switching operation is usually controlled by applying binary signals to the channel select pins of the device. Fig. 6.3 shows a typical arrangement for an eight channel system.

The 4051 analogue multiplexer behaves basically as a single-pole, 8-way switch, the switch position being determined by the binary code presented to the channel select pins. Its truth table and pin-out diagram are shown in Fig. 6.4.

CHANNEL SELECT CODE

In the project described, four channels are required and a CMOS 4052 dual 4-channel multiplexer is employed.

The binary channel select code can be

generated in a number of ways. A single pulse (which could be obtained from the ADC end of conversion signal, EOC) can be used to increment a three-bit binary counter and the code generated then applied to the analogue switch.

An alternative method, employed by the authors in the four channel system described, offers a "software solution" in which the appropriate code is generated by the microcomputer itself. This code is then presented at the user port and routed

to the analogue multiplexer via the two least significant lines available at the user port. Clearly, these switching code signals must only be present on the port lines when the microcomputer is not engaged in a data read operation.

During the channel select period, the tri-state facility of the ZN448 output latches is utilised to effectively disconnect the ADC from the data bus lines; the tri-state enable/disable signal being generated in software.



4 CHANNEL HIGH SPEED ADC




THE PRACTICAL CIRCUIT

Fig. 6.5 shows the circuit of the complete 4-Channel ADC. Each of the four analogue signals to be monitored (in the range 0–100mV) is applied to the input of its signal conditioning amplifier, IC1 to

IC4, CA3140 CMOS devices are used here and offer low power consumption and extremely high input impedances. As mentioned previously, the gain of each amplifier is set at $\times 25$ by the $240\text{k}\Omega/10\text{k}\Omega$ feedback resistor combination.

The amplifiers are situated on a separate p.c.b. to that used for the channel switching and ADC sections of the circuit, thus obviating the possibility of any interaction between the large TTL level pulses present in that part of the

Fig. 6.5. Complete circuit diagram of the 4-Channel High Speed ADC.

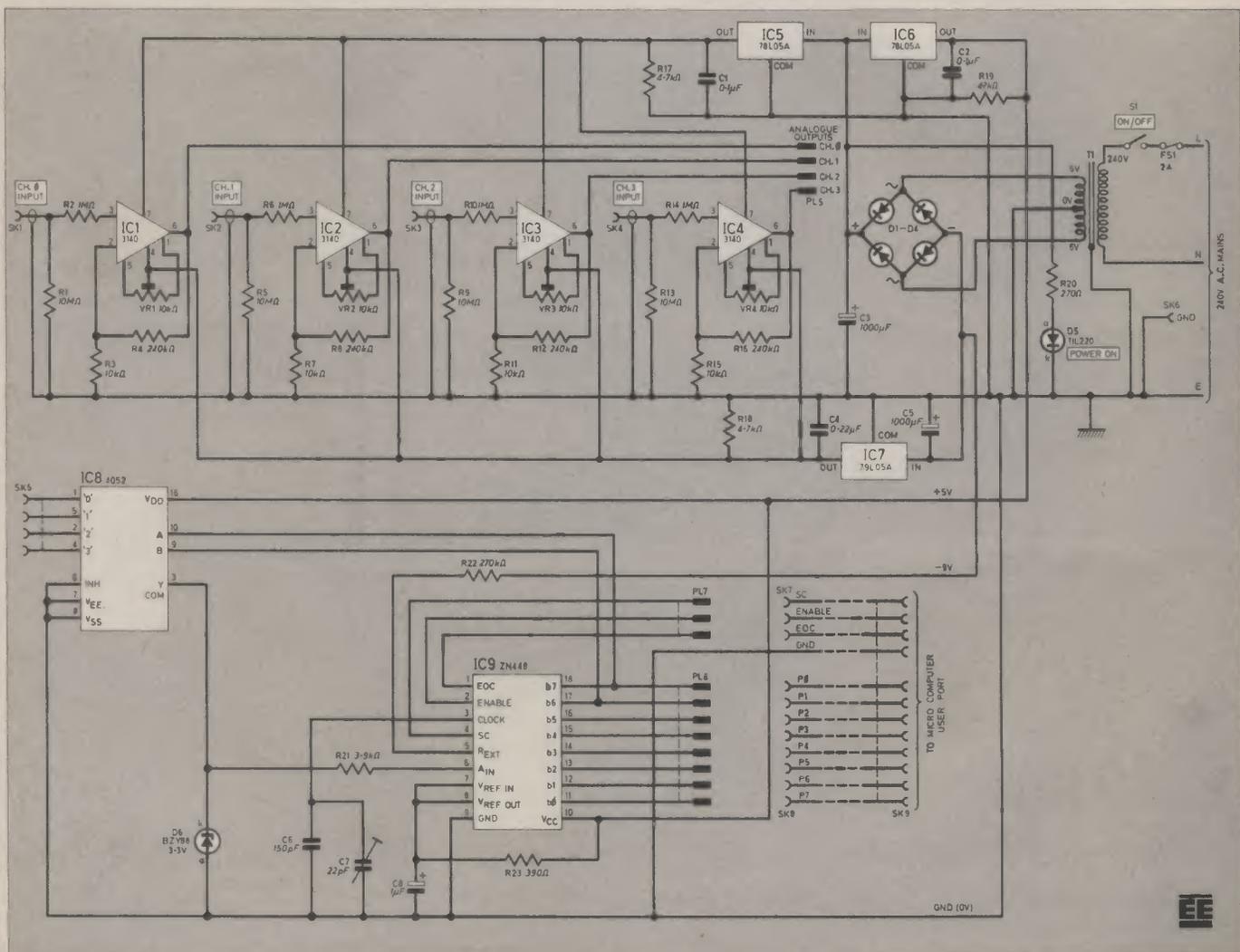

circuitry and the relatively low level analogue voltages present at the op-amp inputs.

The amplifier outputs are connected to the inputs of the 4052 dual, one of four CMOS switch, IC8 (only one half of the i.c. is used), and the output pin of this provides the analogue input to the ZN448 ADC. Zener diode, D6, provides protection for the ADC in the case of over range inputs by simply conducting when the p.d. across it (and the input to the ZN448) exceeds about 3V.

The ADC section of the circuit is similar to that used in the single channel converter in Part 3 except that it has been arranged for unipolar operation (that is, it can only convert input voltages which are positive with respect to ground). Transducers employed with this system should develop voltages suitable for this mode of operation.

The conversion rate has been reduced considerably (to about 30,000 per second) by increasing the size of the clock timing capacitor C6. The slower operating rate, is again, appropriate to the transducers used with the ADC.

The two channel select lines of the 4052 switch are connected directly to the P0 and P1 (two least significant bit) lines of the user port whilst the tri-state enable pin, instead of being grounded (and permanently enabling the latches) is taken, via the ribbon cable to pin M of the user port, this pin being used to output the tri-state control signals.

The power supply section of the circuitry is constructed largely on the analogue board and is quite conventional. A single +5V supply is required for the ZN448 and this is provided by the 78L05A voltage regulator IC6.

CONSTRUCTION OF THE BOARD

Printed circuit boards are used for both analogue and digital sections of the circuit and full size patterns are given for these in Figs. 6.6 and 6.8. These boards are available from the *EE PCB Service*, Order codes 8312-01 and 8312-02, respectively.

Starting with the analogue board, 8-pin d.i.l. sockets should be inserted and carefully soldered, as shown in Fig. 6.7. The five link wires should now be carefully formed and soldered into the appropriate positions. 22 s.w.g. bare tinned copper wire is used here. The seven Veropins should now be inserted, pressed home and soldered to the copper tracks.

PL5 is a 4-way inter-p.c.b. plug and this should be inserted and soldered in next.

All other components should now be inserted and soldered, particular care being taken with electrolytic capacitors and the three voltage regulators. (Readers should note that the p.c.b. appearing in the photograph is the prototype. The layout given in Fig. 6.6 is an improved version and hence differs slightly from the original.)

Construction of the digital board, Fig. 6.9, follows along similar lines and again readers should note that there are slight differences between the p.c.b. layout of original and published designs.

Connection to the microcomputer user port is via a 12-way cable and two inter-p.c.b. plugs, a 10-way and a 4-way type are employed for this purpose. Ribbon or multicore cable can be used.

An aluminium case of dimensions 27.5 x 19 x 9cm was used to house the prototype. The front panel should be drilled to accommodate the four bnc analogue input sockets (SK1-SK4), the mains switch and the power on indicator l.e.d. The rear panel needs drillings for the fuse, mains lead, and ribbon or multicore user port cable.

The mains transformer (6-0-6V at 100mA) should be mounted as shown in Fig. 6.10, which also gives the interwiring arrangement for the boards. With all of these components mounted, the boards should be fixed in place and the various interconnections completed.

SETTING UP AND TESTING THE UNIT

After switching on, power supplies to both analogue and digital boards should be checked. If either is incorrect, switch off immediately and locate the fault. If all is well, the operational amplifier offsets should be nulled.

A digital voltmeter should be connected between GND and the output

COMPONENTS

Resistors

R1,5,9,13	10M Ω (4 off)	
R2,6,10,14	1M Ω (4 off)	
R3,7,11,15	10k Ω (4 off)	1% metal film
R4,8,12,16	240k Ω (4 off)	1% metal film
R17,18,19	4.7k Ω (3 off)	
R20	270 Ω (2 off)	
R21	3.9k Ω	
R22	270k Ω	
R23	390 Ω	
All $\frac{1}{4}$ W carbon $\pm 5\%$ except where stated otherwise		

Capacitors

C1,2	0.1 μ F polyester type C280 (2 off)
C3,5	1000 μ F 16V elect. (2 off)
C4	0.22 μ F polyester type C280
C6	150pF ceramic
C7	22pF compression trimmer
C8	1 μ F 16V elect. radial leads

Semiconductors

IC1-IC4	CA3140 f.e.t. input op-amp (4 off)
IC5,6	78L05A +5V fixed voltage regulator (2 off)
IC7	79L05A -5V fixed voltage regulator
IC8	4052 CMOS dual 4-input analogue multiplexer
IC9	ZN448 analogue-to-digital converter
D1-D4	VM28 0.9A d.i.l. bridge rectifier
D5	TIL220 red l.e.d. plus fixing bush/clip
D6	BZY88C3V3 3.3V 400mW Zener diode

Miscellaneous

SK1-SK4	bnc panel mounting socket (4 off)
SK5	4-way inter p.c.b. socket
SK6	4mm insulated panel mounting socket
SK7	4-way inter p.c.b. socket
SK8	10-way inter p.c.b. socket
SK9	Commodore user port connector 12 + 12-way double-sided card edge type, 0.156 inch pitch
PL5, 7	4-way inter p.c.b. straight plug (2 off)
PL8	8-way inter p.c.b. straight plug
T1	mains primary/6-0-6V 100mA secondary
VR1-VR4	10k Ω miniature horizontal preset (4 off)
FS1	2A 20mm type with panel mounting fuseholder

Printed circuit boards: Analogue board single-sided size 127 x 95mm, *EE PCB Service*, Order code 8312-01, Digital board single-sided size 127 x 95mm, *EE PCB Service*, Order code 8312-02; d.i.l. sockets: 8-pin (4 off), 16-pin (1 off), 18-pin (1 off); single-sided Veropins (18 off); bare tinned copper wire; 12-core cable (1m); rubber grommets (2 off); cable retaining clips (2 off); 4BA fixings (2 sets); 6BA fixings (6 sets) and 20mm spacers (4 off); metal case approx. 280 x 190 x 90mm; rubber feet for case.

COMPONENTS
approximate
cost **£48**

See
**Shop
Talk**
page 801

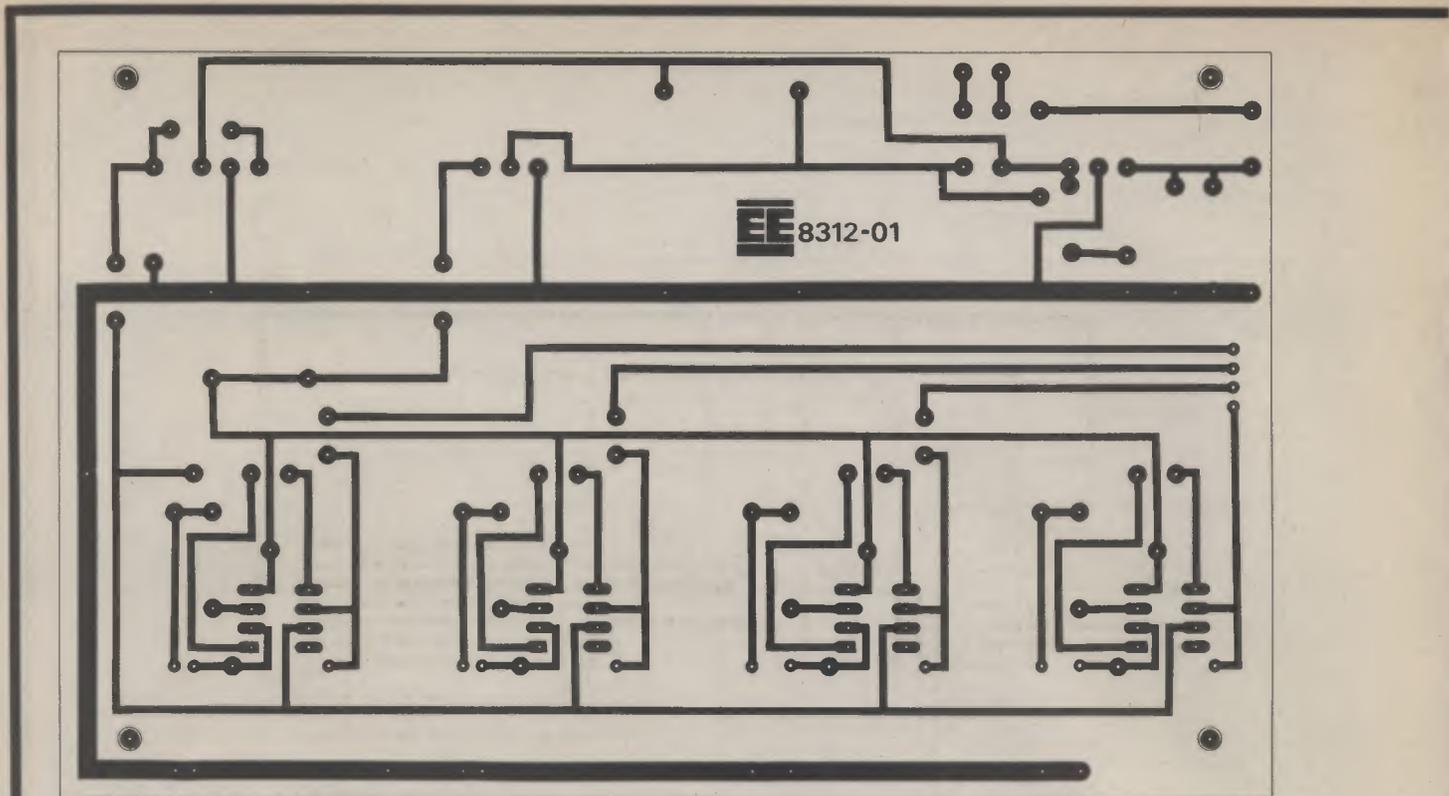


Fig. 6.6. Full-size printed circuit board master for the analogue board.

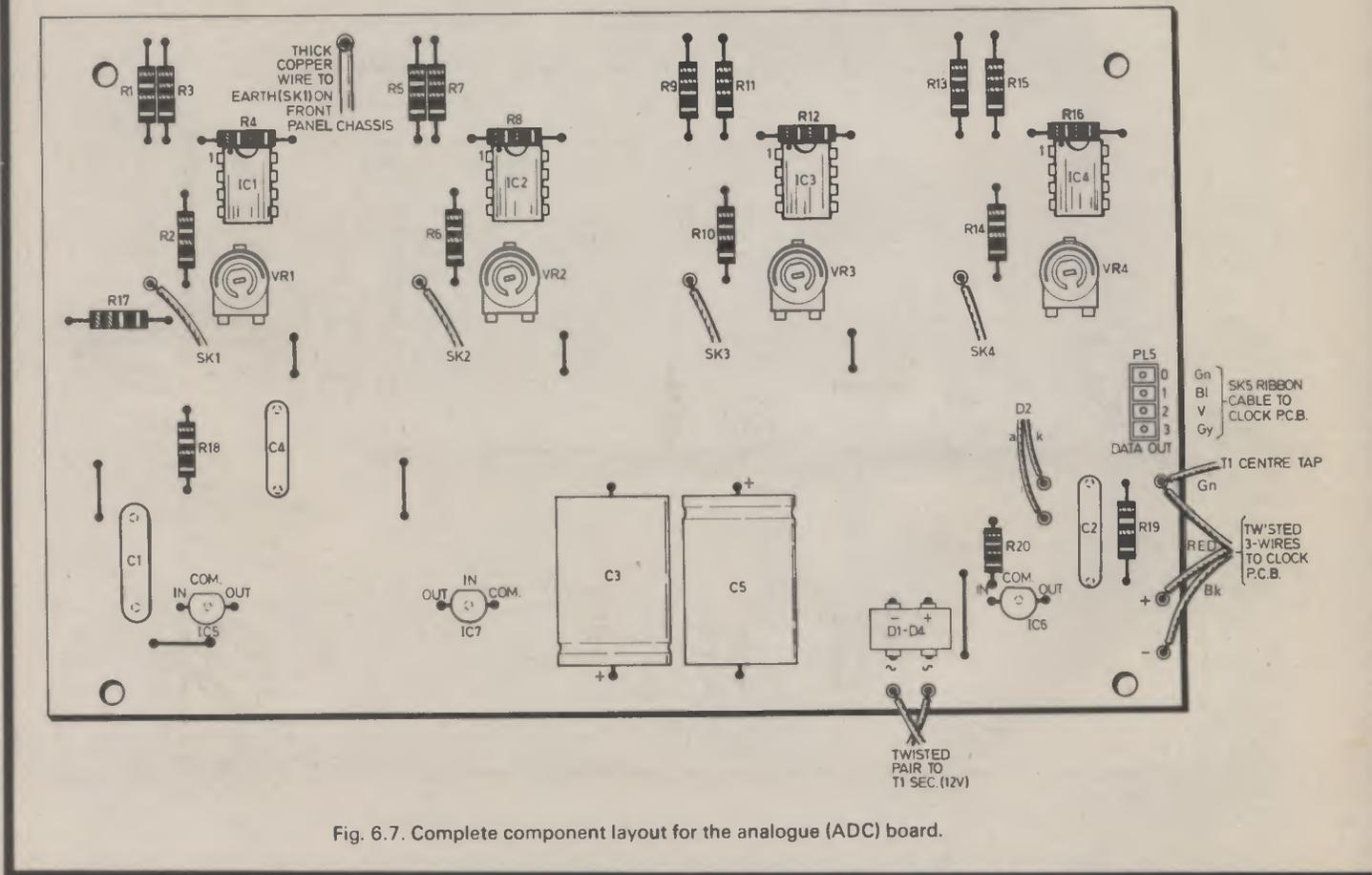


Fig. 6.7. Complete component layout for the analogue (ADC) board.

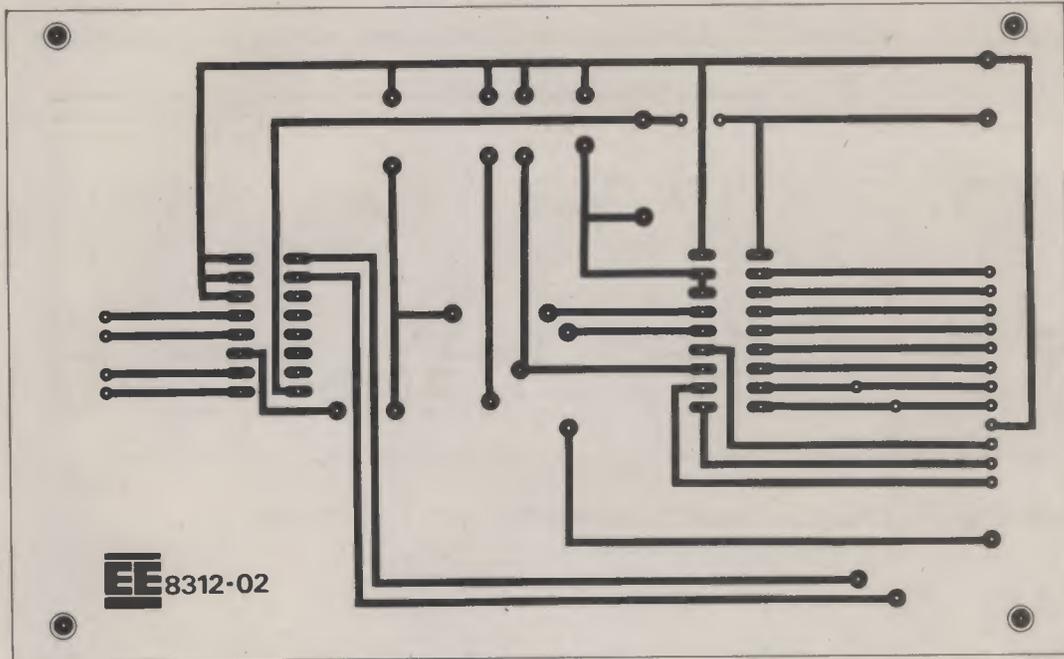


Fig. 6.8. Full-size printed circuit board master for the digital board.

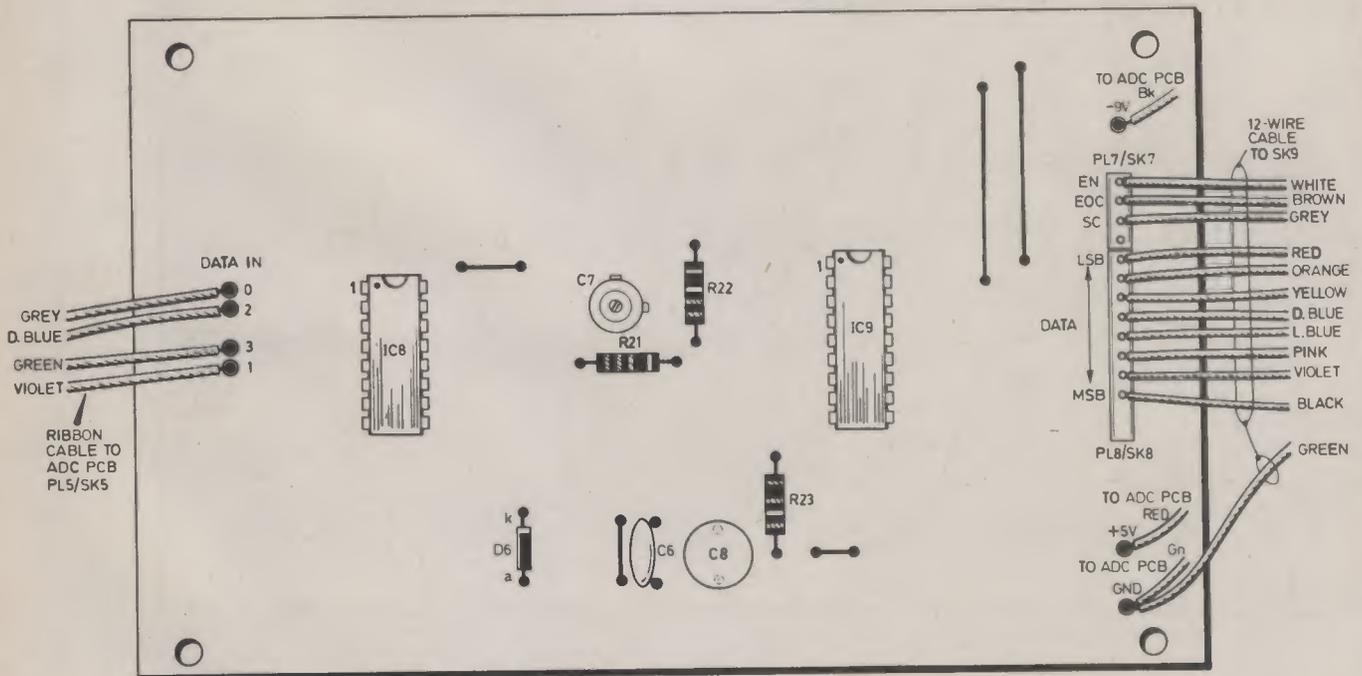


Fig. 6.9. Complete component layout for the digital (clock) board.

EVERYDAY
ELECTRONICS
and computer **PROJECTS**

SUBSCRIPTION SERVICE

A subscription for Everyday Electronics is the most convenient and reliable way of having your copy delivered direct to your home every month. Wherever you live you'll receive a regular copy of one of the foremost electronics magazines available, featuring a wide range of easy-to-build projects for home and leisure use.

Use the addressed envelope attached to this form to register your subscription and start understanding tomorrow's world today.

GIFT SUBSCRIPTIONS

An annual subscription to Everyday Electronics makes an ideal gift, especially at Christmas, for a friend, colleague or particularly a son or daughter as the younger generation are among our most enthusiastic readers. It is easily arranged and we will even send a card announcing your gift, with your own personal message attached. Just complete the appropriate section of the order form overleaf.

SUBSCRIPTION SERVICE

...WE'LL KEEP YOU POSTED!

MOISTEN HERE AND FOLD DOWN

EVERYDAY
ELECTRONICS
and computer **PROJECTS**

4 CHANNEL HIGH SPEED ADC

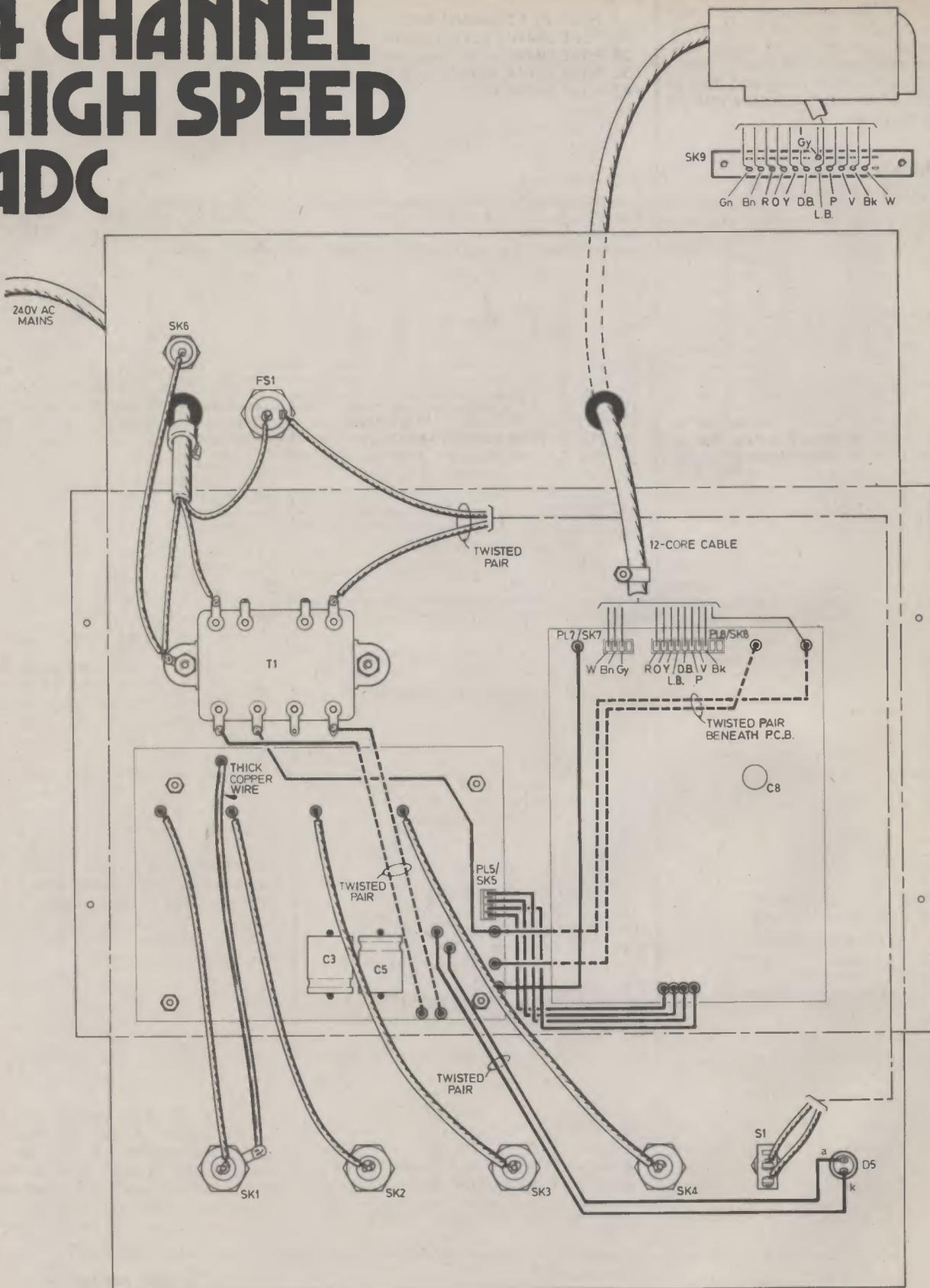


Fig. 6.10. Interwiring diagram for the two boards.

side of the 240kΩ feedback resistor in each channel; the analogue inputs should be short circuited. Rotation of the offset-null potentiometers should bring each output to zero.

The system is now ready and may be connected to the microcomputer with the appropriate plug.

COMMODORE MICROCOMPUTERS

To select one of the four analogue signals for conversion it is necessary to present the binary representation of the channel number to the channel select inputs of the 4052 (IC8). As four channels are employed in this design only two channel select lines are connected to two lower order lines (P0 and P1) available at the user port.

Initially these lines must be configured for output as the microcomputer must select the appropriate analogue input. This is accomplished by setting the requisite bits in the data direction register for the particular port. The ADC must then be instructed to initiate conversion of the selected analogue input into an eight-bit digital form.

One of the lines available at the top of the user port can be selected to provide this start conversion pulse. Pin 7 allows the same pin connections for both PET and VIC-20 microcomputers whereas pin 8 is used with the Commodore 64.

PET: Pin 7 is the cassette-write line which is automatically initialised for output. This can be used to fashion the start conversion pulse as follows:

```
POKE 59456,PEEK(59456)OR8
POKE 59456,PEEK(59456)AND247
POKE 59456,PEEK(59456)OR8
```

VIC-20: Pin 7 is derived from Port A. It is necessary to initialise this line for output by setting bit 5 in the data direction register for the port (37139) before sending the line to logic high by appropriate bit manipulation of the Port A I/O register (37151).

```
POKE 37139,PEEK(37139)OR32
POKE 37151,PEEK(37151)OR32
POKE 37151,PEEK(37151)AND223
POKE 37151,PEEK(37151)OR32
```

Commodore 64: Pin 8 is a handshaking line and allows a one-shot pulse to be output following any read or write of Port B. This is ideal for initiating conversion of the analogue input. For example:

```
POKE 56577,0
```

In this application Pin M at the user port is not used to fashion the start conversion pulse (unlike the single channel ADC detailed in Part 4 of this series). When the line attached to Pin M is held low the tri-state facility is enabled allowing relevant data to be read by the microcomputer.

Full software listings for collecting the data from the ADC are given below for the three Commodore machines catered for in this series.

PET

```
5 REM PET 4 CHANNEL ADC
10 POKE 59468,PEEK(59468)OR192
20 POKE 59468,PEEK(59468)AND223
30 POKE 59456,PEEK(59456)OR8
40 POKE 59459,255
50 INPUT C
60 IF (C-1)*(C-3)*(C-2)
  *C=0 THEN GOSUB 500
70 GOTO 50
500 POKE 59471,C
510 POKE 59456,PEEK(59456)AND247
520 POKE 59456,PEEK(59456)OR8
530 POKE 59459,0
540 POKE 59468,PEEK(59468)AND223
550 PRINT PEEK(59471)
560 POKE 59468,PEEK(59468)OR32
570 POKE 59459,255
580 RETURN
```

VIC-20

```
5 REM VIC-20 4 CHANNEL ADC
10 POKE 37147,PEEK(37147)AND227
20 POKE 37148,PEEK(37148)OR192
30 POKE 37148,PEEK(37148)OR32
40 POKE 37139,PEEK(37139)OR32
50 POKE 37151,PEEK(37151)OR32
60 POKE 37138,255
70 INPUT C
80 IF (C-1)*(C-3)*(C-2)
  *C=0 THEN GOSUB 500
90 GOTO 70
500 POKE 37136,C
510 POKE 37151,PEEK(37151)AND223
520 POKE 37151,PEEK(37151)OR32
530 POKE 37138,0
540 POKE 37148,PEEK(37148)AND223
550 PRINT PEEK(37136)
560 POKE 37148,PEEK(37148)OR32
570 POKE 37138,255
580 RETURN
```

COMMODORE 64


```
5 REM COMMODORE 64 4 CHANNEL ADC
10 POKE 56578,PEEK(56578)OR4
20 POKE 56576,PEEK(56576)OR4
30 POKE 56579,255
40 INPUT C
50 IF (C-1)*(C-3)*(C-2)
  *C=0 THEN GOSUB 500
60 GOTO 40
500 POKE 56577,C
510 POKE 56579,0
520 POKE 56576,PEEK(56576)AND251
530 PRINT PEEK(56577)
540 POKE 56576,PEEK(56576)OR4
550 POKE 56579,255
560 RETURN
```

BBC MODEL B

As previously mentioned, the BBC Model B Microcomputer has an internal 4-channel 12-bit ADC. The full scale analogue voltage of each channel is 1.8V and the analogue board design given can be used to give a 100mV range if the feedback network is modified slightly. The gain required is now $\times 18$ and, using the op-amp gain equation for the non-inverting mode:

$$G = (1 + R_F/R_{IN})$$

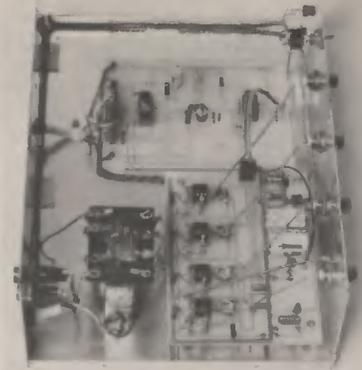gives a ratio of 17 for R_F/R_{IN} . Suitable resistor values for R_F and R_{IN} are 220kΩ



and 13kΩ, respectively (R_F should actually be 221kΩ, but a 220kΩ resistor is within 0.5% of this). Once again, close tolerance resistors should be employed.

The +5V regulator for the digital board supply can be omitted. Outputs from the board should be taken to the BBC analogue input via screened cable and the appropriate miniature 15-way D-type plug.

BBC MICRO SOFTWARE

The form the BASIC statement used, to extract digital information from the BBCs ADC, is

$$X = ADVAL(N),$$

where N refers to the channels numbered 1,2,3,4. The number returned is in the range 0 to 65520 in steps of 16. This may seem odd when the converter itself produces a number in the range 0 to 4095. The reason for this is to allow for future converters with higher resolutions.

It should be added that a resolution of 1 part in 256 (that is, approximately 0.4% for 8-bit resolution), is quite adequate for most applications since transducer and signal conditioning tolerances are seldom better than 1%.

The number for each channel is stored in the twelve most significant bits of two eight-bit memory locations so that the largest digital value is

111111111110000 in binary

which is 65520 in decimal. As the least significant four bits are always zero the numeric results increase in steps of 16. To obtain digital values in the range 0 to 4095 then the actual value must be divided by 16.

As the channel readings are taken sequentially on an interrupt basis every 10 milliseconds then if less than four channels are required it is sensible to disable those channels not in use so that time is not wasted converting them.

The command to accomplish this is

*FX16,N

where N is the number of channels enabled. (If N = 0 then all channels are disabled.)

Next month: Biological Amplifier with High Speed ADC

EVERYDAY news

... from the world of

NEW ELECTRONICS—*BBC puts schools on right wavelength*

BBC School Radio is breaking new ground with three innovative series designed to prepare schoolchildren for the new electronic age: (1) *Using Your Computer*, a 5-part series for 9 to 12 year olds; (2) *Junior Electronics*, a 5-part series for 9 to 12 year olds and (3) *Microtechnology*, a 10-part series for 'O' level and CSE students. These series have been prepared by the BBC with help from the Microelectronic Education Programme (MEP) and the Department of Industry.



Using Your Computer

Using Your Computer started on Nov. 1, 2.20pm on Radio 4 VHF. It is expected that this series will help teachers in primary and middle schools to introduce children to the computers supplied to schools under the DoI "computers in schools" scheme, that is the BBC Micro model B, the Sinclair Spectrum and the Link 480Z.

The series offers a completely new dimension in educational broadcasting in which recorded radio broadcasts are synchronised with specially prepared software to use the graphic, sound and "computing" abilities of these micros to provide a fully integrated audio/visual presentation. In this way the computer is given a friendly voice (it is in fact the voice of Fred Harris well known to children in the mentioned age group) which guides the children through the initial stages of the operation and application of the machine. Thus children learn to use a computer by using a computer.

Junior Electronics

Junior Electronics begins on Feb. 28, 1984, on Radio 4 VHF at 2.20pm. In this series of programmes the children are piloted through very simple practical work, learning to construct basic electrical and electronic circuits on a custom designed circuit board, which is a component in a special kit of parts, on sale from BBC Publications.


The last of the five broadcasts is a Radiovision programme in which the children are shown the relevance of the real-life applications of the circuits they have been working with, such as—why a street light automatically lights up, and how a burglar alarm works.

This and the previous series are designed so that they can be handled by teachers with little or no previous knowledge of the subjects. Comprehensive teacher's notes are provided.

Microtechnology

Microtechnology starts on Jan. 20, 1984, on Radio 4 VHF at 10.45am. It forms an introduction to basic microelectronics leading to ideas of control technology and is dependent on the medium of Radiovision associated with practical work. There is a kit of parts, film strips and software, as well as a specially developed circuit board and a "safe" power supply unit for the experiments.

electronics

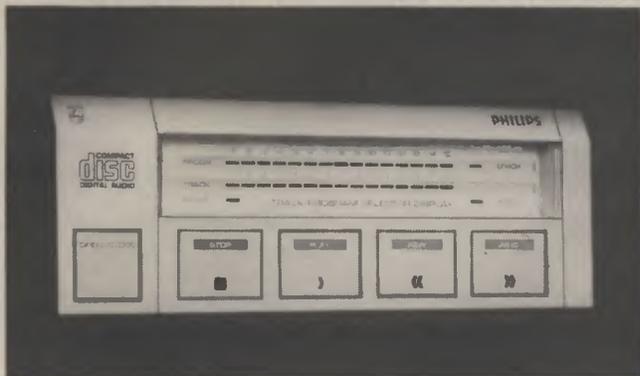

DIGITAL ROUTE FINDER


SIGNS of future developments in the digital audio field were in evidence at the recent *International Audio and Video Fair* held in Berlin.

One of the items that was shown for the first time was the **Philips In-Car Compact Disc Player**. Research, it is claimed, shows that the improved sound quality is clearly noticeable in the acoustic environment of a moving car.

Also, because of the large information storage capacity, the unit is not limited to sound

reproduction applications only. Future developments could include the presentation of route or touring information, for example, with a single disc replacing a number of conventional maps and guide books.

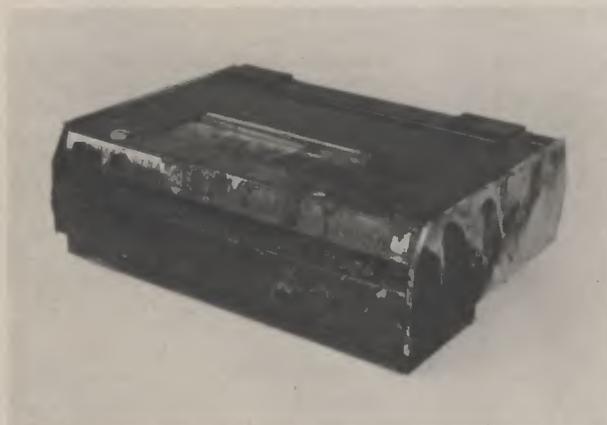The system is based on a 12cm diameter disc, carrying up to one hour of digitally encoded programme material which is read by a focused laser beam. The prototype car player will undergo a number of changes before it finally reaches the market, probably in two years time.



FIRE PROOF

When Data Dynamics claimed that their metal cased ZIP printers would stand up well to rough industrial usage they did not have incineration in mind.

However, when a fire broke out in a warehouse the printer received extensive damage from heat and flames—see Photo. The printer was retrieved from the remains and was found to be in perfect working order.

PLAY IT AGAIN SAM

From the nostalgia of movie classics like "Casablanca" and "Hard Times" to the latest film hits such as "On Golden Pond" and "A French Lieutenant's Woman", Humphrey Bogart (alias Kenny Wymark) was on hand to launch the long awaited CED VideoDisc system and video library from RCA.

This totally new videodisc system, which the manufacturers believe will have a major effect on the market, was announced in London recently. Launched initially as a joint venture by RCA, Hitachi and GEC, the new system is claimed to provide high quality pictures and sound at around half the price of most conventional VCRs.

The CED VideoDisc player—CED stands for Capacitance Electronic Disc—works on a principle similar to that of a hi-fi turntable. The disc is contained in a caddy, rather like a long-playing record sleeve. This is inserted into the player, the caddy is then withdrawn and playing begins automatically.

This simple operation ensures the disc itself need never be touched. A stylus reads the grooves on the disc, playing them back through any black and white

or colour television receiver. The signal produces both audio and visual playback.

The CED VideoDisc players are available in both mono and stereo versions and different models offer infra-red or wired remote control. The three models available include the VIP 101P, incorporating visual search, mono sound, scan and pause, which will sell for around £199.95 and the VIP 202P, which will sell for around £229.95 and which also includes stereo sound, full visual search and as an optional extra, wired remote control.

At the top of the range is the VIP 201P. This player, incorporates stereo sound, full visual search, full scan, pause and infra-red remote control. This will sell at around £259.95.

Disc prices, and there will be 100 titles available, will be £9.95 and £12.95. RCA plan to add new releases each month, starting December.



FOR YOUR ENTERTAINMENT

BY BARRY FOX

Confusing Law

The Olympia "Great Home Entertainment Spectacular" Show typified the confusion that now exists over what electronic gadgets are, and are not, legal.

In this column we have already explained how the law now requires people who sell telephones to mark them either with a green circle, signifying official approval, or with a red triangle, to show that they are prohibited from connection to the British telephone lines. But plenty of prohibited phones are on sale, sometimes but not always marked, and you don't risk a fine or prison if you connect one to your line. What you do risk is disconnection of your service, by British Telecom, if their engineers find out and you refuse to disconnect the prohibited phone yourself.

Although CB is now legal in Britain, it is only legal on the carefully specified frequencies. Likewise cordless telephones, which use a radio link to the handset, are only legal if they operate on carefully specified frequencies. Many cordless radio phones still on sale in Britain are illegal. In this case you don't just run the risk of annoying British Telecom and losing your phone service. You also run the risk of three months in jail and/or a £1,000 fine for contravening the Wireless Telegraphy Act.

Not surprisingly the public is very confused. At the Olympia Show, one stand was manned by the British Electrotechnical Approvals Board, which runs the scheme which tests telephones. They were giving away a leaflet that reminded people that "green is for go" and "red is for no". Literally feet away, another stand was showing telephones, many of them clearly marked with a red triangle as prohibited. They also had cordless telephones marked in the same way because they operate on illegal frequencies!

Citizen's Band TV

Even more confusing was the stand across the hall which was selling what the show catalogue described as "at last—your very own portable colour TV transmitter!" This neat little gadget, which costs £1,000, works as a miniature u.h.f. TV transmitter. You plug in a video camera, or video recorder, and it broadcasts the signal to any TV set tuned to the transmitted frequency.

The unit has three watts output power which, according to the company's salesman, carries up to seven miles. But for another £600 the salesman could offer a 100-watt amplifier that carries the signal 20 to 25 miles.

"Is Citizen's Band TV on the way?" asked the Olympia Show publicity. I asked the firm demonstrating the system about the law, and they told me that they were "speaking to the Home Office".

In fact, the Home Office is no longer responsible for radio regulations. The Department of Trade and Industry took on the job soon after the last election. During the show the DTI confirmed to me that the penalty for illegal TV transmissions was still a £1,000 fine and/or three months in jail.

To be fair, the firm selling the system did say, right at the bottom of the data sheet, that "the unit is not approved for use in the UK". But that's after a suggested list of uses, including amateur TV!

For the record, I *didn't* play spoil-sport and tell the Department of Trade and Industry where they could go to catch someone red-handed breaking the Wireless Telegraphy Act.

Flat-Screen TV

Suddenly flat-screen television, or rather pocket televisions with flat TV tubes, are in the news. Sir Clive Sinclair has finally launched the set which, in February 1981, he promised would be available during 1982.

The price has risen from £50 to £80, and the f.m. radio section has been dropped. One reason for the delay was an industrial dispute at the Timex plant in Dundee earlier this year. But is it really launched, and is it really a multi-standard set as claimed by the company's publicity?

Well, although the flat-screen TV was "introduced" in September, just in time to show at the *Great Home Entertainment Spectacular* at Olympia, no-one could actually buy one. When quizzed over availability, Sir Clive hedged, and talked about going into production.

My bet is that they won't be readily available until around Christmas. But at least Sir Clive has learned from past mistakes. He isn't taking money up-front from mail orders until he is ready to supply.

This is what caused such bad feeling over his computers. People were encouraged to send money for something that wasn't actually available.

On the question of "multi-standard" operation, I don't doubt that the set will, as Sir Clive says, automatically switch between 525-line and 625-line operation and cope with the different sound and vision frequencies used in Europe. But note well that the Sinclair set receives only u.h.f. TV, whereas most television in 525-line countries like America and Japan is on v.h.f. Some Continental TV is also on v.h.f.

Later models will have a tuner which sweeps between 40MHz and 900MHz, to receive all television and f.m. radio broadcasts around the world. But that's in the future. So far the sets are u.h.f. only.

And how will they work on tubes, buses, trains, cars and planes? I asked to borrow a set after the press launch, but wasn't even allowed to buy one to test. They weren't, I was told, ready. So I took a Sony Watchman TV to the press conference and tried one against the other.

The Sony, at three times the price, pulled in a better picture. But watch out for a low cost Watchman in the near future. It's already on sale in America.

I then took the Sony Watchman on some trips. It won't work at all on an underground train. It works reasonably well, but erratically, on overground transport, like a bus.

I can't imagine watching for pleasure, because you keep losing the picture as you

turn a corner or pass a building. Remember that u.h.f. waves travel in straight lines, and don't penetrate into concrete boxes or metal cabins half as easily as long or medium wave radio transmissions.

In The Air

I then tried using the Sony on board an aircraft flying to Munich but was soon stopped by the cabin crew. The airlines are frightened that TV equipment may interfere with their navigation equipment.

I used it long enough to find out about another problem. At ground level a u.h.f. TV set picks up only local stations. That's why different transmitters around the countries can share the same frequency. But up in the air you pick up everything from hundreds of miles around. So nothing is watchable.

The Sony worked well in Germany, picking up both u.h.f. and v.h.f. TV pictures in my hotel room. But most hotels now have a TV set in each room, often colour.

So, who wants to watch a two-inch black and white picture off expensive batteries, if there is a mains-powered large screen colour set on the table? And how often do you want to watch TV while sitting in a park or sight-seeing in a foreign city? And don't forget that foreign TV programmes have foreign language sound-tracks.

Bear all this in mind before rushing out to buy a pocket TV set just for the sake of buying a pocket TV set.

Hot Memory

A few words of advice for anyone buying a memory telephone that stores strings of numbers for repertory dialling.

Some of the most powerful memories on the market are not officially approved and use a two-wire connection to the phone line. This means that the memory jangles the bell of every other phone in the house as you make a call. But approved memory phones, which use three wires and don't cause bell jangle, usually offer less memory capacity for more money.

Check also whether what you are buying has a battery back-up. The more expensive memory phones contain a string of ni-cad rechargeable cells in series across the low voltage d.c. power line.

If the power fails this battery pack keeps the memory alive. Otherwise even a short interruption of power will lose every number you have keyed into the memory.

Cheaper memory phones may not have battery back-up. It is not a condition of official approval. For instance, I bought the Ace-Telcom approved phone, which for just under £100 has a memory store of 50 numbers.

Essentially it's an approved version of a previously unapproved Lamda phone from Hong Kong. But the Ace-Telcom does not have a battery back-up. So even a brief break in the power supply loses every number you have laboriously keyed into the memory.

I solved the problem by stringing six ni-cad pen cells in series with a 50-ohm resistor, and put them across the 9V d.c. supply. The resistor limits charging current, to prevent damaging the cells, but it lets through enough current to keep the memory alive if the mains cuts out.

But far better, in the first place, to buy a memory phone with a battery back-up built in. So check this before buying.

Ace-Telcom in Britain now tell me they are thinking of making some kind of modification. What a pity they didn't think about that before starting to sell a memory phone that is prone to amnesia.

JANUARY FEATURES

*Home Protection
from
Gas and Fire
Hazards*

Gas & Smoke Sentinel

This four-channel monitoring and alarm system gives early warning of gas leaks, and also of imminent danger of fire. Each of the four sensors can be installed in optimum position to detect either gas leaks or smoke in various parts of the house. The master control unit is equipped with red and green l.e.d.s which indicate status of each sensor. External 12V alarms can be connected and extended to any convenient point.

Guitar Tuner Scoreboard

A phase-locked loop is the basis of this tuner. Six tones corresponding to the notes from the open strings of an electric guitar are available for initial tuning and the final accurate adjustment of each string is performed with the aid of the tuning meter.

Adds individual scores of between 1 and 99 and stores the totals for up to four players. Total scores are displayed on a three-digit seven-segment display. The ideal (and indisputable!) electronic scorekeeper for games where running totals are kept.

THERMOMETER for ZX MICROS


Central Heating Pump Delay Unit

Senses the temperature of the circulating water and after the boiler has been switched off at the end of the heating period, keeps the pump running until the water has fallen below a preset temperature. This allows the radiators to extract most of the stored energy and deliver it as useful room heating.

*SAVE FUEL
this
WINTER*

EVERYDAY
ELECTRONICS
and computer PROJECTS

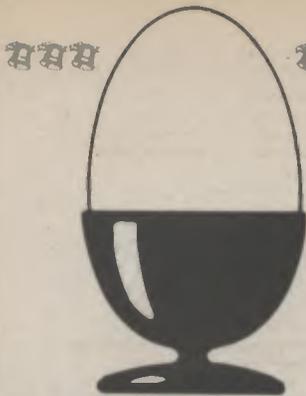JANUARY 1984 ISSUE ON SALE FRIDAY, DECEMBER 16



NOVEL EGG TIMER

BY I. HICKMAN

LET A CHICKEN TELL YOU WHEN YOUR EGG IS COOKED

UNLIKE most normal egg-timers, this project is based on an electronic circuit. The Novel Egg-Timer makes use of a deceptively simple circuit which makes a creditable imitation of a cackling chicken that has just layed an egg.

CIRCUIT DESCRIPTION

The complete circuit diagram is shown in Fig. 1. IC1 is a 14-bit binary counter with built-in oscillator and reset facilities. R2, R3, VR1 and C2 set the oscillation frequency to about 50Hz, the exact value is adjustable by means of VR1.

When the circuit is switched on, pin 12 is momentarily carried to +9V by C1, resetting all 14 counter stages to zero. C1 charges up via R1 releasing the reset and the counter starts counting. For the first 8092 cycles the output of the 14th stage, Q₁₄, stays low (0V) and the outputs of the two 4-input AND gates therefore also remain low.

On the 8093 cycle of the built-in oscillator, after approximately three minutes, Q₁₄ goes high (+9V). This enables IC2a and from then on the gates produce groups of four pulses (pin 13) and single pulses (pin 1) as shown in Fig. 3. Up until now the 555 timer IC3, which has been connected as an oscillator, has been inhibited by the low voltage on its reset pin (pin 2).

However, each time a positive-going pulse appears at pin 13 of IC2 its leading edge is differentiated by C3 and R4. This results in a narrow positive spike being applied to pin 4 of IC3, briefly enabling the oscillator.

The few cycles of oscillation that take place constitute a "cluck". On the fourth cluck the lower end of R4 is taken to +9V by the pulse at pin 1 of IC2, so pin 4 of the oscillator IC3 sees a full width pulse instead of a narrow pulse (Fig. 3).

Simultaneously, the pulse at pin 1 of IC2 turns on TR1 with the result that the voltage at pin 5 of IC3 starts to fall as C4

discharges via R6. This results in the extended fourth burst of tone having a rising pitch, the characteristic chicken's squawk following the three clucks.


The output at pin 3 of IC3 is coupled to the loudspeaker LS1 via C6 and the egg-timer produces sufficient volume to be heard even if there is no-one in the kitchen.

COMPONENT BOARD

The components are laid out on a piece of 0.1 inch matrix stripboard which is 39 strips by 31 holes and the layout is shown in Fig. 2. The use of d.i.l. sockets is recommended for the integrated circuits which should only be inserted when all the soldering is completed. Note that the CMOS devices should be handled with care.

The power supply is provided by a 9V PP3 battery which is contained within the case. The housing used for the project is left to personal choice.


Fig. 1. The complete circuit diagram of the Novel Egg-Timer.

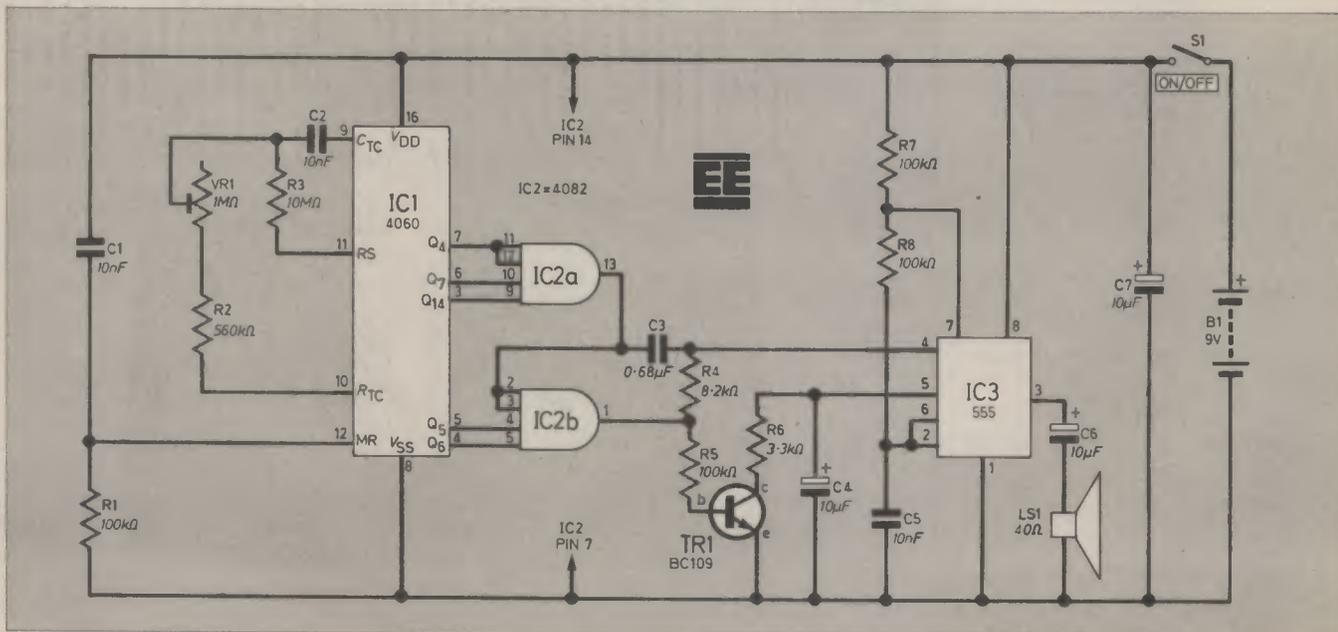

TESTING

Using an oscilloscope, check that groups of four pulses are obtained at pin 13 of IC2 and single pulses at pin 1 as shown in Fig. 3.

Fig. 2. The component layout and trackside view of the Egg-Timer circuit board. Note that on the prototype the author has used unfamiliar style electrolytic capacitors but any suitable type can be used.

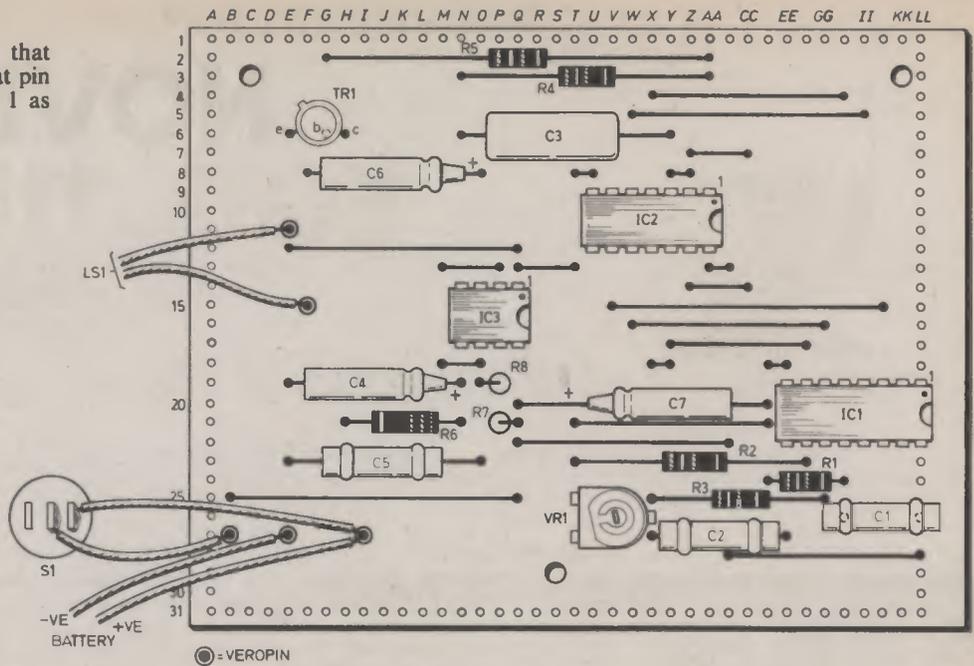

COMPONENTS
approximate
cost **£7**

COMPONENTS

Resistors

R1,5,7,8 100k Ω (4 off)
R2 560k Ω
R3 10M Ω
R4 8.2k Ω
R6 3.3k Ω
All $\frac{1}{4}$ W carbon $\pm 5\%$

See
**Shop
Talk**
page 801

Capacitors



C1,2,5 10nF ceramic (3 off)
C3 0.68 μ F polyester
C4,6,7 10 μ F 16V elect. (3 off)

Semiconductors

TR1 BC109 silicon *n*p*n*
IC1 4060BE CMOS
14-stage ripple counter
and oscillator
IC2 4082BE CMOS dual
4-input AND gate
IC3 NE555 timer i.c.

Miscellaneous

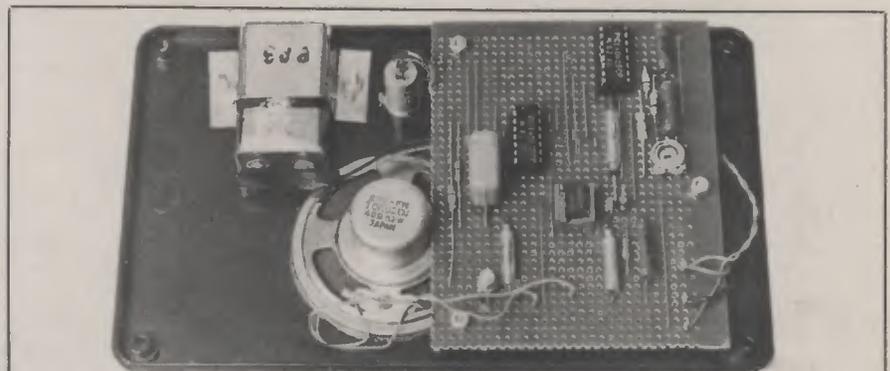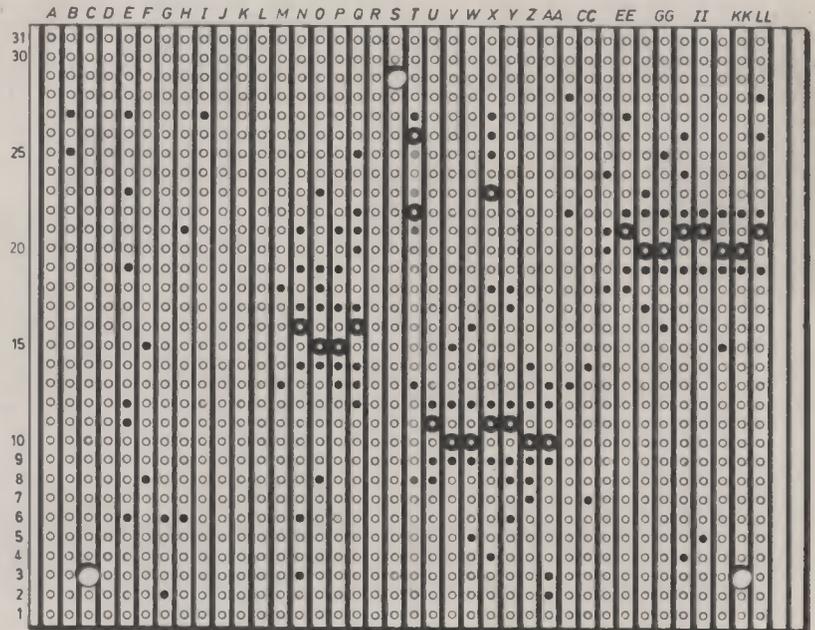VR1 1M Ω lin. miniature
carbon preset
S1 s.p.s.t. miniature toggle
LS1 miniature, 64 Ω , 60mm
dia. approx.
B1 9V PP3
Stripboard: 0.1in matrix size 39
strips by 31 holes; case, 180 x
110 x 50mm; 8-pin d.i.l. i.c.
holder; 7-pin d.i.l. i.c. holder; 4-pin
d.i.l. i.c. holder; battery clip.



Component board shown fitted to the lid of the case, with off-board wiring details also shown.

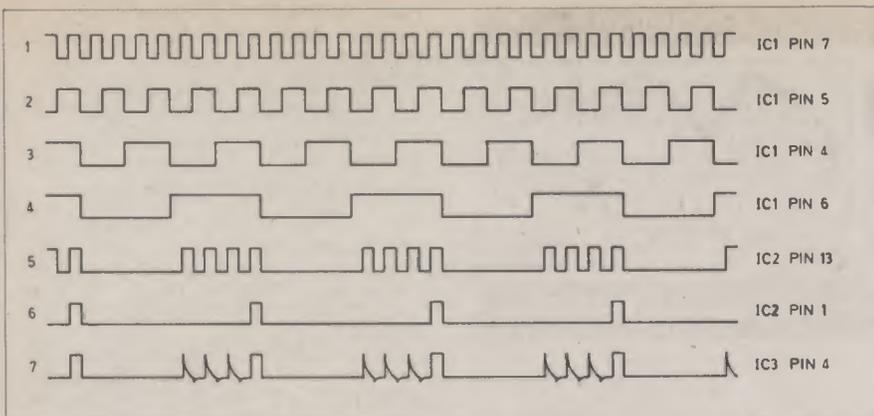


Fig. 3. Shown are the pulses that should be obtained when testing IC1, IC2 and IC3 with an oscilloscope. Note that pin 4 of the oscillator IC3 sees a full width pulse instead of a narrow pulse on the fourth count to produce the "squawk".

Switch the unit on and check that the waveforms at pins 13 and 1 of IC2 only commence after approximately three minutes. Increasing or decreasing the value of C3 will make the clucks longer or shorter. Decreasing or increasing the value of R6 will cause the final squawk to rise higher or not so high.

Reducing the value of C5 will cause the sound of a squawk to rise more rapidly. The final values of these components may be chosen to produce what sounds you like but the values shown will generally prove satisfactory.

One final note, if you leave the egg-timer switched on after it has started to sound, it will continue to do so for the set amount of time (as set by VR1). It will then fall silent for a set time and then start to sound again, this will continue indefinitely. □

BOOK REVIEWS



BEGINNER'S GUIDE TO INTEGRATED CIRCUITS SECOND EDITION

Author I. R. Sinclair
Price £4.35 Limp edition
Size 185 x 124mm. 194 pages
Publisher Butterworth & Co. Ltd. (Newnes Technical)
ISBN 0-408-01301-X

As the name suggests "Beginner's Guide to Integrated Circuits" is a book intended for the comparative new-comer to electronics. The book contains nine chapters and the first deals with basic electronic theory, which gives a good grounding for the more complex chapters to come.

Many examples are given of practical i.c. circuits; and linear, digital integrated circuits are also covered. The microprocessor and associated chips are also described with comprehensive diagrams to support the text. As before Ian Sinclair has managed to produce an outstanding book for the beginner to electronics.

R.A.H.

25 SIMPLE AMATEUR BAND AERIALS

Author E. M. Noll
Price £1.95 Limp edition
Size 178 x 110mm. 63 pages
Publisher Bernard Babani
ISBN 0 85934 100 3

MANY radio enthusiasts construct their own aerials and "25 Simple Amateur Band Aerials" should prove a useful reference book to even the most experienced constructor.

Starting with a simple dipole aerial the book describes how to build 25 amateur band aerials, including a mini-rhombic made from four TV masts.

All the aerials described are inexpensive and easy to construct, and each new aerial has a diagram to support its introduction with clear informative text. Finally, there are a complete set of dimension tables which will help you identify an aerial on a particular frequency. Data is also provided for the spacing and cutting of phase lengths.

R.A.H.

SERVICING MONOCHROME PORTABLE TELEVISION

Author G. R. Wilding
Price £13.50 limp
Size 295 x 210mm. 138 pages
Publisher Butterworth & Co. Ltd. (Newnes Technical)
ISBN 0 408 01143 2

IF YOU are involved with, or merely interested in, the servicing of TV sets, then this book will be an invaluable addition to your library. Mr. Wilding has spent over 40 years servicing and writing about televisions and this guide presents a comprehensive insight into how current portable black and white receivers operate (which, incidentally, represent the largest proportion of "second" sets throughout the world).


Covering a diversity of British, European and Japanese models, the well illustrated text discusses typical faults and their rectification with special emphasis on new and unusual circuitry. A large section of the book is given over to the reproduction of circuit diagrams and board layouts of many popular and currently available portables.

G.P.H.

Books in Brief

IBA Technical Review No 20, "Developments in Teletext" by Technical Editor Paul Gardner (IBA). This 69-page book, with 57 illustrations, includes seven papers written by engineers working the teletext field. The Review covers the ten years of teletext development; the enhancements of additional levels including the possibility of using alpha-geometric coding; networking; integrated circuit decoders; and the NEWFOR system of teletext subtitling developed at the University of Southampton.

RADIO WORLD

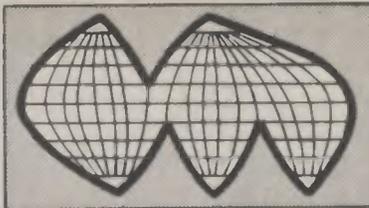

BY PAT HAWKER G3VA

Where Have All The Viewers Gone

Over six years ago, in one of the broadcasting journals, I wrote an article "Broadcasting to the two-set home". In this I pointed out that if, as to me seemed likely, the number of homes with more than one TV set continued to rise (in the period 1970-75 it had doubled from only 3 per cent to about 6 per cent) this would need to be taken into account in the planning of broadcast programmes and schedules.

I began this article as follows: "Generals, it is often said, always prepare to fight the last war all over again. Broadcasters, if they are to avoid this mistake, need to be more perceptive of change; to detect the way in which the public taste and viewing patterns are gradually changing". Programmes I stressed, need to be on the basis of current public viewing habits suitable for the conditions under which the public views, the times when it views, and the sets on which it views.

Not everyone in broadcasting agreed with me. One senior administrator told me that the second set was just a passing phase—amounting to little more than keeping an old black-and-white set when buying or renting a new colour set.

Another was much upset at my suggestion that it could no longer be taken for granted that everybody sitting in a room in which there was a switched-on TV set was necessarily watching the programmes and advertisements with bated breath, but might be doing other things such as reading or even dozing, using the programme as a background accompaniment to other activities. Nor did the quote that "television is the only activity that occupies more time in the home than sleeping—though some would observe that the two pastimes are synonymous"—go down too well. The stream of television, I suggested, goes on—the mind wanders off to its own explorations or just sinks into timeless oblivion!

In the intervening six years the number of two-set homes has continued to increase—until today about a third of UK homes are in this category. But, potentially even more significant, has been the impact of almost three-million video recorders.

This enables viewers both to choose and make up their own programme schedules, either by buying or renting cassettes or by using the recorders as time-machines to view broadcast programmes at convenient

times. A breach of copyright but who takes notice of this?

It now seems certain that two-set homes, and more especially video recorders, are affecting TV audiences, not only the head-counts of people watching top-rated programmes at the time they are transmitted, but also public attitudes to television. The old idea of programmes being "compulsive viewing" is being by-passed by the new technology.

One does not worry over much about bad programmes—more significant is that what, by any standard, are some extremely good programmes seem no longer to attract the audiences that would have watched them six years ago. And as a final straw a scientist is now suggesting that the brain rhythms of a TV viewer are almost the same as those of someone asleep!

Still Spinning

Most people believe that interest in low-definition mechanical television came to a stop in 1935 with the ending of BBC's transmissions of the 30-line Baird system, although a few European radio amateurs continued transmitting low-definition patterns up to about 1939.

Very few seem to have heard about the revival of interest in NBTV (narrow band television) in the past few years, sparked off initially in Australia. Today there is in the UK a very active *Narrow Bandwidth Television Association* made up of members interested in mechanical forms of television, though much of it is considerably more sophisticated than the old spinning Nipkow discs of the Baird era.

The NBTA under chairman D. B. Pitt (1 Burnwood Drive, Wollaton, Nottingham) publishes a quarterly newsletter that reflects a good deal of active interest in closed-circuit home-built mechanical systems and there are plans to transmit 32-line pictures on 144MHz in a bandwidth of 9.6kHz. An NBTV convention was held recently (10 September) near Manchester, and another at Nottingham last May.

One of the developments is a camera based on solar cells. The pictures may seem crude, but enthusiasm still runs high.

Happy Workers

A survey of how electronics engineers feel about their work, based on 650 replies to a questionnaire in the American "Electronics" magazine, suggests that almost 86 per cent are very or reasonably satisfied with their work. Only 14 per cent unsatisfied or

hardly satisfied; 72 per cent believe they are fairly paid, against 24 per cent who think the opposite.

Two-thirds would again study engineering, if they had their time over again, though some 11 per cent would switch to the medical or dental professions. Some 9 per cent would opt for pure science and 6.5 per cent for business administration.

Almost 88 per cent would encourage their children to study engineering; 28 per cent believe that what they are doing is very important to the well-being of society; 54 per cent believe their work is "fairly important", only 1.6 per cent rate it as "unimportant".

Fewer than half American engineers earn more than \$40,000 per year, and average starting salary for fully qualified engineers is about \$25,000. About 10 per cent top the \$60,000 mark.

In the States, as in the UK, the quickest way to top earnings appears to be developing new computer-based video games. However, market-busting software tends to have a meteorite rise but an equally fast fall, often all within a single year.

Tiny TV

It is too early to predict whether Sir Clive Sinclair will succeed in making a financial as well as a technical success of his pocket TV set. I remember an earlier Sinclair model shown at Earl's Court in the 1960s that never really got going.

The flat tube in his new set represents the fulfilment of ideas first proposed in the 1950s by Denis Gabor, the man who also predicted the development of holography. Then again, the Ferranti chip used by Sir Clive succeeds in putting virtually all the basic stages of a black-and-white, multi-standard TV set onto a single chip, a remarkable feat.

Similarly, the 15-hour Polaroid lithium battery must be the first time one of these high-energy batteries has been used in British consumer electronics. It will also be interesting to see whether his mail-order-now, pay-later approach (to cover the possibility of production delays?) will succeed: it is an approach that is unlikely to prove popular with the retail trade! Walk-about audio has proved a winner but does not involve the problem of looking at a picture while watching where you are going!


Pen Radios

For over a year I have had one of those low-cost Japanese digital watches in the stem of a ball-point pen. The watch has worked perfectly, the miniature battery seems easy to replace though this has not been necessary so far. My trouble is that I have never succeeded in finding out how to fit an ink refill! I have a compact watch but a full-size empty pen.

Now I see Mullard/Philips have marketed an integrated circuit (TDA 7000) that contains virtually all the circuitry (except for 14 tiny ceramic capacitors) needed to form a complete v.h.f./f.m. radio small enough to fit inside a pencil, wristwatch or key-ring. I suppose you could also fit a tiny earphone in the pen and then stick it in your ear.

Sounds fine, but I hope the set manufacturers make it simpler to fit those ink refills!

BY R. A. PENFOLD

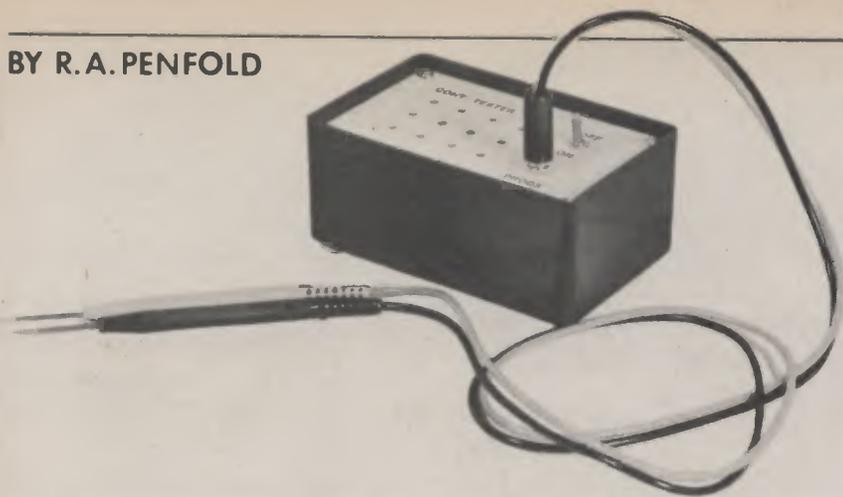

CONTINUITY TESTER

DESPITE the fact that a Continuity Tester is an extremely simple piece of test equipment it can nevertheless be very useful when fault-finding on electronic equipment. Uses of continuity testers include such things as checking fuses, tracing broken wires or printed circuit tracks, checking diodes, and tracing short circuits on printed circuit boards.

An ordinary multimeter switched to a low resistance range can be utilised as a continuity tester, but this method is often inconvenient in use due to the need to look away from test prods or probes and at the meter each time a check is made.

When checking complex circuit boards, switches or something of this nature, it is often necessary to concentrate on the test prods in order to keep them in good contact with the appropriate two points. Another problem is simply that some multimeters pass quite a high current when used on a low resistance range and there is a consequent risk of damaging delicate semiconductor components.

AUDIO TONE

This simple Tri-State Continuity Tester design provides an audio tone to indicate continuity, and the maximum current that can flow through the circuit under test is only a little over 1mA. This means that there is no real risk of components being damaged while making tests using the unit. An unusual feature of the circuit is its indication of three levels of continuity rather than the usual two.

It provides a low frequency tone if a very low resistance of just a few ohms is detected, a higher tone if a higher

resistance is detected, and no tone if a resistance of more than a few hundred ohms is present across the test prods.

Many continuity testers will indicate continuity if a forward biased semiconductor junction is present between the test points. This can produce misleading results when checking circuit boards for broken tracks or short circuits as there are likely to be numerous semiconductor junctions present in the circuit, bearing in mind that these junctions can be part of a

transistor or integrated circuit and do not have to be present in the form of a diode.

This tester clearly differentiates between a true low resistance path, a slightly higher resistance or semiconductor junction, and a high resistance path, so that much of the ambiguity that can occur when testing circuit boards with a conventional continuity tester is avoided.

CIRCUIT DESCRIPTION


The full circuit diagram of the continuity tester is shown in Fig. 1, and the only active device used in the unit is an MC3302P quad comparator (IC1). A voltage comparator of this type has an *npn* output transistor which is used in the common emitter mode, but does not have a built-in load resistor or other form of collector load.

The output transistor is switched off if the inverting (-) input is taken to a higher voltage than the non-inverting (+) input, and is switched on if the comparative input states are reversed.

There is no built-in triggering in the comparators and they can have the output transistor partially switched on if the input voltages are balanced. It is therefore possible to use a comparator as an operational amplifier by adding a load resistor at the output and IC1c is used in this way. R10 is the load resistor and this comparator is used in what is a well-known operational amplifier oscillator configuration. The values specified for R9 and C1 set the operating frequency of the oscillator at a fairly low audio frequency of only about 100Hz.

The potential divider chain consisting of R1, R2, D1 and R3 biases the inverting input of IC1a to about 0.75V, and the inverting input of IC1b to only a few millivolts above the negative supply potential. R4 takes the non-inverting

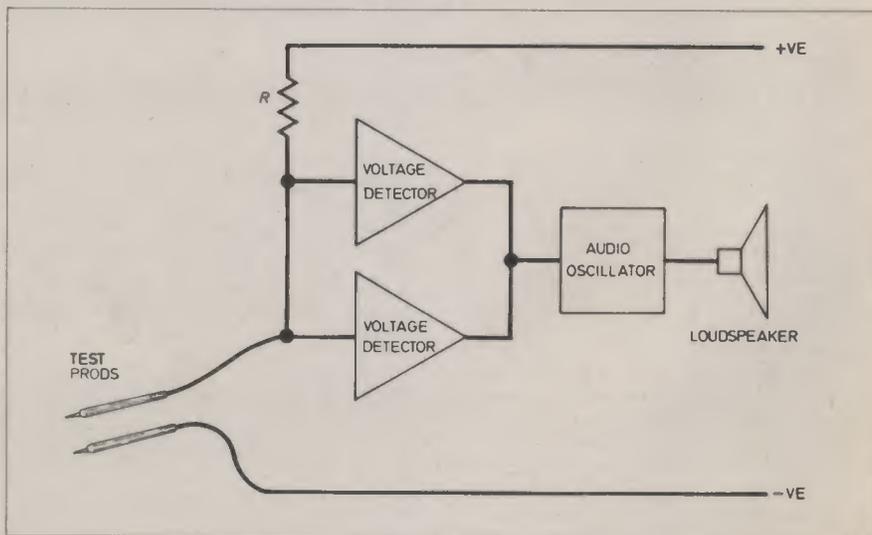The circuit is based on two voltage detectors and an audio oscillator. The oscillator drives a loudspeaker which then produces the audio tone and indicates continuity between the test prods. By indicating two degrees of continuity the unit eliminates the misleading results that can be produced by a simple continuity tester.



COMPONENTS

Resistors

R1	10k Ω
R2	100 Ω
R3	10 Ω
R4	8.2k Ω
R5	47k Ω
R6,7,8	220k Ω (3 off)
R9	100k Ω
R10	5.6k Ω
R11,12	270k Ω (2 off)
R13	470 Ω
All $\frac{1}{4}$ W carbon $\pm 5\%$	

See
**Shop
Talk**

page 801

Capacitors

C1	10nF polyester
C2	100 μ F 10V elect.


Semiconductors

D1	1N4148 silicon signal diode
IC1	MC3302P quad comparator

Miscellaneous

S1	s.p.s.t. miniature toggle
LS1	miniature, 64 Ω , 66mm dia. approx.
B1	9V PP3

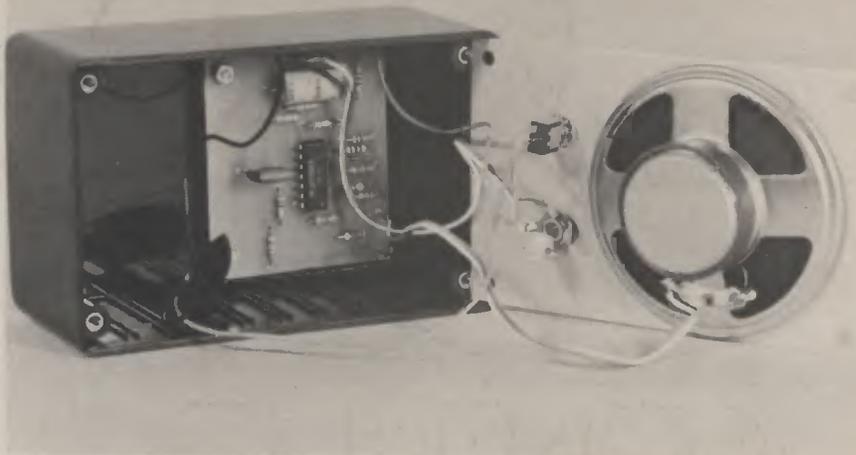Printed circuit board: single-sided size, 64 x 51mm, EE PCB Service, Order code 8312-08; case 111 x 71 x 48mm; battery connector; 6BA fixings.



Lid removed showing the inter-wiring details inside the case.

COMPONENTS
approximate
cost **£9.00**

inputs of both IC1a and IC1b to virtually the full positive supply voltage, and the output transistors of both devices are switched on with the circuit as it stands. The output transistor of IC1a holds the input of IC1c at little more than the negative supply potential and prevents the oscillator from operating.

If a low enough resistance is connected across the test prods the non-inverting input of IC1a will be pulled down to a lower voltage than the 0.75V bias fed to

the inverting input, causing IC1a's output transistor to switch off and the oscillator to operate.

However, the oscillator will not operate normally unless a resistance of about 8 ohms or less is placed across the test prods, so that the input voltage to the non-inverting input of IC1b is taken below the minute bias voltage fed to the inverting input of this comparator. Unless this requirement is met the output transistor of IC1b effectively connects R5

in parallel with R7 so that the operating frequency of the oscillator is boosted to around 300Hz.

Thus the required tri-state indication is obtained with a high resistance giving no oscillation, a very low resistance giving low frequency oscillation, and an intermediate resistance giving a higher frequency tone. IC1c could be used to drive the loudspeaker (LS1), but its output transistor is switched on under stand-by conditions and this would result in a rather high quiescent current consumption.


The loudspeaker is therefore driven via IC1d which is used as an inverter, and this gives a quiescent current drain of only about 3mA, with the current consumption rising to about 10mA when the unit is activated. R13 ensures that the current fed to LS1 does not exceed the maximum permissible output current for comparators in the MC3302P device and this 20mA limit means that the unit does not generate a very loud tone.

In this application high volume is not necessary and this is not of any practical importance.

CASE

A plastic case having an aluminium front panel and approximate outside dimensions of 111 x 71 x 48mm is suitable for this project, and represents about the smallest case that will comfortably accommodate all the components. A matrix of holes about 3mm to 5mm in diameter are drilled in

Fig. 1. The complete circuit diagram of the Continuity Tester.

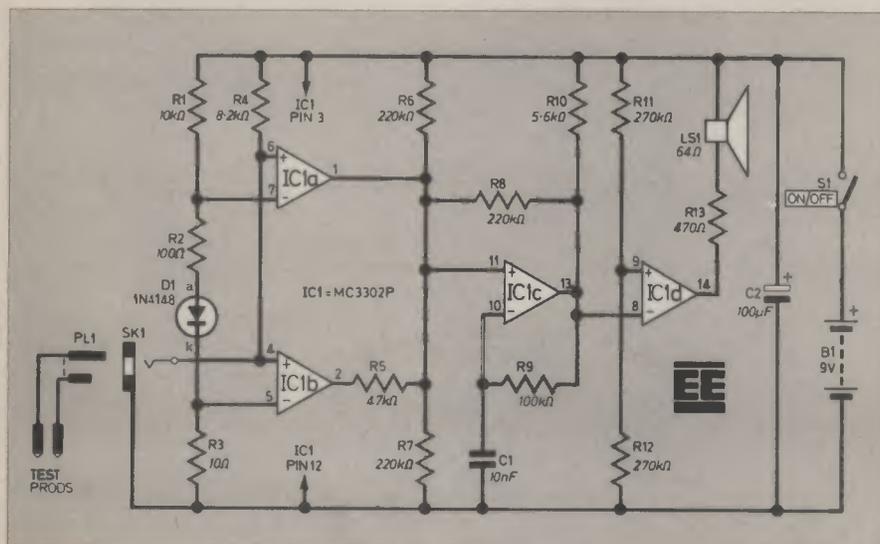


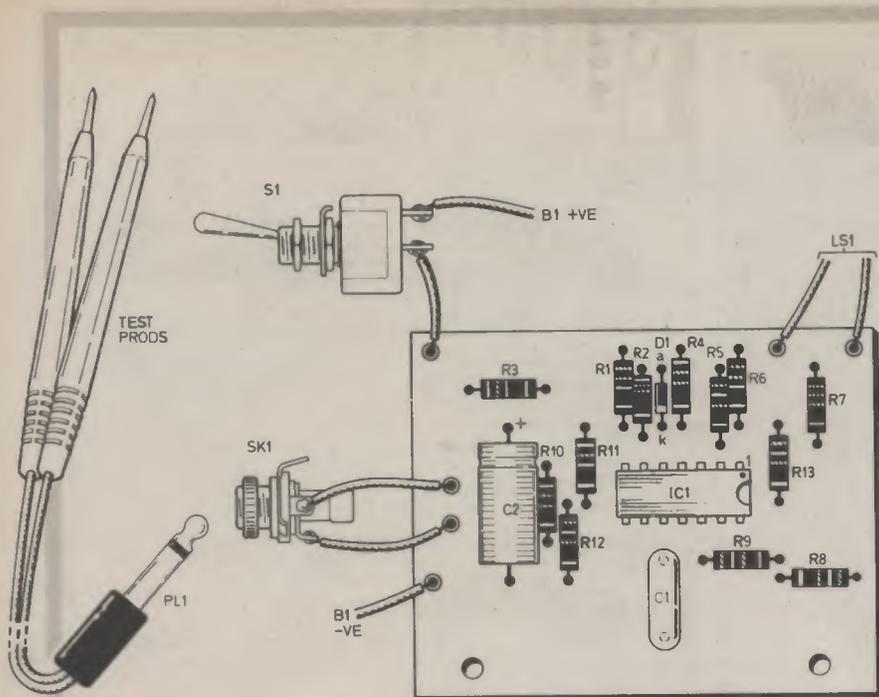
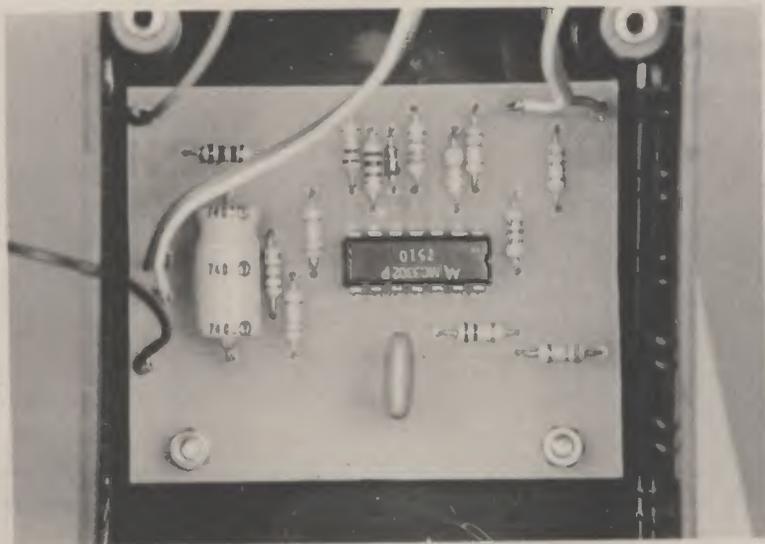


Fig. 2. The printed circuit board master, which is available from the *EE PCB Service*, Order code 8312-08. The component layout and wiring details are shown above.

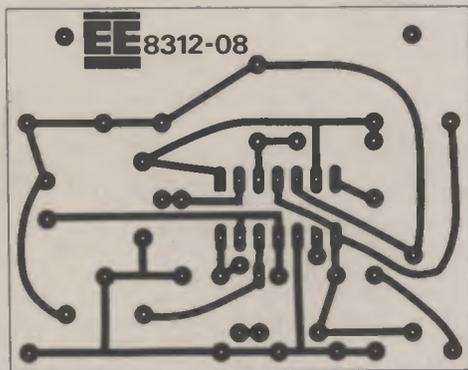

the left-hand portion of the front panel to produce a speaker grille, and as miniature speakers invariably lack any provision for screw fixing it will be necessary to glue the speaker in place behind the grille using a good quality general purpose adhesive.

The test prods connect to the unit via a 3.5mm jack or any other convenient type of socket. This is mounted on the front panel on the right-hand side, beneath the ON/OFF switch.

PRINTED CIRCUIT BOARD

The components are mounted on a single-sided printed circuit board as shown in Fig. 2 measuring 64 x 51mm. The board is constructed using the usual techniques and this should be perfectly straightforward. The board is available from the *EE PCB Service*, Order code 8312-08.

The completed board is mounted on the rear panel of the case using 6BA fixings and this leaves sufficient space for the battery on the right-hand side of the case. The power source is provided by a 9V PP3 battery and after wiring the battery clip into the circuit and completing the component interwiring, the unit is then ready for testing.

TESTING

When the unit is switched on there should be no tone or other sounds from the speaker, but with the test prods touched firmly together there should be a low frequency tone of reasonable volume. Placing a resistor of between 10 ohms and 470 ohms in value across the test prods should give the higher frequency tone, and the difference in pitch should be large enough to be readily apparent. □

PRACTICAL ELECTRONICS

DECEMBER 1983

Projects

GAS SAVER

Reduce central heating costs

ZAP GUN

Star Wars type "Directed Energy Weapon" for fun only with excellent sound effects

Feature

DINORWIG

We investigate the Welsh pumped storage power station.

Plus

Microbus, Semiconductor Circuits, Patents, Spacewatch, Bazaar etc. etc.

ON SALE NOW

TWO FABULOUS OFFERS FROM

ALCON

SUPER 20
20k Ω /V a.c. & d.c.

A SUPER PROTECTED UNIVERSAL MULTIMETER

Undestructible, with automatic protection on all ranges but 10A.

ONLY £33.50

inc. VAT, P&P, complete with carrying case, leads and instructions.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £20.00.

Accuracy: d.c. ranges and Ω 2% a.c. 3% (of f.s.d.)
39 ranges: d.c. V 100mV, 1-0V, 3-0V, 10V, 30V, 100V, 300V, 1000V.
d.c. I 50 μ A, 100 μ A, 300 μ A, 1.0mA, 3mA, 10mA, 30mA, 100mA, 1A, 10A
a.c. V 10V, 30V, 100V, 300V, 1000V.
a.c. I 3mA, 10mA, 30mA, 100mA, 1.0A, 10A.
 Ω 0-5.0k Ω , 0-50k Ω , 0-500k Ω , 5M Ω , 50M Ω .
dB from -10 to +61 in 5 ranges.

Dimensions: 105 x 130 x 40mm.



SUPER TESTER 50 50k Ω V a.c. and d.c.



A 39 ranges fool-proof multimeter with protective diodes, quick acting 1.25A fuse and resettable cut-out.

PROFESSIONAL SOLUTION TO GENERAL MEASUREMENT PROBLEMS

ONLY £36.30

incl. VAT, P&P, complete with carrying case, leads and instructions. Goods normally by return of post.

The best instrument for the workshop, school, toolbox, TV shop and anywhere accurate measurement is needed quickly and simply.

Accuracy: d.c. ranges and Ω 2% a.c. 3% (off.s.d.)
39 ranges: d.c. V 150mV, 1V, 3V, 10V, 30V, 100V, 300V, 1000V;
d.c. I 20 μ A, 100 μ A, 300 μ A, 1-0mA, 3mA, 10mA, 30mA, 100mA, 1A, 3A.
a.c. V 10V, 30V, 100V, 300V, 1000V;
a.c. I 3mA, 10mA, 30mA, 100mA, 1A, 3A.
Ohms 5k Ω , 50k Ω , 500k Ω , 5M Ω , 50M Ω .
dB from -10 to +61 in 5 ranges.

Dimensions: 105 x 130 x 40mm.

For details of these and the many other instruments in the Alcon range, including multimeters, components measuring, automotive and electronic instruments, please write or telephone:

ALCON Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

Everyday Electronics, December 1983

SECURITY

Build your own system and SAVE POUNDS!

DIGITAL ULTRASONIC DETECTOR US 5063



- 3 levels of discrimination against false alarms
 - Crystal control for greater stability
 - Adjustable range up to 25ft.
 - Built-in delays
 - 12V operation
- This advanced new module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions. The module has a built-in next delay and timed alarm period, together with a selectable entrance delay, plus many more outstanding features. This advanced new module is available at

only £13.95 + V.A.T.

ULTRASONIC MODULE US 4012



- Adjustable range from 5-25ft.
- This popular low cost ultrasonic detector is already used in a wide range of applications from intruder detectors to automatic light switches and door opening equipment. Featuring 2 LED indicators for ease of setting up, the unit represents outstanding value at

£10.95 + V.A.T.

INFRA-RED SYSTEM IR 1470



Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft, operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications, the system is available at

only £25.61 + V.A.T. Size: 80 x 50 x 35mm.

POWER SUPPLY & RELAY UNIT PS 4012

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470. Price £4.25 + V.A.T.

SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces S.P.L.'s of 110db at 2 metres. Operating from 9-15V, the module contains an inhibit facility for use in 'break to activate' circuits. Price £2.95 + V.A.T.

5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110db at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price £4.95 + V.A.T.

3-POS. KEY SWITCH 3901

Single pole, 3-pos. key switch intended for use with the CA 1250. Price £3.43 + V.A.T.

All modules are supplied with comprehensive instructions.

Units on demonstration. Shop hours 9.00-5.30 p.m. Wed. 9.00-1.00 p.m. SAE with all enquiries.

Add 15% to all prices. Add 50p post & packing to all orders. Please allow 7 days for delivery. Order by telephone or post using your credit card.

ALARM CONTROL UNIT CA 1250



- The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation, or simply controlling a single magnetic switch on the front door.
- Built-in electronic siren drives 2 loud speakers
 - Provides exit and entrance delays together with fixed alarm time
 - Battery back-up with trickle charging facility
 - Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
 - Anti-tamper and panic facility
 - Stabilised output voltage
 - 2 operating modes - full alarm/anti-tamper and panic facility
 - Screw connections for ease of installation
 - Separate relay contacts for switching external loads
 - Test loop facility

Price £19.95 + V.A.T.

SIREN & POWER SUPPLY MODULE PSL 1865



A complete siren and power supply module which is capable of providing sound levels of 110db at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 or US 4012 to form a complete alarm.

Price £9.95 + V.A.T.

HARDWARE KIT HW 1250

only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size: 200 x 180 x 70mm.

HARDWARE KIT HW 5063

only £9.95 + V.A.T.

This hardware kit provides the necessary enclosure for a complete self-contained alarm system which comprises the US 5063, PS 1865, loud speaker type 3515 and key switch 3901. Attractively styled, the unit when completed, provides an effective warning system without installation problems. Size: 200 x 180 x 70mm.

ULTRASONIC MODULE ENCLOSURE

only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.

RISCOMP LIMITED

Dept. EE6, 21 Duke Street, Princes Risborough, Bucks. HP17 0AT Princes Risborough (084 44) 6326

an astable multivibrator with a high frequency output. The output frequency is in fact set by the values of R6, R7 and C2, and is about 700Hz. The output from the timer is connected to the CP (clock pulse) input of IC2, which is a CMOS 4510 programmable up/down counter. This device is used because it has the ability to be reset to any number from 0 to 9, set on the P_0 to P_3 inputs, by a logic 1 signal to the PL (parallel load) input.

Whilst the touch pads are bridged, the input to the CE pin of IC2 is held at logic 0. This allows the output pulses from IC1 to be clocked through IC2. Pin 10 of IC2 is held at logic 1 by being connected to the 9V line via R8 causing the counter to count up. The outputs Q_0 to Q_2 are connected to the display and cause it to change so rapidly that the actual value shown is not apparent.

The outputs are also connected to IC3 which is a triple 3-input NAND gate configured so as to reset the counter by producing a logic 1 state at the PL input every time the count reaches 7. When the PL input goes to logic 1 the counter is set to the value set on the P_0 to P_3 inputs. P_0 is held at logic 1 and the other inputs are held at logic 0, so the counter is reset to 1 every time the outputs Q_0 to Q_2 are all at logic 1. This causes the counter to cycle through the numbers from one to six for as long as the touch pads are bridged.

When the user's finger is removed from the touch pads, TR1 and TR2 no longer conduct and the CE input to IC2 is pulled up to logic 1 by R2. This causes the counter gate to be disabled and the count to stop at the value it reached immediately before the finger was removed. The b.c.d. (binary coded decimal) value of this number is present on the output lines and is decoded and displayed on the chosen display system.

As soon as TR1 and TR2 stop conducting, TR3 also ceases to conduct and C1 starts to discharge through R4, but as

it is also connected to the base of TR4 through R5, this causes TR4 to continue conducting for a time dependent on the values of C1, R4 and the base current of TR4.

As long as the base-emitter voltage of TR4 exceeds about 0.7V, it conducts. This enables the counter and display circuitry to remain operative for a short period after the touch pads are released. When TR4's base-emitter voltage falls below the turn on voltage, the transistor turns off and the display fades and eventually, is switched off.

DOT DISPLAY

To operate the dot display it is necessary to decode the outputs from the counter to illuminate the required number of i.e.d.s which are arranged as shown in Fig. 2. Decoding of the b.c.d. information is accomplished by the use of two 2-input NAND gates and two diodes.

The standard packaging of the 2-input NAND gates in the CMOS 4011 i.c. provides four gates in one package. Advantage has been taken of this to use two of these gates as a buffer, thereby reducing the load on the outputs of the counter. The truth table for the display is shown in the table below.

No.	IC2 outputs			I.e.d. groups			
	Q_2	Q_1	Q_0	D6	D5, D7	D3, D9	D4, D8
1	0	0	1	on	off	off	off
2	0	1	0	off	on	off	off
3	0	1	1	on	on	off	off
4	1	0	0	off	on	on	off
5	1	0	1	on	on	on	off
6	1	1	0	off	on	on	on

The single i.e.d. (D6) mounted at the centre of the display is required to be on for the odd numbers (1, 3 and 5). Inspection of the truth table shows that this coincides with the presence of a logic 1 level on output Q_0 . This i.e.d. can

therefore be wired, through resistor R9 directly to the Q_0 output. The remaining i.e.d.s are operated as pairs in series.

When the truth table is consulted, it can be seen that i.e.d.s D3 and D9 are on only when output Q_2 is at logic 1. This pair could be connected via a suitable resistor directly to this output but as Q_2 is also used to drive other i.e.d.s they are in fact wired through the two spare gates, which are each wired as inverters. These buffer the output and reduce the load on it.

The two i.e.d.s D5 and D7 are required to be on when either output Q_1 or Q_2 are at logic 1. This could be achieved by using an OR gate but is more easily done by using the simple matrix of D1 and D2 as shown. The final pair of i.e.d.s (D4 and D8) are required to be illuminated only when both Q_1 and Q_2 are at logic 1. This is in fact the AND function which has been obtained by using a NAND gate followed by another NAND gate wired as an inverter.

The circuit diagram for the dot display is shown in Fig. 2. The only component not mentioned in this description is C4 which is merely a decoupling capacitor which should be mounted as close as possible to IC5.

NUMERIC DISPLAY

The alternative display to the traditional spot pattern is to use a 7-segment display as shown in Fig. 3. This circuit is conventional and uses CMOS 4543 decoder/driver i.c. This device enables either a common anode (as used on the prototype) or a common cathode display.

If a common cathode display is used, the p.c.b. must be modified to provide the correct connections to the display and pin 6 of IC5 must be connected to the 0V line instead of the 9V line. C5 is included as a decoupling capacitor and should be mounted as close as possible to IC5.

Fig. 2. Circuit diagram of the dot matrix display.


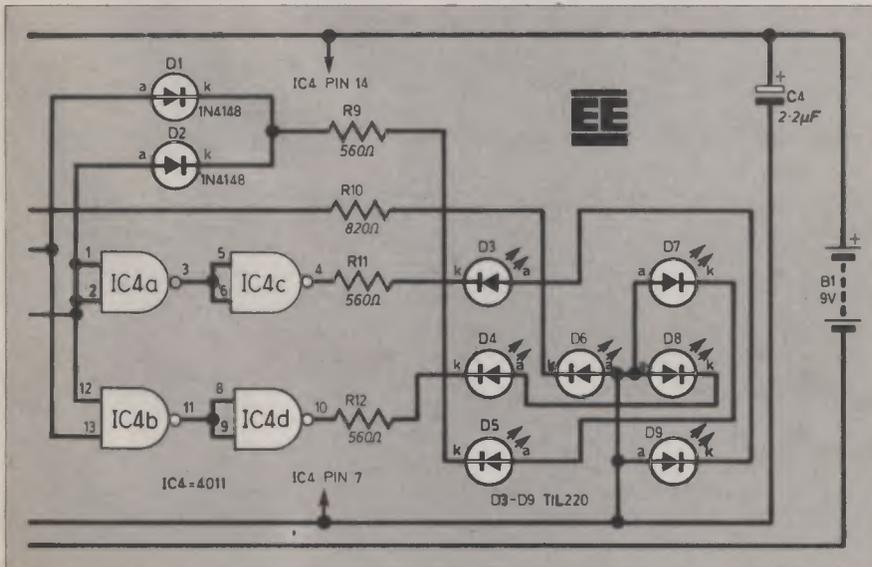


Fig. 3. The 7-segment display circuit.

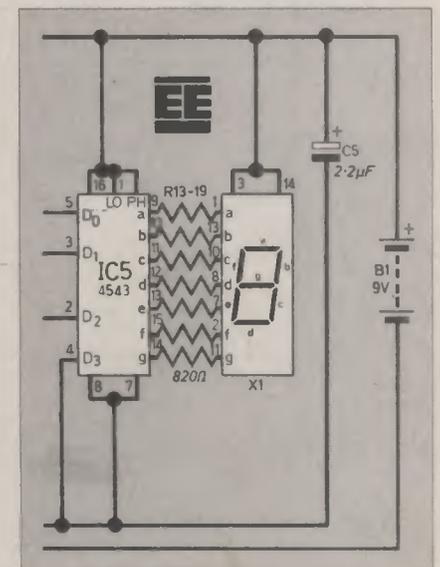

CONSTRUCTION

LOGIC BOARD

The unit has been designed to fit inside the specified case, size 85 x 56 x 35mm. Other cases can be used but care should be taken to ensure that the p.c.b.s will fit. The components for the main logic circuit are mounted onto the p.c.b. as shown in Fig. 4, and the full size track layout is also shown. This can be made using conventional techniques or ordered from the *EE PCB Service*. Care should be taken wherever the tracks are closely packed or pass between the pins of the i.c.s. When the board has been etched and drilled it should be closely inspected for broken or short circuited tracks.

The components can then be mounted as shown starting with the smallest components. C1 must be left until last as it is mounted above the adjacent resistors with its leads passing between R3 and R4. Care must also be taken to ensure correct polarity of the capacitors.

The components are very closely packed on this board and it should be thoroughly inspected before attaching the battery or installing the i.c.s.

DISPLAY BOARDS

The track design for dot display board is given in Fig. 5. It is important that the cut-out in the corner, which enables the face plate mounting screw to be fitted, is made before attempting to fit any of the components. Care must be taken to ensure the correct polarity of *all* the components as incorrect orientation will produce a strange display and some extremely interesting problems in fault diagnosis!

The display board is mounted directly under the face plate and, in order to reduce the space required, IC4 is soldered directly onto the p.c.b. and not fitted into a socket. This operation should be done with care, taking precautions to avoid the risk of static electricity destroying the device. In practice, this should not present any problems providing that a buffered type of 4011 is used.


When making this board care should be taken to ensure that the resistors do not foul the holes used for mounting the board to the face plate.

7-SEGMENT DISPLAY

The 7-segment display board is constructed using the track diagram shown in Fig. 6. As with the dot display, the driver/decoder, IC5, is soldered directly to the p.c.b. and the same precautions as detailed earlier should be taken to avoid damage.

In common with the other display board, there should be no major problems but the cut-outs should be made before mounting any of the components.

Fig. 4. Printed circuit board component layout and track pattern for the control logic section.

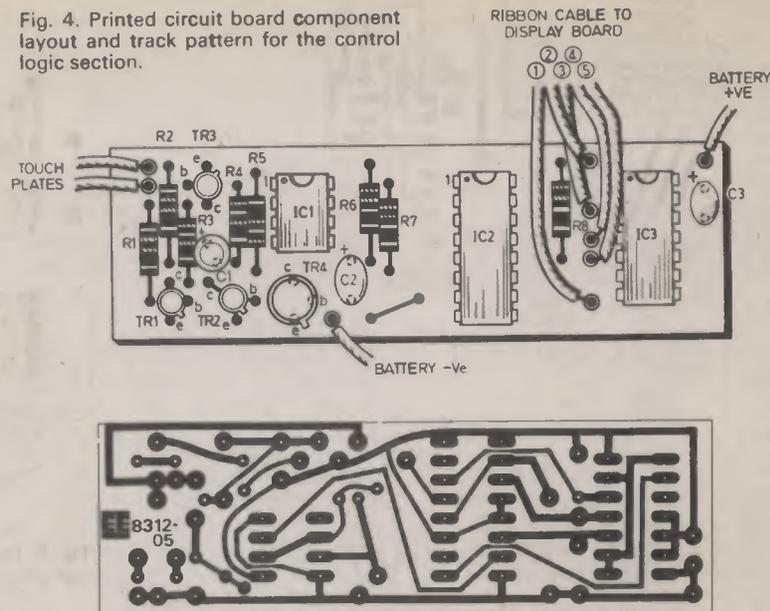

COMPONENTS

CONTROL LOGIC

Resistors

R1,3	1M Ω (2 off)
R2,6,8	10k Ω (3 off)
R4	2.7M Ω
R5	3.9k Ω
R7	1 Ω
All $\frac{1}{4}$ W carbon film $\pm 5\%$	

Capacitors

C1	100 μ F 10V miniature elect.
C2	0.1 μ F 10V tantalum bead
C3	2.2 μ F 10V tantalum bead

Semiconductors

TR1,2	BC107 npn silicon (2 off)
TR3	BC479 pnp silicon
TR4	BFY51 npn silicon
IC1	7555 CMOS timer
IC2	4510B CMOS presettable up/down counter
IC3	4023B CMOS triple 3-Input NAND gate

Miscellaneous

Printed circuit board: single-sided, size 80 x 20mm, *EE PCB Service*, Order code 8312-05; moulded plastic case with internal guide slots and aluminium lid size 85 x 56 x 35mm; material for face plate size 85 x 56mm (see text); touch pads; 16-pin d.i.l. holder; 14-pin d.i.l. holder; 8-pin d.i.l. holder; battery clip; self-tapping screws; 6BA screws and nuts; ribbon cable (7-way x 150mm).

DOT MATRIX DISPLAY

Resistors

R9,11,12	560 Ω (3 off)
R10	820 Ω

Capacitor

C4	2.2 μ F 10V tantalum bead
----	-------------------------------

Semiconductors

D1,2	1N4148 silicon (2 off)
D3-9	TIL220 0.2In red l.e.d. (7 off)
IC4	4011B CMOS quad 2-input NAND gate

Miscellaneous

B1 9V PP3
Printed circuit board: single-sided, size 55 x 35mm, *EE PCB Service*, Order code 8312-06.

7-SEGMENT DISPLAY

Resistors

R13-19	820 Ω (7 off)
--------	----------------------

Capacitor

C5	2.2 μ F 10V tantalum bead
----	-------------------------------

Semiconductor

X1	0.3in common anode 7-segment display
IC5	4543B CMOS b.c.d. to 7-segment decoder

Miscellaneous

B1 9V PP3
Printed circuit board: single-sided, size 73 x 32mm, *EE PCB Service*, Order code 8312-07.

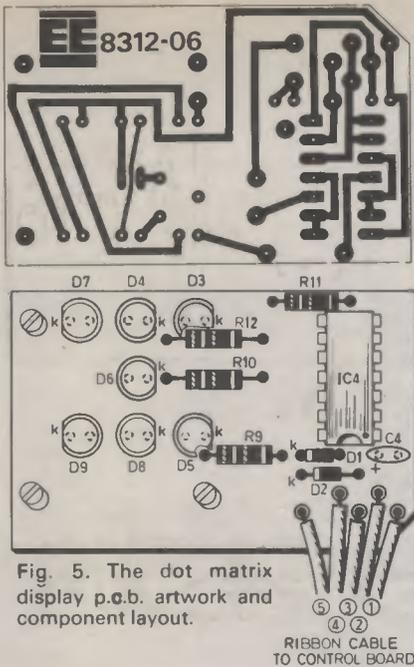


Fig. 5. The dot matrix display p.c.b. artwork and component layout.

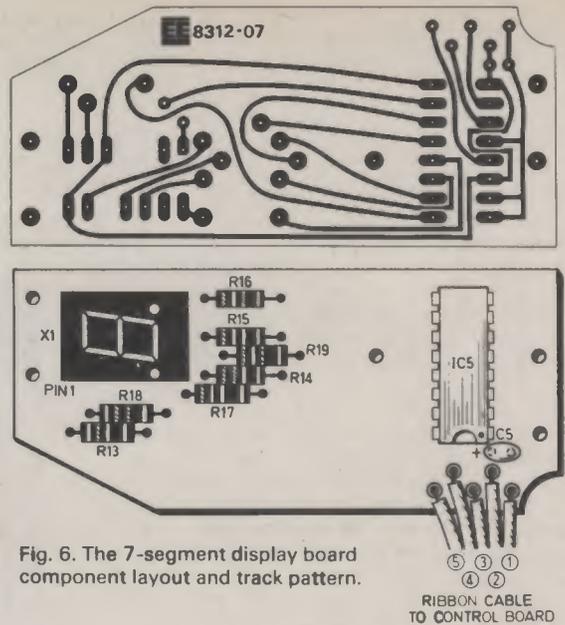


Fig. 6. The 7-segment display board component layout and track pattern.

TESTING

After both the main logic board and the display board have been constructed and checked, they should be connected together and tested. It is advisable to use ribbon cable to join the main board and display board together since this will reduce the problems of the "spaghetti" like tangle that would otherwise result every time the die is opened.

To check the boards for correct operation, the battery should be carefully inserted into its clips without either of the p.c.b.s being touched. If all is well, there should be no sign of life on the display. The touch pads should then be touched with the finger so that a current flows to the base of TR1.


The display should immediately light, showing either the figure "eight" on the numeric display or all seven dots on the matrix display. In the latter case, i.e.d.s D4 and D8 will appear to be at low brightness. This is perfectly normal and results from the fact that as the device cycles rapidly through the numbers from one to six, these diodes are only lit for one-sixth of the cycle period.

When the contact to the touch pads is released, the display should stop cycling and show a number between one and six for a short while before fading away. The test should be repeated several times in order to check that the die is not "loaded".

If it is suspected that the die does not

give a random result but is biased to a particular number or set of numbers, then the operation of the number generator can be checked by temporarily connecting a 100µF capacitor across C1 and letting the die pulse slowly through the sequence from one to six. The first few numbers displayed may be random or out of the required range but after a maximum of four changes, the die should reset and start to go through the repetitive sequence from one to six.

If the time for which the die remains illuminated after the touch pads are released is incorrect, this can be adjusted by altering the value of C1. Increasing the value increases the delay time and reducing it will reduce the delay time.

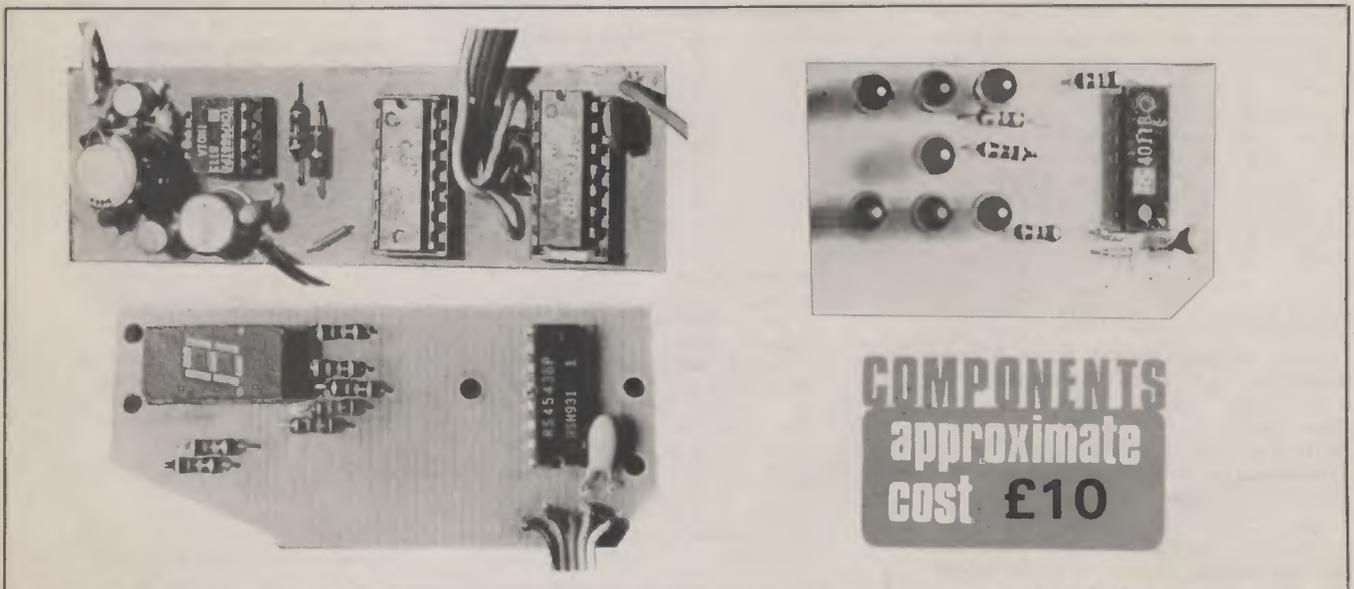

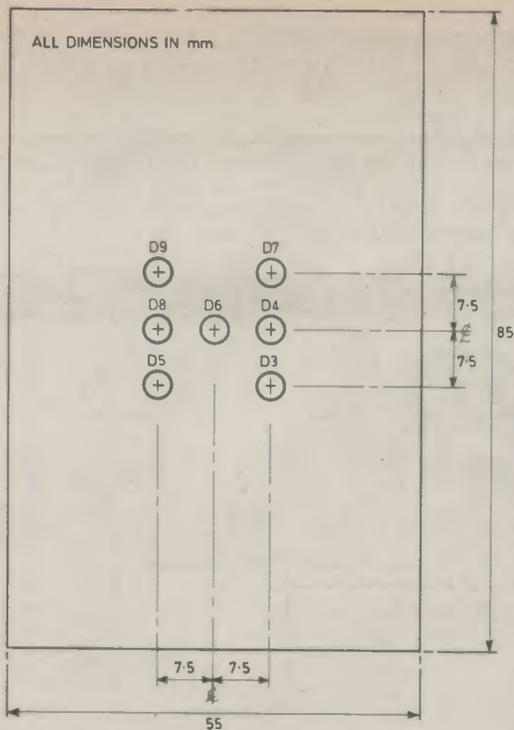


Fig. 7. The face plate drilling details. The mounting holes are positioned using the p.c.b. as a template.

FACE PLATE

The face plate of the unit must be made of an insulating material and not the aluminium panel supplied with the case. If it is desired to make the touch plates as printed circuit tracks, this can be done by the same method as that used for making p.c.b.s. Alternatively, commercially available touch pads can be screwed through suitable material. In each case, it is important to ensure that the pads are placed at least 2mm apart and are not fouled by the display or mounting screws.

It is important to note that the face plate fits on top of the case and is not inset into the recess in the case, as is the aluminium plate supplied. The face plate

Face plate of the dot matrix display version made from a piece of p.c.b. material with two tracks forming the touch switch.


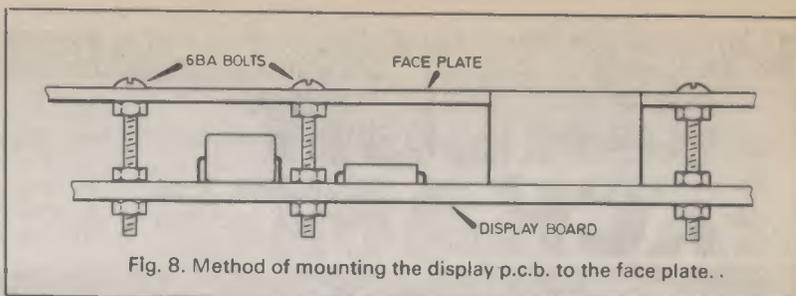
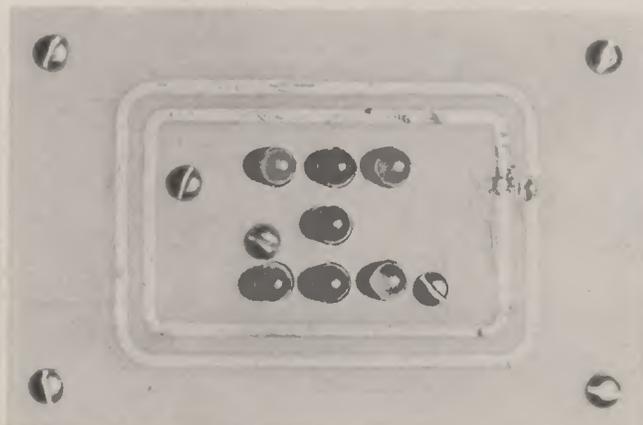


Fig. 8. Method of mounting the display p.c.b. to the face plate.

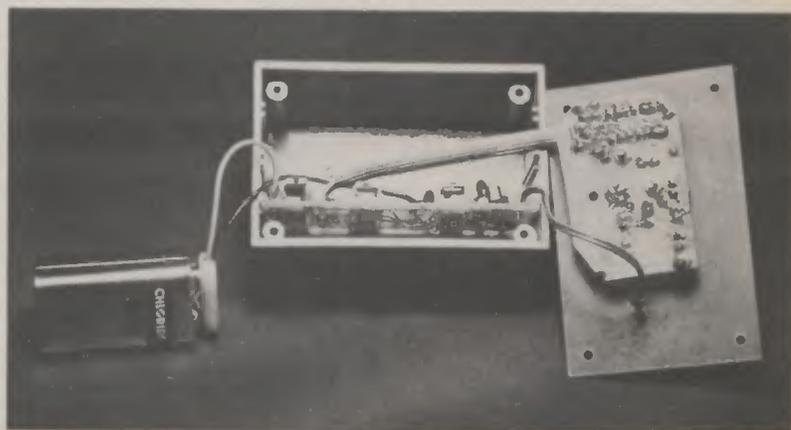

The prototype Touch Operated Die with face plate removed to show the assembly using the dot matrix display board.

must be cut to the same size as the outside of the case and appropriate mounting holes drilled through it to line up with the pillars moulded into the inside of the case.

The appropriate display board is fixed to the underside of the display panel so that the l.e.d.s protrude through the face plate or the 7-segment display fits flush into a cut-out in the face plate.


The mounting holes are then marked and drilled ready for mounting the board as shown in Fig. 7. If the 7-segment display is used, the shape should be marked out on the face plate and then carefully drilled and filed out until a good fit is obtained. The positions of the mounting holes can then be determined.

With both types of display, it is impor-

tant that a dry run is conducted with the boards to ensure that they will fit into the case, leaving room for the battery, in the marked positions before committing the face plate to the attention of the cutting tools.

The face plate and display board are fixed together by using three screws, each fitted with three nuts, as shown in Fig. 8. After the holes have been drilled, the boards should be given a final check before being assembled. The control logic p.c.b. should then be fitted into place in the grooves moulded in the main case. The battery is then connected and placed in the case and the face plate fixed to the case using longer self-tapping screws than those supplied with the case. □

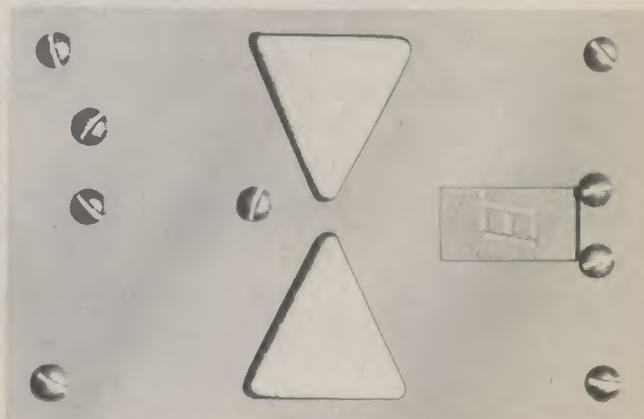Face plate of the 7-segment numeric display die with the touch switch made from commercially available touch plates.



CIRCUIT EXCHANGE

This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised. Payment is made for all circuits published in this feature. Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.


CAR LIGHTS ALARM

MY CAR is a Ford Falcon with a negative earth and as such I thought your *Car Lights Alert* (October 1982) circuit would work. The main trouble I found was with the courtesy lights. As I considered the circuit and logic behind the circuit too good not to use, I re-designed the circuit still using the same logic. I feel other readers may have had the same trouble as myself so I am offering the circuit I "designed" for my car's existing wiring.

The pillar switches are positioned between the lamp and positive. I have taken out the transistor and used the circuit, so that with the switches open, the reset of IC1 (pin 4) is held low through the lamp filament.

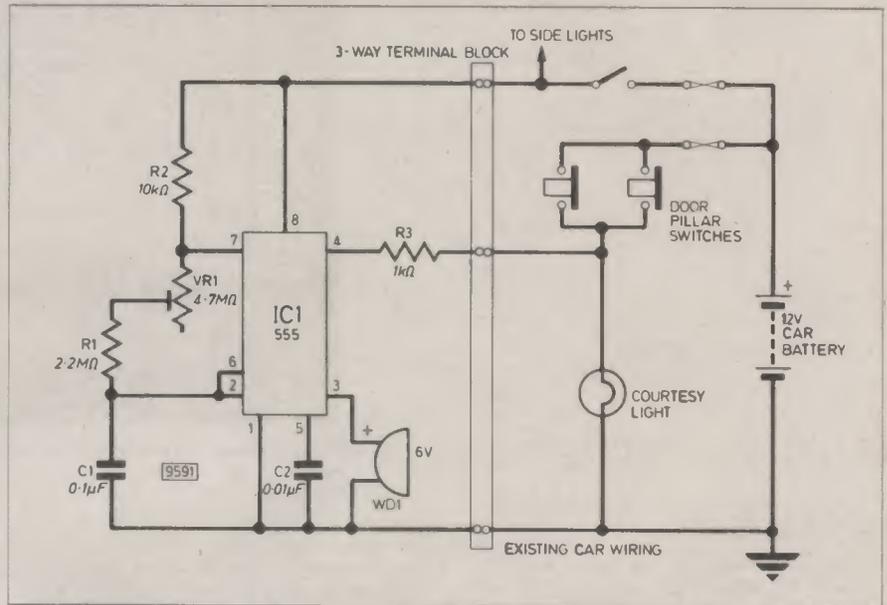E. Westerman, Victoria, Australia.

Editorial note: This circuit will not work with cars having earthed door pillar switches.



TRAFFIC LIGHT SIMULATOR

THIS circuit simulates the sequence of lights at a typical cross-roads. The circuit is based upon a 16-bit counter which provides the inputs to the combinational logic gates.

The clock for the 16-bit counter is derived from a 555 timer which is connected as an astable multivibrator.

The components around the 555 are chosen so that its period of oscillation is approximately five seconds, meaning that the lights change at a realistic rate.


The 16-bit counter is based on four JK flip-flops connected in such a way that each divides the clock frequency by two.

The outputs of the 16-bit counter are used for the inputs for the logic gates

which have been arranged to generate the necessary sequence of lights.

Since the logic gates are required to drive i.e.d.s, each output needs buffering. All six buffer stages are identical, except of course for the colour of the i.e.d. used. Any i.e.d. can be used but for realism it is best to use red, orange and green.

W. Barlow, Basildon, Essex.

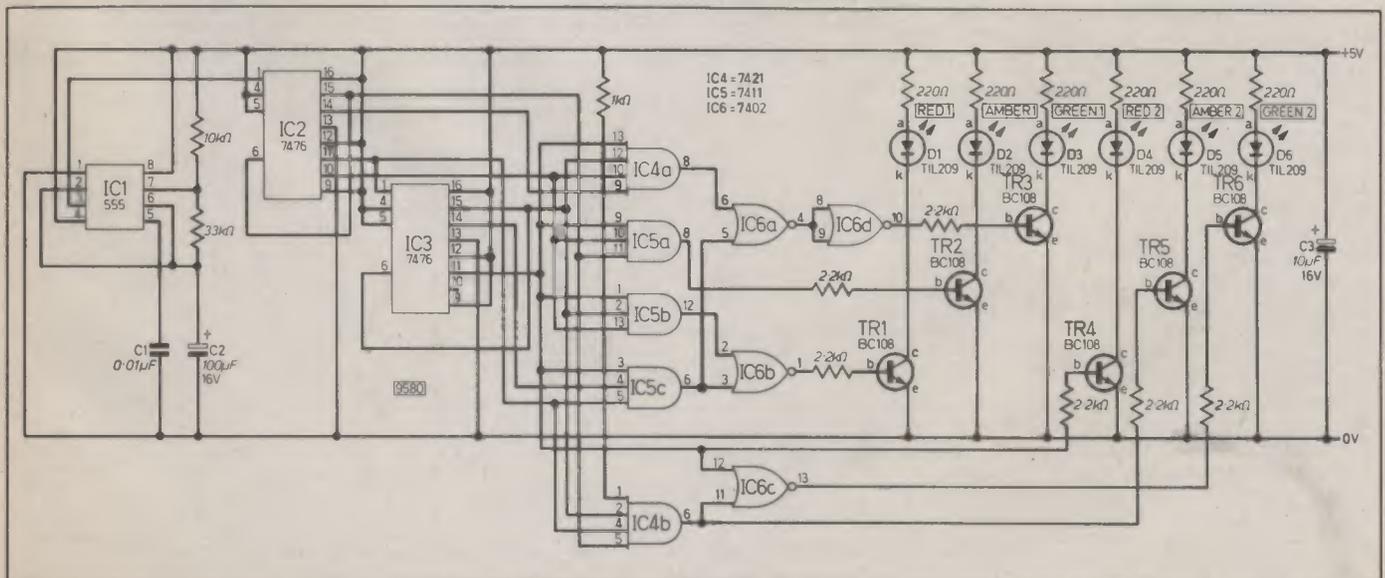

NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW

FUNCTION GENERATOR

A VERSATILE function generator providing sine, square, triangle, ramp and pulse waveforms over the frequency range 0.1Hz to 2MHz in seven decade ranges has just been marketed by House of Instruments.


Output is continuously variable to 20V p-p from and into 50 ohms, with switchable d.c.

offset available to +10V. A variable duty cycle and symmetry control enables adjustment of main, square and TTL outputs.

Other facilities include: external sweep over a 1000:1 frequency range; polarity invert and sync output.

The IFG422 Function Generator is guaranteed for one year and costs £195, excluding VAT and carriage.

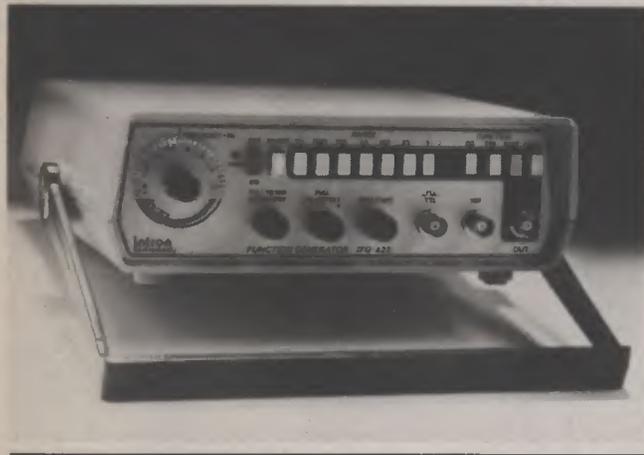House of Instruments,
Dept EE, Clifton Chambers,
62 High Street, Saffron Walden,
Essex CB10 1EE.



EPROM ERASERS



THREE new low-cost EPROM Erasers have been specifically designed by J. P. Designs, for use in the laboratory, classroom and by the hobbyist. All three versions use the same simple drawer construction which allows easy access.

The drawer section, with antistatic foam, holds either 20 EPROMs (Model 82) or 40 EPROMs (models 84 and 84T).

A timer version, model 84T, is available to preset exposure times and safeguard against "cooking" EPROMs. The timer gives intervals of 10 and 30 minutes. An l.e.d. shows when the unit is erasing.

The price for the basic unit, Model 82, is £31.25; Model 84, £44.95; and Model 84T, with timer, £54.95.

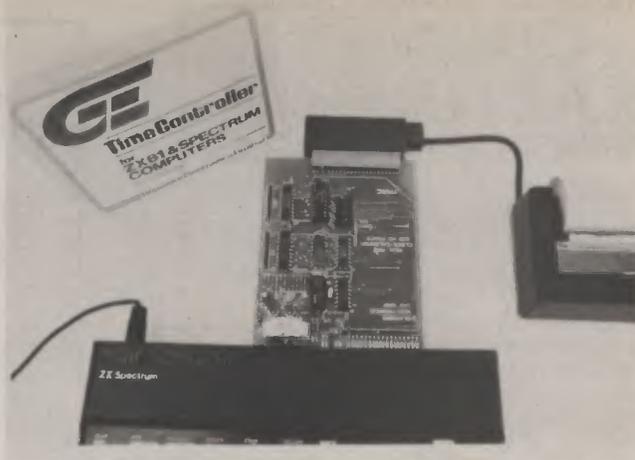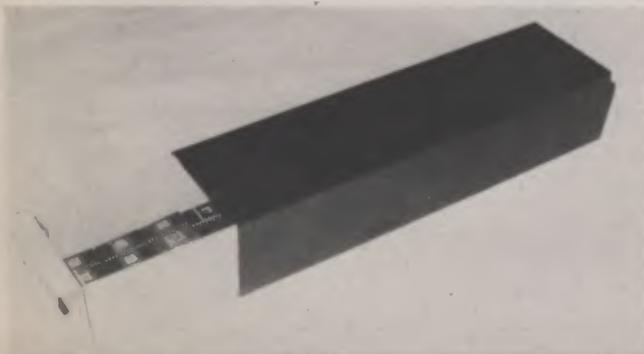J. P. Designs,
Dept EE, Oyster Row,
Cambridge CB5 8LJ.



TIME CONTROLLER

A TIME CONTROLLER for the ZX81 and Spectrum computers is now being marketed by Glanmire Electronics.

The timer consists of a battery back-up real time clock with eight programmable inputs and eight programmable outputs. It provides the computer with the month, day, date, hours, minutes and seconds.

The controller has its own built-in program, in PROM

memory. Only a single instruction in the users program is required to read or write the time or date.

Applications include: diary with alarm; home control; burglar alarm; sound effects; games and process control. The recommended retail prices for the Time Controller for ZX81 and Spectrum are £34.50 and £38.50 respectively.

Glanmire Electronics Ltd.,
Dept EE, Westley House,
Trinity Avenue, Bush Hill Park,
Enfield EN1 1PH.



DIGITAL FREQUENCY METER

THE launch of a new range of professional quality low-cost test instruments designed and manufactured in the UK is announced by Black Star.

The first products to be released come under the Meteor series and consist of three Digital Frequency Counters with a measurement range up to 100MHz, 600MHz and 1GHz.

The Meteor 600 is the first meter available and has a typical frequency range of 2Hz to 700MHz; sensitivity of about 25mV at 600MHz and resolution down to 0.1Hz. The counter also features eight 7-seg l.e.d. displays, three gate times, two inputs, trigger level control and an integral low-pass filter.

Black Star Ltd.,
Dept EE, 9A Crown Street,
St. Ives, Huntingdon,
Cambs PE17 4EB.

EVERYDAY ELECTRONICS and computer PROJECTS

VOLUME 12 INDEX

JANUARY 1983 TO DECEMBER 1983

Pages	Issue	Pages	Issue
1-64	January	401-472	July
65-128	February	473-544	August
129-192	March	545-616	September
193-256	April	617-688	October
257-328	May	689-760	November
329-400	June	781-852	December

CONSTRUCTIONAL PROJECTS

ACORN ATOM EPROM PROGRAMMER	113, 178	DOUBLE DICE <i>by D. W. Crabtree</i>	50
ADC, 4-CHANNEL HIGH SPEED	816	DUAL POWER SUPPLY	159, 518
ALARM, CARAVAN FRIDGE	336	EGG TIMER, NOVELTY	212, 826
ALARM, CAR INTRUDER	519	ELECTRONIC DIE <i>by G. P. Hawksford</i>	500
ALARMS FOR PUSHBIKE OR MOTORBIKE <i>by J. Duffy</i>	74	ELECTRONIC PENDULUM <i>by M. Cragg</i>	670
AMPLIFIER, DIGI ALARM WRISTWATCH	430	ENVELOPE SHAPER FOR BASS GUITAR <i>by A. Niemiro</i>	378
AMPLIFIER, GUITAR HEADPHONE	282	ENVIRONMENTAL DATA RECORDER <i>by M. Lawrie and L. Wilkinson</i>	807
AMPLIFIER, PERSONAL LS	10	EPROM PROGRAMMER <i>by B. W. Terrell and J. W. Terrell</i>	338
AMPLIFIER, ZX SPECTRUM	202	EPROM PROGRAMMER FOR THE ACORN ATOM <i>by D. C. Grindrod</i>	113, 178
APPLE II REAL-TIME CLOCK	266, 461, 518	EPROM PROGRAMMER, GENIE	338, 518
A to D CONVERTER FOR PET COMPUTER <i>by J. Adlington, L. Chapman and L. Monk</i>	30	EPROM PROGRAMMER, TRS-80	338, 518
A to D CONVERTER FOR RM380Z COMPUTER <i>by A. A. Chanerley</i>	559	EXPANDED ADD-ON KEYBOARD FOR THE ZX81	170, 234
AUTOMATIC GREENHOUSE WATERING SYSTEM <i>by J. Lewis</i>	424	FLANGER SOUND EFFECT <i>by R. A. Penfold</i>	221
BASS GUITAR, ENVELOPE SHAPER	378	FLASH GUN/CAMERA TRIGGER	726
BBC MICRO REAL-TIME CLOCK	266	FUNCTION GENERATOR	205
BBC MICRO SPEECH SYNTHESISER	698, 800	GAUSS METER, DIGITAL	738
BBC MICRO STORAGE 'SCOPE INTERFACE	482	GENIE EPROM PROGRAMMER	338, 518
BEEHIVE TEMPERATURE METER <i>by D. Allewell, A. Green, J. Green and A. Smith</i>	82	GREENHOUSE WATERING SYSTEM	424
BINARY BANDIT GAME <i>by F. G. Rayer</i>	452	GUITAR HEADPHONE AMPLIFIER	282
BZZ OFF! <i>by T. R. de Vaux-Balbirnie</i>	154	GUITAR TONE CONTROLLER, TRI BOOST	432
CAMERA/FLASH GUN TRIGGER	726	HIGH POWER DAC DRIVER BOARD	655
CANDLE, MAGIC	798	HIGH POWER INTERFACE BOARD	493
CARAVAN FRIDGE ALARM <i>by T. R. de Vaux-Balbirnie</i>	366	HIGH SPEED ANALOGUE-TO-DIGITAL CONVERTER	582
CARAVAN POWER SUPPLY <i>by T. R. de Vaux-Balbirnie</i>	362	HOME INTERCOM <i>by R. A. Penfold</i>	626
CAR INTRUDER ALARM <i>by P. Barber</i>	519, 644	HOME SYSTEMS MONITOR <i>by H. G. Field</i>	508
CAR ON/OFF TOUCH SWITCH <i>by P. Barber</i>	744	IMMERSION HEATER TELL-TALE <i>by T. R. de Vaux-Balbirnie</i>	630
CAR RADIO BOOSTER <i>by C. Lare</i>	242	INTERCOM, MULTI-STATION	138
CAR THERMOMETER <i>by M. Plant</i>	150	LABORATORY AMPLIFIER	291
CHILDREN'S DISCO LIGHTS <i>by T. R. de Vaux-Balbirnie</i>	796	LIGHTS, CHILDREN'S DISCO	796
COMPUTER A to D CONVERTER FOR PET	30	LOCK, PUSHBUTTON COMBINATION	352
COMPUTER A to D CONVERTER FOR RM380Z	559	LONG RANGE CAMERA/FLASH GUN TRIGGER <i>by R. A. Penfold</i>	726
CONTROLLER, MODEL TRAIN	306	MAGIC CANDLE <i>by T. R. de Vaux-Balbirnie</i>	798
CONTINUITY TESTER <i>by R. A. Penfold</i>	830	MAINS POWER CONTROLLER, 1kW	526
DATA RECORDER, ENVIRONMENTAL	807	METER, DIGITAL GAUSS	738
DETECTOR, MOISTURE	314	MODEL CAR "PETROL TANK" <i>by A. P. Donleavy</i>	640
DIE, TOUCH OPERATED	834	MODEL TRAIN CONTROLLER <i>by R. A. Penfold</i>	306
DIGI ALARM WRISTWATCH AMPLIFIER <i>by D. E. Smith</i>	430	MOISTURE DETECTOR <i>by N. Kay</i>	314
DIGITAL GAUSS METER <i>by R. Rowe</i>	738		
DIGITAL TO ANALOGUE BOARD	652		
DISCO LIGHTS, CHILDREN'S	796		
DISTRESS BEACON <i>by P. E. Hopkins</i>	566		

MOTORBIKE ALARM	74	TEMPERATURE METER, BEEHIVE	82
MULTIMOD <i>by J. D. Rogers</i>	704, 800	TEMPERATURE SENSOR <i>by J. Adlington, L. Chapman and J. Monk</i>	278
MULTI-STATION INTERCOM <i>by T. Rufe</i>	138	TEMPERATURE TRANSDUCER AMPLIFIER <i>by A. A. Chanerley</i>	646
MW PERSONAL RADIO	286	TEST GEAR 83 <i>by J. R. W. Barnes</i>	159, 205, 291, 370, 456
NEON NIGHTLIGHT <i>by D. A. Corder</i>	232	1—Dual Power Supply	159, 518
NOVEL EGG TIMER <i>by I. Hickman</i>	826	2—Function Generator	205
NOVELTY EGG TIMER <i>by L. S. Cook</i>	212	3—Laboratory Amplifier	291
OPTO REPEATER <i>by A. R. Winstanley</i>	42	4—Transistor Tester	370, 518
PEDESTRIAN CROSSING SIMULATION BOARD	496	5—Pulse Generator	456
PENDULUM, ELECTRONIC	670	THERMOMETER, CAR	150
PERSONAL LS AMPLIFIER <i>by L. Cohen</i>	10	TIMER, EGG	212, 826
PET COMPUTER, A to D CONVERTER FOR	30	TIMER, SHORT INTERVAL	90
PET COMPUTER, TEMPERATURE SENSOR	278	TOUCH OPERATED DIE <i>by C. J. Bowes</i>	834
POWER SUPPLY, CARAVAN	362	TOUCH SWITCH, CAR ON/OFF	744
POWER SUPPLY DUAL	159	TRAFFIC LIGHT SIMULATOR <i>by N. P. Naughton</i>	602
PULSE GENERATOR	456	TRAIN CONTROLLER, MODEL	306
PUSHBIKE ALARM	74	TRANSISTOR TESTER	370, 518
PUSHBUTTON COMBINATION LOCK <i>by J. Hadley</i>	352	TRI BOOST GUITAR TONE CONTROLLER <i>by J. D. Rogers</i>	432
RADIO BOOSTER, CAR	242	TRS-80 EPROM PROGRAMMER	338, 518
RADIO, MW PERSONAL	286	TRS-80 TWIN CASSETTE INTERFACE <i>by S. Rainey</i>	790
REAL-TIME CLOCK <i>by O. N. Bishop</i>	266	TTL/POWER INTERFACE FOR STEPPER MOTOR	718
SHORT INTERVAL TIMER <i>by A. P. Donleavy</i>	90	USER PORT CONTROL BOARD	417
SHORT WAVE RADIO <i>by R. A. Penfold</i>	664	USER PORT INPUT/OUTPUT BOARD	414
SIGNAL CONDITIONING AMPLIFIER	586	VIC 20 TEMPERATURE SENSOR	278
SOUND EFFECT, FLANGER	221	VOLTAGE DUALISER <i>by L. S. Cook</i>	606
SOUND EFFECTS	704, 800	ZX SPECTRUM AMPLIFIER <i>by V. Terrell</i>	202
SPEECH PROCESSOR <i>by R. A. Penfold</i>	106	ZX81, EXPANDED ADD-ON KEYBOARD FOR	170
SPEECH SYNTHESISER FOR THE BBC MICRO <i>by R. A. Penfold</i>	698, 800	ZX81 SPEED COMPUTING SYSTEM <i>by D. Wilkes and A. Williams</i>	78
STEPPER MOTOR MANUAL CONTROLLER	720	4-CHANNEL HIGH SPEED ADC	816
STORAGE 'SCOPE' INTERFACE FOR BBC MICRO <i>by R. A. Penfold</i>	554	1kW MAINS POWER CONTROLLER <i>by T. R. de Vaux-Balbirnie</i>	526
STYLUS ORGAN <i>by R. A. Penfold</i>	554	8+8V POWER SUPPLY	606
SWITCH, CAR ON/OFF TOUCH	744		

SPECIAL SERIES

CIRCUIT EXCHANGE	115, 118, 173, 216, 232, 237, 238, 241, 304, 309, 317, 358, 384, 423, 435, 439, 450, 462, 530, 532, 578, 611, 663, 678, 748, 800, 839, 840	Seat Belt Reminder	533
Alarm Circuit	611	Shaky Hand Game	450
Auto Water Feeder	578	Simple Reaction Meter	358
Bleeper Circuit	611	Speed Chess and Draughts Timer	173
Burglar Alarm	304	Stabiliser for use with low cost Battery Eliminators	384
Car Circuit Tester	435	Strength Meter	384
Car Light Alert	530	Tampering Detector	237
Car Lights Alarm	839	Telephone Ring Simulator	840
Car Overheating Indicator	241	Temperature Sensor	800
Car Voltage Monitor	462	Three-way Snap Indicator	241
CB Rig Light	317	Tilt Alarm	238
Chirping Bird	115	Traffic Light Simulator	839
Combination Lock	317, 532	Trailer Flashing Direction Indicator Switching Unit	533
Converting a Multimeter to a 'VU' Meter	384	Two-way Doorbell	423
Digital Darkness/Light Measurer	216	Utility Audio Amplifier—Doorbell-Latch Alarm	532
Disco Traffic Lights	118	V.H.F. Aerial Preamplifier	530
Door Alarm with L.E.D. Indicator	241	Variable Sequential Switch	304
Electronic Dice Generator	450	Warbling Oscillator	232
Electronic House Register	663	COMPUTER AIDED EXPERIMENTS <i>by A. A. Chanerley</i>	600, 674, 732
Electronic Key	317	1: Investigation of diffraction patterns	600
Electronic Switch/Doorbell Alarm	309	2: Naphthalene cooling characteristic	674
Electronic Timer	678	3: Transistor Voltage-Transfer Characteristic	732
FET Darkroom Timer	663	ELECTRONICS AND THE ELECTRON <i>by J. B. Dance</i>	289, 356, 428, 504, 576
Fire Alarm—Electronic Temperature Controller	840	1: Introducing the Electron	289
Flashing Light Bleeping Siren	439	2: Conduction in Various Materials	356
Four-Digit Combination Lock	800	3: Conduction in Various Materials (cont.)	428
Fuzz Box	317	4: Conduction in Semiconductors	504
Jogger's Pacemaker	118	5: Doped Semiconductor Materials	576
Model Traffic Lights	439	FOR YOUR ENTERTAINMENT <i>by Barry Fox</i>	46, 97, 158, 227, 285, 361, 440, 507, 579, 649, 736
Op-Amp Tester	462	Cordless Call, Almost Legal	46
Outside Light Switch	678	Mysteries of hi fi, Shopping in Tokyo	97
Probeless Continuity Tester	358	Why Markets Are Lost, Buying a Home Computer	158
Programmable Divider	450		
Quick Polarity Tester	173		
Rear-Light Failure Indicator	173		

Cellular Radio, Recording with Videodiscs	227
Sounds of Video, Calculating Time	285
Computer Forecast, Video In a Spin, Hospital Radio	361
Wrong Line, Japanese Way, Computer Tip	440
Surround-Sound Video, Stereo Film	507
Video Facts, Teleprompting	579
Technology, Digital War	649
Computer Record, Radio Litter	736
Confusing Law, Flat-screen TV, Hot Memory	824

INTRODUCING ELECTRONICS <i>by George Hylton</i>	24, 86, 146, 302
4: Amplifiers	24
5: Radio Receivers	86
6: Digital Electronics	146
7: Summing Up	302

MICROCOMPUTER INTERFACING TECHNIQUES	
<i>by J. Adams and G. M. Feather</i>	410, 490, 580, 650, 716
1: The Microprocessor and User Ports	410
2: Experiments using the User Port Control Board	490
3: Analogue-to-Digital Conversion	580
4: Digital-to-Analogue Conversion	650
5: Stepper Motor Control	716
6: 4-Channel High Speed ADC	814

SPECIAL REPORTS	174, 276, 350, 488, 598, 724
Acorn Atom User's Report <i>by T. J. Johnson</i>	174

FX Computer Kit <i>by R. A. Hooper</i>	276
In/Out Port Board for ZX81 <i>by B. W. Terrell</i>	488
RML380Z Microcomputer <i>by A. A. Chanerley</i>	724
Sinclair ZX Spectrum <i>by J. W. Terrell</i>	350
ZX81 Personal Computer <i>by G. P. Hodgson</i>	598

SQUARE ONE	54, 116, 246, 318, 448, 531, 610, 668, 750
Light Emitting Diodes	54
Earphones	116
Electrolytic Capacitors	246
Capacitors	318
Diodes	448
Polarity Conscious Components	531
Circuit Symbols	610
Switches	668
Audio Amplifier Integrated Circuits	750

TEACH-IN 84 <i>by G. Hylton</i>	634, 710, 802
1: A.C., D.C. and Signals	634
2: Batteries and Resistors	710
3: Potentiometers & Transistors	802

THE ELECTRONICS OF INFORMATION TECHNOLOGY	
<i>by T. Ivall</i>	38, 100, 166, 218
3: Transmission Methods	38
4: Time Division Multiplex (t.d.m.)	100
5: Information Units	166
6: Information Storage	218

GENERAL FEATURES

ACORN ATOM USER'S REPORT <i>by T. J. Johnson</i>	174
--	-----

BOOK REVIEWS	53, 81, 110, 238, 288, 376, 454, 604, 608, 648, 741, 795, 828
--------------	---

BRIGHT IDEAS	
Circuit Board Drill	23

COUNTER INTELLIGENCE <i>by Paul Young</i>	29, 89, 165, 238, 296, 376, 461, 518, 564, 633, 714, 812
---	--

CYCLIC REDUNDANCY CHECK for the ACORN ATOM	
<i>by R. A. Hall</i>	422, 518

EDITORIAL	9, 73, 137, 201, 265, 337, 409, 481, 553, 625, 697, 789
-----------	---

ELECTRONIC HOBBIES FAIR	94
-------------------------	----

EVERYDAY NEWS	36, 104, 176, 228, 298, 442, 516, 590, 660, 734, 822
---------------	--

FREE TRANSISTORS	284
------------------	-----

JACK PLUG & FAMILY <i>by Doug Baker</i>	29, 77, 225, 296, 348
---	-----------------------

LOGIC SYMBOLS	349
---------------	-----

MEASUREMENT OF AUDIO AMPLIFIER PARAMETERS	
<i>by A. E. Rule</i>	436

NEW PRODUCTS	300, 385, 447, 534, 609, 676, 749, 841
--------------	--

PLEASE TAKE NOTE	226, 461, 518, 709, 800
Analogue to Digital Converter Board	709
Apple II Real Time Clock	461, 518
Beat the Relay	226
Car Intruder Alarm	644
Cyclic Redundancy Check for the Acorn Atom	518
Dual Power Supply	518

Eprom Programmer for the TRS-80 & Genie	518
Multimod	800
Speech Synthesiser for BBC Micro	800
Transistor Tester	518

RADIO WORLD <i>by Pat Hawker</i>	49, 98, 182, 230, 310, 382, 446, 536, 605, 659, 742
----------------------------------	---

Cost of TV, Cable Vision, CB Success	49
Exit the Pirates, Telecommunications Bill	98
The Electronics Epoch, Crystal-Ball Gazing	182
Your Personal Humanoid, Vintage Valves, The Young Tutor	230
Cost of Quality, A.M. and CB, Teddy on the Dole	310
SW Broadcasting, Sporting Ploy, Teletext 10	382
RTTY Legal Maze, Vintage Form-Filling	446
European DX Council, CB Collapse, Long Distance TV, Topic in the Air	536
Political No-speak, Museum of Television, Japanese No-code	605
All Change, Merriman Report, Signals from Space	659
Age of Contestants, Talkabout, Radio Marti, Standing Hazard	742
Where have all the viewers gone, Tiny TV, Pen Radlos	829

READERS' LETTERS	226, 297, 387, 445, 506, 608, 662, 747
------------------	--

SHOP TALK <i>by Dave Barrington</i>	23, 85, 145, 217, 281, 369, 427, 487, 565, 629, 703, 801
-------------------------------------	--

SCHOOL RADIO CLUB <i>by D. J. Fry</i>	444
---------------------------------------	-----

SEDAC 1983	592
------------	-----

SEDAC 1984	645, 715, 813
------------	---------------

TRANSISTOR DATA	312
-----------------	-----

WIRE BENDING GAUGE	156
--------------------	-----

SPECIAL INSERTS AND OFFERS

WIRE BENDING GAUGE (Cover Mounted) March 1983

FREE TRANSISTORS—BCY65EP—2N4123 (Cover Mounted) May 1983

VERO MICROBOARDS (Special Offer) May 1983

SMOKE DETECTOR/FIRE ALARM (Special Offer) June 1983

EAGLE KEW7S MULTIMETER (Special Offer) October 1983

The Proto-Board[®]

Now circuit designing is as easy as pushing a lead into a hole . . .
 No soldering
 No de-soldering
 No heat-spilt components
 No manual labour
 No wasted time



For quick signal tracing and circuit modification
 For quick circuit analysis and diagramming
 With or without built-in regulated power supplies
 Use with virtually all parts — most plug in directly, in seconds.
 Ideal for design, prototype and hobby

NO	MODEL NO	NO OF SOLDERLESS TIE-POINTS	IC CAPACITY (14-pin DIP's)	UNIT PRICE	PRICE INC P&P 15% VAT	OTHER FEATURES
1	PB6	630	6	11.00	13.80	Kit
2	PB100	760	10	14.25	17.53	Kit
3	PB101	940	10	19.65	24.32	
4	PB102	1240	12	24.95	30.41	
5	PB103	2250	24	40.95	48.81	
6	PB104	3060	32	51.45	61.46	
7	PB105	4560	48	74.50	87.97	
8	PB203	2250	24	76.00	89.70	5V@1A
9	PB203A	2250	24	105.00	124.20	5V ±15V
10	PB203AK	2250	24	85.00	100.05	5V ±15V & Kit

Tomorrow's tools for today's problems

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 4U
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex. CB11 3AQ.
 Telephone: Saffron Walden (0799) 21682
 Telex: 817477

G.S.C. (UK) Limited, Dept. 4U Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

1 Qty Req	2 Qty Req	3 Qty Req	4 Qty Req	5 Qty Req	6 Qty Req	7 Qty Req	8 Qty Req	9 Qty Req	10 Qty Req
-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	------------

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard, Access, American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The G.S.C. 24 hour 5 day a week service Telephone (0799) 21682 and give us your Barclaycard, Access American Express number and your order will be in the post immediately

For FREE catalogue tick box

TEACH-IN 84

Once again GREENWELD will be supplying a complete set of parts for this ever popular series — as we have done for all previous series.

Our experience in this field means your kit can be supplied from stock at the best possible price, so order with confidence. Price for complete kit is only £18.95 inc post and VAT.



MOTORIZED GEARBOX

These units are as used in a computerized tank, and offer the experimenter in robotics the opportunity to buy the electro-mechanical parts required in building remote controlled vehicles. The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors etc. £5.95. Suitable wheels also available: 3" Dia plastic with black tyre, drilled to push-fit on spindle. 2 for £1.30 (limited qty). 3" dia aluminium disc 3mm thick, drilled to push-fit on spindle. 2 for 68p.



TREAT YOURSELF TO A NICE NEW DIGITAL MULTIMETER!!

KD55C A DVN for the professional — this 3½ digit multimeter has overload protection, low battery and over range indication. Full auto polarity operation. AC Volts: 0.2-700
DC Volts: 0.2-1000
AC Current: 200µA-10A
DC Current: 200µA-10A
Resistance: 200R-200M
Total 28 ranges for just £44.95

1 PRICE 2 SALE

Any of the goods listed below — for every one bought at full price, another may be purchased at HALF PRICE!!

(Offer ends Jan 31st 1984)

RIBBON CABLE

Special purchase of multicoloured 14 way ribbon cable — 40p/metre; 50m £18; 100m £32.00; 250m £65.00.

TTL PANELS

Panels with assorted TTL inc LS types. Big variety. 20 chips £1.00; 100 chips £4.00; 1000 chips £30.00.

"THE SENSIBLE 64"

David Highmores new book on the Commodore 64 now available. £5.95.

THE 1984 GREENWELD CATALOGUE

Now in the course of production, the 1984 GREENWELD catalogue will be published in November. It's Bigger, Brighter, Better, more components than ever before. With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00! Order now for early delivery!

COMPUTER GAMES

Z901 Can you follow the flashing light/pulsating tone sequence of this famous game? Supplied as a fully working PCB with speaker (no case) plus full instructions. Only £4.95

Z902 Probably the most popular electronic game on the market — based on the old fashioned pencil and paper battleship game, this computerized version has brought it bang up to date! We supply a ready built PCB containing 76477 sound effect chip, TMS1000 micro-processor chip, R's, C's etc. Offered for its component value only (board may be cracked or chipped, it's only £1.95. Instructions and circuit, 30p.

PACKS! PACKS! PACKS!

K517 Transistor Pack. 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114, 117, 172, 182, 183, 198, 239, 251, 214, 225, 320, BF198, 255, 394, 2N3904 etc etc. Retail cost £7+. Special low price 275p

K523 Resistor Pack 1000 — yes, 1000 ½ and ½ watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several megohms. Only 250p. 5000 £10; 20,000 £36.

K520 Switch Pack. 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p

K522 Copper clad board. All pieces too small for our etching kits. Mostly double sided fibreglass. 250g (approx 110 sq ins) for 200p

K541 It's back!! Our most popular pack ever — Vero cutoffs. This has been restricted for some time, but we have now built up a reasonable stock and can once again offer 100 sq ins of vero copper clad cutoffs, average size 4x3". Offered at around ½ the price of new board 320p

K530 100 Assorted polyester caps — all new modern components, radial and axial leads. All values from 0.01 to 1µf at voltages from 63 to 1000V! Super value at 395p

K602 Electrolytics — all long leaded radial type — most values from 10µf to 1000µf, nearly all 10V, few 16V. Bag of 100 assorted £3.50

GREENWELD

443D Millbrook Road Southampton SO1 0HX
Tel (0703) 772501
ALL PRICES INCLUDE VAT; JUST ADD 60p P&P

FREE CAREER BOOKLET

Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today — at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

TV & AUDIO SERVICING

ELECTRICAL ENGINEERING

RUNNING YOUR OWN BUSINESS

Name

Address

ICS
Division of National Education Corporation

ICS
Dept P268
160 Stewarts Road,
London SW8 4UJ



01-622 9911
(all hours)

ELECTROVALUE

Oct. 1983

THE E.E ENTHUSIAST'S
A-Z
BUYING GUIDE

It's amazing what you'll find in the pages of our current autumn price list, be you beginner, expert or professional. The list below gives some idea of the enormous stocks we carry, and our service is just about as good as meticulous care and nearly twenty years of specialised experience can make it. WRITE, PHONE OR CALL FOR OUR AUTUMN PRICE LIST NOW!

IT'S
FREE!

Good Bargains
Good Service
Good Choice

Please mention this journal when applying

Access facilities
Aerosols
Batteries
Boxes
Breadboards
Computers & Eqpmt
Capacitors

Connectors
Discounts
Electrolytics
Ferrites
Grommets
Hardware
I.C.s
Knobs

Lamps
Meters
Opto-electronics
Potentiometers
Pot Cores
Quantity prices
Resistors
Relays


Semi-conductors
Switches
Solder tools
Tools
Transformers
Vero products
Visa facilities
Zener diodes

ELECTROVALUE LTD., 28 St Jude's Road, Englefield Green, Egham, Surrey TW20 0HB, (0784) 33603. Telex 264475: Northern Shop (Callers only) 680 Burnage Lane M/c M19 1NA. (061-432 4945) EV Computing Shop, 700 Burnage Lane, Manchester (061-431 4866).

NEW ITEMS FROM OUR BARGAIN LIST

- Screws enable wires to be quickly joined and insulated in one simple operation without screwdriver or pliers. Ideal for hooking up experimental circuits but quite safe to use inside metal or plastic boxes for joining mains wiring. Sample pack, 5 large, 5 small **£0.57**
- 2Kw immersion heater — 10" long standard mounting **£2.30**
10 for **£17.25**
- Clockwork timer — basically a 2 hr timer, very easily adaptable to 1 hr or ½ hr. Approx 2" diameter. 2 screw mounting ¼" spindle **£2.30**
10 for **£17.25**
- BC to 2 Twin Adaptors for operating Christmas tree lights etc from a lamp holder **£0.75**
10 for **£5.00**
- Multimeter Stand — a neat plastic adjustable holder. Ideal for pocket sized multimeter, calculator etc. Makes it so much easier to read and at the same time protecting the instrument from being damaged **£0.69**
- PP3 Replacer Kit comprising plastic case, transformer, rectifiers, condensers, and wiring diagram **£1.95**
- Fixing staples — always useful to have a few of these around the house. Consist of hardened pin on plastic piece shaped to take cable. Various sizes to suit wires from speaker wires, to ring main cable 100 assorted **£1.15**
- Trigger Mats — a simple and sure way of setting off a burglar alarm. Place this under the carpet at windows or doorways, directly it is walked on it will switch on the alarm. Ideal for use with our burglar alarm panel. Size 24" x 18" **£2.30**
- Wall Mounting Thermostat by Danfoss has a really pretty 2 tone grey case with circular white scale and dial. Setting temperature from 0-30c 13 amp 250v contacts **£4.95**
- Thermo Couple Prod — when used with a suitable millivolt meter this could be used to find the centre temperatures of say, meat or liquids **£3.45**

3 CHANNEL SOUND TO LIGHT KIT

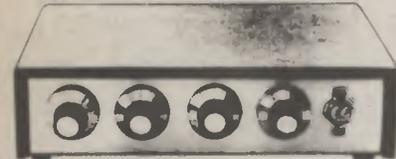

Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by ¼" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

12 volt MOTOR BY SMITHS

Made for use in cars, etc, these are series wound and they become more powerful as load increases. Size 3½" long by 3" dia. They have a good length of ¼" spindle — Price **£3.45**
Ditto, but double ended **£4.25**
Ditto, but permanent magnet **£3.75**



EXTRA POWERFUL 12v MOTOR

Probably develops up to ¼ h.p. so it could be used to power a go-kart or to drive a compressor, etc. **£7.95 + £1.50 post.**

THERMOSTAT ASSORTMENT

10 different thermostats, 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for **£2.50**.

MINI MONO AMP on p.c.b., size 4" x 2" (app.)

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of **£1.15 each**, or 10 for **£10.00**.



— BARGAIN OF THE YEAR —

The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 270 KHz, medium wave band 525 — 1850KHz, FM band 87 — 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00**
+ £1.50 post + insurance.

THIS MONTH'S SNIP

12v DRILL WITH CHUCK to take up to 2.5mm drills — miniature but very powerful. Ideal model for p.c.b. work. Wonderful present for dad or son. Only **£8.50**.

REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Franco Company this is a very robust motor, size approximately 7½" long, 3¼" dia. 3/8" shaft. Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

1 Franco motor with gear box	1 push to start switch
1 manual reversing & on/off switch	2 limit stop switches
	1 circuit diag. of connections

£19.50 plus postage £2.50

FOR SOMEONE SPECIAL

Why not make your greeting card play a tune? It could play "Happy Birthday", "Merry Christmas", "Wedding March", etc, or "Home Sweet Home", etc. Wafer thin 3 part assemblies, for making cards musical. Mini microchip speaker and battery with switch that operates as the card is opened. Please state tune when ordering. Complete, ready to work **£1.25**.

REEL TO REEL TAPE DECKS

Ex-Langage Teaching School. Second, but we understand these are in good order; any not so would be exchanged. The deck is a standard BSR with normal record, replay facilities and an additional feature is tape re-connector. Nicely finished in teak type box. We have 30 only of these. Price **£8.50 each + £3 carriage**.

MAINS CLOCK SWITCH

Bold, easy to read clock with coupling to operate 25a switch. Made for cookers but if you throw away the switch section you can have a very neat and accurate clock at a fraction of today's cost. We are overstocked with these and are making a special offer price of 10 for **£6.50 + £2 post**. Or 100 for **£50 carriage paid**.

6v POWER SUPPLY UNIT

Mains operated fully smoothed 6v 200 ma output. Enclosed in neat plastic case only **£1.15 each**, but we are offering these at such a silly price because they are intended to plug into shaver sockets but it is a simple matter to remove the pins and solder on a flex lead. The 6v output termination is a 3.5 jack plug, thus making it suitable for many cassettes and radios.

A PRESTEL UNIT, brand new and complete except for 7

plug in ICs — so far as we know the unit would work once the missing ICs are fitted. Price: **£19.75 + £2.00 post**.



WATERPROOF HEATING WIRE

100 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with pvc. Dozens of uses — around water pipes, under grow boxes, in gloves and socks. Price: **23p per metre**.

TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs **FOR ONLY £2.50**.

ROPE LIGHT

4 sets of coloured lamps in translucent plastic tube arranged to give the appearance of a running or travelling light. With variable speed control box, ideal for disco or shop window display. Complete, made up, ready to plug into mains. **£36.00 + £2 post**.

50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Top way telephone, Memory jogger, Live line tester, Continuity checker, etc, etc., and you will still have hundreds of parts for future projects. Our 10Kg parcel contains not less than 1,000 items — panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

YOURS FOR ONLY £11.50 plus £3.00 post.

MINI-MULTI TESTER Deluxe pocket size precision moving coil instrument, Jewelled bearings — 2000 o.p.v. mirrored scale.

11 instant range measures: DC volts 10, 50, 250, 1000, AC volts 10, 50, 250, 1000, DC amps 0 — 100 mA.



Continuity and resistance 0 — 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only **£6.75 + 60p post and insurance**.

FREE Amps range kit to enable you to read DC current from 0 — 10 amps, directly on the 0 — 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send **£2.50**.

J. BULL (Electrical) Ltd.

(Dept. EE), 34 — 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU **Established 50 YEARS**

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote. Shop open 9.00 — 5.30, Mon to Fri, not Saturday.

EXTRACTOR FANS — MAINS OPERATED

- Woods extractor:
5" — **£5.75**, Post **£1.25**
6" — **£6.95**, Post **£1.25**
5" Plannair extractor **£6.50**, Post **£1.25**
4" x 4" Muffin 115v. **£4.50**, Post **75p**
4" x 4" Muffin 230v. **£5.75**, Post **75p**
All the above ex-computer, those below are unused.
4" x 4" **£8.50**, Post **75p**
9" American made **£11.50**, post **£2.00**
Tangential Blower 10x3 air outlet, dual speed **£4.60**, Post **£1.50**.



TANGENTIAL BLOW HEATER

by British Solartron, as used in best blow heaters. 2Kw approx 9" wide **£5.95**, 3Kw either 9" or 12" wide (your choice) **£8.95** complete with 'cold' 'half' and 'full' heat switch, safety cut out and connection dig. Please add post **£1.50** for 1 or **£2.30** for two.



2.5 Kw KIT Still available: **£4.95 + £1.50 post**.

BLEEP TONE

These work off 12v and have an unusual and pleasant bleep. **69p each**.

CONNECTING WIRE PACK 48 lengths of connecting wire, each 1 metre long and differently colour coded, and a making for those difficult interconnecting jobs. **85p the lot**.

GPO PLUG & SOCKET Ideal for connecting extension telephone, Prestel and similar equipment. Socket fits onto skirting. **£3.45 per pair**.

RED LEDS 10 for 69p. 100 for **£5.75**. 1000 for **£52**.

IN LINE SIMMERSTAT Ideal heat controller for soldering iron and many other hand-held appliances. **£2.30**, 10 for **£17.25**.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs, repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only **£2.95**. These are without case — but we can supply a plastic case — **£1.75**. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is **£2.30**.

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included. **£11.95 plus £2.00 post**.

OTHER POPULAR PROJECTS

- Short Wave Set — covers all the short wave bands using plug-in coils. Kit complete **£14.50**
- R C Bridge Kit **£9.95**
- 3 Channel Sound to Light — with fully prepared metal case. **£14.95**
- Ditto — made up **£25.00**
- Big Ear, listen through walls **£9.50**
- Robot controller — receiver/transmitter **£9.50**
- Ignition kit — helps starting, saves petrol, improves performance **£13.95**
- Silent sentinel Ultra Sonic Transmitter and receiver **£9.50**
- Car Light 'left on' alarm **£3.50**
- Secret switch — fools friends and enemies alike **£1.95**
- 3 — 30v Variable Power Supply **£13.80**
- 2 Short & Medium wave Crystal Radio **£3.99**
- 3v to 16v Mains Power Supply Kit **£1.95**
- Light Chaser — three modes **£17.50**
- Mullard Unilex HiFi stereo amplifier with speakers **£16.75**
- Radio stethoscope — fault finding aid **£4.80**
- Mug stop — emits piercing squawk **£2.50**
- Morse Trainer — complete with key **£2.99**
- Drill control kit **£3.95**
- Drill control kit — made up **£6.95**
- Interrupted beam kit **£2.50**
- Transmitter surveillance kit **£2.30**
- Radio Mike **£6.90**
- FM receiver kit — for surveillance or normal FM **£3.50**
- Seat Belt reminder **£3.00**
- Car Starter Charger Kit **£15.50**
- Soil heater for plants and seeds **£16.50**
- Insulation Tester — electronic megger **£7.95**
- Battery shaver or fluorescent from 12v **£6.90**
- Matchbox Radio — receives Medium Wave **£2.95**
- Mixer Pre-amp — disco special with case **£16.00**
- Aerial Rotator — mains operated **£29.50**
- Aerial direction indicator **£5.50**
- 40 watt amp — HiFi 20Hz — 20kHz **£9.50**
- Microvolt multiplier — measure very low currents with ordinary multimeter **£3.95**
- Pure Sine Wave Generator **£5.75**
- Linear Power output meter **£11.50**
- 115 Watt Amplifier 5Hz 25kHz **£13.50**
- Power supply for one or two 115 watt amps **£17.50**
- Stereo Bass Booster, most items **£8.95**

Build and test your own circuit with the New Verobloc Kit



Try the new prototyping method of building and testing circuits with the British-made Verobloc kit. It consists of:

1. Verobloc. 2. A pad of design sheets for planning the circuits. 3. A component mounting panel for the larger components, i.e. switches, etc.

You can expand the circuit area by simply interlocking two or more Veroblocs and, of course, with normal usage, they can be used time and time again without damaging contacts or component leads. The glass nylon material is virtually unbreakable and able to withstand temperatures from -60°C to $+120^{\circ}\text{C}$.

So take advantage of our special price of £5 per kit (including VAT) by completing the coupon below, or telephone (04215) 62829 (24 hours). This offer closes December 31st, 1983.

BICC Vero-Electronics Limited,
Retail Dept., Industrial Estate,
Chandlers Ford, Hampshire,
SO5 3ZR.



Please allow 2-3 weeks for delivery.

I wish to purchase _____ Verobloc kit/s
at £5 per kit inclusive of VAT for a total of £ _____
I enclose my cheque/postal order or I debit my
Access/Barclaycard No. _____ Delete where appropriate
Name: _____
Address: _____
Postcode _____

SOLDERING/TOOLS

ANEX X6 SOLDERING IRON 25W £5.48
SOLDERING IRON STAND £1.98
SPARE BITS. Small, standard, large. 65p each. For X5+X25
SOLDER. Handy size 99p
SOLDER CARTON £1.84
DESOLDER BRAID 69p
HEAT SINK TWEEZERS 29p
DESOLDER PUMP £6.48
HOW TO SOLDER LEAFLET 12p
LOW COST CUTTERS £1.89
LOW COST LONG NOSE PLIERS £1.68
WIRE STRIPPERS & CUTTERS £2.69

PRECISION PETITE £11.67
12V PCB DRILL £7.98
DRILL STAND 50p
GRINDING STONE 50p
GRINDING WHEEL 50p
SAW BLADE 85p
BRASS WIRE BRUSH 50p
BURR 50p

VERO SPOT FACE CUTTER £1.49
PIN INSERTION TOOL £1.98
VEROPINS (pk of 100) 0.1" 82p
MULTIMETER TYPE 1 (1,000 opv) £5.48
CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips 99p

RESISTOR COLOUR CODE 21p
CONNECTING WIRE PACK TYPE ED. 11 colours 40p

ILLUMINATED MAGNIFIERS £1.14
Small 2" dia. (5x mag) £2.40
Large 3" dia. (4x mag) £2.98

CAST IRON VICE £1.98
SCREWDRIVER SET £3.98
POCKET TOOL SET £2.95
DENTISTS INSPECTION MIRROR £1.50
JEWELLERS EYEGLASS 69p

Speakers Min 8 ohm 87p; 64 ohm 89p; 80 ohm 98p.
Crystal earpiece 65p
Magnetic earpiece 18p
Stethoscope attachment 69p
Mono headphones £2.98
Stereo headphones £4.35
Telephone pickup coil 72p
Min buzzer 6V 50p. 12V 65p.
Euro breadboard £6.40
S Dec breadboard £3.98
Bimboard breadboard £6.98
Verobloc breadboard £4.20



MULTIMETER TYPE 2. (YN360TR) 20K o.p.v. with transistor tester. £14.75
AC + DC volts. DC current, 4 very useful resistance ranges. We've used it and we like it.



HELPING HANDS JIG £6.80
Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5 magnifier attached), used and recommended by our staff.

PAIR OF PROBES WITH LEADS (oc). 77p
Q MAX PUNCHES
3/8" £2.98; 1/2" £3.06; 5/8" £3.17; 3/4" 3.24.

PCB etching kit £5.98
ZX81 edge connector £2.25
Ferrite rod 5 inch 59p
PP3 clips 10p. PP9 clips 11p.
2 Station intercomm £7.48
IC Sockets 8 pin 16p; 14 pin 17p; 16 pin 18p.
Traditional Style Bell £1.75
Public Address Mic 50K £4.40
Mic Insert Crystal 45p
Cassette Mic £1.29p
Pillow Speaker 98p
Horn Speaker 5" 8 ohm £6.75

MAGENTA ELECTRONICS LTD.

BIMBOARDS

Type	Number of Contact Points	
Eurobreadboard	500	6.25
Bimboard 1	550	6.55
Bimbusstripe	80	2.50
Bimboard PCB	630	1.44
Bimboard Layout Pad		0.46
MPUbreadboard	1422	17.25
Bimboard Designer		77.00



All prices inc VAT. Add 50p per order on Bimboards, £1.50 per order on Bimconsole. SAE for full list. Mail Order only.

BIMSALES

Dept EE1, 48a Station Road, Cheadle Hulme, Cheshire, SK8 7AB. Tel: 061 485 6667.

Prototype with plug-in breadboards. Component support brackets supplied with all except Eurobreadboard

Bimconsole—Metal Brown base, Beige top

Part No.	A	B	C	D	E	
BIM 2601	178	51	210	38.5	70	9.15
BIM 2602	280	51	210	38.5	70	10.15
BIM 2603	381	51	210	38.5	70	11.75
BIM 2604	483	51	210	38.5	70	13.35
BIM 2605	483	51	261	38.5	70	14.90
BIM 2701	178	76	210	38.5	70	9.60
BIM 2702	280	102	210	38.5	70	11.20
BIM 2703	381	102	210	38.5	70	12.40
BIM 2704	483	102	210	38.5	70	14.15

Bimconsole—ABS Black or Grey base with Grey Aluminium top

BIM 6005	105	55.5	143	31.5	37.5	2.25
BIM 6006	170	55.5	143	31.5	37.5	2.80
BIM 6007	170	81.8	213.8	31.5	57.8	3.85

Please mention
EVERYDAY ELECTRONICS
When replying to
Advertisements

E.E. PROJECT KITS

TEACH IN 84

Full Kits inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.
If you do not have the issue of E.E. which includes the project - you will need to order the instruction reprint as an extra - 50p each. Reprints available separately 50p each + p&p 50p.

- SPEECH SYNTHESIZER FOR BBC MICRO** Nov. 83 less cable and sockets £21.98
MULTI-MOD Nov. 83 £21.98
LONG-RANGE CAMERA FLASH GUN, TRIGGER Nov. 83 £13.50
HOME INTERCOM less link wire Oct. 83 £14.38
IMMERSION HEATER TELL-TALE Oct. 83 £9.98
TEMPERATURE TRANSDUCER AMP Oct. 83 £14.87
SHORT WAVE RADIO less phones, Oct. 83 £25.63
Mono headphones extra £2.98
ELECTRONIC PENDULUM Oct. 83 £17.98
less wire & hardware for electromagnet
DIGITAL TO ANALOGUE BOARD Oct. 83 £19.98
less cable, case & connector
HIGH POWER DAC DRIVER BOARD Oct. 83 less case £12.52
A TO D CONVERTER FOR RM3802 Sept. 83 inc plug £35.98
HIGH SPEED A TO D CONVERTER Sept. 83 less cable & connector £27.98
SIGNAL CONDITIONING AMP Sept. 83 no case £8.98
STORAGE 'SCOPE INTERFACE FOR BBC MICRO Aug. 83 less software £13.98
PEDESTRIAN CROSSING SIMULATION BOARD Aug. 83 no case £41.58
HIGH POWER INTERFACE BOARD Aug. 83 no case £9.44
CAR INTRUDER ALARM Aug. 83 £15.52
TRI BOOST GUITAR TONE CONTROLLER July 83 £7.99
USER PORT I/O BOARD less cable + plug £5.54
USER PORT CONTROL BOARD July 83 less cable + plug £22.86
PULSE GENERATOR July 83 £34.97
BINARY BANDIT GAME July 83 less case £8.98
EPROM PROGRAMMER Jun. 83 less software £40.99
TRANSISTOR TESTER Jun. 83 £26.31
ENVELOPE SHAPER Jun. 83 less case £11.21
REAL TIME CLOCK May 83 less software and cases
Apple II £30.98 BBC £35.99 less power plug
MODEL TRAIN CONTROLLER May 83 £25.17
GUITAR HEADPHONE AMPLIFIER May £37.20
MW PERSONAL RADIO less case, May £6.93
LABORATORY AMPLIFIER May 83 £30.98
MOISTURE DETECTOR May 83 £4.97
CAR RADIO POWER BOOSTER April 83 £10.98
FUNCTION GENERATOR April 83 £41.98
FLANGER SOUND EFFECTS April 83 £21.98
ZX SPECTRUM AMPLIFIER April 83 £8.98
DUAL POWER SUPPLY March 83 £53.98
BUZZ OFF March 83 £4.10
SPEECH PROCESSOR Feb. 83 £10.56
PUSH BIKE ALARM Feb. 83 £11.32
MOTOR BIKE ALARM Feb. 83 £14.46
DOUBLE DICE Jan. 83 £10.82
ELECTRONIC V/I METER Dec. 82 £11.38
ZX TAPE CONTROL Nov. 82 £6.48
SINE WAVE GEN Oct. 82 £14.65
G. P. PRE-AMP Oct. 82 £5.64
LIGHTS ON ALERT Oct. 82 £4.25
CONTINUITY CHECKER Sept. 82 £4.97
SOUND SPLITTER Sept. 82 £15.77
SOUND RECOMBINER Sept. 82 £3.70
SCREEN WASH DELAY Sept. 82 £4.48
INSTRUMENT PRE AMP Aug. 82 £7.82
2-WAY INTERCOM Aug. 82 no case £4.11
TWO TONE TRAIN HORN WITH REMOTE TRIGGER OPTION May 82 £11.26
CAR LED VOLTMETER less case May £22.89
V.C.O. SOUND EFFECTS UNIT Apr. 82 £11.56
CAMERA OR FLASH GUN TRIGGER Mar. 82 £12.41 less tripod bushes
POCKET TIMER Mar. 82 £3.71
GUITAR TUNER Mar. 82 £15.63
SIMPLE STABILISED POWER SUPPLY Jan. 82 £24.58
MINI EGG TIMER Jan. 82 £3.94
SIREN MODULE Jan. 82 less speaker £5.57
MODEL TRAIN CHUFFER Jan. 82 £8.27
GUITAR ADAPTER Dec. 81 £3.76
ELECTRONIC IGNITION NOV 81 £25.98
SIMPLE INFRA RED REMOTE CONTROL Nov. 81 £16.98
PRESSURE MAT TRIGGER ALARM Nov. 81 £6.27 less mats
EXPERIMENTER CRYSTAL SET Nov. 81 less aerial £5.99
Headphones £2.98 extra
CAPACITANCE METER Oct. 81 £23.51
SUSTAIN UNIT Oct. 81 £12.76
TAPE NOISE LIMITOR £4.57

- HEADS AND TAILS GAME** £2.52
CONTINUITY TESTER £3.95
PHOTO FLASH SLAVE £3.46
FUZZ BOX £7.29
OPTO ALARM £5.78
ICE ALARM £7.89
0-12V POWER SUPPLY Sept. 81 £17.98
CMOS CAR SECURITY ALARM Sept. 81 £9.08
CMOS DICE Sept. 81 £7.99
CMOS METRONOME Aug. 81 £8.23
COMBINATOR LOCK July 81 less case £19.58
BURGLAR ALARM SYSTEM Jun. 81 less bell, loop & Mic's £40.98
LIGHTS REMINDER AND IGNITION LOCATOR E.E. May 81 £5.66
SOIL MOISTURE INDICATOR E.E. May 81 £4.09
GUITAR HEADPHONE AMP E.E. May 81 £4.23
PHONE BELL REPEATER/BABY ALARM E.E. May 81 £5.66
SIMPLE TRANSISTOR & DIODE TESTERS Mar. 81 Ohm meter version £2.02
Led version £2.04
MINI SIREN Mar. 81 £8.04
LED DICE Mar. 81 £8.44
MODULATED TONE DOORBELL Mar. 81 £6.64
POWER SUPPLY Mar. 81 £5.47
3 CHANNEL STEREO MIXER Feb. 81 £18.69
Ni-Cd BATTERY CHARGER Feb. 81 £13.81
ULTRASONIC INTRUDER DETECTOR Jan. 81 less case £53.47
GUITAR PRACTICE AMPLIFIER Nov. 80 £3.88
SOIL MOISTURE INDICATOR less case extra £21.34
SOUND TO LIGHT Nov. 80 3 channel £11.63
SIGNAL TRACER Jun. 80 £13.11
AUDIO EFFECTS UNIT FOR WEIRD SOUNDS Oct. 80 £13.11
IRON HEAT CONTROL Oct. 80 £5.86
TTL LOGIC PROBE Sept. 80 £5.18
ZENER DIODE TESTER Jun. 80 £6.66
SIGNAL TRACER Aug. 79 £11.63
BATTERY VOLTAGE MONITOR May 80 £5.16
CABLE & PIPE LOCATOR less coil former Mar. 80 £4.11
KITCHEN TIMER Mar. 80 £14.65
STEREO HEADPHONE AMPLIFIER Mar. 80 £18.15
8000 £16.25
MICRO MUSIC BOX Feb. 80 £16.25
Case extra £3.60
SLIDE/TAPE SYNCHRONISER Feb. 80 £12.30
MORSE PRACTICE OSCILLATOR Feb. 80 £4.62
SPRING LINE REVERB UNIT Jan. 80 £25.86
UNIBAND BURGLAR ALARM Dec. 79 £6.03
BABY ALARM Nov. 79 £9.60
CHASER LIGHTS Sept. 79 £23.40
ELECTRONIC TUNING FORK Aug. 79 £10.68
Suitable mic & plug extra £1.79
WARBLING TIMER Aug. 79 £7.35
DARKROOM TIMER July 79 £2.89
ELECTRONIC CANYON Jun. 79 £5.86
TRANSISTOR TESTER Apr. 79 £4.86
ONE TRANSISTOR RADIO Mar. 79 no case £8.15
MICROCHIME DOORBELL Feb. 79 £15.85
THYRISTOR TESTER Feb. 79 £3.78
HEADPHONE ENHANCER Jan. 79 £3.06
FUSE CHECKER Sept. 78 £2.31
SOUND TO LIGHT Sept. 78 £8.42
CAR BATTERY STATE INDICATOR less case Sept. 78 £2.09
R.F. SIGNAL GENERATOR Sept. 78 £26.72
IN SITU TRANSISTOR TESTER Jun. 78 £6.77
FLASHMETER less calc & diffuser May 78 £14.98
WEIRD SOUND EFFECTS GENERATOR Mar. 78 £5.59
AUDIO VISUAL METRONOME Jan. 78 £5.98
ELECTRONIC TOUCH SWITCH Jan. 78 £2.73
RAPID DIODE CHECK Jan. 78 £2.74
PHONE/DOORBELL REPEATER July 77 £7.46
ELECTRONIC DICE Mar. 77 £5.68

FUN WITH ELECTRONICS
* Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners - children and adults. Only basic tools needed, 64 full colour pages cover all aspects - soldering - fault finding - components (identification and how they work).
* Also full details of how to build 6 projects - burglar alarm, radio, games, etc. Requires soldering - 4 pages clearly show you how.
* COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.
* Supplied less batteries & cases.
* FUN WITH ELECTRONICS, COMPONENT PACK £15.78
* BOOK EXTRA £1.25
* Book available separately.

* **NEW SERIES - ALL COMPONENTS IN STOCK NOW FOR FAST DELIVERY.** All top quality components as specified by Everyday Electronics. Our kit comes complete with **FREE COMPONENT IDENTIFICATION SHEET.** Follow this educational series and learn about electronics - Start today.
* **MAGENTA'S TEACH IN KIT INCLUDES ALL OF THESE TOP QUALITY ITEMS:** resistors, pot, capacitors, semiconductors, varicap diode, leds, ferrite rod, sockets, crystal earpiece, terminal blocks, wire and of course 2 breadboards. **PLUS A FREE COPY OF OUR CATALOGUE & PRICE LIST. AVAILABLE NOW**
* **- TEACH IN 84 KIT. £18.98 inc VAT. P+p 50p.** Send now for fast delivery. Reprints of previously published parts 50p each.
* **Official school/college orders welcome.**

BOOKS: ELECTRONICS & COMPUTING

- First Book of Hi-Fi Loudspeaker Enclosures** 95p
28 Tested Transistor Projects £1.25
50 Projects Using IC CA3130 £1.25
A Practical Introduction to Digital IC's £1.25
How to Build Advanced Short Wave Receivers £1.95
Essential Theory for the Electronics Hobbyist £1.95
50 (FET) Field Effect Transistor Projects £1.75
How to Design and Make Your Own PCBs £1.95
Fun with Electronics £1.25
50 Simple L.E.D. Circuits £1.50
How to Make Walkie-Talkies £1.95
Projects in Opto-Electronics £1.95
Multi-Discotheque Handbook £1.35
Electronic Projects for Beginners £1.95
Popular Electronic Projects £1.95
Electronic Security Devices £1.95
50 Circuits Using 7400 Series IC's £1.50
Second Book of CMOS IC Projects £1.50
Beginners Guide to Digital Techniques 95p
Transistor Radio Fault-Finding Chart 50p
Electronic Household Projects £1.75
Electronic Test Equipment Construction £1.75
Practical Computer Experiments £1.75
Radio Control for Beginners £1.75
Popular Electronic Circuits - Book 1 £1.95
Electronic Synthesiser Projects £1.75
Electronic Projects Using Solar Cells £1.95
International Transistor Equivalents Guide £2.95
Simple L.E.D. Circuits - Book 2 £1.35
Easy Electronics - Crystal Set Construction £1.75
Electronic Projects for Cars and Boats £1.95
Popular Electronic Circuits - Book 2 £2.25
How to Identify Unmarked IC's 65p
Multi-Circuit Board Projects £1.95
International Diode Equivalents Guide £2.25
The Art of Programming the 1K ZX81 £1.95
Handbook of Integrated Circuits (IC's) Equiv. & Substitutes £1.95
Solid State Short Wave Receivers for Beginners £1.25
Beginners Guide to Building Electronic Projects £1.95
First Book of Transistor Equivalents and Substitutes £1.50
Second Book of Transistor Equivalents and Substitutes £1.75
Chart of Radio, Electronic, Semi-conductor and Logic Symbols 50p
How to Build Your Own Metal and Treasure Locators £1.95
50 Circuits Using Germanium, Silicon and Zener Diodes £1.50
50 Projects Using Relays, SCR's and TRIACS £1.95
Electronic Music and Creative Tape Recordings £2.95
Practical Electronics Calculations and Formulae £1.95
How to Build Your Own Solid State Oscilloscope £1.45
Practical Construction of Pre-amps, Tone Controls, Filters & Attn. £1.75
IC Projects for Beginners £1.75
Control, Driver and Numerical Display Projects £1.75
An Introduction to BASIC Programming Techniques £1.95
30 Solderless Breadboard Projects - Book 1 £2.25
How to Get Your Electronic Projects Working £1.95
Practical Electronic Building Blocks - Book 1 £2.25
Practical Electronic Building Blocks - Book 2 £1.95
Elementary Electronics. Sladdin. Excellent theory and 35 constructional projects. Uses S-Dec. First steps to CSE level. £3.98
Interfacing to Microprocessors and Microcomputers £5.75
- The Art of Programming the 16K ZX81** £2.50
The Art of Prog the ZX Spectrum £2.50
Semiconductor Data Book Newnes £6.95
Basic Electronics. Theory and practice £7.98
Microprocessors for Hobbyists £2.70
Burglar Alarm Systems £3.90
Electronics, Build and Learn £3.90
Electronic Projects in Music £3.90
Electronic Projects in Photography £3.90
Electronic Projects for Home Security £3.90
Questions and Answers Electronics £2.70
Electronic Projects in the Car £2.90
20 Solid State Projects Car and Garage £4.80
110 Electronic Alarm Projects £5.98
Computing is Easy £4.25
ZX81 Users Handbook £5.75
ZX81 Basic Book £1.75
50 CMOS IC Projects £1.35
52 Projects using IC741 £1.25
IC555 Projects £1.95
IC LM3900 Projects £1.35
Single IC Projects £1.50
Electronic Games £1.75
A Microprocessor Primer £1.95
Remote Control Projects £1.95
Electronic Music Projects £1.75
Power Supply Projects £1.75
VMDOS Projects £1.95
Digital IC Projects £1.95
How to use Op-Amps £2.25
Audio Projects £1.95
Electronic Timer Projects £1.95
Model Railway Projects £1.95
IC Projects for Beginners £1.95
Mini Matrix Board Projects £1.95
Aerial Projects £1.95
Modern Op-Amp Projects £1.95
The Pre-Computer Book £1.95
Electronic Science Projects £2.25
More books in our price list
- *****
CHRISTMAS DECORATIONS
* Same styl as usual E.E. Projects. Instructions/reprint included in project price. Please use code * when ordering.
* **CM1. TWINKLING STAR DECORATION** £6.98
* Plug in power supply extra £3.89
* **CM2. TABLE DECORATION** £9.98
* **CM3. TREE LIGHTS FLASHER** £12.54

INTRODUCING ELECTRONICS

INTRODUCING ELECTRONICS
6 part series E.E. Oct. 82-Mar. 83.
No soldering. Connections via screw terminal blocks. Very clear drawings showing how to connect components. Covers the basis of electronics. Components (less batteries) parts 1-6 £6.98. Reprints 50p each extra.

30 SOLDERLESS BREADBOARD PROJECTS

Book 1 by R. A. Pentold
Clear verobloc layouts and circuit diagrams. Includes fuzz box, radio, metronomes, timers, transistor checker, switches, etc. Introduction gives basic information on components including resistors, capacitors, IC's, transistors, photo-cells etc. Ideal for beginners as well as those with some experience.
Complete kit includes verobloc, book and components (less batteries) £24.75. Less book £22.50, less verobloc £20.25. Book only £2.25.

ADVENTURES WITH DIGITAL ELECTRONICS

Entertaining and instructive. Includes details of some digital IC's and 8 projects: shooting gallery, 2 way traffic lights, electronic adder, computer space invaders game etc. No soldering.
Adventures with Digital Electronics Book £3.25
Component pack including Breadboards £42.50 less batteries

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses IC's. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board.
Adventures with Microelectronics £3.20
Component pack £29.64 less battery.

ADVENTURES WITH ELECTRONICS

by Tom Duncan
An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures, 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.
Adventures with Electronics £2.85. Component pack £18.98 less battery.

MORE KITS AND COMPONENTS IN OUR LISTS
FREE PRICE LIST
Price list included with orders or send sae (9 x 4)
CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

ELECTRONICS CATALOGUE
Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery.
Send 80p in stamps or add 80p to order.
Free to Schools/Colleges requested on official letterhead.

MAGENTA ELECTRONICS LTD.
EE11, 135 HUNTER ST., BURTON-ON-TRENT STAFFS, DE14 2ST. MAIL ORDER ONLY. 0283 65435, Mon-Fri 9-5. Access/Barclaycard (Visa) by phone or post.

Add 50p p&p to all orders. Prices include VAT. See all enquiries. Official orders welcome. OVERSEAS: Payment must be sterling. IRISH REPUBLIC and BFPO: UK PRICES. EUROPE: UK PRICES plus 10%. ELSEWHERE: write for quote.




Miscellaneous

Learn to make your own Printed Circuit Boards EXPERIMENTER'S PRINTED CIRCUIT KIT

Laminate Board, Chemicals, Instruction Book, also, Plans & Circuits for 50 Interesting Projects you can build with own parts. £2.50, p&p 50p. Protect your premises with an efficient ALARM. PHOTOELECTRIC KIT £5.50 p&p 50p INVISIBLE-BEAM OPTICAL KIT £4.50 p&p 50p.

Send SAE for details of all Kits & Circuits
EXPERIMENTAL ELECTRONICS
335 Battersea Park Road,
London SW11. Tel. 01-720 2683

DOUBLE BEGINNER'S KIT. A light-activated switch plus a lamp dimmer/d.c. motor speed controller. Two P.C.B.'s plus components, diagrams, useful applications. £7.50 inclusive. E.I.D. & C., (J.F. Gregory), Loweswater Road, Burlish Park Estate, Stourport, DY13 8LL.

PCB's MANUFACTURED TO YOUR DESIGN, any quantity. Write for free quote. 6 Birchwood Drive, Heathfarm, Shrewsbury, SY1 3DX.

BARGAIN PACKS. PCB's, components, pots, pre-sets, toggle switches, terminal, heatsinks and much more. £5.00 incl. or bumper pack £10.00 incl. Send Chqs, PO's, BC/AC to: BIEM Limited, 28 St. Benedict Street, Norwich, Norfolk, NR2 4QA. Tel: 614254.

LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec.

This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Send cheque or P.O. to:
Roden Products, Dept EE
High March, Coventry,
Northants, NN11 4QE.

£4.99

including p & p

Courses

CONQUER THE CHIP—master modern electronics the practical way by seeing and doing in your own home. Write for your free colour brochure now to **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**, Dept C3, Reading, Berks RG1 1BR.

EVERYDAY ELECTRONICS and computer PROJECTS

Reach effectively and economically to-days enthusiasts anxious to know of your products and services through our semi-display and classified pages. Semi-display spaces may be booked at £7-80 per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 33 pence per word (minimum 12 words), box number 60p extra. All cheques, postal orders, etc., to be made payable to

Receivers & Components

300 SMALL COMPONENTS, including transistors, diodes £2.20; 7 lbs assorted components £6.00; fifty 74 series ICs on panel £2.20; post paid. List 25p refundable. J.W.B. RADIO, 2 Barnfield Crescent, Sale, Cheshire, M33 1NL.

BUMPER BOX OF BITS

WOW!!! We've got so many components in stock, we can't possibly list them all!! - So buy a box, in it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's etc, coils, pots... and so on. All modern parts - guaranteed at least 1000 items, minimum weight 10lbs. ONLY £8.50 inc.

"JUST OUT!! 40 page catalogue ONLY 50p."

ELECTRONICS WORLD
1d Dews Road, Salisbury, Wilts, SP2 7SN
(Prop: Westbrough Ltd)

ELECTRONIC COMPONENTS MERSEYSIDE, Myca Electronics, 2 Victoria Place, Seacombe Ferry, Wallasey, L44 6NR. 051-638 8647.

NOW OPEN IN NEWCASTLE
For the best in Electronic Components,
Test Equipment and Accessories.
MARLBOROUGH
ELECTRONIC COMPONENTS
15 Waterloo Street, Newcastle NE1 4DE
Tel. 618377
Open 9am-6pm Mon-Sat - Easy Parking
Stockists of:
Transistors, Resistors, Capacitors, I.C. Diodes,
Electronic Books, Etc.

AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20dbs, Tunable over the complete UHF TV band. PRICE £8.70.

BH-VHF/FM RADIO, gain about 14dbs, when on the off position connects the aerial direct to the radio. £7.70.

All Boosters we make work off a PP3/006p/6F22 type battery or 8v to 18v DC. P&P 30p PER ORDER.

ELECTRONIC MAILORDER LTD, 62 Bridge St, Ramsbottom, Lancs BLO 3AG. Tel (070642) 3036

Access/Visa Cards Welcome SAE Leaflets

TURN YOUR SURPLUS capacitors, transistors etc., into cash. Contact Coles Harding & Co., 103 South Brink Wisbech, Cambs. 0945-584188. Immediate settlement.

RESISTOR PACKS FOR ALL PROJECTS

1/2 watt carbon film resistors 5% 1 ohm to 10M E24 series. Packs of 10 each value (1690 resistors) £12.50. Your choice of quantities/values 100 for £1.00. VAT and Post Free.

GORDON HALLETT
20 Bull Lane, Maiden Newton,
Dorchester, Dorset DT2 0BQ.

MERCURY TILT SWITCHES. Suitable for 'Distress Beacon' (E.E. Sept. '83) and many other projects. Supplied with free leaflet detailing use as normally-open, normally-closed, changeover or omnidirectional switch with information for use as 'Audio Spirit Level', Car Brake Efficiency tester, Automatic Car Boot Light, Intruder Alarm etc. £1.50 ea., 3 for £4, 10 for £10 P&P free. **MODULUS**, (B. J. McNaughton), 45 Camplin Crescent, Handsworth Wood, Birmingham, B20 1LT.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for
Insertions. I enclose Cheque/P.O for £
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to **Everyday Electronics**)

NAME
ADDRESS

EVERYDAY ELECTRONICS

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street, London SE1 9LS
Telephone 01-261 5942

Rate:
33p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered-Office: King's Reach Tower, Stamford Street, London SE1 9LS.

12/83

AT YOUR SERVICE

Everyday Electronics and Computer Projects and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics and Computer Projects, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St, London SE1 9LS. (Telephone 01-261 5942).

Security

BURGLAR ALARM EQUIPMENT. Free catalogue. C.W.A.S. Ltd., 0274-308920, showrooms open 9-5, Mon-Sat.

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C-TEC SECURITY, Dept EE,
60 Market St, Wigan WN1 1HX
Telephone (0942) 42444



Service Sheets

BELL'S TELEVISION SERVICE for service sheets on Radio, TV etc. £1.50 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to: BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

COMPLETE, FULL-SIZE SETS ANY PUBLISHED service sheets £2 & Isae, except CTVs/Music Centres from £3 & Isae. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications for Isae. Repair data/circs almost any named TV/VCR £8.50 by return. T.I.S.E.E., 76 Church Street, Larkhall, Lanarks, ML9 1HE, Phone (0698) 883334.

TO ADVERTISE ON THESE PAGES
ring
SUE PALMER on
01-261 5942

★ BAKER ★

GROUP P.A. DISCO

AMPLIFIERS

150 watt Output, 4 input Mixer pre-amp. Illustrated	£99
150 watt Output, Slave 500 mv. Input 3 Speaker Outputs	£80
150+150w Stereo, 300w Mono Slave 500 mv. Inputs	£125
150w P.A. Vocal, 8 inputs, High/Low Mixer Echo Socket	£129
100 watt Valve Model, 4 inputs, 3 Outputs, Heavy duty	£125
60 watt Valve Model, 4 inputs, Low imp and 100w line output	£69
60 watt Mobile 240v AC and 12v DC. 4-8-16 ohm+100v line	£89

BAKER LOUDSPEAKERS

Make	Model	Size	Watts	Ohms	Post £2 each	Price
Baker Hi-Fi	Major	12in	30	4/8/16		£16.00
Baker Hi-Fi	Superb	12in	30	8/16		£26.00
Baker P.A.	Group 45	12in	45	4/8/16		£16.00
Baker Hi-Fi	Auditorium	12in	45	8/16		£24.00
Baker Hi-Fi	Auditorium	15in	60	8/16		£37.00
Baker P.A.	DG75	12in	75	4/8/16		£20.00
Baker P.A.	Group 100	12in	100	8/16		£26.00
Baker P.A.	Disco 100	12in	100	8/16		£26.00
Baker P.A.	Group 100	15in	100	8/16		£35.00
Baker P.A.	Disco 100	15in	100	8/16		£35.00

BAKER DISCO

150 Watts twin turntables, twin speakers, headphones, microphones, slide controls. Complete £300, 300 Watt system £399.

RCS SOUND TO LIGHT CONTROLLER KIT

Printed circuit. Cabinet, 3 channels, 1,000 watts each. Will operate from home Hi-Fi or Disco. £19, Post £1.

OR READY BUILT IN CABINET £27.

THE "INSTANT" BULK TAPE ERASER

A.C. 200/240V (120V to order). Ideal Computer Recorder. Post £1

Tapes, Discs, Cassettes. **£10.50**

HEAD DEMAGNETISER PROBE £5.00

ALUMINIUM CHASSIS 18 s.w.g. Undrilled, 4 sides, riveted corners: 6 x 4 x 2jin. £1.75; 8 x 6 x 2jin. £2.20; 10 x 7 x 2jin. £2.75; 14 x 9 x 2jin. £3.60; 16 x 6 x 2jin. £3; 12 x 3 x 2jin. £1.80; 12 x 8 x 2jin. £3.20; 16 x 10 x 2jin. £3.80.

ALL ANGLE BRACKET 6 x 1 x 1in. 30p.
ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75; 6 x 4in. 55p; 12 x 8in. £1.30; 10 x 7in. 90p; 8 x 6in. 90p; 14 x 3in. 72p; 12 x 5in. 90p; 16 x 10in. £2.10; 16 x 6in. £1.30 up.

ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK. 4 x 2 1/2 x 2in. £1.00; 3 x 2 x 1in. 80p; 6 x 4 x 2in. £1.60; 8 x 6 x 3in. £2.50; 12 x 5 x 3in. £2.75; 6 x 4 x 3in. £1.80; 10 x 7 x 3in. £3.

HIGH VOLTAGE ELECTROLYTICS 32+32/350V 50p
8/450V 45p 8+8/500V £1 32+32/500V £2
32/350V 45p 8+16/450V 75p 125/500V £2
32/500V 95p 16+16/350V 75p 16+32+32/500V £2

SINGLE PLAY DECKS

Post £2.

Make Model Cartridge Price

BSR P170 Ceramic £20

GARRARD SP25 Magnetic £35

GARRARD 6200 Ceramic £22

GOLDRING

G102, belt drive, magnetic £30

RADIO COMPONENT SPECIALISTS

Dept 4, 337, WHITEMORSE ROAD, CROYDON

SURREY, U.K. TEL: 01-884 1665

Post 50p Minimum. Callers Welcome

Access-Barclay-Visa Lists 32p PHONE YOUR ORDER

BUY NOW WHILE STOCKS LAST!

SPECIAL PRICE RUSSIAN MULTI-METER UA4324 including Rechargeable Batteries, VAT, P/P
£12

TRANSFORMERS British made transformers at very attractive prices.

Primary	Secondary	Current	1+	10+	100+
240v	4.5-0-4.5v	400m/a	50p	45p	35p
240v	6-0-6v	100m/a	58p	52p	43p
240v	6-0-6v	500m/a	65p	60p	48p

(Postage & Packing: 45p per transformer or £1.60 per 10, £4.50 per 100)

JACK CHASSIS SOCKETS Each 10 100

Each	10	100	3.5mm Mono Plg. 6.35mm Stereo Socket	45p ea.
	14p	£1.20	3.5mm Ster. Plg. 6.35mm Stereo Socket	50p ea.
	20p	£1.75	6.35mm Ster. Plg. 2x6.35mm Ster. Scks	£1.00 ea.
	30p	£2.50	3.5mm Ster. Plg. 2x3.5mm Ster. Scks	£1.00 ea.

Send now for our latest catalogue, 35p plus 30p P+P. Over 72 pages packed with complete range of components. Includes Special Offer list, order form and pre-paid envelope. Please add 15% VAT to the above prices. All orders despatched by return of mail.

MARCO TRADING, DEPT. EE12,

THE MALTINGS, HIGH STREET, WEM, SHROPSHIRE, SY4 5EN. Tel: (0939) 32763

SPECIAL BUYS

Battery eliminator plugs direct into a 13 amp socket, complete with lead and 3.5 jack plug. Ideal for radios, TV games etc. 9v500 £2.50 inc. VAT. Quantity prices upon request.

JEE DISTRIBUTION LTD.

43 Strathville Road BS9000 & CECC Approved 267 Hanworth Road
London SW18 4QX Hounslow, Middx.
Tel: Sales 01-870 0075 EX VAT Tel: 01-570 6502

HOBBY KITS	£ p		£ p
K2 BABYPHONE	7.30	K8 STEREO PREAMPLIFIER:	
K3 STABILIZED POWER SUPPLY	13.44	TONE & VOLUME CONTROL	13.44
K4 STEREO PREAMPLIFIER	9.97	K9 DIGITAL THERMOMETER	25.20
K5 STEREO AMPLIFIER 2 x 10W	13.65	K10 SPEED REGULATOR	9.40
K6 STEREO AMPLIFIER 2 x 40W	24.15	K11 3W F.M. TRANSMITTER WITH AERIAL	11.45
K7 STEREO PREAMPLIFIER WITH PUSH BUTTONS	12.39	K13 SINGLE CHANNEL TRANSMITTER	9.40
CARRIAGE & VAT EXTRA		K14 SINGLE CHANNEL RECEIVER	15.23
		007 COMPACT TRANSMITTER	10.08
		SOS GAS COMPACT GAS DETECTOR	24.15

CALL OR PHONE FOR A WIDER RANGE OF ELECTRONIC COMPONENTS

SUPERKITS! FOR BETTER MUSIC & EFFECTS

Sets include PCBs, Electronic Parts, Instructions, Boxes, Wire, Solder, Batteries not included, but most will run from 9V to 15V DC supplies. Fuller details in list.

CHORUS UNIT: A solo voice or instrument sounds like more!	..KIT162	£31.40
COMPRESSOR: Limits & levels maximum signal strength	..KIT133	£10.86
COMPUTER RHYTHM GEN: 9 drums for digital control	..KIT185	£30.64
COMPUTER-SYNTH INTERFACE: Sequencing & composing aid	..KIT184	£17.44
ECHO UNIT: With double tracking	..KIT168	£44.30
FREQUENCY DOUBLER: Raises guitar frequency by 1 octave	..KIT198	£9.80
FREQUENCY CHANGER & WAVEFORM MODIFIER - Tunable	..KIT172	£34.46
FLANGER: Fascinating effects plus phasing	..KIT153	£22.74
FUZZ: Smooth distortion whilst keeping natural attack & decay	..KIT191	£10.57
GUITAR EFFECTS: Multiple variation of level & filter modulation	..KIT142	£15.40
GUITAR OVERDRIVE: Fuzz plus variable filter quality	..KIT56	£19.73
GUITAR SUSTAIN: Extends effective note duration	..KIT75	£10.04
GUITAR TO SYNTH INTERFACE: With voltage & trig outputs	..KIT173	£32.87
JABBERVOX: Voice disguiser with reverb & tremolo	..KIT150	£23.84
MAD-ROJ: Variable sirens, incl. police, galaxy, machine guns	..KIT146	£9.96
METRONOME: With audible & visual beat & down-beat	..KIT143	£13.81
MICROPHONE PRE-AMP: with base & treble switching	..KIT144	£9.21
NOISE LIMITER: reduces tape & system hiss	..KIT145	£9.97
PHASER: with automatic & manual depth & rate controls	..KIT164	£18.40
REVERB: with variable delay & depth controls	..KIT122	£21.02
RHYTHM GENERATOR: 15 switchable rhythms	..KIT170	£35.64
RING MODULATOR: with integral oscillator control	..KIT179	£15.76
ROBOVOX: versatile robot type voice modifier	..KIT165	£21.03
ROGER 2-GONG: 2 gongs sounded at end of transmission	..KIT126	£11.38
SCRAMBLER: Codes & decodes authorised chans	..KIT117	£22.09
SPEECH-PROCESSOR: for clearer transmission	..KIT110	£9.68
STORM EFFECTS: Automatic & manual, wind, rain, surf	..KIT154	£15.86
TREMOLLO: deep tremolo with depth & rate control	..KIT136	£9.71
VOCODER/VOX: modular vocoder	..KIT152	£64.31
VODALEK: Robot type voice modulator	..KIT155	£12.44
VOICE-OP-SWITCH: with variable sensitivity & delay	..KIT123	£13.41
WAH-WAH: with auto-trigger, manual & oscillator control	..KIT140	£17.26

MANY OTHER GREAT KITS IN CATALOGUE such as Autowah, bass boost, call sign, comparator, frequency generator, Funky-wobulol, hamonola, hum-cut, mixers, sequencers, synthesiser interface, treble boost, tone control, vibrato, voice filter, voice operated fader, Wheezy-jeebly, wobble-wah. Plus digital synthesiser, junior synthesiser, envelope shapers, D-A converter, multiwaveform VCO, keyboards, contacts, etc. - Send S.A.E. for comprehensive catalogue (overseas send £1).

YES - WE ALSO HAVE A KIT MAINTENANCE & REPAIR SERVICE!

Add £1 P&P & 15% VAT to all orders. (Overseas post details stated in cat). Payment CWO, Chq, PO, Access, Barclay, or pre-arranged collection. Despatch usually 10-14 days. Details correct at press, E&OE.

PHONOSONICS, DEPT. EE3D, 8 Finucane Drive, Orpington, Kent, BR5 4ED.

Tel: Orpington (STD 0689) 37821. Mon-Fri 10-7. Callers by appointment.

ambit INTERNATIONAL

The ideal Christmas Gift!

A topical selection from the current ambit parts and equipment catalogue — 148 pages plus 3 £1 discount vouchers! Send 80p for your copy now!
★ mix quantity prices apply for callers to our sales counters

ambit INTERNATIONAL 80p



CH4/RX4

£7.49

01-02204



CHARGERS

Will recharge AA, C, D and PP3 size cells with automatic voltage selection. Will recharge following combinations: 4xD, 4xAA, 4xC, 2xPP3, 2xD+2xC, 2xD+2xAA, 2xD+1xPP3, 2xC+2xAA, 2xC+1xPP3, 2xAA+1xPP3. Charge rate: 11mA for PP3, 45mA for AA size, 120mA for C and D size, for 16 hrs. Power: 240V 50Hz. Output Voltage: 2.9V for AA, C and D size, 11.0V for PP3 size. Weight: 0.475kg. Size: 100x109x55mm.

NiCad battery bonanza time

0.5Ah

2.2Ah

4.0Ah

0.11Ah

AA	C	D	PP3
1-9	80p	£2.35	£3.05
10-49	74p	£1.99	£2.65
Stockcode	01-12004	01-12024	01-12044
			01-84054

200 North Service Road, Brentwood, Essex CM14 4SG
Tel: (0277) 230909

REMEMBER to add 15% VAT & 60p postage to all orders — THANKS!

CALL AT OUR SALES COUNTERS AT
SOLENT COMPONENT SUPPLIES,
53 Burfields Road, Portsmouth, Hants
BROXLEA ELECTRONICS, Park Lane,
Broxbourne, Herts.
& at Brentwood, of course!

BATTERY ADAPTORS
01-12001



A unique battery sleeve adaptor set that converts AA to C or D dimensions, and C to D, ideal for emergencies.

1-9 10-24
96p 65p

if

you have trouble understanding chopper circuits and protection arrangements, want to know about flywheel line sync, are deeply interested in all things from pattern generators to satellite TV receiving techniques—well, have we got the magazine for you.

What would you say to a unique specialist magazine which offers guidance to enthusiasts as well as electronics technicians on all aspects of TV and Video, including servicing, news and developments?

It's well worth a closer look...
December issue on sale NOW

SWITCH ON TO...



INDEX TO ADVERTISERS

Alcon Instruments	833
Ambit International	852
Bicc Vero	848
Bimsales	848
Bi-Pak	786
BK Electronics	Cover III
B.N.R.E.S.	782
Bull J.	847
C-Scope	784
Cricklewood Electronics	783
C-Tec Security	851
Electronics Mail Order Ltd.	850
Electronics World	850
Electronix Design	Cover II
Electrovalve	846
Enfield Electronics	788
Experimental Electronics	850
Gardners Precision	784
Global Specialties	845
Gordon Hallett	850
Greenweld Electronics	846
ICS Intertext	846
Jee Distribution	851
Magenta Electronics	848, 849
Maplin Electronics	Cover IV
Marco Trading	851
Marlborough Electronic Components	850
Phonosonics	851
Radio Components Specialties	851
Riscomp Ltd.	833
R & TVC	787
Roden Products	850
Sparkrite	785
T.K. Electronics	784



MULLARD SPEAKER KITS

Purposely designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 215 x 445mm
 Price £14.90 each + £2.00 P & P.
 5" 30W system — recommended cabinet size 160 x 175 x 295mm
 Price £13.90 each + £1.50 P & P.

Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc.
 8" system cabinet kit £8.00 each + £2.50 P & P.
 5" system cabinet kit £7.00 each + £2.00 P & P.



STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.
 Price £28.70 + £2.50 postage and packing.
 Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50



LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See Photo) Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Prices.**

15" 100 watt R.M.S. Impedance 8 ohms 50 oz magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P
 12" 100 watt R.M.S. Impedance 8 ohms. 50 oz magnet. 2" aluminium voice coil. Res. Freq. 25 Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P
 8" 50 watt R.M.S. Impedance 8 ohms. 20 oz magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille. Price: £9.99 each P&P £1.50



12" 85 watt R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £23.00 + £3 carriage.
 12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price: £23 + £3 carriage.
 15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each.


TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each.

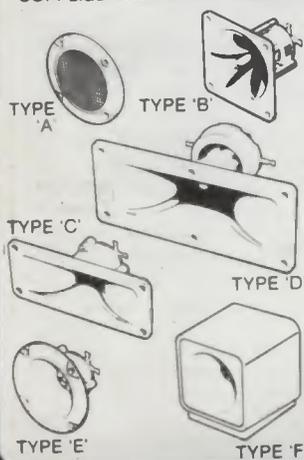TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each
 P&P 20p ea. (or SAE for Piezo leaflets).



OMP 80 LOUDSPEAKER

The very best in quality and value.

Ported tuned cabinet in hard-wearing black vynide with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each
 £90 per pair
 Carriage: £5 each £7 per pair

BK ELECTRONICS

Prompt Deliveries
 VAT inclusive
 prices
 Audio Equipment
 Test Equipment
 by
 Thandar
 and
 Leader

PANTEC

HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt)
 Price: £7.99p

DIGITAL THERMOMETER -9.9 C to +99.9 C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled. professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p


SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm 9/12 volt) Price: £16.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.




3 watt FM Transmitter

BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disc and studio use where all the advantages of a manual arm are required.
 Price £31.35 each. £2.50 P&P

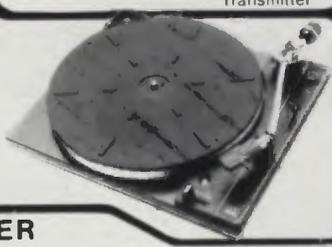

OMP POWER AMPLIFIER MODULE

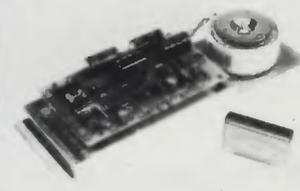

New model.
 Improved specification

NEW OMP100 Mk.II POWER AMPLIFIER MODULE. Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

SPECIFICATION
 Output Power:— 110 watts R.M.S.
 Loads:— Open and short circuit proof 4/16 ohms.
 Frequency Response:— 15Hz - 30KHz -3dB.
 T.H.D.:— 0.01%
 S.N.R. (Unweighted):— -118dB ±3.5dB
 Sensitivity for Max Output:— 500mV @ 10K.
 Size:— 360 x 115 x 72 mm Price:— £31.99 + £2.00 P&P. Vu Meter Price:— £7.00 + 50p P&P

MOSFET versions available up to 300W. R.M.S.

HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable **FULLY GUARANTEED.**

Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.
 Indoor Alarm — Electronic swept freq siren 104dB output.
 Outdoor Alarm — Electronic swept freq siren 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £128 Usual price £228.85
 BKE's PRICE £99.p&p£4
 S.A.E. for colour brochure



MIXERS DISCO

OMP PRO MIX MONO

OMP PROMIX MONO DISCO MIXER (As illustrated), 4 Inputs — 2 Mag. Disc. 1 Aux plus Mic with override. Active bass and treble tone cont's. Individual level controls plus master volume. Monitor output (headphone) for all inputs. Output: 775mV Supply 240Vac. Size: 19" x 5 1/4" x 2 1/2"
 Price: £49.99 + £2.00 P&P

ALSO Stereo Version as above price £69.99 + £2 p&p



B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR



★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★
 ★ All items packed where applicable in special energy absorbing PU foam. ★ Please phone 0702 527572 ★

THE NEW MAPLIN CATALOGUE FOR 84!

NOW WITH PRICES ON THE PAGE

More data, more circuits, more pictures, in the brand new 480 page Maplin catalogue. Take a look at the completely revised Semiconductor section or the new Heathkit section with descriptions and pictures of dozens of kits and educational products from digital clocks to 16-bit business computers. The much expanded computer section itself, gives details of hundreds of pieces of software for Atari, BBC, Commodore 64, Dragon, Spectrum and VIC20. In addition to all this you'll find hundreds of fascinating new items spread through the rest of the catalogue.

As always, the Maplin catalogue is tremendous value for money and now has prices on the page!


Pick up a copy at any branch of W.H.Smith or in one of our shops for just £1.35 or send £1.65 including postage to our Rayleigh address. On sale from 1st Nov 1983.

PROJECTS FOR THE HOME CONSTRUCTOR

Choose from our huge range of value-for-money projects. Projects like our Modem, Mosfet Stereo Amplifier, Home Security System, Frequency Counter and Home Computer add-on kits. Full construction details in our Project Books and brief specifications in our new catalogue. Dozens of fascinating new projects coming soon including a Keyboard for the ZX Spectrum with electronics to make all shifts, single-key operations. Full details in Project Book 9 on sale 11th November 1983. Order As XA09K. Price 70p.



MAPLIN

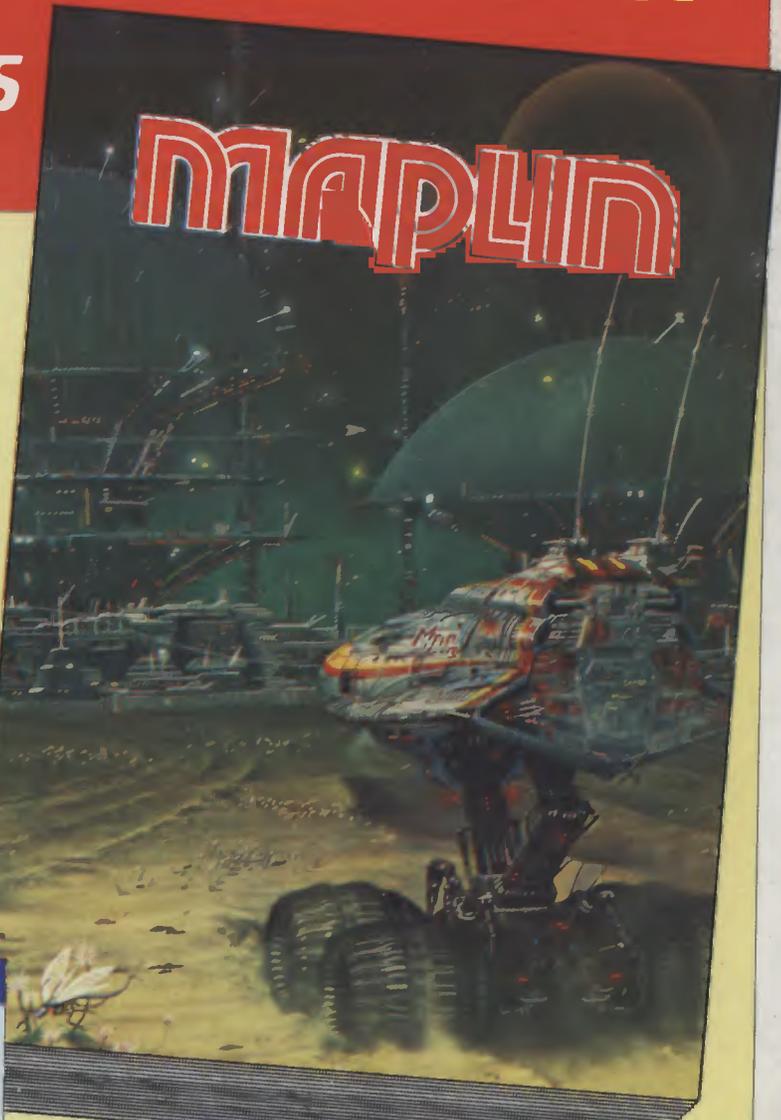

NEW MAPLIN STORE IN SOUTHAMPTON

Opening on 1st November 1983, our new south coast store is at 46-48 Bevois Valley Road, Southampton (Tel: 0703 25831). You will find our full range of components, projects and computers on sale. We are within easy reach of the city centre with good parking close by. Call in and see us soon.



Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packing. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65.

Name

Address

EE12/83

MAPLIN ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 ● Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926 ● 8 Oxford Road, Manchester. Tel: 061-236-0281 ● Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292 ● 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000 ● *46-48 Bevois Valley Road, Southampton. Tel: 0703 25831.

*Opens 1st November 1983. All shops closed Mondays. All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

Despatch by return of post where goods available