

**EVERYDAY**


461

# **ELECTRONICS** and computer **PROJECTS**

JULY 1984

90p

**Part 1**

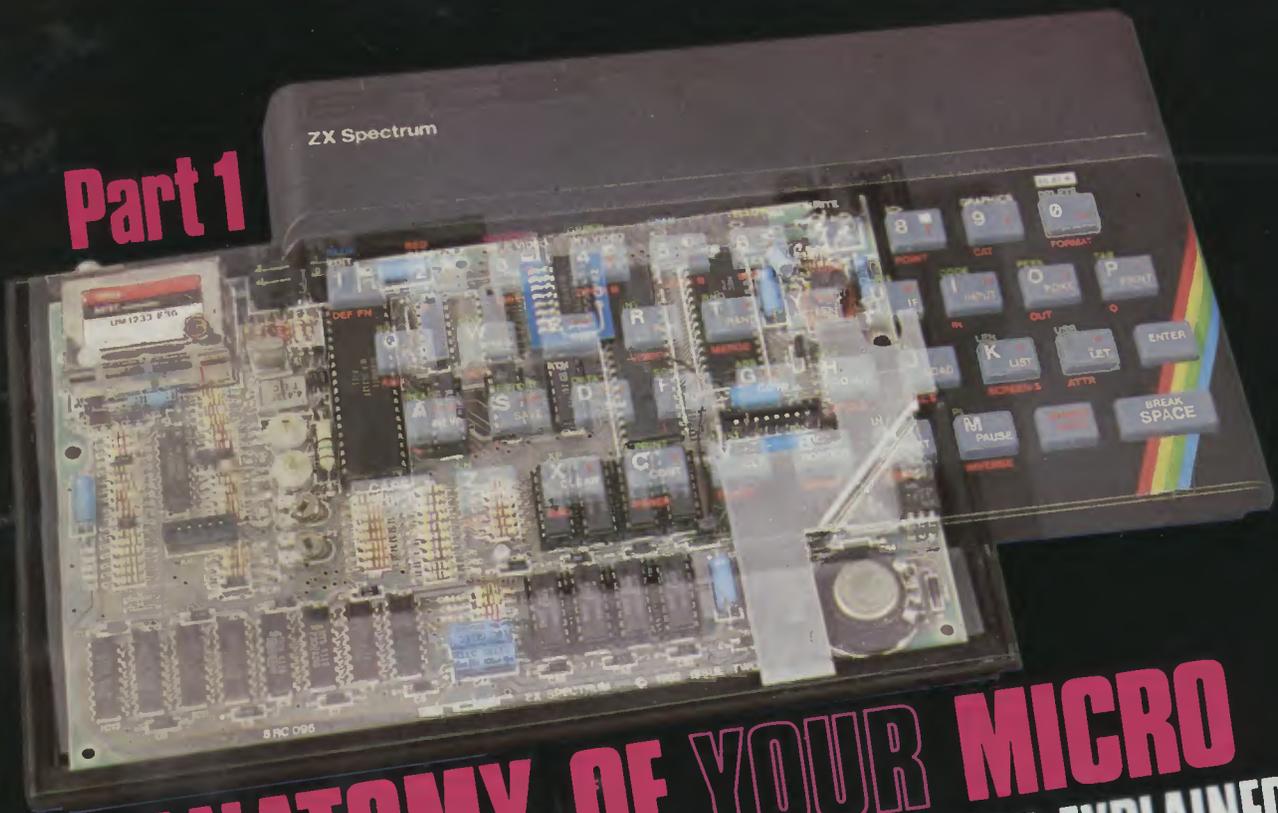




**ANATOMY OF YOUR MICRO**  
COMMON ELEMENTS OF MICROCOMPUTERS EXPLAINED

**CAR LIGHTS REMINDER**  
**ULTRASONIC ALARM SYSTEM**  
**ELECTRONIC LOCK**
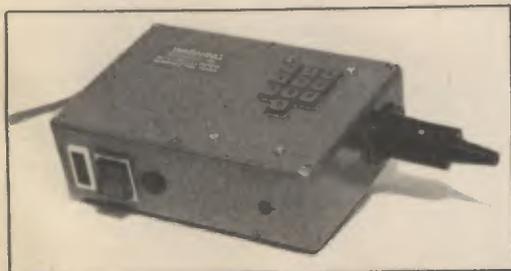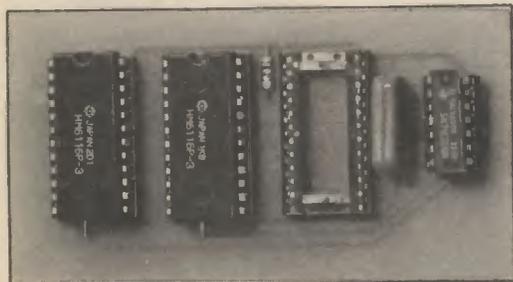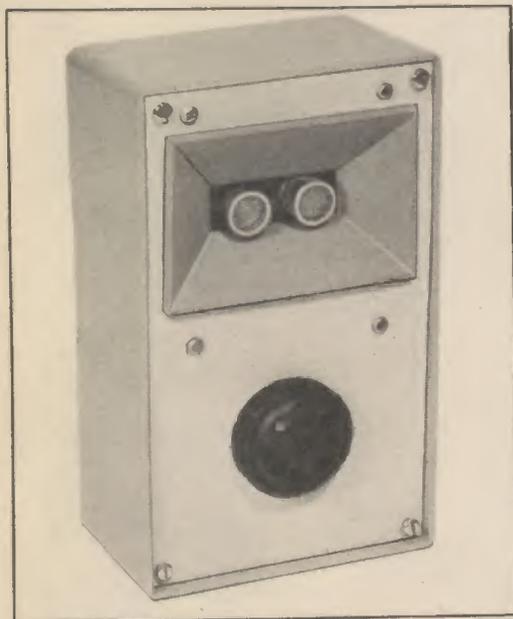
# EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 13 NO. 7 JULY 1984

PROJECTS . . . THEORY . . . NEWS . . .  
COMMENT . . . POPULAR FEATURES . . .



© IPC Magazines Limited 1984. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our August 1984 issue will be published on Friday, July 20. See page 447 for details.

## PROJECTS

- ELECTRONIC CODE LOCK** by Dr. W. D. Phillips 426  
Prevent unauthorised use of electronic equipment
- CAPACITANCE COMPARATOR** by L. S. Cook 431  
Quick check for unmarked devices
- ATOM EPROM SIMULATOR** by J. R. W. Barnes 444  
Low cost program adaptor
- ULTRASONIC BURGLAR ALARM** by I. H. F. Goult 454  
Rumble the quietest burglar with an even quieter whistle
- CB MINI POWER SUPPLY** by T. R. de Vaux Balbirnie 470  
Allows hand-held transceivers to be used at home without constant battery replacement
- CAR LIGHTS WARNING** by H. B. Foster 472  
Don't drive in the dark

## SERIES

- TEACH-IN 84** by George Hylton 436  
Part 10: Digital Circuits
- ANATOMY OF YOUR MICRO** by Owen Bishop 448  
Part One: Introduction—The Microprocessor
- OSCILLATORS** by J. R. Davies 463  
Part 2: Using the 555 and ICM7555

## FEATURES

- EDITORIAL** New Technology 425
- SHOPTALK** by Dave Barrington 434  
Product news and component buying
- CIRCUIT EXCHANGE** 441, 475  
A forum of readers' ideas
- FOR YOUR ENTERTAINMENT** by Barry Fox 442  
Computer Time; Video Dropouts; Microchip Clean-up
- PRINTED CIRCUIT BOARD SERVICE** 443
- COUNTER INTELLIGENCE** by Paul Young 446  
A retailer comments
- EVERYDAY NEWS** 452  
What's happening in the world of electronics
- NEW PRODUCTS** 460  
Facts and photos of instrument, equipment and tools
- RADIO WORLD** by Pat Hawker G3VA 462  
New Licences; Baby Broadcasters; High-Speed Satellite
- SQUARE ONE** 474  
Beginners' Page: Integrated circuits

Readers' Services ● Editorial and Advertisement Departments 425

# Cirkit. A new name

This year Ambit will stop being Ambit. And become Cirkit.

Cirkit is more than just a change of name. It means a better service for you. Faster delivery.

A bigger range of the best and latest products with well over 10,000 different items available.

Everything for the home and industrial user. A whole new Cirkit range of constructional kits, graded for the student, expert and enthusiast.

Modules to build for everyone.

Cirkit is a go ahead company that believes in giving service to its customers.

There's a technically skilled staff to help you. We keep in touch with the manufacturers and we know what's going on.

As soon as new products are available, Cirkit has them.

Cirkit means a bigger catalogue. A better company to deal with.

And a wider than ever range of products that's growing all the time.

For you, Cirkit means a bigger stock and better service.

For further information send for our latest catalogue or visit one of our three outlets at: 200 North Service Road, Brentwood, Essex, CM14 4SG; 53 Burrfields Road, Portsmouth, Hampshire, PO3 5EB; Park Lane, Broxbourne, Hertfordshire, EN10 7NQ.

To: Cirkit Holdings PLC, Park Lane, Broxbourne, Hertfordshire.  
I enclose 80p. Please send me your latest catalogue and 3x£1 discount vouchers!  
If you have any enquiries please telephone us on Hoddesdon (0992) 444111.

Name

Address

Telephone

Area of Special Interest


## Cirkit

Bigger Stock. Better Service.

EE7
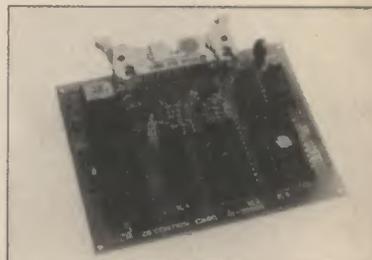
## Computer Products

A complete range from Connectors to Board Level product



C12 Computer Cassette	21-00012	0.55
BBC to Centronics Printer	03-10019	7.25
BBC to 25 way D Male	03-10021	4.50
25 way D Socket	10-25200	1.90
25 way D Plug	10-25100	1.30
Cover for 25 way D	10-25322	0.93
20 up Eprom Eraser	40-82100	31.25
Z80 A Industrial Controller	40-82000	49.95
6802 Industrial Controller	40-68020	49.95
6502 Industrial Controller	40-65020	49.95
Z8 Basic/Debug Controller	41-00904	50.00

## Nicad Batteries & Chargers

Minimum life 600 (300 PP3 size) full charge/discharge cycles. Batteries must be charged from a constant current source only. All batteries are supplied only with a residual charge and should be charged before used.

AA	1.2V	500mAH	01-12004	0.80	10-49	0.74
C	1.2V	2.2AH	01-12024	2.35		1.99
D	1.2V	4.0AH	01-12044	3.05		2.85
PP3	8.4V	110mAH	01-84054	3.70		3.50
CH1/22 PP3 Charger	11mA for 16 hours		01-00159			4.30

CH8/RX Multi-purpose Charger	01-02204	9.40
------------------------------	----------	------

Will recharge AA, C, D and PP3 size cells with automatic voltage selection. Will recharge following combination: 6x D, 6x AA, 6x C, 2x PP3, 2x D + 2x C, 2x D + 2x AA, 2x D + 1x PP3, 2x C + 2x AA, 2x C + 1x PP3, 2x AA + 1x PP3.

Battery Adaptor	01-12001	0.96
-----------------	----------	------

Sold in pairs: one to convert AA size to C size and one to convert C to D size. Both may be used together to convert an AA to D size.


## Semiconductors

### Linear IC's

LM301AN	DIL version	61-03011	0.44
LM308CN	DIL version	61-03081	0.65
LM311CN	Popular comparator	61-00311	0.46
LM324	Low power quad op amp	61-03240	0.67
LM339N	Low power quad comparator	61-03390	0.68
LM346	Programmable quad op amp	61-00346	3.72
LF347	Quad Bi-FET op amp	61-00347	1.82
LM348	Quad 741 type op amp	61-03480	1.26
LF351	Bi-FET op amp	61-03510	0.49
LF353	Dual version of LF351	61-03530	0.76
LM380N	1W AF power amp	61-00380	1.00
NE555N	Multi-purpose low cost timer	61-05550	0.45

# for a better service.

NE556N	Dual version of the 555	61-05560	0.50
uA741CN	DIL low cost op amp	61-07411	0.22
uA747CN	Dual 741 op amp	61-07470	0.70
uA748CN	741 with external frequency comp	61-04780	0.40
HA1388	18W PA from 14V	61-01388	2.75
TDA2002	8W into 2 ohms power amp	61-02002	1.25
ULN2283	1W max. 3-12V power amp	61-02283	1.00
MC3357	Low power NBFM IF system and detector	61-03357	2.85
ULN3859	Low current dual conversion NBFM IF and detector	61-03859	2.95
LM3900	Quad norton amp	61-39000	0.60
LM3909N	8-pin DIL LED flasher	61-39090	0.68
KB4445	Radio control 4 channel encoder and RF	61-04445	1.29
KB4446	Radio control 4 channel receiver and decoder	61-04446	2.75
ICM7555	Low power CMOS version of timer	61-75550	0.98
ICL8038CC	Versatile AF signal generator with sine/square/triangle OP's	61-08038	4.50
TK10170	5 channel version of KB4445	61-10170	1.87
HA12002	Protection monitor system for amps, PSU's, TX's etc	61-12002	1.22
HA12017	83dB S/N phono preamp 0.001% THD	61-12017	0.80
MC14412	300 baud MODEM controller (Eduro/US specs)	61-14412	6.85

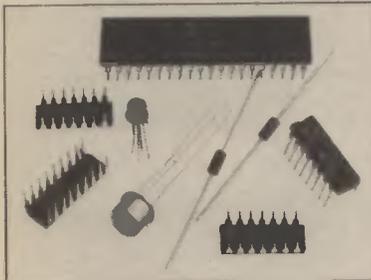

## Microprocessor & Memories

Z80A	Popular and powerful 8-bit CPU	26-18400	3.40
Z80AP10	2 port parallel input/output	26-18420	2.95
Z80A CTC	4 channel counter/timer	26-18430	2.90
Z8671	Z8 Micro comp. and Basic	26-08671	17.50
6116-3	16K (2Kx8) CMOS RAM 200ns	26-36116	6.68
Z6132-6	32K (4Kx8) quasi RAM 350ns	26-06132	15.00
4116-2	16K (16Kx1) 150ns	26-24116	1.59
2764	64K (8Kx8) 450ns	26-02764	9.50
2732	32K (4Kx8) 450ns	26-02732	5.70

## Voltage Regulators

7805	5V 1A positive	27-78052	0.40
7812	12V 1A positive	27-78122	0.40
7815	15V 1A positive	27-78152	0.40
7905	5V 1A negative	27-79052	0.49
7912	12V 1A negative	27-79122	0.49
7915	15V 1A negative	27-79152	0.49

## Transistors

BC182	General purpose	58-00182	0.10
BC212	General purpose	58-00212	0.10
BC237	Plastic BC107	58-00237	0.08
BC238	Plastic BC108	58-00238	0.08
BC239	Plastic BC109	58-00239	0.08
BC307	Complement to BC237	58-00307	0.08
BC308	Complement to BC238	58-00308	0.08

BC309	Complement to BC239	58-00309	0.08
BC327	Driver/power stage	58-00327	0.13
BC337	Driver/power stage	58-00337	0.13
MPSA13	NPN Darlington	58-04013	0.30
MPSA63	PNP Complement to MPSA13	58-04063	0.30
J310	JFET for HF-VHF	59-02310	0.69
J176	JFET analogue switch	59-02176	0.65
3SK51	Dual gate MOSFET-VHF amp	60-04051	0.60
3SK88	Dual gate MOSFET-Ultra lo noise	60-04088	0.99
TIP31A	Output stage	58-15031	0.35
TIP32A	Complement to TIP31A	58-15032	0.35
VN66AF	VMOS Power FET	60-02066	0.95
ZTX3866	E-line version 2N3866	58-03866	0.45
IN4001	Rectifier diode	12-40016	0.06
IN4002	Rectifier diode	12-40026	0.07
IN4148	General purpose silicon	12-41486	0.05

## Silicon Controlled Rectifiers

BRY55-100	100V 8A	52-55100	0.50
C106DI	400V 4.0A	52-00106	0.70
C122DI	400V 8.0A	52-00122	1.45

## 3mm Diameter LEDs

V178P	Red	15-01780	0.15
V179P	Green	15-01790	0.16
V180P	Yellow	15-01800	0.18

## 5mm Diameter LEDs

CQY40L	Red	15-10400	0.12
CQY72L	Green	15-10720	0.15
CQY74L	Yellow	15-10740	0.15


## Infra-Red LEDs

CQY99	Emitter	15-10990	0.56
BPW41	Detector	15-30410	1.51

## Tri Colour LED

V518	Orange-Green-Yellow	15-05180	0.60
------	---------------------	----------	------

## Capacitors

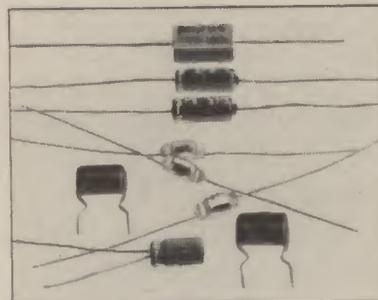

## Aluminium Electrolytics Radial PCB Mounting

10u	16V	05-10606	Pack of 4	0.24
47u	16V	05-47606		0.28
47u	25V	05-47607		0.28
470u	6.3V	05-47705		0.36
470u	16V	05-47706		0.48

## Tantalum Beads

1uF	35V	05-10501	Each	0.18
10uF	16V	05-10601		0.28
47uF	6.3V	05-47601		0.45
47uF	16V	05-47602		0.92

## Monolithic Capacitors

		Pack of 3
1n	04-10204	0.39
10n	04-10304	0.42
100n	04-10404	0.45


## Low Voltage Disc Cermaic

		Pack of 5
1n	04-10203	0.20
10n	04-10303	0.20

## Polyester (C280)

		Pack of 3
10n	04-10305	0.18
47n	04-47305	0.24
100n	04-10405	0.24
470n	04-47405	0.51
1uF	04-10505	0.66

## R F Components

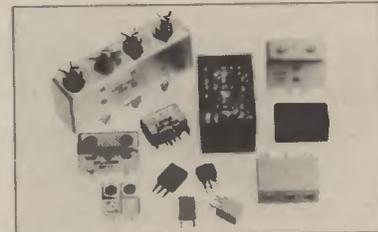

## Filters

### CFU/LFB CFW/LFH SERIES

Miniature 455kHz filters. I/P and O/P impedance 2K.

	-6dBW	-40dBW		
LFB6/CFU455H	6kHz	18kHz	16-45512	1.95
LFB12/CFU455F	12kHz	26kHz	16-45515	1.95
LFH6S/CFW455HT	6kHz	14kHz	16-45525	2.45
LFG12S/CFW455FT	12kHz	22kHz	16-45528	2.45
CFM2455A	Mechanical IF Filters for 455kHz		19-45530	0.77

## Crystal Filters 2 Pole Types

10M15A	10.7 Centre Freq.	20-10152	2.10
10M08AA	10.695 Centre Freq.	20-11152	3.49

## Inductors

We offer the complete Toko range of fixed and variable inductors. Over 500 coils from audio to V.H.F. See catalogue for details.

## Soldering Irons (Antex)

CS240	Iron 240VAC 17 Watts	54-22300	5.20
XS-240	Iron 25W 240V High heat capacity	54-22500	5.40
SK6	Presentation pack of one XS-240 with ST4 stand	54-22510	7.20
MLXS	Handy 12V 15W soldering iron complete with crocodile clips and solder	54-20004	5.60

Please add 15% VAT to all advertised prices and 60p post and packing. Minimum order value £2 please. We reserve the right to vary prices in accordance with market fluctuation.



**METERS: 110 x 82 x 35mm**  
30µA, 50µA, 100µA. **£6.90**  
Post 50p.

**METERS: 45 x 50 x 34mm**  
50µA, 100µA, 1mA, 5mA, 10mA,  
25V, 1A, 2A, 5A 25V.  
**£3.54.** Post 30p.

**METERS: 60 x 47 x 33mm**  
50µA, 100µA, 1mA, 5mA, 10mA,  
100mA, 1A, 2A, 25V, 50V,  
50-0-50µA, 100-0-100µA. **£6.04.**  
VU meters **£6.04.**  
Post on above meters 30p.

**Silicone grease 50g £1.32.**  
Post 16p.

**NI-CAD BATTERY CHARGER**

Led indicators charge-test switch. For PP3, HP7, HP11 & HP2 size batteries.  
Price **£5.85.** Post 94p.

**Motorola Piezo Ceramic Tweeter**  
**£5.20** Post 33p

T.V. UHF Aerial Amplifier 300-890MHz **£6.03** post 57p  
Desoldering Pump **£4.25** post 27p  
Resistance Substitution Box **£3.97** post 17p  
Vernier Dial 50mm Dia. **£2.31** post 17p  
Tape Head Demagnetizer **£2.60** post 39p  
Min. Buzzer 6 or 12V **63p** post 21p

**TRANSFORMERS 240v Primary**

3-0-3v	100mA	<b>82p</b>
6-0-6v	100mA	<b>£1.20</b>
6-0-6v	250mA	<b>£1.33</b>
12-0-12v	50mA	<b>£1.13</b>
12-0-12v	100mA	<b>£1.21</b>
9-0-9v	75mA	<b>£1.20</b>
9-0-9v	250mA	<b>£1.37</b>

Post on above transformers 48p.

9-0-9v	1A	<b>£2.05</b>
12-0-12v	1A	<b>£2.52</b>
15-0-15v	1A	<b>£3.11</b>
6-0-6v	1½A	<b>£2.20</b>

Post on above transformers 94p.

**Rotary Switches: 1 Pole 12 Way 2P6W, 3P4Way, 4P3W** **42p**  
Post 16p

**Illuminated Rocker Switch 240V 6A Red** **88p** Post 16p

All above prices include V.A.T. Send £1 for a new comprehensive 1983/84 fully illustrated catalogue with a new price list. Send S.A.E. with all enquiries. Special prices for quantity on request.  
*All goods despatched within 3 days from receipt of the order.*

**M. DZIUBAS**  
158 Bradshawgate, Bolton,  
Lancs. BL2 1BA.

**ELECTROVALUE**

Your SPECIALIST SUPPLIERS for  
**CONNECTORS**



Not only will you find a wide selection of all the usual types you may require in our A-Z products list; there are also many others made necessary by today's ever-advancing electronics - just one more example of how much better Electrovalue serves you.

Please mention this journal when getting in touch with Electrovalue

**D SERIES CONNECTORS**

9, 15, 25, 37 or 50 way connectors with corresponding covers and retainers. Gold-plated contacts. Max current per contact - 5A.

**ID CONNECTORS**

For connecting ribbon cable to PCBs. Insulation Displacement Type: 16, 20, 26, 34 or 40 way. 1A per contact. Straight or right angle plug fitting; cable socket has strain relief.

**RPC CONNECTORS**

5 way and 7 way chassis plus and sockets. DIN style layout. Gold-plated pins 250V/5A rating per socket.

**OTHER TYPES**

Edge connectors, DIN, jack plugs and sockets, phono, XLR, BNC, UHF and power.

**BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 36 PAGE A-Z LIST**  
ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

**ELECTROVALUE LTD**

28 St. Jude's Road  
Englefield Gm, Egham  
Surrey TW20 0HB

Phone (0784) 33603. Telex 264475

North: 680 Burnage Lane, Manchester (061) 432 4945

EV Computing Shop: 700 Burnage Lane, Manchester (061) 431 4866

ACCESS AND  
BARCLAYCARD  
Phoned Orders  
Welcome

Fig 1, B.F.

**MASTER ELECTRONICS NOW!**  
The **PRACTICAL** way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY  
**THIS IS THE AGE OF ELECTRONICS!**  
the world's fastest growth industry...

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer. All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



**British National Radio & Electronics School Reading, Berks. RG1 1BR**

**FREE!**  
COLOUR  
BROCHURE

Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

Post now to:

**British National Radio & Electronics School Reading, Berks. RG1 1BR**

BLOCK CAPS PLEASE



OR TELEPHONE US  
0734 51515 OR  
TELEX 22758  
(24 HR SERVICE)

# Rapid Electronics

MAIL ORDERS:  
Unit 3, Hill Farm Industrial Estate,  
Boxted, Colchester, Essex CO4 5RD.  
Tel. Orders: Colchester (0206) 36412.  
Telex: 987756.

ACCESS AND  
**BARCLAYCARD**  
WELCOME

### MIN. D CONNECTORS

9 way	15 way	25 way	37 way
Plugs solder lugs	60p	85p	125p
Right angle	120p	180p	240p
Sockets lugs	90p	130p	195p
Right angle	160p	210p	290p
Covers	100p	90p	110p



### SOLDERING IRONS

Anies CS 17W Soldering iron	495
2.3 and 4.7mm bits to suit	85
CS 17Wor XS 25W element	210
Anies XS 25W	525
3.3 and 4.7mm bits to suit	85
Solder pump/desoldering tool	480
Spare nozzle for above	70
10 metres 22awg solder	100

### CONNECTORS

DIN Plug Skt Jack	Plug Skt
2 pin 9p	2.5mm 10p 10p
3 pin 12p	3.5mm 9p 9p
5 pin 13p	11p Standard 16p 20p
Phono 10p 12p Stereo	24p 25p
1mm 12p 13p 4mm	18p 17p

CR106D	30
400V BA	70
400V 12A	95

### VOICE SYNTHESISER!

Now your computer can talk.  
The GI SP0256 speech processor is able through stored program to synthesise speech. Allophone (extended phoneme) system gives unlimited vocabulary.  
Easily interfaced with any digital system. TTL compatible signals are used to select the allophones.  
SP0256AL2 . 550 Data: 50p.

### VERO

Verobloc 4	375
Verobloc Size 0.1 matrix	
2.5 x 1	22
2.5 x 3.75	75
2.5 x 5	85
3.75 x 5	95
New size 3.75 x 17	330
VO board	415
Veropins per 100:	
Single sided	160
Double sided	60
Spot face cutter	130
Pin Insertion tool	162
Wiring pen	330
Spare spool 75p	6

### SWITCHES

Submit toggle	
SPST 55p, SPDT 60p, DPDT 65p.	
Miniature toggle	
SPDT 80p, SPDT centre off 90p, DPDT 90p, DPDT centre off 100p.	
Standard toggle:	
SPST 35p, DPDT 48p	
Miniature DPDT side 14p.	
Push to make 14p	
Push to break 22p	
Rotary type adjustable stop.	
1P12W, 2P6W, 3P4W all 55p each.	
DIL switches:	
4SPST 90p, 6SPST 80p, 8SPST 100p.	

### MICRO

6116P3	600	6852	240	8228	220
8502CPU	325	6875	495	8251	320
6522VIA	295	6880	100	8253	390
6521ACIA	650	81L395	85	8255	225
81L396	85	81L396	85	8259	390
6800CPU	220	81LS97	85	MC1488	55
6802CPU	250	80B0A	250	MC1489	55
6809CPU	620	80B5AC	340	Z80A CPU	290
8105	350	Z80APIO	260		
2732	440	8810RAM	115	8156	350
2764	680	6821	140	8212	110
2764	600	6840	360	8216	100
4116P20	85	6850	110	8224	120

### SOCKETS

8 pin	6p	28p
14 pin	8p	45p
16 pin	9p	55p
18 pin	12p	60p
20 pin	13p	68p
22 pin	16p	75p
24 pin	18p	82p
28 pin	23p	95p
40 pin	25p	135p

### COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. **AW 5% Resistor Kit.** Contains 10 of each value from 4.7ohms to 1M (total 530)  
**Capacitor Kit.** 5 of each value - 22p to 0.01u (135 caps) 370  
**Polyester Cap. kit.** 5 of each value from 0.01 to 1uF (65 caps) 575  
**Preset kit.** Contains 5 of each value from 100ohms to 1M (total 425)  
**65 Presets**  
**Nut and Bolt kit (total 300 items):** 180p  
25 6BA 1/2" bolts 50 6BA washers 50 6BA nuts  
25 6BA 3/4" bolts 25 4BA 1/2" bolts 50 6BA washers  
25 6BA nuts

### LINEAR

555CMOS	80	ICL7106	680
555CMOS	150	ICL7611	95
709	25	ICL7621	180
741	14	ICL7622	180
748	15	ICL8038	295
9400CJ	350	ICL8211A	200
AY-3-1270	70	ICM7224	785
AY-3-1800	370	ICM7555	80
AY-3-8912	540	LF351	48
CA3046	60	LF353	85
CA3080	95	LM309	90
CA3089	190	LM10	325
CA3090A	375	LM301A	50
CA3130E	85	LM311	70
CA3140E	36	LM318	120
CA3151E	100	LM319	200
CA3189	290	LM3342	100
CA3240E	100	LM3352	125

LM339	40	LM3911	120	NE566	140	TLO64	96
LM348	60	LM3914	225	NE567	100	TLO71	30
LM358	50	LM3916	225	NE570	370	TLO72	45
LM377	10	LM13500	16	NE571	370	TLO74	95
LM381	120	MC3340	135	PC4158	55	TLO81	28
LM382	120	MC3340	135	PC4356	40	TLO82	45
LM384	130	ML922	400	SL480	170	TLO84	90
LM386	90	ML924	195	SL7601B	150	UA2240	120
LM387	120	ML925	210	SN76477	380	ULN2003	70
LM393	40	ML926	140	SP0256AL2	550	ULN2004	70
LM397	25	ML927	140	TBA1205	70	XR2206	290
LM711	60	ML928	140	TB8A00	75	ZNA14	80
LM725	350	ML929	140	TB8A10	95	ZNA23	135
LM733	75	MM5387A	465	TB8A20	70	ZNA24	135
LM741	14	NE529	225	TB8A50	220	ZNA25E	350
LM747	60	NE531	140	TDA1008	320	ZNA26E	300
LM1458	40	NE544	205	TDA1022	450	ZNA27E	600
LM2917	200	NE555	16	TDA1024	125	ZNA28E	410
LM3900	40	NE566	45	TLO61	40	ZNA29	285
LM3911	120	NE565	110	TLO62	60	ZNA30E	200

### TRANSISTORS

BC126	30	BC149	9	BC548	7	BF494	23	TIP29A	30	ZTX109	12	ZN3442	120
BC127	30	BC158	10	BC549	10	BF498	23	TIP29B	35	ZTX110	12	ZN3702	8
BC128	30	BC159	8	BC550	10	BF499	23	TIP29C	37	ZTX111	16	ZN3703	8
BC176	25	BC160	45	BCY72	18	BF585	25	TIP30A	35	ZTX112	16	ZN3704	8
BC187	22	BC186C	10	BD115	15	BF586	28	TIP30B	50	ZTX113	16	ZN3705	9
BC188	22	BC189C	10	BD131	35	BF587	25	TIP30C	37	ZTX114	16	ZN3707	10
AD142	120	BC170	8	BD132	35	BF588	25	TIP31C	37	ZTX150	15	ZN3708	10
AD149	80	BC171	10	BD133	50	BF589	25	TIP32A	35	ZTX151	15	ZN3709	10
AD181	40	BC172	8	BD135	40	BFY50	23	TIP32C	37	ZTX152	18	ZN3712	170
AD182	40	BC177	18	BD136	40	BFY51	20	TIP33A	50	ZTX153	25	ZN3713	195
AF124	60	BC178	18	BD137	30	BFY52	23	TIP33B	75	ZTX154	20	ZN3719	20
AF125	40	BC179	18	BD138	30	BFY53	32	TIP34A	60	ZTX155	40	ZN3820	65
AF139	40	BC182	10	BD139	38	BRY39	40	TIP35A	105	ZTX156	20	ZN3823	65
AF186	70	BC182L	8	BD140	20	BSX20	20	TIP35B	125	ZTX157	20	ZN3866	90
AF239	75	BC183	10	BD204	110	BSX29	35	TIP35C	125	ZTX158	20	ZN3903	10
BC107	10	BC183L	10	BD205	100	BSY95A	25	TIP36A	125	ZTX159	22	ZN3904	10
BC108	12	BC184	10	BD222	85	BSY95B	25	TIP36B	135	ZTX161	30	ZN3905	8
BC108C	12	BC184L	7	BF180	35	BU205	160	TIP36C	135	ZTX162	30	ZN3906	8
BC108H	12	BC212	10	BF182	35	BU206	180	TIP36D	135	ZTX163	30	ZN3907	8
BC108L	12	BC212L	10	BF184	25	MJ2550	30	TIP36E	135	ZTX164	30	ZN3908	8
BC109	10	BC213	10	BF185	25	MJ2958	30	TIP36F	135	ZTX165	30	ZN3909	8
BC109C	12	BC213L	10	BF194	12	MJ3040	30	TIP36G	135	ZTX166	30	ZN3910	8
BC114	18	BC214	10	BF195	12	MJ3055	30	TIP36H	135	ZTX167	30	ZN3911	8
BC115	22	BC214L	8	BF196	12	MJE3052	70	TIP36I	135	ZTX168	30	ZN3912	8
BC117	18	BC237	8	BF197	12	MPF102	10	TIP36J	135	ZTX169	30	ZN3913	8
BC119	35	BC238	14	BF198	10	MPF104	40	TIP36K	135	ZTX170	30	ZN3914	8
BC137	40	BC308	12	BF199	18	MPSA05	22	TIP36L	135	ZTX171	30	ZN3915	8
BC139	40	BC327	14	BF200	30	MPSA06	25	TIP36M	135	ZTX172	30	ZN3916	8
BC140	28	BC328	14	BF201	30	MPSA07	25	TIP36N	135	ZTX173	30	ZN3917	8
BC141	30	BC337	14	BF202	30	MPSA08	25	TIP36O	135	ZTX174	30	ZN3918	8
BC142	25	BC338	14	BF258	45	MPSA09	30	TIP36P	135	ZTX175	30	ZN3919	8
BC143	25	BC477	8	BF259	32	MPSA10	30	TIP36Q	135	ZTX176	30	ZN3920	8
BC147	8	BC478	30	BF259	35	MPSU06	55	TIP36R	135	ZTX177	30	ZN3921	8
BC148	8	BC479	30	BF259	35	MPSU06	55	TIP36S	135	ZTX178	30	ZN3922	8

BC517	40	BF337	40	MPSU66	60	ZTX108	10	ZN3055	50
BC547	7	BF480	23	TIP29A	30	ZTX109	12	ZN3442	120
BC548	7	BF494	23	TIP29B	35	ZTX110	12	ZN3702	8
BC549	10	BF498	23	TIP29C	37	ZTX111	16	ZN3703	8
BC550	10	BF499	23	TIP30A	35	ZTX112	16	ZN3704	8
BCY72	18	BF585	25	TIP30B	50	ZTX113	16	ZN3705	9
BCY77	18	BF586	28	TIP30C	37	ZTX114	16	ZN3707	10
BD115	15	BF587	25	TIP31C	37	ZTX150	15	ZN3708	10
BD131	35	BF588	25	TIP32A	35	ZTX151	15	ZN3709	10
BD132	35	BFY50	23	TIP32C	37	ZTX152	18		


### BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm  
● Belt driven ● Aluminium platter ● Precision  
calibrated counter balance ● Anti-skate (bias  
device) ● Damped cueing lever ● 240 volt AC  
operation (Hz) ● Cut-out template supplied ●  
Completely manual arm. This deck has a com-  
pletely manual arm and is designed primarily  
for disco and studio use where all the advan-  
tages of a manual arm are required.  
Price £33.60 each, £2.50 P&P


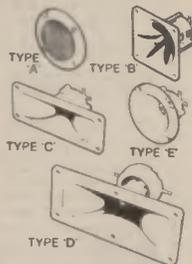
### PIEZO ELECTRIC TWEETERS — MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.




**TYPE 'A'** (KSN2036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each + 30p P&P  
**TYPE 'B'** (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each + 30p P&P.  
**TYPE 'C'** (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each + 30p P&P.  
**TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each + 30p P&P.  
**TYPE 'E'** (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each + 30p P&P.

**LARGE S.A.E.**  
For details of  
disco mixers,  
speakers, kits,  
amp - modules,  
burr alarms,  
turntables, etc.

### OMP POWER AMPLIFIER MODULE

READY BUILT

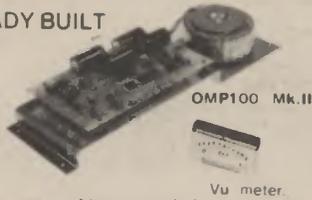

OMP100 Mk II

Vu meter.

New model.  
Improved specification

**NEW OMP100 Mk II POWER AMPLIFIER MODULE** Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

**SPECIFICATION**  
Output Power:— 110 watts R.M.S.  
Loads:— Open and short circuit proof 4/16 ohms.  
Frequency Response:— 15Hz - 30KHz - 3dB  
T.H.D.:— 0.01%  
S.N.R. (Unweighted):— 118dB ± 3.5dB  
Sensitivity for Max Output:— 500mV at 10K.  
Size:— 360 X 115 X 72mm Price:— £31.99 + £2.50 P&P. Vu Meter Price:— £8.50 + 50p P&P

MOS-FET  
HIGH SPEC.  
MODULES

MOS-FET VERSIONS AVAILABLE UP TO 300 W. R.M.S.  
100 Watt 300mm X 123mm X 60mm Price: £39.99 + £2.50 P&P.  
200 Watt 300mm X 150mm X 100mm Price: £62.99 + £3.50 P&P.  
300 Watt 330mm X 147mm X 102mm Price: £79.99 + £4.50 P&P.

### PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

**FM MICROTRANSMITTER (BUG)** 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P.

**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £13.74 + 75p P&P.

**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82. Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.27 P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★

## B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
ESSEX. SS2 6TR TEL 0702-527572



# KITS FROM £7 ...TO £60

## Sparkrite

Buy Sparkrite Brand Leading Auto Electronics  
in self-assembly kit form — And save pounds!!

- Electronic Ignition systems — contact triggered and contactless
- Electronic Car Security Systems — including a new ultrasonic unit
- Car Drive Computer — with 12 functions

SEND FOR FREE LITERATURE PACK — TODAY!

8 SOPHISTICATED  
KITS TO CHOOSE  
FROM.



To:

SPARKRITE (A Division of Stadium Ltd.), Queensway, Enfield, EN3 4SD.  
Telephone: 01-804 4343

NAME .....

ADDRESS .....

EE7

### MOTORIZED GEARBOX

As featured in 'Computer Control of Small Vehicles' in May issue. Complete set of components (not PCB) + Gearbox & Wheels (as recommended by the authors) for £37.



These units are as used in a computerized tank, and offer the experimenter in robotics the opportunity to buy the electro-mechanical parts required in building remote controlled vehicles. The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors etc. £5.95. Suitable wheels also available: 3" Dia plastic with blue tyre, drilled to push-fit on spindle. 2 for £1.30 (limited qty). 3" dia aluminium disc 3mm thick, drilled to push-fit on spindle. 2 for 68p.

### NICAD CHARGERS

Versatile unit for charging AA, C, D and PP3 batteries. Charge/test switch, LED indicators at each of the 5 charging points. Mains powered. 210 x 100 x 50mm £7.95.  
Model A124. Unit plugs directly into 13A socket, and will charge up to 4 AA cells at a time. Only £4.80.

### NI-CAD BATTERIES

AA size 99p each; C size 199p; D size 220p; PP3 size 395p.  
SPECIAL!! 6 x 'D' size, only £11.00!!

### THE 1984 GREENWELD 84 PAGE CATALOGUE NOW AVAILABLE!!

It's Bigger, Brighter, Better, more components than ever before. With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00!

### PACKS! PACKS! PACKS!

**K517 Transistor Pack.** 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114, 117, 172, 182, 183, 198, 239, 251, 214, 225, 320, BF198, 255, 394, 2N3904 etc etc. Retail cost £7+. Special low price 275p

**K530 100 Assorted polyester caps** — all new modern components, radial and axial leads. All values from 0.01 to 1uf at voltages from 63 to 1000V! Super value at 395p

**K541 It's back!!** Our most popular pack ever — Vero outcuts. This has been restricted for some time, but we have now built up a reasonable stock and can once again offer 100 sq ins of vero copper clad outcuts, average size 4x3". Offered at around 1/3 the price of new board 320p

**K523 Resistor Pack.** 1000 — yes, 1000 1/2 and 1/2 watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several megohms. Only 250p. 5000 £10; 20,000 £36.

**K520 Switch Pack.** 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p

Official orders welcome — minimum invoice charge £10. No. min. on CWO.

Our shop has enormous stock of components and is open from 9.5.30 Mon-Sat. Come & see us!!


**GREENWELD**  
443D Millbrook Road Southampton  
SO1 0AK Tel (0703) 772801/783740  
ALL PRICES INCLUDE VAT. JUST ADD 80p P&P

## PREVIOUSLY ADVERTISED STILL AVAILABLE

Tape punch and reader	£22.50
Bench isolating transformer 250 watt	£7.75
BOAC in-flight stereo unit	£1.50
Drill assortment 4 each 25 sizes between .25mm & 2.5mm	£11.50
Battery condition tester, less box	£1.75
Nicad chargers, mains	£0.75
Flourescent inventor 13 watt from 12v	£3.50
Ten digit stitch pad-pb phone etc.	£1.95
Uniselect 2 pole 25 way	£4.60
Water valve mains operated	£2.50
Counter 6 digit mains operated	£1.15
ditto 12v resettable	£3.45
Double glazing clear PVC sheet, 23% wide-per running ft.	£0.15
Locking mechanism with 2 keys	£1.15
Magnetic Clutch	£4.50
Mouth operated suck or blow switch	£2.30
Solenoid with slug 8-12v battery op.	£1.82
ditto 230v mains	£2.30
Timer Omron STP NH 110v AC Coil	£6.90
Key switch with 2 keys dp mains	£1.75
Air valve mains operated	£3.75
Latching relay mains operated	£3.50
Dry film lubricant aerosol can	£0.65
Coin op switch, cased with coin tray	£4.60



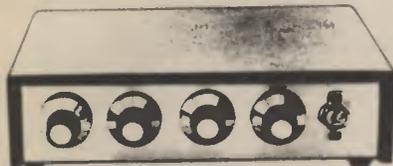**8 POWERFUL MODEL MOTORS (all different)**  
for robots, meccanos, drills, remote control planes, boats, etc. £2.95.



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

### 12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle — Price £3.45.  
Ditto, but double ended £4.25.  
Ditto, but permanent magnet £3.75.



### EXTRA POWERFUL 12v MOTOR

Probably develops up to 1/2 h.p. so it could be used to power a go-kart or to drive a compressor, etc. £7.95 + £1.50 post.

### THERMOSTAT ASSORTMENT

10 different thermostats, 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

### MINI MONO AMP

on p.c.b., size 4" x 2" (app.)  
Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms.  
More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



### — BARGAIN OF THE YEAR —

#### The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 270 KHz, medium wave band 525 — 1650KHz, FM band 87 — 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00**  
+ £1.50 post + insurance.

## THIS MONTH'S SNIP

Hi Fi sound from your Spectrum 1 watt amp — pm speaker & instructions £2.45

**REVERSIBLE MOTOR with control gear** Made by the famous Franco Company this robust motor is approx 7 1/2" long, 3 1/2" dia. 3/8" shaft. Very powerful, almost impossible to stop. Ideal for operating stage curtains, doors, ventilators, etc. Even garage doors if properly balanced. Offered complete with control gear as follows:  
1 Franco motor with gear box 1 push to start switch  
1 manual reversing & on/off switch 2 limit stop switches  
1 circuit diag. of connections **ONLY £19.50 + postage £2.50.**

### FOR SOMEONE SPECIAL

Why not make your greeting card play a tune? It could play 'Happy Birthday', 'Merry Christmas', 'Wedding March', etc. or 'Home Sweet Home', etc. Wafer thin 3 part assemblies, for making cards musical. Mini microchip speaker and battery with switch that operates as the card is opened. Please state tune when ordering. Complete, ready to work £1.25.

### JOYSTICK

**WHY PAY £10 OR MORE** — Make yourself a Joystick — full details were given in Dec/Jan 'Sinclair Projects'. We will supply complete kit for £2.30. Although designed for the Spectrum or ZX81 it is equally suitable for any home computer.

### TELEPHONE ITEMS (ex-GPO)

Plug and Wall socket — 4 pin or 5 pin	£3.45
Plugs only 4 pin or 5 pin	£1.15
Modern desk telephone	£7.50
Heavy black old type	£5.50
External bell unit	£8.50
Bell ringing power unit	£8.50
Pick up coil	£1.15

### STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) — Ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation .1% with input variations up to 20% — load regulation 1% from no load to full load — or full load to no load. Complete in heavy duty case — Models available: 5v - 9A £23. 12v - 1.5A £13.25. 15v - 1.2A £13.25. 24v - 2A £23.

### PRESTEL UNIT

— brand new and complete except for 7 plug in IC's — Price: £19.75 + £2.00 p&p.  
Note: British Telecom may not connect this equipment as there is no manufacturer to guarantee it, however it is well worth buying for its immense breakdown value — sold originally at over £150.



### 25A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you wake — switch on lights to ward off intruders — have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. Independent 60 minute memory jogger. A beautiful unit at £2.50.



### BELLS & ALARMS

Hooter/Siren 6v - 12v	69p
Loud, med & soft buzzer	75p
Open buzzer ex G.P.O.	50p
12" Gong cast iron cased ALARM BELL 12v dc	£19.50
6" Gong 12v dc	£7.50
6" Gong mains	£8.50

## 50 THINGS YOU CAN MAKE

Things you can make include: Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc., and you will still have hundreds of parts for future projects. Our 10Kg parcel contains not less than 1,900 items — panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

**YOURS FOR ONLY £11.50 plus £3.00 post.**

### TELEPHONE & INTERCOM CABLES

15 conductors colour coded 200m coil	£59.00
10 conductors colour coded 200m coil	£39.00
Flex extension lead twin rubber	
5mm ideal grass cutters etc. 250m coil	£25.00
50 meter coil	£5.75

### MAINS TRANSFORMERS

4 volt 4 amp	£1.75	24 volt 4 amp	£4.85
6 volt 1 amp	£1.15	25 volt 1 amp	£2.25
12 volt 1/2 amp	£1.15	35 volt 2 amp	£3.95
12 volt 1/4 amp	£1.55	38 volt 2 1/2 amp	£4.95
12 volt 1 amp	£1.75	26 volt 10 amp	£9.95
15 volt 2 amp	£3.45	50 volt 2 amp	£5.50
15 volt 4 amp	£4.60	25.0.25 1/2 amp	£3.95
18 volt 1 amp	£1.95	12.0.12 2 amp	£4.95
20 volt 1 amp	£2.30	115v 100w auto	£3.95
24 volt 2 amp	£3.45	115v 250w auto	£5.75

## J. BULL (Electrical) Ltd.

(Dept. EE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from electric and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454553. Bulk orders: phone for quote. Shop open 9.00 — 5.30, mon to Fri, not Saturday.

### STORE CLOSING SALE

All stocks must go from one of our big warehouses, 10,000,000 items, everything from AERIALS to ZENER will be cleared at fantastically low prices — if you are a manufacturer you can save yourself a fortune — send for our Sale List, not for small buyers as minimum order £100.

### EXTRACTOR FANS — MAINS OPERATED

Woods extractor	
5" — £6.75, Post £1.25.	
6" — £6.95, Post £1.25.	
5" Plannell extractor	
£6.50, Post £1.25.	
4" x 4" Muffin 115v	
£4.50, Post 75p.	
4" x 4" Muffin 230v.	
£5.75, Post 75p.	
All the above ex-computer, those below are unused.	
4" x 4" £8.50, Post 75p.	
9" American made	
£11.50, post £2.00.	
Tangential Blower 10x3	
air outlet, dual speed	
£4.60, Post £1.50.	



### LIGHTING & POWER CABLES

Made by Volex to BRITISH STANDARD SPECIFICATIONS

P.V.C. sheathed outer-copper clad conductors	
1.5mm flat twin 100 metres	£4.50
1.5mm flat 3 core BE metres	£11.00
8mm flat 3 core metres	£54.00
16mm flat twin BE metres	£115.00

### MINIATURE WAFER SWITCHES

2 pole, 2 way — 4 pole, 2 way — 3 pole, 3 way — 4 pole, 3 way — 2 pole, 4 way — 2 pole, 6 way — 1 pole, 12 way.	
All at 25p each or 10 for £2.00	



OTHER TYPES IN STOCK — PLEASE ENQUIRE

**BLEEP TONE** These work off 12v and have an unusual and pleasant bleep. 69p each.

**CONNECTING WIRE PACK** 96 lengths of connecting wire, each 1 metre long and differentially colour coded, a must for those difficult interconnecting jobs. 85p the lot.

**RED LEDS** 10 for 69p. 100 for £5.75. 1000 for £52.

**IN LINE SIMMERSTAT** Ideal heat controller for soldering iron and many other hand-held appliances. £2.30. 10 for £17.25.



### VENNER TIME SWITCH

Mains operated with 20 amp switch, on and on and off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic case — £1.75 or metal case — £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

Ex-Electricity Board. Guaranteed 12 months.

### IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included. £11.95 plus £2.00 post.

## OTHER POPULAR PROJECTS

Short Wave Set — covers all the short wave bands using plug-in coils. Kit complete	£14.50
R C Bridge Kit	£9.95
3 Channel Sound to Light — with fully prepared metal case.	£14.95
Ditto — made up	£25.00
Big Ear, listen through walls	£9.90
Robot controller — receiver/transmitter	£9.50
Ignition kit — helps starting, saves petrol, improves performance	£13.95
Silent sentinel Ultra Sonic Transmitter and receiver	£9.50
Car Light 'left on' alarm	£3.50
Secret switch — fools friends and enemies alike	£1.95
3 — 30v Variable Power Supply	£13.80
2 Short & Medium wave Crystal Radio	£3.99
3v to 16v Mains Power Supply Kit	£1.95
Light Chaser — three modes	£17.50
Mullard Unilux HiFi stereo amplifier with speakers	£16.75
Radio stethoscope — fault finding aid	£4.80
Mug stop — emits piercing squawk	£2.50
Morse Trainer — complete with key	£2.99
Drill control kit	£3.95
Drill control kit — made up	£6.95
Interrupted beam kit	£2.50
Transmitter surveillance kit	£2.30
Radio Mike	£6.90
FM receiver kit — for surveillance or normal FM	£3.50
Seat Belt reminder	£3.00
Car Starter Charger Kit	£15.50
Soil heater for plants and seeds	£16.50
Insulation Tester — electronic megger	£7.95
Battery shaver or fluorescent from 12v	£6.90
Matchbox Radio — receives Medium Wave	£2.95
Mixer Pre-amp — disco special with case	£16.00
Aerial Rotator — mains operated	£29.50
Aerial direction indicator	£5.50
40 watt amp — half 20Hz — 20KHz	£9.50
Microvolt multiplier — measure very low currents with ordinary multimeter	£3.95
Pure Sine Wave Generator	£5.75
Linea Power output meter	£11.50
115 Watt Amplifier 5Hz 25KHz	£13.50
Power supply for 115 watt amps	£8.50
Stereo Bass Booster, most items	£9.95

### HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting

- TDR300K Remote Control Dimmer £14.95
- MKB Transmitter for above £4.50
- TD300K Touchdimmer £7.75
- TS300K Touchswitch £7.75
- TDE/K Touch kit for 2-way switching for TD300K £22.50
- LD300K Rotary Controlled Dimmer £3.95



### DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. **Price £15.50**



### 3-NOTE DOOR CHIME

Based on the SA80600 IC, the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. An IDEAL PROJECT FOR BEGINNERS. Order as XK 102. **£5.50**

### ELECTRONIC LOCK KIT

With hundreds of uses in doors, garages, car anti-theft devices, electronic equipment etc. Only the correct easily changed four digit code will open it!

Requires a 5 to 15V dc supply. Output 750mA. Fits into standard electrical wall box. Complete kit (excl. front panel) XK101 **£11.50**

Electronic lock mechanism for use with the above kit. 70 150 **£14.95**

**WE ALSO STOCK A WIDE RANGE OF ELECTRONIC COMPONENTS**

SEE CATALOGUE FOR DETAILS

### MINI KITS

**MK1 ELECTRONIC THERMOSTAT** Uses LM3911 IC to sense temperature (80°C max) and track to switch heater (1KW). Mains powered. **£4.80**

**MK2 SOLID STATE RELAY** Switches 240V ac motors, lights, heaters from logic/computer circuits. Zero voltage switching, opto isolated. Supplied without track. **£2.80**

**MK4 PROPORTIONAL TEMPERATURE CONTROLLER** Uses 'burst fire' technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine making, etc. Max. load 3KW (240V ac). Temp. range up to 90°C. **£8.50**

**MK5 MAINS TIMER** Mains powered timer enabling a load up to 1KW at 240V ac to be switched on (or off) for a variable time from 20 mins to 25 hrs. Longer or shorter periods possible with minor component changes. **£6.50**

**MK16 DUAL LATCHED SOLID STATE RELAY** Comprises two MK2s with latch circuit enabling the MK12 kit to control two mains loads independently. Two output tracks not supplied. **£4.80**

**NEW! MK19 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

**MK15 DC CONTROLLED AUDIO AMPLIFIER** May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

### MICROPROCESSOR CONTROLLED MULTI-PURPOSE TIMER

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, eg. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it - the clock will do the rest.



**NOW ONLY £39.00**

- 7mm LED 12 hour display
- Day of week, am/pm and output status indicators
- 4 open collector outputs for driving relays, traps, etc.
- 50-60Hz mains operation
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
- Display blanking during power failure to conserve battery power.
- 18 programme time sets
- Powerful 'Everyday' function enabling output to switch every day but use only one time set
- Useful 'sleep' function - turns on output for one hour immediately or after a specified time interval.
- 20 function keypad for programme entry

Kit includes all components PCB, box, assembly and programming instructions. Order as CT8000.

**KT14 OPTIONAL RELAY KIT** Kit includes one relay PCB to accommodate up to 4 relays, terminal blocks, etc., to fit inside CT8000 box. Provides up to 4 3amp 240V AC changeover contacts. **£3.90**

Additional relays £1.85 each

**COMPONENT PACKS**

PACK 1 650 Resistors 47 ohm to 10 Mohm - 10 per value £4.00

PACK 2 40 x 10V Electrolytic Capacitors 10uF to 1000uF - 5 per value £3.25

PACK 3 60 Polyester Capacitors 0.01 to 1uF 250V 5 per value £5.95

PACK 4 45 Sub-miniature Presets 100 ohm to 1 Mohm - 5 per value £2.90

PACK 5 20 Low Profile IC Sockets B, 14 and 16 pin - 10 of each £2.40

PACK 6 25 Red LEDs (5mm dia) £1.50

### HOME CONTROL CENTRE

This kit enables you to control up to 16 different appliances by means of coded pulses in the mains wiring which may be decoded by special receivers anywhere in the house.

The transmitter may be controlled manually or by the computer interface enabling your favourite micro to make your coffee in the morning, switch lights anywhere in the house, or your electric blanket in your bedroom. Just think of the possibilities - and no wiring!

The Kit comprises a transmitter with pre-drilled box and two receivers.

**XK112 £42.00**

**ADDITIONAL RECEIVERS XK111 £10.00**

**XK103 £25**

**Extra transmitters XK105 £10.00**

**XK104 £25**

**Extra transmitters XK106 £10.00**

**XK107 £25**

**Extra transmitters XK108 £10.00**

**XK109 £25**

**Extra transmitters XK110 £10.00**

**XK111 £10.00**

**XK112 £42.00**

**XK113 £42.00**

**XK114 £42.00**

### DISCO LIGHTING KITS

**DL 1000K** This value for money kit features a bi-directional sequencer, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£15.95**

**DL2 1000K** A lower cost version of the above featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **£8.95**

Optional opto input DL A1 Allowing audio ('beat') - light response. **80p**

**DL3000K** This 3 channel sound to light kit features zero voltage switching, automatic level control and built-in time. No connections to speaker or amp required. No knobs to adjust - simply connect to mains supply and lamps (11W channel). **Only £12.95**

**24 HOUR CLOCK/APPLIANCE TIMER KIT** Switches any appliance up to 1kW on and off at preset times once per day. Kit contains: AY-51230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions. **£17.40**

CT1000K Basic Kit **£14.90**

CT1000K with white box (56/31 x 71mm) **£17.40**

(Ready Built) **£22.50**

**LCD 3 1/2 DIGIT MULTIMETER** 19 ranges including DC voltage (200mV to 1000V) and AC voltage, DC current (200mA to 10A) and resistance (10 - 2M) - NPN & PNP transistor gain and diode check. Input impedance 10M. Size 180 x 140 x 50mm. Complete with battery, test leads and carrying case. **ONLY £32.00**

**REMOTE CONTROL KITS** These kits have been designed to enable infra red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The exact application will determine the interface circuitry (not supplied) between the receiver and the device to be controlled. In many cases this could be a relay or triac. General instructions and applications are supplied with the kits. The kits are coded and provide a high degree of noise immunity and security.

**MK10 Transmitter Kit** For use with MK11 MK12 Receivers and MK3 10 1/2 keyboards. Requires PP3 battery. Size 8 1/2 x 1 1/2 cms. Range approximately 60M. **£6.80**

**MK11 Receiver Kit** Mains powered. Provides 10 latched plus 3 analogue outputs (one for controlling audio amplifiers, TV or lighting circuits where control of lamp brightness is required). **£13.50**

**MK13 Transmitter Keyboard** **£4.35**

**MK13 DC Controlled Stereo Amplifier Kit** If control of stereo amplifier is required, the MK13 may be used providing for remote control of base, treble and volume or balance. This kit also includes a one of 10 decoder with LEDs for remote selection of programme or channel. May be connected between the line amp and power amp sections of almost any audio amplifier. **£10.70**

**MK12 Receiver Kit** Mains powered. Provides up to 16 latched or momentary on/off outputs. The latched version is suitable for applications where only one of the 16 outputs is to be on at any one time eg. TV channel selection. The momentary version provides an output only during transmission. Lines may be latched separately if required (not supplied). This may be used in conjunction with the MK15 Dual Latched Solid State Relay to switch mains loads eg. radio lights, TV. **£13.50**

**MK12 (state latched or momentary)** **£13.50**

**MK9 8-way Transmitter Keyboard** **£1.90**

**MK10 16-way Transmitter Keyboard** **£5.40**

**MK15 Dual Latched Solid State Relay** **£4.50**

**SINGLE CHANNEL UNCODED INFRA RED KITS**

**MK6 Transmitter** - supplied with hand held pre-drilled box. Requires a 9V PP3 battery. Range approximately 20M. **£4.50**

**MK7 Receiver** Mains powered with track output to switch up to 500W at 240V ac. On/off momentary output available. **£10.50**

**MK16 Mains Powered Transmitter** For continuous operation such as burglar alarms, automatic door operators, etc. Range approximately 60M. May also be powered from 9V dc. **£3.50**

**MK17 12V d.c. Receiver** For use with MK6 or MK16. Relay output with DP3A change over contacts. May be used as latched, momentary or break beam receiver. Operates from 6 1/2V dc. **£10.50**

Send SAE 9" x 6" for our FREE YELLOW CATALOGUE. It's packed with a full list of our stock range all at very competitive prices.

Add 65p postage & packing + 15% VAT to total Overseas Customers; Add £2.50 (Europe), £6.00 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability.

**OPEN** 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)



**COMPUTER SHOWROOM TOP HARDWARE, LATEST SOFTWARE PERIPHERALS, ACCESSORIES AND MUCH, MUCH MORE!**

**FAST SERVICE - TOP QUALITY - LOW LOW PRICES**

No circuit is complete without a call to -

**TELE**

**ELECTRONICS**  
11-13 Boston Road  
London W7 3SJ

01-567 8910 ORDERS  
01-579 9794 ENQUIRIES  
01-579 2842 TECHNICAL AFTER 3PM



**ALL PRICES EXCLUDE VAT**

# EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 13 NO. 7 JULY 1984

**Editor**  
MIKE KENWARD

**Consultant Editor**  
FRED BENNETT

**Assistant Editors**  
DAVE BARRINGTON (Production)  
DAVID SHORTLAND (Technical)

**Technical Editor**  
MIKE ABBOTT

**Projects Editor**  
DAVID BRUNSKILL

**Technical Sub-Editors**  
RICHARD BARRON  
BRIAN BUTLER

**Art Editor**  
JACK POUNTNEY

**Assistant Art Editor**  
KEITH WOODRUFF

**Senior Technical Illustrator**  
JOHN PICKERING

**Technical Illustrator**  
ISABELLE GREENAWAY

**Editorial Offices**  
EVERYDAY ELECTRONICS EDITORIAL  
WESTOVER HOUSE  
WEST QUAY ROAD, POOLE, DORSET BH15 1JG  
Phone: Poole (0202) 671191  
We regret that lengthy technical enquiries  
cannot be answered over the telephone

**Advertisement Manager**  
DAVID TILLEARD 01-261 6676

**Secretary**  
CHRISTINE POCKNELL 01-261 6676

**Advertisement Sales Executives**  
ALFRED TONGE 01-261 6819  
RICHARD WILLETT 01-261 6865

**Classified Supervisor**  
BARBARA BLAKE 01-261 5897

**Advert Make-Up and Copy Department**  
JULIE FISH 01-261 6615

**Advertisement Offices**  
EVERYDAY ELECTRONICS ADVERTISEMENTS  
KING'S REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS  
Telex 915748 MAGDIV-G

#### Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope or international reply coupons.

We cannot undertake to engage in lengthy discussions on the telephone.

#### Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

#### NEW TECHNOLOGY


OVER THE years of my involvement with the electronics industry many high technology companies have spoken of the difficulties in getting business to accept new ideas and innovations. Of course there are a number of reasons, not the least being that hard headed businessmen need to know that the product is reliable, can be serviced quickly, will not be outdated as soon as they get it and will actually be of benefit to the company. Most of the above reasons take some time to establish and are, in my book, precisely the reasons that the new Sinclair QL will probably not become the business machine Sinclair are marketing it as.

There are, however, a couple of other reasons why new technology is not taken up more quickly. One of these is the poor back-up service, including supply delays and even over-pricing of replacements and add-ons by the suppliers. Many companies find more difficulties once the installations are in operation, simply because they are not flexible enough to reorganise operating procedures to make the best possible use of new equipment. This is often why things like "computer errors" occur on invoicing systems, etc. Take a recent outstanding example of lack of co-ordination within British Telecom—an organisation that does now appear to be moving with the times even though they have a long way to go yet. About a year ago we had a Prestel system in the editorial office, having discovered what we wanted to know about the system and found it rather cumbersome and of little value to the magazine (that is another story) we decided to have it taken out.

Both the installation, operation and removal were reasonably efficient and I felt that BT were just beginning to catch up with the service offered in countries like Canada—of which I have some experience. However, what followed after the removal of the service goes to show that they still need to rearrange some operating procedures and improve their own communications. We were billed for use of the system after its removal, followed by a reminder and a threat to bar our access to the service. Having telephoned the Prestel office each time we were promised things would be sorted out, but now, three months later, we have been billed for a further quarterly rental. Another phone call to Prestel followed by a further reminder and threat to bar our access if we do not pay within seven days.

Once again we called and were informed that the billing was done by a different department and that it would now be sorted out. We hope so, because it would be awful to be barred from a service we do not have! Incidentally we still get the Prestel Directory mailed to us as well.

What I hope, is that as a new generation of computer-oriented youngsters grows up and fills many jobs in the UK, such problems will be overcome. At least the next generation of businessmen will understand the technology, know that, used properly, it will make us more efficient and not be worried about unknown v.d.u. emissions making their hair fall out. With so many of you being computer users perhaps the future of UK industry will be bright.

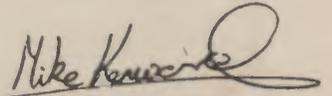

#### Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

#### Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.


#### Subscriptions

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £13.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

# electronic LOCK

## For mains operated equipment

W.D. PHILLIPS BSc PhD

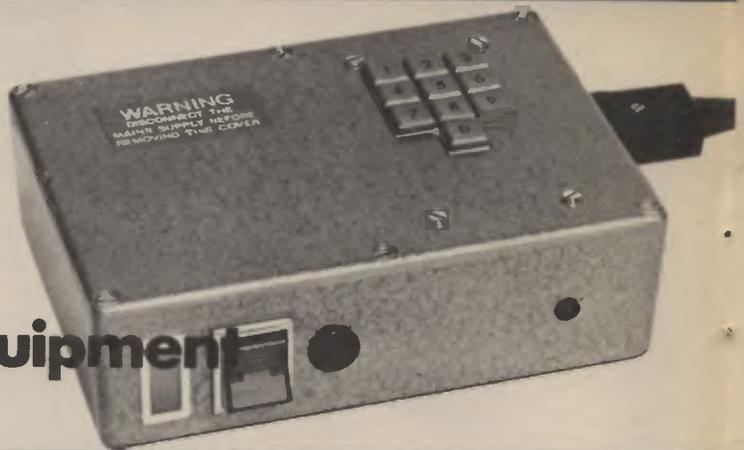

**T**HIS device is designed to prevent unauthorised use of mains-operated equipment up to 5A (1.2kW), including microcomputers, CB radio home-base stations, hi-fi systems and video recorders. The codelock unit is connected to the domestic mains supply as shown in Fig. 1. The correct 4-digit code must be entered using the keyboard before power is switched to the protected equipment by means of a 2-pole relay, switching both LIVE and NEUTRAL. The code is selected from 5040 possible combinations during construction and must be entered within a 5-second period in order to operate the device. Although the codelock gives good protection against casual misuse, it can be overcome by a determined person, prepared to cut and rewire the mains supply.

### CIRCUIT DESCRIPTION

Figure 2 gives the complete circuit diagram for the codelock. Almost all the work is done by a single integrated circuit, IC1. This is the LS7225 keyless lock i.c., as shown in Fig. 3.

An internal circuit (*power on reset*) sets the device to the "locked" condition when power is first applied. Pins 11-14 provide the 4-digit *sequence input*. Pressing S5

enters the first digit of the code by applying the positive supply voltage (logic 1) to pin 11. At the same time, C3 is charged to supply potential. C3 discharges slowly, the potential at pin 11 gradually declining as charge leaks away. When a critical level is reached, the internal *sequence detector* is reset.

With  $C3 = 1\mu\text{F}$  and  $V_{SS} = 12\text{V}$ , there is a delay of approximately 5 seconds during which the remaining digits of the code must be entered. This is done by pressing S4, S3, and S2. The remaining keyboard switches, S6-S11, are connected to the *unselected input*, pin 10. Logic 1 at this pin immediately resets the sequence detector.

Three important outputs are available from IC1. The *lock indicator*, pin 7,



drives an l.e.d. directly, with no need for a series resistor. The l.e.d. is illuminated to indicate that the device is "locked" and becomes extinguished only after entering the correct code. The *unlock output*, pin 8, is used here. This is toggled to logic 1 following a correct entry and remains in this condition indefinitely, being reset only by re-entering the code or switching off the supply. The output from pin 8 drives the relay, RLA1, via R2 and TR1, thereby switching the mains supply. The *momentary unlock output* is not used in this circuit.

### MAINS SAFETY

In any project involving connection to the domestic mains supply, very high

Fig. 3 (Right). LM7225 pin connections.

Fig. 1 (Below). Block diagram of electronic codelock system.

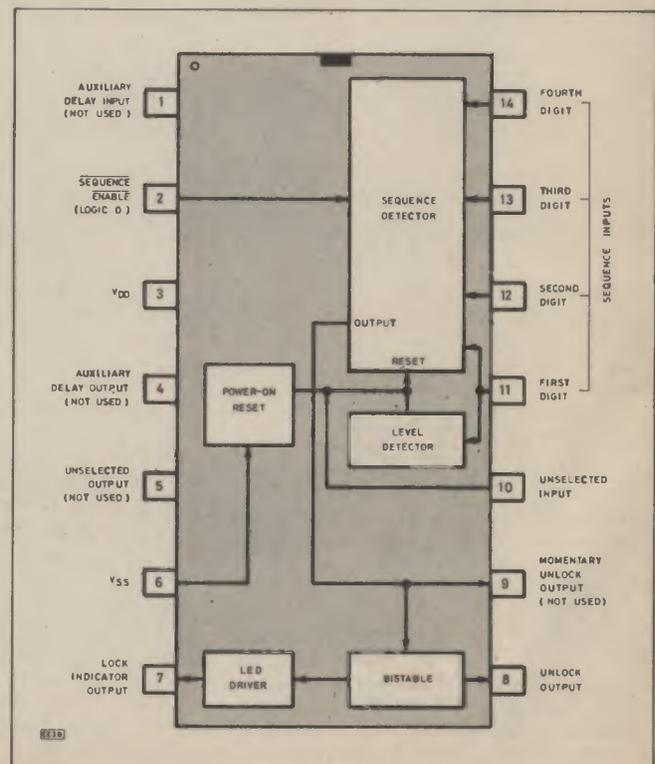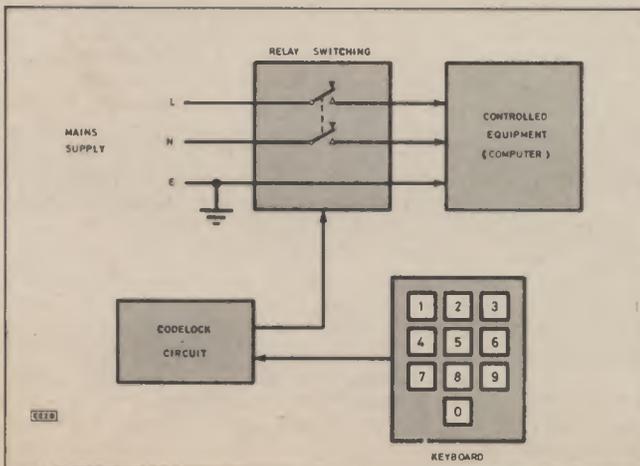



must be firmly fixed, including circuit boards, which are securely bolted to the box. Interwiring between components is colour-coded using several different colours of stranded wire, and all the connections are kept short but strain-free. Spaghetti-type wiring in one colour is difficult or impossible to check and must be avoided.

**MAIN CIRCUIT BOARD:** The two printed circuit boards are shown in Figure 4a and 4b. Begin construction by assembling the main circuit board as shown in Figure 5. It is generally more convenient to insert the low-lying components, including resistors R1 and R2, D5, and the socket for IC1, first, followed by the larger components. Take care to insert the electrolytic capacitor (C1) and tantalum capacitor (C3) with the correct polarity. Do not insert IC1 at this stage. Complete the assembly of the main circuit board by soldering in various colours of flying leads about 15cm long, using of stranded wire and ribbon cable, as indicated.

**SETTING THE CODE:** The keyboard p.c.b. is assembled simply by soldering S2-S11 in position. The code is set using the method illustrated in Figure 6. This shows the wiring matrix of the keyboard viewed from the component side. The switch terminal corresponding side. The switch terminal corresponding to the first digit of the code, in this case 7, is connected by an insulated wire link to the copper track E. In the same way, the switch terminal for the second digit (2) is connected to copper track D, the third digit (5) to track C, and the fourth digit (1) to track B. This sets the code 7251. However, any combination using four different switch terminals can be set, so that constructors can choose from  $10 \times 9 \times 8 \times 7 = 5040$  different codes. It is a simple matter to reset the code from time to time by rewiring the matrix.

The six "unselected" switch terminals are connected to track F. Track A is connected to  $V_{SS}$  and provides the common positive supply to all ten keyboard switches. The insulated wire links must be

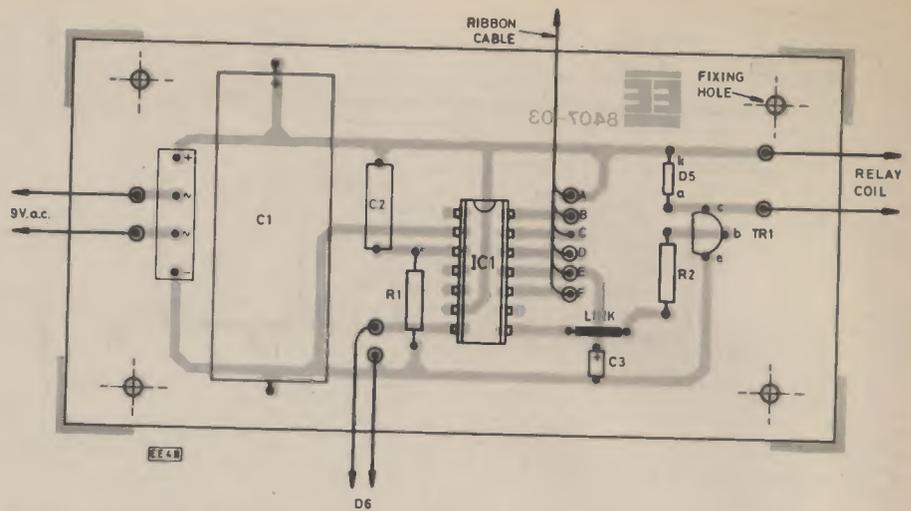


Fig. 5. Main p.c.b. component layout.

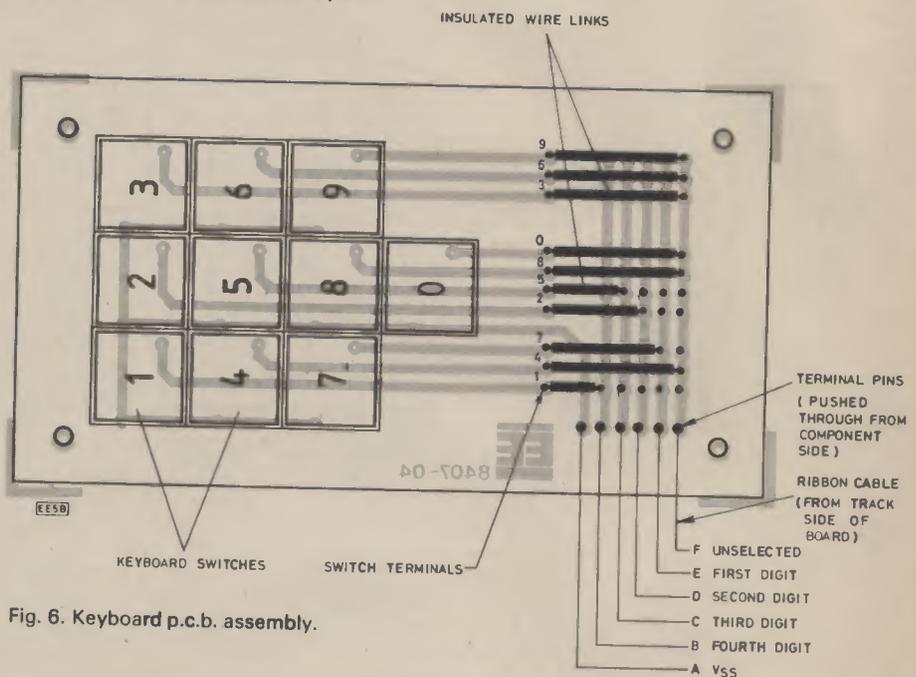


Fig. 6. Keyboard p.c.b. assembly.

## COMPONENTS

### Resistors

- R1 2k $\Omega$
- R2 3.9k $\Omega$
- All  $\frac{1}{4}$ W carbon film  $\pm 5\%$

### Capacitors

- C1 2200 $\mu$ F 25V elect. axial leads
- C2 47nF polyester
- C3 1 $\mu$ F 35V tantalum

### Semiconductors

- D1-4 200V, 1.6A bridge rectifier
- D5 1N4001 silicon diode
- D6 TIL220 (0.2in red l.e.d.)
- IC1 LS7225 keyless lock l.c.
- TR1 BC109 silicon npn

### Miscellaneous

- FS1 20mm mains fuse (maximum 5A—see text)
- LP1 240V a.c. mains neon with integral resistor d.p.d.t. 12V d.c. 110 $\Omega$  coil
- RLA1 S1 d.p.s.t. with 240V a.c. neon indicator
- S2-11 (10 off) p.c.b. mounting keyboard switch (RS337-605)
- SK1 shuttered power outlet socket (RS489-245) shrouded plug (RS489-251)
- PL1 6VA main transformer, 0.4.5, 0.4.5, or 9V secondary

Approx. cost  
Guidance only

**£16.00**

**PRINTED CIRCUIT BOARDS:** maincircuit board size 100 x 50mm; keyboard size 100 x 55mm; aluminum diecast box 170 x 120 x 55mm; screw release 20mm fuseholder; sleeved grommet; i.e.d. fixing clip; P-clip; 6A mains cable.

See  
**Shop  
Talk**

page 434

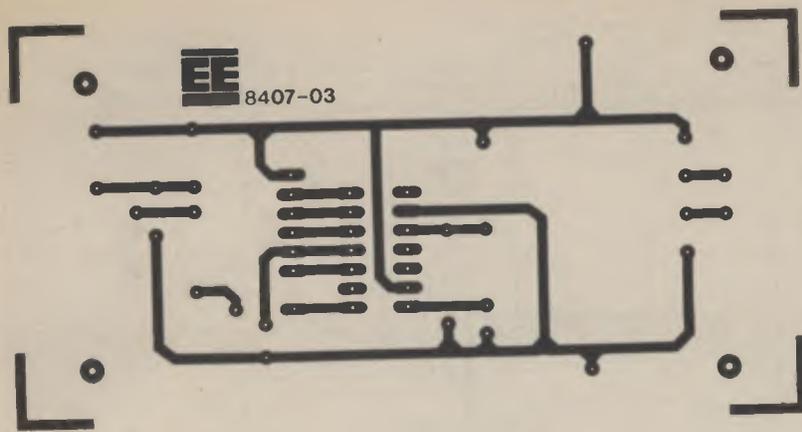


Fig. 4a. Main p.c.b. layout.

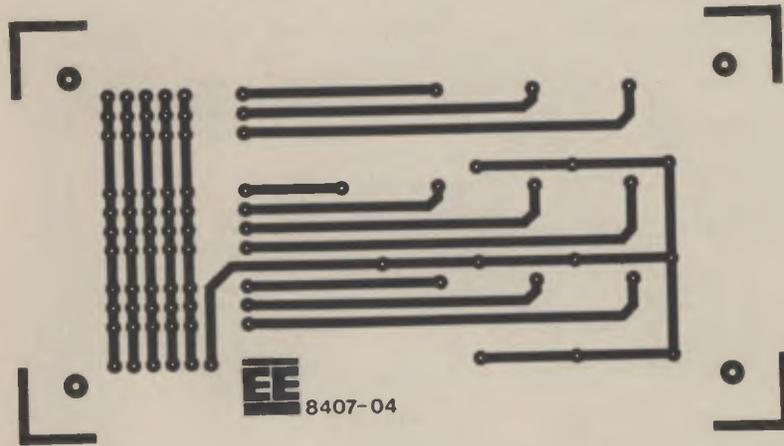


Fig. 4b. Keyboard p.c.b. layout.

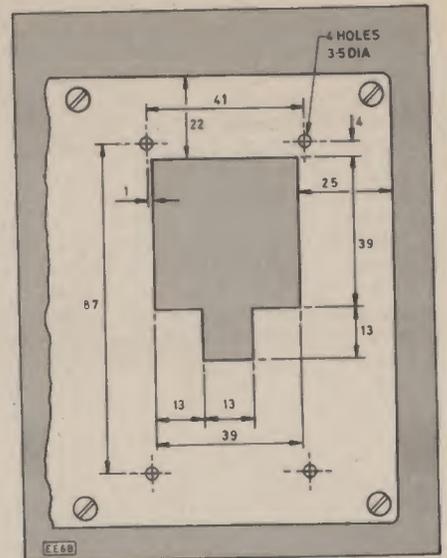


Fig. 7. Top panel drilling details.

complete the interwiring procedure. The trickiest part of this procedure is connecting the ribbon cable to the terminal pins projecting from the track side of the keyboard p.c.b. To avoid shorting between these connections, only a short length of wire from the cable should be exposed and the soldered joints should be insulated using PVC tape.

#### TESTING


One method of circuit testing widely in use is to "switch on and see if it works". With mains-operated equipment this should NEVER be attempted. The proper procedure for testing the completed code lock is as follows.

1. Carefully check all wiring and

kept close to the surface of the p.c.b. so that the completed board can be mounted flush to the inside of the box. To complete the keyboard assembly, terminal pins are pushed through from the component side at the end of each track and soldered in position.

**BOX PREPARATION:** Drilling details for the aluminum diecast box used in the prototype are given in Figure 7. Mark the box carefully and check component sizes before you begin. Patience and care taken at this stage will help to ensure a good final appearance. Large areas of metal are best removed using a small hacksaw fitted with a tension file in place of the normal blade. With drilling completed, the box can be cleaned and spray painted if desired.

**FINAL ASSEMBLY:** Once LP1, S1, the fuseholder FS1, and the transformer T1, have been fitted, the major part of the mains wiring can be carried out (Figure 8). Constructors are advised to check carefully that this is completed correctly. Next, fit RLA1, the output socket SK1 and the main circuit board together with its flying leads. When the board is bolted in position these leads are cut to the correct length, stripped, and soldered to

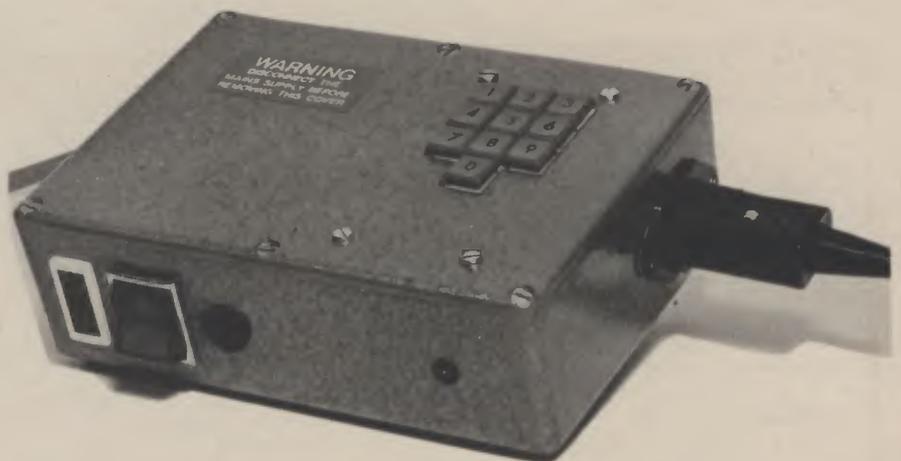

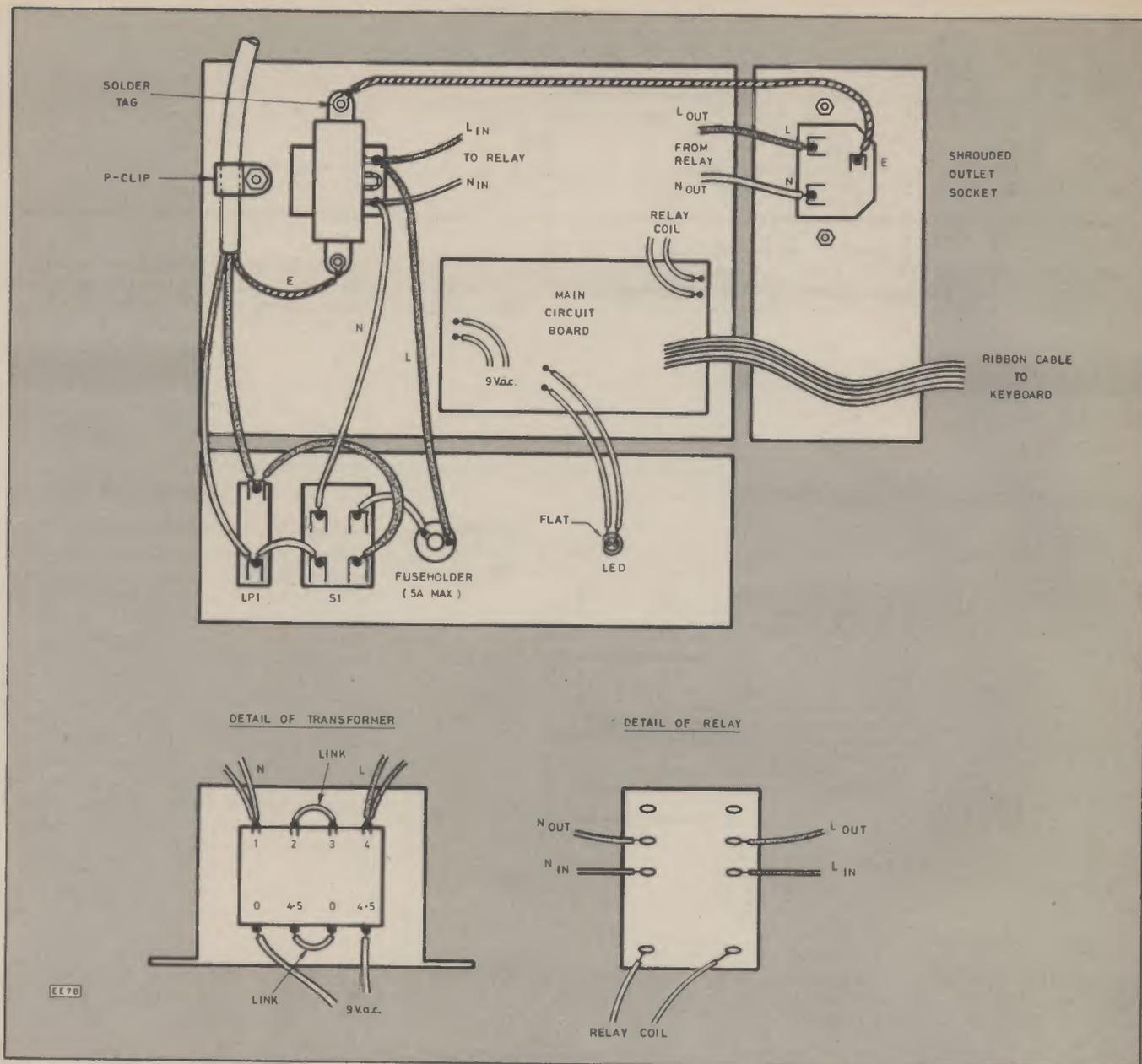


Fig. 8. Codelock wiring diagram.

make sure that the soldered connections on both circuit boards stand well clear or are insulated from the metal box.

2. With a multimeter set to read resistance, check that the exposed metal of the box is directly connected to the EARTH terminal (centre pin) of the mains plug.

3. Remove the mains fuse FS1 from its holder, plug in the mains lead and check the operation of LP1 and S1.

4. Disconnect the mains, replace FS1, and then reconnect the mains supply. Using a multimeter switched to a suitable d.c. voltage scale, check the low voltage power supply across the large smoothing capacitor (C1) on the main circuit board. N.B. KEEP YOUR FINGERS WELL AWAY FROM ANY MAINS WIRING

AND HANDLE ONLY THE INSULATED ENDS OF THE METER PROBES. A reading of 12–16V should be obtained.

5. Switch off again, allow time for C1 to discharge, and only then fit IC1 in its socket, checking for correct orientation.

6. Place the lid loosely on the box, switch on again and check that LED1 is illuminated. Now enter the selected code and listen for a slight 'click' indicating relay operation. At the same time, LED1 should be extinguished.

7. If everything is in order, disconnect the mains and screw down the lid of the box. Finally, connect the computer or other codelock controlled equipment via SK1, PL1 and check operation of the complete system. □

## OTHER APPLICATIONS

The LS7225 is a very versatile device. The circuit given here can easily be adapted for other uses. For example, a general purpose combination lock can be made by using the relay to switch current to a solenoid operated bolt instead of switching the mains supply. Alternatively, the codelock could be used to arm and disarm domestic burglar alarms or other security systems. The quiescent current consumption of the device is extremely low (40µA), allowing battery operation if desired.

Only experienced constructors should attempt such modifications. Interested readers are referred to "PRACTICAL ELECTRONICS", May 1983, pp 26–28 for further information. □

# CAPACITANCE COMPARATOR

L.S. COOK

**C**APACITORS are manufactured from various materials in many shapes, physical sizes and nominal values, and with tolerances commonly from  $\pm 1$  per cent to  $+100/-20$  per cent. Very often the value required in a particular position is not critical, but there are limits; so a method determining the approximate value of a suspect capacitor, or one which has lost its markings, can be useful.

The comparator described here readily performs this function, being easy to use and relatively inexpensive.

## PRINCIPLES OF OPERATION

Let the value of the unknown capacitance be  $C$  and that of an accurately known one be  $C'$ . These are incorporated into two separate monostables, using a 556 dual timer i.c., with associated resistances  $R$  and  $R'$ , respectively, giving "on times" (high output,  $kRC$  and  $kR'C'$  where  $k$  is a constant. If these are made equal  $RC = R'C'$  hence  $C = C'R/R$ .  $C'$  and  $R$  are known and  $R'$  is the value at a particular setting of a potentiometer, which can be measured or, as will be seen later, a scale can be calibrated directly in capacitance values.

Five ranges are provided, each covering values ten times those in the preceding range (see photographs).

## CIRCUIT DESCRIPTION

Fig. 1 shows the circuit diagram.  $R$ , referred to above, is  $R1, 2, 3, 4$  or  $5$  and  $R'$  is the value of  $VR1$  (between its wiper and  $R6$ ).  $C'$  is  $C2$ .

Initially, the outputs (call them outputs  $A$  and  $B$  from the 556  $IC1a, b$ ) are low, so the output of  $IC2c$  is high and that of  $IC2b$  low, thus triggering both sections of  $IC1$  and taking their outputs high, the reset input of  $IC1a$  being held high by  $IC2a$ ; the trigger inputs then rise. When the output from either monostable drops to zero its effect is momentarily transferred through  $C5$  or  $C6$  to the corresponding input of  $IC2d$  and when, and only when, the two zero-bound spikes coincide (i.e., equal "on times" since the monostables were triggered simultaneously) a high output is obtained from  $IC2d$ , illuminating  $D5$  via  $TR1$ . With output  $B$  now low the monostables are retriggered and the cycle is repeated.  $C9$  acts as a reservoir capacitor prevented from discharging through  $IC2d$  by  $D4$ .

If output  $A$  drops before output  $B$ , it remains in that state until retriggered. If output  $B$  drops first it is possible for  $IC1b$

to be triggered again, perhaps more than once (depending on the setting of  $VR1$ ), before output  $A$  drops so when the latter does eventually fall it could coincide with the second, third, etc., fall of output  $B$ , thus indicating a false coincidence. To avoid this occurring, when output  $B$  falls  $IC1a$  is reset via  $IC2a$  but not immediately, otherwise a coincidence would automatically be indicated, again falsely;  $R7$  and  $C4$  introduce a suitable delay.  $R13$  and  $C8$  provide a further delay to allow  $IC2a$ , and hence the reset input of  $IC1a$ , to recover before retriggering takes place.  $D1, 2, 3$  allow  $C4, 7, 8$  to rapidly charge or discharge (as appropriate) when output  $B$  rises.

Switch  $S2$  provides a COARSE/FINE control. With the switch open (COARSE)  $D5$  is illuminated for a wide range of values of  $VR1$  to enable its approximate required setting to be located quickly. Closing  $S2$  (FINE) enables a more accurate setting to be found.

## CONSTRUCTION

### CIRCUIT BOARD

The circuit board is quite straightforward, and Fig. 2 shows the breaks to be made in the tracks on the underside

and the layout of the components on top. Make the breaks, first checking there are twenty-seven, and add the five wire links on the trackside (also shown in Fig. 2). Next, solder in the i.c. holders and the twelve wire links on top, allowing those joining  $E19-F19$  and  $F25-G25$  to stand above the board in order to attach flying leads. Then add the resistors, capacitors (remembering  $C10$  is polarised) and finally the semiconductors. Leave the flying leads until their lengths are known.

### INTERWIRING AND CASE

In the prototype, the circuit board and all the remaining components are mounted on a removable panel (3mm plywood) with a section arranged to sit in a rectangular hole in the top of the case. Fig. 4 shows this panel with all the interwiring details. The circuit board is screwed onto pillars attached to the panel and lies above  $C2$ ; alternatively, it could be bolted to the panel using spacers of a suitable length. Ensure that the screws used do not short adjacent tracks. Cut the shafts of  $VR1$  and  $S1$  to the required length, filing a flat side if necessary, before mounting these components.



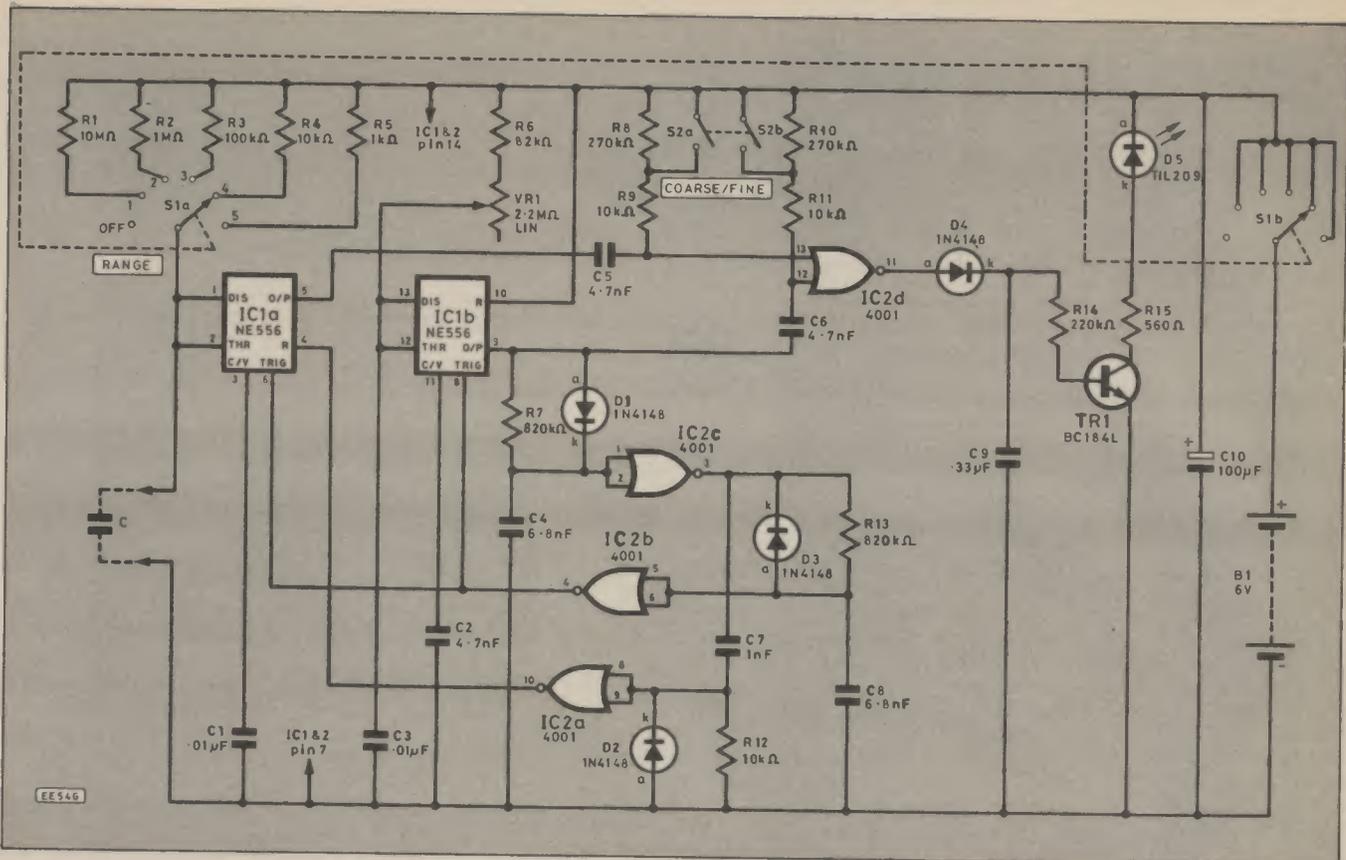


Fig. 1. Complete circuit diagram of the Capacitance Comparator.

## COMPONENTS

Approx. cost  
Guidance only

£9

### Resistors

R1	10M $\Omega$
R2	1M $\Omega$
R3	100k $\Omega$
R4	10k $\Omega$
R5	1k $\Omega$
R6	82k $\Omega$
R7,13	820k $\Omega$ (2 off)
R8,10	270k $\Omega$ (2 off)
R9,11,12	10k $\Omega$ (3 off)
R14	220k $\Omega$
R15	560 $\Omega$

R1-5  $\pm 1\%$  metal film  
0.4W (or  $\frac{1}{2}$ W)  
R6-15  $\pm 5\%$  carbon film  $\frac{1}{4}$ W

### Capacitors

C1,3	10nF ceramic (2 off)
C2	4.7 $\mu$ F $\pm 1\%$ polystyrene
C4,8	6.8nF ceramic (2 off)
C5,6	4.7nF ceramic (2 off)
C7	1nF ceramic
C9	33nF polyester (C280)

C10 100 $\mu$ F 10V electrolytic  
radial leads  
Various close tolerance types for  
calibration purposes (see text)

### Semiconductors

D1-4	1N4148 silicon diode (4 off)
D5	TIL209 3mm red i.e.d.
TR1	BC184L npn silicon
IC1	NE556 dual timer
IC2	CM05 4001 quad 2-input NOR gate

### Miscellaneous



VR1	2.2MHz linear potentiometer
S1	6-way, 2-pole rotary switch


S2 d.p.d.t. miniature slide  
switch

B1 HP7 1 $\frac{1}{2}$ V cells (4 off)

0.1in matrix stripboard, 13 strips  
x 25 holes; 14-pin d.i.l. holders (2  
off); battery holder (4 x HP7  
square) and connector; 3mm i.e.d.  
clip; miniature crocodile clips (1  
red, 1 black); connecting wire,  
rigid and flexible; pointer knobs  
(approximately 37mm and 25mm  
diameter); case, minimum internal  
dimensions: length 142mm, width  
64mm (back), 32mm (front); 6BA  
nut, screw (13mm), washer,  
solder tags (2 off); screws for slide  
switch.

See  
**Shop  
Talk**  
page 434

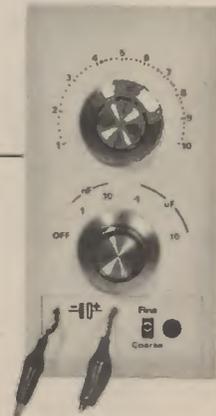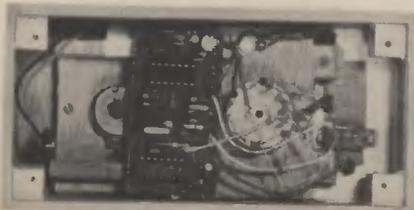

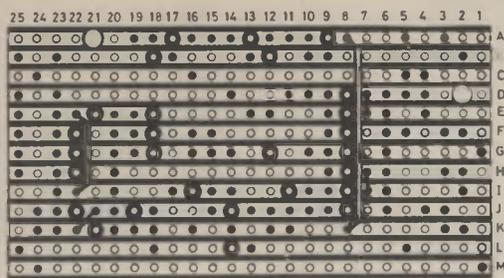

EE556A Fig. 2. Track-side of the circuit board.

The dimensions of the case (also 3mm plywood) are given in Fig. 5. Glued butt joints are used, with short lengths of 12mm square wood strengthening the four vertical corners. These do not quite reach the bottom of the case and provide points for screwing on a base panel and rubber feet. Ensure they do not obstruct the removable component panel. The case is covered with an adhesive plastic film.


Alternatively, the case could be a suitable sized plastics box, the components being mounted on the underside of the lid with a similar layout to that shown.

Whatever case is used, complete the wiring as shown in Fig. 4, adding flying leads to the circuit board before fixing the latter and attach crocodile clips to the test leads. Screw on the removable panel (if used) using spacers as necessary and add suitable pointer knobs. The battery holder just fits in the prototype, but if found to be loose a piece of foam rubber will hold it in place.
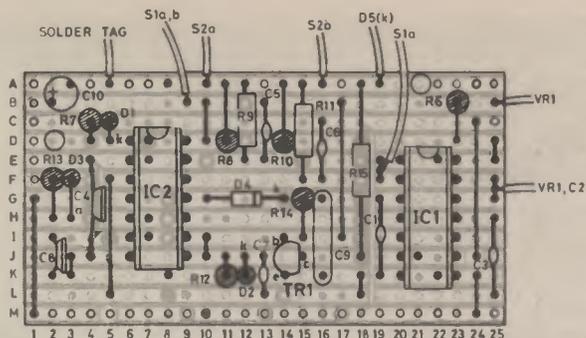
## CALIBRATION

There are two alternative methods for calibrating the comparator. The first requires a reliable resistance measuring device that can measure up to about 2M $\Omega$ . The resistance to be measured is the section of VR1 in use, that is from its wiper to R6. (Leave IC1 out of the circuit when doing this.) Points numbered 1 to 10 on the dial are given by resistances of 212766 $\Omega$  and its multiples (for example, 212766 $\Omega$  for "1", 425532 $\Omega$  for "2", etc.) rounded to about two significant figures in practice. Further division of the scale can be estimated sufficiently accurately for this instrument. The "1" then corresponds to the lowest capacitance in the selected range and the "10" to the highest.

It could be that a multimeter is the only resistance measuring device available and the accuracy of this, particularly for the higher values, may well be questionable. The second method of calibration, although involving some expense, may be considered preferable. Using the 1 $\mu$ F to 10 $\mu$ F range (the i.c. is now inserted and the battery connected) measure the capacitances of several 1 per cent tolerance capacitors within this range and mark the dial accordingly, again estimating the intermediate values. (Remember that 1 per cent polystyrene



EE556B Fig. 3. Component layout (actual size).

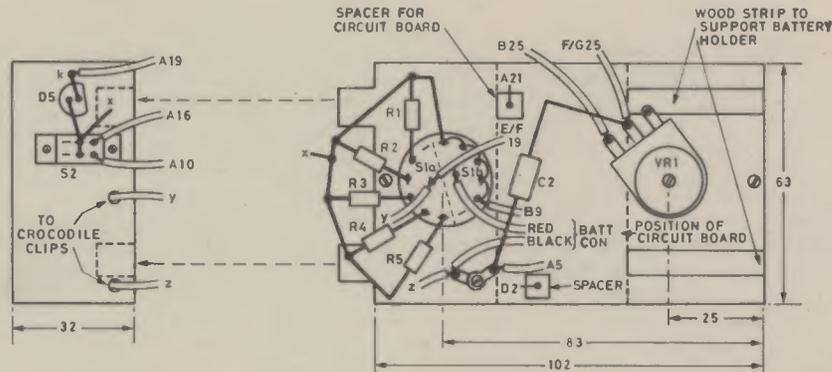


Fig. 4. Components and wiring on the "removable panel". The two sections are glued or screwed together with suitable spacers between. Identical thickness spacers are used between the panel and the case top.

capacitors are generally considerably less expensive than equivalent silvered mica types.) If this method of calibration is employed, a 5 per cent polystyrene capacitor will suffice for C2.

## RANGES

Potentiometer VR1, C2 and R1 to R5 have been chosen to produce the ranges described earlier, with continuity from one to the next. If the actual value of VR1 is well below its nominal one the top end of the scale could be lost. In this case R1 to R5 could be reduced to 82052, 8.2k $\Omega$ , etc., or C2 increased to 5.6 $\mu$ F.

## USING THE COMPARATOR

Grip the leads of the capacitor under test in the crocodile clips observing polarity where applicable. Switch to COARSE and scan the dial on each range until the l.e.d. lights. Then switch to FINE, readjust the setting of VR1 to obtain the brightest steady light and read off the required value. Do not touch the capacitor or leads when doing this.

Some residual capacitance must be expected, but it is significant only on the lowest range. To estimate its value, measure a few close tolerance capacitors from 100pF to 1 $\mu$ F. The differences between these known values and the readings obtained can be averaged to give the required figure. (On the prototype it is around 20pF.) Remember to allow for this when using the lowest range; alternatively, mark a second scale on the dial.

To measure values below 100pF the

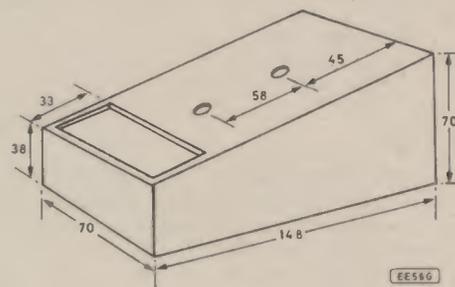


Fig. 5. Case dimensions. The circuit board stands 18mm off the panel, screwed onto pillars of wood, or bolted using spacers.

scale could be extended, but a more reliable result may be obtained by first measuring the value of a capacitor of, say, about 150pF then repeating with this and the one under test in parallel. Subtraction gives the required figure, automatically cancelling the resident capacitance.

A similar method can be used for values greater than 10 $\mu$ F measuring a 10 $\mu$ F capacitor first, then this in series with the one under test. The required value can be obtained from the series connection formula.

Note that the value of R5 (top range) is below that recommended for the resistance in this position (5kHz), but no error has been detected as a result. □

# SHOP TALK



BY DAVE BARRINGTON

## Catalogue Received

The new 28-page TK Electronics catalogue contains several new items of interest. Also, it is interesting to note that not only have they put their stocks on computer but the catalogue has been produced by the same machine.

The readout or "printing" is very clear (for a printout) and easy to read, and is another example of the excellent progressive service this company runs.

Amongst new products added to their listings are a new range of telephone connectors and a collection of security accessories. These include pressure mats, door/window contact sets, window tape connectors, bell box and passive infra-red detection unit.

Copies of the TK Electronics "Yellow Catalogue" are available free from TK Electronics, Dept EE, 11-13 Boston Road, London W7 3SJ. A self-addressed envelope (9in x 6in) would be appreciated.

## Link Up

With the sales of video recorders and home computers now running into millions, the Reeler TV extension cable from Pullway will undoubtedly find many applications around the home.

Apart from the common domestic application, it is a god-send for the growing band of home computer and video game users. Here a portable TV is often used as a monitor, or even the family colour set is usurped, to display programs or play games.

By using the extension lead, would-be games "masters" and budding programmers need not run the risk of headaches or blurred vision from being too close to the screen.

For the caravanner, camper and boating enthusiast the extension reel will also prove an asset where storage space is often at a premium. They can position their remote aerial for optimum reception without yards of unwieldy cable, and, after use, the cable can be rewound and stored in any convenient small space.

Moulded in tough ABS plastics, the Reeler incorporates a carrying handle with integral socket and moulded coaxial plug. It is available in two capacities of either 30 or 45 feet of standard 75-ohm coaxial cable and has a recommended selling price of £7.95, including VAT.

For details of local stockists readers should write to: Pullway Ltd., Dept EE, Venn House, 11 Clayton Road, Hayes, Middlesex.



Please mention  
**EVERYDAY  
ELECTRONICS**

when replying  
to products  
mentioned  
on this page  
and to  
Classified Ads

## Change of Name

With all the recent changes at Ambit International and their opening of new premises at Portsmouth and Broxbourne, we have just received news that the component side of their operation is now trading under the name of Cirkit.

The change of name coincides with an increased product line (10,000 items now stocked) and the introduction of a range of Cirkit constructional kits, graded for the student, expert and enthusiast.

They have also issued a new catalogue which covers such items as: computer connectors and printers; microprocessors and memories; voltage regulators and semiconductors. Their listings of capacitors and r.f. components is probably one of the most extensive amongst component suppliers.

Copies of the new Cirkit catalogue cost 80p and may be obtained from: Cirkit Holdings PLC, Dept EE, Park Lane, Broxbourne, Herts. Included with each catalogue are three £1 discount vouchers.

## CONSTRUCTIONAL PROJECTS

### Electronic Lock

The LS7225 "keyless" lock i.c. used in the *Electronic Lock* is a P-MOS device which performs the code sequencing. Also included, within the device but not used, is an auxiliary delay facility.

The LS7225 integrated circuit is available from TK Electronics or RS Components, Order code: 304-554. It should be pointed out that RS will NOT supply to the general public but must be ordered through a local stockist.

Most of our advertisers now stock suitable keypads for the "master" combination keyboard.

### Ultrasonic Burglar Alarm

The 40kHz transducers used in the *Ultrasonic Burglar Alarm* are usually sold in pairs and can be purchased with pin or phono plug connectors. The ones required are of the pin type. These are available from: Riscamp, Rapid, Enfield and Maplin.

The warning sander, X70 W06, is available direct from: Avionic Systems (Heathrow) Ltd., Dept EE, Viscount Way, Hounslow, Middx TW6 2JW. The TOKO coil, CAN1A350ER, is stocked by Cirkit.

### Car Lights Warning

Almost any type of 12V d.c. buzzer would be suitable for the *Car Lights Warning* project.

If difficulties are experienced in locating the MCR102 thyristor for this circuit, then it would appear that the C103YY from RS would be an alternative device.

### Atom EPROM Simulator

The 2K by 8 static CMOS RAM memory i.c.s used in the *Atom EPROM Simulator* are currently listed by Rapid Electronics and Cirkit.

We cannot envisage any component buying problems for the *CB Mini Power Supply* or the *Capacitance Comparator*.



# ENFIELD ELECTRONICS

208 Baker Street, Enfield,  
Middlesex. EN1 3JY. Tel: 01-366 1873




### TRANSISTORS

AC125	30p	BC183C	12p	TIP29C	45p	2N1304	80p
AC126	30p	BC183L	12p	TIP30A	40p	2N1305	70p
AC127	30p	BC183LB	12p	TIP30C	50p	2N1307	80p
AC128	30p	BC184	12p	TIP31	38p	2N1308	80p
AC132	30p	BC184B	12p	TIP31A	40p	2N2222A	30p
AC141	30p	BC184L	12p	TIP31C	45p	2N2369A	28p
AC176	30p	BC186	30p	TIP32A	40p	2N2646	68p
AC187	30p	BC187	30p	TIP32C	40p	2N2904A/5A	30p
AC188	30p	BC212A	14p	TIP36C	140p	2N2907A	30p
AD149	80p	BC213	12p	TIP41A	50p	2N2926G	12p
AD161	45p	BC213B	12p	TIP41B	50p	2N2926R	12p
AD182	45p	BC213L	12p	TIP42A	60p	2N2926Y	12p
BC107	12p	BC214	12p	TIP120	80p	2N3053	30p
BC107A	14p	BC214B	14p	TIP121	80p	2N3055E	60p
BC107B	14p	BC214L	12p	TIP142	120p	2N3442	150p
BC108	12p	BC217	18p	TIP2955	70p	2N3615	200p
BC108A	14p	BC238B	18p	TIS43	36p	2N3702	12p
BC108B	14p	BC307	18p	TIS44	40p	2N3703	12p
BC108C	14p	BC308	18p	TIS90	30p	2N3704	12p
BC109	12p	BC327	16p	TIS91	30p	2N3705	12p
BC109B	14p	BC328	16p	VS99	30p	2N3706	12p
BC109C	14p	BC337	16p	VS99A	30p	2N3707	12p
BC140	35p	BC338	16p	VS99B	110p	2N3708	12p
BC141	35p	BC441	15p	BU205	200p	2N3710	12p
BC142	35p	BC461	36p	BU208A	220p	2N3711	12p
BC143	35p	BC477	40p	MJE2955	40p	2N3772	200p
BC147	12p	BC478	40p	MJE300	50p	2N3773	200p
BC148	12p	BC517	45p	MJE371	90p	2N3774	200p
BC157	12p	BC547	15p	MJE2955	110p	2N3819	25p
BC158	12p	BC548	15p	MJE305T	170p	2N3710	12p
BC159	12p	BC549	16p	MPSA06	25p	2N3823	50p
BC160	50p	BC556	20p	MPSA05	30p	2N3866	100p
BC161	45p	BC557	16p	MPSU56	65p	2N3903	15p
BC167	15p	BC558	16p	MPSU6	60p	2N3905	15p
BC168	12p	BC570	20p	OC22	16p	2N3906	15p
BC170	20p	BCV71	20p	OC26	100p	2N5172	30p
BC171	13p	BCV72	23p	OC28	200p	2N5194	42p
BC172A	12p	BD131	50p	OC36	220p	2N5458	48p
BC173	13p	BD132	50p	OC41	75p	2N5488	85p
BC177	20p	BD133	60p	OC42	60p	2N5490	85p
BC178	20p	BD135	50p	OC70	60p	2N706A	25p
BC179	25p	BD136	40p	OC76	60p	2N708	30p
BC181	23p	BD137	40p	OC81	60p	2N914	36p
BC182	12p	BD138	40p	OC82	60p	2N918	36p
BC182B	14p	BD139	45p	OC84	50p	2N930	30p
BC182L	12p	BF146	45p	TIP29	30p	40406	80p
BC183	12p	BF194	14p	TIP29A	35p	40407	80p
BC183B	12p	BF195	14p	TIP29B	50p	2N1303	80p

### TTL

7400	18p	7417	26p	7447	75p	7486	35p	74119	70p	74180	65p	74190	55p
7401	18p	7420	20p	7448	55p	7489	140p	74121	35p	74161	55p	74191	55p
7402	18p	7422	28p	7450	21p	7490	37p	74122	41p	74162	46p	74192	55p
7403	18p	7424	28p	7451	20p	7491	35p	74123	41p	74163	46p	74193	55p
7404	18p	7426	28p	7452	21p	7492	40p	74124	70p	74164	46p	74194	52p
7405	18p	7427	30p	7453	21p	7493	41p	74125	65p	74165	80p	74195	52p
7406	32p	7428	30p	7454	21p	7494	21p	74126	65p	74166	80p	74196	55p
7407	32p	7429	30p	7455	21p	7495	41p	74127	65p	74167	185p	74197	55p
7408	25p	7430	30p	7456	25p	7496	41p	74128	65p	74168	185p	74198	55p
7409	25p	7431	30p	7457	25p	7497	60p	74129	65p	74169	185p	74199	55p
7410	18p	7432	26p	7458	25p	7498	41p	74130	65p	74170	120p	74200	60p
7411	25p	7433	35p	7459	25p	7499	41p	74131	65p	74171	120p	74201	60p
7412	26p	7434	35p	7460	21p	7500	41p	74132	65p	74172	120p	74202	60p
7413	26p	7435	35p	7461	21p	7501	41p	74133	65p	74173	120p	74203	60p
7414	37p	7436	35p	7462	21p	7502	41p	74134	65p	74174	120p	74204	60p
7415	28p	7437	30p	7463	21p	7503	41p	74135	65p	74175	120p	74205	60p
7416	28p	7438	30p	7464	21p	7504	41p	74136	65p	74176	120p	74206	60p
7417	28p	7439	30p	7465	21p	7505	41p	74137	65p	74177	120p	74207	60p
7418	28p	7440	30p	7466	21p	7506	41p	74138	65p	74178	120p	74208	60p
7419	28p	7441	30p	7467	21p	7507	41p	74139	65p	74179	120p	74209	60p
7420	28p	7442	30p	7468	21p	7508	41p	74140	65p	74180	120p	74210	60p
7421	28p	7443	30p	7469	21p	7509	41p	74141	65p	74181	120p	74211	60p
7422	28p	7444	30p	7470	21p	7510	41p	74142	65p	74182	120p	74212	60p
7423	28p	7445	30p	7471	21p	7511	41p	74143	65p	74183	120p	74213	60p
7424	28p	7446	30p	7472	21p	7512	41p	74144	65p	74184	120p	74214	60p
7425	28p	7447	30p	7473	21p	7513	41p	74145	65p	74185	120p	74215	60p
7426	28p	7448	30p	7474	21p	7514	41p	74146	65p	74186	120p	74216	60p
7427	28p	7449	30p	7475	21p	7515	41p	74147	65p	74187	120p	74217	60p
7428	28p	7450	21p	7476	21p	7516	41p	74148	65p	74188	120p	74218	60p
7429	28p	7451	20p	7477	21p	7517	41p	74149	65p	74189	120p	74219	60p
7430	28p	7452	21p	7478	21p	7518	41p	74150	65p	74190	120p	74220	60p
7431	28p	7453	21p	7479	21p	7519	41p	74151	65p	74191	120p	74221	60p
7432	28p	7454	21p	7480	21p	7520	41p	74152	65p	74192	120p	74222	60p
7433	28p	7455	21p	7481	21p	7521	41p	74153	65p	74193	120p	74223	60p
7434	28p	7456	21p	7482	21p	7522	41p	74154	65p	74194	120p	74224	60p
7435	28p	7457	21p	7483	21p	7523	41p	74155	65p	74195	120p	74225	60p
7436	28p	7458	21p	7484	21p	7524	41p	74156	65p	74196	120p	74226	60p
7437	28p	7459	21p	7485	21p	7525	41p	74157	65p	74197	120p	74227	60p
7438	28p	7460	21p	7486	21p	7526	41p	74158	65p	74198	120p	74228	60p
7439	28p	7461	21p	7487	21p	7527	41p	74159	65p	74199	120p	74229	60p
7440	28p	7462	21p	7488	21p	7528	41p	74160	65p	74200	120p	74230	60p
7441	28p	7463	21p	7489	21p	7529	41p	74161	65p	74201	120p	74231	60p
7442	28p	7464	21p	7490	21p	7530	41p	74162	65p	74202	120p	74232	60p
7443	28p	7465	21p	7491	21p	7531	41p	74163	65p	74203	120p	74233	60p
7444	28p	7466	21p	7492	21p	7532	41p	74164	65p	74204	120p	74234	60p
7445	28p	7467	21p	7493	21p	7533	41p	74165	65p	74205	120p	74235	60p
7446	28p	7468	21p	7494	21p	7534	41p	74166	65p	74206	120p	74236	60p
7447	28p	7469	21p	7495	21p	7535	41p	74167	65p	74207	120p	74237	60p
7448	28p	7470	21p	7496	21p	7536	41p	74168	65p	74208	120p	74238	60p
7449	28p	7471	21p	7497	21p	7537	41p	74169	65p	74209	120p	74239	60p
7450	28p	7472	21p	7498	21p	7538	41p	74170	65p	74210	120p	74240	60p
7451	28p	7473	21p	7499	21p	7539	41p	74171	65p	74211	120p	74241	60p
7452	28p	7474	21p	7500	41p	7540	41p	74172	65p	74212	120p	74242	60p
7453	28p	7475	21p	7501	41p	7541	41p	74173	65p	74213	120p	74243	60p
7454	28p	7476	21p	7502	41p	7542	41p	74174	65p	74214	120p	74244	60p
7455	28p	7477	21p	7503	41p	7543	41p	74175	65p	74215	120p	74245	60p
7456	28p	7478	21p	7504	41p	7544	41p	74176	65p	74216	120p	74246	60p
7457	28p	7479	21p	7505	41p	7545	41p	74177	65p	74217	120p	74247	60p
7458	28p	7480	21p	7506	41p	7546	41p	74178	65p	74218	120p	74248	60p
7459	28p	7481	21p	7507	41p	7547	41p	74179	65p	74219	120p	74249	60p
7460	28p	7482	21p	7508	41p	7548	41p	74180	65p	74220	120p	74250	60p
7461	28p	7483	21p	7509	41p	7549	41p	74181	65p	74221	120p	74251	60p
7462	28p	7484	21p	7510	41p	7550	41p	74182	65p	74222	120p	74252	60p
7463	28p	7485	21p	7511	41p	7551	41p	74183	65p	74223	120p	74253	60p
7464	28p	7486	21p	7512	41p	7552	41p	74184	65p	74224	120p	74254	60p
7465	28p	7487	21p	7513	41p	7553							

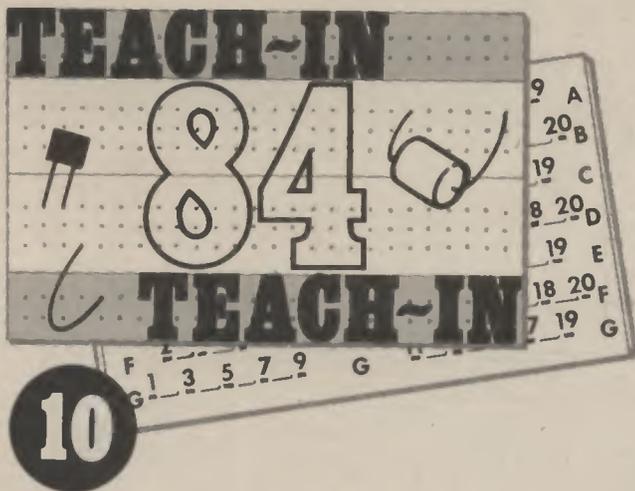

A TWELVE-PART HOME STUDY COURSE IN THE PRINCIPLES AND PRACTICE OF ELECTRONIC CIRCUITS. ESSENTIALLY PRACTICAL, EACH PART INCLUDES EXPERIMENTS TO DEMONSTRATE AND PROVE THE THEORY. USE OF A PROPRIETARY BREADBOARD ELIMINATES NEED FOR SOLDERING AND MAKES ASSEMBLY OF CIRCUITS SIMPLE. THE IDEAL INTRODUCTION TO THE SUBJECT FOR NEWCOMERS. ALSO A USEFUL REFRESHER COURSE FOR OTHERS.

By GEORGE HYLTON

# DIGITAL CIRCUITS

**T**HIS month we look at a few digital circuits and indulge in a bit of philosophy on the art of designing things. As I explained earlier, it's not the intention of this series to go into logic circuits as such. That's well covered in other articles. All the same, some of the digital integrated circuits developed for computing and similar uses can quite easily be adapted for use in analogue or linear circuits.

## EXPERIMENT 10.1

### COMPLEMENTARY INVERTER

Let's start by building a simple circuit which illustrates some aspects of digital electronics. In Fig. 10.1, two bipolar transistors TR1 and TR2, one *pnp* and the other *npn*, are connected "back to back" across the power supply. Circuits in which devices of opposite polarity work together like this are called "complementary" circuits.

The component layout is given in Fig. 10.2.

With S1 in position 2, bias current flows out of the base of TR1 (the *pnp* transistor) through R1 and R2 and into the base of TR2. Both transistors therefore have the same bias current and both are turned on.

What voltage does the meter read? In an ideal world, with identical transistors, the circuit would be perfectly symmetrical and the collectors would sit at just half Vcc. In the real world, one transistor has a higher gain and the output voltage is driven as far positive or as far negative as it can go. The meter reads either HIGH (nearly 9V) or LOW (nearly zero).

Moving S1 changes the situation. In position 3, TR1 is turned on harder and the output must go HIGH. In position 1, TR2 is turned on and the output is LOW.

If you connect a pair of l.e.d.s as shown and switch S1 back and forth they light alternately.

Note that the output goes low when the input is high and vice-versa. This reversal of the input signal is called inversion and the circuit is an inverter. Its symbol is an "amplifier" triangle with a small circle at the apex. (As with op-amps, the supply

voltages are usually omitted from the diagram.)

Inverters are common building bricks for more complex circuits. They exist in integrated circuit form in all the common "families" of digital i.c.s.

Some of these families (TTL, ECL, and so on) are designed round bipolar transistors; others (CMOS, NMOS) round field-effect transistors. It so happens that CMOS (pronounced like "sea moss") lends itself well to the sort of uses we are concerned with, so let's take a look at a CMOS inverter (Fig. 10.3).

### CMOS INVERTERS

It could hardly be simpler. TR1 and TR2 are field-effect transistors, of opposite polarity. They are connected like TR1 and TR2 in Fig. 10.1, except that no biasing resistances are needed. Each transistor acts as a "load" for the other.

Note that in Fig. 10.3 TR1 and TR2 are drawn as discrete f.e.t.s, that is, with enclosing circles. This is to help identification and comparison of these devices with the ordinary transistor symbol. In

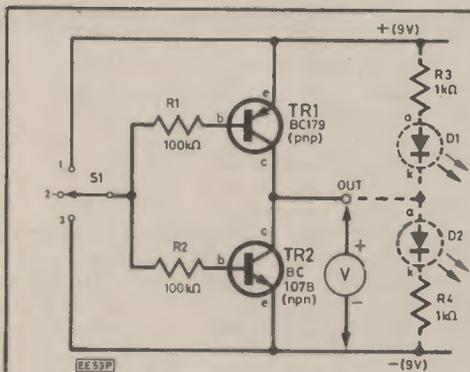


Fig. 10.1. Circuit to illustrate inverter action, with two transistors, one *pnp* and one *npn*, connected "back-to-back" as a complementary pair.

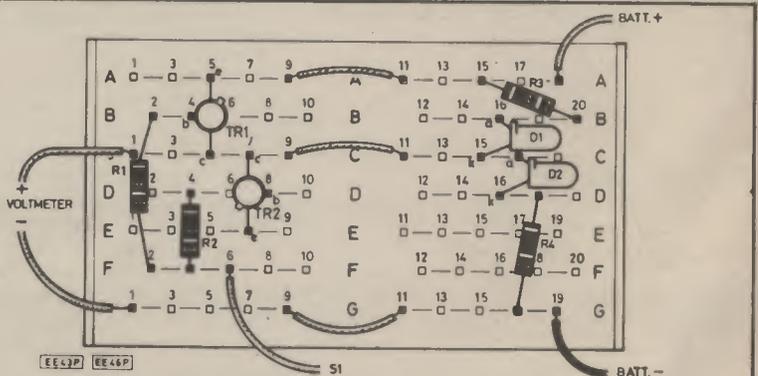


Fig. 10.2. Layout for Fig.10.1 using EBBO discrete module. Note that the layout shows the final circuit: the l.e.d.s and the link between points C9 and C11 are not needed for the first experiment.

actual fact we shall be using f.e.t. transistors that are elements within an integrated circuit, and such elements are normally drawn without any enclosing circle. The pin numbers given in Fig. 10.3 relate to the i.c. type 4069UB.

The three electrodes of a field-effect transistor (f.e.t.) have different names from those of bipolar transistors:

The SOURCE (s) of a f.e.t. corresponds to the EMITTER.

The GATE (g) corresponds to the BASE.

The DRAIN (d) corresponds to the COLLECTOR.

There is another connection, to what's called the substrate, but this is usually connected internally to the source and you don't have to worry about it.

F.e.t.s are controlled by applying voltages to their gates. No gate current flows, so the f.e.t. has virtually infinite input resistance.

The two polarities of f.e.t. are:  
*n*-channel, corresponding to *n*pn,  
 requiring a positive drain voltage.

*p*-channel, corresponding to *p*np and requiring a negative drain voltage.

## BIASING F.E.T.S

Biasing the kind of f.e.t.s used in CMOS is similar to biasing bipolars. To turn on a f.e.t. its gate-source bias (V<sub>GS</sub>) must have the same polarity as its drain-source voltage (V<sub>DS</sub>). So for an *n*-channel f.e.t., V<sub>GS</sub> is positive and for a *p*-channel f.e.t. V<sub>GS</sub> is negative.

F.e.t.s which require this kind of bias to turn them on are called enhancement-mode f.e.t.s.

There are other kinds, including depletion-mode f.e.t.s, which turn on without any bias; that means gate and source are at the same voltage. Indeed, they usually need a reverse bias to keep their drain current down to a safe value. We shan't use any depletion-mode f.e.t.s but you may well come across them as discrete transistors in radio and TV receivers and audio amplifiers.

In a CMOS inverter when the input goes high the output goes low and vice-versa. In digital electronics inverters are driven from high to low with no intermediate states. The output is always either close to V<sub>DD</sub> or close to V<sub>SS</sub> as the power supply rails are called.

## INVERTERS AS AMPLIFIERS

For our purposes it's more useful to turn each f.e.t. half-way on. They then cooperate to act as a single-stage push-pull voltage amplifier. To arrange this, all you need do is connect a resistance from output to input (Fig. 10.4). The output voltage then adjusts itself to roughly half the supply voltage. Since there is no current through the added resistance the voltage at the input is the same as at the output.

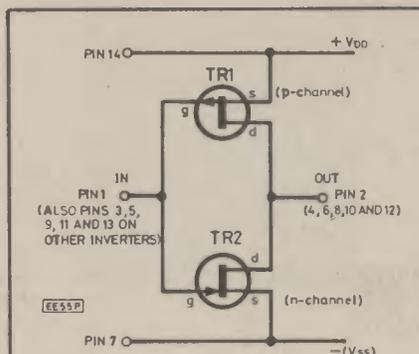


Fig. 10.3. CMOS inverter as contained in the 4069UB i.c. (Numbers refer to 4069 pins.)

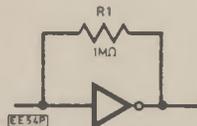


Fig. 10.4. Biasing a CMOS inverter for use as an amplifier.

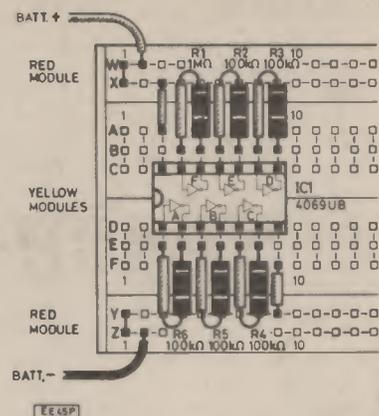


Fig. 10.5. EBO i.c. layout for biasing experiment. The positions of the six inverters are shown on IC1 outline.

## SAFETY PRECAUTIONS

The f.e.t.s in CMOS (called MOSFETS, where MOS stands for metal-oxide-silicon) can be destroyed by static electricity of the kind that builds up on one's clothing in dry weather. To avoid discharging yourself through a CMOS i.c., follow this safety rule: Before handling the i.c. or working on a circuit which incorporates it, touch the table-top or the "earth" line V<sub>SS</sub>.

## HEX INVERTER

You can buy a CMOS i.c. which contains six inverters, like the one in Fig. 10.3, for a few tens of pence. It's the hextuple ("hex") inverter type 4069. Letters may be added; for example, HEF4069UB. The "front" letters are the manufacturer's code. "UB" at the end (or sometimes "A") means that the circuit is "unbuffered". This means that the inverter is not followed, inside the i.c., by an extra amplifier.

Many CMOS circuits are buffered (B). This means that there is a buffer amplifier to prevent the inverter from being affected much by its load. A buffered CMOS inverter has three circuits like Fig. 10.3 in each of its six inverters. Three stages are needed because two would invert twice and turn the inverter into a non-inverter. The third inverts again and restores the status quo.

Don't try to use buffered CMOS for your experiments. Because of its very high gain it has a habit of oscillating instead of amplifying.

## EXPERIMENT 10.2

### SETTING UP

Use two yellow EBO modules, sandwiched between two red ones (Fig. 10.5). Put a blue (discrete component) module beneath these. The red modules are terminal strips, each with two rows. Connect the two rows of the upper strip together and use it as the positive (+9V) supply rail. Similarly, connect the rows of the lower strip for use as the negative (V<sub>SS</sub>) rail.

It would be convenient to begin circuit assembly by inserting the 4069UB i.c. into the board to act as a marker for the connections. But this would increase the risk of static damage while you are setting up.

Instead, insert an i.c. holder (14-pin d.i.l. holder). The empty holder then becomes the marker and you put the i.c. itself in the holder when everything else has been completed.

Connect the negative supply line V<sub>SS</sub> before you start. This is very important when mains power units are used in place of a battery; the rule for connecting the "earthy" or common line is: first in, last out. Working on an "unearthed" circuit can allow mains leakage currents to flow through f.e.t.s and damage them.

Connect a 100μF, 25V capacitor between positive and negative rails (use the spare holes on the battery holder). This reduces stray a.c. voltages which might creep from one part of the circuit to

another via the power supply, with up-setting results.

First connections to the i.c. socket are battery negative (-) to pin 7 and positive (+) to pin 14. Now connect the output of each inverter back to its input via a resistor (Fig. 10.4).

You'll probably find it convenient to bend the resistors into "hairpins" and cut off part of one lead to match the bent one. Short direct connections, when needed, can be made with bare wire, but you don't need any at the moment.

"Earth" yourself to the negative line, insert the 4069UB and connect the battery. Measure the voltage at each output; that is, pins 2, 4, 6, 8, 10 and 12. All should be within about 1V of 4.5V, demonstrating that the added d.c. feedback resistors have had the desired effect of setting the outputs near the half-supply-voltage mark. (In my case they were all 5V, but individual i.c.s vary.)

If you run into trouble, switch off, check all connections, make sure the i.c. is plugged in the right way round and that each pin is really in. (It's quite easy to bend back a pin on the i.c. or the holder by accident. Check.)

It's unlikely that a hex inverter will fail on all six amplifiers, but if one happens to develop an internal short between  $V_{DD}$  and  $V_{SS}$  it will remove battery voltage from the rest. If all connections are correct but you still have problems try a different 4069UB.

## EXPERIMENT 10.3

### OSCILLATORS


We'll now turn the amplifiers labelled F and E on Fig. 10.5 into a square-wave oscillator (Fig. 10.6a). This generates a low frequency (about 6Hz), audible as clicking in your crystal earphone. (Connect the earphone between any point and the negative rail.)

Next we'll use amplifier D as a buffer (Fig. 10.6b). If  $R_2 = R_3$  the gain is very nearly 1. With this kind of feedback the signal voltage at amplifier D input is very much reduced, as you can check with your earphone: compare volumes at pins 9 and 8.

## EXPERIMENT 10.4
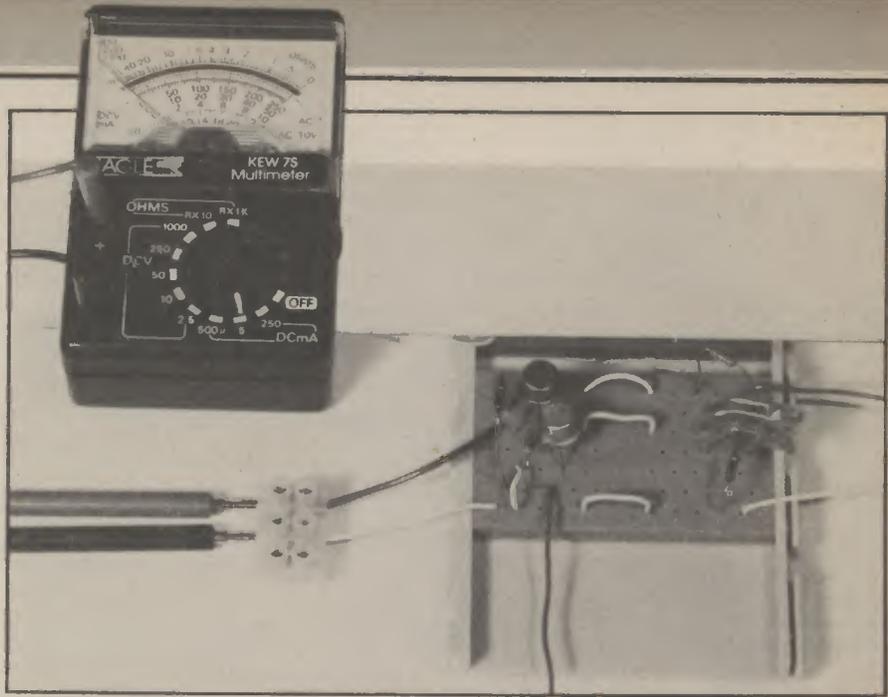
### SINE-WAVE OSCILLATOR

Our next step is more ambitious. It will call for more connecting points than the EBBO i.c. module can conveniently provide. So we'll off-load the extra connections on to the "discrete" module, Fig. 10.8. Your circuit is Fig. 10.7. This is a sine-wave oscillator and buffer. To get a



good sinewave, VR1 is set so that the circuit just oscillates steadily. The frequency is about 1-6kHz.

## EXPERIMENT 10.5

### GATES

Now we'll make the two frequencies interact. To do this we'll use another standard digital circuit, a "gate". A CMOS gate is a sort of switch which is opened or shut

by applying a large voltage (for example, the full battery voltage) to its control terminal.

The gate we'll use is part of a 4001UB integrated circuit. Its symbol (Fig. 10.9) shows two inputs (1, 2) and one output (3). The little circle at the apex indicates that it's an inverting gate. That is, its output goes low when its input is high. Which input? In this case, either.

The 4001 contains four such gates. Their outputs go high if neither input 1 or input 2 is high. So this type of gate is

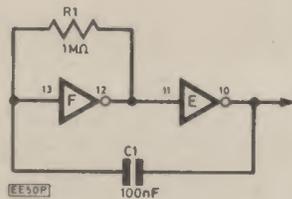


Fig. 10.6(a). Square-wave oscillator made from two inverters ("F" and "E") of a 4069 (IC1). Frequency about 6Hz.

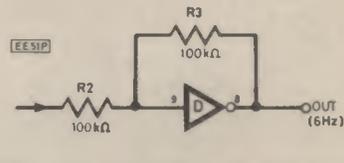


Fig. 10.6(b). Unity gain buffer amplifier (inverter "D").

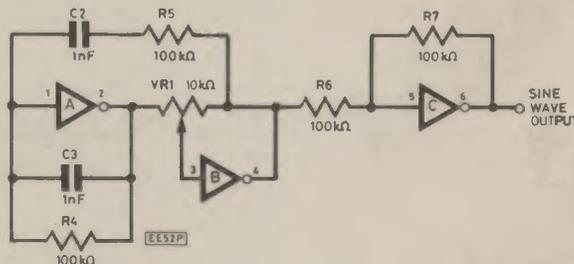


Fig. 10.7. Sine-wave oscillator using two inverters ("A" and "B") followed by unity gain buffer "C". VR1 sets the amplitude, which is greatest when the spindle is turned fully anti-clockwise.

called a NOR gate, and in this case it's a 2-input NOR Gate.

Insert the 4001UB integrated circuit (IC2) onto the yellow module, to the right of IC1. See Fig. 10.10.

If input 1 is driven low, for example, by connecting it to Vss) and input 2 is connected to the output of the sine-wave oscillator, then a 1.6kHz square-wave appears at pin 3, provided that the sine-wave input is big enough. What is happening is that positive peaks of the sinewave drives the gate output low, negative ones high. The crests of the wave are flattened in the process, turning the sinewave into a rectangular wave. The gate output goes low, high, low, high . . . at 1.6kHz. If input 1 is now connected to VDD (that is, driven permanently high) the 1.6kHz output is suppressed because the high on input 1 makes the output permanently low.

Now connect the output of your square-wave oscillator (Fig. 10.6a) to input 1. This makes input 1 sometimes high and sometimes low. When low, the

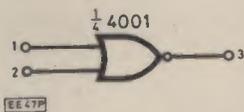


Fig. 10.9. A 2-input NOR gate. Four such gates are contained in the 4001 i.c., as shown on the accompanying EBBO layout (Fig. 10.10).

sinewave on input 2 can switch the gate on and off. When high the sinewave has no effect. The result is that the output is 1.6kHz periodically turned on and off at 6Hz. The sound in your earphone is a rapid sequence of "pips".

You can change the frequency of either oscillator by changing the R or C values.

Increasing R or C reduces the frequency. In the sine-wave oscillator (Fig. 10.7), use equal values for R4, R5 and C2, C3. If the sinewave is set to about 4kHz and the square to about 20Hz the combined output is a passable imitation of the ringing of an electronic telephone, if you turn the circuit on and off in the correct rhythm.

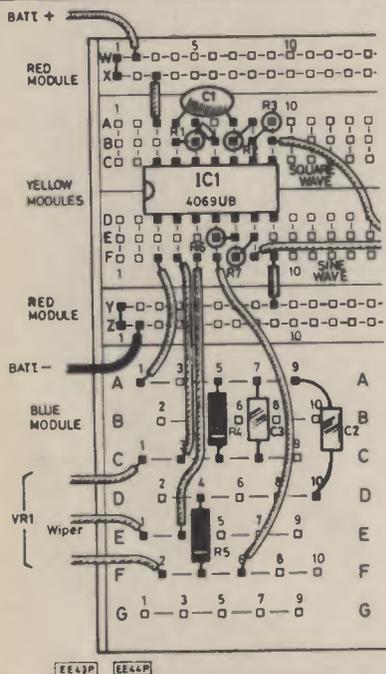
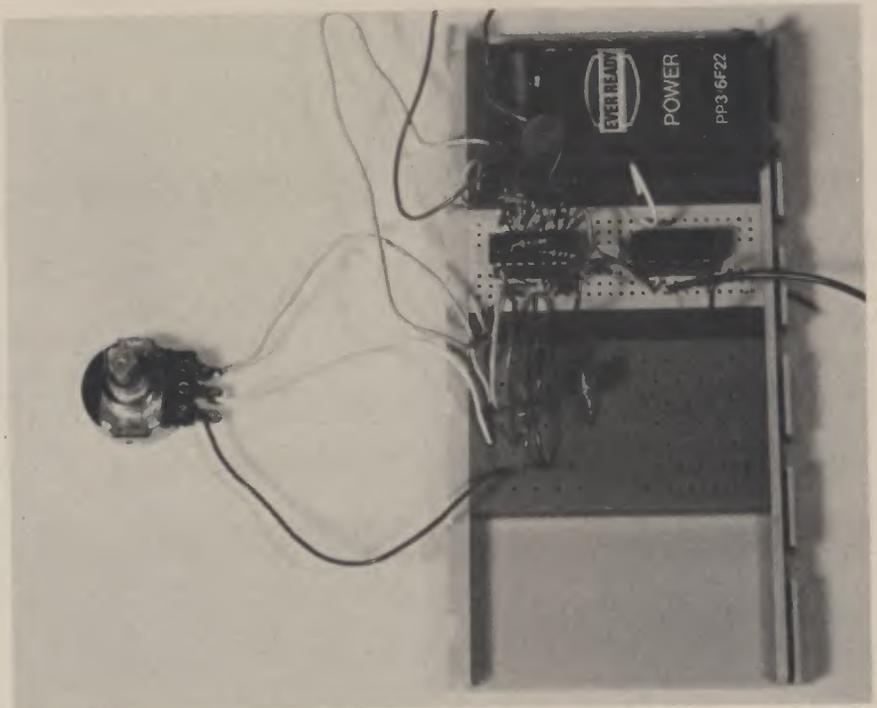


Fig. 10.8. Complete EBBO i.c. board layout for square and sine-wave oscillators and buffers, Fig. 10.6 and Fig. 10.7, respectively.

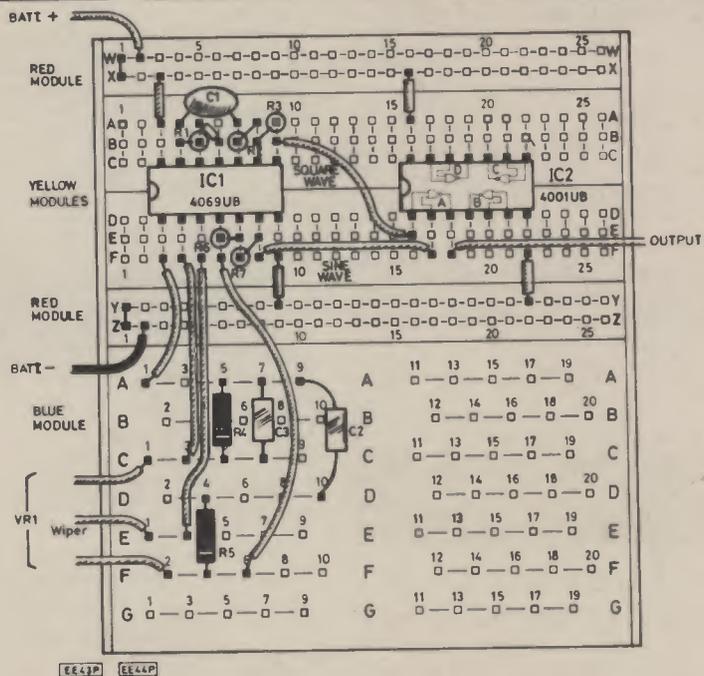


Fig. 10.10. The EBBO i.c. board layout for the 4001UB.

## USE YOUR IMAGINATION

Gates are very useful to the experimenter. In Fig. 10.11 a 2-input NOR gate (as in the 4001) has audio applied to one input and a "high" to the other via R1 and R2. Result: no audio output because the "high" on input 2 keeps the output low. If terminals A and B are connected together this removes the high from input 2 and audio reaches the output.

One possible use for this circuit is as an audible "continuity tester". If A and B are used as test terminals, when they are connected to opposite ends of a conductor audio reaches the output, indicating that the conductor is intact.

Clearly, the circuit could be used as an alarm, activated by closing a contact between A and B. It can check the polarity of a diode, connected across A and B. Sound emerges only if the anode is connected to A and the cathode to B, not the other way round.

For this sort of job it is useful to connect a loudspeaker to the output. Ordinary moving-coil loudspeakers cannot be used, but you can use a piezo-electric "sounder", which is a sort of grown-up version of a crystal earphone, tuned to particular frequencies. (An inexpensive type, the Toko PB2720, works well at about 4kHz.)

Note that R2 and C1 protect the gate against static; R2 limits the current and C1 absorbs much of the charge.

No doubt you can think of other possible uses. You get four gates in every 4001, at a cost of (at the time of writing this) about 15 pence. Incidentally, I've been rather slipshod with mine, because I've left the unused gates disconnected.

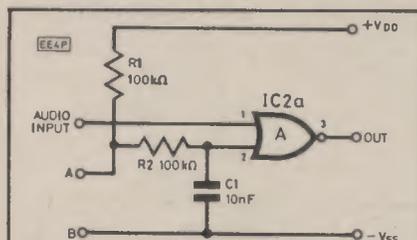


Fig. 10.11. This gate arrangement can be made to do many useful jobs.

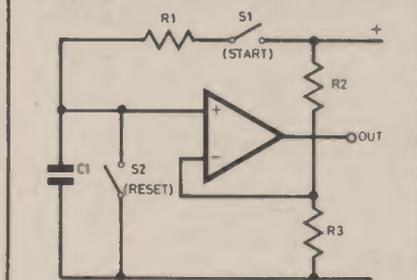


Fig. 10.12. Essentials of a timer circuit. Closing S1 allows C1 to charge via R1. Closing S2 discharges C1 and so resets the circuit. In timer i.c.s the functions of S1 and S2 are performed electronically.

It's good practice to connect unused inputs permanently to the + or - line to avoid the possibility of stray voltages getting to them.

Gates can be used as amplifiers. Connect the two inputs together and add a feedback resistance from output to input just as we did with the 4069. Two gates with strapped inputs can be used to make oscillators.

## NAND GATES

There's another common type of gate, the NAND gate. Its output goes low only when all its inputs are high. These can also be connected as amplifiers. A cheap example in i.c. form is the 4011 quadruple 2-input NAND gate.

## TIMERS

There are lots of integrated circuits designed for special purposes. Some are too specialised for general use, but there are many which are very adaptable. One such is the "timer" i.c.

The essence of a timer is illustrated in Fig. 10.12. Here a sort of differential amplifier, called a voltage comparator, has one input maintained at a steady voltage, the "reference voltage" via the divider, R2, R3. The other input receives the voltage across a capacitor C1 which at present is discharged. When S1 is closed, C1 charges via R1. When the charge voltage reaches the reference voltage the output of the comparator switches from low to high. The time taken depends on the value of R1 and C1 and on the reference voltage.

The change in output can be made to activate useful functions like switching an appliance on or off. It can also be made to operate a "reset" circuit which acts like S2 to discharge C1. In this case, the circuit can be made to go on charging and discharging C1. It is an "astable" circuit, an oscillator.

For practical purposes it is convenient to start the timing cycle by applying a voltage pulse rather than by throwing a switch like S1. So timer i.c.s incorporate a "start" or "trigger" facility. A type 555 timer i.c. with all these facilities can be bought for about 25 pence. You'll often see this particular i.c. used in designs in this magazine.

## COUNTERS AND FREQUENCY DIVIDERS

It is easy to make two-state circuits which are put into one state by one input pulse and stay in that condition until a second pulse is applied to return them to their original state.

When driven by a sequence of input pulses these circuits give out just half as many output pulses. That is, they divide the number of pulses by two. Two such circuits, one driven by the other, divide by

4, three by 8 ( $= 2 \times 2 \times 2$ ) and so on, doubling up every time.

It is possible to divide by intermediate numbers by arranging feedback which resets the divider when the appropriate pattern of states appears in the chain of two-state circuits. Thus a "divide by 16" circuit can be reset at 10. It then becomes a divide-by-ten, otherwise called a Decade Counter. Three decade counters in succession divide by 1,000 ( $= 10 \times 10 \times 10$ ).

The basic "divide by two" element is called a binary counter (or sometimes a "flip-flop" or a "bi-stable").

Quartz crystal clocks contain long chains of binary counters. Quartz, when vibrated, generates a voltage. This can be picked up by electrodes, amplified, and fed back to sustain oscillation at the natural frequency of the piece of quartz, which can be very stable. In quartz clocks and watches a frequency is chosen which when divided by a chain of binary counters gives one output pulse per second. For example, 4,194,304Hz yields 1Hz when divided by 2 twenty-two times.

In superhet radio receivers a quartz frequency can be used as the "local oscillation". By dividing the frequency one crystal can be made to yield a multiplicity of frequencies, to give, say, one tuning point every 100Hz.

## LOGICAL DESIGN

The starting point for any design is to analyse the requirement very carefully, step by step. Unless you are quite certain what a piece of equipment is intended to do you are unlikely to be successful in making it. At this stage the design is not electronic at all, but rather a written specification.

Suppose, for example, that you want to make a touch-operated switch. The electronics is easy. Indeed, you can get i.c.s to do the job. But the i.c. does only the electronic part. You, the designer, have to make sure that the electronics are compatible with the physical part, the finger on the pad.

You might, for example, use the idea of allowing a tiny current to flow from the pad through the finger and to earth. Very tiny currents (much too small to be noticed) can be used. But what if the person who touches the pad is wearing plastic boots which insulate him from earth?

Thinking of this may steer you in the direction of making a touch-pad split into two parts, so that the finger allows current to flow from one part to the other. If you settle on this solution, you must ensure that the current is sufficient, by making actual tests on fingers, in dry conditions as well as moist ones, and so on. And you must ensure that an accidental accumulation of dirt on the pad doesn't allow enough current for a false operation.

You must also think about what might happen in unusual circumstances. One solution to the touch-switch problem is to make the pad sensitive to the heat of the finger. This, in a particular case, caused a disaster. Somebody used heat-sensitive buttons to summon lifts in a tower block. When the block caught fire the heat activated the controls and brought lifts full of people to the floor where the fire was raging.

## HUMAN FACTORS

That cautionary tale illustrates the need to take all factors into account. Often the most important factors are the human ones. Designs must be compatible with the people who are to use them. Nobody (I hope) would give his grandmother a radio whose tuning control was so stiff that her poor old arthritic fingers couldn't turn it. But why have a tuning knob anyway? If the old dear never listens to anything but Radio Two wouldn't a single-station set be better?

It's surprising how often professional designers forget to think carefully about how their equipment is likely to be used. Recently I went shopping for a small bedside radio.

It should be obvious to any designer that small radios are likely to be used on bedside tables. It should then be apparent that such a radio is likely to be used in the dark. Many of the sets I looked at had to be rejected because their design was of the elegant slimline type which is doomed to be knocked over in the dark, when you wake up, realise you've left the radio on

## CHECK YOUR PROGRESS

Questions on *Teach In 84 Part 10*  
Answers next month

- Q10.1 Ten inverters are connected in cascade; that is, output of the first to input of the second, and so on. If the input to the first is high what is the output of the last: high or low?
- Q10.2 A 3-input NOR gate has all inputs tied together. A resistance of  $10k\Omega$  is connected from output to input. If  $V_{DD} = 10V$ , what is:  
(a) the approximate output voltage  
(b) what is the output voltage if the resistance is increased to  $10M\Omega$ ?
- Q10.3 In the sine-wave oscillator circuit (Fig. 10.7) what would be the likely effect of increasing R4 and R5 to  $1M\Omega$ ?

## ANSWERS TO PART 9

Q9.1 About  $160\mu A$ . There is  $0.5V$  ( $500mV$ ) across R4, which must be passing  $150\mu A$ . ( $mV/k\Omega = \mu A$ ). If  $V_{BE}$  for

TR2 is  $0.7V$ , its base is at  $0.7V + 0.5V = 1.2V$ . This leaves  $7.8V$  across R2, which passes  $7.8\mu A$  ( $V/M\Omega = \mu A$ ). About  $0.8\mu A$  of this is TR2 base current; the rest is TR1 collector current. The total is then  $157\mu A$  or  $160\mu A$  in round terms.

- Q9.2 There are two answers:  $39MHz$  and  $21MHz$ . Each yields a difference frequency of  $9MHz$  when "mixed" with a  $30MHz$  input signal. In the same way, with any given oscillator frequency there are always two signal frequencies which give the same i.f. The unwanted signal frequency, called the image frequency, must be heavily attenuated by a signal-frequency filter preceding the frequency-changer, or it will cause interference. Using a high i.f. makes this easier by placing the image frequency far from the wanted-signal frequency. But to get adequate selectivity at an i.f. of  $9MHz$  calls for an expensive i.f. filter of the quartz-crystal type.

and sleepily fumble for the off switch. I eventually chose one which was not only broad-based but had a tuning i.e.d. which shows up in the dark.


Commercially, good "human engineering" should pay off. Consumer advice

organisations draw attention to design deficiencies so a bad design must suffer. Your designs, I hope, will always be good ones.

Next month: New developments.
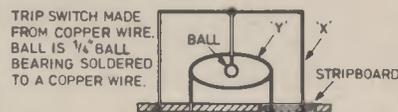
# CIRCUIT EXCHANGE

A project for beginners, using the 555 timer.




## MOTORCYCLE ALARM

In this circuit a 555 timer (IC1) is used as a monostable, and when triggered by pin 2 being brought low, drives another 555 (IC2) which is wired as an astable. The output from IC2 turns TR1, and thus the relay on and off. This gives a series of bursts of the horn for a time set by R2 and C1. Pin 2 can be triggered by a ball bearing tilt mechanism, as shown in the diagram.

This unit can also be used in cars by wiring the trip switch wire to the courtesy light. Pin 2 will be held high via the lamp, and will be triggered by the car door being opened. If this method is used it will be necessary to install an isolation switch outside the car.

G. Bamford,  
Cleckheaton,  
West Yorks.

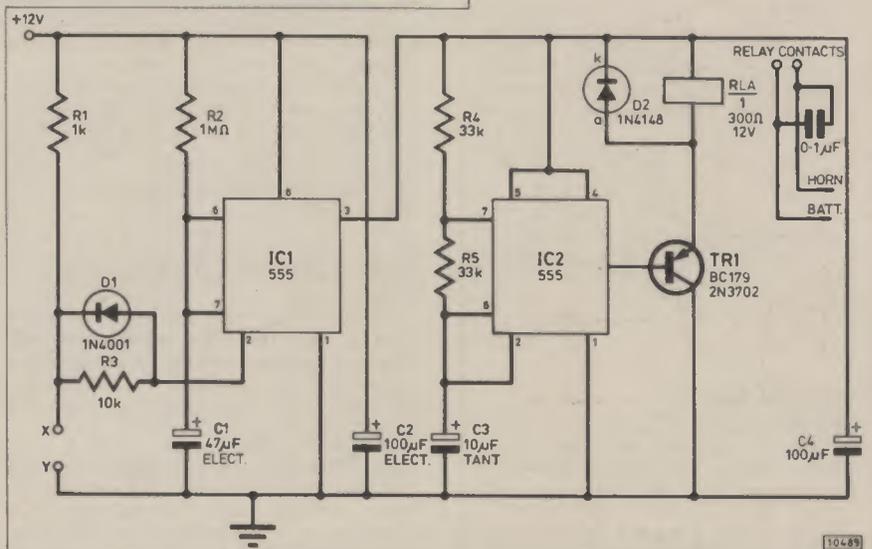

# FOR YOUR ENTERTAINMENT

BY BARRY FOX

## Video Dropouts

Dust is the big enemy of modern electronics. Recently I visited the Agfa tape factory in Munich and was reminded yet again of the lengths manufacturers must go to if they are to keep their product dust free.

Early domestic video tape suffered seriously from "dropout". That's a white blip on the screen caused by a gap in the magnetic coating.

Remember that on a modern video recorder the helical scan tracks are always under 50 microns in width and often half that or even less. That means the track is always narrower than a human hair.

So, if a speck of dust (or fleck of human hair!) gets into the tape coating it will mean that for a split second the video head is reading dirt instead of magnetic coating. As dirt is non-magnetic this means that there will be a (momentary) complete loss of signal.

Video recorders have a dropout compensator which is a small analogue memory, to fill in short gaps. But it can't cope with more than one line of the picture.

A line takes 64 microseconds to scan. When there is dropout shorter than a picture line the compensator just pulls out the last line of memory and uses it again.

Obviously if the dust speck is larger, the compensator is defeated. That's when you see a white blip on the screen—it's just a hole in the recording that the memory can't fill and disguise.

The standard requirement for domestic VHS video tape is usually no more than 50 dropouts a minute, each lasting no longer than 15 microseconds. When you bear in mind that on a VHS recorder the heads are scanning at a rate of 4.85 metres a second (which is 4.85 microns a microsecond), a 15 microsecond dropout is equal to a 73 micron fault in the coating—that's still not much wider than a human hair.

Most tape companies aim for a much lower, or better, dropout rate than the minimum standard requirement of fifty a minute. Agfa, for instance, aims for below 20 dropouts a minute on high grade tape and below 35 a minute on standard grade. Counting is of course electronic, and automatic, on cassettes sampled from the production run.

Incidentally, this helps clear up the age-old question; what is the difference between standard and high grade video tape? When I asked JVC's Japanese engineers once, they told me "high grade is better". When I asked in reply: "You mean standard grade is worse", they became very flustered!

## Down To Earth

All modern tape plants seal off vital areas of the coating machine where the hot mix of plastics binder and magnetic coating is applied to the thin, transparent plastics base film. This way any dust in the factory air cannot get into the coating mix or settle on the tape while it is still sticky.

The factory itself must also have a very clean atmosphere. In fact factory is the

wrong word. Most modern tape plants are more like hospitals. If visitors are allowed anywhere near the tape coating facility, they have to pass through an air shower which blasts any dust from their body. Or they must don protective clothing, hats and shoes. Often both precautions are taken.

At Agfa in Munich I noticed an interesting extra precaution. All the floors near the coating area are made of conductive material which is earthed by thick copper wires.

There are two reasons for this. If there is any build up of static in a building, there can easily be a spark. You know what happens in a dry centrally-heated atmosphere where there is a nylon carpet. Every time you touch metal there's a spark.

In a tape coating plant, where there are potentially explosive solvents in use, a spark could be very dangerous. Also a build up of static can mean a build up of dust. So

## Computer Time

I bought some computer equipment recently. It was like travelling in time back to the early days of the hi fi consumer boom. The ignorance of the people selling expensive equipment is beyond belief.

Several shops could not demonstrate a £500 printer to me because they quite literally didn't have the right connecting lead. Without the right connecting lead even the most expensive printer in the world is just a heap of useless junk.

One shop had the printer I wanted on demonstration and the salesman knew he had to alter the series of d.i.p.-switches to get it working properly. What he did was flip the switches randomly to see what happened.

Repeatedly, I suggested that he check with the instruction book. Only in desperation, after ten minutes of futile switch flicking, did he give in and try reading the instruction book. A specialist shop had Centronics and RS 232 plugs in stock, but not made-up leads.

All this is fine for the devoted computer enthusiast who avidly reads the specialist magazines and treats computing as a hobby. But Heaven help the small business that believes all the hype and tries to buy a personal computer for use as a business tool.

No wonder so many people have paid over the odds to buy an IBM PC. It's quite simply that they want to buy a *total system* from a well-known name which they feel they can trust.

My bet is that the hobbyist market will soon saturate. There is a limit to the number of people who want to play with computers as a hobby, rather than use them. There is also a limit to the number of computers any one hobbyist will buy.

It's what created the boom in hi fi music centres and rack systems. Astute electronics companies started to offer hi fi systems that needed no extra leads or technical knowledge to connect up. It's what made the video boom take off so fast, once it started.

it makes sense on both counts to earth everything from the floor upwards.

## Microchip Clean-Up

The anti-dust precautions needed in a tape plant are as nothing compared to those in a microchip factory. Toshiba in Japan has only now explained what it does to keep dust out of its VLSI plant at Kawasaki, near Tokyo.

It is at Kawasaki that the planning and production of 4-megabit, and even 16-megabit memories using micro lithograph technology to draw circuit lines 0.5 microns wide is carried out. That's 100th the width of a human hair.

This needs "super" clean rooms with dust limited to less than one particle of 0.1 micron size, per cubic foot of air. This is "Class 1" cleanliness. Compare this with around one million particles of such size in a cubic foot of air in a city street, or between 10,000 and 100,000 in a home or office.

The super clean air atmosphere is achieved by very dense air filters and a laminar air flow that comes down from the ceiling and is absorbed through the floor. Wherever possible sterile robots are used to operate machines and carry chips, rather than humans which have the nasty habit of shedding particles of skin and hair, however clean they may be.

Although a video recorder is by far the most complex piece of mechanical and electronic equipment you'll find in any home, it is remarkably simple to operate. Only the clock and timer need care and skill to understand.

Some people never use the timer on their video recorder or even set the clock. When a service engineer visited one home recently he asked why they had a piece of black tape over the window for the clock i.e.d. It was blacked out, the owners said, because it kept flashing "8s". No-one had ever learned how to set it to the right time!

## Friendly Vampire

Although computer firms keep talking about their equipment being "user friendly" most of it is still as friendly as a vampire. Of course when today's school children, who are weaned on computers, grow up and become businessmen and women it won't matter. But for many years yet there will still be a vast population of business people who are too old to have learned computing at school. They represent a vast untapped market for the computer equivalent of a hi fi music centre or domestic video recorder.

For what it is worth, my bet is that it will be the Japanese who cash in on this untapped market by offering low cost computers that are as easy to use as a music centre or video recorder. If you don't believe me, just remember what happened in the video market.

It was Philips who launched the first videocassette recorder, ten years ago. But it was the Japanese who waited a few extra years, learned by Philips's mistakes, and launched the VHS and Beta systems which now dominate the market. In fact Philips is now starting to manufacture VHS format recorders under licence from the Japanese and will be selling them in Europe by the end of this year.

# EVERYDAY ELECTRONICS PRINTED CIRCUIT BOARD SERVICE


Printed circuit boards for certain EE constructional projects are now available from the EE PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: EE PCB Service, Everyday Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Cheques should be crossed and made payable to IPC Magazines Ltd.

We regret that the ordering codes for the August projects have been incorrectly quoted in the Sept-Oct issues. Correct codes are given here.

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps.

Readers ordering both p.c.b.s and software cassettes may send a single cheque/PO for the combined amounts listed.

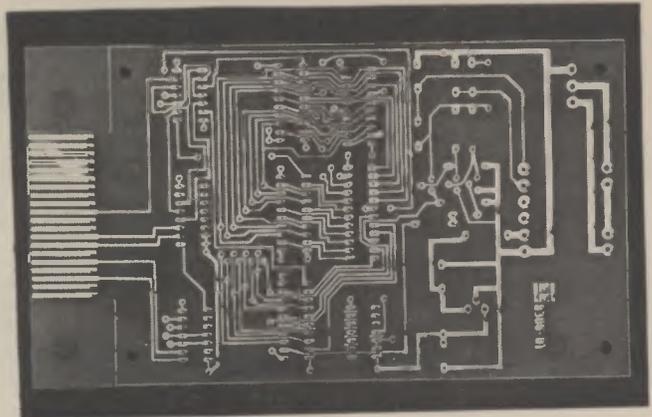**NOTE: Please allow 21 days for delivery. We can only supply boards listed here.**



Readers are advised to check with prices appearing in the current issue before ordering.



\*Set of four boards.

\*\*Calibrated with C1, VR1 and IC3 fitted.

M.I.T.—Microcomputer Interfacing Techniques, 12-Part Series.

PROJECT TITLE	Order Code	Cost
— JUNE '83 —		
Eprom Programmer, TRS-80	8306-01	£9.31
Eprom Programmer, Genie	8306-02	£9.31
Eprom Programmer, TRS-80 & Genie	8306-03	£1.98
— JULY '83 —		
User Port Input/Output M.I.T. Part 1	8307-01	£4.82
User Port Control M.I.T. Part 1	8307-02	£5.17
— AUGUST '83 —		
Storage Scope Interface, BBC Micro	8308-01	£3.20
Car Intruder Alarm	8308-02	£5.15
High Power Interface M.I.T. Part 2	8308-03	£5.08
Pedestrian Crossing Simulation	8308-04	£3.56
Electronic Die M.I.T. Part 2	8308-05	£4.56
— SEPTEMBER '83 —		
High Speed A-to-D Converter	8309-01	£4.53
Signal Conditioning Amplifier M.I.T. Part 3	8309-02	£4.48
Stylus Organ	8309-03	£6.84
Distress Beacon	*8309-04	£5.36
Distress Beacon Pocket Version	8309-05	£3.98
— OCTOBER '83 —		
D-to-A Converter M.I.T. Part 4	8310-01	£5.77
High Power DAC Driver M.I.T. Part 4	8310-02	£5.13
Electronic Pendulum	8310-03	£5.43
— NOVEMBER '83 —		
TTL/Power Interface for Stepper Motor	8311-01	£5.46
Stepper Motor Manual Controller M.I.T. Part 5	8311-02	£5.70
Digital Gauss Meter	8311-03	£4.45
Speech Synthesiser for BBC Micro	8311-04	£3.93
Car On/Off Touch Switch	8311-05	£3.11
— DECEMBER '83 —		
4-Channel High Speed ADC (Analogue) M.I.T. Part 6	8312-01	£5.72
4-Channel High Speed ADC (Digital) M.I.T. Part 6	8312-02	£5.29
TRS-80 Twin Cassette Interface	8312-03/09	£7.43
Environmental Data Recorder	8312-04	£7.24
Touch Operated Die (Dot matrix)	8312-05/06	£4.34
Touch Operated Die (7-segment)	8312-05/07	£4.34
Continuity Tester	8312-08	£3.41

PROJECT TITLE	Order Code	Cost
— JANUARY '84 —		
Central Heating Pump Delay	8401-01	£3.33
Biological Amplifier M.I.T. Part 7	8401-02	£6.27
Temp. Measure & Control for ZX Compr	8401-03	£2.35
Analogue Thermometer Unit	8401-04	£2.56
Analogue-to-Digital Unit	8401-06/07	£9.60
Games Scoreboard		
— FEBRUARY '84 —		
Eprom Programmer/ROM Card for ZX81	**8402-01	£7.84
Oric Port Board M.I.T. Part 8	8402-02	£9.56
Negative Ion Generator	**8402-03	£8.95
Temp. Measure & Control for ZX Compr	8402-04	£3.52
Relay Driver		
— MARCH '84 —		
Latched Output Port M.I.T. Part 9	8403-01	£5.30
Buffered Input Port M.I.T. Part 9	8403-02	£4.80
VIC-20 Extension Port Connector	8403-03	£4.42
Commodore 64 Extension Port Connector	8403-04	£4.71
Digital Multimeter Add-On for BBC Micro	8403-05	£4.63
— APRIL '84 —		
Data Acquisition "Input" M.I.T. Part 10	8404-02	£5.20
Data Acquisition "Output" M.I.T. Part 10	8404-03	£5.20
Data Acquisition "PSU" M.I.T. Part 10	8404-04	£3.09
Timer Module	8404-05	£3.58
A.F. Sweep Generator	8404-06	£3.55
Quasi Stereo Adaptor	8404-07	£3.56
— MAY '84 —		
Simple Loop Burglar Alarm	8405-01	£3.07
Computer Controlled Buggy M.I.T. Part 11	8405-02	£5.17
Interface/Motor Drive	8405-03	£3.20
Collision Sensing	8405-04	£4.93
Power Supply		
— JUNE '84 —		
Infra-Red Alarm System	8406-01	£2.55
Spectrum Bench PSU	8406-02	£3.99
Speech Synthesiser M.I.T. Part 12	8406-03	£4.85
Train Wait	8406-04	£3.42
— JULY '84 —		
Ultrasonic Alarm System	8407-01	£4.72
Atom EPROM Simulator	8407-02	£3.08
Electronic Code Lock	8407-03	£2.70
Main board	8407-04	£3.24
Keyboard		

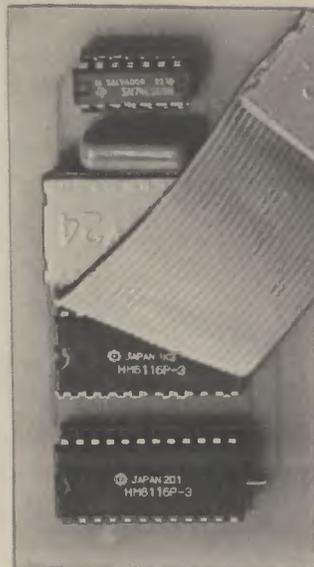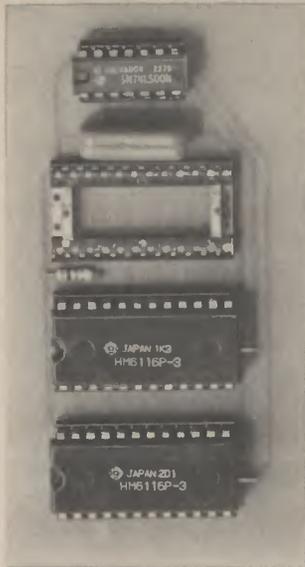

# Atom EPROM Simulator

J.R.W. Barnes

A LARGE number of EPROM programmer circuits have been published over the last two years. A simple programmer can be constructed for about twenty pounds. But, to develop EPROM-based software is a very lengthy procedure. To blow an EPROM takes fifty milliseconds per location, for example, a 2532 4K EPROM takes about four minutes. EPROMs must also be erased, this requires a special ultra violet lamp in its protective housing. These often cost several times the cost of the programmer. When de-bugging the software three or four EPROMs are required so that some can be erased while others are being programmed. The whole system can be very expensive.

## ALTERNATIVE SOLUTION

An alternative to using EPROMs for program development is presented in this article. An adapter has been designed so that RAM can replace ROM. The unit plugs into a 2532 socket and the only other connection required is to the READ/WRITE line. Programs either machine code or Basic can be written and run in the EPROM socket. Once the program has been proved it can be transferred to an EPROM.

Another significant advantage is that an assembler can be used to assemble the machine code directly to where it is going to be used. The alternative is to assemble the machine code elsewhere and then relocate the program by hand. In the case of the 6502 this relocation has to change the addresses of look up tables and jump instructions. Although the unit was originally designed for an Acorn Atom it should be possible to use the unit with several other computers.

## CIRCUIT DESCRIPTION

The complete circuit is shown in Fig. 1.

It is centred around IC1 and IC2, these are 2K by eight static CMOS RAM integrated circuits. A third integrated circuit, IC3, is used to provide address decoding. The truth table for the circuit enable lines is shown in Table 1. Neither of the memory circuits must be enabled if the chip select line of the host socket is high. If the chip select is low then the memory selected is dependent on the state of the highest order address line. This was implemented by four two-input NAND gates.

A11	CE	SELECT <sub>1</sub>	SELECT <sub>2</sub>
0	0	0	1
0	1	1	1
1	0	1	0
1	1	1	1

EE58P

Table 1  
Truth table for the circuit enable lines

Capacitor C1 provides supply decoupling. Resistor R1 is a pull up resistor on the READ/WRITE line.

The circuit obtains its power from the host computer.

## CONSTRUCTION

### CIRCUIT BOARD

The circuit was built on a printed circuit board 100 x 50mm. The track layout is shown in Fig. 2 with the component layout shown in Fig. 3. If readers decide to make their own circuit board great care must be taken where the tracks go

between the pins of the integrated circuits.

It is strongly recommended that sockets are used for the integrated circuits. Construction should begin with the wire links under the integrated circuits. The sockets and the other components should then be soldered in place. A Veropin can be fitted for the READ/WRITE line. Care should be taken with the orientation of the integrated circuits.

The prototype was not housed as during use it was fastened with double-sided adhesive pads to the bottom of the Atom. A second piece of printed circuit board material was bolted to the underside of the first, using spacers, to provide protection. A 24-way jumper lead is required to connect the circuit to the ROM socket, this can either be home-made or purchased from a supplier. It should not be longer than 30 centimetres.

## INSTALLATION

As the circuit is mainly of CMOS normal handling precautions should be taken. When the unit is not in use it is advisable to keep the spare connector in a piece of anti-static foam.

The unit is connected with the jumper cable to the ROM socket, the utility ROM socket is normally used, but the floating point socket may also be utilised.

A thin piece of flexible connecting wire is connected from pin 34 of the 6502 to the READ/WRITE pin on the board.

## TESTING

The RAM test program in "Atomic Theory and Practice", page 92, was used to test the memory, run the program, and test the memory from #A000 to #AFFF. This test should show the memory to be all right. If this test fails then carefully check the board for whiskers of solder between the tracks and the pads.

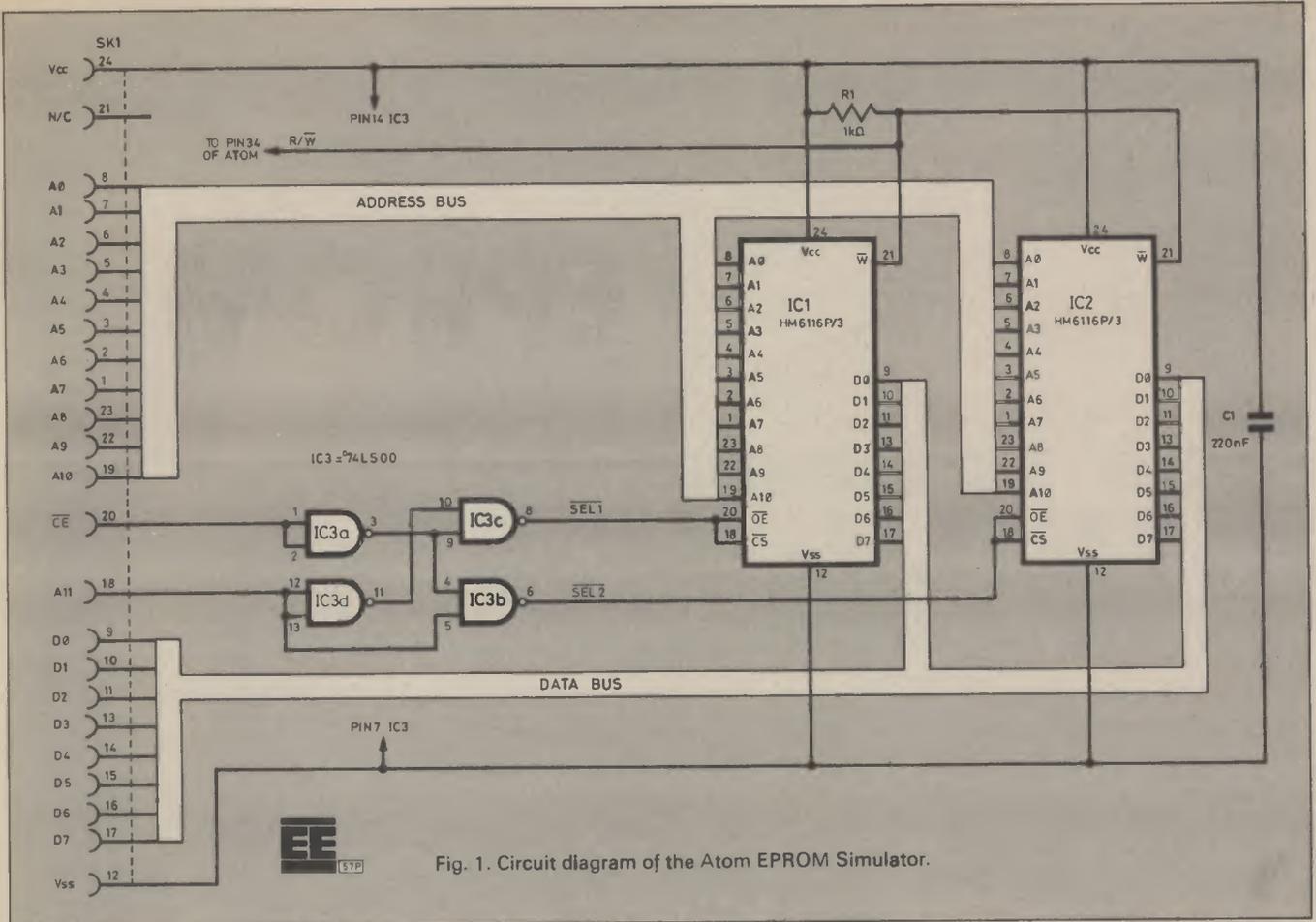


Fig. 1. Circuit diagram of the Atom EPROM Simulator.

## COMPONENTS

Resistor  
R1 1kΩ

See  
**Shop  
Talk**  
page 434

Capacitor  
C1 0.22μF

### Semiconductors

IC1,2 HM6116 2K by eight  
CMOS memories (2 off)  
IC3 74LS00 Quad 2-input  
NAND gate

### Miscellaneous

Single-sided p.c.b. 100 x 50mm,  
*EE PCB Service*, Order code  
8407-02; 24-pin d.i.l. sockets (3  
off); 14-pin d.i.l. socket; jumper  
cable 24-way 30cm long.

Approx. cost  
Guidance only **£18.00**

Fig. 2. Printed circuit board design.


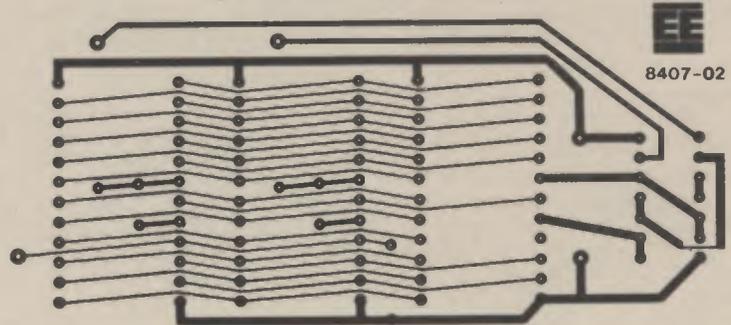


Fig. 3. Component layout.

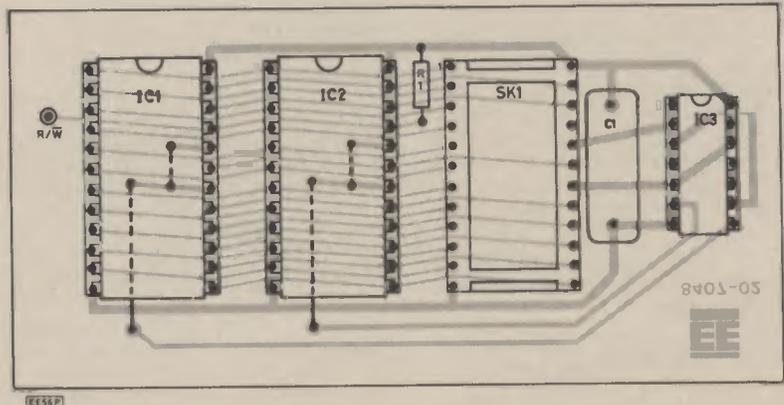

## USE

Basic programs can be written into the new memory by setting the text pointer to #A0.

```
?18=#A0 (return)
```

```
NEW (return)
```

A Basic program can now be typed into the new memory and RUN. It should be noted that the text space pointer has to be reset if the "break" key is pressed.

Machine code can be assembled into the new memory by setting the location counter, P to #A000 prior to assembling. For example:

When you have written your own software and you are sure that it is correct, an EPROM programmer can

```
10 REM RANDOM NOISE
20 DIM LL(2), NN(1), P(-1)
30 C=#B002
35 FOR N=1 TO 2
40 P=#A000
50[
60:NN0 LDA L;STA C
70 AND @#48; ADC @#38
80 ASL A;ASL A
90 ROL L+2; ROL L+1; ROL L
100 JMP NN0
120]
130 NEXT
140 LINK NN0
150 END
```

Table 2  
Program example for setting the location counter

then be used to store the memory from #A000 to #AFFF in a 2532.

Commercial software such as the "Wordpack ROM" and the various utility ROMs may be SAVE on tape using the following command:

```
*SAVE"NAME"A000 B000
```

with the ROM in the utility socket. The software can then be load back into the ROM/RAM unit described here and then run in the normal way. To load the software use:

```
*LOAD"NAME"A000
```

This is one way of avoiding the need for a ROM selector board. □

# COUNTER INTELLIGENCE

BY PAUL YOUNG

## Profile Of A Specialist

Last year I included in some of my articles, potted biographies of one or two of the better known component suppliers. It was a fascinating task, and one that, apart from general interest, I am sure was helpful to the would be entrepreneur, who wished to take up this line of business.

Continuing this trend, I made my way recently to the premises of Radio Component Specialists of 337 Whitehorse Road, Croydon, to meet John Ladd. This company is undoubtedly well known to our readers through their extensive advertising. I had met John Ladd many years ago through our business connections.

The first fact that emerged was, that we were both war-time pilots and we had both continued flying for several years after the war. John is still flying, when business interests permit, and holds a current private licence and an instrument rating.

Unfortunately, these revelations, hindered rather than helped my enquiries, because it meant inevitably we kept on digressing from electronics to aeroplanes. The time flew by, and, "At the end of the day", as the politicians and union leaders say with monotonous regularity, I found myself with only a few notes recorded. Naturally, with our readers in mind, I shall concentrate on the electronic prowess of our subject.

Radio was John's hobby before the war and he soon became proficient enough to take on a part-time job with a radio shop in South Croydon. His next advancement came in 1938 when he was appointed Service Manager for Drubel Radio Distributors. He had then reached the ripe old age of 15½.

In 1939 the war intervened and by 1941 John was flying. He was made a Flying Instructor in 1942. Later he was sent to do a course on heavy bombers, only to find by the time it was completed there was a surplus of bomber pilots.

The result was they sent him off to do a conversion course on *Typhoons* which were being used as fighter bombers. By the time that was finished so were the hostilities.

He returned to Drubels as a salesman which kept him busy for the next five years. In 1951 he went into partnership with Mr. Harold Livesey in a firm called Televox Radio Services. In 1954 he started on his own at 307A Whitehorse Road, Croydon. In 1955 Frank Jackson was taken on and later was made a partner. In 1959 he moved to his present address and in 1964 he acquired the firm of Baker Speakers.

At this point I was able to tell John a story about Baker Speakers that was unknown to him. Many years ago I visited the Baker factory and was intrigued to see a huge tank of goldfish. I was told they were used to test the high frequency response. John then introduced me to Eric Coppard who has been in charge of the Baker Speaker section since 1947. He was able to confirm my story of the fish test.

I asked John if he had had any lucky breaks that set him up. He said no, just steady progress, although the advent of commercial television when everyone wanted to buy Band Three Converter kits certainly gave the business a push in the right direction.

## Sound Approach

His undoubted success is due to sticking to sound policies, which I could sum up as follows:

- (1) Buy your premises (essential).
- (2) Limited objectives. Expand gradually and don't over-trade.
- (3) Concentrate on one or two aspects and do them well. In John's case, audio, hi fi and large wattage amplifiers, including disco equipment. He also stocks an impressive range of standard components which is listed in his 20-page brochure.
- (4) Give good service after-sales and always have at least one technical person on hand. John not only does this but gives a 12-month guarantee on all the goods he supplies.

Like the rest of us, John has felt the effects of the recession and the diversification caused by Home Computers but much of his business comes from good-will and

recommendation. He has been in business for 30 years and I am sure he will be there for many years to come.

## Weathering The Storm

I was naturally very pleased to receive several letters from readers on the subject of Ionisers. There is a divergence of opinion as to whether colour televisions emit positive ions.

Having been in the business for 15 years, Medion Ltd. of Oxted in Surrey say, "We can reassure readers that colour televisions do not emit positive ions". But they go on to say, "that in the vast majority of sets they tested, the television screens built up a large static charge, this resulted in no negative ions, and some 1000 positive ions per cubic capacity at typical VDU operator distance. In the case of the VDU operators this can result in headaches, lethargy, and sore eyes."

Fortunately Medion concludes, "The output of even the smallest negative ioniser is sufficient to suppress the screen charge and to maintain a healthy ion level." They also manufacture an atmospheric ion analyser which can measure the amount of positive or negative ions in a room or in the atmosphere. The price is £1495.

Another reader, Graham Lewis, kindly sent me a leaflet from a firm which markets an ioniser under the name, Mountain Breeze Air Ionisers. They make the claim, "If you feel the difference before and after a thunderstorm, you have already experienced the effect of air ionisation."

I asked Mr. P. Laws, Manager of Medion Environmental Division what the implication of this was, and he explained that before the storm breaks, there is a heavy build up of positive ions, after the lightning it is reversed, resulting in a large surplus of negative ions. They say you learn something new every day, I think in electronics it is more likely to be every hour.

## Changing Times

I suppose it had to happen. The Japanese have made a watch with a built-in computer. Made by Seiko, it can memorise 2000 characters, store 100 words in two languages and costs around £200.

At the other end of the scale, I noticed my Garage offering five function watches for sale at £1.49. "How much to change the battery?" I asked the lad. Back came the answer, "£1.50 Guv". I give up, this high finance is too difficult to work out!

# AUGUST FEATURES...

## MICROWAVE ALARM SYSTEM...

Built into a hi fi speaker cabinet, this microwave doppler intruder alarm has a range of 8m, yet is completely self-contained, requiring no external wires. The unit measures only 245 x 155 x 155mm.

## KITCHEN APPLIANCE TIMER...

Ever needed a third hand in the kitchen? This is it—a useful project with lots of practical applications. A timer which can switch mains appliances up to 5A, with a fully adjustable time setting.

## TEMPERATURE INTERFACE for BBC...


Using the machine's own four channel A to D converter this article shows how a simple temperature interface can be made with good linearity and accuracy over a temperature range of  $-50^{\circ}$  to  $+150^{\circ}$  Centigrade.

**FEATURE ARTICLE: WHAT IS RADIATION?**

EVERYDAY  
**ELECTRONICS**  
and computer PROJECTS

**AUGUST 1984 ISSUE ON SALE FRIDAY, JULY 20**

# ANATOMY OF YOUR MICRO

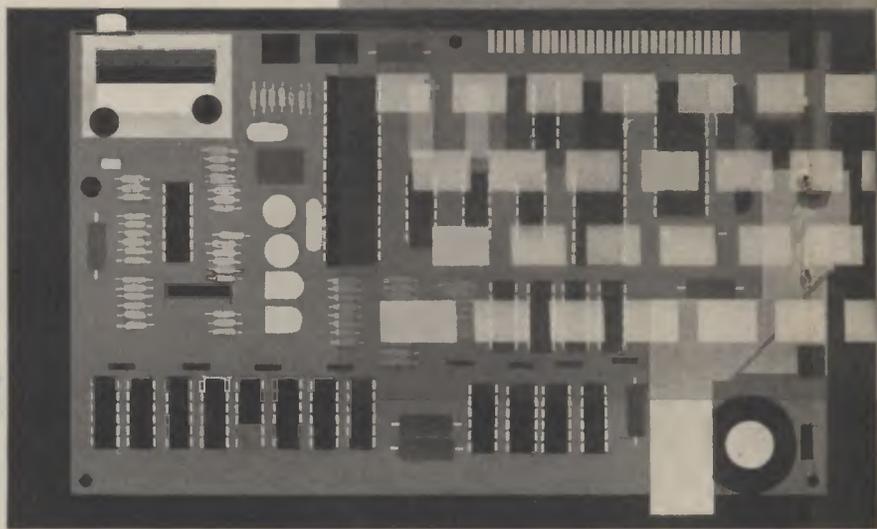

**T**HERE are now more microcomputers per person in the UK than in any other country. But what really goes on underneath the keyboard? This series begins by examining the internal workings of a typical microprocessor—the “heart” of any microcomputer. Later parts will consider how memory space is allocated and how it can be used, and the requirements for interfacing to cassette recorder, disk or TV display.

Of all the devices which have been produced as a result of microelectronics, the microcomputer is the one which seems to have made the greatest impact on the average person. Of course, there are digital watches and clocks, there are pocket calculators in a multitude of designs, and many of the circuits in radio sets and TVs are based on microelectronics, but these developments have been largely taken for granted. They have never roused the public interest to the same extent as has the micro. A glance at the newsagent's shelves, which today carry well over a dozen popular magazines devoted to microcomputing, confirms the extent of this interest. Interest in micros is not only more widespread than interest in other aspects of microelectronics, but is more intense. People rarely want to know what goes on inside a digital watch or a TV set, but they *do* want to know what is happening inside their micro. Perhaps it is the way in which a micro seems to be almost human at times—be it clever, stupid, helpful, or just plain awkward!—that makes us think there is “something” there which we want to know more about.

This is the reason for trying to in-

roduce you to what goes on inside the typical home computer. We know it does not *really* have its own personality, but it does have a complicated assembly of electronic circuits which are somehow made to behave in this almost-human fashion. It is the anatomy of these circuits which is the subject of this article. Although the circuits themselves are complicated, the principles by which they operate are relatively simple. We shall be concentrating on the principles rather than on the details, and only a minimal knowledge of electronics will be assumed.

## BINARY SIGNALS

Although you can “talk” to your micro using a language such as BASIC, which has many ordinary English words, the circuits of the micro really understand only two words—true and false. These words have exactly opposite meanings, and no half-truths are possible. As might be expected, an electronic circuit does not recognise these words as such. Instead, it recognises distinct voltage levels. Micros are normally based on TTL circuits, and these recognise two voltage levels, which we refer to as “high” and “low”. A “high” voltage is one between +2V and +5V (the maximum). A “low” voltage is one between 0V (the minimum) and 0.8V. Having to respond to only two different voltages, the TTL circuits can be designed to be fast-acting and extremely reliable. They can also be manufactured very cheaply, which is one reason that micros are so popular today.

“True” and “false” are opposites. So

are “high” and “low”, in the sense used above, for the circuits do not recognise any in-between voltages. If we make “high” equivalent to “true” and “low” equivalent to “false”, we can now talk to the micro by feeding high or low voltages to the input terminals of its circuits. Sometimes this is done by pressing a key. The key *is* pressed, giving a closed circuit, or not pressed, giving an open circuit. There is nothing in between. Repeatedly, we find this idea of two opposites, with no in-betweens. Everything is in *twos*—everything is *binary*.

This leads us directly to a way of expressing numbers to the computer. If we take “true” (or “high”) to mean “1” and “false” (or “low”) to mean “0”, we can send numbers to the micro. Such numbers consist only of “1”s and “0”s, but this binary system is capable of expressing numbers of any size. Binary numbers tend to have more digits than their decimal cousins, as can be seen in Table 1. When we speak of the digits which make up a binary number, we usually call them “bits”, which is short for “Binary digITS”.

Not only do we express numbers in binary form, but we also design the circuits so that they accept certain combinations of bits as instructions. For example, the number “01001100” instructs the relevant part of the micro to jump from one part of its program to another. Whether a number is taken to be a number or a coded instruction depends upon what stage the micro is at in its cycle of operations.

For most purposes, including sending coded instructions, it is sufficient to have

Table 2, Features of Popular Micros, from Ace to ZX-81

NAME	MPU	ROM (K)	RAM (K)	SPECIAL FEATURES
Ace	Z80-A	8	3	Uses FORTH
Amstrad CPC464	Z80	16	64	Built-in cassette deck
Apple II	6502	12	48	
Apple IIe	6502A	16	64	
Atari 400	6502	8	16	Sound gen.
Atari 800	6502b	8	48	Sound gen.
Atari 1200	6502	8	64	GTIA graphics chip (256 colours) Sound gen.
Atom	6502	8	2	
BBC micro (Model B)	6502	32	32	6522 I/O, D-to-A
Colour Genie	Z80	16	16	Sound gen.
Commodore 64	6510	26	64	Sound gen. Video chip
Dragon 32	6809	16	32	
Electron	6502	32	32	Sound gen.
Epson HX-20	6301	32	16	Portable, l.c.d. display
Lynx	Z80-A	16	48	
Oric Atmos	6502A	16	16	Sound gen.
NewBrain	Z80-A	18	32	Portable l.e.d. display
Sharp MZ-80A	Z80	4	48	No resident language
Sharp MZ-80B	Z80-A	2	64	No resident language
Sord M5	Z80-A	8	4	Sound gen.
Tandy Colour	6809E	16	16	
TRS-80	Z80	12	16	
TI-99/4A	9900	16	16	Sound gen.
VIC-20	6502	16	5	Video Interface Chip
ZX-Spectrum	Z80-A	16	16	
ZX-81	Z80-A	8	1	

## PART ONE OWEN BISHOP

numbers with up to eight bits. This allows them to have 256 different values (0 to 255, inclusive). We can code up to 256 different instructions in this way. If we want to use values greater than 255 in our calculations, there are ways of representing larger numbers as several 8-bit binary numbers. An 8-bit binary number or code is called a *byte*.

Having seen some of the essential features of how the parts of a micro can communicate with each other or with the user electronically, we are ready to see what parts there are and what they each do.

Table 1. Binary Numbers and Their Equivalents in Decimal

BINARY	DECIMAL
0	0
1	1
10	2
11	3
100	4
101	5
110	6
1000	8
1111	15
10000	16
100000	32
1000000	64
10000000	128
11111111	255
100000000	256
1000000000	1024 (1K)
1111111111111111	65535

### THE HEART OF THE MICRO

At the heart of the micro is the microprocessor. This is a complex integrated circuit which controls all other parts of the micro and does most of the work besides. There are dozens of different kinds of microprocessor (or MPU), but two types in particular, the 6502 and the Z80 are commonly used in personal micros (see Table 2). We will look inside the 6502 to see what it contains.

Like all MPUs used in personal micros, the 6502 is an 8-bit device. That is to say it handles eight bits (or one byte) at a time. It has a number of registers, each of which holds a byte (Fig. 1.1). Each register consists of a set of eight bistable circuits (or flip-flops) which can be in one of two states. In one state (flipped) it can be said to hold a "1", in the other (flopped) it can be said to hold a "0". Once again, we come across the binary idea. A flip-flop has no in-between state. Depending on the state of each flip-flop, a register can hold the equivalent of any one of the 256 binary numbers or codes.

The most important register is the *accumulator*. This holds the number upon which the MPU is currently working. Numbers can be transferred between the accumulator and other parts of the micro. While the number is in the accumulator, it can have other numbers added to it, for example, or be operated on in many other ways. Additions and other arithmetical and logical operations are done by the

arithmetic logic unit (ALU). This is where the main activity of the microcomputer takes place.

The X and Y registers can also be used for holding numbers, which can be operated on in various ways. A major part of the activity of the MPU consists of passing numbers between the ALU, the accumulator and the X and Y registers. All these operations are supervised by the control circuits. The operations involved are actually very simple. In order to do anything worth while, the MPU has to do very many operations in succession at extremely high speed. To help it work as quickly as possible, the registers are connected to a set of eight lines, known as the *data bus*. Data can be transferred between registers a byte at a time. This bus also goes to the terminal pins of the MPU (via the data bus buffer) and joins to the data bus of the micro (Fig. 1.2). This carries data (numbers or instructions) between the MPU and the other parts of the computer.

The program counter is the register by which the MPU remembers how far it has got in its program. A program with only 256 steps would not be a very extensive one, so this register stores two bytes, allowing it to hold binary numbers up to 65535. The fifth register is the processor status register. The bits held here act individually as "flags" or indicators. For example, one of them is the *carry flag*. When this is "1" it indicates that the result of the previous addition left a "1" to be carried over to the next addition.

The "zero" flag is set to "1" whenever the result of any operation leaves all zeros in the register concerned. Information stored in this register is very useful for certain types of calculation and logical operation.

## THE CLOCK

With so many numbers being transferred in and out of the MPU and between the various registers, it is essential that all these operations are synchronised. This is the function of the clock, a crystal-controlled oscillator (Fig. 1.3). The frequency of the crystal is usually several megahertz, so that the time taken by one cycle of operation of the MPU is of the order of 1 or 2 microseconds. This is why the micro is able to perform so many operations so very quickly, which is the key to its apparent cleverness. It is not so much that it can do complicated and clever things, but that it does long sequences of very simple things extremely quickly, without making mistakes.

## OP CODES

We have seen that the MPU has the facilities for performing a range of operations on numbers taken into its registers from other parts of the micro, but how does it know which operations to perform? Its instructions are stored in the memory of the computer as a series of bytes. There is more to say about memory later, but let us assume that, when the MPU wants to know what to do next it is able to go to the part of its memory indicated in its program counter register and there find an instruction. It reads this byte in one operation, for the eight bits of it can be transferred to the instruction register of the MPU along the eight lines of the data bus. Let us suppose that the byte it receives is "10101001". Because the MPU is at the stage of its operation when it is looking for an instruction, it interprets this byte as an instruction, not as a number. It puts it in the instruction register. Since this is a coded instruction to the MPU to perform an operation, we refer to this byte as an *op code*. This particular op code tells the control circuit of the MPU that it is to take a number from memory and put it into its accumulator. Which number? Given this op code, the number is to be found stored in memory in the location immediately following that in which the op code itself was stored. So the MPU increments its program counter and goes back to memory and receives the next byte along the data bus. This time it is expecting a number and the byte it receives is put into the accumulator and treated as a number, not as an op code.

Some op codes are sufficient on their own; the code "10011000", for example, tells the MPU to transfer the contents of the Y register to the accumulator. Other op codes are followed by two bytes, both to be taken as numbers. Such a code is the "jump" code mentioned earlier. It is



Any microcomputer system requires an input facility (keyboard), a display for output (TV), and some long-term storage medium (cassette or disk).

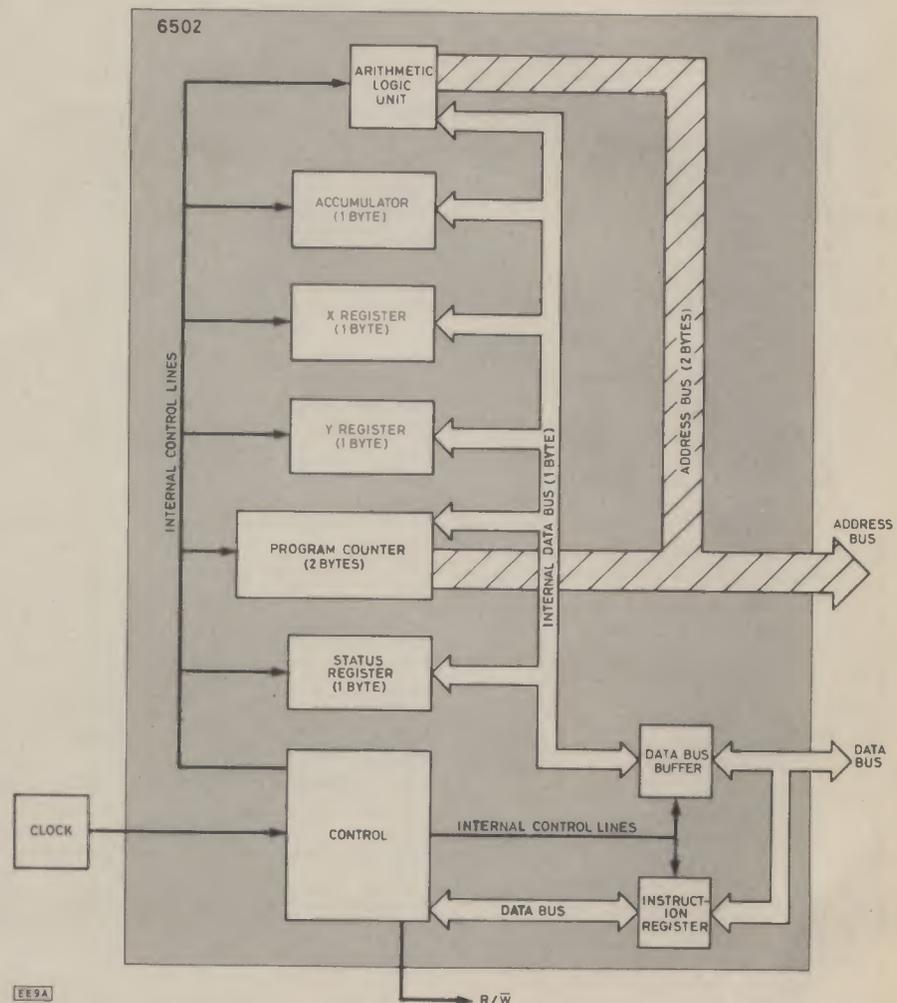


Fig. 1.1. The main sections of the 6502 microprocessor. Arrowheads indicate direction of control, or flow of data.

followed in memory by two bytes, to be put into the program counter, so that the MPU then jumps to the part of memory specified by these two bytes.

From the above, it can be seen that the MPU is programmed by a sequence of bytes stored in a given order in the memory of the micro. Some of these bytes are op codes and the others are numbers. Some of the numbers are values being used in calculations, while others are the addresses of different locations in memory.

## ADDRESSING

We have touched upon the idea of addressing earlier, and now will examine it in more detail. If memory is to hold many bytes and the MPU is to be able to take in these bytes as data or instructions, or perhaps send out data to be stored in memory, it follows that it must be possible to identify every location in memory in which a byte can be stored. This identifying number is what is called its *address*. As we have seen, the program counter holds 16 bits, so an address can be any number between 0 and 65535 (Table 1). Each location in memory must be informed when the MPU wants to receive data from it or put data in it. We therefore need a 16-line bus, the *address bus*, to which all parts of the computer's circuits are connected (Fig. 1.2). Each part responds when and only when its own address is present on the bus. When we say that an address is "present on the bus" we mean that the voltages on the 16 lines are "high" or "low" corresponding to the pattern of "1"s and "0"s which make up the address.

The address bus runs from the MPU to all other parts of the micro. In particular, it goes to the integrated circuits which make up memory, and to circuits concerned with the keyboard, the video screen and the input/output ports. We shall deal with all these later, and will also consider how a device knows when its address is on the bus.

## READING AND WRITING

The address bus gives the MPU control of the flow of data in the system, for it is only when the address of a given device has been put on the bus that the device can become active. In addition to this bus, the MPU has a number of control lines, collectively known as the *control bus*. One of these lines controls the direction in which data flows—this is the "read/write" line, usually shortened to R/W. It is a convention that when a line is normally held in the "high" state, but is made "low" for a given action to occur, we draw a bar over the name of that line. The MPU can read from memory when the line is high, and in order to write to memory, it takes the line low.

**Next Month:** The control of data flow, and how memory is partitioned into areas.

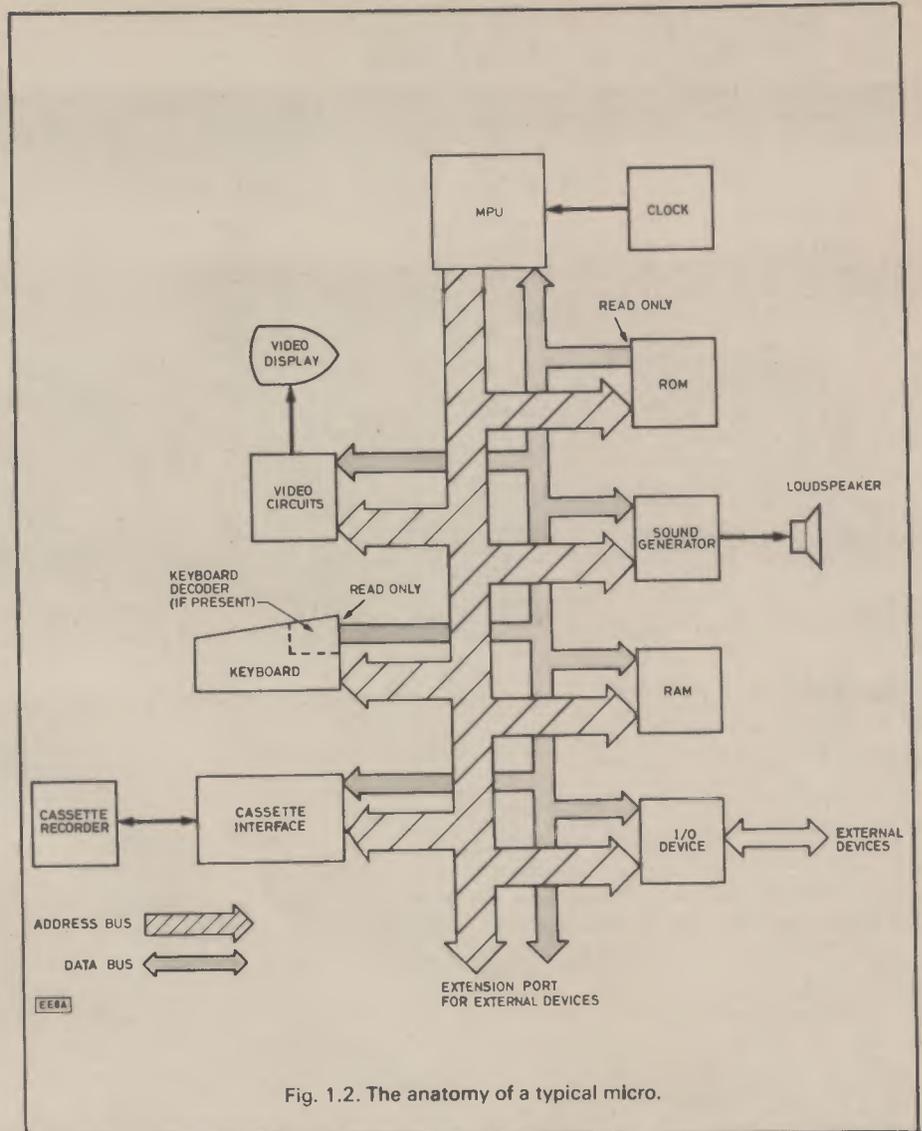


Fig. 1.2. The anatomy of a typical micro.

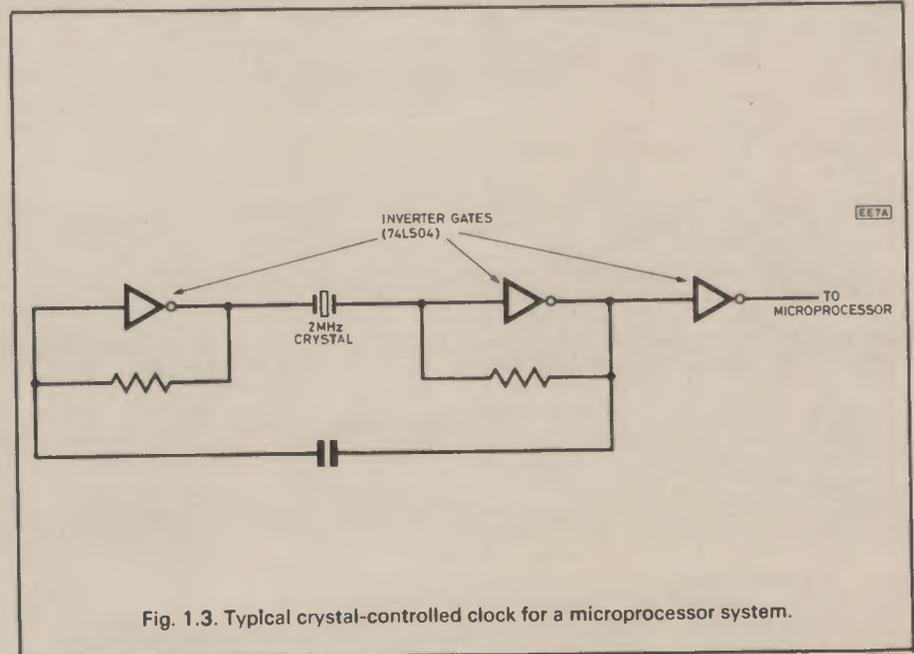


Fig. 1.3. Typical crystal-controlled clock for a microprocessor system.

# EVERYDAY news

... from the world of



— A NEW FAMILY SHOW TO BE HELD IN CENTRAL LONDON  
— ALL ASPECTS OF ELECTRONICS WILL BE ON DISPLAY

**A**N important new event has just been announced for the autumn showtime season and EVERYDAY ELECTRONICS, in conjunction with our sister publications, will be there.

Recognising the importance of this new show we have agreed to join forces with other publications and sponsor this exciting addition.

Called *Leisuretronics*, it promises to be a truly *all* electronics family show that will highlight the impact "amateur" involvement has had on the application of electronics today and also point the way to future developments.

To be held in the heart of London—**8 to 11 November**—at the Royal Horticultural Hall, Victoria; the show will present items from the field of radio controlled models to electronic music; ham radio to hi fi; robots to photography; a synthesiser to satellite broadcasting; and electronic games and computing to disco and light shows.

Special features will be mounted by the organisers to give

visitors the opportunity to see the latest developments in most of the above areas in "live" action.

Although this is a completely new event, the Organisers, Trident International Exhibitions have many years' experience in putting on this type of public exhibition. Commenting on the new event, David Timmins of Trident said, "We are confident that *Leisuretronics* will prove to be an excellent market-place for companies to reach new customers and for the enthusiast to discover and explore new ideas!

"The technology of electronics has brought new life to many leisure-time activities and *Leisuretronics* aims to combine all elements of the hobby industry into a totally new and imaginative show that will excite and attract a large audience."

*Being only a short "bike ride" from Westminster, who knows, perhaps some of the M.P.s, from all parties, might like to come along and see what is really happening in the world of electronics now!*

## ROYAL AWARDS

*Prestel, British Telecom's world-leading communications system has received the Queen's Award for Technological Achievement.*

*The Queen's Award goes to the Videotex Section of British Telecom's research laboratories at Martlesham Heath, Suffolk and Prestel Headquarters in the City of London.*


## DESIGN AWARDS

*A combined plotter and display system, for several*

*applications, including bank note design, and with a digitiser incorporated for automated cartography, has won a 1984 Design Council award for Laser-Scan Laboratories Ltd. of Cambridge.*
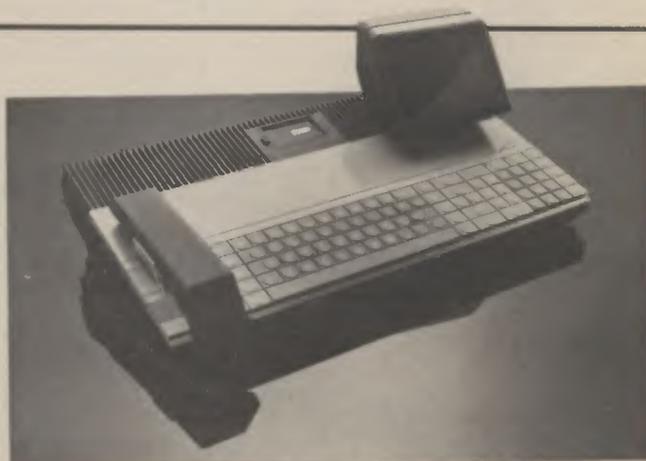
## Executive Award

*Following on from its 1983 Award for the Perfector telex system, STC Telecommunications of Brighton have won the 1984 Award for Executel, a sleek desk-top unit that combines telephone, electronic diary and telex terminal.*



## RAINBOW TOPS

Claimed to be the world's second largest computer manufacturer, Digital Equipment Co. Ltd. have "loaned" five Rainbow 100 personal computers to assist in the retraining of unemployed and redundant people attending a TOPS course at the South Bank Polytechnic, London.

The course entitled *Information Technology and Salesmanship* aims to teach students to use computer technology and to acquire the associated selling skills. The students are taught BASIC and learn to use four applications packages (provided by Digital), including word processing, accounting, spreadsheet and database functions. During the course the students also complete a project.

## Summer School

Nottingham University is the venue for the *Information Technology Summer School* being run by the Information and Word Processing Association, from 17 to 19 July.

This is the fourth of the annual Summer Schools, for which an excellent reputation has been established. The programmes are specially designed to be of value to delegates from both industry and education, providing a forum where teachers and lecturers can exchange ideas and discuss the latest developments in IT with managers and professionals from the business world.

The summer schools are always popular events and intending delegates would be well advised to book early.

## Electromusic Calls The Tune

The British company, Electromusic Research has just produced its first MIDI package for the BBC Computer.

Miditrack is a manual (step) input program that enables music composition on up to six tracks, with full memory assignment of 7500 notes for the number of tracks selected.

Each Miditrack will store details of note pitch, dynamics, length and style as well as voice change and other parameters. Traditional note input is entered from the BBC B keyboard in order to avoid coding unfamiliar to the musician. Full on-screen editing features are included.

## Quality Offer

In support of the National Quality Campaign, The British Standards Institution is now offering its well-known Handbook 22 Quality Assurance at a special price of £8 per copy. This offer is made possible through the help of the Department of Trade and Industry who want to see this publication in the hands of as many British companies as possible. The Handbook is usually priced at £78 to non-members of BSI and £39 to members.

The number of copies available on this special offer is limited and buyers are urged to place orders as swiftly as possible. They should send cash with order to BSI Sales Department, Linford Wood, Milton Keynes, MK14 6LE.

Orders should be submitted on official company headed paper, signed by the chief executive, and cheques should be made payable to the British Standards Institution.

Colchester based microcomputer company Dataview is participating in Britain's first International Garden Festival in Liverpool.

Dataview has joined forces with Stack Computers of Liverpool to display the latest developments of the microcomputer industry.

The London Borough of Ealing will become the first user of a new leisure activity booking system launched by Quota Computer Associates Ltd.

INMOS has appointed *Celdis Italiana SpA* as their distributor in Italy. A member of the successful UK based Unitec Group, *Celdis Italiana*, is the leading high technology components and systems distributor with offices throughout Italy.

## Computer Calls

British Telecom have announced that they are to go ahead with a major computing development programme to provide new business information systems for use in its local offices.

The new system, to be known as customer service systems (CSS), will be fully integrated and controlled locally. Each district will have its own computing centre, and there will be about 30 in all.

The initial systems development will be undertaken by a joint team of BT and Logica staff with support from McKinsey and Co.

## THE PEOPLE'S COMPUTER

The hi-fi and television manufacturers, Amstrad have launched what they call "The People's Computer" claiming that it will bring the home computer within reach of almost every family in the country.

The subject of this claim is called the CPC464; a complete system priced at £229 and featuring a built-in cassette recorder, its own monitor, 64K of RAM and just one mains lead: the power supply for the computer is in the monitor.

There will be four models in the CPC464 range: System 1, keyboard with built-in cassette and green monitor (£229); System 2, keyboard and a colour monitor (£329); System 3, keyboard, disc drive and green monitor (£429); System 4, keyboard, disc drive and colour monitor (£529).


All models of the CPC464 will be available from traditional stockists like Rumbelows, Dixons, Comet and Boots.



# ULTRASONIC BURGLAR ALARM

I.F.H. GOULT

Part 2 of the Surveillance series

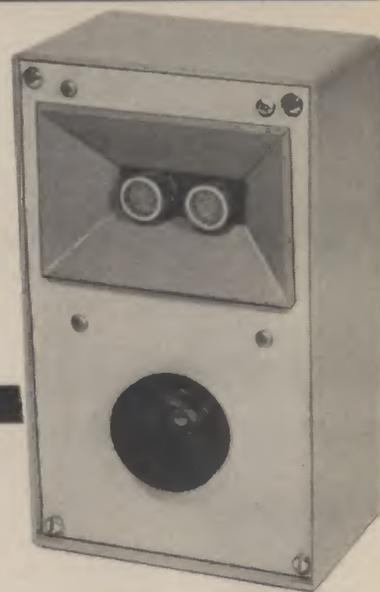

THE Ultrasonic Burglar Alarm has been designed to provide a simple low cost unit which is self-contained, operating from an internal battery. Any person crossing the ultrasonic beam will trigger a screeching piezo-electric sounder mounted in the unit. A relay may be used instead of the sounder to operate an alternative alarm.

The unit is designed to be placed across the access to a room, or across the hallway or stairs. By careful placing it can be arranged that household pets will not trigger the alarm. A beam-break device also has the advantage of enabling movement in other areas away from the guarded access.

Being portable it could also be used to prevent unwelcome visitors in your hotel room when on holiday, without inhibiting your own movement within the room. The unit also illustrates many basic electronic principles, each of which is fully explained in the following circuit description.

Its range is deliberately limited to around two metres, for use across a doorway or landing, in order to eliminate the possibility of false alarms.

## CIRCUIT DESCRIPTION

The circuit diagram is illustrated in Fig. 1. First, the transmitter. IC2 contains four CMOS NOR gates. Two of these are connected as a multivibrator oscillator. VR1 is adjusted to set the frequency of oscillation to 40kHz. The output from the multivibrator is connected to the two remaining gates as illustrated. An ultrasonic transducer is connected between these two gate outputs. When one output is positive the other is negative and vice-versa. Hence the transducer has a signal applied to it alternating at 40kHz. A metallic diaphragm in the transducer vibrates at the input frequency to create air pressure waves at the ultrasonic frequency of 40kHz, in a similar manner to a loudspeaker producing pressure waves at audio frequencies. The geometry of the transducer radiates these waves in a narrow beam. If the input to pin 1 of IC2 is maintained at logic state 0, i.e. zero volts, oscillation will be continuous. If

input is allowed to go to logic state 1, i.e. a positive potential, the gate will give no output and oscillations will be inhibited. In order to conserve battery life, the oscillator and hence the transducer is pulsed on for a small period a few times a second.

IC1 consists of four semiconductor switches with high input resistance on-off control. Two of these switches are interconnected to form an astable multivibrator. Capacitor C14 is alternatively charged and discharged by switches b and c.

Resistors R25 and R23 in conjunction with C14, control the recovery time for this capacitor. This is best understood by reference to the waveforms a, b, and c in Fig. 2. Resistors R23 and R25 are chosen to give a negative pulse to provide logic 0 (zero volts) to the input pin 1 of IC2 for a period of one millisecond, seven or eight times per second. This enables a burst of oscillations and consequent transmission during this pulse period.

## RECEIVER & AMPLIFIER

If the unit is placed facing an opposite wall or door, the ultrasonic waves will be reflected back to the receiving transducer. This acts in a similar manner to a microphone. A metallic diaphragm in the transducer produces an electrical output at the frequency of the received signal. This 40kHz signal is amplified by transistors TR1, TR3 and TR4, each operating at a very low current—a fraction of a micro-amp base current and about 10 micro-amps collector current. This low current operation enables series operation due to the comparatively high input resistance of the base. Battery drain is also minimised.

A parallel resonant circuit is introduced between the second and third amplifiers and presents a high impedance to 40kHz, but cuts down all other frequencies. This reduces circuit noise and inhibits low frequency transient signals from banging doors and other similar sources of mechanical vibration.

Emitter follower TR9 provides a low impedance drive for both the amplitude detectors. Assuming switch a of IC1 to be

closed, the signal detector diodes D3 and D4 will rectify the signal to give a negative d.c. potential at the gate of the field effect transistor TR2.

The d.c. level will be dependent on signal amplitude. TR2 acts as a variable resistance. The more negative the gate the less current is allowed to pass from source to drain and hence the greater is the apparent resistance between the source and drain for a given voltage. Increasing the effective resistance of TR2 lowers the gain of the amplifier TR1. This automatic gain control sets a constant signal level at the output of TR4 independent of the average received signal level. The comparatively large capacitor C4, together with the 10MΩ resistance R11, ensure that once the AGC level at the gate of TR2 has settled, subsequent to switch on, it will not respond to fast changes of signal level. The time constant at the gate is the product of C4 and R11 which is 47 seconds.

A second signal level detector is formed by the transistor TR5. TR5 pumps current into C10 for each positive cycle of the 40kHz signal enabling C10 to become positively charged. Diode D5 prevents the mean d.c. voltage at the base of TR5 from going negative. The positive potential at C10 will remain constant provided the signal level is constant.

## SPECIFICATION

Compact and portable self-contained unit.  
Battery operated.  
Effective Range: 3 metres.  
100dB alarm sounds when intruder crosses protected zone.  
Alarm resets after sounding for one minute.  
Alternative relay may switch external load.

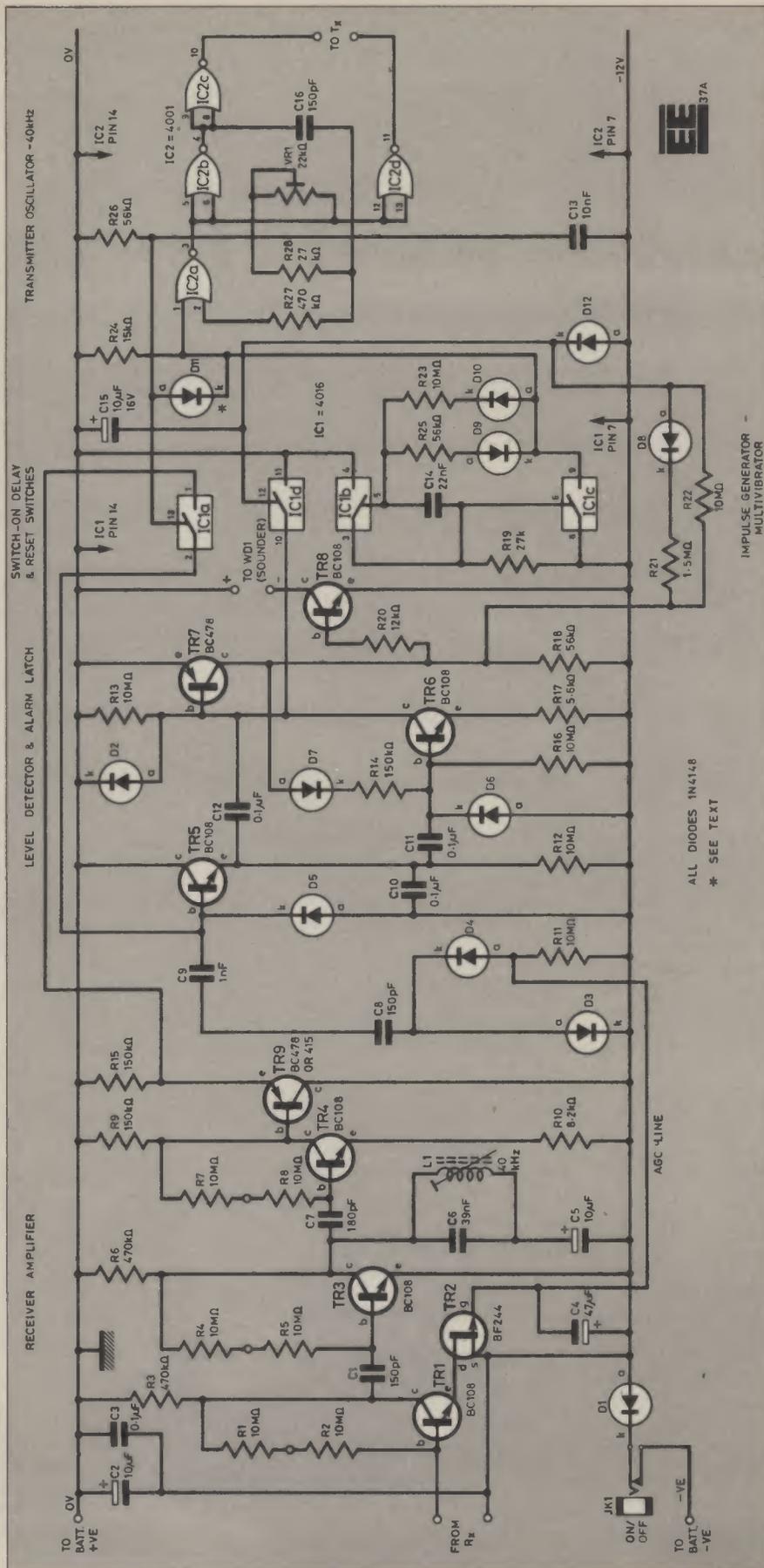


Fig. 1. Complete circuit diagram for the Ultrasonic Burglar Alarm. References Rx and Tx are the receiver and transmitter transducer input/output points.

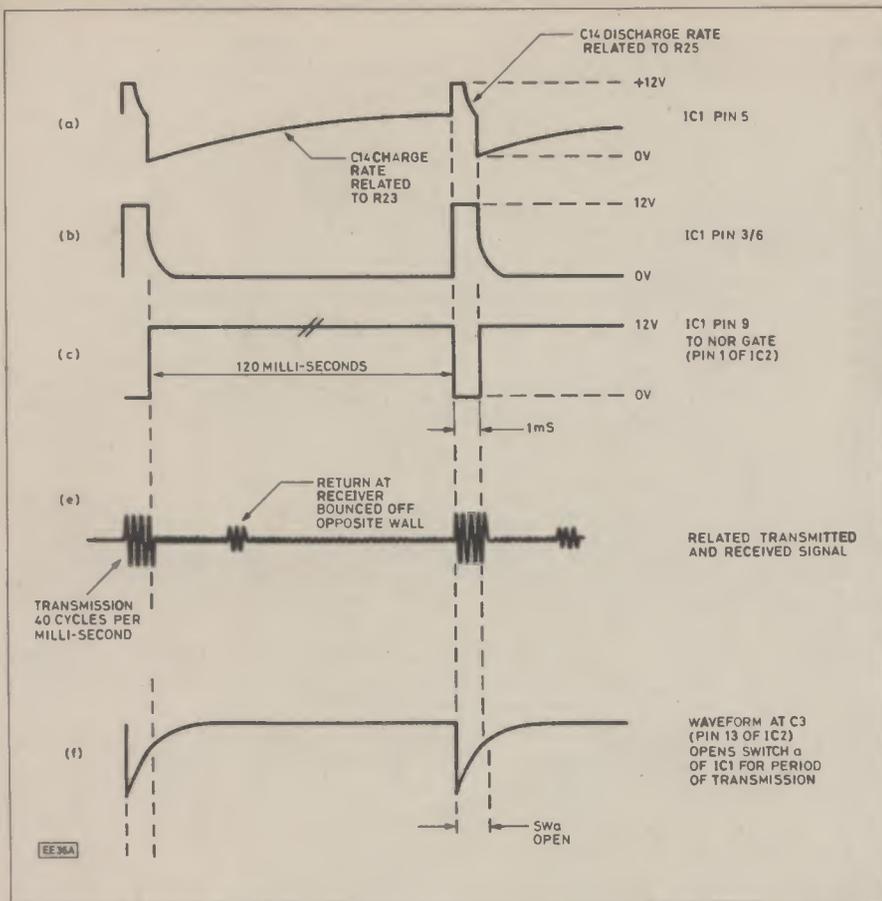


Fig. 2. Timing diagram of the Ultrasonic Burglar Alarm.

A change in signal level due to the disturbance of the ultrasonic beam will change the positive potential on C10, which in conjunction with R12 has a time constant of only one second, allowing change of signal level to give a change of voltage on C10 before the automatic gain control, with its longer time of response, is able to change.

It is important that the detectors respond only to the received pulses and not to the transmitter pulse, part of which leaks directly into the receiver. Hence the detectors are cut off from the amplifier output by switch a of IC1 during the transmission period. The waveform diagram, Fig. 2 shows the various switching sequences of switches a, b and c.

### ALARM LATCH

When there is a stable d.c. level on C10 there is no changing signal applied via C11 to either TR6 or TR7. There is no base current applied to either transistor and they both remain cut off. The collector of TR6 is at the positive supply voltage and the collector of TR7 is at the negative supply voltage. There is therefore no current drive to the alarm output transistor TR8.

Should there be an increase of level on C10 due to an increased received signal resulting from reflections from a person between the unit and the reflecting surface, this will be applied via C11 to the

base of the *nnp* transistor TR6 causing it to conduct, supplying base current to the *pnp* transistor TR7, which will also conduct. The collector of TR7 will move positive supplying current through diode D7 to the base of TR6 holding both transistors in their conducting state. The positive potential at TR7 collector switches on transistor TR8 to provide a continuous current through the sounder or relay coil.

A reduction in signal level will switch on TR7 by applying a negative going signal onto its base. The resulting positive potential on the collector will switch on TR6 via diode D7 to latch on the alarm.

### TIMING CIRCUITS

When the alarm is triggered and latched, TR7 is conducting; voltage at its collector is positive. C15 will slowly charge positively through R22, the time constant of C15 R22 being 220 seconds. C15 will have charged sufficiently positive to activate switch d of IC1 in approximately one minute. Closure of switch d connects TR7 base to its emitter, switching off the current through TR7 and consequently switching off TR6 and the alarm driver TR8. The collector of TR7 returns to zero volts. C15 will now discharge towards zero volts through D8, R21 and R18 in series; after a few seconds switch d will open allowing the alarm latching circuits to respond to any further variations of received signal.

## COMPONENTS

### Resistors

R1, R2, R4, R5, R7, R8, R11, R12, R13, R16, R22, R23	10M $\Omega$ (12 off)
R3, R6, R27	470k $\Omega$ (3 off)
R9, R14, R15	150k $\Omega$ (3 off)
R10	8.2k $\Omega$
R17	5.6k $\Omega$
R18, R25, R26	56k $\Omega$ (3 off)
R19, R28	27k $\Omega$ (2 off)
R20	12k $\Omega$
R21	1.5M $\Omega$
R24	15k $\Omega$

All resistors  $\frac{1}{4}$ W carbon film  $\pm 5\%$

### Potentiometers

VR1	22k $\Omega$
-----	--------------

### Capacitors

C1, C8, C16	150pF metallised ceramic plate (3 off)
C7	180pF metallised
C2, C5, C15	10 $\mu$ F/16V tant. bead (3 off)
C4	47 $\mu$ F tant. bead
C3, C10, C11, C12	100nF monolithic ceramic (4 off)
C6	39nF polycarbonate
C9	1nF monolithic ceramic
C13	10nF monolithic ceramic
C14	22nF monolithic ceramic

### Semiconductors

D1-D11	1N4148 (11 off)
TR1, 3, 4, 5, 6, 8	BC108 or BC238 (6 off)
TR2	8F244
TR7	BC478
IC1	4016
IC2	4001

### Miscellaneous

L1	TOKO coil type CAN1A350ER (Ambit)
JK1	2.5mm chassis socket as switch (use jack plug as keyswitch)
Rx	40kHz ultrasonic receiving transducer
Tx	40kHz ultrasonic transmitting transducer
X1	Sounder X70 W06 (from Avionics)
Relay (optional)	12V (Ambit No. 46-70050)
Battery	(Ambit No. 01-06108) holder
	Battery connector for PP3
	14-pin d.i.l. i.c. sockets (2 off)
	P.c.b.
	Plastic box with metal panel (150 x 90 x 50mm) (Ambit No. 2192751)
	Fixing screws for p.c.b. (4 off)

Approx. cost  
Guidance only

**£17.00**

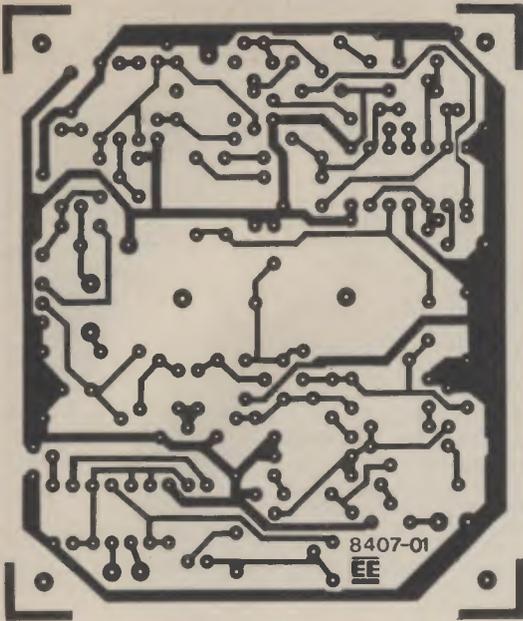


Fig. 3. Actual-size master pattern for the Ultrasonic Burglar Alarm. This board is available from the EE PCB Service, Order code 8407-01.

Switch d also inhibits the operation of the alarm latching circuits for about 30 seconds after initial switch-on, allowing the signal level to settle to its steady state. The negative terminal of C15 is initially positive on switch-on. This holds switch d closed to prevent TR7 conducting and latching on the alarm. C15 discharges to zero voltage through D8, R21 and R18 in series allowing switch d to open, and the detectors to activate the alarm latch circuits for any variation of received signal level.

## CONSTRUCTION

### MAIN CIRCUIT BOARD

Construction of the main circuit board is relatively simple using the printed circuit board in conjunction with the illustrated layout. Care should be taken to see that the diodes are all inserted with the correct polarity, i.e. the cathode, which is marked with a bar on the diode is connected into the position marked +. Note also that IC1 and IC2 are MOS devices. They should be handled with care, removed from their packing and mounted directly into their respective IC mounts.

Electrostatic discharge can damage TR2. Before applying the soldering iron to TR2 the iron should be disconnected from the mains or other power source so that it is completely isolated. It should be momentarily touched onto the earth track (0 volts) before being applied to the pins of TR2. It would also be advisable to mount TR2 before mounting C4 and to ensure that C4 is completely discharged

by shorting its leads together just before mounting. An isolated iron should also be used when mounting the other two components connected to the gate of TR2, namely R11 and D4—it would be preferable to mount R11 before mounting TR2.

### POWER

The unit runs from a 12 volt battery supply. Current consumption on standby is about  $400\mu\text{A}$ . Using eight MN 1500 alkaline batteries this should give standby operation of around 2,000 hrs. Battery consumption is increased by about 100

times during alarm and it is therefore important, once satisfactory operation is established, to minimise the test time.

The tag on the screen of coil L1 on the inside of the p.c.b. should be cut off. The transducers should be cemented into the holes provided, again care being taken to ensure that the transmitter and receiver are correctly connected. They should stand proud of the p.c.b. the base with the two terminals being flush with the component side of the board. It is recommended that they are assembled into the front panel as illustrated. The 45 deg. inset prevents ultrasonic energy being reflected from objects alongside the unit.

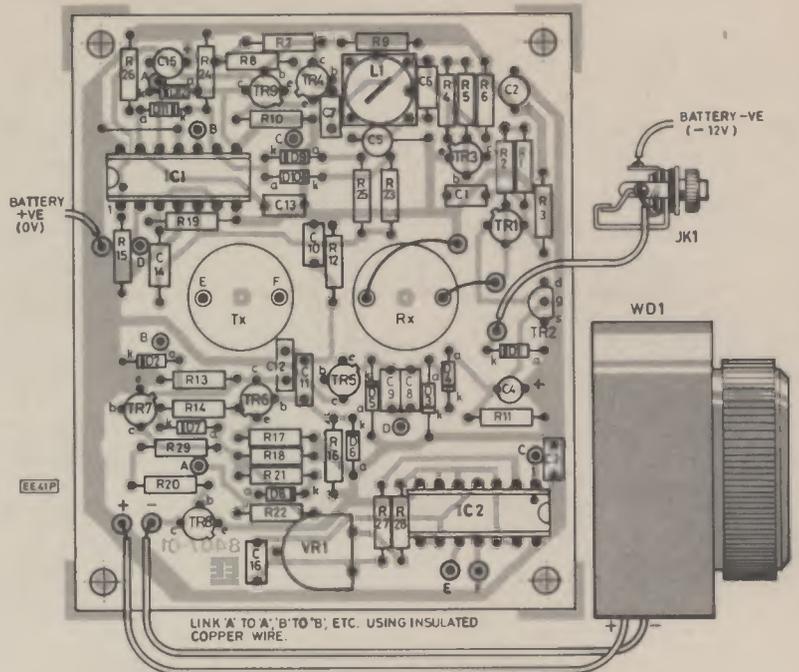


Fig. 4. Layout of components on the top side of the p.c.b. and interwiring to the jack socket/switch and warning device.

Internal view of the Ultrasonic Alarm, showing the large piezo electric sounder, p.c.b. mounted directly on the front panel, and the miniature jack socket which can be used as a "disarm" switch by the holder of the plug.

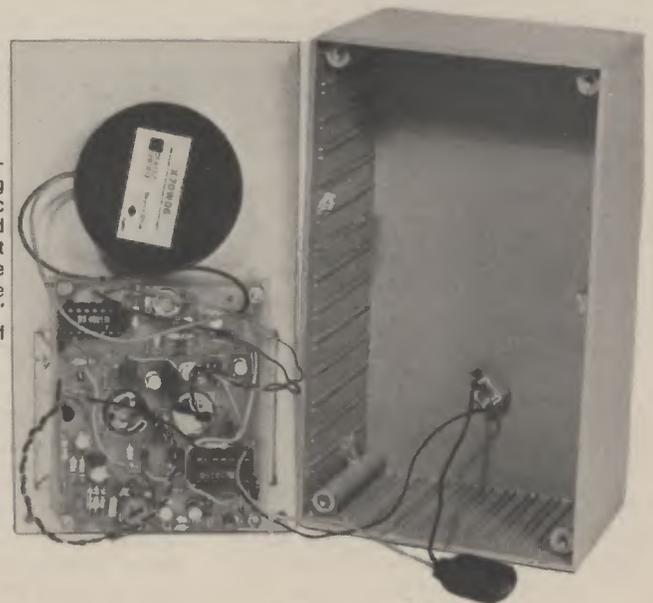


Fig. 5. Block diagram of the Ultrasonic Burglar Alarm. This type of alarm has a limited range. This particular unit is directed primarily at the educational application.

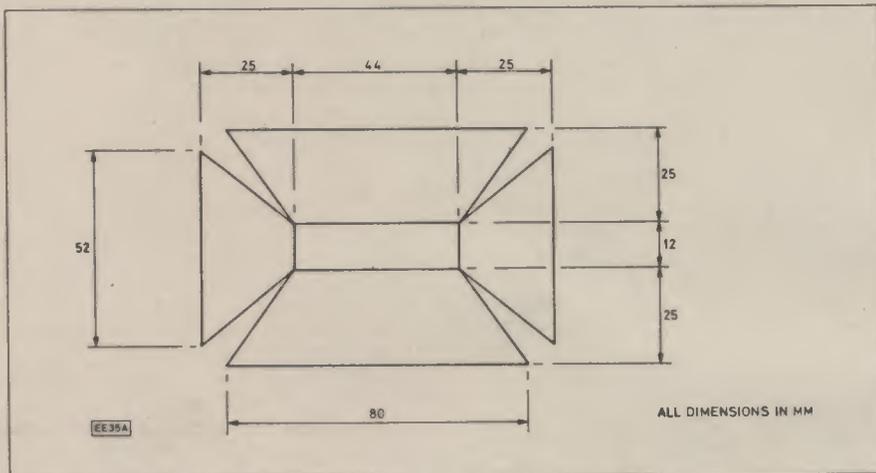
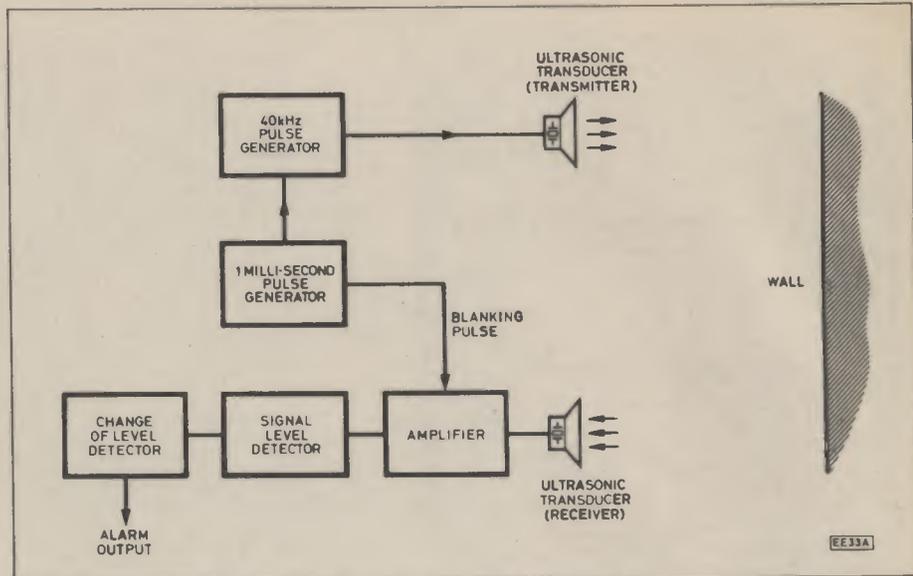


Fig. 6. Window, or horn for the transmitter/receiver aperture. This could be made of stiff card or plastic sheet.

To save the cost of a key on-off switch a 2.5mm jack socket is proposed; the unit is switched off by inserting the jack plug. Front panel cut out and drilling dimensions are shown for the box proposed in the parts list. If the relay is used instead of the sounder, no hole is required and the relay may be glued to the sounder position. The relay coil is connected to the alarm output and the relay contacts may be brought out through a DIN connector, or jack plug and socket.

### OPERATION & SETTING UP

The use of an oscilloscope is recommended for setting the transmitter and receiver frequencies. An alternative procedure is described in case an oscilloscope is not available.

### USING AN OSCILLOSCOPE

Temporarily remove IC1. Connect the earth of the oscilloscope to the supply line. Using Y1 input, observe the signal waveform at the output pins 10 and 11 of IC2. This square wave output may be set

to 40kHz by adjustment of VR1 to give a period of 25 $\mu$ s for one complete cycle.

Alternatively place the unit approximately one metre from a reflecting surface. Observe the waveform at the collector of TR1. Adjust VR1 to give maximum signal. This will be at the optimum operating frequency of the transducers, namely 40kHz.

### TUNING

The coil L1 may now be tuned. Observe the waveform at the emitter of TR8. Adjust the ferrite core of L1 to give a maximum output as observed on the oscilloscope. Fit IC1. Synchronise the oscilloscope using the waveform at pin 9 of IC1. Note waveforms as illustrated in Fig. 2a, b, e and f.

The received signal pulse level at the detectors will now be constant at about 3-4 volt peak-to-peak, this level being determined by the automatic gain control. The effect on level can be noted by pointing the unit at various reflecting surfaces. Note that it is not possible to tune the transmitter and receiver when the a.g.c. is in operation.


### SETTING WITHOUT AN OSCILLOSCOPE

Temporarily remove IC1. Place unit about a metre from reflecting surface. A high resistance voltmeter on the a.g.c. line (negative end of C4), referenced positive clip to GND (0V) will facilitate adjustment alternately of VR1 and L1 for maximum reading. After refitting IC1, a fine adjustment of VR1 and L1 may be necessary. The unit will need to be fairly close to a reflecting surface to obtain a reasonable reading on the a.g.c. line.

### SITING


Ideally the unit should be sited with an uninterrupted "view" of the opposite wall or closed door. Range is deliberately limited to a couple of metres for reliability. Beyond this distance there will be a passage near the wall where the reflection from a body will be neither more nor less than that from the wall allowing a "gate" through the beam. A radiator or window directly opposite the unit will cause fluctuations of the received level due to reflections from air of different density and should be avoided. □

Fig. 7. Front panel cutting details.

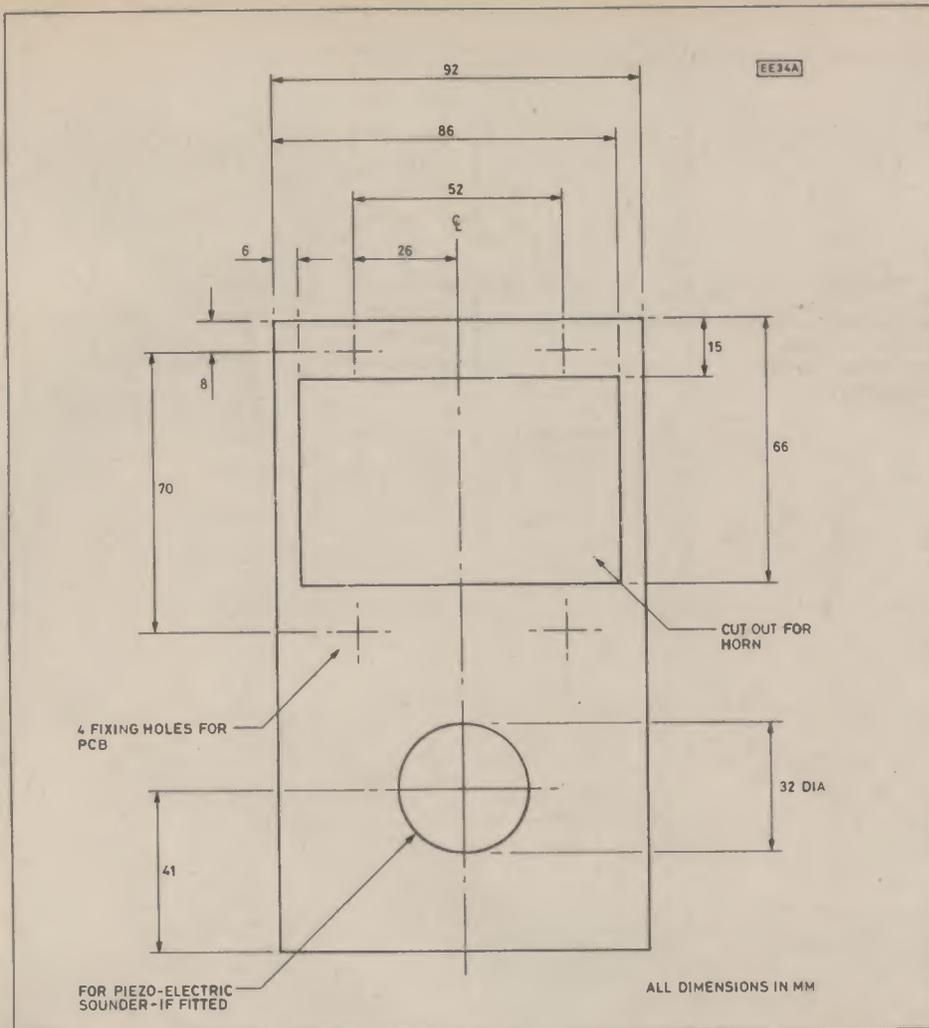

# INFRA-RED ALARM

## ADDITIONAL NOTES


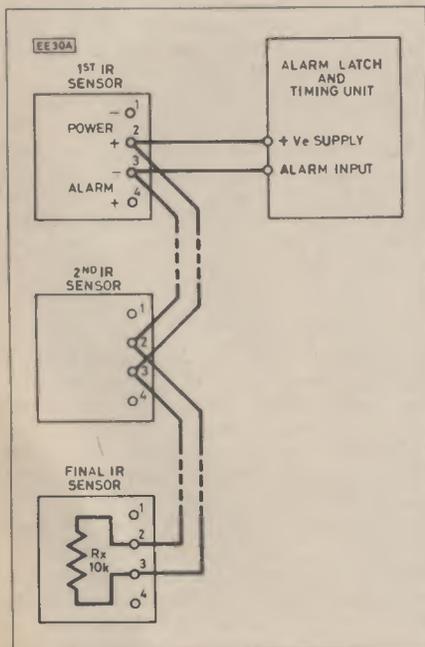


The *Infra-red Alarm System* published last month can incorporate several sensors connected to a single alarm latch unit. Here are some notes on how to do this, and a couple of additional notes on the system's use.

Any number of additional IR Sensors can be added to give greater coverage of the protected premises. The sensors may be wired in parallel but it is recommended that they are wired in sequence as illustrated. Only one resistance Rx should be used. This should be connected to the last sensor in the sequence, then if any of the connecting wires are cut the alarm will be triggered.

An alternative IR Sensor for use with household pets, IR 883, limits the sensitive zones to approximately 3ft. provided it is sited at a height of 3ft. 6ins. or above. The limit of the sensitive zone will have to be established by trial and error, tilting the sensor slightly as necessary.

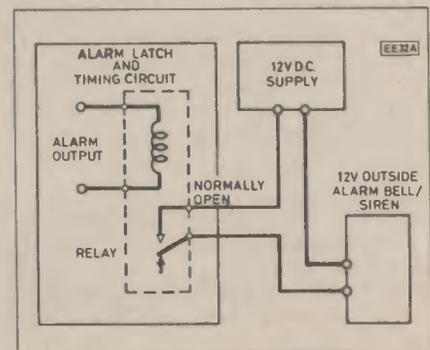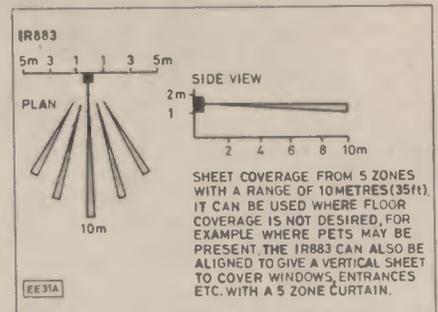The alarm system may be used to set off an outside alarm or siren. The relay specified in the components list has its coil connected to the alarm output as illustrated. The relay contacts act as an ON-OFF switch, switching the 12 volt d.c. supply to the outside alarm when the alarm and latching circuit is triggered.



# NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW

## BENCH POWER

A FAMILY of four high performance bench power supplies, the GPL series, has been introduced by Gresham Powerdyne. The series offers a choice of single, dual and triple output models featuring excellent voltage and current regulation.

The smallest model in the series is the GPL 20, a lightweight unit offering a variable 0V to 30V at 1A maximum output plus a fixed 5V output (1A max). It also features variable current limiting.


The GPL 23, a triple output unit, features two independent variable outputs each of 0V to

30V (2A max) with a choice of constant current or constant voltage modes. In addition, it has a fixed 5V, 3A output rail facility.

Although it is a single output instrument providing 0V to 40V at up to 1A, the model GPL 25 features variable current limiting and two front panel meters for simultaneous indication of voltage and current. Largest unit in the series is the GPL 28, which offers a single 0V to 60V, 2A output with dual tracking (0V to 30V, 2A) facilities as standard.

Further technical details of the complete range of Gresham power supplies can be obtained from:

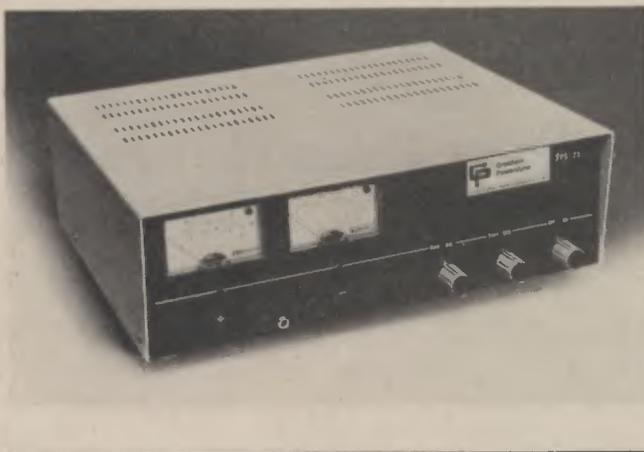*Gresham Powerdyne Ltd.,  
Dept EE, Osborne Way,  
Station Road, Hook, Hants.*



## DIGITAL PANEL METER


THE DPM60 digital panel meter from Lascar Electronics features liquid crystal display, auto-zero, auto-polarity, and a logic switched 200mV or 2V f.s.d., giving a resolution of 10µV. Other features include programmable decimal points, digital hold, low battery indication, continuity indication and a 10mm 4½-digit high contrast l.c.d. readout.

The panel meter can be readily scaled by the user to indicate amps, volts, ohms and other units. Supplied complete with

mounting bezel, clips and connector, it will suit many applications in portable and bench instruments.

The DPM60 is available in kit form and costs £29.95 inclusive. More information can be obtained from:

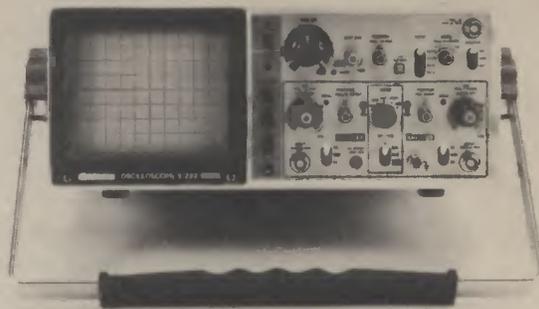*Lascar Electronics Ltd.,  
Dept EE, Module House,  
Whiteparish, Salisbury,  
Wiltshire SP5 2SJ.*



## SLIMLINE SCOPE

THE new V-222 oscilloscope from Hitachi is a 20MHz dual-trace model incorporating a 6in rectangular c.r.t. in an ultralightweight slimline format and is being marketed by Reltech Instruments.

An alternate sweep magnifier enables any section of a waveform to be expanded ten times and displayed simultaneously with the un-magnified signal. A d.c. offset control and offset measurement socket allow a digital voltmeter to be used to moni-

tor voltages on the screen, whilst a low impedance signal output socket enables a frequency meter or counter-timer to be connected.

The 'scope has a sensitivity of 1mV/cm and a maximum sweep speed of 20nsec/cm. Fully variable gain and sweep rate controls have un-calibrated warning lights to avoid accidental measurement errors. Full XY mode and Z modulation facilities are provided.

The V-222 oscilloscope comes complete with two x1, x10 switchable probes. Price in the UK is £340 plus VAT, a lower specification version is also available at £295 plus VAT.

*Reltech Instruments,  
Dept EE, Coach Mews,  
St. Ives, Huntingdon,  
Cambs PE17 4BN.*

## KIT TIME

THREE new kits have recently been announced by Vellerman (UK) Ltd. They are a microprocessor Precision Timer K2584, a Codelock K2585, and a Programmable controller Module K2591.

The Precision Timer, which includes housing, transformer and sheet keyboard, has four programs which can vary from one second to 99 minutes 99 seconds. The timer counts down to zero and activates the output which can also be manually switched on or off.

Running programs can be stopped, interrupted or continued. This makes the unit ideal for dark room timing, process control and light control.

The Codelock has two memory levels, each level capable of storing 20 numbers of six digits. The memory contains a CMOS RAM, which is fed by a battery in case of power failure. All the numbers therefore, are retained even if a mains failure were to last a month.

The codelock has a sheet

keyboard as a front panel and its applications include: protection of machines, protection of rooms where only authorised personnel may enter, entry systems for flats, offices and homes, and burglar protection in general.

The Programmable Controller Module is designed to control measurements of temperature, humidity, acid and chlorine levels. It has a 24-hour clock, four programmable registers and a display for the input signal.

The input signal can be made up of an analogue voltage from 0 to 999mV d.c. This measure value reads and displays by the means of an A/D converter and an interface with the central processor.

The module compares the input signal with the values which are programmed in the memory, and switches on an output relay. Switching occurs with a precision of 10mV to the input signal.

Full technical details and prices are available from:

*Vellerman (UK) Ltd.,  
Dept EE, PO Box 30,  
St Leonards-on-Sea,  
East Sussex TN37 7NL.*

## ELECTRON ADD-ON

A SWITCHED joystick interface for the Electron microcomputer has been developed by First Byte Computers, and should be available now from good High Street retailers.

A free conversion tape is supplied with the interface, to allow games such as "Killer Gorilla" and "Cyclon Attack" to be played under joystick control.



## PANTOGRAPH FOR THE BBC B

A NEW add-on for the BBC model B allows the reproduction of drawings, maps, and diagrams at an affordable price. The Image Plotter comes with calibration sheet and handbook and has a recommended retail price of £49.95.

Even the most complex shapes can be enlarged or reduced, and

Also, major software houses are now writing games programs intended for use with this add-on.

The plug-in cartridge takes all standard "Atari-Style" joysticks, which are cheaper and more popular than analogue joysticks.



FBC intend to launch an extensive advertising campaign, and to demonstrate the new interface at home computer shows during 1984.

*FBC Ltd,  
Dept EE,  
10 Castlefields,  
Main Centre,  
Derby.*

shown in any colour. If a printer is available, a hard copy can be made, or the image can be stored on disk or cassette.

The plotter comes ready assembled, is made of aluminium, and software is available on disk or cassette. Available at present through mail order only.

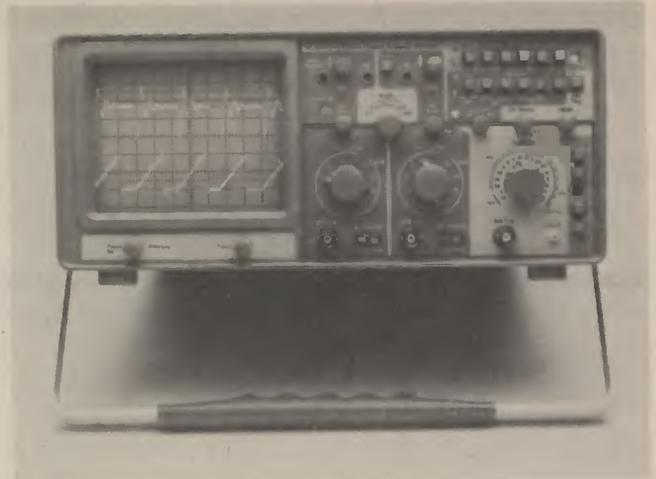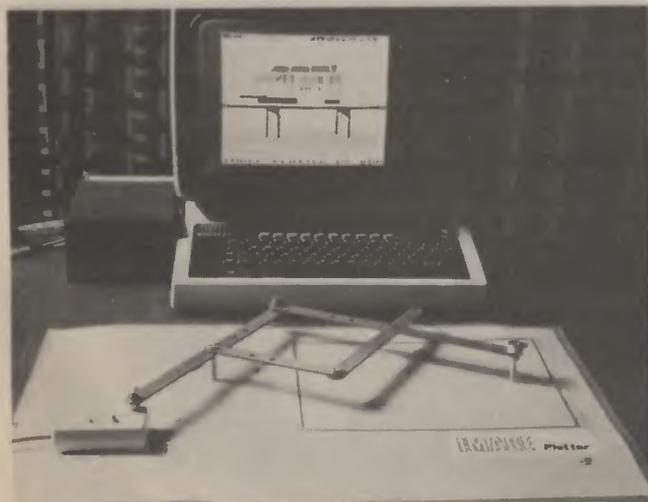*Reekie Technology Company,  
Dept EE, Beaufort Road,  
Off Richmond Road,  
East Twickenham,  
Middlesex TW1 2PH.*



## DIGITAL STORAGE OSCILLOSCOPE

ALL the facilities of a 20MHz dual-trace oscilloscope with the option of switching into digital storage mode; this is the latest offering from Gould Instruments, called the OS1400 series.

Gould claim it is the first instrument of its type to retail at under £1000, and point out that it is entirely U.K.-designed and manufactured.

Used as a normal oscilloscope, the 1400 has continuously variable sensitivity from 2mV/cm to 25V/cm, and timebase variable from 0.5µs/cm to 0.2s/cm.

In storage mode, the OS1400 can sample at rates from 0.5s per sample to 0.5µs per sample, and there are three display modes. Pre-trigger viewing of from 0% to 100% of the display is available in roll mode, and the display can be expanded by ten times after storage.

*Gould Instruments Ltd,  
Dept EE, Roebuck Road,  
Hainault,  
Ilford,  
Essex.*

## 60 WATT MOBILE AMPLIFIER



BAKER Loudspeakers Ltd, announce the addition of a new mobile amplifier to their comprehensive range of disco/public address equipment.

With the accent on portability this amplifier weighs only 12 pounds and measures only 15½ x 8½ x 6 inches yet can deliver 60 watts R.M.S. into 4 ohms with distortion less than 2% at full output. A special feature is its ability to operate from a 12 volt car battery if the normal 200/240 volt mains supply is not available or added safety is required in an outdoor location.


Housed in a robust case that is both attractive and functional the unit has four separate volume controls (for 4 channel mixing) plus a master volume control, a

mains switch and bass and treble controls that give a wide ±10dB variation over the 80-12KHz ±3db claimed frequency response. Four high gain inputs are provided (3 at 20mV 50KΩ plus magnetic phono 3mV) and two standard jack socket loudspeaker outlets for 4, 8 or 16 ohms plus terminals for 100 volt line.

This English made amplifier is fully protected against short and open circuits and is guaranteed for 12 months. The unit costs £89 (plus £3 if ordered by post), including VAT.

*Baker Loudspeakers Ltd.,  
337 Whitehorse Road,  
Croydon,  
Surrey.  
01-684 1665*

# RADIO WORLD

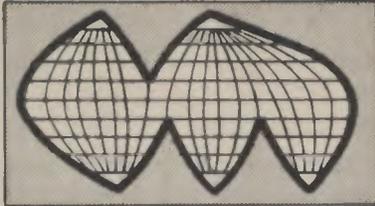

BY PAT HAWKER G3VA

## New licences

During the past few months nearly 4000 amateur (Class B) licences have been issued in the UK with the new "number one" in the callsign (G1AAA, etc.) plus a lesser number of "G4" Class A licences. This is a remarkable indication of the current interest in the hobby.

Less easy to determine is the number of enthusiasts who, after going to the trouble and expense of obtaining a licence, either fail to renew it a year or two later, or else retain their licence but put their equipment away and thereafter make few appearances on the bands. Certainly the drop-out rate is much higher than it used to be, and appears to be higher among Class B operators than those who, after taking a Morse test, are free to use h.f. as well as v.h.f. bands.

In the UK you can get a good idea how long an amateur has held his present licence from his callsign. Most of those with personal "two-letter" callsigns, such as mine, date back to the 1930s or even 1920s. There are a few exceptions since close relatives can apply to take over a callsign and sometimes a club will seek and obtain the callsign of a prominent former member.

Two-letter callsigns with a GB prefix are allocated to repeaters. A "G2" (plus three letter) callsign similarly dates back to 1939 or earlier when these call-letters were issued to persons holding what were called "artificial aerial" licences, permitting holders to build and experiment with transmitters provided that they did not connect an aerial.

## The G-Men

The "G3" (three letter) callsigns began to be issued in 1946 and the sequence was completed in 1971, reaching the G3N series roughly 25 years ago in 1958 to 1960. The "G4" (three letter) series began in 1971 and is not yet exhausted but has now reached the G4X sequence.

The first Class B licences in 1964 started with the "G8" (three letter) series (at first these licences covered only 430MHz and above, and there was limited demand). The G8Zs were exhausted in 1981 but the following "G6" (three letter) sequence lasted only until the autumn of 1983, although some callsigns in this sequence were issued many years earlier to those interested in amateur television transmission.

A "G" prefix, of course, means the station is in England; if the owner moves to Scotland it becomes GM, Northern Ireland GI, Wales GW, and so on. The "G5" (three letter) callsigns are held by foreign amateurs operating the UK and have been much put out by a suggestion that soon

their callsigns may be changed into the "British nationals" sequences.

Amateurs who have held the same callsign for many years intensely resent any suggestion that they could lose their "identity". I must admit that I was not altogether pleased when a repeater in Buckinghamshire acquired GB3VA!

## Baby Broadcasters

Last year the Federal Communications Commission (FCC) conducted an enquiry into the proposals to issue in the USA amateur radio licences without a Morse code examination, akin to the Class B VHF-only licences issued in the UK. However, the FCC invariably invites comments on such proposals before implementing them.

The result was that over 5000 comments were filed with the FCC running 20-to-1 against the proposal which has now been dropped. In the USA even the "novice" amateur licence requires a five words-per-minute code test.

The FCC is now considering a new class of CB licence—a "hobby class" licence that would permit computer hobbyists to establish radio links for the transmission of data. For as long as I can recall most of us have never been ashamed of being called "radio amateurs" although not everyone relishes the sobriquet of "ham" operators.

The international regulations define the amateur radio services and it seems surprising that the Radio Society of Great Britain appears to accept the curious notion that amateur-radio enthusiasts now "suffer" from the alternative use of the word "amateur" in a derogatory sense and have been inviting suggestions of what the hobby should be called! But I hope they do not revive a term of abuse used in the 1930s for 7MHz phone operators: "baby broadcasters".

## Cable In A Twist?

It has been suggested that the only people likely to make real money out of cable television in Britain in the near future are either the market researchers with their high-cost reports or the organisers of the seemingly endless series of conferences, seminars and exhibitions. For all the talk it still looks like being many months before the first of the 25-30 channel systems opens—possibly the one being installed by Rediffusion in Guildford as a "shop window" for its star-switched but all coaxial-cable system.

Meanwhile, satellite-distributed channels have started up on the existing low-

capacity systems, on which the "must-carry" rules for broadcast channels have been waived provided that the subscribers are given an aerial capable of providing good quality off-air signals.

The \$64,000 question is whether the premium TEN film channel will prove capable of attracting and retaining a significant percentage of those served by cable or who are "passed by cable". Most people agree that the earlier, less ambitious, attempt to provide a film channel on a few British cable networks, without satellite-distribution, was far from an unequalled success with only about 5 to 25 per cent of connected households prepared to pay the monthly subscription.

## Door-to-Door Selling

In the USA it has been found that aggressive door-to-door selling is needed, and cable operators then have to worry about the "churn rate", the term used to describe the people who fail to renew their monthly subscriptions. Since British cable firms are convinced that an initial "connection fee" would discourage people from subscribing, a high churn rate soon adds up to a great deal of money buried uselessly in the ground. A buzz term in cable and DBS at the moment is "conditional access" implying a system whereby a viewer who has not paid his monthly sub can be denied access to the channel without the need to remove the decoder.

Surprisingly, one of the most rewarding series of lectures and discussion on cable has been a series of lunch-time lectures at the National Film Theatre in London during February and March. For 60p a time, one heard more balanced and realistic views from both cable people and politicians on the opportunities and problems of cable than at many of the high-cost trade seminars.

However, nobody is finding it easy to predict what percentage of British viewers, with four off-air channels, a substantial licence fee, and with a quarter of homes already having the extra choice provided by a VCR machine, will be willing to pay for "basic" cable channels. Neither are they prepared to predict the numbers willing to pay extra for "super-basic" channels, or extra still for "premium" channels each of which could cost up to £10 per month. It would still be cheaper than frequent visits to the cinema, but how many people these days are regular cinema-goers?

The most depressing forecast comes from the research firm CIT suggesting that the number of British homes cabled in 1990 may actually be less than in 1980, when 1.6 million homes were on commercial cable networks.

## High-Speed Satellite

Congratulations to the team at the University of Surrey who built and tested out their new UOSAT amateur radio satellite carrying scientific and educational experiments in a matter of a few months—possibly the quickest time from planning to launch for any new satellite yet!

Launched into low Earth orbit by NASA on March 1, 1984, at 17.59 UT, the first beacon signals were received at 19.49 UT on 145.825MHz although it will take some time to check out all systems on this second bird from the Surrey woods.

# OSCILLATORS

A variety of different types of resistance capacitance feedback oscillators, all having wide use, are described in this short series. Some of the circuits are based on discrete semiconductors, others on familiar i.c.s. In addition to theory of operation, design pointers for particular needs and applications are given. Each part in the series also includes a detailed circuit for a practical project.

## Part Two: USING THE 555 AND ICM7555

By J. R. DAVIES

THE MAIN uses for the 555 and the ICM7555 are as a timer and as an oscillator. The 555 is a well-established i.c. incorporating bipolar circuitry, whilst the more recently introduced ICM7555 is a CMOS version which requires a considerably lower supply current. The 555 and ICM7555 are pin-compatible and are directly interchangeable in many, but by no means all, applications.

### 555 OPERATION

The internal circuitry of the 555 is shown in simplified form in Fig. 2.1. An internal potential divider between the positive ( $V_{CC}$ ) and negative (ground) rails consists of three equal resistors, each having a nominal value of  $5k\Omega$ .

Reference voltages of two-thirds supply voltage and one-third supply voltage are available as shown, the first being applied to a voltage comparator coupled to pin 6 of the device and the second to another comparator connected to pin 2.

The reference voltages may be altered, if desired, by applying external connections to pin 5. For most applications, pin 5 is left open-circuit or is coupled to the negative rail via a bypass capacitor.

An internal transistor provides a discharge function at pin 7. When this transistor is turned off pin 7 is virtually open-circuit, and when the transistor is turned on pin 7 is effectively short-circuited to the negative rail.

The comparator outputs are fed to a flip-flop which controls the internal discharge transistor. Also controlled by the

flip-flop is an output stage coupling to pin 3. The voltage on pin 3 is high (close to or at the positive supply rail potential) when the discharge transistor is turned off and is low (close to or at the negative rail potential) when the discharge transistor is turned on.

Pin 4 is the reset pin and is normally only employed when the 555 is used for timing applications. For oscillator applications, pin 4 can be left open-circuit. It is preferable, however, to connect it to the positive rail as this completely disables the reset facility and ensures the reset circuitry cannot affect oscillator operation.

Alternatively, pin 4 can be used to enable or inhibit the 555 when used as an oscillator. If pin 4 is high the oscillator runs normally, and if pin 4 is low the oscillator stops with the output at pin 3 low and the discharge transistor turned on.

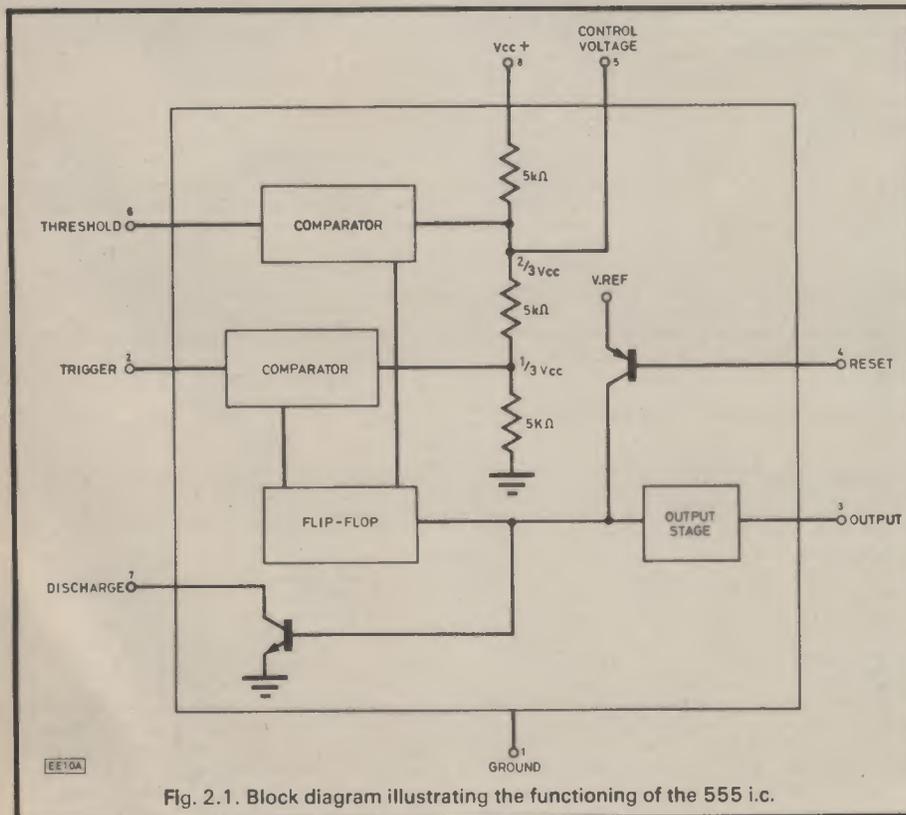


Fig. 2.1. Block diagram illustrating the functioning of the 555 i.c.

### SUPPLY RANGE

The supply voltage range for the 555 is 4.5 to 16 volts and its current consumption is of the order of 6mA at 9 volts. To that current has to be added any current flowing in an output load and in the frequency control components. When the 555 output is high it can source load currents up to 200mA, and when it is low it can sink currents up to the same value.

The ICM7555 has precisely the same pin functions as the 555 and it has a supply voltage range of 2 to 18 volts. The supply current requirement is very much lower, being typically 40 to 50 $\mu$ A only from a 9-volt supply. With an 18-volt supply it can sink output currents up to 100mA, the maximum sink current reducing, roughly proportionately, with supply voltage. The output source current capability is much lower.

We shall consider the output performances of both the 555 and the ICM7555 in more detail later in this article. Although the ICM7555 uses CMOS circuitry, all inputs and outputs are fully protected against damage by static voltages, and it does not need the special handling procedures normally associated with CMOS devices.

## OSCILLATOR CIRCUIT

The basic 555 and ICM7555 oscillator circuit is shown in Fig. 2.2. Pins 2 and 6 are connected together and to the external capacitor C. Two external resistors, RA and RB, couple the capacitor to the positive supply rail, with their junction connected to the discharge pin, pin 7.

When power is applied, pin 7 is open-circuit and the capacitor commences to charge via RA and RB. The i.c. output at pin 3 is high. When the voltage across the capacitor reaches two-thirds of the supply voltage the threshold comparator trips the flip-flop, causing the internal discharge transistor connected to pin 7 to turn on and the pin 3 output to go low.

The capacitor now discharges into RB on its own until the voltage across it falls to one-third of the supply voltage. The trigger comparator then trips the flip-flop to its previous state, causing the discharge transistor to turn off and the output to go high. The capacitor charges once more via RA and RB until, again, the voltage across it reaches two-thirds of the supply voltage.

The cycles proceed in this manner with the capacitor voltage changing continually between one-third and two-thirds of supply voltage. Since the reference voltages are derived from the supply and the capacitor charge and discharge currents are proportional to supply voltage, the frequency of oscillation is independent of the supply voltage. Note that the output voltage is high when the

capacitor charges, and is low when the capacitor discharges.

## FREQUENCY CALCULATION

The charge time in the oscillator cycle is equal to  $0.685(RA + RB)C$ , and the discharge time is equal to  $0.685(RB)C$ . Total time for one cycle is therefore  $0.685(RA + 2RB)C$  and frequency is the reciprocal of this, or

$$f = \frac{1.46}{(RA + 2RB)C}$$

As with the symmetric multivibrator of Part One, convenient units to work with are megohms, microfarads, seconds and hertz.

To take an example, let us say that RA is 820kΩ, RB is 220kΩ and C is 0.47μF. The total cycle time is:

$$0.685(0.82 + 0.44) \times 0.47$$

A calculator soon tells us that this works out as 0.406 second to three significant figures. The reciprocal gives a frequency of 2.47Hz.

Fig. 2.3 (a) shows an oscillator with a calculated frequency of 4.85kHz, and Fig. 2.3 (b) shows one with a calculated frequency of 0.0221Hz and a calculated cycle length of 45.2 seconds. Table 2.1 gives calculated frequencies for different values of (RA + 2RB) over some seven decades of frequency, and will be found helpful in arriving at suitable component values for a specific frequency.

The 555 will oscillate satisfactorily for values of (RA + 2RB) up to 10MΩ and

down to values of 1kΩ. The ICM7555 draws lower input currents at pins 2 and 6 and will operate satisfactorily with values of (RA + 2RB) ranging from 100MΩ to 1kΩ.

If C is an electrolytic capacitor it is preferable to limit (RA + 2RB) to some 500kΩ with either i.c. This will ensure that capacitor leakage current does not significantly affect oscillator functioning.

## OUTPUT PERFORMANCE

The internal output transistors in the 555 have the circuit configuration shown in Fig. 2.4. When the 555 output is low, transistors TRA and TRB are turned off, whilst TRC is turned on. Fig. 2.5 (a) shows the voltage between pin 3 and the negative rail for different currents flowing in a load connected between pin 3 and the positive rail when the supply voltage is 9 volts.

At currents below 40mA the voltage drop across transistor TRC ranges from less than 0.1 volt to some 0.4 volt. At around 50mA the voltage drop increases sharply to around 1.5 volts and then increases to 2 volts at 100mA.

When the 555 output is high, transistors TRA and TRB are turned on, with TRC turned off. Both TRA and TRB are emitter followers with the results that for currents above 0.15mA (at which 0.6 volt is dropped across the 3.9kΩ resistor) the voltage drop across TRB must be at least 1.2 volts because of the voltage drop

Table 2.1: 555 AND ICM7555 FREQUENCIES

(RA + 2RB)	0.01μF	0.022μF	0.047μF	0.1μF	0.22μF	0.47μF	1μF	2.2μF	4.7μF	10μF
1kΩ		66.4kHz	31.1kHz	14.6kHz	6.64kHz	3.11kHz	1.46kHz	664Hz	311Hz	146Hz
3kΩ	48.7kHz	22.1kHz	10.4kHz	4.87kHz	2.21kHz	1.04kHz	487Hz	221Hz	104Hz	48.7Hz
10kΩ	14.6kHz	6.64kHz	3.11kHz	1.46kHz	664Hz	311Hz	146Hz	66.4Hz	31.1Hz	14.6Hz
30kΩ	4.87kHz	2.21kHz	1.04kHz	487Hz	221Hz	104Hz	48.7Hz	22.1Hz	10.4Hz	4.87Hz
100kΩ	1.46kHz	664Hz	311Hz	146Hz	66.4Hz	31.1Hz	14.6Hz	6.64Hz	3.11Hz	1.46Hz
300kΩ	487Hz	221Hz	104Hz	48.7Hz	22.1Hz	10.4Hz	4.87Hz	2.21Hz	1.04Hz	0.487Hz
1MΩ	146Hz	66.4Hz	31.1Hz	14.6Hz	6.64Hz	3.11Hz	1.46Hz	0.664Hz	0.311Hz	0.146Hz
3MΩ	48.7Hz	22.1Hz	10.4Hz	4.87Hz	2.21Hz	1.04Hz	0.487Hz	0.221Hz	0.104Hz	0.0487Hz
10MΩ	14.6Hz	6.64Hz	3.11Hz	1.46Hz	0.664Hz	0.311Hz	0.146Hz	0.0664Hz	0.0311Hz	0.0146Hz

Calculated frequencies for (RA + 2RB) and capacitance

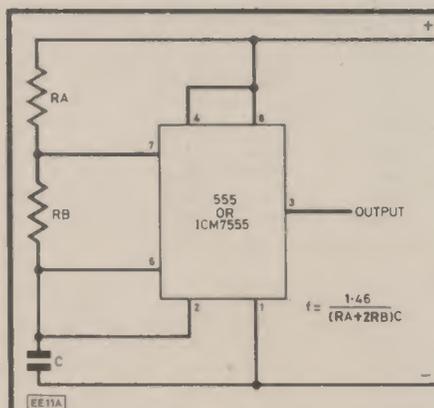


Fig. 2.2. The basic oscillator circuit for the 555 and the ICM7555.

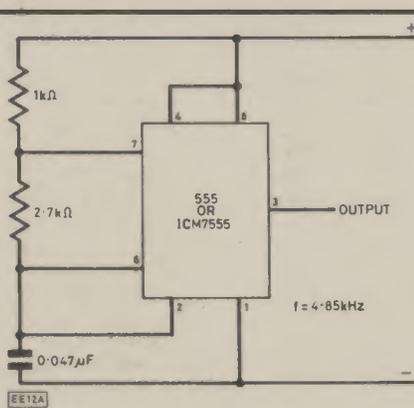


Fig. 2.3(a). A practical example of a 555 or ICM7555 oscillator circuit.

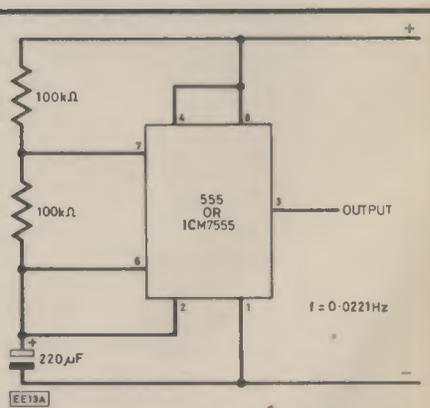


Fig. 2.3(b). The 555 and ICM7555 will oscillate at very low frequencies. The calculated cycle length here is 45.2 seconds.

in each of the two base-emitter junctions. The voltage drop for source currents up to 100mA is shown in Fig. 2.5 (b).

Since, for currents up to around 40mA, there is a much lower voltage drop in the 555 when it is providing a sink current than there is when it provides a source current, it is often more desirable to have the 555 drive a load which is connected between its pin 3 and the positive rail. The load current then flows when the 555 output is low.

The ICM7555 is specified as sinking output currents of up to 100mA maximum with a supply of 18 volts. With a 9 volt supply the maximum sink current to

be expected is a little over 50mA, and a representative current-voltage curve is shown in Fig. 2.6 (a).

The source current capability of the ICM7555 is quite limited and, as can be seen from Fig. 2.6 (b), about 7 volts are dropped in the device at 10mA when the power supply is 9 volts. For load currents in excess of a few milliamps it is obviously better to use the ICM7555 in the sink current mode.

Both the 555 and ICM7555 outputs are compatible with TTL and CMOS inputs. TTL inputs require an input current in the order of microamps only when the input is high, and can be readily driven by the ICM7555. And, of course, CMOS inputs require negligibly low input currents for both the high and low states.

### OUTPUT WAVEFORM

We observed, when discussing Fig. 2.2, that when capacitor C is charging in a 555 or ICM7555 oscillator circuit the output is high, and that when the capacitor discharges the output is low.

Since the capacitor charges via the two resistors RA and RB in series, and discharges only via the single resistor RB, it follows that the period in the output cycle when the output is high must always be longer than the period when the output is low. This effect is shown in Fig. 2.7. As can be deduced, the ratio of the high voltage period to the low voltage period is equal to  $(RA + RB):RB$ .

For some applications it is desirable that the output be a 50:50 square-wave, with the output high in each cycle for the same length of time that it is low. This can be very nearly achieved by making RA very much lower in value than RB. If, for instance, RA were  $1k\Omega$  and RB  $100k\Omega$  the duty ratio (the ratio between the high period and the total cycle period) becomes  $101:(101 + 100)$ , which equals 50.25 per cent.

Duty ratios of 50 per cent or less can be given by inserting two silicon diodes, as shown in Fig. 2.8. Capacitor C then charges through RA and D1 and discharges through D1 and RB. Ignoring the 0.6 forward voltage drop in each diode,

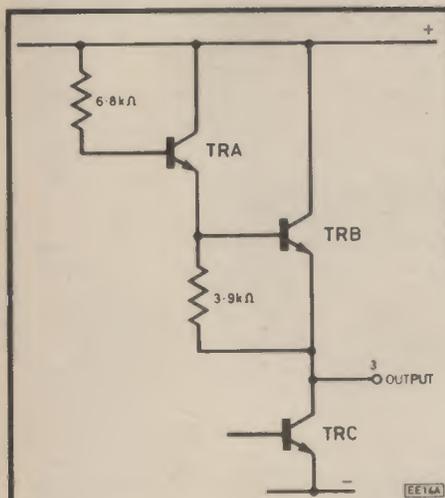






Fig. 2.4 (left). The internal output circuitry of the 555.

Fig. 2.5a (below left). Representative curve illustrating the voltage dropped in the 555 output stage when it sinks currents up to 100mA. Supply voltage is 9 volts.

Fig. 2.5b (below right). 555 voltage drop for source currents up to 100mA.

Fig. 2.6a (bottom left). ICM7555 output voltage drop for sink currents up to 70mA, with a supply of 9 volts.

Fig. 2.6b (bottom right). The ICM7555 has a limited output source current capability.

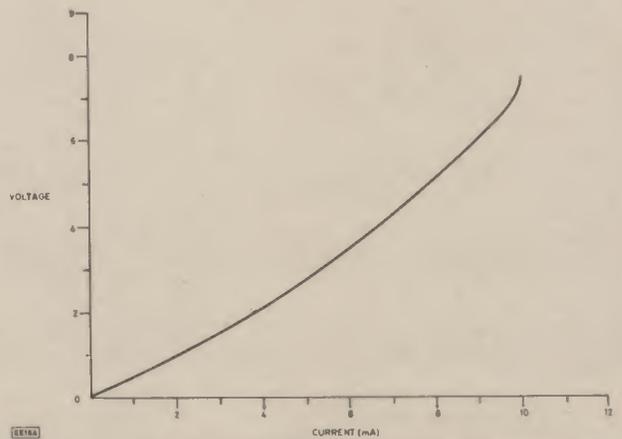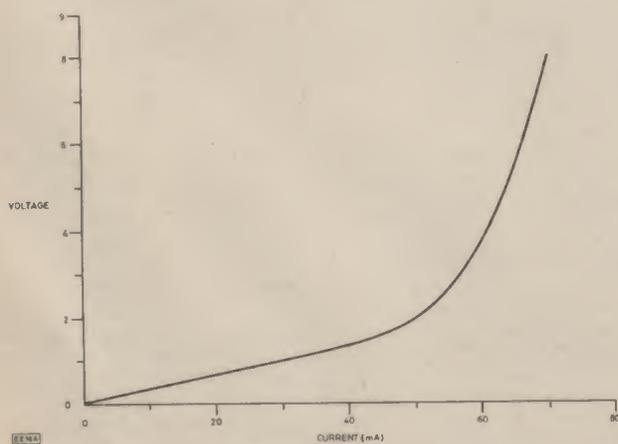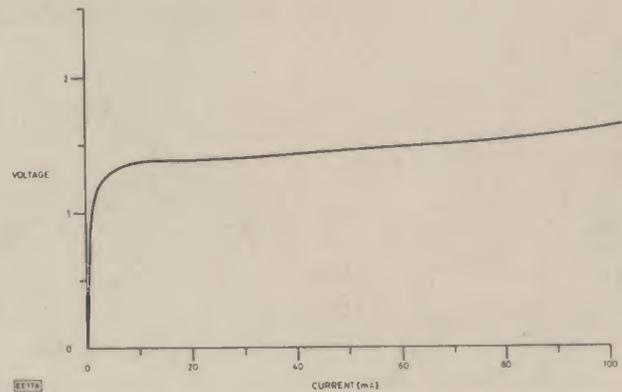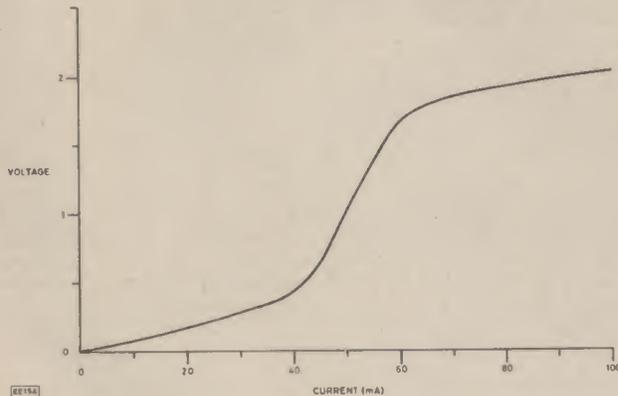

the period in the cycle when the output is high is equal to  $0.685(RA)C$  and the period when the output is low is equal to  $0.685(RB)C$ . To find frequency, the two periods are added and the sum inverted.

### INVERTER FUNCTION

When pins 2 and 6 of a 555 or ICM7555 are connected together and are taken below one-third of the supply voltage, the output at pin 3 is always high. The output is always low when pins 2 and 6 are taken above two-thirds of the supply voltage. This fact enables a 555 or ICM7555 to function as an inverter, using the circuit shown in Fig. 2.9.

If the output of IC1 in this circuit has a duty ratio of, say, 70 per cent, the output

of IC2 will have a duty ratio of 30 per cent. This arrangement enables duty ratios of less than 50 per cent to be achieved without the introduction of the two diodes of Fig. 2.8. An ICM7555 will drive a 555 employed as an inverter and this fact may be of assistance when it is desired to provide high load currents whilst using very high values for RA and RB in the ICM7555 oscillator circuit.

A useful trick for obtaining a 50:50 square-wave from the 555 or ICM7555 is to simply add a third resistor, RC, to RA and RB, as shown in Fig. 2.10. The i.c. gives a 50:50 output when RA is equal to RB and RC is equal to four times RA or RB. The added resistor causes the capacitor charging time to be shorter than that given by RA and RB on their

own, and the discharge time to be longer than that given by RB on its own.

The operating frequency with this circuit is about 12.5 per cent higher than the frequency which would be given with RC removed from the circuit. With the circuit shown in Fig. 2.10 the total cycle period is approximately equal to  $1.8(RA)C$  and the frequency to

$$\frac{0.55}{(RA)C}$$

### CHECKING THE DUTY RATIO

It is possible to check the duty ratio of a 555 or ICM7555 without an oscilloscope. All that is required is to slow down the oscillator by connecting a high value capacitor across C.

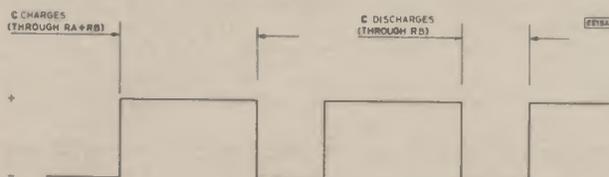


Fig. 2.7 (left). With the basic oscillator circuit of Fig. 2.2, the output is always high for a longer period in the cycle than when it is low.

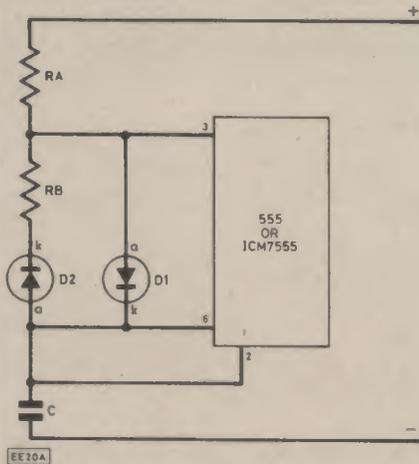


Fig. 2.8. It is possible to obtain duty ratios of less than 50 per cent by adding two silicon diodes. The capacitor charges through D1 and discharges through D2.

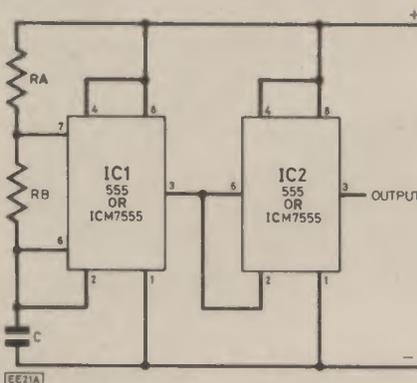


Fig. 2.9. Another way of obtaining duty ratios of less than 50 per cent is to employ a second 555 or ICM7555 as an inverter.

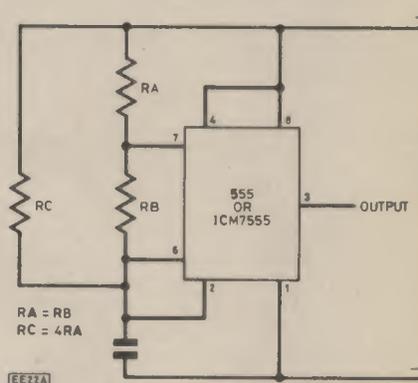


Fig. 2.10. If a third resistor is added and the resistor values are as shown here, the 555 or ICM7555 produces a 50:50 square-wave.

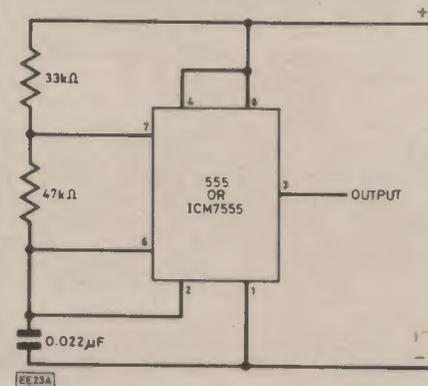


Fig. 2.11(a). An oscillator with a calculated frequency of 523Hz.

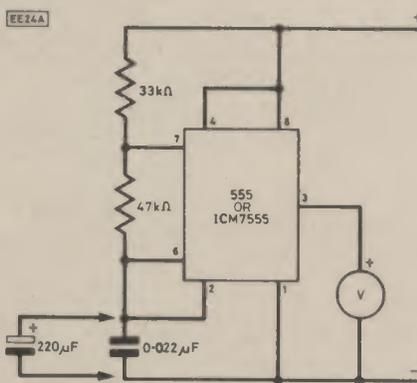


Fig. 2.11(b). The output waveform can be monitored with a voltmeter if the oscillator is slowed down by temporarily connecting a large value capacitor across the frequency control capacitor.

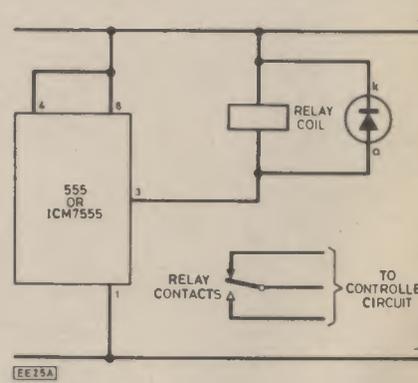


Fig. 2.12. With a very low frequency 555 or ICM7555 oscillator, external high current circuits can be controlled with the aid of a relay.

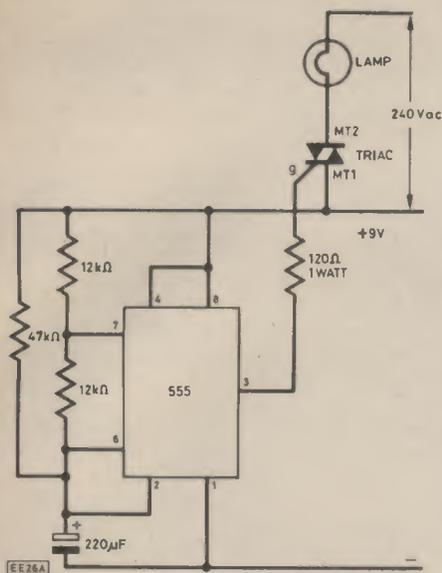


Fig. 2.13. In this circuit a 555 turns on a triac when its output is low.

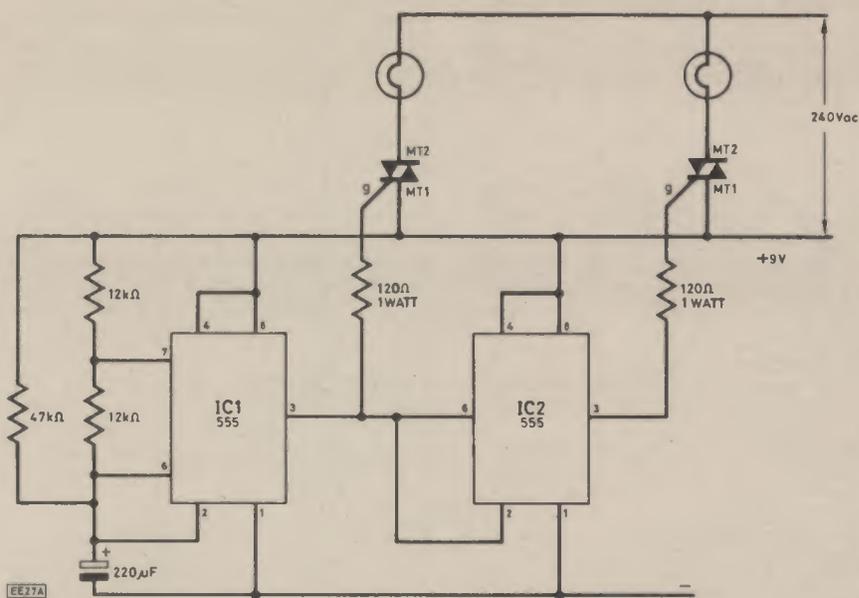


Fig. 2.14. Two 555s are used here to turn on two lamps, or sets of lamps alternately.

As an example, Fig. 2.11 (a) shows an oscillator with a calculated frequency of 523Hz. If a 220μF capacitor is temporarily connected across C, as in Fig. 2.11 (b), the calculated running frequency falls to 0.0523Hz with a total cycle length of 19 seconds.

The lengths of the high and low output periods in each cycle can then be assessed by connecting a voltmeter between the i.c. output and the negative rail and timing the periods with the aid of a watch.

Remember that, when the high value capacitor is initially applied, the i.c. output goes high for a longer period than it will subsequently do in the following cycles. This is because the capacitor has to charge from zero to two-thirds of supply voltage before the regular cycles commence.

## APPLICATIONS

There are a large number of applications for the 555 and ICM7555. Both may be used as oscillators giving a useful performance up to 100kHz, and can function as a.f. tone generators, logic clocks and in many other circuits.

When running at very low frequencies, either i.c. can be caused to turn on and off relatively heavy current circuits, such as lamps in an advertising display, by connecting the output to the coil of a relay, as in Fig. 2.12. The relay should be capable of energising reliably at a coil voltage of slightly less than the supply voltage, and reasonable figures for coil resistance would be such that energising current is less than some 50mA with the 555 and less than 20mA with the ICM7555.

Using a 9-volt supply (and ignoring voltage drop in the i.c.) these currents

correspond to coil resistances of about 180Ω and 450Ω, respectively. Higher relay energising currents within the capabilities of the i.c.s could, of course, be used if desired.

The diode shown in Fig. 2.12 can be any small silicon diode or rectifier, and it prevents the generation of a high reverse voltage across the relay coil when the relay is released.

Fig. 2.13 shows a 555 turning on a triac when its output is low. A triac gate current of around 50mA is given and, since the circuit operates in two of the more sensitive triac quadrants (MT2 positive or negative with gate negative) this current should be satisfactory with most small triacs. Gate current can be increased further, if necessary, by reducing the value of the resistor connecting to pin 3 of the 555.

Adding a second 555 as an inverter, as illustrated in Fig. 2.14, allows two lamps, or sets of lamps, to be turned on and off alternately. The frequency control component values give a nominal 50:50 output at approximately 0.2Hz with a total cycle length of about 5 seconds. The cycle length may be increased by increasing the value of the capacitor, or reduced by reducing that value.

## THE 556

A variant of the 555 is the 556 i.c. This is a 14-pin device which contains two 555s in one package, with pin 7 as the negative supply pin for both and pin 14 as the positive supply pin.

The functions for one of the 555s are available at pins 1 to 6, and those for the other 555 at pins 8 to 13. The pin allocations are shown in Fig. 2.15.

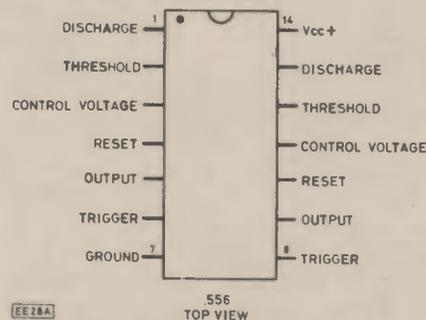


Fig. 2.15. The 556 i.c. comprises two 555s in a single package.

## OSCILLOSCOPE CALIBRATOR

A practical project which can employ either a 555 or an ICM7555 is shown in Fig. 2.16. In this circuit, switch S1 selects positive-going pulses having an amplitude of 1V, 100mV or 10mV, and these can be applied to an oscilloscope to set up its Y axis voltage calibration. The oscilloscope input couples to the Common and D.C. output terminals for a direct coupling, or to the Common and A.C. output terminals for an a.c. coupling.

IC1 produces a nominally 50:50 square-wave with a frequency of approximately 1kHz. IC2 is a 5-volt regulator which holds the emitter of TR1 at a fixed voltage of 5 volts  $\pm$  4 per cent. When IC1 output is high, TR1 is cut off since its base-emitter junction is reverse biased by about 4 volts. (IC2 output remains regulated for zero output current or small currents to the 9-volt positive rail.)

TR1 turns hard on when IC1 output goes low and its collector current flows through the chain of resistors, VR1,

# ★ BAKER ★

## GROUP P.A. DISCO AMPLIFIERS post £2

- 150 watt Output, 4 input Mixer pre-amp. Illustrated ..... £99
- 150 watt Output, Slave 500 mv. Input 3 Speaker Outputs ..... £80
- 150+150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs £125
- 150 watt P.A. Vocal, 8 inputs. High/Low Mixer Echo Socket £129
- 100 watt Valve Model, 4 inputs, 5 Outputs. Heavy duty ..... £125
- 60 watt Valve Model, 4 inputs, Low Imp and 100v line output £69
- 60 watt Mobile 240v AC and 12v DC. 4-8-16 ohm+100v line £89

## BAKER LOUDSPEAKERS

Type	Model	Size	Watts	Ohms	Price
P.A./Disco/Group	DG50/10	10	50	8/16	£18
Midrange	Mid 100/10	10	100	8	£25
Hi-Fi	Major	12in	30	4/8/16	£16
Hi-Fi	Superb	12in	30	8/16	£26
P.A./Disco/Group	DG45	12in	45	4/8/16	£16
Hi-Fi	Wooter	12in	80	8	£25
Hi-Fi	Auditorium	15in	60	8/16	£37
P.A./Disco/Group	DG75	12in	75	4/8/16	£20
P.A./Disco/Group	DG100	12in	100	8/16	£26
P.A./Disco/Group	DG100/15	15in	100	8/16	£35

DISCO CONSOLE Twin Decks, mixer pre amp £105. Carr £12.  
COMPLETE DISCO 150 watt £330; 300 watt £390. Carr £30.

DISCO MIXER, 240V, 4 stereo channels, 2 magnetic, 2 ceramic/ tape. 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, panel or desk mounting; grained aluminium fascia. Tape output facility. £49. Post £1.

DELUXE STEREO DISCO MIXER/EQUALISER as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. Headphone Monitor, Mike Talkover Switch ditto 7 Band Graphic £118. **£108 PP £2**

P.A. CABINETS (empty) Single £230; Double £236. carr £10. WITH SPEAKERS 60W £27; 75W £52; 90W £71; 150W £80. HORNBOXES 200 Watt £30, 300 Watt £35. Post £4.

WATERPROOF HORNS 8 ohms 25 watt £20. 30 watt £23. 40 watt £26. 200V plus 100v line £32. Post £2.  
MOTOROLA PIEZO ELECTRONIC HORN TWEETER 3in. square £5  
100 watts. No crossover required. 4-8-16 ohm. 7 1/2 x 3in. £10

CROSSOVERS TWO-WAY 3000 c/s 30 watt £3. 100 watt £4.  
3 way 350 cps/3000 cps. 40 watt rating. £4. 80 watt £5. 100 watt £8.

LOUDSPEAKER BARGAINS Please enquire, many others in stock.  
4 ohm. 5in. 7x4in. £2.50; 6in. 8x5in. £3. 8in. £3.50. 6in. 20W £7.50.  
8 ohm. 2in. 3in. £2; 5x3in. 6x4in. 7x4in. 5in. £2.50; 6in. 20W £7.50; 8 x 5in. £3; 8in. £4.50. 10in. £5; 12in. £8. 8in. 25W £6.50.  
15 ohm. 2in. 3in. 5x3in. 6x4in. £2.50; 6in. 10W £5. 8in. £4. 10in. £7.  
25 ohm. 3in. £2; 5x3in. 6x4in. 7x4in. £2.50. 120 ohm. 3in. dia. £1.

## LOUDSPEAKER

Make	Model	Size	Watts	Ohms	Price	Post
AUDAX	WOOFER	5in.	25	8	£10.50	£1
GOODMANS	HIFAX	7 1/2 x 4 1/2 in.	100	8	£30	£2
GOODMANS	HB WOOFER	8in.	60	8	£12.50	£1
WHARFEDALE	WOOFER	8in.	30	8	£9.50	£2
CELESTION	DISCO/Group	10in.	50	8/16	£21	£2
GOODMANS	HPG/Group	12in.	120	8/15	£28.50	£2
GOODMANS	HPD/DISCO	12in.	120	8/15	£29.50	£2
GOODMANS	HP/BASS	15in.	250	8	£72	£4
GOODMANS	HPD/BASS	18in.	230	8	£84	£4

## RCS SOUND TO LIGHT CONTROLLER KIT

All parts to build printed circuit. Cabinet, 3 channels, 1,000 watts each. Will operate from Hi-Fi or Disco. £19. Post £1.  
Latest Model Ready Built Deluxe 4 Channel 4,000 watt with chaser + speed + programme controls £69. Post £2.

## MAINS TRANSFORMERS

Model	Price Post
250-0-250V 80mA. 6.3V 3.5A. 6.3V 1A.	£7.00 £2
350-0-350V 250mA. 6.3V 6A CT £12.00 Shrouded	£14.00 £2
250V 60mA. 6.3V 2A.	£4.75 £1
220V 25mA 6V 1 Amp £3.00 220V 45mA 6V 2 Amp	£4.00 £1
Low voltage tapped outputs available	
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00 £2
ditto 2 amp £10.50 3 amp £12.50 5 amp £16.00 £2	

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid 9V, 3A, 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1 1/2A; 30V, 5A-17-0-17V, 2A; 35V, 2A; 20-40-60V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 25-0-25V, 2A.

## £7.50 post 50p MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument. Impedance  $\pm$  Capacity 4000 ohms. Battery included. 11 instant ranges measure DC volts 5, 25, 250, 500, AC volts 10, 50, 500, 1000. DC amps 0-250 $\mu$ A; 0-250mA. Resistance 0 to 600K ohms.  
De-Luxe Range Doubler Meter, 50,000 ohms p.p.v. 7 x 5 x 2in. Resistance 0/20 meg in 5 ranges. Current 50 $\mu$ A to 10A. Volts 0.25-1000V DC, 10v/1000v AC. £19.50 post £1

PANEL METERS £5.50 post 50p  
50 $\mu$ A, 100 $\mu$ A, 500 $\mu$ A, 1mA, 5mA, 100mA, 500mA, 1 amp, 2 amp, 5 amp, 25 volt, VU 2 1/2 x 2 1/2 Stereo VU 3 1/2 x 1 1/2 in.

ALUMINIUM CHASSIS 18 s.w.g. Undrilled, 4 sides, 4 corners: 6 x 4 x 2 1/2 in. £1.75; 8 x 6 x 2 1/2 in. £2.20; 10 x 7 x 2 1/2 in. £2.75; 14 x 9 x 2 1/2 in. £3.60; 16 x 6 x 2 1/2 in. £3; 12 x 3 x 2 1/2 in. £1.80; 12 x 8 x 2 1/2 in. £3.20; 16 x 10 x 2 1/2 in. £3.80.

ALI ANGLE BRACKET 6 x 1 1/2 x 3 1/2 in. 30p  
ALUMINIUM PANELS 18 s.w.g. 12 x 12 in. £1.80; 14 x 9 in. £1.75; 6 x 4 in. 5sp; 12 x 8 in. £1.30; 10 x 7 in. 9sp; 8 x 6 in. 9sp; 14 x 3 in. 7sp; 12 x 5 in. 9sp; 16 x 10 in. £2.10; 16 x 6 in. £1.30.

ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.  
4 x 2 1/2 x 2 1/2 in. £1.00; 3 x 2 x 1 1/2 in. 80p; 6 x 4 x 2 1/2 in. £1.60; 8 x 6 x 3 in. £2.50; 12 x 5 x 3 in. £2.75; 6 x 4 x 3 in. £1.80; 10 x 7 x 3 in. £3

HIGH VOLTAGE ELECTROLYTICS 32 x 32/350V ..... 50p  
20/500V ..... 75p 8 x 8/500V ..... £1 32 x 32 + 32/450V ..... 95p  
32/350V ..... 45p 8 x 16/450V 75p 125/500V ..... £2  
32/500V ..... 95p 16 x 16/350V 75p 16 x 32 + 32/500V ..... £2

## SINGLE PLAY DECKS. Post £2

Make	Model	Cartridge	Price
BSR	P170	Ceramic	£20
GARRARD	6200	Ceramic	£22
BSR	P182	Ceramic	£26
BSR	P232	Magnetic	£28
BSR	P200	Magnetic	£34
AUTOCHANGER	BSR	Ceramic	£20

## DECCA TEAK VENEERED PLINTH

Superior finish with space and panel for small amplifier.  
Board cut for BSR or Garrard 18in. x 14in. x 4in. £5  
Black/chrome fascia trim. Tinted plastic cover £5 Post £1

TINTED PLASTIC COVERS for Decks, Music Centres, etc. Post £1  
17 1/2 x 13 1/2 x 3 1/2 in. £5 18 1/2 x 12 1/2 x 3 in. £5  
17 1/2 x 9 1/2 x 3 1/2 in. £3 16 1/2 x 13 x 4 in. £5  
16 1/2 x 15 x 4 1/2 in. £5 14 1/2 x 13 1/2 x 2 1/2 in. £5  
17 x 12 1/2 x 3 1/2 in. £5 17 1/2 x 13 1/2 x 4 1/2 in. £5  
22 1/2 x 13 1/2 x 3 in. £5 21 x 13 1/2 x 4 1/2 in. £5  
21 1/2 x 14 1/2 x 2 1/2 in. £5 30 1/2 x 13 1/2 x 3 1/2 in. £5

## RADIO COMPONENT SPECIALISTS

Dept 4, 337, WHITEHORSE ROAD, CROYDON

SURREY, U.K. TEL: 01-684 1665

ACCESS

VISA

Post 5p Minimum Callers Welcome Lists 32p Same day despatch Closed Wed

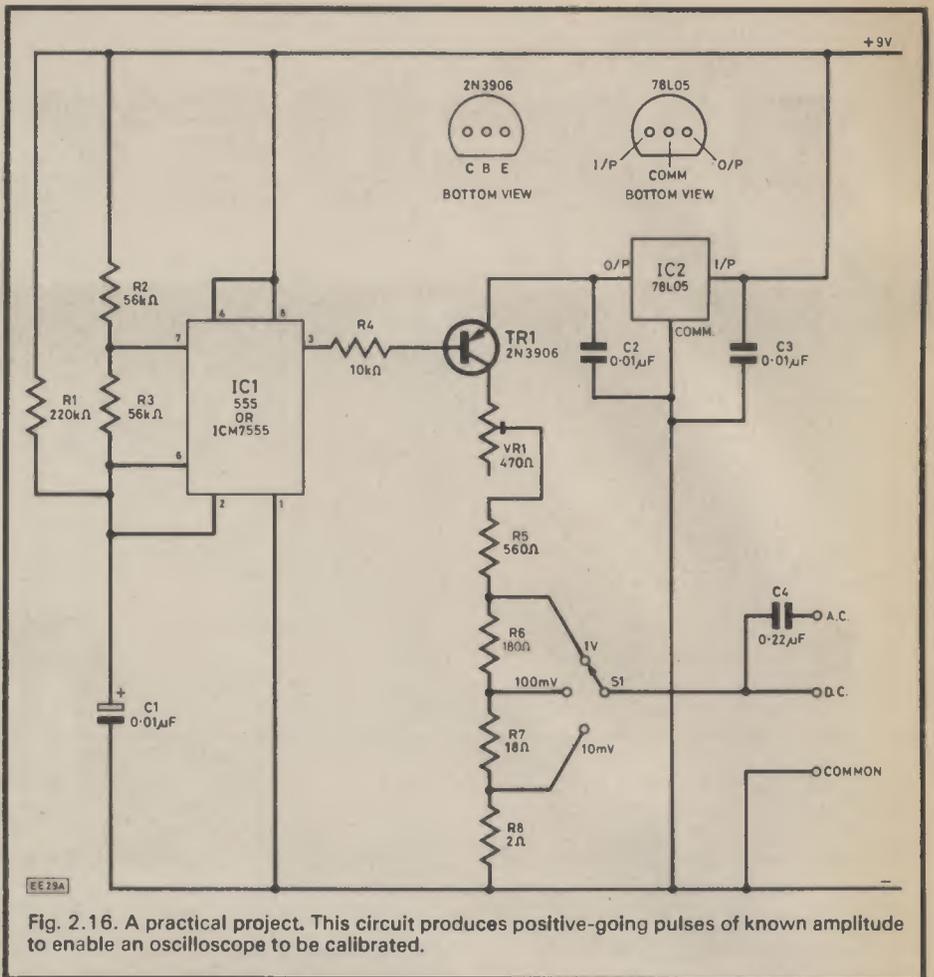


Fig. 2.16. A practical project. This circuit produces positive-going pulses of known amplitude to enable an oscilloscope to be calibrated.

R5-R8. VR1 is adjusted to make this collector current precisely 5mA. In consequence, 10mV is built up across R8, 100mV across R9 and R7, and 1V across R8, R7 and R6. These voltages are tapped off by S1.

After VR1 has been adjusted, the current in the resistor chain maintains its value because the collector-emitter voltage of TR1, when turned on, is always less than 0.1 volt, and because the transistor is supplied by the voltage regulator. The current drawn from the 9-volt supply is about 9mA with a 555, or about 5mA when using an ICM7555.

There are no critical features in the assembly of the circuit, apart from the fact that C2 and C3 should be positioned close to IC2.

## SETTING-UP

Potentiometer VR1 is adjusted in the following manner. Set S1 to the 1V position and connect a voltmeter capable of giving a clear reading of 1 volt between the Common and D.C. terminals. Temporarily short-circuit R1. This takes pins 2 and 6 of IC1 high and drives pin 3 low, turning on the transistor. Adjust VR1 until the voltmeter indicates exactly 1V. Remove the short-circuit across R1, whereupon the calibrator is ready for use.

For optimum accuracy, R6, R7 and R8 should be 1 per cent resistors. If difficulty is experienced in obtaining a close tolerance 2Ω resistor for R8, this can consist instead of a 1 per cent 2.2Ω and a 1 per cent 22Ω resistor in parallel.

Part Three of this series will discuss the use of digital CMOS devices in RC oscillator circuits.

# PLEASE TAKE NOTE

Circuit Exchange (June 84)

Digital Capacitance Meter

The connection from IC6 pin 11 and IC7 pin 6 can be used to extend the range of the display to two digits, by the addition of extra counter and driver i.c.s.

all in the  
**AUGUST**  
issue!



In 1931 Karle Guthe Jansky mounted a make-shift aerial on an old Ford chassis and became the world's first radio-astronomer. This article takes a trip through the fifty-three year history of this fascinating subject and covers the basic principles right up to present day operating techniques.

### **COMMODORE 64 RS232C INTERFACE**

This straightforward project will allow the Commodore 64 to drive a printer directly, or to communicate via a serial line with other machines.

### **FIELD MEASUREMENTS USING A CASSETTE RECORDER**

Any cassette recorder may be turned into a real-time data logger using V-to-F techniques. We describe the principles involved, and present a simple design.

## **PORTABLE CHESS GAME OFFER**

**PRACTICAL**

# **ELECTRONICS**

THE AUGUST ISSUE WILL BE ON SALE FRIDAY, JULY 6th

# C.B. Mini Power Supply

T.R. de Vaux Balbirnie

**H**AND-HELD CB transceivers having an output of 2 watts are of interest to outdoor enthusiasts wishing to extend their hobby beyond home and car. Tests show that portable units are surprisingly good for home-base use. Naturally, they are limited compared with the 4-watt equipment but range is rarely a problem if a good outdoor antenna is employed. Hand-held CB units have a socket for this purpose.

For home use it makes sense to use a mains-operated power supply to maintain maximum power output and to conserve the rather short life of the batteries. Such a power supply is the subject of this article.

## SUITABILITY

The Mini Power Supply is suitable for CB transceivers requiring a 12-volt supply at up to 1 amp. Power is usually provided in these units by eight 1.5V cells

or ten nickel cadmium batteries. The *Harrier WT2* is one such example requiring approximately 500mA in the "transmit" mode and about 70mA when switched to "receive". In this respect, the manufacturer's leaflet seems to over-rate the current requirement.

The project is described as "mini" since it provides sufficient current for the intended purpose with only a little reserve. In this way, the physical size and cost are kept low. Ready-built units are made with mobile equipment in mind. They can supply a higher current and usually operate at about 13.8V. The higher output voltage could damage hand-held equipment.

Before constructing the power supply, read the manufacturer's leaflet to check that less than 1A is required when transmitting (although, as stated previously, this may be over-stated). If this data is not available—or if in doubt—make a direct measurement using an ammeter. This should be connected in series with the battery supply. For this test, make sure that the batteries are fresh so that the *maximum* current is measured.

## CIRCUIT DESCRIPTION

The circuit for the CB Mini Power Supply is shown in Fig. 1. Mains current flows through S1 and the primary winding of T1. The secondary then gives about 12V a.c. This is converted into d.c. by the bridge rectifier D1-D4 then

smoothed by means of C1. This provides about 16V d.c. Regulation is achieved by IC1 so that a steady 12V is obtained at the output whatever the current drawn by the CB equipment. IC1 also gives short circuit, overload and thermal protection.

The mains switch, S1, incorporates a neon indicator. C2 and R1 ensure correct operation of IC1. *Note:* The case of the project, being metal, is connected to the negative of the output so simplifying much of the wiring.

## CONSTRUCTION

Use the aluminium case specified in the parts list. The specified transformer fits the case comfortably with plenty of ventilation space all round. Holes should be made for S1 and for the input and output wires. These latter holes must be fitted with rubber grommets.


Mount T1 and IC1 as shown (see photograph). Note that IC1 makes metal-to-metal contact with the case so providing the common negative connection. For this reason, the centre tag of IC1 is not used and may be cut off short if desired. When mounting T1, include a solder tag beneath one of the fixings for earthing later. A further solder tag is used for the negative connection of C1 and the bridge rectifier. Solder C2 and R1 in parallel to the piece of tag strip. Mount this in position (see photograph) noting that one side of C2 and R1 are connected to the case. The output connections are also made to these tags.

## MAINS LEAD

Pass the mains inlet wire through the grommet and make the soldered connections to S1. A neutral connection is needed here for the neon indicator to work. From S1, connections are made to the 240V primary of T1. In the prototype a connection was needed between the two 120V primary windings (Fig. 2).

Solder the earth wire of the mains lead to the solder tag at T1. This earths the case and the transformer core. *This is essential safety procedure—on no account use this project on a non-earthed supply.*

Complete all wiring (Fig. 2). Check for short circuits. Bend component leads as necessary to allow a free flow of air. Tie string tightly around the inlet and output

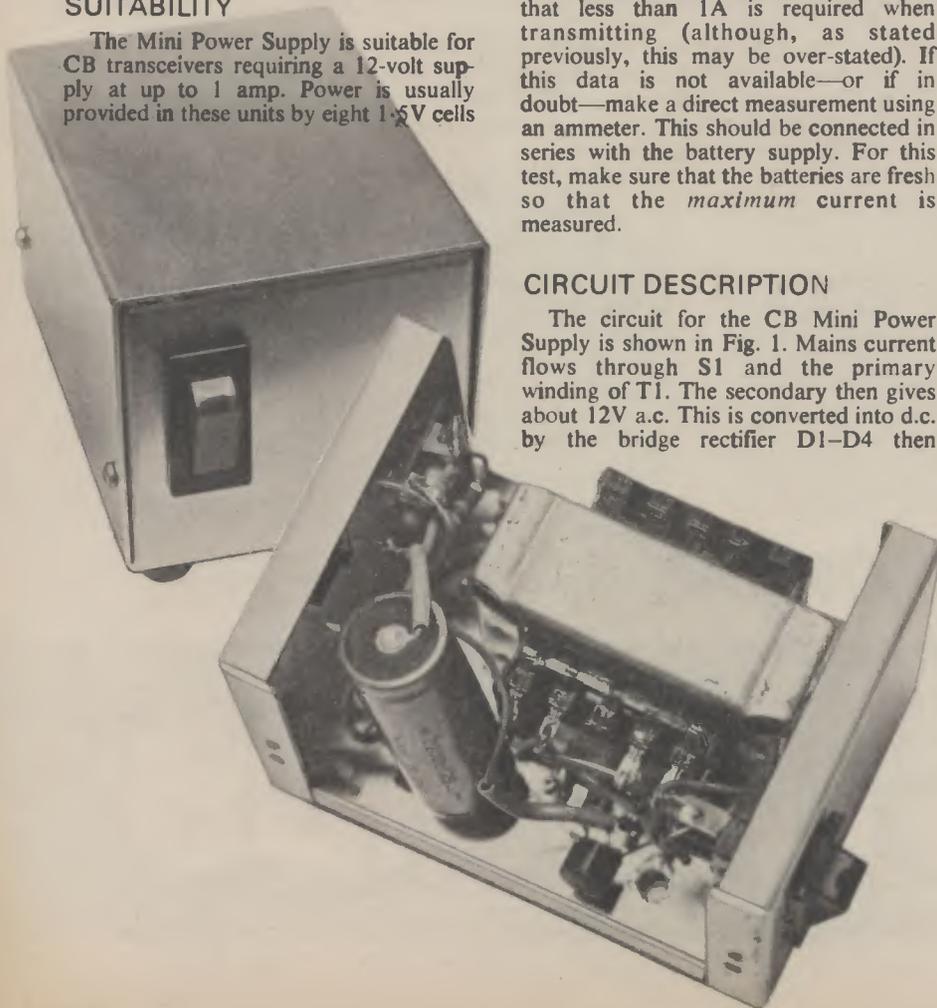

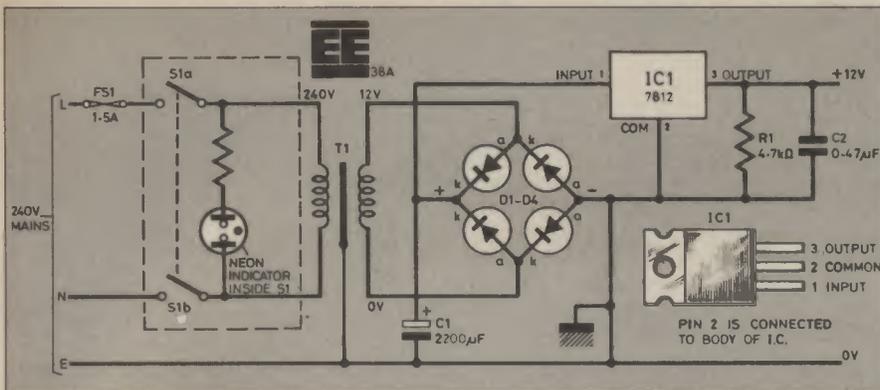


Fig. 1. Complete circuit diagram for the CB Mini PSU.

wires where they enter the case to provide strain relief. Pull the leads to make sure that connections are not dislodged.

Using great care, drill four or five 6mm holes in the base of the box to provide ventilation. These holes must obviously be clear of any wiring or components. Fit the feet on the case. These are necessary not only to prevent scratching of the work surface but also to allow ventilation. Mount the lid on the case slightly higher than normal by lengthening the fixing holes slightly. This will leave 2 or 3mm gaps at the front and rear. These will also assist with ventilation.

### CONNECTING TO THE CB EQUIPMENT

The best way of connecting the output wires to the CB is to use two dummy batteries. Hand-held units usually use HP7 (AA) size batteries. Dummies of this size are freely available. Making certain that the correct polarity is observed, use one

for the positive and one for the negative connection. It is not necessary to remove the bridge linking the two ends of the dummy batteries together, in fact this may be used to accept the soldered connection.

Insert the dummy batteries in the extreme positions normally occupied by the real batteries. Unless the back is to be left off while operating the CB it will be necessary to file a corner off so that the connecting wire may pass with it in place.

If the power supply delivers a continuous 1A output it will become quite warm after a long period of operation. In normal use, there will be periods of receiving as well as transmitting and the current requirement on "transmit" will probably fall well short of 1A anyway. In practice, the case of the prototype remained fairly cool. When using for the first time, however, a frequent check should be made on the temperature of the case. A poor quality component for T1 could cause overheating. □

## COMPONENTS

See  
**Shop  
Talk**  
page 434

### Resistor

R1 4.7kΩ  
½W carbon ±5%

### Capacitors

C1 2200µF elect.  
16V or higher  
C2 0.47µF—any rating  
above 12V

### Semiconductors

IC1 7812 12V/1A regulator  
D1-4 50V 1A silicon bridge  
rectifier

### Miscellaneous

T1 Mains transformer with  
240V (or 2 off 120V)  
primary. 12V (or 2 off  
6V) secondary. 1A  
rating. RS type  
207-633.

S1 Double-pole mains  
rocker switch with  
neon indicator


FS1 1.5A fuse (and holder).  
AB28 aluminium. 102 x  
case 70 x 64mm approx.

Two sections of tag strip; solder  
tag—2 off; rubber grommets—2  
off; 3A 3-core mains cable; 2-core  
output wire; feet for case—4 off;  
connecting wire; solder; sleeving;  
dummy batteries—2 off; open  
construction type (see text).

Approx. cost  
Guidance only

**£10.00**

Fig. 2. Wiring diagram. Note that pin 2 of IC1 is internally connected to the metal tab.

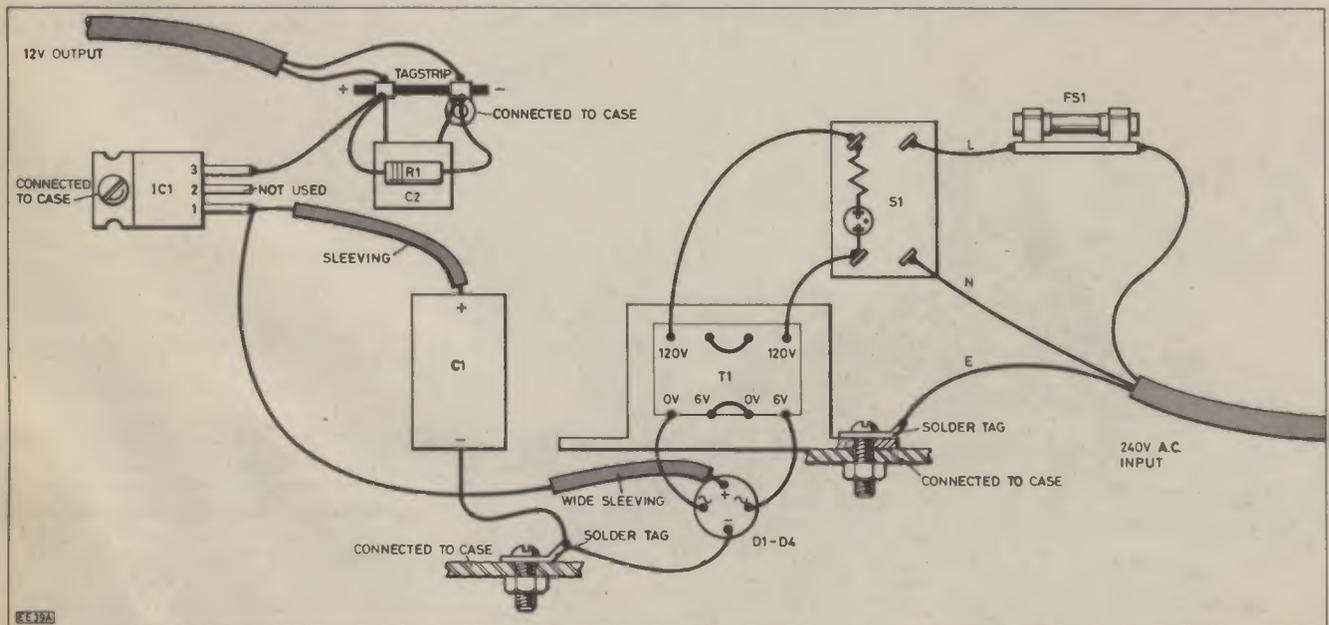

**T**HIS unit has been designed to warn drivers to put their lights on when the amount of daylight falls below a preset level and also to remind them to switch off their lights at the end of a journey should the ignition be switched off before the lights; if parking lights are required then the ignition should be turned off and the lights switched off then on again. The design also includes a charging circuit indicator so that the buzzer will not operate at low light levels if the charging circuit is not supplying current to the battery.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the Car Lights Warning is shown in Fig. 1. The light dependent resistor R1, the preset VR1 and the resistor R2 form a potential divider across the 12 volt supply. The resistance value of the LDR increases as the light level falls, causing the voltage at point A to fall. This falling voltage forward biases the base/emitter junction of TR1 switching TR1 on and therefore TR2 via R3. The voltage at the emitter of TR2 is applied to the buzzer WD1 via D4 and to the gate terminal of CSR2 via R7.

The resistors R7 and R8 together with the capacitor C2 form a time delay of between 18 and 20 seconds after the engine has been turned on. After this time the thyristor CSR2 fires and the buzzer is energised.

Once the alarm has been activated it can be disabled by switching on the car lights which will turn TR1 off via the positive voltage applied through D3 to its base. As TR1 turns off the base current to TR2 is reduced and TR2 turns off,

removing the supply to the buzzer and turning off CSR2. The buzzer would remain on if current was allowed to flow straight to it from the lighting circuit so TR3, CSR1, R3, R4, R5 and C1 are used to form a delay circuit to enable CSR2 to be shut down. Diode D4 is used to isolate the gate of CSR2 when it is required to park with the lights on otherwise the buzzer will sound again.

As soon as the ignition is turned on CSR3 fires but has no effect on TR4 until the ignition is switched off again and providing that the lights are on, TR4 will conduct, supplying gate current to CSR4 regulated by R10 and R11, firing the device, and turning the buzzer on again.

## DIODE PROTECTION

Diode D1 isolates the lighting circuit from the ignition circuit as well as reducing any spikes that may be generated by the ignition circuit. Diodes D5, D6, D7 and D8 are all used as isolators and diode D2 protects the base/emitter junction from any pulses present when the lights are switched on. D9 is included to hold TR3 off when driving with the lights on as it was found that leakage current through C2 can sometimes trigger CSR2 on.

## STRIPBOARD

The components are mounted on a piece of stripboard measuring 18 strips by 26 holes. The component layout and track breaks are shown in Fig. 2.

After the components have been soldered into position the case can then be drilled and the light dependent resistor (R1), the two l.e.d.s (D10 and D11), and

the two in-line fuses fitted and wired to the stripboard. Check there are no solder shorts on the board and that all the track breaks are completely cut through.

## INSTALLATION AND SETTING UP

The unit should be mounted into position using double sided tape and placed where daylight can fall directly onto the LDR. Before finally fixing the unit into position it should be set up correctly. Because the output from different charging circuits can vary by as much as 3 volts a 220kΩ preset can be used in place of R7 to set the operation of the buzzer. A final value of R7 between 150kΩ and 180kΩ should be suitable for most cars.

The two supply leads to the circuit should go to the light switch and the ignition switch. Because it is not always possible to wire directly to both these switches the wiring diagram of the car should be studied to decide the best place to make the connections.

When the unit is in position and it is dark outside the engine should be started and VR1 adjusted to bring on the buzzer. The rest of the operation of the circuit can then be tested. □

## SPECIFICATION

For use on negative earth vehicles only  
Working voltage 10–16 volts d.c.

Current consumption:

- @ 14V (no lights) 6mA
- @ 14V (with lights) 8.5mA
- @ 14V (parking lights on) 3mA

# CAR LIGHTS WARNING

H. B. Foster



Everyday Electronics, July 1984

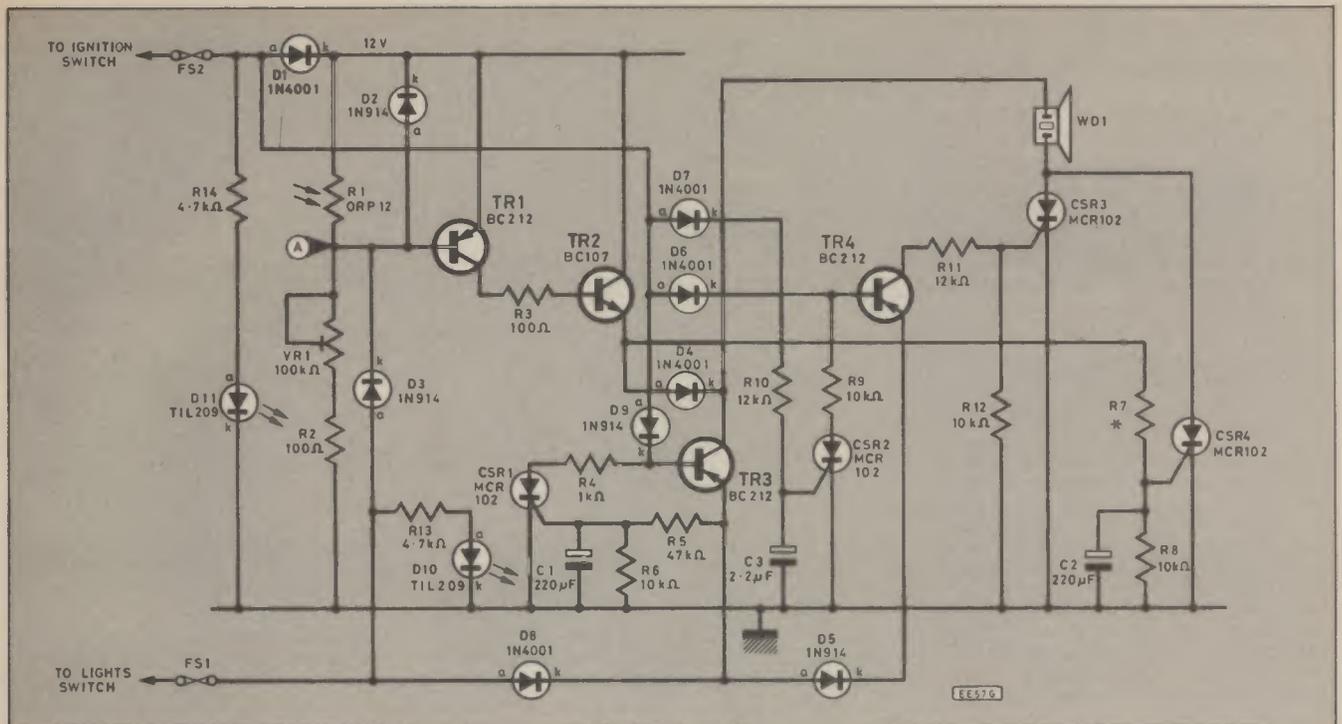


Fig. 1. Circuit diagram of the Car Lights Warning.

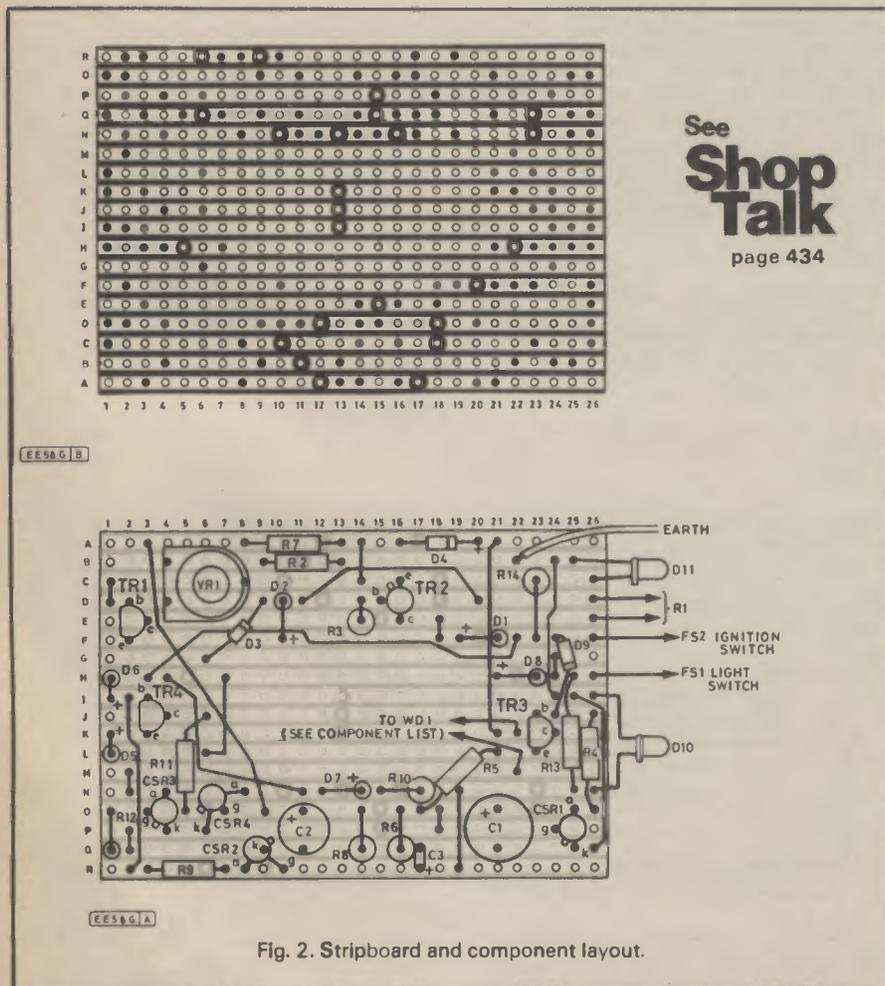


Fig. 2. Stripboard and component layout.

## COMPONENTS

### Resistors

- R1 ORP 12 light dependent resistor
- R2,3 100Ω (2 off)
- R4 1kΩ
- R5 47kΩ
- R6,8,9,12 10kΩ (4 off)
- \*R7 220kΩ
- R10,11 12kΩ (2 off)
- R13,14 4.7kΩ (2 off)
- VR1 100kΩ hor. min. preset
- All resistors ½W 5% carbon

### Capacitors

- C1,2 220µF 16V radial elect. (2 off)
- C3 2.2µF 16V radial elect.

### Semiconductors

- D1,4,6,7,8 1N4001 (5 off)
- D2,3,5,9 1N914 (4 off)
- D10,11 TIL209 red l.e.d. (2 off)
- TR1,3,4 BC212 (3 off)
- TR2 BC107
- CSR1,2,3,4 MCR102 (4 off)

### Miscellaneous

- FS1,2 100mA fuse (2 off)
- WD1 12V d.c. buzzer Maplin FL40T

- Panel mounted in-line fuse holder (2 off)
- Plastic case 78 x 50 x 25mm
- Stripboard 18 strips by 26 holes
- \* See setting up procedure

Approx. cost  
Guidance only

**£11.00**

# SQUARE one FOR BEGINNERS

THE COMPONENTS LIST for any construction project will nowadays usually include some integrated circuits (i.c.s). There are hundreds of different i.c.s now available, costing anything from a few pence to several pounds; generally, the cost reflects the complexity of the device, but very popular complex devices (such as microprocessors) are relatively cheap.

Integrated circuits may be considered as falling into one of two categories; linear, or logic, and it is under these headings that they are usually advertised by component suppliers. The suppliers' catalogues should be consulted for details of power supply requirements and connections for any particular i.c., but it is possible to give some general information, and to explain the numbering system. For beginners, simple projects are obviously best, and the regular *Circuit Exchange* feature should provide plenty of good ideas.

## LINEAR INTEGRATED CIRCUITS

These have been designed to provide, in one package, a commonly-required function; examples include general-purpose amplifiers, voltage regulators and video amplifiers. A very popular device is the 555 precision timer; although essentially this circuit simply provides a time delay, home constructors have found hundreds of applications for it. General-purpose amplifiers include the 741 and 748, and all the devices are available from a number of manufacturers in various package types.

The letters associated with the number indicate the maker and the packaging: common prefixes include LM and NE. The letter after the number, if any, indicates the package type, for example H for a metal can, and N for a dual-in-line package. Because different manufacturers have different conventions, it is the type number which is normally referred to in the text. For example, if a "555 timer" is specified, the device could equally well be LM555CN (National), CA555CE (RCA), or NE555N (Signetics).

Once this is understood, pin numbers on the package can be related to the circuit diagram connections, and a working project can be completed without having to know what is actually inside the i.c. Some common package types for linear i.c.s are shown in Fig. 1.

## LOGIC CIRCUITS

Most of the logic i.c.s used in projects have 14 or 16 pins and are housed in a standard dual-in-line package (Fig. 2). Unlike linear circuits, which may require a number of different power supply connections, TTL (Transistor-Transistor Logic) i.c.s work on only two

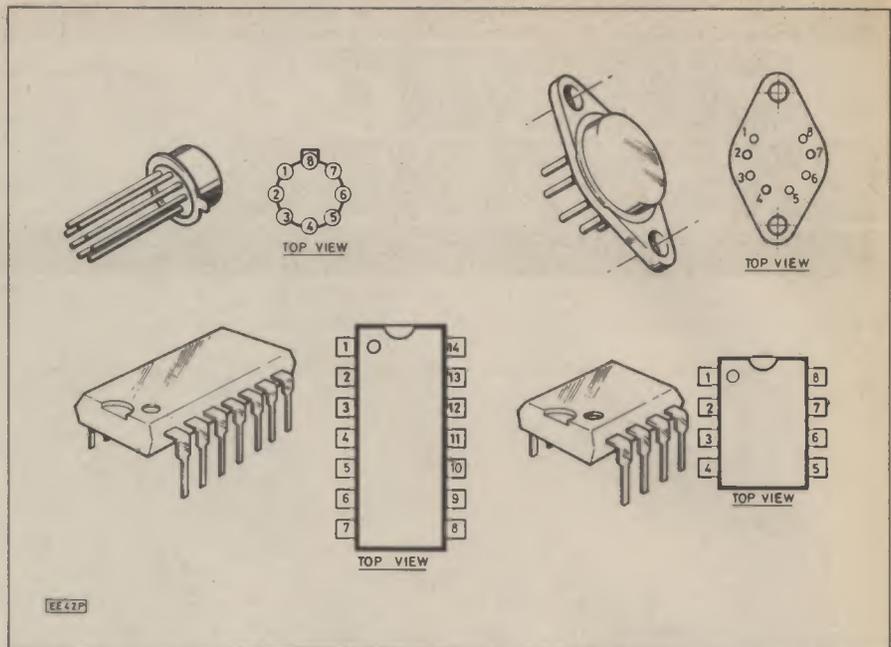


Fig. 1. Pin numbering for linear i.c.s. Metal cans have either a tag or a wider pin spacing to identify pin 8. Dual-in-line packages have a notch and/or a depression to indicate pin 1.

levels: +5 volts and ground (zero volts). For all standard TTL i.c.s, +5 volts is connected to pin 14 (or pin 16 for a 16-pin package), and zero volts to pin 7 (or pin 8). The functions of the other pins depend on the device, but Fig. 3 shows the inputs and outputs for a quad 2-input AND gate. It is called a quad gate because there are actually four separate, independent gates inside the chip. So a design

which indicates the type of circuit. An '08, as shown, is a quad AND gate, while an '02 is a quad NOR gate. The final letter shows the package type, which is usually plastic dual-in-line, indicated by the letter N or P.

Finally the letters "LS", as in SN74LS08N: this stands for "low-power Schottky" and means that the i.c. is a fast-switching type. There are other families of TTL (for example very low power and super-fast) but either LS TTL or standard TTL is usually specified for projects. Different families should not, as a rule, be mixed.

## CMOS

These digital integrated circuits are designed for use where low power consumption is required, or where the power supply may be "noisy" (random fluctuations in voltage level). This makes them ideal devices for some applications, but CMOS operates more slowly than TTL. The part number is made up of a manufacturer's prefix (e.g., MC1 for Motorola), followed by four digits beginning with "4" to indicate function, and then one or more letters to show the package type. A plastic dual-in-line quad 2-input NAND gate could be MC14011BCP (Motorola) or CD4011BE (RCA) or CD4011BCN (National). The number which specifies the function is 4011, and it is this which the supplier advertises.

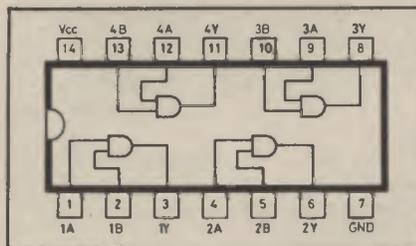


Fig. 3. Internal connections for a 7408 or 74LS08 quad 2-input AND gate.

which required eight such gates, for example, would only need two i.c.s.

The part number is made up of a manufacturer's prefix (usually SN), followed by the number 74 for standard circuits (54 for a wide temperature range), and then the number


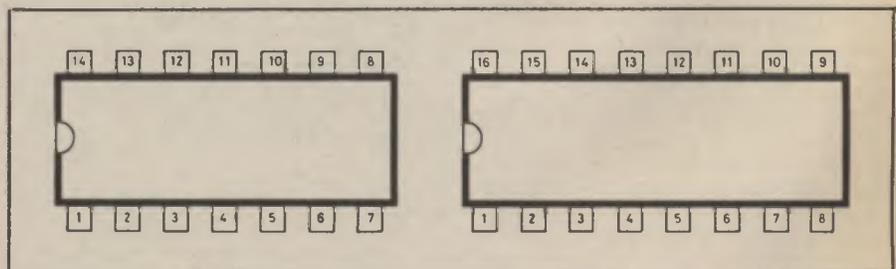


Fig. 2. Dual-in-line 14-pin and 16-pin TTL i.c.s have a notch at the end of the package to identify pin 1.
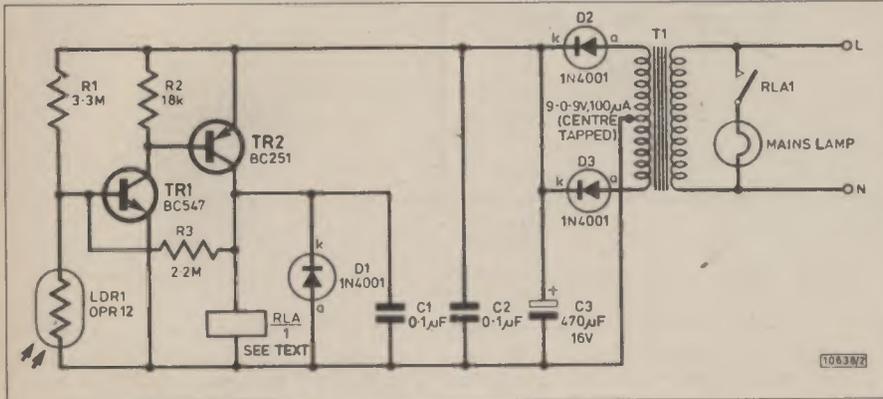
# CIRCUIT EXCHANGE


This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised. Payment is made for all circuits published in this feature. Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.



## SIMPLE PHOTOELECTRIC SWITCH

This circuit requires very few components and is therefore cheap to build, yet despite its simplicity is able to switch at very low light levels, the level being set by R1. Whenever possible the l.d.r. should be kept away from the lamp being controlled to prevent feedback. If difficulty is experienced then R3 can be lowered to increase the difference between Switch-On and Switch-Off light levels, and may also solve feedback problems. None of the component values or types are critical, except that the relay should have a minimum resistance of 185 ohms.

R. Ormston,  
Southampton,  
Hants.

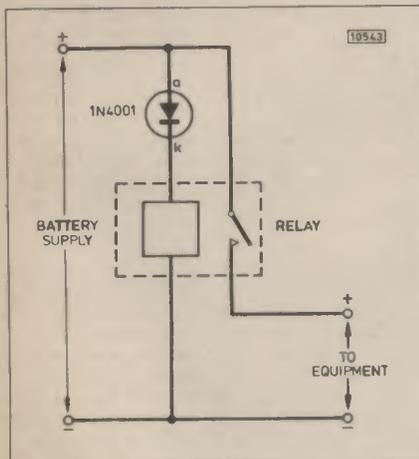

## REVERSED BATTERY PROTECTION

When constructing portable electronic equipment, it is often advisable to have some form of protection should the battery be connected the wrong way around.

A diode connected in series with one of the supply lines will do, but has the disadvantage of producing a forward volt drop of about 1V. A neater solution, which produces no drop in the supply, is to use a relay, as in the circuit shown.

With the battery connected correctly, the diode conducts, operating the relay, and applying power to the equipment. Should it be

reversed, the diode blocks the flow of current through the relay coil preventing it from switching on.



P. Thompson,  
Lennoxton,  
Glasgow.

## MOTORCYCLE ALARM

In this circuit a 555 timer (IC1) is used as a monostable, and when triggered by pin 2 being brought low, drives another 555 (IC2) which is wired as an astable. The output from IC2 turns TR1, and thus the relay on and off. This gives a series of bursts of the horn for a time set by R2 and C1. Pin 2 can be triggered by a ball bearing tilt mechanism, as shown in the diagram.

This unit can also be used in cars by wiring the trip switch wire to the courtesy light. Pin 2 will be held high via the lamp, and will be triggered by the car door being opened. If this method is used it will be necessary to install an isolation switch outside the car.

G. Bamford,  
Clackheaton,  
West Yorks.

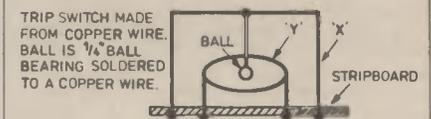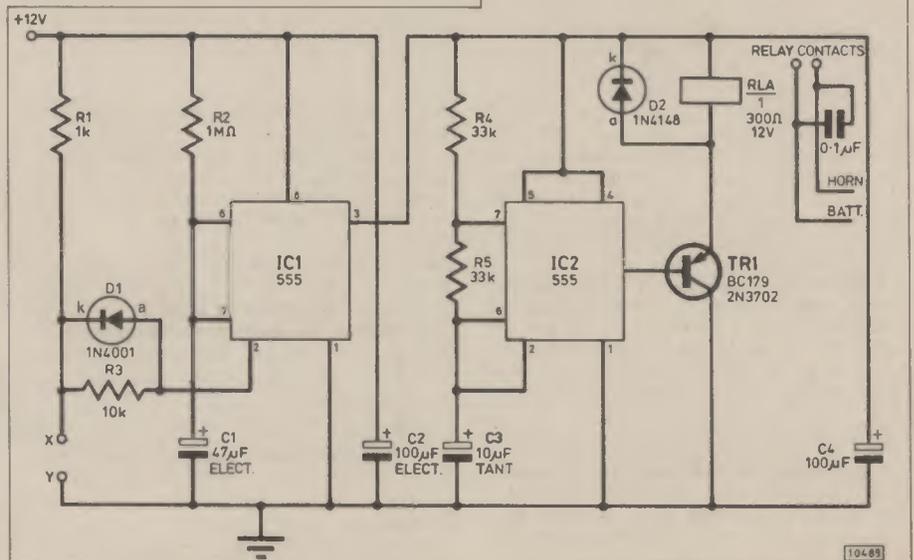

# CIRCUIT EXCHANGE

## LOW NOISE HIGH GAIN PREAMPLIFIER



THIS useful circuit has pre-programmable high gain and can be used for many applications. The gain of the circuit will be set at  $\times 30$ ,  $\times 160$  or  $\times 700$ , by selecting R3 to be

150 $\Omega$ , 680 $\Omega$  or 4.7k $\Omega$ , respectively. The output of the circuit is suitable for most power amplifiers and may also be used to drive headphones independently of power amps.

A small 9V battery can be used as a power supply and because of the low current consumption of the circuit, the life of such a battery will be long. However, if you wish to use this preamplifier with a power amplifier it is better to use the P.A. power supply. In this case the use of a noise filter is essential.

When using the filter R6 should be 1.2k $\Omega$  minimum for a 12V supply. If higher voltages are being used then this should be increased to 4.7k $\Omega$ . The maximum supply voltage should be 18V.

Kamel Alizadeh,  
Tehran,  
Iran.

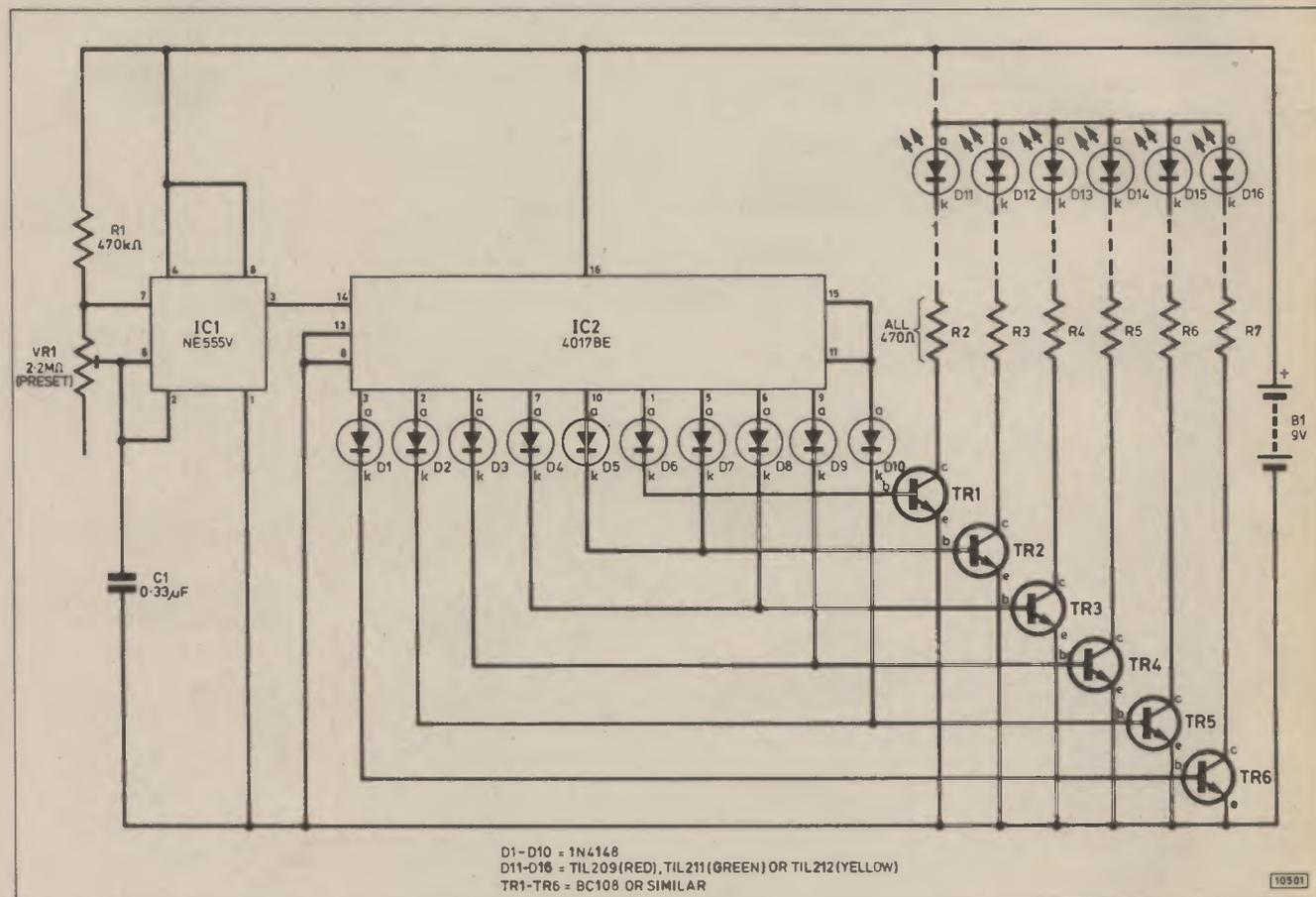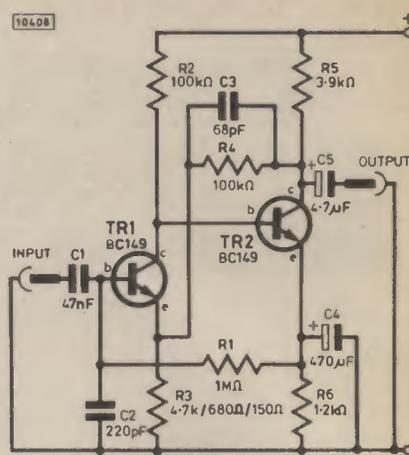

## FLASHING DECORATION LIGHTS

THIS circuit was designed last Christmas to improve on the stationary, rather drab decorations in the living room with the aid of flashing lights arranged to give the appearance of one light moving back and forth. The heart of the circuit is IC2, a CMOS decade counter divider with ten decoded outputs. Therefore, with each positive pulse given to pin 14 (the clock input), the output from one pin drops, and the next pin in the series rises to supply

voltage. The pulses are provided by IC1, a 555 timer, wired up to give astable square waves from the output pin. The resistance across pins 6 and 7 is variable so that the frequency of the pulses can be altered to a pleasing value.

The first six outputs of IC2 are connected via signal diodes to the bases of six transistors controlling I.e.d.s, so that with the first six pulses the I.e.d.s are lit in order. To give the appearance of the light moving back, the seventh output is connected to the transistor base from the fifth, the eighth to that of the

forth and so on. Pin 11 (the tenth output) is also connected to pin 15 (reset) to allow continuous operation. The I.e.d.s situated in order across the room are joined to the main circuit by seven wires; one from each cathode and one for the supply line. The bundle of wires, which incidentally diminish to two at the farthest end, is easily hidden amongst other decorations if bound together and covered with dark insulation.

M. Allen,  
Pinner,  
Middlesex.

# T.V. SOUND TUNER

**SERIES II BUILT AND TESTED** Complete with case. £26.50 + £2.00 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is this for quality reproduction. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10 1/2" x 7 1/2" x 2 1/4". E.T.I. kit version of above without chassis, case and hardware. £16.20 plus £1.50 p&p.



Also available with built-in headphone amp. ONLY £32.50 + £2.00 p&p.

## PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT

COMPLETE WITH CASE ONLY £34.50 plus £2.75 p&p.

- NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TYPES.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Featured in April P.E. reprint 50p. Free with kit.



## 125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

Accessories: Stereo mains power supply kit with trans. £10.50 + £2 p&p. Mono: £7.50 + £2 p&p.



**SPECIFICATIONS:**  
Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £12.00 + £1.15 p&p. BUILT £17.50 + £1.15 p&p.

## GOODMANS SPEAKERS AT BARGAIN PRICES

7" 60 watt Bass/Midrange speaker. 8 ohm impedance. Frequency response: 40 - 6,000Hz. 4 1/4" x 1/2" magnet. £14.95 plus £1.75 p&p.



12", 65W, impedance 4 ohms. Frequency response: 35 - 6,500Hz. Magnet: 3/4" x 4 1/4" dia. Foam surround, vinyl laminated cone. For use in Hi-Fi systems up to 65 watts. Bass/Midrange. £13.95 + £2.50 p&p.



## BSR RECORD DECKS

Auto-Changer model - takes up to 6 records with manual override. Supplied with stereo ceramic cartridge. £12.95 plus £1.75 p&p.

3 speed, auto, set-down; with auto return. Fitted with viscous damped cue, tubular aluminium counter-weighted arm, fitted with ADC magnetic head. Ideally suited for home or disco use. £25.95

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx. £14.95 plus £1.75 p&p.



## HI-FI SPEAKER BARGAINS

**AUDAX 8" SPEAKER** £5.95 + £2.20 p&p.  
High quality 40 watts RMS bass/mid. Ideal for either HiFi or Disco use this speaker features an aluminium voice coil and a heavy 70mm dia. magnet. Freq. Res.: 20Hz to 7kHz. Imp.: 8 ohms.



**AUDAX 40W FERRO-FLUID HI-FI TWEETER** Freq. res.: 5KHz - 22KHz. Imp.: 8 ohms. 60mm sq. £5.50 + 60p p&p.

**GOODMANS TWEETERS** 8 ohm soft dome radiator tweeter (3 1/2" sq) for use in systems up to 40W. £3.95 ea + £1 p&p. £6.95 pr + £1.50.



## STEREO TUNER KIT

SPECIAL OFFER!

£13.95 + £2.50 p&p.



This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July '81). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. Front scale size 10 1/2" x 2 1/4" approx. Complete with diagram and instructions.

## MONO MIXER AMP

Ideal for halls and clubs.

£45.00 + £2 p&p.

50 Watt, six individually mixed inputs for 2 pickups (Cer. or mag), 2 moving coil microphones and 2 auxiliary for tape tuner, organs etc. Eight slider controls - 6 for level and 2 for master bass and treble, 4 extra treble controls for mic. and aux. inputs. Size: 13 1/4" x 6 1/2" x 3 3/4" app. Power output 50 W RMS (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.



CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include VAT.



TWO FABULOUS OFFERS FROM

# ALCON

## The incredible 'MINI 20'

28 ranges  
20kΩ/V d.c. & 4kΩ/V a.c.  
(With protective fuse)

Accuracy: 2% d.c. and resistance, 3% a.c.

28 ranges: d.c. V 100mV, 3V, 10V, 30V, 100V, 300V, 600V. d.c. 150μA, 600μA, 6mA, 60mA. a.c. V 15V, 50V, 150V, 500V, 1500V. a.c. 130mA, 300mA, 3.0A. Ohms 0-2kΩ, 0-2MΩ. dB from -10 to +62 in 6 ranges.


Dimensions: 105 x 130 x 40mm.

The 28 ranges cover all likely requirements. Operation is straightforward, just turn the selection switch to the required range.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10.00.

THE IDEAL INSTRUMENT FOR THE CONSTRUCTOR

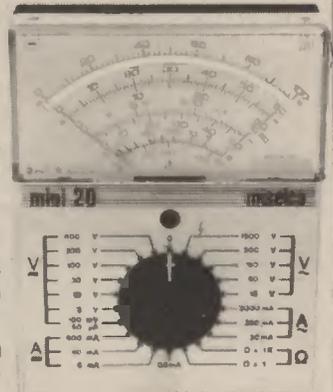(complete with carrying case, leads and instructions)



ONLY £21.60

## 'SUPER 20'

A SUPER PROTECTED UNIVERSAL MULTIMETER



★ 20KΩ/V  
AC AND DC

★ 39 RANGES

★ INDESTRUCTIBLE  
(automatically protected  
on all ranges but 10A)

Accuracy: d.c. ranges and Ω 2% a.c. 3% (of f.s.d.)  
39 ranges: d.c. V 100mV, 1.0V, 3.0V, 10V, 30V, 100V, 300V, 1000V. d.c. I 50μA, 100μA, 300μA, 1.0μA, 3mA, 10mA, 30mA, 100mA, 1A, 10A. a.c. V 10, 30V, 100V, 300V, 1000V; a.c. I 3mA, 10mA, 30mA, 100mA, 1.0A, 10A. Ω 0-5.0kΩ, 0-50kΩ, 0-500kΩ, 5MΩ, 50MΩ. dB from -10 to +61 in 5 ranges.

Dimensions: 105 x 130 x 40mm.

These special offers is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £20.00.

(complete with carrying case, leads and instructions)

ONLY £33.50

PRICES Our prices include VAT and postage and goods are normally despatched by return.

For details of these and the many other instruments in the Alcon range, including multimeters, components measuring, automotive and electronic instruments, please write or telephone:

**ALCON** Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

## Courses

**CONQUER THE CHIP**—master modern electronics the practical way by seeing and doing in your own home. Write for your free colour brochure now to **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**, Dept C3, Reading, Berks RG1 1BR.

## INVENTORS

Think of something new?  
Write it down!

American industry offers potential royalties for your innovations and new products. We offer free confidential disclosure registration and initial consultation in London regarding your idea's potential value. Write without delay for your free information package.

**American Inventors Corporation**  
82 Broad Street, Dept. EV,  
Westfield, Massachusetts 01086,  
United States of America  
A fee based marketing company

## Receivers & Components

**500 SMALL COMPONENTS** including TTL transistors £2.50, 7lbs or 10lbs assorted components £5.00/£6.50. Fifty 74 series I.Cs on panel £2.20. Post Paid. J. W. BLANSHARD, 2 Barnfield Crescent, Sale Cheshire, M33 1NL.

**VERY LARGE PACK** of Mixed Components. Capacitors, Transistors, Resistors, Diodes, Boards, Thyristors, Multipin Plugs & Sockets and many more items. £6.50p post & packing inclusive. G. EVANS, 7, Mendip Close, Pendine Park, Summerhill, Wrexham, Clwyd.

**COMPONENTS & EQUIPMENT**—1984 Catalogue 70p + 20p P&P. Callers: 18 Victoria Road, TAMWORTH. 369 Alumrock Road, BIRMINGHAM. 103 Coventry Street, KIDDERMINSTER. Express Mail Order Service. LIGHTNING ELECTRONICS, PO Box 8, Tamworth, Staffs.

**TURN YOUR SURPLUS** capacitors, transistors etc., into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. 0945-584188. Immediate settlement.

# EVERYDAY ELECTRONICS and computer PROJECTS

Reach effectively and economically to-days enthusiasts anxious to know of your products and services through our semi-display and classified pages. Semi-display spaces may be booked at £7.80 per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 33 pence per word (minimum 12 words), box number 60p extra. All cheques, postal orders, etc., to be made payable to

## Security

**WHO CAN PUT A PRICE ON A PEACE OF MIND**  
PROFESSIONAL EQUIPMENT AT LOW, LOW PRICES.  
**HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES**  
ADVANCED SECURITY PRODUCTS LTD  
2 Ealing Road, Aintree,  
Liverpool L9 0HU, Merseyside.  
Tel: 051-525 3440  
FREE CATALOGUE  
PHONE OR S.A.E.

## For Sale

**WORKING TEST EQUIPMENT**, signal generators, variable P.S.U.s meters, isolating transformers and breakdown units etc. at giveaway prices. S.A.E. to: S.H.E. 5 St. Josephs, Ballycruttle, Downpatrick, BT30 7EN.

## Miscellaneous Cont.

**THE SCIENTIFIC WIRE COMPANY**  
811 Forest Road, London E17. Telephone 01-531 1568

SWG	ENAMELLED COPPER WIRE		
	1 lb	8 oz	4 oz
8 to 34	3.63	2.09	1.10
35 to 39	3.82	2.31	1.27
40 to 43	6.00	3.20	2.25
44 to 47	8.67	5.80	3.49
48	15.96	9.58	6.38

SWG	SILVER PLATED COPPER WIRE		
	1 lb	8 oz	4 oz
14 to 30	9.09	5.20	2.93

SWG	TINNED COPPER WIRE		
	1 lb	8 oz	4 oz
14 to 30	3.97	2.41	1.39

Fluxcore Solder 5.90 3.25 1.82 0.94  
Prices include P&P VAT. Orders under £2 add 20p.  
SAE for list of copper and resistance wire.  
Dealer enquiries welcome.

**TO ADVERTISE ON THESE PAGES PLEASE RING PAT ON 01-261 5942**

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for .....  
Insertions. I enclose Cheque/P.O for £ .....  
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)


NAME .....  
ADDRESS .....  
.....  
.....

## EVERYDAY ELECTRONICS

Classified Advertisement Dept., Room 2612,  
King's Reach Tower, Stamford Street, London SE1 9LS  
Telephone 01-261 5942

Rate:  
33p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

7/84

# AT YOUR SERVICE

Everyday Electronics and Computer Projects and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics and Computer Projects, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St, London SE1 9LS. (Telephone 01-261 5942).

## Service Sheets

**FULL SIZE SERVICE SHEETS** £2 + 1sae; CTV/MusC £3 + 1sae. Repair/circs almost any named TV/VCR £9.50. 1sae free quotations for manuals, sheets - free mag inc. service sheet. T.I.S.E.E. 76 Church Street, Larkhall, Lanarks - Phone 0698 883334.

**BELL'S TELEVISION SERVICE** for service sheets on Radio, TV etc. £1.50 plus S.A.E. Service Manuals on Colour TV and Video Recorders, prices on request. S.A.E. with enquiries to: BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

## OVERSEAS ORDERS

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only. Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

## FREE CAREER BOOKLET

### Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your **FREE CAREER BOOKLET** today—at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

<b>ELECTRONICS ENGINEERING</b>	<input type="checkbox"/>	<b>TV &amp; AUDIO SERVICING</b>	<input type="checkbox"/>
<b>ELECTRICAL ENGINEERING</b>	<input type="checkbox"/>	<b>RUNNING YOUR OWN BUSINESS</b>	<input type="checkbox"/>

Name .....  
Address .....

**ICS**  
Division of National Education Corporation

ICS  
Dept ECS74  
160 Stewarts Road,  
London SW8 4UJ



01-622 9911  
(all hours)

## INDEX TO ADVERTISERS

AC/DC Electronics .....	479
Alcon Instruments .....	477
Bi-Pak .....	Cover II
BK Electronics .....	422
B.N.R.E.S. ....	420
Bull J. ....	423
Circuit Holdings .....	418, 419
Dzuibas M. ....	420
Electrovalue .....	420
Enfield Electronics .....	433
Greenweld Electronics .....	422
ICS Intertext .....	479
Magenta Electronics .....	Cover III
Maplin Electronics .....	Cover IV
Radio Comp. Spec. ....	468
R & TVC .....	477
Rapid Electronics .....	421
Software Index .....	480
Sparkrite .....	422
T.K. Electronics .....	424

*the  
Leader  
of the  
Packs*

### BIG VALUE RESISTOR PACKS

½ WATT CARBON FILM  
1Ω-10MΩ ten values. **£5**  
Total 720 resistors.  
½ WATT METAL FILM  
1% 50ppm 10Ω-1MΩ E24 range. **£25**  
Total 960 resistors.

## FREE CATALOGUE

Sent to every new customer

### AC/DC COMPONENT PACKS

Pack No.	Qty	Description	Price
TF11	12	RED 5mm LED	£1.00
TF12	30	500mz ZENERS 5%	£1.00
TF13	100	IN4148 Diode	£1.00
TF14	100	IN4151 Diode	£1.00
TF15	50	1 amp Rect. Diodes in 4000 series	£1.00
TF16	6	1 amp Bridge Rect.	£1.00
TF17	100	Transistor pads	£1.00
TF18	20	A/S Fuses 20mm	£1.00
TF19	10	3A Rect. Diodes	£1.00
TF110	2	ORP 12	£1.00
TF111	5	BR 100 DIAC	£1.00
TF112	10	BC109B	£1.00
TF113	10	IC's all different	£1.00
TF114	50	BFR86	£1.00
TF115	12	8 pin DIL sockets	£1.00
TF116	20	10mm Horiz. Pre set (10 values)	£1.00
TF21	200	47pf 160v Polystone cap	£2.00
TF22	10	LM 3900 N	£2.00
TF23	10	Mixed DTL	£2.00
TF24	5	4700 mf 25v Tag Elect 2"×1"	£2.00
TF25	10	1000 mf 63v Ax Elect.	£2.00
TF26	50	.022 mf 400v RAD POLY	£2.00
TF27	10	100mf 250v Ax	£2.00
TF28	10	2.2mf 160v Polyester RAD	£2.00
TF51	100	white/red 5mm LED	£5.00
TF52	50	BC 108C	£5.00
TF53	2	10,000mf 63v comp. grade elect.	£5.00
TF54		½ kg reel 22g ersin multicore solder	£5.00
TF55	10	2N3055 H(RCA)	£5.00
TF56	5	OCP71	£5.00

ALL PRICES INCLUDE VAT - ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.

TERMS: Cash with order. POST & PACKING: Please add 75p to total order.

## AC/DC ELECTRONICS COMPONENTS

DEPT E.E. 45 CHURCH STREET, ENFIELD, MIDDLESEX.





# MAPLIN Massive range of components for your hobby....insist on Maplin quality!

## MAPLIN'S TOP TWENTY KITS

THIS LAST MONTH	DESCRIPTION OF KIT	ORDER CODE	KIT PRICE	DETAILS IN PROJECT BOOK
1. (1)	75W Mosfet Amp Module	LW51F	£12.95	Best of E&MM
2. (2)	Modem	LW99H	£44.95	5 XA05F
<i>Case also available: YK62S Price £9.95.</i>				
3. (3)	Car Burglar Alarm	LW78K	£6.95	4 XA04E
4. (4)	Partylite	LW93B	£9.45	Best of E&MM
5. (5)	ZX81 I/O Port	LW76H	£9.25	4 XA04E
6. (7)	Syntom Drum Synthesiser	LW86T	£11.95	Best of E&MM
7. (6)	Spectrum Keyboard	LK29G	£28.50	9 XA09K
<i>Also required: LK30H £6.50; Case: XG35Q £4.95 — Total £39.95.</i>				
<i>Also available complete ready-built: XG36P £44.95.</i>				
8. (50)	Spectrum Easyload	LK39N	£9.95	10 XA10L
9. (9)	8W Amp Module	LW36P	£4.45	Catalogue
10. (11)	Logic Probe	LK43P	£9.95	8 XA08J
11. (13)	Ultrasonic Intruder Detector	LW83E	£10.95	4 XA04E
12. (8)	VIC20/64 RS232 Interface	LK11M	£9.45	7 XA07H
13. (10)	Harmony Generator	LW91Y	£17.95	Best of E&MM
14. (14)	Spectrum RS232 Interface	LK21X	£17.95	8 XA08J
15. (12)	Keyboard for ZX81	LW72P	£23.95	3 XA03D
<i>Case also available: XG17T £4.95. Complete ready-built: XG22Y £32.50</i>				
16. (16)	Noise Gate	LK43W	£9.95	Best of E&MM
17. (28)	Burglar Alarm	LW57M	£49.95	2 XA02C
18. (15)	Hexadrum	LW85G	£19.95	Best of E&MM
19. (17)	Guitar Tuner	LW90X	£10.75	Best of E&MM
20. (30)	Synwave Sounds Synth	LW87U	£10.95	Best of E&MM

Over 80 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.



## MAPLIN'S FASCINATING PROJECTS BOOKS

Full details in our Project Books  
Price 70p each.

In Book 1 (XA01B) 120W rms Mosfet Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • 6 Vero Projects. In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W Mosfet Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to 600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) 300 Baud Duplex Modem to European Standard • 100W 240VAC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Alarm.



In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 • Module to Bridge two of our Mosfet Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20/Commodore 64 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.

In Book 8 (XA08J) Modem (RS232) Interface for Dragon 32 & Spectrum • Synchime • I/O Ports for Dragon 32 • Electronic Lock • Minilab Power Supply • Logic Probe • Doorbell for the Deaf.

In Book 9 (XA09K) Keyboard with Electronics for ZX Spectrum • Infra-

Red Intruder Detector • Multimeter to Frequency Meter Converter • FM Radio needs no alignment • Hi-Res Graphics for ZX81 • Speech Synthesiser for Oric 1 • VIC20 Extendiboard • ZX81 ExtendIRAM • Dynamic Noise Limiter for Personal Cassette Players • TTL Levels to RS232 Converter • Logic Pulsar • Pseudo-Stereo AM Radio • Ni-Cad Charger Timer

Adder-Subtractor • Syndrum's Interface • Microphone Pre-Amp Limiter. In Book 10 (XA10L) Cassette Amateur Receiver • Auto Waa-Waa Effects Unit • Oric 1 Modem Interface • 2.8kW Mains Power Controller • Extendiport for Dragon 32 • 12V Fluorescent Tube Driver • 32-Line Extension for Digi-Tel.

### 1984 CATALOGUE

A massive 480 big pages of description, pictures and data and now with prices on the page. The new Maplin catalogue is the one book no constructor should be without. Now includes new Heathkit section. On sale in all branches of W.H. Smith. Price £1.35 — It's incredible value for money. Or send £1.65 (including p & p) to our mail-order address.

### GREAT PROJECTS FROM E&MM

Our book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first Year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerio Boost, MOS-FET Amp and other musical, hi-fi and car projects. Order As XH61R. Price £1.

Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packaging. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65

Name .....

Address .....



EE/7/84

## MAPLIN ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 • Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926. • 8 Oxford Road, Manchester. Tel: 061-236-0281. • Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292. • 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000. • 46-48 Bevois Valley Road, Southampton. Tel: 0703 25831. All shops closed all day Monday. All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

# BI-PAK BARGAINS

## MINIATURE TOOLS FOR HOBBYISTS

 Miniature round nose side cutters - insulated handles 4 1/2 inch length. Order No: Y043

 Miniature long nose pliers - insulated handles 5 1/2 inch length. Order No: Y044

 Miniature bend nose pliers - insulated handles 5 1/2 inch length. Order No: Y045

 Miniature end nippers - insulated handles 4 1/2 inch length. Order No: Y046

 Miniature snipe nose pliers with side cutter and serrated jaws - insulated handles 5 1/2 inch length. Order No: Y042

### FLEKEY DRIVER


A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch. Order No: FS-1 Flat blade 4mm FS-2 Cross point no. 1 £1.75 each.

### GRIP-DRIVER

8 1/2 inch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No: SD-1 Flat blade 4mm SD-2 Cross point no. D. £95p each.

ALL AT £1.25 each

## 13 PIECE TOOL KIT AND CASE

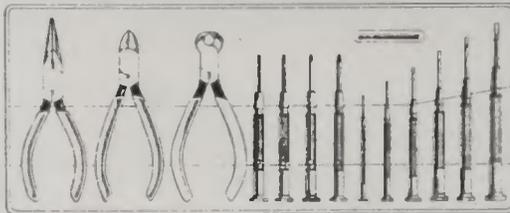

13-piece tool set housed in attractive moulded plastic case with clear sliding cover

- 1 off 5" snipe nose "radio" pliers with side cutters
- 1 off 4 1/2" side cutters
- 1 off 4 1/2" end cutters
- 2 off hex. "Allen" key drivers 2mm and 2.5mm;
- 2 off cross-point "Phillips" drivers No. 0 and No. 1 (with tommy bar)
- 6 off precision screwdrivers. Sizes from 1mm to 3.5mm

ONLY £7.50 ORDER No. VP102

## PRECISION JEWELLERS' TOOLS

Rustproof, Tempered Handles and Blades. Chrome Plated Handles Swivel Heads for use on Precision Work.

### 5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm £1.75

### 5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm £1.75

### 5T41 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers - H0 and H1 Hex key wrenches Sizes - 1.5, 2 and 2.5mm £1.75

### 5T51 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm £1.75

## MULTITESTER

1,000 opv including test leads & Battery

AC volts - 0-15-150-500-1,000  
DC volts - 0-15-150-500-1,000  
DC currents - 0-1ma-150ma  
Resistance - 0-25 K ohms 100 K ohms

Dims - 90 x 61 x 30mm.  
O/No. 1322 OUR PRICE £6.50 ONLY

## BRAND NEW LCD DISPLAY MULTITESTER

RE 188m  
LCD 10 MEGOHM INPUT IMPEDANCE  
3 1/2 digit \*16 ranges plus hFE test facility for PNP and NPN transistors \*Auto zero, auto polarity \*Single-handed, pushbutton operation \*Over range indication \*12.5mm (1/2-inch) large LCD readout \*Diode check \*Fast circuit protection \*Test leads, battery and instructions included.

Max indication 1999 or -1999  
Polarity indication Negative only  
Positive readings appear without + sign  
Input Impedance 10 Megohms  
Zero adjust Automatic  
Sampling time 250 milliseconds  
Temperature range -5°C to 50°C  
Power Supply 1 x PP3 or equivalent 9V battery  
Consumption 20mW  
Size 155x88x31mm

### RANGES

DC Voltage 0-200mV  
0-2-20-200-1000V. Acc. 0.8%  
AC Voltage 0-200-1000V  
Acc. 1.2% DC Current 0-200uA  
0-2-20-200mA. 0-10A. Acc. 1.2%  
Resistance 0-2-20-200K ohms  
0-2 Megohms. Acc. 1%

BI-PAK VERY LOWEST PRICE  
£45.00 each  
Leather Case for 188m £2.50 EACH



## SPEAKER PROTECTOR


Limits voltage to speaker or to the permissible max., by automatically introducing a resistor in series with speakers. When excessive voltage is reduced the unit resets itself. Electronic voltage-sensing relay circuit. Spring terminals. Cut-off level adjustable from 10W-120W. Full instructions included. Dims: 85 x 74 x 25mm.  
O/No. VP 118 £9.95



## ANTENNA SWITCH 2 and 3 WAY

Co-axial switch for one transceiver to two antennae or one antenna to two transceivers. Dims: 86 x 55 x 32mm (Body).  
O/No. VP 113 £4.50

As above but 3-way.  
O/No. VP 114 £4.75

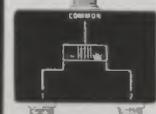

## HIGH PASS FILTER/SUPPRESSOR

CB/TV. High pass filter. Reduces unwanted signals picked up by antenna. Dims: 45 x 25 x 17mm  
O/No. VP 115 45p

## LOW PASS FILTER

Designed to reduce harmonics on the VHS and TV band. Cut-off frequency: 30MHz. V.S.W.R.: Less than 1.2 to 1. Insertion loss: -0.2dB @ 27MHz. Impedance: 50 ohms. Dims: 80 x 55 x 40mm.  
O/No. VP116 £2.75



## DC-DC POWER SUPPLY

DC to DC adaptor. Plugs into car cigar lighter aperture. Output 3, 4.5, 6, 7.5, 9, 12V @ 800mA. Has universal output spider plug, also 9V battery snap and polarity reversing facility.  
O/No. VP 119 £2.45

## SIGNAL INJECTOR

Simple push button operation. Oscillates at 700 - 1k Hz with harmonics to 30MHz. 1.4V p/p output. Impedance 10kΩ. Ideal for trouble shooting with audio equipment. One "AA" penlight battery supplied.  
O/No VP96 £2.50

## LOGIC PROBE

Automatic levelling. White LED indication. Minimum width of measuring pulse 30 milliseconds. Maximum input frequency 10M Hz. Input impedance: 100kΩ. Power consumption: 40mA maximum. 4.5 - 18 V d.c. Power supply.  
ORDER No. VP97 £10.50


## CURRENT/POL CHECKER

Heavy duty test prods with built-in indicators for testing polarity; indicates whether a.c. or d.c. 3.5V to 400V.  
O/No. VP98 £2.50

## TESTER

Universal tester with ceramic buzzer. Tests diodes, transistors, resistors, capacitors and continuity. One "AA" penlight battery included.  
Test current: Max 2µA  
Test voltage: 12V  
Response range: 100MΩ  
Max voltage: 500V  
Internal resistance: 390kΩ £5.00  
Length: 135mm O/No. VP99

 D.C. continuity tester for circuit checking on all low voltage equipment and components. Diode checking also possible. Takes two AA batteries. 90cm lead has crocodile clip. Body length 145mm  
O/No. VP100 75p

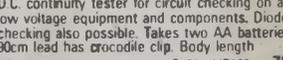 D.C. continuity tester for circuit checking on all low voltage equipment and components. Diode checking also possible. Takes two AA batteries. 90cm lead has crocodile clip. Body length 145mm  
O/No. VP100 75p

## ELECTRONIC SIREN 12v DC

Red plastic case with adjustable fixing bracket. Emits high-pitched wailing note of varying pitch - 100 cycles per minute. Dims - 90mm (dia.) 60mm (depth). Power - 12v DC. O/P 90dB 1m type.  
Our Price: £5.50 O/No. VP79

## TAPE RECORDER SWITCH

Unit to control motor of tape recorder. 1.8m cord and 2.5mm plug attached. On/Off switch. Dims: 55 x 20 x 20mm.  
O/No. VP 127 £1.00

## POWER SUPPLY OUR PRICE £4.25

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug. Input - 240V AC 50Hz. Output - 3, 4, 5, 6, 7.5, 9 & 12V DC Rating - 300 ma VP103


## RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size. 2 cross point size 4 & 6. 1 Ratchet handle. 5-in-1 Kit. £1.45 each. O/No. 329B

## ELECT & PIEZO BUZZERS

 **PIEZO**  
Miniature round piezo-electronic buzzer. White plastic. Low consumption  
Frequency 4kHz approx.  
Output 70dB (A) @ 1 typ.  
Power: 12Vd.c. 4mA  
Dims: 22 (dia.) x 11 5mm  
Fixing Centres: 26 5mm  
O/No VP 107 95p

 **PIEZO**  
Piezo buzzer. White plastic 90mm leads. For use on a.c. mains. Frequency 3.5kHz approx.  
Output 85dB (A) @ 1m typ.  
Power: 240V a.c. 5mA  
Dims: 32 (dia.) x 14mm  
Fixing centres: 38mm  
O/No. VP 108 £1.15

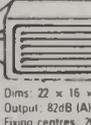 **ELECTRONIC**  
Miniature electronic buzzers. Solid state Ivory plastic. 150 leads. Frequency 500 Hz approx.  
Dims: 22 x 16 x 15mm  
Output: 82dB (A) @ 1m typ  
Fixing centres: 26mm  
3V 25mA O/No. VP 87 6V 25mA VP 83  
9V 25mA O/No. VP 84 12V 25mA. VP 86  
80p each


## SUB-BOX

A neat swivelling disc provides close tolerance substitution resistors of 36 preferred values from 5ohms to 1Kohm. Simply fix clips into circuit and swivel until optimum result is achieved.  
O/No. VP 112 £4.75

## MINIATURE VICE

Miniature plastic and metal vice with strong suction base for portability. Single action to secure or release suction. Plastic jaws with rubber pads 20mm wide, open out to 40mm. Dims: 85 x 65 x 60mm approx.  
FANTASTIC VALUE  
O/No. VP 95 ONLY £1.60

## LEARN A LINGO!

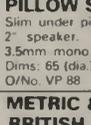 **PILLOW SPEAKER**  
Slim under pillow unit. 8ohms 2" speaker. 1.5m lead with 3.5mm mono jack plug. Black. Dims: 65 (dia.) x 17mm.  
O/No. VP 88 £1.25

## METRIC & BRITISH MEASURES

Steel tapes in sturdy ABS plastic case. Silk wrist strap. These yellow coated convex tapes have inch and metric graduations. Automatic push-button return and meinc graduations. Automatic push-button return.  
2m long x 13mm wide. O/No. VP 85 £1.00  
3m long x 13mm wide. O/No. VP 90 £1.50  
5m long x 16mm wide. O/No. VP 91 £2.00

## BATTERY TESTER

Tests all types of battery including standard NICAD, Alkaline etc. Takes all standard sizes including 6V lantern batteries and watch/hearing aid cells. Also tests fuses and lamps by means of internal 9V (PP3) battery. Can also be used to recharge NICAD batteries by means of external 3.12Vd.c. power supply (not included).  
Full instructions provided. Dims: 185 x 103 x 30mm (approx.)  
O/No. VP 101 £7.00

## FM MONITOR

FM monitor for 2 metre band. All metal. Attached earphone PL259/SO239 connectors. 14MHz 10W maximum. Dims (Body) 55 x 30 x 23mm.  
O/No. VP 120 £4.20

## DUMMY LOAD

50 ohms 30W UHF co-axial plug fitting (PL259)  
O/No. VP 121 £5.20

## PICK-UP COIL

Large telephone pick-up coil for high sensitivity. Suction pad to stick to telephone. 90cm lead to 3.5 jack plug. Connects direct to cassette recorder.  
Dims: 32 (dia.) x 11mm (body) 35mm (dia.) sucker  
O/No. VP 87 £1.00

# BI-PAK

Send your orders to Dept EE7 BI-PAK PO BOX 6 WARE, HERTS SHOP AT 3 BALDOCK ST. WARE, HERTS  
TERMS CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7006  
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your Total order. Postage add 75p per Total order.